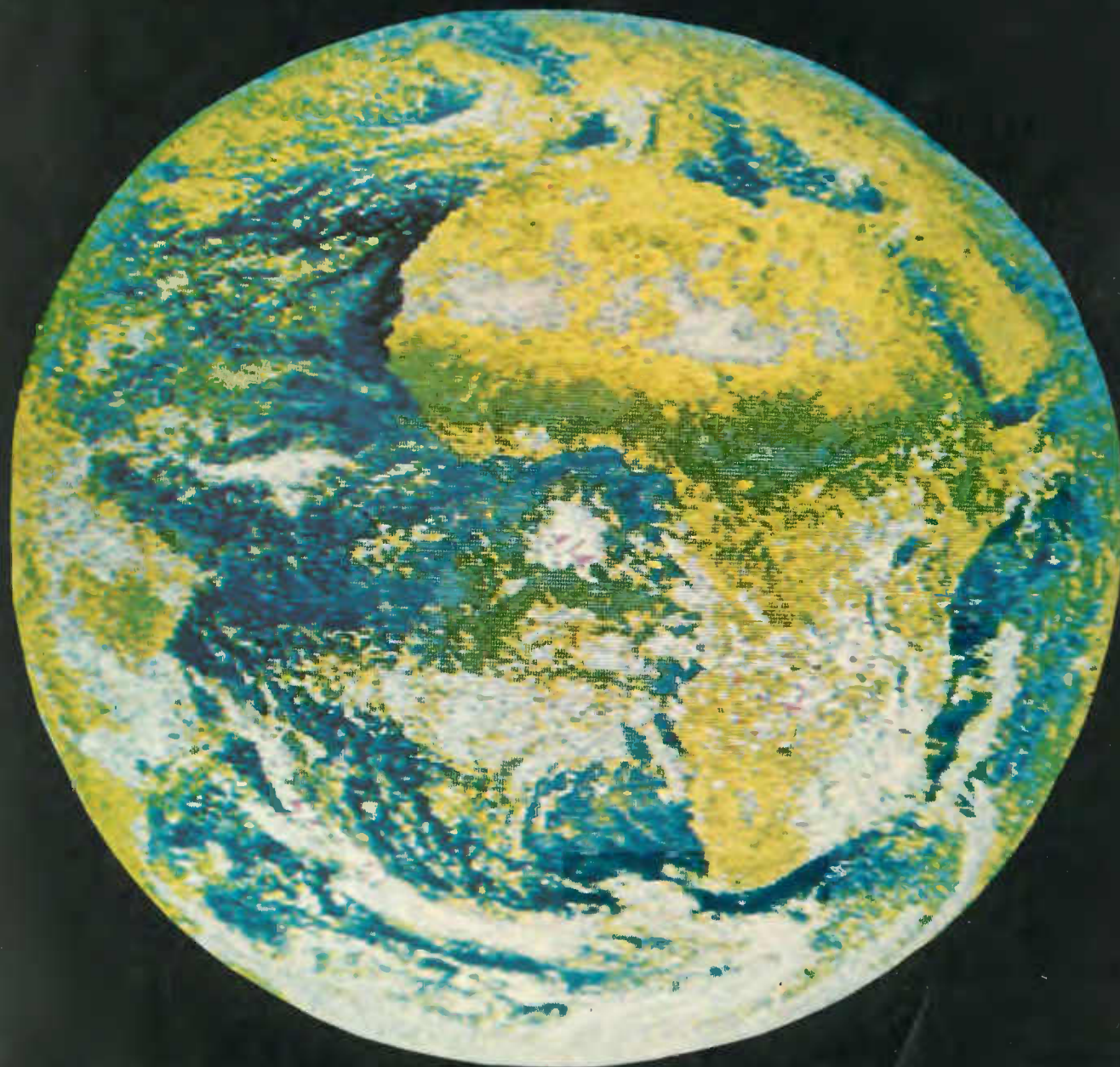


wireless world

JULY 1982 70p

Australia A\$ 2.40
Canada C\$ 3.25
Denmark DKR. 28.25
Germany DM. 6.50
Greece DRA. 160.00
Holland DFL. 8.00
Italy L 3100
Norway NKR. 24.00
Singapore M\$ 5.50
Spain PTS 240.00
Switzerland FR. 6.50
U.S.A. \$ 3.75

Printer mechanism interface
V.d.u. light pen



G.P.I.B./serial interface

ORYX



the new name in quality solder

Now there is another choice in high quality solder. The new Oryx resin cored solder. Try it and you will find it spreads easier than the solder you are using. Specially formulated for fast precision solder work, it is 60% tin, 40% lead alloy with quality flux construction and melts at 183°C. Two gauges are available—18 SWG (1.2mm) and 22 SWG (0.71mm) in 2.5 Kg, 500g, 250g and 100g reels. Pocket size dispenser with 10 feet of Oryx 1 mm solder is also available at only 68p (+VAT). Oryx is competitively priced—write now for details and technical information.

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659

The TC82—a significant development in temperature controlled soldering



The new Oryx TC 82 has features unique to any temperature controlled precision soldering iron. Available in 24 V, 50 V, 115 V and 210/240 V models, the TC 82 has a facility allowing the user to accurately dial any tip temperature between 260°C and 420°C by setting a dial in the handle without changing tips.

This eliminates the need for temperature measuring equipment. You get faster and better soldering.

For 24 V models a special Oryx power unit connects directly to the iron and contains fully isolated transformer to BS3535, a safety stand, tip clean facility and illuminated mains socket switch.

The Oryx TC 82 is also extra-safe. Removing the handle automatically disconnects the iron from power source. Other TC 82 features include: Power-on Neon indicator in handle; burn proof cable; choice of 13 tip styles.

And more good news

The Oryx TC 82 iron costs only £13.00 (+VAT) and the power unit for 24 V operation £23.00 (+VAT).

The TC82 240 volt is also available as a 30 watt general purpose iron at only £3.95 (+VAT).

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659

WW-003 FOR FURTHER DETAILS

wireless world

JULY 1982 70p

Printer mechanism interface V.d.u. light pen



Australia A\$ 2.40
Canada C\$ 3.25
Denmark DKR. 28.25
Germany DM. 6.50
Greece DRA. 160.00
Holland DFL. 8.00
Italy L 3100
Norway NKR. 24.00
Singapore M\$ 5.50
Spain PTS 240.00
Switzerland FR. 6.50
U.S.A. \$ 3.75

WIRELESS WORLD JULY 1982 VOL 88 NO 1558

G.P.I.B./serial interface

TRANSMITTER TEST SET, TTS520

Tests transmitters up to 100 watts rating

For testing base stations: mobile or fixed radios: pocket phones: pagers, etc

Instrument incorporates: r.f. counter • modulation meter • directional power meter • a.f. voltmeter • a.f. synthesizer • distortion analyser • a.f. counter • weighting filters • r.f. power load/attenuator

Transmitter measurements include: frequency • power • modulation (a.m. or f.m.) level, frequency, distortion, sensitivity, bandwidth, capability • call tone modulation check • aerial efficiency

Many measuring functions automatic—fewer controls, easier to understand and operate

Helps speed up test throughput

Reduces operator error and fatigue


Compatible with Farnell SSG520 synthesized signal generator to provide full transceiver testing facilities

Split concept (receiver/transmitter testing) offers distinct advantages over dedicated test set or discrete instruments

Programmable. Also IEEE488 option available for low cost computer controlled A.T.E.

Releases skilled engineers from routine tests. More time for repairs and other tasks

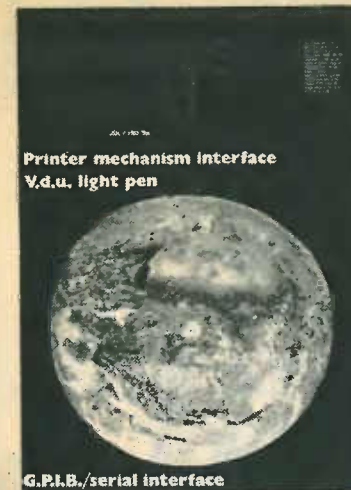Pre-service diagnostic tool. Use printer to record condition of radio as received and to verify performance to specification after repair or recalibration



G.P.I.B./serial interface
Front cover shows one of the more familiar parts of the universe, scanned by Meteosat and received and photographed by Mike Christieson.

NEXT MONTH

100W mosfet amplifier — John Linsley Hood concludes his three-part series with a description and full circuit and layout details of the final power amplifier design.

Meteosat high-resolution images — Mike Christieson presents expansions for the weather-satellite picture receiver to cover Meteosat-II's primary data.

Circuit modelling by microcomputer — the use of programming techniques to reduce computing time in circuit modelling.

Current issue price 70p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.6p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3130.

Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £12 UK and £15 outside UK.

Student rates: 1 year £8 UK and £10 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA: \$39 surface mail, \$98.30 airmail. US subscriptions from IPC B.P. Subscriptions Office, 205 E.42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1982 ISSN 0043 6062

ELECTRONICS
BROADCASTING
AUDIO

wireless world

COMMUNICATIONS
COMPUTING
VIDEO

JULY 1982 Vol 88 No 1558

- 29 A JOB TO BE DONE**
- 30 A LIGHT PEN FOR MICROCOMPUTERS**
by M. Shepherd
- 33 LEAKY FEEDER COMMUNICATION IN TUNNELS**
by D. J. R. Martin
- 38 WIDE-RANGE NOISE GENERATOR**
by Ian Hickman
- 41 PATENTING AN INVENTION**
by Barry Fox
- 45 CRISIS CONTROL**
by R. E. Young
- 48 CIRCUIT IDEAS**
- 51 MICRO-CONTROLLED, RADIO-CODE CLOCK**
by N. E. Sand
- 52 FAST STABILIZATION OF RC OSCILLATORS**
by I. M. Filanovsky
- 54 DIGITAL MULTI-TRACK TAPE RECORDER**
by A. J. Ewins
- 59 LETTERS TO THE EDITOR**
- 63 80-100W MOSFET AUDIO AMPLIFIER**
by J. L. Linsley Hood
- 67 NEWS OF THE MONTH**
- 71 GPIB-SERIAL INTERFACE**
by C. Jay
- 75 COMMUNICATIONS**
- 77 MICROCOMPUTER LINE PRINTER**
by P. L. Woods
- 80 DISC DRIVES**
by J. R. Watkinson
- 83 NEW PRODUCTS**

From **Farnell**
WETHERBY LS22 4DH UK
TEL.0937 61961
TELEX 557294 FARIST G

WW-001 FOR FURTHER DETAILS

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

— As a stand alone unit for editing and duplicating EPROMs.

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

BP4 (TEXAS) Bipolar PROM Programming module - £190
Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.
VAT should be added to all prices

DISTRIBUTORS REQUIRED ● EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW - 020 FOR FURTHER DETAILS

Electronic Brokers Second User Test Equipment. Makes engineers smile without making accountants cry.

Electronic Brokers are Europe's leading Second User Equipment Company. We carry large stocks of the very latest test equipment which is refurbished in our own service laboratories and calibrated to meet the

manufacturer's sales specifications. When you buy used equipment from Electronic Brokers, it can be yours in just days. No waiting for manufacturers lengthy production schedules. All equipment is fully guaranteed.

ANALOGUE VOLTMETERS

Avo
EA113 Electronic Multimeter £115.00

Bruel & Kjaer
2409 TRUE RMS. Average and Peak 2Hz-200KHz £250.00

Fluke
845AB Null Detector £610.00
883A AC/DC Differential Voltmeter. £615.00
931AB TRUE R.M.S. Differential Voltmeter £750.00

Hewlett Packard
3400A True RMS 1mV-300V 10Hz-10MHz £600.00
3406A 1mV-3V FSD 10KHz-1.2GHz £850.00

Marconi
TF2600A 1mV-100V FSD 10Hz-10MHz £245.00
TF2603 RF Millivoltmeter 300µV Sensitivity. 50KHz-1.5GHz £525.00

Racal
9301A RF Millivoltmeter £525.00

Rohde & Schwarz
URV RF-DC Millivoltmeter DC 50µV-1050V RF 10KHz-2GHz £950.00

Analysers
Dymar
1771 Wave Analyser (Sold Working - No Warranty) £150.00

Hewlett Packard
3580A Spectrum Analyser 5Hz-50KHz £2950.00

141T/8552B/8555A 10MHz-18GHz £9750.00
332A Distortion Meter 5Hz-600KHz £495.00
333A Distortion Meter with Auto null £675.00
8407A/8412A Network Analyser £1950.00
8555A Plug in. 10MHz-18GHz £5000.00

Marconi
TF2331 Distortion Meter 20Hz - 20KHz £475.00
TF2370 Spectrum Analyser. 30Hz-110MHz. 0.1dB and 5Hz resolution £6500.00

Racal
9008 Automatic Modulation Meter £425.00

Solartron
1172 TFA £4000.00

Sound Technology
1700A measures distortion down to 0.002%. AC voltage 30µV-300V, S/N Ratio 100dB Dynamic range, power into 8Ω. 0.001% distortion Oscillator £950.00

Tektronix
7D01/F2 Logic Analyser in 7704A Mainframe £4950.00

BRIDGES
Marconi
TM4520 Set of Inductors £350.00

Rohde & Schwarz
LRT (8N6100) Inductance Meter. 1pH-100µH. 2.2-285KHz £395.00

Wayne Kerr
B642 LCR 0.1% £795.00
SR 268 Source & Detector £875.00

DVM's AND DMM's
Fluke
8300A 5 1/2 Digit DC only 1µV sensitivity 5 ranges to 1100V £750.00

Phillips
PM 2523-01 LED 3 1/2 Digit DMM £95.00

Solartron
7055 Microprocessor DMM. Scale Length 20,000. AC/DC volts, resistance, 1µV resolution £495.00

FREQUENCY COUNTERS

Fluke
1920A with Option 139 Digit 1GHz £750.00
1925A Multifunction. EMI Proof 9 Digit 1.25MHz £625.00

Hewlett Packard
5340A 8 Digit 10Hz-18GHz £3750.00

Marconi
2432A 8 digit 10Hz-560MHz Battery/Mains £650.00

OSCILLOSCOPES

Marconi
TF2213/1 +TK2214 X-Y Display and memory £550.00

Phillips
PM 3234 True Dual Beam Storage Oscilloscope 10MHz New CRT £1750.00
PM 3244 50MHz 4 Channel Delay Tr Base £1500.00

Tektronix
465 Dual Trace Portable Oscilloscope. DC - 100MHz. 5mV-5V/div. Full delayed sweep £1395.00
465 with DM40 £1450.00
475 Dual Trace 200MHz Portable £2000.00
7313 100MHz Storage Mainframe. £2225.00
7603 100MHz Mainframe with 7A18N and 7B53N £3000.00
7704A 200MHz Mainframe c/w 7A22 Diff. Amplifier, 7A26 Dual Channel, 7B80 Timebase and 7B85 Delaying Timebase £4610.00
7904 500MHz Mainframe £4500.00
S1 Sampling Head, As New £450.00
7D14 Digital Counter plug-in 525MHz £850.00
434 Option 01 Storage Oscilloscope 25MHz £2250.00
1502 TDR £3500.00
P6015 HV Probe £295.00

Telequipment
DM63 Storage Oscilloscope Fitted with 2 x V4 Plug-ins to give 4 Trace 15MHz £1350.00
CT 71 Curve Tracer £450.00

Texscan
DU120 12" Display £425.00

RECORDERS

Hewlett Packard
7045A X-Y Plotter T Base Metric. £1150.00

Racal
Store 4DN RM Recorder £2500.00

Watanabe
MC641 6 Channel 250mm Chart Recorder £1495.00

Yokagawa
3047 2 Channel 2 cm/HR - 60cm/MIN £550.00

SIGNAL SOURCES

Hewlett Packard
4204A Decade LF Oscillator. 10Hz-1MHz. 1mV-10V into 600Ω £995.00
606B AM Signal Generator. 50KHz-65MHz. AM 0-95% £850.00
608F 10-455MHz AM/PCM Modulation 0.1µV-1V output £600.00
616B 1.8-4.2GHz int or ext PCM/FM 0.1µV-0.224V £1000.00
651B Test Oscillator. 10Hz-10MHz. 0.1mV-3.16V £415.00
3200B 10-500MHz Signal Source £475.00
3320A Frequency Synthesizer. 0.01Hz-13MHz. £995.00
8616A Signal Generator 1.8 - 4.5GHz £2000.00
8620C + 86250B Sweep Oscillator P.O.A.
8-12.4GHz P.O.A.
8640B c/w options 001, 002, 003 500KHz-1024MHz £4850.00

Marconi
TF144H/4 AM Signal Generator. 10KHz-72MHz. 2µV-2V £750.00
TF2002B AM/FM 10KHz-88MHz £1200.00
TF2170B Synchronizer for TF2002B £450.00
TF995B/2 AM/FM 200KHz-200MHz £695.00
TF2005R 2 Tone Signal Source. 20Hz-20KHz. 0-111dB in 0.1dB steps £295.00
TF2008 AM/FM 10KHz-510MHz built in sweeper. Output 0.2µV-200mV £3500.00
TF2016 + TF2173 Synchroniser AM/FM 10KHz-102MHz £2000.00
TF2169 Pulse Modulator for use with TF2015 or TF2016 £200.00
TF 2000 AF Signal Source £365.00

MISCELLANEOUS

Bruel & Kjaer
2209 Sound Level Meter £975.00

Dymar
2085 AF Power meter 20Hz-30KHz 10µW-50W input imp 1.2-1000Ω £250.00

Ferroglyph
RTS 2 Test Set £355.00

Fluke
332A DC Calibrator 0-1111 Volts 0.003% £950.00
3010A Logic Tester. Self Contained. Portable Full Spec. on Request £8500.00

Hewlett Packard
355E 12dB Programmable Attenuator unused £90.00
8403A Modulator Fitted With 8732B PIN MODULATOR £1500.00
8412A Phase Magnitude CRT display for network analyser £1500.00
8482H Power Sensor 100KHz-4.2GHz. AS NEW £520.00
8745A S Parameter Test Set. Fitted with 11604A Universal Arms 0.1-2GHz. £2750.00
59308A HP-IB Timing Generator £300.00

Marconi
TF2162 M.F. Attenuator 0-111dB £135.00
TF 2502 RF Power Meter DC - 1GHz 10W £525.00

Racal
9081 Synthesized AM/FM, Phase and Pulse modulation 5-520MHz £2200.00

Radiometer
SMG1 Stereo Generator £375.00

Telonic
1006A Sweep Oscillator 450 - 850MHz £750.00

Phillips
PM5715 Pulse Generator 1Hz-50MHz £675.00
PM6456 Stereo Generator £250.00

Racal
9081 Synthesized AM/FM, Phase and Pulse modulation 5-520MHz £2200.00

Transmission Measuring Equipment
Siemens
D2040 Selective Level Analyser and Voltmeter. 10Hz-60KHz £1200.00
D2072 + W2072 Level Meter and Oscillator 50KHz-100MHz £2200.00
W2006 + D2006 Carrier Level Test Set. 10KHz-17KHz - 100 to + 10dB £1650.00
W2007 + D2007 Carrier Level Test Set. 6KHz-18.6MHz. -120 to + 20dB £1800.00

Wandel and Goltermann
PF-1 Digital Error Rate Measuring Set. Consisting of PFM, Digital Error Rate Meter and PFM-1 Pattern Generator £2490.00
SPM-6 and PS-6 Level Measuring Set. 6KHz-18.6MHz. -110dB to + 20dB. Mains/battery operation £2150.00

Schaffner
NSG 509 Pulse Test Generator £785.00

Shackman
Super 7 MKII Camera £275.00

Tektronix
141ANPAL Test Signal Generator £1750.00
1481C PAL TV Waveform Monitor. £2375.00
191 Constant Amplitude Sig. Gen. 350KHz-100MHz 5mV-5.5V £250.00
106 Square Wave Generator 1ns risetime 10Hz-1MHz without accessories £175.00
284 Pulse Generator 70ps risetime £950.00
1502 TDR £3500.00
2901 Time-Mark Generator £195.00

Miscellaneous
Phillips
PM9380 Camera and Accessories (as new) £5000.00

Rohde & Schwarz
MSC Stereo Coder. 30Hz-15KHz £500.00

Schaffner
NSG 509 Pulse Test Generator £785.00

Shackman
Super 7 MKII Camera £275.00

Tektronix
141ANPAL Test Signal Generator £1750.00
1481C PAL TV Waveform Monitor. £2375.00
191 Constant Amplitude Sig. Gen. 350KHz-100MHz 5mV-5.5V £250.00
106 Square Wave Generator 1ns risetime 10Hz-1MHz without accessories £175.00
284 Pulse Generator 70ps risetime £950.00
1502 TDR £3500.00
2901 Time-Mark Generator £195.00

Please note: Prices shown do not include VAT or carriage.



Electronic Brokers
Electronic Brokers Limited
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 200 FOR FURTHER DETAILS

NRDC-AMBISONIC UHJ SURROUND/ SOUND DECODER



The first ever kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77. The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ. 10 input selections. The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 2 input signals and 4 or 6 output signals are provided in this most versatile unit. Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee £57.70 + VAT or ready built and tested £76.95 + VAT

INTRUDER 1 Mk. 2 RADAR ALARM

With Home Office Type approval

The original "Wireless World" published Intruder 1 has been re-designed by Integrex to incorporate several new features, along with improved performance. The kit is even easier to build. The internal audible alarm turns off after approximately 40 seconds and the unit re-arms. 240V ac mains or 12V battery operated. Disguised as a hard-backed book. Detection range up to 45 feet. Internal mains rated voltage free contacts for external bells etc.

Complete kit £52.50 plus VAT, or ready built and tested £68.50 plus VAT.

Wireless World Dolby noise reducer

Trademark of Dolby Laboratories Inc.



Complete Kit **PRICE: £49.95** + VAT (3 head model available)

Also available ready built and tested **Price £67.50** + VAT

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £2.75** + VAT

All kits are carriage free.

INTEGREX LIMITED

Typical performance
Noise reduction better than 9dB weighted
Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output
Dynamic range > 90dB
30mV sensitivity

ACCESS and VISA welcome

Please send SAE for complete lists and specifications

Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Burton-on-Trent (0283) 215432 Telex 377106

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



Applications

- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive
Ruislip, Middlesex. Ruislip 76962

WW - 033 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

FAST ERECTING CLARK MASTS

Here is the expertise
you can depend on -


25
years in this
specialist
field

When you choose a mast from the comprehensive Clark range you are assured of a high standard of Engineering and operational reliability.

Why compromise?

Extended heights 4 metres-30 metres, capable of lifting headload 1 kg-200 kgs.

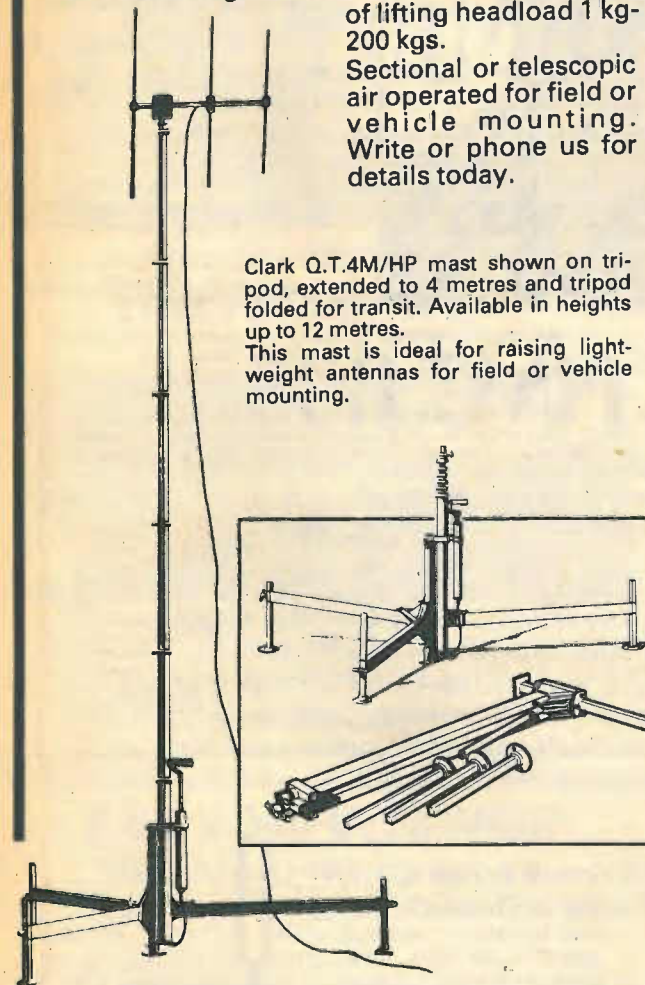Sectional or telescopic air operated for field or vehicle mounting. Write or phone us for details today.



Clark Q.T.4M/HP mast shown on tripod, extended to 4 metres and tripod folded for transit. Available in heights up to 12 metres. This mast is ideal for raising light-weight antennas for field or vehicle mounting.

CLARK MASTS LTD.
Binstead,
Isle of Wight,
PO33 3PA, England.
Telephone: Ryde (0983) 63691, Telex: 86686.




WW - 029 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

New Fluke 4 1/2 Digit Hand-held D.M.M.s

Now in Stock

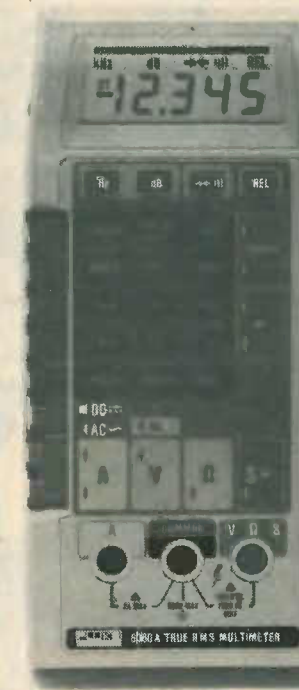

Basic dc accuracy 0.04%; 10 μV, 10 nA and 10 mΩ sensitivity.
Display annunciators for low battery (BT) and special functions: frequency (kHz), dB, continuity (---, ||) and relative reference (REL).
Autoranging MΩ measurements from 2 MΩ to 300 MΩ.
Conductance functions for resistance measurements to 10,000 MΩ.
Separate constant-current source diode-test function for checking semiconductor junctions.
Full range capability for voltage, current, resistance (200 μA, 200 mV and 200 Ω ranges).
Wideband True RMS AC measurements to 100 kHz.
Overload protection to 750 VAC or 1000 VDC on voltage inputs and 500 V on resistance. Protection on current inputs provided by a 2A/250V fuse in line with a heavy-duty 3A/600V fuse. Sophisticated self-diagnostics provided for all range and function selections plus LCD display, battery and CMOS circuitry.
Fluke's 8060A makes many of the same measurements as the 8060A, at a lower price.
Continuity and relative reference functions identical to 8060A.
True RMS measurements to 30 kHz.
Basic dc accuracy 0.05%; 10 μV, 10 nA and 10 mΩ sensitivity.

Fluke 8060A £275.00
Fluke 8062A £210.00

Fluke 8022B. With 2 year warranty £85.00
Fluke 8021B. With 2 year warranty £95.00
Fluke 8020B. With 2 year warranty £125.00
Fluke 8024B. With 2 year warranty £155.00
Fluke 8050A Mains Model £255.00 Mains Battery £285.00
Fluke 8012A Mains Model £229.00 Mains Battery £257.00
Fluke 8010A Mains Model £175.00 Mains Battery £203.00

ACCESSORIES

A81-230 Battery eliminator £14.00
C90 Carry case for hand held £10.00
801-600 Amp clamp £68.00
80J-10 Current shunt 10A £22.00
80K-40 H.V. probe 40kV £56.00
80K-6 H.V. probe 6kV £40.00
80T-150 Temperature probe £72.00
80T-H Touch hold probe £36.00
83RF R.F. probe 100MHz £40.00
85RF R.F. probe 500MHz £69.00
Y8102 Thermocouple probe £41.00
Y8103 Bead thermocouple £18.00
Y8104 K type thermocouple termination £8.00
Y8133 Deluxe test leads £14.00


Full Specs. on Request.
The above prices do not include carriage or VAT (15%).

**EXPRESS
DELIVERY
SERVICE**

Simply Phone or
Telex your order for
immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 201 FOR FURTHER DETAILS

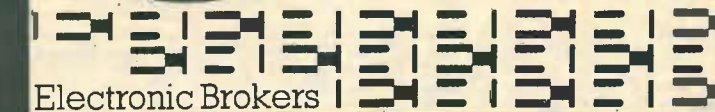

Electronic Brokers

The new CES micropad



The microphone for mobile radio, with DTMF signalling and optional ANI, brings greater system flexibility to your telecom network.

Interface
Quartz
Devices
Limited

For further information contact the sole agents

IQD

29 Market Street
Crewkerne
Somerset TA18 7JU

Crewkerne (0460) 74433
Telex 46283 infac g

WW - 016 FOR FURTHER DETAILS

THE HEADSET THAT'S WAY AHEAD OF ITS TIME.



THE DANAVOX HMT 808.

The Danavox HMT 808 is the most advanced headset of its kind that you can buy today. Employing Danavox expertise and quality throughout, it offers many unique features at a remarkably low price.

- Lightweight. Weighs only 35 grams
- Comfortable and hygienic. Does not go in the ear so it can be comfortably positioned in seconds
- Versatile. Can be worn under the chin or over the head using single ear or binaurally
- Multiple version microphone. Available with either magnetic microphone or electret with noise cancelling feature and pre-amplifier for matching into telephone systems

- Technically advanced. Pre-amp employs latest thick film technology
- Easy servicing and repairs. Quick changing of earphones, cords, earpieces and switches
- Realistically priced
- Danavox quality engineering and guarantee.

For full details contact John Carter at Danavox.

Danavox

DANAVOX (Gt. Britain) Ltd.,
1 Cheyne Walk, Northampton NN1 5PT
Tel: (0604) 36351 Telex 312395

WW - 030 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

Time's running out...
for Ni-Cads!

NEW
NEC
SUPERCAPS



Available from stock NOW!

1.0 FARAD SUPERCAP + 5101 C.MOS R.A.M. 1 MONTH	1.0 FARAD SUPERCAP + 1703 Programmable Tuner Chip 1 WEEK	1.0 FARAD SUPERCAP + 7507 C.MOS Microcomputer 1 DAY
--	--	---



Only part of the
Anglia range of
NEC components

Anglia

COMPONENTS

Burdett Road, Wisbech,
Cams, PE13 2PS
Telephone 0945 63281
Telex 32630 ANGLIA G

THE PARTS YOU NEED
- fast!

WW - 031 FOR FURTHER DETAILS

STEREO DISC AMPLIFIER 2

THE MOST THOROUGHLY RESEARCHED DISC AMPLIFIER THERE IS
for Broadcasting, Disc Monitoring and Transfer



Ring or write for full specifications of this or PPM Boxes * PPM2 and PPM3 drive circuits *
Ernest Turner movements 640, 642, 643 and TWIN with flush mounting adaptors and
illumination kits * Peak Deviation Meter * Programme and Deviation Chart Recorders *
Moving Coil Pre-amplifier * 10 Outlet Distribution Amplifier * Stabilizer * Fixed Shift
Circuit Boards * Broadcast Monitor Receiver 150kHz-30MHz.

SURREY ELECTRONICS LTD., The Forge, Lucks Green, Cranleigh
Surrey GU8 7BG. Tel. 04866 5997

P.&R. COMPUTER SHOP

IBM GOLFBALL PRINTER 3982, £70

EPSON MX-80 80.GPs 3982 IBM I/O PRINTERS DOT
MATRIX PRINTER WITH SPECIAL INTERFACES.
VDUs, ASCII KEYBOARDS, ASR, KSR, TELETYPES,
PAPERTAPE READERS, PAPERTAPE PUNCHES,
SCOPES, TYPEWRITERS, FANS 4" 5" 6". POWER
SUPPLIES, STORE CORES, TEST EQUIPMENT AND
MISCELLANEOUS COMPUTER EQUIPMENT.
OPEN: MONDAY TO FRIDAY 9 a.m.-5 p.m.,
SATURDAY TILL 1 p.m.

COME AND LOOK AROUND
SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, ESSEX
PHONE MALDON (0621) 57440

WW - 051 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

We supply HAMEG for Industry



HM 307 OSCILLOSCOPE

Single trace. DC to 10MHz. Rise time
35ns. 5mV/cm to 20V/cm. Timebase
0.5µs-0.25. Built in component tester.
LPS technique provides stable and
reliable triggering up to 30MHz **£138.00**



HM 203 PORTABLE OSCILLOSCOPE

Dual Trace. DC to 20MHz. 8 x 10cm
display. Rise time 17.5ns. Sensitivity
5mV/cm-20V/cm. Timebase 0.5µs-0.25.
x 5 magnifier. X-Y operation. Auto or
variable trigger. Channel 1, Channel 2,
line and external. Coupling AC, or TV
low pass filter. Weighs only 6Kg. Size
(m.m.) H. 145, W. 285, D. 380 **£220.00**



HM412-5

Dual Trace. DC to 20MHz 8 x 10cm
display with internal graticule. Rise time
17.5ns. Variable input 2mV-20V/cm.
Add and invert modes. Timebase
0.5µs-0.25 with sweep delay 100ns-15
x 5 expansion. X-Y operation Z
modulation. Trigger CH1, CH2, CH1/2,
Line or EXT. **£350.00**



HM705

Dual Trace DC-70MHz 8 x 10cm display
with internal graticule. Rise time 5ns.
Variable input 2mV-20V. Add and invert
modes. 95ns Signal Delay Line.
Timebase 50ns-15/cm with Sweep delay
100ns-15 x 10 expansion. XY
operation. Z modulation. Trigger CH1,
CH2, CH1/2 line or EXT. **£580.00**

The above prices do not include carriage
or VAT (15%).

Simple Phone or
Telex your order for
immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 202 FOR FURTHER DETAILS




Electronic Brokers



NICADS: UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -

Price on the page

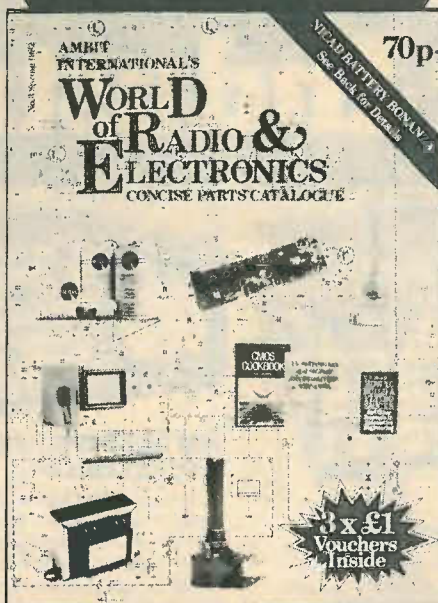


Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 x £1 discount vouchers. Here's a few examples of some super low prices:

- 78XX 1A 37p
- BC237/8/9 8p
- 3SK51 54p
- 10MHz XTALS £2
- 8 Pole 10.7MHz XTAL filters £14.50
- 2GHz coax relay 150W £10.95

+ all the usual stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micrometals toroids, Fairite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.

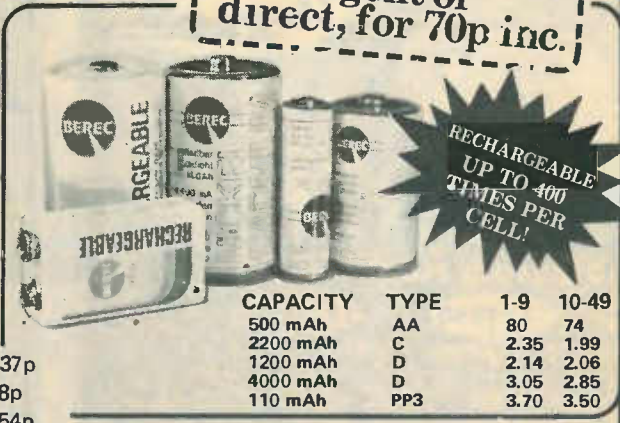Available at your newsagent or direct, for 70p inc.




CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.
POSTAGE and PACKING 50p per order

AMBIT international 200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

WW - 049 FOR FURTHER DETAILS

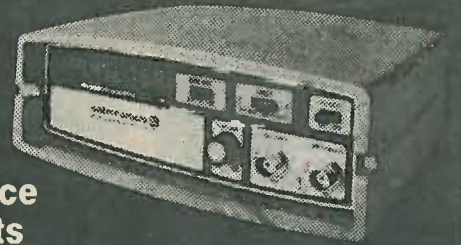An entire range of low-cost high-performance instruments



sabtronics

'Making Performance Affordable'

- *2010A 3 1/2-Digit L.E.D. Bench DMM
 - *2015A 3 1/2-Digit L.C.D. Bench DMM
 - 2020 3 1/2-Digit L.E.D. Bench DMM with Microcomputer Interface
 - 2033 3 1/2-Digit L.C.D. Hand DMM
 - *2035A 3 1/2-Digit L.C.D. Hand DMM with Temp.
 - LP-10 10MHz Logic Probe
 - 5020A 1Hz-200KHz Function Generator
 - *8110A 100MHz 9-Digit Frequency Meter
 - *8610A 600MHz 9-Digit Frequency Meter
 - *8610B 600MHz 9-Digit Frequency Meter
 - 8000B 1GHz 9-Digit Frequency Meter
 - 8700 10MHz Universal Frequency Counter/Timer
 - P8C-85 800MHz Prescaler
 - 9005 5MHz Single Trace Oscilloscope
- * Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from:
BLACK STAR LTD.,
9a Crown Street, St. Ives,
Cams. PE17 4EB
Tel: (0480) 62440. Telex 32339



WW - 032 FOR FURTHER DETAILS

EV88 - A low-cost evaluation system for the 8088 microprocessor

EV88 is a single board microcomputer that is ideal for evaluating the 8088 8-bit/16-bit microprocessor. EV88 can also be used as a powerful controller, and, with a suitable cross-assembler running on a standard microcomputer, and an EPROM programmer, for low-cost development of 8088-based systems.

EV88 is supplied fully assembled and tested, with comprehensive documentation, and a copy of The 8086 Book, by Rector and Alexy. All you need is a 5V 1A power supply and a terminal or a suitable microcomputer.


- ★ 8088 microprocessor in minimum mode (software compatible with the 8086 16-bit microprocessor).
 - ★ Comprehensive monitor in 2K EPROM.
 - ★ 2K CMOS RAM.
 - ★ Cassette interface.
 - ★ 24 lines of I/O.
 - ★ Eight levels of interrupt.
 - ★ RS-232 compatible serial interface (300 baud to 9600 baud).
 - ★ Three-channel counter/timer.
 - ★ Buffered data, address and control lines.
 - ★ Double Eurocard.
 - ★ On-board expansion to 16K EPROM/RAM (sockets provided).
 - ★ Breadboarding area.
 - ★ All bus signals available on 64-way DIN 41612 connector.
 - ★ Single 5V supply.
 - ★ Price £300 plus VAT. Includes delivery.
- 8088/8086 design service available (software and hardware).

LFH Associates Ltd.
40A High Street
Stony Stratford
Milton Keynes
(0908) 566660

WW - 061 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

METER PROBLEMS?

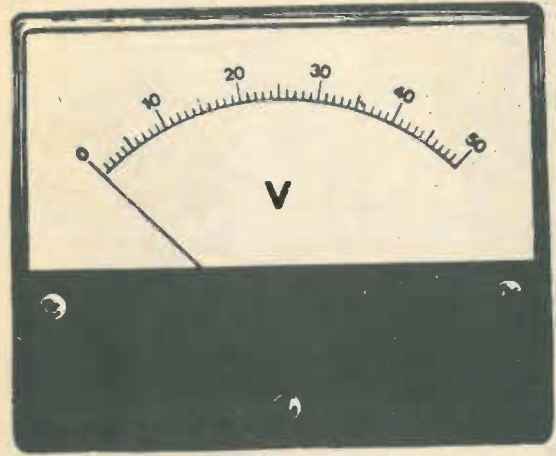


137 Standard Ranges in a variety of sizes and stylings available for 10-14 days' delivery. Other Ranges and special scales can be made to order.

Full information from:
HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1 Phone: 01-837 7937
Telex: 892301 HARTO G

WW - 015 FOR FURTHER DETAILS

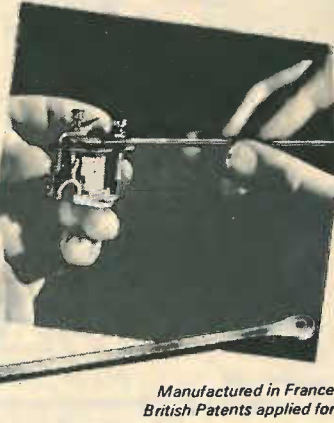Keep those Contacts CLEAN
BY USING A
DIACROM SPATULA



Manufactured in France
British Patents applied for

- No other cleaner has all these advantages:—
1. Only 100% pure, natural diamond grains are utilised.
 2. Blades are treated with hard chrome to reinforce the setting of the diamond grains, to obviate loosening or breakaway during use. This process also prevents clogging of the diamond surface by residues resulting from use.
 3. All diamond blades are rectified to ensure an absolutely smooth surface by eliminating diamond grains which may rise above the surface. This eliminates all excessive scratching during use.
 4. All diamond grains are rigidly calibrated to ensure a perfectly uniform grain size of either 200, 300 or 400.
 5. The chrome gives a very weak co-efficient of friction and the rigidity of the nylon handle is calculated to permit proper utilisation and yet pliant enough to avoid undue pressures on highly delicate relays.
- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
 - Grain size 300, thickness 55/100mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
 - Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tiny contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.

Sole Distributors for the United Kingdom
SPECIAL PRODUCTS (DISTRIBUTORS) LTD
81 Piccadilly, London W1V 0HL. Phone: 01-629 9556
As supplied to the M.O.D., U.K.A.E.A., C.E.G.B. British Rail and other Public Authorities; also major industrial and electronic users throughout the United Kingdom.

WW - 017 FOR FURTHER DETAILS

Electronic Brokers DEC SALE

a selection from our huge stocks

- All items reconditioned unless otherwise stated
- DISK DRIVES**
 - RK06 Add-on Drive (NEW) ... £2,200
 - RP06 Add-on Drive ... £12,500
 - RWM05 Drive and Control (NEW) ... £24,500
 - RX8E Dual Floppy & Ctl (NEW) ... £995
 - RX11 Dual Floppy & Ctl (NEW) ... £995
 - RXV1 1 Dual Floppy & Ctl (NEW) ... £995
 - RX211 Dual Floppy & Ctl ... £1,250
 - MMB4B 16KW Core Memory ... £995
 - MS8CB 32KW MOS Memory ... £750
 - RX8E Dual Floppy & Ctl (NEW) ... £995
 - RX28 Dual Floppy & Ctl ... £1,250
 - SYSTEMS**
 - PDP11/44 SYSTEM
 - 11/44 CPU 256KB MOS
 - Dual TU58, H9642 Cab
 - RK711 28MB Disk & Ctl
 - RK07 Add-on Disk
 - LA120 Console
 - RSX11M Licence
 - PDP11/44 SYSTEM (NEW)
 - 11/44 CPU 512KB MOS
 - Dual TU58, H9642 Cab
 - RJM02 67MB Disk & Ctl
 - RIM02 Add-on Disk
 - LA120 Console
 - RSX11M Licence
 - PDP11/44 UPGRADES
 - Complete service offered including supply and installation of 11/44 CPU and trade-in of redundant processor } **P.O.A.**
 - PDP11/24 SYSTEM (NEW)
 - 11/24 CPU, 256KB, H9645
 - RL211 Disk Drive & Ctl,
 - RL02 Add-on Disk Drive
 - KT24 PAX option
 - VT100 Console with AVO
 - RSX11M Licence
 - PDP11/70 SYSTEM (NEW)
 - 11/70 CPU, 512KB MOS,
 - Data System Cab,
 - RWM05 Disk Drive & Ctl,
 - TWU77 Mag Tape & Ctl,
 - LA120 Console

HAZELTINE VDUS NEW SCOOP PURCHASE



Special purchase of Hazeltine 1500 series VDUs - manufacturer's surplus - ALL BRAND NEW BOXED

- HAZELTINE 1510 - SAVE £330**
- ★ 24 x 80 Upper/Lower case ASCII
 - ★ 7 x 10 dot matrix
 - ★ Dual intensity
 - ★ 8 Switch-Selectable baud rates 110/9600 baud
 - ★ Full/Half duplex plus format mode
 - ★ Remote XY Cursor addressing
 - ★ 12" non-glare screen
 - ★ EIA/20mA Interface
- Manufacturer's list price £880
OUR PRICE £550

- HAZELTINE 1520 - SAVE £425**
- All the features of the 1510 plus buffered serial/parallel printer interface. Manufacturer's list price £1050
OUR PRICE £625
- Also available - Reconditioned Hazeltine H2000 VDUs @ £299 while stocks last

ADD 15% VAT TO ALL PRICES Carriage and Packing extra
Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694

Electronic Brokers

TEST INSTRUMENTS


THANDAR

Quality British-made Portable Instruments

MULTIMETERS:

DM450 £107
DC 10µV-1200V AC 100µV-750V
DC 0.1nA-10A AC 1nA-10A
0.01Ω-20MΩ 4½ digit LED

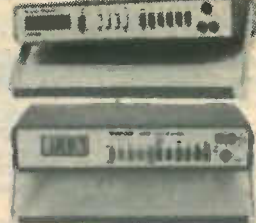TM351 £99
DC 100µV-1000V AC 100µV-750V
DC 100nA-10A AC 100nA-10A
0.1Ω-20MΩ 3½ digit LCD



FUNCTION GENERATOR:
TG102 £145
Freq. Range: 0.2Hz-2MHz

PORTABLE OSCILLOSCOPE:
SC110 £139

Carriage for all Thandar Orders £1

SABTRONICS

★ Available in KITS ★

Making Performance Affordable

HANDHELD DMMs

2033 £36.75	2035A £62	Asm Kit
AC/DC 100µV-1000V	AC/DC 100µV-1000V	£62 £49
AC/DC 10µA-2A	AC/DC 0.1µA-2A	
Ohms 1Ω-20MΩ	Ohm 0.1Ω-20MΩ	



FREQUENCY METERS: 8 digit LED

8110A 20Hz-100 MHz	Asm Kit
8610A 20Hz-600 MHz	£67 £56
	£82 £68



FREQUENCY METERS: 9 digit LED

8610B 10Hz-600MHz (0.1Hz Resolution)	Asm Kit
8000B 10Hz-1000MHz (0.1Hz Resolution)	£99 £84
	£155 -


Carriage for all SABTRONICS orders £1

SAFGAN BRITISH-MADE SCOPES

- ★ DUAL TRACE
- ★ 5mV/Div Sensitivity
- ★ XY Facility
- ★ Z Modulation
- ★ Calibration Output
- ★ Portable/Lightweight

DT 410 10MHz £179
DT 415 15MHz £185
DT 420 20MHz £198
XI-REF-X10 probe £11.50

p&p £2

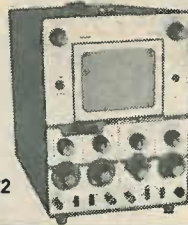


LEADER

When Quality Counts

LSG-16 £55

A compact solid state RF Signal Generator, most suited for checking the IF circuits and tuners in AM, FM and TV sets.

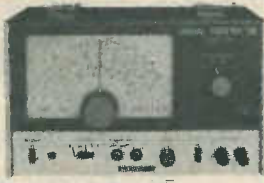Frequency range up to 100MHz (300MHz on Harmonics).
Carriage £1



LCR-740 £149
A highly efficient impedance bridge for measuring resistance, capacitance and inductance. The D factor of a capacitor and the Q sector of a coil can also be measured.

Carriage £1

Many more instruments available from all these ranges

ADD 15% VAT ON ALL PRICES

All prices correct at 2-92 E&OE
Cash with Order or Credit Card

CALLERS WELCOME

OPEN MONDAY TO FRIDAY 9am-5.30pm

DAROM SUPPLIES

4 SANDY LANE
STOCKTON HEATH
WARRINGTON
CHESHIRE, WA4 2AY
(0925) 64764

Catalogue available just send A4 size 22p s.a.o.

WW - 026 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC
OUTPUT 2: 0-70v, 10A AC
OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW - 039 FOR FURTHER DETAILS

SOUND INVESTMENT



QUALITY REEL TO REEL & CASSETTE TAPE HEADS

FITTING A NEW TAPE HEAD CAN TRANSFORM THE PERFORMANCE OF YOUR TAPE RECORDER. OUR FULL CATALOGUE (PRICE 50p) ALSO INCLUDES TAPE TRANSPORTS, DISC DRIVES, PRE-AMPLIFIERS AND ACCESSORIES

POPULAR UNIVERSAL CASSETTE HEADS TO EIAJ STANDARDS

C21RPS18 MONO R/P	£4.82	Hole Centres 17mm Apart, 12mm From Head Face
B24-02 STEREO R/P	£7.66	C42RPH20 STEREO R/P SENDUST FOR CHROME/METAL TAPES
B24-07 STEREO R/P FOR DOLBY SYSTEMS	£9.05	C42RPH04 STEREO R/P GLASS FERRITE
C21ES18 MONO/STEREO ERASE HEAD	£2.13	THE ULTIMATE LONG LIFE, HIGH PERFORMANCE HEAD £13.34

POST AND PACKING 40p EX STOCK DELIVERIES, ALL PRICES INCLUDE V.A.T.

The Monolith Electronics Co. Ltd.,
5/7 Church Street, Crewkerne,
Somerset TA18 7HR
Tel: 0460 74321
Telex: 46306 MONLTH G.

MONOLITH

electronic products

WW - 047 FOR FURTHER DETAILS

CLEF ELECTRONIC MUSIC

PIANOS



SPECIALISTS SINCE 1972
DOMESTIC OR STAGE
SIX OR 7¼ OCTAVES
KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.
Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

DOMESTIC PRICES		
£	SIX	7¼
Comp	217	244
Full	363.90	399.90
MFD	595	675

VOCAL & INSTRUMENTAL SOLOISTS!

Kit £289
Mfd £399

MASTER RHYTHM DRUM MACHINE

Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.


Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr., & Ins. and we operate Telephone BARCLAY CARD/ACCESS. Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W, 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 042 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

The Professional Choice

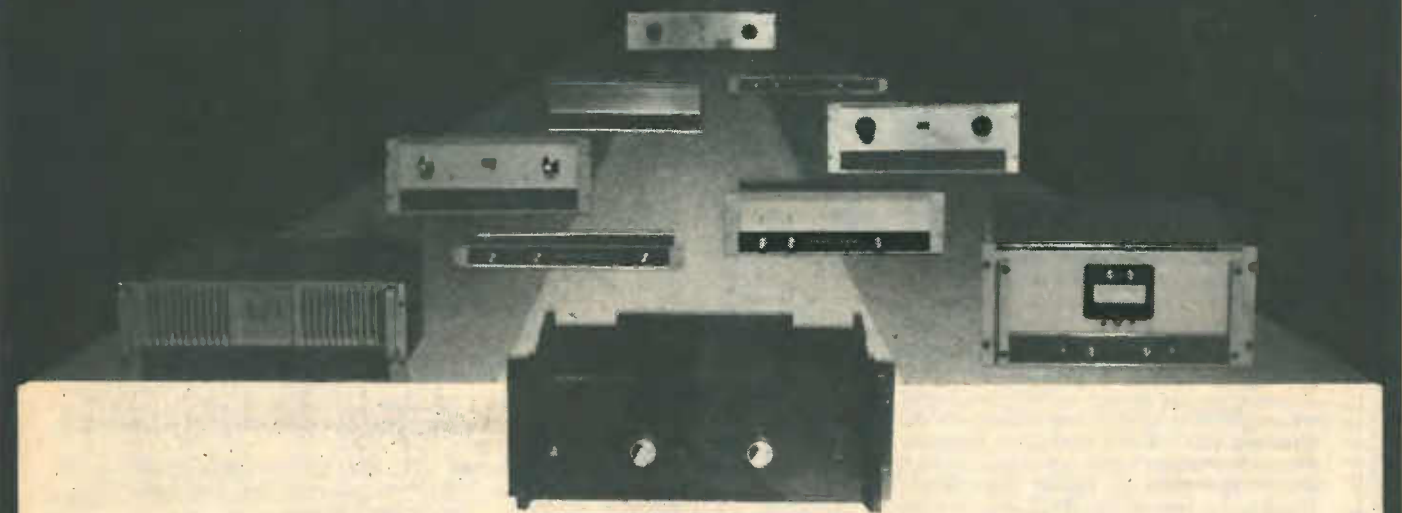

AMCRON

Since the introduction of the DC300 in 1967, AMCRON amplifiers have been used worldwide - wherever there has been a need for a rugged and reliable amplifier. Their reputation amongst professional users, throughout industry, has made the name of AMCRON synonymous with power amplification. For power you can depend on - choose AMCRON, the professional choice.

For further details contact the UK Industrial distributor:

G.A.S.

G.A.S. ELECTRONICS

16, ST. ALFEGE PASSAGE, LONDON SE10
TELEPHONE: 01-853 5295
TELEX: 923393 LASER G

WW - 019 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

Join us in Madison


Put my name in the hat and send me details of your new scope.

Name _____
 Company _____
 Address _____
 Tel No. _____

Draw to take place at TESTMEX 82 Wembley.



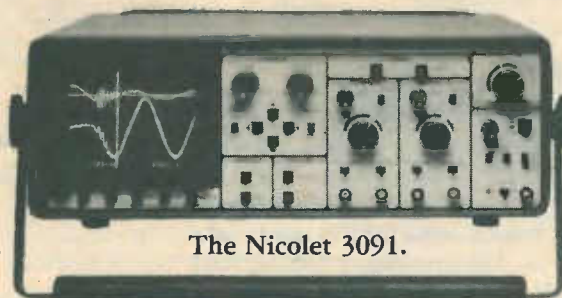To celebrate the launch of this new digital oscilloscope, we are offering you the opportunity to visit the manufacturing plant of this product in Madison, U.S.A. Bonafide enquirer's names will go into the hat for a straight draw to determine the winner who will receive a round trip flight and accommodation for 3 days by courtesy of Nicolet



The Nicolet 3091.

- A small, lightweight, high precision instrument.
- £2,750
- Dual differential inputs with 12 bit resolution.
- 4K words memory per channel.
- "Roll" mode for monitoring continuous signals.
- Full alphanumeric display & electronic grid.
- x64 Expansion on both axes.
- Digital Interface as standard.
- Plus Unique option of permanent Data Storage on magnetic bubble cassette.

Nicolet Instruments

Nicolet Instruments Limited. (A Nicolet Instrument Subsidiary).
 Buddbrook Road, Warwick, England. CV34 5XH.
 Telephone (0926) 494111 Telex 311135

TECHNOMATIC TECHNOMATIC TECHNOMATIC

SPECIAL OFFER

2114L-200NS	1-24	100p	25-99
2114L-450NS	100p	90p	
2716 (+5v)	250p	85p	
2532	400p	375p	
2732	400p	375p	
6116P-3	500p	475p	

CONNECTOR SYSTEMS

I.D. CONNECTORS	D CONNECTORS	DIP PLUGS	FLAT CABLE
(Speedblock Type)	9 way 15way 25way 37way		(Grey)
No. of Header	MALE	Solder IDC	10 way 80p
Ways	Female	Type Type	14 way 90p
10 ... 90p	Solder 90p 130p 160p 250p	14 pin 40p 90p	20 way 105p
20 ... 145p 125p 240p	Angled 160p 230p 265p 425p	18 pin 50p 100p	26 way 140p
25 ... 175p 150p 300p	Solder 110p 160p 210p 350p	24 pin 100p 175p	34 way 220p
34 ... 200p 160p 380p	Head 95p 95p 125p	40 pin 200p 225p	40 way 265p
40 ... 220p 190p 550p	Head 95p 95p 125p	50 way 300p	50 way 300p
50 ... 235p 200p 600p	IDC Type 25 way M £4.50. P £5.00.	64 way 370p	

JUMPER LEADS

24" Cable with DIP Headers	EDGE CONNECTORS	EURO CONNECTORS
1 End 145p 165p 240p 380p	0.1" 0.156"	Plug Skt
2 Ends 210p 230p 345p 540p	2 x 18 way - 140p	DIN1512 2 x 32 220p 290p
Cable with Sockets	2 x 22 way 200p 170p	Pins 230p 330p
No. of Ways 20 26 34 40	2 x 23 way 210p -	(psa specify a + b + c + d)
1 End 160p 210p 270p 300p	2 x 25 way 225p 220p	1 x 32 way 250p 380p
Cable with D Connectors	1 x 43 way 280p -	IDC 2 x 32 way 475p
24" Single End Male £5.50 Female £6	2 x 43 way 395p -	DIN 4161/31 21 way 180p 180p
36" Double End Male £11.50 Female £11.50	1 x 77 way 700p -	21 way 170p 170p
36" Male/Female £11.00		

ACORN ATOM

Built 8K + 2K £135 5K + Coloured Card £175 12K + 12K £180 (p & p £3/unit)
 Atom PSU £7 (p & p 70p) 3A 5V Regulated PSU £24 (p & p £1.50)
 F.P. ROM £20 1K RAM (2 x 2114L) £2 Tool Box Room £25
NEW COLOUR ENCODER CARD £39.00
ATOM SOUND BOARD: Kit comprises of a PSG, VIA and a 2K ROM with resident demo program. The board plugs onto ATOM BUS to parallel and serial output ports and audio output mini speaker or hi fi amplifier. Complete kit £35.00
ATOM VISION: An ultrasonic transducer is rotated by a software controlled stepper motor. Data collected by the sensor is processed as displayed on the screen either as a radar type plot or as distance. Complete kit £46.00
ATOM DISC Module: with PSU for both drive & 12K + 12K ATOM, Controller card, Connector cable, instruction manual £299 + £6 carr.

PRINTERS

SEIKOSHA GP100A dot matrix printer, full graphics double width characters, up to 10" wide paper, self testing parallel interface £199 + Carriage £6
EPSON MX80 Friction and Tractor, 9 x 9 matrix 80 CPS bi-directional with logic seeking, variety of charac. £360 + £6
BMC 12" Green Screen Monitor £100 + £6 carr.
BBC COMPUTER UPGRADE MEMORY
 IC61-68 16K RAM 100ns AP3 £25.60
PRINTER & USER PORTS
 IC69, 70, PL9, 10 £8.50 SK10 with 36" Cable £2.20
 36" Printer Connector Lead Complete £13.50
 SK9 with 36" Cable £3.30
ANALOGUE PORT
 IC73, SK6 £6.80 PL6 £1.60 PL6 + Hood with 36" Cable £5.00
F.D. PORT
 IC77-87 + PL8 £44 SK8 with 36" Cable £3.50
BUS PORT
 IC71-72 + PL11 £3.30 SK11 with 36" Cable £3.50
TUBE PORT
 PL12 £3.00 SK12 with 36" Cable £3.90

SOFTY II


The complete microprocessor development system for both Engineers and Hobbyists. You can develop programs, debug, verify and commit them to EPROMs. Will accept most +5V EPROMs. Can also be used as a ROMULATOR. Full review in September '81 P.E. Built unit complete with PSU and TV lead £169

TECHNOMATIC TECHNOMATIC TECHNOMATIC

74 SERIES				LINEAR ICs				COMPUTER COMPONENTS					
7401	11p	74285	175p	741S374	60p	4076	48p	AN103	200p	LM382	120p	SN76477	480p
7402	12p	74290	100p	741S375	85p	4077	18p	280ADMA	600p	LM386	90p	SN76478	480p
7403	12p	74293	100p	741S376	60p	4078	18p	280ADAT	600p	SN8515	750p	CPUs	
7404	12p	74298	100p	741S377	60p	4081	16p	280SIO-01/1/2	600p	74120	160p	7805	700p
7405	12p	74365	50p	741S378	60p	4082	16p	280SIO-1	600p	74130	160p	280SIO-2	600p
7406	20p	74366	50p	741S379	50p	4083	16p	280SIO-2	600p	74140	160p	280SIO-2	600p
7407	20p	74367	50p	741S380	50p	4084	16p	280SIO-2	600p	74150	160p	280SIO-2	600p
7408	20p	74368	50p	741S381	50p	4085	16p	280SIO-2	600p	74160	160p	280SIO-2	600p
7409	20p	74369	50p	741S382	50p	4086	16p	280SIO-2	600p	74170	160p	280SIO-2	600p
7410	14p	74370	50p	741S383	50p	4087	16p	280SIO-2	600p	74180	160p	280SIO-2	600p
7411	18p	74371	50p	741S384	50p	4088	16p	280SIO-2	600p	74190	160p	280SIO-2	600p
7412	18p	74372	50p	741S385	50p	4089	150p	280SIO-2	600p	74200	160p	280SIO-2	600p
7413	18p	74373	50p	741S386	50p	4090	100p	280SIO-2	600p	74210	160p	280SIO-2	600p
7414	28p	74374	50p	741S387	50p	4091	100p	280SIO-2	600p	74220	160p	280SIO-2	600p
7415	20p	74375	50p	741S388	50p	4092	100p	280SIO-2	600p	74230	160p	280SIO-2	600p
7416	20p	74376	50p	741S389	50p	4093	100p	280SIO-2	600p	74240	160p	280SIO-2	600p
7417	20p	74377	50p	741S390	50p	4094	100p	280SIO-2	600p	74250	160p	280SIO-2	600p
7418	20p	74378	50p	741S391	50p	4095	75p	280SIO-2	600p	74260	160p	280SIO-2	600p
7419	20p	74379	50p	741S392	50p	4096	75p	280SIO-2	600p	74270	160p	280SIO-2	600p
7420	15p	74380	50p	741S393	50p	4097	340p	280SIO-2	600p	74280	160p	280SIO-2	600p
7421	20p	74381	50p	741S394	50p	4098	90p	280SIO-2	600p	74290	160p	280SIO-2	600p
7422	20p	74382	50p	741S395	50p	4099	100p	280SIO-2	600p	74300	160p	280SIO-2	600p
7423	20p	74383	50p	741S396	50p	4100	100p	280SIO-2	600p	74310	160p	280SIO-2	600p
7424	20p	74384	50p	741S397	50p	4101	100p	280SIO-2	600p	74320	160p	280SIO-2	600p
7425	24p	74385	50p	741S398	50p	4102	100p	280SIO-2	600p	74330	160p	280SIO-2	600p
7426	28p	74386	50p	741S399	50p	4103	100p	280SIO-2	600p	74340	160p	280SIO-2	600p
7427	28p	74387	50p	741S400	50p	4104	100p	280SIO-2	600p	74350	160p	280SIO-2	600p
7428	28p	74388	50p	741S401	50p	4105	100p	280SIO-2	600p	74360	160p	280SIO-2	600p
7429	28p	74389	50p	741S402	50p	4106	100p	280SIO-2	600p	74370	160p	280SIO-2	600p
7430	14p	74390	50p	741S403	50p	4107	100p	280SIO-2	600p	74380	160p	280SIO-2	600p
7431	18p	74391	50p	741S404	50p	4108	100p	280SIO-2	600p	74390	160p	280SIO-2	600p
7432	18p	74392	50p	741S405	50p	4109	100p	280SIO-2	600p	74400	160p	280SIO-2	600p
7433	22p	74393	50p	741S406	50p	4110	100p	280SIO-2	600p	74410	160p	280SIO-2	600p
7434	28p	74394	50p	741S407	50p	4111	100p	280SIO-2	600p	74420	160p	280SIO-2	600p
7435	28p	74395	50p	741S408	50p	4112	100p	280SIO-2	600p	74430	160p	280SIO-2	600p
7436	28p	74396	50p	741S409	50p	4113	100p	280SIO-2	600p	74440	160p	280SIO-2	600p
7437	28p	74397	50p	741S410	50p	4114	100p	280SIO-2	600p	74450	160p	280SIO-2	600p
7438	28p	74398	50p	741S411	50p	4115	100p	280SIO-2	600p	74460	160p	280SIO-2	600p
7439	28p	74399	50p	741S412	50p	4116	100p	280SIO-2	600p	74470	160p	280SIO-2	600p
7440	15p	74400	50p	741S413	50p	4117	100p	280SIO-2	600p	74480	160p	280SIO-2	600p
7441	15p	74401	50p	741S414	50p	4118	100p	280SIO-2	600p	74490	160p	280SIO-2	600p
7442	20p	74402	50p	741S415	50p	4119	100p	280SIO-2	600p	74500	160p	280SIO-2	600p
7443	20p	74403	50p	741S416	50p	4120	100p	280SIO-2	600p	74510	160p	280SIO-2	600p
7444	20p	74404	50p	741S417	50p	4121	100p	280SIO-2	600p	74520	160p	280SIO-2	600p
7445	20p	74405	50p	741S418	50p	4122	100p	280SIO-2	600p	74530	160p	280SIO-2	600p
7446	20p	74406	50p	741S419	50p	4123	100p	280SIO-2	600p	74540	160p	280SIO-2	600p
7447	20p	74407	50p	741S420	50p	4124	100p	280SIO-2	600p	74550	160p	280SIO-2	600p
7448	20p	74408	50p	741S421	50p	4125	100p	280SIO-2	600p	74560	160p	280SIO-2	600p
7449	20p	74409	50p	741S422	50p	4126	100p	280SIO-2	600p	74570	160p	280SIO-2	600p
7450	15p	74410	50p	741S423	50p	4127	100p	280SIO-2	600p	74580	160p	280SIO-2	600p
7451	15p	74411	50p	741S424	50p	4128	100p	280SIO-2	600p	74590	160p	280SIO-2	600p
7452	15p	74412	50p	741S425	50p	4129	100p	280SIO-2	600p	74600	160p	280SIO-2	600p
7453	15p	74413	50p	741S426	50p	4130	100p	280SIO-2	600p	74610	160p	280SIO-2	600p
7454	15p	74414	50p	741S427	50p	4131	100p	280SIO-2	600p	74620	160p	280SIO-2	600p
7455	15p	74415	50p	741S428	50p	4132	100p	280SIO-2	600p	74630	160p	280SIO-2	600p
7456	15p	74416	50p	741S429	50p	4133	100p	280SIO-2	600p	74640	160p	280SIO-2	600p
7457	15p	74417	50p	741S430	50p	4134	100p	280SIO-2	600p	74650	160p	280SIO-2	600p
7458	15p	74418	50p	741S431	50p	4135	100p	280SIO-2	600p	74660	160p	280SIO-2	600p
7459	15p	74419	50p	741S432	50p	4136	100p	280SIO-2					

10 into 1 Does Go.

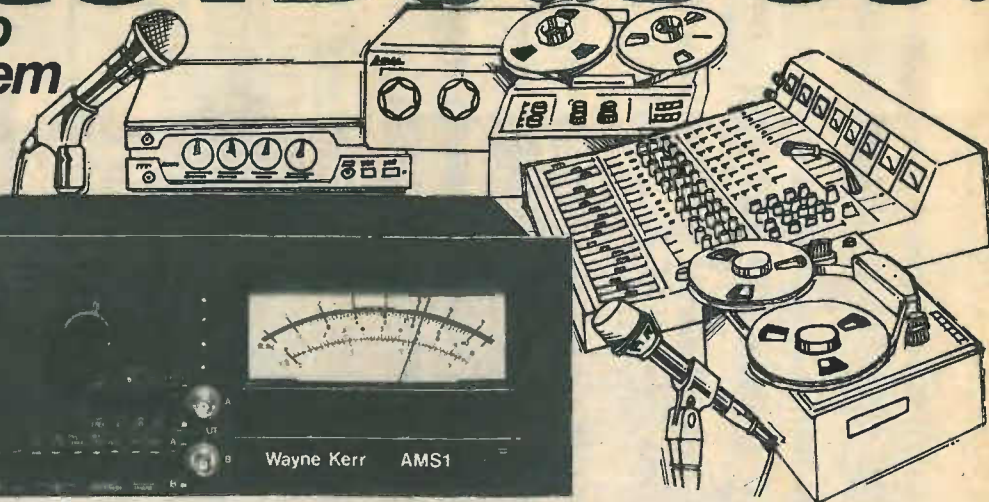Complete audio measuring system see the 10 features...



1. Freq. Counter,
2. Oscillator,
3. Noisemeter,
4. Wow & Flutter meter,
5. Level Meter,
6. Distortion,
7. Phase,
8. Power,
9. Drift,
10. Rumble.

Already in use from the small service workshop to Audio Equipment manufacturers to professional studio to IBA Broadcast station to the "BBC". AMS1 provides the solution.

Saves time, saves space, saves capital equipment cost, saves earthing problems. Transportable and easy to use. This low cost comprehensive audio workshop meets the latest specifications for Audio Measurement with accuracies equivalent to many of its stand alone counterparts.

10 Instruments, 15 Measurements
for the price of One. That's the AMS1...
from Wayne Kerr.

Belgium - Simac Electronics SPRL. Tel: 022192453. Telex: 23662. France - Tekelec Airtronic. Tel: 5347535. Telex: 204552. Netherlands - C.N. Rood B.V. Tel: 996360. Telex: 31238. Sweden - Scandia Metric AB. Tel: 20400. Telex: 10766. West Germany - Keithley Instruments GmbH. Tel: 7144065. Telex: 5212160. Italy - Telav International SRL. Tel: 4455741. Telex: 312827. Spain - Unintronic SA. Tel: 2425204. Telex: 22596. Eastern Europe, USSR, China - Data Loop Ltd. Tel: 0306 81166. Telex: 859417. South Africa - Telkor Pty Limited. Tel: 011 489740. Telex: 4-22171.

WAYNE KERR
WKR Limited Durban Road
Bognor Regis
West Sussex PO22 9RL England
Tel: (0243) 825811 Telex: 86120

WW - 008 FOR FURTHER DETAILS

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV Tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology. Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Sealoffs, and all other associated items for TV Tube Production. A Full Technical Back-up and Advisory Service is available to all customers Worldwide.

Please request our current catalogues and Data Information.

GRIFTRONIC EMISSION LTD
2 SWAN STREET
ALCESTER
WARWICKSHIRE
B49 5DP
ENGLAND

Telephone: (0789) 76452/764100. Telex: 312354 Grifem G

WW - 045 FOR FURTHER DETAILS

NOW!
FROM SESCOM
ORDER YOUR FAVOURITE
AUDIO ACCESSORIES BY MAIL
SEND FOR YOUR FREE COPY
OF OUR 1982 CATALOG

OVER 250 ITEMS
INCLUDING DIRECT BOXES, MIC-SPLITTERS,
SIGNAL PROCESSING, AUDIO MODULES,
TRANSFORMERS & MANY OTHER ACCESSORIES
WITH TECHNICAL DATA
& USE DIAGRAMS

We Ship the fastest & most convenient way for you! Most Shipments From Stock

SESCOM, INC.
RETAIL SALES DIVISION
1111 Las Vegas Blvd. North
Las Vegas, NV 89101-1197 U.S.A.
(702)384-0993
(800)634-3457
TWX (910)397-6998

WW - 062 FOR FURTHER DETAILS

L&J COMPUTERS

192 HONEYPOT LANE, QUEENSBURY, STANMORE, MIDDX HA7 1EE. 01-204 7525

THE "PET" SPECIALISTS

4016 16K Computer	£460
4032 32K Computer	£575
2031 171K Single Drive Floppy Disk	£350
4040 343K Dual Floppy Disk	£575
4022 Tractor Feed Printer	£350
8032 32K Computer	£750
8096 96K Computer	£995
8050 950K Dual Drive Floppy Disk	£750
8023 Tractor Feed Printer	£750
8422 22 Megabyte Winchester Disk	£3250
9000 SuperPet 134K Multilanguage Computer	£1295

TOOL KITS (BASIC 2 & 4), SUPERCHIPS
AND ALL SORTS OF OTHER CHIPS

WE HAVE A DAZZLING ARRAY OF
CONNECTIONS WITH THE OUTSIDE WORLD!
D TO A CONVERTERS (8, 12 & 16 BIT
A TO D CONVERTERS RESOLUTIONS
X/Y PLOTTERS (A3 SIZE UPWARDS)
DIGITAL INPUTS/OUTPUTS
RS 232C: IEEE: CENTRONIC INTERFACES

AS WELL AS BUSINESS SOFTWARE, WE ALSO
CAN SUPPLY ENGINEERING
REQUIREMENTS, LIKE:
DATA ANALYSIS/STATISTICAL PACKAGES
TAPEPREP FOR ONC MACHINE TOOLS
SECTION CALCULATIONS FOR DRAWING
OFFICES
ANALYSIS FOR CONTROL SYSTEMS

COME AND
SEE THE NEW
VIC-20
£165

FULLY WORKING AND OPERATIONAL
ASK US ABOUT ALL THE ADD-ON-GOODIES
THAT GO WITH THE VIC

MASSSES OF BOOKS ON THE
PET & VIC
+ INTERFACING & CONTROL

SEND US A LARGE STAMPED ADDRESSED
ENVELOPE (12x9) AND WE WILL BE DE-
LIGHTED TO SEND YOU ALL OUR CURRENT
INFORMATION!

* PRICES DO NOT INCLUDE VAT

ALL GOODS SENT SAME DAY WHEREVER POSSIBLE
LARGE S.A.E. FOR LISTS ETC.

WW - 053 FOR FURTHER DETAILS


WIRELESS WORLD JULY 1982

HANDSOME!

First there was the 130. A handheld D.M.M. which still sets the standards our competitors strive to match. Next came the 131. The introduction of the 135 saw 4½ digits on a handheld D.M.M. for the very first time.

And that same commitment to innovation has resulted in the latest additions to the range. The Keithley 128 D.M.M. with audio-tone and 870 Digital Thermometer with centigrade and fahrenheit readout.

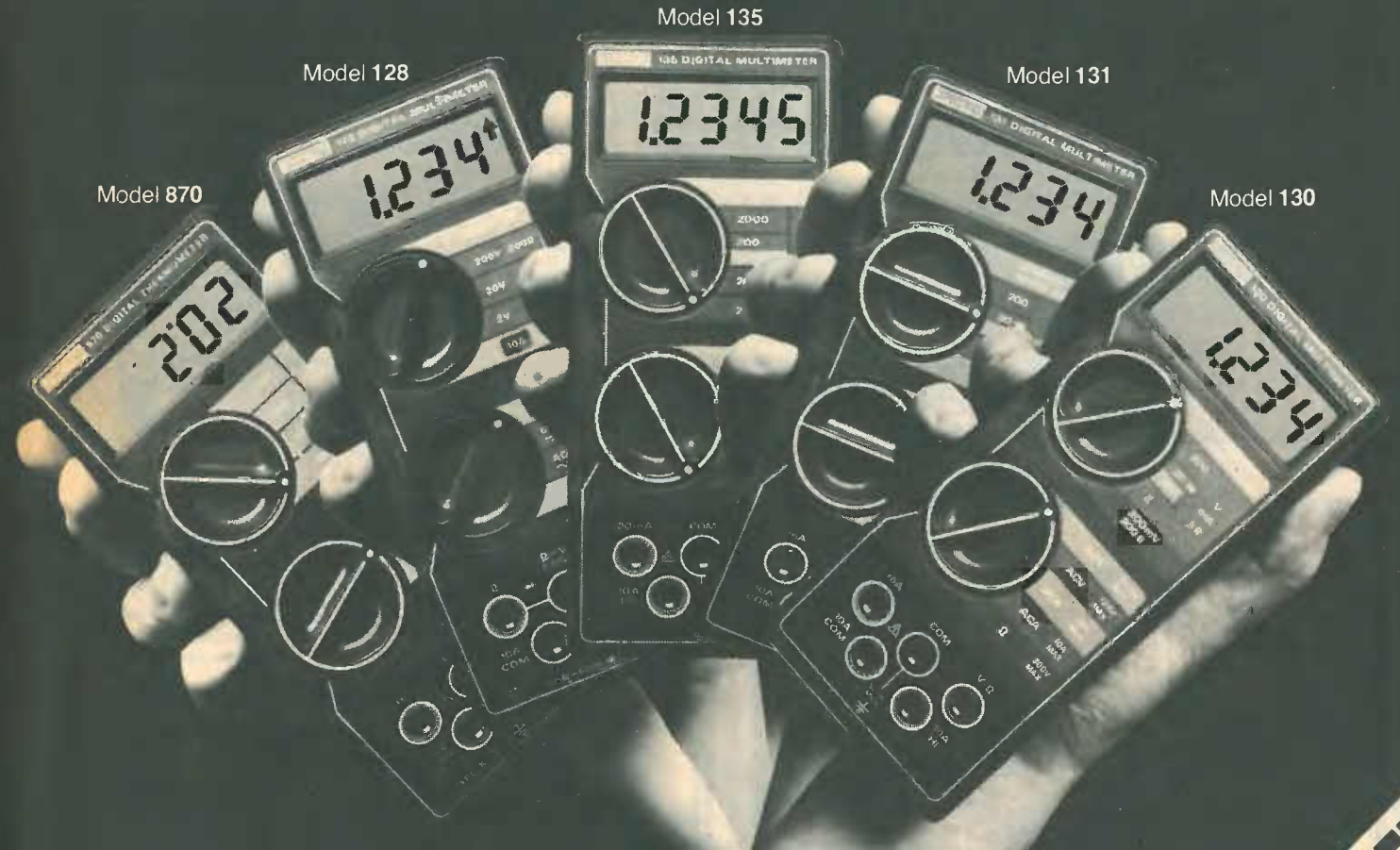The result is an unrivalled selection of handheld measuring devices. Each specification carefully matched to a given need. With performance that looks pretty good on paper. And even better in the field!



Model 870 • 0.025% accuracy • Centigrade and fahrenheit readout • Measures up to 1370°C

• 0.1° resolution up to 200°C

Model 128 • Audio-tone with adjustable threshold • 25 ranges: 5 functions • 10 amp span

Model 135 • 0.05% accuracy • Full overload protection • ACU bandwidth to 20 KHz

Model 131 • 0.25% accuracy • 25 ranges: 5 functions • 10 amp span

Model 130 • 25 ranges: 5 functions • 10 amp span • 0.5% accuracy

All models are guaranteed accurate for one year. And built to the high standards of quality expected of the Keithley name. For more information simply fill in the coupon. And learn about a range which will serve you... handsomely!

KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

Also available from
I.T.T. Instrument Services, Tel. Harlow 29522

WW - 011 FOR FURTHER DETAILS

I would like to know more about your Handheld Units.
Please send me details on D.M.M.'s 870 Thermometer


Name _____ Position _____
Company _____
Address _____
Telephone _____

WW/782

PORTABLE MAINS DISTRIBUTION NOW WITH EARTH LEAKAGE

OLSON

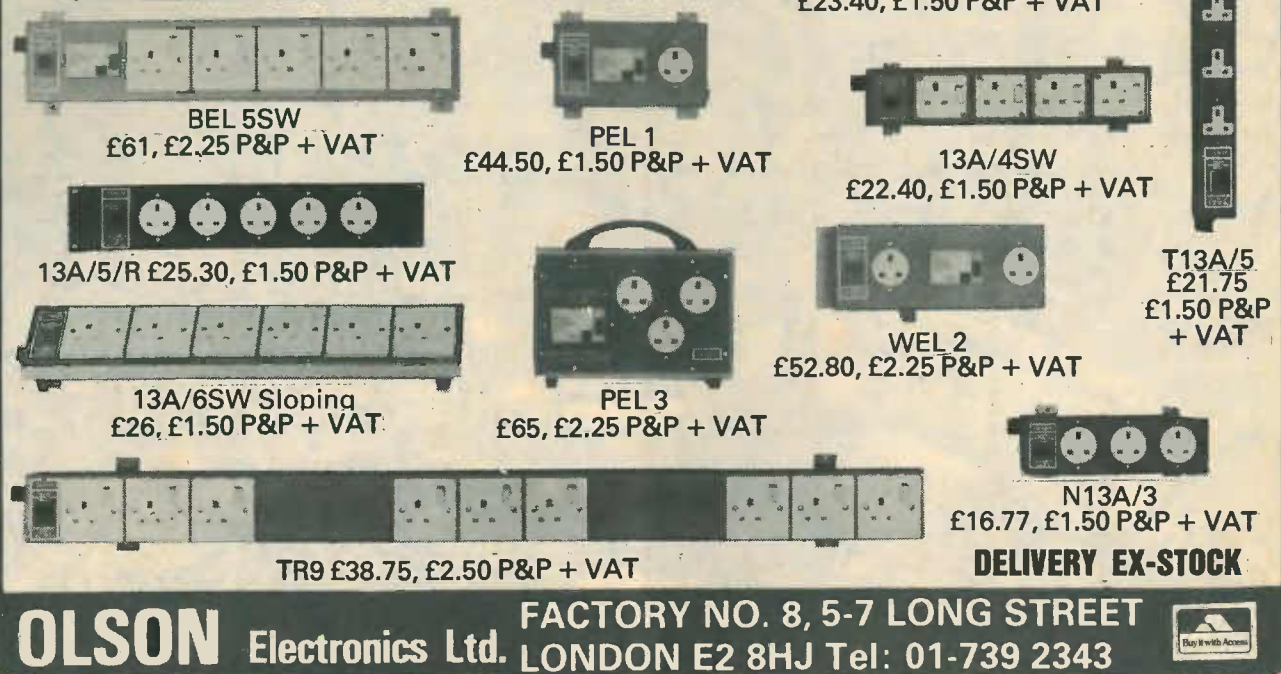FOR INSTANT MAINS DISTRIBUTION IN OFFICES, LABORATORIES, WORKSHOPS AND FOR MAXIMUM SAFETY



N13A/6
£23.40, £1.50 P&P + VAT

BEL 5SW
£61, £2.25 P&P + VAT

PEL 1
£44.50, £1.50 P&P + VAT

13A/4SW
£22.40, £1.50 P&P + VAT

T13A/5
£21.75
£1.50 P&P + VAT

13A/5/R £25.30, £1.50 P&P + VAT

WEL 2
£52.80, £2.25 P&P + VAT

13A/6SW Sloping
£26, £1.50 P&P + VAT

PEL 3
£65, £2.25 P&P + VAT

N13A/3
£16.77, £1.50 P&P + VAT
DELIVERY EX-STOCK

TR9 £38.75, £2.50 P&P + VAT

**FACTORY NO. 8, 5-7 LONG STREET
OLSON Electronics Ltd. LONDON E2 8HJ Tel: 01-739 2343**

WW - 024 FOR FURTHER DETAILS

SAFGAN DT-400 Series BRITISH MAKE DUAL TRACE 'SCOPES



NEW 20MHz

LOW COST
DT-410 £179*
DT-415 £189*
DT-420 £199*
* Ex V.A.T.

RELIABLE WITH 18 months GUARANTEE

DT-410, 10 MHz	DT-415 15MHz	DT-420 20MHz
★ CH1, CH2: 5mv/div - 20v/div.	★ External Trigger	
★ Time Base: 1 sec/div - 100ns/div.	★ Z-Modulation.	
★ XY Facility: Matched XY inputs.	★ CAL output 1v 1kHz.	
★ Trigger: Level control, ± Slope selection.	★ Graticule blue ruled 8x10 div. (4in. CRT).	
★ Auto, Normal, TV Triggering.	★ Size: H215mm, W165mm, D280mm.	
	★ Weight: 4kg.	

PROBE (XI-REF-X10) £11.50

SAFGAN ELECTRONICS LTD.
OMEGA ROAD, WOKING, SURREY TEL. WOKING (04962) 69560
Carrage: England & Wales £7.50 + V.A.T.; Scotland £10.50 + V.A.T.

London Stockist: Audio Electronics - Tel: 01-724 5564
North-West Stockist: Daron Supplies, Warrington, Ches. - Tel: Warrington 64764
Avon Stockist: L. F. Hanney, Bath. - Tel: Bath 24811
Cardiff Stockist: Steve's Electronics Supply Co., Cardiff - Tel: (0222) 41905
Chesterfield Stockist: Keys Electronics, Chesterfield - Tel: (02461) 31696
Newcastle Stockist: Alden Bros. & Co., Newcastle - Tel: 0632 26729
Birmingham Stockist: P.A.T.H. Electronic Services - Tel: 021-327 2339
Derby Stockist: R.T.S. Derby - Tel: (0332) 41236

WW - 036 FOR FURTHER DETAILS

MICROCOMPUTER COMPONENTS LOWEST PRICES - FASTEST DELIVERY

Device	Price	Device	Price	Device	Price	Device	Price
MEMORIES		78L15	0.29	4017	0.45	74LS13	0.22
2114 Low Power		7905	0.58	4018	0.58	74LS14	0.37
200ns	0.84	7912	0.55	4019	0.29	74LS15	0.12
2708 450ns	2.93	7915	0.55	4020	0.58	74LS20	0.12
2716 450ns	2.40	79L05	0.58	4021	0.80	74LS21	0.12
(+5v)		79L12	0.59	4022	0.82	74LS22	0.12
2716 350ns	3.59	79L15	0.59	4023	0.17	74LS26	0.18
(+5v)		LM309K	0.99	4024	0.35	74LS27	0.12
450ns (fan)	5.95	LM317K	3.20	4025	0.18	74LS28	0.18
2732 450ns	3.90	LM324K	4.95	4026	0.80	74LS30	0.12
2732 350ns	4.40	LM338K	4.75	4027	0.30	74LS32	0.12
2532 450ns	3.90			4028	0.55	74LS33	0.18
4116 200ns	0.70	Z80 FAMILY		4031	1.85	74LS37	0.15
4116 150ns	0.84	Z80 CPU	3.49	4033	1.80	74LS38	0.15
4118 200ns	3.38	Z80A CPU	3.99	4034	1.55	74LS40	0.12
4164 200ns	4.65	Z80A DMA	4.95	4035	0.72	74LS42	0.33
4516/4816		Z80A CTC	3.10	4040	0.54	74LS47	0.36
100ns	3.25	Z80 DART	5.45	4041	0.89	74LS48	0.59
5516 200ns	0.38	Z80 DART	5.70	4042	0.54	74LS49	0.59
6116 200ns	5.10	Z80 DMA	9.85	4043	0.59	74LS51	0.14
6116P 200/150ns	7.81	Z80 DMA	11.95	4044	0.84	74LS54	0.15
		Z80 PIO	2.85	4045	1.85	74LS55	0.15
		Z80A PIO	3.15	4046	0.88	74LS73	0.18
		Z80 SIG-0	10.99	4047	0.54	74LS74	0.12
		Z80 SIG-1	11.00	4048	0.54	74LS75	0.24
		Z80 SIG-2	11.00	4049	0.28	74LS76	0.20
		Z80A SIG-1	11.80	4050	0.28	74LS78	0.18
		Z80A SIG-2	11.00	4051	0.59	74LS83	0.44
		MK 3886-4	14.47	4052	0.88	74LS85	0.80
				4053	0.59	74LS86	0.15
				4054	1.20	74LS90	0.28
				4055	0.79	74LS91	0.74
				4060	0.33	74LS92	0.33
				4063	0.95	74LS93	0.33
				4066	0.34	74LS95	0.42
				4068	0.17	74LS109	0.21
				4069	0.17	74LS112	0.23
				4070	0.17	74LS113	0.21
				4072	0.17	74LS114	0.30
				4073	0.16	74LS122	0.39
				4075	0.17	74LS123	0.39
						74LS124	1.20

SUMMER MADNESS

10% DISCOUNT

FOR ANY ORDER OVER £100 (CWO ONLY)

LOW PROFILE - TIM GOLD
8 pin 0.77
14 pin 0.90
16 pin 0.90
18 pin 0.13
20 pin 0.17
24 pin 0.26
28 pin 0.15
40 pin 0.29

ZERO - INSERTION FORCE DIL
24 pin 6.30
28 pin 7.40
40 pin 8.80

CRYSTALS
1 MHz 2.90
1.008 MHz 2.90
1.8432 MHz 2.20
3.6864 MHz 2.95
4 MHz 1.85
6 MHz 1.90
8 MHz 1.95

UNF MODULATORS
6 MHz 3.70
8 MHz 4.40

BBC MICRO-COMPUTER UPGRADES
BBC 1 RAM Upgrade Kit 26.00
BBC 2 Printer User Y/O Kit 9.50
BBC 4 Analogue V/P Kit 6.50
BBC 5 Serial I/O and RGB Kit 11.45
BBC 6 Expansion BUS Kit 7.95
Connectors for BBC 4 2.25
Connectors for BBC 5 0.80
The above kits make up the full Model 'A' to Model 'E' Upgrade for the BBC Microcomputer Special Price when bought complete 62.00


NEW NEC 12" MONITOR
Custom made computer display inc built in speaker and amp. Green phosphor display 149.00 (E10 carriage & VAT)

EPROM Erasers
UM141-14 eprom capacity-built in tuner 78.00 (+£5 carriage & VAT)

HF ANTENNAS



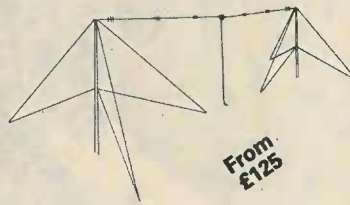- ★ MODE; Full half wave operation.
- ★ BANDS; Up to 4 spot frequencies.
- ★ POWER; Receive to 800W (PEP).
- ★ SWR; Better than 1.5:1 on channel.



THE SMC TRAPPED DIPOLE ANTENNA

has been developed to satisfy the needs of commercial and military users. It is capable of operation between 2 and 30 MHz on as many as four spot frequencies - each capable of accommodating many channels. Excellent matching and efficiency with a single coaxial feed is offered by the use of SMC H1Q traps and the incorporation of a ferrite balun in a full half wave design. NB: Power absorbing terminating resistors are not employed. The antenna may be deployed using one or two support masts, installation (incorporating SMC light duty portable masts) can be easily effected by two people in half an hour.



FT180 "PIONEER" HF SSB TRANSCEIVER. 1.8-18MHz, 6 channels 100 watts RF output measuring only 95(H) x 240(W) x 30(D) mm and weighing 6kg. May be operated as a base or mobile transceiver, complementing our trap dipole and HW4 mobile aerials. Prices start at £500, making this unit not only very attractive but highly competitive.


SOUTH MIDLANDS COMMUNICATIONS LTD.

OSBORNE ROAD, TOTTON Telex: 477351 SMCMM G
SOUTHAMPTON SO4 4DN Tel: Totton (0703) 867333

WW - 009 FOR FURTHER DETAILS

Digital Video Noise Measurement System

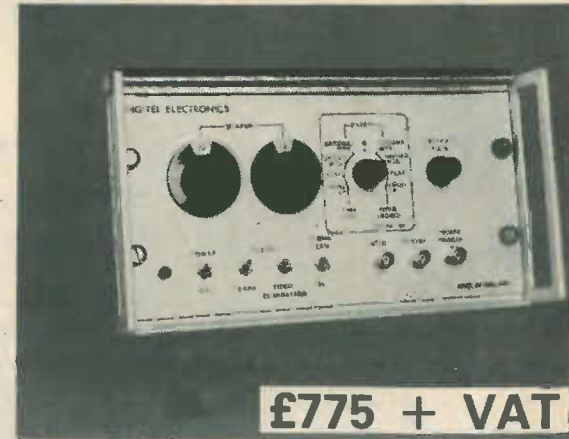The Digital D4060 Noise Measurement System offers an accurate and economical method of measuring video signal to noise ratio on broadcast or industrial TV systems.



£775 + VAT


- Measures signal to noise ratio down to 65dBs SNR
- Field interval SNR measurements are possible with the D4060 option 01
- SNR measurement is possible in the presence of sync pulses, some test signals or free running
- Visual display on oscilloscope ensures measurement confidence
- Full CCIR weighting filter sets are available

DIGI-TEL ELECTRONICS 20 Trenches Road Crowborough, Sussex Tel: Crowborough 5069

WW - 013 FOR FURTHER DETAILS

HBED

PARABOLIC DISHES

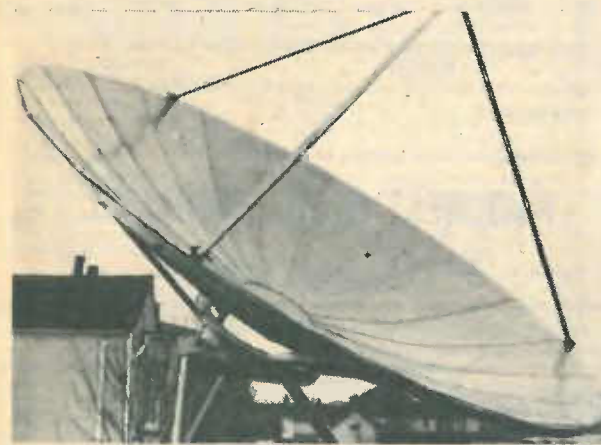

6ft dia. for use in satellite reception and microwave transmissions. Please send S.A.E. for full details and data sheet.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
Tel: Southend (0702) 32338

WW - 035 FOR FURTHER DETAILS

Sowter Transformers

With 42 years' experience in the design and manufacture of several hundred thousand transformers we can supply

AUDIO FREQUENCY TRANSFORMERS OF EVERY TYPE

YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES:

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching

transformers (all powers), Column Loudspeaker transformers up to 300 watts or more. We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal despatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, EEC, USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.

E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941), Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich, IP1 2EG, Suffolk, P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 & 0473 219390; Telex: 987703G SOWTER

WW - 058 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner
Telephone 445 2713/0749 (9461)

WW - 041 FOR FURTHER DETAILS

TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

4 Union Road, Croydon, CR0 2XX
01-684 1422/01-684 0246

WW - 044 FOR FURTHER DETAILS

THE MOST ECONOMICALLY - PRICED PROFESSIONAL EPROM PROGRAMMERS AROUND

SUITABLE FOR EPROMS:
2708, 2516, 2716, 2532, 2732, 2732A
plus option for 2564, 2764

DATAPROM

STARTING AT £395 + VAT
Albetros (Products) Limited Frances Road Basingstoke Hampshire RG21 3DA
Telephone (0256) 57551



WW - 057 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL LONDON'S TEST EQUIPMENT CENTRES CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY

PROFESSIONAL 100 K OHM/VOLT MULTIMETER

30 ranges 15A AC/DC
1.5 KV, 200 meg ohms.
Features mirror scale, polarity reverse, electronic overload protection, taut band suspension.
As advertised by us at £67.50
+ case i.e. £84.00
NOW **£49** inc. VAT
(UK c/p £1.50) with leather case
Exclusive to Audio Electronics



LCD LOW COST MULTIMETERS

DD401 3 1/2 digit LCD 26 range push button 2A AC/DC 20 meg ohm Basic 0.5% **£37.95**
2033A Sabtronics version of above **£39.95**
HC703 0.1% version of above **£54.00**
DM4011A/100m 3 1/2 digit LCD 15 range push button plus Hfe Tester 10A DC (No AC A) **£43.50**
100m 3 1/2 digit LCD 30 range Rotary switch plus Hfe Tester 10A AC/DC **£69.95**
Callers will always find a range of low cost test equipment accessories, tools, irons and boards in stock, also special offers for certain equipment which will vary from time to time
Price correct at time of preparation E&OE
All prices include VAT




CHOOSE FROM UK'S LARGEST RANGE

STOP PRESS Few only £110 23 range 10A AC/DC range hold continuously buzzer plus much more Rotary switch **£59.95**

TRIO CS1566A 20 + 20 MHZ TRIGGERED SWEEP SCOPE

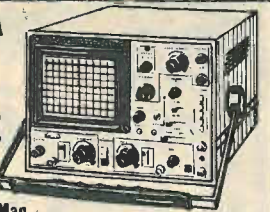5 1/2" (140mm) RECT. TUBE
Video/Norm/Auto. Sync.
5mV/ 0.5pS/CH2 Inv. / X10 Mag.
DC to 20 MHZ/
19 Sweep Ranges.



As advertised by us at **£363.40** inc. VAT
LIMITED QUANTITY **£320.00** inc. VAT
(£278.26 + VAT) (UK c/p £4.00)

Optional Probes X1:7.95, X10:9.45, X1-X10:10.50



TRIO OSCILLOSCOPES

Range of mains operated Scopes with 5" displays, triggered sweep (UK c/p £3.50)

DUAL TRACE
CS1562A 10 MHZ; 10mV; 1 micro sec. **£267.95**
CS1560A 11 15 MHZ; 10mV; 0.5 micro sec. **£341.55**
CS1566A 20 MHZ; 5mV; 0.5 micro sec. **£320.00**
CS1577A 35 MHZ; 2mV; 0.1 micro sec. **£523.25**
CS1820 20 MHZ; 2-5mV 1 micro delay sweep **£483.00**
CS1830 Mk II 300 MHZ; 2mV; 0.2 micro sec (fitted delay line) **£626.75**
CS1575 5 MHZ; 1mV; 0.5 micro sec. Multi display Audio scope. **£312.80**


SINGLE TRACE
CD1303D 5 MHZ; 10mV, low sweep for observation below 1 HZ and up to 450 MHZ; 75mm display (UK c/p £2.00) **£124.20**

DIRECT READ HV PROBE

(UK c/p 65p)

0/140KV: 20K Volt **£18.40**

MULTIMETERS

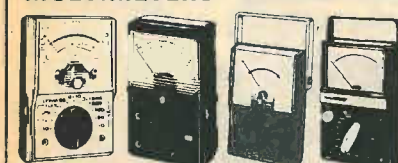

(UK c/p 65p or £1.00 for two)

CHOOSE FROM UK'S LARGEST RANGE

KRT101 10 range pocket 1K/Volt **£4.95**
KRT100 12 range pocket 1K/Volt **£5.50**
T10L 12 range 1K/Volt + overload **£5.75**
NH55 10 range pocket 2K/Volt **£6.50**
RT5 11 range pocket 4K/Volt **£7.50**
AT1 12 range pocket Deluxe 2K/Volt **£8.95**
NH50R 22 range pocket 20K/Volt **£11.50**
YK300TR 19 range plus Hfe test 20K/Volt **£14.95**
KRT6001 16 range 10 amp DC range double 50K/Volt **£17.95**
ST303TR 21 range plus Hfe Test 20K/Volt **£18.95**
AT1020 19 range Deluxe plus Hfe Test 20K/Volt **£18.95**
EC15000 As KRT5001 plus colour scales 50K/Volt **£18.95**
7081 18 range double 10A DC 50K/Volt **£23.75**
TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt **£24.50**
168m 36 range large scale 10A AC/DC 50 K/Volt **£28.50**
AT2050 17 range Deluxe plus Hfe tester 50K/Volt **£29.95**
AT210 23 range Deluxe 12A AC/DC 100K/Volt **£32.50**
300TR 23 range large scale 10A AC/DC Hfe test 50 meg ohm. 1KV AC/DC 100 K/Volt **£39.95**


SCOPE ADD ON UNITS

LTC905 Semiconductor Curve tracer **£95.45** (post 85p)
HZ65 Component Tester **£29.95** (Post 55p)

OSCILLOSCOPE PROBE KITS

(UK c/p 50p per 1 to 3) Available BNC plug or Banana X1 **£7.95**; X10 **£9.45**; X1-X10 **£10.50** Also X100 (BNC only) **£16.95**

CLAMP-ON-METERS INSULATION TESTERS

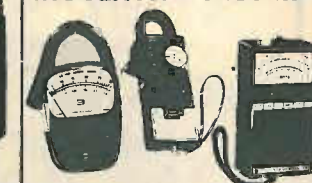

Multi-range clamps all with resistance range, carry case & leads. Also digital and DC clamp in stock (UK c/p 75p)
ST300 300A 600V 9 ranges **£25.95**
ST310 300A 600V 9 ranges **£28.95**
K2602 150A, 600V, AC 7 ranges **£35.95**
*K2606 300A, 600V, AC 8 ranges **£49.50**
K2803 300A, 600V, AC 9 ranges **£59.95**
K2903 900A, 750V, AC 9 ranges **£77.50**
K2103 1000A, 750V, AC 9 ranges **£95.00**
*Optional temperature probe **£13.80**

ELECTRONIC INSULATION TESTERS

Battery operated complete with carry case (UK c/p £1.00)
YF500L 500V/100Meg. Plus 0-100 ohm **£85.00**
K3103 600V/100Meg. Plus 0-2.6K ohm **£109.00**
K3106 500V & 1000V, 1000 & 2000Meg. **£119.00**
K4101 Earth resistance tester **£149.00**
M500 Hand cranked insulation tester 500V/100Meg. **£79.50**



LOGIC PROBE

(UK c/p 45p)
Leader LDP076 50 MHZ 10MEG ohm, 10n Sec with carry case, LPT6 10Mhz probe **£29.50**
£56.90

GROTECH OSCILLOSCOPES

Range of Portable Scopes mains and battery operated. Plus special features (UK c/p £3.00)

3030 Single trace 15 MHZ, 5mV, 0.5 micro secs. Plus built in component tester. 95mm tube **£172.50**
3131 Dual trace 15 MHZ, trg to 35 MHZ, 5mV, 0.5 micro sec. 130mm tube, plus component tester. **£276.00**
3034 Battery-mains dual trace 15 MHZ, trig to 20 MHZ built in Nicads, 5mV, 0.5 micro secs. (Eliminator charger optional **£28.75**) **£356.50**
Also Available 3033, single trace 3034 3337, dual MHZ, 130mm **£322.00**
£454.00

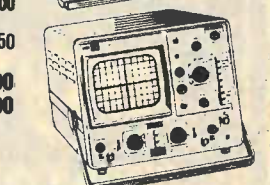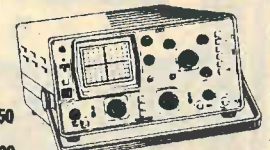


STOP PRESS Model 3035 was **£189.75** - Special Offer **£168.50**

THANDAR - SINCLAIR

Reliable low cost portable instruments, bench models all 25.5 x 15 x 15cm. Generators mains operated rest battery (supplied). UK c/p Hand models 65p, bench £1.15)

DIGITAL MULTIMETERS (3 1/2 digit LCD)
TM354 Hand held, DC 2A, 2m ohm, 1mV - 1000V DC, 500v AC. **£45.94**
TM352 Hand held, DC 10A, Hfe test. Continuity test **£57.44**
TM353 Bench 2A AC/DC 1000V AC/DC 20M ohm. Typical 0.25% **£86.25**
NEW LOW PRICE
TM351 Bench, 10A AC/DC, 1000V AC/DC, 20M ohm Typical 0.1% **£113.85**
FREQUENCY COUNTERS (8 Digit)
PFM200A Hand held LED 200 MHZ 10mV (600 MHZ with TP600). New Model fitted BNC sockets. **£67.50**
TF040 Bench LCD. 40 MHZ, 40mV (400 MHZ with TP600) **£126.50**
TF200 Bench LCD. 200 MHZ, 10-30mV (600 MHZ with TP600) **£166.75**
TP600 600MHZ + 10 Prescaler 10mV **£43.13**
GENERATORS (All bench models) mains operated
TG100 Function 1HZ-100 KHZ. Sine/SQ/Triangle/TTL **£90.85**
TG102 Function 0.2 HZ-2 MHZ Sine/SQ/Triangle/TTL **£166.75**
TG105 Pulse. 5 MHZ-5HZ (200nS-200mS) various outputs **£97.75**
OSCILLOSCOPE (Bench model low power portable) 10 MHZ 2" trace, 10mV, 0.1 micro sec. All facilities. Model SC 110 **£159.85**
Rechargeable battery pack **£8.83**, AC adaptor / charger **£5.69**
OPTIONAL ITEMS
Carry case (bench only) **£6.84** AC Adaptors (state model) **£5.69**

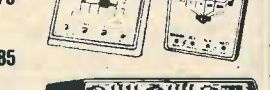

KEITHLEY PROFESSIONAL DIGITAL MULTIMETER UK c/p 75p

Model 130, 25 range. Easy to hold and use!
LCD, DMM, Size 7 x 3.1 x 1.5
Ranges
DC Volts 200mV-1000V 0.5% 100 micro volt
AC Volts 200mV-750V 1% 100 micro volt
DC current 2mA-10AMP 1-2% 1 micro amp
AC current 2mA-10AMP 2% 1 micro amp
Resistance 200 ohm-20 Meg 0.5% 0.1 ohm **£102.35**
Model 129 as above **£79.35**



TV COLOUR GENERATORS

PAL UHF and VHF Models
LCG383 VHF 6 pattern **£143.75**
LCG382u UHF 15 pattern **£228.85**
LCG382v VHF 15 pattern **£231.15**
LCG399 VHF/UHF 13 pattern **£572.70**
MC101 UHF pocket colour } **£162.50**
Fitted NICADS

AUDIO ELECTRONICS CUBEGATE LIMITED
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564
ALSO AT HENRY'S RADIO, 404/406 EDGWARE ROAD, LONDON W2
WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order
Allow up to 10 days for delivery


Send large SAE (20p UK) Schools, Companies, etc. free on request.

ALL PRICES INCLUDE VAT

WIRELESS WORLD JULY 1982

WW - 005 FOR FURTHER DETAILS

Testing...
Testing...
Testing...

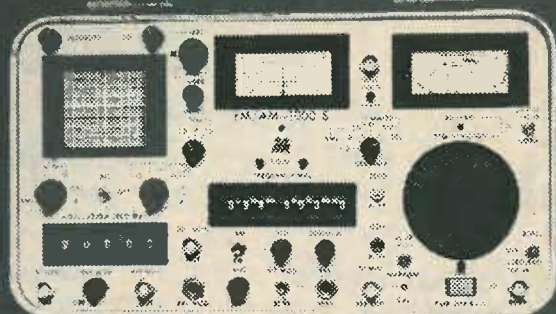

anywhere!

FM/AM 1000s with Spectrum Analyser — we call it the SUPER — S

A portable communications service monitor from IFR, light enough to carry anywhere and good enough for most two-way radio system tests. The FM/AM 1000s can do the work of a spectrum analyser, oscilloscope, tone generator, deviation meter, modulation meter, signal generator, wattmeter, voltmeter, frequency error meter — and up to five service engineers who could be doing something else!

**A PRACTICAL TOP UP!
MM-100 MULTI-METER**

Simply replaces the protective lid of the FM/AM 1000s. It includes a modified probe, PB-114, and a built in speaker unit with independent volume control for audible response to signal measurement. This practical 'top up' will perform the following functions.

Sinad: Measurements for 1 kHz tone (± 20 Hz)

Distortion: To 30%
DC Volts: Up to 300 volts and up to 800 volts when the X10 probe is used

AC Volts: 600 VRMS maximum for frequencies between 25 Hz and 25 kHz

Ohms: Using the modified probe, part number PB-114, Ohms can be measured on scales X1 to X10 K
% AM Measured on the RF signal applied to the FM/AM-1000 unit

OPTIONAL ACCESSORIES

A choice of R.F. power attenuators and protective carrying cases.



For further information contact Mike Taylor



**Fieldtech
Heathrow**

Fieldtech
Heathrow Ltd.
Huntavia House
420 Bath Road
West Drayton
Middlesex UB7 0LL
Tel: 01-897 6446
Telex: 23734
FLDTEC G

IFR precision simulators

WW - 025 FOR FURTHER DETAILS



Just 50p will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS — PLUS MICROPHONES — AMPLIFIERS — MIXERS — COMBOS — EFFECTS — SPEAKER STANDS AND BRACKETS — IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our listening lounge. (Customer operated demonstration facilities)
- ★ Ample parking ★
- ★ Access · Visa · American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



WW - 040 FOR FURTHER DETAILS

**INDUSTRIAL MUSCLE
AT A REALISTIC PRICE**




- * POWER BANDWIDTH DC to 100KHZ \pm 1db
- * OUTPUT POWER IN EXCESS OF 500 WATTS PER CHANNEL INTO 2 OHMS OR IN EXCESS OF 1KW SINGLE CHANNEL IN BRIDGE MODE INTO 6 OHMS
- * HARMONIC DISTORTION LESS THAN 0.01% DC TO 100KHZ AT 1KW INTO 6 OHMS
- * INTERFACE BOARDS CAN BE CUSTOM DESIGNED AND BUILT TO CATER FOR A WIDE RANGE OF SPECIALISED USES
- * OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD
- * UNCONDITIONALLY STABLE INTO ANY LOAD
- * BASIC PRICE INCLUDING BRIDGE MODE SWITCHING AND HANDLES £455

S & R AMPLIFICATION

6 Tanners Hill, London S.E.8
Telephone: 01-692 2009

WW - 038 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

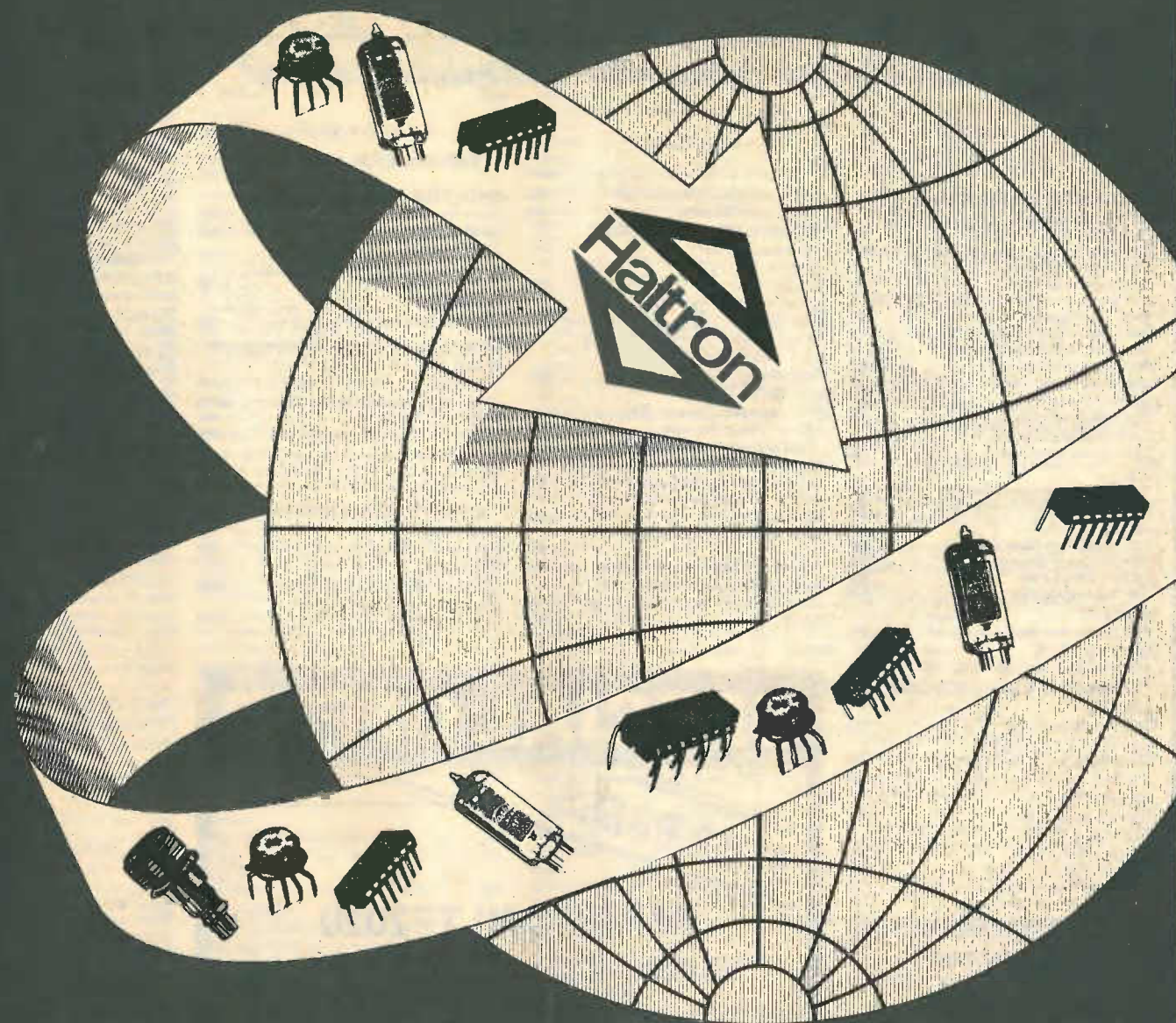

The Professionals

VALVES, SEMICONDUCTORS & COMPONENTS for:-

Communications, Displays, Radar, Computer, Audio etc.

Hall Electric Limited
Electron House
Cray Avenue, St. Mary Cray
Orpington, Kent BR5 3QJ
Telephone: Orpington 27099
Telex: 896141

MIN DEF APPROVAL 0529/0531

WW - 021 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

Carston

Used test equipment, calibrated to Manufacturer's original specification.

ACOUSTIC & VIBRATION

BUELL & KJAER	
1621 Tunable Band Pass Filter	550
2113 Audio Frequency Spectrometer	1400
2203 Sound Level Meter	450
2215 Sound Level Meter inc. Oct. Filter	1050
2218 Sound Level Meter inc. Leq.	1475
2305B Level Recorder inc. 50 dB pot.	1350
2625 Vibration pick-up amplifier	350
2808 Power Supply/Mains Adapter	90
2972 Tape Signal Gate	200
4230 Sound Level Calibrator	120
4423 Noise Dosimeter	350
4424 Noise Dosimeter	375
CASCADE ACOUSTICS	
CS181 Sound Level Meter & Calibrator	295
C.E.L.	
112 Environmental Noise Analyser	300
144 Environmental Noise Analyser	500
DAWE	
419C Audio White Noise Generator	190
1461CV Vibration Analyser	350
1463B 1/2 Octave Filter	200
1465 Octave Band Filter	150
KISTLER	
504A Charge Amplifier	200
WAYNE KERR	
8731B Vibration Meter inc. probe	270

BRIDGES & V AND I STANDARDS

CINTEL	
2773 Inductance Bridge	160
HEWLETT PACKARD	
4261A Digital Automatic LCR Bridge	975
4342 QLC Meter 22 KHz-70 MHz	2600
MUIRHEAD	
D30A DC Bridge 0.15%	180
WAYNE KERR	
8224 RCL Bridge 0.1%	500
8521 LCR Bridge	115
8901/CU681/Q801/SR268 VHF	
Admittance Bridge with source and	
detector transistor adapter & D.C. Control	
Unit for transistor measurements	750

COMMS & CABLE TEST EQUIPMENT

DYMAR	
BC282 Battery charger for 883 Radio	
Telephone	80
883 Radio Telephone - VHF band - hand	
held	245
MARCONI	
TF2091 White Noise Generator (exc. filters)	1000
TF2092 White Noise Receiver (exc. filters)	1000
TF2809 Data Line Analyser	600
NORTHEAST ELECTRONICS	
TT537B Psophometer/VU Meter	200
SEIMENS	
U2033 Psophometer	475
S.T.C.	
74106 Bridge Unit	135
74184B Selective Level Measuring Set	600
74216A Noise Generator	300
74261A Psophometer	300
74262B White Noise Generator & Receiver	2000
74307C Level Measuring Set	175
74834C Distortion Measuring Set	500
96016 Selective Null Detector	200

Carston Electronics Ltd
01-267 5311

Shirley House, 27 Camden Road, London NW1 9NR. Telex: 23920.

GTA-2 Quantization Distortion Tester	800
GTA4B Pattern Generator	900
COMPUTER EQUIPMENT (90 day guarantee)	
CENTRONICS	
702 matrix printer	500
HEWLETT PACKARD	
9835A Desktop Computer 64K + expanded	
I/O ROM + HP - IB interface. Includes	
C.R.T. Cartridge Tape Drive - Full	
documentation test tapes etc.	5900
TEKTRONIX	
4610-1 Hard copy printer for 4010 series	
computer display terminals	1500
COMPUTERS & TIMERS	
FLUKE	
1912 520 MHz 7 digit Counter	375
1912A01 As 1912A but inc. re-charging	
batteries	430
1920A 520 MHz 9 digit Counter inc. Brst.	
mode	575
1920A14 1250 MHz otherwise as 1920A	750
HEWLETT PACKARD	
5300A/5305B 1300 MHz 6 Digit Counter	425
5345 500 MHz 11 Digit Counter Timer	2000

SYSTRON DONNER	
6053 3 GHz 9 digit Counter BCD O/P	790
5103B Strip Printer for 6053/6054	375
TEKTRONIX	
DC501 7 Digit 100 MHz Counter - TM500	
Plug-in	180
VENNER	
1000F 32 MHz 7 digit counter/timer	190
DIGITAL TESTING EQUIPMENT	
HEWLETT PACKARD	
1600A Logic Analyser 16 ch 20 MHz	1150
1600S Logic Analyser 32 ch 20 MHz	2250
1602A Logic Analyser 16 ch 10 MHz	900
1615A Logic Analyser 24 ch 20 MHz	4850
TEKTRONIX	
832 Datacom Tester R5232/V24	1150
833 As 832 plus BERT/BLERT feature	1300
MAINS TEST EQUIPMENT	
DATALAB	
DL019 Mains Interface for DL905	300
DRANETZ	
606 3ch Volts Av/Spike/Time/Printer	2950
616 2ch AC 1ch DC Volts/Av/Spike/	
Time/Printer	3300

SPECIAL OFFER

STOP PRESS

MARCONI TF2020

50 KHz - 520 MHz Synthesised Signal Generator
High Accuracy - High Stability
High Performance - Full AM/FM Facilities

LOW PRICE!

Two units only available at this price

£5500

MARCONI	
TF 2432 560 MHz 8 Digit Counter	350
PHILIPS	
PM6614/02 520 MHz 9 Digit Counter TCXO	480
PM6624/02 520 MHz 9 Digit Counter Timer	750
TCXO	180
PM6661 80 MHz 8 Digit Counter	
RACAL-DANA (E.I.P.)	
371 18 GHz 11 Digit Counter with Source	
Locking facility	4950
371 18 GHz 11 Digit Counter with high stab	
xtel option. Source Locking facility.	
HP-IB opt	5500
8110 50 MHz 8 Digit Counter Timer	320
9025 1 GHz 8 Digit Counter	450
9903 50 MHz 7 Digit Counter Timer	350
9905 200 MHz 8 digit Counter Timer	360

GAY	
LDM AC/DC/Spike/Time inc. Printer	900
MISCELLANEOUS	
A.I. INDUSTRIES	
TCS General Purpose Gas Leak Detector -	
intrinsically safe	290
BRADLEY	
192 Oscilloscope Calibrator	825
COMARK	
1601BLS Thermom 10ch 87 + 1000°C type K	50
N.B. Thermocouples not included	
CROWCON	
71P Inflammable Gas Detector/Alarm	125
DATALAB	
DL905 Digital Transient Recorder/Display	1050
Storage	

FLANN

16/11 Rotary Vane Attenuator WG16	
HEWLETT PACKARD	
342A Noise Figure Meter	
X382A Rotary Vane Attenuator WG16	
536A 0.96-4.2 GHz Cavity Frequency Mejer	
MEGGER	
BM6 500V 0 - 200 mΩ tester. Batt op.	
MJ4 1 kV 0 - 200 mΩ tester. Hand Drive	

MULTIMETRICS	
AF120 Dual H/Pass L/Pass active	
filter 20 Hz - 2 MHz	790
PHILIPS	
PM 5501 Colour TV Pattern Generator	375
PM 5519 Colour TV Pattern Generator	
PM 5456 Stereo FM Generator	
RADIOMETER	
SMG1 Stereo FM Generator	
ROHDE & SCHWARZ	
BN252 Transistor Y Parameter Test Set	150
SCHLUMBERGER	
4010A VHF/UHF Radio Telephone Test Set	650
S.T.C.	
74600J Attenuator 0-9 dB 50Ω in 1 dB	
steps	12
74616A Attenuator 0-100 dB 600Ω in 0.1 dB	
steps	18
TEKTRONIX	
184 Time Mark Generator	29
521PAL Vectorscope	275
528 TV Semicom Monitor	75
575 Semiconductor Curve Tracer	42
1485C TV Waveform Monitor PAL/NTSC	310
TELONIC	
6001 RF Detector with Log Amplifier -	
Analogue display & recorder O/P. 0.4-130	
MHz - 80 dB range	
YELLOW SPRINGS	
YS157 Water Pollution Measurement	
System	30

NETWORK ANALYSERS/ PHASEMETERS	
DRANETZ	
301A Analogue Phase Meter 5 Hz-500 KHz	7
GENERAL RADIO	
1710/11/12/14 0.4-500 MHz 115 dB range	370
HEWLETT PACKARD	
8405A Vector Voltmeter 1-1000 MHz	310
8407A/8412A/8601A 100 KHz-110 MHz	
complete Network Analyser system	
comprising Analyser, Phase/Magnitude	
display and Sweep Generator. 50Ω or 75Ω	
system available. 80 dB dynamic range	
8745A S Parameter Test Set 0.1-2 GHz	650
11570A Accessory Kit for 8405A	310
11600A Transistor Test Fixtures	
TO18/TO-72	12
11602A Transistor Test Fixtures	
TO5/TO-12	12
11604A Universal extension arm for 8745A	28
11605A Flexible arm for 8743A	28

OSCILLOSCOPES & ACCESSORIES	
CROTECH Oscilloscopes	
These are brand-new instruments	
3030 15 MHz 1 Trace 5mV built-in	
component tester	150
3033 15 MHz 1 Trace 5mV battery	
operation	150
3034 15 MHz 2 Trace 5mV battery	
operation	150
3131 15 MHz 2 Trace 5mV built-in	
component tester	240
3337 30 MHz 2 Trace 5mV with signal	
delay	395
BIOMATION	
350 Compact XYZ Display	4
GOULD ADVANCE	
OS1000B 20 MHz 5mV 2 Trace	14
HEWLETT PACKARD	
1740A 100 MHz 5mV 2 Trace 2T B	13
182C 100 MHz Mainframe	
182T 100 MHz Mainframe with digital	
normaliser interface	15
1804A 50 MHz 20mV 4 Trace Plug-in	62
1825A Dual Timebase Plug-in	50
1805A 100 MHz 5mV 2 Trace Plug-in	62

PHILIPS	
PM3207 15 MHz 5mV 2 Trace TV trig	25
PM3211 15 MHz 2mV 2 Trace TV trig	299
PM3212 25 MHz 2mV 2 Trace TV trig	499
PM3233 10 MHz 2mV 2Ch fixed delay Dual	
Beam	250
PM3244 60 MHz 5mV 4 Trace 2T base	1250
PM3260 120 MHz 5mV 2 Trace 2T base	1475
PM3262 100 MHz 5mV 2 Trace 2T base	
Tr View	1150

TEKTRONIX	
465 100 MHz 5mV 2 Trace 2T B	60
465B 100 MHz 5mV 2 Trace 2T B	
475 200 MHz 2mV 2 Trace 2T base	1750
476A 250 MHz 2mV 2 Trace 2T base	2200
485 350 MHz 5mV 2 Trace 2T base	3600
5842 2 T base plug-in 50 MHz Trig for 5000	
series Mainframe	325
681/4S3/5T1A 1 GHz Sampling scope	595
7A18 75 MHz 5mV 2 Trace Plug-in	420
7A22 1 MHz 10µV Differential Plug-in	595
7A28 200 MHz 5mV 2 Trace Plug-in	655
7953A 2 Timebase Plug-in 100 MHz Trig	650
7403N 75 MHz 3 slot M/Frame	990
7603 100 MHz CRT r/out 3 slot M/Frame	1350
TELEQUIPMENT	
D83/V1/V1 15 MHz 2 Trace 1mV	370
D83/V5/V5 15 MHz 5mV 2 Trace & fixed	
delay	390
561 5 MHz 5mV 1 Trace	135
TEXSCAN	
DU120 Large CRT XY Display with	
z modulation	280
Note: we hold a range of cameras	P.O.A.

OSCILLOSCOPES (STORAGE)	
HEWLETT PACKARD	
181A 100 MHz Mainframe 5cm/µs	2500
1703A 35 MHz 10mV 2 Tr 2TB 1000 Div/µs	1400
TEKTRONIX	
466 100 MHz 5mV 2 Tr 2TB 1350cm/µs	2950
7313 25 MHz 3 slot M/ frame split screen	
5cm/µs	1700
7613 100 MHz 3 slot M/ frame 4.5cm/µs	2700

POWER MEASUREMENT	
HEWLETT PACKARD	
432A RF-Microwave Powermeter for use	
with 470 series sensors	430
478A Co-ax sensor for 432 meter	
10 MHz-10 GHz	160
X488A Power sensor for 432 meter W.G. 16	
432A/478A combined price	560
432A/X488A combined price	560
8482H Co-ax sensor for 435/436	
100 KHz-4.2 GHz	220
MARCONI	
2502 R.F. Powermeter DC-1 GHz 10W max	475
2503 R.F. Powermeter DC-1 GHz	
100W max	800
6480/6421 Microwave Powermeter &	
sensor 0.01-12.4 GHz	500

POWER SUPPLIES etc	
ADVANCE	
MG5-20 Switching PSU module 5V-20A	
fixed	90
BRANDENBURG	
800 EHT Power supply 3-30 KV-1mA	450
FARNELL	
B30/5 0-30V-5A variable	110
B30/20 0-30V-20A variable	225
FFSL 5V - 20A PSU module	80
S830/10 0-30V-10A variable	190

HEWLETT PACKARD	
6268B 0-40 V variable 30 A Metered V + I	575
PULSE GENERATORS	
ADVANCE	
PG 52A Modular pulse generator system -	
wide range of configurations - cost	
dependent on modules - typical	650


PG5002D 0.1 Hz-1 MHz 50V 100Ω Double	
pulse R.T. 15ns	290
HEWLETT PACKARD	
8011A 0.1 Hz-20 MHz 16V 50Ω RT 10ns inc	
Burst mode	475
8016A Digital word generator to 50 MHz	
9 x 32 bit	3400
LYONS	
PG73N 20 MHz 10V 50Ω R.T. 5ns	390

RECORDERS & ACCESSORIES	
BRYANS SOUTHERN	
BS314 Chart 10" 4 Pen 16 speed	1900
DCM	
8100W Wow & Flutter Analyser	800
EM	
LVDT Linear Displacement & Transducer	50
FYLDE	
154 Bridge supply and Amplifier	110
HEWLETT PACKARD	
680M Chart 5" 1 pen 8 speed	760
7015A XY 1 pen A4 size	700
HONEYWELL	
5900B Instrumentation tape recorder 14 ch	
FM/DR	9000
MICRO-MOVEMENTS	
M10-120/A Compact UV 10 ch 7 speed	
recorder (inc. galvanos)	4900
PHILIPS	
PM8251 Chart 10" 1 pen 12 speed	375
SE LABS	
994 6 ch galvo preamp + DC bridge supply	450
6008 UV chart 8" 25 ch 16 speed	950
6150/51 UV recorder 12 ch-inc 6 ch amps	1275

SEIMENS	
M336 Chart 5" 1 pen 0-20 mA F.S.D. but	
can readily be adapted by internal links to a	
wide range of volt and current	
measurements	150
SOLARTRON	
3240 Modular Data Logger system	P.O.A.
Notes: UV recorders are priced less galvanos	

SIGNAL ANALYSIS EQUIPMENT	
AIRMEC	
210 AM/FM Mod Meter 2.25 MHz-	
300 MHz	235
248A Wave Analyser 5-300 MHz	200
853 Wave Analyser 30 KHz-30 MHz	200
MARCONI	
TF2330A Wave Analyser 20 Hz-76KHz	900
RADFORD	

PCI 1002 IEEE THERMOCOUPLE CONVERTER

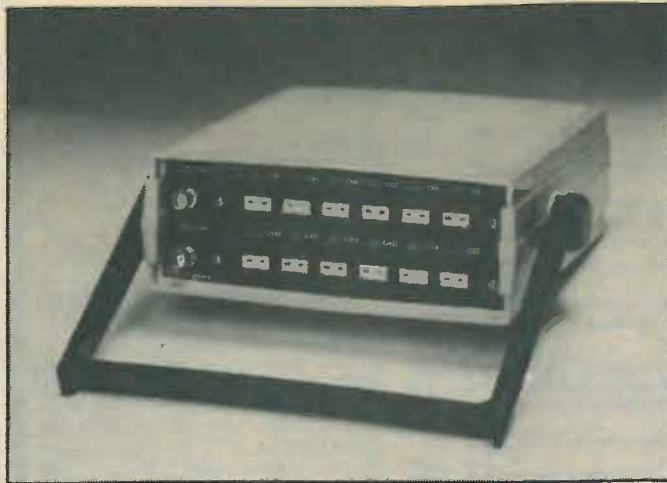

The PCI 1002 is a 12 Channel IEEE compatible thermocouple converter having two input ranges of $\pm 10\text{mV}$ or $\pm 100\text{mV}$ F.S.D. selected by an internal switch. It has 12 Bit resolution of the A to D converter giving a resolution of 0.06 deg.C on 10mV range and covers all common thermocouple types.

Cold Junction Compensation is provided giving a resolution of 0.2°C on 100mV range and 0.02°C on 10mV range.

Linearising software in Basic using optimised coefficients for ranges and thermocouple types.

Two other channels are provided via BNC input sockets on the front panel. Input ranges are 1/V for 10 mV range and $\pm 10\text{V}$ for 100mV range.

CIL MICROSYSTEMS LTD
DECOY ROAD, WORTHING, SUSSEX.
TEL: 210474.



WW - 055 FOR FURTHER DETAILS

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£4.25
Cassette recorder—May 1976—1 s.s.	£5.00
Audio compander—July 1976—1 s.s.	£4.25
Audio preamplifier—November 1976—2 s.s.	£8.50
Additional circuits—October 1977—1 s.s.	£4.00
Stereo coder—April 1977—1 d.s. 2 s.s.	£8.50
Low distortion disc amplifier (stereo)—September 1977—1 s.s.	£2.00
Low distortion audio oscillator—September 1977—1 s.s.	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s.	£12.00
Morsemaker—June 1978—1 d.s.	£4.50
Metal detector—July 1978—1 d.s.	£3.75
Oscilloscope waveform store—October 1978—4 d.s.	£18.00
Regulator for car alternator—August 1978—1 d.s.	£2.00
Wideband noise reducer—November 1978—1 d.s.	£5.00
Versatile noise generator—January 1979—1 s.s.	£5.00
200MHz frequency meter—January 1979—1 d.s.	£7.00
High performance preamplifier—February 1979—1 s.s.	£5.50
Distortion meter and oscillator—July 1979—2 s.s.	£5.50
Moving coil preamplifier—August 1979—1 s.s.	£3.50
Multi-mode transceiver—October 1979—10 d.s.	£35.00
Amplification system—Oct. 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s.s.	£7.50
Colour graphics system—April 1980—1 d.s.	£18.50
Audio spectrum analyser—May 1980—3 s.s.	£10.50
Multi-section equalizer—June 1980—2 s.s.	£8.00
Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V)	£4.00
Nanocomp 6802 or 6809—Jan., July, 1981—1 d.s. 1 s.s.	£9.00
Cassette interface—July, 1981—1 s.s.	£1.50
Eprom programmer—Jan., 1982—1 d.s.	£4.50
Logic probe—Feb., 1981—2 d.s.	£6.00
Modular frequency counters—March, 1981—8 s.s.	£20.00
Opto electronic contact breaker (Delco)—April, 1981—2 s.s.	£4.00
CB synthesiser—Sept.—1 d.s.	£6.00
Electronic ignition—March, 1982—1 s.s.	£4.00

Boards and glassfibre roller-tinned and drilled. Prices include VAT and UK postage. Airmail add 30%, Europe add 10%. Insurance 10%. Remittance with order to:
M. R. SAGIN, NANCARRAS MILL, THE LEVEL CONSTANTINE, FALMOUTH, CORNWALL

WW - 037 FOR FURTHER DETAILS

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sealed base ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin DIL socket. Ten at 65p ea.; per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR LP1171 Integral amplifier, 8v. D.C. £3.50 ea. PHOTO CONDUCTIVE CELL LP1186 High-power CdS cell, 600mW, for control circuits. Resistance 800 ohm to 4k. Max. volts 240. Size 1 1/2 x 1/2in. RIBBON MICROPHONE LP1157 with pre-amp. on chassis. £1.75.	MULLARD MODULES LP1179 IF, Strip AM, FM Front end. Pair £5.75 Complete with Data LP1186 LP1157 varicap Med. & Long Tuner £2.50	ULTRA SONIC TRANSDUCERS 40K/C.S. Complete on 18in. Screened cable. £1.75 each, pair £2.95. ULTRA SONIC TRANSMITTER Complete unit (uncased requires 1.5V) £3.25 FOSTER DYNAMIC MICROPHONES 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
U.H.F. MODULATORS Latest type, adjustable, ideal for computers. with data circuit. Size 3x2 1/2x1 inch. Only £3.50 In screened case	LM380 Amplifier 85p LM318N Hi-Slew Op. Amp. £1.50 LM323K, 5v. 3-amp. reg. £3.50 LM310N Volt. follower £1.20 LM311H High Perf. Volt. Comparator £1.00 LM384N, 5-watt Amp £1.20 LM393N Dual Com. 50p 7905 Reg. 75p	MINIATURE HIGH-QUALITY FANS "Whisper Model" by Rohm. Low-power consumption (less than 10 watts). Silent running. 115v. (also in series for 230v.). 50/60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY £6.50 EACH incl. V.A.T. BRAND NEW 50% less than manufacturer's price	STEREO CASSETTE MECHANISMS 6 or 12 volt. Complete with Heads + Erase and Solenoid. Brand new..... £5.90 ea. TV CONVERGENCE POTS (LW) 50 ohm ALL 100 " 50p 200 " 50p 5K " 50p
MONSANTO INDICATOR METER With illuminated dial scale 0-10. F.S.D. 100 microamp. Size 1 1/2 x 1 1/2 x 1/2 deep. Only £1.65.	STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate. Record/Replay £2.00 MARRIOTT TAPE HEADS Quarter track. Type XRP518 Record/Replay (each)..... £2.00 XRP538 Record/Replay (each)..... £3.00 XES11 Erase (each)..... £1.00	NEWLETT-PACKARD DISPLAYS 5062-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each Set of 6 for £5 Half-inch red common anode will replace DL70/14-pin DIL	EX-MOTOROLA 5 + 5-WATT CAR STEREO AMPLIFIERS Complete and tested units. Supplied as two built units (5 x 2 x 2in) with circuit and data. Only £5 pair. includes pre-amp.
BRIDGE RECTIFIER 800 PIV 35 amps 1 1/2 x 1 1/2 x 1/2in. £3.50	RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC. M/AA 225..... £1.50 DRYFIT 6-volt, 4.5 amp. £7.50	"CHERRY" ADD-ON KEYPAD A compact 12-button keypad suitable for use with Keyboard extend its functions plus four extra keys. Supplied brand new LIST PRICE £22.00 OUR PRICE ONLY £7.50 incl. V.A.T.	
NATIONAL P 8000A Chips £2.95 6216 £1.75 INTEGRAL BIDDIES Full spec. but no polarity band. Per 1,000..... £10 MINIATURE M.P.C. POTENTIOMETERS Model M2. High quality, 5% tolerance, 2-watt, with tin. solderless. All values, 47 ohms-47k only 60p each per 10; 50p each per 100; 40p each.	XTAL FILTER 10.7 mc/s. 12.5dB separation. 1 1/2 x 1 1/4 x 1 inch. £7.00 100K/C/S + 1 meg. 3-pin single mode keyboard £2.00		

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated). DELIVERY from stock - Add post 35p per order.

HENRY'S EXPORT enquiries invited
01-723 1008/9
TELEX 262284 Transonics Mono 1400
Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

WIRELESS WORLD JULY 1982

The Logic Probes

Spend Less

Test More

LP-1 Logic Probe
The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

£31.00*

*Model LP-3 illustrated

LP-2 Logic Probe
The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,

replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £12.50)

£18.00*

*Model LP-3 illustrated

*price excluding P.&P. and 15% VAT

LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

£49.00*

*Model LP-3 illustrated

The New Pulsar DP-1

The Digital Pulsar: another new idea from G.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

£51.00*

*Model LP-3 illustrated

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 7ii
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

G.S.C. (UK) Limited, Dept. 7ii, Unit 1, Shire Industrial Estate, Saffron Walden, Essex CB11 3AQ.

Prices include P.&P. and 15% VAT

LP-1	£37.38	Qty.	LP-2	£22.42	Qty.	LP-3	£58.08	Qty.	DP-1	£60.95	Qty.	LPK-1	£15.52	Qty.
------	--------	------	------	--------	------	------	--------	------	------	--------	------	-------	--------	------

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The G.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately. For FREE catalogue tick box


WW - 054 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC - 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

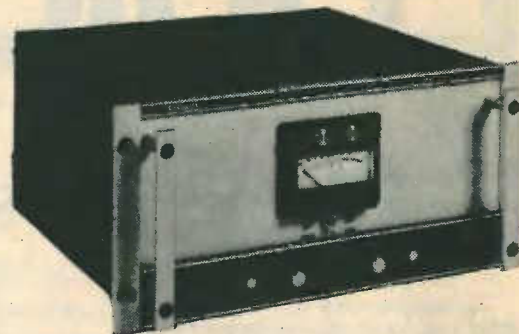

Model - M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 060 FOR FURTHER DETAILS

ERASERS FOR THE DEVELOPMENT LAB



UVIT
Powerful, compact unit to erase up to six EPROM's quickly and safely. 10-60-minute electronic timer.
£59.13 + V.A.T.

UVIB
As above but without timer.
£46.95 + V.A.T.

Carriage paid (U.K.)

Send cheque or official order for prompt delivery.

Also available in London from:
Technomatic Ltd
Henrys Radio
Ambit International

IN USE IN DESIGN
LABS & EDUCATIONAL
ESTABLISHMENTS
AROUND THE WORLD

NORTHERN ELECTRONICS

51 Arundel Street, Mossley, Lancashire Tel: Mossley (04575) 4119

WW - 050 FOR FURTHER DETAILS

RADIATION DETECTORS

BÉ PREPARED VIEW THRU LENS

- Ideal for the experimenter
- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R
- British design & manufacture.
- Tested and fully guaranteed. Ex-stock delivery.
- As supplied to Fire Services/Civil Defence

FREE RECHARGE SERVICE AFTER PURCHASE

£6.95

Add. VAT, Post & Packing

COMPLETE WITH DATA

Henry's


Official Orders welcome

01-723 1008/9

CALLERS: 404 EDGBWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 PADDINGTON GREEN, LONDON W2



Box Clever!

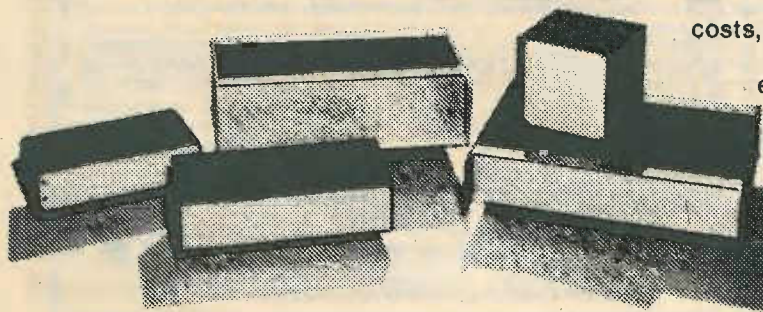

With 1,100 instrument cases in over 750 sizes, and some 250,000 case parts currently in stock, we certainly enable you to *box clever*. A practical solution to every electronic packaging requirement, without the problem of high tooling costs, that's our aim at West Hyde. By being able to supply an 'off the shelf' enclosure for just about any electronic or electrical instrument, we can certainly make sure when it comes to enclosing your particular product, we can help you to *box clever*! For more information send for our catalogue, price £1.00 inc. P&P.

WEST HYDE


West Hyde Developments Ltd., Unit 9,
Park Street Industrial Estate, Aylesbury, Bucks. HP20 1ET.
Telephone: Aylesbury (0296) 20441. Telex: 83570 W HYDE G.

WW - 012 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

FYLDE

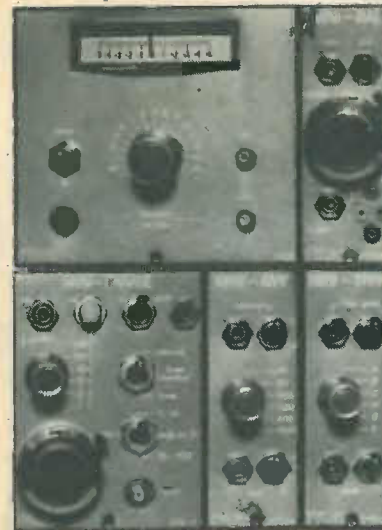TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston PR1 2XQ
Telephone 0772 57560

WW - 014 FOR FURTHER DETAILS

ELECTROVALUE

A SPECIAL SUMMER PROMOTION

FREE VOUCHERS TO SAVE YOU UP TO

£2.10



Send for Catalogue 82 before August 31 (60 pages, A4-70p post paid) and we give you THREE 70p REFUND VOUCHERS FREE valid for spending singly at any time on any one C.W.O. order minimum list value £10 to quickly save you a total of £2.10. Send 70p now for your EV Catalogue 82 + 3 free vouchers by return... and all in addition to the other benefits (discounts, guarantees to spec., brand new stock, etc) you enjoy by buying from Electrovalue.

+ USUAL DISCOUNTS + FREE POSTAGE

DISCOUNTS
5% on orders over £23 (inc. V.A.T.)
10% on orders over £57.50 (inc. V.A.T.)

on most catalogue items but not on payments by credit cards.


POSTAGE
Not charged on U.K. orders over £5.75 (inc. V.A.T.). If under, add 40p handling charge.

ELECTROVALUE LTD. 28A St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Telephone Egham 33603 (London 87 33603; STD 0784 33603) Telex 264475 Northern Branch (Shop service only) 680 Burnage Lane, Manchester M19 1NA. Telephone 061-432 4945.

- ★ SEMICONDUCTORS/ICs/OPTRONICS
- ★ COMPUTERS/SOFTWARE, etc
- ★ CAPACITORS/RESISTORS
- ★ CONNECTORS/SWITCHES/KNOBS
- ★ POTS/FERRITES/METERS
- ★ BOOKS/SOLDER TOOLS

and more and more and more

The Keithley 179A

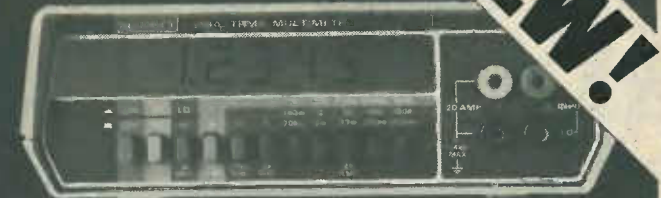

A MEASURE OF ACHIEVEMENT.

Specification... Versatility... Accuracy... Price. In almost every major area the new 179A—a 4½ digit bench/portable DMM—from Keithley Instruments sets some pretty impressive standards:

- 20 amp capability
- Full function: 27 ranges including true RMS AC Measurement
- Year's guarantee on spec
- 0.04% DC accuracy
- IEEE option
- Large display and 10µV dc resolution.

For those requiring 10 times more sensitivity and an analogue output there's the 177, a unit with similar specification to the 179A. Both models are part of a vast range of test equipment from one of the world's leading manufacturers.

For more information fill in the coupon at the bottom of the page.

Alternatively, phone our Instant Information Service on 0734 864784 now.



KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

I'd like to know more...

Name _____
 Position _____
 Company _____
 Address _____
 Telephone _____

WW - 027 FOR FURTHER DETAILS

Twice again: Shure sets
the standard for the industry!



Introducing two new microphone mixers

Ten years ago—with the introduction of the M67 and M68—Shure set the standards of the industry for compact, portable micro-

phone mixers. Shure is now introducing two new mixers with features and improvements that will make them the *new* industry standards.

NEW

M267

For Professional Broadcasting
Both TV and Radio—in the studio and for remote broadcast applications

For Professional Recording

For Professional Sound Reinforcement

For more complex public address systems.

With all these new features:

- Switchable, fast-attack limiter
- LED peak indicator
- All inputs switchable for mic or line
- Simplex power
- Greater headphone power
- Built-in battery supply
- Lower noise
- Reduced distortion

...and all of the famous M67 original features.

For complete information on the M267 and M268 send in for a detailed product brochure (ask for AL669).

The Sound of the Professionals[®]

SHURE

For full details write to:
Shure Electronics Ltd., Eccleston Road, Maidstone ME15 6AU or telephone: 0622 59881.

NEW

M268

For Public Address and Paging
In hotels, schools, churches, community centers, hospitals, etc.

For the Serious Tape Recording Enthusiast

As an Add-On Mixer for Expanding Current Equipment

With all these new features:

- Lower noise
- Dramatic reduction in distortion
- Mix bus
- Automatic muting circuit
- Simplex power

...and all of the famous M68 original features.

Both new models include the same ruggedness and reliability that have made the M67 and M68 the top-selling mixers in the industry.

wireless world

Editor:
PHILIP DARRINGTON

Deputy Editor:
GEOFF SHORTER, B.Sc.
01-661 8639

Technical Editor:
MARTIN ECCLES
01-661 8638

News Editor:
DAVID SCOBIE
01-661 8632

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 8641

BARBARA MILLER
01-661 8640

Northern Sales:
HARRY AIKEN
061-872 8861

Midland Sales:
BASIL MCGOWAN
021-356 4838

Group Classified Manager:
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production:
BRIAN BANNISTER
(Make-up and copy)
01-661 8648

A job to be done

At a press conference on mobile radio held by the UK's Electronic Engineering Association earlier this year there was much discussion on the small amount of frequency spectrum allocated to private mobile radio (p.m.r.) relative to that given to broadcasting, military communications and other services. At least, the EEA officials *claimed* that it was too small for the needs of the p.m.r. service and emphasized their argument with a diagram showing the p.m.r. bands as thin slices sandwiched between large chunks of other bands. One must remember, of course, that the EEA represents the mobile radio manufacturers, who have a vested interest in the frequency space available to p.m.r. But this doesn't alter the fact that nobody is in a position to refute the EEA's assertion — only to rebut it. The whole question of what is an appropriate allocation of spectrum for a given service is entirely a matter of claim and counter claim. And the actual decisions on allocations are made on this same basis by the activities of pressure groups in international conferences, with the ITU acting as umpire and simply confirming the results of the contests.

Of course, other methods of allocating frequencies have been proposed. One is that spectrum space should be sold to the highest bidder. The thinking behind this is that the more you have to pay for your piece of territory the more economic pressure there will be on you to use it efficiently. Another suggestion is to allow a free-for-all in certain bands (as in citizens' bands at present) on the principle that some kind of adjustment will occur naturally and make formal regulation unnecessary. Thankfully, neither of these uncivilized methods has been considered too seriously.

The central problem, as pointed out by the chairman of the EEA's mobile radio committee, Mr J. W. Carlton, is the lack of some kind of "value analysis". In other words, frequency space would be allocated more fairly if it were done on the basis of relative social needs. But there is no

objective data from which these relative needs can be calculated straightforwardly. They can only be derived from the value systems prevailing in a society. We therefore have to analyse these values in such a way that would allow us to attach numerical indices to the various needs for frequency space. To be accepted the analysis would have to be demonstrably rational and so obviously right that no reasonable person could disagree with it.

Who is capable of such an analysis? At first sight the politicians and their permanent bureaucrats seem to have the necessary experience in attaching measurable quantities to social needs; but their decisions are too often a facile response to popular opinion and swayed by party dogmas. Perhaps the nearest type of analysis we have already is the mathematical model of the economy — sets of equations into which changing data are fed to obtain forecasts — because this type of model does have to take human behaviour into account. There are, however, several research organizations with particular interests in studying the interaction of technology with society. In the UK, for example, we have the Social Science Research Council and two new bodies both of which already have some experience with telecommunications and electronics — the Technical Change Centre in London and the New Technology Research Group at Southampton University. In the USA the National Academy of Engineering has looked at the problem and at least recognized the importance of social and economic factors in spectrum management. It should not be beyond the abilities of such organizations to find a method of analysis which, if not completely rigorous, would be greatly superior as a rational basis for allocation to the empirical procedures using political and commercial pressures that we rely on at present.

Fastidious people may well reject instinctively any attempt to equate quantities with qualities. This is understandable in so far as social values are subjective and rooted in the ethical or religious beliefs of individuals. But ethics are a guide to conduct: if there is no conduct resulting from them they are worthless. There is a good case for testing our values in the worldly business of sharing out a natural resource.

A LIGHT PEN FOR MICROCOMPUTERS

Light pens provide an alternative means of interactive communication with a computer via the visual display, and are often used with mainframe computers in graphics oriented applications. They are less common with microcomputers, but this article describes a simple, inexpensive light pen which can be easily adapted for use with most microcomputers which use a memory-mapped video display.

by M. Shepherd.

The light pen can detect individual characters on the screen and return, via two parallel 8-bit ports of the microcomputer, the address of that character. Through the use of appropriate software, individual characters may be changed or deleted or specific actions can be initiated when certain characters are detected. This capability may be used in a number of ways such as in 'menu' applications, where a large number of choices are available, in interactive games, etc.

Video displays

A memory-mapped video display system is shown schematically in Fig. 1. Essentially this comprises a video ram, a character generator (usually a mask-programmed rom), a shift register and associated timing circuitry. The address and data lines of the video ram are multiplexed so that the memory can be accessed either by the c.p.u., to update or read data, or by the dedicated video circuitry which produces the display. The video ram usually occupies a 1K block of memory in the memory map of the microcomputer and stores the m lines of n characters which make up the display. Each position on the screen, p(row,column), corresponds to a unique location in the video ram. The characters are displayed as a dot matrix pattern (Fig. 2). Unless locked out by the c.p.u., the video divider chain continuously addresses the video ram in a predetermined order and, in turn, the video ram output word addresses the character generator. In addition, the divider chain sequences the row address lines of the character generator so that the output word of the generator corresponds to a particular row i of the relevant character at position p(row,column). This word is then loaded into the shift register from which the appropriate series of dots and blanks are clocked out to form part of the video signal. The shift register is typically clocked at around 8 MHz, giving a time separation between adjacent dots of, say, 125 ns. The video display of most microcomputers in the UK uses a 50 Hz frame rate scanning 312 lines without interlace.

Sensor

The light pen and its associated circuitry must detect the rising edge of phosphor emission when a dot is drawn on the screen and simultaneously latch the current address on the video ram. From this

address, one can deduce the memory location corresponding to the character containing the dot and hence the actual position of the light pen. Since we are only concerned with locating characters, rather than individual pixels, the particular dot detected within the character is not important. The optical sensor must have a fast risetime preferably much less than the interval between adjacent dots, say, much less than $\ll 100$ ns. Another requirement for a successful sensor is that it should have a field of view which is comparable to

or preferably smaller than a single character when it is held on the surface of the screen. With a 9 in monitor, a character is likely to be of the order of 5 mm square; the exact size depends on the format of the character generator, the number of characters per line, etc. Both of these requirements can be adequately met using a polymer-fibre light guide and an associated planar silicon p-i-n photodiode.

The polymer-based light guide has an overall diameter of 2.2 mm and a core diameter of 1 mm: it is considerably cheaper and physically much more flexible than equivalent glass light guides. Although its attenuation is markedly greater

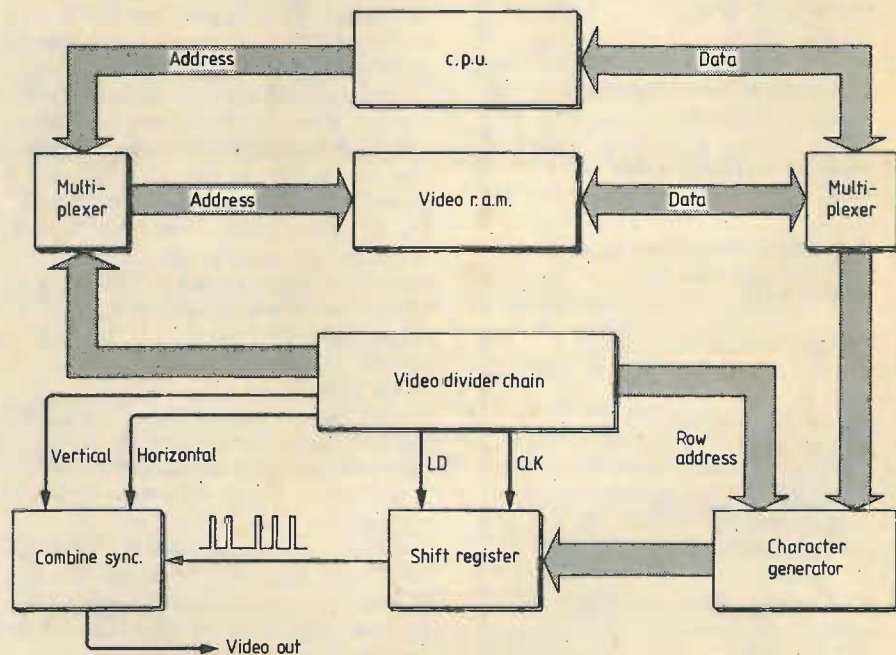


Fig. 1. Block diagram of memory-mapped visual display circuitry in typical microcomputer.

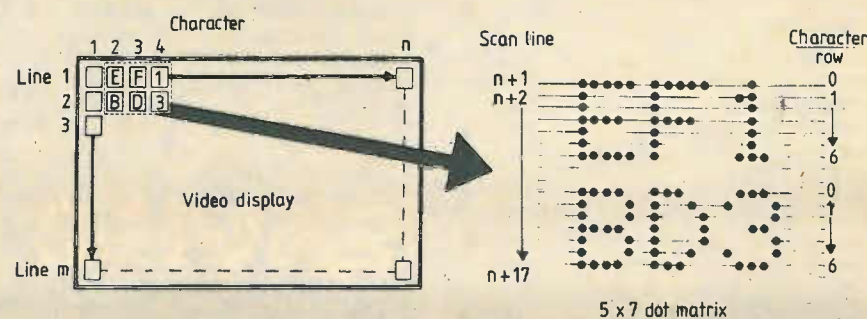


Fig. 2. Dot-matrix representation of characters on screen for 5x7 matrix format.

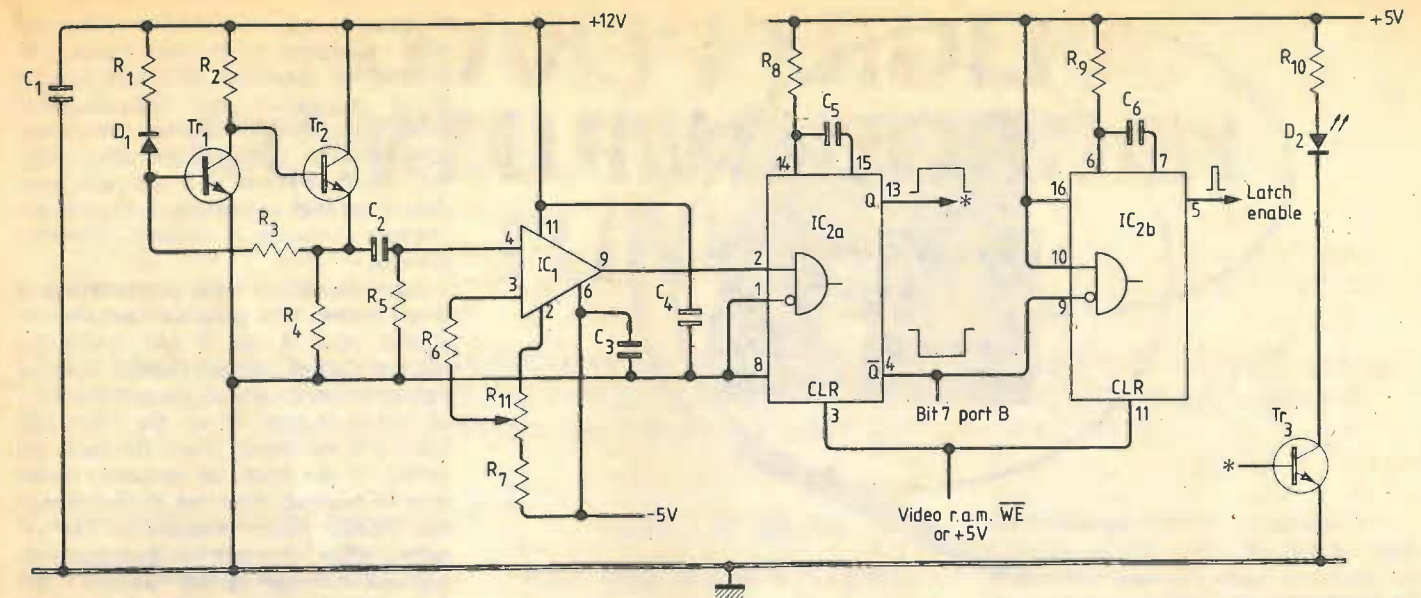


Fig. 3. Circuitry to detect dots and produce latch-enable pulses.

than its glass equivalent this is not a serious problem over the length of about one metre required for this application. The photodiode has a risetime of < 5 ns and can be coupled directly onto the polymer optic using the special termination. This does not require the use of special tools.

The use of a light guide has the advantages that (a) it has inherently a sufficiently narrow field of view to preclude the need for further optics and (b) it isolates the photodiode and related circuitry from the appreciable radiation fields found near the surface of a display tube.

With most opto sensors the sensitivity decreases with increasing speed of response. However the instantaneous brightness of spots on a video screen can be very high and sufficient to give a satisfactory signal-to-noise ratio even with this otherwise relatively insensitive detector. It is, however, worth noting that the maximum instantaneous brightness is a function of the phosphor 'lifetime' and for these purposes screen with short-lived phosphors are preferable. Their distinction is not visually obvious since the eye is integrating the total light output and, at least to a good approximation, is oblivious of instantaneous brightness levels.

Circuitry

Figure 3 shows the circuitry which detects the phosphor emission, as the electron beam draws a dot, and produces the t.t.l. pulse which latches the video ram address. An increase in incident light intensity on the diode produces an increased base current for Tr_1 . Tr_2 acts as an emitter follower, with R_3 providing some d.c. stabilization for the base of Tr_1 . Negative-going pulses at the inverting input of the 710 are compared with the preset negative threshold voltage on the non-inverting input. The potentiometer R_{11} acts as a sensitivity control for the light pen and typically the negative threshold is set at about -50mV.

The first half of the 74123 retriggerable monostable responds to a positive going 'spot detected' pulse from the comparator

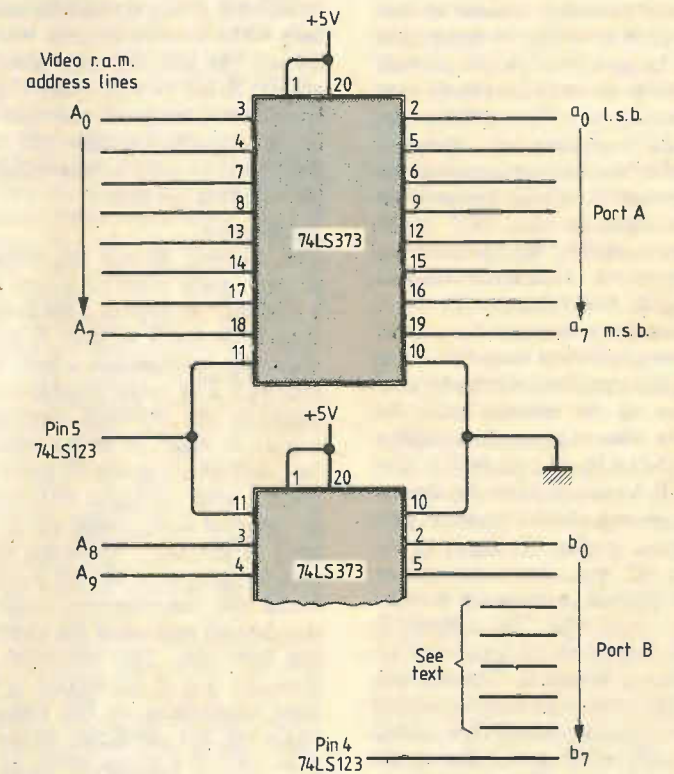


Fig. 4. Latching of video ram address lines.

by ignoring any further pulses for about 18ms, i.e. effectively until the next frame. This prevents multiple triggering of the 74123 by different dots within the same character. For example, two vertically coincident dots would produce pulses separated by 64 microseconds. To ensure that a spot is never detected while the c.p.u. is addressing the video ram, the write enable, WE, of the video ram is shown connected to pins 3 and 11 of the 74123; if this is not required, these pins should be tied high. The Q output of the 74123(a) is used via a transistor switch to light a led, which indicates that a spot has been detected during the current frame. The \bar{Q} output is used by software and is discussed below. The second half of the 74123 produces a nominal 100 ns pulse used to latch the video ram address.

This section of the light pen can be checked using the led and without any connexion to the microcomputer. With the screen brilliance set to a normal working level the sensitivity should be set using R_{11} so that the led emits when the probe is placed on a character on the screen. It will be found that some characters are more easily detected than others, notably those with several contiguous horizontal dots such as E, F or T. Increasing the sensitivity too far will allow the comparator to trigger continuously on noise and a compromise setting may be necessary. Further adjustments can then be made using the brightness control of the video display.

The circuitry to latch the video ram address is shown schematically in Fig. 4. It is assumed, for simplicity, that a 1K video ram is used and therefore that ten address lines A0 - A9 must be latched. De-

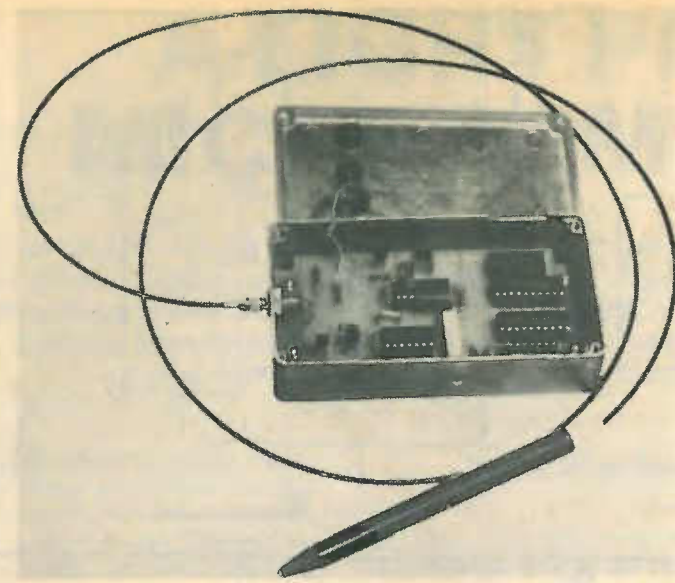


Fig. 5. Prototype light pen.

pending on the actual microcomputer, the video ram will probably consist of one 4118 or two 2114 or seven or eight 2112 memory i.c.s. In each case the ten address lines are available at the i.c. socket(s) and these must be accessed; they will not normally be taken to an external connector. Two 74373 octal latches were used in the prototype (leaving 6 unused latches) but other latches such as the 7575 could equally well be used. The ten latch outputs corresponding to A0-A9 are fed into two 8-bit parallel ports of the computer.

The actual memory address of a character on the screen is 16 bits long. The most significant six bits indicate the location of the video ram in the memory map for example, if the video ram occupies 0800-0BFFF, then bits A16-A11 are 00010. The relevant port B inputs could be hardwired in this way to provide the full address. One problem remains in that the input to the parallel ports will now always be a video ram address but not necessarily a valid address. To ensure that the address is valid, the \bar{Q} output of 74123(a) can be input to the m.s.b. of port B. The software can then decide whether an address is valid by checking the state of this bit; if it is zero then a spot has been detected during the current or the previous frame. In some applications, one may only wish to accept an address as valid if a button is also pressed in addition to the condition noted above; this can be done by allowing the button to ground, for example, bit 6 of port B. The state of this bit can then also be checked by software.


Construction

The entire light pen circuitry and photodiode can be built into a small diecast box (Fig. 5). In the prototype, the video address lines and the power supplies were accessed on the main c.p.u. and video board and taken via ribbon cable to d.i.l. sockets in the box. The sixteen lines from the box taking the video address to the ports also used a ribbon cable. The layout was not found to be particularly critical, but some care should be taken with the front end to avoid spurious responses. The casing of the photodiode was grounded

through the box. Two leds were used, one to indicate power on and the other to indicate when a valid address was being received. The polymer optic fibre had terminations fitted to both ends. One end was fitted into a ballpoint pen case to make it easier to handle; the other end, as shown in Fig. 5, screws onto the photodiode through the standard connexion.

Software

The essential part of the software which recovers valid video addresses is shown as a flowchart in Fig. 6. This flowchart does not check bit 6 of port B as suggested above for applications where a button is required. The actual programming may be done in the machine language of the c.p.u., in Basic, or in any other available language which allows the ports to be read. Since a valid character can only, at most, be detected every frame i.e. every 20 ms, there is not likely to be any problems in processing speed. At this stage it will be found that the recovered video address is not the real address of the character under the light pen. The recovered address is probably that of the second or third character (depending on the video circuitry) following the character under the light pen. This is a consequence of the delays between a particular video ram location

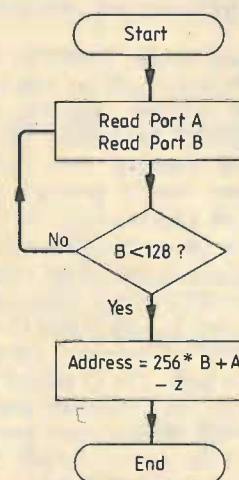

(z = appropriate offset - see text)

Fig. 6. Flowchart for recovery of valid video ram address.

being addressed and the relevant dots and blanks appearing in the video signal. The number of characters difference can be found empirically and the necessary subtraction made by software. Since some alphanumeric characters are more easily detected than others it is obviously prudent to use such characters, or appropriate graphics characters if available, wherever possible.

Some illustrative basic programming is shown below. This program reads the two parallel ports A and B and determines whether the light pen has recently detected a character on the screen, i.e. whether bit 7 of port B is zero. If so, the video ram address is calculated; if not the ports are reread. If the ports are memory, rather than i/o mapped, then line 20 should contain PEEKs rather than INPs. The required offset, Z, must be determined by trial and error; appropriate values of A and B must also be inserted in line 10.

```
10 A = :B = :Z =
20 X=INP(A):Y=INP(B)
30 IF Y>127 THEN GOTO 20
40 VA=Z+X+Y*256
```

That particular character can now be 'deleted' by writing an ASCII space (decimal 32) to its video ram address, VA.

```
50 POKE VA,32
60 END
```

Alternatively, by using

```
50 IF VA=POSITION THEN GO-
SUB 100
60 GOTO 20
```

the program will jump to a given subroutine only when the light pen is held on the character with video ram address, POSITION.

These simple examples illustrate the types of programming techniques which can be used with the light pen.

Components

Capacitors

1,3,4 10n
2 100n
5 470n polyester
6 10p silvered mica

Resistors

1 100p
2,3 100k
4 330
5,6 81 All 0.25W, ±5%
7 10k
8 120k
9 4.7k
10 270
11 500 multiturn trimmer

Semiconductors

D₁ Silicon p-i-n photodiode.
D₂ led
IC₁ 710
IC₂ 74123
Tr_{1,2} Any general-purpose Si n-p-n with f_t>100MHz should be suitable, e.g. BC182L
Tr₃ General-purpose Si n-p-n.

Polymer optic cable (367-791)

Photodiode (309-307)

Terminations (456-396)

All from RS Components. □

LEAKY FEEDER COMMUNICATION IN TUNNELS

For short ranges, a simple installation using the techniques outlined in the first part of this article is effective. Outside the limits of the basic system, more elaborate equipment is needed, the remainder of the discussion being centred on this.

by D. J. R. Martin

B.Sc., Ph.D., F. Inst. P., F.I.E.R.E.

It was shown in Part 1 that the reliable radiocommunication range obtainable in a tunnel or mine can usually be dramatically improved by running a 'leaky feeder' through the tunnel or region where communication is required, and connecting one end to a conventional v.h.f. base station. Communication is then through the leakage fields of the feeder, and the total system loss - which in conjunction with the transmitter power and receiver sensitivity will determine the actual range available - is made up of the 'coupling loss', between a mobile set and the feeder, and the feeder loss between that region and the base station.

A typical reliable range from such a simple system, using conventional mobile radio equipment and a practical type of leaky feeder, would be 2 km - equal perhaps to ten times the unassisted or 'natural' range obtainable in the tunnel without a feeder. If such a range is adequate for the purpose, then little more in the way of systems engineering is required. The major factors to be determined will be the type of leaky cable to use and the nature of its mounting or suspension in the tunnel. These decisions will be based largely on the considerations detailed in Part 1, together with a discerning study of cable manufacturers' data, experience gained in similar situations, specialist advice or even a pilot experiment in the tunnel concerned.

From the standpoint of systems performance it is not even necessary to terminate the free end of the feeder in its characteristic impedance; the short-standing-wave effect caused by a mistermination will normally be masked by the general multipath effects in the tunnel, and it can be argued that residual energy is more usefully reflected back down the feeder than dissipated in a termination. However, if the feeder is not carrying additionally any d.c. or a.f. signals, a resistive termination can be of value in facilitating d.c. continuity and short-circuit checks in case of trouble.

The range of the simple system may be effectively doubled by connecting the base station at the middle of the total span rather than at one end; the few decibels lost from each limb in such a two-way split represents only about 5% of the range. However, this option may not always be

convenient, involving perhaps the extension of control lines and the provision of a power supply in an awkward place. The same splitting principle, it may be noted, can be used at any point in the line to serve a branch tunnel; again, strict impedance matching at such junctions is unimportant.

A few other expedients may be available if the predicted range falls slightly short of requirements. Use of a lower frequency band - say v.h.f. low band instead of v.h.f. high band - will often give a worthwhile advantage (radio regulatory considerations are not normally a restriction if the system is wholly underground); or the expensive decision could be taken to specify a heavier grade of leaky cable and so reduce line loss. It is also possible to 'grade' the feeder, by using a more leaky type towards the extremities of the system in an attempt to preserve the diminishing field. But generally in such circumstances one is better looking towards the active techniques to be described.

On the other hand, if the absolute maximum range is being sought for the very minimum of active equipment then the INIEX systems should be considered, especially if a rather lower frequency - say, in the h.f. range, can be used.

Multiple base stations

When the economic limit of range from a single base station has been reached, one obvious course left is to borrow a technique from land-mobile and aeronautical schemes and deploy further base stations as necessary to achieve the desired cover. This was the solution adopted in the early railway systems such as that for the New York Subway. It was also used in the first coalmine system, commissioned at Longannet, Scotland, in 1970.


The leaky coaxial cable serving the 9 km tunnel there is divided into three sections, with a base station serving each near its centre, as shown in Fig. 4. The base stations are operated under a common control from the surface over telephone lines. Operating frequencies are in the v.h.f. low band (70-90 MHz) as with all subsequent National Coal Board systems, and the cable is a braided coaxial type with a rather

lower leakage than is usual nowadays.

Such systems suffer the familiar land-mobile problem of 'overlap' interference in the regions receiving signals from two base transmitters, resulting from lack of synchronization. At Longannet, the line was simply gapped for a metre or so midway between base stations; by the use of frequency modulation (25 kHz channelling), and relying on tunnel attenuation (about 0.5 dB/m) and capture effect, the extent of confused signals was restricted to a few metres. Nowadays, the land-mobile technique of quasi-synchronous operation would probably be used in a multi-base system; but it would also be quite feasible to use the leaky feeder itself as a synchronization link, passing a ready-modulated pilot signal to outlying transmitters at a frequency of one or two megahertz, where line losses are low.

Line repeaters

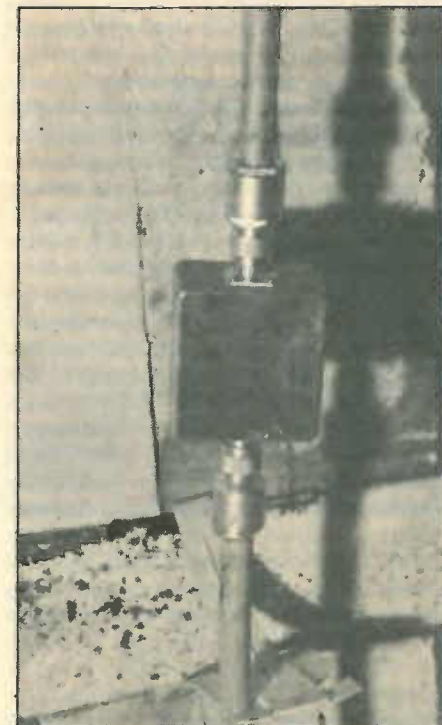Since leaky-feeder communication is basically a hybrid technology, borrowing from both radio and line transmission, it is logical to look also to the latter field for pos-



Line-powered repeater in a coal mine. This example has a consumption of 2.5 mA at 12 V, and is installed at 500 m intervals.

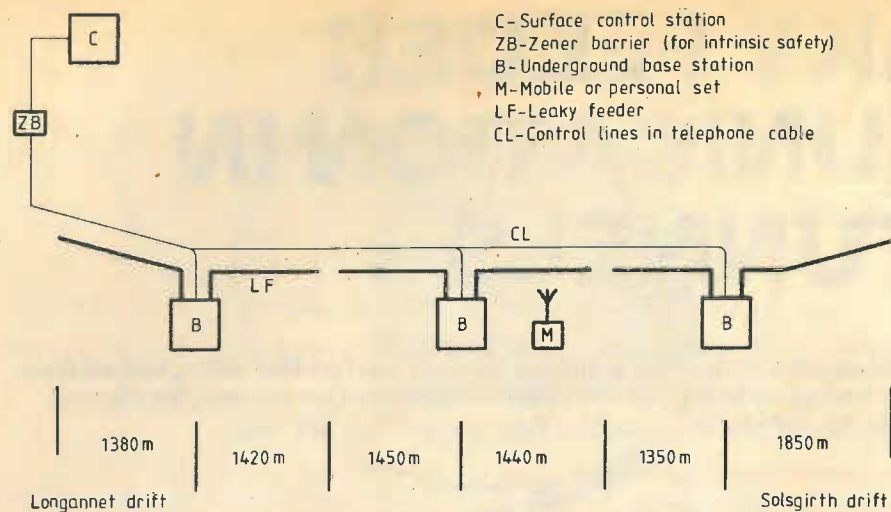


Fig. 4. Multiple-base-station system operating at Longannet Mine, Scotland, since 1970. The 9-km tunnel rises to the surface at each end, at Longannet and Solsgirth. The leaky feeder is divided into three roughly-equal sections, each served by a base station near its centre.

sible means of extending the range of a single base station. The obvious technique which line technology offers is the use of in-line repeaters or 'signal boosters' to amplify signals and so compensate for line losses periodically.

An immediate attraction of the idea is that a repeater can easily be made to handle a band of frequencies and so allow multichannel operation for little additional complexity. But the overwhelming advantage is that by spacing the repeaters comparatively closely, with correspondingly lower gain and line loss between repeaters, one can provide a consistency and reliability of signal level undreamed-of in conventional radio systems. In the same process the output power requirement of each repeater is dramatically reduced, typically to a few milliwatts compared with a base station of several watts. It then becomes possible and logical to power all such repeaters by d.c. over the leaky feeder itself, giving a remarkable saving in cost of a system over one using multiple base stations.

All this assumes that the repeater design itself can be made cheap and simple. But in fact there is a complication in the apparent need for such a device to amplify in both directions. If simplex operation is adequate, then it is not too difficult to arrange that the repeater reverses its direction of operation in sympathy with the base-station switching, perhaps through the polarity of the line-fed supply. But if there is a system requirement for talk-through operation, where the base station simultaneously retransmits everything it receives, then a two-way repeater would need to amplify in both directions simultaneously. The design thereupon becomes complex, with the involvement of elaborate filters and perhaps hybrids to ensure stability. This prospect discouraged the development of repeatered leaky-feeder systems for several years.

Daisy-chain systems

The innovation that opened the way for the development of practical repeatered systems was the 'daisy chain' principle¹⁷. In the basic form of this arrangement,

shown in Fig. 5, the base station is split into its constituent transmitter and receiver, which are then sited at the opposite extremities of the system. All signals, whether from base to mobile or from mobile to base, now travel in the same direction in the feeder and so simple one-way wide-band repeaters serve to amplify them all, simultaneously if necessary, to provide duplex or talk-through operation. A disadvantage shared with the multiple-base-station system is the need for a parallel audio-frequency link, though for a single channel the leaky feeder can be made to double for that purpose. Excessive branching of the system can also be uneconomic, since every extremity has to be terminated in either a transmitter or a receiver (again with its attendant a.f. link), but the system adapts admirably to twin-tunnel situations where the daisy chain can loop back down the second tunnel and allow the transmitter and receiver to be co-sited.

Following its successful introduction at Cadley Hill colliery in 1973, the daisy-chain system rapidly became the standard leaky-feeder arrangement for British coal mines. A typical repeater now in widespread use has a gain of about 16 dB over the range 70 to 90 MHz. Drawing only 2.5 mA from the line-fed 12 V supply, it delivers a power of 12.5 mW for the base-transmit signal. With the cable normally used, such repeaters are installed at 500 m intervals. A simple calculation based on these figures shows the minimum performance to be equal to that of a 20 W base station feeding 1500 m of feeder.

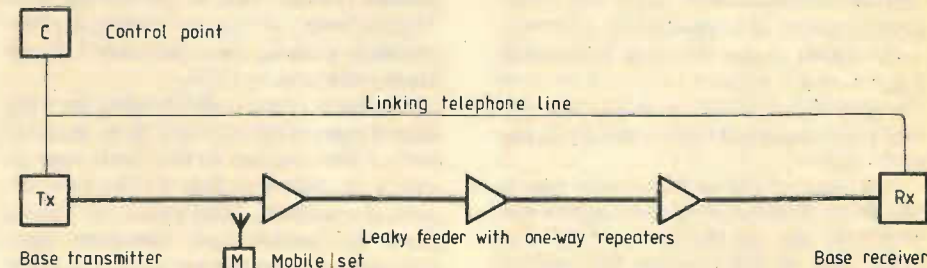


Fig. 5. Simple 'daisy-chain' system, using a split base station and simple one-way repeater-amplifiers to allow two-way communication (including duplex or talk-through operation) over long ranges.

In the more recent coal-mine installations the improved arrangements shown in Figs. 6 and 7 are used. Both replace the telephone line by a medium-frequency link over the feeder itself, the signals passing through the repeaters in the 'wrong' direction without being affected. In the 'i.f. return' version, shown in Fig. 6, it will be seen that the frequency-changer portion only of the base receiver is located at the tail end, and all signals originating at a mobile transmitter are returned to the main base station in intermediate-frequency form, conveniently at 455 kHz. In-line amplification at this frequency is unnecessary, and the v.h.f. repeaters used will pass the i.f. signals in the reverse direction with negligible attenuation.

As indicated in the diagram, the arrangement also adapts easily to the provision of spurs, since the frequency changers can be line-powered and are inexpensive enough to be used at every extremity without significantly increasing the total system costs. The line filters shown serve to prevent signals from a mobile reaching more than one frequency changer and so giving rise to heterodyne interference resulting from lack of synchronism between the frequency changers, and also eliminate undesirable recombination effects (and perhaps phase cancellation) of any base-station signals having taken more than one path through the system. Any residual interference effects are confined to the immediate vicinity of the filters.

The i.f.-return system lends itself neatly to multichannel operation. If the carrier frequencies used are reasonably closely spaced - say, grouped within a 500 kHz range - the frequency changers can be common to all channels; a corresponding group of i.f.s is produced having the same spacing and lying, for example, in the range 1.5 to 2.0 MHz. It may then be convenient to introduce a further common frequency-changer at the base-station end of the feeder, to restore all the i.f.s to their original carrier frequencies for processing by conventional v.h.f. receivers.

Figure 7 illustrates the converse arrangement, known as 'forward drive'. Here, the repeaters are polarized in the reverse direction and the frequency conversion is now applied in the base-transmit path. The output from a normal frequency-modulated transmitter is divided in frequency, using digital techniques, by a factor of (say) 48 or 64. The resulting signal in the region of 1-2 MHz is passed along the line and through the repeaters the 'wrong' way, again with low

loss, to each extremity, where they are multiplied back to the original frequency for transmission through the system the 'right' way and out to the mobiles. Again, a moderate degree of filtering is included at each junction to prevent, in this case, the possibility of phase cancellation between signals from two or more remote converters.

The forward-drive technique is best suited to single-channel systems. It has proved particularly successful in coalmining applications for ranges up to about 4km; beyond that distance it becomes necessary to introduce some intermediate amplification of the forward-drive signal. The i.f.-return system using a single 455 kHz i.f. is generally capable of a greater range - say, up to 10 km - without intermediate amplification.

Repeaters, frequency converters and filters are available commercially for both these 'medium-frequency link' systems.

Other configurations

The main alternative to these daisy-chain configurations is the 'conventional' approach using some form of two-way repeater. In the v.h.f. low and middle bands in particular, the standard transmit-receive frequency spacing is sufficient to allow a practical two-way device to be engineered, though at the cost of some complexity. Generally, such a solution is unattractive except for short systems where only one or two repeaters would be required, or perhaps to accommodate short repeatered spurs in an otherwise daisy-chain system.

A consideration which becomes important in large repeatered systems is the cumulative noise introduced into the base-receive path by the repeaters. If the repeaters themselves were noiseless, and there were no external interference to the system, then the power of a mobile transmitter need only match that of a single repeater for equal performance to that of the base-transmit direction - perhaps only a few milliwatts. But in practice the signal in the base-receive path is inevitably degraded by repeater noise. If the noise introduced by one repeater is equal to that of the final receiver itself - a realistic assumption - then the mobile power needs to be greater than the repeater power by a factor equal to the number of repeaters in the system (strictly, plus one). This does not threaten to be an embarrassment except in the very largest of systems, and even there it will still leave a substantial advantage over the corresponding multiple-base-station solution. It does become important, however, in coalmining applications, where the need for intrinsic safety* and the absolute minimum of battery weight can restrict practical powers to about 50 mW.

In this connexion, the two-way repeater is at a disadvantage, since the inevitable

*Intrinsic safety is a concept applied to apparatus used in potentially explosive atmospheres, and demands that the apparatus is not capable of causing an incendive spark in either normal or faulty operation. Its practical effect is a severe limitation on power levels, though circuit techniques can mitigate this disadvantage to some extent.

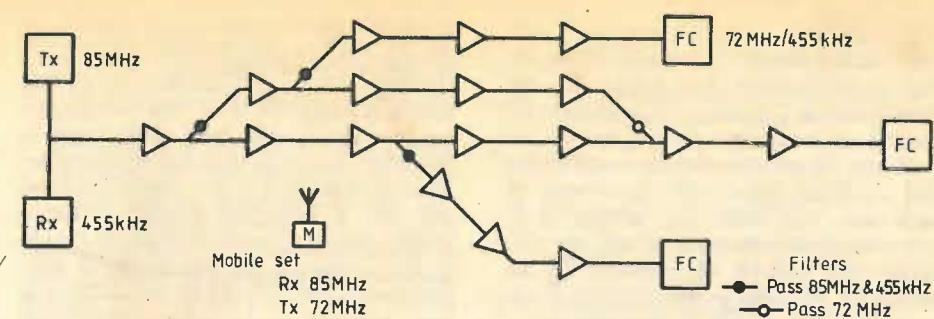


Fig. 6. Daisy-chain system using 'i.f. return' principle, allowing the base transmitter and main receiver to be re-united and avoiding the need for a parallel telephone line. Every remote extremity is terminated in a small line-powered frequency changer which returns any received mobile signals to the main receiver at (typically) 455 kHz.

losses introduced by hybrids and filtering increase the noise figure, typically by about 5 dB in practice. This is reflected directly as a required increase of mobile transmitter power for a given performance.

On the other hand, the i.f.-return system of Fig. 6 lends itself to a method of substantially reducing the overall noise figure of a daisy-chain system. For by suitable design the terminal frequency converters can be made 'squelching', so that only the particular converter receiving a signal passes on any noise. The system effectively becomes sectionalized for noise, and if necessary even an unbranched system may be treated in this way by introducing intermediate converters and filters.

Despite the consequent increase in total repeater noise, increasing the number of repeaters in a system by reducing their space will normally improve the overall signal/noise ratio in the base-receive path because of the overriding improvement to the minimum signal level from the reduction in span loss. The break-even point - unlikely to be reached in practice - comes when the span loss (or repeater gain) is only 3dB; beyond that point, the signal/noise ratio would suffer with further reduction in spacing. The base-transmit path also benefits, of course, from any reduction in repeater spacing, and in this case there is no offsetting noise factor.

In large systems particularly it is important to maintain a good overall balance between line loss and repeater gain; the effect of any substantial discrepancy shows up as a variability in signal/noise ratio of the received signal through the system, over and above that normally expected over the extent of a single span. It may be advisable to design the system for excess gain and then pad with additional attenuation as shown necessary during commissioning tests using an injected pilot signal.

Techniques exist for adjusting repeater gain to line conditions, including control through the line-fed supply. Daisy chain repeaters may also be designed so that the small-signal (base-receive) gain follows that for the high-level base transmission, itself largely self-compensating by virtue of a non-linear static characteristic of the repeater. This assumes that the base carrier is permanently present; it may be necessary to shift it off-channel when not in use to avoid keeping the mobile receiver mutes open and possibly wasting battery energy,

or else to use tone squelch.

For a multichannel system, any choice or design of repeater may need to take into account intermodulation performance, which is governed by the linearity of the dynamic characteristic. Repeater linearity is also important in single-channel systems using any form of amplitude modulation. Multichannel a.m. systems suffer the additional risk of cross-modulation, and here the highest linearity is essential.

To some extent, it may be possible to avoid the effects of intermodulation by careful choice of carrier frequencies, allowing the repeaters to be designed for high efficiency rather than linearity. This can be especially important in coalmining applications, where d.c. power is limited by intrinsic-safety considerations.

The most difficult effects to counter are often the high-order products of two or more base transmissions falling within the base-receive band. The safest course then is to separate the base-transmit carriers as widely as possible - perhaps by several megahertz - to guard against the multiplicative effect on any frequency drift. Preferably, the use of discrete base-station carriers should be minimized by recourse to multiplexing (even though this will not be possible in the return direction). Where power supply permits, the use of linear repeaters is recommended, but such devices are complicated by the need for some form of automatic level control to prevent overload (non-linear repeaters are to some extent self-compensating for variations in line loss).

At first sight, a two-way repeater using separate amplifiers for the send and receive paths should be capable of a better 'cross function' intermodulation performance, but in practice the 'retro-gain' of the receive amplifier destroys or even reverses any such advantage unless very good filtering is incorporated. A better solution is to use wide-band daisy-chain repeaters and group the channel frequencies over a broad spectrum.

A radically different method of avoiding cross-function intermodulation is by using a double-daisy-chain configuration, shown in Fig. 8. In a multichannel system, such use of a double feeder can sometimes be justified by the simplicity it retains in the repeaters. The separate transmit and receive feeders can be combined in a single cable without cross-talk becoming a problem.

The addition of yet a third feeder may then be worthwhile. As shown in Fig. 9, this is sectionalized and serves the two directions alternately. The additional lengths are connected as 'tailbacks' to the repeaters, in parallel with the main feeder and extending back as far as midspan in each case. The effect of a tailback is to halve the span variation of signal; this allows the number of repeaters to be halved for the same performance, and advantage felt primarily in increased range from a single power-feed point.

The tailback principle may also be applied to single-daisy-chain systems, in which case each repeater has two tailbacks, one from each side, and the total requirement is for a double feeder. The further addition of filters linking the juxtaposed free tailback ends and in the main feeder gives the 'bi-directional routing' (BDR) system, which allows the base transmitter and receiver to be sited at the same end of the system¹⁸.

Operational systems

The world's largest user of leaky-feeder systems is probably still the UK National Coal Board, with over 100 mines at least partially equipped. Most of these employ one or other of the daisy-chain variants, the forward-drive arrangement having proved particularly convenient and economic for single-channel applications. A BDR system has been in very satisfactory service at Maltby colliery for several years, and a practical design of two-way repeater is also being evaluated for systems of modest extent.

All such techniques, including i.f. return for multichannel use, are brought together in a very flexible new system for coal mines known as Ariadne¹⁹. This is intended to cover a network of mine tunnels up to 100 km in total extent, with the total power requirement kept within intrinsic-safety limits. A key feature of the Ariadne concept is the division of the base-station carriers into two groups, according to function, spaced 6 MHz apart to ease intermodulation problems and allow selective propagation by the insertion of bandpass filters into the feeder runs. The corresponding base-receive signals are segregated where necessary at intermediate frequency after conversion by the line-powered frequency changers.

Principal among other UK users, London Transport have adopted the simple daisy-chain configuration, with linking

telephone line, for the tunnel sections of the London Underground²⁰; this follows the abandonment of an earlier pilot scheme employing multiple 25 W base stations and a bifilar feeder. The new arrangement is probably unique in that the repeaters are powered through d.c.-d.c. converters from the 110 V signalling supply. Initially, single-channel operation (in the v.h.f. high band) is allowing the use of simple non-linear repeaters, but the future addition of two further channels (unhappily, at equal spacing) will require a change to a linear type.

British Rail, while relying primarily on natural propagation in the u.h.f. band for train communication, has engineered a daisy-chain system for a tunnel section of the Great Northern line, recently taken over from London Transport²¹.

Isberg^{22,23} has made a particular study of such European leaky-feeder practice, and has himself led the recent trend towards repeater techniques in the USA (where repeaters, to avoid confusion in terminology, are often referred to as 'signal boosters'). His papers collect together useful technical information, some of it not published elsewhere.

In Vienna²², the single-channel high-band v.h.f. system in the new U-Bahn (subway) uses a simple daisy-chain configuration with a linking telephone line; 19 repeaters serve a total tunnel length of 9 km. The leaky feeder in this case is of the type having small holes or slots in a solid outer conductor.

Delogne^{22,24} has engineered a particularly ambitious scheme for extending broadcast and selected two-way radio channels into road tunnels in Brussels, using off-air relaying techniques. The INIEX-Delogne system serves a.m. (150 kHz-1.5 MHz) and f.m. (88-108 MHz) broadcasting and the v.h.f. low (c.70 MHz) and high (c.170 MHz) mobile radio bands. The tunnels are relatively short (maximum length 395 m) and so the only repeaters required are in the elaborate interfacing arrangements between the tunnel cable and the special wide-band aerial system. Unique problems of system stability had to be solved in this pioneering project.

For the far longer road tunnels in Switzerland, the PTT authority there has developed a system having a broadly similar function but using land-line links to remote control centres and other outside sources rather than off-air feeds²⁵. In a

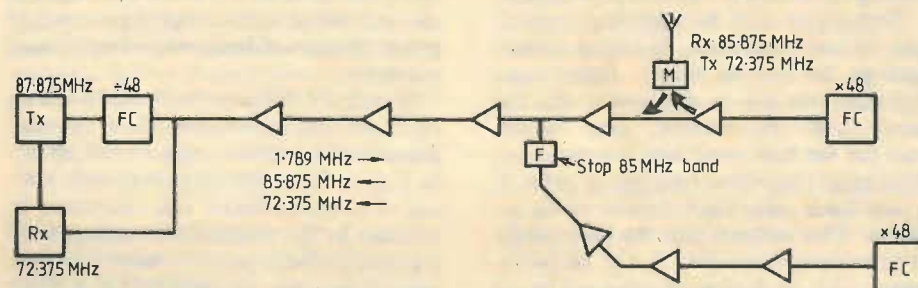


Fig. 7. Daisy-chain system using 'forward drive', achieving the same advantages as IF return but using frequency-conversion in the base-transmit path.

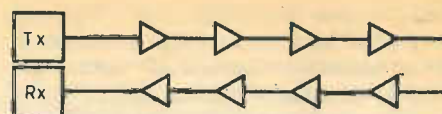


Fig. 8. Double daisy chain, in which signals in the two directions of communication are kept separate to minimize intermodulation effects.

typical installation²⁶ two separate daisy chains are used: one serves the police, highway maintenance and driver-information (f.m. broadcast) channels, while the other carries the public radiotelephone service. In the event of failure in the first system, the public radiotelephone service gives up its chain to the essential channels. Furthermore, the chains are oppositely polarized, so can operate together as a double-daisy-chain system if necessary to cope with a variety of fault conditions.

All services are contained within the repeater range of 63.5-180 MHz. The Gotthard tunnel, in particular, is about 16 km long and employs 24 repeaters in each chain. Over such a distance, careful attention has to be paid to gain balance through the system. The repeaters, in fact, are rather complicated assemblies. Every third one incorporates automatic gain-adjustment and equalization circuits responding to two pilot carriers permanently transmitted, one at each end of the frequency range.

On the continent of America, as in remaining parts of the world, most operational systems still apply the original multiple-base-station concept. Some recent installations (such as at Sesser Mine, Illinois, and Black River Mine, Kentucky) employ a successful but somewhat elaborate and expensive form of two-way repeater, while in Washington, DC, a particularly awkward requirement in the under-river section of the Metro system is being met by installing a daisy-chain arrangement using i.f. return, probably the first embodiment of such principles in that continent. A similar trend is evident in new systems being engineered for Canadian mines.

The principle and techniques that have been described in the two parts of this article represent established theory and practice in leaky-feeder communication. But the subject also gives particular scope for 'armchair innovation', with frustratingly too few opportunities or facilities for demonstrating such ideas in practical systems.

For example, leaky-feeder systems generally would stand to benefit from the application of diversity to overcome or mitigate the local variations in signal strength which are so characteristic of all v.h.f. communication in enclosed or urban environments. Most of the standard techniques used or proposed for conventional mobile radio could be applied with advantage, but leaky-feeder systems that include tailbacks lend themselves peculiarly to a principle known as 'direction diversity'^{18,27}. Treen²⁸ has described an ingenious combination of space and frequency diversity particularly

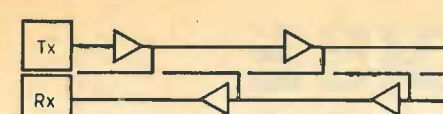


Fig. 9. Double daisy chain to which 'tailback' feeders have been added to halve the variation in signal level between repeaters.

well suited to leaky-feeder operation. The increased demands on bandwidth or spectrum made by all these proposals would not be serious in enclosed environments.

It could similarly be speculated that a development of line-powered 'mini-base-stations' of extremely low power might challenge the now-established repeater technology, exploiting the frequency-conversion devices developed for the i.f.-return and forward-drive systems. A striking property of such systems would be their ability to operate over wide ranges with 'flea powered' mobiles of a milliwatt or so, perhaps in conjunction with a revived form of superregenerative receiver.

For the present, however, there is a wealth of proved and established technology in repeated leaky-feeder systems,

capable of meeting the most demanding requirements for radio communication in mines, tunnels and other enclosed environments.

The author is grateful to the National Coal Board for permission to reproduce the photographs accompanying this article. It is stressed that the author alone is responsible for any statements or opinions expressed about equipment or systems depicted.

References

- 17 Brit. Pat. 1371291
- 18 D.J.R. Martin: Systems aspects of leakage-field radio communication, Conf. on Civil Land Mobile Radio, Teddington, 18-20 Nov. 1975 (IERE Conf. Proc. No. 33, pp. 153-64)
- 19 D.J.R. Martin: Ariadne - a radio propagation highway for mines, National Telecommunications Conf., Houston, 30 Nov.-4 Dec. 1980 (NTC80 Conf. Record, pp. 9.5.1-9.5.5, IEEE)
- 20 M. Wheat: Track to train communication and control (Part 3), *Railway Engineering International*, Vol. 4, No. 5, pp. 31-2, Sept./Oct. 1979
- 21 L.J. Giles and R.E. Simson: The British Rail signal-box-to-train radio-communication system, *Electronics and*

Power, Vol. 27, No. 9, pp. 611-614, Sept. 1981

- 22 R.A. Isberg: A study of the technology of underground radio communication in Europe, 1980 Rapid Transit Conference, San Francisco (American Public Transit Association, 1100 17th Street N.W., Washington, D.C. 20036)
- 23 R.A. Isberg: Radio Communication in subways and mines through repeater amplifiers and leaky transmission lines, 28th Vehicular Technology Conf., Denver, Colorado, March 1978 (VT28 Conf. Record, pp. 248-54, IEEE)
- 24 P.P. Delogne: Radio goes underground, *IEEE Spectrum*, Vol. 17, No. 7, pp. 26-9, July 1980
- 25 O. Grüssi and P. König: Radio links for highway tunnels, *PTT Technical Bulletin* (Switzerland), No. 7, 1978, pp. 285-93
- 26 H.-R. Meyer: Autophon's assignments at Gotthard highway N2, 31st Vehicular Technology Conf., Washington, D.C., April 1981 (IEEE)
- 27 D.J.R. Martin and R.W. Haining: Leaky feeder radio techniques for mines and tunnels, Conf. on Land Mobile Radio, Lancaster, Sept. 1979 (IERE Conf. Proc. No. 44, pp. 305-17)
- 28 K.F. Treen: Radiating cable system, *Wireless World*, Vol. 84, No. 1512, pp. 42-4, Aug. 1979

LITERATURE RECEIVED

Power Transistor Selection Guide from Marconi Electronic Devices Ltd has three pages of data and a selection table for their Powerline range, which are intended for high power switching circuits, choppers, inverters, motor-drive circuits and i.f. transmitters. MEDL, Doddington Road, Lincoln LN6 0LF. WW400

Thick-film microcircuits are the subject of a brochure from Newmarket Microsystems Ltd, Exning Road, Newmarket, Suffolk CB8 0AU. They offer a custom service for hybrid microcircuits and the brochure details their standards and facilities. WW401

Technical handbooks and manuals, along with data sheets for Advance, Alpha, Intersil, Motorola and Texas instruments' products are available from Hawke Electronics, 45 Hanworth Road, Sunbury-on-Thames, Middlesex. They are listed in a Data Library Services brochure. WW402

Spectrol Reliance are manufacturers of precision trimmer potentiometers, subminiature switches and multiaids. They have detailed their products in a shortform catalogue which also includes technical data and information on their facilities for manufacturing special potentiometers. Copies are available from Spectrol Reliance Ltd, Drakes Way, Swindon, Wilts SN3 3HY. WW403

Thousands of gears, pulleys and drive couplings, especially all those hard-to-find mechanical bits are listed in a American publication. The Handbook of Small Standardised Components, some 750 pages long, is published by Stock Drive Produces, 55 South Denton Avenue, New Hyde Park, New York 11040. WW404

Inductive Transducers is the self-explanatory title of a catalogue from R.D.P. Electronics Ltd, Grove Street, Heath Town, Wolverhampton. Specification details are given for the range of precision gauging, waterproof, long stroke and miniature displacement transducers and devices for measuring pressure, velocity and angular tilt using inductive and i.v.d.t. sensors. WW405

Portastudio is the brandname for a Tascam 244 portable recording and mixing system which can record four tracks onto a standard microcassette which is incorporated into it. It includes dbx noise reduction and is described in a brochure, copies of which are available from Harman U.K., St Johns Road, Tyldesley, High Wycombe, Bucks. WW406

Thomson-CSF has published a new issue of its catalogue on active components for 0.84µm optical applications. Twenty-five data sheets devoted to i.e.d.s, p.i.n. diodes and laser diode transmitters are included in the 108-page publication. Thomson-CSF, 101 Boulevard Murat, 75781 Paris Cedex 16, France. WW407

Burndy Ltd are a new company producing connectors for shielded or coaxial cables. Their catalogue shows the full range, most of which is available from stock. Burndy Ltd, Colney Street, St Albans, Herts AL2 2ED. WW408

Standards from the International Electrotechnical Commission seem to be published at a phenomenal rate. A selection of those received include Publication 679-2, Quartz crystal controlled oscillators; 147-ID, Essential ratings and characteristics for semiconductor devices, Part 1, Chapter 1/I, Integrated circuits; Publication 705, Measuring performance in microwave ovens; Publication 717, Method for the determination of the space required by capacitors and resistors with unidirectional terminations. Publication 698, Measuring methods for television tape machines. There are a number of additions to Publication 487, dealing with standards for

equipment in radio-relay systems; and to Publication 708, cable standard. I.E.C. 1 Rue de Varembe, 1211 Geneva 20 Switzerland. WW409

An application reference book has been published by Zilog which is of use to all employers of Zilog processors and peripherals. Chapters are devoted to the Z8 family, Z80 and Z8000 together with their appropriate peripheral devices. Other chapters are on the Z6132 quasi-static r.a.m., the Z-bus and on the applications of the devices and the Unix operating system. Copies cost £8.50 and are available from Zilog distributors and from Zilog (UK) Ltd, King Street, Maidenhead, Berks SL6 1DU. WW410

Integra Microwave Catalog (1982) gives general descriptions and specifications for microwave test equipment operating to 40GHz. Equipment consists of sweep generators, frequency and power meters, spectrum analysers, mixer test sets, v.c.o. test sets, sweeping voltage and current supplies. All equipment is compatible with IEEE-488. Copies may be obtained from Farnell International Instruments Ltd, Wetherby, W. Yorkshire LS22 4DH. WW411

A very wide range of **loudspeaker kits** to their own designs are detailed in a catalogue from Badger Sound Services Ltd, 46 Wood Street, Lytham St Annes, Lancs FY8 1QG. In the catalogue they point out that although loudspeaker designs are highly sophisticated, they are often easy to build and it is the building which is the most expensive factor when purchasing commercial speakers. By constructing them oneself, often only requiring a screwdriver it is possible to save greatly on the cost. WW412

Becoming Comfortable with Computer Graphics is the title of a booklet from Hewlett Packard. It is a useful introduction to graphics and the methods for generating them, with some fine colour illustrations. Hewlett-Packard Ltd, Winnersh, Wokingham, Berks RG11 5AR. WW413

WIDE-RANGE NOISE GENERATOR

Although intended to form part of an electronic organ, in which the noise simulated the sound of a pipe 'chiff', the circuit is useful in synthesizer systems. The circuit was designed some time ago and uses 74-series i.cs, but nevertheless illustrates valid techniques.

Like many others, the author has been experimenting for years, on and off, with tone generators and keying circuits designed to simulate to a greater or lesser degree the sound of a pipe organ. Efforts have been centred on devising an economical system using an independent free running oscillator for each note. Keying circuits were also considered necessary, as it has not proved possible to key an RC oscillator (and LC types work out more expensive and bulky, though they have other advantages) without "chirp". Attempts have also been made to key noise along with the tone, to simulate the characteristic "chiff" or starting transient of a flue pipe. The noise was obtained from a very simple noise generator knocked up hurriedly and very promising results were obtained, which indicated that band-pass filtered rather than white noise was appropriate to the chiff circuit. Further experiments in this direction were therefore postponed whilst a versatile a.f. noise generator was produced. In addition to a maximal-length-feedback shift-register-type noise generator, a universal filter of the Sallen and Key variety was incorporated, providing low-pass, high-pass and band-pass filtering facilities.

Noise generator

The noise is generated by an n-stage feedback shift register (see Fig. 1(a)). This is a shift register clocked in the normal way and having for its input the output of an exclusive-Or gate. The two inputs to the exclusive-Or gate are taken from the last stage of the shift register and an earlier stage. Under these conditions, the output from the shift register is an apparently random string of 0s and 1s and the longest pseudo-random pattern results if the input is taken from the correct earlier stage. Under these conditions, the output pattern will repeat after $2^n - 1$ clock pulses. When the generator is switched on, some other sequence may appear briefly, but provided at least one of the shift register stages comes on with a 1 output the maximal length pattern of $2^n - 1$ digits will establish itself. (The all 0s condition would circulate indefinitely also, but is of no use to us and is avoided.) During one cycle of the complete sequence, the shift register will hold during one clock period or another every possible combination of n 0s and 1s, so that the longest string of 1s which occurs is n in a row and the longest string of 0s is (n-1). It can be shown mathematically that the output sequence has a frequency

by Ian Hickman

spectrum consisting of all harmonics of (clock frequency)/($2^n - 1$). Thus a 10-stage register clocked at 1023 Hz would have an output spectrum consisting of all harmonics of $1023/(2^n - 1)$, i.e. of 1 Hz. These harmonics are all of equal amplitude up to about one sixth of the clock frequency, so up to this frequency the maximal length pattern is quite a good approximation to a source of 'white' noise.

Naturally occurring noise may or may not be 'white', but it usually has a "Gaussian" or 'normal' amplitude distribution. This can be very closely approximated by low-pass filtering the maximal length pattern with a cut-off frequency lower than (clock frequency)/n. This is shown in Fig. 2 where it is obvious that the occasional large positive and negative peaks found in random Gaussian noise correspond with the occasional longish strings of 1s and 0s in the pseudo-random pattern respectively.

In the full circuit of the pseudo-random feedback shift register (Fig. 3) an additional exclusive-Or gate used as an inverter has been included in the feedback path. The effect of this is that the combination of

shift register states which does not occur is all 1s rather than all 0s. Owing to the internal architecture of the 7495 i.cs (which each contain four shift-register stages plus various control gates) on switch-on, all outputs usually come up in the 0 state. Thus the maximal length pattern is self-starting. With seven 7495s, the length of the pseudo-random pattern is $2^{28} - 1$ or 268,435,455 clock pulses. Clock generator IC₉ runs at approximately 6MHz and so Gaussian white noise is available up to somewhat less than 6 MHz/28 or approximately 200 kHz. The 3 dB attenuation frequency of R₂, C₆ is accordingly set at 100 kHz.

At the other end of the scale, the pattern will repeat at a frequency of $6 \times 10^6 / (2^{28} - 1)$ or about once every 43 seconds. So with a spectrum consisting of harmonics spaced 1/43 Hz apart, the output is a very good approximation to the continuous frequency distribution of true white noise, even when the filter is set to 10 Hz low pass. The wide band noise is not low-pass filtered at all. Its level can be set by 'wide-band noise level' control R₃₈ and it is made available via an emitter-follower at Belling Lee socket SK₁, as in Fig. 4. It is not Gaussian (but may be externally filtered, if desired) but is

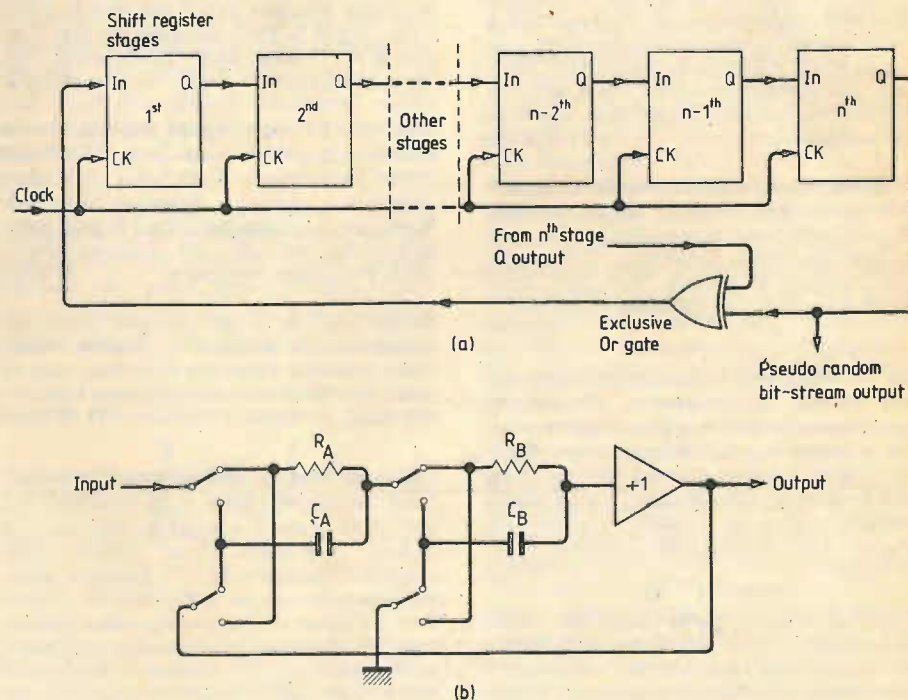


Fig. 1. Block diagram of n-stage shift register (a). Length of sequence is determined by stage from which second ex-Or input is taken. Sallen/Key filter at (b) can be of high-pass or low-pass configuration


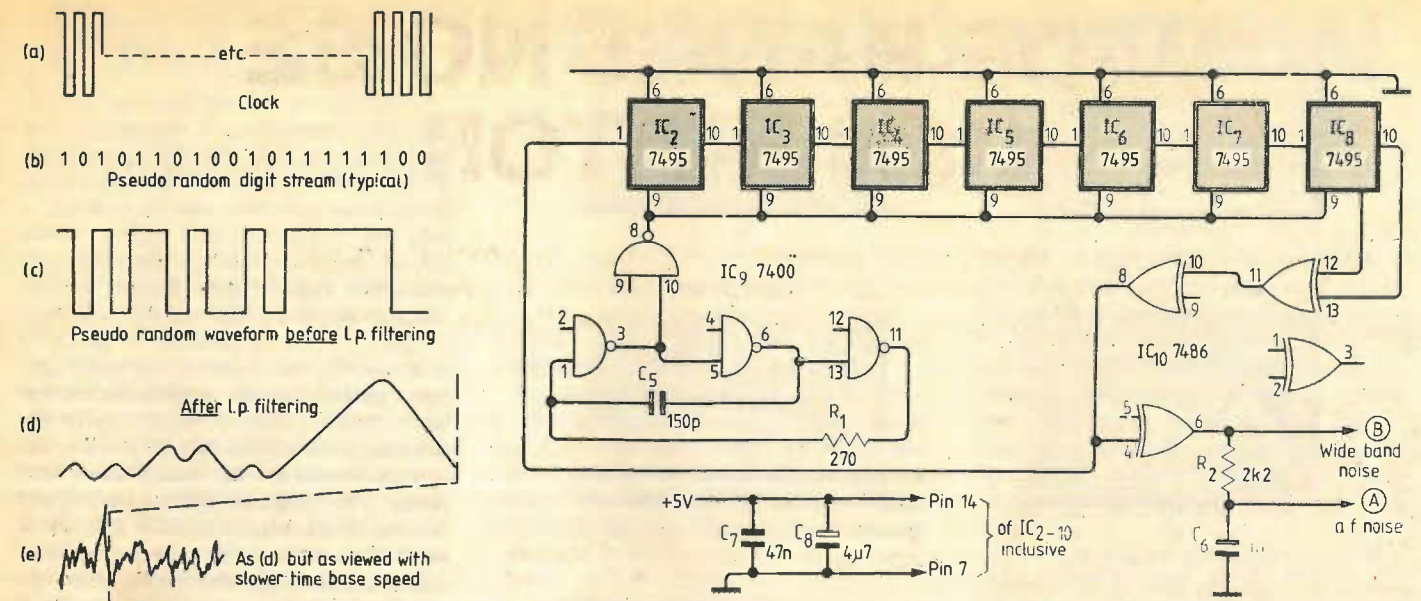


Fig. 2. Waveforms in the pseudo-random sequence generator. Waveform at (c) shows output before filtering. Filtered output shown at (d) and (e), which is gaussian white noise.

Fig. 3. Practical maximal-length shift register

Fig. 4. Filter, attenuator and output circuits

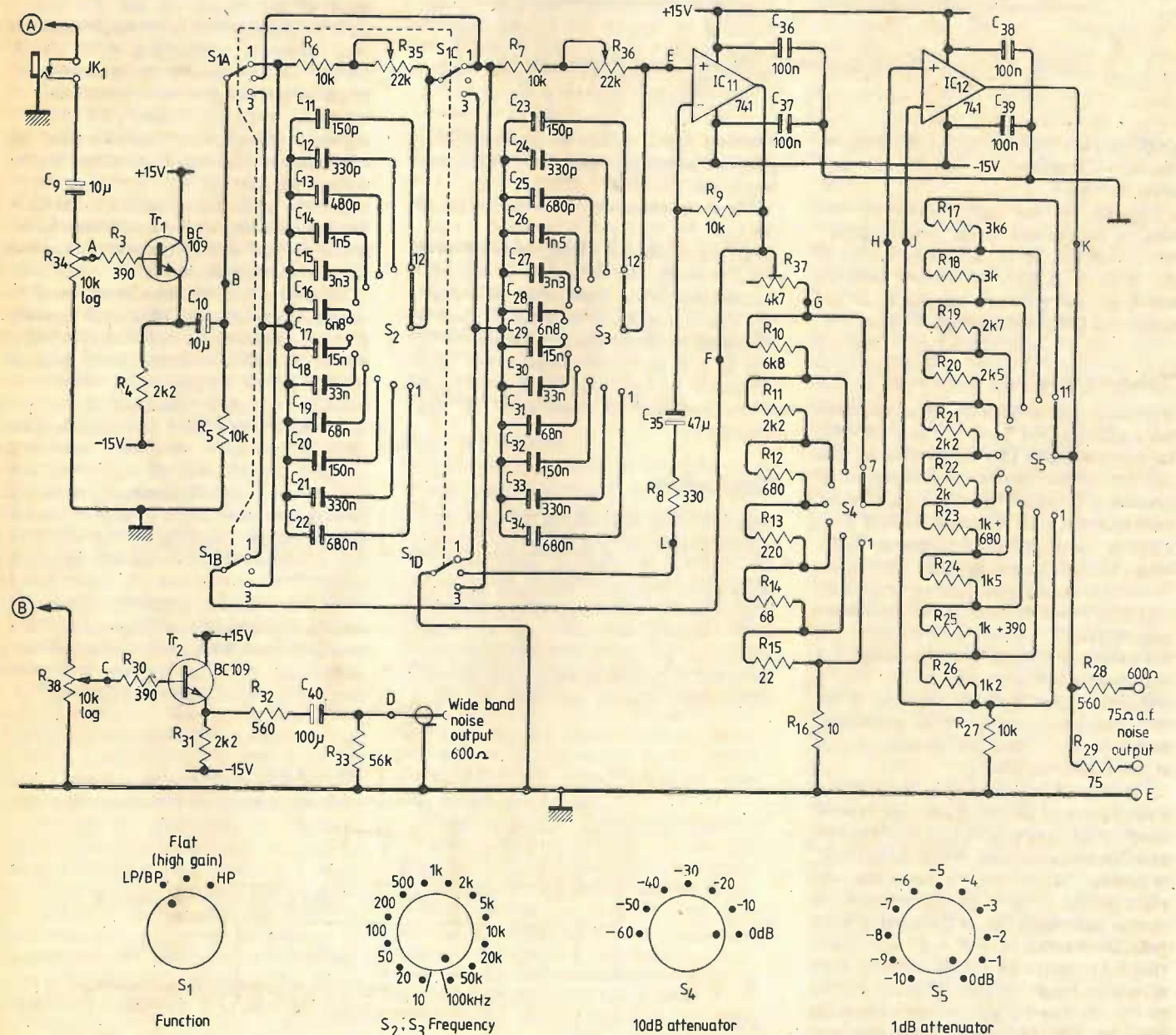

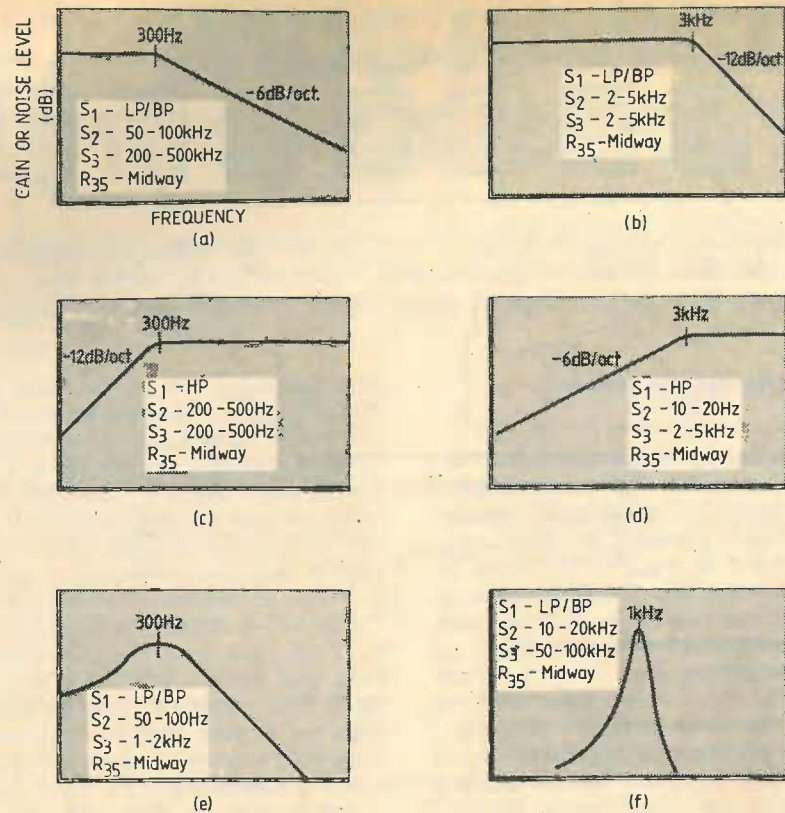


Fig. 5. Typical responses obtained at various settings of filter controls

approximately white from 1 MHz down to the cut off frequency of C_{40} , R_{33} , i.e. approx. 1/30 Hz.

The a.f. noise is band limited to 100 kHz by R_2 , C_6 and at the low frequency end, to 1.6 Hz, by C_9 , R_{34} and C_{10} , R_5 . It can also, of course, be further limited, high-pass, low-pass or band-pass as required by the filter section. Typical responses and the control settings producing them are shown in Fig. 5. The a.f. noise is available at either 600 Ω or 75 Ω output impedance and its level can be set in 10 dB and 1 dB steps by S_4 and S_5 respectively. An external input JK_1 is provided so that the filter section can be used to shape the frequency response of any audio signal. Alternatively, with 'function' switch S_1 at position 2, the frequency response is flat, but up to 40 dB of voltage gain is available. This position may also be used to produce high-level white noise, but the occasional large-amplitude spikes characteristic of white noise will be somewhat reduced due to slew rate limitations in $IC_{11,12}$. R_{37} is provided to permit the adjustment of the maximum noise output level to a predetermined value. It may be omitted if this facility is not required.

For either a high-pass or a low-pass response with a 12 dB per octave fall beyond the cut off frequency, S_2 and S_3 should be set to the same position. When using h.-p., increasing the l.f. cut-off frequency will progressively remove the low-frequency noise components, but as these represent a small percentage of the total a.f. bandwidth, the effect of overall volume does not appear large; except of course for the last few positions. This is because the noise power per unit bandwidth is constant and

therefore when, in the l.-p. mode, the cut-off frequency is reduced, so is the output amplitude.

The b.-p. response is a modification of the l.-p. response and is obtained by setting S_3 to a more clockwise position than S_2 . The larger the difference in settings, the narrower is the 'band-pass' characteristic. The frequency of the peak is equal to the mean of the frequency settings of S_2 and S_3 and fine adjustment to the peak frequency, without affecting the sharpness of the peak, can be made with R_{36} 'fine frequency'.

Application

Before dealing with uses of the generator, it is worth emphasizing again that although the circuit is self-starting, there will be a delay after switch on before the maximal length pseudo-random pattern establishes itself. During this start up sequence, which may last up to 40 seconds or more, there will be periods of silence interspersed with sundry whistles and hisses. So if you

switch on and apparently nothing happens, fear not! Thirty to forty seconds can seem an awful long time!

In addition to the use for which it was originally required, i.e. experiments in producing a realistic electronic simulation of the sound of a pipe organ, the completed noise generator can be used for a wide variety of purposes. It is a very useful adjunct to a synthesizer and can contribute to a whole range of novel effects. For instance, with 'Function' switch S_1 set to l.-p. and S_2 , S_3 set to position 11 (20 to 50 kHz cut-off), the output of the noise generator passed through a synthesizer envelope circuit set for rapid attack and decay will sound like a pistol shot in the open air. A slightly longer decay sounds like a shot inside a building and repeated envelopes like an automatic or machine gun. Even without a synthesizer, a wide range of effects can be demonstrated. For example, with the output of the noise generator feeding an amplifier and speaker, set 'function' switch S_1 to l.-p. R_{34} to maximum and S_2 , S_3 to position 5, 200-500 Hz cut off. With the volume set rather loud, the sound is very like that experienced in a tube train, apart of course from the regular noise of the wheels on the rail joints. Slowly reducing the cut off frequency with 'fine frequency' control R_{36} whilst reducing the 'volume' (R_{34}) gives the impression of the train slowing down for a station.

Setting S_2 , S_3 to position 7, 1-2 kHz cut off and S_1 (function) to high-pass gives the sound of waves hissing on a shingle beach. Again, adjustment of 'fine frequency' control in conjunction with R_{34} can give the deeper sound of a wave breaking, followed by the hiss of the water receding through the shingle.

Band-pass-filtered noise lends itself to some dramatic effects. Thus with S_2 set to 200-500 and S_3 set to 2-5kHz, ('function' switch at LP/BP) the sound can be made to sound like the sighing of the wind in a woodland setting by manipulating R_{36} . Set S_2 to 100-200 and S_3 to 20-50kHz and we have the sound of the wind screaming round a climber belayed on an exposed ledge. Set S_2 to 10-20 Hz and S_3 to 50-100 kHz (again tweaking R_{34}) and it sounds like the blizzard howling through the gaping windows of the ruins of Dracula's castle!

The ear will recognise the centre frequency of the band-pass response as a musical pitch even with a very modest amount of peaking, e.g. Fig. 5(e) and it is quite easy to play tunes simply by adjusting R_{34} □

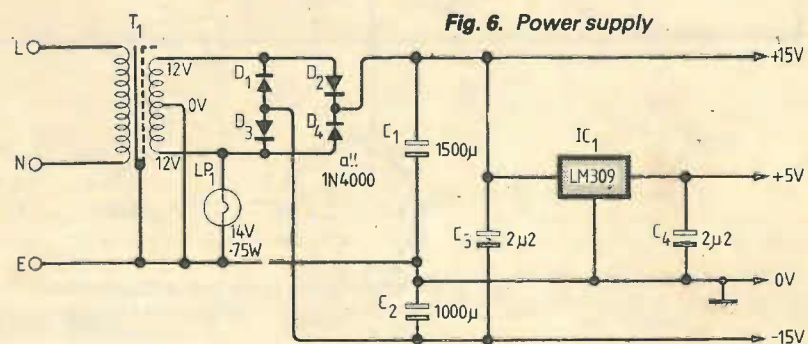


Fig. 6. Power supply

PATENTING AN INVENTION

Protecting your invention is neither as simple nor as cheap as it is sometimes imagined, and the protection it affords is often illusory. Barry Fox explains the pitfalls and shows the way round them.

by Barry Fox

drafted or is anticipated by earlier knowledge, it will be of no real value.

As a rule of thumb, it is usually easier to secure a patent on a worthless idea because the chances are that no-one has previously wasted time and money on patenting it. As another rule of thumb, the more valuable the idea protected, the stronger the patent

Everyone has, at some time in their life, had an idea which they felt was important. "You should patent it", says a friend, "and earn some money from it". If only it were that simple!

Some good ideas aren't patentable. Others ideas are patentable, but not worth patenting. And the whole business of patenting is much more complicated and expensive than most people realise. Patenting an invention can sometimes bring very considerable financial rewards, not to mention fame. But more often, patenting an invention brings only disappointment and financial loss.

What is a patent?

Although everyone has heard of patents, few people can even pronounce the name correctly. It's patent as in cat, not patent as in latent. Even fewer people understand what patenting is all about.

A patent is, in effect, a bargain struck between the Government and an inventor. The inventor discloses full details of a new idea to the public through the government-controlled Patent Office and in return is rewarded with a legal monopoly on that idea for a limited period of time. The public gains because the inventor's idea is published and adds to the sum of human knowledge. The inventor gains because a patent monopoly can be potentially very valuable. For instance a patent which is legally strong enables the inventor, or anyone who has legitimately taken over the patent rights, to control the manufacture, sale and use of an invention. But patents, unlike trademark registrations, are not permanent. Whereas the first British trademark, Bass for beer, is still in force after over 100 years, patents can only last for up to twenty years. Before a major change in British patent law took place, in June 1978, the life of a British patent was sixteen years. It's also part of the bargain that once the patent monopoly period has expired, the patented idea becomes public property — or passes into the "common domain".

It is expensive to obtain a patent and in most countries of the world (including Britain) it is also expensive to keep a patent in force. Annual renewal fees must be paid. There are also many pitfalls for the unwary inventor, and the grant of a patent is certainly no guarantee of financial reward. There is, for instance, no point in having a legally strong patent on a commercially valueless idea. The whole point of a patent is that it gives the owner a temporary right to prevent plagiarism. If the patented idea isn't worth plagiarising, there is no value in holding a patent on it. Likewise if a patent is not legally strong, for instance if it has been inexpertly



will have to be if it is to withstand the legal attacks which will be brought against it by competitors who want to use the same idea. Incidentally, although "idea" is a convenient term to use in the context of patenting, it is not strictly correct. You can't patent a bright idea as such, only some way of putting it into action.

Success stories

Perhaps the most famous example of a commercially successful patent is that which was filed by Percy Shaw of Halifax, shortly before World War II. Shaw's invention was what we now know as "cat's eyes". In fact the idea of marking a road with glass reflectors wasn't new, but the idea had never caught on because the reflectors soon became dirty. Shaw's brainwave was to mount the glass eyes under rubber lids which, in the manner of a blink, closed and cleaned the glass every time a car ran over them. When war broke out, and car headlights had to be shielded for the black-out, Shaw's invention came into its own.

When Percy Shaw died, forty years and 15 million cat's eyes later, he was still paying around £37,000 a year in income tax on the profits from his original invention. His patents had of course long since run out. But Shaw continued to manufacture cat's eyes himself and thereby capitalized from a commercial monopoly long after his legal monopoly had expired.

Of course, the fact that Shaw's patents

have run out does not mean that anyone else can re-patent the same idea. It is now in the public domain. But there is no reason why a modern inventor should not come up with a new idea relating to cat's eyes. Indeed I noticed recently that an inventor is currently trying to patent a new type of cat's eye which is temperature sensitive and so gives drivers a signal of road conditions.

It's important to understand that every country has its own patent laws which apply only to that particular country. A British patent, for instance, cannot be used to control the manufacture of a patented invention abroad. But it can be used to control the sale here of foreign-made goods. So a British inventor can block the import of foreign copies or "infringements".

Consider the case of a now-famous invention by German engineer Walter Bruch of AEG Telefunken. This has not only rewarded the German company but helped shield the entire European tv industry from cut price competition from the Far East. In the early 60's Bruch developed a colour tv system which was an improvement on the NTSC system then being used in the USA. The new system, which became known as PAL, is of course used in most European countries and thus in most colour tv sets suitable for use in Europe. Because the patents on PAL were legally strong, Telefunken, (with the help of EMI, and now Thorn-EMI, as the company's British agent) was able to insist that any firm making or selling PAL colour tv sets did so under a patent licence. The licence not only earned money for Telefunken on every PAL set but also put very strict limits on the number and type of PAL sets imported into Europe from the Far East.

Now the PAL patents are expiring. But thanks to the different laws in different countries the expiry dates are confused. Also because new patents on PAL improvements have been granted over the years to create the illusion of an everlasting patent folio, electronics companies are still unwilling to dispute the illusion in court. The Taiwanese firm Tatung recently bought the old Decca tv factory at Bridgnorth to secure a PAL licence. No licence has ever been given to a company operating out of Taiwan or Korea, or for that matter Portugal. This has been deliberate policy on the part of Telefunken and Thorn-EMI to protect Europe from a flood of cheap sets made in countries where production worker wages are still much lower than in European factories.

Another invention in the electronic field which has proved financially rewarding is that made in the late 1960s by the US firm

Sanders Associates. The company filed a patent application for a "television gaming and training apparatus and method". This, and a series of follow-up patents, covered the broad concept of generating blips on a tv screen and offering the viewer the opportunity to control them. Sanders eventually sold the patent rights to Magnavox, Philips US subsidiary. Virtually every tv game sold today is now made under licence to these patents, with a royalty paid to Magnavox. The Sanders patents could well prove to be the most valuable electronics folio of all time.

Because every country has its own patent laws, and a patent in one country only protects an invention in that country, it clearly makes sense for an inventor to file patents on a new idea in as many countries as possible around the world. But to patent an invention on a worldwide scale is prohibitively expensive. So all the largest firms, with the most important inventions, must take a value judgement on which countries warrant the cost of patent protection. Phrases like "world patented" or "world patent pending" are almost always bluff.

Disputes and delays

Bluff is an important part in patent procedures. Suing on a patent in court is even more expensive than obtaining one. Once a patent dispute reaches court, only the lawyers will win. A classic example and a warning to anyone involved in a patent dispute, is the case between British Celanese and Courtaulds in the early 30's. For four years the two textile companies fought a patent dispute in court which, even then, cost them around £100,000. Even the Celanese-Courtaulds battle was short and cheap compared to that between the Glacier Metal Company of Britain and the Cleveland Graphite Bronze Company of the United States. In 1934 CGB was granted a patent on the method of making main bearings for car engines. In 1937 the two companies started a legal battle over the intertwined issues of whether the CGB patent was valid and whether Glacier was infringing it. Thanks to delays caused by the outbreak of war, and a series of appeals, it took until the early 1950's before the House of Lords finally reached a decision. The protagonists agreed to settle their costs out of court because by then the patent had died of old age!

Patent disputes can be so wearing to all parties concerned that they will quite literally drive the litigants to suicide. This is exactly what happened in the case of Major Edwin Howard Armstrong, inventor of f.m. radio. While still a young man Armstrong patented regenerative feedback, and the super-heterodyne principle. In 1920 he signed over these patents to Westinghouse for half a million dollars. He needed the money to help pay his legal fees arising from a bitter patent dispute with Lee de Forest over the patents on feedback. Armstrong and de Forest fought each other through twelve separate court hearings, winning six each. Then in 1934 the Supreme Court in Washington handed down a final judgement. It was against Armstrong, leaving him no longer the true

inventor of feedback. Although the decision soon achieved legendary status as classic proof that the law is sometimes an ass, Armstrong was terribly disillusioned with patents. Nevertheless he still found the time and enthusiasm to work on super regeneration and then f.m. communication, which he patented in early 1933.

In the late 1930's the major US radio manufacturers, including Westinghouse, GE and Zenith, took licences to manufacture f.m. receivers under the Armstrong patents. But RCA refused. The outbreak of war postponed a legal confrontation between Armstrong and RCA. But in 1948 Armstrong sued. The pre-trial work necessary just to prepare the case for court took five years. The patents expired on Boxing Day 1950 but the court case continued. On the evening of 31st January 1954, Major Armstrong, exhausted by it all, just walked out of his 13th storey apartment window in New York to instant death.

Armstrong's widow, Marian, continued the case in Armstrong's name. Shortly before his death he had filed twenty fresh court actions against a string of smaller f.m. set manufacturers. To pay for these cases, Marian Armstrong made an out of court settlement with RCA for one million dollars. It was not until 1967, seventeen years after the Armstrong f.m. patents had expired and thirteen years after the inventor's death that the most crucial Armstrong case - against Motorola - was decided in Armstrong's favour. The inventor was posthumously vindicated on all 13 points in dispute and 10 million dollars of back royalty payments were collected from Motorola and the others. This payment was for just three years of activity on f.m. in the United States between the end of the war and expiry of the patents.

Our own Alan Blumlein was less lucky. He died, in 1942, ten years after his invention of stereo and long before there were any commercial rewards. It is often said that inventions are ahead of their time and Blumlein is a classic example of an inventor ahead of his day. His master patent on stereo, BP 394 325, was filed between 1931 and 1932. It was hopefully kept in force by his employer EMI for the whole of its sixteen years natural life, despite the fact that there was no commercial call for what it protected. As Arthur Keller of Bell Labs in America, who was working on stereo at exactly the same time as Blumlein (unbeknown to each other) told me in America last year: "It was the recession and people couldn't afford one loudspeaker, let alone two".

The EMI-Blumlein patent routinely expired in 1947, but EMI made an application to have its life extended because of the hiatus created by the war years. Under special provisions a new patent on stereo was sealed in 1949 and had a five year life. So Blumlein's original patent did not finally expire until the 13th December 1952. This was just a couple of years before the first stereo tape recordings were issued. Discs came at the end of the fifties. So neither Blumlein, who was dead, nor EMI, whose patents were dead, reaped any financial reward from the invention.

Ideas exposed

To patent an invention, then, can be as demoralizing as it can be rewarding. But it is fortunate for the general public that inventors do still continue to file patents. The reason is in the word "patent", which means to lay open. As previously explained, a patent is a bargain struck between the Government and an inventor, with the inventor disclosing full details of the new idea in return for that elusive and limited period of legal monopoly. The resultant value of patents as a source of information is widely misunderstood and grossly underestimated. Patents are probably the only technical publications which remain permanently published "in print". It is possible today for anyone to read a copy of British patent Number One of 1617, simply by visiting any patent library which houses a full collection of British patents. A full xero-copy can be bought for the same price and as easily as a copy of any other British patent. Of course, BP No. 1 is now only of value as a curiosity. Although it ostensibly describes a new process for printing "mappes", the five pages of text are filled mainly with prosaic "know ye's", "whereas we's", and "uttermost peril" threats. But some of the millions of more recent patents are much more informative.

An inventor is legally obliged to give a full working description of his idea, and a method or means of putting it into practice. Even if only a small aspect of the idea is new, and patentable, the description must still be full. It must put the new idea into perspective and enable someone who understands the general field of technology to put it into working practice. So a patent can tell all, or almost all, about a company's research project. Quite often a company with a supposedly secret idea will already (and unrecognised by most of the staff) have published that idea to the public in the form of a patent! This is particularly likely now because under the new patent laws pending patent applications are published. (Under the previous British laws only granted patents were published). For instance while the technology of the new Sinclair flat-screen tv tube was supposedly still under wraps, full details had already been published in pending patent applications. The press was thus quite free to publish information which the company and its PR people regarded as secret. And a search through Kodak's patents tells much more than the company tells. Its important to understand that you don't infringe a patent simply by reading it. You can also talk and write about what it describes. It's only when you start to use the invention that the legal problems arise. Even so, the effective scope of a patent is defined by a set of claims at the end, not the detailed description and drawings that precede them. These claims may be very limited in scope, even though the preceding description is lengthy and detailed. USA patents number 3,852,787 on the Nimslo 3-D process is a good example of this. The text and drawings describes in fine details of the process but the patent claims are much more limited.

What to patent - and when

Patent claims must be very carefully drafted. If they are too broad, or greedy in scope, they will raise official objections from the Patent Office examiners, whose job it is to process every application before granting a patent. And even if the Patent Office can be persuaded to grant excessively broad claims, the resulting patent may be open to legal attack because its claims also cover well known devices. When a patent describes a broad field of technology in detail, but claims only a specific fine point of detail, this is usually a sure sign that most of the field is already covered by other patents or is no longer patentable because almost everything is well known and in the public domain.

This point underlines a basic canon of patent law. To be legally valid a patent must claim an invention that is truly new when the application is filed. If anyone, including the inventor, has previously disclosed the idea, then any patent granted on it will be open to legal attack and probably worth no more than the paper on which it is printed.

There was a good example of this in the field of quadraphonics. American inventor David Hafler had a clever idea of deriving surround-sound from stereo. This was the so-called "Hafler system". Different information is extracted from the stereo pair of outputs from an amplifier and fed to extra speakers. Hafler patented the system but only after he had published an article describing it. So at least part of his patent monopoly was automatically invalidated. The inventors of the Aerostat anti-static pistol have faced a similar problem. Their pistol was shown on the tv programme *Tomorrow's World* before a patent application was filed.

Under the new British laws (but not under the old laws) an invention must be truly inventive as well as new. Suppose you came up with the idea of soldering a joint by clamping a soldering iron in a vice, and moving the joint and solder over the fixed iron. Strictly speaking this could be new, because it's unlikely that anyone has ever patented the idea before or suggested it in print. Everyone has previously clamped the joint and moved the iron across it. But the new idea is plainly obvious, not inventive, and thus not now patentable.

Although a narrow patent claim, which seeks monopoly on just one specific technical advance, may be legally valid, it may also be of little commercial value. It is too easy for a would-be infringer to avoid. In the mid-1960s the National Research Development Corporation filed a patent application on the use of carbon fibre as a material strengthener. But the claims in this patent were drafted in narrow terms to cover only carbon fibres made from a particular raw material (polyacrylonitrile). After the NRDC patent was granted other firms devised and patented other ways of making carbon fibres from other materials e.g. pitch and rayon. So the NRDC patent was enforceable only against carbon fibres made from the particular raw material specified in its claims.

By now it should be clear that securing a patent is a tricky legal business. In fact it's even more tricky than you would think. Some people would say it's as easy and safe as taking out your own appendix. So inventors should seek professional advice from a patent agent. And of course they should do so before saying anything to anyone about their invention. Remember always that the grant of a patent is no guarantee of legal validity. The Patent Office examiners cannot possibly be expected to know of every prior sale, publication or disclosure which can undermine the legal strength of a patent. But you can be sure that if you are granted a patent on a commercially valuable idea, if you have disclosed that idea before the filing date, someone will subsequently use that disclosure to attack your patent if it is to their commercial advantage.

Taking advice

The Chartered Institute of Patent Agents (Staple Inn Buildings, London WC1V 7PZ) publishes a list of qualified or chartered agents. But be warned that patent agents are, like solicitors, expensive. They can charge you at least £30 or £40 an hour for advice and patent aid. This is of course on top of all the official legal fees (like stamp duty) involved in securing a patent. And then there are those renewal fees which in Britain must be paid annually from the fifth year of life of any patent you are granted. These fees are heavy and run on a sliding scale of several hundred pounds a year.

Unlike the Government Patent Office, patent agents don't operate on a fixed charge of fees so ask for a rough estimate of costs when you talk to a patent agent about your invention, or you may find yourself faced with a surprisingly heavy bill. Also, although in theory any patent agent should be able to handle any case, in practice of course some specialise in chemical matters, others in mechanical matters and others in electronics. Some patent agency firms employ several qualified agents to cover a wide spectrum of science and technology. Inevitably word of mouth recommendations can be very valuable.

A patent agent's advice is needed not just when you have invented something and want to patent it; you should also take a patent agent's advice when you are planning to manufacture something, perhaps in the face of a prior patent. If you know of a patent's existence it's easy to establish whether it is still in force, has expired through natural old age or been allowed to lapse through non payment of renewal fees. But it is much more difficult to establish whether what you are doing does or does not infringe the claims of some unknown patent.

There is also now some confusion under British law over the relevance of artistic copyright to inventions. Artistic works in the UK are automatically afforded copyright protection and as a result of various legal precedents created over the last decade, a court may decide that the artistic copyright in a set of engineering drawings or blueprints is infringed by someone who produces a closely similar

item. There is even some legal doubt over whether or not an inventor forfeits artistic copyright when a patent has been granted on the idea. So it is possible that a design not covered by a live patent may be covered by artistic copyright and drawings. There is also of course the possibility that a recent improvement on an old unprotected idea may be covered by a new patent. Frankly anyone who relies on their own judgement to decide whether or not they are infringing someone else's patents is asking for trouble. There really is no useful advice to give, other than take legal advice from a patent agent.

It's here worth pointing out that under a quirk of British law a solicitor is entitled to act as a patent agent, even though solicitors are not required to take the same very tough examinations faced by trainee patent agents. There are some solicitors who specialise in patent matters and are every bit as competent in this areas as a qualified patent agent. But there are other solicitors who know little of patents. Some know enough to recognise their limitations and sub-contract patent work to a patent agent. This can put up the end price to the inventor and make the chain of communication confused. Worst of all, some solicitors know so little about patent matters that they don't recognise how little they know, and thus feel confident to advise on patent affairs.

Even if you take advice from a patent agent, it can help to have some background knowledge of the law. Apart from anything else it can cut down the time, and thus the cost, of initial consultation. What follows therefore is not, repeat not, intended as a do-it-yourself guide to patenting. It's simply a briefing on patents which is intended to make any subsequent consultation with a patent agent more efficient, more effective and more economical.

Because patent law in every country is different, what follows applies only to the United Kingdom. British patent agents have associates in foreign countries through whom they file foreign applications. If this is done within one year of the British filing date, the original British filing date can be claimed for the foreign applications. There is also now a European scheme, which makes it easier (and under some circumstances cheaper) to file in a number of European countries. One day, but not yet, inventors will be able to obtain a single patent covering the whole Common Market. There also exists a Patent Cooperation Treaty which takes in countries all round the world. This, rather like the European scheme, makes it easier, and sometimes cheaper to file in several countries at once. But the over-riding consideration is that foreign filing is extremely expensive. Unless you have good reason to believe that your invention is a potential worldwide money spinner, then a British application is the best compromise between doing nothing, with the risk of seeing someone else reap the rewards from your idea, and patenting in a string of foreign countries and going bankrupt in the process.

This prompts one further point. If you

are hoping to sell an idea, rather than exploit it yourself, then you must first file a patent application. The very act of offering an idea to a third party may well spoil your chances of subsequently securing a legally valid patent on it. This is because most firms will refuse to consider an idea in confidence. They are scared that the inventor may disclose in confidence what they already have on their own secret drawing board. Such a clash can create the most awful legal tangles. So usually a firm will insist that before looking at any invention it must be covered by a pending patent application and disclosed without any seal of confidence.

The basics of British patent procedure

For the sake of this section let's assume that an inventor dreams up a new idea for noise reduction which is different from Dolby and dbx. It's not strictly necessary for him to build a working system before filing a patent application. But obviously there's little point in filing a patent application on something that won't work. Some experimental testing is thus usually worthwhile. But the inventor shouldn't experiment for too long or in the meantime someone else may come up with the same idea and file their own patent application first. Also the inventor should not talk about the circuit, except to friends and colleagues in confidence. Certainly he should not try and sell it to anyone or publish it, for instance in a magazine article.

Let's assume that the idea seems to work. The next stage is to stop and think hard about whether it's commercially viable. Is there really room in the world for another noise reduction system as well as Dolby and dbx? What does it offer that Dolby and dbx can't offer? Is it cheaper, better, or what? In other words, is it a better mousetrap, or just another mousetrap?

Let's now suppose that the inventor has good reason to believe that the new noise reduction system not only works, but will sell in competition with Dolby and dbx. Some people would say that the next step is to carry out a patent search and see whether the idea is new. But in practice this may not be the best course of action. Searching for prior patents in a field of subject matter (in this case noise reduction systems) is a lengthy, complicated, expensive and not always very conclusive business. It takes years of practical experience to become an efficient patent searcher. There are professional firms which specialise in patent searching, and these are often employed on a sub-contract basis by patent agents. Other patent agents have "tame" searchers on the payroll. Some very large manufacturers employ their own searchers. But whoever does the work, it's never easy and it's never cheap. A search will cost hundreds even thousands of pounds. Also the fact that no relevant patents are found in a search isn't proof positive that no relevant patents exist. The British Patent Office has been heavily criticised over recent years for mis-filing some patents, so even the most diligent

searcher couldn't be expected to find them.

Of course it makes sense to pay for a patent search before embarking on an expensive development project, for instance to produce chips and market equipment incorporating the new noise reduction system. But first priority, assuming the idea works and the inventor thinks it has a commercial future, is to get a patent application on file and so establish a priority date.

Under the old British patent laws (prior to 1978) the inventor could cheaply file a provisional specification which gave a rough outline of an invention. Then, a year later, a complete specification told the whole story and claimed monopoly. Today an application can still be filed cheaply without claims and lie dormant at the Patent Office for twelve months. During this period the inventor can continue to work on the project, perhaps trying to sell it to a manufacturer. The application has established a priority date and generated the freedom to talk and write. If the idea proves to be less exciting than at first seemed likely, then the application can simply be abandoned. If the idea looks hopeful, then within twelve months the inventor must pay extra fees and file a set of claims to define the scope of the legal monopoly sought. These claims would for instance distinguish the new noise reduction system from whatever the inventor knows about all the many noise reduction systems which have been described and patented over the last half century. The further fees pay for an official search by the Patent Office. (This is another good reason for not bothering too much about an earlier, privately-financed, search). After that more fees buy a thorough examination. If all goes well the application is accepted and granted. But it can take up to 4½ years. An important point to remember is that after eighteen months from the filing date, the application and the results of the search report will be published for anyone to read. So any secrecy is then forfeited for ever. Objections by the Patent Office examiners, for instance that the idea isn't new, or is obvious and without any inventive step, or that the application is unclear, have to be dealt with in correspondence, logged phone calls or meetings. Although there is nothing to stop an inventor drafting his own application documents and handling or "prosecuting" the case through the Patent Office, it's a daunting procedure. Also most patents which are obtained by inventors, acting on their own behalf, are legally very unsound.

By far the best course of action is for the inventor to have a patent agent draft the original description, follow through after a year with the claims and then argue all the matters that arise with the Patent Office examiners. The pitfalls for d.i.y. patenters are too numerous to mention. If, for instance, vital information is left out of the original case papers, it can't later be included. A new application will have to be filed. This can cause terrible problems for the inventor. Suppose, for instance, that

the Patent Office searcher finds a previous disclosure of a similar noise reduction circuit, but the new circuit has a quite different attack and release time which provides immunity from undesirable breathing noises. This small difference might be enough to secure the grant of a patent on the new circuit, with the claims limited to circuits for generating the particular beneficial range of new attack and release time constants. This feature might turn out to be the vital selling point of the system. But if it wasn't adequately described in the original application documents, then the inventor won't be able to claim it and the application will fail. This holds good even if the inventor had worked on and solved the problem of attack and release time constants before filing the application. If a description of that work isn't in the patent it's legally valueless. A second application might come after someone else's work on the same invention. There's also a risk from over-specific description. Suppose, that the time constants have been too closely defined in the original document, with only a very limited range of constants listed. If it subsequently turns out that time constants outside that range are ideal, then the inventor may end up with a patent but one that only protects a circuit that isn't of commercial value.

Patent fees are continually rising and so are patent agent fees. It can easily cost several hundred pounds to secure a patent on even a very simple idea that runs into no prosecution difficulties. But most ideas that are worth patenting aren't simple and they don't sail through the Patent Office without problems. Although the Patent Office official fees are fixed, for the most part irrespective of the invention and problems of prosecution, patent agents charge by the hour. So the more complicated the case the more it costs to secure a patent. And of course there's no guarantee that the inventor will be granted a patent in the end, however much he spends, if the Patent Office doesn't agree that the idea is new and inventive.



The Patent Office, 25 Southampton Buildings, London WC2A 1AY provides free official pamphlets on applying for a patent. The current scale for official fees is also available from the same address. Copies of all British patents and the list of patent agents who are registered to practise in Britain are available for free reading in the Science Reference Library (once the Patent Office Library) which is housed in the same building as the Patent Office. □

CRISIS CONTROL

In the first part of this article, R. E. Young dealt with the problems faced by control engineers in moments of crisis. The second part is a description of methods of data presentation and operator training.

by R. E. Young,
B.Sc. (Eng.), M.R.E.E.S., F.I.E.E.

separate instrumentation chains, each working on an entirely different physical basis from the other.

In many of the applications proposed for emergency working — and as used for aerospace development — closed-circuit television provides the second chain, with conventional transducers used for the first. There are several advantages in adopting such a system, not least the facility it gives to make calibration checks on remote transducers which are virtually inaccessible under working conditions, and which cannot even be approached in a hostile local environment.

The main argument for independent check — again backed by aerospace experience — lies in its relative invulnerability,

when compared with straightforward duplication, an obvious alternative. Taking a severe break-down condition in a duplicated system, failure of one component due to, for example, abnormal mechanical shock, will almost certainly be accompanied by the corresponding component in the other (parallel) set failing in the same way. Even the suggestion of triplication can be countered by the same reasoning, particularly if only one system element fails completely and the other two are on the 'break-point', i.e. are in a 'false indication' type of fault condition. Furthermore, it must be pointed out that the 'voting' equipment generally used in these cases is, by the same token, open to doubt in itself, and especially under far-reaching crisis conditions. Incidentally, this classic voting problem, whether it is carried out by human assessment or by some form of comparator equipment, demands for its final solution comparison with some form of external reference.

Besides the use of c.c.t.v., alternative types of transducer can be used in the second (checking) chain; but as part of the overall philosophy of independent check, the minimum amount of equipment

Independent-check principle

Independent-check methods, which originated in aerospace and similar instrumentation, use the principle of a specific measurement covered by two completely

Fig. 4. Closed-circuit television monitoring can form one of the chains in an independent-check system. System at (a) uses a conventional camera, while that at (b) has a flying-spot scanner and detector.

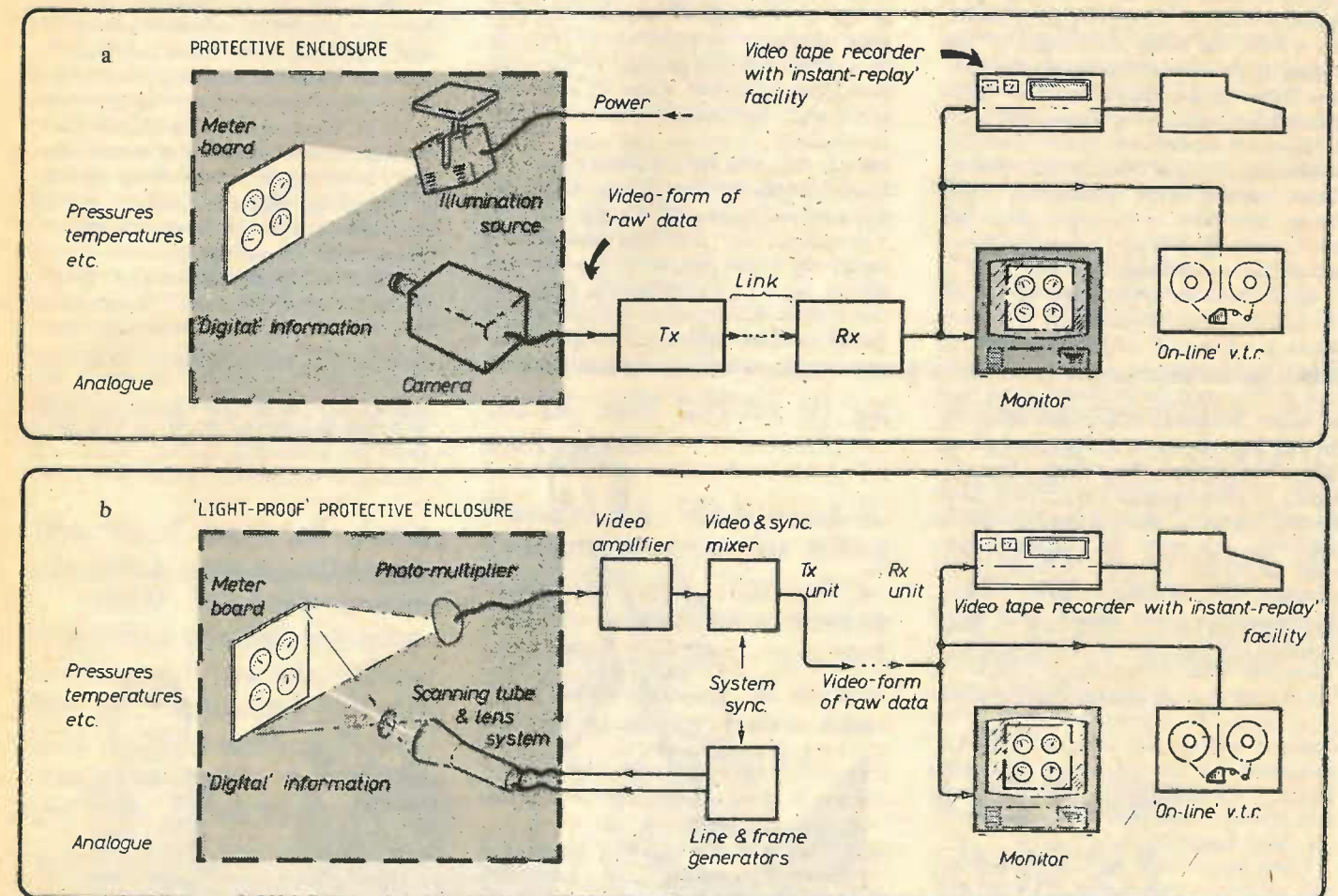




Fig. 5. Sine-wave raw-data trace of balanced-oscillator type of transducer, aided by digital frequency display, discriminates between required reading and interfering pulses. Photo by Manchester Polytechnic.

should be interposed between the instrument output and the data presentation points. In other words, ideally no equipment (liable to cause unreliability or error by its very presence) should come between the measuring instrument and the display.

The considerations lead to the concept of working at 'raw-data' level where the transducer feeds a v.d.u. and, with the balanced-oscillator or other frequency output transducer, presents a sine-wave-type trace. As shown in the photograph (Fig. 5) the c.r.t. trace can be backed up by a digital counter or other frequency meter, but one of the main advantages of this display is that the operator can discriminate between the required 'value' signal and spurious interfering signals which can be expected during the totally abnormal conditions of crisis breakdown. For instance, under such conditions, high-energy impulsive interference alone can reach such proportions as to obliterate completely a coded signal pattern.

Similar considerations apply to the use of c.c.t.v. for independent checking, where it works as a telemetering medium. It has, in addition, an outstanding advantage in that once the intelligence has been in effect 'encoded' in pictorial form, no further degradation in its data content can take place through the system. Also, the ability to read through interference given by the 'frequency' signal is enhanced in the television case since the operator knows what the picture should be and can read it through near-saturation interference. Furthermore - and this is vital for a multiple breakdown due, for example, to 'knock-on' fault development - failure of the tv system as an instrumentation chain is obvious. In comparison with other chains it is effectively 'fail-safe' in that no indication by an individual instrument within a televised group means that the instrument, rather than the remainder of the chain, has developed a fault.

Using these visual methods, which can only be surveyed here in broad terms, does

put a significant load on the observers/operators; but means for reducing this load form part of the treatment in 'Control in Hazardous Environments'² of control room organization which includes a 'two-tier' control structure. The picture of Fig. 6 is a representation of a small, highly-trained crisis management team of engineers working under full emergency conditions at their special positions on the master consoles. The team is operating in a two-tier grouping with the senior engineer at the back in control overall, having access to all levels of information, with their selection determined by him in accordance with his 'reading' of the situation. Communication is also on a two-tier basis with information 'filtered' (data-marshalled) to ensure that only 'mainstream' data and speech reach those concerned primarily with taking immediate decisions and crisis-control actions.

Although the preceding descriptions cover only visual analysis of raw data and similar displays, the writer has suggested that future development should include 'super-software' techniques to replace routine human observation by computer in-

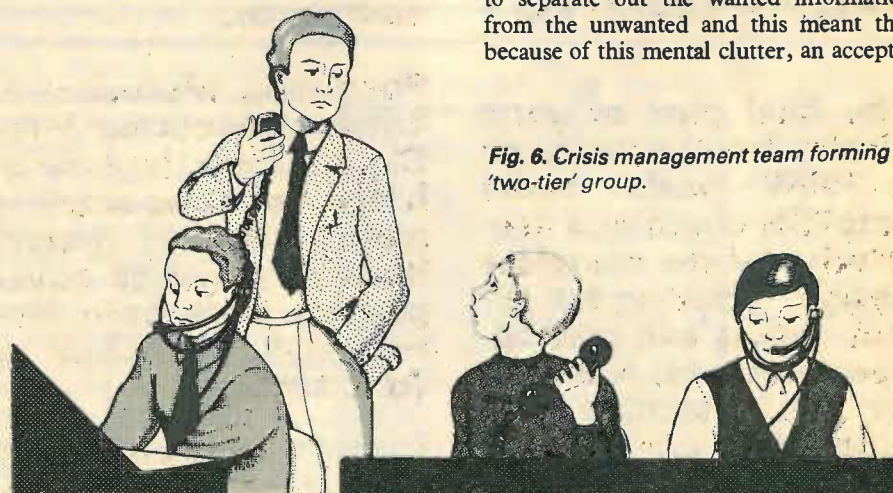


Fig. 6. Crisis management team forming a 'two-tier' group.

terpretation of a number of raw-data television pictures. Thus, for example, a group of (say) simple instrument dials, would be kept under computer-based observation (image analysis) to detect changes, in an anticipatory control rôle, but this would be brought into use for crisis control to take some of the load off the operators under emergency saturation conditions.

Training

These new methods of operational working place a heavy 'thinking' demand on the engineers; and it is suggested that the corresponding levels of training and preparation which are required are such that they should be largely subliminal in nature. This means that the training mechanisms should not be obvious; a 'from-within' type of intuitive element is needed, ideally on both sides (teacher and pupil).

That conventional methods, even most types of simulator training, should be avoided, comes out of the consideration of (stress) conditions A and B and the manner in which individuals enter them. As a general rule, those in condition A had developed an absorbing technical interest in, and grasp of, the system they were operating, and had been helped to reach this position by on-the-job training. Here, they had been allowed to do specific pieces of responsible work, but at the same time were given an overall view of the system at suitably timed intervals without any of the tasks being made over-taxing, either in length of time spent or in unnecessary mental effort (e.g. in memorizing facts not directly concerned with the work).

These points may seem unimportant, but the conclusion which emerged was that, by what amounted to subliminally-induced learning, those in condition A were able to arrive at correct interpretations of situations, and to make correct decisions, without any lengthy mental search (and 'back-comparison') time being required.

In contrast, those in condition B were not able to achieve these near-instantaneous results in such a crisis and this appeared to be due, at least in part, to the way in which their standard (classroom) courses had to be conducted - they had to absorb a great deal of inessential material along with the essential. This meant that, under the stress of an emergency, they had to separate out the wanted information from the unwanted and this meant that because of this mental clutter, an accepta-

ble time of response could not be achieved. In turn, the thinking fatigue generated was sufficient to cause a relapse into condition B.

The importance of these statements needs no emphasis; but it was not until correlation was established with the results of the mental handicap research already mentioned that they were seen to be based on two very different kinds of observation and two different kinds of theoretical follow-up, both of which nevertheless gave, in effect, the same answers.

With this background, it was possible, for example, to embark on various pieces of 'system modelling'; and from them, to predict certain effects such as the delay time which can elapse between question and answer with mental handicap hyperautism, and the distortion (inversion) of words in speech, making a word completely unrecognizable, which appears to be set up as the result of imperfect mental data marshalling (selection) and checking.

Turning to the question of mental handicap itself, "this most mysterious of human complaints", the 'shell' effect not only represents the isolation of the hyperautistic state, but also throws into relief the need to help the mentally handicapped person to communicate 'from within'.

The word 'shell' - put forward by the parent of a mentally handicapped girl - is probably unequalled to describe the state reached when conditions are at their worst, with energy sapped by thinking fatigue, itself set up by, for example, attempts at conversation with no allowance made for delay time, or by unknown visitors appearing without warning. This need to avoid intrusion by strange visitors is not always recognized; but it is understood that in at least one centre in Europe, visitors are not allowed to watch the mentally handicapped students during working hours to avoid disturbing them.

The two-way mirror which permits shielded observation without causing disturbance forms an important part of the Embryo Language Laboratory shown in Fig. 6; and which in this case is being used to give the mentally handicapped the opportunity to use the telephone under controlled conditions. It can be predicted

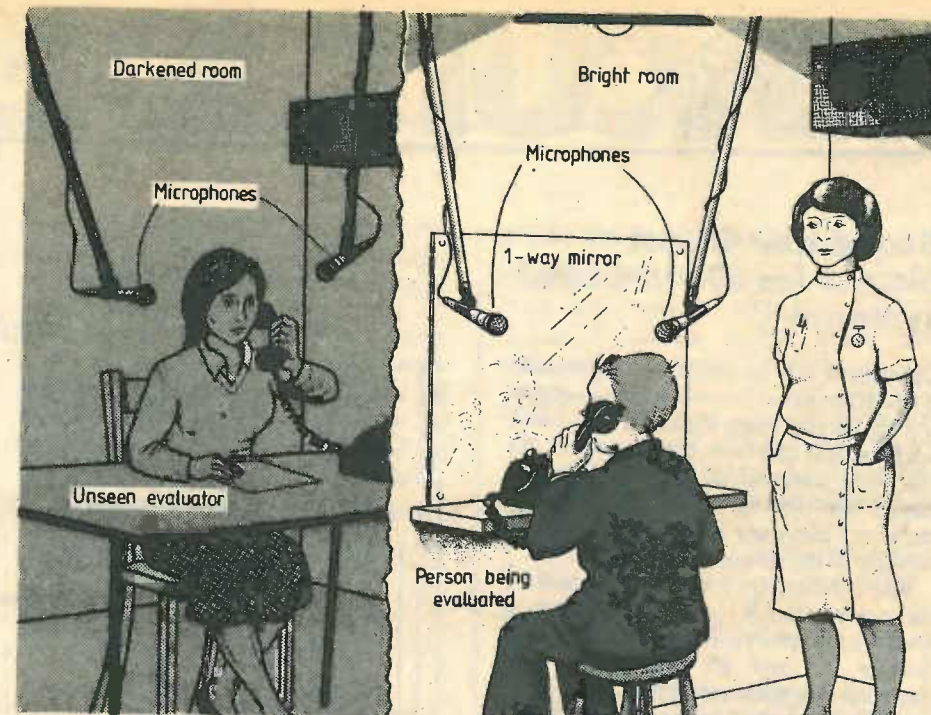


Fig. 7. Embryo language lab. for training the mentally handicapped - in this case in using the telephone.

that, provided the telephone is 'accepted', this can be helpful in reducing the shell, i.e. in reducing the obstacles to communication. It does seem that side-tone and similar effects may well be clutter-reducing, while the interest engendered by using adult technical equipment can reduce the shell enormously.

In the arrangement shown, the student using the telephone, and looking into the obscured side of the mirror, is talking to the instructor on the other side. Microphone/loudspeaker monitoring is provided back to the instructor giving local assistance to the student in this particular instance.

One of the objectives here was to gain information on the degree of confidence given to the student by using the telephone, and the amount which can be attributed to side-tone anti-clutter reinforcement, and how much to the use of the telephone itself. This information is obviously of value on the mentally handi-

capped side, but perhaps even more to study of the B condition.

In general terms, "the mentally handicapped never look at themselves in mirrors"; and the extent to which this is true for the individual shown - looking into the mirror - provides additional information for the assisting instructor. This is typical of the indirect methods which may be used to obtain information unobtrusively so as not to cause distress and to prevent the development of the shell.

Full acknowledgement must be made of the major contribution of Dr. Gordon Avery, when District Community Physician of the Warwickshire Area Health Authority, South District, in his interest in the research programme on mental handicap.

Corresponding recognition must also be given to Professor Harold C. A. Hankins of the University of Manchester Institute of Science and Technology for invaluable discussion of this subject.

Next Month

The final part of John Linsley Hood's series on a 100W mosfet audio amplifier contains a description of the complete design, including full circuit details and printed-board layouts. A design for the matching pre-amplifier, which possesses several novel fea-

tures, will follow in an early issue.

Receiving Meteosat-II. Enhancements for Mike Christieson's high-resolution weather-satellite picture system extend its capabilities to cover primary data from Meteosat-II, launched in June 1981.

Circuit modelling by micro-computer. By re-

moving repetition from a circuit modelling program and using macro-codes for certain routines, a 16-node circuit can have its gain and phase parameters plotted in minutes instead of hours.

On sale July 21

CIRCUIT IDEAS

Sequential digital display for 8080A-based systems

Eight digits can be displayed sequentially in two steps using seven-segment displays. During the first step, segments a, b, c and d are enabled and show the contents of the first byte assigned to this digit in the display ram. During the second step, segments e, f and g are enabled and show the contents of the second byte.


When the display r.a.m. is addressed by the c.p.u. line X (one output from a memory-mapped i/o decoder) goes low and disables IC₄ and all displays. In the meantime IC₂ selects the four lowest-order bits AO-A3 of the address bus to address the required byte in the display r.a.m. IC₃. With the MEMW line low (in response to a store-in-memory instruction) the lowest-order bits D0-D3 of the data bus are stored in the addressed byte of display r.a.m.

When the write operation is terminated, X goes high and the refresh circuit is enabled. Outputs of the hexadecimal counter IC₁ (Q_A, Q_B, Q_C, Q_D) are selected by IC₂ to address the 16-byte r.a.m. (IC₃). When Q_A is high, the output of IC₃ is passed to segments e, f, g of the display chips. The seven-segment chip addressed and selected by IC₆ will be the only one to respond to the output of the display r.a.m.


Decimal points are excluded in this design. To permit control over decimal points, connect pin 11 of IC₃ to pin 12 of IC₅ and pin 11 of IC₅ to the cathode of the decimal points. The circuit is expandable to display more than eight digits, but other components such as 2112-4 ram are recommended, instead of a multiple of 7489 rams, to reduce cost and size.

The word byte refers to a word of four bits in the display r.a.m.

G. A. M. Labib
Heliopolis
Cairo

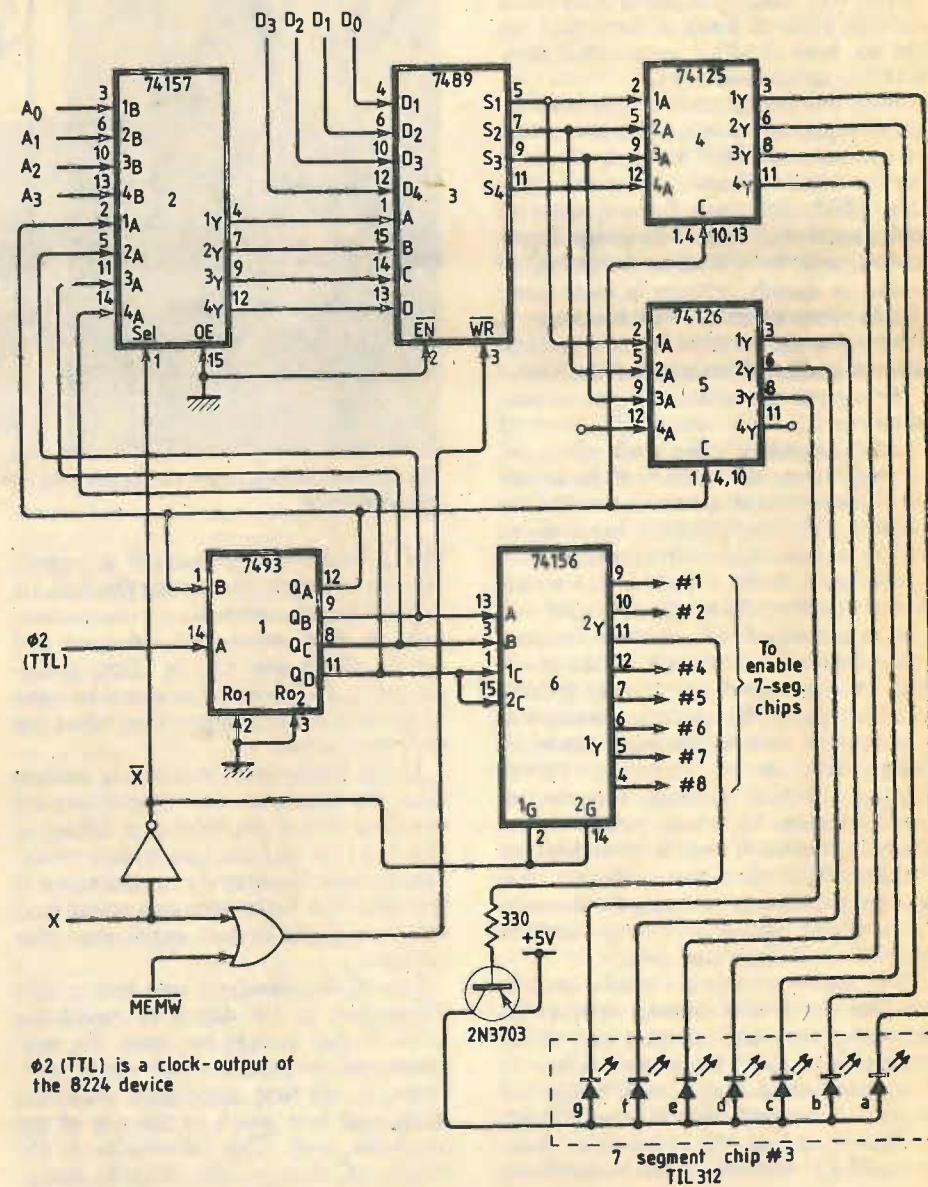

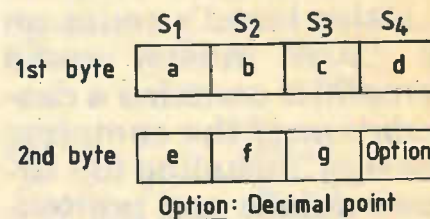φ2 (TTL) is a clock-output of the 8224 device





As data sensed at the outputs of IC₃ is the complement of data stored, and as seven-segment chips are common anode, a logic 1.0 data-bus bits (D₀, D₁, D₂, D₃ or all) will cause the corresponding segments to light when enabled.

Loudspeaker displacement detector

Used as part of a motion-feedback system, this circuit detects the dynamic displacement of a loudspeaker optically using an led and phototransistor. The small infrared led is attached to the loudspeaker cone and the photo-transistor positioned to give between 20 and 30mA led current. Optical bias for the photo-transistor and compensation for changes in ambient lighting are provided by the op-amp. Sensitivity is high, and for practical displacements, the

output is quite linear and does not require square-law conversion. Simple shielding from artificial lighting may be required to prevent 100Hz ripple on the output, and screened cable should be used for the transistor lead. Construction of the prototype is shown in the diagram. 'Blue-tak' was used to secure the led and leads to the loudspeaker. The cross-piece and transistor mountings should be as rigid as possible.


Simon Young
Cambridge

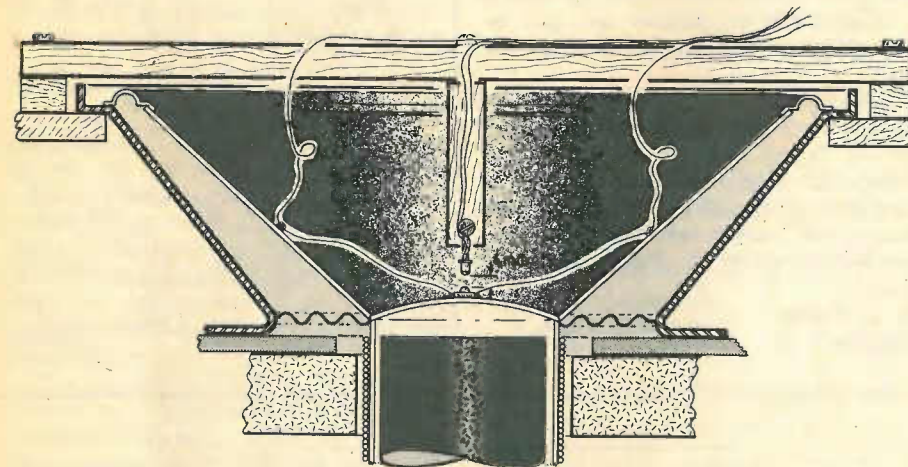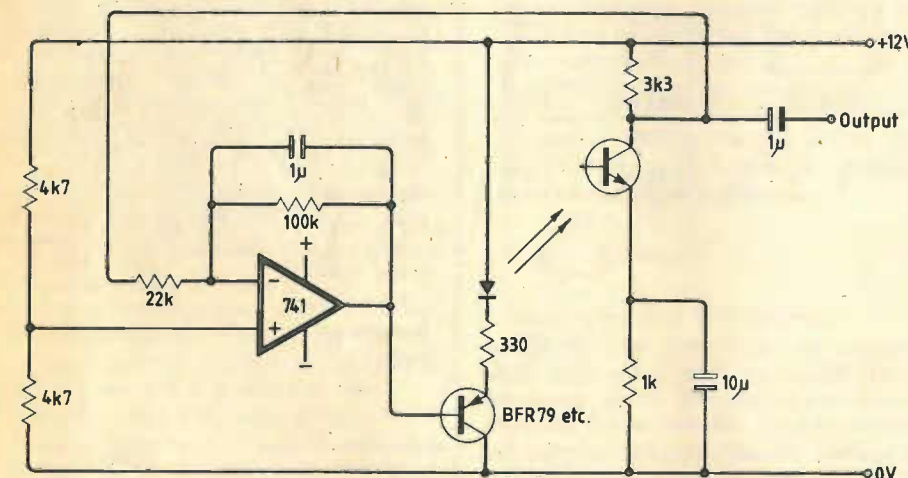

Non-polarizing R-to-V transducer

Circuit shows a resistance-to-voltage transducer designed for a soil-moisture measuring instrument. It uses complementary j.f.e.t.s to provide positive and negative constant-current sources for R₂. The resulting voltage is rectified by IC₁ and IC₂ to produce V_o = I_{const} × R₁.

A. Bartram
University of Exeter
Devon

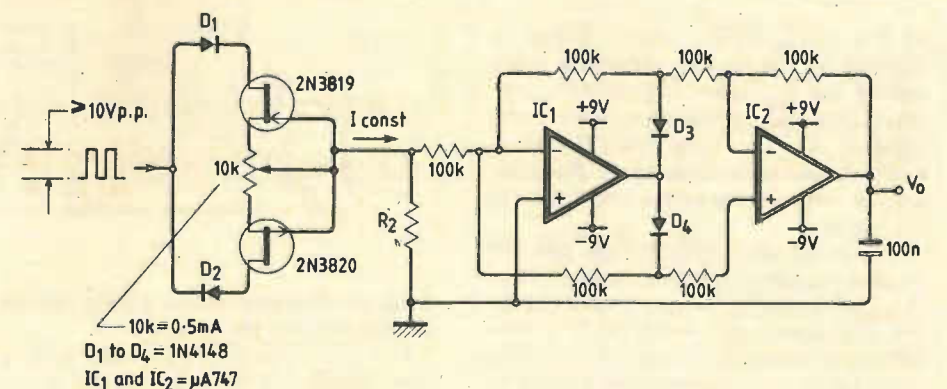

10k = 0.5mA
D₁ to D₄ = 1N4148
IC₁ and IC₂ = μA747

Full-wave precision rectifier



This circuit has two advantages over other forms of precision rectifier - for unity gain only two matched resistors are required, R₁ and R₂, and with capacitive loads, the circuit becomes peak reading. The peak-reading configuration decay-time constant is defined by the capacitance, C, and the parallel combination of R₂ and R₃.

If the rectifier is required to have gain, then R₄ may be included, in which case;

$$\text{Gain} = \frac{R_2}{R_1} \frac{R_3 + R_4}{R_4}$$

The circuit is accurate at high frequencies and responds to greater than 100kHz with TL082 amplifiers. If high-frequency response is not required, D₁ and D₄ may be eliminated and R₃ reduced to zero. Note that without D₁, there must be a d.c. path at the input.

C. W. Beal
Baildon
West Yorkshire

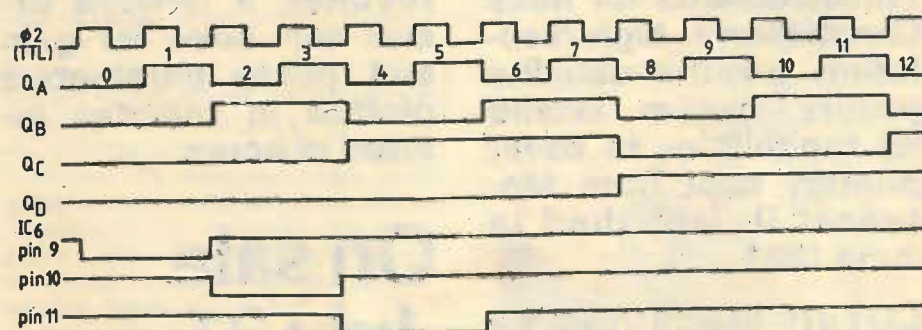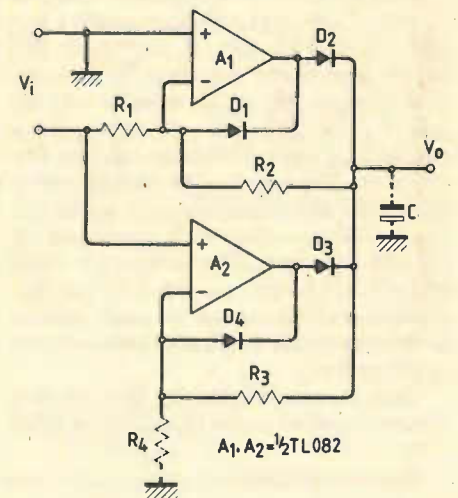


Connecting answering machines

This circuit connects a telephone answering machine (tam) to an exchange line and includes relay switching so that all the facilities may be used automatically, without restriction.

For automatic call answering the tam senses a.c. ring current from the line via the n.c. contacts of relay 1 and, after a predetermined period set by the user (1 to 10 rings), answers the call by connecting a d.c. loop across its terminals. After exchange of outgoing and incoming audio messages, the tam opens the d.c. loop and returns to a state of readiness. This automatic process may be interrupted at any stage by picking up manually and answering any of the associated telephones, energizing relay 1. If this is done before the tam answers, relay 2 does not energize. If interruption happens after the tam has answered, the d.c. loop of the tam causes relay 2 to be energized and its n.o. contacts place the attenuator, comprising relay 2 coil and 250µF capacitor, blocking the audio path between the tam and line. Sensing the resulting silence, the tam resets and returns to readiness.

Outgoing calls may be dialed normally from any of the associated telephones; the n.o. contacts of relay 1 (whose coil is slugged by 2000µF) and the n.c. contacts of relay 2 connect to the tam network and effectively block the 50 volt 10Hz dial pulses from falsely operating the ring-current detector. The diode in series with the coil of relay 2 stops the 250µF capacitor discharging while dialling and so aids this blocking. The tam may be used to record both sides of a telephone input across the line via the n.c. contacts of relay 2 and the 0.33µF capacitor. The 250µF capacitor and silicon diodes connected in parallel-opposition limit signals to some 600mV peak-to-peak but do not affect recording of conversations.

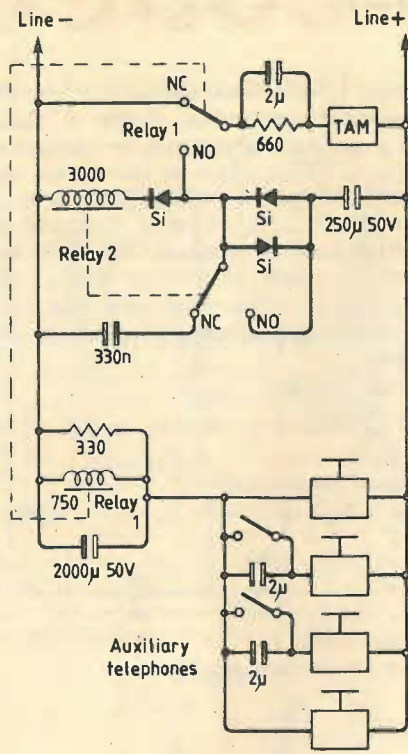Calls being answered by the tam may be monitored by means of its internal loud-



speaker and interrupted manually if desired. Monitoring may also be done from other rooms using one of the associated telephones if d.c. through the coil of relay 1 is blocked. This may be achieved by means of a series 2µF capacitor shunted by an n.c. press switch which is pressed when it is desired only to monitor calls and released (or not pressed) to interrupt the tam.

Normal line polarity should be observed, as shown. The 660Ω resistor and its 2µF bypass capacitor, and the 330Ω resistor across relay 1 coil adjust the d.c. level through the tam and the sensitivity of relay 1 for reliable operation when any auxiliary telephone is picked up or replaced.

H. T. Wynne
Glasgow


Thermometer for d.m.m.

The circuit shown can be combined with an inexpensive digital-panel meter to form a compact, accurate digital thermometer.

A dual op-amp and a PRT-100 platinum resistance thermometer, whose resistance is a linear function of temperature, are the main elements. The first op-amp is used as a precision constant-current source and the second as an amplifier. Any 3½-digit meter with a 1999mV range will indicate temperature directly in degrees centigrade, from 0 to 199.9 with 0.1 degree resolution.

The sensor is pre-calibrated and its resistance is linear from -40° to + 400°C, so the circuit can be calibrated by replacing the sensor with two known resistances. First, using 100Ω, zero adjustment is made with the '0° set' potentiometer ($R_T=100Ω$ at 0°C). Next, the gain is adjusted for 200°C on the second potentiometer using 180Ω ($R_T=180Ω$ at 200°C). This thermometer can replace thermocouples in many applications and provide better accuracy (± 1%) and linearity (2%) between 0 and + 200°C.


Dil Sukh Jain,
Hyderabad,
India.

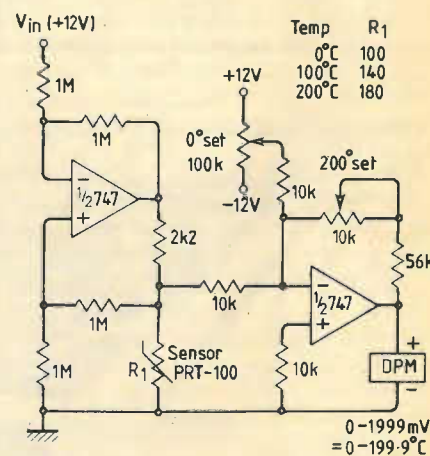

Poor man's current dumper

At low output levels, output current is supplied by the op-amp through a 100Ω resistor and at higher output levels, current is provided by the output transistors. Because of this, cross-over distortion would appear to be eliminated. Quiescent current through the output transistors is not required.

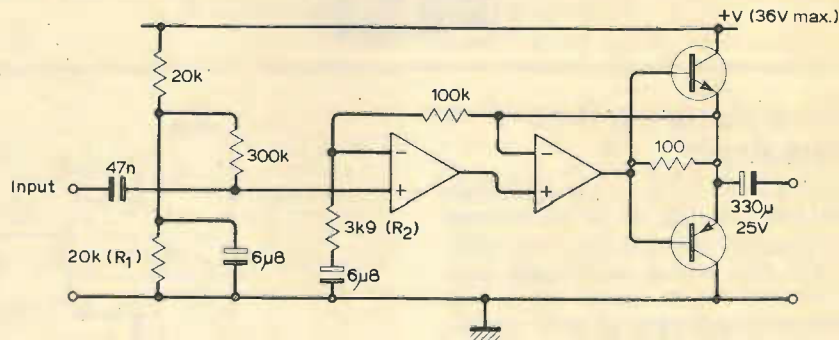The maximum supply voltage that can be used is limited by the op-amp, and was 36V (stabilized) for the prototype using an MC3403 device. An output of 10W into 8Ω was obtained. If the supply is unstabilized, the resistor connected to ground in



the input-biasing potential divider should be replaced with a zener diode.

For the circuit shown, voltage gain is about 28dB, but this may easily be in-

creased at the expense of h.f. response by reducing the 3.9kΩ resistor, R2.

R. C. Cross,
Felixstowe.

MICRO-CONTROLLED RADIO-CODE CLOCK

Based on a 6502 microprocessor, this clock decodes and displays serial information from a v.l.f. receiver. Although requiring powerful and complex firmware for best possible performance in difficult areas, a system for non-critical applications can use only 2K of object code. This second article describes alignment and firmware for a basic clock which can be contained in a low-cost 2716. For future expansion, this ram can be replaced by link selection with a 2732 device.

by N. E. Sand

Because most of the processing is real-time, fast and efficient assembly language must be used to decode and display the transmitted information. In the flow chart for the basic clock, shown in Fig 1, the program starts with a short initialization sequence which sets the interface adapter i/o configuration, the timer for regular lms interrupts, and clears part of the ram area. After initialization, the processor enters the main software loop which is followed continuously. Flags are passed by routine which mainly maintains a series of timers. The receiver output is sampled in the main loop by a routine which searches for level changes from low to high or vice versa. When a change is detected, one of the timers is read and reset. The low-to-high transition usually occurs at the end of a carrier break, the duration of which determines a logic 1 or 0 in the serial code.

Invalid timer values signal error conditions which reject the block of code being received. The various double pulses that occur in the code are detected and ignored. While the main program loop is operating, a continual search is made for the unique eight-bit synchronizing sequence 01111110 which indicates the end of each time frame. When this sequence is recognized, a further timer, also updated by the lms interrupts, is initialized. On time-out a window is set for a further short period, during which a high-to-low transition in the receiver output will synchronize the decoded seconds counter and relevant timers. A software loop is then initialized and maintained in-phase with the received second pulses.

The display is updated whenever a change could have occurred in the display registers. Digit-select codes are set with the relevant data for each digit, and strobing of the display drivers is achieved by writing to these locations in sequence using the chip selects inputs. When the decoded seconds count and timer are at a certain value the error status, including a parity check, is examined and if error-free, the decoded time is transferred to the back-up clock.


This design provides better error protection than the parity bit alone can offer, and does not use too much memory space. A commercial system which offers foolproof operation requires greatly extended error detection and analysis together with optimization techniques to maintain accuracy; far more memory space would be needed

to accommodate the software and this would depart from the "evaluation-system" concept. The present design provides good performance in normal operating conditions and only requires one 2K rom. A high interrupt rate provides good measurement accuracy and resolution in the timers. Overall accuracy of the clock after synchronization with the transmission is approximately 50ms.

The most important part of this clock, or any other design based on a time-coded transmission, is the receiver. Although complex logic circuits or powerful software and microprocessors can be used to detect and analyse any error or noise transient in the transmitted code, unless a carefully designed receiver is used in conjunction with this processing, practically every clock or code will be rejected and the clock will suffer from the usual crystal drift over long periods, or worse still, will not be

Continued on page 56

Fig. 1. Flow chart for the basic clock system.

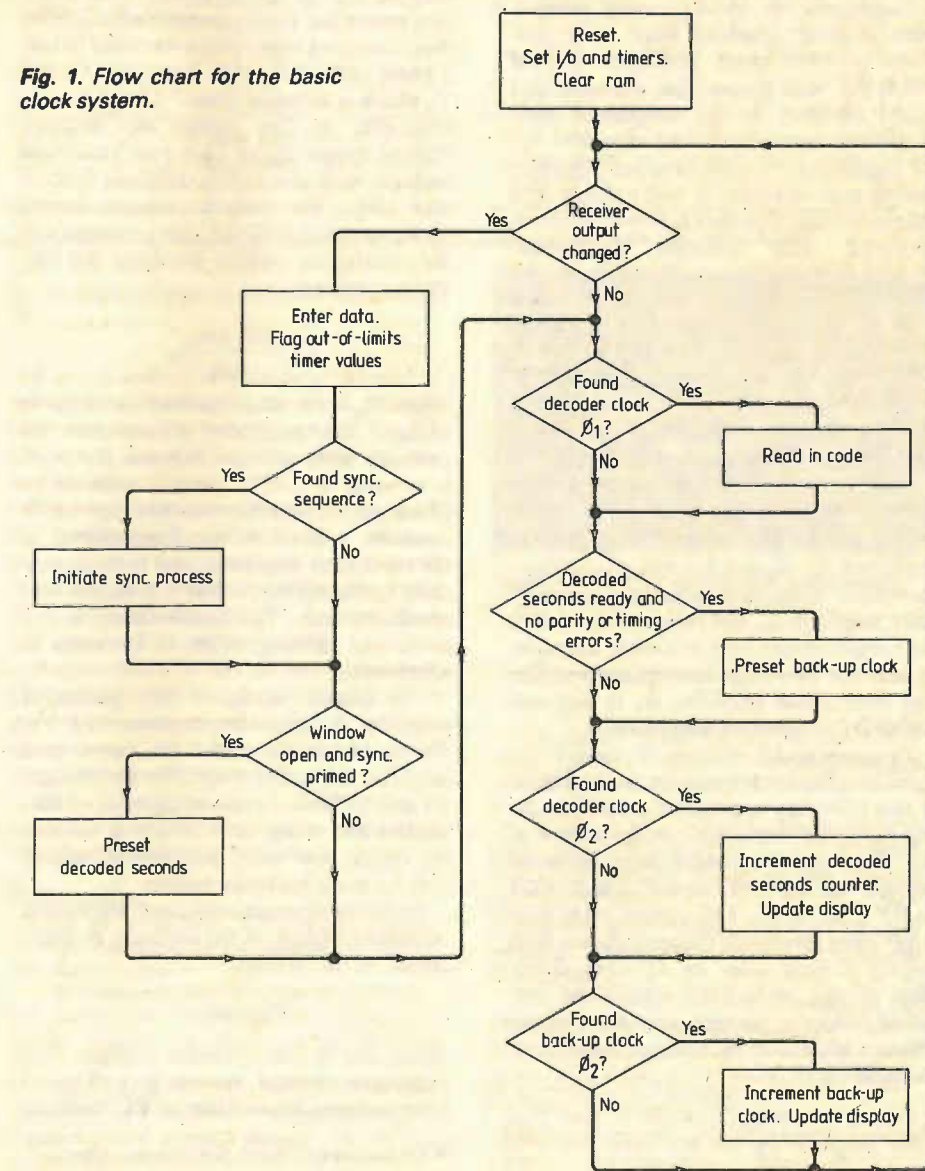

FAST AMPLITUDE STABILIZATION OF AN RC OSCILLATOR

This technique for stabilizing the output amplitude of an RC sine-wave oscillator uses a multiphase rectifier to convert the oscillator output to d.c. This voltage does not require further filtering, which results in a short amplitude settling time. An experimental circuit demonstrates the technique.

by I. M. Filanovsky
V. A. Piskarev
and K. A. Stromsmoe*

A stable sine-wave oscillator with amplitude control usually incorporates a voltage-controlled attenuator. The d.c. input to this attenuator must have a very small ripple to avoid excessive distortion of the output waveform. If this direct voltage is derived from the usual half-wave rectifier, an extremely large filter time constant is required: the oscillator output level consequently settles very slowly. This behaviour is undesirable in low-frequency applications. Several solutions have been proposed to solve these problems, one of which has been to combine analogue and digital circuitry to use amplitude sampling^{1,2} or correction to the capacitor initial conditions.^{3,4} This involves relatively complicated circuits. A more direct and simpler circuit approach is to use oscillator networks with available four-phase voltage⁵ or multiphase oscillators⁶ with the rectified, multiphased voltage obtained from the oscillator. The circuit proposed here also uses multiphase rectified voltages, but these voltages are obtained in a special circuit from two sinusoidal voltages shifted by 90°. The circuit consists of summing operational amplifiers.

The full circuit of the RC oscillator with the eight-phase rectifier is shown in Fig. 1. It includes an RC resonator (operational amplifiers A₁, A₂ and A₃) with the voltage-controlled attenuator (the transconductance amplifier g_m and resistors R₇ to R₈); the control circuit with the error amplifier A₄ and the two-stage multiphase rectifier (the operational amplifiers A₅ to A₁₀ and diodes D₁-D₈) mentioned above.

Two sinusoidal voltages V₁ and V₇ of equal amplitudes are applied to the inputs of two inverting operational amplifiers A₅ and A₆ in the first stage. At the output of this first stage we obtain four sinusoidal voltages shifted with respect to each other by 90° (Fig. 2(a)). The second stage produces eight sinusoidal voltages shifted with respect to each other by 45° (Fig. 2(b)). Here we use the fact that operational amplifier produces vector summation of the voltages applied to its inverting input. For example

$$\dot{V}_6 = -\frac{1}{\sqrt{2}}\dot{V}_1 - \frac{1}{\sqrt{2}}\dot{V}_3 \quad (1)$$

where \dot{V}_1 , \dot{V}_3 and \dot{V}_6 are phasors corresponding to v₁, v₃ and v₆.

The multiplying factor 1/√2 in (1) is achieved by the special choice of the resistors connected to the operational amplifier A₁₀. Changing their values we could obtain a phase shift of V₆ with respect to V₁ and V₃ which is different from ±135°. Thus, in principle, we can obtain any m-phase voltage system if we have two sinusoidal voltages with phase shift different from 0° and 180°. The output voltages appear simultaneously with the input voltages and the multiphase rectifier produces the output d.c. voltage.

$$V_R = \frac{\sin \pi/m}{\pi/m} V_m$$

where V_m is the amplitude of the m-phase voltage. The multiplier $\sin \pi/m \div \pi/m$ approaches unity when m increases (for m=8 it is equal to 0.975). Hence, such an m-phase rectifier can be used as a unit which produces a direct voltage proportional to the oscillation amplitude and without any delay (theoretically, at least), with low harmonic content. The requirement of any additional filtering when m increases is eliminated.

The output voltage of the operational amplifier A₁ coincides in phase with V₅. We could use it and save one operational amplifier in the first stage. But the voltages V₁ and V₇ have the lowest amount of harmonics and using only these two voltages we obtain less total harmonic distortion (t.h.d.) at the oscillator output.

In the steady-state condition, the output voltage amplitude of the oscillator is determined by the equality

$$V_R = E_R$$

where E_R is the reference voltage. The amplitude control system is a Type 1 system due to the fact that an RC oscillator

* University of Alberta, Edmonton, Alberta.

acts as an integrator with respect to an amplitude change^{1,7} in the amplitude control system.

During the static oscillations the condition

$$g_m \frac{R_7}{R_6 + R_7} = \frac{1}{R_5}$$

is satisfied.

The transconductance g_m is determined by the d.c. control current I_c in the resistor R₈ and, for the CA 3080 transconductance amplifier which we used in our experiments,

$$g_m \approx \frac{I_c}{2V_T}$$

where V_T is threshold voltage⁸ (V_T ≈ 26mV at 300°K). The resistors R₆ and R₇ are chosen from the condition that

$$V_7 \cdot \frac{R_7}{R_6 + R_7} \leq V_T$$

where V₇ is the amplitude of v₇. This ensures the linear operation of the transconductance amplifier. The value of R₈ was chosen in such a way that the control current I_c (in the steady state condition) is approximately equal to one half of the maximum control current allowable for linear operation. The control input (pin 5) d.c. potential is close to the negative of the power supply for CA 3080. In this case, the linear operation will be preserved for the whole output voltage range of the error amplifier A₄ and at the same time the value of R₅ will be low. As a result the displacement of poles from the jω-axis into the left

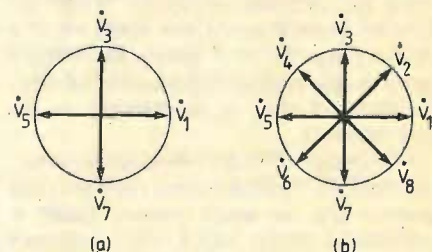


Fig. 2. Output voltages in multiphase rectifier (a) first stage (b) second stage

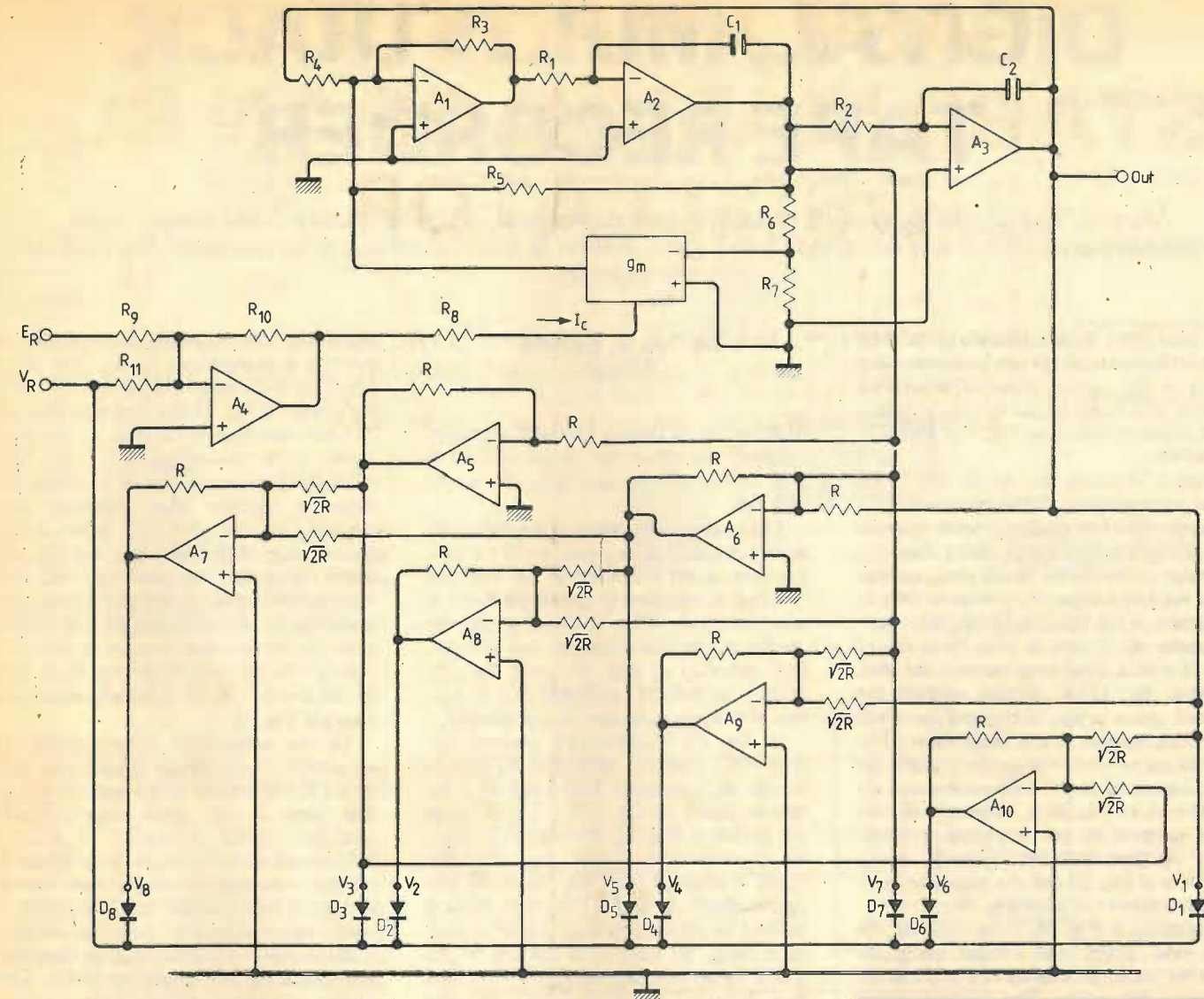


Fig. 1. RC oscillator with multiphase rectifier

or right half plane due to the sudden change in the E_R level will be maximum and the transient response duration will be shortened.

The output voltage of the multiphase rectifier includes the small ripple voltage also. The amplitude of the k-th harmonic equals

$$a_k = 2V_m \cdot \frac{\sin \pi/m}{\pi/m} \cdot \frac{(-1)^{k+1}}{k^2 m^2 - 1}$$

This ripple voltage will be amplified in A₄ and applied to the control input modulating the transconductance g_m. The approach used by Vannerson and Smith⁵ allows us to calculate the output distortion voltage which consists of only two significant harmonics given by

$$v_d = \frac{1}{2} \frac{R_3}{R_8} \cdot \frac{R_{10}}{R_{11}} \cdot \frac{V_m^2}{V_T} \cdot \frac{R_7}{(R_7 + R_6)} \cdot \frac{\sin \pi/m}{\pi/m}$$

$$\left[\frac{1}{(m^2 - 1)} \left(\frac{\cos(m-1)\omega_0}{(m-1)^2 - 1} + \frac{\cos(m+1)\omega_0}{(m+1)^2 - 1} \right) \right]$$

where ω₀ is the oscillator frequency.

In the test oscillator,

- R₁, R₂, R₃, R₄ 15kΩ
R₅ 47kΩ, R₆ 39kΩ
R₇ 100Ω, R₈ 33kΩ
R₉, R₁₁ 75kΩ
R₁₀ 220kΩ, R 15kΩ
C₁, C₂, 10nF.

For the output amplitude of V₁=10V, the total harmonic distortion is 0.2% approximately. Further reduction of the t.h.d. can be obtained by reducing the ratio R₁₀/R₁₁.

Figure 3 shows the transient response of this oscillator when the reference voltage E_R is modulated by a 60Hz square wave that changes from 10 to 6.6V. The transient response duration is not more than two periods of the output voltage.

If the ratio R₁₀/R₁₁ is decreased to 1 (decreasing the t.h.d. to less than 0.01%) the transient response duration will increase from 2 to 5 periods which is also acceptable in many cases.

The control zone is from 0.7V (or 0.3V if we use germanium diodes) to saturation voltage of operational amplifiers.

References

- D. Meyer-Ebrecht. Schnelle Amplitudenregelung harmonischer Oszillatoren. Phillips Res. Repts. Suppl. 1974 No. 6.
- E. Vannerson, K. C. Smith. A low distortion oscillator with fast amplitude stabilization. *Int. J. Electronics*, vol. 39, No. 4., pp. 465-472, 1975.
- N. Vannai, L. Pap. RC-oscillator with extremely low harmonic distortion period. *Polytech. Electr. Engrg* (Hungary), vol. 24 No. 1-2, pp. 59-65, 1980.
- J. Pahor, J. Fettich, M. Tavzes. A harmonic oscillator with low harmonic distortion and stable amplitude. *Int. J. Electronics*, vol. 37, No. 6, pp. 765-768, 1974.
- E. Vannerson, K. C. Smith. Fast amplitude stabilization of an RC-oscillator. *IEEE Journal of Solid-state circuits*, vol. SC-9 No. 4, pp. 176-179, 1974.
- A. D. Ryder. Multiphase low-distortion oscillator. *Wireless World*, vol. 87, No. 1540, pp. 59-60, 1981.
- E. M. Kashoro, I. M. Filanovsky, K. A. Stromsmoe. A high frequency RC-oscillator with amplitude stabilization. *Proc 24th Midwest Symp. on Circuits and Systems*, Albuquerque, N. M. 1981 (to be published).
- D. Gray, R. Meyer. *Analysis and Design of Analog Integrated Circuits*, J. Wiley, N. Y. 1977.

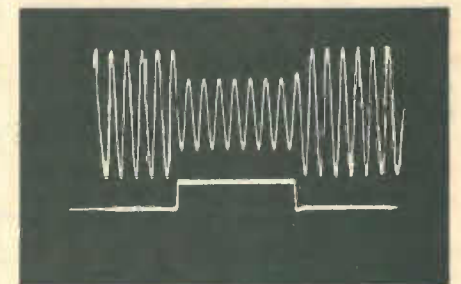


Fig. 3. Modulation of the reference voltage and the oscillator output voltage.

DIGITAL, MULTI-TRACK TAPE RECORDER

Most of the digital playback circuitry was described in the February 1982 issue – the remaining sections are covered in this part, which is published out of order with the rest of the series.

by *A. J. Ewins,
B.Tech.

The final block circuit diagram of the digital 'playback' electronics to be discussed in detail is the 12-bit, serial-in/parallel-out register and 12-bit latch, sample/hold and demultiplexer shown in Fig. 9 of Part 2 of the series.

Figure 34 shows the circuit of a 12-bit serial-in/parallel-out shift register and a 12-bit latch. The i.cs used are shown in detail and no further comments about them are necessary. The NRZ serial data, output from the four temporary storage buffers in sequence, is fed into the 12-bit shift register under the control of D/C. Once the 12 bits of a data word have entered the shift register, the 12-bit parallel outputs are latched across to the 12-bit latch upon the positive transition of the Latch pulse. The 12 bits output from the latches remain for the duration of twelve D/C pulses, and are numbered in the same sequence as they were entered in the recording process. They are passed to the 'Odd-bit' parity checkers of Fig. 35 and the digital-to-analogue converter circuit of Fig. 36.

Referring to Fig. 35, P1 and P2 are the two 'odd' parity bits created using the 'odd-bit' parity generators of Fig. 21 in the January 1981 article. The 'odd-bit' parity checkers produce outputs, PC1 and PC2, which are both logic 1 if the parity check is GO, but logic 0 if the parity check is NO-GO. PC1 and PC2 are passed to the circuit of Fig. 37 to control the transfer of analogue data to the appropriate analogue output channel.

Figure 36 is the circuit of the digital-to-analogue converter circuit using the Analogic 10-bit d-to-a converter i.c., AD561K. As shown, the circuit produces an analogue output in the range ± 5 V for the full range of ten digital inputs. The AD561K is the complement of the AD571K (a-to-d converter) used in the recording digital electronics and has similar tolerances of accuracy and temperature sensitivity: the circuit of the digital-to-analogue converter as shown in Fig. 36 is that recommended by Analogic for a buffered output. The fixed resistors of 10 ohms and 24 ohms can be replaced by trimmers of 20 ohms and 50 ohms, respectively, for greater accuracy: with the fixed values, scale and offset errors are typically $\pm 0.1\%$. If trimmers are used, then the 20 ohm trimmer should be adjusted for 0.000 output volts with the m.s.b. only ON, and all other bits OFF – the 50 ohm trimmer should be adjusted to give a reading of -5.000 volts with all bits OFF. Using the

fixed values, as shown, it is only necessary to adjust the offset zero of the op-amp to give 0.000 volts output with the m.s.b. only ON.

The analogue output from the digital-to-analogue converter is passed to all six sample/hold output stages of Fig. 38, only one of which is switched to its sample mode at any one time. This is done under the control of the demultiplexer and sample/hold circuitry of Fig. 37, such that the correct, converted, analogue data is presented to the appropriate output channel.

In Fig. 37, a divide-by-8 counter, i.c. type 4022, produces sequential outputs to enable six two-input And gates in turn. Synchronized by the (D/C)/72 pulse from the circuit of Fig. 30, the counter is reset, via a monostable circuit, as each data frame is emptied from the temporary storage buffers. As each 12-bit data word is latched for conversion from digital to analogue form, the counter is clocked by the Latch pulse, enabling the appropriate And gate. Provided the parity checks, PC1 and PC2, are GO (at the logic 1 level) the appropriate control output will go to the logic 1 level when the Latch pulse goes negative,

triggering the second monostable to produce a sample/hold pulse. The logic sequence of the control pulses produced by the circuit of Fig. 37 was shown in Fig. 10. The two monostables of Fig. 37 are contained in a dual-monostable i.c., type 4538. Both monostables may be either positive or negative edge triggered, that clocked by the (D/C)/72 pulse being positive-edge triggered and that by the Latch pulse, negative-edge triggered. The resistor and capacitor values of both monostables are selected to produce an output pulse whose duration is equal to five D/C pulses. The six control outputs from Fig. 37 are passed to the sample/hold output stages of Fig. 38.

The six sample/hold circuits of Fig. 38 are constructed from six sample/hold i.cs, type LF398, which is the same device as that used in the input stages of the recording digital electronics. A sample/hold circuit is in its sample mode when its control input (pin 3) is at the logic 1 level and in the hold mode when it is at logic 0.

The value of the hold capacitor, $0.1 \mu\text{F}$, is chosen for optimum speed of sampling and minimum droop during 'hold'. The diodes connected between the various control inputs and the 8-way pin connector are included so that the effective number of channels used may be reduced from six

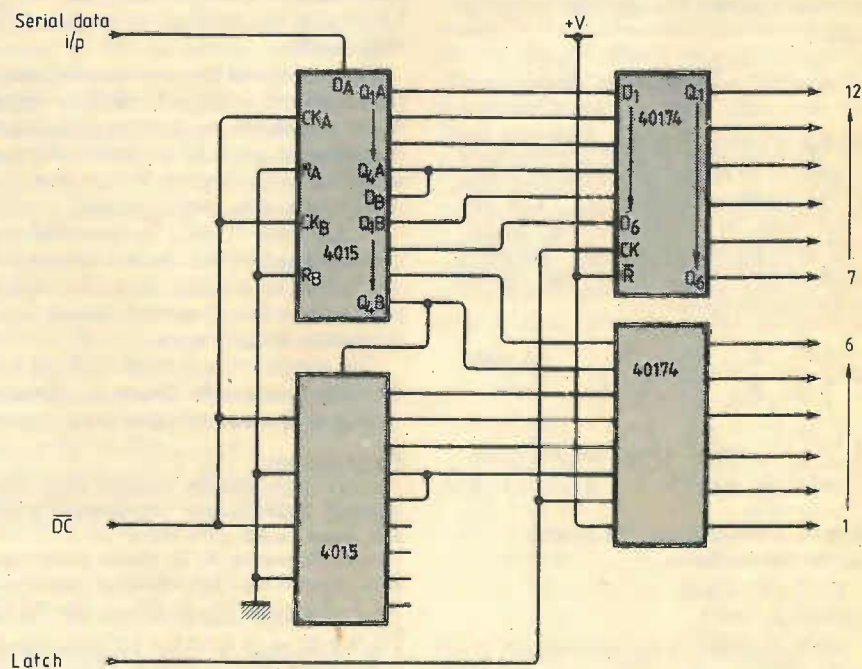


Fig. 34. 12 bit serial-in/parallel-out shift register and 12 bit latch.

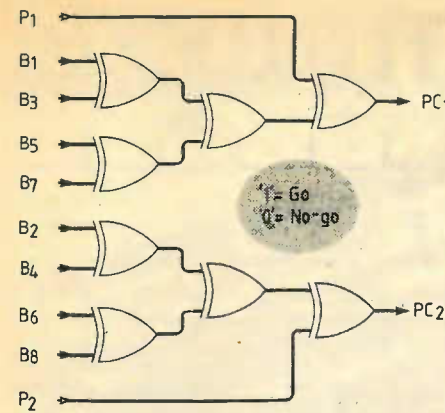


Fig. 35. 'Odd-bit' parity checkers.

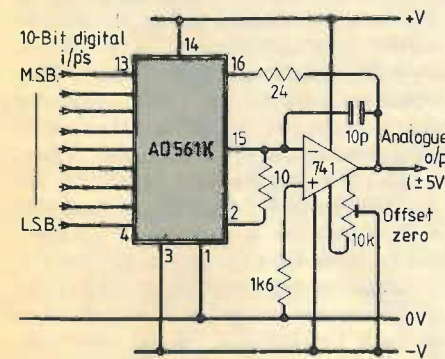


Fig. 36. Digital-to-analogue converter, gives -5V to $+5\text{V}$ swing when all inputs present.

to three, two or one. If all six channels are used, no interconnexions are made between the eight pins of the 8-way pin connector. If three channels have been selected during the recording process then the analogue inputs to the recording electronics will have been linked such that channels 1 and 4, 2 and 5 and 3 and 6 are connected together. On playback, the corresponding control lines thus need to be Ored together, producing analogue outputs from channels 1, 2 and 3. This is achieved by connecting the following pins of the 8-way pin connector together: 3 to 6, 2 to 7 and 1 to 8.

Similarly, if two channels have been selected during the recording process, then analogue inputs to the 'recording' electronics 1, 3 and 5 and 2, 4 and 6 will have been linked together. On playback, control lines 1, 3, and 5 and 2, 4 and 6 thus need to be Ored together, producing analogue outputs from channel 1 and 2, by connecting pins 2, 4 and 6 and pins 1, 3 and 7 of the 8-way pin connector together.

If only one channel has been selected during the recording process then all six analogue inputs will have been connected in parallel – all six control lines must be Ored by connecting pins 1, 2, 3, 4, 5 and 6 of the 8-way pin connector together. The analogue output will be from channel 1. All the electronics of the demultiplexer, d-to-a converter and sample/hold circuits, etc. are constructed on the final circuit board, board 7.

This concludes the detailed description of the digital recording and playback electronics associated with one track of the tape-recorder.

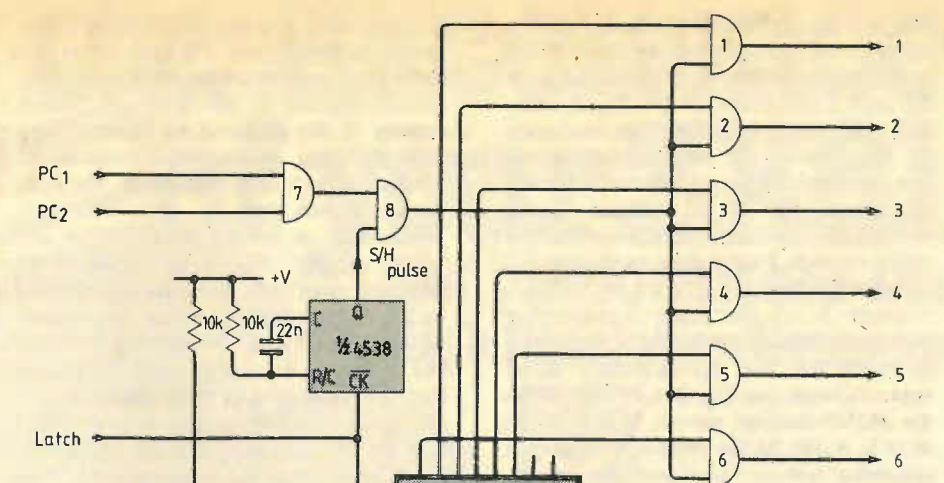


Fig. 37. Demultiplexer, using divide-by-eight counter 4022, and sample/hold control circuits.

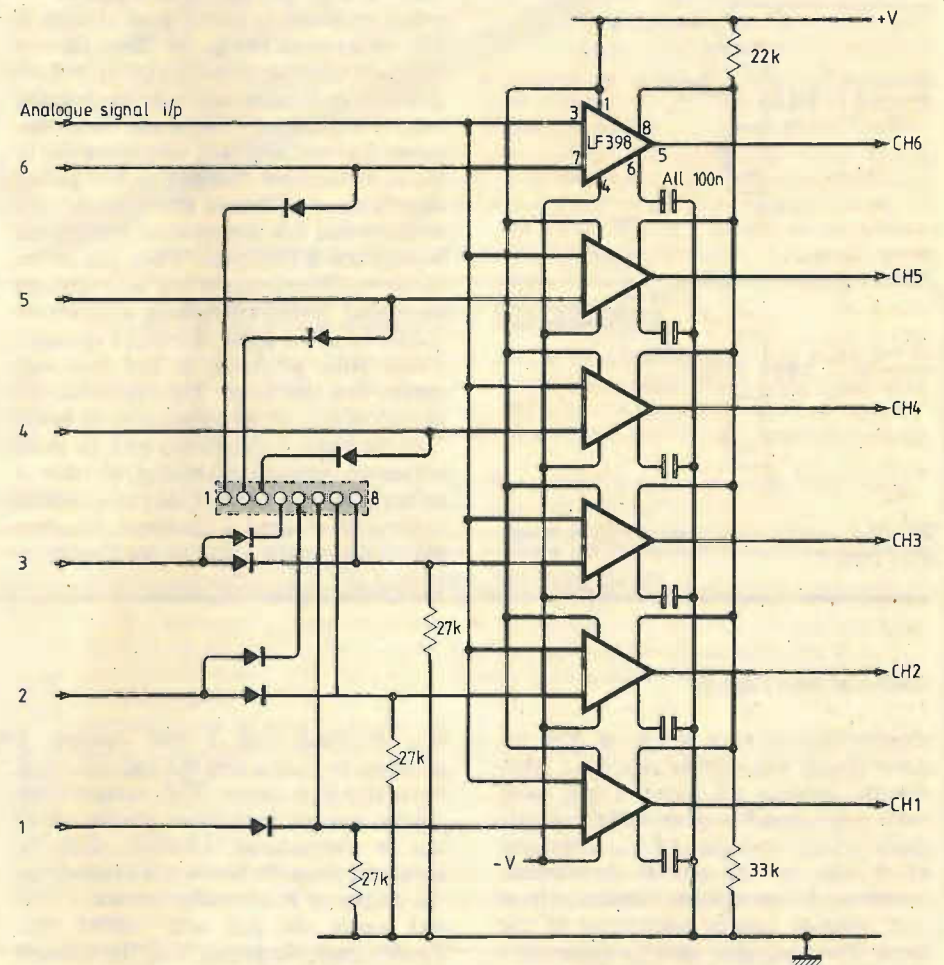


Fig. 38. Sample/hold analogue output stages, controlled by circuit of Fig. 37.

Track 2 synchronizing electronics

For simplicity of construction, in modular form, most of the digital electronics of the second track of the tape-recorder is a duplicate of the first. This leads to some redundancy of circuitry, but considerably reduces the amount of labour necessary in designing new board layouts and in the problems associated with inter-board connexions.

In the recording electronics, the input stages comprising the circuits of block cir-

cuit diagram, Fig. 4 are duplicated. Similarly it is necessary to duplicate the two temporary storage buffers and Miller encoder of the block circuit diagram of Fig. 2. However it is not necessary to duplicate the control circuitry: the same control circuitry used in the recording stages of the track 1 electronics could be used to control the flow of serial data into and out of the temporary storage buffers of the track 2 electronics. For the reasons outlined at the beginning of this section

*Research Department, London Transport

this was not in fact done, and the only components omitted from the detailed circuit of the control circuitry of Fig. 13 (a) in the track 2 electronics are the crystal oscillator and the D-type flip-flop producing the Reset pulse. For perfect synchronization of the track 2 electronics to the track 1 electronics, the crystal oscillator output and the Reset pulse from the control circuitry of track 1 are passed to the track 2 control circuitry.

Board 3 of the track 1 recording electronics contain the reference frequency generator for the tape-recorder's speed control system (see Fig. 23), in addition to the Miller encoder circuit. There is no need to duplicate the reference-frequency generator circuit, because the speed-control circuit of the tape-recorder needs only to be synchronized to the recovered tape-clock of one track.

Coming now to the playback electronics,

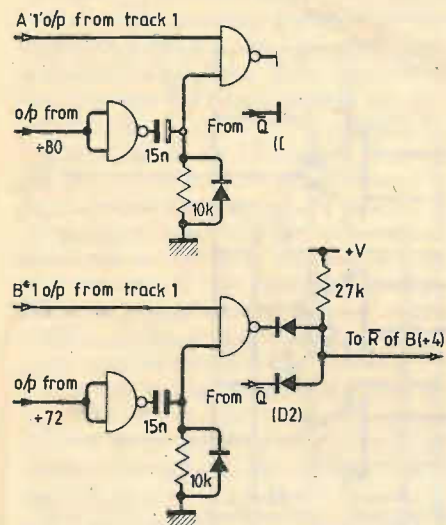


Fig. 39. Sync. circuitry to synchronize 'track 2' to 'track 1'.

Continued from page 51

automatically set after switch-on. This receiver design was chosen as a good compromise between the complex and more costly professional receivers and the simple phase-locked loop or r.f. i.c. designs which, due to the special interference problems, do not operate satisfactorily at v.l.f. without careful positioning of the aerial. Provided that care is taken with construction and alignment, this receiver will provide good performance in most conditions and at long range.

The 3dB bandwidth of the tuned circuit is about 300Hz, so if a signal generator is used it must be set to $60\text{kHz} \pm 30\text{Hz}$. Short the receiver input at the aerial terminals and adjust the potentiometer for 4V at the output of IC1. Remove the short, set the aerial trimmer capacitor to the mid point, and position the aerial coil so that the centre is about 65mm from the centre of the ferrite rod. Adjust the tuning core of the transformer for maximum output at

it is necessary to duplicate all the circuitry associated with board 4. i.e. the peak detector, Miller decoder and clock-recovery circuit. Because of the wow and flutter content of the data and the relative tape skew between tracks, it is essential to produce a recovered tape-clock for each recording track used.

Referring to the playback control circuitry of Fig. 30, it is necessary to duplicate most of it. However, the divide-by-72 counter need not be duplicated: neither need the B divide-by-4 counter, but is done so for convenience. To ensure that the replayed data from both tracks is in perfect synchronization, it is essential that the two divide-by-4 counters, A and B, of each track are synchronized. The problem of synchronising the two A divide-by-4 counters is that they are clocked by two different recovered tape-clocks, divided by eighty, and that they must be allowed to contain the wow and flutter content of each track's tape-clock.

This problem is overcome using the circuits of Fig. 39, the logic sequence of pulses produced by one of these circuits of Fig. 39 is shown in Fig. 40. (Both circuits operate on the same principle and therefore it is necessary only to describe one.) The problem of wow and flutter between the two tracks will only cause one of the A divide-by-4 counters to be clocked slightly ahead or behind the other and it is unlikely that this timing error will extend beyond one RT/C cycle. When one of the divide-by-80 counters is half way through its cycle, both A divide-by-4 counters should be in the same state and a synchronizing pulse produced at this time will ensure that this is so. The synchronizing circuits of Fig. 39 are constructed on board 5 of the track 2 electronics and all pulse sequences referred to belong to track 2 unless otherwise stated. Using an inverting buffer (1/4 of quad 2 i/p Nand, i.c. type 4011), the negative edge of the divide-by-

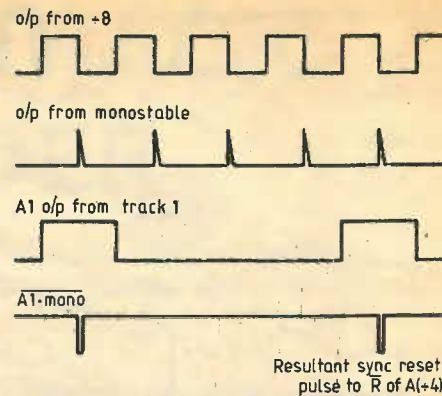


Fig. 40. Sequence of pulses in sync. circuit of Fig. 39.

80 counter's output pulse produces a short-duration positive pulse via the monostable constructed of the 15 nF capacitor, 10kΩ resistor and silicon diode. This is Nanded (negative Ored) with the Q output from DI and fed to the reset input, R, of the A divide-by-4 counter. The B divide-by-4 counter of the track 2 electronics is synchronized in an exactly similar manner using the B' output from the track 1 electronics. All the rest of the track 2 electronics is an exact duplicate of boards 6 and 7 of the track 1 electronics.

This digital, multi-track tape-recorder was designed and developed by the A. J. Ewins in the Research Laboratories of London Transport. Inquiries into its practical application and usefulness will be welcomed by the head of the research laboratories and should be addressed to: The Scientific Adviser, L.T.E. Research Laboratories, 566 High Road, Chiswick, W4 5RR.

Reference 1. Digital data recording without f.s.k. by Brian T. Evans, Wireless World, April 1979

IC4, ensuring that a true reading is achieved by tuning well through the maximum and back again. With eccentric adjusters, two or even three smaller peaks can be encountered. Carefully slide the aerial coil along the ferrite rod to maximize the output at IC4 (usually around 1.35V) and secure the coil with melted wax. Finally, peak the tuning with the trimmer capacitor and recheck the adjustment of the transformer.

When correctly tuned to 60kHz the receiver produces regular inverted pulses at the output. Resistor 9 has been included to disable the a.g.c. loop and is normally left disconnected as shown. When the clock has been assembled and the receiver aligned, feed the receiver output to pin 15 of the v.i.a. and check that a 1Hz output is produced at pin 14. If no output is present, test the receiver output, check that the supply voltage is present on all i.c.s and check that the oscillator is operating cor-

rectly. Connect the display board and check that the correct time is loaded into the registers. This may take two or three minutes after switch-on, depending on where in the code the processor starts to operate. When the correct time appears, select the date display by switching pin 10 of the v.i.a. to 0V. The remaining pins on the control port have been provided for future expansion to select and control other functions. If sporadic operation occurs check that the aerial is not in the signal-null position (axis pointing to the transmitter) and check for sources of local interference such as television receivers, lamp dimmers and noisy fluorescent tube fittings.

A kit of parts for the clock is available from Circuit Services, 6 Elmbridge Drive, Ruislip, Middx (telephone 71 76962). Copies of the object code listing are obtainable from the editorial office, in return for a stamped envelope.

Explore the Excellence of your ZX81



With MEMOTECH Add-Ons High Resolution Graphics

MEMOTECH ADD-ON £52.00 plus VAT

- Fully programmable high resolution (192x248 pixels).
- Video page is both memory and bit mapped.
- Video page can be located anywhere in the RAM.
- The number of video pages is limited only by your RAM size (each page occupies about 6.5K RAM) and pages can overlap.
- Instant inverse video.
- Switching inverse video on and off gives flashing characters/numerals etc.
- Video pages can be superimposed by software switching.
- Access to video page is similar to plot and unplot commands in BASIC.

Unique 3 month trade-in offer!

For your future needs, we'll allow you £10 against your purchase of our 64K model if:

- you return your 16K pack within 3 months of receipt;
- you supply evidence of purchase;
- your 16K model is received by us undamaged and unopened.*

*We reserve the right to reject, for discounting purposes, units which have been either opened or damaged in any way.

The pack comes in an elegant aluminium case, anodised black and styled to fit onto the back of the ZX81, allowing more add-ons (Memopak RAM, Sinclair printer, etc) to be connected without a further power supply. It contains a 2K EPROM monitor, holding a full range of graphics subroutines which can be called by the BASIC USR function or by machine code.

MEMOTECH ADD-ON £26.00 plus VAT



Memopak 16K Memory Extension

It is a fact that the ZX81 has revolutionised home computing and coupled with the new Memopak 16K it gives you a massive 16K of Directly Addressable RAM, which is neither switched nor paged. With the addition of the Memopak 16K your ZX81's enlarged memory capacity will enable it to execute longer and more sophisticated programs, and to hold an extended database. The 16K and 64K Memopaks come in attractive custom-designed and engineered cases which fit snugly on to the back of the ZX81 giving firm, wobble-free connections.

MEMOTECH ADD-ON £68.70 plus VAT



Memopak 64K Memory Extension

The 64K Memopak is a pack which extends the memory of the ZX81 by a further 56K, and together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts BASIC commands such as 10 DIM A(9000).

BREAKDOWN OF MEMORY AREAS

0-8K... Sinclair ROM 8-16K... This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines. 16-32K... This area can be used for BASIC programmes and assembly language routines. 32-64K... 32K of RAM memory for BASIC variables and large arrays. With the Memopak 64K extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

Coming Soon...



A complete range of ZX81 plug-in peripherals
Centronics Interface & Software Drivers
Digitising Tablet RS232 Interface

We regret we are as yet unable to accept orders or enquiries concerning the above products, but we'll let you know as soon as they become available.

© R. Branton & G.A.C. Boyd 1982

We want to be sure you are satisfied with your Memopak - so we offer a 14-day money back Guarantee on all our products. Memotech Limited, 3 Collins Street, Oxford OX4 1XL, England Tel: Oxford (0865) 722102 Telex: 837220 Orchid G WIRELESS WORLD JULY 1982

WW - 048 FOR FURTHER DETAILS

Please make cheques payable to MEMOTECH Ltd.		Please send me		Price	No	Total
Please Debit my Access/Barclaycard* account number		16K RAM @ £26.00 + £3.90 VAT	£29.90			
		64K RAM @ £68.69 + £10.31 VAT	£79.00			
		HRG @ £52.00 + £7.80 VAT	£59.80			
		Packaging & Postage @ £2.00 per unit				
			TOTAL ENC			
*Please delete whichever does not apply						
SIGNATURE _____		DATE _____				
NAME _____		ADDRESS _____				
		TELEPHONE _____				

THE QUAD FM4; SEVEN PRESET STATIONS; STORED AND RECALLED UNDER THE CONTROL OF A DEDICATED MICROPROCESSOR, WITH A LEVEL OF AUDIO PERFORMANCE LIMITED ONLY BY THE QUALITY OF THE INCOMING SIGNAL. DECEPTIVELY SIMPLE AND ORIGINAL, AS ONE WOULD EXPECT FROM QUAD.



Radio 2: 417m (720kHz), VHF; Radio 3 - 247m (1,215kHz), VHF; Radio 1 - 285m (1,053kHz), 275m (1,089kHz), VHF.

Radio 2

- 7 45 Terry Wogan.
- 8 0 Jimmy Young.
- 9 0 Gloria Hunniford.
- 10 0 Ed Stewart.
- 11 0 David Hamilton.
- 12 0 News.
- 13 0 John Dunn.
- 14 0 Dance Band Days.
- 15 0 New Swingle Singers.
- 16 0 Folk Entertainers.
- 17 0 Sounds of the Sun.
- 18 0 You've Got to be Joking.
- 19 0 Be My Guest.
- 20 0 Brian Matthew.
- 21 0 Truckers' Hour.
- 22 0 and the Night Music.

Radio 3

- 7 45 Weather.
- 8 0 News.
- 9 0 Your Choice. Part 1: Bach.
- 10 0 News. Midweek.
- 11 0 Your Choice. Part 2: Copland.
- 12 0 News. Midweek.
- 13 0 Your Choice. Part 1: Rossini, Greig, Kodaly.
- 14 0 News. Midweek.
- 15 0 This Week's Composer: Liszt - Symphony Northern Symphony.
- 16 0 BBC Northern Symphony Orchestra: Mozart (Prague Symphony).
- 17 0 Lutoslawski (Concerto for Orchestra).
- 18 0 Elizabeth Maconchy Concert.
- 19 0 Bournemouth Symphony Orchestra: Mahler Symphony No 8.
- 20 0 News.
- 21 0 Concert Hall. Oboe recital: Hermann.
- 22 0 and the Night Music.

Radio 4

- 6 0 News Briefing.
- 6 10 Farming Today.
- 6 30 Today.
- 8 33 Yesterday in Parliament.
- 9 0 News.
- 9 5 Midweek: Kelly.
- 10 0 News.
- 10 2 Electrostatic loudspeakers by Peter Walker.
- 11 0 News.
- 11 5 Fossil hunting for beginners.
- 11 30 You and Yours.

Radio 5

- 8 55 Concert. Part 2: Bruckner (Symphony No 3).
- 10 0 Music in Our Time: Richard Rodney Bennett, Robert Webber, Johnson Sherlaw-Jones, Vernallia (Carmina frat broadcast).
- 11 0 News.
- 11 5 Durufle.

Simply write or phone for more information to The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs. PE18 7DB. Telephone: (0480) 52561.

QUAD 
for the closest approach
to the original sound

WW - 018 FOR FURTHER DETAILS

WIRELESS WORLD JULY 1982

LETTERS

POWER TRANSISTOR FAILURE

This is in reply to your letter about transistor failures in your power amplifier, published in *Wireless World*, May 1982, page 60.

The most likely cause of the failures you describe is secondary breakdown of the power transistors, probably during the turn-off transient, during the fall time of collector current and rise time of collector voltage. An aggravating factor might be unequal sharing of collector current between the two paralleled transistors during the turn-off transient. That would cause the already-severe stress to be increased, on whichever of the paralleled transistors has the dubious privilege of carrying the larger fraction of the unequally shared load current. (Especially onerous is the case of large difference in turn-off times. In that case, the transistor which turns off later has the privilege of carrying all of the load current, instead of half of it, during the most stressful part of the cycle of operation.)

See the Motorola data sheet for the 2N6547, Fig. 13. That shows the allowed instantaneous combination of voltage and current. If the transistor operation falls outside of the lower-left boxed-in area, even momentarily, the transistor might be destroyed. Typically, the symptom is a collector-emitter short-circuit. In especially severe cases, the emitter bonding wire might be melted open, so you might have to de-lid the transistor to make contact to the emitter bonding pad. Is that the symptom you see?

Another thought: you mention rise and fall times typically being 5µs; that seems to be surprisingly slow, and such slow switching would aggravate the stress on the transistors.

Nathan O. Sokal
Design Automation, Inc.
Lexington
Massachusetts

NETWORKING SMALL COMPUTERS

I have recently read an article, very similar to that by P. G. Barker in the May issue, in the *Commodore PET User Group Newsletter* (CPUCN). It seems that, put simply, a couple of programs are presented which convert text files into internal format files. Programs of this type have been widely published for some time and are also known as merge programs for which they are usually used. The best known is the 'Templeton' merge - a one line set of immediate-mode instructions for pre-opened cassette files. It does not suffer from the major disadvantage of Dr Barker's program. I have written a short (121 bytes) merge program for either cassette or memory-based text data, from which cassette files must have originated, but found that the Templeton merge made it redundant. Unfortunately, a number of practical communication problems were not touched on in the article.

Stephen H. Binns, Ph.D., G8EWX
Sproatley,
Hull

The author replies:

I think Dr Binns has missed the point of my article which was to show (a) the feasibility of transferring programs via the public switched network, (b) the conversion problems likely to

be encountered in target machines, and (c) the relative speeds of tape and disc loading. The existence of his loader, the 'Templeton' merge or any other loading technique is totally irrelevant unless they can be shown to be substantially faster than the code which I presented. Code compactness is not necessarily a question at issue in this particular case since the 3000 series PET has a 12K memory expansion area that could be used to accommodate programs such as mine which may be a little larger than 121 bytes. As your correspondent will appreciate there is likely to be a multitude of approaches to the conversion problem. I do not claim that there is any novelty involved in the logic underlying the algorithms I have employed - but again, this was not the point of the article, which was: program transfer via the PSN.

The similar article to which Dr Binns referred is one which I wrote called 'Computer Networks and Program Distribution'. It is an 'unofficial' newsletter of the PET users' group which has now ceased circulation. The article that was published in *WW* was a re-written abstracted version of the item that appeared in CPUCN.

MICROCHIPS AND MEGADEATHS

It was interesting to read Steve Coleman's letter in April's *Wireless World*, asserting that other correspondents were "wrong to imagine that refusal to fight in wars will avert their occurrence".

The two world wars of the century were the first (and may be the last) in which it could be reasonably asserted that "we are all fighters now" soldiers, sailors, airmen (airpersons?), farmworkers, factory workers, transport workers, miners, journalists, doctors, nurses - clergymen! - even some politicians!

To refuse to fight means to refuse to design, make, provide, transport, service, organize and use materials of war. More than that, it means to reject violence itself as acceptable human behaviour (some training in semantics is necessary in order to wrinkle out every form of violence - possibly only two or three human beings have managed it to date, but millions have come so near that we know what it is like).

To refuse to fight in this sense (what other sense is there?) is the highest form of political action. When people really care enough about each other - and all creation - problems dissolve, appropriate action is taken in every situation (remember semantics!) and the kingdom of heaven is revealed - as it always has been and always will be, in patches, in every place, in every day. *Experto crede!*

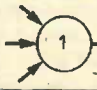

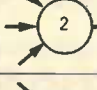
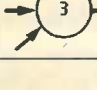
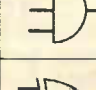
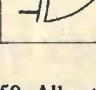
Ronald Gill
Allestree
Derby

INTENTIONAL LOGIC SYMBOLS

The protracted and confused correspondence started by Tony Cassera's article (*WW* November 1980) goes to prove the inadequacies of the new system of logic circuit symbols which has so undeservedly supplanted the old.

Mr. J. E. Kennaugh (Letters October 1981) has even gone part of the way towards reinventing the old system of logic gate symbols. I first met that system (Fig. 1) on joining an Admiralty


Fig 1

	Old	New
OR gate		
Quorum gate		(Lacking)
AND gate		
Exclusive OR gate	(Lacking)	

equipment design team in 1959. All gates were represented by circles, and bistables and counters by rectangles, whereas the D symbol now used for And gates then indicated a delay circuit, a monostable being drawn as a delay with a feedback loop. Connections could be drawn to the gates from any direction and the inputs were distinguished by arrow-heads.

These older symbols had to have the greater flexibility to meet the versatility of the usually customized circuitry, most of which was derived from a famous light blue booklet on r.t.l. widely esteemed until several well-advanced design teams began to run into the same fundamental large-system snags simultaneously.

An inhibit could be introduced by adding a single resistor to the base of the second transistor in any of these gates, and this was indicated by a stroke through the symbol as in Fig. 2 which illustrated how an exclusive-Or gate might have been achieved in the old logic if anyone had ever called for such a circuit in those days - the earliest Ex-Or gate I ever saw was on page 88 of *Electronic Design* No. 26, dated November 22, 1966.

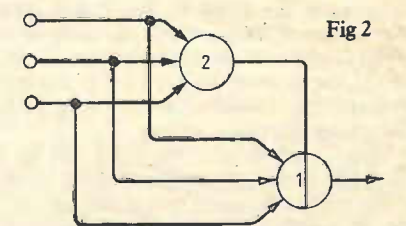

Why the Quorum gate has lapsed from favour has long puzzled me, especially those types in which the inputs could be weighted to give all sorts of weird truth tables; however, a lecturer in the American Institute has assured me that they are still used in some places where they are known as voting circuits.

There was but one polarity of (cheap) transistor available in those happy days so that nobody ever had cause to mix-up all the And and Or gates by turning the logic polarity upside-down.
John C. Rudge
Harlington
Middlesex

In the debate about Nand and Nor gates, and their relationship to other gates, J E Kennaugh (Letters, May 82) seems to imply that Nand and Nor gates only predominate in 'practical logic'.

In what might be termed 'theoretical logic', Pierce's 'dagger' (\downarrow) and Sheffer's 'stroke' (\uparrow) have both been put forward as candidates for the basic logical connective, from which all other connectives can be derived. (The dagger is equivalent to Nand, and the stroke is equivalent to Nor.) Bertrand Russell in the second edition of 'Principia Mathematica' actually suggested the exclusive use of the Sheffer stroke (i.e. Nor) in mathematical logic.

It is worth remembering that (A Nand A) is equivalent to (A Nor A) is equivalent to (Not A), so in theory we do not even need the negator.

G. J. Boris Allan
Stockport
Cheshire

ARMS AND THE MAN

I am writing to support your editorial 'Arms and the Man' in the May issue. The electronics industry employs about 60-70% of its engineers in the 'defence' of the developed world, whose only task is to provide large profits for the companies concerned and to make weapons of mass murder, while a large part of the developing world is struggling to find enough food to eat.

There are alternatives to working to kill people, as shown by the example of the efforts of the Lucas Aerospace Combine Shop Stewards Committee. Instead of providing the means for our own destruction, the electronics industry has the ability to provide safe and efficient tools for a caring society. If the only alternative to military work is unemployment, do as others are doing - start a cottage industry.

William Sigmund
Omega Systems
Trebullert,
Launceston,
Cornwall

CAR IGNITION SYSTEMS

Referring to the article by Rod Cooper in the March issue of *Wireless World*, in which he described a capacitive discharge ignition system, I should like to draw the attention of readers to the problems encountered on many modern cars when using this type of system.

Vehicle manufacturers designing cars for the European market are under increasing pressure to improve fuel economy and, unlike the American and Japanese markets, they are not faced in Europe with particularly stringent exhaust emission regulations. Sophisticated air-to-fuel ratio control systems have, therefore, to be justified solely on improved fuel economy and not on the grounds of complying with emissions legislation and so it is that the low cost of the carburettor remains a compelling attraction.

Considering its relative simplicity the carburettor does a remarkably good job of controlling the air: fuel ratio, but compromises have to be made and with increasing pressure for improved economy the designers walk the tight rope of the borderline between maximum economy and flat spots. More and more the compromise is being chosen in favour of economy at the expense of flat spots and excessively lean ratios are tolerated under certain operating conditions where the effect, it is hoped, will not be too noticeable.

It is under these conditions, however, that spark energy and spark duration are critical,

and substituting a capacitive discharge system for an inductive system runs the gauntlet of partial misfire, particularly on light throttle and under transient conditions or during warm up. This is not merely a theoretical consideration but a practical fact of life experienced unfortunately by all too many owners of capacitive discharge systems.

There are undoubtedly advantages in a capacitive discharge system but nowadays these can best be realised by using a "reactive" combination of inductive and capacitive systems to give you the best of both worlds.

A. P. M. Bull
Director
Eda-Sparkrite Ltd.

The author replies:

The observant owner of a car of recent manufacture cannot have failed to notice a relatively new addition to the carburettor - tamper-proof seals fitted to the fuel/air mixture controls.

These seals are fitted at the factory as a direct result of the Dept. of Environment's Vehicle Emission Regulations (available at H.M.S.O. at £2.50). To comply with the regulations it is necessary to use an exhaust gas analyser as the old methods of trial and error are no longer good enough.

This does not leave the engine designer much latitude for running the engine on weakened fuel/air mixtures and he no longer has the free hand that Mr Bull suggests he has in designing for economy of fuel at the expense of pollution, although as pointed out, our regulations are not as strict as America's or Japan's are . . . yet.

Now, the circuit described in my article has been tried on several cars of recent origin which are fitted with the tamper-proof carburettor and they have all worked perfectly well.

I suggest that the misfiring experienced with some types of electronic ignition is to be found on cars of the pre-tamper-proof era whose owners have "tweaked" the carburettor to give an excessively lean fuel/air mixture in the misguided belief that this is the best way to fuel economy. Also, the interference effects described in the article play a large part in such misfiring even on correctly-set fuel/air mixtures; and there is always the problem of matching the electronics to the ignition coil, which can give similar effects if there is a mismatch.

When correctly designed and used, there is nothing wrong in principle or practice with the capacitor-discharge ignition system, and it is particularly suitable for the relatively low-performance 4-cylinder family saloon which my design was intended for, because it is inexpensive, and this cannot be said for some commercial systems.

THE RIGHT FORMULA

I have been reading with considerable fascination the various controversies about basic theory in your letters pages. 'Death of Electric Current', 'Einstein was Wrong' and 'Electromagnetic Units', to name but three.

No one seems to acknowledge the fact that all such 'theories' are purely human artifacts, designed to make predictions of the way things work! Such equations, when it comes down to it, have to obey one rule - do they give sensible answers, given the measuring techniques open to the one wishing to design a piece of apparatus.

We use ohms, volts, amps and unit of charge, not because such units would mean anything to a scientist from, say, Betelgeuse, but so that we can tell what will happen if changes are made. But any working (hands-on) engineer will tell you that even the simplest of devices can display some very odd behaviour! The trick is to use the 'right' formula! Ask any engineer if he can name a single text-book which will invariably give the correct answers to whatever he needs to know! I can't, and I doubt if any can - no matter how 'simple' his needs!

Does Mr Catt find his theories enable him to do better design work? I very much doubt it! In my experience of designers, all have 'private' data notebooks without which their jobs would collapse. So whilst arguments about units are interesting, no final formulae can or ever will exist. So far as Einstein is concerned the whole thing hinges upon whether any object with mass can move at a relative speed (to that of the universe) greater than the velocity of photons. The answer is less clearcut than physicists would have us believe. Indeed, at this very moment I am informed that certain objects have been observed by astronomers that may be moving faster than lightwaves. Information is scanty and I have no references I can quote.

Incidentally, if atomic particles moving near the speed C do get heavier, how come wires don't weigh heavier when current flows? (Yes - I know the 'peas in a drainpipe' analogy, but a moment's thought will disclose that whilst the electrons may not move very far, they have to have peak speeds approaching C when they 'bounce', for the impulse cannot move faster than the peak speed of the 'peas' - ask Steve Davis!)

Ronald G. Young
Peacehaven
East Sussex

CITIZENS' BAND

I wish to support the views of S. Frost in the March issue about the "arrogance and lethargy of civil servants who have neglected their duty to serve the people who pay them". This criticism may be applied equally to 'our obedient servants' in both national and local governments.

Part of the problem lies in the historical conditioning which says that 'we' are only permitted to do what is not forbidden by 'them'. Fortunately for the future of freedom, young people are less inclined to accept this limitation - at least until they have themselves become part of the establishment.

The fact is, of course, that we are free to do what we like unless forbidden by law; but, if we have retained our flexible intelligence and not been deeply distressed by oppressive social conditioning, we will not regard the law as our criterion of reasonable behaviour. The law is after all, the lowest common denominator of acceptable behaviour, not the highest.

Peter Hartley, in his penetrating article "Educating Engineers" in December *WW* has neatly sewn up all the loose ends of your never-ending correspondence about responsibility, currently running under the heading "Microchips and Megadeaths". But surely his article should be called "Educating Human Beings". In the sense in which he uses the word, we are all professionals now.

R. Gill
Allestree
Derby

In my letter about CB in the March issue certain words were transposed; and this makes it very difficult to understand the sentence in question.

The second sentence of paragraph 6 should read as follows: "If the people have a legitimate demand of government, and government fails to do its duty to meet that demand, the people will take the law into their own hands . . ."

S. Frost,
Edinburgh.

As the secretary of a local c.b. club, I would like to offer my personal views on the letter from Mr Frost in *Wireless World*, March 1982.

His most disagreeable point is where he quoted someone as saying that c.b. was (presumably before legalization) a symbol of 'young revolt'. The long-term c.b. pirates known to myself were operating their equipment for nothing more than the enjoyment of talking to like-minded enthusiasts and forming new friends with common interests. Politics has never entered into it.

Another aspect of this view is that c.b. users are much of a sameness and young whereas in practice a good proportion of breakers were and are such as lorry drivers, company reps and radio amateurs (RSGB take note), with a few policemen and similar adults in responsible positions thrown in for good measure. There were and are also a good many youngsters about for whom c.b. is really only a toy, a passing novelty, but again there is no political motive.

Mr Frost's political comment about people reacting against improper democracy is probably quite true, witness Poland, but hardly relevant and out of place in a journal of this standing.

It was not realistic to blame officials for not granting c.b. when it was first asked for and then going on to imply that legal f.m. was a political move without any technical merit. We are to suppose then that the existing users of 27MHz allocations should have instantly re-equipped and moved to other frequencies and that this would not have counted as a problem. The Home Office are to be blamed for hoping that c.b. would disappear if it was ignored, probably egged on by RSGB stalwarts. They are still to be blamed for not taking a positive lead and maybe a little enthusiasm to the problems of legal c.b., like channel usage (9, 14 and 19 in particular) and official guidelines to the use and operating procedure of c.b. It is probably asking too much for the H.O. to liaise with and recognise the usefulness of c.b. clubs like ours.

As far as the legal system is concerned, breakers in my area (which is next to 'The Republic of Barnsley') have taken to it very well and are pleasantly surprised by the technical quality with very little activity remaining on the old a.m. channels. Incidentally, this area is far enough away from hospital paging systems, etc., for it to ever have been troublesome in this way on a.m.

For those who think that c.b. is fading fast, I would like to point out that at the time of writing (February), membership of my club is increasing at about four new members at each 'eyeball'. That's about 120 so far in a small township.

In conclusion, I would like to say that I see Mr Frost's letter as trying to entice c.b. enthusiasts to follow his political views rather than make any serious point.

J. Briggs,
Secretary GCBC,
Penistone.

I was initially surprised that so much space was allocated in the *Wireless World*, (Letters, March, 1982), to the petulant, semi-political diatribe about c.b. by S. Frost of Edinburgh. Whatever the merits or otherwise of c.b. itself and of the arguments concerning channel allocations, modulation methods, etc., this kind of emotive rubbish clearly has no place in a supposedly technical journal. However, I then read the leader article in the same issue. In the penultimate paragraph the remark ". . . when the present government is but a bad memory" . . . gave the game away! When an editor allows his political prejudice to intrude into his production of a technical magazine, then I suppose we must expect an increasing contamination of its contents by half-baked political propaganda.

What a pity that *Wireless World* does not stick to its proper function, i.e., technical information; we can all get enough of the other thing from any of the vast range of politically biased media.

M. G. T. Hewlett,
Midhurst,
W. Sussex.

WHAT HAPPENED TO THE PANADAPTER?

I have taken your magazine for about 37 years, during which time I have been a Merchant Navy Radio officer, and more recently proprietor of a small electronics shop.

Over the years I have seen a wealth of design circuitry in *Wireless World*, relating to Audio amplifiers, Audio pre amplifiers, power supplies, microprocessors, etc. etc.

However I would respectfully submit that designs for test equipment seem to be somewhat thin on the ground. Also designs for HF communications receiving equipment.

As an ex radio amateur (GM3GYB) I lament the fact that the vast majority of modern amateurs no longer build equipment; perhaps the shortage of modern design material is one reason?

As you will know, spectrum analysers even second hand, cost thousands of pounds. You will also remember the end of WW2 saw the release of some American surplus 'panadapters' for connecting to the mixer stages of receivers, to display a segment of the RF band on a CRT. These I believe had inputs of 455kHz, and 30MHz is another model.

You will appreciate that there is some marked similarity between panadapters, and spectrum analysers.

Having designed and built two valve panadapters about 18 years ago, for my own use, I can vouch for their usefulness in searching a specific band for instant visual location of signals.

In view of the cost of second hand spectrum analysers, and the lack of commercial panadapters (Heathkit made one years ago) I wonder if it would not be an interesting and challenging project for one of your design contributors to come up with a modern solid state unit using varicaps etc, that could double as both a simple low cost spectrum analyser for test purposes, and also a practical Panadapter suitable for at least several I.F. inputs as used on modern HF amateur communications receivers - such as the Yaesu FRG7 FRG7700 and Trio R1000 etc.

Such a low cost design would appeal to both

test engineers and communications people, as at present, the cost of such equipment is placing it completely outside anywhere but the laboratories of large companies, and government establishments, etc.

Martin S. Lebbon,
Harrogate,
Yorkshire

DATA RECORDING ON AUDIO CASSETTE

I read with interest the article entitled "Data Recording on Audio Cassette" by P. Smith and P. I. Zorkoczy in your February issue. However, two points puzzle me. Firstly, the coder circuit as drawn is unlikely to work reliably, since the output of IC₁ has an undefined phase relationship with the data input to the coder. As a consequence, the coder output is likely to adopt an asymmetrical mark-space ratio, dependent on the switch-on state of the counter IC₁. To remedy this problem, the data should be re-synchronized to the counter output by means of a clocked flip-flop.

Secondly, the authors state that the voltage induced in the playback head is proportional to the rate of change of the recorded waveform, and yet that the associated 90° phase shift would not normally be expected with such a frequency response. Unless prolonged exposure to microprocessors has affected my understanding of circuit theory, that is precisely the phase shift one does expect to see, the head acting as an ideal differentiator in the mid-band. This phase lead should be accurately compensated by the 90° lag in the equalization circuit, to yield an overall flat response in frequency and phase.

While I am no expert on transducers, I suspect that the region in which the head phase response differs from the amplitude correction circuitry is at those frequencies where the head response ceases to match the 6dB/octave rise due to losses.

P. G. Hinch
Stockport
Cheshire

The author replies:

Let me first assure Mr Hinch that the coder circuit as described does work reliably and does not suffer from the asymmetry of "mark-space ratio" you describe. The coded output at Q of IC_{2(b)} is symmetrical because the clock input to IC_{2(b)} from Q₃ of IC₁ is a symmetrical waveform. By adding a flip-flop as you suggest we would be doing the same job twice.

The 6 dB/octave rise in playback voltage with frequency at frequencies below which losses take effect is characteristic of the ubiquitous first order highpass filter. The phase response is however not that which is associated with such a filter. Over this frequency range the amplitude equalization filter is in essence a first-order, low-pass filter, giving a fall of 6 dB/octave to provide an overall flat amplitude response. The phase response of any such low-pass filter depends upon frequency:

Phase = - arctan f/f_0 where f Hz is frequency, and f_0 Hz is corner frequency of filter. The phase response of this filter is therefore not the constant -90° that you assume. The amplitude equalization filter does give an overall flat amplitude response but not phase linearity.

SYMMETRICAL OUTPUT DIVIDERS

The symmetrical output dividers described by Gerard Girolami and Philippe Bamberger are based on a very ingenious principle — inverting the clock input for half the count. It is a pity that they then use such awkward techniques to design their dividers.

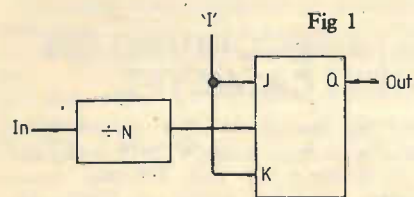


Figure 1, as shown above, is a $\div 2n$ circuit with symmetrical output — this is trivial. By using the output to invert the clock input, a $(2n-1)$ circuit is produced. Using this principle, Fig. 2 shows a programmable divider which can be extended 4 bits at a time by simply cascading 74168 counters in a standard configuration. Using decade counters produces the b.c.d. version of Fig. 3. An extra data selector is required to make the least significant 4 bit counter divide by 5 rather than 10, so that the correct weightings are achieved for the inputs.

These two circuits give a much more easily extended and general solution than the ones described in the article. They require lower device counts and only need one device rather than two — for each 4 bits added since they eliminate the need for binary comparisons. In addition, the binary version gives one extra bit of binary input. Note that for a divide ratio of n , the binary (or b.c.d.) inputs must be set to $n-1$. For most applications this does not matter, as the input circuitry can be adjusted accordingly, e.g. by simple relabelling a switch or, in the cause of microprocessor control, by software. If absolutely necessary, 7485 adders can be used to add "all ones" to the inputs, which is equivalent to subtracting 1 in two's complement arithmetic.

Philip Nye
Edinburgh

LAWS OF MOTION

In his letter of November 1980 Mr Walton wondered how far back the principle of inertia goes, and he suggested that Galileo might have thought of it before Newton. In fact, since the fossil record shows that modern man is at least 100,000 years old, the laws of motion must have been thought of thousands of years ago, but the geniuses of those days had no writing with which to express themselves.



As far as modern times are concerned (and we can say that modern times began about 10,000 years ago), there are a couple of references on the subject which may be of interest.

Galileo died in 1642 and Newton's laws of motion were published in 1687, but here is what Thomas Hobbes said in 1651:

"That when a thing lies still, unless somewhat else stir it, it will lie still for ever, is a truth that no man doubts of; but that when a thing is in motion it will eternally be in motion, unless somewhat else stay it . . ."

And here are the thoughts of the Roman poet Lucretius in about 50 B.C.:

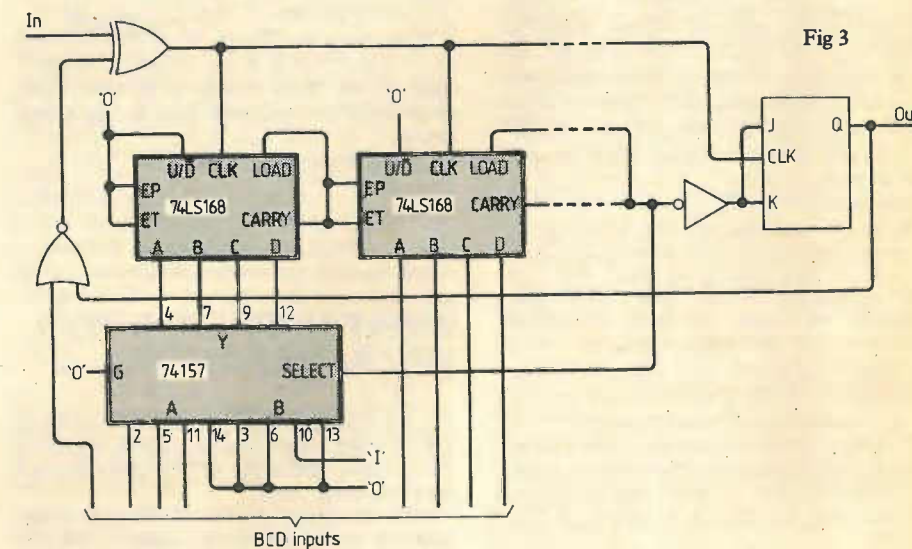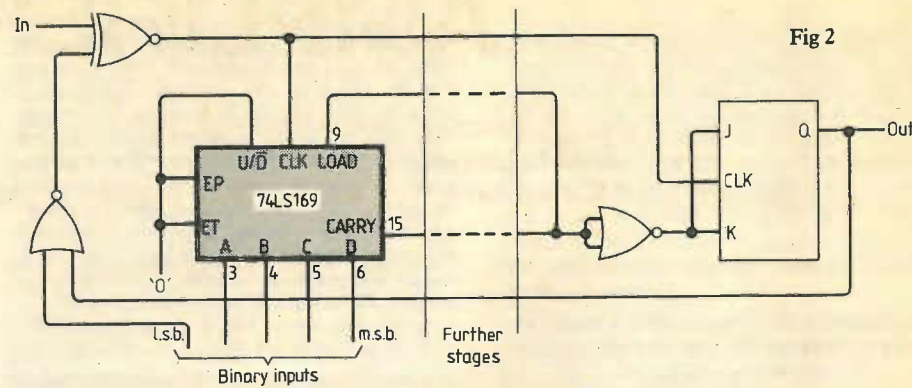" . . . the light and heat of the sun . . . are



composed of minute atoms which, when they are shoved off, lose no time in shooting right across the interspace of air in the direction imparted by the shove . . .

A very slight initial impetus far away to the rear sufficed to launch them, and they continue on their course at a velocity proportional to their lightness."

All the three laws seem to be in Lucretius, even if not very well expressed. There is no doubt however that he knew that a continuous force is not necessary. He was aware, in other words, that a body continues in its state of rest or uniform motion in a straight line unless impressed forced act on it.

Did Newton ever read Lucretius?

S. Frost
Edinburgh

References

1. Leviathan; chapter 2. (Fontana p.63.)
2. On the Nature of the Universe; Book 4 (Penguin pp 135, 136).

DISC DRIVES


Following the article by J. R. Watkinson in the March issue, I wish to comment on the conceptual aspect which makes discs necessary, viz. that we must have a machine and store programs in it, either in the spatial sense (enormous memories) or in the temporal sense (disc drives but enormous programs).

Due to the difficulties we have experienced with the development of programs for the solution of engineering problems we were bold enough to make the suggestion that the flow-chart must be the beginning and the end of

software, e.g. will be a package to be calibrated according to the conditions set by the problem. This amounts, of course, to assembling the program before the computer. We hear sometimes from leaders in engineering that programming is a medieval remnant in our technology, but no alternative was forthcoming. I think this alternative is implicitly suggested in the WW editorial of January 1982 and it was as always so close and so remote to us; nature is doing programming, therefore the alternative is but *experiment*.

By the way we have speculated lately that if the concept of e-m queues is correct (my letter in the January 1982 issue of WW) then the initial troubles experienced in running complex programs are due to the inertia of particles or waves in forming queues, therefore this famed software problem is really a hardware phenomenon.

G. Xenoulis
Edmonton
Alberta, Canada

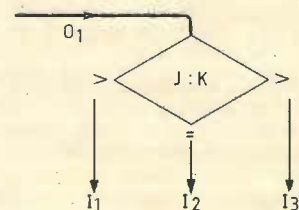

80-100W MOSFET AUDIO AMPLIFIER

One solution to the problem of low mosfet g_m — using the mosfet with bipolar small-signal devices — was described in the first part of this article. Here, John Linsley Hood presents an alternative, which is to improve the gain of the voltage-amplifier stage.

by J. L. Linsley Hood

A considerable amount of development work has been done over the past decade in the design of high gain class A amplifier stages, mainly in the evolution of integrated circuit operational amplifiers, in which the design requirements in this application are high gain, good immunity from supply line breakthrough, and wide bandwidth. In addition, some attention has been paid to cost-effectiveness which, in discrete component terms, means the use of active elements to provide the best performance for the lowest number of components.

Although this work has been done, largely, by the designers of i.c. op-amps, it is profitable for those working on discrete-component circuitry to look over their shoulders to see what they are up to.

The Class 'A' amplifier stage

It is a fundamental requirement of any feedback amplifier design that it should be absolutely and unconditionally stable, and this requirement applies with as much force to audio amplifiers of this type as to closed-loop servo-mechanisms. This consideration, coupled with the need for audio-amplifier designs to operate satisfactorily with a wide range of load reactances, leads to designs in which there is a substantial gain or phase margin at the unity-gain point on the Bode plot.

This requirement is easy to satisfy in a single-stage amplifier, of the type shown in Fig. 6, where it is unlikely that the internal phase shift, without feedback, will exceed 90° until frequencies are reached at which the gain is very much less than unity. However, the stage gain from such an amplifier will only lie in the range 50-250, with a conventional resistive collector load. It is true that gains of several thousand can be obtained from such a stage if the

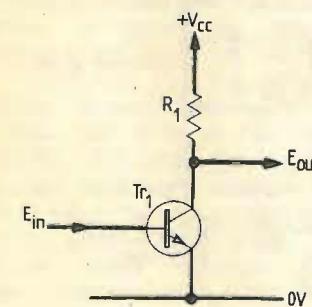


Fig. 6. Basic single-stage amplifier. At reasonable collector currents, stage gain is modest, but phase shift is less than 90° at frequencies below f_1 .

collector load resistor is replaced by a constant-current source, as in the 'Linac' configuration² and this figure can be increased towards the hundred thousand mark if the amplifier transistor is operated in cascode with a device such as a junction fet, to increase its output resistance. Unfortunately, such high gains are only obtainable at very low collector currents, which imply very high output impedances and a relatively poor h.f. performance, which would not allow an adequate loop gain at the upper end of the audio band.

The use of a two-stage voltage amplifier gives a much greater degree of design freedom, and while such an amplifier may not automatically guarantee, under all load conditions, that the internal phase shift does not approach 180° until the open-loop gain is negligible, the necessary conditions for an adequate phase margin, at unity gain, are much easier to contrive in this type of design than in circuits with more amplifying stages. For this reason, the possibilities of two-stage voltage amplifiers have attracted the attention of many designers working in the audio and operational-amplifier fields, where large amounts of negative feedback are deliberately employed to improve bandwidth, transient response, and linearity.

Because of the relatively low input impedance of Tr_2 , a simple two-stage amplifier of the type shown in Fig. 7(a) will not give a gain which is that of a single stage, squared, but nevertheless a stage gain in the range 2000-3000 can be obtained, and this can be increased by a further factor of ten if a constant-current source is used as the load for Tr_2 instead of the load resistor R_2 . Moreover, this order of stage gain can be achieved with collector currents in Tr_2 which are high enough to allow a relatively low output impedance at Tr_2 collector. In practice, the input transistor will most commonly be replaced by a long-tailed pair, as in Fig. 7(b), which reduces the odd harmonic distortion introduced by the input stage, as shown by Taylor^{3,4}. This arrangement also facilitates the design of direct-coupled amplifier systems, in which the long-tailed pair input cancels the voltage offset otherwise introduced by Tr_1 .

Circuit configurations of this type, using one or other of the arrangements of Fig. 7, with the constant-current source sometimes replaced by a bootstrapped load

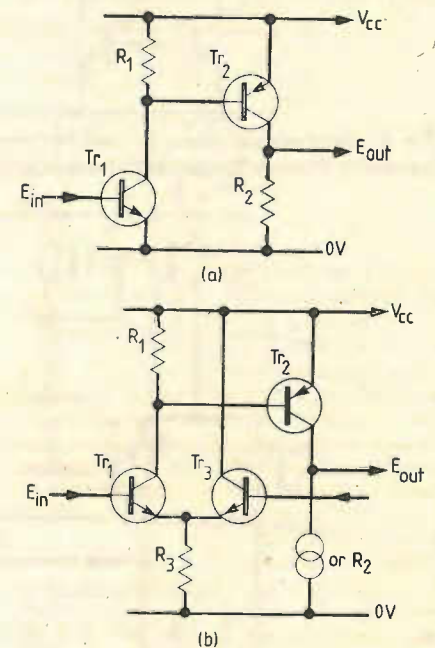


Fig. 7. Much higher gain is obtained from two-stage circuit at relatively high Tr_2 collector currents. Long-tailed pair input at (b) reduces odd harmonics.

resistor, formed the bulk of class A gain stages used in commercial audio amplifiers up to a few years ago. In these designs, the output-impedance transformation was accomplished by a complementary, or quasi-complementary, compound emitter-follower pair, using bipolar junction transistors, and overall negative feedback would be taken from the output to the inverting input connexion. With careful design, circuits of this type give overall harmonic distortion figures of 0.01-0.02%, as measured at 1kHz, and at a few dB below clipping point. Although the t.h.d. figures will worsen somewhat at lower power output levels, the signal-to-noise ratio of such an amplifier is only some 80-90dB, which means that the residual distortion is soon swamped by circuit noise.

The approach has changed somewhat in the last few years with the marketing of amplifiers, mainly of Japanese origin, having distortion levels in the 0.002-0.008% bracket, apparently in an attempt to obtain more impressive consumer reviews. In these designs, changes have been made in both the output stage biasing arrangements to minimize crossover discontinuities, and also in the number and complexity of the preceding gain stages. Where the improvement in

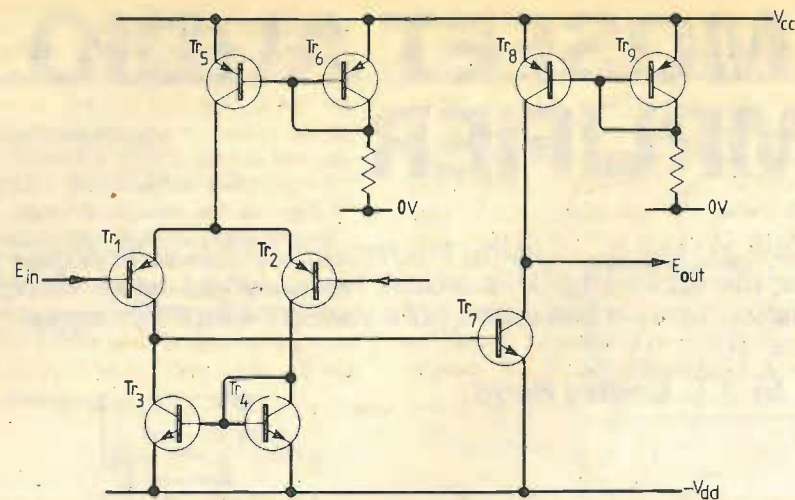


Fig. 8. Use of current mirror as load for Tr_1 offsets lower gain of long-tailed pair over single transistor. Process is repeated at output stage.

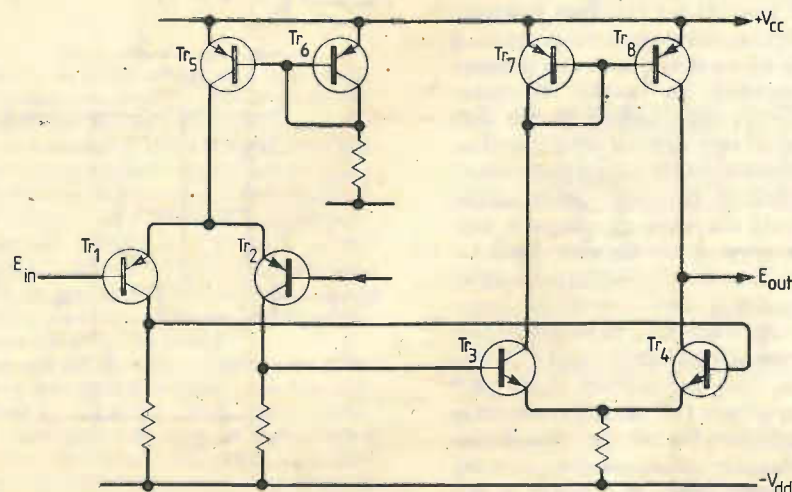


Fig. 9. Symmetrical, push-pull version of Fig. 7(a) circuit, with current-mirror load for Tr_4 .


linearity has been made at the expense of stability margin, or has led to a less ideal response to a step function input, the final result may be less good in the ear of the listener. Nevertheless, there is one trend amongst those currently being explored which is of interest, particularly since it follows techniques developed earlier for operational-amplifier integrated circuits,

and I propose to consider this in greater detail.

Higher-gain configurations

One of the penalties in the use of a symmetrical-input long-tailed pair is that

Fig. 10. Two commercial circuits using form of Fig. 9.

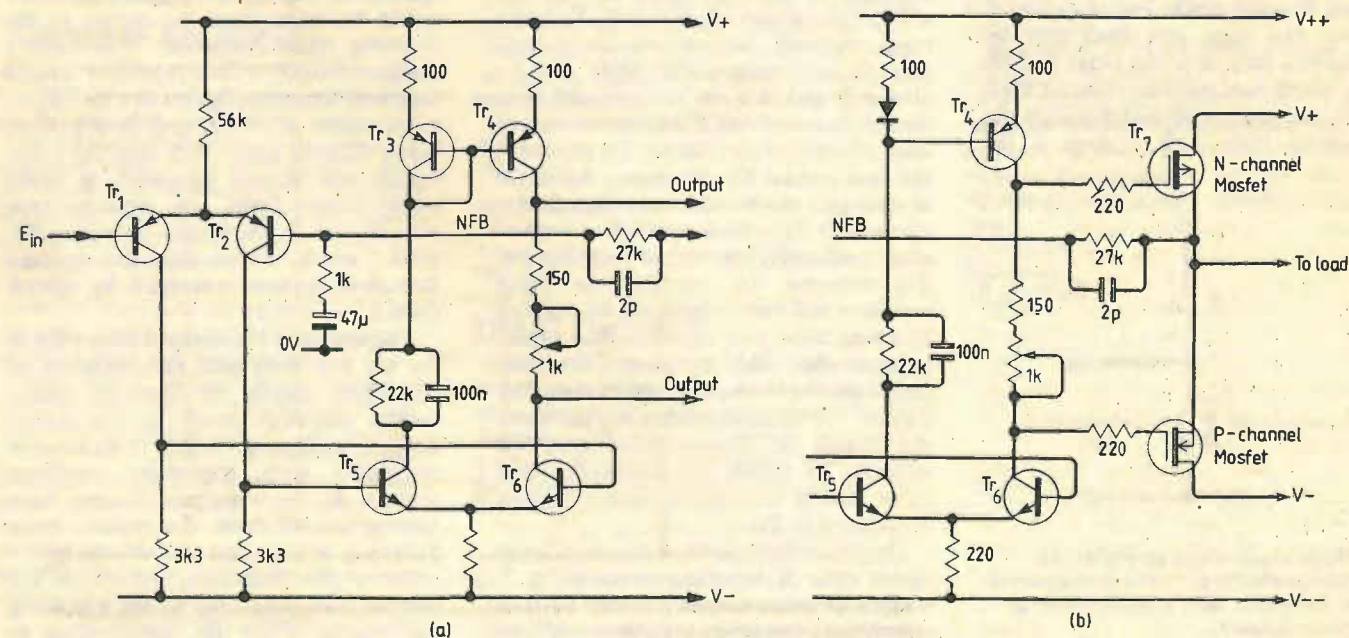

the g_m of the input device is halved, with a consequent reduction in the gain in comparison with a similar amplifier having only a single input resistor. This loss of gain can be minimized by the use of an asymmetrical input stage, with the feedback transistor operated at a higher current than the gain transistor, as in the earlier design of my own⁵, provided that the loss of the inherent d.c. balance is within tolerable limits.

A better method of avoiding this loss of gain, and very commonly used in i.c. operational amplifiers such as the 741, is to use a current mirror as the load for the amplifying transistor, with the operating current being set by the feedback one. This type of arrangement is shown in Fig. 8, and when used with a constant current load — normally yet another current mirror — on the output of Tr_7 , will give stage gains of the 50,000-100,000 range at low frequencies. Although this approach is easier to adopt in 'single-chip' fabrications, where the simultaneous fabrication of all the transistors will ensure identity of the base-emitter turn-on characteristics necessary for proper current-mirror operation, it has also been used in discrete-component designs.

This circuit employs nine transistors, and while the actual transistor count may be of little moment in an integrated circuit where the fabrication of active components presents no difficulty and little extra cost, it is nevertheless interesting to observe that a better stage gain can be obtained using the arrangement of Fig. 9, which uses one less transistor. In this circuit, the two-stage amplifier remains a symmetrical push-pull version of that shown in 7(a), but with the current-mirror active load moved back to the output of the second stage. This particular version of the two-stage amplifier was used first, so far as I can discover, in the National Semiconductors LH0001 low-power operational amplifier. Low-frequency small-signal voltage gains of up to 200,000 are possible using this layout.

The good gain and phase characteristics of this particular circuit arrangement have

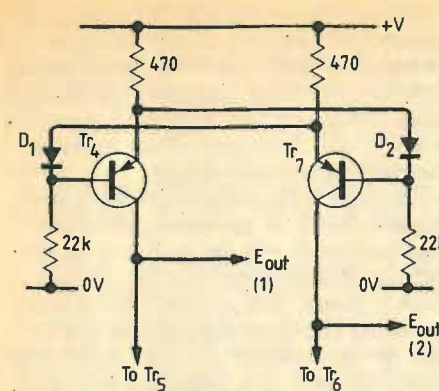


Fig. 11. 'Double-mirror' allows high gain, but with push-pull operation.

attracted the attention of Japanese designers seeking a circuit to provide enough gain to compensate for the relatively poor dynamic transfer characteristics of a simple, complementary-pair, power-mosfet source follower. The circuit design of Fig. 10(a) with emitter resistors in $Tr_{3,4}$ helping to minimize V_{be} differences, is normally simplified to that in Fig. 10(b), which is recommended by Hitachi for use with their 2SJ and 2SK-series complementary devices.

Because of the low impedance presented at the collector of Tr_5 (Fig. 10) by the input to the current-mirror active load, this circuit provides only a 'single-ended' output. This restriction may be avoided, with a further improvement in voltage gain, if the simple current mirror of Figs 9 and 10 is replaced by the 'double-mirror' circuit shown, on its own, in Fig. 11. This permits an l.f. voltage gain in excess of 500,000, with a balanced push-pull output, which would be of advantage in circuits employing identical rather than complementary output devices.

There is, however, a point which must be borne in mind in this usage, that in any straightforward embodiment of this circuit arrangement, the d.c. output potential at the collector of only one of the two second stage amplifier transistors can be controlled by the use of the internal d.c. negative feedback path; the output potential at the collector of the other could lie at any point between the +V and -V supply limits, which would preclude any significant undistorted output swing being obtained from the uncontrolled output. This difficulty can be removed, however, by using the output from the uncontrolled amplifier to regulate the input current supplied to the initial long-tailed pair, as shown in Fig. 12. This effectively stabilizes the output potential of this point as well, and leads to the interesting possibility of a truly symmetrical, very high-gain stage with antiphase outputs, both of which can swing within nearly the total voltage range of the supply.

Power mosfet amplifiers using the general circuit structure of Fig. 3(b) (Part 1), and any of the gain blocks of Figs. 9-12, will give very satisfactory steady-state t.h.d. and transient (step function) performance, but there is a fairly substantial snag in respect of the output

stage quiescent current. This is normally controlled by some circuit arrangement such as the variable resistance in the collector circuit of Tr_6 in Fig. 10, which produces a suitable voltage drop to maintain an appropriate forward bias on the output devices, and which may be adjusted to set the output stage quiescent current to a suitable value. This chosen value of forward bias must be stable, and maintained at the set value throughout the life of the amplifier, and affected as little as possible by changes in ambient temperature, supply line voltages

or ageing of components. Current mirrors, while providing excellent active loads to gain stages, are not, in any sense, constant-current sources, but merely circuit arrangements which reflect into the output limb the current fed into the input limb. In the circuit configuration of Fig. 10, the current through Tr_4 and Tr_6 is determined by the potential applied across the 'tail' resistor of Tr_1 and Tr_2 , and the current gains and forward V_{be} potentials of Tr_5 and Tr_6 : in the circuit of Fig. 11, this current is determined mainly by the V_{be} characteristics of Tr_4 and Tr_7 and

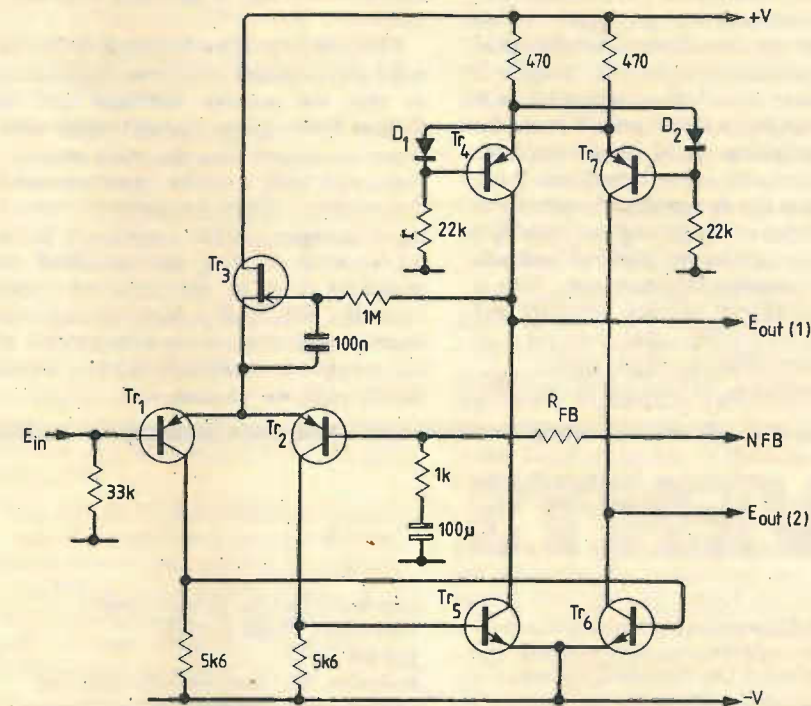


Fig. 12. Amplifier using circuit of Fig. 11, d.c. stabilized by connexion from Tr_5 collector to gate of Tr_3 . Provides symmetrical output, very high gain and large voltage swings.

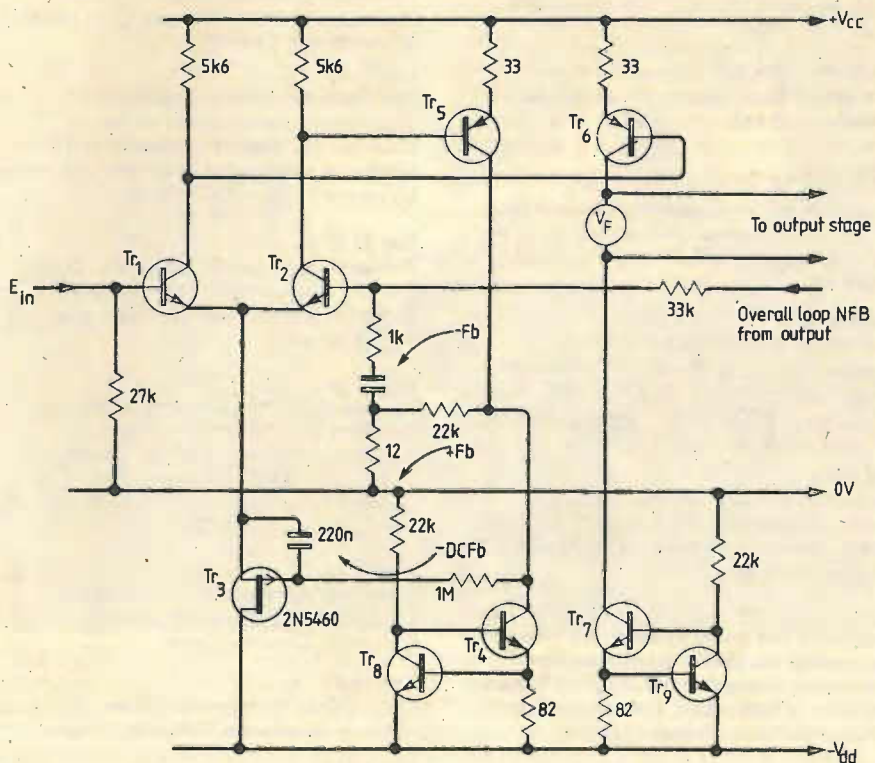


Fig. 13. Ordinary constant-current loads used in conjunction with positive feedback give same results as current mirrors.

the supply potential across the 22k feed resistors.

In such circuit configurations it is difficult to achieve quiescent current stability in the output stage over the expected range of supply voltage variations and fluctuations in ambient temperature. So, with regret, I concluded that a more formal constant-current source was necessary as the load element in Fig. 12, at least for T_{R6} , if a straightforward voltage dropper circuit in this path was to be used to generate the forward bias of the output devices.

While it is difficult to envisage any standard constant-current source which would have the same dynamic advantage as a current-mirror active load, an analysis of the behaviour of such an active load (which is that of positive feed-forward from the parallel antiphase limb) in an amplifier having an overall negative-feedback loop, shows that it is substantially identical in its characteristics to any arrangement giving a similar gain increase by 'positive feedback within the negative-feedback loop'. This is a circuit technique of some antiquity and more widely used, deliberately or inadvertently, than one might guess.

This realization, in addition to focusing

attention upon the possibilities and penalties of the technique, opens the door to the use of such a symmetrical amplifier configuration, with each half operating against a standard constant-current load, and an open-loop gain equal to or greater than that of the same circuit using a current mirror as the second-stage load by the use of a suitable positive-feedback path, as shown in the circuit of Fig. 13. In this, the polarities of the transistors have been reversed to take advantage of the slightly more favourable characteristics of the p-channel junction fet constant-current source in the 'tail' of the input long-tailed pair.

This use of positive feedback meets the main requirements of such an application, in that the positive feedback path is derived from a stage operated under more linear conditions than the main amplifier loop, and with a wider gain/bandwidth characteristic. Since the positive feedback signal is applied to the same point as the n.f.b. one, it can be visualized as cancelling part of the distorted signal normally fed back, thus leaving the distortion components as a larger part of the negative-feedback input, which facilitates their reduction.

This type of circuit, as an application of positive feedback, may be contrasted with the very commonly employed output-stage 'bootstrap', in which the positive-feedback signal is derived from a stage having worse linearity, and less good phase linearity, than the overall amplifier loop.

The practical power mosfet audio amplifier based on this design of voltage-amplifier stage, will be described in the next part of this article. This circuit has an output power of up to 100 watts, depending on supply line voltage, and has very good stability of d.c. operating conditions, gain and phase margins, and offers a significant advantage in audible quality over conventional bipolar power transistor designs.

References

2. Linsley Hood, J. L., *Wireless World*, Sept. 1971 pp 437-441.
3. Taylor, E. F., *Wireless World*, Aug. 1977 pp 28-32.
4. Taylor, E. F., *Wireless World*, Sept. 1977 pp 55-59.
5. Linsley Hood, J. L., *Hi-Fi News and Record Review*, Nov. 1972 pp 2120-2123.

To be concluded

EVENTS

June 19
RSGB H.f. Convention 1982 to be held at the Belfry Hotel and conference centre, Milton Common, Oxford. One day exhibition and lecture programme organised by the Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE.

June 21-22
Cable-casting in Europe - The commercial future. A conference on cable tv to be held at the International Press Centre, Shoe Lane, London EC1. Further information from International Broadcasting, 3-5, St John St, London EC1M 4AE.

June 22-24
Lab design '82, Joint Meeting of the Laboratory of Government Chemists and the IEE, at Church House, Westminster, London SW1. Details from IEE, Savoy Place, London WC2R 0BL.

June 29-July 1
The influence of microelectronics on measurements, instruments and transducer design. Conference to be held at UMIST. Details from the Conference Registrar, IERE, 99 Gower Street, London WC1E 6AZ.

July 4-9
Electronics systems. Summer school for teachers. Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ.

July 5-7
Distributed computing systems. A Conference sponsored by the SERC, to be held at (and details from) Department of Computer Science, University of Strathclyde, Livingstone Tower, 26 Richmond Street, Glasgow G1 1XH.

July 6-9
Man/machine systems. IEE international conference to be held at University of

Manchester Institute of Science and Technology. Details from IEE.

July 6-8
Reliability '83. Fourth national conference organised by the National Centre of Systems Reliability, and the Institute of Quality Assurance. To be held at the Metropole Hotel, National Exhibition Centre, Birmingham. Details from National Centre of Systems Reliability, UKAEA, Wigshaw Lane, Culcheth, Warrington, WA3 4NE.

July 12-15
The Video Revolution. A residential symposium organised by the Society of Electronic and Radio Technicians, 57-61 Newington Causeway, London SE1 6BL, to be held at the University of Reading.

July 12-16
Electronic application for teachers. Details from the Administrative Assistant, Room 110, Registrar's Department, University of Salford, Salford M5 4WT.

July 12-16
Integrated circuit engineering. Short course presented by the George Washington University, at Imperial College, London. Details from the UK/European office of the George Washington University, Hanover Square, London W1R 9DE.

July 12-16
Spectrum Management. Short course presented by The George Washington University. Details as above.

July 18-23
Optical fibre telecommunications. IEE Vacation school at the University of Essex.

July 19-23
Optical engineering including electro-optics. A short course presented by the George

Washington University at Imperial College, London.

July 19-23
Satellite systems for navigation, traffic control and surveillance. A short course presented by the George Washington University at Imperial College, London.

July 19-22
Acoustical imaging '82. Twelfth international symposium to be held at the IEE, Savoy Place, London.

July 21
IEEE Annual General Meeting. Savoy Hill, London WC2R 0BS.

July 26-28
Electronic Image Processing. IEE international conference at the University of York.

July 26-30
Data Communications Systems and Networks. Short course presented by the George Washington University at Imperial College, London.

July 26-30
Communications satellite engineering. Short course presented by the George Washington University at Imperial College, London.

July 26-28
Electromagnetic pulse and its effects on systems. Short course presented by the George Washington University at Imperial College, London.

A light pen for microcomputers. For this project, described on p.30 of this issue, glass fibre printed circuit boards and a fibre optic cable assembly is available from M. R. Sagin, Nancarras Mill, The Level, Constantine, Falmouth, Cornwall.

NEWS

The re-wiring of Britain

Following the recommendations of the Cabinet Office Information Technology Advisory Panel, (ITAP), the Home Secretary asked Lord Hunt of Tanworth to chair an inquiry into the implications of cable technology and its effect on broadcasting policy. The inquiry to be complete by the end of September 1982.

Various bodies will be making representations to the Hunt inquiry and two that we have received are from British Telecom and from the Post Office Engineers' Union. For once employers and employees are in accord and their submissions are very similar.

The BT and POEU submissions both point out that broadcasting and telecommunications are converging industries. Multi-channel cables can offer both broadcast channels and 'narrow-casting', the transmission of specialised, minority programmes. There is an overlap in the screen information services with teletext and viewdata. Electronic mail services can direct information to one terminal or to many and BT believes that the borderline between broadcasting and telecom services will eventually disappear.

Both submissions discuss the two principal cable techniques; tree networks in which all channels are presented to all customers, and the switched star network where the broadband service is available to

a local exchange and a narrower service may be switched to the customer according to the service selected and/or subscribed to. The switched star system is recommended as being more suitable for an interactive service and most easily realised with a mixture of fibre optic transmission for the broadband with co-axial cable for the local distribution.

The most important part of each submission is an answer to the question as to who would provide the physical cable network as opposed to the programmes. The BT report says, "There should be a clear distinction between the providers of the network and those purveyors of programme material which require franchises. This policy would permit franchises to be awarded and discontinued and for the introduction of competition between programme purveyors without replacement, disturbance or duplication of the physical network.

"The providers of the network then fill the role of carriers who provide the network for both tv and telecommunications services. Programme purveyors who need to seek franchises to offer their services should not have monopoly ownership of local broadband networks."

All this leads, of course, to the logical conclusion that BT should not only pro-

vide the cable network, but indeed have a unique ability to do so. They already provide point-to-point transmission of radio and tv signals along their landlines. There is an established force of engineers in the field and are the owners of wayleaves, ducts, poles and street furniture. They are providers of cable tv to some areas including an experimental fibre optic network in the City of Milton Keynes. Improvements to the telecommunication network will need a certain amount of re-cabling; if independent franchised programme companies were to provide the cable system, unnecessary duplication would result.


Another aspect that the Hunt inquiry has been asked to investigate is a supervisory system. ITAP suggest that programme providers should be self-regulating with a supervisory body such as the Press Council. BT suggests that there could be an extension of the IBA's franchising responsibilities.

The POEU highlights some of the political implications. The Labour party has promised that when they are next in power, they will put Project Mercury, the private telephone network, under BT's wing. Similar policies are likely to be applied to any cable service, and such political uncertainty will deter potential commercial providers of cable systems.

3-D tv - did it work?

When we wrote about the TVS *Real World* 3-D experiments it was before the event, so we hadn't seen it. Now we have. Frankly the results were rather disappointing. There were some close up sequences of a man blowing smoke through the screen and other people poking different things out at the viewer. These were very effective but somewhat limited in application. Other sequences of vehicles skidding on a test pad in Holland and of underwater examination of a sunken aircraft, were less successful and offered little enhancement over conventional two-dimensional tv images. One possible explanation may not be because of any failure in the system but in production techniques. We also saw recently a transmission (in two dimensions) of the Hollywood musical *Kiss Me Kate*, which was originally made in 3-D: it was noticeable how often deep perspective and out-of-focus backgrounds were used to enhance the three-dimensional effect. When the anaglyph effects were added, the original film must have been very spectacular.

The transmission of the *Real World* not

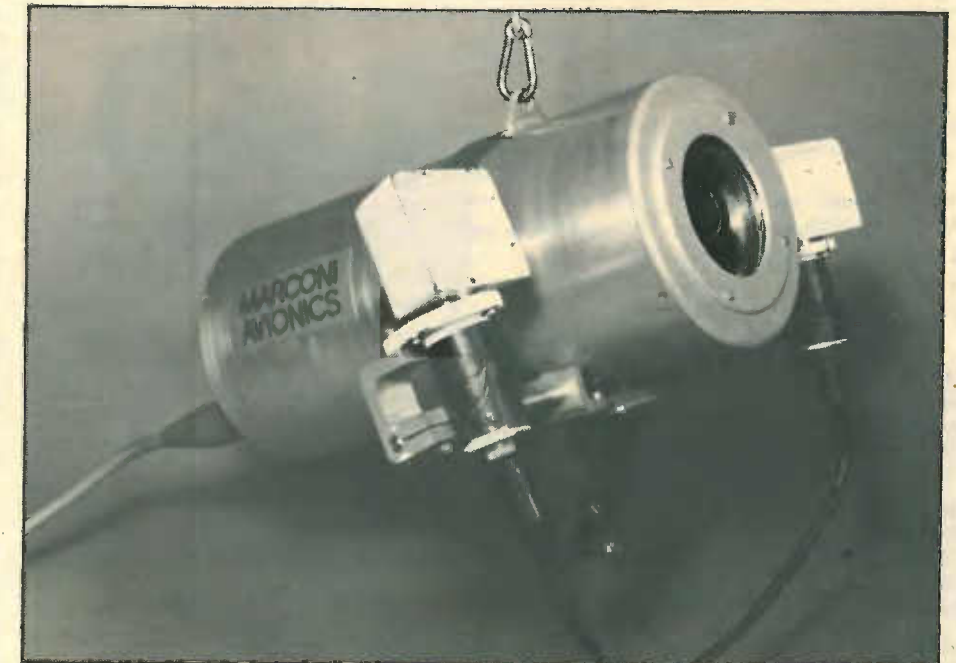

The recent edition of TVS's *The Real World*, devoted to the development of 3-D television, included some underwater sequences taken with this Marconi camera. The camera is designed for industrial use where the depth perception can be used for the remote inspection and control of underwater work, exposing divers to fewer risks. The cameras are used to produce images on two tv screens, combined by polarizing optics and then viewed through polarized goggles. For the tv programme, the images were transformed into the red/green anaglyph system. The camera has also been used to record the wreck site of the Tudor warship *Mary Rose*.

only included the 3-D sequences but was about 3-D images and gave a history and some examples of modern use of 3-D systems. The most important use seems to be in remote control for hazardous areas, such as inspection of undersea drilling platforms or inspection at nuclear power plants. For these purposes the system is not restricted to the red/green anaglyph system as two independent channels can be

processed and displayed on two displays where they may be combined optically to present one of the displays to each eye. This enables full colour displays without any of the crosstalk of the anaglyph system.

TVS tell us that they have no further plans to transmit 3-D material, although the possibility of late-night films in 3-D has been mooted.

Computer controlled radio station

ATAC is a system for switching between transmitters and aerials. One to be used for the BBC's overseas service in Cyprus will allow any of the ten transmitters to be connected to any of 32 aerial arrays, or to artificial loads, at a preselected time, frequency and mode dictated by operational requirements. The equipment has been designed, developed and manufactured by Drallim Davis Electronics.


Switching of the r.f. power between aerials and transmitters is accomplished by 250kW r.f. switches, pneumatically actuated and controlled by solenoid valves. Up to 250 of these switches are arranged in a matrix, housed in a special building.

Routing the signals through the matrix is achieved through a switching program module. Numbered plugs are inserted in sockets and actuate four switches corresponding to a number in b.c.d. Each group of plugs represents a code, for a

transmitter mode or time switching instruction, which is stored in a computer memory. The condition of each r.f. switch is recorded by the computer which can send the appropriate signals to the actuating solenoids. An important requirement is the ability to revert to manual control if needed. There is a keyswitch system which can do this and can also disconnect an aerial or transmitter for safety during maintenance.

The computer controls all the switching automatically and also maintains a record of all operations which is stored on disc and may be retrieved to diagnose, for example, any malfunction.

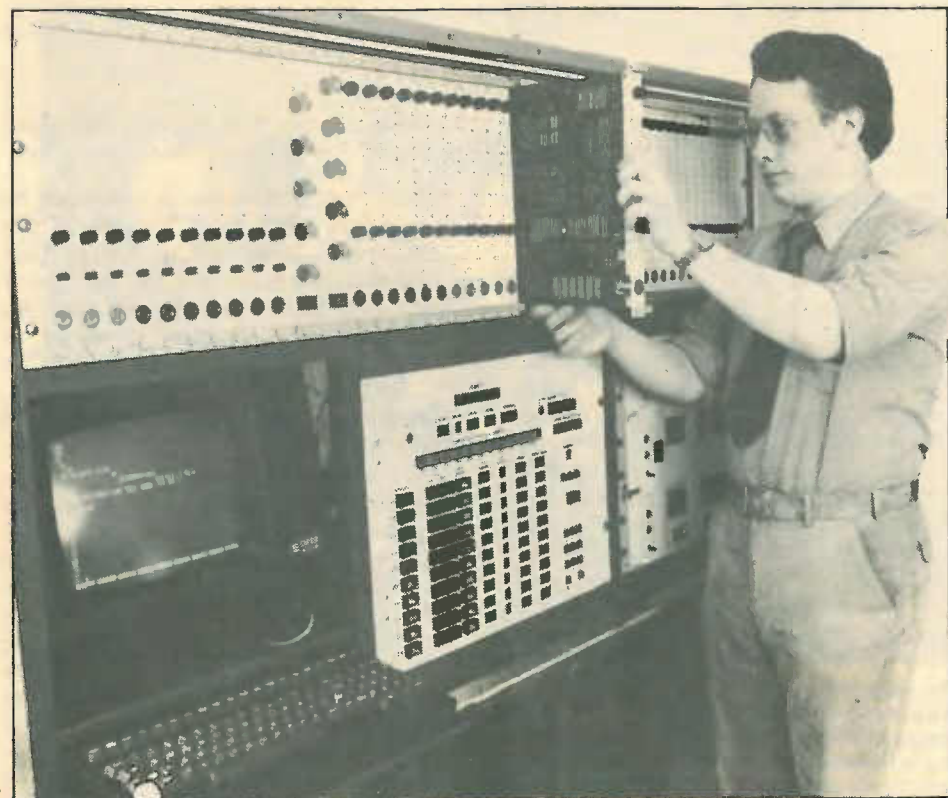Drallim have supplied switching systems to all the Independent Local Radio stations. They are quick to point out that such a system, although designed for use with a radio station, is suitable for a wide range of industrial applications where the computer switches mechanical movement in a pre-arranged sequence.



The Drallim ATAC (aerial/transmitter automatic control) system nearing completion at Bexhill-on-Sea before its installation in the overseas service transmitter in Cyprus

Are you sitting comfortably?

... because Bruel & Kjaer have developed an environment transducer which can measure a combination of air temperature, air velocity, and humidity to indicate the overall thermal comfort of a human being. The six-inch ellipsoidal transducer is combined with a control and display instrument which gives a numerical display to indicate the percentage of people likely to be dissatisfied with the thermal conditions if subjected to them. Such factors as the type of clothes likely to be worn, the activities to be undertaken, the prevailing vapour pressures can all be entered into the control unit and included in the calculations. Six different readouts are given and may be used as a guide to any modifications which may be necessary to provide optimum thermal comfort at a particular location. The system is battery-powered and portable and may be used wherever the maintenance of better thermal conditions is required in buildings, public vehicles and the like.

Dolby for personal stereo

One recent explosive expansion in the audio market has been the headphone cassette player exemplified by the Sony Walkman. Good as the reproduction is on these units, Dolby Laboratories hopes to improve them by re-designing the Dolby-B noise reduction system so that it can work at the lower voltages associated with the portable players. It not only needs to work at the lower voltages, but also be physically small enough to fit into these minuscule units. According to Dolby the development work is well advanced and integrated circuit manufacturers are primed to produce devices to be available to Dolby licensees very soon.

Plessey: a correction

In our March issue we reported that there is a six-month backlog in orders for the BBC computer used in conjunction with the current television series.

Our report stated that the cause of the backlog was the high drop-out rate in a gate array integrated circuit from Plessey.

In fact, Plessey do not supply any gate arrays for the BBC computer; nor are they in any way concerned with their design.

We apologise for any inconvenience caused by our mistaken statement that Plessey are responsible for any delays in fulfilling orders for the BBC computer.

BBC's micro — users comment

In this, the first BBC computer user's newsletter, the editors say they, "hope to adopt a reasonably neutral and objective stance on all questions relating to the BBC machine." The words 'hope to' and 'reasonably' may imply some cover for future comment but in this issue, honesty abounds. Besides the usual presentation of programs and tips for using the computer, Beebug, who call themselves the 'registered referral centre for the BBC project', inform readers as to how they might claim interest lost between Acorn cashing their cheque and their receiving their goods, of what they might expect if the computer they eventually receive is faulty and has to be returned to the manufacturer (illustrated by a typical reader's letter), and as to how long they might have to wait to receive a computer ordered. Users and potential buyers of this computer, which, according to published specifications and prices is one of the better buys on the market, should find this newsletter interesting. A cheque for £8.90 (or £10.40 outside UK) sent to Beebug, Dept 1, 374 Wandsworth Rd, London SW8 4TE, will secure a year's membership.

Banknote reader

A machine that can accept banknotes and reject forgeries is difficult to design because the ratio, between the acceptance of genuine notes and the rejection of the others, has to be finely adjusted. If it rejects too many genuine notes the customer becomes dissatisfied and will prefer to use some other facility. On the other hand if it accepts too many forgeries it becomes unprofitable. Landis & Gyr, a Swiss manufacturer settled on a 90% acceptance level as being the right compromise. Their acceptance machine, type SN25, incorporates a microprocessor which enables it to measure the bank note and to analyse the colour at pre-selected spots on the note. The m.p.u. can also be used to record the use of the machine. It monitors its own operation and adjusts its parameters on a statistical basis to give a final acceptance rate of 99% of all genuine notes. The machine may be fitted to a wide range of vending equipment and is thought to be of particular use in petrol vending.

Radiotelephones from Neve

When E.S.E. Ltd acquired the mobile radio division of Nolton Communications, they decided to use the name of one of their subsidiaries in a related field and launched Neve Radio Telephones. They are



Specifically designed for currency dealers and stock brokers, the City Business System from British Telecom has a v.d.u. terminal with a touch-sensitive screen. The surface of the screen is crossed by a matrix of infra-red beams which can sense which part of the screen is being touched. Each square on the screen enables the dealer's telephone to be connected to a pre-set number and the name or number of the dealer's contact is displayed within the square. Several pages of the 'electronic telephone directory' are available to the user and can automatically connect his telephone to any number displayed. Part of the screen can also be used to 'dial' any number not programmed into the system. The computer controlling the system has access to 5,000 pages of data and can also be connected to other data bases. The first commercially operational system has been installed at the treasury of Williams and Glyn's Bank. Ginger Brooks, the bank's treasurer, said how pleased he was with the system. The dealers had become familiar with its operation within a day and were completely at home within a very few days. Tony Booth of BT London, whose engineering staff invented the system, told us that a large number of enquiries and orders were being processed and that they were obviously 'backing a winner'.

continuing to manufacture market and service the Nolton range of mobile radios and radio telephones, but have wasted little time in getting new Neve products off the ground. One is a frequency-synthesised a.m./f.m. mobile radio telephone which is the subject of an order from the North West Gas authority and, claims Neve RT, is especially suitable for similar fuel and power customers who may have a large number of service vehicles. The mid-band model will shortly become available and is to be followed by low and high-band models. The set has 80 channel capability which can be extended to 160 channels.

In brief

In order to make communications between combat aircraft more secure, Lockheed are working on an optical communication link. The system would transmit and receive laser and non-coherent light in the infra-red range of the spectrum. Sets on each aircraft would be directed automatically and would be carried in addition to conventional radio. Experiments are being

carried out on both intensity-modulated and pulse-modulated systems.

The National Wireless Museum has recently been given a vast collection of very old service sheets, wiring diagrams and workshop manuals dealing with early radios, television receivers and even tape recorders. The Museum is willing to supply data and technical information free of charge to owners of very old equipment. The honorary curator is Douglas Byrne, 34 Pellhurst Road, Ryde, Isle of Wight.

Enamelled steel substrates are likely to replace conventional p.c.bs in electronic equipment of advanced design, according to a report following a nine-month evaluation by ERA Technology. The principal reason is the thermal conductivity of the metal substrate combined with the ability of the enamelled surface to withstand high temperatures. This will allow high density packing of integrated circuits with high-speed switching. Fine-line metallization suitable for solder attachment of surface mounted devices is available; flow soldering techniques are being investigated.

GPIB-TO-SERIAL INTERFACE

Economical and practical design has 'talker/listener' capability

by Chris Jay

There are a number of large-scale integrated circuits designed to make an instrument GPIB-compatible, so it is possible to develop an instrument interface without detailed knowledge of the protocols. Most of these are register oriented, implying the need for host processor, ram and rom circuitry. But a costly handicap will be the time required for software development. The Fairchild 96LS488 i.c. has the ability to perform a logic interface as a stand-alone unit independent of any host processor, so an interface may be quickly realised with a few logic chips, no host processor and no software development. Total chip count for the entire talker/listener unit was 14 i.c.s, including a 6402 uart for parallel/serial and serial/parallel data conversion and generator chip, MC14411. (The serial interface used RS232C signal levels synchronized to a predetermined speed, link selectable to 1200, 600, 300 or 150 baud.) It is possible to depopulate the circuit board if fewer functions are required, for example a single keyboard might require only the talker capability. All the circuit components necessary for the complete interface were assembled with ease onto a single Eurocard prototyping board. The interface function subset incorporated in the GPIB/RS232C circuit are listed as

- SH1 source handshake
- AH1 acceptor handshake
- T6 talker
- TE0 no extended talker addressing
- L4 listener
- LE0 no extended listener addressing
- SR1 service request
- RL0 remote/local
- C0 no controller capability.

Connections of the 96LS488 to the signal lines, address and mode switches, and the clock and master reset circuitry are shown in Fig. 1. This configuration will be standard for most interface designs. The clock pulse is generated on-chip, but requires an external RC network to provide the necessary time constant for oscillation; 220Ω and 220pF yield a clock of about 7MHz. The master reset pin is connected to a "power up" reset circuit using a 10kΩ resistor pull-up and 10μF capacitor to ground. The diode can be any medium current signal diode to provide a rapid discharge path for the capacitor when power is removed from the circuit.

The talk and listen address assignment of the instrument is programmed on the five-way switch pack. The A1-A5 inputs to the 96LS488 will be individually set to either a logic high or low; Table 1 lists the range of addresses available. This switch pack should be located at the rear panel of the instrument chassis to make it easy to reprogram the address assignment. Table 2 shows the range of operating modes: M0-M3 inputs may be set high or low by the

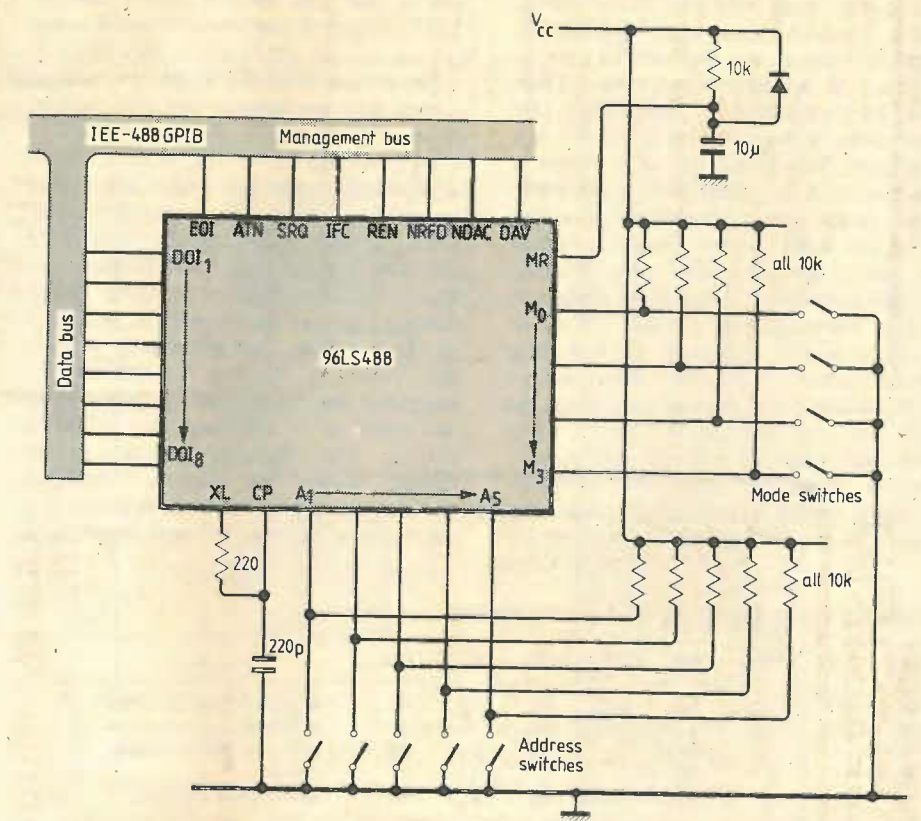


Fig. 1. Connections of the 96LS488 to bus signal lines, address and mode switches, and the clock and master reset circuitry. This configuration will be standard for most interface designs. The clock pulse is generated on-chip, but requires an external RC network.

What is GPIB?


The general-purpose instrument bus, originally defined in the Standard Digital Interface for Programmable Instrumentation ANSI/IEEE Std 488-1975, and revised in 1978 and 1980 as "Standard 488A", is now a standard instrument interface offering a universal approach to automatic operating, testing and measurement, and defines mechanical, electrical and functional specifications. It is a byte-serial, bit-parallel party line structure organised to provide asynchronous communication of digital data between a maximum of 15 devices called instruments, including at least one controller. The devices are classified into four categories

- talker - capable of sending data
- listener - capable of receiving data
- talker/listener - capable of either sending or receiving data
- controller - capable of controlling the overall interface functions, talking and listening.

All instruments configured to the bus will fall into one of these categories. Electrical interconnection comprises a 16-wire structure where all the

devices are connected in parallel, these lines subdivided into three groups

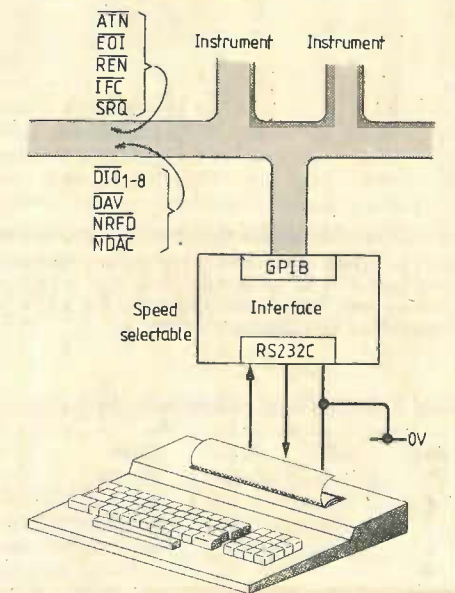- data - eight signal lines
- byte transfer handshake - three signal lines
- general interface and management - five signal lines.



Semiconductor Supplies International Ltd.

Dawson House, 128/130 Carshalton Road
Sutton, Surrey, England SM1 4RS
Tel: 01-643 1126 (Sales) 01-643 0829 (A/C Dept.)
Telex: 946650



CAT. NO. KD-55C
3 1/2 DIGIT LCD READOUT

WE'VE BROKEN THE £24 PRICE BARRIER ON L.C.D. MULTIMETERS!!!

LOOK AT THESE PRICES!!!

★

★

★

L.C.D. MULTIMETERS TYPE	14	5.9	10.49	18.5.82
KD55C	38.05	34.32	32.18	50 +
KD30C	32.80	31.32	29.37	30.90
KD25C	23.10	21.89	20.82	28.20
				19.80

All prices subject to VAT at current rate



CAT. NO. KD-30C
3 1/2 DIGIT LCD READOUT

INTRODUCTION

This Digital Multimeter is a portable 3 1/2-digit, compact sized multimeter, ideally suited for field, lab, shop, bench and home applications. Here's a review of some of the features that qualify your new Digital Multimeter as a real "pro". The latest IC and display technology is used to achieve the lowest possible component count. This, in turn, ensures reliability, accuracy, stability and a really rugged, easy-to-handle instrument.

Low battery voltage automatically detected and displayed. No needles to bend. No parallax and no zero adjust. Just a high contrast, easy-to-read, 3 1/2 digit, LCD.

Effective overload and transient protection on all ranges.

Over-range indication on each range.


Full auto-polarity operation.

Dual-slope integration to ensure fast, accurate, noise-free measurements.

GENERAL SPECIFICATION

Operating Temperature: -10°C to 50°C
Storage Temperature: 0°C to 50°C
Input Impedance: 10 megohms (DC/AC VOLTAGE)
Polarity: Auto-polarity, (-) sign when minus
Over Range Indication: The number of "1" only display
Power Source: 9 Volt rectangular battery
Low Battery Indication: "BT" on left side of display
Zero Adjust: Auto Zero-Adjustment
Weight: 580g (Battery and Test Lead included)
Dimension: 165 x 95 x 41 (H.W.D.)

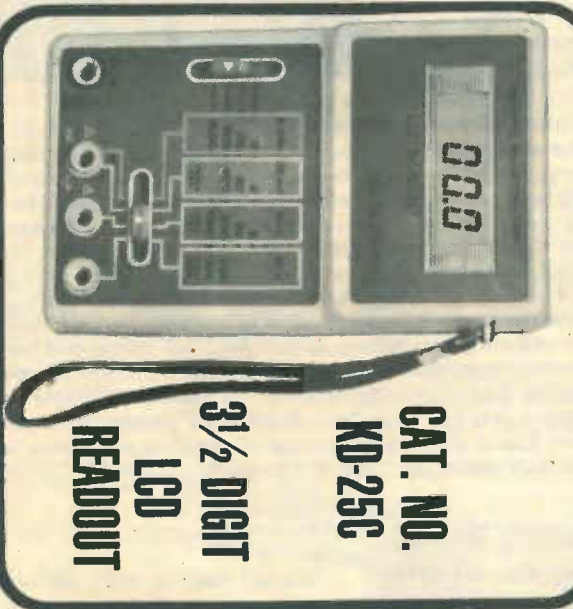Accessories: ★ Complete with 9V Battery, Test Lead, Spare Fuse and Optional Carrying Case



CAT. NO. KD-25C
3 1/2 DIGIT LCD READOUT

SEND FOR OUR FULL CATALOGUE (£1 incl. P&P) SENT FREE TO COMMERCIAL AND EDUCATIONAL USERS ON APPLICATION

ITEM NO.	NAME	FUNCTION
1.	Display	A 3 1/2 digit display (1989 max.) with decimal point and minus polarity indication. Indicates measured input values plus over-range and low battery condition.
2.	POWER switch	Turns the instrument ON and OFF.
3.	Input +/jack	Connect +/red lead for all voltages, current and resistance measurements.
4.	Input -/jack	Connect -/black lead for all measurement.
5.	Input 10A/jack	Connect +/red lead for over 1 to 10A (KD-55C only).
6.	Mode switch	For selecting modes: DC Volts, AC Volts, Ohms, DCA, ACA.
7.	Range switch	For selecting ranges: Voltage: 200mV, 2V, 20V, 200V, 1000V/DC, 700V/AC. Current: 200μA, 2mA, 20mA, 200mA, 1000mA(1A), 10A/KD-55C. Resistance: 200Ω, 2k, 20k, 200k, 2000k, 20MΩ.
8.	Compartment	Battery and Fuse.
9.	Lamp	Over load indication. (Resistance Range only)

£8.0E

four-way switch pack shown in Fig. 1 or alternatively, by jumper links. The talker low or high-speed mode depends on whether the bus is configured around open-collector or three-state drivers. Table 3 shows the range of logic signals that reflect the state of the interface. The TAD, LAD, and D/S/E outputs may be used as inputs to combinational logic or to drive LEDs to give visual indication of instrument status. Two additional logic outputs, not listed in Table 3, are also used to provide interface state information. The DRB output goes active low when the instrument is required to drive the bus data lines. When this output goes low it indicates that the instrument interface is either in the talker active state or in the serial poll active state. The R/L output provides remote or local status indication, but this feature is not used in the design.

The talker/listener interface circuit is shown in Fig. 2. Although the data lines are connected to the 96LS488 interface chip (necessary for message decoding) no data will pass through the device. The 6402 uart eight-bit transmit and receive register lines are connected through inverting buffer drivers to the bus data lines. The 96LS488 provides the necessary

handshake signals to ensure asynchronous transfer of data to the 6402 transmit buffer register when the interface is in the listener active state, and from the 6402 receiver buffer register when the interface is in the talker active state.

When power is applied to the interface the master reset circuit resets the 96LS488 chip and 6402 uart through the inverter and or-gate. The 74LS74 latch is cleared. The Q output of this device is wired to the request service input of the 96LS488. In response the 96LS488 pulls the service request line low inviting the controller to conduct a serial poll; the line is used as wired-or function for instruments configured to the bus. Any instrument requiring attention will assert this line by taking it low. The controller may then conduct a serial poll to determine the source of the service request. When initially powered the instrument will be in an off-line state, but requesting service, see Table 3. This is to inform the controller that the interface is powered up and ready to be addressed as a talker or listener. The controller responds to the service request as follows. First the unlisten message is sent to all instruments, necessary to prevent listeners responding

to status bytes as though they were data bytes, then the serial poll enable message is issued over the bus. The controller then issues the talk address of each instrument, and sets the attention line inactive to take the status byte of the instrument currently in serial poll active state.

When the serial interface receives its talk address the instrument enters the serial poll mode. The controller may listen to read the active low assertion of the request service output from the 96LS488 on data line seven (the other data lines float passive high). When the controller accepts this status byte, STST will pulse high, driving STRDY low through the inverter. This illustrates the automatic response of the STST/STRDY handshake. The controller's command program may now recognize that power has been applied to the serial interface and it may be addressed as a talker or listener. The rising edge of STST will clock a high onto the Q output of the 74LS74 removing the request for service.

Listener Interface

For a printer interface the instrument will be addressed as a listener. The LAD output goes low to illuminate the green LED when the listen address is received. More than one listener may be active on the bus at any one time but only one talker is permitted.

During the listener active state valid data on the data lines will be present at the TBR inputs of the 6402 from the outputs of the 74LS240 inverters. The 96LS488 will decode the three-bus handshake lines to assert RXST high when data has settled. The rising edge of RXST triggers the 121 monostable to its quasi-stable state. Its Q output will be low for a time constant of $0.7CR$, then go high, the rising edge transferring data in the 6402 transmit buffer register to the internal transmitter register (delayed if the transmitter register is not empty). The 6402 serially transmits this data byte and automatically inserts the appropriate stop, start and parity bits. The format is pre-programmed by a binary data pattern set on the switch pack and resistor combination wired to the PI, EPE, SBS, CLS inputs, see Table 4. These control register inputs require that CRL be high during control register load. Data speed at the TRC input, 16 times the rate of the serialized data. The RXST/RXRDY handshake is completed when the transmit buffer register is empty. TBRE goes high informing the 96LS488 i.e. that the uart is ready to accept the next data byte for serial transmission. The local handshake is therefore achieved by RXST/TBRL and TBRE/RXRDY signals, decoded from the handshake signals. The actual speed of data byte transfer over the bus depends on the slowest active listener. If the printer interface is the only active listener, then the data lines will be ready for the talker to transmit the next data byte.

The signal conditioning and inversion required to drive the RS232C input from the 6402 output is achieved by the $\mu A1488$ line driver circuit (pin 3).

Table 1. Talk and listen address assignment

DIO ₈	DIO ₇	DIO ₆	DIO ₅	DIO ₄	DIO ₃	DIO ₂	DIO ₁	
X	H	L	A ₅	A ₄	A ₃	A ₂	A ₁	primary listen address
X	H	L	L	L	L	L	L	unlisten
X	L	H	A ₅	A ₄	A ₃	A ₂	A ₁	primary talk address
X	L	H	L	L	L	L	L	untalk
X	L	L	S ₅	S ₄	S ₃	S ₂	S ₁	secondary address

Table 2. Operating modes set by four-way switch pack

Mode inputs				Operating mode	Function
M ₀	M ₁	M ₂	M ₃		
L	L	L	L	off line	device cannot take part in bus operations
L	L	L	H	T on low speed	device goes directly to talk addressed state and can source data to bus
L	L	H	L	L on	device goes directly to listen addressed state and can receive data from bus
L	L	H	H	T on high speed	as for T on (low speed)
L	H	L	L	T low speed	talker only, single address mode
L	H	L	H	TE low speed	talker only, extended address mode
L	H	H	L	T high speed	talker only, single address mode
L	H	H	H	TE high speed	talker only, extended address mode
H	L	L	L	L	listener only, single address mode
H	L	L	H	LE	listener only, extended address mode
H	H	L	L	T/L low speed*	talker/listener, dual address mode
H	H	L	H	TE/LE low speed	talker/listener, extended address mode
H	H	H	L	T/L high speed*	talker/listener, dual address mode
H	H	H	H	TE/LE high speed	talker/listener, extended address mode

* For dual-address talker/listener modes the talk and listen addresses can be different.

Note: Low speed talker option is selected where open-collector data drivers are used. Delay from putting valid data on bus to DAV going true is 2.0µs. High speed option is selected where three-state drivers are used. Settling delay (data to DAV) is 1.1µs for first byte sent after a low-to-high transition of ATN and 500ns for subsequent bytes.

Table 3. Codes that reflect interface state

TAD	LAD	D/S/E	State
H	H	L	off line
H	L	L	addressed to listen (LADS)
L	H	L	addressed to talk (TADS)
L	H	H	serial poll mode (SPM)
H	L	H	receiving end message (LACS)

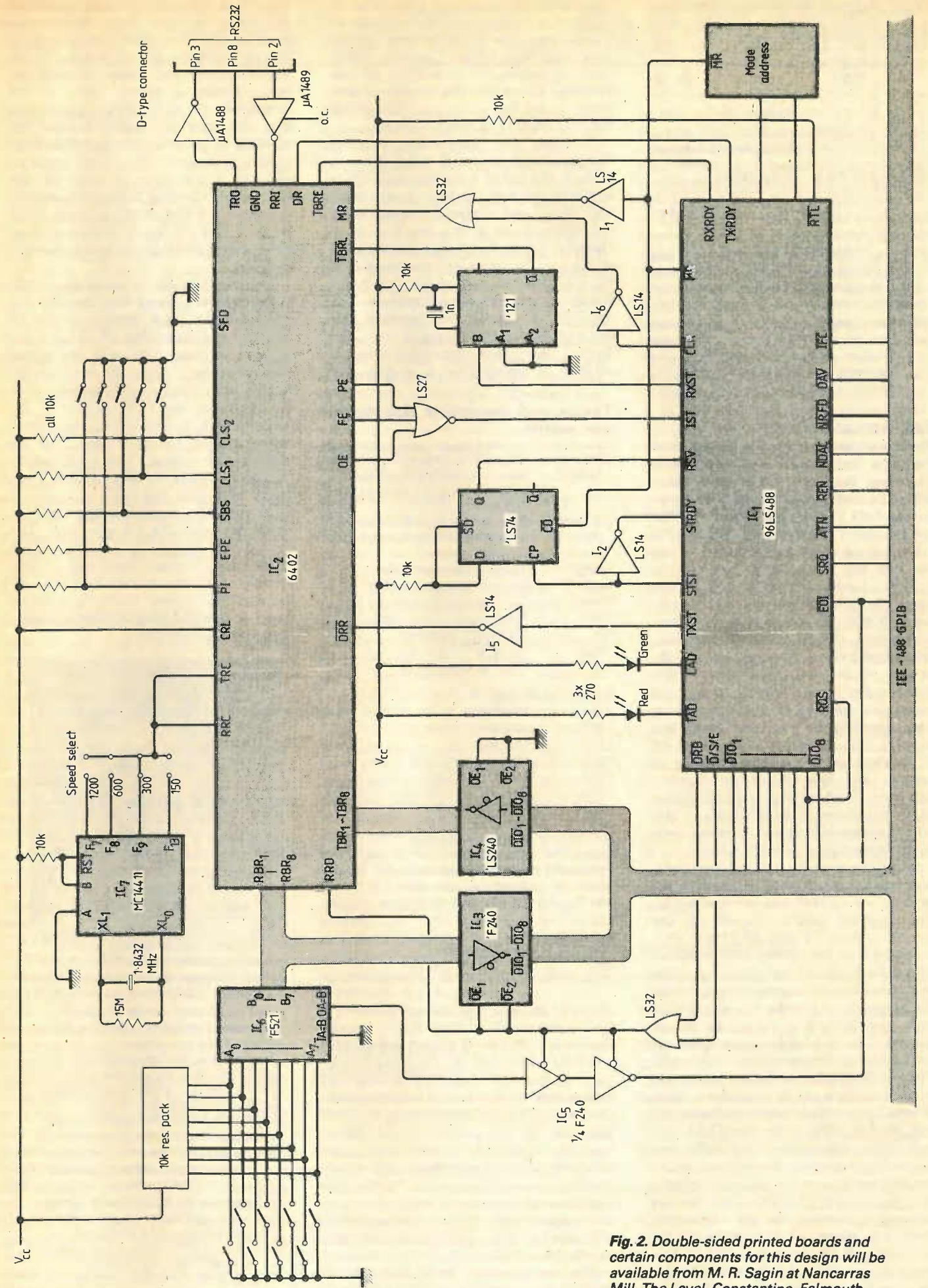


Fig. 2. Double-sided printed boards and certain components for this design will be available from M. R. Sagin at Nancarras Mill, The Level, Constantine, Falmouth, Cornwall.

Table 4. Codes required for character length and stop bit format in 6402.

Character length (bits)	5	6	7	8
CLS1	L	H	L	H
CLS2	L	L	H	H

Character length selected			
SBS input	5 bits	6, 7 or 8 bits	} Stop bits
L	1	1	
H	1½	2	

PI—Parity inhibit — A high level on this input inhibits the generation of a parity bit. A low level enables the generation of a parity bit.

EPE—Even parity enable — When PI is set low, a high level on the EPE input enables even-parity checking and generation. A low enables odd parity checking and generation.

Talker Interface

Keyboard data may be transmitted over the data lines when the interface is addressed into the talker-active state. When the interface receives its talk address the 96LS488 TAD output goes low and the red led lights. When the controller drives ATN high it relinquishes control of the bus data and management lines and the keyboard interface enters the talker active state. The D/S/E output would already be low in TADS, and on entry to the talker-active state, the DRB output goes low, relieving the three-state condition via the or-gate at the output of the 74F240 inverting bus driver. Note that during the serial poll active state D/S/E would be high, disabling the bus driver device and allowing data line seven to be driven by RQS. The 74F240 was chosen because its outputs can sink 64mA and therefore satisfy the 48mA current sink requirement of the bus electrical specifications. It also offers considerable power economy over the functionally equivalent 74S240.

Serial data from the RS232C interface is inverted and conditioned to a t.t.l. signal level by the μ A1489 line receiver circuit. The serialized data is clocked into the receive register of the 6402 and then transferred to the receive buffer register with the appropriate start, stop and parity bits automatically inserted, according to the program set on the five-way switch pack (see Table 4 for character format details). The data-ready output from the 6402 drives the transmit-ready input high. The 96LS488 informs the listeners active on the bus that a data byte present is valid. When all active listeners have accepted this byte the 96LS488 asserts the TXST line high. The inverted output drives the data received reset input to the 6402 low, clears the data-ready output permitting the next byte to be received without an overrun error. It is assumed that the rate of the serial data generated by a typist at the keyboard will be slower than the of data reception by the active listeners on the bus, therefore no overrun error will occur. It is up to the instrument designer to

ensure a speed compatibility of instruments on the bus. If a fast talker is required to transmit data to one or more slow listeners then the listeners should have some kind of fast front-end buffer store, to reduce the probability of data overrun. The talker will transfer a data string to the bus using the TXST/DRR and DR/TXRDY as local handshake.

Provision has been made for the transmission of an end-of-string character to mark the end of a transmission. When an instrument is in the talker-active state it may use the end-or-identify line to signify the transmission of the last byte in a character string. A low signal transmitted on the line concurrent with transmission of the final data byte may be decoded by the listeners as receiving the end message. The 96LS488 is capable of decoding this message in the listener-active state, see Table 3 status codes. This talker design is capable of recognizing a unique end

Terms and acronyms describing bus events

GPIB	General purpose interface bus
TALKER	Device forming part of bus interface which can send data to DIO lines
LISTENER	Device forming part of bus interface which can receive data from DIO lines
TADS	Talker addressed state
LADS	Listener addressed state
SPAS	Serial poll active state
PPAS	Parallel poll active state
CIC	Controller in charge
TACS	Talker active state
LACS	Listener active state

Remote Messages

ATN	Attention
UNT	Untalk
UNL	Unlisten
MLA	My listen address
MTA	My talk address
SRQ	Service request
RQS	Request service
SPE	Serial poll enable
SPD	Serial poll disable
STB	Status byte
PPE	Parallel poll enable
PPD	Parallel poll disable
PPC	Parallel poll configure

Local Messages

rsv	Request service
ist	Instrument status

character and asserting the end-or-identify line automatically. The 74F521 octal comparator chip A=B output will go low when the code set on the eight-way switch pack matches the data byte waiting for transmission in the receiver buffer register output. A 74F240 inverting buffer provides the necessary current drive capability to the line. This device will only be enabled during the talker-active state, so other instruments may use the line for end message generation when they are addressed as active talkers. The controller may also use this as the identify line to invoke a parallel poll.

The interface has been designed to respond to a parallel poll. The individual status input to the 96LS488 will remain

high if no error occurs during transmission but will go low if either a parity, framing or overrun error occurs during transmission. The 6402 status bits are latched internally, so the output of the three-input nor gate stays low until the 6402 receives a master reset. If the comparison bit of the PPE message was low, the interface would respond by asserting its assigned data line during the parallel poll active state. The controller will read this as an error condition, the error having occurred during transmission or reception of data. A non-assertion of the assigned data bit would indicate that no error had occurred during transmission or reception.

A master reset may be issued to the 6402 in the form of a device clear message or a selected device clear message. It will be necessary to clear the PE, FE or OE if one or more of these flags were set during transmission. When the instrument receives such a master reset message from the controller the CLR output of the 96LS488 will go low setting the master reset input to the 6402 high, via the inverter and or-gate. The CLR output remains low while the instrument is in the accept data state and ATN is active. If ATN goes false or the interface exits the accept data state the line goes high. The interface will be reset, and the ist line will return high. Normal talker and listener activities may be resumed after the uart has received a master reset, via a device clear or selected device clear message issued by the controller. □



Chris Jay is applications engineering manager for digital bipolar and l.s.i. products at Fairchild's Bristol design centre, providing technical support for customers and marketing. Joining GCHQ in Cheltenham as a trainee technician straight from school, he obtained City and Guilds (Telecommunications) and HNC qualifications at day release and evening classes. These qualifications helped him qualify as a mature student for a full-time degree course at Essex University. On graduation in 1977 he joined Texas Instruments as part of the engineering design effort on the 9911 DMA controller chip. Preferring to be involved with device applications he joined Linotype Paul in Cheltenham where he designed computerized file storage equipment for the newspaper and printing industries. He left to take up his present job two years ago.

The expanding spectrum

It is now 70 years since American engineers decided that radio waves of "200 metres and down" were of little or no practical value and could safely be given to experimenters and radio amateurs who, they confidently predicted, would find it difficult to radiate far beyond their own back yards! By the 1930s not only had h.f. been opened but "microrays" were spanning the English Channel and frequencies up to about 100 MHz were coming into general use. The development of the magnetron, the klystron and (later) the travelling-wave-tube opened up an extensive microwave spectrum, and the process of expanding the useful frequencies continues. Japan now has some local urban broadband links on 40 GHz, possibly the highest frequency to be used for commercial telecommunications, and one notes that the Rutherford and Appleton Laboratories have developed methods of measuring molecular absorption by atmospheric gases in the 100 to 1000 GHz region.

Conferences galore

Over the past couple of decades, large engineering conferences, seminars and associated trade exhibitions seem to have become ever more frequent and more specialised. This is certainly true of the telecommunications, radio communications and broadcasting scene. For example in the space of the one month of April there was the enormous annual NAB (National Association of Broadcasting) event at Dallas, Texas involving some 30,000 people and 400-plus trade stands in what has become an increasing international exhibition; Communications 82 at NEC Birmingham; the IEE's second "International Conference on Antennas and Propagation" at York University; and the IERE's fourth "International Conference on Video and Data Recording" at Southampton University — and possibly others that I have remained blissfully unaware of. And once again those concerned with broadcasting face the prospect of the International Broadcasting Convention at Brighton in September, another NAB at Las Vegas next April and the Montreux Technical Symposium a few weeks later.

NAB succeeds in keeping it all down to 3½ days (engineering papers 2½ days) and the papers tend to be of a much more practical and operational nature than those delivered, for example, at IBC. As someone who has attended every IBC since its start in 1967, some five Montreux and three NAB events I have little doubt that NAB comes nearest to meeting the real needs of the broadcaster — its size alone ensures that firms concentrate on introducing new ideas and new equipment at

that event. The papers at IBC, admittedly, are usually of a higher technical level, but the "workshops" and panel discussions at NAB often mean more to those who attend — and can sometimes be in advance of even the R and D conferences. NAB 1982, for example, provided much more information about the latest non-composite analogue video recording techniques, such as the ½-inch Chroma Trak format used in the one-piece RCA "Hawkeye" camera/recorder (and also ¼-inch and 1-inch component formats) than the specialized recording conference at Southampton — though this has more to say about the ultimate all-digital component recording systems that have not yet reached the market place.

Antennas and propagation

Browsing through the formidable 839 pages of IEE Conference Publication No 195 "Antennas and Propagation" one cannot but sense the gap that separates R and D people and the communications practitioners. For example, a number of the papers reflect the intensive study of s.h.f. transionospheric propagation, including the effects of heavy rain and ice crystals on 12 to 20 GHz satellite circuits, including the extent of attenuation and depolarization in different parts of the world. Clearly these studies are of practical importance both for communications and satellite broadcasting — and indeed show that these effects are rather more severe than originally thought. But, at least for European DBS systems, the main technical parameters were determined in 1977 and one suspects that the R and D results, important though they are, will have only limited influence on the systems planning for 12 GHz despite the additional fade margins etc. that theoretically should be provided in those parts of the world subject to monsoons, tropical rainfall or where ice crystals can reduce the co-channel interference protection provided by polarization discrimination.

Modelling h.f. propagation

The conference also underlined the continued search for accurate "modelling" of h.f. propagation. Despite some 60 years of study, it is clear that nobody can yet predict with confidence either tomorrow's optimum working frequencies or those for ten years ahead. Neither the short-term daily variations of up to 10 or 15 per cent, or the maxima or minima of future sunspot cycles can yet be delivered with confidence by even the most complex, computer-based models. This does not stop R and D from trying — and the scientific journals

as well as the conferences are full of attempts. But such predictions remain as uncertain as long-range weather forecasting, though one notes that one of the leading experts in this field, C. M. Rush of the Institute of Telecommunication Sciences, is convinced that "the limitations imposed upon h.f. propagation systems by the ionosphere must be assessable, quantifiable, and predictable". That will be the day! In the world of antennas, the keyword still seems to be "adaptive" and the mathematicians reign supreme; and one notes that most of the more practical innovations described at York had already appeared in the journals or around the conference circuit. This is not to criticize the R and D work but only to wonder what impression some of it will make outside the laboratories. Yesterday's R and D is often a closed chapter.

Above the m.u.f.

At York University, H. P. Williams noted the way in which, at h.f., it is possible to use frequencies above the m.u.f. though surprisingly he made no mention of the regular "long-path" type of chordal hop propagation now well established. But he does make the interesting suggestion of using frequencies as low as 14 MHz for commercial or military "meteor-scatter" communications links (usually operated at v.h.f.). Some of the original investigations by Professor O. G. Villard of Stanford University in 1947-53 showed that reflections from meteor trails can be detected as an almost continuous weak-signal background on frequencies down to about 10 MHz. H. P. Williams believes that meteor-burst communications at h.f. could be of practical value for medium-distance paths of about 1000 km, at times when the path is otherwise closed to ionospheric reflections.

Noted at NAB

American medium-wave (a.m.) broadcasters are worried at the prospect of reduced night-time "clear channel" coverage following the walk-out of Cuba from the Region 2 planning conference after filing a plan for 187 m.f. stations (without directional aerials) including two 500 kW installations . . . another problem is the FCC's decision to leave the choice of an a.m. stereo system to the market place while there are still four aggressively competing and non-compatible systems: Magnavox AM-OM; Motorola C-QUAM; Harris V-CPM; and Kahn/Hazeltine Independent Sideband . . . FCC is to authorize a whole new category of tv broadcasting as a "Low power television service" with a minimum of regulations. . . . Three competing systems are being investigated for multichannel sound on tv; a Japanese

system proposed by EIAJ and two American systems by Zenith and Telesonics. . . . Network radio is back in fashion using a great deal of satellite distribution. . . . Japanese firms are making ever deeper inroads into the American broadcast-equipment market including growing use of small Saticon pick-up tubes in the increasingly fashionable compact colour cameras. For 25 or 30mm sizes the lead-oxide vidicon remains the first choice.

AMATEUR RADIO

First moonbouncer

The ability to make world-wide contacts on v.h.f. and u.h.f. by utilizing the earth-moon-earth path continues to attract more enthusiasts into this branch of the hobby, despite the demanding requirements in terms of aerials, transmitter powers and low-noise receivers. Stuart Jones, GW3XYW, near Swansea recently became the first amateur in Wales to "work all continents" on 432 MHz moonbounce. G3WDG and G4KGC of Towcester have successfully used a 4-metre dish aerial designed for 1296 MHz on 432 MHz, and this is believed to be one of the smallest dishes yet used on this band.

During the now well-established annual amateur radio reception at NAB a plaque was presented to John De Witt, N4CBC (formerly W4ER1 and W4FU) who as a lieutenant colonel in the U.S. Army Signal Corps at the end of the war was officer in charge of the project at the Evans Signal Laboratory that led to the first successful "moonbounce". This was realised on January 10, 1946 when a quarter-second pulse was transmitted on 111.5 MHz, and 2½ seconds later a faint returning 'beep' was heard. Earlier, in May 1940 while chief engineer of WSM, Nashville, Tennessee "Jack" De Witt had attempted to achieve moonbounce and shortly after V-J day he again turned his attention to the question, this time based on modified radar equipment with a 64-dipole aerial array and narrow-band quadruple-superhet receiver tuned to take account of doppler frequency shift. The first engineer actually to hear the moon-echoes was Herbert Kauffman, W2OQU. The idea of hearing radio signals from the moon was even then not new. As early as September 1921, QST had warned:

"A whimsical lad called Maloney,
A ham in the art of Marconi,
Once essayed to tune
A spark from the moon.
With suspicion regarded
He's now always guarded
Beware lest you follow Maloney!
Fortunately many amateurs have been able to follow in the steps of Maloney, De Witt

and Kauffman without incurring excessive suspicion as to their sanity. Indeed nature's passive satellite system e-m-e is now well established.

Amateur tv

In *CQ-TV*, D. J. Long, G3PTU suggests that for amateur television transmissions on bands above 432 MHz consideration should be given to frequency-modulation of the vision channel. With the approach of direct broadcasting from satellite, components for f.m.-type tv receivers will become more readily available. Problem may be to find 27 MHz or so of available radio spectrum. Grant Dixon, G8CGK draws attention to the availability of one-chip analogue/digital converters (at around £66) that provides 6-bit (64 level) coding, sufficient for experimental digital-video systems. The British Amateur Television Club will hold its 1982 convention at the Post House Hotel, Leicester on September 4-5. John Wood, G3YQC, editor of *CQ-TV*, has started trying to compile a history of amateur television from the earliest pre-broadcast days. Amateur tv enthusiasts in the Bath and Leicester areas are seeking to establish atv repeaters.

It was just 30 years ago, in May, 1952 that what is believed to have been the first amateur two-way high-definition tv contact was made on 432 MHz by Harold Jones, G5ZT/T of Plymouth and Fred Rose, G3BLV/T who lived in Sunderland but brought his equipment by car down to the Plymouth area. The a.t.v. stations had taken some three years to build.

Here and there

Just after World War II, when many amateurs were eagerly buying up surplus military equipment, there were frequent warnings that some airborne equipment contained explosive devices intended to prevent the equipment falling intact into enemy hands. However, R. C. Field, G3IPM, recently had an unpleasant surprise when an old IFF (Identification Friend or Foe) unit which had been in his possession for 36 years exploded without warning, wrecking his garden shed but fortunately resulting in no human casualties.

British amateurs are participating in a study being carried out for CCIR into the extend of v.h.f. sporadic-E propagation on the v.h.f. bands. On 144MHz this has been found to exceed greatly that predicted by methods currently recommended by CCIR. Of particular importance will be the observation of the duration of such events as established by the large network of European v.h.f. enthusiasts.

At the recent IEE Conference at York University, R. G. Flavell, G3LTP described the work of European amateurs in determining the limits of long-range tropospheric propagation on 144MHz and 432MHz in anticyclonic weather condi-

tions. He pointed out that although doubts had sometimes been raised on some quarters about the genuineness of the long distance claimed by amateurs, there was good independent evidence relating to the long oversea path of 2635km (a European record) achieved in a two-way contact on 144MHz between Devon and the Canary Islands on August 6, 1980.

The revised schedule for the British amateur radio licences finally appeared in the London, Belfast and Edinburgh Gazettes on April 16 and the Home Office has resumed the issue of new licences.

The ARRL has formally asked the FCC to ban the use of amateur frequencies by American cable television operators claiming "amateur radio operators in many states have suffered severe interference caused by operation of cable systems which 'leak' radio frequency energy on amateur frequencies . . . worse, consumers of cable television are subjected to interference from amateur v.h.f. stations". It is noted that problems arise from inadequate shielding of the cable systems, the use of poor quality components, inferior installation procedures and that the problem cannot be resolved in the context of the present rules due to the proximity of the two services in residential areas . . . even hand-held 144MHz transmitters can destroy a cable channel for several city blocks". ARRL have also formally opposed the relaxation of cable leakage regulations which currently limit radiation to 20µV/m at 10ft between 54 and 216MHz but which may be relaxed to 100µV/m.

In brief

ZD9GI a 28.212MHz beacon station on Gough Island in the South Atlantic is now operational, tended by members of the weather station . . . Some Swedish amateurs are active on 1.8MHz c.w. and more and more countries are now permitting operation on this band. . . . The ARRL DX countries list currently totals 318 different "countries". . . . The GB3ANG 70.06MHz beacon station has a two-speed keyer in order to provide high-speed (100 w.p.m.) identification during meteor-scatter bursts. . . . Hans Meurer, W2TO has achieved 100 countries confirmed using a 2-watt Heathkit HW8 transceiver among the high-power stations in New Jersey. 60 per cent of his contacts were on 21MHz, 35 per cent on 14MHz and 5 per cent on 7MHz. . . . The Americans are shortly to begin operating an over-the-horizon radar between 5 and 35MHz located near Moscow, Maine. It will have an effective radiated power of the order of 1.2MW. The American military users have promised to co-operate with h.f. users to minimize interference which should prove less than that suffered from the Russian "woodpecker" system. . . . The FCC have suspended licences of two American amateurs who have deliberately jammed an amateur net on 14MHz.

PAT HAWKER, G3VA

MICROCOMPUTER LINE PRINTER

Requiring 'hard copy' from a Z80-based microcomputer to aid program compilation, the author obtained a 40-column dot-matrix printer mechanism with a dedicated controller i.c. and designed an interface around them. The result — a cost-effective line printer with few components — lends itself to modification and to other applications.

by P. L. Woods

Generally, and excluding the cassette recorder, a printer is the most useful peripheral for a small computer. Hard copy of program listings or computed results for documentation and dissemination purposes are the first applications that spring to mind, but probably the most interesting aspect of a printer as far as serious microcomputer users are concerned is its value as an aid to program debugging and compilation. It is far easier to find an error in a complete listing on paper than it is from a partial listing on a c.r.t. screen.

Given these merits, it is surprising to find that for some small computers, directly compatible printers are not readily available. Many complete units requiring only a standard serial or parallel interface are available, but for my purposes, they were found too expensive, too large and too heavy. For these reasons I decided to choose one of several bare printer mechanisms now on the market, and design an interface around it.

Of the mechanisms available, many have only between 16 and 20 printing positions, since they are intended for use in cash registers and similar equipment. For

practical listings in Basic or assembly language, more columns are needed. Another variable to take into account when choosing a mechanism is that of paper type. Many drives using thermal or electrosensitive paper are inexpensive, but then again, the paper they use is relatively expensive. The final choice was a plain-paper dot-matrix printer.

Mechanism

The DP-824F-24 is a 24 volt d.c. mechanism capable of printing 40 characters per line on a roll of plain paper 114cm (4.5 inches) wide. This gives a character density of about 12 characters per inch, which is the same as that given by many typewriters. The printer prints 6 lines per inch at about 1.2 lines per second, the actual rate depending on the microcomputer software. Some idea of the quality of printing provided by this unit can be obtained from the listings shown.

In this, and most dot-matrix printers, a

vertical row of seven solenoid-operated needles are drawn across the surface of the paper and carefully timed pulses are sent to the solenoids to leave a pattern of dots on the paper, forming the selected character. A standard (group 24) typewriter ribbon is used in this case. The print head is driven along the line by a motor driven lead screw, while a timing signal derived from a pickup coil driven by this motor ensures a correctly proportioned character. The motor also drives the paper advance mechanism through a series of gears.

The mechanism is quite small, measuring 5.7cm high by 15.8cm wide by 14.7cm long, and can easily be mounted in a small container. My container measures 12.5cm high by 17.5cm wide by 21.5cm long, the extra height being needed to house the solenoid driver circuits in the bottom of the box.

Dot-matrix printers need a character generator to form the pattern of dots for the desired character set. For this mechan-



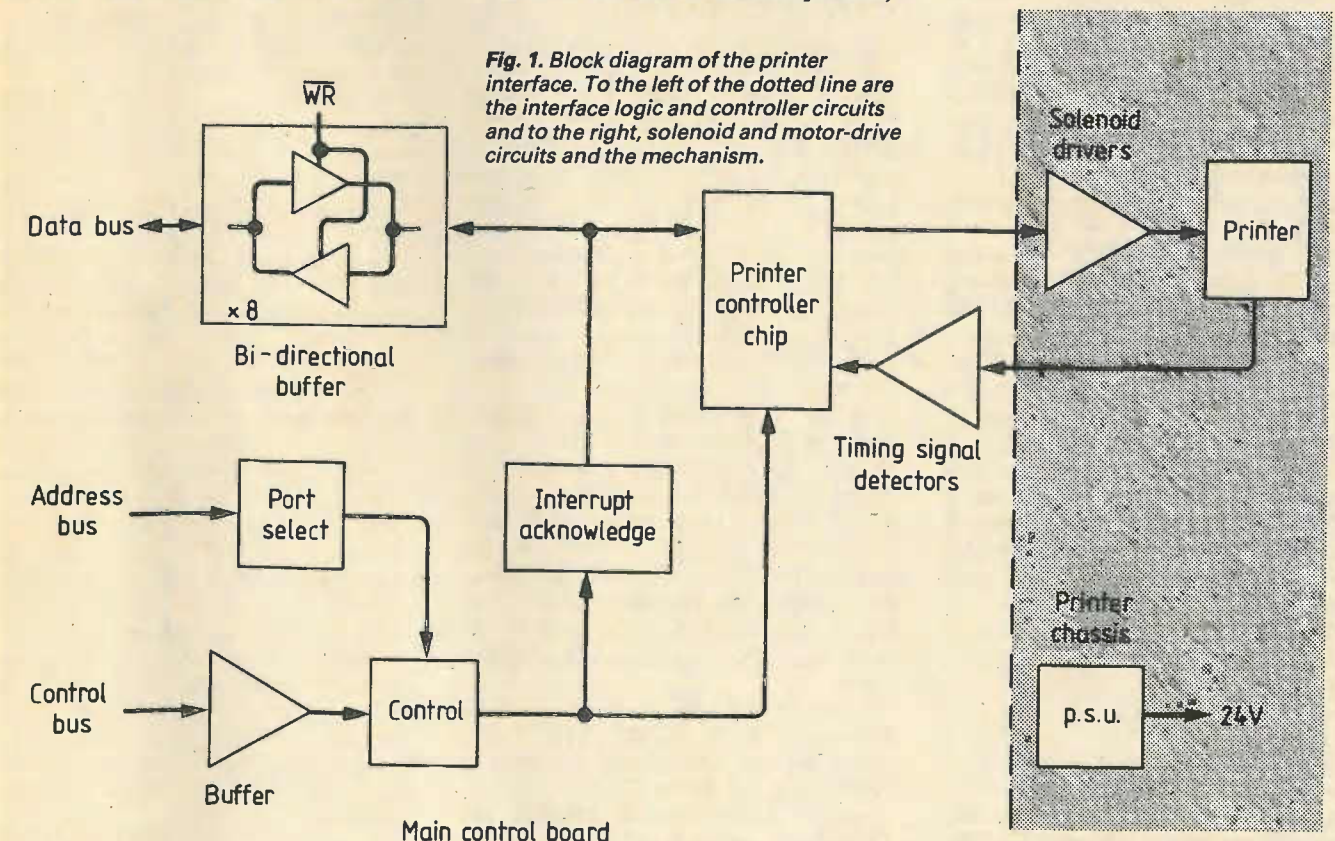


Fig. 1. Block diagram of the printer interface. To the left of the dotted line are the interface logic and controller circuits and to the right, solenoid and motor-drive circuits and the mechanism.

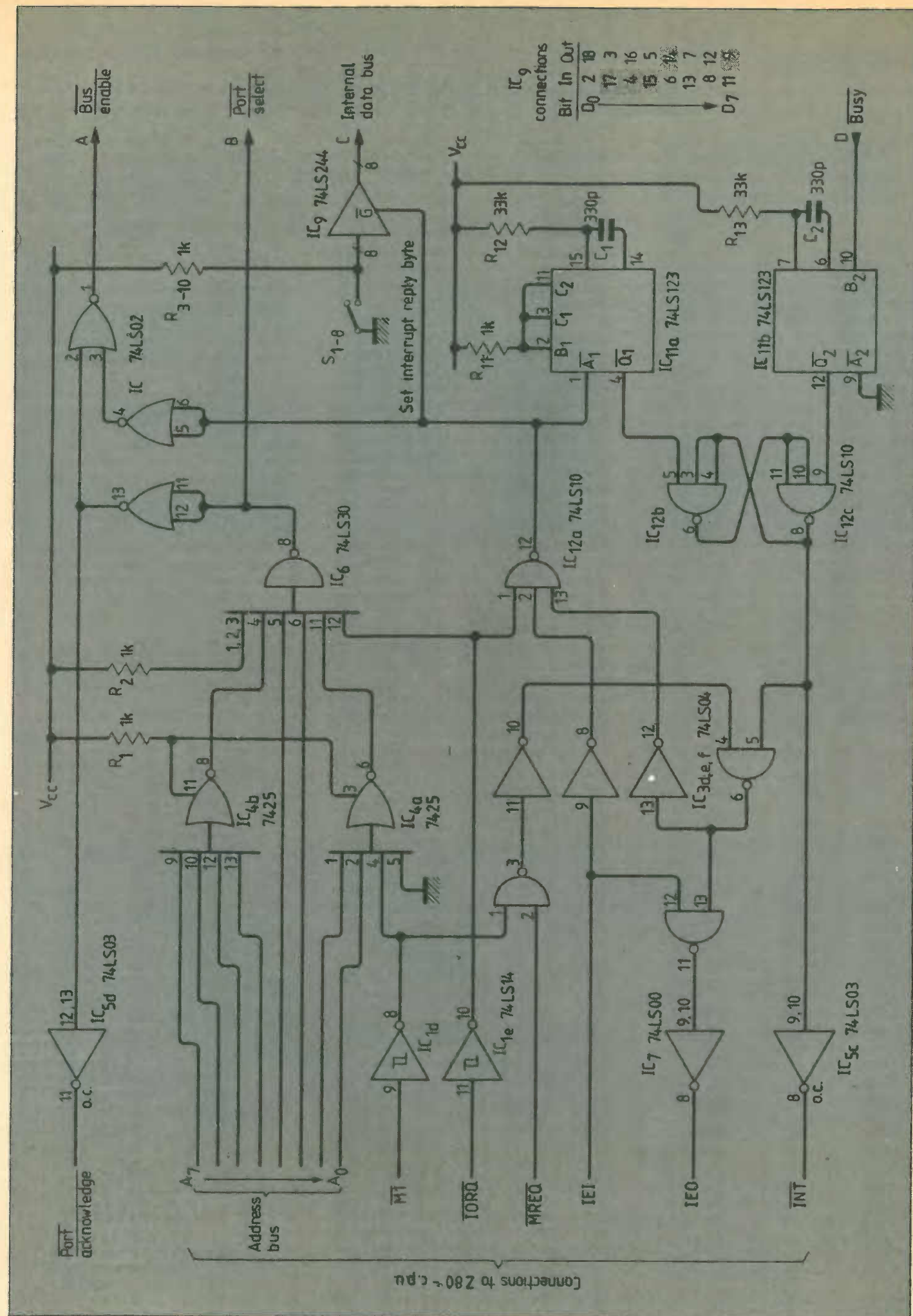

◀ Fig. 2. Port select and interrupt circuits. Address decoding may be varied (see text) and in most situations, the interrupt circuits may be ignored and pin 3 of IC₈ connected to ground.

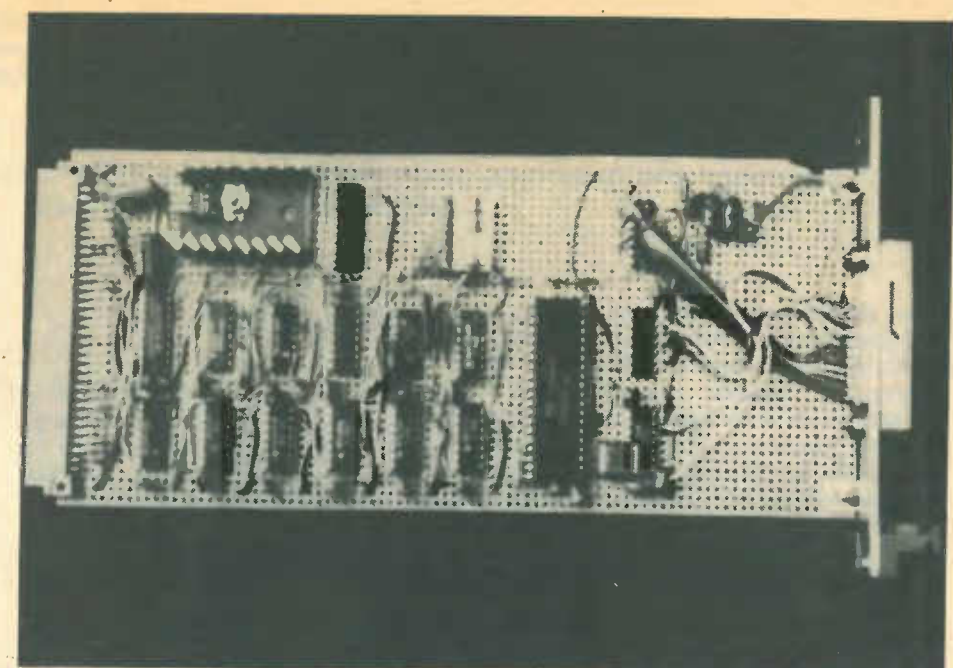Interface board. This circuit serves to connect the printer to the microprocessor. The DIN41612 connector on the left plugs into the back plane of the author's computer system and the signals to and from the printer are conveyed via the 'D' connector at the right. The large integrated circuit in the centre is the printer controller chip.



ism, a matching controller i.c. is available from the same manufacturer. This i.c. also takes care of all the timing, paper feed and character buffering problems associated with driving a printer of this type. A self test facility is also built into the controller.

So, given the controller and mechanism, designing the interface is a simple matter of adapting the microcomputer's bus to suit the requirements of the controller, and providing drive circuits for the motor and solenoids. Here, the interface is designed to accept Z80-bus signals but modifying the circuit to suit other microprocessor buses should not be a difficult task.

Circuit description

Figure 1 shows a block diagram of the interface, separated into two parts by a dotted line. Circuits to the left of the line form the controller and carry low-level t.t.l. signals, while those on the right are for driving the motor and solenoids and thus carry high-voltage/high-current signals. These two sections are kept separate as the current surge caused when all the solenoids are switched at once is around 30A. The driver circuits are mounted in the container with the printer mechanism and connected by a ribbon cable to the controller section, which is kept close to the computer.

Port-select and control logic

A detailed circuit diagram of the controller is shown in Figs 2 and 3. First consider Fig. 2. This is the printer port-select logic, and general and interrupt-control logic. Although designed into the circuit, the interrupt function is not needed to successfully operate the circuit and may thus be omitted.

Z80 (and 8080) devices have input/output instructions to activate their peripherals. Thus the first step in the interface design is to establish whether an i/o instruction is occurring, and whether it is addressing the printer board.

IC₄ and IC₆ perform the address-decoding and port-select functions. Depending on the precise address required for the

printer, the address lines are fed either into one of the two NOR gates, IC_{4a}, IC_{4b}, or into the NAND gate, IC₆. The IORQ signal is active when the current instruction is an i/o instruction, and the MI signal is used for synchronisation purposes.

The controller, as shown, is set to respond to port 0C (hexadecimal), but any other address could be used if needed. Only the least significant lines of the address bus (A0 to A7) are used by i/o instructions. Connect any line of the address bus which must be high when the printer is to be active to an input on the NAND gate, IC₆, and all of the other address lines (A0 to A7) to an input on the NOR gate, IC₄. The circuit is designed such that when the port is selected, the output of IC₆ (pin 8) goes low. This is the Port select signal.

IC_{5d} buffers the Port acknowledge signal on its way back to the microprocessor. My computer's hardware needs this signal but in most cases it will either remain unused or, in systems with a fast microprocessor such as the Z80A or Z80B, used to generate a processor wait signal.

Interrupt logic

The remainder of Fig. 2 is the interrupt handling circuit and comprises IC_{5c}, IC₇, IC₉, IC₁₁, IC₁₂ and S₁-S₈. If unwanted, this section may be omitted, in which case pin 3 of IC₈ is connected to ground.

When the printer controller chip, IC₁₄, becomes idle, a 4µs pulse is generated by IC_{11b} which sets an interrupt request latch formed by IC_{12b} and IC_{12c}. This signal is buffered on its way to the microprocessor by IC_{5c}. When the Z80 microprocessor generates an interrupt acknowledge cycle, IC_{7b} and IC_{7c} will establish the priority chain, and, if selected, will send the output of IC_{12a} (pin 12) low. This enables IC₉ to connect switches S₁ to S₈ onto the internal data bus, and then through IC₂ to the system data bus. Further, IC_{11a} automatically clears the interrupt request latch. Switches S₁ to S₈ are used to set up the interrupt reply byte to the microprocessor

and serve to tell the software that it is the printer that needs attention. The value set on the switches will depend on the system software written, and so is outside the scope of this article. □

To be continued

Componets		Resistors	
Integrated circuits			
1	74LS14	1-11	1k
2	74LS245	12,13	33k
3	74LS04	14,15	1k
4	7425	16	10k
5	74LS03	17	120k
6	74LS30	18	22k
7	74LS00	19,20	4.7k
8	74LS02	21	120k
9	74LS244	101	3.3k
11	74LS123		(8 off)
12	74LS10	201	10k
13	74LS367	202,203	4.7k
14	DPC-2	204	10k
15	74LS14	205	150
16	7406		
17	7406	301	100k
301	7805	302	390
302	741	303,304	1k
Diodes			
101	1N4001	Capacitors	
	(8 off reqd.)	1,2	330p
102	6.2 V, 1 w	3,4	22p
	Zener diode.	5	1n
	(8 off reqd.)	6	100n
301-304	1N4001	7,8	10n
305, 306	1N5402	301	2500µ 25V
307	24 V, 1 W	302	300n
	Zener diode.	303	100n
		304,305	6800µ 25V
		306	500µ 30V
Transistors			
1	BC109	Others	
101	TIP120	XL ₁	6.0 MHz
	(8 off)		(HC25/U)
201, 202	2N3702	Transformer	
203	TIP120		9V, 1A and
204	TIP42A		12V, 2A.
301	BC109		
302	TIP120		

DISC DRIVES

Turning first to how discs are driven, John Watkinson briefly discusses motors, mountings and bearings, and rotation sensing. How and why cooling and filtration techniques are used follows.

by J. R. Watkinson*

Now, after having covered head selection and positioning, we move onto the third dimension of disc access — rotation.

Alignment between read/write heads and data tracks is not only determined by the head positioning system's accuracy. Play in the drive spindle can also cause problems in this area. 'Runout', the term used to describe this phenomenon, becomes more critical as the disc's track spacing decreases, and is usually minimized by the use of axially-preloaded tapered roller bearings on the drive spindle as shown in Fig. 1.

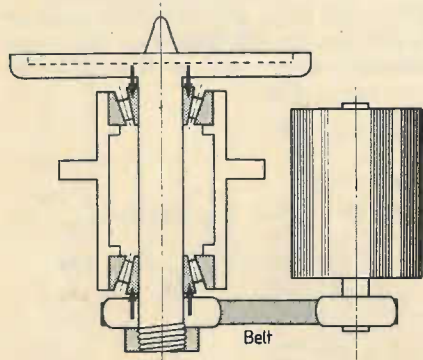


Fig. 1. Axial preload applied to tapered roller bearings takes up all play in the spindle. The motor's speed is frequency dependent, therefore, the domed pulleys on which the flat belt runs are interchangeable for either 50 or 60Hz mains frequencies.

Squirrel-cage type induction motors are most commonly used to drive the spindle. Electrical interference, mechanical noise and physical wear from brush type motors make them unacceptable for this application, and the power required to turn a relatively heavy disc pack at speeds of up to 3600 r.p.m. discounts shaded-pole motors. Two types of spindle motor are often encountered; one, the so called two-phase or capacitor-run motor, has a second winding fed by a phase-advance capacitor to achieve field rotation and the other has an auxiliary starting winding switched in and out by a centrifugal switch.

Larger drives use three-phase motors with windings designed to work at between 200 and 240V, and the windings may easily be configured to suit either 110 or 240V mains supplies.

Almost every spindle is coupled to its motor by a textile-belt and pulley arrangement, the pulleys of which may be changed to suit either 50 or 60Hz mains frequencies and thus compensate for the

motor's speed change. A conductive drive belt may be used to provide a discharge path for static electricity on the motor rotor and for the same reason, a carbon brush is fitted at the end of the spindle.

For several seconds during start up, a motor driving a large multi-platter disc pack may draw 10A from each phase, after which the normal running current is around 1A. Where a number of drives are being used together, an automatic mains switching circuit allows only one drive to be started up at once to avoid mains overload.

A disc pack without some form of braking would turn for several minutes after its motor had been switched off. Often the spindle motor is used as a brake by applying around 50V direct to its windings, Fig. 2, but this can lead to overheating in the motor is frequently stopped and started since the windings heat up on both occasions. Therefore, a thermal switch is often included in the drive circuit.

Rotational position sensing

To position the head for reading or writing, the drive's circuits need to know which cylinder the head is at, as was discussed in the previous article, and which sector is currently under the head. Sector information is usually obtained from a sensor detecting slots cut in either the hub or lower protection platter of the disc pack. There are three main types of sector transducer — one uses light emitting and detecting devices, with the advantage that precise physical tolerances are not required, one relies on varying reluctance, and the last is an eddy-current detector working on the same principle as some metal detectors.

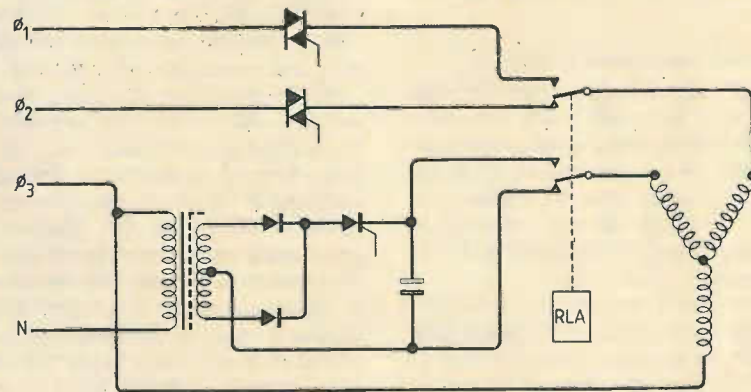


Fig. 2. Three-phase motor control with dynamic braking. Drive power to the motor is controlled by the two triacs, and d.c. braking by the thyristor. The relay only switches when both braking and drive control devices are off. During braking, the d.c. supply floats at the phase voltage since only two phases are triac controlled. The thyristor gate is driven by a reed relay or optical isolator.

Timing of the sector pulse occurring between data blocks is critical because this signal is used to initialize logic circuits for reading a header. There are two ways in which the timing of the pulse may be adjusted, depending on the type of drive. Sometimes a fixed transducer is used and the pulse is varied by altering the setting of a monostable circuit; in other cases, the pulse is varied by moving the transducer tangentially in relation to the disc. Whatever method is used, the adjustment is made using a reference disc pack to ensure that all the drives concerned have exactly the same setting.

Pulses from the transducer increment the sector counter. In Fig. 3, it can be seen that the sector detection disc has a double slot at one point on its circumference. When these slots pass the detector, the timing logic circuit generates a separate pulse to reset the sector counter.

The desired-sector register is loaded from the host c.p.u. as part of the disc address. This register is compared with the sector counter by the disc-control logic. When the two match, the desired sector is located. This process is referred to as a search, and usually takes place after a seek to the desired cylinder. Having found the correct physical block on the disc, the next step is to read the header of that block to confirm that the disc address it contains is the same as the desired address. Following this confirmation the data transfer proceeds. This process will be detailed in the section on disc-control logic.

The sector counter is often accessible by the host c.p.u. as the current-sector register. In a multi-drive system, part of the operating system has to decide in what order to carry out the many data transfers requested. In Fig. 4, two drives are on the correct cylinder, waiting for the desired block to come under the heads. By refer-

ence to the current-sector register in the two drives, the system can decide which data transfer to make first for maximum efficiency. For this reason the current sector register is often called the look-ahead register.

Cooling and filtration

It has been stated that the 'flying height' of the head is very low indeed. Figure 5 shows the relationship between flying height and common contaminants. Air in the vicinity of the disc and head must be totally free from contaminants or serious problems may result. Any particle carried under the head is likely to weld itself in place owing to the high relative speed, then acting as a nucleus for the collection of further debris. In the absence of a regular inspection programme, the build up of debris continues until the flying characteristics of the head are so impaired that contact is made with the disc surface. A regenerative process now begins as the oxide torn from the pack, welded to the head by the heat generated, makes a more effective tool to remove more oxide. This rare occurrence, resulting from neglect, is called a head crash and usually destroys both head and disc.

Most of the heat from the spindle motor, which may be up to 500W, is dissipated in the air surrounding the disc, so some form of cooling is required. Cooling and filtration systems are usually combined as, for example, in the full-flow air system, in which room air is drawn in through a pre-filter to remove large contaminants, such as hair and fluff, and then forced through an absolute filter by the blower. The pores of the absolute filter are so small that nothing much larger than a gas molecule can pass through them.

The filter is made of a special grade of paper, which is corrugated and folded to present a large surface area. Some filters may have a working area of over 20 square feet, and yet are no larger than a cereal packet. The condition of the filter is monitored by measuring the pressure drop across it, typically half an inch of water. Air from the filter passes into the shroud surrounding the disc, from which the only exit is through the e.m.a. As a result the head area is kept clean and heat generated by the disc and the e.m.a. coil carried away.

On some units the blower motor also drives a fan to cool the logic circuits, power supply and servo-amplifier modules. On others the blower motor is dispensed with, and the rotation of the disc itself draws air through the system. In a full-flow system, the environment must be clean if the absolute filter is to have a reasonable service life.

Where a drive is expected to operate in an office environment, a closed-circuit clean air system can be used, in which clean air recirculates through the disc, the positioner and the absolute filter, and through the 'clean side' of a heat exchanger. Room air is blown through the 'dirty side' of the heat exchanger to cool the disc and positioner. Mechanical noise

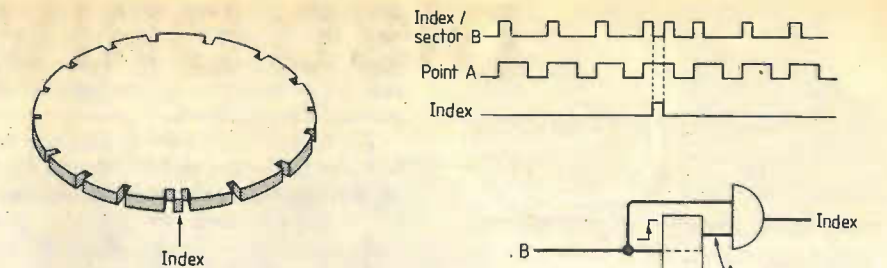


Fig. 3. Pulses indicating sector positions on a disc are derived from slots cut in the edge of the protection platter or in the disc hub. A double slot, detected by the circuit shown, is used to derive a separate pulse for resetting the sector counter.

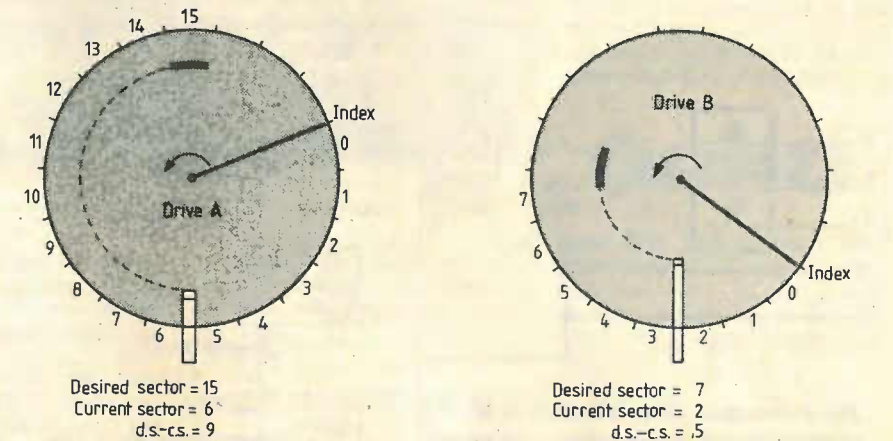


Fig. 4. A comparison between the desired-sector register and the current-sector register tells the logic circuits when the required transfer will take place. Using this information, the system can schedule data transfers from different discs for greater efficiency. In the example shown, it is clear that the data block on the right-hand disc should be read first. Because of this function, the current-sector register is often referred to as the look-ahead register.

from a closed-circuit system is lower than with a full-flow system, a further asset in an office environment. Noise from conventional disc-drive blowers is appreciable, but seldom adds to the existing noise level in a computer room.


Air conditioning is often necessary in computer installations, to carry away the heat dissipated by the equipment and to filter the air. Humidity control is also needed because a low moisture content causes static electricity problems, whereas high moisture content causes dimensional changes to most papers and plastics. The readability of punched cards, paper tape and magnetic tape may be affected.

Dimensions of the disc and the components of the positioner are affected by thermal expansion, and temperature control may be necessary to prevent head/track misalignment. As the drive may take some time to reach thermal equilibrium with its surroundings, manufacturers often specify a maximum temperature gradient for a particular unit. Many air conditioners control temperature by turning on and off the compressor, resulting in temperature steps in the air supply. For this reason disc drives should not be situated close to air conditioner outlets, but should be allowed to take in air which has had the opportunity to mix. When installing a disc-cooling system, thought has also to be given to the airflow requirements of adjacent equipment. Many disc drives take in air at the bottom and exhaust leaves at the top, whereas many processors take in air at the

top and exhaust at the bottom. If the units are badly positioned, used air will recirculate, rather than flow back to the air conditioner.

Power supplies and grounding

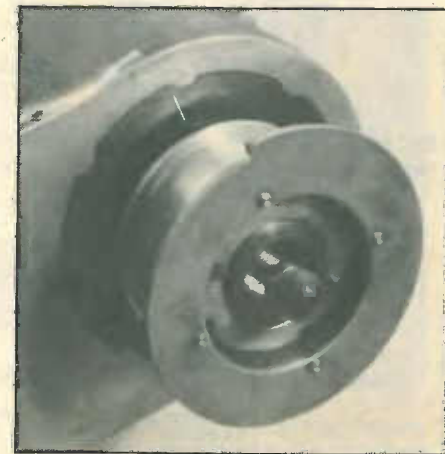A typical disc drive will contain circuits of many different kinds, both analogue and logical, from low-noise linear amplifiers at



Spindle speed and direction of rotation information is provided by a snail cam, shown here, in conjunction with a transducer. At the end of the spindle, a small carbon ground button makes contact with its mating part when assembled to provide a discharge path for static electricity.

*B.Sc., M.Sc., Digital Equipment Co.

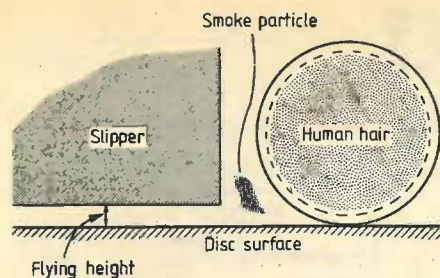


Fig. 5. Common contaminants dwarf the flying height of a typical disc head, illustrating the need for air filtration, clean surroundings and careful handling.

the heads, to high-power e.m.a. drivers; from slow transistor logic to e.c.l. in the serial-binary data channel. Many supply rails are necessary to feed the various component families, Fig. 6.

The signal from a reading head may only be a few millivolts, and in order to ensure reliable operation, the read channel has to be as noise immune as possible. In an earlier article it was explained that the read amplifiers are differential for noise rejection, and the read-write matrix is usually entirely screened for the same reason. The remaining circuits must be designed to cause as little interference as possible.

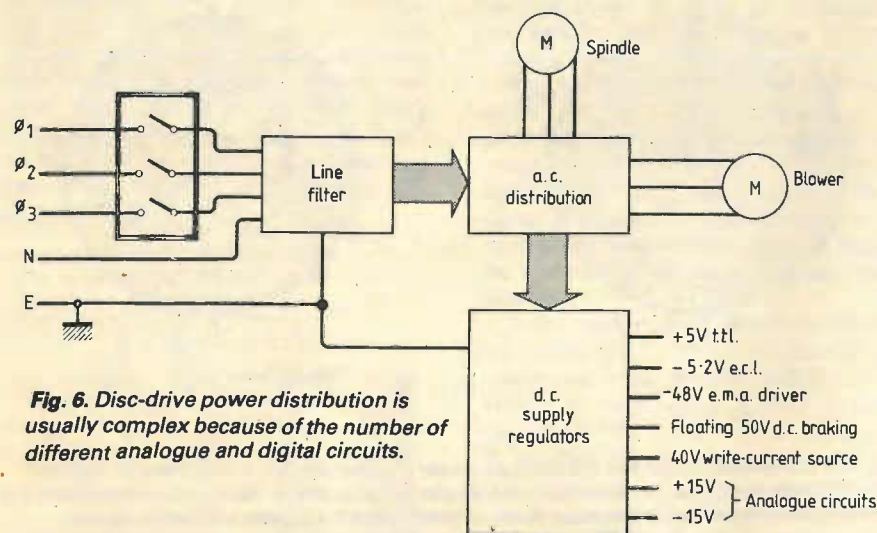


Fig. 6. Disc-drive power distribution is usually complex because of the number of different analogue and digital circuits.

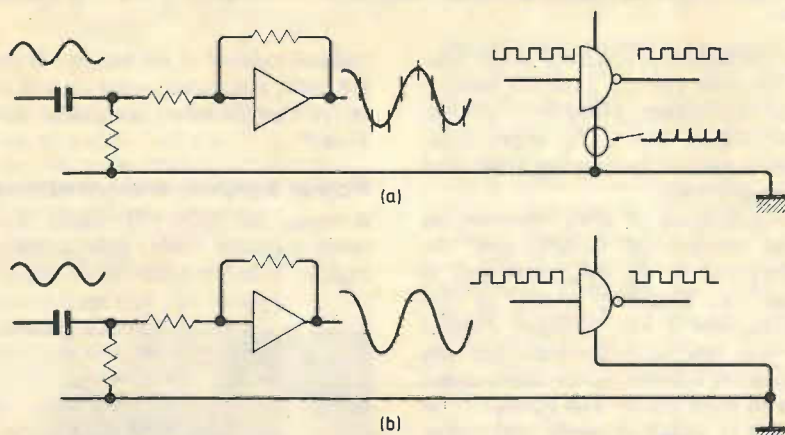


Fig. 7. Incorrect grounding at (a) results in current spikes from the t.t.l. circuit appearing on the analogue output. Separate grounding, as shown in (b), eliminates this problem.

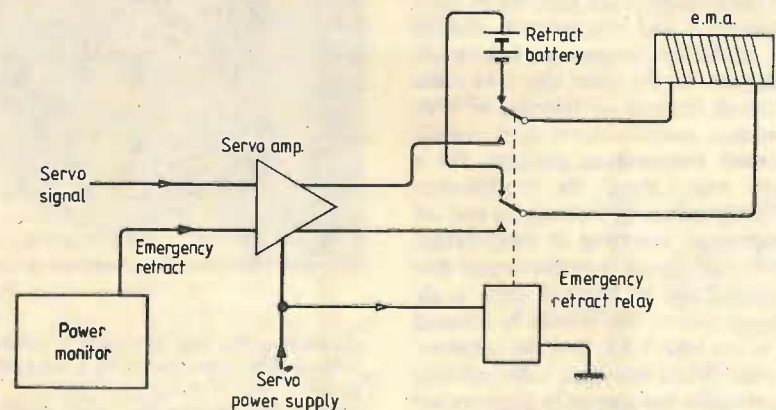


Fig. 8. An emergency retract circuit. In the event of a logic circuit or low-level signal power failure, the positioner retracts by the normal means. Should the power supply to the servo amplifier fail, power is supplied to the retract mechanism by an NiCd battery or, in the case of larger drives, by an electrolytic capacitor.

Switched-mode power supplies are excluded from the disc drives, but pulse-width modulated e.m.a. drivers are acceptable since no data transfer takes place during a seek, and the servo reverts to linear operation during track following.


Linear-circuit supplies usually have current foldback protection, and the circuit can usually withstand the raw supply should the regulator fail. The logic supply, will, however, have an over-voltage crowbar. Some circuit breakers used have a trip coil whereby the drive can turn off its own power in the case of an over-temperature condition or insufficient airflow.

As with all mixed circuitry, the problem of ground return currents must be eliminated by careful design. Figure 7(a) shows analogue and logic signals sharing the same return. Currents from the logic inject noise into the analogue signal owing to the poor layout; Figure 7(b) shows a better layout. Many mixed circuit modules have separate connections for logic ground and analogue ground, which may find their way to the frame through quite different back-plane routes. The usual precautions must be taken with the analogue circuitry to ensure stability, which means, for example, that e.m.a. driver currents must not cause ground potentials in the analogue servo circuit.

In some drives, the grounding is split, the disc, positioner and circuitry being grounded to the host processor, and the frame and spindle motor being grounded to the a.c. supply lead.

Figure 8 shows an emergency-retract circuit used to protect the disc and heads in the event of a supply failure.

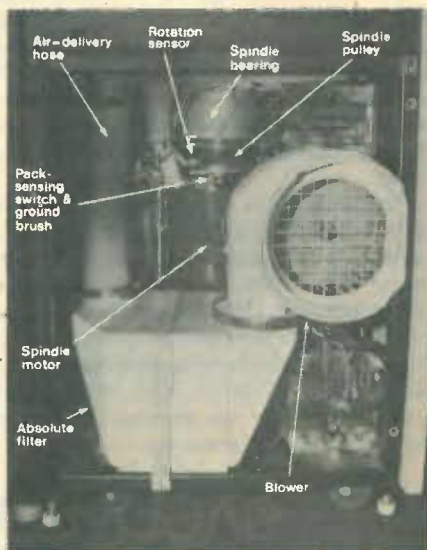Drastic reductions in track spacings, and hence increases in storage capacity, may be made if the read/write head's position is determined by information on the disc surface. Servo systems using these techniques are described in the next article.



An interior view of a multi-platter disc drive showing major rotation and cooling components.

NEW PRODUCTS

DATA ACQUISITION UNITS

These small data-acquisition units are designed for use by engineers and scientists who are not necessarily familiar with computers. Analogue inputs are converted to 12-bit digital information, linearized, and sent to a computer, v.d.u. or printer in serial form as ASCII characters. The linearization process, which may be bypassed, is selectable for J, K, T, S and R type thermocouples, platinum resistance thermometers and square-law sensors; cold-junction compensation is internal but may also be bypassed. Single character commands, in ASCII form may be used to control the data flow through a 20mA loop (RS232 is optional) to the computer. Alternatively, for applications such as data logging, data may be transmitted automatically. Up to 256 units, each with its own address may be connected to a single loop. Field Electronics Ltd, Gill House, Conway Street, Hove, East Sussex BN3 3LW. WW301



peak hold facility may be used to store maximum readings. Up to 200°C, the meter's readings are within 2° of the actual temperature and above 200°, ±1.5%, ±1 digit. Complete with sensor, the thermometer costs £445. ProLab Instruments Co., Greenside House, Lisle Way, Emsworth, Hants P010 7XN. WW303

PRINTER BUFFER/INTERFACE

Most microcomputers may not be used while they are sending information to a printer. If the printer is slow, or the amount of hard copy required large, a buffer memory may be used to take information from the computer quickly and send it out to the printer slowly, leaving the computer free. Sprinter, from Mutek, is such a buffer with RS232, Centronics and IEEE inputs and outputs that may be used in any combination. Protocol conversion, from say ASCII to Telex or TTS photo-typesetting code, is possible and the unit may be used as an interface-standard converter. With 32K of buffer memory, the Sprinter costs £255 excluding v.a.t., or with 16K, £185. A 6502 microprocessor running at 2.4MHz is used in the unit. Mutek, Quarry Hill, Box, Wilts. WW302

INFRA-RED THERMOMETER

A non-contact thermometer with an infra-red sensing device, from ProLab instruments, can be used to measure temperatures from 50 to 750°C, with a resolution of 1°C. The meter has a thermocouple input so adjustments may be made to suit the emissivity of the material being measured; the thermocouple range is 0 to 700°C. A 1mV/digit analogue output is provided and a

GRAPH SOFTWARE

As a follow up to their recently introduced software for solving mathematical problems, ISM have brought out Graphmagic, a program which turns mathematical data into graphs or diagrams. Pie charts, line graphs and bar graphs are among the examples given. At the moment, the graph software can only be run on the Apple computer but there are plans to adapt the program to run on the IBM personal computer and with CP/M. Mathmagic, however, is available for Apple, TRS80, and IBM personal computers and for use with any Z80-based microcomputer

running CP/M. International Software Marketing, Hayden House, 5-6 Millmead, Guildford, Surrey GU2 5BZ. WW304

64K DYNAMIC R.A.M.

Plastic-packaged 64K r.a.ms for industrial use are available from Hitachi in 150 or 200ns access time versions. The HM4864P may be used as a direct replacement for conventional ceramic-packaged types and costs £6.89 or £6.47 in 10-off quantities for the 150ns and 200ns types respectively. Hitachi (UK) Ltd, Hitec House, 221-225 Station Rd, Harrow, Middx. WW305

WIDEBAND ANTENNA

A relatively small 50W wideband antenna with a frequency range of 150 to 2000MHz is produced by Applied Communications. With a gain approximately equal to a half-wave dipole, the 9014 has circular polarization and is suitable for both, receiving and transmitting. The manufacturers claim that the antenna may be used with frequencies from 70 to beyond 3000MHz. With its fibre-glass housing, the 9014 measures 650 by 600 by 40mm and weighs 5.5kg. Applications in-



clude wideband laboratory measurements and general surveillance. Applied Communications (UK), Tower Street, Coventry CV1 1JP. WW306

TO-3 INSULATING PLATE


Usually, four plastic washers are required to keep a TO-3-packaged transistor's leads and mounting screws electrically isolated from its



heat sink. Richco International have introduced a glass-filled nylon plate that will replace these four shoulder washers. Richco International, West Street, Erith, Kent DA8 1AA. WW307

P.C.B. PROTOTYPING AID

Boards fitted with numerous pillars are the heart of BICC-Vero's Speedwire system. On the component side of the board, these pillars form selectively gold-plated contacts into which the leads of i.c.s or discrete components may be inserted. Each pillar is terminated by an insulation displacing time for point-to-point wiring on the underside of the board; the tines are reusable and can accept two wires.

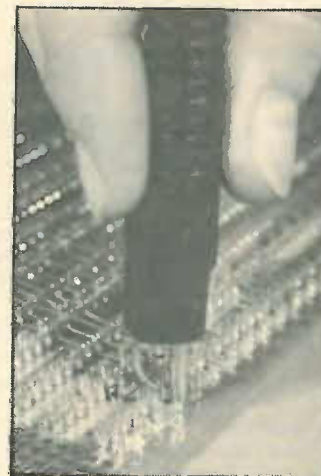

Initially, two kits are being offered. One kit contains a 100 by 160mm Eurocard board, a wiring pen and wire, and contacts with a manual insertion tool. A more comprehensive kit comprises a plated-through-hole Eurocard fitted with contacts, wiring pen and wire. BICC-Vero Packaging, Industrial Estate, Chandlers Ford, Eastleigh, Hants SO5 3ZR. WW308

NEW PRODUCTS

HARMONIC SCALES

Digital displays are accurately readable, can contain as many digits as the associated electronics can support and give the impression (though not always the reality) of authority. For many purposes they are ideal: for others they cannot be used at all. If the reading changes, the display can be confusing and gives a poor indication of the direction of change, its speed or of what proportion of full scale the reading occupies. In these circumstances, an analogue indicator of some kind is a great deal more informative, so that the use of two meters is the ideal.

In a development claimed by Sifam to be unique, both kinds of indicator are used in one instrument. The Harmony is a multi-purpose meter which possesses the usual kind of liquid-crystal, numerical display (albeit in several colours), but with an associated bar indicator on the same panel. Measurement accuracy is the province of the digital readout, the function of the bar being to indicate the reading fairly coarsely, following changes to show the direction and rate of change and the position of the digital reading against a background of full scale. The bar can be left, right, centre or offset zero, and both displays may be of the suppressed-zero type.


By means of a built-in microprocessor and e.p.r.o.m., the meter can be used for a variety of functions, can display any desired unit, and can cope with non-linear characteristics. Relevant information on range, units in use, decimal-point position and function selected appears on the display.

Harmony is made by Sifam Ltd, Woodland Road, Torquay, Devon TQ2 7AY and costs £35 in small quantities.

WW309

BRIGHT LEDS

Seven-segment l.e.d. displays giving light outputs in excess of 5mcd at 10mA/2V are available through IMO Electronics. Both common-anode and common-cathode types are available in heights of 8, 10, 12.5 and 15mm. Pin spacings of the 6000 series displays conform to the standard 0.1in matrix. These displays are "ten times brighter than other manufacturers' equivalents", and "have an unsurpassed uniformity of brilliance", claims the distributor. IMO will not say who manufactures these leds, but they assure us that they are made in Japan. We encountered exactly the same response when we approached the blue led's distributors (WW, May) but we are almost certain that there are only two major Japanese

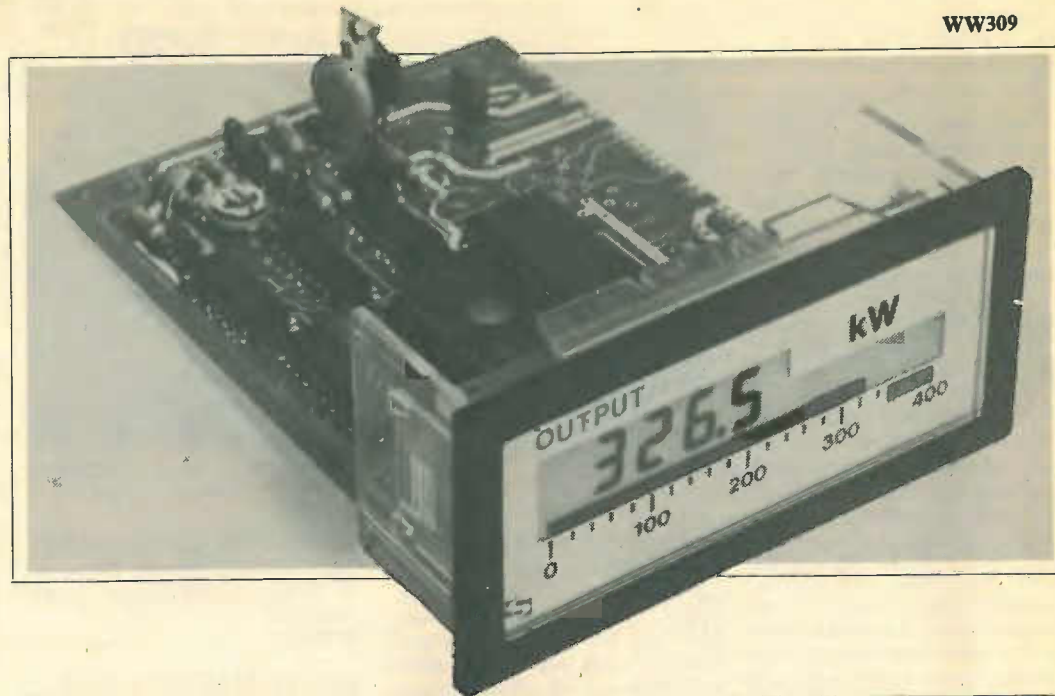


WW309

manufacturers making blue leds - Matsushita and Sanyo (neither UK subsidiary has these blue leds or any knowledge of a deal). Finding out who might manufacture these seven-segment displays is going to be a harder task. IMO Electronics Ltd, 1000 North Circular Road, Staples Corner, London NW2 7JP.

WW310


16K STATIC R.A.M.

A second-source device, the MV5516 c.m.o.s. static r.a.m., is the first large-scale integration memory to appear from Plessey Semiconductors. The manufacturers say that their 2K by 8-bit word memory will be attractive to UK buyers requiring large quantities and reliable after-sales back up. Two chip-enable inputs are used, one for memory access in 250ns and the second, for 0.25µW power consumption in standby mode. While operating, the device consumes

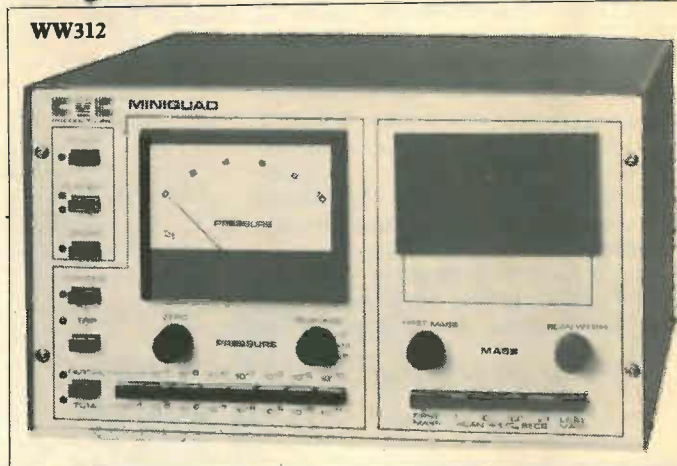

around 200mW. The 24-pin package has the same configuration as the 2716 e.p.r.o.m., and its outputs and inputs are t.t.l. compatible. Plessey Semiconductors Ltd, Cheyney Manor, Swindon, Wilts SN2 2QW.

WW311

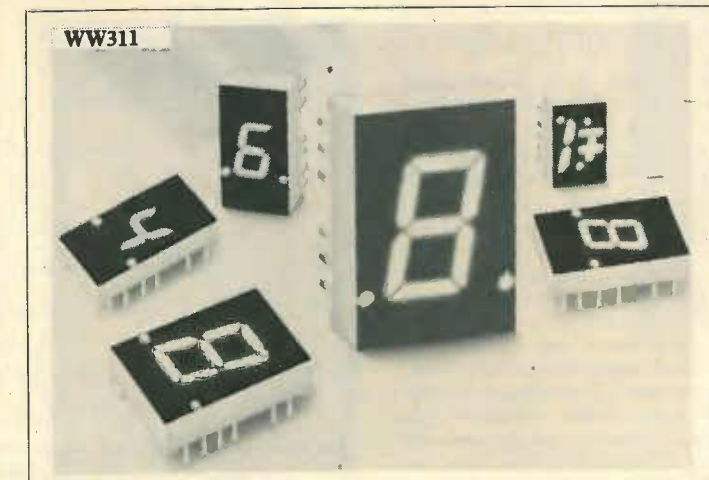

WW311

RESIDUAL-GAS ANALYSER

Sputtering-vacuum impurities cause problems in semiconductor manufacturing processes. According to CVC, manufacturers of the Miniquad gas analyser, total-pressure gauges often used to judge impurities in this application have limitations in that they are not capable of measuring individual residual gases accurately. Their instrument will detect partial pressures of all gases of interest and can be used to initiate a sputtering process automatically once a desired partial pressure has been reached. Besides gas analysis, the apparatus aids detection of leaks, vacuum fingerprinting and impurities. Detector heads are interchangeable so the unit may be used for monitoring in different types of system. CVC Scientific Products Ltd, Eastheath Avenue, Wokingham, Berks RG11 2PW.

WW312

DP-824-24 PRINTER KIT SPECIAL OFFER SAVE £33.89 (UK ONLY)



To compliment the excellent article in this issue of Wireless World, Roxburgh Printers Ltd are making an offer of:

- 1pc DP-824F-24 Printer Mechanism
 - 1pc DPC-4A Controller Chip
 - 1pc 82910180 Paper Tear Bar
 - 1pc 8002 Paper Roll Holder
 - 1pc 114080-RO-000-SP-P Paper Roll
- Normal price with carriage and VAT would be £119.38
Offer price inclusive of carriage and VAT is **£85.49**

Cheques should be made payable to Roxburgh Printers Ltd.



If you would like further data on this or the complete range of Printers and Interfaces, please contact us.

WW - 069 FOR FURTHER DETAILS

RUSH Cleaning Brushes for Gold Edge Connectors

A long lasting brush where a light brushing action will remove oxidation, dirt, grease, etc., and polish the gold surface without reducing the thickness of the gold plating, or damaging the work surface. The brushes are manufactured from pure spun glass and will not alter the electrical properties of the surface or leave any contamination. No need for solvents etc.




Eraser International Ltd.,
Unit M, Portway Industrial Estate,
Andover, Hants SP10 3LU.
Tel: Andover (0264) 51347/8 Telex: 477291

WW - 067 FOR FURTHER DETAILS

LION TELETEXT PRESTEL ADAPTOR

why buy two separate adaptors when one will do?

★ PRESTEL

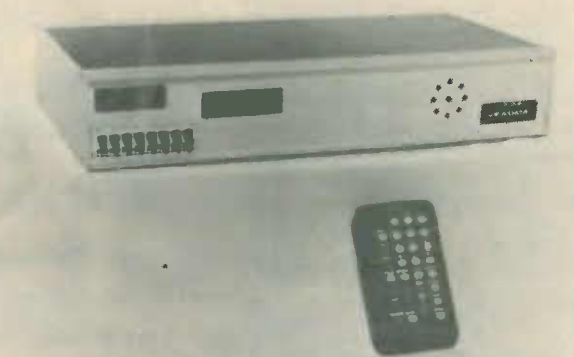

★ TELETEXT

Our adaptor has the plug-in Lion Teletext or Prestel and Teletext board which is used in our Television TXV 56 and our Ferguson Colourstar adaptor. Features include: full infra-red remote control, printer facility, full alphanumeric keyboard or microcomputer input, cassette recording output, autodial of Viewdata numbers, eight-page memory option, local editing facility and many other features.

Realistic Prices:
AXV03 £250 AXV04 £199 (Teletext only)
**LION TV, 18 HARCOURT TERRACE
LONDON SW10. 01-373 5218**

WW - 072 FOR FURTHER DETAILS

HEMMINGS ELECTRONICS AND MICROCOMPUTERS

16 BRAND ST
HITCHIN
HERTS
SG5 1JE

Tel: (0462) 33031
Shop open Mon.-Sat. 9 a.m.-5.30 p.m.
Closed all day Wednesday



Professional quality electronic components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/POs or Banker's Draft with order, payable to Hemmings Electronics Ltd.

Official orders from schools, colleges and universities welcome. Trade and export enquiry welcome.

P.&P. add 60p to all orders under £10. Telephone your Access orders, using our 24-hr. Anaphone service.

VAT - All prices exclusive of VAT - Please add 15% to total cost including P.&P. No VAT on export orders or books.

74LS TTL	LS138	35p	LS373	75p	4035	90p	4522	110p	LM339	55p	BC307C	15p	TIP31B	48p	2N2904A	30p	88840	820p	
LS00	LS139	37p	LS374	75p	4038	120p	4526	110p	LM348	80p	BC308	15p	TIP31C	55p	2N2905	30p	8844	125p	
LS01	LS145	85p	LS375	45p	4040	50p	4527	110p	LM358	60p	BC308A	15p	TIP32	50p	2N2906A	30p	8845	75p	
LS02	LS151	40p	LS377	75p	4042	62p	4528	90p	MC1465	66p	BC308B	15p	TIP32A	50p	2N2907A	25p	8850	165p	
LS03	LS153	40p	LS378	75p	4043	70p	4529	120p	MC1458	135p	BC308C	15p	TIP32B	60p	2N3053	30p	8852	250p	
LS04	LS155	40p	LS379	65p	4044	70p	4530	90p	MC1458	45p	BC309	15p	TIP32C	60p	2N3054	70p	8854	75p	
LS05	LS156	40p	LS385	260p	4046	65p	4531	95p	MC3302	95p	BC309C	15p	TIP33	65p	2N3055	50p	8854	75p	
LS08	LS157	35p	LS386	45p	4049U	20p	4532	120p	MC3401	65p	BC327	15p	TIP33A	65p	2N3439	80p	8795	485p	
LS09	LS158	35p	LS387	45p	4051	72p	4536	290p	MC3456	107p	BC337	15p	TIP33C	75p	2N3440	80p	8796	105p	
LS10	LS160A	42p	LS390	85p	4050	28p	4534	480p	MC34001	58p	BC338	15p	TIP34	75p	2N3771	180p	8797	105p	
LS11	LS161A	42p	LS395	150p	4052	72p	4538	105p	NE555	18p	BCY70	20p	TIP34A	75p	2N3772	180p	8798	105p	
LS12	LS162A	42p	LS398	130p	4053	72p	4539	105p	NE555	18p	BCY70	20p	TIP34B	75p	2N3773	250p	8728	140p	
LS13	LS163A	42p	LS399	120p	4060	60p	4541	110p	NE556	45p	BCY71	20p	TIP34C	90p	2N3821	120p	8080A	360p	
LS14	LS164	45p	LS400	120p	4066	30p	4543	120p	NE556	155p	BCY72	20p	TIP34D	90p	2N3822	120p	8085A	595p	
LS15	LS165	70p	LS401	105p	4068	18p	4544	176p	NE567	140p	BD135	48p	TIP35	180p	2N3823	95p	8155	880p	
LS20	LS166	80p	LS41	105p	4069U	18p	4547	130p	SN76477	175p	BD136	48p	TIP36	180p	2N3904	15p	8224	200p	
LS21	LS168	120p	LS42	105p	4070	20p	4549	380p	TL061	60p	BD140	45p	TIP36A	175p	2N3905	15p	8226	275p	
LS22	LS169	120p	LS43	105p	4071	20p	4551	105p	TL062	60p	BD165	45p	TIP36B	175p	2N3906	15p	8228	250p	
LS26	LS170	120p	LS44	105p	4072	20p	4553	295p	TL064	98p	BD166	45p	TIP36C	175p	2N4400	20p	8255	300p	
LS27	LS173	70p	LS441	105p	4073	20p	4554	165p	TL071	30p	BD166	45p	TIP36D	175p	2N4401	25p	8257	800p	
LS28	LS174	63p	LS42	105p	4075	20p	4555	70p	TL072	50p	BD169	45p	TIP36E	175p	2N4402	25p	8259	800p	
LS30	LS175	55p	LS43	105p	4076	85p	4556	75p	TL074	100p	BD170	45p	TIP35C	185p	2N4403	25p	8279	950p	
LS32	LS181	125p	LS44	105p	4077	20p	4557	290p	TL081	25p	BD177	80p	TIP41	55p	2N4410	45p	MC1408	295p	
LS33	LS182	120p	LS45	105p	4078	20p	4558	125p	TL082	45p	BD678	80p	TIP41A	55p	2N4411	45p	MC1488	80p	
LS37	LS183	120p	LS46	105p	4081	20p	4559	410p	TL084	95p	BD679A	80p	TIP41B	60p	2N4412	45p	MC1489	80p	
LS38	LS190	160p	LS47	105p	4082	20p	4560	180p			BD680A	80p	TIP41C	60p	2N4413	45p	MC3459	265p	
LS40	LS191	80p	LS48	105p	4093	40p	4561	100p			BY51	25p	TIP41D	60p	2N4414	45p	7812	80p	
LS42	LS192	80p	LS49	105p	4094	120p	4562	395p			BY51	25p	TIP42	80p	2N4415	45p	7814	65p	
LS43	LS193	80p	LS50	105p	4095	110p	4562	395p			BY51	25p	TIP42A	80p	2N4416	45p	7814	65p	
LS44	LS194A	45p	CMOS 4000B	4160	80p	4568	280p			BC107	12p	BY51	25p	TIP42B	75p	2N4416	45p	7814	65p
LS48	LS195A	45p	4000	14p	4161	80p	4569	170p			BC107B	15p	TIP42C	75p	2N4416	45p	7814	65p	
LS49	LS196	65p	4001	14p	4162	80p	4572U	38p			BC108	12p	TIP42C	75p	2N4416	45p	7814	65p	
LS54	LS197	65p	4001U	14p	4163	80p	4580	395p			BC108B	15p	TIP47	60p	2N4416	45p	7814	65p	
LS55	LS221	55p	4002	14p	4174	80p	4581	240p			BC109	12p	TIP48	60p	2N4416	45p	7814	65p	
LS73A	LS240	80p	4002U	14p	4175	100p	4582	65p			BC109B	15p	TIP49	50p	2N4416	45p	7814	65p	
LS74A	LS241	80p	4006	65p	4194	100p	4583	105p			BC109C	15p	TIP50	48p	2N4416	45p	7814	65p	
LS75	LS242	80p	4007	18p	4433	820p	4584	50p			BC117	25p	TIP110	30p	2N4920	30p	2N4920	30p	
LS76A	LS243	80p	4008	65p	4433	390p	4585	35p			MJE3055	65p	TIP111	75p	2N4921	105p			
LS77	LS244	80p	4011	14p	4447	390p	4585	35p			MJE3055	65p	TIP112	80p	2N4922	95p			
LS78A	LS245	95p	4011U	14p	4493	320p	4588	295p			MFP102	45p	TIP115	40p	2N4923	95p			
LS83A	LS251	40p	4012	18p	4494	320p	4589	295p			MPS2369	25p	TIP116	73p	2N5190	75p			
LS85	LS252A	40p	4012U	18p	4495	320p	4589	295p			MPS3640	30p	TIP117	45p	2N5191	75p			
LS86	LS255	35p	4013	33p	4495	320p	4410	625p			MPS3640	30p	TIP120	39p	2N5192	75p			
LS89	LS257A	35p	4014	70p	4501U	25p	4411	450p			MPS3640	30p	TIP121	100p	2N5192	75p			
LS90	LS258A	42p	4015	85p	4502	89p	44115	426p			MPS3640	30p	TIP122	99p	2N5193	40p			
LS91	LS258	80p	4016	35p	4503	80p					MPS3640	30p	TIP125	45p					
LS92	LS260	22p	4017	48p	4504	100p					MPS3640	30p	TIP126	60p					
LS93	LS266	22p	4018	65p	4506	68p					MPS3640	30p	TIP127	45p					
LS95B	LS272	80p	4020	65p	4508	240p					MPS3640	30p	TIP128	45p					
LS107A	LS273	80p	4021	72p	4510	75p					MPS3640	30p	TIP129	45p					
LS109A	LS278	80p	4022	70p	4511	75p					MPS3640	30p	TIP130	45p					
LS112A	LS283	45p	4023	16p	4512	75p					MPS3640	30p	TIP131	45p					
LS113A	LS290	45p	4023U	16p	4513	75p					MPS3640	30p	TIP132	45p					
LS114A	LS293	45p	4024	18p	4514	180p					MPS3640	30p	TIP133	45p					
LS122	LS295A	95p	4025	18p	4515	180p					MPS3640	30p	TIP134	45p					
LS123	LS298	90p	4025U	18p	4516	180p					MPS3640	30p	TIP135	45p					
LS125A	LS352	95p	4027	37p	4517	250p					MPS3640	30p	TIP136	45p					
LS126A	LS353	95p	4028	40p	4518	56p					MPS3640	30p	TIP137	45p					
LS132	LS368A	40p	4029	80p	4519	36p					MPS3640	30p	TIP138	45p					
LS133	LS368A	40p	4032	120p	4520	80p					MPS3640	30p	TIP139	45p					
LS136	LS367A	40p	4034	165p	4521	195p					MPS3640	30p	TIP140	45p					
LS137	LS368A	45p									MPS3640	30p	TIP141	45p					

WW - 059 FOR FURTHER DETAILS

pantechnic

THE POWERFET SPECIALISTS

POWERFET AMPLIFIER MODULES

The people at Pantechnic have been designing with powerfets since they first became commercially available. Their experience of powerfet amplifiers, coupled with their insight into the sources of non-linearity often neglected by others, has resulted in a new range of powerfet amplifiers that are fast, tough, linear and cheap.

MODEL	POWER RANGE (Continuous RMS)	TYPICAL LOADS	NOTES
PFA 100	50W-150W	4Ω, 8Ω	Physically small 26mm x 76mm x 108mm High Watts per £ ratio
PFA 200	100W-300W	4Ω, 8Ω	25A continuous output current
PFA 500	250W-600W	2Ω, 4Ω, 8Ω	5dB dynamic headroom Drives 70V line direct
PFA HV	200W-300W	4Ω, 8Ω, 16Ω	

- Key features:
- 1) RELIABLE - Powerfet freedom from thermal runaway and secondary breakdown
 - 2) LINEAR - TID zero, IM/THD < 0.01% (full power, mid band THD down to 0.0015%)
 - 3) FAST - Slew rate > 30V/μs, (45V/μs type)
 - 4) QUIET - Signal to noise ratio 120dB
 - 5) BRIDGEABLE - (100, 200, 500 without extra circuitry)
 - 6) STABLE - Unconditionally
 - 7) LOW COST - 10watts to 20watts per £, depending on model and quantity

As they stand these modules suit most P.A. and industrial applications and satisfy all foreseeable audiophile requirements. (The HV is aimed at digital audio.) Where aspects of performance fail to meet specific requirements (e.g. in speed or power) low cost customising is often a possibility. Alternatively entirely new boards can be produced.

Pantechnic make more than just PFAs. Loudspeaker protection boards and the quietest, lowest distortion preamp boards currently available are just two of an ever-expanding range.

Pantechnic sell high quality power supply and other components at excellent prices.

CHECK US OUT

Price and Delivery
PANTECHNIC (Dept WW7)
17a WOOLTON STREET
LIVERPOOL L25 5NH
Tel. 051-428 2651

Technical Enquiries
contact
Phil Rimmer
on
01-800 6667

WW - 065 FOR FURTHER DETAILS

RADFORD

Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.

10 BEACH ROAD
WESTON-S-MARE, AVON BS23 1AU
TEL. 0934 416033

WW - 066 FOR FURTHER DETAILS

MICROPROCESSOR APPLICATIONS HANDBOOK

by D. F. Stout £31.00

Electronic Components and Systems by W. H. Dennis £13.50
The Electronic Office by D. Jarrett £13.50
H/B of Semiconductor and Bubble Memories by W. A. Triebel £19.70
Practical Techniques of Electronic Circuit Design by R. L. Bonebreak £25.00
Digital Integrated Electronics by H. Taub £9.95
Electronic Devices and Circuit Theory by R. L. Boylestad £10.95
The Soul of a New Machine by T. Kidder £8.50

★ PRICES INCLUDE POSTAGE & PACKING ★

THE MODERN BOOK CO

Specialist in Scientific and Technical Books

15/21 Praed Street, London, W2 1NP


PHONE: 01-402 9176 - Closed SATURDAY 1 p.m.

Please allow 14 days for reply or delivery

WW - 07

HART

LINSLEY HOOD CASSETTE RECORDER 2

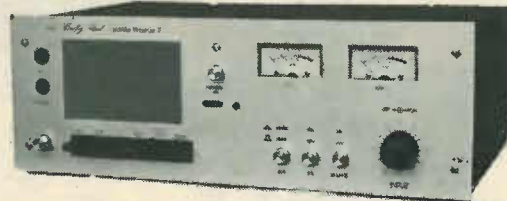

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother-and-daughter arrangement used on our Linsley-Hood Cassette Recorder 1.

This latest version has the following extra features: Ultra low wow-and-flutter of .09% - easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto-stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents rerecording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest. £94.90 + V.A.T. we ask for the complete kit.

LINSLEY-HOOD CASSETTE RECORDER 1



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily-built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our latest HS 16 Sendus Alloy super head, available separately at £8.20 but included free with the complete kit at £75 plus VAT.

Reprints of the 3 original articles describing this design 45p. No VAT.
Reprint of the subsequent postscript article 30p. No VAT.

PRACTICAL WIRELESS 'WINTON' TUNER

Brilliant new Ted Rule designed Tuner with everything! Gives you fantastic stereo f/m reception with pilot cancelling decoder i.c., fluorescent display, digital frequency readout along with clock and timer functions. In addition to f.m. covers l.w., m.w., s.w. and even TV sound. Further details are in our lists; send for your copy.

Part Cost of Post, Packing and Insurance
Order up to £10-50p
Orders £10 to £49-£1 P&P Export Orders - Postage or shipping at cost plus £2 Documentation and Handling
Over £50-£1.50

Please send 9 x 4 S.A.E. or telephone for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on Oswestry (0691) 2894.

AUDIO SIGNAL GENERATOR FIRST-CLASS PERFORMANCE AT VERY LOW COST



Distortion below .002%
10Hz/100 KHz
£41.60
(Model 149)


+ P.P. £2.25

1v RMS
Output, Attenuated
Sine/Square Wave
(Kit £35.65)
(Model 146)

Also available with frequency readout meter. Send for lists on function gen, THD meters, millivoltmeters, etc.

Based on Linsley Hood designs
TELERADIO ELECTRONICS, 325 FORE STREET, LONDON N9 0PE
Telephone 01-807 3719 Closed Thursdays

LINSLEY-HOOD 300 SERIES AMPLIFIERS

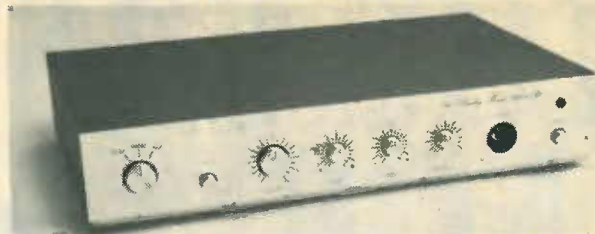

These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform, on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design.

Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2.

As with all Hart kits the constructors interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction.

Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment.

30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits £72.

35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits, £87.40.

45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £94.80.

(Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT.
Reprints of MOSFET article 25p. No V.A.T. Post free.

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 60p postage.

CASSETTE HEADS

HS16 SENOST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data £8.20
HC20 Stereo Permalloy R/P head for replacement uses in car players, etc £4.25
HM80 Stereo R/P head for METAL tape. Complete with data £7.20
HS61 Special Erase Head for METAL Tape £4.90
HS24 Standard Ferrite Erase Head £1.50
4-Track R/P Head. Standard Mounting £7.40
R484 2/2 (Double Mono) R/P Head. Std. Mtg £4.90
ME15 1/2 Ferrite Erase. Large Mtg £4.25
CCE/8M 2/2 Erase. Std. Mtg £7.90

All prices plus VAT

HART

HART ELECTRONIC KITS LTD
OSWESTRY
SHROPSHIRE
phone (0691) 2894
Telex 35661
Hartel G

INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol £2.50 (30p) Developer £0.30 (15p)
Ferric Chloride £0.60 (45p) Acetate Sheet £0.15 (15p)

Copper-clad Fibre-glass Boards: Single-sided £2 ft. sq. (45p)
Double-sided £2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:
8"x4 1/2" £1.75 (25p) 16"x9" £7 (60p) 24"x18" £18 (£1.70)
8"x9" £3.50 (45p) 24"x12" £13 (£1.20) Eurocard £1.25 (25p)

Double-sided Board (all sizes) add 20%
Postage individual items in brackets. Maximum charge £2 per order.

WHITE HOUSE ELECTRONICS
P.O. Box 19, Praa Sands, Penzance TR20 9TF
Telephone: Germoe (073-676) 2329

Toroidal Transformers



THE COTSWOLD
"BUDGET RANGE" OFFERS
BUILT-IN QUALITY COUPLED
TO A RELIABLE
DELIVERY SERVICE
MOST TYPES
FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Budget Range Stockist
BARRIE ELECTRONICS LTD.
3 The Minories, London EC3N 1BJ. 01-488 3316

Cotswold Electronics LTD.

Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX
Tel: 0242-41313 Telex: 897106

WW - 078 FOR FURTHER DETAILS

Chiltern Electronics

B.C.M., Box 8085, London WC1N 3XX. Tel: 0494 714483

MAIL ORDER BARGAINS
All prices include VAT and Postage - Same-day despatch

PROFESSIONAL ASCII KEYBOARDS

Beautiful 75-key ASCII encoded keyboards in very attractive case. Reed switch keys, all control keys, and 8 LED status indicators. Single 5v rail, all TTL encoding. Complete with circuit. List price £475.
Our price New £46. Or slightly used £34.50

GOULD SWITCH-MODE POWER SUPPLIES, 5v 20 amps (BRAND NEW). These little pocket size modules weigh less than 4lbs. but deliver full 20 amps at 5v. Add a pot to make variable 0-6v, or connect in series for higher voltages. 0.1% Regulation and full over V/I protection. List price £250+
Our price £40.25

PROTOTYPE PC CARDS. Over 200 Common ICs (most 7400 series) in wire wrap sockets on useful wire-wrap cards. ICs/Sockets easily removed - no unsoldering
Only £11.50

DEC PDP-11 BARGAINS (Exc. VAT)

PDP 11/34A 256KB MOS KY11-LB + CDC 9760 40MB Disk. New £12000
PDP 11/34A 256KB MOS RK05 Disk + Control £5000
PDP 11/04 32KB MOS. New with DL11 £2500
SYSTEM 3000 (11/04) 128K 2 x 5MB DRI32 Disk + RSTS £3500
PDP 11/40 96K Core KT11-D DL11 £1700
PDP 11/03 64K + 5MB DRI-32 Disk and Control £2500
PDP8E Processor 16K Core, Prog. Console £400
PDP8E + TU56 Dectape + OS8 Operating System £800

THIS MONTH'S SPECIAL OFFERS

Ventek Datapoint 1100 Computer in desk with VDU, twin floppy drives and QUME daisy wheel printer. Only £800+VAT
Diablo Hy-type daisy wheel printer, with no case £220+VAT

FOR MORE DETAILS
TELEPHONE NIGEL DUNN ON 0494 714483, ANY TIME
For regular copies of our catalogue please send postcard with address

WW - 081 FOR FURTHER DETAILS

D&R MARKETING Ltd.

SERIES 600

The D&R SERIES 600 range of professional mixing consoles has found its way into hundreds of (hospital) broadcast studios, discotheques, clubs, entertainment and outdoor Public Address systems and recording studios. Available in 6, 12, 18 or 24 channel configuration with, as standard, separate balanced mic. and line inputs, insertion points, gain, three band tone controls, two auxiliary lines, pan-pot and linear fader, plus pre-fade-listening and overload LED per channel. The output section includes four master faders, echo return and phones controls and two large V.U. meters. Optional XLR-3 connectors, 48 volt phantom powering, stereo channels with R.I.A.A. correction, talkback, fader controlled start switches, balanced outputs and 24 volt D.C. mains powering are available.

See our stand at A.P.R.S. '82, International Exhibition of Professional Recording Equipment, 23-24-25 June, 1982, Kensington Exhibition Centre, London

D.S.N. MARKETING LTD, Westmorland Road, London NW9 9RJ
Telephone: 01-204 7246. Telex: 895 4243.
Trade, Wholesale, O.E.M. & Export enquiries welcome.



WW - 007 FOR FURTHER DETAILS

D&R Electronica was founded over 10 years ago with the aim of developing and manufacturing high quality mixing consoles for the studio and entertainment industry with a special emphasis on value for money design engineering. The result is a range of five basic models with a large number of channel configurations and options. All models are highly flexible in use and give the best quality possible at today's state of technology.

SERIES 200 - A small mixer specially designed for four track recording.

SERIES 600 - A range of mixers for live amplification, broadcast studios and two track recording.

SERIES 400 - 'In-Line' mixing consoles for budget 4, 8 or 16 track recording.

SERIES 1000 - A range of comprehensive 'In-Line' consoles for professional recording studios.

SERIES 8000 - Top of the range 'In-Line' consoles with integral patch bay for top recording studios. A large number of ancillary signal processing units complement the D&R programme.

Please complete this coupon for further details:-

D&R Series 200 D&R Series 600
 D&R Series 400 D&R Series 1000
 D&R Series 8000 D&R Ancillary Equipment

BULLET loudspeaker components
 VITAVOX loudspeaker equipment
 HELIOS mirror balls

NAME _____
ADDRESS _____

WW 782

Item No.	Description	Price	Item No.	Description	Price
1	TEKTRONIX PORTABLE OSCILLOSCOPE type 422. Dual Trace	£350	53	POLAROID MICROWAVE SIGNAL GENERATOR Model MSG-1 950-2400MHZ	£150
2	TEKTRONIX STORAGE MONITOR type 613	£495	54	POLAROID MICROWAVE SIGNAL GENERATOR Model MSG-2 2150-4600MHZ	£150
3	TEKTRONIX Dual Trace Oscilloscope type E51A with CA Plug-in	£150	55	GENERAL RADIO MICROWAVE OSCILLATOR type 1360B 1.7-4.1GHz	£275
4	TEKTRONIX CURVE TRACER type 575	£150	56	GENERAL RADIO FREQUENCY/DISCRIMINATOR METER type 1142A 0-1.5MHz	£95
5	TEKTRONIX AMPLIFIER type 1121	£40	57	GENERAL RADIO OSCILLATOR 1293C, 1299L1, 1215C with Power Unit type 1263B 50-360MHz	£95
6	TEKTRONIX SAMPLING PUG-IN type 1S1	£175	58	GENERAL RADIO DECADE CAPACITOR 1413 with ANALOG LIMIT COMPARATOR	£150
7	TEKTRONIX PUG-IN type D Single Trace High Gain DC Differential	£20	59	STODDART RADIO INTERFERENCE & FIELD INTENSITY METER type N-M 52A	£195
8	TEKTRONIX PUG-IN type E Single Trace Low Level AC Differential	£20	60	KEITHLEY REGULATED HIGH VOLTAGE SUPPLY type 241	£145
9	TEKTRONIX PUG-IN type G Single Trace Wide Band DC Differential	£20	61	BRANDENBURGH HIGH VOLTAGE GENERATOR type MR50	£75
10	TEKTRONIX PUG-IN type M 4 Trace OC-20MHz	£125	62	BRANDENBURGH HIGH VOLTAGE P.U. Model 705, Metered 0-15KV +/-	£100
11	TEKTRONIX PUG-IN type O Operational Amplifier	£75	63	BELUX POWER UNIT type CM2301 +/- 0-1000 Volts in 3 ranges	£40
12	TEKTRONIX PUG-IN type Q Transducer & Strain Gauge	£75	64	PLEYX TELEGRAPH SIGNAL GENERATOR TSG10 with TOMES type 70, Speed 50-75-100 (2 units)	£50
13	TEKTRONIX PUG-IN type R Transistor Rise Time	£75	65	As Above but SELECT 45.5-50-75	£90
14	TEKTRONIX PUG-IN type W Differential Comparator	£125	66	RACAL H.F. SPEED ANALYSER type 9056	£235
15	TEKTRONIX PUG-IN type X Differential Comparator	£75	67	RACAL UHF FREQUENCY METER type 9839 10-560MHz	£225
16	HEWLETT PACKARD CR BRIDGE type 4261A	£150	68	RACAL 600MHz DECADE DIVIDER type 9010	£40
17	HEWLETT PACKARD DC METER type 4342A	£75	69	RACAL AUTO FREQUENCY CONVERTOR type 9839 500MHz	£40
18	HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V; 0-250mA	£125	70	RHOIDE & SCHWARZ NOISE GENERATOR SKTU BN4151/2/60 3-1000MHz	£75
19	HEWLETT PACKARD WIDE RANGE OSCILLATOR type 200CD	£35	71	R & S UHF TEST RECEIVER BN1523 280-940MHz	£50
20	HEWLETT PACKARD AUDIO OSCILLATOR type 200U	£35	72	R & S FREQUENCY METER VHF-UHF 300-300MHz type W1D BN442	£40
21	HEWLETT PACKARD PULSE GENERATOR Model 212A	£25	73	R & S RESONANCE FREQUENCY METER type 500MHz WAM BN4312/2	£50
22	HEWLETT PACKARD DC MICRO VOLT AMMETER type 425A	£40	74	R & S ATTENUATOR type OPR BN1804/50	£25
23	HEWLETT PACKARD OSCILLOSCOPE 182A with 1808A and 1825A 75MHz Dual Trace Delayed Sweep	£960	75	R & S SELECTOR type UFW BN1804/50	£25
24	HEWLETT PACKARD DIGITAL VOLTMETER type 3430A	£35	76	R & S UHF MILLIVOLTMETER URV BN1091	£85
25	HEWLETT PACKARD VOLTAGE VOLTMETER type 410B with Probes	£85	77	R & S CAPACITANCE METER BN5201	£50
26	MARCONI IN SITU UNIVERSAL BRIDGE type TF12701, Battery Operated	£95	78	ISOLATING TRANSFORMER 240V Input 240V Output 1300 Watts	£15
27	MARCONI WIDE RANGE OSCILLATOR type TF1370, 10Hz-10MHz	£65	79	AUTO TRANSFORMER +/- KVA Pri Volts 90/240 Sec Volts 115	£15
28	MARCONI ISANDERS' MICROWAVE POWER METER type 6598	£150	80	DC SERVO MOTOR 110V 2.5A Cont. Double Shaft 4 Wires 4 Brush, New	£15
29	MARCONI UHF SIGNAL GENERATOR type TF1080	£150	81	CLAUDE LYONS AUTOMATIC VOLTAGE STABILISER, Input 204-252 Volts Output 240V +/- 0.3% 13A 3.12KVA	£75
30	MARCONI FM SIGNAL GENERATOR type TF1077, 187-102.5MHz	£150	82	PHILIPS VIDEO COLOUR TEST GENERATOR type PM5522	£175
31	MARCONI UNIVERSAL BRIDGE type TF1313, 0.25%	£185	83	As Above but NO GASE	£145
32	MARCONI VARIABLE ATTENUATOR type TF1073A/25 (CT421)	£30	84	PHILIPS FM STEREO GENERATOR type PM4456, Separate L & R Signals Carrier Freq 100MHz +/- 1% RF O/P 3mV pk-pk	£125
33	MARCONI UNIVERSAL BRIDGE type TF12700	£195	85	PHILIPS COMPARTOR 278KHZ	£30
34	MARCONI AM/FM SIGNAL GENERATOR TF995A/3/S (CT402) 1.5-220MHz	£200	86	PHILIPS AUTOMATIC ELECTRIC VOLT OHM METER type PM2405	£50
35	MARCONI AC MILLIVOLTMETER type TF2800 10Hz-5MHz; 1mV-300V	£150	87	PHILIPS AUTOMATIC ELECTRIC VOLT OHM METER type PM2405	£50
36	B & K ACCELERATION PREAMPLIFIER type 282	£30	88	HEWLETT PACKARD DC POWER SUPPLY type 6448B, 0-800 Volts 0-1.5 Amps	£295
37	B & K DEVIATION BRIDGE type 1503	£30	89	ADVANCE UHF SIGNAL GENERATOR S669 370-1040MHz	£125
38	B & K DEVIATION BRIDGE type 1504	£30	90	ADVANCE PULSE GENERATOR type P9500ZD	£20
39	B & K MICROPHONE AMPLIFIER type 2802	£35	91	ADVANCE LF OSCILLATOR type S668A	£20
40	B & K MICROPHONE AMPLIFIER type 2803	£35	92	ADVANCE FREQUENCY METER type 82A 150kHz-220MHz	£35
41	B & K BEAT FREQUENCY OSCILLATOR type 1013	£30	93	ADVANCE BATCH CONVERTER type 4B41	£20
42	B & K BEAT FREQUENCY OSCILLATOR type 1018	£35	94	ADVANCE AUDIO SIGNAL GENERATOR type J1A	£30
43	B & K AUDIO FREQUENCY SPECTROMETER type 2112	£225	95	ADVANCE SIGNAL GENERATOR type E2 100kHz-100MHz	£45
44	B & K LEVEL RECORDER type 2386, 50dB Potentiometer; Brand new with accessories	£650	96	PYE SCALAMP 40KV RMS Max ELECTROSTATIC VOLTMETER	£58
45	TEXAS SILENT 700 PRINTER Model KSR733 - 300 baud	£775	97	RANK AGENA E.H.T. METER 0-30KV	£35
46	CALCOMP DRUM PLOTTER Model 564	£785	98	SINE & SQUARE WAVE AUDIO GENERATOR type TE-22 20Hz-200KHz	£35
47	MOSLEY WAFORM TRANSLATOR type 10	£35	99	BLACK & WHITE 20" MONITOR by IKGEMINI type PM20T5, Solid State	£85
48	HOUSTON INSTRUMENTS VOLTAGE CONVERTOR Model HLVC150	£75			
49	POLAROID FIELD STRENGTH METER type FM-82 with RF Tuning Unit FM-X2 100MHz	£95			
50	POLAROID MICROWAVE RECEIVER MODEL R with RF Tuning Units covering 400-2050MHz and 7400-22,000MHz	£150			

MARCONI AM/FM SIGNAL GENERATOR
type TF1066B/6S
10-470 MHz in 5 bands
£275 each

WAYNE KERR COMPONENT BRIDGE
type BS21 (CT 375)
Resistance 1M Ohm - 5000 Meg Ohm
Capacitance 1pF - 1000 pF
Inductance 1µH - 500 KHz
with copy of manual
ONLY £40 each

AVO VALVE TESTER type CT160
(22 valve bases) with copy of manual
£20 each
Copy of Valve Data £5
(only available with unit)

AVO TRANSISTOR ANALYSER
type CT446 with copy of manual
£20 each
Copy of Transistor Data £5
(only available with unit)

AVO SIGNAL GENERATOR
No. 2 AM/FM
AM 0.45-225 MHz; FM 20-100 MHz
with copy of manual
£75 each

MARCONI COUNTER/FREQUENCY METER
TF1417/2 with Converter type
TF 2400/TM7164 - 500 MHz
£95

SINE & SQUARE WAVE AUDIO GENERATOR
type TE-22, 20Hz-200KHz, Portable as new
ONLY £35 each, P&P £4

MULTIMETER
Russian Type 4324
AC/DC volts; AC/DC current; ohms, etc.
Brand new, boxed.
£12.50 each, P&P £2.50

IKGEMINI MONITOR
20" Black & White
Solid state. Video in, int. ext. Sync.
£65 each


TELETYPE PRINTERS
KSR 33 - ASCII Keyboard £50
ASR 33 - as above with 8-bit Punch and Reader £75
PDP 8 in 6ft RACK CABINET £100

PLEASE CHECK AVAILABILITY BEFORE ORDERING
COMPONENT LIST AVAILABLE S.A.E. OR PHONE

LANGREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED
Tel: 01-677 2424 Telex: 946708

SEMICONDUCTORS	BD131 0.51	BF257 0.31	GEX541 5.75	OAZ207 1.73	OC205 3.16	ZTX504 0.24	ZN1671 5.75	ZN3819 0.95
AA119 0.12	ASZ125 1.38	BC127 0.13	GD135 0.22	OC16 2.88	OC206 3.16	ZTX530 0.28	ZN1893 0.37	ZN3820 0.65
AA130 0.20	ASZ126 1.27	BC173 0.13	GM0578A 2.30	OC27 2.88	OC207 2.88	ZTX550 0.29	ZN2147 4.00	ZN3823 0.49
AA132 0.48	ASZ127 1.15	BC177 0.32	K3100A 0.52	OC28 2.88	OC21 2.30	IN914 0.06	ZN2148 4.31	ZN3826 1.15
AA133 0.47	ASZ20 2.64	BC178 0.16	MJE304 0.84	OC29 4.60	OC24 3.60	IN919 0.10	ZN2218 4.31	ZN3830 0.20
AA135 0.17	ASZ20 2.64	BC179 0.32	MJE307 0.84	OC30 4.60	OC25 4.60	IN921 0.10	ZN2219 0.37	ZN3905 0.20
AAZ17 0.17	AUI13 2.88	BC182 0.13	MJE310 0.84	OC31 1.15	OC26 1.73	R2009 2.59	ZN2220 0.23	ZN3906 0.18
AC107 0.63	AUI10 3.45	BC183 0.13	MJE311 0.84	OC32 2.30	OC27 2.30	R2029 2.59	ZN2221 0.23	ZN4058 0.20
AC125 0.29	AUI10 2.88	BC184 0.13	MJE312 0.84	OC33 1.73	OC28 2.30	R2049 2.59	ZN2222 0.23	ZN4059 0.23
AC126 0.29	BAI45 0.15	BC185 0.13	MJE313 0.84	OC34 1.73	OC29 2.30	R2069 2.59	ZN2223 4.89	ZN4060 0.18
AC127 0.29	BAI45 0.15	BC186 0.13	MJE314 0.84	OC35 1.73	OC30 2.30	R2089 2.59	ZN2224 4.89	ZN4061 0.18
AC128 0.35	BAI54 0.12	BC187 0.13	MJE315 0.84	OC36 1.73	OC31 2.30	R2109 2.59	ZN2225 4.89	ZN4062 0.18
AC141 0.32	BAI55 0.13	BC237 0.13	MJE316 0.84	OC37 1.73	OC32 2.30	R2129 2.59	ZN2226 4.89	ZN4063 0.18
AC142 0.42	BAI56 0.12	BC238 0.13	MJE317 0.84	OC38 1.73	OC33 2.30	R2149 2.59	ZN2227 4.89	ZN4064 0.18
AC142K 0.30	BAW62 0.06	BC239 0.13	MJE318 0.84	OC39 1.73	OC34 2.30	R2169 2.59	ZN2228 4.89	ZN4065 0.18
AC176 0.35	BAW62 0.06	BC240 0.13	MJE319 0.84	OC40 1.73	OC35 2.30	R2189 2.59	ZN2229 4.89	ZN4066 0.18
AC187 0.32	BAW62 0.06	BC241 0.13	MJE320 0.84	OC41 1.73	OC36 2.30	R2209 2.59	ZN2230 4.89	ZN4067 0.18
AC188 0.32	BAW62 0.06	BC242 0.13	MJE321 0.84	OC42 1.73	OC37 2.30	R2229 2.59	ZN2231 4.89	ZN4068 0.18
AC189 0.32	BAW62 0.06	BC243 0.13	MJE322 0.84	OC43 1.73	OC38 2.30	R2249 2.59	ZN2232 4.89	ZN4069 0.18
AC191 0.32	BAW62 0.06	BC244 0.13	MJE323 0.84	OC44 1.73	OC39 2.30	R2269 2.59	ZN2233 4.89	ZN4070 0.18
AC192 0.32	BAW62 0.06	BC245 0.13	MJE324 0.84	OC45 1.73	OC40 2.30	R2289 2.59	ZN2234 4.89	ZN4071 0.18
AC193 0.32	BAW62 0.06	BC246 0.13	MJE325 0.84	OC46 1.73	OC41 2.30	R2309 2.59	ZN2235 4.89	ZN4072 0.18
AC194 0.32	BAW62 0.06	BC247 0.13	MJE326 0.84	OC47 1.73	OC42 2.30	R2329 2.59	ZN2236 4.89	ZN4073 0.18
AC195 0.32	BAW62 0.06	BC248 0.13	MJE327 0.84	OC48 1.73	OC43 2.30	R2349 2.59	ZN2237 4.89	ZN4074 0.18
AC196 0.32	BAW62 0.06	BC249 0.13	MJE328 0.84	OC49 1.73	OC44 2.30	R2369 2.59	ZN2238 4.89	ZN4075 0.18
AC197 0.32	BAW62 0.06	BC250 0.13	MJE329 0.84	OC50 1.73	OC45 2.30	R2389 2.59	ZN2239 4.89	ZN4076 0.18
AC198 0.32	BAW62 0.06	BC251 0.13	MJE330 0.84	OC51 1.73	OC46 2.30	R2409 2.59	ZN2240 4.89	ZN4077 0.18
AC199 0.32	BAW62 0.06	BC252 0.13	MJE331 0.84	OC52 1.73	OC47 2.30	R2429 2.59	ZN2241 4.89	ZN4078 0.18
AC200 0.32	BAW62 0.06	BC253 0.13	MJE332 0.84	OC53 1.73	OC48 2.30	R2449 2.59	ZN2242 4.89	ZN4079 0.18
AC201 0.32	BAW62 0.06	BC254 0.13	MJE333 0.84	OC54 1.73	OC49 2.30	R2469 2.59	ZN2243 4.89	ZN4080 0.18
AC202 0.32	BAW62 0.06	BC255 0.13	MJE334 0.84	OC55 1.73	OC50 2.30	R2489 2.59	ZN2244 4.89	ZN4081 0.18
AC203 0.32	BAW62 0.06	BC256 0.13	MJE335 0.84	OC56 1.73	OC51 2.30	R2509 2.59	ZN2245 4.89	ZN4082 0.18
AC204 0.32	BAW62 0.06	BC257 0.13	MJE336 0.84	OC57 1.73	OC52 2.30	R2529 2.59	ZN2246 4.89	ZN4083 0.18
AC205 0.32	BAW62 0.06	BC258 0.13	MJE337 0.84	OC58 1.73	OC53 2.30	R2549 2.59	ZN2247 4.89	ZN4084 0.18
AC206 0.32	BAW62 0.06	BC259 0.13	MJE338 0.84	OC59 1.73	OC54 2.30	R2569 2.59	ZN2248 4.89	ZN4085 0.18
AC207 0.32	BAW62 0.06	BC260 0.13	MJE339 0.84	OC60 1.73	OC55 2.30	R2589 2.59	ZN2249 4.89	ZN4086 0.18
AC208 0.32	BAW62 0.06	BC261 0.13	MJE340 0.84	OC61 1.73	OC56 2.30	R2609 2.59	ZN2250 4.89	ZN4087 0.18
AC209 0.32	BAW62 0.06	BC262 0.13	MJE341 0.84	OC62 1.73	OC57 2.30	R2629 2.59	ZN2251 4.89	ZN4088 0.18
AC210 0.32	BAW62 0.06	BC263 0.13	MJE342 0.84	OC63 1.73	OC58 2.30	R2649 2.59	ZN2252 4.89	ZN4089 0.18
AC211 0.32	BAW62 0.06	BC264 0.13	MJE343 0.84	OC64 1.73	OC59 2.30	R2669 2.59	ZN2253 4.89	ZN4090 0.18
AC212 0.32	BAW62 0.06	BC265 0.13	MJE344 0.84	OC65 1.73	OC60 2.30	R2689 2.59	ZN2254 4.89	ZN4091 0.18
AC213 0.32	BAW62 0.06	BC266 0.13	MJE345 0.84	OC66 1.73	OC61 2.30	R2709 2.59	ZN2255 4.89	ZN4092 0.18
AC214 0.32	BAW62 0.06	BC267 0.13	MJE346 0.84	OC67 1.73	OC62 2.30	R2729 2.59	ZN2256 4.89	ZN4093 0.18
AC215 0.32	BAW62 0.06	BC268 0.13	MJE347 0.84	OC68 1.73	OC63 2.30	R2749 2.59	ZN2257 4.89	ZN4094 0.18
AC216 0.32	BAW62 0.06	BC269 0.13	MJE348 0.84	OC69 1.73	OC64 2.30	R2769 2.59	ZN2258 4.89	ZN4095 0.18
AC217 0.32	BAW62 0.06	BC270 0.13	MJE349 0.84	OC70 1.73	OC65 2.30	R2789 2.59	ZN2259 4.89	ZN4096 0.18
AC218 0.32	BAW62 0.06	BC271 0.13	MJE350 0.84	OC71 1.73	OC66 2.30	R2809 2.59	ZN2260 4.89	ZN4097 0.18
AC219 0.32	BAW62 0.06	BC272 0.13	MJE351 0.84	OC72 1.73	OC67 2.30	R2829 2.59	ZN2261 4.89	ZN4098 0.18
AC220 0.32	BAW62 0.06	BC						

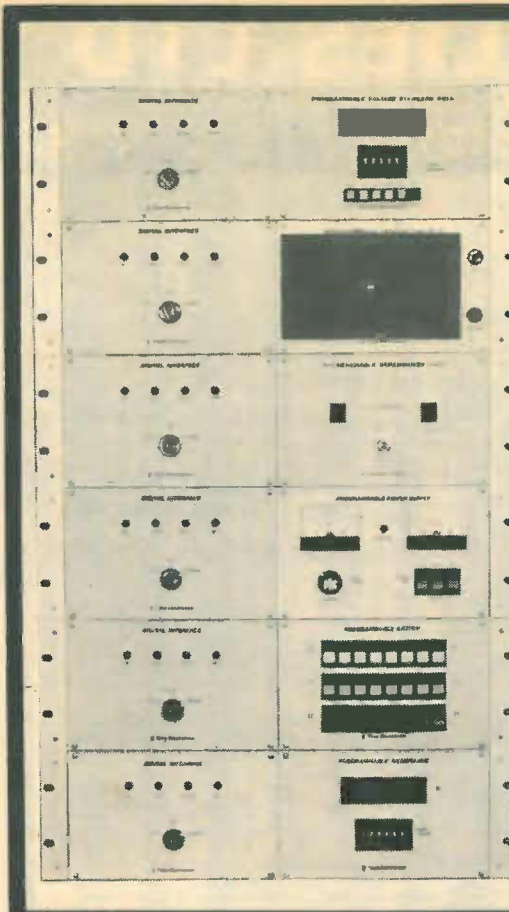

IEEE PROGRAMMABLES from TIME

9814 IEEE PROGRAMMABLE VOLTAGE STANDARD
A high performance voltage standard with 4 ranges from 0.1 volt to 10 volt output. Accuracy is 0.01% and the resolution of setting is 1 in 200,000. Output resistance is less than 0.01 ohms, and output current adjustable 20mA-200mA. Temperature coeff is less than 20ppm/°C and long term stability better than 50ppm per year. Full manual control is available via front panel controls. Available for benchtop use or 19" rack mounting.

9816 IEEE PROGRAMMABLE VOICE
A high quality speech synthesizer which has a 280 word vocabulary. By suitable programming via the IEEE bus it is possible to output single words, phrases and sentences. The vocabulary has been chosen to be applicable to many ATE applications.

9815 IEEE PROGRAMMABLE SCREWDRIVER
The unit has been designed to overcome the problems of adjusting large numbers of multi-turn trimmers in ATE systems. The screwdriver is fully programmable via the IEEE bus with 3 speeds of rotation and 2 selectable torque values available. The unit is supplied complete with a flexible drive shaft and drill chuck into which various adjusting tools can be located.

9810 IEEE/PROGRAMMABLE POWER SUPPLY
0-33V in 0.1V steps. Local or remote (IEEE) operation. Fully programmable on the IEEE bus with 3 settable current limits 1mA, 10mA and 1.1A. A dual version of the 9810 is also available. The unit is 3 Euro units high and standard 19" rack mounting width.

9812 IEEE PROGRAMMABLE SWITCH
24 double pole changeover switches are available with full IEEE control. Each switch is rated at 1 Amp, 30V dc or 100V ac. Thermal emfs have been minimised to less than 1µV per switch. All outputs are on the rear panel along with the IEEE address selector switch and bus connector. Manual control of the switches is also provided via a set of front panel switches which also incorporate LED indicators.

9811 IEEE PROGRAMMABLE RESISTANCE
0-1 Megohm in 1 Ohm steps, fully programmable via the IEEE bus. Accuracy is 0.1% over most of the resistance range. Resistors are rated at 1 watt each. An attractive feature is the option to switch to local operation when the output resistance can be set up manually via front panel switches.

TIME ELECTRONICS LTD, Botany Industrial Est., Tonbridge, Kent, England TN9 1RS. Tel: (0732) 355993. Telex: 954841

WW - 068 FOR FURTHER DETAILS

RECHARGEABLE BATTERIES

PRIVATE & TRADE ENQUIRIES WELCOME
Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.45 for booklet, "Nickel Cadmium Power," plus catalogue.
★ New sealed lead range now available ★

Write or call at:
SANDWELL PLANT LTD.
2 Union Drive, Boldmere
Sutton Coldfield, West Midlands, 021-354 9764
After Hours 0977 84093

WW - 063 FOR FURTHER DETAILS

VALVES			VALVES VAT IS INCLUDED		
	Minimum Order	£1			
A1065	1.40	EL821	8.20	SC1/600	4.50
A2293	8.80	EL822	9.95	SP61	1.80
A2900	13.75	EM80	0.85	TT21	23.00
ARR	0.75	GZ67	1.30	TT22	6.00
ARP3	0.70	EY51	0.95	U25	1.15
ATP4	0.80	EY81	0.85	U26	1.15
B12H	3.90	EY86/87	0.80	U27	1.15
CY31	1.40	EY88	0.85	U191	0.95
DAF96	0.70	EZ60	0.70	U281	1.30
DET22	26.95	EZ81	0.70	U301	0.85
DF96	0.70	GM4	5.90	UB60	11.50
DH76	0.75	GY501	1.30	UB01	0.90
DL92	0.80	GZ35	1.05	UB21	1.20
DY86/87	0.85	GZ32	4.20	UBC80	0.75
DY802	0.70	GZ34	2.75	UAF42	1.20
E55L	14.90	GZ37	3.95	UBF80	0.70
EBBC/1	1.80	KT66	8.30	UBF89	0.70
EBBC/0	3.10	KT88	8.95	UBF89	0.70
E92CC	2.80	KT88	8.95	UCB54	0.85
E180CC	4.20	MH4	2.50	UCB85	0.70
E180F	7.70	ML6	2.80	UCB85	0.70
E182CC	6.25	MX10/01	2.150	UCB81	0.75
EA76	0.80	N78	3.90	UCL82	0.95
EABC80	0.80	OA2	0.70	UF41	1.35
EB91	1.15	OB2	0.80	UF80	0.95
EB339	0.90	PAB380	0.90	UF85	0.95
EBF80	0.80	PC35	0.85	UM60	0.85
EBF83	0.80	PC86	0.85	UM80	0.90
EBF89	0.80	PC88	0.90	UM84	0.70
EC52	0.85	PC97	1.25	UY82	0.70
EC91	4.40	PC900	0.90	VR85	0.85
EC92	0.85	PC94	1.50	VR105/30	1.25
EC98	0.85	PCC89	0.85	VR150/30	1.35
ECC81	0.60	PCC189	0.85	X66	0.95
ECC82	0.60	PCF80	0.80	X61M	1.70
ECC83	0.60	PCF82	0.80	XH1-6400A	82.90
ECC84	0.60	PCF84	0.75	82.90	82.90
ECC86	1.70	PCF86	1.50	2759	19.00
ECC88	0.80	PCF87	0.50	2749	0.75
ECC89	0.95	PCF200	1.45	2800U	3.45
ECC90	0.80	PCF89	0.85	2801U	3.45
ECF80	0.85	PCF80	0.50	2803U	16.00
ECF82	0.85	PCF801	1.75	2900T	2.45
ECF801	1.05	PCF802	0.70	1A3	0.85
ECF84	2.25	PCF86	1.20	1L4	0.50
ECF85	1.70	PCH200	1.35	1S4	0.45
EH42	1.20	PCL81	0.75	1S5	0.45
ECH81	0.70	PCL82	0.95	1T4	0.45
ECH84	0.80	PCL84	0.90	1U4	0.60
EL80	0.75	PCF84	0.75	6L6C	2.75
EL82	0.75	PCF85/85	0.95	2D21	1.10
EL83	1.40	PCF86/86	0.95	2D21	1.10
EL85	0.80	PFL200	1.10	2K25	18.95
EL86	0.80	PL16	2.80	2X2	24.50
EL87	2.15	PL81	0.85	3A4	0.70
EL88	0.85	PL82	0.70	3AT7	2.40
EL89	1.75	PL83	0.80	3D6	0.90
EL90	0.95	PL85	0.80	3D7	2.20
EL91	4.20	PL84	0.85	3D7	2.20
EL95	0.80	PL84	0.85	3D7	2.20
EL96	1.05	PL86	1.95	354	0.80
EL99	1.50	PL509	3.20	4832	18.25
EF92	2.90	PL519	6.85	5B/25M	18.90
EF95	0.90	PL519	6.10	5B/25M	12.50
EF96	0.80	PL802	3.20	5C22	29.90
EF183	0.80	PL803	0.70	5Y4GT	1.80
EF184	0.75	PL804	0.75	5Y4GT	1.80
EL200	1.85	PY81/800	0.85	5Y4GT	1.80
EH90	0.85	PY82	0.85	5Y3GT	0.95
EL32	1.10	PY83	0.80	5Z3	1.50
EL34	1.80	PY88	0.80	5Z4G	0.75
EL81	2.90	PY80A2.10	5.24GT	1.85	5Z4
EL82	0.70	PY801	0.80	6AB7	0.90
EL84	0.80	QV03/10	7.50	6AC7	1.15
EL86	0.95	QV03/20A	6AC6	0.90	9D6
EL90	1.00	QV03/25A	6AC5	0.85	10C2
EL91	4.20	QV03/25A	6AK5	0.85	10F18
EL95	0.80	QV03/25A	38.50	6AK8	0.80
EL96	1.70	QV03/40A	6AL5	0.80	11E2
EL99	5.90	QV03-12	16.10	6AL5W	0.85
EL802	1.70	SC1/400	4.50	6AM6	1.50
EL81	2.50	SC1/400	4.50	6AM6	1.50
EL82	0.70	SC1/400	4.50	6AM6	1.50
EL83	0.70	SC1/400	4.50	6AM6	1.50
EL84	0.70	SC1/400	4.50	6AM6	1.50
EL85	0.70	SC1/400	4.50	6AM6	1.50
EL86	0.70	SC1/400	4.50	6AM6	1.50
EL87	0.70	SC1/400	4.50	6AM6	1.50
EL88	0.70	SC1/400	4.50	6AM6	1.50
EL89	0.70	SC1/400	4.50	6AM6	1.50
EL90	0.70	SC1/400	4.50	6AM6	1.50
EL91	0.70	SC1/400	4.50	6AM6	1.50
EL92	0.70	SC1/400	4.50	6AM6	1.50
EL93	0.70	SC1/400	4.50	6AM6	1.50
EL94	0.70	SC1/400	4.50	6AM6	1.50
EL95	0.70	SC1/400	4.50	6AM6	1.50
EL96	0.70	SC1/400	4.50	6AM6	1.50
EL97	0.70	SC1/400	4.50	6AM6	1.50
EL98	0.70	SC1/400	4.50	6AM6	1.50
EL99	0.70	SC1/400	4.50	6AM6	1.50

VALVES			VALVES VAT IS INCLUDED		
	Minimum Order	£1			
A1065	1.40	EL821	8.20	SC1/600	4.50
A2293	8.80	EL822	9.95	SP61	1.80
A2900	13.75	EM80	0.85	TT21	23.00
ARR	0.75	GZ67	1.30	TT22	6.00
ARP3	0.70	EY51	0.95	U25	1.15
ATP4	0.80	EY81	0.85	U26	1.15
B12H	3.90	EY86/87	0.80	U27	1.15
CY31	1.40	EY88	0.85	U191	0.95
DAF96	0.70	EZ60	0.70	U281	1.30
DET22	26.95	EZ81	0.70	U301	0.85
DF96	0.70	GM4	5.90	UB60	11.50
DH76	0.75	GY501	1.30	UB01	0.90
DL92	0.80	GZ35	1.05	UB21	1.20
DY86/87	0.85	GZ32	4.20	UBC80	0.75
DY802	0.70	GZ34	2.75	UAF42	1.20
E55L	14.90	GZ37	3.95	UBF80	0.70
EBBC/1	1.80	KT66	8.30	UBF89	0.70
EBBC/0	3.10	KT88	8.95	UBF89	0.70
E92CC	2.80	KT88	8.95	UCB54	0.85
E180CC	4.20	MH4	2.50	UCB85	0.70
E180F	7.70	ML6	2.80	UCB85	0.70
E182CC	6.25	MX10/01	2.150	UCB81	0.75
EA76	0.80	N78	3.90	UCL82	0.95
EABC80	0.80	OA2	0.70	UF41	1.35
EB91	1.15	OB2	0.80	UF80	0.95
EB339	0.90	PAB380	0.90	UF85	0.95
EBF80	0.80	PC35	0.85	UM60	0.85
EBF83	0.80	PC86	0.85	UM80	0.90
EBF89	0.80	PC88	0.90	UM84	0.70
EC52	0.85	PC97	1.25	UY82	0.70
EC91	4.40	PC900	0.90	VR85	0.85
EC92	0.85	PC94	1.50	VR105/30	1.25
EC98	0.85	PCC89	0.85	VR150/30	1.35
ECC81	0.60	PCC189	0.85	X66	0.95
ECC82	0.60	PCF80	0.80	X61M	1.70
ECC83	0.60	PCF82	0.80	XH1-6400A	82.90
ECC84	0.60	PCF84	0.75	82.90	82.90
ECC86	1.70	PCF86	1.50	2759	19.00
ECC88	0.80	PCF87	0.50	2749	0.75
ECC89	0.95	PCF200	1.45	2800U	3.45
ECC90	0.80	PCF89	0.85	2801U	3.45
ECF80	0.85	PCF80	0.50	2803U	16.00
ECF82	0.85	PCF801	1.75	2900T	2.45
ECF801	1.05	PCF802	0.70	1A3	0.85
ECF84	2.25	PCF86	1.20	1L4	0.50
ECF85	1.70	PCH200	1.35	1S4	0.45
EH42	1.20	PCL81	0.75	1S5	0.45
ECH81	0.70	PCL82	0.95	1T4	0.45
ECH84	0.80	PCL84	0.90	1U4	0.60
EL80	0.75	PCF84	0.75	6L6C	2.75
EL82	0.75	PCF85/85	0.95	2D21	1.10
EL83	1.40	PCF86/86	0.95	2D21	1.10
EL85	0.80	PFL200	1.10	2K25	18.95
EL86	0.80	PL16	2.80	2X2	24.50
EL87	2.15	PL81	0.85	3A4	0.70
EL88	0.85	PL82	0.70	3AT7	2.40
EL89	1.75	PL83	0.80	3D6	0.90
EL90	0.95	PL85	0.80	3D7	2.20
EL91	4.20	PL84	0.85	3D7	2.20
EL95	0.80	PL84	0.85	3D7	2.20
EL96	1.05	PL86	1.95	354	0.80
EL99	1.50	PL509	3.20	4832	18.25
EF92	2.90	PL519	6.85	5B/25M	18.90
EF95	0.90	PL519	6.10	5B/25M	12.50
EF96	0.80	PL802	3.20	5C22	29.90
EF183	0.80	PL803	0.70	5Y4GT	1.80
EF184	0.75	PL804	0.75	5Y4GT	1.80
EL200	1.85	PY81/800	0.85	5Y4GT	1.80
EH90	0.85	PY82	0.85	5Y3GT	0.95
EL32	1.10	PY83	0.80	5Z3	1.50
EL34	1.80	PY88	0.80	5Z4G	0.75
EL81	2.90	PY80A2.10	5.24GT	1.85	5Z4
EL82	0.70	PY801	0.80	6AB7	0.90
EL84	0.80	QV03/10	7.50	6AC7	1.15
EL86	0.95	QV03/20A	6AC6	0.90	9D6
EL90	1.00	QV03/25A	6AC5	0.85	10C2
EL91	4.20	QV03/25A	6AK5	0.85	10F18
EL95	0.80	QV03/25A	38.50	6AK8	0.80
EL96	1.70	QV03/40A	6AL5	0.80	11E2
EL99	5.90	QV03-12	16.10	6AL5W	0.85
EL802	1.70	SC1/400	4.50	6AM6	1.50
EL81	2.50	SC1/400	4.50	6AM6	1.50
EL82	0.70	SC1/400	4.50	6AM6	1.50
EL83	0.70	SC1/400	4.50	6AM6	1.50
EL84	0.70	SC1/400	4.50		

RHODE & SCHWARZ
Selective UHF V/Meter. Bands 4 & 5. USVF Selectomat Voltmeter USWV £450.
UHF Sig. Gen. type SDR 0.3-1GHz
UHF Signal Generator SCH £175.
XUD Decade Synthesizer & Exciter.
POLYSKOPS SWOB I and II.
Modulator/Demodulator BN17950/2.

MARCONI
TF995B/2 AM/FM Signal Generator.
TF2500 Audio power meter
TF1101 RC oscillators £65.
6551 SAUNDERS 1400-1700MHz. FM.
TF1066B/1. 10-470MHz. AM/FM.
TF1152A/1. Power meter. 25W. 500MHz £50.
TF1370A RC Oscillator £135.
TF791D Carrier Deviation Meter.


BECKMAN TURNS COUNTER DIALS
Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

★ **VIDEO EQUIPMENT SALE ★**
CONTENTS OF COMPLETE MONOCHROME STUDIO
MARCONI Video/Audio mixing desks. Monochrome Video cameras complete with on-board monitors. Video monitors types CONRAC II (9" tube) PROWEST 13".
To be sold in first-class working condition. Offers invited for complete lot.

GPO JACK SOCKET STRIPS. 20-WAY Type 320 (3-pole) £2.50 ea. Type 520 (3-pole with switching contacts) £4 ea. Please include 35p each for postage on these. GPO type 316 jack plugs for above 20p ea. (10+ post free). Plus VAT please.

PHILIPS Model PM6456/01 FM STEREO GENERATOR. RF Output frequency 1MHz Standardised Stereo multiplex output signal. As new with handbook. £195.

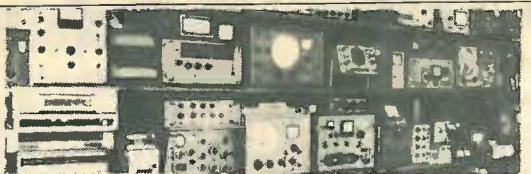P. F. RALFE ELECTRONICS
10 CHAPEL STREET, LONDON, NW1
TEL: 01-723 8753



RANK KALEE 1742 Wow & Flutter Meter.
AIRMEC 314A Voltmeter. 300mV (FSD)-300V.
AIRMEC Wave Analysers types 853 & 248A.
HEWLETT-PACKARD 6260A DC Power supply unit. 0-10V at 100 Amps. Metered output.
BPL High-speed automator and component comparator. Complete with test jig.
BPL RM215L Breakdown and Ionisation tester.
AVO Type No. 1. LC&R Component bridge.
WAYNE KERR AF signal generator S121 model..... £85
RADIOMETER Distortion Meter BKF6 £125.

SPECIAL PURCHASE OF TEKTRONIX 454 PORTABLE OSCILLOSCOPES

Tektronix 454 DC-150MHz dual-beam oscilloscopes in stock now. 5mV/cm Y-amplifier (1mV cascaded). 2.4ns risetime. Calibrated sweep delay. We can offer these units in first-class operational condition complete with three months' guarantee, for a once only price of £850.

SPECIAL OFFER FOR THIS MONTH REDUCED TO £650.00

CABLE & WIRELESS
Telegraph Signalling Twin DC Power supply units. 240V AC Input. DC output 80-0-80V. Dimensions 8x7x19". Model No. DD30. Price ea. £12.50. Carriage £1.50.

★ TEKTRONIX ★
Type 565 with 2 off 2A63 Y-Amps (Differential) (1mV/Div. DC-300KHz) 2 1/2" Bases in main frame 0.1us/Div. -5s/Div. Excellent condition.

PLEASE NOTE: All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES
★ APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.)
★ APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)
★ We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25.
★ Mullard Dual supplies. Brand new with handbook. Pos & Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + (£1 p.p.)
★ FARNELL Current limited. Dimensions 7x5x4ins. Following types available: 13-17 Volts @ 2A £15. 27-32 Volts @ 1A 5V £15. 5V @ 3A £15. (pp £1.50).


SPECIAL PURCHASE
LAMBDA POWER SUPPLIES
Excellent LXS Series DC power units at less than a tenth of new price. The snag? - they're all 110V AC input. Prices as follows:
5V at 24A. LXS D5 0V R. £25. (List £350). Carriage each £2.50 extra
5V at 14A. LXS C5 0V. £20. (£258)
24V at 3.1A. LCS C24. £16. (£223).
Special note: The 5V power supplies may be operated (both primary from 230V) and DC output to give a maximum output voltage of 12.5DC when connected in series. Deduct 10% from price for two off or more, i.e., 12V DC at 24A for £45 + Tax! Very cheap!

VARIABLE VOLTAGE BENCH SUPPLIES
Variable voltage DC power supplies for workshop use. Constant voltage, variable 0-30V output at 1A. Cased, free standing, volt-metered output. Short circuit proof. Size 4 x 5 x 7". Only £30 - each (pp £1.50).

COMMUNICATIONS TEST EQUIPMENT
★ MARCONI TF1066B/1. AM/FM Signal Generator. 10-470MHz. 0.2uV-200mV output. FM Deviations up to ±100kHz from 30Hz-15KHz £550
★ MARCONI TF995A/5 AM/FM Signal generator. Narrow deviation model 995 covering 1.5-220MHz..... £450
★ MARCONI TF1064B/5 FM signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. Modulation FM fixed deviations of 3.5 and 10KHz. AM fixed 30%..... £225
★ MARCONI TF791D FM Deviation meter..... £185

ROTRON INSTRUMENT COOLING FANS
Supplied in excellent condition, fully tested
V. 4.5 x 4.5 x 1.5" £4.50. 230V
£5. 115V. 3 x 3 x 1.5" £4 + postage ea. 35p.

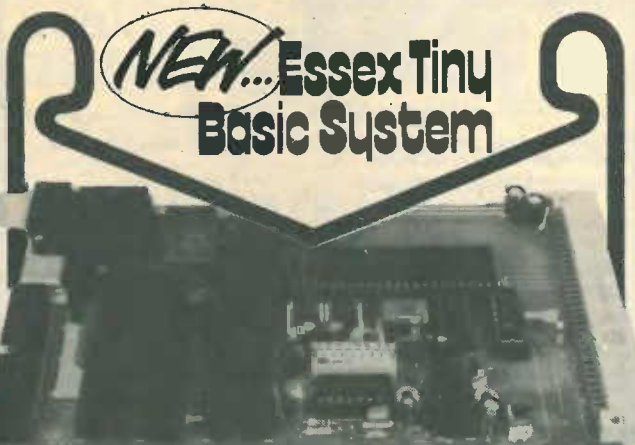SYNCHRONOUS STEPPING MOTORS
Superior Electric (USA) make. 10V DC 1/2A. 200 Steps per Rev. Torque (HOLD) 53 oz.in. Condition brand new. £9.50 ea. Including postage and VAT.



NEW... Essex Tiny Basic System

★ RS232 Interface 48 I/O Lines
★ Powerful Tiny Basic Processor
★ Autostart Operation with Watchdog Timer
★ Up to 16K Byte EPROM EPROM Programmer
★ Accommodates Instant ROM Modules

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.

INSTANT ROM is the trademark of Greenwich Instruments

PRICE EXCLUDING VAT: £185 - CARRIAGE WITHIN THE UK £2 - PLEASE SEND FOR FULL INFORMATION

Essex Electronics Centre
University of Essex, Colchester, CO4 3SQ.
Telephone: Colchester (0206) 865089

WW - 034 FOR FURTHER DETAILS

ScheTronics Limited

For repair and calibration of test equipment. We also have the following second user LF/HF equipment for sale.

Siemens including Pegamat - W & G - H.P. - Hatfield
Anritsu - Marconi - Fluke - STC - etc...

**Unit 10, Dunstall Estate
Crabtree Manorway
Belvedere, Kent DA17 6AW
Telephone: 01-311 9657**

WW 073 - FOR FURTHER INFORMATION

ANY MAKE-UP OR COPY QUERIES CONTACT BRIAN BANNISTER

01-661 3500 extension 8648

WIRELESS WORLD JULY 1982

MINI-DISK DRIVE TEST BOX

A simple aid to test and alignment of drives without tying up valuable system time. Neatly presented in handy case with leads and connectors for 2 drives. Needs +12V and +5V through standard drive connectors (provided). Circle number for further details.

Price £135 + carriage and VAT

MELKUIST LTD.
35A Guildford Street, Luton LU1 2NQ
Tel: 0582/416028
Telex: 825828 MELKST G

WW - 075 FOR FURTHER DETAILS

SUPERSEM

PLYMOUTH 0752 21256

MEMORIES AT UNFORGETTABLE PRICES

	1-24	25-99	100+	1,000+
4116 P-3 200ns.....	.90	.85	.80	.75
2114 LP 450ns.....	.90	.87	.85	.80
2708k 450ns.....	2.70	2.50	2.30	2.25
2716k 450ns.....	2.45	2.30	2.10	2.00
2732k 450ns.....	3.85	3.65	3.60	3.25
8981 P-45 Cmos.....	2.25	2.15	2.05	1.85
8725 S 200ns.....	7.05	6.55	6.05	5.55
K4164 200ns.....	5.00	4.75	4.50	4.25
8039 8-bit.....	3.05	2.90	2.75	2.45
8080AP CPU.....	2.15	2.05	1.95	1.75
8085A CPU.....	2.80	2.65	2.50	2.20
8155P + Timer.....	3.10	2.95	2.80	2.50
8156P + Timer.....	3.45	3.25	3.05	2.65
8212P i/o Port.....	1.10	1.05	1.00	.85
8216 Bus Driver.....	1.05	1.00	.95	.85
8224P Clock Gen.....	1.30	1.20	1.15	1.05
8226P Bus + B/Drives.....	.92	.87	.82	.75
8228P System Cont.....	2.25	2.15	2.05	1.85
8243P i/o Exp.....	2.00	1.95	1.90	1.80
8251AP Prog. Int./Face.....	2.60	2.50	2.40	2.30
8253P Prog. Int./Time.....	3.60	3.40	3.20	2.85
8255AP Perip./Inter.....	2.25	2.15	2.05	1.85
8257P DMA Cont.....	3.75	3.65	3.35	3.00
8259 Inter Cont.....	3.60	3.40	3.20	2.85
8279P Key Disp.....	4.60	4.50	4.00	3.50
4044 P-3 300ns.....	1.90	1.80	1.70	1.55

Please add V.A.T. to all orders
FAST DELIVERY: TOP QUALITY
Send for our NEW Semi-Conductor Catalogue
Phone 0752 21256

SUPERSEM
Export enquiries welcome

3rd Floor
Britannic House
Drake Circus
Plymouth PL4 8AQ

WW - 070 FOR FURTHER DETAILS

TRANSFORMERS

Despatch by return

CONTINUOUS RATINGS

MAINS ISOLATORS Pri 0-120V; 0-100-120V (120, 220, 240V) Sec 0-CT-115Vx2				12 or 24-VOLT RANGE Separate 12V windings Pri 220-240V			
Ref.	VA (Watts)	£	P&P	Ref.	12v Amps	24v £	P&P
074	20	5.32	1.50	213	1	0.5	3.19
149	60	8.37	1.60	71	2	1.0	4.25
150	100	9.38	1.84	18	4	2.0	4.91
151	200	13.69	2.12	85	5	2.5	6.78
152	250	16.31	2.64	70	6	3.0	7.69
153	350	18.07	2.12	108	8	4.0	8.98
154	500	25.02	2.90	72	10	5.0	9.82
155	750	35.91	OA	116	12	6.0	10.89
156	1000	45.89	OA	17	16	8.0	12.97
157	1500	60.02	OA	115	20	10.0	17.46
158	2000	72.43	OA	187	30	15.0	21.89
159	3000	101.12	OA	226	60	30.0	44.45
161	6000	203.85	OA				

*115 or 240v sec only. State volts required.
Pri 0-220-240V.

30 VOLT RANGE
Sec. Volts available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V

Ref.	30v	15v	£	P&P
112	0.5	1	3.19	1.20
79	1	2	4.32	1.40
3	2	4	6.99	1.60
20	3	6	8.10	1.85
21	4	8	9.67	1.90
51	5	10	11.95	2.00
117	6	12	13.52	2.02
88	8	16	18.10	2.26
89	10	20	20.88	2.24
90	12	24	23.20	OA
91	15	30	26.60	3.00
92	20	40	35.64	4.83

50 VOLT RANGE
2x25V tapped sec's. Volts available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 20V-0-20V or 25V-0-25V

Ref.	50v	25v	£	P&P
102	0.5	1	4.13	1.40
103	1	2	5.03	1.40
104	2	4	8.69	1.84
105	3	6	10.36	1.90
106	4	8	14.10	2.12
107	6	12	16.37	1.84
118	8	16	24.52	2.70
119	10	20	30.23	OA
109	12	24	38.18	OA

60 VOLT RANGE
Pri 0-120Vx2
2x30V tapped sec's volts available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V; or 24V-0-24V or 30V-0-30V

Ref.	60v	30v	£	P&P
124	0.5	1	4.70	1.50
126	1	2	7.15	1.50
127	2	4	9.20	1.90
125	3	6	13.31	2.02
123	4	8	15.15	2.26
40	5	10	19.16	2.24
120	6	12	21.88	2.64
121	8	16	30.72	OA
122	10	20	35.76	OA
189	12	24	41.22	OA

400/440V ISOLATORS
400/440 to 200/240V

VA	Ref.	£	P&P
60	243	8.11	1.50
250	246	16.07	OA
350	247	19.88	OA
500	248	24.77	OA
1000	250	50.53	OA
2000	252	74.79	OA
3000	253	104.86	OA
6000	254	207.92	OA

SCREENED MINIATURES Pri 240V

Ref.	mA	Sec Volts	£	P&P
238	200	3-0-3	3.11	1.90
212	1A, 1A	0-6, 0-6	3.45	1.20
13	100	0-0-9	2.59	.80
235	330, 330	0-9, 0-9	2.41	.90
207	500, 500	0-8-9, 0-8-9	3.36	1.20
208	1A, 1A	0-8-9, 0-8-9	4.27	1.40
236	200, 200	0-15, 0-15	2.41	.90
239	50mA	12-0-12	3.11	.90
214	300, 300	0-20, 0-20	3.39	1.20
221	700 (DC)	20-12-0-12-20	4.13	1.20
206	1A, 1A	0-15-20, 0-15-20	5.60	1.60
203	500, 500	0-15-27, 0-15-27	4.63	1.50
204	1A, 1A	0-15-27, 0-15-27	7.30	1.60

AUTO TRANSFORMERS
Voltages available 105, 115, 190, 200, 210, 220, 230, 240. For step up or step down.

Ref.	VA (Watts)	TAPS	£	P&P
113*	15	0-10-115-210-240V	2.39	1.20
64	80	0-10-115-210-240V	4.84	1.40
67	150	0-10-115-210-240V	6.48	1.20
84	1000	0-10-115-210-240V	22.70	2.24
93	1500	0-10-115-210-240V	28.17	2.80
95	2000	0-10-115-210-240V	42.14	OA
73	3000	0-10-115-210-240V	71.64	OA
80s	4000	0-10-115-210-240V	93.01	OA
57s	5000	0-10-115-210-240V	108.30	OA

CASED AUTOS
240V cable input USA 115V outlets

VA	Price	P&P	Ref
20	£7.21	1.25	56W
80	£9.35	1.50	64W
150	£12.10	1.84	4W
200	£12.02	1.44	65W
250	£14.73	1.80	69W
500	£22.14	2.24	67W
1000	£33.74	2.80	84W
2000	£80.47	OA	95W

CONSTANT VOLTAGE TRANSFORMERS
For 'clean' mains to computers, peripherals...
250VA £137.36 + P&P
500VA £159.43 + P&P
1KVA £213.12 + P&P

TOROIDALS NOW AVAILABLE
EX-STOCK
30VA 60VA 100VA 160VA 230VA 330VA 530VA
Send stamp for list
PLEASE ADD 15% VAT AFTER P&P
Overseas post extra

OTHER PRODUCTS

AVO TEST METERS
8 Mk 5 Latest Model £122.10
71 (Electronics & TV Service) £49.30
MM5 Minor £43.60
DA211 LCD Digital £58.50
DA212 LCD Digital £81.90
DA116 LCD Digital £131.30
Megger 70143 500v Megger Battery BM7 £71.60
Avo Cases and Accessories P&P £1.32 + VAT 15%

7.5-0-7.5V (15VCT)

Ref.	Amp	Price	P&P
171	500mA	2.53	.90
172	1A	3.59	1.20
173	2A	4.35	1.20
174	3A	4.54	1.20
175	4A	6.93	1.40

MAINS BATTERY ELIMINATORS
No wiring, ready to



COMPUTER WAREHOUSE

**NOW OPEN
MONDAY-SATURDAY
9.30-5.30**

**BULK
BUY
SPECIALS**

RAM SCOOP

4116 200 NS 8 for £12.95
4164 200 NS £8.50 each
2102-650 NS 8 for £5.50
INC VAT

25 WAY "D" CONNECTORS

50+ 100+
25p 1.70 1.10 0.95
25s 1.90 1.20 1.00
ALL + VAT

WIRE WRAP SKTS.

24 Pin Vero 28p
14 Pin Gold 22p
16 Pin Gold 24p
100 PCS Min Ord.


C10 DATA CASSETTES

10 for £5.75
INC. VAT

RF CONNECTORS

50Ω BNC PLG 50p
75Ω BNC PLG 50p
PL259 PLG 40p
S0239 SKT 35p
100 PCS MIN ORD.

TELETYPE ASR33 I/O TERMINALS

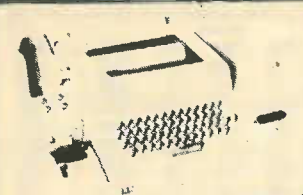

From £195 + CAR + VAT
Fully fledged industry standard ASR33 data terminal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT
KSR33 With 20ma loop interface £125.00 + VAT.
Sound proof enclosure £25.00 + VAT

"OLIVETTI TE300" PRINTER/TERMINALS



A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input-output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat

MPU EXPERIMENTORS +5v, 12v, 12v, 24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 160mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:
+5v @ 2 amps DC +12v @ 800 ma DC
-12v @ 800 ma DC +24v @ 350 ma DC
and if that's not enough a fully floating 5v output @ 50 ma DC which may be sensed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!!

STOP PRESS

SUPER SCOOP CENTRONICS 739-2 PRINTERS

£299+VAT+£10 carr.
Datasheet on request

DISTEL ©

"Dial our Database!"

Get information on 1000's of stock items and order via your computer. 300 baud on 01-689 6800
18.30 to 0900 6 days a week and all day Sundays. IT'S FREE!

DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.
S30 front loader, pack change via front door £550 + vat
S30 fixed, pack change via removal of top cover £295 + vat
+ & - 15v PSU for 2 drives £125 + vat
Carriage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

MAINS FILTERS

Professional type mains filters as used by 'Main Frame Manufacturers' ideal for curing those unenvying hang ups and data glitches, fit one now and cure your problems! Suppression Devices SDS A10 5 amp £6.95
Corcom Inc F1900 30 amp £13.95 + pp £1.00

DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240 V ac input with the following DC outputs 5V @ 11 amps +15-17v @ 8 amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 8"

NATIONAL MA1012 LED CLOCK MODULE

★ 12 HOUR
★ ALARM
★ 50/60 HZ

The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only
Suitable transformer £1.75. **£5.25**


ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

**66%
DISCOUNT**

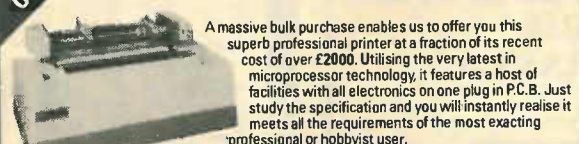2.5kds £ 4.75 + pp £1.25 5kds £ 6.75 + pp £1.80
10kds £11.75 + pp £2.25 20kds £19.99 + pp £4.75

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232C/V24 serial interface ★ 7x120mm controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eproms easily reconfigured for custom fonts etc.

All this and more, not refurbished but BRAND NEW At Only **£525 +VAT**

8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring, IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART. BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.

7100 single sided £225.00 + 9.50 carr + vat
7200 double sided £295.00 + 9.50 carr + vat
full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive.
Data sheet on request.
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat
8" single sided, single or double density diskettes £1.80 each £15.00 for 10 **2b case + vat.**

COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.
ETRI99XU01 Miniature equipment fan 240 vac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Makers price £16 our price £10.25
BUHLER 69.11.22 micro miniature 8-16 VDC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor, almost silent running ideal portable equipment. Life in excess of 10,000 hours. BRAND NEW manufacturers price £32.00 our price £13.95
MUFFIN/CENTAUR cooling fans, tested ex equipment 240v £6.50, 115v £5.50 + p.p. £1.90
KOOL TRONICS Powerful snail type blower gives massive air movement with centrifugal rotor. DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50 Hz ac working ONLY £9.95 + £1.90 p.p.

ELECTRONICS

Dept. W.W., 64-66 Melfort Rd., Thornton Heath, MAIL ORDER
Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800 INFORMATION
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £20.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fide account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

SOFTY 1 & 2

EPROM BLOWER
Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.
Softy 2 for 2716/2732 **£169 + VAT**
Write of phone for more details.

9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. **£39.99 + £7.50 carriage + VAT. Complete with circuit.**

SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge recs., etc. etc. All devices guaranteed brand new full spec with manufacturer's markings, fully guaranteed. 50+ bag £2.95 100+ bag £5.15 TTL 74 Series
A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy.
Fully guaranteed at I.C.'s full spec. 100+ £6.90 200+ £12.30 300+ £19.50

RCA FULLY CASED ASCII CODED KEYBOARDS

IDEAL -
TANGERINE,
OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5v rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. **£43.95**
VP611 Same as VP601 with numeric pad. **£54.95**
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. **£64.26**
VP616 Same as VP606, with numeric pad, plug and cable for VP601, VP611 **£2.25**
Plug for VP606, VP616 **£2.10**
Post, Packing and Insurance. **£1.95**
ORDER NOW OR SEND FOR DETAILS.

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply.
Supplied complete with circuit at only **£10.95 + £1.75pp.** Believed working but untested, unguaranteed.

To obtain further details of any of the coded items mentioned in the Editorial or Advertisement pages of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct in due course. Cards posted from abroad require a stamp. These Service Cards are valid for six months from the date of publication.

Please Use Capital Letters

If you are way down on the circulation list, you may not be getting the information you require from the journal as soon as you should. Why not have your own copy?

To start a one year's subscription you may apply direct to us by using the card at the bottom of this page. You may also apply to the agent nearest to you, their address is shown below.

OVERSEAS SUBSCRIPTION AGENTS

- Australia:** Gordon & Gotch (Australia) Ltd, 380 Lonsdale Street, Melbourne 3000, Victoria
- Belgium:** Agence et Messageries de la Presse, 1 Rue de la Petite-ILE Brussels 7
- Canada:** Davis Circulation Agency, 153 St. Clair Avenue West, Toronto 195, Ontario
- Cyprus:** General Press Agency Ltd, 131 Prodromou Street, P.O. Box 4528, Nicosia
- Denmark:** Dansk Bladdistribution, Hovedvagtsgade 8, Dk. 1103 Kobenhavn.
- Finland:** Reutakirja OY, Koivuvaarankuja 2, 01640 Vantaa 64, Finland.
- France:** Dawson-France S.A., B.P.40, F-91121, Palaiseau
- Germany:** W. E. Saarbach GmbH, 5 Koln 1, Follenstrasse 2
- Greece:** Hellenic Distribution Agency, P.O. Box 315, 245 Syngrou Avenue, Nea Smyrni, Greece.
- Holland:** Van Diltmar N.V., Oostelijke Handelskade 11, Amsterdam 1004
- India:** International Book House, Indian Mercantile Mansion Ext, Madame Cama Road, Bombay 1
- Iran:** A.D.A., 151 Khaban Soraya, Tehran
- Israel:** Stelmatsky's Agency Ltd, Citrus House, P.O. Box 828, Tel Aviv
- Italy:** Intercontinental S.A.S. Via Veracini 9, 20124 Milano
- Japan:** Western Publications Distribution Agency, 170 Nishi-Okubo 4-chome, Shinjuku-Ku, Tokyo 160
- Lebanon:** Levant Distributors Co., P.O. Box 1181, Makdesi Street, Halim Hanna Bldg, Beirut
- Malaysia:** Times Distributors Sdn. Bhd., Times House, 390 Kim Seng Road, Singapore 9, Malaysia.
- Malta:** W. H. Smith Continental Ltd, 18a Scots Street, Valletta
- New Zealand:** Gordon & Gotch (New Zealand) Ltd, 102 Adelaide Road, Wellington 2
- Nigeria:** Daily Times of Nigeria Ltd, 3 Kakawa Street, P.O. Box 139, Lagos
- Norway:** A/S Narvesens Kioskompagni, Bertrand Narvesens vei 2, Oslo 6
- Portugal:** Liversia Bertrand s.a.r.l Apartado 37, Amadora
- South Africa:** Central News Agency Ltd, P.O. Box 1033, Johannesburg
- Spain:** Comercial Athenum s.a. Consejo de Ciento, 130-136 Barcelona 15
- Sweden:** Wennegren Williams A.B. Fack S-104, 25 Stockholm 30
- Switzerland:** Neville & Cie S.A. Rue Levrier 5-7, CH-1211 Geneva 1 Schmidt Agence AG, Savogelstrasse 34, 4002 Basle
- U.S.A.:** John Barrios, IPC Business Press, 205 East 42nd Street, New York, N.Y. 10017

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No 12045

WIRELESS WORLD
Reader Enquiry Service
429 Brighton Road
South Croydon
Surrey CR2 9PS

Enquiry Service for Professional Readers **WIRELESS WORLD** Wireless World, July 1982 WW 267

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Name of Company

Address

Telephone Number

PUBLISHERS USE ONLY		A/E	
---------------------	--	-----	--

Position in Company

Nature of Company/Business

No. of employees at this establishment

I wish to subscribe to Wireless World

VALID FOR SIX MONTHS ONLY

Wireless World: Subscription Order Form

To become a subscriber to Wireless World please complete the reverse side of this form and return it with your remittance to:

**Subscription Manager,
IPC Business Press,
Oakfield House, Perrymount Road,
Haywards Heath, Sussex RH16 3DH,
England**

U.S.A.: John Barrios, IPC Business Press, 205 East 42nd Street, New York, N.Y. 10017

Enquiry Service for Professional Readers ONLY.

WIRELESS WORLD Wireless World, July 1982 WW 267

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Position in Company

Name of Company

Address

Telephone Number

Nature of Company/Business

No. of employees at this establishment

VALID FOR SIX MONTHS ONLY

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No 12045

WIRELESS WORLD
Reader Enquiry Service
429 Brighton Road
South Croydon
Surrey CR2 9PS

Wireless World Subscription Order Form Wireless World, July 1982 WW 267

UK subscription rates
1 year: £12.00

USA & Canada subscription rates
1 year: \$39.00

Overseas 1 year: £15.00

Please enter my subscription to Wireless World for 1 year

I enclose remittance value.....made payable to
IPC BUSINESS PRESS Ltd.

Name

Address



BEFORE



AFTER!

PUT A SMILE BACK ON
YOUR OLD AVOMETER!

Send it now for estimate,
repair or recalibration

Quick turn round
on estimates/repairs

Large stocks of new
AVOMETERS

Avo Sales and Service

Farnell International

Farnell International Instruments Ltd.,
Sandbeck Way, Wetherby
West Yorkshire LS22 4DH

Tel 0937 61961 Telex 55478 Farint G

WW-004 FOR FURTHER DETAILS

YOU DON'T NEED ME TO DETECT CROTECH'S VALUE

Its elementary. Just look at the **3030** at £150 and the **3131** at £240, both are 15MHz scopes with 5mV/Div maximum deflection coefficient. And the Dual Trace 3131 has matched X-Y, Algebraic Add and Subtract, and TV Trigger, all selected on easy to use clearly marked push buttons.

But that's not all, both incorporate a Component Tester, yes, even the Single Trace 3030, for the in or out of circuit testing of semiconductor and passive devices. With the resultant characteristic being displayed directly on the CRT.

Theres only one thing left to say . . .
Do you want a Violinist?

For full details just fill in the enquiry card or call us direct.

Crotech Instruments Limited
5 Nimrod Way · Elgar Road · Reading · Berkshire
RG2 0EB · United Kingdom
Telephone: (0734) 866945 · Telex: 847073 POWLIN G

WW - 010 FOR FURTHER DETAILS

JOIN THE PROFESSIONALS...

If you are looking for amplification, take advantage of the same superb quality Crimson modules that the BBC, IBA, KEF and numerous recording studios have been using for years! Our expertise in this field of electronic design is internationally renowned, our reputation is based on quality, reliability and value for money and when it comes to technology, our modules feature possibly some of the world's most advanced audio circuitry yet devised. The Crimson range of audio amplifier modules is available to industry and public alike and is backed by full technical data, free technical advisory service, fast delivery and a full range of complimentary components available such as toroidal power supplies and heatsinks, etc.

SPECIFICATIONS

Type	O/P 8ohms*	O/P 4ohms	PSU	H/sinks	Slew limit	S/N	Sensitivity	THD (typ)	FR (-3dB)	Size
CE 608	38	—	CPS 80	H550	30VU5	110dB	775mV	0.0035%	1.5Hz-50KHz	80-120-25
CE1004	44	70	CPS150	H550/100	30VU5	110dB	775mV	0.0035%	1.5Hz-50KHz	80-120-25
CE1008	65	—	CPS150	H550/100	30VU5	110dB	775mV	0.0035%	1.5Hz-50KHz	80-120-25
CE1704	85	121	CPS250	H5100/150/FM1	30VU5	110dB	775mV	0.0035%	1.5Hz-50KHz	80-120-25
CE1708	125	—	CPS250	H5100/150/FM1	30VU5	110dB	775mV	0.0035%	1.5Hz-50KHz	80-120-25
CE3004	170	250	CPS250	H5150/FM2	30VU5	110dB	775mV	0.008 %	1.5Hz-50KHz	161-102-35
CPR1X	output	775mV	REG1	—	3VU5	70dB	2.8mV	0.008 %	10Hz-50KHz	138-80-35
MC1X	output	2mV	REG1	—	3VU5	65dB	70/150UV	0.008 %	10Hz-50KHz	80-120-35
XO2/3	output	775-2500mV	REG1	—	9VU5	90dB	775mV	0.01 %	Preset	150-50-20

* Power output is quoted in WRMS and is given for two modules off the same power supply. Higher powers can be obtained if using our dual power supplies or one module per PSU or if using a stabilised power supply.

NEW: We now have a completely new Hi-Fi Kit package to offer:
CK 1010 contains pre-amp circuitry, all metalwork, connectors, wire, etc., to make a complete pre-amplifier.
CK 1040 contains power amp modules, all metalwork, dual power supply, connectors, heatsinks, wire, etc., to make a complete 40 w/channel power amplifier.
CS 1100 as CK 1040 but at 100 w/channel

Unlike other module manufacturers CRIMSON have a major share of the esoteric, specialist Hi-Fi market. Unlike many manufacturers we acknowledge the massive audible differences that small component/circuit changes can produce. However our amplifiers are technically outstanding and have been subjectively 'tuned' to a stunning level of crisp and detailed reproduction.

All prices include VAT. Please add £1.10 for orders up to £20.00, £2.50 up to £50 and £2.65 £50 and over. To allow for post and packing (UK only).
 Export—No problem. Please write for quotation or quote your Visa/Master-Charge card number.

CRIMSON modular audio amplifiers feature
 * low values of transient and steadystate distortions * envelope distortion (below 500 Hz) less than 0.05% * on board electronic protection * PCB pin and edge connector termination * full range of complimentary components available ie. PSUs, heatsinks, etc.

PRICES

Power amp modules	Power supply modules	Heatsinks			
CE 608	£21.00	CP580	£26.24	HS 50	£ 1.84
CE1004	£24.50	CP580D	£31.77	HS100	£ 2.99
CE1008	£27.50	CPS150	£29.74	HS 50	£ 4.20
CE1704	£35.00	CPS150D	£36.40	FM1	£36.95
CE1708	£35.00	CPS250	£36.83	FM2	£41.52
CE3004	£49.00	CPS250D	£45.34		

Pre amp modules
 CPR1X £36.00
 MC1X £32.00
 REG1 £ 9.30
 TR6 £ 3.30

Active crossovers
 XO2
 XO3
 MU1

COMPLETE KITS
 PRE-AMP CK1010£90.00
 POWER AMP CK1040£119.00
 POWER AMP CK1100£149.00
 (MOVING COIL ADD-ON£25.00)

Crimson Elektrik
 9 Claymill Road, Leicester LE4 7JJ • Tel 0533 761920 • Telex 34964 Chamco C Crimlek

Please send more details of all CRIMSON Elektrik amplifier modules

Name
 Address

Ref: WW7

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	.95	.85	.70
4116 250ns	.90	.80	.65
4816 100ns For BBC comp	3.30	2.95	2.70
4164 200ns	6.15	5.25	4.65
AN612	1.25	1.15	.95
2114 200ns Low power	1.20	1.10	.90
2114 450ns Low power	1.20	1.10	.90
4118 250ns	3.45	3.15	2.65
6116 150ns CMOS	4.95	4.45	3.65
2708 450ns	1.95	1.90	1.80
2716 450ns 5 volt	2.25	2.15	1.95
2716 450ns three rail	6.40	6.00	4.95
2732 450ns Intel type	4.25	3.95	3.35
2532 450ns Texas type	4.25	3.95	3.35

Z80A-CPU £4.75 Z80A-P10 £4.25 Z80A-CTC £4.25

Low profile IC sockets: Pins 8 14 16 18 20 22 24 28 40
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case:
5 inch SSSD £17.00 5 inch SSD £19.25 5 inch DSDD £21.20
8 inch SSSD £19.25 8 inch SDD £23.65 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or telephone for list.

Please add 30p post & packing to orders under £15 and VAT to total. Access & Barclaycard welcome. 24hr. service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated.

Telephone or write for details:

HAPPY MEMORIES (WW)
Gladestry, Kingston
Herefordshire HR5 3NY
Tel. (054 422) 618 or 628

TEST EQUIPMENT

Tequipment D75 Scope	£550
Tek. 2901 Time/Mark Gen.	£150
Tek. 191 Const. Amp. Gen.	£155
Tek. 577 Storage Curve Tracer	£1,750
Tek. 577 Non-Storage C/Tracer	£1,000
Tek. 545A Main Frame	£50
Tek. 521A Vectorscope	£1,750
Tek. 1030 Spec. Anal. Plug-in	£250
Tek. 5103 Storage Scope complete	£775
Tek. 475 200MHz Portable	£1,750
H.P. 140A Mainframe	£75
H.P. 1400A, 1422, 1401 Plug-in, each	£35
H.P. 5246L/5253B 500MHz Counter	£130
H.P. 1707B 75MHz Scope	£550
Singer Synchro Test System	£750
Marconi TF2700 Bridge	£175
Bryans X-Y Recorders	£135
Data Dynamics Teletype	£125
R & S Polyskop II	£250
Flann WG16 90dB Rotary Atten. (New)	£375
Optimization AC Calibrator System	£950
Hitachi VT8300 Video Recorders. (New)	£450
525/625 Line Monitor Servicing Gens.	£185

All prices exc. VAT. Carriage extra

TIMEBASE

94 ALFRISTON GARDENS
SHOLING, SOUTHAMPTON
SO2 8FU
TEL. 431323 (0703)

Callers welcome

Access, Barclaycard
Telephone your order

WW 082 - FOR FURTHER INFORMATION

PM COMPONENTS LTD

VALVE & COMPONENTS SPECIALISTS

PHONE
0474 813225
3 LINES

P. M. COMPONENTS LTD

SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
965966
WEST ST G

INTEGRATED CIRCUITS

AN124	2.60
AN124Q	2.60
AN240P	2.90
AN612	3.25
AN7150	2.95
BA551	3.35
BRC1330	0.76
BT1822	2.10
ETT6016	1.75
HA1151P	2.50
HA1268W	2.95
LA3350	2.50
LA4031P	2.70
LA4032P	2.50
LA4400	4.15
LC7120	3.50
LC7130	3.50
LC7137	5.50
LC7137	5.50
LM380N	1.90
M51513L	2.30
M51515L	2.50
MB3712	2.00
MC1307P	1.00
MC1310P	1.50
MC1327	1.50
MC1350P	0.76
MC1349P	0.78
MC1350P	0.78
MC1351P	1.30
MC1352P	1.00
MC1357	2.50
MC1495	3.00
MC140118CP	0.32
ML231B	1.75
ML232B	1.75
ML237B	1.95
ML238B	4.20
ML239B	2.10
ML230	4.12
ML222	3.29

SEMICONDUCTORS

AC126	0.22
AC127	0.20
AC128	0.20
AC128K	0.32
AC141K	0.30
AC142K	0.34
AC176K	0.22
AC187	0.18
AC187K	0.22
AC188K	0.22
AD142	0.80
AD143	0.87
AD149	0.70
AD161	0.39
AD182	0.39
AD161/2	0.39
AF124	0.34
AF125	0.32
AF126	0.32
AF127	0.32
AF128	0.32
AF150	0.42
AF239	0.42
AJ106	2.08
AJ107	1.75
AJ110	2.00
AJ113	1.85
BC107	0.10
BC107A	0.10
BC107B	0.10
BC108	0.10
BC108A	0.10
BC108B	0.10
BC109	0.10
BC109B	0.10
BC114	0.10
BC116	0.13
BC117	0.19
BC119	0.24
BC125	0.12
BC140	0.30
BC141	0.25
BC142	0.24
BC143	0.24
BC147	0.25
BC148A	0.09
BC148B	0.09
BC149	0.09
BC157	0.10

DIODES

AA119	0.68
BA102	0.17
BA115	0.13
BA145	0.16
BA148	0.17
BA155	0.16
BA156	0.15
BAX13	0.04
BAX16	0.06
BB105B	0.30

WIREWOUND RESISTORS

4 Watt	4R7-1K8	0.15
	K2K-6K3	0.15
	10K	0.24
7 Watt	R47-4K7	0.18
	5K6-12K	0.19
	15K-22K	0.24
11 Watt	1R-10K	0.20
	15K-22K	0.24
17 Watt	1R-10K	0.26
	15K-22K	0.28

BASES ETC.

B7G Skirted	0.15
B8G	0.30
B9A	0.20
B9A Skirted	0.30
B10B	0.18
B13B	0.16
8 Pin DIL	0.10
14 Pin DIL	0.12
14 Pin DIL	0.10
16 Pin DIL	0.15
OCTAL	0.35
CANS	0.27

ZENER DIODES

BZX61 0.15	6V2 7V5 8V2 9V1 10V 11V 12V 13V 15V 16V 18V 20V 22V 24V 27V 30V 33V 36V 39V 47V 51V 56V 68V 75V
BZY88 0.07	2V7 3V 3V3 3V6 3V9 4V3 4V7 5V 5V6 6V 6V8 7V5 8V2 9V1 10V 11V 12V 13V 15V 16V 18V 20V 22V 24V 27V 30V

THERMISTORS

VA1040	0.23
VA1055	0.23
VA1104	0.70
VA850	0.45

BATTERIES

7V Power Mike	batteries
TR175 £1.40 ea	
other prices on request	

A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714	14.50
A1998	11.50
A2087	11.50
A2134	14.50
A2293	7.20
A2426	22.50
A2521	19.00
A2589	37.50
A2800	15.00
A3042	24.00
AC/HL/DD	2.50
AC/PHI	2.50
AC/PEN	2.50
AC/SP3	4.50
ACP	3.50
ACVP1	3.50
ACVP2	3.50
AH201	1.50
AH221	39.00
AH238	31.50
AP4	1.50
APV4	1.50
ARB	0.70
ARP12	0.70
ARP3	0.70
ARP36	1.50
ARPP2	1.50
AU13	1.50
AZ31	2.00
B2A	6.00
B36	1.85
B719	0.80
B729	1.20
B733	1.20
B742	1.20
B810	63.00
B818	43.50
BT17A	35.00
BT19	32.50
CK	14.00
C3JA	18.00
C143	18.50
C180	18.50
C1108	58.00
C1111	15.50
C1112	52.15
C1134	16.50
C1148A	1.00
C1534	32.00
CB131	2.00
CCA	2.00
CL30	1.85
CMG25	1.50
CMG29	10.00
CMV25	10.85
CV Nos	prices on request
D3a	38.00
D63	0.80
DA107	6.00
DAC32	1.20
DAF91	0.45
DAF92	0.45
DCX4-1000	35.00
DCX4-1000	35.00

VALVES

BD139	0.32
BD193	0.30
BD159	0.65
BD166	0.46
BD179	0.72
BD182	0.70
BD191	0.83
BD202	0.65
BD203	0.78
BD204	0.70
BD222	0.48
BD223	0.48
BD225	0.48
BD233	0.35
BD234	0.35
BD236	0.45
BD237	0.40
BD238	0.40
BD240	0.55
BD243A	0.55
BD247	0.60
BD251	0.60
BD252	0.60
BD253	0.60
BD254	0.60
BD255	0.60
BD256	0.60
BD257	0.60
BD258	0.60
BD259	0.60
BD260	0.60
BD261	0.60
BD262	0.60
BD263	0.60
BD264	0.60
BD265	0.60
BD266	0.60
BD267	0.60
BD268	0.60
BD269	0.60
BD270	0.60
BD271	0.60
BD272	0.60
BD273	0.60

VALVES

BF336	0.34
BF337	0.29
BF338	0.32
BF355	0.37
BF362	0.38
BF363	0.38
BF371	0.20
BF394	0.19
BF457	0.23
BF458	0.28
BF459	0.28
BF460	0.28
BF461	0.28
BF462	0.28
BF463	0.28
BF464	0.28
BF465	0.28
BF466	0.28
BF467	0.28
BF468	0.28
BF469	0.28
BF470	0.28
BF471	0.28
BF472	0.28
BF473	0.28
BF474	0.28
BF475	0.28
BF476	0.28
BF477	0.28
BF478	0.28
BF479	0.28
BF480	0.28
BF481	0.28
BF482	0.28
BF483	0.28
BF484	0.28
BF485	0.28
BF486	0.28
BF487	0.28
BF488	0.28
BF489	0.28
BF490	0.28
BF491	0.28
BF492	0.28
BF493	0.28
BF494	0.28
BF495	0.28
BF496	0.28
BF497	0.28
BF498	0.28
BF499	0.28
BF500	0.28

VALVES

BF501	0.28
BF502	0.28
BF503	0.28
BF504	0.28
BF505	0.28
BF506	0.28
BF507	0.28
BF508	0.28
BF509	0.28
BF510	0.28
BF511	0.28
BF512	0.28
BF513	0.28
BF514	0.28
BF515	0.28
BF516	0.28
BF517	0.28
BF518	0.28
BF519	0.28
BF520	0.28
BF521	0.28
BF522	0.28
BF523	0.28
BF524	0.28
BF525	0.28
BF526	0.28
BF527	0.28
BF528	0.28
BF529	0.28
BF530	0.28
BF531	0.28
BF532	0.28
BF533	0.28
BF534	0.28
BF535	0.28
BF536	0.28
BF537	0.28
BF538	0.28
BF539	0.28
BF540	0.28
BF541	0.28
BF542	0.28
BF543	0.28
BF544	0.28
BF545	0.28
BF546	0.28
BF547	0.28
BF548	0.28
BF549	0.28
BF550	0.28

VALVES

BF551	0.28
BF552	0.28
BF553	0.28
BF554	0.28
BF555	0.28
BF556	0.28
BF557	0.28
BF558	0.28
BF559	0.28
BF560	0.28
BF561	0.28
BF562	0.28
BF563	0.28
BF564	0.28
BF565	0.28
BF566	0.28
BF567	0.28
BF568	0.28
BF569	0.28
BF570	0.28
BF571	0.28
BF572	0.28
BF573	0.28
BF574	0.28
BF575	0.28
BF576	0.28
BF577	0.28
BF578	0.28
BF579	0.28
BF580	0.28
BF581	0.28
BF582	0.28
BF583	0.28
BF584	0.28
BF585	0.28
BF586	0.28
BF587	0.28
BF588	0.28
BF589	0.28
BF590	0.28
BF591	0.28
BF592	0.28
BF593	0.28
BF594	0.28

★ SOLE UK BULLET AGENT ★ SOLE UK BULLET AGENT

APPLEDORE ELECTRONICS ^{AE}
(Proprietor: M. J. Nurse)
4 MEETING STREET, APPLEDORE, NEAR BIDEFORD, NORTH DEVON EX39 1RJ
TELEPHONE: BIDEFORD (S.T.D. Code 02372) 5629

ORDERING INFORMATION: TERMS OF BUSINESS
- CASH/CHEQUE/P.O.s OR BANKER'S DRAFT
WITH ORDER, GOVERNMENT AND EDUCATIONAL
INSTITUTIONS' OFFICIAL ORDERS ACCEPTED.
TRADE AND EXPORT INQUIRY WELCOME. P. AND
P. ADD 60p, EXPORT ORDERS ADD £2

SE-01 Sound Effects Kit
The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and posts to program the various combinations of the SIF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op. Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4in. x 3in. PCB board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosion, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 74677 chip specifications. It runs on a 9v battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included.)
Main chip SN76477 is included in kit.
COMPLETE KIT ONLY £16

AY-3-8910
CLANG BEEP ZAP!
COMPUTER SOUND CHIP. The amazing AY-3-8910 is a fantastically powerful sound and music generator, perfect for use with any 8-bit microprocessor. Contains 3 tone channels, noise generator, 3 channels of amplitude controls, 16-bit envelope period control, 2 parallel I/O, 3D/A converters plus much more. All in 40-pin DIP Super easy to interface to the S100 or other Busses.
£5.50 EACH
£2.25 for 60-page data manual

SN76477N SOUND CHIP
£1.60 each
Data £1

A single chip versatile SOUND EFFECTS GENERATOR SN76477N, is ideally suited for applications such as arcade or home video games, alarms, sound effects boxes and toys.

EPROM 2716
Single 5v 450ns
£2.25 EACH

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED

The DOOMSDAY Alarm
THE BEST NOISE-MAKER FOR BURGLAR ALARM
Four separate adjustable oscillators are mixed, stepped and disabled at a rate that is adjustable. The 10-watt output gives ear-splitting volume. The kit comes with all electronics and drilled and plated PC board. Requires 12v DC at 1 amp. Also reqs. 8 ohm speaker (not included). TOTALLY DEFIES INATTENTION.
£10 COMPLETE KIT

CLOCK KIT ZULU II
★ Operates on 12v AC or 12v DC
★ On board XTAL timebase
★ Automatic battery back-up
★ 24-hour format and 31-day calendar
★ 1/2in. readouts show hrs., mins., secs.
★ Unique NOX™ circuit activates readouts with a handclap
★ Readouts can be constantly on
★ Special noise suppression and a battery reversal circuit
COMPLETE KIT £14.50 EACH
Case optional extra
Plastic Case in BLUE with ruby lens £4.95

Music Boxes
Commercial Toys
★ BULLET ★
NEW SUPER MUSIC MACHINE KIT!
AT LAST - an affordable kit that can be PROGRAMMED TO PLAY ANY SONG OR GROUP OF SONGS! Instead of a nightmare of numerous ICs and special expensive Bipolar ROMs the SUPER MUSIC MACHINE uses a SPECIAL MASK PROGRAMMED COMPUTER CHIP, one CMOS gate and the most popular erasable EPROM, the 2708/2716 series. BASIC KIT includes drilled, plated and screened PCB board and ALL components except the EPROM and 12v transformer. The basic kit will play short renditions of 25 tunes through its 7-WATT AMPLIFIER SECTION. Add an optional ROM and any tune programmed will be played.
FEATURES:
★ Basic kit contains 25 short tunes in the main IC.
★ Will address external ROM for up to 1,000 MORE NOTES per ROM (ROM is not included).
★ Operates on 12v AC or 12v DC at 500mA (using unit on 12v DC and with optional ROM requires 9v bias battery, not included).
★ 7 watts of audio power will drive 8 or 16 ohm speakers or horn speakers (not included).
★ DIP switches not included.
★ NEXT TUNE provision steps sequentially through all tunes.
★ Tune address can be wire jumper selected or board is designed to take DIP switches.
★ PITCH, VOLUME and TEMPO are all adjustable.
★ SPECIAL 'CHIME' SEQUENCES can be activated regardless of tune address to provide for multiple doorbell applications.
★ All tunes consist of electronic musical notes played one at a time. There are no chords or harmony sound to the music.
★ STEP-BY-STEP ASSEMBLY INSTRUCTIONS provided.
COMPLETE KIT £21

★ SOLE UK BULLET AGENT ★ SOLE UK BULLET AGENT

WW-083 FOR FURTHER DETAILS

19" Rack Mounting Cabinet - Or Free Standing

£23.95
£19.50

OFFER ENDS SOON

Front Panel 480x150 mm. Rear Case 425x250x140 mm
★ Top, bottom and rear cover removable for access ★ Plates have heavy duty grey paint finish ★ Front panel is heavy gauge - 3mm aluminium ★ Strong, screwed, construction throughout - screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panel is of brushed aluminium finish enhanced with heavily chromed handles ★

Many sold to 'TANGERINE' users and INDUSTRY

ADD VAT AT STD. RATE & ORDERS UNDER £5. P&P 50p ABOVE ITEMS £1 P&P

Ask for our FREE Catalogue

'metal cabinets'

a £1.70
b £2.55
c £3.04
d £4.08

SLIDE SWITCHES

1P2T 10p
2P2T pcb 12p
2P2T 12p
2P3T 20p
1P4T pcb 26p
4P2T pcb 28p
4P3T pcb 35p
6P3T pcb 42p
4P4T pcb 45p

Bridge WOODS 16p

EXPORT EXPORTEUR

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of
WIRELESS WORLD
why not take advantage of our reprint service.
Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)
For further details contact
Michael Rogers, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To Michael Rogers, Reprints Department
Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS

I am interested in copies of the article / advertisement headed featured in
WIRELESS WORLD
on page(s) in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife), louvred for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

DIODES 1N4002 - 3p
1N4148 - 2p 1N4003 - 4p
1N4001 - 3p 1N4004 - 5p

TRADE P.O.A.
"SEIKO"
80w Iron
£2.95

RELAY-A-QUIP PRODUCTS

Moat Lodge, Stock Chase
MALDON, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.

WW - 086 FOR FURTHER DETAILS

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of
WIRELESS WORLD
why not take advantage of our reprint service.
Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)
For further details contact
Michael Rogers, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To Michael Rogers, Reprints Department
Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS

I am interested in copies of the article / advertisement headed featured in
WIRELESS WORLD
on page(s) in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

C.T. ELECTRONICS (ACTON) LTD.
Registered in England 11 79820
267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-747 1555 01-994 6275
Telex 291429 9.30 a.m. - 6 p.m. MON.-SAT. CONTINUOUS

STABILISED POWER SUPPLIES
FARNELL A15: 210/240V 1P. Dual Op. 12-17v per rail at 100mA. Remote sensing, current limit protection. (164x130x38mm), with manual. £12.
COUTANT OA2: Op. amp, psu, 120/240V IP. Dual Op. 12-15v at 100mA. (138x80x45mm.) £12 ea. or 2 for £22.
BRANDENBURG Photomultiplier PSU. 19in. rack mounting. Metered, current limit protection.
374 300V-1KV at 5mA 376 660V-1K6V at 10mA
375 500V-1K5V at 6mA. All models £40.
PIONEER MAGNETICS POWER SUPPLIES . . . 5V 150 amp, output input 115 vac. (Switchmode) Price £120 each.
GOULD POWER SUPPLY MG5-40A. Input 115-120V nominal 3 amps RMS max 45-440Hz. Output 5V 40 amps. Price £30 each.
Various other makes of power supplies in stock.

D TO A CONVERTERS
15MHz, 8 BIT
By Micro Consultants Ltd. 50Ω cable drive op. Linearity 0.25%, max. 0.125% typ. Settling time: 2V step 70nS typ. 2MV step 50nS colour television transmission standard. Diff. gain 0.5% diff. phase shift 0.5° types rad 802 and MC2208/8. Unused. Ex-maker's pack.
SPECIAL OFFER PRICE: £20

NEW IN STOCK
A range of high quality transformers SPECIALLY WOUND for us. By buying direct we can offer these superb SPLIT PRIMARY & SECONDARY transformers at highly competitive prices.

6VA	0-12, 0-12	0-12V, 0-12V	3.80
	0-15, 0-15	0-15V, 0-15V	
12VA	0-4V5, 0-4V5	0-20V, 0-20V	
	0-6V, 0-6V	0-6V, 0-6V	
	0-9V, 0-9V	0-9V, 0-9V	
	0-12V, 0-12V	0-12V, 0-12V	4.75
	0-15V, 0-15V	0-15V, 0-15V	
	0-20V, 0-20V	0-20V, 0-20V	
20VA	0-4V5, 0-4V5	0-30V, 0-30V	
	0-6V, 0-6V	0-40V, 0-40V	8.90
	0-9V, 0-9V		

CASED AUTO TRANSFORMERS
240V Cable input. American outlet socket.

Rating	Price	750VA	£23.50
300VA	£13.00	1000VA	£27.00
500VA	£18.00	1500VA	£36.00

Other Transformers

1.2VA. 6-0-6, 9-0-9, 12-0-12	all 1.14
1.5VA	
12V	80p
15V	1.00p
2.4VA	
12-0-12	1.48p
24V(pcb)	1.00p
4VA	
5-0-5	1.25
6VA	
24V	1.50

ALUMINIUM BOXES		PLASTIC BOXES	
AB7 2.75x5.25x1.5in.	£1.06	75x50x25mm black or white	65p
AB8 4x4x1.5in.	£1.06	180x110x55mm black	£1.95
AB9 4x2.75x1.5in.	£1.06	80x60x40mm black	32p
AB10 4x5.25x1.5in.	£1.23	215x130x85mm black or white	£3
AB11 4x2.5x2in.	£1.06	120x100x45mm black	£1.18
AB12 3x2.1in.	77p	100x75x40mm black	93p
AB13 6x4x2in.	£1.43	150x100x60mm black	£1.35
AB14 7x5x2.5in.	£2.18	BLUE REXINE COVERED ALUMINIUM BOXES	
AB15 8x8x3in.	£3.05	RB1 6x4.5x2.5in.	£2.15
AB16 10x7x3in.	£3.05	RB2 8x5x3in.	£2.77
AB17 10x4.5x3in.	£2.52	RB3 9x5x3.5in.	£2.99
AB18 12x5x3in.	£2.77	RB4 11x8x4in.	£3.45
AB19 12x8x3in.	£3.34	RB5 11x7.5x4.5in.	£4.29

SPECIAL OFFERS

Headers Blue Mac 16-pin 50p; 24-pin 80p. Brand new and boxed.
Speakers: 2in. 16 ohm 200mW 60p; 7x4in. dual-cone 8ohm high quality 5V LS £1.60. Brand new and boxed
Multiturn Pots. We have large stocks, all makes, multiturn pots, cermet, etc.
Bourns type 3299X 1K/50K 30p each
Bourns type 3386P 5K/trimpot 30p each
Spectrol 3/4in. 22ohm/100K 30p each
Also large stocks of cermet presets type 62 by Beckman and AB type 81E 30p each
Discounts available on quantity

Full range available of Plessey moulded track presets, screwdriver or knob operation 25p each
Cassette Decks: With stereo heads, mechanically complete, but with no electronics. Brand new, smart black modern finish £7.45 inc. VAT + P&P
VU Meters: 40x30x23mm deep. White/red scale on black background. Brand new 25p each
Polyester Capacitors by Siemens, Mullard and Rifa.
2.2µF at 100/250v radial block 15p each
3.3µF at 100v radial block 25p each
4.7µF at 100v radial block 30p each
10µF at 63v radial block 40p each
Mains Filters by Erie/Corcom from 3A to 15A, 250v AC rated £3 each

SPRAGUE: Series 36D Computer grade electrolytics 3,300 at 40V. Brand new and boxed 35p ea.
SIEMENS: Procond Radial Polyester Film Capacitors. 10µF at 63V. Brand new Only 40p
Quantity available

VIDEO GAME BOARD

FIELD GOAL VIDEO GAME, BY TAITO. A top quality board complete with 6800 CPU system with 2716 eproms with circuit diagram, plus all connections for either colour or black and white monitors (TV sets). Price £20 + VAT £3. P/P £2.55.

POWER SUPPLY KIT TO SUIT + circuit diagram.
Price £15 + VAT £2.25. P/P £3.45.

2 x 22-WAY GOLDPLATED DOUBLE-SIDED 0.156" EDGE CONNECTORS to suit videoboard.
Price £1.60 pair + VAT 24p. P/P included.

THE COMPLETE KIT £46 INCLUSIVE. Full details on application.

WE PURCHASE

Surplus component stocks, redundant materials, obsolete computers, for cash.

We also collect - distance no object. Just call:

C. T. Electronics (Acton) Ltd.
267 & 270 Acton Lane, London W4 5DG
Telephone 01-747 1555; 01-994 6275
Telex 291429

MAIL ORDER: Gds. + 15% VAT, plus VAT-INCLUSIVE Adm/Pkg/Post:
1/4Kg £1.30 2Kg £3.00 6Kg £4.40
1/2Kg £1.70 3Kg £3.45 6-10 £5.00
3/4Kg £2.20 4Kg £3.90 Over 10Kg: Quote
1Kg £2.55 5Kg £4.20

This advertisement is mainly of our excess stockholding. We also have excellent stocks of semiconductors, hardware, cables, etc., etc. For further details send for our lists and retail price catalogue, phone or visit our shop. All prices are exclusive of VAT (and P&P). Minimum Mail Order £5 + P&P + VAT. Government departments, schools, colleges, trade and export welcome.

WW - 084 FOR FURTHER DETAILS

BSR DE LUXE AUTOCHANGER £20

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2 x 11 1/4 in. 3 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. Post £2 Cut Board £1 extra



HEAVY METAL PLINTHS Post £2

Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4 in. £4

DECCA TEAK VENEERED PLINTH Post £1.50

Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 3/4 in. x 14 1/4 in. x 4 in. Black/chrome facia trim. Also with boards cut out for Garrard £3. Plastic cover £6

TINTED PLASTIC COVERS

17 1/2 x 13 3/4 x 3 1/4 in.	£6	18 1/4 x 12 1/2 x 3 in.	Post £2
17 1/4 x 9 3/8 x 3 1/2 in.	£3	14 3/8 x 12 1/2 x 2 7/8 in.	£5
13 3/4 x 12 x 2 7/8 in.	£3	16 3/8 x 12 x 2 in.	£5
15 1/4 x 13 1/2 x 4 in.	£6	14 7/8 x 13 3/4 x 2 3/4 in.	£5
17 x 12 3/4 x 3 1/2 in.	£6	17 1/4 x 13 3/4 x 4 1/8 in.	£6

Callers Only (not suitable for post)

21 1/2 x 14 1/4 x 2 1/2 in.	£6	21 x 13 7/8 x 4 1/8 in.	£6
23 3/4 x 14 x 3 7/8 in.	£6	30 3/4 x 13 3/8 x 3 1/4 in.	£6

BSR SINGLE PLAYER DECKS

BSR P232 BELT DRIVE QUALITY DECK

Manual or automatic play. Precision ultra slim arm. Cueing device. Bargain price. With stereo ceramic cartridge



£24 Post £2

BSR P204 SINGLE PLAYERS SPECIAL OFFERS

Two speed 33/45 r.p.m. hi-fi decks with stereo cartridges, cueing device and snake arm. Ceramic - 240V AC £15 or 9V DC £19. Magnetic - 240V AC £20 or 12V DC £24 Post £2 ea

GARRARD 6-200 SINGLE PLAYER DECK £22 Post £2

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device. Ready cut mounting board £1 extra.

GARRARD 730SP. 240V. £27.50. Magnetic Cartridge

Snake arm, 3-speed single player, p.p. £2

BATTERY ELIMINATOR MAINS TO 9 VOLT D.C.

Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 65p.

DE LUXE SWITCHED MODEL STABILISED. £7.50. Post £1.

3-6-7.2-9 volt 400mA DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit.

Controls up to 480 watts AC mains, £3. Post 65p.

DE LUXE MODEL READY-BUILT 900 watts. Front plate fits standard box, £5. Post 65p.

EMI 13 1/2 x 8 in. LOUSPEAKERS

Model 450, 10 watts R.M.S. with moving coil tweeter and two-way crossover; 3 ohm or 8 ohm. £9.50 post £1.50. "Final Clearance".

SUITABLE BOOKSHELF CABINET £6.50.

Size 18x11x6 in. Post £1.50.

RELAYS. 6V DC 95p. 12V DC £1.25. 18V £1.25.

BLANK ALUMINIUM CHASSIS. 6x4-£1.45; 8x6-£1.80; 10x7-£2.30; 12x8-£2.80; 14x9-£3; 16x6-£2.90;

16x10-£3.20. All 2 1/2 in. deep, 18 swg. ANGLE ALL 6x3/4x3/4 in. 18 swg. 30p.

ALUMINIUM PANELS. 18swg. 6x4-45p; 8x6-75p; 14x3-75p; 10x7-95p; 12x8-£1.10; 12x5-75p;

16x6-£1.10; 14x9-£1.45; 12x12-£1.50; 16x10-£1.75.

PLASTIC AND ALI BOXES IN STOCK, MANY SIZES

ALUMINIUM BOXES. 4x4x1 1/2 in. £1. 4x2 1/2 x 2 in. £1. 3x2x1 in. £1. 6x4x2 in. £1.80. 7x5x3 in. £2.40. 8x6x3 in. £2.50. 10x7x3 in. £3. 12x5x3 in. £2.75. 12x8x3 in. £3.60. All with lids.

BRIDGE RECTIFIER 200V PIV 2a £1. 4a £1.50. 8a £2.50.

TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.

RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 2p, 2W 10p.

HIGH STABILITY. 1/2w 2% 10 ohms to 1 meg. 10p.

Ditto 5%. Preferred values, 10 ohms to 1 meg. 3p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p.

PICK-UP CARTRIDGES SONOTONE 9TA £2.50. 9TACH £3.80.

BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD. Stereo Ceramic. AU1020 (G306 - GP310 - GP233 - AG3306 - AG3310) £2.

LOCKTITE SEALING KIT DECCA 118. Complete £1.

ANTEX SOLDERING IRON 240V 15W 3mm bit £5.25.

JACK PLUGS Stereo Plastic 25p; Metal 30p.

JACK SOCKETS Stereo Plastic 30p; Metal 35p.

JACK SOCKETS Mono Open 20p; Closed 25p.

JACK SOCKETS Stereo Open 25p; Closed 30p.

FREE SOCKETS - Cable end 30p. Metal 45p.

2.5mm and 3.5mm JACK SOCKETS 20p. Plugs 20p.

DIN TYPE CONNECTORS

Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p.

Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 20p; Sockets 15p.

PHONO PLUGS and SOCKETS ea. 15p.

Free Socket for cable end 20p. Screened Phono Plugs 25p.

300 ohm TWIN RIBBON FEEDER 10p yd.

U.H.F. COAXIAL CABLE SUPER LOW LOSS, 25p yd.

COAX PLUGS 30p. COAX SOCKETS 20p.

NEON PANEL INDICATORS 250V 30p.

POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Open 9-6. Closed all day Wed. Open Sat. 9-5. Radio Books and Components Lists 31p stamps. (Minimum post/packing charge 65p.) Access or Barclaycard Visa. Tel: 01-884 1665 for SAME DAY DESPATCH. Cash prices include VAT. WIRELESS WORLD JULY 1982

MINI-MULTI TESTER NEW

Da luxa pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included.

11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Continuity and resistance 0 to 600K ohms

De Luxa Range Doubler Model. 50,000 o.p.v. £18.50. 7x5x2 1/2 in. Post £1

NEW PANEL METERS £4.50

50µA 100µA, 500µA, 1ma, 5ma, 50ma, 100ma, 500ma, 1 amp, 2 amp 25 volt, 50 volt, VU Meter. 2 1/4x2x1 1/4 in. Post 65p

RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit, 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Post 95p

RCS "MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 x 2 in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

RCS STEREO PRE-AMP KIT. £2.95

All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers. Post 65p

MAINS TRANSFORMERS

250-0-250V 70mA, 6.5V, 2A £4.50 £2
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A £5.00 £2
350-0-350V 250mA, 6.3V 6A CT £12.00 £2
300-0-300V 120mA, 2x6.3V 2A C.T.; 5V 2A £12.00 £2
220V 45mA, 6.3V 2A £2.50 £1

GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available

2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	Price Post
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£8.00 £2
2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£10.50 £2
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£12.50 £2
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£18.00 £2
5-8-10-16V, 2 amp.	£2.50 80p
6V, 12 amp.	£2.00 £1
6-0-6V, 12 amp.	£2.00 £1
9V, 250mA	£3.50 £1
9V, 3 amp	£1.50 80p
9-0-9V, 50ma	£1.50 80p
10-0-10V, 2 amps	£3.00 £1
10-30-40V, 2 amps	£3.50 £1
12V, 100ma	£1.50 80p
12V, 750 ma	£2.00 80p
12V 3 amps	£3.50 £1
12-0-12V, 2 amps	£3.50 £1

CHARGER TRANS

6-12 volt 3a £4.00+£2 Post
6-12 volt 4a £6.50+£2 Post
8-12 volt 4a £2.00+80p

OPUS COMPACT SPEAKERS £22 pair

TEAK VENEERED CABINET 11x8 1/2x7 in, 15 watts 50 to 14,000 cps. 4 ohm or 8 ohm

OPUS TWO 15x10 1/2x7 1/4 in 25 watt

2-way system £39 pair. Post £3.

LOW VOLTAGE ELECTROLYTICS

1mf, 2mf, 4mf, 8mf, 10mf, 16mf, 25mf, 30mf, 50mf, 100mf, 250mf. All 15 volts. 22 mf/6V/10V; 25 mf/6V/10V; 47 mf/10V; 50 mf/10V; 68 mf/10V; 100 mf/10V; 150 mf/6V/10V; 200 mf/10V/16V; 220 mf/4V/10V/16V; 330 mf/4V/10V; 500 mf/6V; 680 mf/6V/10V/16V; 1000 mf/2.5V/4V/10V; 1500 mf/6V/10V/16V; 2200 mf/6V/10V; 3300 mf/4V; 4700 mf/4V. 5000mf 12V 15p; 25V 20p; 50V 30p; 1200mf 76V 86p. 1000mf 12V 20p; 25V 35p; 50V 50p; 100V 70p. 2000mf 6V 25p; 25V 42p; 40V 60p; 1200mf 76V 80p. 2200mf 63V 90p. 2500mf 50V 70p; 3000mf 50V 65p; 4500mf 64V 92. 4700mf 63V 1.20. 2700mf/76V £1.

HIGH VOLTAGE ELECTROLYTICS

2/500V 45p 8-8/450V 75p 32+32+16/350V 90p
8/450V 45p 8-8/450V £1 100+100/275V 65p
16/350V 45p 8-16/450V 75p 150+200/275V 70p
32/500V 75p 32+32/350V 50p 220/450V 95p
32/350V 50p 32+32/500V £1.80 32+32+32/325V 75p
50/450V 95p 50+50/300V 50p 50+50+50/350V 95p

CAPACITORS WIRE END High Voltage

.001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 5p.
.1MF 200V 5p. 400V 10p. 600V 15p. 1000V 25p.
.22MF 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.
.47MF 1500V 10p. 400V 20p. 630V 30p. 1000V 60p.

VALVE OUTPUT TRANSFORMERS (small) 90p.

TRIMMERS 30pF, 50pF, 10p. 100pF, 150pF, 500pF 30p.

MICROSWITCH SINGLE POLE CHANGEOVER 40p.

SUB-MIN MICROSWITCH, 50p. Single pole changeover.

TWIN GANG, 120pF 50p. 500 pfd 200pF £1.

GEARED TWIN GANGS 25pF 95p.

GEARED 365+365+25+25pF £1.

TRANSISTOR TWIN GANG. Japanese Replacement £1

SOLID DIELECTRIC 100pF £1.50, 500pF £1.50.

HEATING ELEMENTS, WAFER THIN

Size 11x9x1/4 in. Operating voltage 240V, 250W approx. Suitable for Heating Pads, Food Warmers, Convecter Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc.

ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

NEW baker Star sound

high power full range quality loudspeakers produced to give exceptional reproduction. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results. The high flux ceramic magnet ensures clear response.



MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£14	£2
DELUXE MK II	12	8	15	HI-FI	£14	£2
SUPER	12	8-16	30	HI-FI	£24	£2
AUDITORIUM	12	8-16	45	HI-FI	£22	£2
AUDITORIUM	15	8-16	60	HI-FI	£34	£2
GROUP 45	12	4-8-16	45	PA	£14	£2
GROUP 75	12	4-8-16	75	PA	£18	£2
GROUP 100	12	8-16	100	Guitar	£24	£2
DISCO 100	12	8-16	100	Disco	£24	£2
GROUP 100	15	8-16	100	Guitar	£32	£2
DISCO 100	15	8-16	100	Disco	£32	£2



BAKER 150 WATT MIXER/POWER AMPLIFIER £89 Post £2

SLAVE VERSION £75

For Organs, Discotheque, Vocal, Public Address. Three loudspeaker outlets for 4, 8 or 16 ohms. Four high gain inputs, each 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. 150 watts into 8 ohms R.M.S. Music Power. Distortion less than 1%. Slave output 500 M.V. 25K ohm. Frequency Response 25 Hz - 20kHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Compact - 16" x 8" x 5 1/2". Lightweight - 14lb. Master volume control. Made in England. 12 months guarantee. 200/250V A.C. mains or 120V to order. All transistor and solid state devices. 100 Volt Line £15 extra.

New Stereo Slave Model 150 + 150 watt £125. Post £4.

BAKER'S NEW PA150 MICROPHONE PA AMPLIFIER £125. PP £3

4 channel 8 inputs, dual impedance, 50K-600 ohm 4 channel mixing, volume, treble, bass. Presence control, Master volume control, echo/send/return socket. Slave input/output sockets.

BAKER £69 50 WATT AMPLIFIER Post £2

Ideal for PA systems, Discos and Groups. Two inputs, Mixer, Volume, Controls, Master Bass, Treble Gain.

RCS offers MOBILE PA AMPLIFIERS. Outputs 4-8-16 ohms

20-watt RMS 12v DC, AC 240v, 3 inputs. 50K £66 PP £2.
40-watt RMS 12v DC, AC 240v, 4 inputs. 50K 100v Line £75 PP £2.
Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 and 100v line
60-watt RMS, Mobile 24 volt DC & 240-volt AC mains. inputs 50K. 3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95 PP £2

FAMOUS LOUSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
SEAS	TWEETER	4in	50	8	£9.50	£1
GOODMANS	TWEETER	3 1/2 in	25	8	£4.00	£1
AUDAX	TWEETER	4in	30	8	£6.50	£1
SEAS	MID-RANGE	4in	50	8	£7.50	£1
SEAS	MID-RANGE	5in	80	8	£12.00	£1
SEAS	MID-RANGE	4 1/2 in	100	8	£12.50	£1
GOODMANS	HIFAX	7 1/2 x 4 1/2 in	100	4/8/16	£22	

Space and Microwave INSTALLATION ENGINEERS

Marconi Communication Systems has an international reputation for the design, development and manufacture of high technology communications equipment and systems.


Right now we need adventurous Engineers, keen to use their engineering and technical skills to the full, to join our installation teams operating throughout the world. We can offer challenging and exciting opportunities in both the U.K. and overseas. Some appointments will be on a fixed term contract.

We are seeking men or women with an electronics qualification or HM


Forces experience who have a minimum of three years' practical background of installing and commissioning satellite earth stations, line of sight or tropospheric scatter systems. A current U.K. driving licence is also required.

Excellent salaries, and overseas benefits where applicable, are offered with these posts.

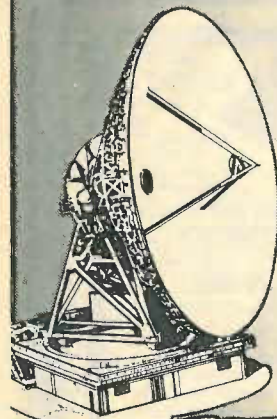If you are interested send a full c/v or telephone for an application form to **Gordon Short, Marconi Communication Systems Limited, New Street, Chelmsford, Essex, CM1 1PL. Telephone Chelmsford (0245) 353221, extension 592.** (1672)



Marconi
Communication Systems

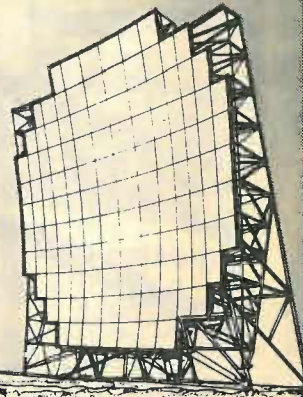

Teleco Oilfield Services, as a recognised world leader involved in the research, manufacture and operation of the oil industry's first commercial wireless directional-drilling telemetry service, offers career opportunities to experienced and technically qualified

ELECTRONICS TECHNICIANS

The incumbents will be based onshore and will be working within our Aberdeen facility.

Ideally, the successful candidates will possess practical experience of digital and analogue systems as well as having formal qualifications such as O.N.C. or equivalent C. and G. qualifications in Electronic Engineering.

Attractive salaries for the above positions are enhanced by a comprehensive benefit package including contributory pension scheme, AVC scheme, free life assurance, good working conditions and the excellent prospects offered by an international service company with expanding interests worldwide.

Applicants should send a c.v. stating salary required in confidence to:

The Personnel and Administration Manager
TELECO OILFIELD SERVICES LIMITED
Hareness Circle, Altens Industrial Estate, Aberdeen
Agency enquiries are not requested

(1660)



RED ROSE RADIO

The new ILR station for Lancashire due on the air in the autumn requires the following staff:

**SENIOR ENGINEER (ILR1)
ENGINEER (ILR2)**

Applicants for both positions should have considerable broadcasting experience, technically and operationally. A clean driving licence is preferred.

For the senior position, an HND or equivalent qualification in Electronics is essential, and a knowledge of digital techniques would be an advantage.

Applications including C.V. with full career details should be sent to:

David Cockram, Chief Engineer
Red Rose Radio PLC
49a Fishergate, Preston PR1 8BH

quoting reference WW.

(1675)



CAPITAL
APPOINTMENTS LTD.

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
Ask for Brian Cornwell

SALES to £15,000 plus car
Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.

Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

(291)

CAPITAL HOUSE
29-30 WINDMILL
STREET
LONDON W1P 1HG
TEL: 01-637 5551

Enthusiastic AUDIO SYSTEMS ENGINEER

required by international consultancy practice specialising in installations in theatre, television and conference buildings. Candidates should have a background in the electrical and electronics business, an understanding of technical drawings and an interest in the performing arts. Selected person will work with small team in Covent Garden area and will be trained to use computer-aided design system.

Salary will depend on experience and contribution made to this leading practice of theatre consultants.

Apply with c.v. to:

John Pilcher
Theatre Projects Consultants Ltd.
14 Langley Street, London WC2H 9JG
Telephone: 01-836 0386

(1663)



APEX VIDEO LTD.
1/8 Banbury Avenue, Slough
Berkshire SL1 4LR, England

Are you a travel hassle hater and a competent video engineer? We have broadcast TV facilities and need an additional **ENGINEER**. Excellent salary with even more money for the right experience. Please send CV or telephone for more information on SLOUGH 25142 and speak to **Barry Blight or Ian Browning.**

(1679)

NO CONCESSION TO RECESSION!


In communications, the industry of the 21st Century, the BBC is forging ahead with its programme of expansion. This year we are seeking 150 young, enthusiastic Engineers both in London and throughout the United Kingdom to work in the expanding field of Television.

The ability to handle new technology long before it appears in other industries, a thorough understanding of traditional electronics and the motivation to have found out about Broadcasting technology, together with the right personality are just some of the qualities we are seeking.

Many have already accepted the challenge and joined us, but there are vacancies in the Television Service, London for those men and women with the right qualities. If you are qualified, or soon to be qualified, with a Degree in Electrical and Electronic Engineering, Applied Physics or equivalent and have both normal hearing and colour vision why not fill in the coupon for further details, quoting reference number 82.E.4029/W.W.

Starting salary in the Television Service, London is in the range £7314 to £7892 plus shift working allowance of between £800 and £1000pa.

We are an equal opportunities employer.

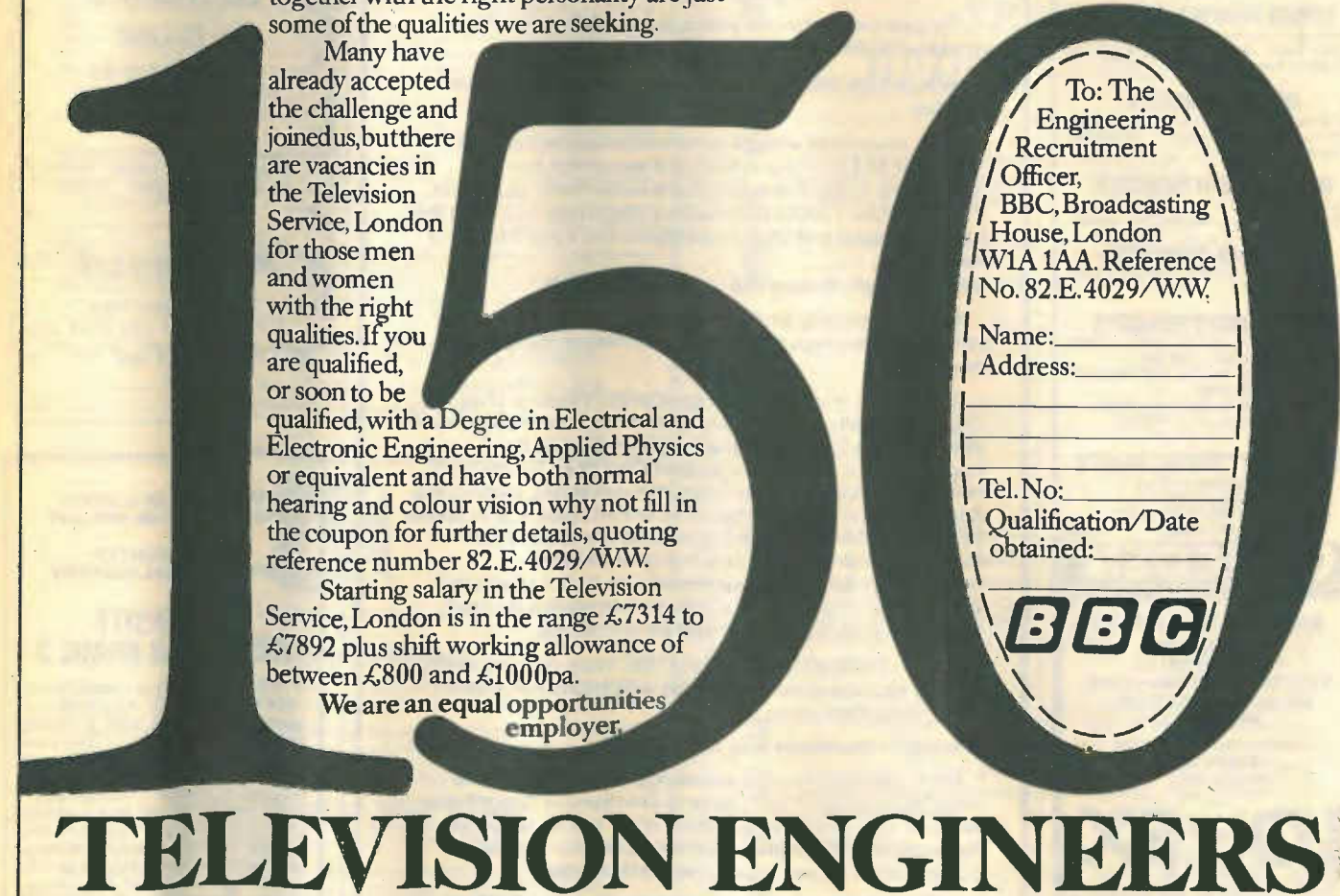

To: The
Engineering
Recruitment
Officer,
BBC, Broadcasting
House, London
W1A 1AA. Reference
No. 82.E.4029/W.W.

Name: _____
Address: _____

Tel. No: _____
Qualification/Date
obtained: _____



TELEVISION ENGINEERS

(1616)

Engineers & Scientists

£8,589

Communications R & D...
...the leading edge

At HM Government Communications Centre, we're applying the very latest ideas on electronics and other technologies to the problems of sophisticated communications systems, designed to enable and protect the flow of essential information.

The work is of the highest technical challenge, offering full and worthwhile careers to men and women of high ability, on projects covering the following areas of interest:—

RADIO - from HF to microwave, including advanced modulation systems, propagation studies, applications of Microcircuitry.

ACOUSTICS **SIGNAL ANALYSIS**
MAGNETICS **SYSTEMS ENGINEERING**

Applicants, under 30 years of age, should have a good honours degree or equivalent qualification in a relevant subject, but candidates about to graduate may also apply.

Appointments are as Higher Scientific Officer (£6,530-£8,589) or Scientific Officer (£5,176-£6,964) according to qualifications and experience. Promotion prospects.

For an application form, please write to the Recruitment Officer (Dept. WW7), HM Government Communications Centre, Hanslope Park, Milton Keynes, MK19 7BH.

(1589)

CHANNEL FOUR will be transmitting nationally from November 1982 and applications are invited for the following posts:

TECHNICAL SUPERVISOR
£16,267 p.a.

SENIOR ENGINEERS
£12,495 p.a.

SUBSTANTIVE ENGINEERS
£8,284 - £11,167 p.a.

VIDEOTAPE EDITOR
£15,612 p.a.

Applicants should have had some previous experience of television operation and a formal qualification such as an HNC or degree would be an advantage.

Please write enclosing a C.V. to Ellis Griffiths, Channel Four Television Company Ltd., 60 Charlotte St., London W1P 2AX, or telephone 01-631 4444 for an application form.



CHANNEL FOUR TELEVISION

(1671)

Channel Four is an equal opportunity employer: applications are welcome from candidates regardless of marital status, race, nationality, ethnic or national origins or sex and from registered disabled persons.

£25,000?

1. PROJECT LEADER
VHF/UHF equipment. Some microwave involvement. To £14,000 - Herts.

2. SENIOR DESIGN ENGINEER
Working on transmission systems or for digital beam forming equipment. To £11,000 - Essex.

3. DESIGN ENGINEER
For power amplifier design on satellite communications equipment. To £10,000 - Hants.

4. DEVELOPMENT MANAGER
Lead team of 4 on RF surveillance equipment development. To £16,000 - Berks.

5. ANALOGUE DESIGNER
VHF/UHF commercial equipment. £9,000 - Bucks.

6. DEVELOPMENT ENGINEER
Command and control systems for MOD vehicles. To £10,000 - Surrey.
100s of other electronics and computer vacancies. To £25,000.

Phone or write: Roger Howard
C.Eng, M.I.E., R.E., M.I.E.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road
Windsor, Berks.
Windsor (07535) 57818/58022
24-hour service (1640)

CLIVEDEN

DIGITAL EXPERIENCE?

FIELD SUPPORT
R & D AND SALES
VACANCIES IN COMPUTERS
NC, COMMS., MEDICAL
VIDEO, ETC.

For free registration ring
0453 883264
01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
LOGEX HOUSE, BURLEIGH, STROUD
GLOUCESTERSHIRE GL5 2PW
TEL. 0453 883264, 01-290 0267 (1621)

Telecommunications Officers

Up to £9270

The posts available are varied, but broadly they fall into 2 groups at 5 different locations.

Hanslope Park (Milton Keynes), North Bucks and Central London

Work associated with HF communications equipment, VHF, UHF and microwave links and associated test equipment; teleprinters, telephone subscribers' apparatus, PMBXs, PAXs, PABXs and ancillary equipment including that using analogue and digital techniques and voice frequency telegraph.

Crowborough, Sussex and Orfordness, Suffolk

The maintenance and operation of high power, medium and short wave broadcasting transmitters and associated equipments.

Candidates must have had appropriate training. They should normally have 4 years' relevant experience, and hold either ONC in Engineering (with pass in Electrical Engineering 'A') or ONC in Applied Physics or TEC/SCOTEC certificate or City & Guilds Telecommunications Technicians Certificate Part II (Course No. 271), or Part I plus 3 'B' subjects or a pass in the Council of Engineering Institutions Part I examination or an equivalent or higher relevant qualification. Ex-Service personnel who have had suitable training and at least 3 years' appropriate service (as Staff Sergeant or equivalent) will also be considered.

Salary: £5980-£8180; London £1087 more. Starting salary may be above minimum for those with additional relevant experience. Promotion prospects.

Relocation assistance may be available.

For further information and an application form (to be returned by 8 July, 1982), write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/5782.

Foreign and Commonwealth Office

(1685)

APPOINTMENTS IN ELECTRONICS to £15,000

**MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO**

Design, test, field and support engineers - for immediate action on salary and career advancement, please contact

Technomark
Engineering and Technical Recruitment

11, Westbourne Grove
London W2. 01-229 9239 (9257)

**UNIVERSITY OF LONDON
INSTITUTE OF NEUROLOGY**

**DEPARTMENT OF
NEUROLOGICAL SURGERY**

UNIVERSITY TECHNICIAN GRADE 3

is required to join an established research group working on laboratory projects with a strong neurological orientation. The post calls for someone with an aptitude for electronics and instrumentation and an interest in physiology. Initial salary will be in the range £4,672-£5,473 plus £1,087 London Allowance. Applications in writing, with names of two referees, to the Secretary, Institute of Neurology, Queen Square, London WC1N 3BG.

(1688)

As the old song says 'A good man nowadays is hard to find'.

- Design Development Engineers for a thermal imaging system that will hopefully develop into a family of systems. Analog engineers for power supplies, processing low-noise signals for display. Digital Engineer for control of same. Essex, to £11,000.
- Programmer capable of writing innovative software for microprocessor based data recorders and display products using the new Motorola range of microprocessors. Must be experienced graduate who can write programs that work. Sussex, up to £15,000 for the man who's worth it!
- Customer Liaison Engineer who besides providing technical and applications support for an extensive range of printers can organise and provide technical training for customers and engineers. Must have strong technical and hands-on background, if possible with experience of printers and be qualified at HNL or equivalent level. Berks, up to £10,000 with car provided.
- Software Engineer capable of writing good software and also de-bugging existing programs, trouble-shooting clients' software as required. Most is on PDP11/LS1, 11 or 8080/8086. Main operating system is RSX-11M, but macro-11, Coral and Intel operating system and assembler knowledge will come in useful. South London, salary starting at up to £10,500.
- Consultant Design Engineer to work in-house on dedicated real-time microprocessor process control systems to meet specifications as laid down, mainly Intel devices. Must be good graduate, with experience. Berks, salary up to £10,000.
- Computer Engineers for field service, permanent site, systems test or technical support. Vacancies throughout U.K.

Charles Airey Associates

Tempo House, 15 Falcon Road, Battersea London SW11 2PJ
Tel: 01-223 7662 or 228 6294 (1357)



CELESTION INTERNATIONAL LIMITED
require
DESIGN ENGINEER

A chance has arisen for a suitably qualified person to join Celesion's High Fidelity loudspeaker design team. These designs range from conventional loudspeaker systems up to state of the art transducer technology. The successful candidate should have an Honours Degree in Physics, Electrical Engineering or related discipline and have some experience in either loudspeaker design or vibration analysis. Such a person is likely to be in the age group 24-30 years old, and should be capable of contributing to the theoretical aspects of transducer technology.

ELECTRONICS ENGINEER

A vacancy exists for an Electronics Engineer to join the Celesion Development team. The successful candidate will be initially responsible for the development and maintenance of both Development and Factory test equipment. The candidate should have experience in both analogue and digital test equipment, including a working knowledge of microprocessor systems as well as experience in audio amplification. Graduates seeking First Appointments will be considered for both appointments. Candidates should apply in writing, giving details of their experiences in the above fields to the Personnel Manager, Celesion International Limited, Ditton Works, Foxhall Road, Ipswich, Suffolk IP3 8JP. (1676)

TRAINEE RADIO OFFICERS

First-class, secure career opportunities.

A number of vacancies will be available in 1982/83 for suitable qualified candidates to be appointed as Trainee Radio Officers.

If your trade or training involves Radio Operating, you qualify to be considered for a Radio Officer post with the Composite Signals Organisation.

Candidates must have had at least 2 years' radio operating experience or hold a PMG, MPT or MRGC certificate, or expect to obtain this shortly.

On successful completion of between 36 and 42 weeks specialist training, promotion will occur to the Radio Officer grade.

Registered disabled people may be considered.

SALARY & PROSPECTS

TRAINEE RADIO OFFICER: £4159 at 19 to £4897 at 25 and over. On promotion to **RADIO OFFICER:** £5698 at 19 to £6884 at 25 and over. Then by 4 annual increments to £10,034 inclusive of shift working and Saturday and Sunday elements. Salaries reviewed annually.

For full details please contact our Recruitment Officer on Cheltenham (0242) 21491 Ext. 2269 or write to her at:

Recruitment Officer, Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Gloucestershire GL52 5AJ

(1531)

GCHO

SULTANATE OF OMAN
ROYAL OMAN POLICE

TELECOMMUNICATIONS TECHNICIAN

The Royal Oman Police are seeking persons for appointment as Telecommunication Technician, applicants should be suitably qualified with at least 12 months' experience in the following subjects:

- (A) HF, VHF, UHF Fixed/Mobile Equipment
- (B) Teleprinters (Electronic)
- (C) Microwave/Multiplex Equipment
- (D) Marine Radar

Applicants should possess at least City & Guilds intermediate or equivalent. Previous Police/Military experience and a knowledge of Arabic would be an advantage, but is not essential.

GENERAL

This appointment is offered on contract terms of service for an initial period of two years. Conditions of service include annual emoluments of the equivalent of R.O.6624.000 (£10,700 at current rate of exchange) and normal benefits which are associated with working overseas including furnished air conditioned accommodation, medical treatment, 60 days' leave per annum with paid passages, plus an end of contract benefit equal to 25% of basic salary.

Applications with detailed curriculum vitae attached to be forwarded to:

Inspector General of Police and Customs
Attn.: Assistant Commissioner of Police
(Personnel & Training)
Royal Oman Police
P.O. Box 2, Muscat
Sultanate of Oman

(1688)

SYSTEMS PROPOSAL ENGINEER

Ampex requires a self-motivated Engineer capable of applying systems knowledge, to the design of television studio and outside broadcast vehicles.

Key requirements are:

- ★ Thorough knowledge of video and audio principles - HNC or equivalent.
- ★ At least three years' practical experience in the broadcast industry.
- ★ Ability to originate technical write-ups to price and present proposals to customer requirements.

Excellent salary, pension, life assurance and permanent health insurance schemes. Relocation expenses as appropriate.

AMPEX

Send cv, write to, or
phone Maureen Brake at:
Ampex Great Britain Ltd
Acre Road, Reading RG2 0QR
Berkshire, England
Tel. Reading (0734) 875200

(1670)

T.V. Technicians

Salary: £11,619 per annum tax free*

for the

**King Faisal Specialist Hospital and Research Centre
Riyadh, Saudi Arabia**

If you have at least 5 years preventive maintenance experience working on a range of T.V. systems, here is a unique opportunity to work in the T.V. studio attached to a modern hospital in the capital city of Saudi Arabia. You should have had some formal training or possess a qualification in electronics.

Your duties will include maintenance on a wide range of video and audio equipment including patient monitoring systems, video and audio tape recorders, T.V. cameras (colour and black and white), T.V. monitors, film and slide projectors.

Benefits will include:

- 2 year single status contracts, extendible by mutual agreement.
- Air passages.
- Medical and dental facilities.
- 50 days leave per year.
- End of contract bonuses.
- Excellent facilities for sport and recreation.

*Salary is paid in Saudi Riyals — 6,100 Riyals per month. Sterling exchange rate at the time of going to press: 6.3 Riyals to the £.

Please apply in writing with brief career details, or telephone for application form to:

Jim Hawkins
HCA United Kingdom Ltd
49 Wigmore Street
London W1H 9LE
Tel 01-935 7185

HCA
United Kingdom Ltd

Employment agency reg. no. SE(A) 4698 (1687)

EAST HAM COLLEGE OF TECHNOLOGY High Street South, London E6 4ER

Principal: K. R. BISHOP, B.Sc(Econ.) FRSA

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING LECTURER I IN ELECTRONICS/ ELECTRICAL ENGINEERING

Required to teach in one of the following areas: Electronics and Microprocessors, Electrical Power and Machines, Radio and TV. Appropriate industrial experience with a keen interest in development of practical and project work will be an advantage. Minimum qualification is a City and Guilds Full Technological Certificate or equivalent.

Salary (under review): £5,034-£8,658 plus £759 p.a. London Allowance.

Application form and further details may be obtained by writing to the Vice-Principal enclosing a self-addressed envelope. Completed forms should be returned within 14 days of the appearance of this advertisement.

 LONDON
BOROUGH OF
NEWHAM

(1688)

SITUATIONS VACANT

Metropolitan Police Office Telecommunications Officers

... in Central London to maintain on a shift basis the data and radio networks associated with the New Scotland Yard Command and Control function and other operational systems.

The successful candidate will implement maintenance policy; maintain systems within agreed parameters; liaise with Operations (Technical) Support Group on system failure and the duty Police Officer; take responsibility for calling out additional staff and contractors in emergencies; ensure that faults are documented for subsequent investigation and supervise the Telecommunications Technical Officers Grade II.

Candidates must have TEC/SCOTEC certificate in Electronics, Telecommunications or similar discipline; or City & Guilds Telecommunications Technicians Certificate Part II, or Part I plus Mathematics B, Telecommunications Principles B and, either Radio Line Transmission B or Computers B; or ONC in electrical, Electronic or Telecommunications Engineering or similar discipline; or a pass in the Council of Engineering Institutions Part I examination; or an equivalent or higher qualification. All candidates must have had appropriate training and should normally have four years' experience in a related field of work. Senior ex-service personnel with TEC/C&G recognised exemptions will also be considered.

Starting salary £8955 rising to £10320. In addition these posts attract £1087 Inner London weighting and a 20% shift allowance. Promotion prospects.

Relocation assistance may be payable.

For further details and an application form (to be returned by 7 July, 1982) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/5697.

(1686)

Design Engineers Satellite Communications

To work on:

Spacecraft Systems,
Communications Systems,
Antennae Design,
Radar and Signal Processing,
Electronic Circuit Design,
RF and Microwave Equipments,
Mechanical, Thermal and Dynamics Design

Recently awarded contracts have created a need for immediate expansion of on-site facilities and the design team. Some senior appointments have been filled from within, but there are still opportunities for Engineering Managers and Group Leaders to head-up additional teams now being formed.

At Senior Engineer/Engineer levels there are several vacancies in each of the above work areas.

Qualifications required are Degree/HND/HNC in a relevant discipline, plus experience.

Excellent salaries are offered, together with relocation assistance if required.

Please write or telephone briefly stating your qualification, recent experience and area of interest, to

Jack Burnie, Marconi Space and Defence Systems, Browns Lane, The Airport, Portsmouth. Tel. Portsmouth 664966. Ref. BL12.

(All posts are open to both male and female applicants).

 **Marconi**
Space & Defence Systems

A GEC Marconi Electronics Company.

(1665)

Junior Radio Officers

The Royal Fleet Auxiliary has a number of vacancies for Junior Radio Officers. These appointments are short term engagements of 6 months duration, (with the possibility of extension/permanent employment) and offer recently qualified personnel the opportunity to gain the required seetime.

Minimum qualifications: MRGC and DTI Radar Maintenance Certificate.

Apply, in the first instance, by telephone to:- Kevin McNicholas, RFA Personnel Officer, (Radio), on 01-385 1244 ext. 3103.

(1683)

ROYAL FLEET AUXILIARY

RFA

SOUTH & WEST £6,000—£13,000

Several of our clients seek the following personnel urgently...

1. UHF/VHF/HF DESIGN ENGS.
2. RF DESIGNERS
3. MICROWAVE DESIGN ENGS.
4. UHF/VHF/HF SYSTEMS ENGS.
5. TELECOMMS HARDWARE DESIGNERS
6. ATE PROGRAMMERS
7. PRODUCTION ENGS.
8. QUALITY ENGS.
9. SCIENTISTS
10. PHYSICISTS
11. SOFTWARE DESIGN ENGS.
12. SOFTWARE PROGRAMMERS
13. HARDWARE DESIGN ENGS.
14. TECHNICAL AUTHORS
15. TRANSMITTER ENGINEERS
16. MICROPROCESSOR DESIGN ENGS.
17. FIELD SERVICE ENGS.
18. PROCESS CONTROL DESIGN ENGS.

Our clients offer excellent salaries, conditions and relocation. Vacancies in DEVON/DORSET/HANTS/SUSSEX/WILTS/BERKS/SURREY.

Please ring or write to
CBS APPOINTMENTS
1 WOOTTON GARDENS
BOURNEMOUTH
(0202) 292155 or evenings 825408

(1680)

TELEVISION SERVICE ENGINEER

We are an expanding Television Rental and Retail company with a vacancy for an additional Television Service Engineer.

Suitable applicant will preferably hold an R.T.E.B. certificate or be training towards this qualification.

The post is directly responsible to the Service Manager.

A clean driving licence is essential.

A spacious flat is available if required.

Hydes of Chertsey Ltd., 56/60 Guildford Street, Chertsey, Surrey. KT16 9BE. Chertsey 63243.

(1434)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Redifusion Radio Systems on 01-874 7281.

(1162)

ARTICLES FOR SALE

PRINTED CIRCUITS. Make your own simply, cheaply and quickly. Golden Fotolab Light Sensitive Laquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714)

EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QF. 01-684 9917. (9678)

VINTAGE RADIO COLLECTOR? Full 1982 Catalogue now available £1.50 post paid from the Vintage Wireless Co., 64 Broad Street, Staple Hill, Bristol BS16 5NL. Tel. 0272 565472. (1638)

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236. (1627)

SITUATIONS VACANT

MOVE INTO MICROS WITH TOP BRITISH MANUFACTURER

COMPUTER SERVICE ENGINEER

£5.6K to £8.4K, OXFORD-BASED

Research Machines is looking for an experienced electronics engineer to join the small in-house team servicing our very successful and widely used microcomputers.

With several thousands of our 380Z systems in use, and a major range of very exciting new products about to be launched, the ability to maintain a high level of customer satisfaction is extremely important. Fast, efficient, effective servicing and repair is, therefore, particularly important to us.

Successful candidates should have:

- Experience of working with complex TTL logic boards;
- ONC, HNC, or A Level qualifications, but good relevant experience would outweigh any lack of formal qualifications;

- Initiative and a sense of responsibility;
- Good personal skills for working with customers;
- Knowledge of microprocessors is not necessarily required, as long as you have a strong desire to acquire expertise in this field.

Starting salary is between £5,600 and £8,400, depending on age and experience, and we also offer a number of valuable benefits such as: a 35 hour week; 20 days paid holiday; free BUPA; life and disability insurance; a pension scheme.

If you are interested in this vacancy, please contact Ann England, by phone or letter, for an application form, quoting WW6.

RESEARCH MACHINES MICROCOMPUTER SYSTEMS

RESEARCH MACHINES LTD Mill Street, Oxford OX2 0BW, Tel: (0865) 726136

ARTICLES FOR SALE

RACAL COMMUNICATIONS RECEIVERS

500 Kc/s - 30Mc/s 1MHz wide. RA17L - £175. RA117E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal louvered cases for above sets £25 each. RA96D - ISB - SSB - £75. RA216 - SSB - ISB and fine tune for RA117 - £50. TRANSMITTER DRIVE UNIT RA79. 1.5mc/s - 30mc/s - SSB - ISB - DSB - FSK - CW - £150. AERIAL TUNING UNIT and protection unit MA197B - £25 to £50. DECADE FREQUENCY GENERATOR MA250B Solid state synthesiser for MA79 or RA117 - RA217 - £150 to £200. MA250 - 1.6mc/s to 31.6mc/s - £150 (New). MA259G - precision frequency standard - 5mc/s lmc/s 100kHz - £100 to £250. RACAL MA152 - Standing wave ratio indicator. FX2mc/s - 25mc/s Power up to 1000watts - 50 ohms - Auto trip switch - Transistor mains 100 - 250AC, new and boxed - £40. RACAL COUNTER 836 (9036) 32mc/s TTL circuit design - tested with manual - £50 to £75. OSCILLOSCOPES COSSOR CDU150 - 35mc/s - Twin Beam - Solid State - £175 with manual. TEXTRONIC OSCILLOSCOPE 647, and 647A Solid State - 50mc/s and 100mc/s bandwidth - £250 and £350. Tested, circuit and instructions. AERIAL MASTS - we have three masts approx. 130ft high, complete with all fittings. Base insulators, etc. Mast steel tube 8" all parts galvanised, supplied brand new, all items boxed - £1000 - or each complete mast - £400. All items are bought direct from H.M. Government, being surplus equipment. Price is ex-works. SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. (0274) 684007. V.A.T. and Carriage extra.

PARAMETRON 477 Spectrum Analyzer Freq. 200KHz-50MHz. £275
HEWLETT-PACKARD 350D Attenuator DC-1MHz 600 Ohm. £75
MARCONI 968B Universal Bridge 1K, 10K & 100K. £100
WAYNE KERR B901/5261/1/25 Admittance Bridge 50-250MHz. £120
MARCONI TF2424 VHF/UHF Freq. Meter 4 Digit DC-512MHz. £100
GAUMONT KALEE Flucto Meter. £95
MARCONI TF 833 Power Meter. £95
MARCONI TF 2800 Sens. Valve Voltmeter 10V-300V f.s.d. ±1%. £35
WAVETEK 740 Phase meter 10Hz-2MHz. £225
TEKTRONIX 564 Storage Scope DC-10MHz c/w 342 & 383 Plug-ins. £275
ADVANCE SG62B Signal Generator 150KHz-220MHz A.M. to 30%. £280
ADVANCE H1E Signal Generator 15Hz-50KHz Sine/Sq. O/P. £38
ADVANCE SG65A Oscillator 10Hz-100KHz Sine/Sq. O/P. £85
MARCONI TF 2950 Mobile Radio Test Set. £395
MARCONI TF 1068B AM/FM Signal Generator 10MHz-470MHz. £290
MARCONI TF 1101 R-C Oscillator 20Hz-200KHz. £80
PHILIPS PM 6456 Stereo Generator. £185
PROSSER A100/A340 Wave Form Generator. £375
TAYLOR SG 82A AM/FM Signal Generator. £125
TEKTRONIX L26 Pulse Generator. £120
KORTING 82515 Colour TV Service Generator. £280
I.C.I. ULV 2518 Ultra Sonic Cleaner, 3 Compartments, Filtration, Cont. distillation. OFFERS OVER £2800
BPL CZ 4574 Component Comparator and CPU 4574 3 Channel Automator. £115
FERROGRAPH RTS 2 Recorder Test Set. £225

Send SAE for list to:
MARTIN ASSOCIATES
"PARTHA", BECKHAMPTON
NEAR MARLBOROUGH, WILTS.
TEL: AVEBURY (067-23) 219 (1384)

WORLD'S BIGGEST INFORMATION SERVICE
By return post - service/workshop manuals. Over 2,000 Serv - over 300 different CTV plus huge stocks VCR/TV Audio/foreign and UK.
Any single service sheet £1 + s.a.e. Repair data named TV £9.50 (with circ. £9.50). SAE brings free - 50p magazine/price lists/bargain offers/quotations - unique TV publications.
TISWWW, 76 Church Street, Larkhall (0698 883334), Lanarkshire ML3 1HE. (1637)

ARTICLES FOR SALE

SAVE 33% on PCB 2H holders, in boxes of 15. Limited offer 30. Hurry and phone 0353 778756, 9 a.m. to 9 p.m. Save time. We represent over 30 leading manufacturers. Free index of hand tools and production aids. Batvale Mkt. Ltd., 50 High Street, Sutton, Ely, Cambs. Tel: (0353) 778756. (1667)

80 x 24 VDU
All the electronics for a 24 lines by 80 characters visual display unit on one assembled and tested printed circuit board measuring 9.75 inch x 8.50 inch.
You provide: power supply +5v at 1.2 amps +12v/-12v at 25mA, ASC11 encoded keyboard, video monitor.
The VDU-1 will talk to the R.S.232 serial port on your computer, at up to 19,200 Baud 56 features including cursor (X, Y) addressing.
VDU-1 Assembled and tested PCB £135
PSU-1 VDU-1 power supply £32
All prices subject to £2.50 registered delivery, plus VAT.

SIRIUS CYBERNETICS
Comyn Lodge, 66 Holly Walk
Leamington Spa, Warwickshire
Tel: (0928) 316110 (1645)

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC.
LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL
SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.
ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.
ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE
TELEPHONE: 445 0749/445 2713
BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, North Finchley, London, N.12 (5 minutes from Tally Ho Corner) (1613)

ARTICLES FOR SALE

INVERTERS
High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916 (910)

THE SCIENTIFIC WIRE COMPANY
P.O. Box 30, London, E.4

ENAMELLED COPPER WIRE			
SWG	1lb.	5oz.	2oz.
8 to 29	2.76	1.50	.80 .60
30 to 34	3.20	1.80	.90 .70
35 to 40	3.40	2.00	1.10 .80
41 to 43	4.75	2.60	2.00 1.42
47	8.37	5.32	3.19 2.50
48 to 49	15.96	9.58	6.38 3.69

SILVER PLATED COPPER WIRE			
14 to 30	6.50	3.75	2.20 1.40
14 to 30	3.38	2.36	1.34 .90

Prices include P.P. VAT and Wire Data SAE for list. Dealer enquiries welcome. Reg Office: 22 Coningsby Gardens. (9063)

POWER V MOS-FET TECHNOLOGY
We specialise in all aspects of this important subject. A comprehensive service is offered to individual or OEM users, including:
★ Hitachi Supermet and RCA V MOS-FET from stock.
★ V MOS-FET power modules from stock.
★ Competitive prices (120 watt modules £15.45, 1 off).
★ Printed circuits and kits.
★ Data books and application notes.
★ Design, evaluation and advice service.
Catalogue/sample data sent free (50p stamp appreciated towards post and packing).
Phone 02514 22383 and ask Richard Walsh about your application requirement or write to:
AUDIO TECHNOLOGY
Freepost, Church Crookham
Aldershot, Hants. GU13 0BR

TIME WRONG?
ALWAYS CORRECT with an MSF CLOCK - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, auto GMT/BS1 and leap year, also parallel BCD output for computer or alarm, etc, and STOPCLOCK.
Receives Rugby 60KHz atomic time signals, built-in antenna, 1000km range.
Fun-to-build kit (ready made to order) includes all parts, printed circuit, case, instructions, postage etc, £62.80, money back assurance so GET the TIME RIGHT now.
CAMBRIDGE KITS
45 (WG) Old School Lane
Milton, Cambridge. (1682)

Crystal Units
ACCURATE RELIABLE
Private enquiries, send 13p in stamps for brochure
THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988 (8493)

WORKBENCHES, secondhand. Ex-ITT TV factory. Open- or cubicle-style, need space. Details: 042 486 3464. 9a.m. to 9p.m. (Sussex).

SERVICES

Micro Processor Design
Our team of experts offer the complete service from Design to Manufacture
● Artwork ● Prototype Development ● Testing
● Board Manufacture ● Assembly ● Packaging
For more information contact Micro Control, 1 Cherrywood Drive, Aspley, Notts. NG8 3NN. Telephone 0602 298281 (24 hour service). (1597)

CIRCOLEC
THE COMPLETE ELECTRONIC SERVICE
Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly.
Quality workmanship by professionals at economic prices.
Please telephone 01-767 1233 for advice or further details.
1 FRANCISCAN ROAD
TOOTING, LONDON SW17 (1391)

Design Engineers
DIGI-TEL ELECTRONICS
● Video character & image generation systems
● Microprocessor-controlled video systems
● Prototype & small batch production capacity
20 Trenches Road, Crowborough, Sussex. Tel. (089 26) 5069

FACILITIES AVAILABLE
★ Circuit Design & Development Digital and Analogue
★ Artwork Layout Free prototype bd. (non PTH) Supplied with orders over £100.
★ Board Manufacture Prototype to semi-production.
★ Wiring & Assembly PCB assembly, wiring and cable forming.
★ Test Full test facilities available.
★ Copper Clad Board D/S fibreglass 1000 Sq inches of assorted useful sizes. £8.00 inc. post.
One or all services available, no order too small. Please telephone Chelmsford 357935 or write to H.C.R., 1 Bankside, off New Street, Chelmsford, Essex. (1769)

DESIGN AND DEVELOPMENT, ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production. - Adenore Limited, Unit 103 Liscombe, Bracknell, Berks. Tel: Bracknell 52023. (656)

SMALL BATCH PCBs produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. **FAST TURN-AROUND.** - Details: Winston Promotions, 3 Hatton Place, London EC1N 9RV. Tel: 01-405 4127/0960. (9794)

SHEET METAL WORK, fine or general front panels chassis, covers, boxes, prototypes, 1 off or batch work, fast turnaround. - 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812)

DESIGN SERVICES. Electronic design development and production service available for digital and analogue instruments. RF Transmitters and receivers, telemetry and control systems. 20 years' experience. R.C.S. Electronics, Wolsey Road, Ashford, Middlesex. Phone Mr Falkner 53661. (8341)

ARTICLES FOR SALE

NEW BOXED VALVES: 212E/£150, 304H/£40, 12A/£3, 2GA/£3, 35TG/£5, 46/£2, 5R4G/£1, 6AL5/50p, 808/£4, 8012/£3, 101D/£3, 1616/£2, C6A/£5, CV177/£15, DET10/£5, DET25/£10, EF50/£1, B91H/£1, B92CC/50p, EL81/£1, GT1E/£5, LS7B/£3, LS8/£3, PT1S/£2, PEN25/£1, VT25/£3, TT11/£1. SAE catalogue or phone 0803 28489, Radel Electronics, 86 Union Street, Torquay. (1673)

CAPACITY AVAILABLE

TW ELECTRONICS LTD.
THE PCB ASSEMBLERS
More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.
TW are able to satisfy all of them - quality, competitive pricing, firm delivery, and close co-operation with the customer.
Assembled boards are 100% inspected before flow soldering and re-inspected after automatic cropping and cleaning.
Every batch of completed boards is issued with a signed certificate of conformity and quality - our final assurance.
For further details, contact us at our new works:
Blenheim Industrial Park
Bury St. Edmunds
Suffolk IP33 3UT
Tel: 0284 3931 (1466)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDear Electricals Ltd, 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)
ELECTRONIC DESIGN SERVICE. Immediate capacity available for circuit design and development work, PC artwork, etc. Small batch and prototype production welcome. - E.P.D.S. Ltd., 1A Eva Road, Gillingham, Kent. Tel: Medway (0634) 577854. (9667)
PCB ASSEMBLY/WIRING from drawings/sample. Fast turnaround. J. Forsyth. Tel. (0604) 65011. (1517)
BATCH PRODUCTION, printed circuit or wiring assembly, to sample or drawing. Quotations free. Contact B. Rose, Remploy Ltd., P. & A., Mile Cross Lane, Norwich, Norfolk NR6 6SV. 0603 414949. (1665)

ARTICLES WANTED

WANTED
Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, any quantity. Prompt service and cash. Member of A.R.R.A.
M & B RADIO
86 Bishopgate Street
Leeds LS1 4BB
0532-35649
WANTED FOR CASH: 7F7, 7N7, 53, 6L6 metal, 304TL, 4CX1000A, all transmitting, special purpose valves of Eimac/Varian, DCO, INC, 10 Schuyler Avenue, North Arlington, New Jersey 07032, USA. (1625)
SURPLUS WANTED. Radio and electronic components, aerials, cable wire, test equipment, switches, valves, connectors, relays, PCBs. A.C. Townley Ltd., Windsor Road, Todmorden, Lancs OL14 5YA. Todmorden 4934. (1664)

30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE
TV Monos £2, Transistor Radios £2, Tuners £2, Tape Recorders, Record Players and Stereograms £2. Stamped addressed envelopes with all quotations. Also colours available. Car Radios £3 + stamped addressed envelope. All valve radios £2. Stamped addressed envelope please. Quote advert. no. with order.
C. CARANNA
71 Beaufort Park, London NW11 6BX
01-458 4882 (Mail Order) (1325)

BOARDRAVEN LTD.
PRINTED CIRCUIT BOARDS
Manufactured to your specifications. Single/double sided. Very speedy deliveries on prototypes and quantity. Master layouts if required.
Contact:
J. K. Harrison, Camaby Industrial Estate, Bridlington, North Humberside YO15 3QY. Tel. (0262) 78788. (1168)

PCB/equipment assembly/wiring from prototype/drawings. Fast turnaround. Tel. 01-390 0424. (1626)


PHONE YOUR CLASSIFIEDS TO IAN FAUX ON 01-661 3033

ARTICLES FOR SALE

CLEARANCE. 40-metre reels of 38-way screened cable, £39 each. Computer spec. capacitors, 20,000 MSD at 55 volts, £2.50. Phone Mike at Mirage Lighting on Hitchin (0462) 73388 between 10 a.m. and 7 p.m. (1662)

8086/8088 Personality module for millennium series 1000 Microsystem designer £575 or will exchange for 80A Personality module. 01-212 0937 days or 041-644 3455. Box No. 1678. (1662)

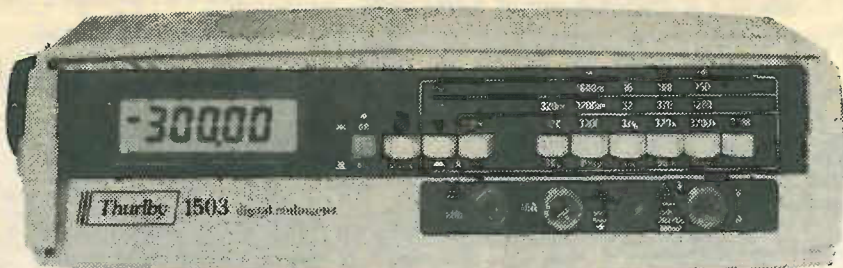NEW! 1503-HA high resolution multimeter even higher accuracy
— at remarkably low cost



● 0.03% accuracy on dc volts
● 4 1/4 digits (±32,768 counts)
● 10µV, 10mΩ, 1nA resolution
● 7 functions including Frequency
● Current measurement to 25 amps
● Mains/Battery, fully field portable
● Full range of accessories available

Thurlby 1503 (0.05% acc.) —£149 + VAT available ex-stock.
1503-HA(0.03% acc.) —£165 + VAT

Full data from Thurlby Electronics Ltd. Coach Mews, St. Ives, Cambs. PE17 4BN Telephone: 0480 63570

Thurlby designed and built in Britain

WW - 056 FOR FURTHER DETAILS

INDEX TO ADVERTISERS JULY

Appointments Vacant Advertisements appear on pages 103-111

PAGE	PAGE	PAGE
Acoustical Mfg. Co. Ltd. 58	Faircrest Engineering..... 18	Nicolet Instruments Ltd..... 12
Albetros (Products) Ltd. 18	Farnell Instruments Ltd. Cover ii, Reader Card	Northern Electronics..... 26
Ambit International..... 8	Fieldtech Heathrow Ltd..... 20	Olson Electronics Ltd. 16
Analogue Associates..... 26	Fylde Electric Laboratories..... 27	Pantechincs..... 86
Anglia Components..... 7	GAS Electronics..... 11	PM Components..... 98, 99
Audio Electronics (Cubegate Ltd)..... 19	Global Specialities Corp. (UK) Ltd..... 25	P. & R. Computer Shop..... 7
Avel Lindberg (Cotswold Electronics Ltd)..... 89	GP Industrial Electronics Ltd..... 2	Radford Lab..... 86
Appledore Electronics..... 100	Greenwood Electronics Ltd..... cover iv	Ralfe, P. F., Electronics..... 94
	Griftronic Emission Ltd..... 14	Relay-A-Quip Ltd..... 100
Barrie Electronics Ltd..... 95		Reprints..... 100
Black Star Ltd..... 8	Hall Electric Ltd..... 21	Roxburgh Printers Ltd..... 85
Broadfields & Mayco Disposals..... 18	Happy Memories..... 98	RST Valves..... 91
	Harris Electronics (London)..... 9	
	Harrison Bros Electronic Dist..... 17	Safgan Electronics Ltd. 17
Carston Electronics Ltd..... 22, 23	Hart Electronic Kits Ltd..... 88	Sagin, M. R..... 24
Chiltern Electronics..... 89	Hembrook Recording Ltd..... 92	Sandwell Plant Ltd..... 93
Chilthead Ltd..... 90	Hemmings Electronics Ltd..... 86	Sche Tronics Ltd..... 94
CIL Microsystems Ltd..... 24	Henry's Radio..... 24, 26	Sescom Inc..... 14
Circuit Services..... 4		Shure Electronics Ltd..... 28
Clark Masts Ltd..... 5		Sinclair Research..... Loose Insert
Clef Products (Electronics) Ltd..... 10	ILP Electronics Ltd..... 87, 93	South Midlands Communications Ltd..... 16
Colomor (Electronics Ltd.)..... 93	Interface Quartz Devices Ltd..... 4	Sowler, E. A. Ltd..... 18
Crimson Elektrik..... 97	Intergrex Ltd..... 4	Special Products (Distributors) Ltd..... 9
Crotech Instruments Ltd..... 97	Irvine Business Systems Ltd..... 92	S. & R. Amplification..... 20
CT Electronics (Acton) Ltd..... 101		Supersem..... 95
	Keithley Instruments Ltd..... 15, 27	Surrey Electronics Ltd..... 7
	Kelsey Acoustics Ltd..... 90	Semiconductor Supplies Inter. Ltd..... 70
Danavox (Gt Britain) Ltd..... 6		Technomatic Ltd..... 12, 13
Darom Supplies..... 10	Langrex Supplies..... 91	Tektronix UK Ltd..... Cover iii
Dataman Designs..... 90	LFH Associates Ltd..... 8	Teleradio Electronics Ltd..... 88
Digi-Tel Electronics..... 16	Lighting Electronic Company..... 92	Thanet Electronics Ltd..... 90
Display Electronics..... 96	Lion TV..... 85	Thurlby Electronics Ltd..... 112
DSN Marketing Ltd..... 89	L&J Computers..... 14	Time Base (Dutchgate)..... 98
		Time Electronics Ltd..... 92
		Valradio Ltd..... 10
	Meikuist..... 95	West Hyde Developments Ltd..... 26
	Memotech Ltd..... 57	White House Electronics..... 88
	Midwich Computer Co. Ltd..... 17	Wilmslow Audio..... 20
	Modern Book Co. Ltd., The..... 86	WKR Ltd..... 14
	Monolith Electronics Co. Ltd., The..... 10	

OVERSEAS ADVERTISEMENT AGENTS:
France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.
Hungary: Mrs Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget. Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE
Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 - Telex: 37342 Kompass.
Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.
United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.
 Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.
 Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.
 Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 4415 - Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.
Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.

TEK MULTI-PURPOSE OSCILLOSCOPES SO ADVANCED THEY COST YOU LESS

The Tektronix 2200 Series. Simply great.



Tektronix traditions of excellence in designing and manufacturing oscilloscopes are recognised all over the world. But rather than rest on past laurels, we have veered dramatically from the well established design paths we ourselves have laid down.

With the 2213 priced at £670* and the 2215 at £850*, these 60 MHz dual trace oscilloscopes are an entirely new form of instrument.

Their most remarkable characteristic is the way in which major design advances have provided full-range capabilities at prices significantly below what you would expect to pay. How has this been accomplished? To begin with, we have reduced the number of mechanical parts by more than half. This not only saves manufacturing time, it lowers costs and improves reliability.

Board construction has been greatly simplified and the number of boards reduced. Board connectors have also been reduced substantially and cabling cut by an amazing 90%.

The 2213 and 2215 have a high efficiency regulated power supply which does away with the need for a heavy power transformer. There are no line-voltage adjustments. Just plug the instrument into a power socket supplying anything from 90 to 250 volts, 48-62 HZ, switch on and you are ready to measure. Power saving circuitry has eliminated the cooling fan, resulting in further economies in size and weight.

These scopes have it all. Dual trace. Delayed sweep for fast, accurate timing measurements. Single time base in the 2213, dual time bases in the 2215. An advanced triggering

system, automatic focus and intensity. Beam finder - and much more. Interested? Then why not telephone your nearest Tektronix office or circle the enquiry number for further information.

Performance Specifications
Bandwidth
 Two channels, DC-60 MHz to 20 mV/div, 50 MHz to 2 mV/div.
Light Weight
 6.1 kg (13 1/2 lbs). 6.8 kg (15.0 lbs) with cover and pouch.
Sweep Speeds
 Sweeps from 0.5s to 0.05 µs (to 5 ns/div with x10 magnification).
Sensitivity
 Scale factors from 100 V/div (10x probe) to 2 mV/div (1x probe). Accurate to ± 3%. AC or DC coupling.
 Also available from Electroplan:
 * Prices subject to change without notice.

Tektronix UK Limited
 PO Box 69, Harpenden, Herts. AL5 4UP
 Tel: Harpenden 63141 Telex: 25559
 Regional Telephone Numbers: Maidenhead 0628 73211, Manchester 061 428 0799, Livingston 32766, Dublin-850685/850796



ORYX



the new name in quality solder

Now there is another choice in high quality solder. The new Oryx resin cored solder. Try it and you will find it spreads easier than the solder you are using. Specially formulated for fast precision solder work, it is 60% tin, 40% lead alloy with quality flux construction and melts at 183°C. Two gauges are available—18 SWG (1.2mm) and 22 SWG (0.71mm) in 2.5 Kg, 500g, 250g and 100g reels. Pocket size dispenser with 10 feet of Oryx 1mm solder is also available at only 68p (+VAT). Oryx is competitively priced—write now for details and technical information.

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659

The TC82—a significant development in temperature controlled soldering



The new Oryx TC 82 has features unique to any temperature controlled precision soldering iron. Available in 24 V, 50 V, 115 V and 210/240 V models, the TC 82 has a facility allowing the user to accurately dial any tip temperature between 260°C and 420°C by setting a dial in the handle without changing tips.

This eliminates the need for temperature measuring equipment. You get faster and better soldering.

For 24 V models a special Oryx power unit connects directly to the iron and contains fully isolated transformer to BS3535, a safety stand, tip clean facility and illuminated mains socket switch.

The Oryx TC 82 is also extra-safe. Removing the handle automatically disconnects the iron from power source. Other TC 82 features include: Power-on Neon indicator in handle; burn proof cable; choice of 13 tip styles.

And more good news

The Oryx TC 82 iron costs only £13.00 (+VAT) and the power unit for 24 V operation £23.00 (+VAT).

The TC 82 240 volt is also available as a 30 watt general purpose iron at only £3.95 (+VAT).

Greenwood Electronics

Greenwood Electronics Limited, Portman Road, Reading, Berkshire RG3 1NE. Telephone: (0734) 595844. Telex: 848659