

Half price wireless RS232 link – exclusive reader offer

ELECTRONICS WORLD

Austria Asch. 70.00
Denmark DKr. 70.00
Germany DM 18.00
Greece Dra. 1400.00
Holland Dfl. 12.95
Italy L. 9400.00
Malta Lm. 1.80
IR £3.30
Spain Pts. 925.00
USA \$6.75

INCORPORATING WIRELESS WORLD

OCTOBER 1999 £2.55

A REED BUSINESS PUBLICATION
SOR DISTRIBUTION

VHF receiver in DSP

Anti-jitter:
exclusive circuits

PC engineering:
Lisa review

OTA designs

Interfacing with Java

VGA tester

Low-voltage analogue circuits

Crystal oscillator circuits

Make prototype enclosures
look professional



MORE PERFORMANCE, MORE CHOICES FOR YOUR SMPS DESIGNS. HEXFET® POWER MOSFETS.

BENCHMARK SERIES Best performance available



New P/N	Package	BV _{dss}	R _{os(on)}	I _d	R _{os(on)} Improvement over Industry Standard
IRFP559N60C	Super-247™	600V	45mΩ	59A	89%
IRFBA40N60C	Super-220™	600V	70mΩ	40A	94%
IRFBL10N60A	Super-D ² ™ Pak	600V	600mΩ	10A	50%
IRFB9N65A	TO-220	650V	930mΩ	8.5A	No Equivalent
IRFIB5N65A	TO-220 Fullpak	650V	930mΩ	5.1A	No Equivalent

STANDARD SERIES Industry standard performance



New P/N	Package	BV _{dss}	R _{os(on)}	I _d	R _{os(on)} Improvement over Industry Standard
IRF740A/S	TO-220/D ² -Pak	400V	550mΩ	10A	Same
IRF730A/S	TO-220/D ² -Pak	400V	1000mΩ	5.5A	Same
IRFP460A	TO-247	500V	270mΩ	20A	Same
IRFP450A	TO-247	500V	400mΩ	14A	Same
IRF840A/S	TO-220/D ² -Pak	500V	850mΩ	8A	Same
IRF830A/S	TO-220/D ² -Pak	500V	1400mΩ	4.5A	Same
IRFPC50A	TO-247	600V	600mΩ	11. A	Same
IRFBC40A/S	TO-220/D ² -Pak	600V	1200mΩ	6.2A	Same
IRFBC30A/S	TO-220/D ² -Pak	600V	2200mΩ	3.6A	Same
IRFR1N60A	D-Pak	600V	7000mΩ	1A	Same

HIGH PERFORMANCE SERIES Up to 40% better



New P/N	Package	BV _{dss}	R _{os(on)}	I _d	R _{os(on)} Improvement over Industry Standard
IRFP22N50A	TO-247	500V	230mΩ	22A	15%
IRFB11N50A	TO-220	500V	520mΩ	11A	39%
IRFS11N50A	D ² -Pak	500V	520mΩ	11A	39%
IRFIB7N50A	TO-220 Fullpak	500V	520mΩ	6.6A	39%
IRFB9N60A	TO-220	600V	750mΩ	9.2A	37%
IRFIB6N60A	TO-220 Fullpak	600V	750mΩ	5.5A	37%
IRFSL9N60A	TO-262	600V	750mΩ	9.2A	37%
IRFS9N60A	D ² -Pak	600V	750mΩ	9.2A	37%

Available in UK from: Abacus Polar, Arrow, Farnell, Future Electronics, RS Components, Solid State Supplies, WBC.

Now it's easier to make the best choice in power MOSFETs. HEXFET® Power MOSFETs.

Because *only* IR gives SMPS designers a complete range of solutions. From benchmark performance that sets tomorrow's performance standards, to cost-effective solutions that meet today's.

So make the right choice. Log on or call your local IR representative for more information today.

More power to you.

International
IR Rectifier

For technical assistance call +44 (0)1883 733 309 or the Fax-on-Demand system on +44 (0)1883 733 420.

www.irf.com

CONTENTS

795 COMMENT

Aromatherapy and audiophools

797 NEWS

- Recovery for Europe's chip market
- 2000 fix turns off 2000 lights
- Tiny microphone responds to air flow
- Phone tapping needed for mobiles, etc?
- Gigabit comms via light beam
- E-commerce – UK industry boom?

802 VHF RECEIVER IN DSP

In this VHF broadcast band receiver, everything from tuning to demodulating is done in software by a high-performance DSP chip. **Michael Slifkin et al** explain how with a fully worked design example.

811 LOW VOLTAGE DESIGN II

Four leading researchers in the field of low-voltage, low-power analogue ICs explain how new topologies are being used to overcome the limitations of working with low supply voltages and currents.

818 CIRCUIT IDEAS

- Battery dynamo bicycle lighting
- Line-powered music on hold
- Sleep switches for lamps
- AC continuity testing
- 10V to 3kV voltage converter
- Water detector
- Peak-video-to-dc converter
- Synchronous am detector
- Voltage control for a digital delay line
- Quick-on, delayed-off switching
- Using a 555 for speed control
- Lead-acid battery charger
- Electronic load

831 THE ROUTE TO SIMULATION IV

Rod Cooper investigates the comprehensive circuit CAD package Proteus, which has recently benefited from a new simulation engine.

836 FINISHING OFF

Ian Hickman looks at some of the many short cuts for making a prototype or one-off instrument look professional.

841 NEW PRODUCTS

New product outlines, selected and edited by **Richard Wilson**



Save 45% on an RS232 wireless link

Need a wireless RS232/485 link for your PC? As an EW reader, you can obtain two wireless serial-link modems almost for the price of one. These licence-exempt 19.2kbaud units are complete plug-in-and-go modules. See page 840 for details.

849 CRYSTALS MADE CLEAR II

Joe Carr describes the benefits and trade-offs of a variety of quartz crystal oscillator circuits covering all frequencies ranging from 50kHz to 110MHz.

859 ANTI-JITTER: NEW CIRCUITS


Most analogue building blocks used today were invented decades ago. Here, **Neil Downie** details a brand new circuit that can offer significant advantages relative to the PLL in combating jitter.

865 HANDS-ON INTERNET

All-pass filters, instrumentation amplifiers, simulated inductors and single-wire bidirectional communications links among applications that can benefit from transconductance op-amps, as **Cyril Bateman** has been finding out.

870 SVGA GENERATOR

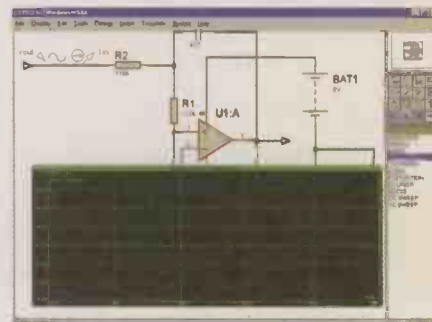Roy Harding's complete test generator design uses a PIC variant that's so fast that it's capable of producing SVGA signals without any external timing circuitry.



Proteus differs from circuit simulation packages reviewed so far in that it has no virtual instruments. But might its alternative analysis tools suit you better? Turn to page 831 to find out.



A microphone whose sensing elements are so tiny that they react to air flow rather than sound pressure. Read how on page 797.

New sensor detects a moving human body using four 1.35 by 1mm sensing elements – one of dozens of new products featured on pages 841-846.

November issue on sale 9 September

CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road,
Ely, Cambs. CB4 7PW

Tel: +44 (0)1353 666709 Fax: +44 (0)1353 666710

Low cost professional quality Smart Card Systems

CHIPDRIVE

The intelligent programmer for Smart Cards using the International Standard T=0 or T=1 protocols also Memory and Secure Memory using PC, 2-wire & 3-wire interfaces. From April 1 1999 all ChipDrives are supplied with software to read and write to most popular secure smart cards, inc GSM, PAY PHONE and ACCESS CONTROL cards. Drivers are available for Apple Macintosh, Linux, Unix, Solaris, Microsoft PC/SC and of course WINDOWS 95/98 and NT. Supplied with CARDSEVER API for easy development of SmartCard Applications using Visual Basic, Delphi or C++.



CHIPDRIVE INTERN

£49.95 + P&P £7.50

Exclusive of VAT

CHIPDRIVE ExTERN

£49.95 + P&P £7.50

Exclusive of VAT



CHIPDRIVE Micro

£39.95 + P&P £7.50

Exclusive of VAT

All Chipdrives are supplied with a Windows API and full documentation. ChipDrives are CE Compliant ChipDrives conform to ISO7816, T=0 or T=1 @ 3.579MHz, RS232 @ 9600-11500 bps, Internal Supply/Ni-MH. Under normal conditions power is derived from the host Serial Port. Operation is simple, full telephone and email support is provided for Windows developers.

APP-LOCK

Protect any Windows applications from
Unauthorised access under Win 95/98/NT
Inclusive of Chipdrive Intern, Smart Card
and Software.

£79.95 + P&P £5 exclusive of VAT

FREE
GSM CARD READING application
supplied with CHIPDRIVE-micro

CHIPDRIVE Developer Kit

CDK consists of: CD ROM containing cardserver.dll. Applications and Source code examples. CHIPDRIVE-micro a selection of Smart Cards offering protected memory, processor and memory cards. Typical uses are Control access, Pay Phone cards and Data transport. PIN codes for the cards are supplied along with data sheets and programming data for use with cardserver.dll. A useful application with source code shows how the CHIPDRIVE can be used to identify any

Smart card inserted, giving manufacturer info, and memory map if available. Applications produced with the developer kit will operate under Windows 3.11/95/NT and are compatible with the whole CHIPDRIVE family. The CDK uses easy to use 16 bit or 32 bit DLLs with just one function call to the 'CardServer' to identify the card or carry out any instruction. Cardserver is a powerful Background task which relieves the application programmer from device and card administration. Featuring automatic protocol and card type detection. Allowing several applications to access one terminal dependent only on the type of card inserted.



£69.95 +
P&P £5 Exclusive of VAT

Supplied with CHIPDRIVE micro,
Smart Cards and Source Code.
Full Tech Support via Email.

<http://www.towitoko.co.uk>

<http://www.crownhill.co.uk>

<http://www.edsim2000.com>

Ease'IT

£149.95

13.5Mhz-technology Contactless Smart Card Development System

Access Control, Identification, Payment, Loyalty, Transport.....

- Ease'IT the development tool for systems integrators and reader manufacturers, providing access to contactless Smart Card technology at an affordable price and with less than one weeks integration effort.
- Ease'IT integration system contains: 10 X contactless Smart Cards, 1 X contactless 5V Reader/Writer, 1 X 13.5Mhz antenna with connector cable, Comprehensive technical documentation and a CD ROM containing all the necessary software drivers including an easy to follow integration users guide with detailed examples.
- Communication distance of up to 10cm, data exchange at 106 Kbits per second!
- Ease'IT Contactless Smart Card Reader/Writer can replace an existing Contact Card socket, pin for pin or it may be connected directly to a PC or an embedded system.
- Detailed documentation enables fast integration to existing systems, allowing contactless cards to be used with most existing applications.
- Fastest integration time to an existing application so far..... **3 Hrs !!!**

CIRCLE NO.104 ON REPLY CARD

hitex
DEVELOPMENT TOOLS

The First Rung On The Microcontroller Ladder



Siemens uC starter kits are a great way to get into the world of embedded systems. With peripherals like ADC, Capture/Compare and Controller Area Networking, you will be able to get your ideas going fast - you can choose between the popular 8-bit C500 CPU family or the 12.5 MIPS 16-bit C167 family to get the best fit for your project.

From £110 +VAT

For further details see our website

www.hitex.co.uk

Hitex (UK) Ltd. University of Warwick Science Park, Coventry, CV4 7EZ

Tel: 01203 692066 Fax: 01203 692131

Email: sales@hitex.co.uk Web: www.hitex.co.uk

KIT

CIRCLE NO.105 ON REPLY CARD

Aromatherapy and audiophools

EDITOR

Martin Eccles
0181 652 3614

CONSULTANTS

Ian Hickman
Philip Darrington
Frank Ogden

EDITORIAL ADMINISTRATION

Jackie Lowe
0181-652 3614

EDITORIAL E-MAILS

jackie.lowe@rbi.co.uk

ADVERTISEMENT MANAGER

Richard Napier
0181-652 3620

DISPLAY SALES EXECUTIVE

Joannah Cox
0181-652 3620

ADVERTISEMENT E-MAILS

joannah.cox@rbi.co.uk

ADVERTISING PRODUCTION

0181-652 3620

PUBLISHER

Mick Elliott

EDITORIAL FAX

0181-652 8111

CLASSIFIED FAX

0181-652 8938

NEWSTRADE ENQUIRIES

0171 261 7704

ISSN 0959-8332

SUBSCRIPTION HOTLINE

01622 778000

SUBSCRIPTION QUERIES

rbp.subscriptions@rbi.co.uk
Tel 01444 445566
Fax 01444 445447

For a full listing of
RBI magazines:
<http://www.reedbusiness.com>



In most fields of electronics charging £120 for a short piece of wire with a plug at either end would not win you many customers. The audiophile, or rather audiophool, business is different; it turns the rules of business – and of science – apparently on their head.

Let me explain, for those of you unfamiliar with this fascinating market.

Successful retailing, they say, is the painless extraction of money from the pockets of satisfied customers. This is normally achieved by providing them with goods at competitive prices that meet their genuine needs.

Supplying audiophools is different; it's akin to selling aromatherapy essences, or those copper bracelets that combat rheumatism.

It's a profitable business too, with apparently rational adults – all men by the way; womankind is honourably exonerated – spending serious amounts of money on something they cannot see, cannot feel and cannot justify the cost of.

No scientific backup is offered for the claims made for the betterment of music. If these traders were selling patent medicines, they'd be outlawed within weeks, but in audiophool circles the Trades Descriptions Act appears not to apply.

Looking through current British hi-fi magazines I see vendors offering:

- mains plugs with rhodium-plated pins for better audio listening;
- 'sublime' glass platter mats for sheer three-dimensional detail resolution;
- overlay mats for realising better sound from CDs;
- interconnects (you mustn't called them connecting leads any more, oh no!) made from oxygen-free copper with crystals aligned in the direction of the music;
- other interconnects containing 'a particular inorganic chemical' to

- improve sonic qualities;
- replacement capacitors of guaranteed 'musical' sound quality;
- long-grain pure silver wire for building better amplifiers.

The strange thing is that most audiophools are not ignorant peasants; far from it. To be duped in this way implies significant material achievement (put another way, deep pockets) and a maturity of personal development that properly appreciates high-end sound and musicality, if not music for its own sake.

Music has to be chosen very carefully of course; most audiophools are aggressively analogue and will not countenance those silver beer mats. A few, however, will embrace CDs – so long as these are the remastered gold substrate variety. In either case, whatever individual preference the audiophool once had for music is now subjugated since he now listens only to reference recordings, for facilitating participation in comparisons with other audiophools.

In all this pursuit of aural excellence, the established techniques developed and proven over the years by audio professionals are studiously ignored. So signal cables made of sensible, affordable copper are rejected in favour of sexier affairs made of pure silver – or else of refined virgin unobtainium.

Sensible, solid XLR connectors with contacts having large surface areas are abandoned for slender phono plugs with expensive gold plating. Proper balanced audio cables with a grounded lapped foil screen are ignored in favour of interference-prone twin-line.

Design logic counts for little in the equipment too. Even though MOVs for eliminating mains-borne transients are very cheap, it would not occur to the manufacturer of a £1500 CD player to build suppression into the device. Instead the solution is sold as an outboard add-on –

naturally with an audiophool seal of approval. Its price is a drop in a bucket compared with the price of the other toys so vendors are laughing all the way to the bank.

The effects of mains-related quackery may be positively dangerous too.

There's a story – it may be urban legend – of one audiophool who short-circuited his house fuses in order to reduce the internal resistance of the mains supply, thus improving his equipment's voltage regulation.

His house burned down. Responsibility for perpetrating all this pseudo-science lies with the audiophool journals. An unhealthy collusion between advertisers and publishers perpetuates this aura of mystique, with few titles prepared to prejudice their revenue stream by exposing the emperor's new clothes.

Sanity still exists in some quarters of course, particularly in the letters department of this very journal. Anything to do with audio that's loopy or even slightly subjective soon gets knocked down to Earth here.

Some refreshing candour is also appearing in some of the Internet discussion groups for high-end audio; one pundit recently suggested that for genuine 'liquid sound' the only solution was to use mercury-filled speaker cables – and then devalued this advice by admitting this was an April Fool's joke.

But perhaps we should live and let live. If aromatherapists or other practitioners of fringe medicine can successfully relieve suffering and make the world a happier place, then why shouldn't audiophools enjoy their expensive pleasures too? It's easy to misjudge people anyway; some audiophools regard 'professionals' as cloth-eared cretins, who are too stupid and/or deaf to appreciate the audio art at the (superior) audiophool level.

Keep smiling!

Andrew Emmerson

Electronics World is published monthly. By post, current issue £2.45, back issues (if available) £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx:892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd. **Newstrade:** Distributed by Markforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108. **Subscriptions:** Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00 ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre Mussord, 18-20 Place de la Madeleine, Paris 75008. United States of America: Roy Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel; (212) 679 8888 Fax; (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd, Filmsetting by JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex S52 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332

Get on board the Easy-PC For Windows revolution!!


Power-Packed PCB Layout for Windows '95/'98/NT at Computer Store Prices!!

Easy-PC - Number One Systems - [PCB Design, Cps.pcb]


Unlimited pins,
or 2000 pin
1000 pin
500 pin
versions

From
£97

33,000 Easy-PC users must be right!!

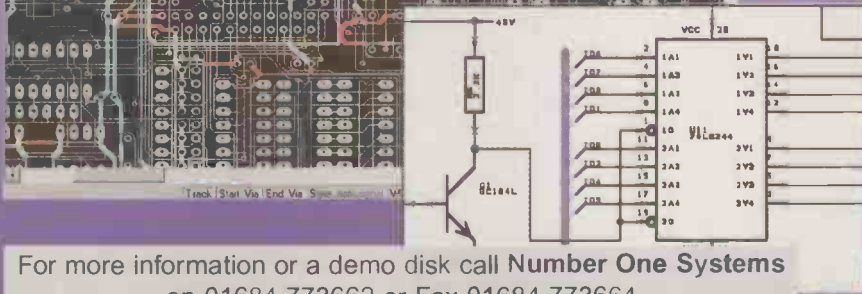

- True 32 bit Windows application
- Schematic and PCB Design editors as standard
- Design in Imperial, Metric or mixed units (no rounding errors)
- Drawing area up to 1m x 1m (39" by 39")
- Design precision down to 10th Micron (0.00001mm)
- Rotation to 1/10th degree
- Intelligent Cut, Copy and Paste across designs
- Multi-level Undo and Redo
- Integrated component Autoplace
- Integrated shape based Autorouter (Optional extra)
- Intelligent bussing in schematics
- Supports SMT, Through-hole and mixed technology
- Intelligently supports SMT on both sides of the design
- Unlimited number of PCB design layers
- Cross probing schematics to PCB design and Projects
- Forward annotation of design changes from schematics
- Back annotation of net name/component name changes
- Dynamic Pan, Zoom In/Out and Frame Views
- Dynamic drag and drop to/from component bin
- All design elements per design are unlimited
- Graphical Design Rule Checker
- Integrity and Connectivity Checker
- Professional manufacturing outputs

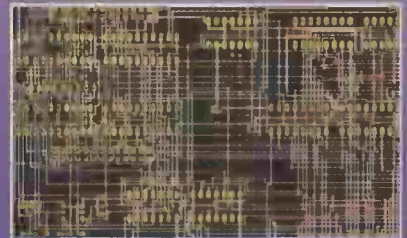


For more information or a demo disk call Number One Systems
on 01684 773662 or Fax 01684 773664
Email info@numberone.com
Number One Systems, at Sightmagic Ltd, Oak Lane,
Bredon, Tewkesbury, Glos, GL20 7LR. UK

Visit our WEB site www.numberone.com

Now with optional autorouter!!

CIRCLE NO.106 ON REPLY CARD

Not just a pretty interface

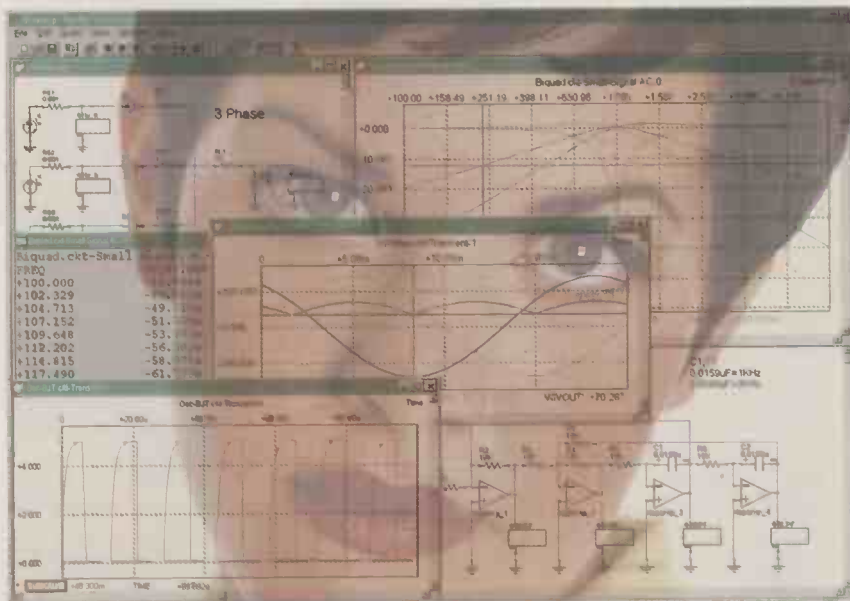

Available on 30 day evaluation
Free technical support
Mac version also available



B² Spice for analogue simulation £199
B² Logic for digital simulation £199
Special bundle price £295

All prices shown exclude VAT
Postage & Packing £5.00

B² Spice & B² Logic

Professionals, universities and designers need software that produces results they can rely on. B² Spice and B² Logic will give you the accurate results you need - fast.

The best way to find out if a package is really what you need is to try it, which is what we're giving you the chance to do, risk free for 30 days.

We guarantee you will be 100% satisfied with the results or your money back.

RD Research

Tel: 01603 872331

Research House, Norwich Road, Eastgate, Norwich NR10 4HA Email rd.research@paston.co.uk www.looking.co.uk/spice

CIRCLE NO.107 ON REPLY CARD

UPDATE

Recovery showing for Europe's chip market

Despite the continuing DRAM debacle, the semiconductor market recovery in Europe is under way, according to a report from analysts Future Horizons of Sevenoaks, called 'The European Semiconductor Market Report 1996-2004.'

Describing the DRAM market as a 'Fubar' (Fouled Up Beyond All Reason), Malcolm Penn, chairman of Future Horizons, commented: "It's out and out obsession with who's going to be No 1 in worldwide DRAM production,

whatever the cost."

A price war between Micron of Idaho and the Korean companies has seen prices of 64Mbit DRAMs drop from \$8 to \$4. "At these prices no one is profitable," says the report.

On the upside, business at silicon foundries is growing at twice the industry rate, with product allocations threatened later this year. High-end logic and flash are also rebounding.

The report warns of a capacity shortage later this year and next which may accelerate plans for 12in

wafer production. It believes the first users of 12in wafers will be Infineon, Intel, NEC, Samsung, STMicroelectronics and TSMC.

European semiconductor market forecast. (\$bn)

Year	1999	2000	2001
Discretes	3.3	3.7	4.1
Opto	0.9	1.2	1.6
IC	28.3	35.1	45.5
Total	32.5	40.0	51.2

2000 fix turns off 2000 lights

Two thousand Londoners were left without electricity recently when a Year 2000 upgrade to pre-pay meters went wrong.

London Electricity was trying to make its meters millennium compliant before the date change, but ended up cutting off over 2000 customers.

"Our Powerkey meters don't recognise the date change," said a London Electricity spokesperson. "They would continue to supply electricity, but wouldn't recognise

any price changes."

The electric company came up with a plan to upload new software when customers next recharged their meters.

"About 8000 people tried to do the fix, of which 2000 did not work," said the spokesperson. When the credit on these meters ran out, customers were left without power.

"The majority were put back on within 24 hours," he said "We're not aware of anyone that's been off any longer than 48 hours."

London Electricity's remaining 400 000 Powerkey customers will wait until the problem with the keys is rectified before having their meters upgraded.

The government's Year 2000 watchdog, Action 2000, and Offer, the electricity watchdog, has graded 95 per cent of electricity firms as 'blue' in their traffic light grading system of compliance. This indicates 'no material risk of disruption', although the London Electricity case shows disruption several months before the date change.

Smaller, lighter microphone responds to air flow, not pressure

Researchers at the University of Twente in the Netherlands have developed a microphone that is smaller and lighter than conventional units.

Rather than measuring sound pressure, the device, called a 'microflow'n', measures particle velocity, or air flow.

Micromachining is used to create two closely spaced silicon-nitride wires. These are coated with a platinum resistor. Each wire is 1mm long.

Current passed through the platinum elements heats the wires to between 200°C and 400°C. The flow of air due to sound waves causes the wire closer to the sound source to be cooled, with the amount of cooling being linearly dependent on the velocity of the airflow.

Because the wires are close

together, convective heat flow causes the temperature of the other wire to rise. The temperature difference is measured as a voltage output by placing the resistive wires in a Wheatstone bridge.


The sensor acts as a low pass filter, because thermal mass of the wires limit their ability to follow fast changing signals. At low frequencies the response is flat while higher frequencies show a 6dB/octave drop.

Two types of microflow'n have different responses. The cantilever type (pictured) has a relatively low corner frequency of 400Hz. The bridge type, where both ends of the wires are supported, has a higher corner frequency of 1kHz.

Both types can be used for speech, providing the low pass behaviour is corrected electrically, or through

digital signal processing.

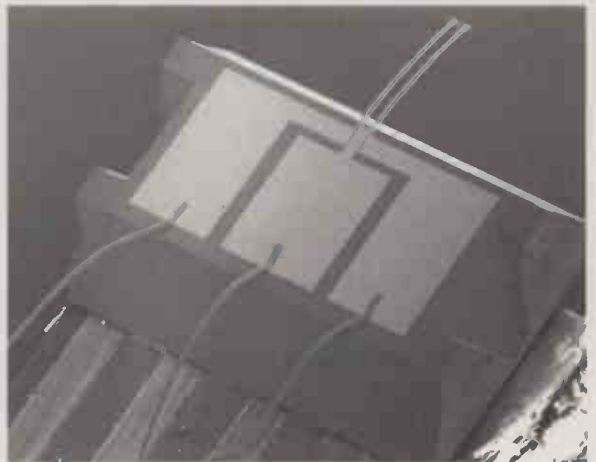A frequency range of 100 to 3.4kHz is possible, the researchers claim.



PROBLEMS IDENTIFYING EUROPEAN EMC STANDARDS?

EMC Master

Get the EMC Master Info CD instead of a consultant for only \$ 395

EMC pre-compliance test sets for both radiated and conducted immunity as well as emission tests. LogPer antenna's, Tem-Cell's RF-amplifiers and ESD generators at unbeatable prices. Software controlled Spectrum Analyser suitable for both US and European standards (June 1998). The unique EMC Master Info CD does not only help you to select the proper European EMC standards, it also suggests the test set-up and requirements.

Check www.emcmaster.com or call (International: ++31-3569-41774)



Innovative EMC Test Set for less

New tapping measures for Internet and mobiles

Are you and 'arf-a-dozen of yer chinas down the East End' planning a bank job? Are you worried about the old Bill listening in on your dog-and-bone?

No problem, my son. Today you can get instant, off-the-shelf, secure communications that will cost you only the price of a drink. Just buy a few pre-pay mobile phones down at Dixons. Set up a free Internet account, preferably with ready-made encryption software. The police will have no idea who owns them, or which company is transmitting your conversations. Throw your equipment away afterwards, and most of the incriminating evidence is gone forever.

This is the problem now facing the police. Because of the boom in new types of telecoms networks and the Internet, they can no longer

With the boom in telecoms networks, phone tapping is getting harder for the police. Now the Home Office plans to bring police phone tapping into the era of mobiles and the Internet. Pete Mitchell reports

reliably eavesdrop on criminal activities through telephone tapping – or so claims the Home Office.

Authority for the police to listen in on suspects' phone conversations comes from the Interception of Communications Act. Passed in 1985, the IOCA merely confirmed the decades-old gentleman's agreement between the former GPO – which operated the public switched network – the exchange suppliers such as GEC and Plessey, and the Home Office. It enables the police to get a warrant to monitor any fixed subscriber line owned by a public telecommunications operator, using purpose-built functions in the BT switch.

But the IOCA's authors had obviously never heard of cellphones, satellites, the Internet, or even cable. They completely ignored the existence of private voice or data networks, which were much rarer and more localised then than they are today, and which now carry a substantial amount of public traffic for much of its journey.

An even bigger limitation is that the IOCA warrants only apply to licensed public telecommunications operators, whereas the industry now contains many unlicensed service providers. It, and the crooks, have moved on, and the Home Office now wants to move with them.

So it recently produced a consultation paper outlining its plans for an extended IOCA, and sent it for comments to the telecoms industry – an industry now consisting of cellular network operators, Internet service providers, about 150 fixed-line phone companies (rather than two when IOCA was written), bandwidth-resale companies, and private network owners.

ISPs, comms and net operators in panic

These firms are now in some panic. Not only will the reborn IOCA require all firms to install new infrastructure – capable of secretly monitoring the entire traffic of any of their customers within a few minutes of receiving a warrant – but it will also demand that the operators themselves pay the entire cost of this privilege. As the consultation paper puts it, "... communication service providers will be required to take reasonable steps to ensure that their system is capable of being intercepted. This will be an ongoing requirement which CSPs will have to consider each time they develop their network or introduce new services".

The costs will run into millions. And some of the functions that the Home Office is demanding cannot be delivered at all using current technology, said Keith Mitchell, chairman of the LINX association of Internet service providers.

"The requirements were constructed by police officers who seem to have assumed that the Internet works just like the voice telephone network, which it doesn't at all," he said. "They want listening devices installed on every Internet backbone router. Personally, I don't see how that could be done, but even if it could, it might be open to abuse and could potentially compromise the overall security of the Internet.

"Some of the services they want could degrade the performance seen by someone who was being monitored, and it's quite possible that they could detect that they were being monitored as a result."

Cost implications

Such performance penalties would affect the innocent Internet user too, he adds. So, of course, would the cost – estimated at between

20 and 40 per cent of the total infrastructure costs of a typical ISP – that would be passed on to customers. Some ISPs would probably even have to re-design their backbones to match the topology assumptions made in the proposals, he said.

"It's most unfair that they are proposing service providers should pay for this," he said. "Some of the technology isn't available off the shelf yet, so it's not just a question of ISPs going out and buying a box. The equipment manufacturers would have to commit R&D money to develop it."

The cellphone operators are equally alarmed, and much less well prepared. The Federation of Communications Services, the mobile operators' trade association, has not yet agreed on its response. It is still consulting its members and trying to work out the financial impact on their business, said Chris Webb, an FCS spokesman: "What is certain is that it will affect both the service providers and the networks quite dramatically."

It is expected that some of the larger networks – those linked to telecoms companies who have dealt with the Home Office for many years – will have seen this coming and made at least some preparations for it. But the smaller operators have been caught completely on the hop.

What will the customers think?

And re-engineering their network management systems is not the only issue: operators are privately worried about how the new legislation will affect their relations with customers, too.

"It will be a tricky balancing act to convince our subscribers we are respecting their confidentiality at the same time as we have to work in the new framework," said one.

To forestall objections, the Home Office is trying to bluff the industry into believing that, "these proposals are consistent with existing legislation and practice in many other countries including France, Germany, the Netherlands, Sweden, the USA, Canada and Australia".

But, "What they mean is that other countries have signed up for this, but not implemented it yet," said Mitchell. He warns that the UK is in severe danger of giving its Internet industry the most stringent monitoring requirements in the world.

"Other countries will then choose not to route their traffic through here for fear that confidentiality safeguards will be breached, and that could be very harmful to our information economy."

NEED A GOOD ESD GUN WITHOUT A BUDGET FIGHT?

EMC Master

Buy the EMC Master pre-compliance ESD Generator for just \$ 1.695

EMC pre-compliance test sets for both radiated and conducted immunity as well as emission tests. LogPer antenna's, Tem-Cell's RF-amplifiers and ESD generators at unbeatable prices. Software controlled Spectrum Analyser suitable for both US and European standards (June 1998). The unique EMC Master Info CD does not only help you to select the proper European EMC standards, it also suggests the test set-up and requirements.

Check www.emcmaster.com or call (International: +31-3569-41774)



Innovative EMC Test Set for less

PLUG IN AND MEASURE

8-12 bit
200kHz-50MHz
100mVolt-1200Volt

STORAGE OSCILLOSCOPE
SPECTRUM ANALYZER
VOLTMETER
TRANSIENT RECORDER



TiePie introduces the HANDYSCOPE 2

A powerful 12 bit virtual measuring instrument for the PC

The HANDYSCOPE 2, connected to the parallel printer port of the PC and controlled by very user friendly software under Windows or DOS, gives everybody the possibility to measure within a few minutes. The philosophy of the HANDYSCOPE 2 is:

"PLUG IN AND MEASURE".

Because of the good hardware specs (two channels, 12 bit, 200 kHz sampling on both channels simultaneously, 32 KWord memory, 0.1 to 80 volt full scale, 0.2% absolute accuracy, software controlled AC/DC switch) and the very complete software (oscilloscope, voltmeter, transient recorder and spectrum analyzer) the HANDYSCOPE 2 is the best PC controlled measuring instrument in its category.

The four integrated virtual instruments give lots of possibilities for performing good measurements and making clear documentation. The software for the HANDYSCOPE 2 is suitable for Windows 3.1 and Windows 95. There is also software available for DOS 3.1 and higher.

A key point of the Windows software is the quick and easy control of the instruments. This is done by using:

- the speed button bar. Gives direct access to most settings.
- the mouse. Place the cursor on an object and press the right mouse button for the corresponding settings menu.

- menus. All settings can be changed using the menus.

Some quick examples:

The voltage axis can be set using a drag and drop principle. Both the gain and the position can be changed in an easy way. The time axis is controlled using a scalable scroll bar. With this scroll bar the measured signal (10 to 32K samples) can be zoomed live in and out.

The pre and post trigger moment is displayed graphically and can be adjusted by means of the mouse. For triggering a graphical WYSIWYG trigger symbol is available. This symbol indicates the trigger mode, slope and level. These can be adjusted with the mouse.

The oscilloscope has an AUTO DISK function with which unexpected disturbances can be captured. When the instrument is set up for the disturbance, the AUTO DISK function can be started. Each time the disturbance occurs, it is measured and the measured data is stored on disk. When pre samples are selected, both samples before and after the moment of disturbance are stored.

The spectrum analyzer is capable to calculate an 8K spectrum and disposes of 6 window functions. Because of this higher harmonics can be measured well (e.g. for power line analysis and audio analysis).

The voltmeter has 6 fully configurable displays. 11 different values can be measured and these values can be displayed in 16 different ways. This results in an easy way of reading the requested values. Besides this, for each display a bar graph is available.

When slowly changing events (like temperature or pressure) have to be measured, the transient recorder is the solution. The time between two samples can be set from 0.01 sec to 500 sec, so it is easy to measure events that last up to almost 200 days.

The extensive possibilities of the cursors in the oscilloscope, the transient recorder and the spectrum analyzer can be used to analyze the measured signal. Besides the standard measurements, also True RMS, Peak-Peak, Mean, Max and Min values of the measured signal are available.

To document the measured signal three features is provided for. For common documentation three lines of text are available. These lines are printed on every print out. They can be used e.g. for the company name and address. For measurement specific documentation 240 characters text can be added to the measurement. Also "text balloons" are available, which can be placed within the measurement. These balloons can be configured to your own demands.

For printing both black and white printers and color printers are supported. Exporting data can be done in ASCII (SCV) so the data can be read in a

spreadsheet program. All instrument settings are stored in a SET file. By reading a SET file, the instrument is configured completely and measuring can start at once. Each data file is accompanied by a settings file. The data file contains the measured values (ASCII or binary) and the settings file contains the settings of the instrument. The settings file is in ASCII and can be read easily by other programs.

Other TiePie measuring instruments are: HS508 (50MHz-8bit), TP112 (1MHz-12bit), TP208 (20MHz-8bit) and TP508 (50MHz-8bit).

Convince yourself and download the demo software from our web page: <http://www.tiepie.nl>. When you have questions and / or remarks, contact us via e-mail: support@tiepie.nl

Total Package:

The HANDYSCOPE 2 is delivered with two 1:1:10 switchable oscilloscope probe's, a user manual, Windows and DOS software. The price of the HANDYSCOPE 2 is £ 299.00 excl. VAT.

TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340

TiePie engineering (NL)
Koperslagersstraat 37
8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416
Fax +31 515 418 819

Gigabit speed comms through air via a light beam

Lucent Technologies' Bell Labs has put dense wave division multiplexing, or DWDM, technology into use for transmitting data through the air using beams of light.

The optical system called WaveStar OpticAir is claimed to be the first to use DWDM directly through the air and can cope with voice, data or video traffic. The system builds on Lucent's existing fibre optic system using a lot of the same technology.

A high power optical amplifier is used to boost the signal up to 1W before it is transmitted down a single-mode fibre optic cable to a telescope.

The signal is coupled to four 3cm transmitting apertures in the telescope which are configured in a square pattern around a 20cm

receiving aperture. The light from the apertures diverges as it is transmitted so at a distance of 2km the diameter of the beam will be approximately a metre.

In the multichannel system each signal is sent on a different frequency boosted by its own amplifier. At the telescope the signals are mixed and each aperture sends all the signals.

The four transmitting apertures are all focused on the receiving aperture at the other end. When the signal is received it is sent down a multi-mode fibre into an avalanche photo diode. A DWDM multi-mode demultiplexer splits out the signals.

The system is still being worked on in the lab and Jim Auburn, Bell

Labs' head of communications technology department, is very enthusiastic about its performance. "In principle you can do just about what you can do with fibre systems," explains Auburn.

The first version is expected in March 2000 and will support one wavelength at speeds up to 2.5Gbit/s. This will be followed in the summer by a four wavelength system with a maximum capacity of 10Gbit/s for distances up to 5km.

Auburn says that the transmission distance can be greater depending on the atmospheric conditions. "We can really transmit as far as you can see," he comments. "If the weather gets bad you can increase the power or transmit data at a lower rate."

E-commerce could spark UK industry boom

British electronics manufacturers have a major opportunity to prosper through the use of the Internet. That is the message of Dr David Cleevely, a member of the government's steering group on e-commerce.

"The UK is very good at inventing and has a strong understanding of how things are made," said

Cleevely. Where it is less effective is in volume production.

What e-commerce offers, claimed Cleevely, is a way of bridging the gap between idea generation and innovation, and final distribution. "You don't need to manufacture here," said Cleevely, who is also managing director of telecoms consultancy Analysys. "What is important is to understand how things are made."

"I agree with him 100 per cent," said Cliff Hardcastle, chairman of display manufacturer Densitron. "I also think it [this approach] is the only way forward."

His belief is that the UK is unique in its ability to respond quickly to development

opportunities. "It is good at design and it is good at organising it."

Hardcastle plans to exploit these strengths by setting up a propagation company that will use the Internet to offer customers access a raft of key companies not just for manufacturing but design too. "It will take advantage of opportunities wherever they occur," he said.

Meanwhile, Cleevely argues is that if UK manufacturers successfully exploit e-commerce, "we could start to see year-on-year growth way above anything we've seen since the Second World War."

Engineers patently spy on rivals

Engineers are using patent information to keep a close eye on their competitors, according to a survey commissioned by Derwent Information. The Europe-wide survey showed that 55 per cent of respondents use patent information for 'competitive intelligence'.

They're no test dummies... Test dummies certainly did not design the airbag deployment test system that Rugged Systems is offering to vehicle manufacturers. The system designed by ARIES in Spain allows manufacturers to determine the threshold trigger speeds and decelerations of airbags.



Chips form part of pet passport plan

The government is to introduce a microchip-based pet passport scheme. A pilot scheme for Western Europe will start next April with a wider scheme planned for 2001. Under the scheme, the animals travelling from Britain or entering the country from abroad will have to be vaccinated against rabies and have an identifying microchip inserted under their skin. The process will cost £150 with a further £30 a year for annual booster injections, compared to £2000 for six months in quarantine.

TIRED OF OVERPRICED ANTENNAS & RF-AMPLIFIERS?

EMC Master

Select EMC Master's 10W 150 kHz - 250 MHz amplifier for \$ 1995

EMC pre-compliance test sets for both radiated and conducted immunity as well as emission tests. LogPer antenna's, Tem-Cell's RF-amplifiers and ESD generators at unbeatable prices. Software controlled Spectrum Analyser suitable for both US and European standards (June 1998). The unique EMC Master Info CD does not only help you to select the proper European EMC standards, it also suggests the test set-up and requirements.

Check www.emcmaster.com or call (International: ++31-3569-41774)



Innovative EMC Test Set for less

WINRADIO


TAKING THE EUROPEAN RADIO MARKET BY STORM

TAKE A LOOK AT WINRADIO'S DIGITAL SUITE SOFTWARE (AWARDED 5 STARS BY WRTH)

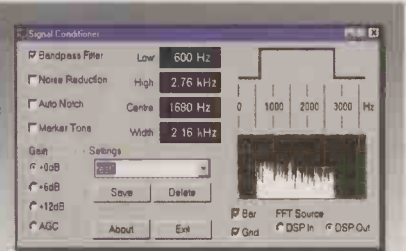1. WEFAX / HF Fax
2. Packet Radio for HF and VHF
3. Aircraft Addressing and Reporting System (ACARS)
4. Audio Oscilloscope, real time Spectrum Analyzer with calibration cursors
5. Squelch-controlled AF Recorder
6. DTMF, CTSS decode and analyse

The DSP applet provided with the WR3100i spectrum monitor ISA card (£995+VAT) allows continuous control of audio bandwidth and other signal conditioning functions.

ONLY £81.07 inc vat
(requires SoundBlaster 16 compatible sound card)



WINRADIO™ PC RECEIVERS

Available as either an internal ISA card that slips inside your PC, or as an external (portable) unit. WINRADIO combines the power of your PC with the very latest, and greatest, synthesised receivers.

YOU CAN USE WINRADIO™ SCANNING PC COMMUNICATION RECEIVERS FOR: Broadcast, media monitoring, professional & amateur radio communications, scanning, spot frequency, whole spectrum monitoring, instrumentation surveillance and recording.

If you're after the ultimate receiver-in-a-PC with full DSP then smile and say, "Hello" to the new **WR31000i-DSP** with its hardware for real-time recording, signal conditioning and decoding applications. It's all you need.

NEW EXTERNAL MODELS

EXTERNAL WINRADIO™
We are now able to offer you a complete range of stand-alone WINRADIO comms systems:

- **WR1000e - £359 inc vat**
- **WR1500e - £429 inc vat**
- **WR3100e - £1169 inc vat**

Each stand-alone unit connects to your PC through either the basic RS232, or through an optional PCMCIA adapter (for high speed control).

The units are powered through either your existing 12v supply, or through an (entirely optional) NiMH rechargeable 12v battery pack.

"It's software is excellent.. more versatile and less idiosyncratic than that of the Icom IC-PCR1000"
WRTH 1999 Review

"Five stars for its mechanical design"
WRTH 1999 Review

"Most Innovative Receiver"
WRTH 1998 Awards



Model Name/Number	WR-1000	WR-1500	WR-3100
Construction of internals	WR-1000i/WR-1500i-3100iDSP- Internal full length ISA cards		
Construction of externals	WR-1000e/WR-1500e - 3100e - external RS232/PCMCIA (optional)		
Frequency range	0.5-1300 MHz	0.15-1500 MHz	0.15-1500 MHz
Modes	AM,SSB/CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W	AM,LSB,USB,CW,FM-N,FM-W
Tuning step size	100 Hz (5 Hz BFO)	100 Hz (1 Hz for SSB and CW)	100 Hz (1 Hz for SSB and CW)
IF bandwidths	6 kHz (AM/SSB), 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)	2.5 kHz(SSB/CW), 9 kHz (AM) 17 kHz (FM-N), 230 kHz (W)
Receiver type	PLL-based triple-conv. superhet		
Scanning speed	10 ch/sec (AM), 50 ch/sec (FM)		
Audio output on card	200mW	200mW	200mW
Max on one motherboard	8 cards	8 cards	3-8 cards (pse ask)
Dynamic range	65 dB	65 dB	85dB
IF shift (passband tuning)	no	±2 kHz	±2 kHz
DSP in hardware	no - use optional DS software		YES (ISA card ONLY)
IRQ required	no	no	yes (for ISA card)
Spectrum Scope	yes	yes	yes
Visitone	yes	yes	yes
Published software API	yes	yes	yes (also DSP)
Internal ISA cards	£299 inc vat	£369 inc vat	£1169.13 inc
External units	£359 inc vat	£429 inc vat	£1169.13 inc (hardware DSP only internal)
PCMCIA Adapter (external): £69.00 inc when bought with 'e' series unit (otherwise: £99 inc)			
PPS NiMH 12v Battery Pack and Charger: £99 inc when purchased with 'e' series unit (otherwise: £139 inc)			
The WINRADIO Digital Suite: £74.99 inc when purchased with a WINRADIO receiver (otherwise: £81.05 inc)			

To receive your completely free (no obligation) info pack and WINRADIO software emulation demo disk all you have to do is get on the internet and go to our website at <http://www.broadercasting.com>. If you don't yet have easy access to the internet then by all means feel free to telephone us or send a fax.

Please send all your enquiries to: info@broadercasting.com or Telephone: 0800 0746 263 or +44 (0)1245 348000 - Fax: +44 (0)1245 287057
Enformatica Limited, Unit B, Chelford Court, Robjohns Road, Chelmsford, Essex, CM1 3AG, United Kingdom

VHF receiver in DSP

Michael Slifkin, Ziv Mayan
and Zachy Globinsky

A DSP VHF FM push-button receiver

Digital techniques are very much the in-thing in electronics, but most radio receivers still use analogue circuitry. Some fully-digital radios are available – as for example advertised on page 801 of this issue – but they are expensive.

The techniques used in digital receivers of this kind are very different from those used in their analogue counterparts. It would be a daunting task even for a very experienced radio ham to design such a receiver. Nevertheless, one who built his first 1-v-1 radio some forty-five years ago has attempted it – with the aid of younger hands.

In this article we discuss digital signal processing, or DSP, techniques in radio and then describe a working push-button VHF FM radio that we have developed and built. A good introduction to DSP techniques can be found at <http://www.bores.com/courses/intro/>.

Note that this is not a cheap design. While prices of DSP ICs are going down all the time, they are currently still expensive.

Design outline

Controlling the receiver are an EPROM and a programmed microprocessor. If you intend implementing this design, you will need access to an EPROM programmer. Putting the design together is easy since most of the components are ICs.

The circuit diagrams are presented in two sections, the analogue section and the digital section. Using eight voltage regulators may seem rather excessive, but this reflects the rather specialised needs of the various ICs. Note the separation of digital and analogue earths.

Programming can be arduous, but *Electronics World* is supplying the necessary assembly language programs on disk for anyone wanting them.

So what's wrong with analogue receivers?

The big question is why would one want to abandon techniques of radio reception which have served us well for over 60 years? Currently the answer would be not to do so because of the high cost. But clearly in the not too distant future, the costs will plummet.

A major advantage of a digital receiver is that changing its programming can alter the entire reception mode, tuning range or channel width. The tuning frequency, bandwidth, mode etc., can all be entered through a key pad, making for very simple use. In addition, a digital receiver's characteristics remain constant throughout its lifetime, resulting in much lower maintenance costs and greater reliability.

By contrast, analogue communication receivers can be difficult to tune. Furthermore, their performance and features cannot be readily changed. In addition, their characteristics can drift, requiring periodic retuning for maximum performance.

In a digital receiver, the use of wide band receivers allows much of the hardware to be shared over all the channels. Thus a completely general-purpose receiver can be built and then programmed to suit the user. It can be changed as conditions and requirements change simply by reprogramming.

Mass production of such radios could

VHF tuner – outline specifications

Frequency range	88-108MHz
Audio frequency	to 15kHz
Channel width	200kHz
Tuning resolution	0.1MHz
Dynamic range	40dB*

Audio AGC is provided. The default channel at switch on is 101MHz
*See panel entitled 'Dynamic range'

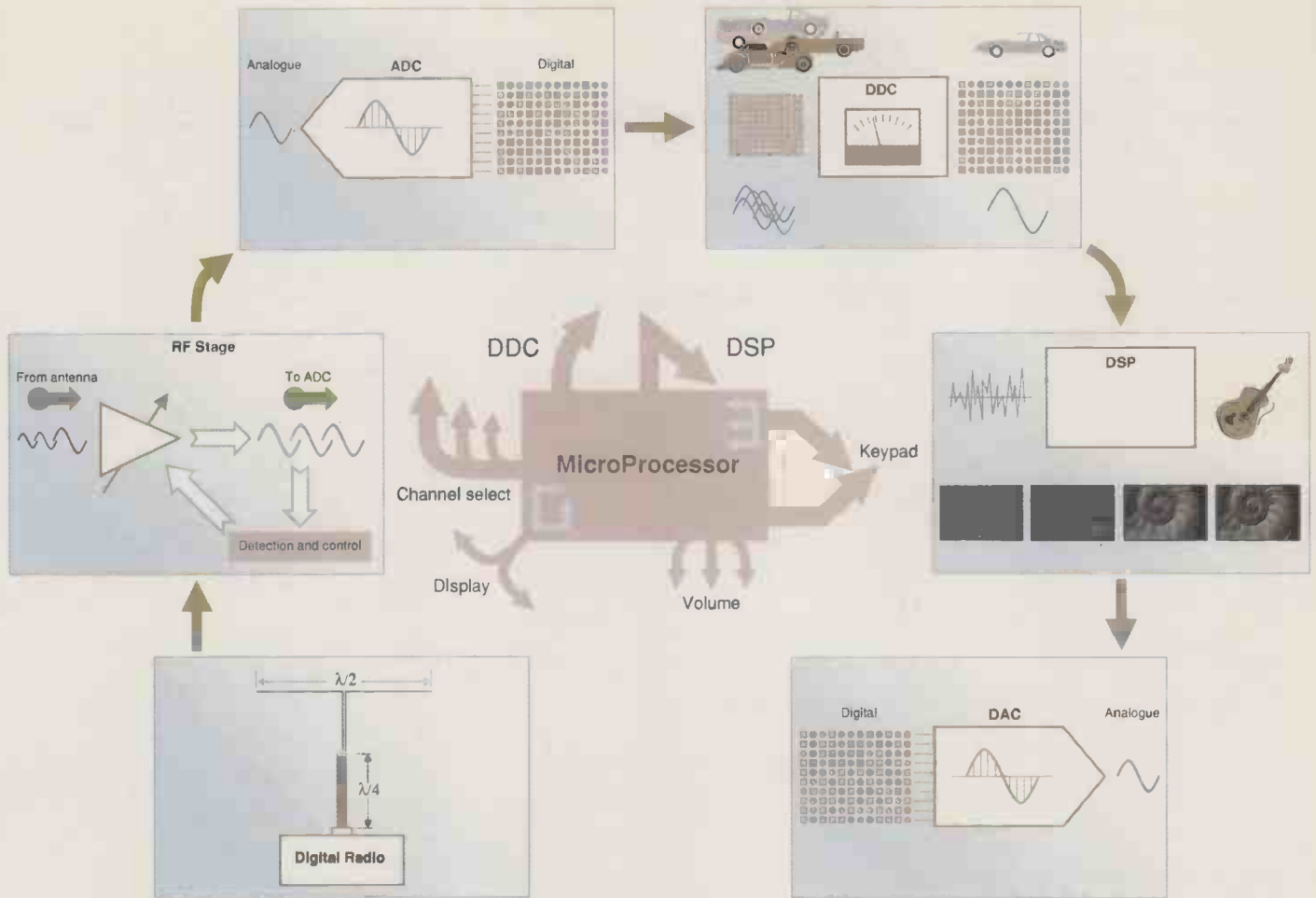


Fig. 1. Schematic Diagram of the DSP VHF FM Receiver

bring the cost to less than that of the analogue communications receiver. In addition to being cheaper, digital radios should offer more versatility and features. An excellent summary of the advantages of digital radio receivers over analogue receivers has been given by B. Brannon.¹

No superheterodyne

The techniques used for DSP in radio reception are quite different from the usual superheterodyne methods used in analogue radio receivers. A DSP receiver works as follows. The signal is digitised after being received on the aerial and will contain all signals in the

frequency range. This digitised signal is then down converted to zero frequency – i.e. base band.

The process so far selects a particular signal at some frequency, which is now at zero frequency but still in the form of the original transmitted signal. A digital signal processor now applies a mathematical algorithm to transform the signal into audio, but still in a digitised form. This digital audio signal is converted to audio sound by a digital-to-analogue converter.

Receiver outline

First we'll describe the general arrangement of the receiver, then the

specific stages in more detail.

The radio signal enters the system via the aerial and is amplified by an RF amplifier with a band-pass filter. This amplifier includes an automatic gain control, or AGC, so that the output is about a volt, this being the optimal voltage for the following stage.

Normally of course with a superheterodyne arrangement, AGC is derived from the audio or IF stages, not the RF stage.

This 1V signal now enters a 10-bit analogue-to-digital converter. This converter samples the analogue signal but at a frequency less than the Nyquist frequency – a technique discussed in



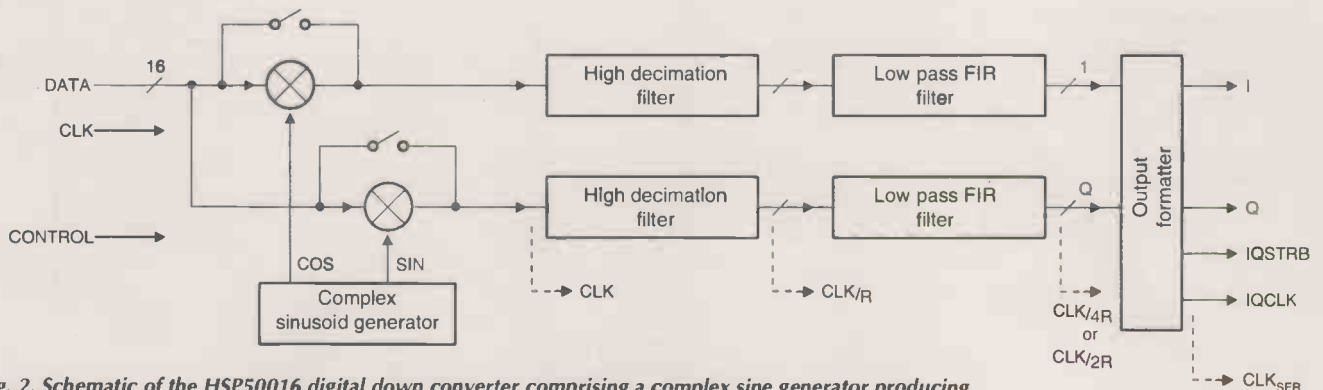



Fig. 2. Schematic of the HSP50016 digital down converter comprising a complex sine generator producing two mixing signals, 90° out of phase. It is fully programmable, but rather complicated.

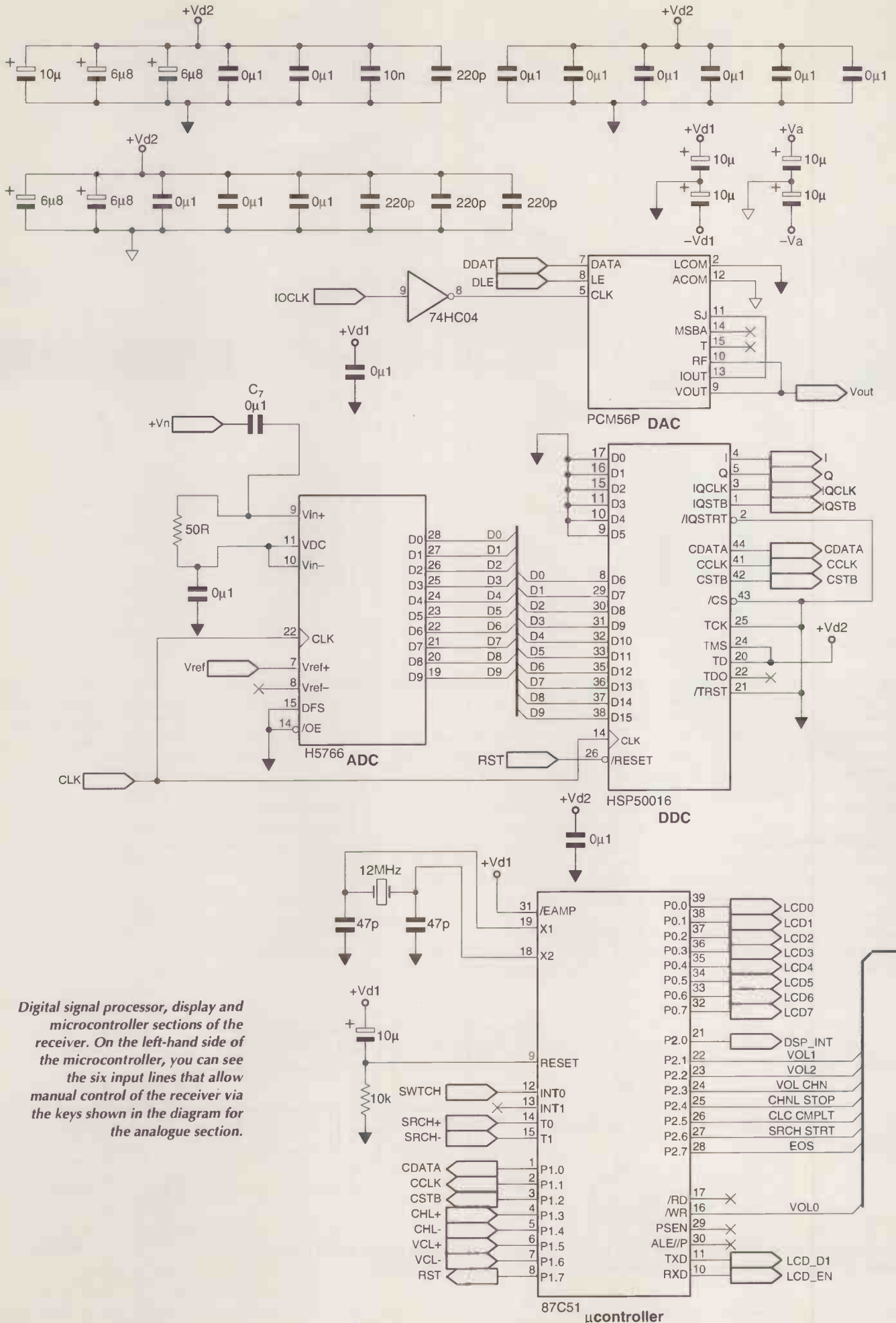

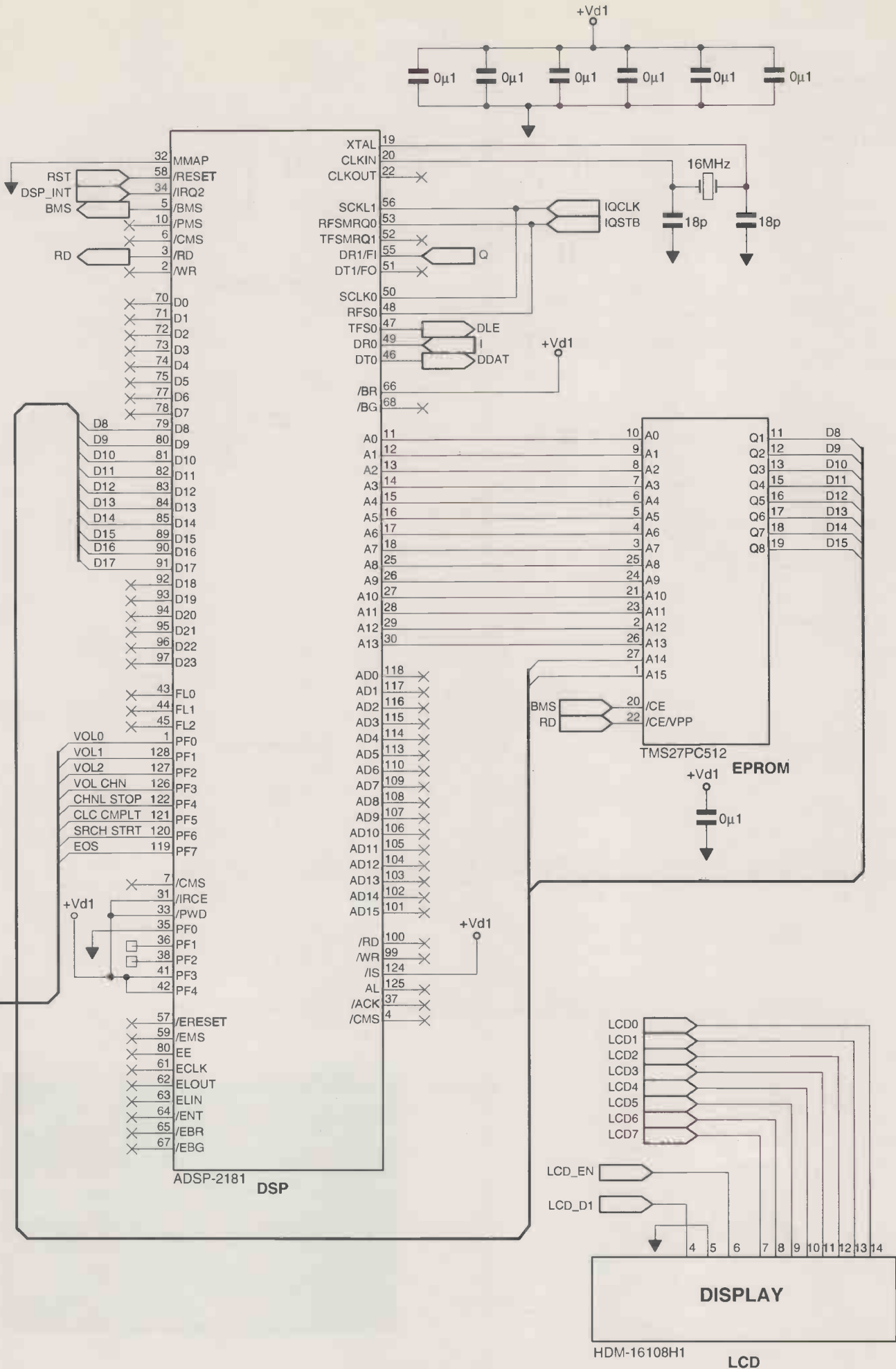Digital signal processor, display and microcontroller sections of the receiver. On the left-hand side of the microcontroller, you can see the six input lines that allow manual control of the receiver via the keys shown in the diagram for the analogue section.



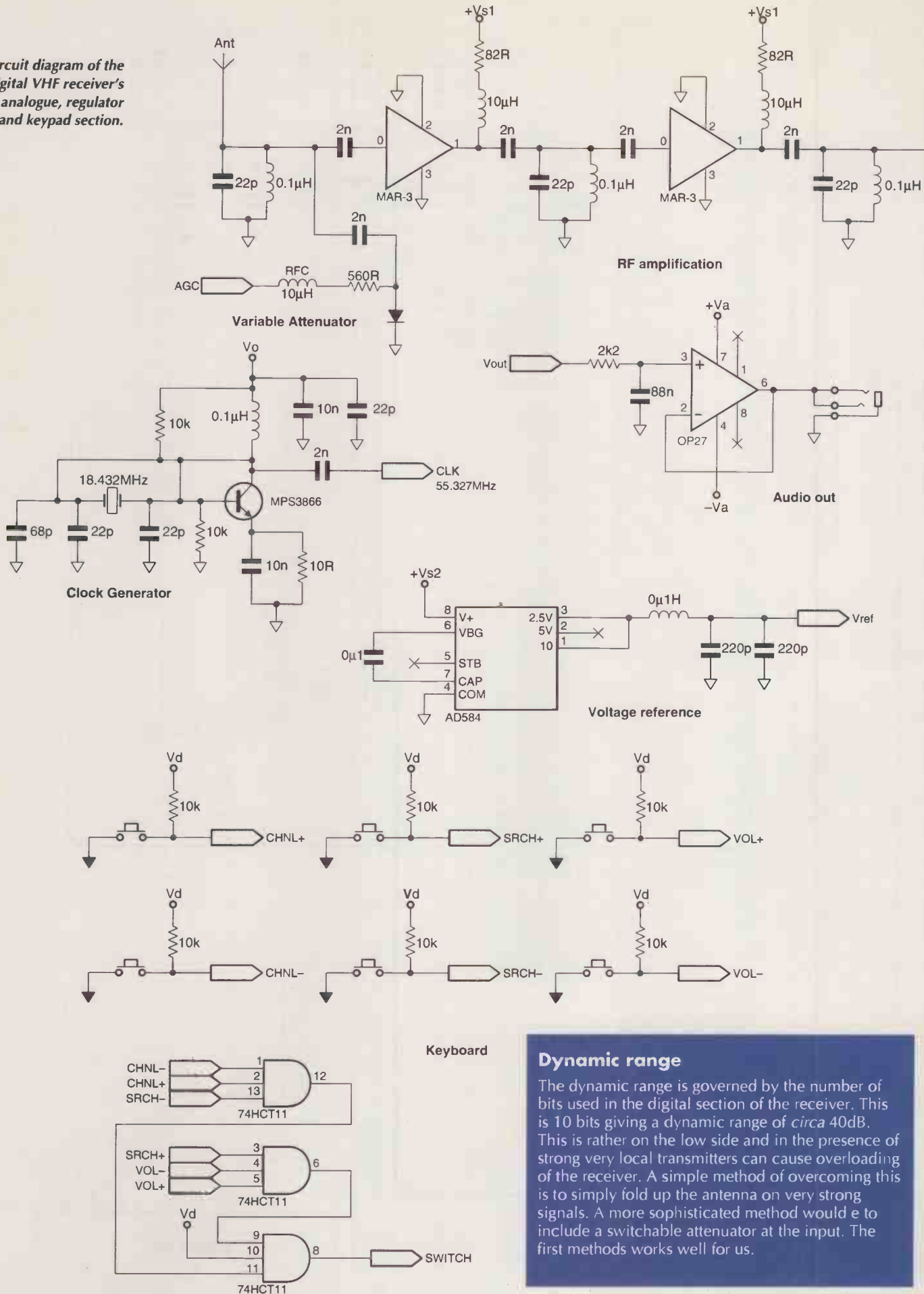Circuit diagram of the digital VHF receiver's analogue, regulator and keypad section.












Dynamic range

The dynamic range is governed by the number of bits used in the digital section of the receiver. This is 10 bits giving a dynamic range of *circa* 40dB. This is rather on the low side and in the presence of strong very local transmitters can cause overloading of the receiver. A simple method of overcoming this is to simply fold up the antenna on very strong signals. A more sophisticated method would be to include a switchable attenuator at the input. The first method works well for us.


Software availability

If you want the object code in electronic form, e-mail jackie.lowe@rbi.co.uk and it will be forwarded to you as text embedded in an e-mail. It will not be sent as an attachment to avoid distributing viruses. If you want the object code on disk, again free of charge, send us a PC formatted 3.5in floppy with a protective self-addressed envelope and enough stamps to allow us to return the disk to you. Post it to the Quadrant House address below

For those of you wanting to exploit the design further, the source code is available on disk, or as an e-mail attachment, for £25 fully inclusive. E-mail the above address with your credit card number, expiry date and card-holder address or fax 0181 652 8555 with the details. Alternatively, send your order to Receiver software, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

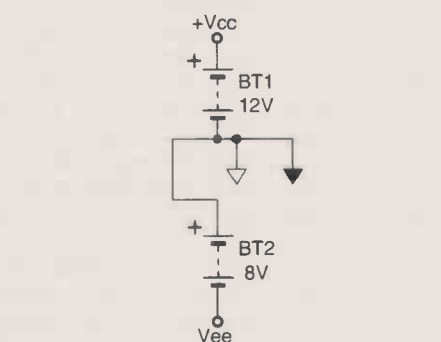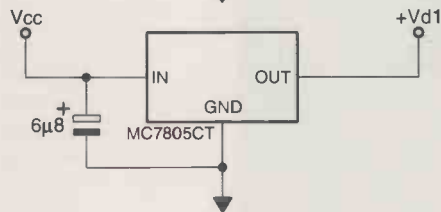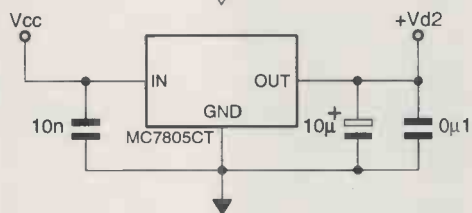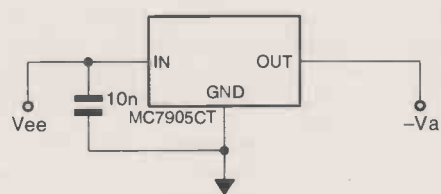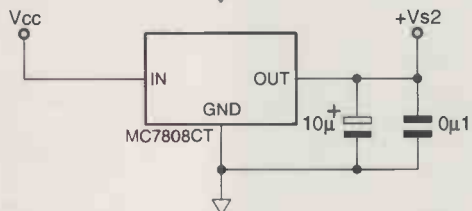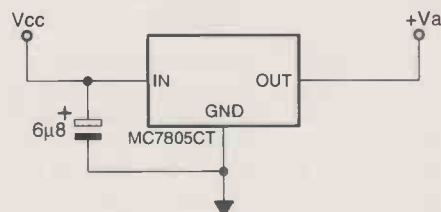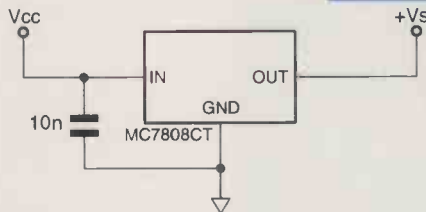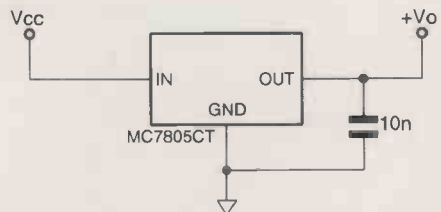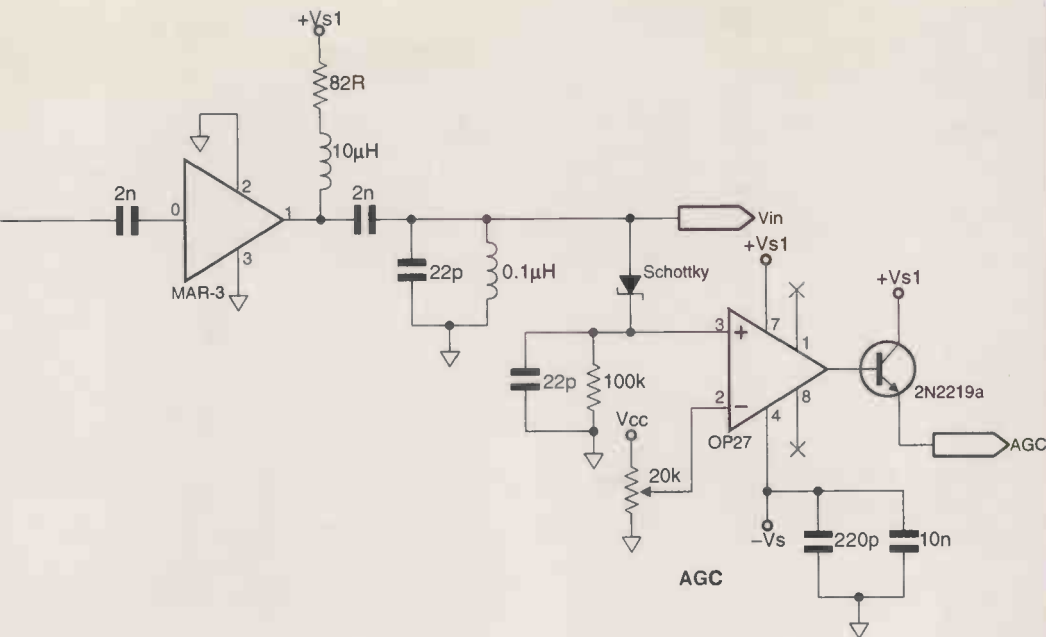

Voltage supply

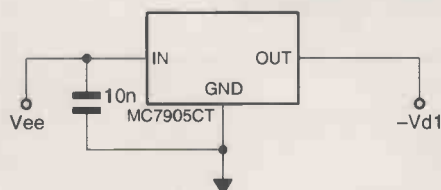

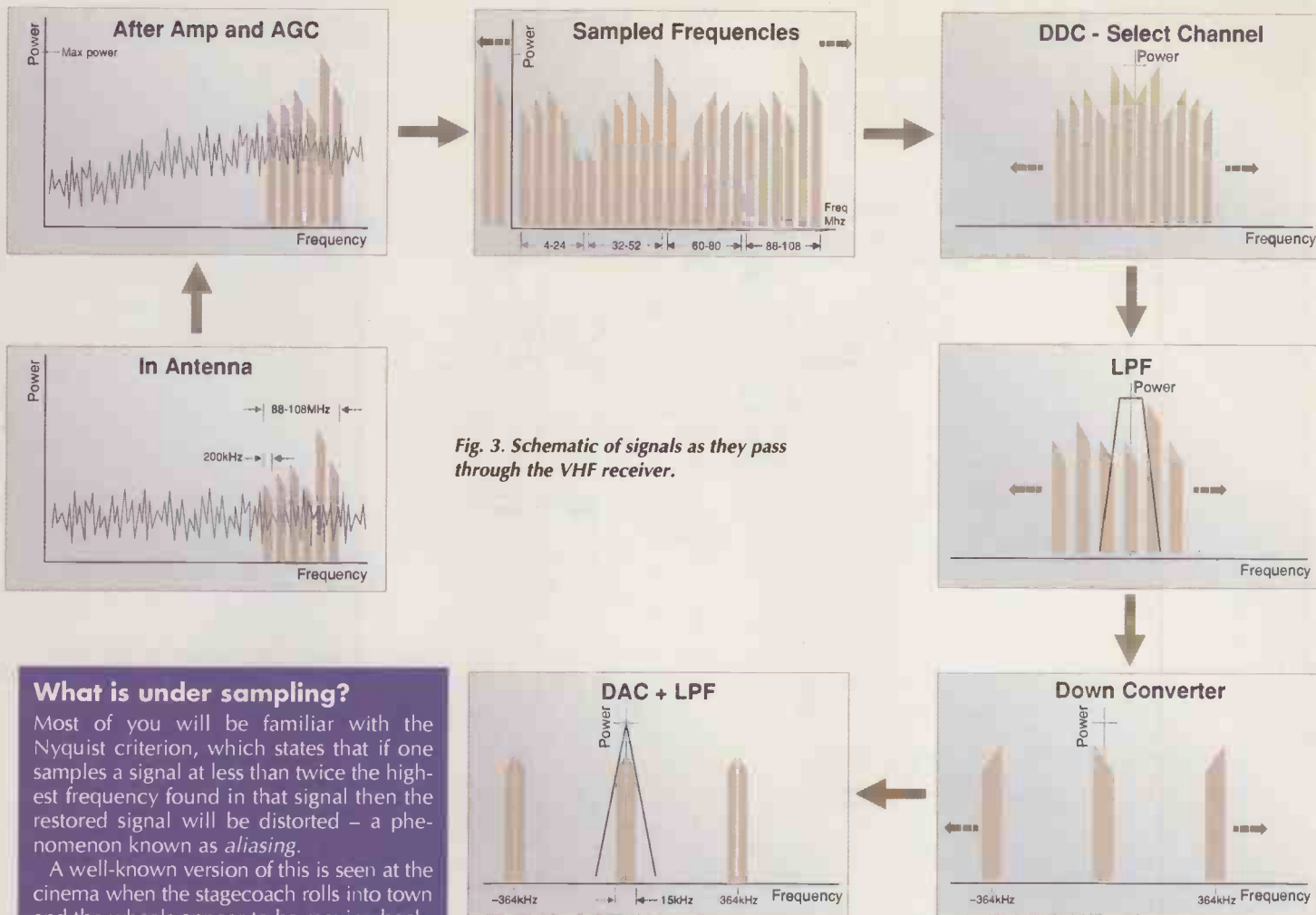


Fig. 3. Schematic of signals as they pass through the VHF receiver.

What is under sampling?

Most of you will be familiar with the Nyquist criterion, which states that if one samples a signal at less than twice the highest frequency found in that signal then the restored signal will be distorted – a phenomenon known as *aliasing*.

A well-known version of this is seen at the cinema when the stagecoach rolls into town and the wheels appear to be moving backwards. This occurs because each film piece is shown at 24 times a second. When the spokes are rotating at more than 12 times a second, the wheel appears to be moving backwards.

The stroboscope works on the same principle by flashing a powerful light at a frequency just slightly lower or higher than that of some repetitive motion. This makes the motion appear to move very slowly backwards or forwards or be stationary.

However, where you have a band-pass limited signal – in our case we are looking at signals in a 20MHz range from 88 to 108MHz – then it can be shown that you only need to sample at very slightly more than twice this bandwidth. This means that you sample at 40MHz, rather than 217MHz, without distorting the reconstructed signal. This technique is known as under sampling.

the box entitled 'What is under-sampling'.

Containing digitised components lying within a 20MHz bandwidth, the sampled signal is down converted using a special digital IC called a digital down converter, or DDC. This device converts the signal in the frequencies between 88 and 108MHz down to DC.

Note that this is not a simple down conversion as used for instance in the synchrodyne receiver as described recently in *Electronics World*.² Instead, in this IC there is a complex process in which the incoming digital signal is mixed with a local oscillator which has both sine and cosine components.

After some processing, the mixed signal becomes an output which is a digitised FM signal at DC. This is then passed through a low-pass filter to minimise the bandwidth.

Now, the FM signal has to be demodulated using a digital signal processor to reform the original signal in a digitised form. This signal is then passed through a 16-bit digital-to-analogue converter to produce an analogue audio signal, which is passed through a low-pass filter to the speaker.

Control of the receiver is by an on/off switch and a simple six-key touch pad. There are up and down buttons for volume. In addition, a frequency up/down button moves up one FM channel or down one FM channel. There is also a button that searches up, and one that searches down. When a signal is encountered the search then stops.

The whole process is controlled by a microcontroller, which also functions as a user-interface. This microcon-

troller is responsible for getting the desired radio frequency by sending the mixing frequency to the DDC and outputting the frequency to an LCD display. It also searches for active channels and enables volume control.

The controller sends the volume control data to the signal processor, which is responsible for the output amplitude. Other than that, a program stored in the EPROM controls the signal processor.

Elements of the receiver

Figure 1 shows the various stages of this receiver in a pictorial form. The first stage is the antenna, a conventional ribbon dipole VHF aerial, which often comes with a music centre but can be bought from any radio shop.

The following RF stage is conventional. It consists of three *MAR3* monolithic broad-band amplifiers and four band-pass filters to give good selectivity.

Each filter has 3dB points at 80 and 145MHz. While consistency might demand that we use only digital filters, this option provides us with the simplest and cheapest solution to get the correct selectivity and gain.

Automatic gain control is derived from the output of this stage via the Schottky diode, the *OP27* operational amplifier and the *2N2219A* transistor.

The derived voltage is fed back to the first *MAR3* in the chain to maintain the output at around 1V peak to peak. The RF chokes are used as high pass filters to remove higher frequencies and maintain stability in the amplifier chain.

The RF signal is next fed to the a-to-d converter for digitisation. The converter is a Harris *HI5766* with a 250MHz full-power input bandwidth and a maximum 60MS/s sampling rate. The sampling frequency of 55.296MHz is obtained as the third harmonic (second overtone) signal from an 18.432MHz crystal.

Next, the digitised signal is fed to the DDC. This is a Harris *HSP50016*, made to be compatible with the a-to-d converter, having a maximum 75MS/s input data rate.

The DDC is fully programmable and is rather complicated. It consists of a complex sine generator to produce two mixing signals, 90° out of phase.

When two signals are mixed together in a non-linear device, i.e. mixer, the sum and difference of the two frequencies are obtained. Thus, one of the results of mixing two signals of the same frequency is an output riding on DC plus a signal at double the original frequency.

Frequency-modulated signals are rather complex. One cannot simply down convert by mixing with a frequency the same as the carrier, as with AM or SSB signals. Instead in-phase (I) and quadrature (Q) signals have to be produced and recombined to reform the FM, as is done in this device. The block diagram taken from the manufacturers data sheet is shown in Fig. 2.

To prevent the doubled frequency produced in the mixing process breaking through, a low-pass filter has to be added. This is accomplished with a decimation filter followed by a fixed finite-impulse-response filter.

The decimation filter is not quite as lethal as it sounds. It passes every *N*th pulse, not every tenth pulse, as its name implies. Its effect is to divide the clock frequency by *N* and to reduce the bandwidth by this ratio.

Output from the DDC is a digitised FM signal at DC. The signal processor performs the mathematical operation on this signal to convert it to a digitised audio signal. The signal processor is an *ADSP-2181* from Analog Devices. It is a microprocessor optimised to carry out all kinds of arithmetical functions.


This signal processor is the heart of this receiver and it is only with the introduction of such devices that a digital receiver becomes possible. These devices are of course fully programmable. The software can be altered to operate on any kind of signal

Object code for the microcontroller.

```
:060000002002B0200CEFD
:01000B0032C2
:0100130032BA
:01001B0032B2
:0100230032AA
:10002B00C29775401FD540FDD29775A805758805F9
:10003B007581607520041202EA12007812025612C2
:10004B0001D712022BD2AF80FED291D292C291C2B3
:10005B00927830754005E60875410833D29192903D
:10006B00C291D541F6D540EED291C29122C2927582
:10007B00507B7551E77552EC7558AC755988755AAC
:10008B00A2755B177544009000B075420675430569
:10009B007830E54493F6080544D543F61154D54220
:1000AB00EC753A472238000000015000000007048
:1000BB0000000009000000069B002DA0B01D01DB7
:1000CB00524003C0D0C0E07545FF309518309622E2
:1000DB0030934F30943C30B40630B50602013D02EC
:1000EB0001A202016C7407B5200302013D05200239
:1000FB000106E520603C1520020106D2A3A2029264
:10010B00A2A20192A1A20092B6D2A0C2A0D2A0023A
:10011B00013D74C9B53A06753A0102013A053A0236
:10012B00013A7401B53A06753AC902013A153A1209
:10013B0002561201D712022B8545407541FF7542BD
:10014B0001D542FDD541F7D540F175454030959528
:10015B0030969F3093CC3094B9758805D0E0D0D0D1
:10016B0032C2A3C2A7D2A0C2A0D2A000000C2A6D6
:10017B00D2A630A5FD20A41B74CAB53A0B753A0064
:10018B00D2A7C2A6D2A680D9053A120256C2A6D2CF
:10019B00A680DF153A8098C2A3C2A7D2A0C2A0D274
:1001AB00A0000000C2A6D2A630A5FD20A41AE53AF5
:1001BB00700B753ACAD2A7C2A6D2A680DA153A122C
:1001CB000256C2A6D2A680E0053A213AC374C9955D
:1001DB003A75F00A8485F03B245875F00A8485F053
:1001EB003C75F00A8485F03DF53E12032DD2B1E546
:1001FB003E6005243002020574201202FCE53D240A
:10020B00301202FCE53C24301202FC742E1202FC6C
:10021B00E53B24301202FCC2B190034512031322BA
:10022B00120332900351120313D2B1AB200B743D66
:10023B001202FCDBF97408C39520FB74201202FC3C
:10024B00DBF9C2B190035612031322E53AC3F553FF
:10025B008550F0A4F54685F047E5538551F0A4F59C
:10026B004885F049E5538552F0A4F54A85F04BC318
:10027B00854657E5472548F556E549354AF555E492
:10028B00354BF554C3E5572558F557E5563559F514
:10029B0056E555355AF555E554355BF554D291D2A3
:1002AB0092C291C292743075410433D2919290C232
:1002BB0091D541F67854754004E60875410833D260
:1002CB00919290C291D541F6D540EE7410754104D0
:1002DB0033D2919290C291D541F6D291C29122C262
:1002EB00B174381202FC740E1202FC74011202FC7F
:1002FB0022F580D2B012033CC2B012033C22D2B121
:10030B0051FCC2B112033C22D2B1E4FB93B4000303
:10031B00C2B122C083C08251FCD082D083EB048057
:10032B00EA22748051FC2274C051FC22740151FCEE
:10033B00227F017E10DEFEDFFA224D487A20464DE9
:0F034B002020202000564F4C20002020200092
:00000001FF
```


Four leading researchers in the field of low-voltage, low-power analogue ICs explain how new topologies are being used to overcome the limitations of working with low supply voltages and small currents, to help you get the best from these new building blocks.

Low voltage design II

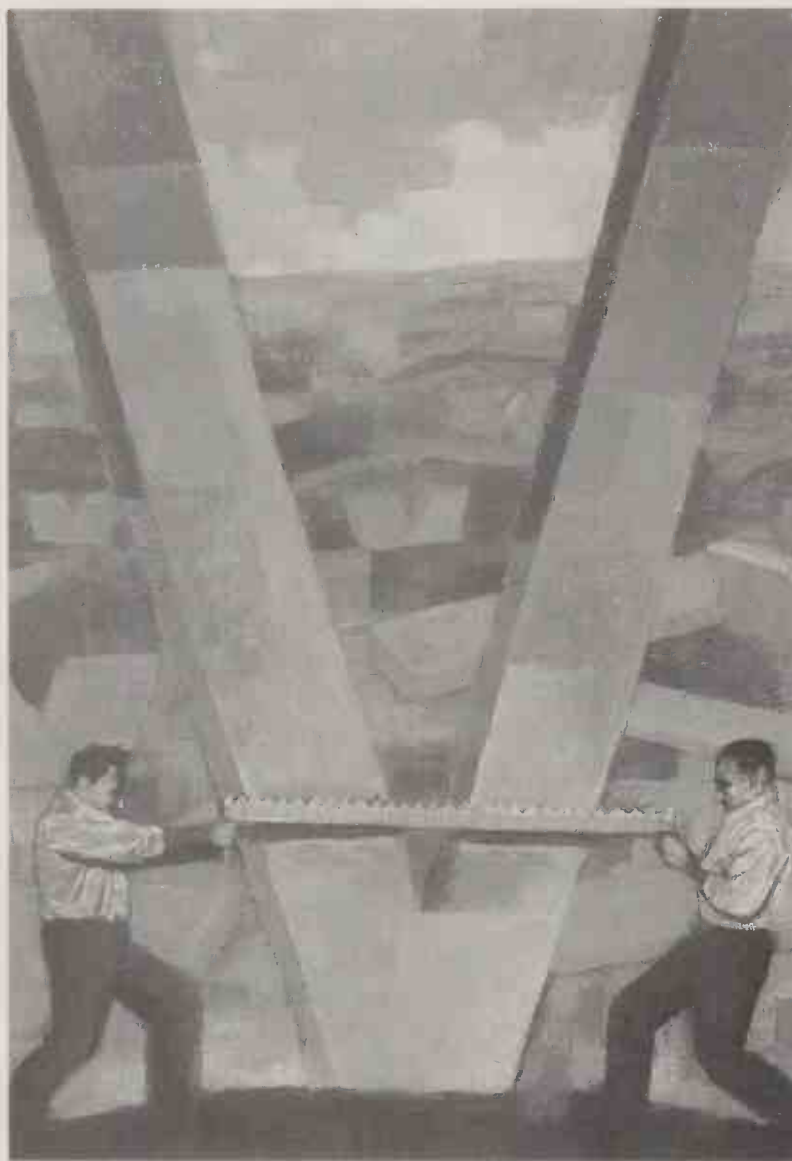

The design of CMOS low-voltage op-amps is an important topic in low-voltage, low-power research. A primary aspect of this research is that amplifiers operating under these conditions have inherent limitations placed on their dynamic range and bandwidth.¹

Dynamic range is limited by supply voltage and resistor noise. To achieve best results, both input and output stages have to be carefully designed.

In this article, input configurations compatible with low-power, low-voltage operation are presented. These inputs are capable of handling rail-to-rail signal swings. Low-voltage output stages also capable of handling rail-to-rail signal swings are the topic of a subsequent article. Their fundamental characteristics are: for the input stage; volt-

age efficiency and rail-to-rail swing; for the output stage; voltage and current efficiency. An output stage operating in class-AB is needed to minimise quiescent current.

Available bandwidth depends on how the frequency compensation is implemented. It needs an optimised constant- g_m input stage. In particular, the multipath nested

The authors

Giuseppe Ferri, Università di L'Aquila, L'Aquila, Italy.
Pierpaolo De Laurentiis, Università di L'Aquila, L'Aquila, Italy.
Arnaldo D'Amico, Università di Tor Vergata, Roma, Italy.
Giovanni Stochino, Ericsson Telecomunicazioni SpA, Roma, Italy.

Fig. 1.
Conventional differential pMOS input stage.

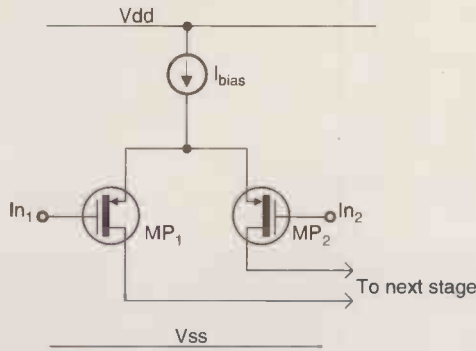


Fig. 2. Rail-to-rail input stage, for applications where both high and low common-mode inputs need to be handled.

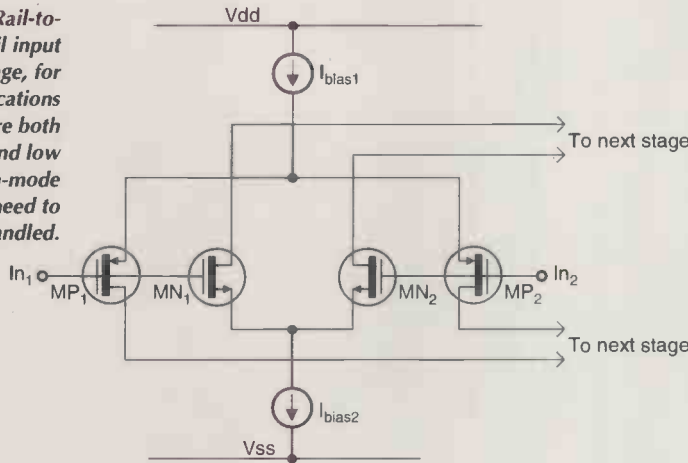


Fig. 3. Total input transconductance versus input common-mode voltage.


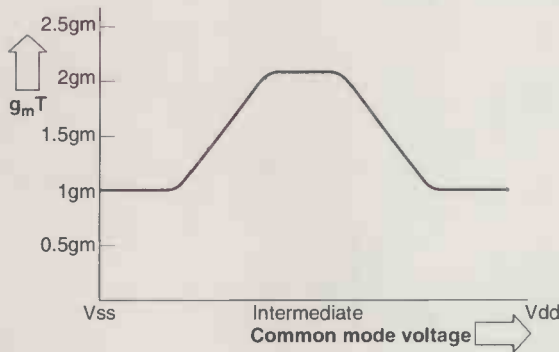


Fig. 4. CMOS rail-to-rail input stage with constant gm using a 'one-times' current mirror.

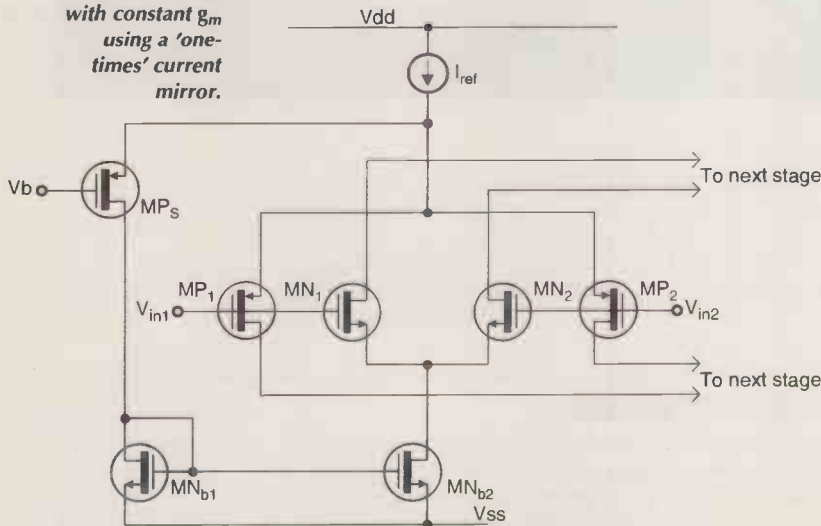

Miller compensation configuration combines a high bandwidth with a high gain.

Traditional op-amps are typically single ended, but fully differential topologies can also be useful. In this case, common-mode feedback is needed to control the output common-mode level.²

Typical low-voltage op-amps target specifications are set out in Table 1.

New architectures for low voltage operation

Realising efficient CMOS low-voltage stages implies the design of new analogue circuit architectures. To make best use of the reduced supply voltage, each circuit has to be able to handle signals that swing from rail to rail at its outputs and inputs.

To maximise dynamic range, the signal voltages have to be as large as possible. Since the signal voltages can extend from rail to rail, the input and output stages of analogue systems – especially operational amplifiers – must be able to handle these signals correctly.

In the CMOS low-voltage field, it is possible to make a rough distinction based on the number of stacked gate-source voltages and saturation voltages. The term 'low-voltage' is consequently used for circuits capable of working at a supply voltage of two gate-source voltages and two saturation voltages; on the other hand, circuits that need only one gate-source voltage and a saturation voltage are called 'very low voltage' circuits.

Rail-to-rail input stages

The conventional differential pMOS input stage is shown in Fig. 1. It is appropriate where low common-mode input voltages are considered. For high input levels, a complementary input stage with nMOS transistors has to be used.

In applications where both low and high input values of common mode are needed, a rail to rail input stage is needed, Fig. 2. It comprises both a p-channel input pair and an n-channel input pair.

The n-channel pair allows the common-mode input voltages to reach the positive supply rail and the p-channel pair the negative rail. In this manner, the common-mode input range can extend from negative to positive supply rails.

The common-mode input range of Fig. 2 can be analysed considering the following three input signals:

- low common-mode input voltages (only the p-channel pair operates);
- intermediate common-mode input voltages (both the input pair operates);
- high common-mode input voltages (only the n-channel input pair operates).

A drawback of this input stage is the fact that its transconductance, gm, changes by a factor of two

Minimum supply voltage	1.8V
Quiescent current	250mA
DC gain	≥60dB
GBW	≥1MHz
Maximum output current	1mA
Input and output voltage range	Full (rail-to-rail)

within the common-mode input range, as in Fig. 3. Here it is assumed that the g_m of the p-channel and the g_m of the n-channel input pairs are equal. This can easily be achieved by selecting the right W/L ratio of the input transistors.

Owing to the fact that the bandwidth of an operational amplifier is proportional to the g_m of its input stage,

varying g_m doesn't allow optimal frequency compensation. Moreover, it causes undesired additional distortion.

In order to overcome these drawbacks, the transconductance has to be kept constant. The next section describes how to realise such input stages.

Constant- g_m rail-to-rail input stages. The total transcon-

A new universal input stage for low-voltage op-amps³

Several methods for achieving a constant- g_m with complementary, rail-to-rail input stages are given in the literature. All of these are based on an opportune control of the DC tail currents of the differential input stages.

The proposed examples include bipolar and CMOS input pairs operating in weak inversion. To achieve this, the sum of tail currents flowing through both the n and p type input pairs has to be kept constant.

Another set of examples is represented by CMOS input pairs operating in strong inversion. Here, constant transconductance is achieved by keeping the sum of the square roots of the tail currents constant.

None of these types of control can be applied universally at the same time to both bipolar and CMOS input stages operating in weak and/or strong inversion. In this section though, we present a novel and universal concept that is independent of input transistor types and their operating regions.

The new concept is based on the processing of signal currents rather than handling DC tail currents, Fig. A. The operating principle is based on the well known equation of the total instantaneous output current of a simple differential pair,

$$I_{o,lor2} = \frac{I_{tail}}{2} \pm g_m \frac{V_{id}}{2} \tag{P1}$$

Here, V_{id} is the small signal differential input voltage, and g_m is the transconductance depending on device type and its biasing.

With the notation and current direction shown in Fig. B, considering equation (P1) and assuming that $V_{in+} > V_{in-}$, the drain current pairs I_{n1} , I_{n2} and I_{p1} , I_{p2} of the complementary input stage can be expressed as follows,

$$I_{n1} = \frac{I_n}{2} + g_{m,n} \frac{V_{id}}{2} \tag{P2}$$

$$I_{n2} = \frac{I_n}{2} - g_{m,n} \frac{V_{id}}{2} \tag{P3}$$

$$I_{p1} = \frac{I_p}{2} + g_{m,p} \frac{V_{id}}{2} \tag{P4}$$

$$I_{p2} = \frac{I_p}{2} - g_{m,p} \frac{V_{id}}{2} \tag{P5}$$

With respect to the common-mode input voltage, three operating regions exist. In region I, when V_{CM} is close to negative supply rail,

$$I_n < I_p (= I_b), \quad g_{mn} < g_{mp} (= g_{m(max)}) \tag{P6}$$


In region II, when V_{CM} is at middle rail,

$$I_n = I_p = I_b, \quad g_{mn} = g_{mp} = g_{m(max)} \tag{P7}$$

And in Region III, when V_{CM} is close to the positive rail,

$$I_n (= I_b) > I_p, \quad g_{mn} (= g_{m(max)}) > g_{mp} \tag{P8}$$

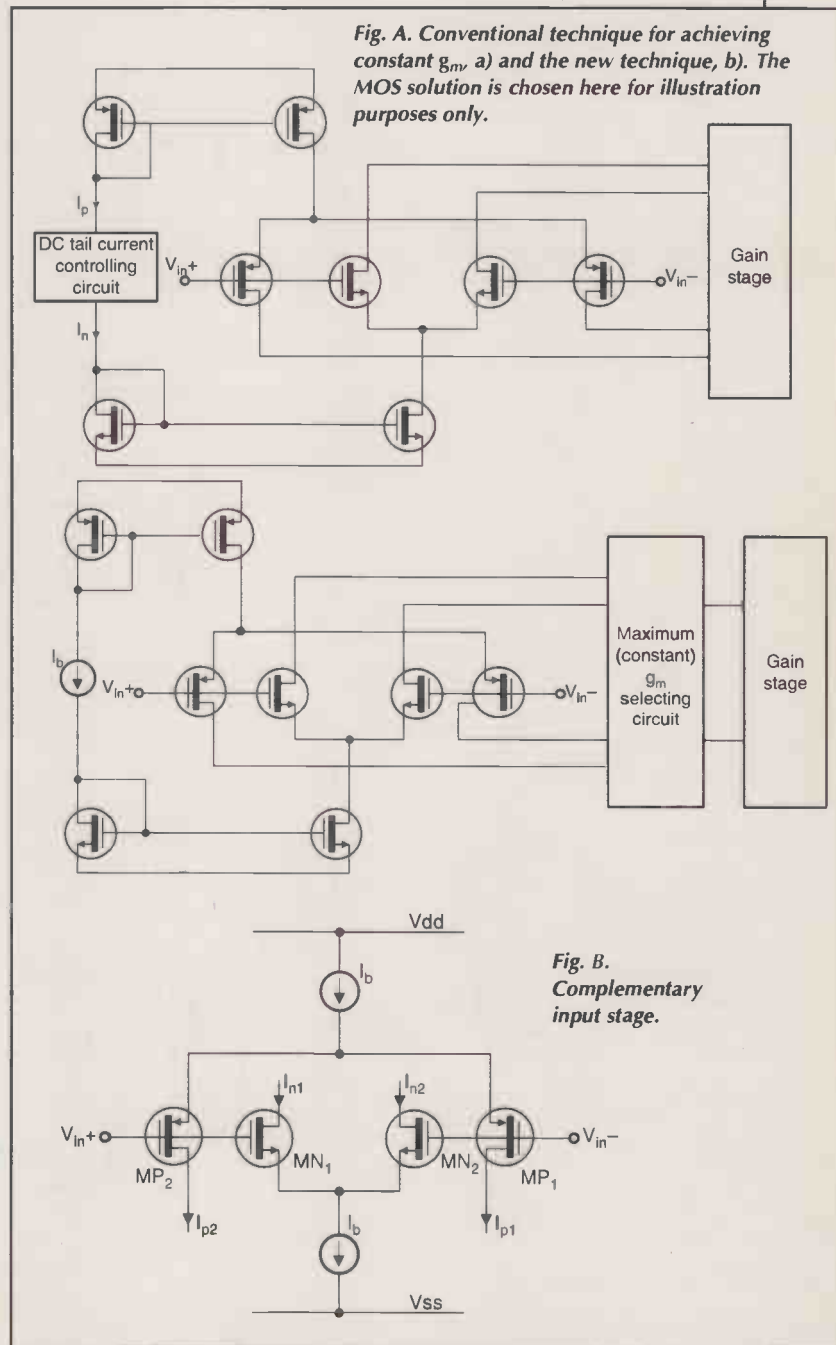Considering equations (P2) to (P5), and under the condition developed for each region in equations (P6) to (P8), the main principle is that only $g_{m(max)}$ is selected and used throughout the entire input common-mode voltage range. The result is a rail-to-rail constant- g_m input stage.



ductance of the input stage, g_{mT} , is the sum of the transconductance of n and p-channel differential stages, respectively g_{mn} and g_{mp} :

$$g_{mT} = g_{m1} + g_{mp} \tag{1}$$

If the input transistors operate in weak inversion, the total transconductance is given by,

$$g_{mT} = \frac{1}{nkT/q} (I_n + I_p) \tag{2}$$

where I_n and I_p are the biasing currents, respectively of n and p pairs.

If the input stage is biased in strong inversion, the total g_m is given by,

$$g_{mT} = \sqrt{2\beta_n I_n} + \sqrt{2\beta_p I_p} \tag{3}$$

or, from a voltage point of view,

$$g_{mT} = 2\beta_n (V_{gsn} - V_{Tn}) + 2\beta_p (V_{srp} - V_{Tp}) \tag{4}$$

From equation (2), it can be concluded that the g_{mT} of a rail-to-rail input stage operating in weak inversion can be controlled by the tail currents of the input transistors. In strong inversion, according to expressions (3) and (4), g_{mT} can be regulated by either the input tail currents, or the gate-source voltages or even the transistors aspect ratios.

Input stages with current-based g_m control

Several methods exist to make the g_{mT} constant by regulating the tail currents of the complementary input pairs. Constant g_m input stages operating in weak and strong inversion are now described.

Controlling g_m by one-time current mirror. In weak inversion, the transconductance of a MOS transistor is

Fig. 5. CMOS rail-to-rail input stage with constant g_m using 'three-times' current mirrors.


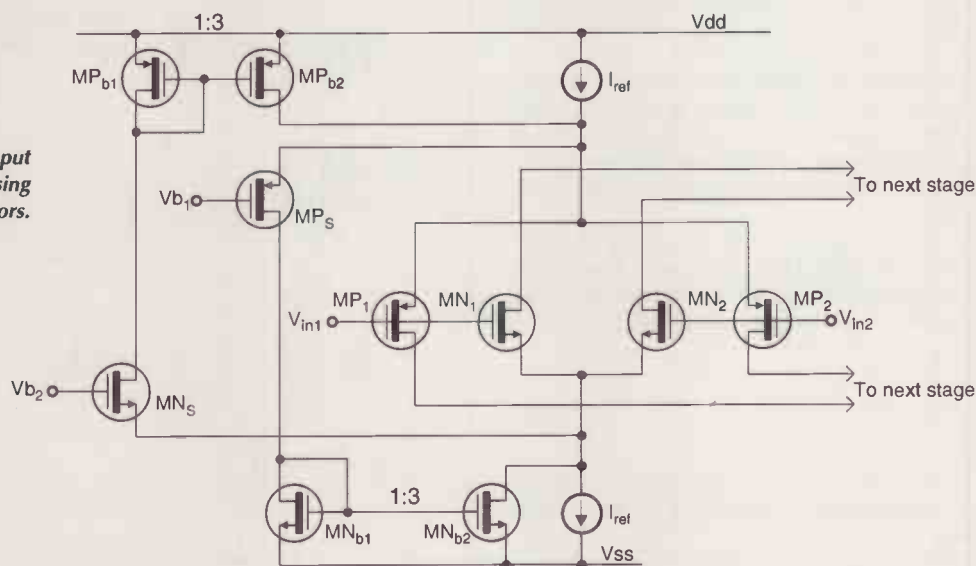


Fig. 6. In this CMOS rail-to-rail input stage g_m is held constant using a square root circuit.

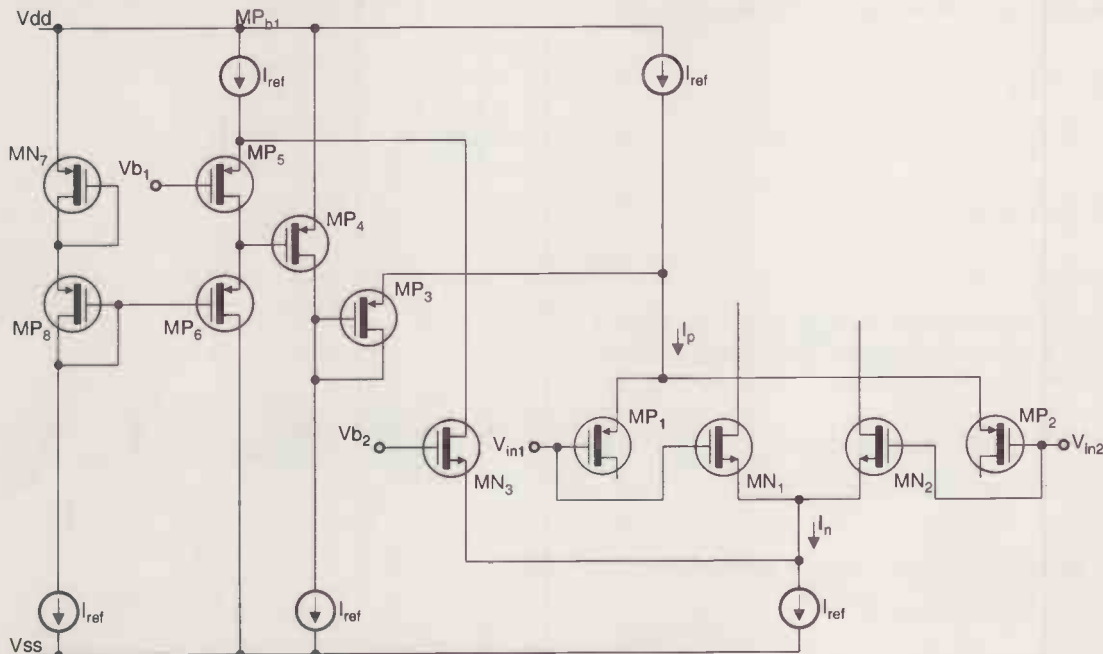

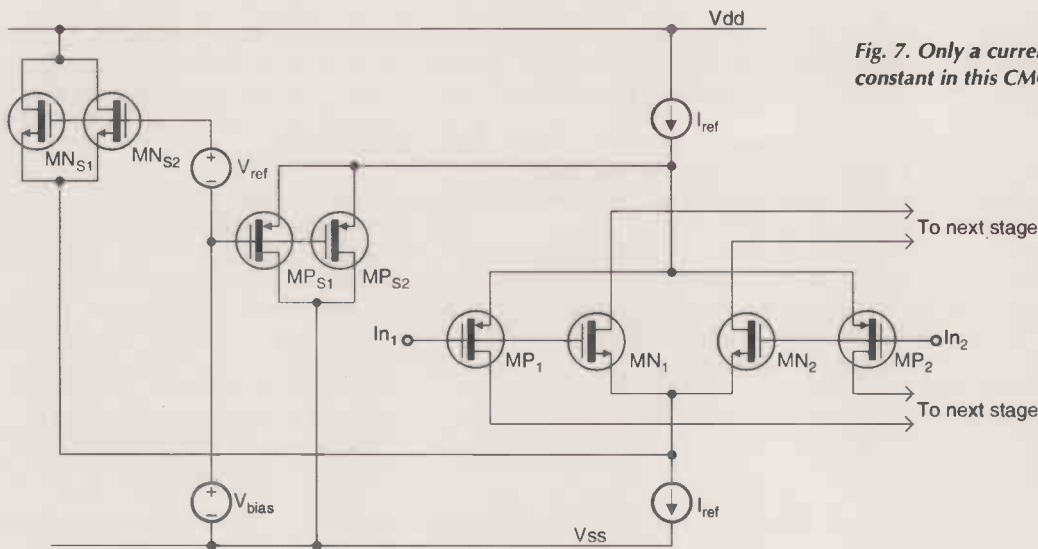


Fig. 7. Only a current switch is used to keep g_m constant in this CMOS rail-to-rail input stage.

directly proportional to its drain current. As a result, the g_{mT} term can be held to a constant value simply making sure that the sum of I_n and I_p is kept constant.

In Fig. 4, the sum of tail currents is constricted to obey the following law, consistently with (4),

$$I_n + I_p = I_{ref} \quad (5)$$

If the input stage of Fig. 4 is biased in strong inversion, the dependence of the transconductance on the tail current changes; it follows a square-root law. As a result, the g_{mT} of the complementary input stage can be proved to vary by about 41% over the common-mode input range. Therefore, for input stage transistors operating in strong inversion, a different method to control g_m has to be developed.

Controlling g_m via 'three times' current mirrors. From Fig 3, you can see that if g_m is increased by a factor of two at the lower and the upper part of the common-mode input range, the same g_m is constant with all input signals.

In order to increase the g_m when only one input pair is operating, the tail-current of the actual active input pair has to be increased. Since the g_m of an input pair is proportional to the square root of its tail current, the tail-current of the actual active input pair has to be increased by a factor of four.

This principle can be realised as in Fig. 5, by using 'three-times' current mirrors.

In this manner, the sum of the square roots of the tail currents is held constant. In fact,

$$\sqrt{I_n} + \sqrt{I_p} = 2\sqrt{I_{ref}} \quad (6)$$

This yields in all the three common-mode input ranges, except in the turn over range of the current switch, where the g_m variation is only of about 15.5%.

Controlling g_m control by square-root current control. Controlling g_m with 'three times' current mirrors only roughly complies with equation (6). To obtain a more precise implementation of this control, I_n and I_p have to vary gradually with the input common-mode voltage.

In Fig. 6 is an input stage where the g_m control is implemented by means of a square-root circuit. The heart of this circuit is the translinear loop comprising transistors $MP_{4,6,7,8}$. Applying Kirchoff's voltage law to the

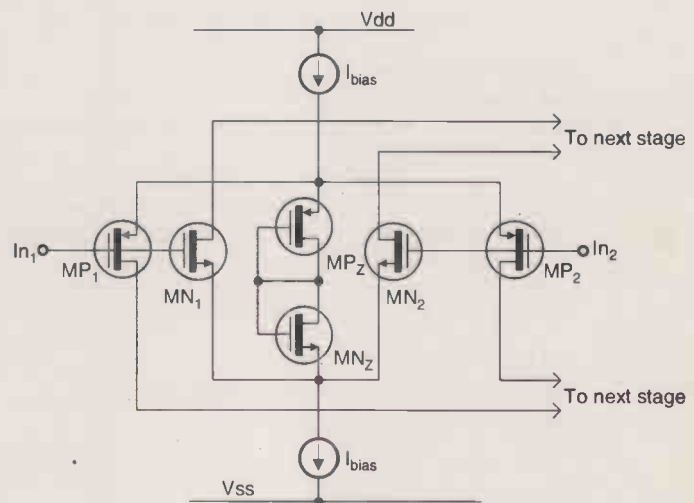


Fig. 8. Another way to keep g_m constant in a rail-to-rail input is to use a zener diode.

translinear loop, it can be easily proved that,

$$\sqrt{I_{MP6}} + \sqrt{I_{MP4}} = 2\sqrt{I_{MP7,8}} \quad (7)$$

where the aforementioned transistors are all matched.

In order to obtain a constant transconductance, the translinear loop is biased so that equation (7) matches expression (6). The diode-connected transistors are biased with a constant current of I_b , fixed at $I_{ref}/4$. Moreover, the currents through MP_6 and MP_7 are made equal to the tail current in the n- and p-channel input pairs, respectively.

As a result,

$$\sqrt{I_n} + \sqrt{I_p} = 2\sqrt{I_b}$$

Controlling g_m using current switch only. In the circuit of Fig. 7, g_m control is implemented by four current switches. The current switches compare the common-mode input voltage with their respective gate voltage and subtract current to differential pairs in an opportune manner.

For low common-mode voltages, MP_{s1} and MP_{s2} , and consequently the n-channel input pair, are off. In this case,

all of I_{ref} is flowing through the p-channel pair. For high common-mode voltages, MN_{s1} and MN_{s2} and the p-channel input pair are off, so I_{ref} is flowing through the n-channel pair.

For common-voltages between the $V_{ss}+V_{bias}$ and $V_{ss}+V_{bias}+V_{ref}$, the current switches take away a portion of the current of both tail current sources, controlling the g_m over the whole common-mode input range.

If the input stage of Fig. 7 is biased in weak inversion, a constant- g_m can be obtained by connecting the gates of both pairs of current switches to the same voltage V_{bias} , provided that the input and switch pairs are equal. In Fig. 7 it is sufficient to make V_{ref} equal to 0.

This last circuit, with $V_{ref}=0$, can be improved for strong inversion operation by sizing the input transistors and the current switches as follows,

$$\left(\frac{W}{L}\right)_{MNs} = \left(\frac{W}{L}\right)_{MPs} = 3 \left(\frac{W}{L}\right)_{MNI} = \left(\frac{W}{L}\right)_{MPI} \quad (8)$$

This allows you to recover the condition (6).

Rail-to-rail input stages with voltage-based g_m control

In the previous sections, examples of input stage with current-based control have been given.

If the input stage is biased in strong inversion, its g_m can also be made constant by manipulating the gate-source voltage. In fact the g_m of a MOS transistor is proportional to its gate-source voltage.

Now, for a constant g_m , the gate-source voltages of the input devices have to obey the following relationship,

$$(V_{sgp} - |V_{tp}|) + (V_{gsn} - V_{tn}) = V_{ref} \quad (9)$$

As a result, in each part of the common-mode input range the following g_m is obtained,

$$g_m = \beta V_{ref} = \sqrt{2\beta I_{ref}} \quad (10)$$

where it is assumed that $\beta_n = \beta_p = \beta$.

The voltage reference can be realised with a zener voltage. A very simple implementation of an electronic zener is shown in Fig. 8.

In this diagram, the zener diode has been realised by means of two stacked diodes, MP_z and MN_z . In order to give a zener voltage according to (9) to the two diodes, the diodes' W/L s are made six times larger than those of the input transistors.

Rail-to-rail input stages with W/L based g_m control. In the previous section, the g_m -control circuits work properly in either weak or strong inversion. This limits the programming range of these types of input stage.

A control method can be realised that works in weak as well as in strong inversion. The basic principle of this method is to double the g_m at the outer parts of the common-mode input range by placing an additional input pair in parallel to the actual active input pair, Fig. 9.

Since this principle does not make use of transistor $I-V$ relationships, it operates not only in weak and strong inversion, but also in moderate inversion.


The panel entitled, 'A new universal input stage for low-voltage op-amps,' shows a further solution for implementing constant- g_m -input stages. ■

The next and final article in this set discusses CMOS output stages. The first article on this topic appeared last month. It introduced low-voltage analogue ICs and discussed bipolar designs in particular. It carried the full list of 19 references.

References

1. R. Hogervorst, J.H. Huijsing, 'Design of low-voltage low-power operational amplifier cells', Kluwer Academic, 1996
2. G. Ferri, W. Sansen, V. Peluso, 'A low voltage fully differential constant- G_m CMOS operational amplifier', *Analogue Integrated Circuits and Signal Processing* Vol. 16 No 1 April 1998, pp. 5-15.
3. C. Hwang, A. Motamed, M. Ismail, 'Universal Constant- G_m Input-Stage Architectures for Low-Voltage Op Amps', *IEEE Transactions on Circuit and Systems - Fundamental Theory and Applications*, Vol. 42, No 11, November 1995, pp. 886-894.

Fig. 9. To increase a rail-to-rail input stage's g_m at the outer limits of the common-mode input range, multiple input pairs can be applied.

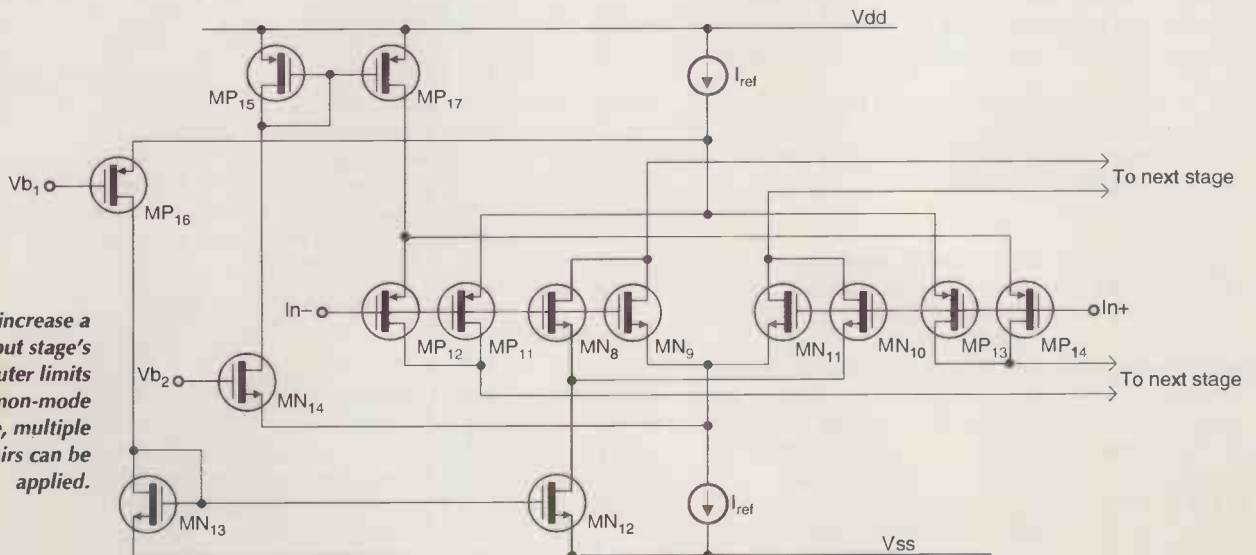

Telnet

Tel: 02476 650702

Hewlett Packard
8642A – high performance R/F synthesiser
 (0-1-1050MHz) £5500
3335A – synthesiser (200Hz-81MHz) £2400

Hewlett Packard
436A power meter and sensor (various) from £750
437B power meter and sensor (various) from £1100

Hewlett Packard
8753A network analyser (3GHz) from £2500
8753B network analyser (3GHz) from £3250
 'S' parameter test sets 85046A and 85047A
 available at £2000 & £3000

Wandel & Goltermann
PFJ-8 – error and fitter test set
 (all options fitted) £9950
PCM 4 – PCM channel measurement set £7500

Marconi
2305 – modulation meter £1250
6310 – programmable sweep generator
 (2 to 20GHz) – new £3250

Hewlett Packard
5342A – microwave frequency counter
 (500MHz-18GHz) ops 1 & 3 £700
5370B – universal time interval counter £1750

OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual channel £150
 Hewlett Packard 54100D - 1GHz Digitizing £1250
 Hewlett Packard 54201A - 300MHz Digitizing £1250
 Hewlett Packard 54512B (300MHz-1G s/s) - 4 channel £POA
 Hewlett Packard 54600A - 100MHz - 2 channel £750
 Hitachi V152/V212/V222/V302B/V302F/V353F/V550B/V650F from £125
 Hitachi VI 100A - 100MHz - 4 channel £900
 Intron 2020 - 20MHz - Dual channel D.S.O. (new) £450
 Iwatsu SS 5710/SS 5702 - £1250
 Klkusul COS 5100 - 100MHz - Dual channel £350
 Lecroy 9450A - 300MHz/400 MS/s D.S.O. 2 channel £2250
 Meguro MSO 1270A - 20MHz - D.S.O. (new) £450
 Philips 3055 - 50MHz - Dual channel £500
 Philips PM 3335 - 50MHz - D.S.O. Dual channel £950
 Philips 3295A - 400MHz - Dual channel £1600
 Philips PM3392 - 200MHz-200Ms/s - 4 channel £1995
 Tektronix 465 - 100MHz - Dual channel £350
 Tektronix 464/466 - 100MHz - (with AN. storage) £350
 Tektronix 475/475A - 200MHz/250MHz - £450
 Tektronix 468 - 100MHz - D.S.O. £650
 Tektronix 2213/2215 - 60MHz - Dual channel £350
 Tektronix 2220 - 60MHz - Dual channel D.S.O. £1250
 Tektronix 2225 - 50MHz - Dual channel £395
 Tektronix 2235 - 100MHz - Dual channel £600
 Tektronix 2221 - 60MHz - Dual channel D.S.O. £1250
 Tektronix 2245A - 100MHz - 4 channel £900
 Tektronix 2440 - 300MHz/500 MS/s D.S.O. £2950
 Tektronix 2445A - 150MHz - 4 channel £1250
 Tektronix 2445 - 150MHz - 4 channel + DMM £1200
 Tektronix TAS 475 - 100MHz - 4 channel £995
 Tektronix 7000 Series (100MHz to 500MHz) from £200
 Tektronix 2211 - 50MHz - 2 channel DSO £950
 Tektronix 7104 - 1GHz Real Time from £2500
 Tektronix 2465A - 350MHz - 4 channel £1995

SPECTRUM ANALYSERS

Ando AC 8211 - 1.7GHz £1500
 Avcom PSA-65A - 2 to 1000MHz £850
 Anritsu MS 2601B 9KHz to 2.2GHz £5000
 Anritsu MS 62B - 50Hz to 1700MHz £1450
 Anritsu MS 610B 10KHz - 2GHz - as new £3500
 Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz £1500
 Hewlett Packard 3562A Dual channel dynamic signal analyser
 64µHz - 100KHz £5500
 Hewlett Packard 3585A - 20Hz to 40MHz £3950
 Hewlett Packard 8505A - 1.3GHz - Network Analyser £1995
 Hewlett Packard 8756A/8757A Scaler Network Analyser from £1000
 Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz) £2750
 Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz) £2250
 Hewlett Packard 8569B (0-01 to 22GHz) £3950
 HP 8754A - Network Analyser 4MHz-1300MHz £1500
 IFR A7550 - 10KHz-1GHz - Portable £1950
 Meguro - MSA 4901 - 30MHz - Spec.Analyser £700
 Meguro - MSA 4912 - 1 MHz - 1GHz Spec.Analyser £995
 Wandel & Goltermann TSA-1 system analyser (100Hz-180MHz) £2,750
 Tektronix 495P Spec analyser prog. - 1.8GHz £3500

Quality second-user test & measurement equipment

NEW PHONE CODE FOR COVENTRY 02476

Radio Communications Test Sets

Marconi 2955 – calibrated £2000
 Marconi 2958/2960 £2250
 Anritsu MS555A2 £1200
 Hewlett Packard 8920A £2000
 Hewlett Packard 8922B (GSM) £6950
 Schlumberger Stabilock 4031 £3995
 Schlumberger Stabilock 4040 £1500
 Racal 6111 (GSM) £1750
 Racal 6115 (GSM) £3995
 Rhode & Schwarz CMS 54 (new) £6250
 Rhode & Schwarz CMTA 94 (GSM) £5950
 IFR 1200S (calibrated) £2995



Fax 02476 650 773

Tektronix 469P - 1KHz to 1.8GHz £3400
 Willtron 6409 - 10-2000MHz R/F Analyser £1750

MISCELLANEOUS

Eaton 2075 – 2ANoise Gain Analyser at £2250
 Farnell AP30250 - Power Supply 30v-250amp £1500
 Fluke 5100A/5100B/5220A/5200A - Calibration Units (various available) from £1000
 Fluke 2625/2635 Data Buckets (various) £5000
 GN ELMI EPR31 - PCM Signalling Recorder £1500
 Hewlett Packard 6033A - Autoranging System PSU (20v-30a) £750
 Hewlett Packard 6632A - System Power Supply (20V-5A) £800
 Hewlett Packard 3784A - Digital Transmission Analyser £5000
 Hewlett Packard 3785A - Filter Generator & Receiver £1250
 Hewlett Packard 8660D - Synth'd Sig. Gen (10 KHz-2600MHz) £3,250
 Hewlett Packard 4192A - LF Impedance Analyser £6750
 Hewlett Packard 16500C - Logic Analyser Mainframe £3250
 Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame from £2000
 Hewlett Packard 6624A – Quad Output Power Supply £2000
 Hewlett Packard 6652A – 20V-25A System PSU £750
 Hewlett Packard 8350B – Sweep Generator Mainframe £2000
 Hewlett Packard 75000 VXI Bus Controllers £POA
 HP 339A Distortion measuring set £1200
 HP 3488A - Switch/Control unit £475
 HP 435A + 435B Power meters from £100
 HP 8656A Synthesised signal generator £850
 HP 8656B Synthesised signal generator £1450
 HP 8657A - Signal generator 100KHz - 1040MHz £1900
 HP 37900D - Signalling test set £3750
 HP 5385A - 1 GHz Frequency counter £650
 HP 8901B - Modulation Analyser £2750
 HP 8903A and E - Distortion Analyser from £1250
 HP 8112A - 50MHz Pulse Generator £2250
 HP 16500A + B - Logic Analyser Mainframes from £1500
 HP E4418A Powermeter with ECP-E18A Power Sensor £2100
 HP 778D Dual-Directional Couplers £650
 HP 6622A - Dual O/P system p.s.u. £1250
 HP 6623A - Triple o/p system p.s.u. £1300
 Keytek MZ-15/EC Minizap ESD Simulator (15kv - hand held) £1750
 Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT) NEW £1750
 Marconi 2610 True RMS Voltmeter £550
 Marconi 6950/6960/6960B Power Meters & Sensors from £400
 Philips 5515 - TN - Colour TV pattern generator £1400
 Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at £795
 Racal 9087 - 1.3GHz Synthesised Signal Generator, low noise £1995
 Racal 1992 - 1.3GHz Frequency Counter £500
 Rhode & Schwarz SMY-01 Signal Generator (9KHz-1040MHz) £2250
 Rhode & Schwarz NRV Power Meter & NRV-Z2 Sensor £1250
 Systron Donner 6030 - 26.5GHz Microwave Freq Counter £1995
 Tektronix 1721 - PAL Vectorscope £1000
 Wandel & Goltermann PRA-1 – Frame Analyser £5250
 Wayne Kerr 3245 – Precision Inductance Analyser £1995
 Willtron 6747A-20 - 10MHz-20GHz - Swept Frequency Synthesiser £4950


817

All equipment is used - with 30 days guarantee and 90 days in some cases
 Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate, Coventry CV3 2SE

Tel: 02476 650 702

Fax: 02476 650 773

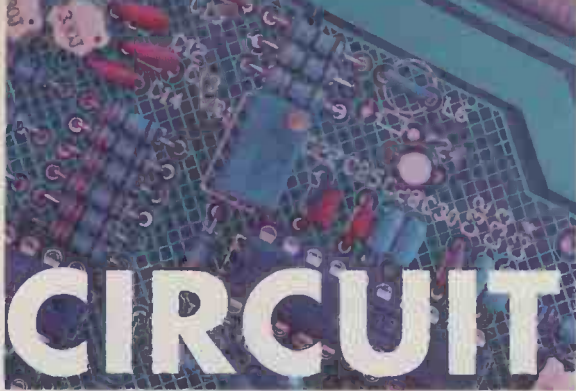

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.


Battery/dynamo bicycle lighting

A combination of battery and dynamo – isolated from the frame – makes sure you have lights when your bike's stationary. You can use the circuit as a battery-backed dynamo system, or as a dynamo-backed

battery system, in which case the batteries would be charged periodically.

*A J Bird
Burntwood
Staffordshire*

D41

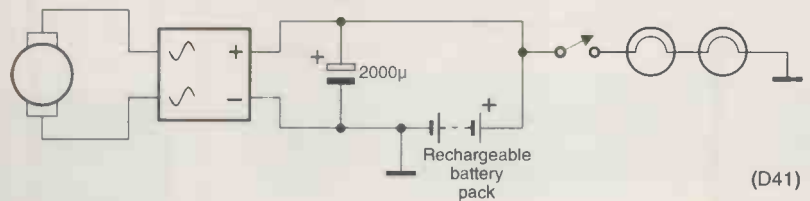

(D41)

Charge the bicycle lighting battery from the dynamo or run from battery alone for easier riding.

Line-powered music while you change 'phones

If you have two or more telephone handsets, this scr-based circuit holds the line while you go to another room to pick up the call, the handset having been replaced, and the caller hears music until you pick up the other handset.


The music comes from those little chips found in greetings cards, which need a 1.2V button cell, provided here by the line voltage via a pair of 1N4001 diodes and a 100-150µF smoother. Output of the chip goes to the 'phone line by way of an audio output transformer, the 0.1µF capacitor making the sound a little less shrill.

Pressing the switch and keeping it

pressed applies voltage to the chip, this being held on by the scr. The led illuminates and, when the 'phone is replaced on its hook, lights up a little brighter. When the handset is replaced the switch can be released. When the remote handset is picked up, the music stops and the led goes out since there is insufficient holding current for the scr.

Further such circuits may be used in parallel.

*Robert L A Trost
Duiven
Holland
D33*

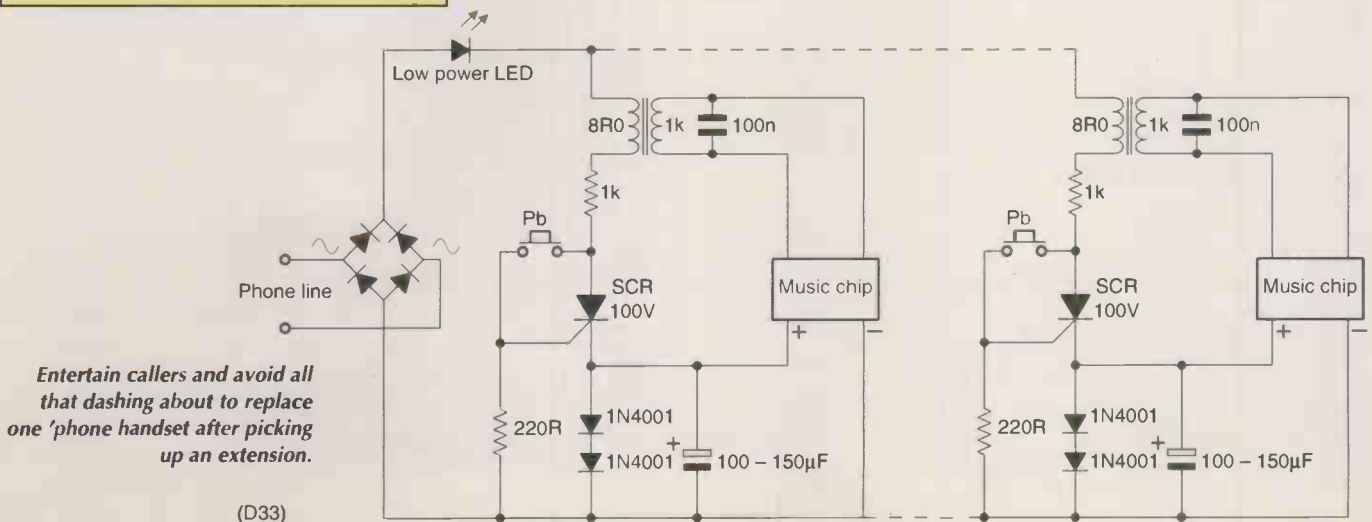

(D33)

Entertain callers and avoid all that dashing about to replace one 'phone handset after picking up an extension.

Sleep switch for lamps


This device will switch off a reading lamp after about half an hour, the reader then probably being asleep. After switching the circuit on, the led illuminates for around 25 minutes; at 19min, it starts to blink for two minutes, stops blinking for two minutes and blinks for another two, just before switching the lamp off.

The n-p-n and p-n-p combination are either both on or both off, taking very little current in the off state. Pressing P_1 starts things off by turning the relay on to power the ics. The lamp comes on and the 4060 oscillator/counter is reset on pin 12. It oscillates at a frequency determined by its CR and pin 3 goes high after around 30min, turning the transistors off.

Blinking of the lamp is the function of the outputs 1, 2 and 15 of the 4060 to the nand gates, which are in parallel for a greater lamp current, the oscillator output at pin 9 setting the blinking frequency. You can connect a piezoelectric sounder, if required, to pins 1 and 14 of the nand pair.

Flavio Delliprave
Genoa
Italy
D22

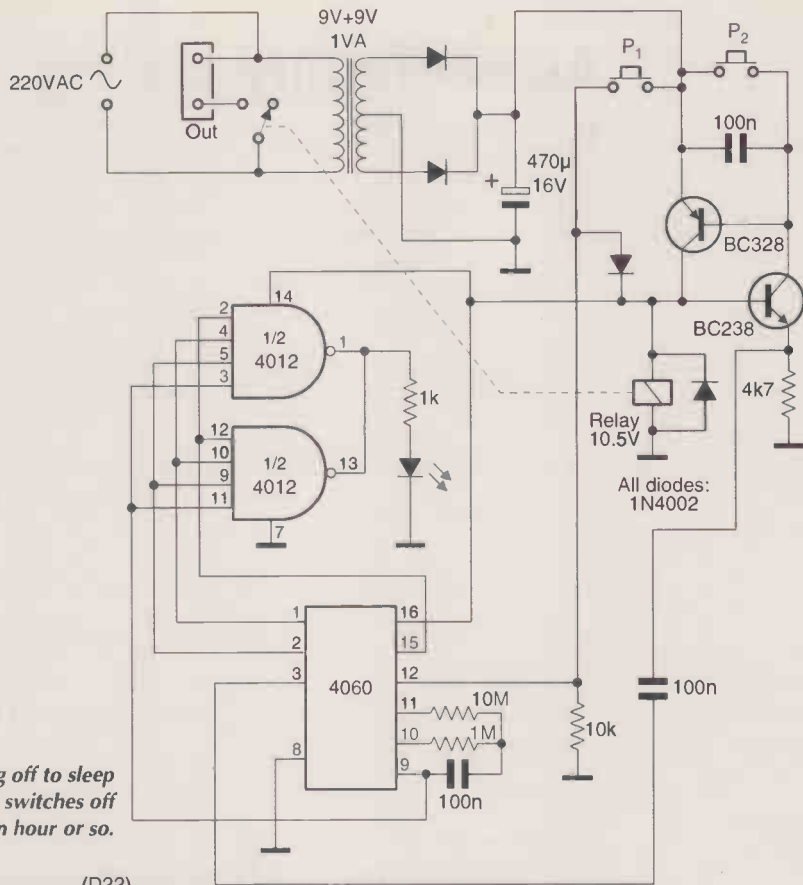If you are in the habit of drifting off to sleep when reading in bed, this circuit switches off the reading lamp after half an hour or so.



(D22)

Ten year index: new update

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format. Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* index
Indexes on paper for volumes 100,101, and 102 are available at £2 each, excluding postage.

TABLE OF CONTENTS

- Applications
 - Applications by description
 - Applications by part numbers
 - Company addresses
- Author Index
- Books
 - Circuit Ideas
 - Information
 - Subject Index
- Analogue Design
- Audio
- Avionics
- Broadcast
- Communications
- Components
- Computing
- Consumer Electronics
- Control Electronics
- Digital & DSP Design
- History

The *Electronics World* SoftIndex runs from January 1988 to May 1996 and contains references to 1300 articles and 800 circuit ideas. There is a separate author index with full cross references. Reprints can be obtained for all the articles in this index - see the information section for more details. For up to date information about *Electronics World* see our website at <http://www.softcopy.co.uk>

Buttons: Report, Note, About, Exit

www.softcopy.co.uk

Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sase to SoftCopy Ltd. **Send your orders to SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

e-mail at SoftCopy@compuserve.com, tel 01242 241455

Water detector


Normally, circuits using transistors are used in this type of circuit, but often need mains power because of the current drain when working constantly. This uses a fet and takes no current except when the buzzer sounds.

The circuit is simple: when the two probes are in water, or even damp earth, the positive 6V supply is connected through the water to the gate of the fet, turning it on and sounding the buzzer.

Resistance, set to around 50kΩ, between gate and 0V dissipates stray voltages picked up by the high-impedance gate. Other types of sensor could be used: photocells or thermistors, for example.

F O Eliason
Weston
Australia

D23

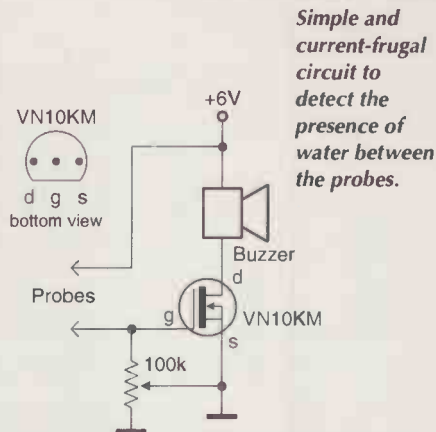

Peak-video-to-dc converter

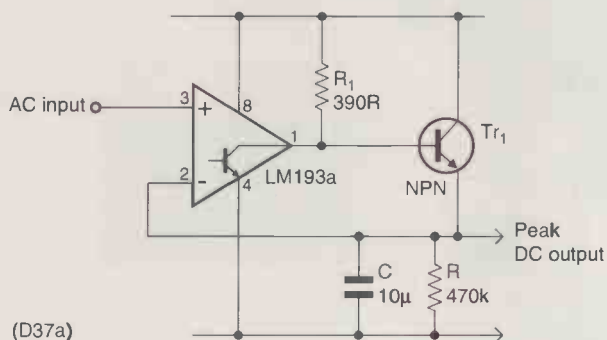


Fig. 1. Comparator for detecting the positive peak.

Peak-to-peak video voltage is converted by this circuit arrangement to a direct voltage.


Figure 1 shows the comparator circuit to detect the positive peak. Voltage at pin 2 follows that at pin 3, the input. If the input is greater than the voltage at pin 2, the op-amp open collector is off and base current for Tr_1 comes through R_1 , allowing the capacitor to charge to the input voltage. When the input reduces, the position is reversed and the transistor

turns off, the peak voltage remaining on the emitter, since the emitter CR is long.

Negative peaks require a modification, as shown in the complete diagram of Fig. 2, in which the extra n-p-n transistor ensures rapid turn-off of the p-n-p device after the peak input voltage is past.

J M Rowe
Kowloon
Hong Kong
D37

£50 WINNER

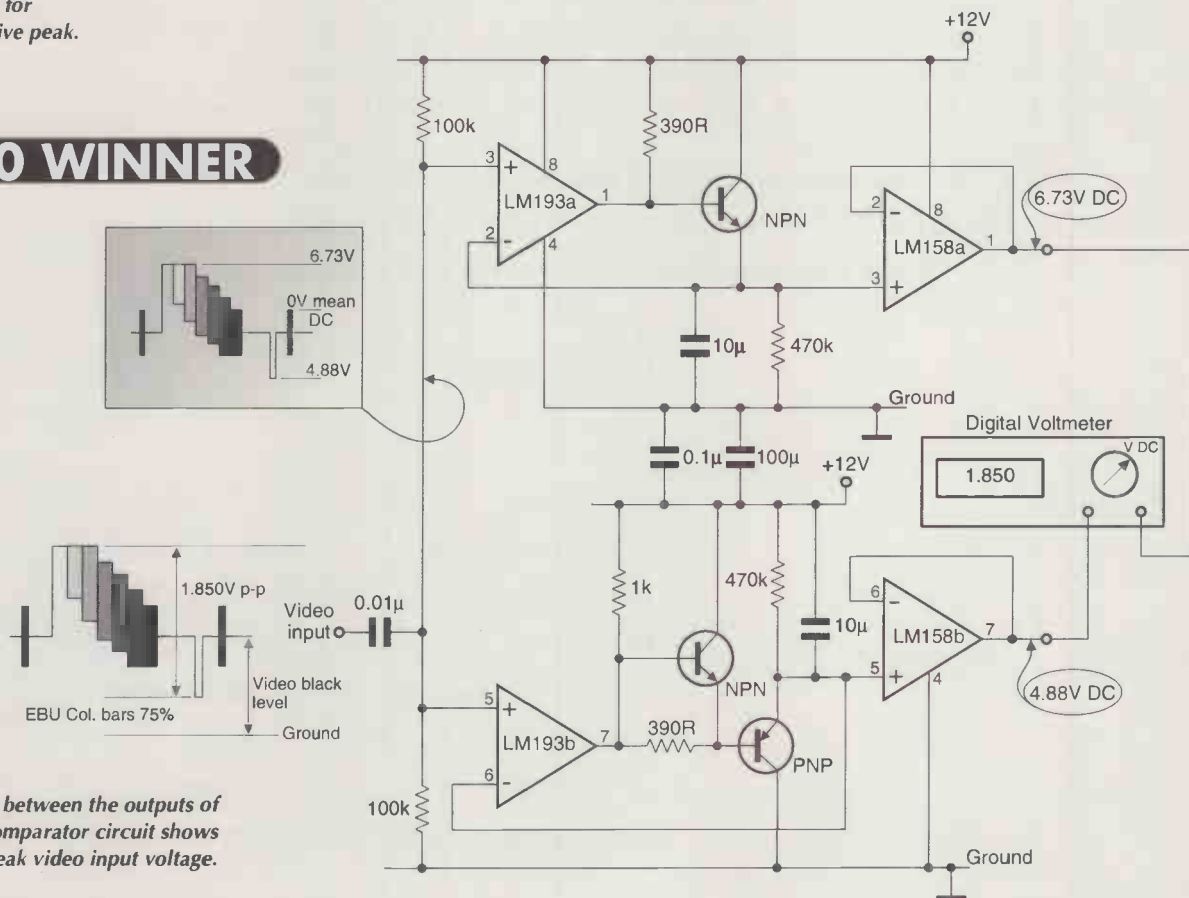


We make our programmers work harder

FEATURES


- ◆ Supports EPROMs, EEPROMs, Flash, Serial PROMs, BPROMs, PSDs, PALs, GALs, PEELs, MACH, MAX, EPLDs, and over 200 Microcontrollers including 87C48/51, 89C51/52, PIC, MC705/711, ST6, Z86, COP etc.
- ◆ Hands free programming so you can produce batches of the same chip without pressing a key
- ◆ Correct programming and verification at 1.8, 2.7, 3.3 and 5V
- ◆ Serial number mode supports date/time stamping, unique IDs
- ◆ Progress indicator shows number of devices programmed
- ◆ No adapters required for DIL parts upto 48-pins. Universal adapters for 44-pin PLCC, 44-pin PSOP and 48-pin TSOP parts
- ◆ Programmes and verifies Intel 28F400 in under 15 seconds
- ◆ Connects to parallel port - no PC cards needed
- ◆ Tests 7400, 4000, DRAM and SRAM
- ◆ Mains or battery operation
- ◆ FREE software device support upgrades via bulletin board and www



Easy device selection.

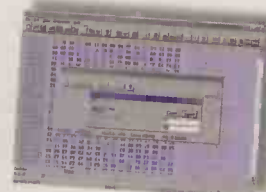

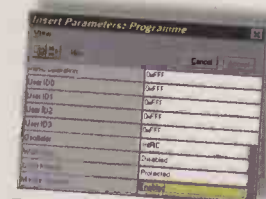Programming, Emulation, Testing all in one easy to use application.



Full support for device-specific features



Store your favourite projects...

48-pin Universal Programmer STILL ONLY

£695



SPEEDMASTER GLV32 £695



LV40 PORTABLE £995

PROGRAMMER MODELS AND PRICES

SINGLE SOCKET PROGRAMMER			EMULATOR OPTIONS			GANG PROGRAMMERS		
			FOR ALL PC BASED PROGRAMMERS					
MICROMASTER LV48	48-pin universal programmer	£695	LVECEMUL8	128kx8 ROM/RAM emulator with modify on the fly feature Upgradable to 512x8	£125	SPEEDMASTER GLV32	8-way 32-pin EPROM/Flash Gang/Set programmer	£695
SPEEDMASTER/MICROMASTER	40-pin programmer range (see website or call for model details)	FROM £395				SPEEDMASTER GLVCOP	8-way 40-pin gang programmer for National Semiconductor COP micros	£1500
EPMASER LV	40-pin EPROM/Flash programmer	£295	LVECEMUL16	128x16 ROM/RAM emulator with modify on the fly feature Upgradable to 512x16	£195	SOCKET ADAPTERS	Full range of adapters for PLCC, SOIC, TSOP, PSOP etc...	FROM £65
LV40 PORTABLE	As Micromaster LV, plus completely portable with built in keypad and LCD display.	£995						

All prices exclude VAT and delivery

See for yourself - download a demo from our Website at www.icetech.com

ORDER NOW - ALL PRODUCTS IN STOCK. CREDIT CARD ORDERS: 01226 767404

For a copy of our catalogue giving full details of programmers, emulators, erasers and adapters, call, fax or e-mail us. You can also access our BBS or Home page. All our products are in stock now for next day delivery - call our credit card hotline now.



ICE Technology Ltd. Penistone Court, Sheffield Road, Penistone, Sheffield, UK S36 6HP

Tel: +44 (0)1226 767404 Fax: +44 (0)1226 370434 BBS: +44 (0)1226 761181 (I4400, 8N1)

Web: www.icetech.com Email: sales@icetech.com



CIRCLE NO. 115 ON REPLY CARD

£50 WINNER

Synchronous am detector

This produces a low-distortion baseband output after a 455kHz if strip, the NE564 linear phase-locked loop generating a 455kHz signal in phase with the if carrier.

Output of the pll is 1820kHz, set by C_2 , applied to the 4027 divide-by-four ic to produce 455kHz outputs in phase quadrature. One of these, from pin 15 of the 4027, is fed back to the reference of the NE564 and is in quadrature with the if when the loop is locked. Outputs from pins 1 and 2 form a balanced drive, in phase with

the if, for the 1496 mixer/demodulator.


Components C_1R_1 are the pll filter to set the open-loop characteristics and therefore the critically damped closed-loop response, bandwidth being around 5kHz. The pll will track the input over ± 150 kHz.

The only adjustment is that of C_2 , which is set to give a vco free-running frequency of 455kHz on pin 10 of the 4027, with no input connected and after a warm-up time

of two minutes. A dc level at pin 14 of the 564 may be used to drive a centre-zero tuning meter. The pll needs a small heatsink to reduce temperature effects; all components are of 5% tolerance.

Distortion was measured at 0.2% although, since this was also the distortion of the rf generator used, it is probably a good deal less than that.

P Goodson
Bracknell
Berkshire
D42

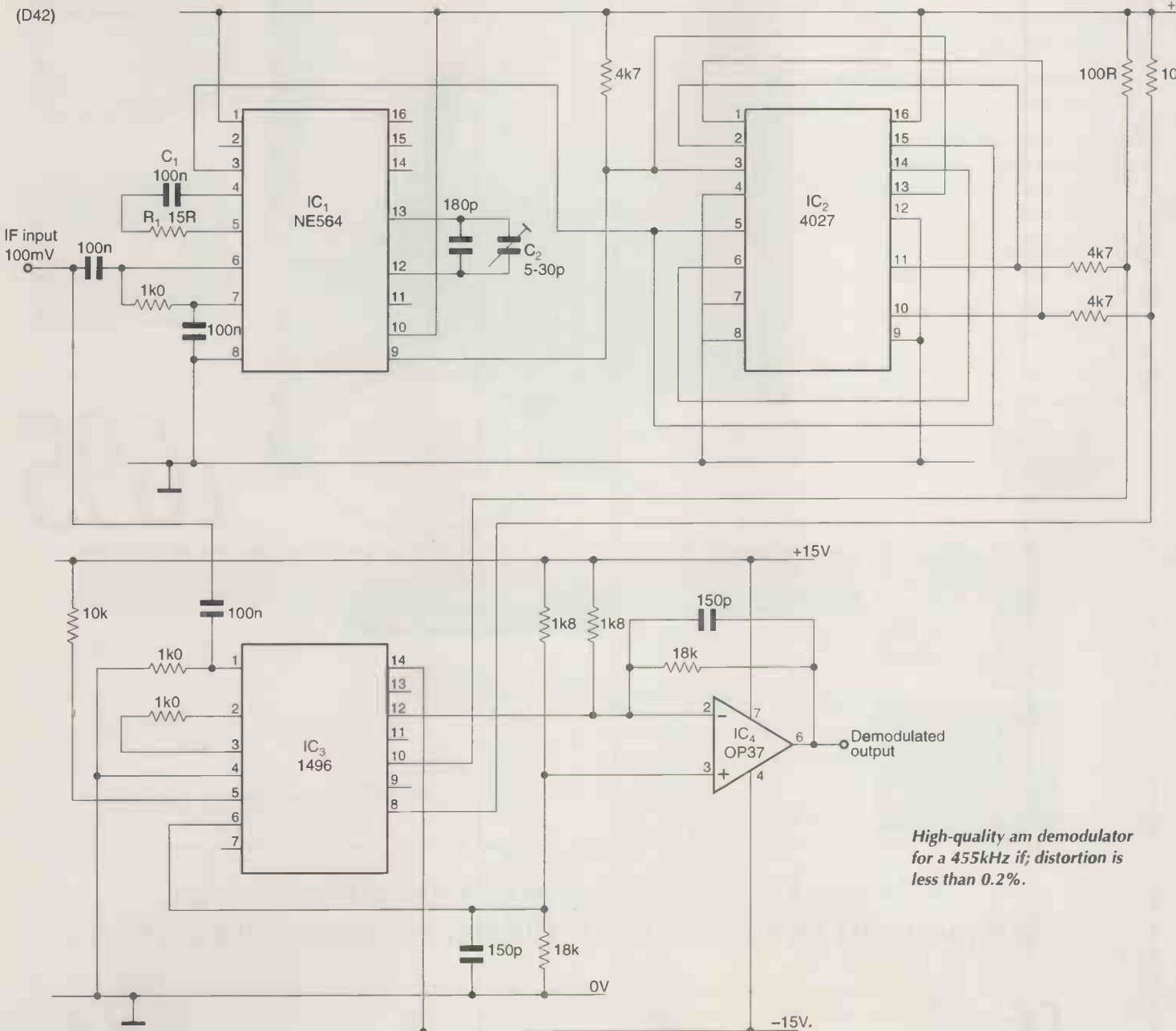

High-quality am demodulator for a 455kHz if; distortion is less than 0.2%.


Save over 60% on QR4 Full Access. Just £99 (normal price £249. Offer ends 31 October '99. Price excludes post, packing and VAT.



QUICKROUTE

www.quickroute.co.uk

THE QUICKROUTE

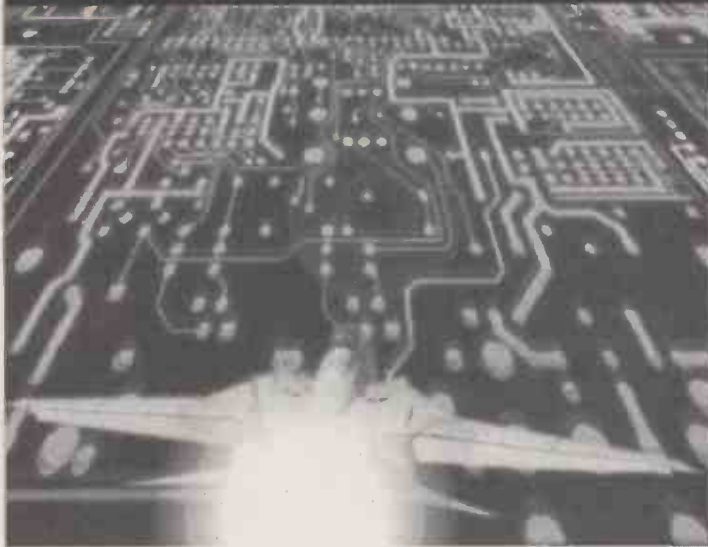

Simulation Circuit Capture PCB Autorouting CAD/CAM

Imagine an electronics design system that lets you draw schematics onto the screen and then simulate them at the touch of a button. Now imagine pressing another button and seeing the schematic replaced with a PCB rats-nest. Pressing another button starts the autorouter, and finally you can click on File then Save As to create a complete set of CAD/CAM files.

Too easy? We hope so. Quickroute has always been designed first and foremost to be easy to use. That's why simulation, circuit capture, PCB autorouting and CAD/CAM support are all integrated into **one** package, so that you only have to learn **one** package.

If you would like to find out more about Quickroute, why not call us on FREEphone 0800 731 28 24, or visit our web site on www.quickroute.co.uk. Prices start at under £100 including UK P&P and VAT for a complete system.



**"modern, powerful
and easy to use"**

Elekta Electronics 97

FREEphone
0800 731 28 24


Int +44 161 476 0202 Fax 0161 476 0505




Copyright © 1998 Quickroute Systems Ltd Regent House Heaton Lane Stockport SK4 1BS UK

CIRCLE NO.116 ON REPLY CARD

Test equipment lacking functionality?

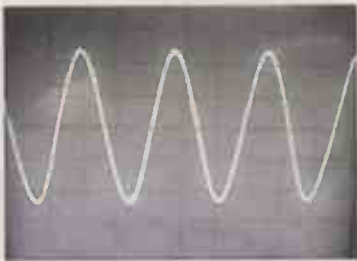

or

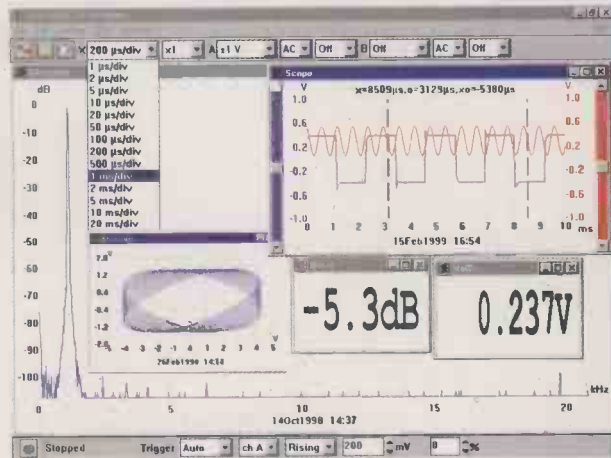

Easy choice? Then send for the Pico Technology full colour PC based test & measurement catalog and software demonstration disk. Alternatively, visit our web site at:

www.picotech.com



- ▼ Up to 100MS/s
- ▼ Up to 16 bit resolution
- ▼ Prices from £59
- ▼ Software included
- ▼ Easy to use
- ▼ Compact & portable units

oscilloscopes data acquisition spectrum analysers multimeters signal conditioning environmental monitoring

Tel: +44(0)1954 211716, Fax: +44 (0)1954 211880, E:mail: post@picotech.com, Web: www.picotech.com

CIRCLE NO.117 ON REPLY CARD

PICO
Technology Limited

Voltage control for a digital delay line

Figure 1 shows the arrangement of a tapped digital delay line, the precise delay between input and taps being determined by a control voltage.

Input $v_i(t)$ is applied to a sample-and-hold whose clock is the output of a voltage-controlled oscillator. From the s/h, the sampled voltage $v_i(nT)$ goes to a fast a-to-d converter whose output shifts into the first 8-bit parallel shift register of 12 in a line, the shift for the first being provided by the end-of-conversion signal from the a-to-d converter. Sampling clock pulses for the s/h are also used as

clock pulses for the shift registers, each of which shifts right on every clock pulse.

Output from the fourth, eighth and twelfth registers are taken to d-to-a converters, which then provide the delay-line output in analogue form after the relevant delay: $4T$, $8T$ and $12T$, T being the clock period, so that the output from the fourth register will be

$$\Phi_1 = v_i((n-4)T),$$

and so on. The result of all this is that the delay periods are controlled by the

control voltage to the voltage-controlled oscillator. More registers and taps would, clearly, be used and perhaps the delay line could be developed as an ic.

One use of this delay line would be as a phased antenna array to provide electronic scanning.

K Balasubramanian

H B Gayathri





H Camur

European University of Lefke

Turkish Republic of Northern

Cyprus

D25

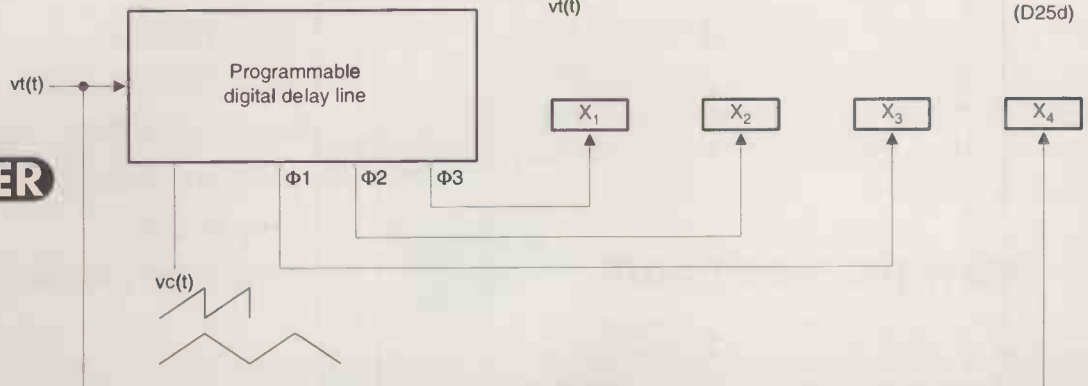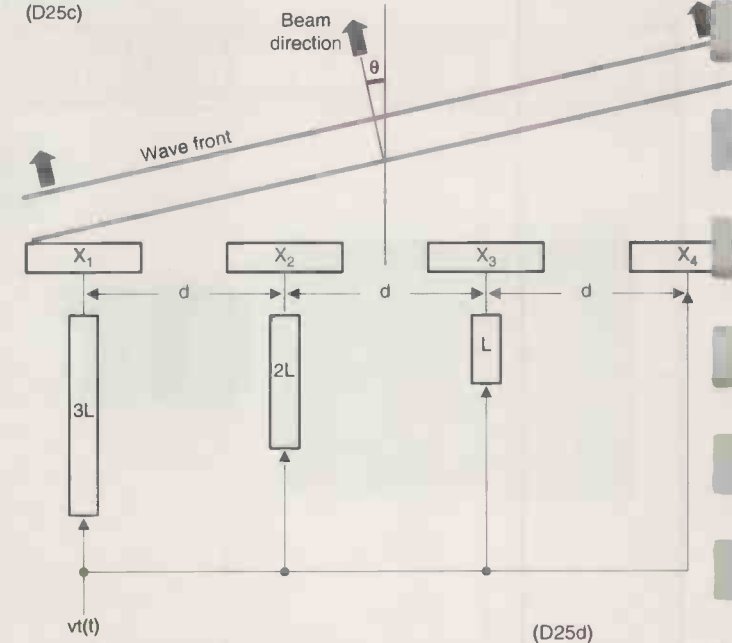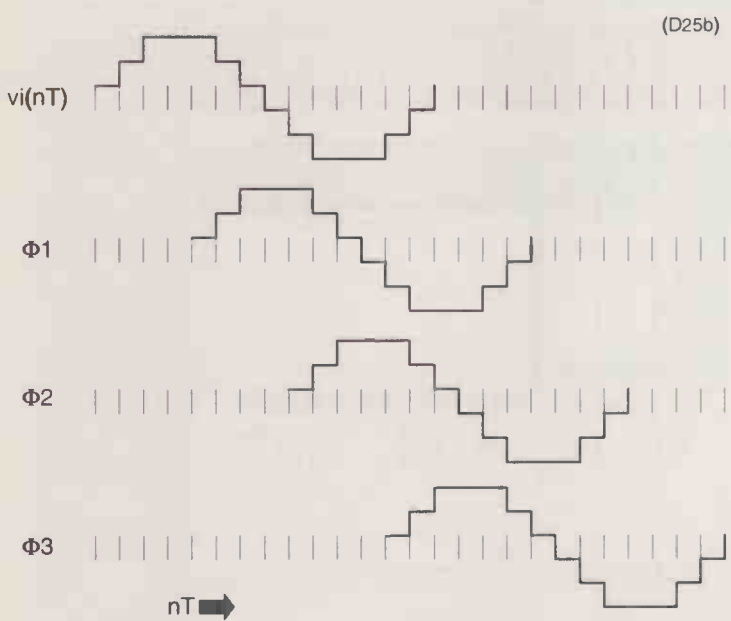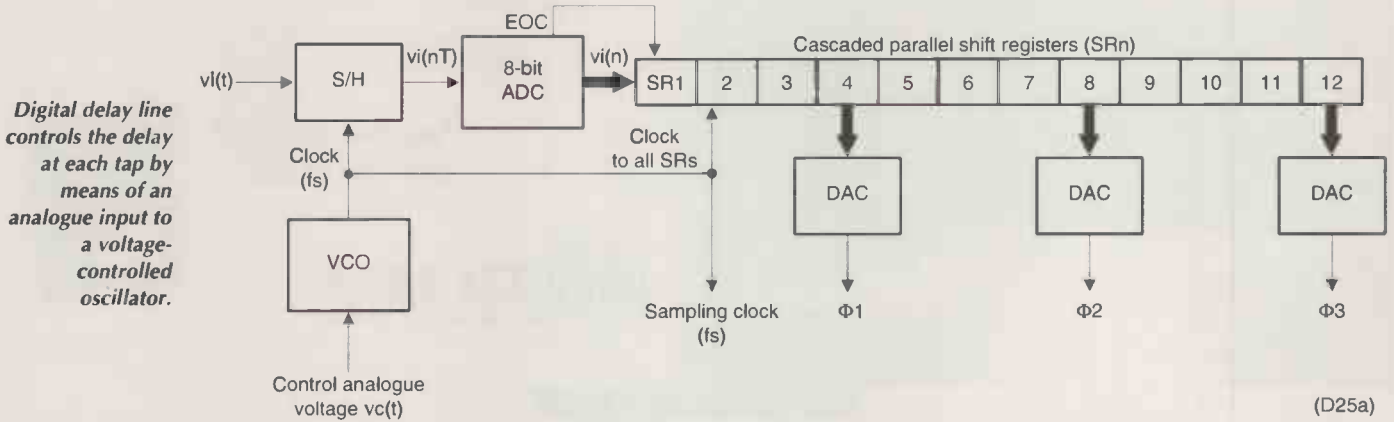

£100 WINNER

EUROPE'S NUMBER ONE BROADBAND CONVENTION

NATIONAL HALL OLYMPIA, LONDON

18, 19, 20 OCTOBER 1999

The most comprehensive exhibition

The big names in broadband meet at ECC. You'll see everything from network hardware to the latest in broadband content.

"so much more to see"

BROADBAND bistro

Experience working demonstrations of both hardware and broadband content.

"seeing the future of broadband"

www.eurocab.com

Be a part of the industry's future.

The conference addresses broadband's major topics, on a pan European level.

"speakers who really matter"

Technical Seminars

A free, continuous, programme of seminars organised in conjunction with the SCTE.

"genuinely informative"

A place to meet.....

Meet key members of the industry at ECC's social programme.

"really rounds off a great convention"

Website: www.eurocab.com

email: ecc@cablenet.co.uk

Fax: +44(0) 171 222 3198

Tel: +44(0) 171 460 4220

ecc99



EUROPEAN CABLE CONVENTION
SEE THE FUTURE - SHAPE THE FUTURE

Quick-on, delayed-off switching

It is sometimes required to switch a piece of equipment on by means of a push-button switch operating a toggle of some kind, such as a flip-flop, immediate accidental switching off being prevented. This circuit consists simply of a 4013 flip-flop and part of a 40106 inverter.

Output Q is initially logic zero, operating the switch charging C through the diode and the flip-flop output impedance; the output now becomes 1. Releasing the switch discharges C through R₁, further switching having no effect since the diode will not conduct. However, holding the switch on for long enough for C to charge via R₂ clocks the flip-flop and the output goes back to logic zero.

For delays of around 1s, R₂=10MΩ and C=100nF. On power-up, the flip-flop's set and reset inputs should be used to put the output into the required state.

B Vojnovic

R G Newman



Gray Laboratory Cancer Research Trust

Mount Vernon Hospital

Northwood

Middlesex

D39

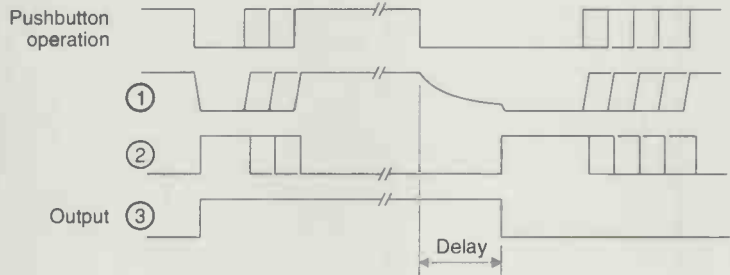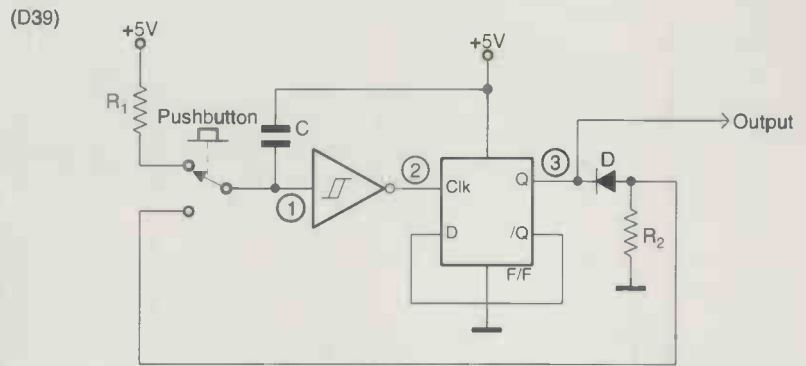

Power switching circuit to impose a delay after switch-on before switch-off can occur.

Using a 555 for speed control

Offset circuit avoids problems in the use of the 555 for pwm speed control.

Since the capacitor voltage in NE555 applications must be limited to between 33% and 67% of V_{CC}, there are problems with the ic when used for pulse-width modulation in speed control, as the


speed setting is usually between, for example, zero and 10V. This circuit provides an offset between capacitor voltage and the 555 sensed voltage to overcome that drawback.

Inserting R₂ between R₁ and C₂, makes the capacitor discharge to a lower level before it triggers the 555; the threshold is unaffected.

As shown, the capacitor starts to charge at 1.8V and to discharge at 10V. In this case, a pwm minimum duty cycle was 5%, so the capacitor voltage comes from pin 7 of the 555 to allow the negative input of the op-amp to stay near ground during the discharge. Bypassing the diode causes the pwm signal to disappear and the output to remain low during the capacitor discharge.

The reference voltage for the potentiometer comes from the internal reference in the 555, the transistor on the control-voltage pin, pin 5, allowing it to drive low impedances without affecting the control voltage.

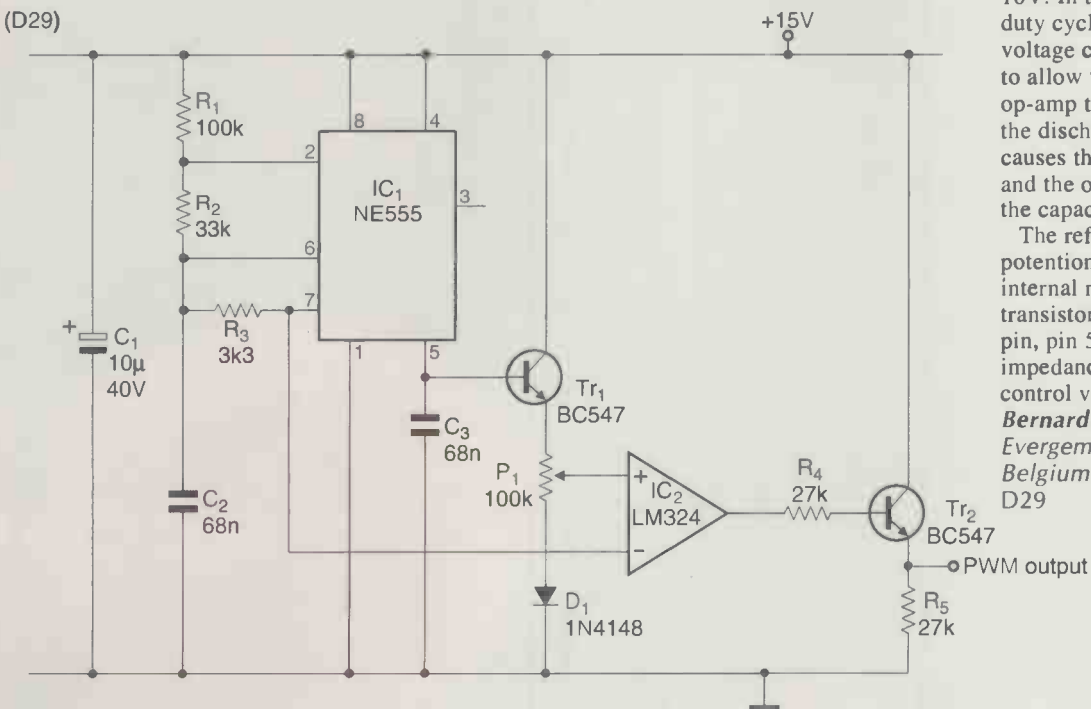Bernard van den Abeele
Evergem
Belgium
D29



PROFESSIONAL Development Tools

from Milford Instruments

Milford Instruments Tel 01977 683665, Fax 01977 681465
www.milinst.demon.co.uk info@milinst.demon.co.uk
Milford House, 120 High Street, South Milford, LEEDS LS25 5AQ



PIC Emulators from Tech Tools

Mathias In-Circuit Emulator

- 16C5X to 20MHz
 - 16CXX to 25MHz and data breakpoints
 - Modular design
 - True Integrated Windows Environment
 - Supports standard assemblers and compilers
 - True Bondout Chip set based
 - Programmers and adaptors also available
- Full details at www.tech-tools.com




New to PICs or just wanting to learn new tricks?

We stock the excellent Square 1 series of PIC primers. See our web site for contents.

BASIC Stamps

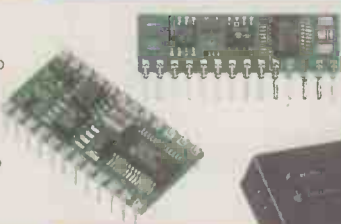Still the easiest and fastest way to get your project up and going. 8 or 16 I/O pins, easy-to-read BASIC instructions plus on-board comms and simple interfacing to peripheral chips.



Scenix Emulators from Parallax



SX-Key Emulator
SX chips are EEPROM based, PIC16C5x pin compatible micros with up to **100mips** performance.

- Full speed debugging on production chips
- Integrated Windows environment
- Software configured oscillator
- 18 to 52 pin reprogrammable devices
- SX Blitz low cost programmer also available. Full details and software at www.parallaxinc.com

ROM Emulators from TechTools



EconoROM, FlexROM and UniROM

- Fast 90ns, 45ns and 35ns access times
- Fast download (up to 2.5Mbit/second)
- Read-back, Verify and Self-Test modes
- Full editor and utilities included
- Live editing (UniROM only)
- 8bit & 16bit up to 32Mbit
- EPROM, FLASH and SRAM emulation

Full details and demo software at www.tech-tools.com



SERIAL LCDs reduce display hassle

We stock a range of alphanumeric and graphic displays all fitted with serial RS232 interface boards: 2x16 to 4x40 and up to 128x64 graphics size.

RS232 data entry terminal unit also available

CIRCLE NO.119 ON REPLY CARD

LANGREX SUPPLIES LTD
DISTRIBUTORS OF ELECTRONIC VALVES
TUBES AND SEMICONDUCTORS AND I.C.S.

PHONE 0181 684 1166 FAX 0181 684 3056
1 MAYO ROAD • CROYDON • SURREY CR0 2QP

24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS
email: langrex@aol.com

Part No.	Price	Part No.	Price	Part No.	Price
AZ31	6.00	KT66 Special	20.00	5Z4G	6.00
CL33	10.00	KT88 Special	20.00	5Z4GT	3.00
EB8CC	8.50	KT90	17.50	6A05	2.00
E180F	3.50	N78	8.00	6AR5	20.00
E810F	20.00	OA2	3.00	6AS7G	7.50
EAB8C80	2.00	OB2	3.00	6AU5GT	4.00
EB91	1.50	OC3	3.00	6AU6	2.00
EBF80	1.50	OD3	3.00	6AW8A	4.00
EBF89	1.50	PCF80	2.00	6B4G	22.00
EBL31	15.00	PCL82	2.00	6BA6	2.00
ECC33	12.00	PCL85/805	2.50	6BE6	1.50
ECC35	12.00	PCL86	2.50	6BH6	2.00
ECC81	3.00	PD500	6.00	6B07A	2.00
ECC82	3.50	PL36	3.00	6BR7	4.00
ECC83	3.00	PL81	2.00	6BR8	4.00
ECC85	3.50	PL504	3.00	6BW6	4.00
ECC88	6.00	PL508	3.00	6BW7	3.00
ECC808	15.00	PL509/519	10.00	6BZ6	3.00
ECF80	1.50	PL802	4.00	6C4	2.00
ECH35	3.50	PY500A	3.00	6CB6A	3.00
ECH42	3.50	PY800/801	1.50	6DC6G	5.00
EQH81	3.00	QOV02-6	12.00	6CL6	3.00
ECL82	3.50	QOV03-10	5.00	6CG7	7.50
ECL86	3.50	QOV03-20A	10.00	6CH6	3.00
ECLL800	25.00	QOV06-40A	12.00	6CW4	6.00
FE37A	3.50	U19	8.00	6D05	17.50
EF39	2.75	UABC80	1.50	6D06B	10.00
EF40	4.00	UCH42	5.50	6F6G	6.00
EF86	10.00	UCL82	2.00	6FQ7	7.50
EF91	2.00	UCL83	2.00	6GK6	4.00
EF183/4	2.00	UF89	4.00	6J5G	6.00
EL33	15.00	UL41	12.00	6J5M	4.00
EL34	5.00	UL84	3.00	6J7	3.00
EL34G	5.00	UY41	4.00	6JB6A	27.50
EL36	5.00	UY85	2.00	6JE6C	27.50
EL41	3.50	VR105/30	5.00	6JS6C	27.50
EL84	2.25	VR150/30	3.00	6KEGT	4.00
EL95	2.00	Z759	10.00	6LG6	15.00
EL360	15.00	Z803U	15.00	6LGGC	15.00
EL509/519	7.50	2D21	3.50	6LWGB	10.00
EM34	15.00	3B28	12.00	6O7	3.00
EM814/7	4.00	4CX250B	45.00	6SA7	3.00
EN91	7.50	5R4GY	7.50	6SC7	3.00
EZ80/81	5.00	5U4G	10.00	6SG7	3.00
GZ32	8.50	5U4GB	10.00	6SJ7	3.00
GZ33/37	6.00	5V4G	4.00	6SK7	3.00
KT61	15.00	5Y3GT	2.50	6SL7GT	5.00
		5Z3	5.00	6SN7GT	5.00

Prices correct when going to press.

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY

This is a selection from our stock of over 6,000 types. Please enquire for types not listed. Obsolete items are our speciality. Valves are new mainly original British or American brands. Terms CWO/min order £10 for credit cards.

P&P 1-3 valves £2.00 4-5 valves £3.00
Add 17.5% VAT to total including P&P.



CIRCLE NO.120 ON REPLY CARD

CROWN HILL ASSOCIATES

LAB PROG 48LV

LOW COST - HIGH PERFORMANCE DEVICE PROGRAMMING SYSTEM

- Programs and verifies at 2, 2.7, 3, 3.3, and 5 V
- True no-adaptor programming right up to 48-pin DIL devices
- Built-in 240v AC/12c AC PSU
- Package adaptors for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator
- Plugs straight into the parallel port of PC or Laptop
- Download Comprehensive Device List

Includes:

- Connection Cable
- Diagnostic POD for Self Test
- User manual
- 3.5" diskette with software

Also Available:
SEEPROM
Universal EEPROM
Programmer
£49.95 +Delivery +VAT

PREPROGRAMMED EPROM, (E)EPROM, Flash EPROM Microprocessors Programmer
£132.00 +Delivery +VAT

£356.00 Plus Delivery Plus VAT

The Old Bakery, 54 New Barns Road, Ely, Cambs, CB7 4PW
Tel: +44 (0)1353 666709 Fax: +44 (0)1353 666710
E-mail: Sales@crownhill.co.uk
www.crownhill.co.uk

CIRCLE NO.121 ON REPLY CARD


Lead-acid battery charger

This battery charger for lead-acid batteries switches the charge when the battery voltage rises above that of a fully charged battery, which has been used for calibration.

The potential divider incorporating VR_1 must be adjusted so that the op-amp output just becomes high when the calibrating battery is in position, so that when the battery under charge is in place, an increase in its voltage to more than 100mV above that of a fully charged battery turns on the transistor by way of the led and the relay is activated to stop the charge.

Ejaz Ur Rehman
ACD-Pinstech
Islamabad
Pakistan

D30

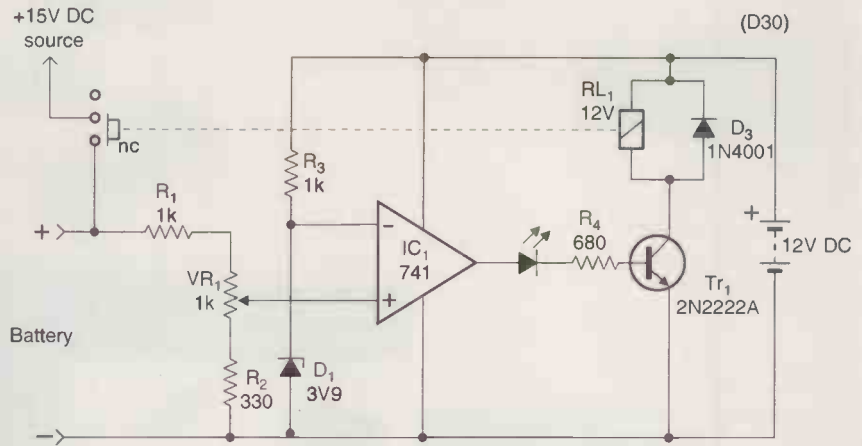

Lead-acid battery charger stops the charge automatically when the battery is fully charged.

Electronic load

There are several methods of testing DC power supplies using variable loads, but they turn out to be unwieldy and difficult to adjust (rheostats), or to need heat sinks and insulation (power transistors). Wirewound resistors suffer from neither defect and can be obtained in metal-clad types with insulation.

Figure 1 shows one method. A fast-switching mosfet with a choke in

its drain draws the supply current, dissipation being low in the Class-D operation adopted. Waste power is simply dumped in the resistor, which is of fixed value, the variation being taken care of by varying the pulse width. In testing the circuit, it became clear that the diode is unnecessary, which gives more current from the supply; the choke L_1 may also be left out to leave only the resistor in circuit.

However, it is best to keep the choke as part of a filter using $C_{1,2}$ to smooth the pulses to the supply, as seen in Fig. 2. Variable-width pulses come from the 555, which takes its own supply from terminal B or from a secondary winding on the choke via $D_{2,3}$.

Pulse width is varied by P_1 to

provide effectively a variable resistive load from around 33Ω to 2.7Ω . Switching frequency, determined by $P_1R_{2,3}C_3$, is about 15-60kHz, the off time of the mosfet being $15\mu s$ and the on time variable from 1.5 μs to 50 μs , so the duty cycle is theoretically 9%-77%, although switching times mean a lower limit of 6%.

The turns ratio of L_1 is such that at least 12V goes to $D_{2,3}$ from the ripple across the primary. Capacitor C_2 must withstand the ripple caused by switching and must be a multiple unit. Resistance R_1 , which consists of five resistors, is fixed to a 25 by 15cm aluminium sheet and the mosfet is fitted with a $10^\circ C/W$ heat sink.

C J D Catto
Cambridge

D32


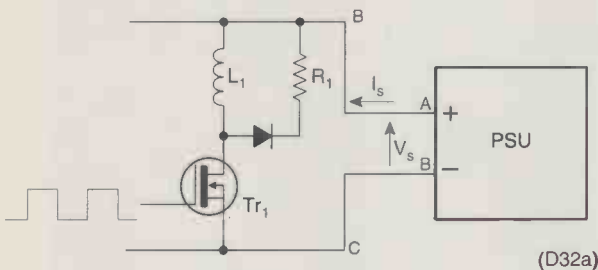


Fig. 1. One way of providing a variable load for power supply testing is to pulse-width modulate a mosfet and dump the power into a fixed resistor.

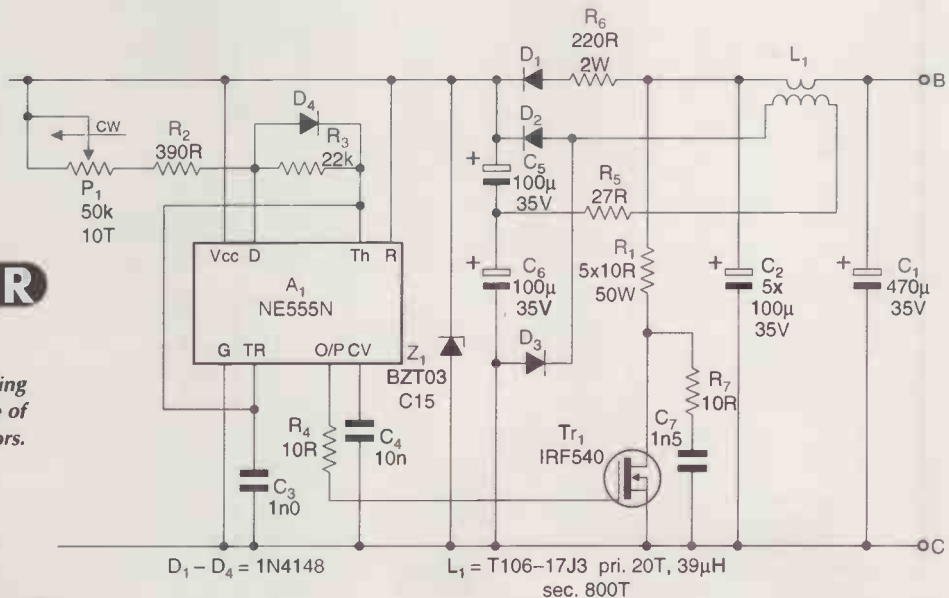

(D32b)

£50 WINNER

Fig. 2. Variable load for testing power supplies avoids the use of rheostats and power transistors.



Review subjects

The first review covered *Electronics Workbench* version 5.12, whose maker is IIT Ltd of Canada. Workbench's UK supplier is Adept Scientific plc, tel 01462 480055. *Electronic Workbench's* price is £199.

Rod looked at *CircuitMaker* in the August issue. This £199 package is made by MicroCode in the US and supplied by Labvolt in the UK, tel. 01480 300695.

Tina Pro, priced at £299, was featured in the September issue. Quickroute supplies Tina in the UK, tel 0161 4760202.

Pulsar and Analyser from Number One Systems, which are modules from the *Easy PC* package, are the subjects of Rod's next review.

Rod Cooper investigates the comprehensive circuit CAD package Proteus, which has recently benefited from a new simulation engine. This design tool is different from those reviewed so far in that it has no virtual instruments. But does that matter?

The route to simulation IV

Prospice is the newly developed engine at the heart of the LISA simulator, which is part of the Proteus IV version 4.6 package. LISA is an acronym that simply stands for Labcenter Integrated Simulation Architecture.

The other two parts of Proteus are ISIS, the schematic drawing and capture program, and ARES, the pcb drafting and routing program. All three are tightly integrated into Proteus, with the same style of operation, menus, graphics and screen layout. The considerable benefits of having all three combined into one package have already been extolled.

Labcenter's Prospice is based on Spice 3F5 and is a true mixed-mode simulator, and a complete replacement for the analogue and digital engines previously used. LISA is fully integrated with ISIS; that is, you do not have to transfer out of ISIS into LISA to run a simulation.

When it comes to simulation, LISA and ISIS are fully integrated. Graphs and other results appear as an overlay on the schematic screen, and in this respect it is very similar to the other programs reviewed to date.

Pay for what you need

There are several levels of ISIS with corresponding prices. The aspect usually of most interest here is the pin and node limit. The price starts at £295 for the low-

est level with a schematic limit of 1000 pins and a simulator limit of 250 nodes.

Having a node limit overcomes the frequent complaint that a pin-limited simulator gives a false impression of its capacity. This is because there can be several pins used up in just one node.

A few features are omitted from the lowest levels, such as the sweep ability. In view of so much variability, it is probably best to discuss your design requirement, and what you can afford, with the company. If you subsequently find the limit is too small, it is possible to upgrade at reasonable cost.

Documentation

Proteus's documentation is comprehensive. It covers every aspect of operation, including tutorials and technical reference. It comes as a single hefty A5 loose-leaf book in three sections covering ISIS, LISA and ARES. Being loose leaf, the manual can be readily upgraded.

Like other makers, Labcenter has its own terminology, but this is well explained.

Background on the reasons for certain types of operation is also provided. This can be helpful in getting to grips with some aspects of Spice. Generally, the literature is clear, concise and plentiful. It is well complemented by the program's Help files. The CD includes a useful animated tutorial.

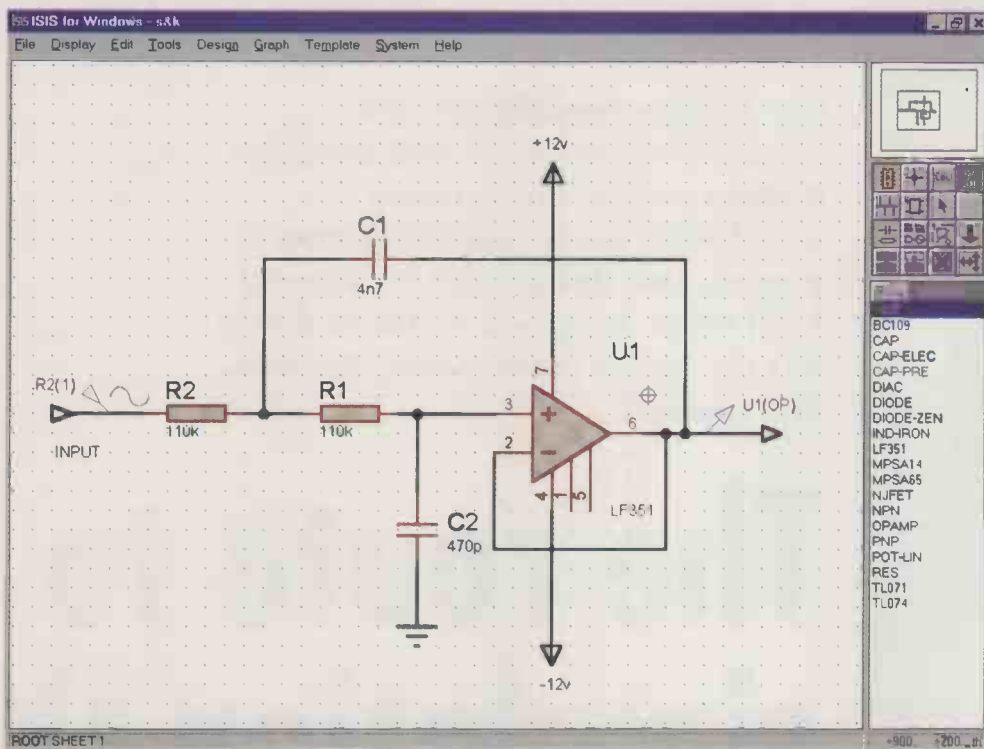


Fig. 1. This simple Sallen & Key filter shows the uncluttered drawing area of the schematic capture and simulator, with the parts bin on the right set up for general work on filters, from which a handful of symbols has been chosen for this circuit. Note how the signal generator on the input is attached, and the voltage probe on the output.

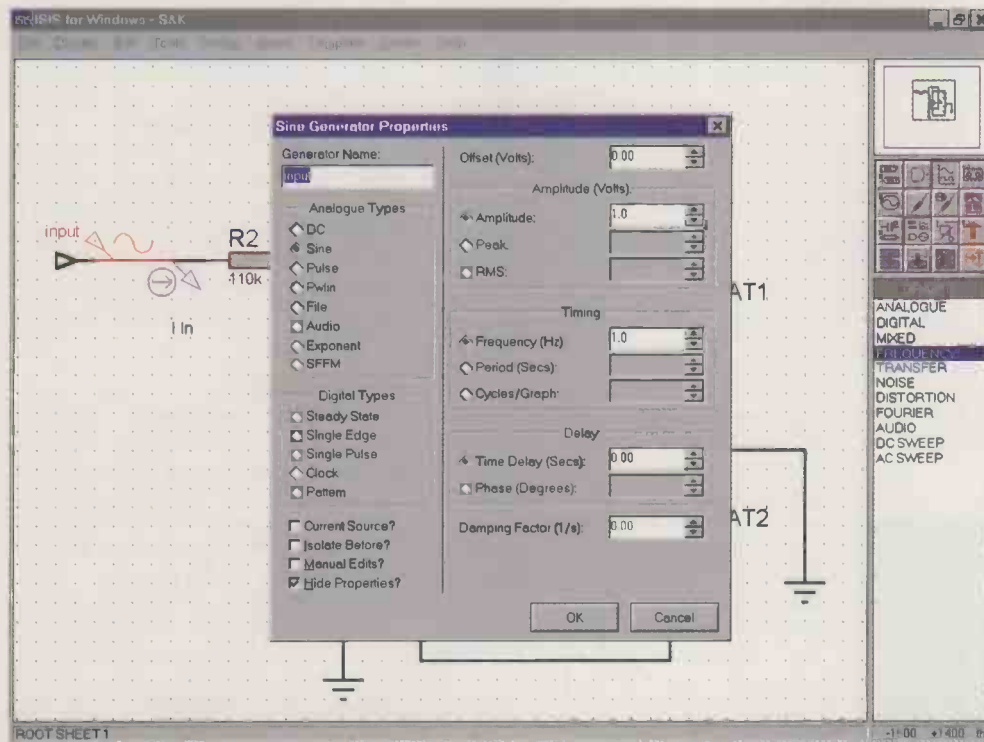


Fig. 2. The signal generator – the symbol highlighted in red on the left – is set up by this menu, contrasting with the virtual instrument approach. This type of menu system is used throughout the simulator.

Schematic capture

In brief, ISIS is an efficient schematic drawing program. It is well-endowed with features without being over-complex, and it has notably good graphics quality.

ISIS has a different style from the other Windows programs reviewed to date. For example there are no Windows-style scroll bars.

Panning is carried out by bumping the mouse against the edge of the drawing area. There are no expandable tool and symbol bars. Instead there is Labcenter's own method of accessing symbols, tools, etc., Fig. 1. On the right of the screen, the map area, tool area and parts bin all take up a fixed part of the monitor screen.

There are several other features characteristic only of Proteus, but this is a well-developed system, which has stood the test of time. It takes a little getting used to, but is rapid and effective in use once you have familiarised yourself with it.

The package has maintained its consistency through several upgrades. If you are an existing user of an earlier version, you should find upgrading reasonably painless.

Unlike Tina, Workbench and CircuitMaker, ISIS does not have pre-determined parts bins. However, it is easy to set up the ISIS parts bins with a permanent stock of symbols of your choice and save it if you wish. This makes ISIS suitable for experimental designing on-screen. I covered this important aspect in the Introduction in the August 1999 issue.

Figure 1 shows a parts bin set up as a type of permanent template for designing audio filters. It contains some generic and some specific devices. I could just as easily have loaded the template with all-generic devices for use as a purely experimental tool, and added other selections for, say, power supply or RF design.

On the subject of templates, Proteus has a sophisticated system where every detail from background colour to font type can be stored as a template.

The number of available symbols has been increased to 6000, including a small volume of thermionic valves, backed by 4000 Spice models.

New symbols can be created or modified via a graphics editor. A substantial section of the manual describes how Spice models can be generated, either from scratch or imported from manufacturers' Spice data, and attached to them.

Labcenter offer the best support in this review for other makers' net lists, in addition to its own SDF format. These include Boardmaker (Tsien), EEDesigner, Futurinet, Multiwire, Racal, Tango, Valid, Vutrax, Spice-Age (Dos) and of course Spice.

If you want more detailed information on schematic capture in ISIS, you will find it in my review in the May 98 edition of *Electronics World*.

Simulation

The new Prospice true mixed-mode simulator brings Labcenter's product into line with the other simulators reviewed so far. Most importantly, Prospice fulfils all the requirements for basic analyses listed in the introduction to these reviews. There are also several additional features, such as Fourier analysis, parameter sweeping and temperature modelling. Two points of special interest are described later.

Prospice does not use the virtual instrument concept. Instead, it uses icons that are handled within ISIS like ordinary schematic symbols. The icons are not wired in to terminals or nodes as they are in Workbench or Tina for example. Rather, they are dragged from the appropriate toolbox on the right-hand side of the screen, and dropped onto wires in the schematic as shown in Fig. 1. The various icons representing signal sources, probes, etc., are then edited by a menu like that shown in Fig. 2 to set up the required parameters.

If you are a first-time buyer, don't be

put off by the absence of virtual instruments. True, the symbol/menu method is less intuitive, and you will need to read the manual a little more. However, symbols and menus are easy to learn, and efficient in use. Some will

prefer this method.

Generally, the range and scope of the menu system was good, and not too complex.

Analysis graphs are placed directly onto, or over, the schematic drawing,

Fig. 3. Analysis graphs, like this one of input impedance, are drawn on the schematic drawing area at a size to suit the user.

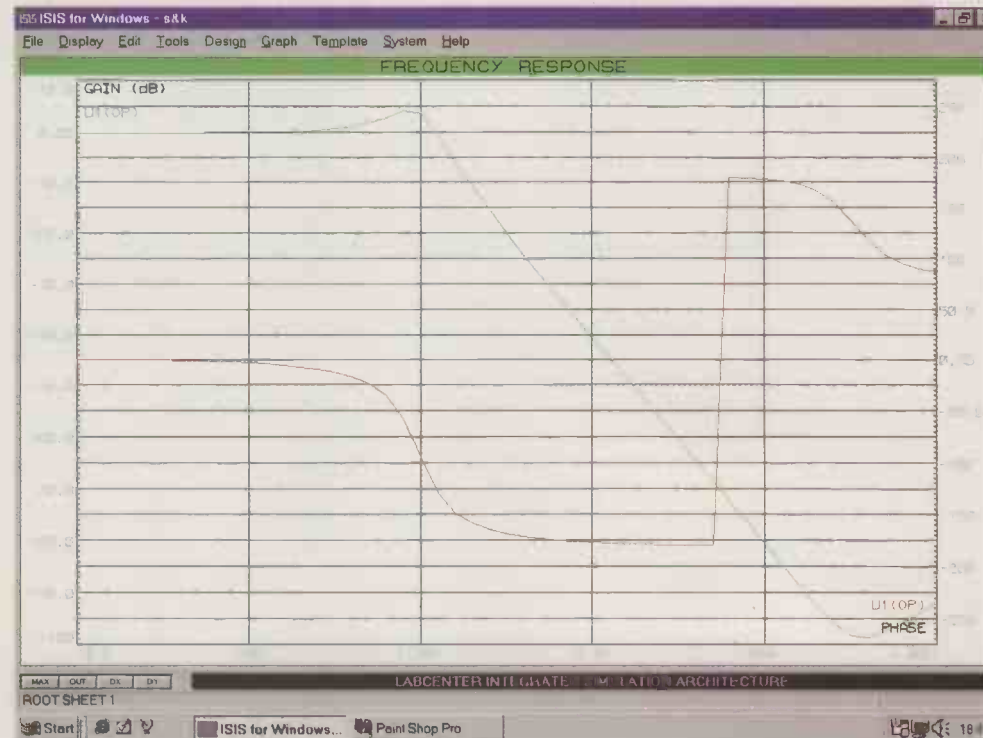
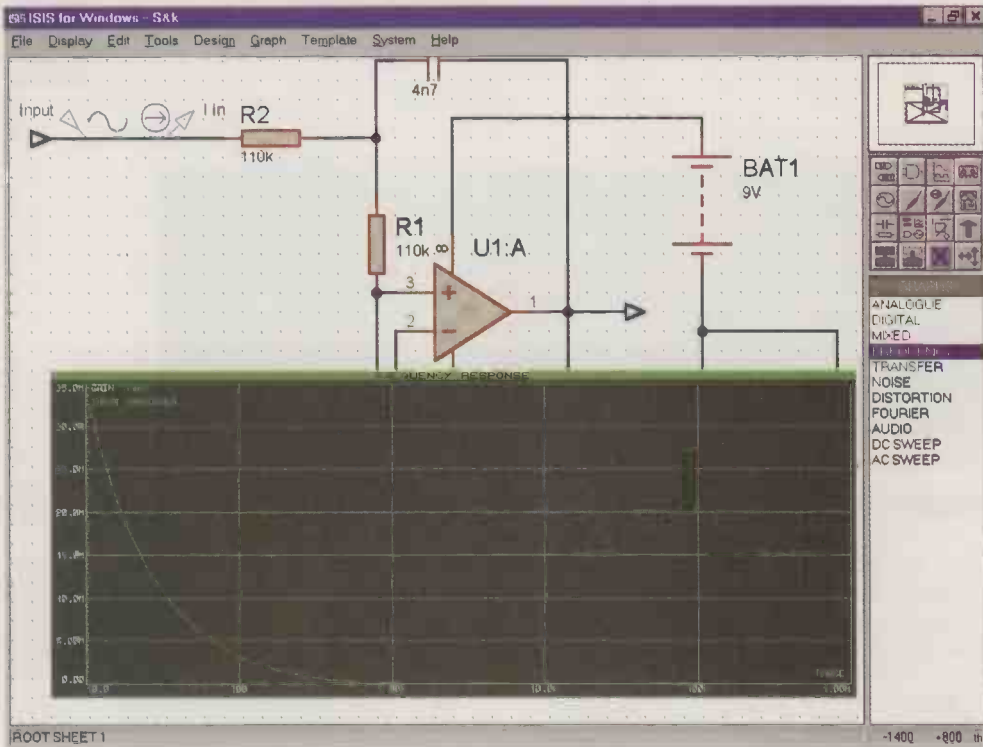


Fig. 4. Once you have produced your graph, in this case gain and phase, it can be run full-screen for closer examination or taking measurements.

Requirements

The Proteus software comes on a CD or six floppy disks. Installation is easy, with security by the registration name-and-number method.

This is a 32-bit program so runs naturally under Windows 95/98/NT. But it also runs under Windows 3.1 with the Win32s extension.

Labcenter has announced this is the last version that will run on Windows 3.1. All future versions will be for Windows 95/NT, or whatever OS Microsoft replaces them with.

A 50MHz 486DX with 12Mbyte RAM for Win3.1, or 16Mb RAM for NT are suggested as minimum hardware requirements. In addition, 20Mb of hard disk space is needed.

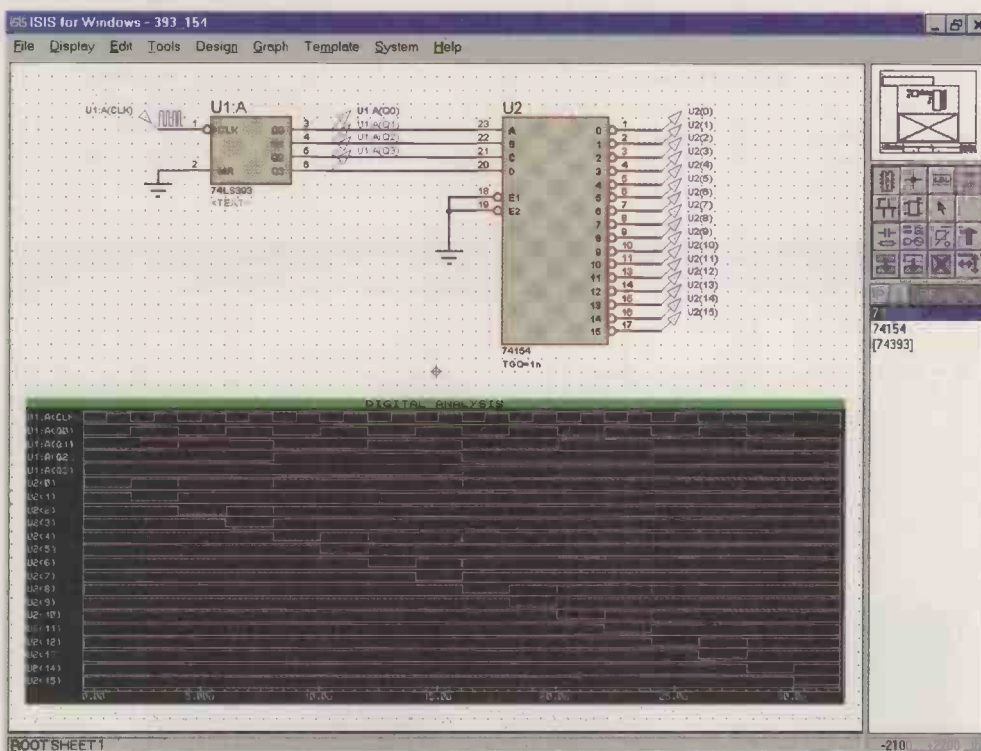


Fig. 5. A typical timing chart in digital analysis. Note the glitches. The glitch threshold time can be easily set in order to discriminate the various glitches by editing the properties of the devices in the schematic.

Fig. 3. First, the outline is drawn to whatever size and shape the user finds suitable. Conveniently, the graph is slotted into an unused corner of the drawing sheet, or over an unimportant part of the schematic. This is the opposite of other Windows programs, where you may get a pre-sized window after simulation, which you then have to resize and reposition.

For taking accurate measurements, the graphs can be expanded to full-screen as shown in Fig. 4.

Signals are extracted for analysis by attaching probes to schematic wires in the same way that icons are placed. The required analysis is picked from the menu bar and can be run from the menu system. For example, if you want a graph of amplitude and phase versus frequency, you click on 'graph' then use the menu to set the graph up.

There is often a choice of routes for manipulating the analysis. Some of the setting up is intuitive, but not all. For example, to set up the graph of Fig. 4, one voltage probe was dragged onto

the left 'y' axis to assign this to amplitude and another dragged onto the right to assign this to phase, to produce the familiar double graph. This method has to be learned from the manual, but once assimilated it is a rapid and adaptable system. Such methods are repeated throughout the program. They allow flexibility, but also demand a fairly steep learning curve.

Like CircuitMaker and Tina, Prospice can produce graphs of input and output impedance versus frequency, as Fig. 3 shows. The method used is indirect, but easy to apply.

There are two features that I found interesting. One is the ability to listen to audio frequency signals, providing your PC has a sound card. If you are working on music effects such as flanging or phasing, frequency shifting for public address, or audio filters, this could be very useful.

Another feature offers an easy way for a part of a circuit to be simulated in isolation. This is an advantage on large or complex circuits.

In digital analysis Prospice has a good method of allowing the operator to set the glitch threshold time. Having this control enables you to view only the glitches that you deem significant, avoiding the large numbers of small and unimportant glitches that some circuits produce when simulated. This avoids the idealised timing diagrams that other programs favour.

The digital analysis recognises strong high and low, weak high and low, floating, contention and three other states. Colours are allotted to the first six states so that they can be readily observed on the timing chart.

There are no concessions to education in Proteus. This is not to say it could not be used for teaching students in the later stages of their education. Indeed it would give them a good insight into a system they could be using for commercial designs in the outside world.

However, it is in the completeness and scope of the basic analyses where Prospice scores particularly well.

In summary

Once again, Labcenter has concentrated on the essentials and presented these in depth rather than providing a lot of peripheral features of marginal use. In doing so the company has produced an excellent all-round simulator.

You are unlikely to be in a position of needing a detailed basic simulation, but finding the program cannot do such a simulation. This is often the case with other programs in this sector of the market.

However, Prospice is not without its share of specialised features. The ability to listen to sounds is one example. Where these are provided though, they tend to have a strong practical purpose.

On the whole, Proteus has a moderately steep learning curve. This is offset by having the three functions of schematic drawing, simulation and pcb routing all in one program. As I have pointed out, this means you only have to learn one system of operation.

The Labcenter method of offering a range of prices for various versions of the program, limited by the number of pins or nodes it can handle, is a good one. It means that, even if you are on a strict budget, you can start small and still get all the basic simulations. If you want, you can spread the capital expenditure by choosing to upgrade at a later date.

In last month's review, of Tina, Figs 4 and 5 were transposed. Sorry. Ed.


Proteus

Produced and distributed by Labcenter Electronics, tel. 01756 753440, fax 01756 752857. Prices range from £295 to £1625 excluding VAT. Lower cost packages upgradable. E-mail info@labcenter.co.uk site address http://www.labcenter.co.uk.

RANGER

Too good for words

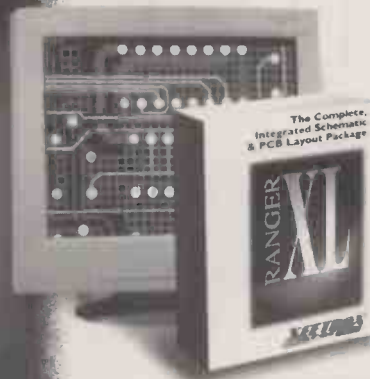The Complete Integrated Schematic PCB Layout Package



The New Ranger XL Series

- Ranger 2 for Windows £170
- NEW** Ranger 2XL £500
- NEW** Ranger XL from £950
- FREE** Website Download Demo



Email: sales@seetrax.com Website: www.seetrax.com

Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ
Tel: (44) 01730 260062 Fax: (44) 01730 267273

CIRCLE NO.122 ON REPLY CARD

HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS SCOPE FOR IMPROVEMENT!

PHILIPS PM3217 - Dual Trace 50MHz Delay
Very good oscilloscope including 2 probes, Pouch and Front Cover **£300**
Grey version not included. Probes etc from **£200**

GOULD OS300 Dual trace 20MHz. Lightweight. Very good value **ONLY £160**

THIS IS THE BEST CHEAP SCOPE YOU WILL EVER BUY!!!

GOULD OS1100 Dual trace, 30MHz delay, very bright. Supplied with manual and 2 probes. **£200**

TEKTRONIX 2215 - Dual Trace 60 MHz Sweep Delay, Includes 2 probes, Only **£350**

TEKTRONIX 400 SERIES

- 468 Digital Storage Dual Trace 100MHz Delay...£550
- 466 Analogue Storage Dual Trace 100MHz Delay...£250
- 485 Dual Trace 350MHz Delay Sweep...£750
- 475 Dual Trace 200MHz Delay Sweep...£450
- 465 Dual Trace 100MHz Delay Sweep...£350

HC 3502 5mV/20Div; 0.2u secs-0.5 Sec/Div; X-Y; X5 Magnifier; TVSync etc. Un-Used **£180**

TEKTRONIX 2445 4ch 150MHz delay sweep cursors readout **ONLY £700**

MARCONI 6311 Prog Sweep Gen 100MHz-20GHz...£4000
H.P. 8657A Syn Sig Gen 100KHz-1040MHz...£2500
H.P. 8656B Syn Sig Gen 100KHz-990MHz...£1500
H.P. 8656A Syn Sig Gen 100KHz-990MHz...£1250
GIGATRONIC 7100 Syn Sig Gen 10MHz-20GHz...£6000

MARCONI 2017 AM/FM Phase Locked Sig Gen 10KHz-1024MHz...£1200
PHILIPS PM5328 Sig Gen 100KHz-180MHz with 200MHz Freq Counter. IEEE...£650
MARCONI 6500 Amplitude Analyser...£2000
H.P. 4275A LCR Meter 10KHz-10MHz...£2750
H.P. 4192A LF Impedance Analyser 5Hz-13MHz...£5000

H.P. 8903E Distortion Analyser...£750
MARCONI 2305 Mod Meler 500KHz-2GHz from...£900
FARNELL AMM2000 Automatic Mod Meter 10Hz-2.4GHz Unused...£1250
STABLOCK 4015 Radio Comm Test Set...£2250
H.P. 5350B Freq Counter 20GHz...£2000
H.P. 346B Noise Source 10MHz-18GHz...£500
H.P. 11692D Dual Dir Coupler 2-18GHz...£1600
H.P. 11691D Dual Dir Coupler 2-18GHz...£1250
WAYNE KERR Inductance Analyser 3245...£2000
H.P. 8112A Pulse Generator 50MHz...£1250
DATRON AutoCal Multimeter 5 1/2-7 1/2 digit. 1065/1061A/1071...from £300-£800
RACAL 1998 Freq Counter 1.3GHz IEEE etc...£400
MARCONI 2440/2442 Freq Counter 20GHz/26GHz...from £1250

H.P. 8640A AM/FM Sig Gen 500KHz-1024MHz **£450**
500KHz-512MHz Version - £250

SPECTRUM ANALYSERS

- H.P. 8595E 9KHz-6.5GHz with Opts 004/041/101/105/110. 857171A card & 85024A high freq probe...£9000
- H.P. 8590A 10KHz-1.8GHz (75ohms)...£2250
- H.P. 8558B with Main frame 100KHz-1500MHz.£1250
- H.P. 853A (Dig Frame) with 8559A 100KHz-21GHz...£2750
- H.P. 3582A Dual Channel 25KHz...£2000
- MARCONI 2382 100Hz-400MHz High Resolution.£2250
- B & K 2033R Signal Analyser...£1500
- ADVANTEST TR4131 10KHz-3.5GHz...£3000
- MARCONI 2370 30Hz-110MHz...from £500
- HP141 Systems 8553 1KHz-110MHz from...£500, 8554 500KHz-1250MHz from £750; 8555 10MHz-18GHz...from £1000

MARCONI TF2015 AM/FM sig gen 10-520MHz **£175**

OSCILLOSCOPES

- RACAL 9008 Automatic MoD meter 1.5MHz-2GHz **£200**
- PHILIPS PM3082 2x2 Ch. 100MHz Delay etc...£900
- TEKTRONIX TAS465 Dual Trace 100MHz Delay etc...£900
- TEKTRONIX 2465A 4 Ch. 350MHz Delay etc...£2250
- TEKTRONIX 2445B Dual Trace 150MHz Delay etc...£1500
- TEKTRONIX 2205 Dual Trace 20MHz...£300
- KIKUSUI 6100 5 Trace 100MHz Delay...£425
- TEKTRONIX 2430 Dig Storage Dual Trace 150MHz...£1000

UNUSED OSCILLOSCOPES

- TEKTRONIX TD3350 Dual Trace 200MHz 1GS/Sec...£1500
- TEKTRONIX TAS485 4 Channel 200MHz etc...£1100
- H.P. 54610B Dual Trace 500MHz 20M/S...£2000
- H.P. 54600B Dual Trace 100MHz 20M/S...£1000
- GOULD 465 Dual Trace 100MHz 200M/S...£1400
- GOULD 400 Dual Trace 20MHz 100M/S...£800
- FLUKE SCOPEMETER Type 93 50MHz etc...£400
- FLUKE SCOPEMETER 96 Series II 50MHz etc...£520
- FLUKE SCOPEMETER 99 Series II 50MHz etc...£650

GOODWILL GFC 8010G Frequency Counter Range 1Hz-120MHz 8 digit display 15MV RMS sensitivity **Unused £75**

SPECIAL - LIMITED QUANTITY

MARCONI 2022E SYN AM/FM SIG GEN 10GHz - 1.01GHz
Up to +10dBm output, phase mod, LCD display, keyboard entry etc. Small, lightweight **only £525**

LOOK - NOW ONLY £475

MARCONI 2019A
Synthesised AM/FM Sig Gen 80KHz-1040MHz LCD Display Keyboard entry. **FULLY TESTED - IN GOOD CONDITION**

POWER SUPPLY Model HSP3010 0-30 volts; 0-10 amps current limiting. 2 meters **Used £160**

GOODWILL GVT427 DUAL CHANNEL AC MILLIVOLTMETER
10pV 300V in 12 ranges Frequency 10Hz-1MHz **Used £100 Unused £125**

FARNELL LF1 Sine/Sq Oscillator 10Hz-1MHz **£75**

GOULD J3B Sine/Square Oscillator, 10Hz-100KHz, low distortion **Only £95**

SOLATRON 7150 DMM 6.5 digit True RMS IEEE **£225**

A Classic Bench Multimeter - SOLARTRON 7045
4 1/2 digit bright LED, working with leads. **ONLY £30**
It's so cheap you should have it as a spare.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (0118) 9268041 Fax: (0118) 9351696
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

USED EQUIPMENT - GUARANTEED. Manuals supplied
This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

CIRCLE NO.123 ON REPLY CARD

Finishing off

Ian Hickman looks at some of the many ways a prototype or one-off instrument can be given a professional look without the expense of using professional techniques.

I have made a number of instruments for my own laboratory, and I have found that it is often possible to make them perform as well as expensive commercial equivalents, but at a fraction of the cost.

In the early stages of my career, I took a pragmatic view, being satisfied with the outcome however it looked, provided it functioned as desired. But for many years now, I have striven for a more professional looking finish. There are quite a few ways of achieving this and some of them are discussed below.

Working the enclosure

Unless you have a penchant for metalwork, and access to the necessary guillotine, bender etc, you will probably build most of your equipment in commercial ready-made cases. That way, whatever the innards may look like, you are guaranteed a professional finish, given only that the front panel legending is well laid out and neatly executed.

Legending can be done in various ways, of which one of the earliest was via 'Letraset'. This consists of rub-down lettering on transparent carrier sheets carrying letters, numbers and other symbols. Such sheets are available in various point sizes and colours, most commonly black.

With care and practice, a very neat front panel appearance can be created, on either metal or plastic surfaces. The art is to get all the letters of any particular legend exactly in line. This makes the process fairly time consuming, but that should not be a great problem for a one-off.

There are however one or two drawbacks to applying Letraset directly to a front panel in this way. The first con-

cerns durability; it is advisable to protect the lettering with a clear coating of some description.

Clear copal varnish has been used, brushed over each legend individually. But the various varnished areas are usually visible – especially after a while when the varnish has yellowed a little.

A better result is obtained by spraying the whole panel with an aerosol clear lacquer, I use RS stock No 567-480. This no longer appears in the current catalogue, having been replaced by clear lacquer 562-307. This newer spray should work as well as its predecessor, but I have not yet tried it. Alternatively, you could use clear acrylic lacquer 215-1217.

The second drawback concerns applying Letraset after an instrument has been built and tested. You are faced with an awkward choice. You can either dismantle the front panel controls, to enable the lettering to be applied in a straightforward manner to a flat surface, or you can try to work around projecting switch shafts, panel connectors, meters etc.

Dismantling the instrument can be undesirable for a number of reasons, but working round projections is extremely inconvenient, and furthermore requires masking of connectors, etc., when spraying lacquer.

Other panel techniques

Another very neat panel legending method that I have used in the past involved an RS photo-imaging system. This consisted of negative-working photo-imaging film 556-553, a choice of laminating film in various colours, and aerosol developer 556-610.

I used the white/yellow laminate 556-575 on an instrument of mine pub-

lished a while ago.¹ It resulted in smart yellow lettering on a black background.

Positive artwork of the required panel legend was used to expose the photo-imaging film, using e.g. the small RS ultra-violet exposure unit. The exposure time is not critical, and indeed contact printing using daylight is possible.

After exposure, the matt black side of the film is sprayed with the aerosol developer and left for 15 seconds. It is then washed off under running cold water, leaving clear lettering against a black background.

The developed film is dried and stuck to the double sided sticky laminating film, the white or yellow surface of the latter showing through as lettering at choice, against the black background. The other side fixes the finished artwork to the front panel of the instrument.

Alternatively, the developed film may be used as an intermediate artwork, to expose another sheet of the material. This gives four possibilities: white or yellow lettering on a black ground, or black lettering on a white or yellow ground.

The material does not seem to feature in the current RS catalogue. But it is so useful that I am sure it must be available from stockists of supplies for the graphics industries, along with laminating film of other two-colour combinations, giving a wide choice of lettering or background colouring.

If you make your own PCBs...

Speaking of UV exposure units, many of you are doubtless geared up for making your own PCBs. The same facilities can be used for making a front panel overlay. The result will be copper letters on a light brownish background

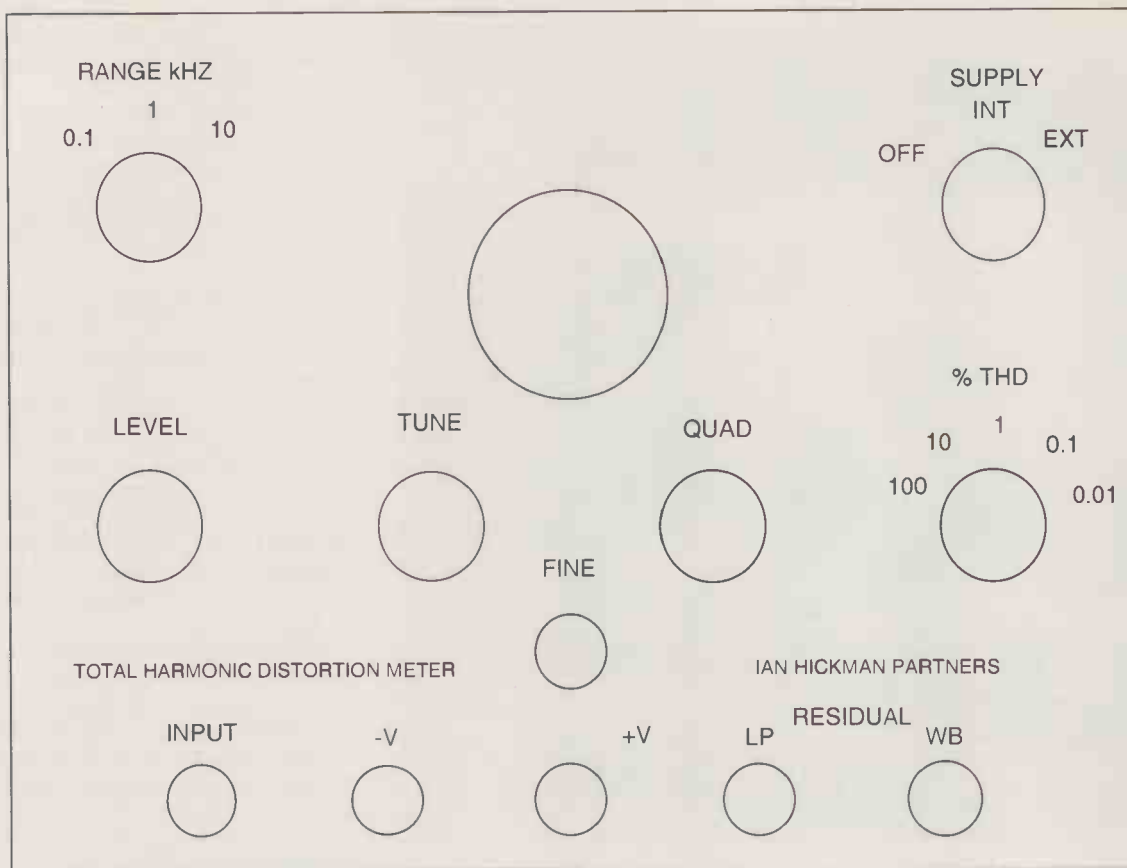


Fig. 1. The front panel of the THD Meter, shown 75% full size.

– assuming the common SRBP base material.

Tinning the letters then results in attractive silver lettering, which should then however be lacquer-sprayed to prevent tarnishing.* If single sided SRBP is used, the lettered panel can be secured to the metal front panel of the instrument by means of the nuts securing the bosses of switches, pots, coax sockets etc.

If double sided material is used, it can do duty as the front panel in its own right, the rear copper providing screening.

Sometimes the technique is useful for just a small subpanel, to hold a BNC socket the outer of which must be insulated from the instrument case, for example. The single-sided material can also carry the legend relating to the function of the socket.

However, where the legend is carried on the same artwork as the rest of the front panel, the easiest solution to use an isolated BNC socket is the ready made variety, such as RS stock No 456-706 (50Ω) or 456-946 (75Ω).

Or if you don't...

Those of you not yet into making your own PCBs might find a transfer system involving a photocopier more interesting.

This scheme makes use of a transfer medium, consisting of a clear plastic

carrier sheet, obtainable in A4 size from a UK supplier.² Onto this is printed the desired pattern, which should be in reverse, i.e. a mirror image. The printing is applied to the matt side of the sheet, which is indicated by its protective layer of paper.

The printed sheet is then laid onto the copper-clad board – which should be scrupulously clean – and the pattern is transferred under pressure and heat to the copper.

I have tried this material, transferring not a PCB pattern to copper-clad, but lettering onto a front panel. A little patience is needed to master the technique. If need be, any unsatisfactory results can be cleaned off the front panel with an organic solvent such as acetone (nail polish remover)† prior to repeating the operation.

While an ordinary domestic iron on its hottest setting can be used to apply both the heat and the pressure, a better scheme is to lay the panel on a hotplate and apply the pressure with a rubber roller. A suitable roller can be obtained, also from the company mentioned in reference 2.

Afterwards, the panel should be allowed to cool to room temperature, before carefully peeling off the clear carrier sheet. The finished lettering should be protected, either with one of the clear sprays already mentioned, self adhesive library film, or any other

suitable method.

One wonders if the special sheets obtainable from some colour printer manufacturers, for printing tee shirts for example, could also be used for this purpose. This would allow the front panel to be livened up using colours rather than black.

My current method

I used the following method just recently to legend the front panel of my total harmonic distortion meter.³

This instrument was housed in a case previously used for another design. As a result, the front-panel layout of the new instrument was constrained by the already existing holes.

In the event, just two new holes were needed, one for the 'fine' tuning control, and one to accommodate the barrel of the meter. The panel of the meter also covered two redundant holes from the earlier use.

Positions of all the holes to be used were measured and plotted on half centimetre squared paper. Fortunately it turned out that I had been quite methodical with the original construction, all measurements being sensible metric quantities.

As the panel drawing would have been a tight fit across an A4 page, it was drawn rotated through 90° to a sideways 'portrait' orientation.

The circles drawn on the paper were



Fig. 2. Completed battery-powered THD meter, showing the flying supply lead, via which the unit can alternatively be powered from an external source of ± 15 to 18V dc.

marked in at a suitable size to just clear the retaining nuts of rotary switches and pots, and the front-of-panel flanges of BNC sockets. This meant that later, applying the legending would require only the removal of knobs and the meter; the inconvenience of dismantling controls and sockets from the front panel being avoided.

The squared paper with its panel outline and hole positions was scanned in to my computer. It was exported from Paperport™ as a bit-mapped .BMP file, for use as a template in an Adobe Illustrator™ .AI file. Illustrator files are vector files similar to Corel .CDR and .WMF files, as opposed to bit map files like .bmp and .tif.

As Illustrator complained that the area was too large to load as a template, it was suitably reduced in size first, using Paintshop Pro™. Using the template as a guide, an Illustrator .AI file was created, showing the panel outline and the clearance holes.

The portrait panel drawing was then rotated through 90° so that the legending relating to the various controls and sockets could be added conveniently.

Afterwards, the drawing was rotated 270° to restore the portrait orientation. A copy was run off, and the panel outline dimensions as printed were measured. These were compared with the actual panel dimensions, and the .AI file scaled to restore the required drawing size, the result being as shown in Fig. 1.

Protecting the print-out

The final version of Fig. 1 was printed out on white paper, the front surface of which was sprayed lightly with 3M Spray Mount™ adhesive. After waiting the recommended few seconds to allow the surface to become tacky, the print was carefully laid down onto a blank view-foil sheet, as used for overhead projectors.

Next, with a surgical scalpel, the holes were cut out, the ones for the BNC sockets being slightly undersize. The holes for controls were less critical, being completely covered by the flanges of knobs.

The view-foil/paper composite was then cropped to size using a small guillotine I bought many years ago for photographic work. The composite was offered up to the instrument, and slight enlargement adjustments made to the holes for the BNC sockets, to suit.

Finally, the reverse side of the composite was sprayed and, when tacky, placed in position on the instruments front panel. The result is a neat appearance, with the legending protected from dirt and smudging behind the plastic sheet.

Like some of the other methods mentioned, this scheme blanks off and hides any redundant holes, which is particularly useful when you are reusing an enclosure. However, two of the holes in the front panel that I originally intended to hide were in fact equipped with BNC sockets labelled

-V and +V. These sockets are connected directly to the internal +18V and -18V battery supplies.

These sockets make it possible to measure the battery voltages with the instrument switched either on or off. The difference between the on and off voltages provides an indication of the state of the batteries.

A variant for plastic cases

I recently produced a special-to-type test box for a well known electronics company. This was built in one of the popular range of glossy grey ABS boxes, namely RS stock No 503-650.

The grey lid of the box, forming the front panel, was entirely acceptable aesthetically. It just needed legending added. So in this case, the front panel legending was produced as a .AI file, which was then reversed to give back to front lettering.

The legending was printed out on my Laserjet 5MP printer, on an overhead projector view-foil. The lettering thus looked the right way round when the foil was mounted on the front panel. Having the printing in contact with the panel protects it from dirt, abrasion etc.

A word of warning though. Do not use the grade of overhead projector foil sold for use in photocopiers. It might be alright, or it might result in an expensive repair. Be sure to use foil specifically stated as suitable for laser printers.

The foil could have been laid down as a whole, as described in the preceding section. However, this was another case where it was desirable to avoid dismantling the finished, tested product.


Most of the items on the front panel were LEDs, push-buttons, connectors etc., neatly arranged in rows. So instead of producing and fitting an overlay the size of the whole front panel, strips of the foil carrying the relevant legends were mounted where appropriate, as separate items, using 3M Spray Mount™ adhesive.

The result was a neat appearance produced in the minimum of time, the separate areas of foil with their bold lettering blending in almost invisibly with the light-grey front panel. ■

References

1. The EnviroSynth, Ian Hickman, *Maplin Magazine*, June 1992.
2. TEC 200 Image Film, obtainable from PSS Services Ltd, 217 Prestbury Road, Cheltenham, Gloucs GL52 3ES.
3. Measure THD below 0.001%, Ian Hickman, *Electronics World*, Aug. 1999, pp 626 - 633.

Frequency precision from DC to GHz

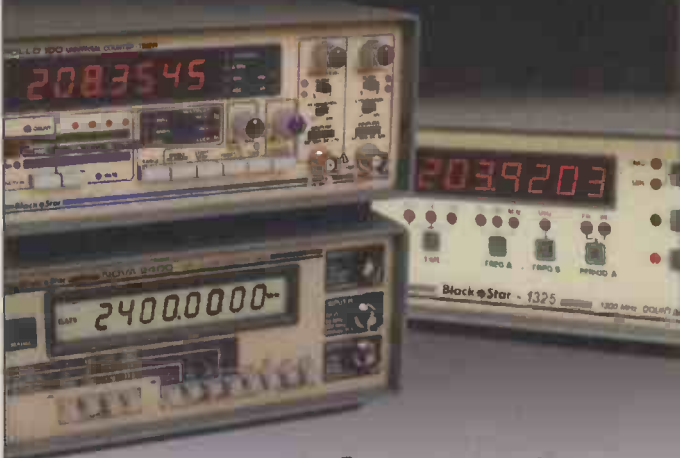

Black★Star

The Black Star range of frequency counters and universal counter timers provides precision measurement in both the time and frequency domains from dc up to 2.4GHz with the option of TCXO timebases.

The model 1325, for example, provides frequency or period measurement from 5Hz up to 1.3GHz using reciprocal measurement technology to give high resolution at all input frequencies. The 8 digit LED display is large and bright and the unit operates from AC line or batteries.

It costs just £165 +vat (or £179 with RS-232 interface).

Products illustrated:

- Apollo 100 - Universal 2 channel timer counter
- Nova 2400 - 2.4GHz 8.5 digit timer counter
- 1325 - 1.3GHz reciprocal measurement counter

To get full technical details and prices for the Black Star range of counters, please use the reply number below or contact us by 'phone, fax or Email.

Black Star is a TTI group company. All Black Star products are designed and manufactured in the U.K.

TTI Black★Star

Measurably better value

Black Star Instruments

2 Glebe Road, Huntingdon, Cambs. PE18 7DX
 Tel: 01480 412451, Fax: 450409, e-mail: sales@ttinst.co.uk
 Web Page: www.ttinst.co.uk/blackstar

THURLBY THANDAR INSTRUMENTS

CIRCLE NO.110 ON REPLY CARD

PIC BASIC



The new PicBasic Pro Compiler makes it even easier for you to program the fast and powerful Microchip Technology PICmicro microcontrollers. PicBasic Pro converts your BASIC programs into files that can be programmed directly into a PICmicro.

The PicBasic Pro Compiler features: BASIC Stamp I and II commands, direct and library routine access to pins on PORTA, C, D, E, as well as PORTB, arrays, real IF...THEN...ELSE and interrupt processing in BASIC.

The PicBasic Pro Compiler gives you direct access to all of the PICmicro registers - I/O ports, A/D converters, hardware serial ports, etc. - easily and in BASIC. It automatically takes care of the page boundaries and RAM banks. It even includes built-in commands to control intelligent LCD modules, I2C Read and Write. Serial comms to 19.2K, Smart Card routines are available.

The PicBasic Pro Compiler instruction set is upward compatible with the BASIC Stamp II and Pro uses BS2 syntax. Programs can be compiled and programmed directly into a PICmicro, eliminating the need for a BASIC Stamp module. These programs execute much faster and may be longer than their Stamp equivalents. They may also be protected so no one can copy your code.

The PicBasic Pro Compiler is a DOS command line application (it also works in Windows) and runs on PC compatibles. It can create programs for the PIC12C67x, PIC12CE67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 9xx, PIC16CE62x, PIC16F8xx and PIC17Cxxx microcontrollers and works with most PICmicro programmers including our EPIC Plus Pocket PICmicro Programmer. A printed manual and sample programs are included to get you started.

The PicBasic Pro Compiler can also be used inside Microchip's MPLAB IDE. This allows programs to be edited and simulated within Windows.



PIC BASIC (Basic Stamp I compatible) - £49.95
 PIC BASIC + EPIC programmer inclusive of utilities suite £84.95
 PIC BASIC PRO (Basic Stamp II compatible) - £149.95
 PIC BASIC PRO + EPIC programmer inclusive of utilities £184.95
 Upgrade PIC BASIC to PIC BASIC PRO £99.95
 EPIC PIC PROGRAMMER £49.95

Download full Compiler data sheet including manual from web site

Crownhill Associates Ltd

The Old Bakery, 54 New Barns Road, Ely
 Cambridgeshire CB7 4PW
 Tel: +44 (0)1353 666709 Fax: +44 (0)1353 666710
 E-mail: Sales@crownhill.co.uk
 www.crownhill.co.uk



ORDER via ON-LINE CATALOGUE

CIRCLE NO.111 ON REPLY CARD

Why Settle for AM when you can afford High Quality FM !

Transmitters & Transceivers

418, 433, 868 & 916MHz

Prices from £5.00

Made in UK

We can offer the lowest prices on high quality FM Radio Data Modules both in the UK and overseas !

Our qualified engineers offer full technical support from simple advice to system design & integration.

For a free catalogue, wall chart or quotation just e-mail sales@radtec.demon.co.uk, alternatively fax or telephone quoting ref: WWRM1



Telephone +44(0)1992 576107
 Fax +44(0)1992 561994
 http://www.radio-tech.co.uk

Radio-Tech Limited

Your official Radiometrix Distributor

CIRCLE NO.112 ON REPLY CARD

Reader offer - save over 45%

Radio-Tech's RTcom-Universal, available on 418MHz for the UK and 433.92MHz for Europe, is the easiest of wire-free modems to use. Simply plug one unit into one RS232 port and a second unit into another RS232 port and the two ports can then talk to each other at speeds of up to 19200 baud securely and without wires.

Serial data in gives serial data out, making the RTcom-Universal the ideal replacement for cabled point-to-point or star connected scanning cabled telemetry systems.

Units are fully approved and have EMC Class-1 type examination certificates.

The units normally sell for the trade price of £189.95 each + £10.00 carriage + VAT.

Radio-Tech is happy to offer a pair of these modems at the special price of £249.95 inclusive of postage, packing and VAT exclusively to readers of *Electronics World*. The offer is limited to one pair per person.

Send the coupon presented on this page to Radio-Tech at the address shown below, together with a cheque made payable to Radio-Tech Ltd, or send your credit card number, type and expiry date together with the address of the card holder.



Easy to use

Unlike other modems of this type, RTcom offers truly transparent operation. There are no buffers to introduce long delays so your receiving device can acknowledge receipt or reject errors within 5ms of the end of the data packet.

You can even avoid the cost of RS232 to RS485 conversion by using the RS232 port at one end and the RS485 at the other.

Frequency range	Approval	Country
418MHz, 0.25mW	MPT1340 UK	UK
433.92MHz 0.1mW	MPT1340/ ETS-300-220	UK, Europe

Radio-Tech Limited, Radio House, The Old Brewery, Lindsey Street, Epping, Essex. CM16 6RD
Telephone +44 (0)1992 576107
Fax +44(0)1992 561994
e-mail sales@radtec.demon.co.uk. <http://www.radio-tech.co.uk>

RTcom-Universal wire-free modem
normal price £469.90 per pair

Offer price £249.95 per pair
inclusive*

* limited to one pair per reader

COUPON

This coupon entitles the holder to one pair of RTcom-Universal wireless RS232 modems at the special all-inclusive price of £249.95.

- * Licence Exempt in the UK to MPT1340 & Europe and Scandinavia to ETS-300-220
- * Fully EMC Type Examined to ETS-300-683, Passed at Class 1 level.
- * RS232 + RS422 + RS485 interfaces, 2 or 4 wire operation, ESD and collision protected
- * 4800, 9600 and 19200 bps half duplex with on air encryption and code balancing
- * Transmission range from 25m to 100m depending upon antenna and topology
- * Less than 60mA for 7.5V to 15V d.c operation
- * Smart wall mounting enclosure with fixed 1/4 wave antenna.
- * Operates without need of special drivers. Compatible with protocols such as Modbus.
- * Automatic solid-state antenna switch for single antenna use.
- * Microcontroller with watchdog timer for added security.

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Potentiometers

Xicor has announced two non-volatile, digital potentiometers. The X9250 and X9258 are quad, 256-tap devices with a standby current of 1µA maximum. They can be used to preset analogue system values or trim offset voltages during manufacture. The settings can be made automatically. The circuit has long-term temperature and time stability.

Xicor
Tel: 01993 700544
Enquiry No 502

16-bit d-to-a converter

SPT has announced the SPT5510 16-bit digital-to-analogue converter. This 200MHz part has a settling time of 35ns to 16-bit accuracy and 15ns to 14-bit accuracy with glitch impulse energy of 30pV-s. Non-linearity is less than 1LSB typical INL and DNL. It comes in a 44-lead metric quad flat pack and works from -40 to +85°C.

Signal Processing Technologies
Tel: 001 719 528 2300
Enquiry No 503

Design software

Fast Analog Solutions has announced a version of its development software



with support for Windows NT for its Trac reconfigurable analogue circuit. The software has the look and feel of the existing versions, which support Windows 3.11, 95 and 98. It provides design and simulation tools, and lets designs be downloaded and uploaded to and from the device.
Fast Analogue Solutions
Tel: 0161 622 4567
Enquiry No 504

Dual UART

Philips Semiconductors has available the SC28L92 dual UART – the third member of its Impact line. It operates at 3.3 and 5V with the Intel or Motorola bus and supports commercial and industrial temperature ranges. The single-chip CMOS LSI chip provides two full-duplex asynchronous receiver and transmitter channels. It interfaces directly with microprocessors and can be used in polled or interrupt driven systems. It is a pin and function




equivalent to the company's other dual UARTs. Features include 16 character receiver, 16 character transmit first-in-first-out buffers, watchdog timer for each receiver, and a mode register. The chip comes in a 44-pin PLCC or PQFP.
Philips semiconductors
Tel: 00 31 40 272 2091
Enquiry No 506

ADSL chip set

Two fully-programmable DSP-based ADSL chip sets for central office and customer premises applications are available from Texas Instruments. Both use the firm's TMS320C6000 DSP core. The TNETD4000C supports four full-rate or G.lite ADSL lines in central office applications while the TNETD4000R is for equipment such as external modems and remote access routers.
Texas Instruments
Tel: 01604 663000
Enquiry No 508

Motor controller

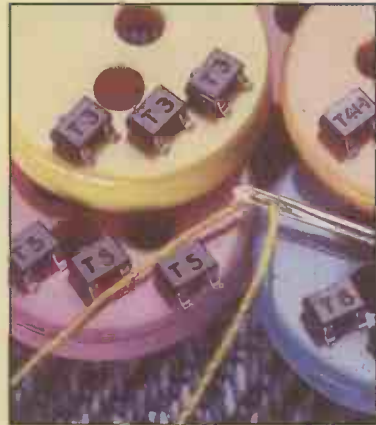Omnirel has introduced the OMC507 three-phase brushless DC motor controller. Rated at a 5A continuous average phase current, 10A peak for 10s and 28V DC bus voltage without needing a heatsink, the unit provides linear control of motor current (torque) in proportion to the input current command. The controller contains the power, driver and logic




RF transistors

Zetex has introduced RF transistors in SOT323 surface mount packages. Six NPN types are available, from the ZUMTS20 with a transition frequency of 450MHz to the ZUMTS17 at 1.3GHz. Power dissipation is 330mW at an ambient temperature of 25°C. Typical noise performance is 4.5 or 6.0dB. The ZUMT5179 has a maximum collector-base capacitance of 1pF at 1MHz. Maximum collector-emitter voltages are between 12 and 20V. Applications include RF security systems, crystal oscillators, FM tuners and IF amplification.
Zetex
Tel: 0161 622 4422
Enquiry No 505

Chip trio give voice to DSL

Ericsson has introduced three chips for voice over DSL, providing users with up to four additional telephone lines over their xDSL connection. The PBM 990 08/1 ATM multi-service chip handles circuit emulation for up to four POTS lines. The PBM 397 06/1 is a dual-channel PCM codec with on-chip DTMF support. The PBL 387 10/1 ring slicer is an analogue POTS interface, including voice, signalling and ringing. To incorporate them into existing data modems, no additional processing power is required because most of the ATM handling and circuit emulation are performed by the multi-service chip.

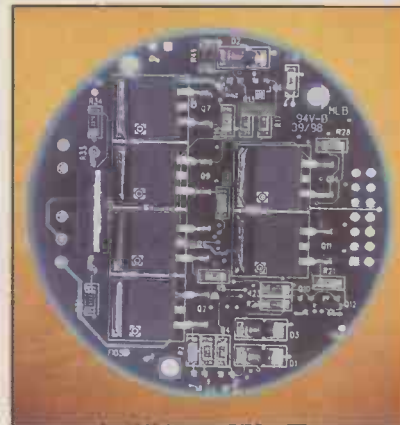Ericsson Microelectronics
Tel: +46 8 757 47 00
Enquiry No 501



Please quote *Electronics World* when seeking further information

analogue or TTL PWM input command, or an analogue command can be provided onboard.

Omnriel
Tel: 01435 867499
Enquiry No 509

Power relay

Matsushita has introduced the CP1-SA surface mount power relay for the automotive industry. Measuring 13 x 14 x 10.5mm, it has a nominal current rating of 20A at 14V DC, but it can switch 40A for up to two minutes.

Infineon Technologies
Tel: 01908 231555
Enquiry No 511



It works from 2 to 15V supply over a range of -25 to +55°C.
Infineon Technologies
Tel: 01252 811777
Enquiry No 512


IR sensor

Murata's IRA-E940ST1 IR sensor detects a moving human body using four 1.35 by 1mm sensing elements and two outputs with an OR-AND logic circuit. Applications are security systems, lighting and household appliances. Typical response at 1Hz is 5120V/W. Field of view is 50 x 55°.

D-sub connectors

Conec has developed D-subminiature combination connectors using planar technology to increase attenuation, reducing EMI and RFI. Attenuation is up to 45dB at 100MHz and 90dB at higher frequencies. Standard peak capacitance is 360pF. Voltage capability is up to 1500V DC as standard and up to 2500V DC as an option. There are five shell sizes and various signal, power and coaxial pin combinations. Power pins are rated at up to 40A with AWG8 contacts.

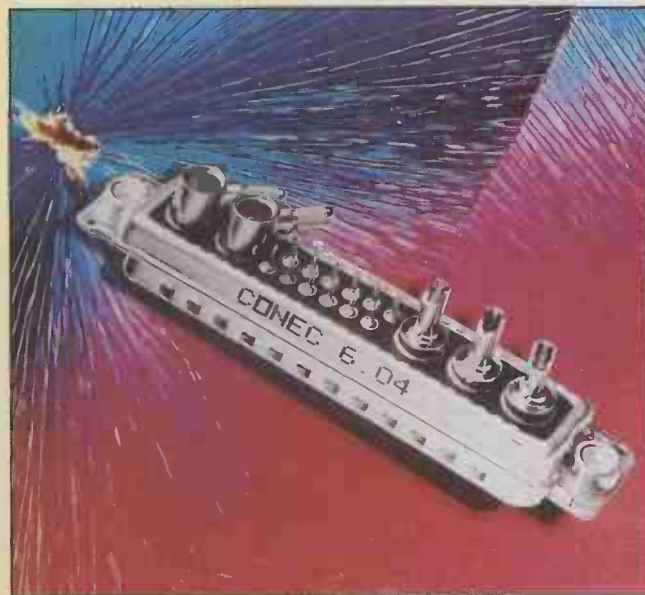Infineon Technologies
Tel: 01344 396313
Enquiry No 510



GTLT clock driver

Fairchild Semiconductor's latest addition to its GTLP portfolio is a low drive clock driver that is a device capable of LVTTTL to GTLP (and vice versa) signal level translation in the same package. The device is designed for high-speed performance in back-plane and bus applications in data networking and telecoms. The GTLP6C817 is designed with internal edge-rate control and is process, voltage, and temperature compensated. The device also features 50mA GTLP drive capability and bi-directional LVTTTL to GTLP signal level translation.

Fairchild Semiconductor
Tel: 01793 856811
Enquiry No 514

0.5 to 2.5GHz amplifier

Maxim's latest wideband buffer amplifier provides dual open-collector outputs capable of delivering -5dBm while maintaining harmonic suppression of better than -25dBc. The dual output of the MAX2472 makes these devices suitable for simultaneously driving two mixers, or a mixer and a PLL, according to the company.

There is also a single open-collector output version (MAX2473) with an



Modem chip set for VDSL

Infineon has introduced a modem chip set for the VDSL standard, using frequency division duplexing (FDD). VDSL over conventional twisted-pair copper provides symmetrical and asymmetrical data transmission up to 13Mbit/s. Based on the firm's Potswire technology, the three-device chip set uses FDD and QAM line code to handle POTS and ISDN services on the same twisted pair and XDSL services on the same bundle. It can also be configured to support spectral compatibility with amateur radio. The chip set comprises the PEB22810 VDSL line driver, the PEB22811 VDSL analogue IC and the PEB22812 digital IC. The analogue IC handles analogue-digital conversion, pre and post filtering and power control, including a power down mode with warm-start capability in less than 100ms.

Infineon Technologies
Tel: 01344 396313
Enquiry No 507

added feature of a bias control pin to vary the output power as needed to save current. Output power can be adjusted from -10dBm to -2dBm while maintaining harmonic suppression of better than -25dBc. Both amplifiers operate over a 500MHz to 2500MHz frequency range providing 12dB gain and greater than 40dB isolation at 900MHz.

Maxim
Tel: 0118 930 3388
Enquiry No 515

2.5Gbit/s I/O driver cores

LSI Logic claims that its current generation of Gigablaze integrated gigabit per second CMOS transceiver cores support the physical requirements of next generation I/O (NGIO). The cores meet NGIO's double-speed serial transfer rate of 2.5Gbit/s. The transceiver cores can be integrated into system-level Asics. The firm's I/O cores were the basis of a number of Fibre Channel and Gigabit Ethernet products and it claims they will play their part in the volume launch of NGIO products.

LSI Logic
Tel: 01344 413204
Enquiry No 516

2.5Gbit/s SONET/SDH interface

Vitesse's latest chip set implements a 2.5Gbit/s channelised SONET/SDH interface for ATM, packet-over-SONET and SONET/SDH transmission equipment. The V-Frame 2.5/SLT offers full SONET/SDH section and line termination, including byte interleaving/de-



interleaving and multiplexing/demultiplexing functions. The chip set is the second group of products in the company's V-Frame 2.5 family. It includes the VSC9111, a section/line terminator, which acts as the framer, and the VSC8140 16-bit transceiver with integrated clock generation capabilities. Both chips work from a single 3.3V supply rail.

Vitesse
Tel: 01634 863494
Enquiry No 517

Switched regulator

National Semiconductor has launched its first dual output switched capacitor regulator designed for portable communications applications. The device integrates a switched capacitor doubler, a low-dropout (LDO) regulator and a switched capacitor

Those
Engineers Ltd



Version 2
now on
sale

It is terrific!
What POWER!
What ALSO!

Spicycle™

The World is onto Spicycle!

Jump onto the future today - tomorrow's electronic design software tools from the U.K.'s leading simulation engineers.

- Schematic editing with TrueType fonts
- Drag and drop from component bins
- Analogue + mixed mode digital simulation with SPICE and extended algebraic functions
- PCB layout facilities - optional extra
- PCB facilities include regional DRC, copper fill, BOM, ratsnest connectivity from schematic
- CAM outputs (printer, plotter, drill and Gerber)
- Re-use existing PCB layouts with Gerber import
- Hook up the simulator directly to PCB for the ultimate in design validation
- Back annotation from simulator to schematic
- Library includes electronic + mechanical engineering behavioural devices
- Convert SPICE net lists into ratsnestrated schematic - reverse engineering made easy
- Upgrade path for existing customers - competitive upgrades available.

Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP. Tel +44 (0) 20 8906 0155

FAX +44 (0) 20 8906 0960

e-mail sales@Those-Engineers.co.uk

web http://www.spiceage.com

CIRCLE NO.124 ON REPLY CARD

TELFORD ELECTRONICS

Old Officers Mess, Hoo Farm, Humbers Lane
Horton, Telford, Shropshire TF6 6DU, UK
Phone: (00 44) 01952 605451 Fax: (00 44) 01952 677978
e-mail: telfordelectronics@telford2.demon.co.uk
Web: http://www.telford-electronics.com
Carriage: £10+VAT @ 17.5% to be added to all UK orders
Overseas orders welcome - Please call

ALL OUR EQUIPMENT HAS A 30 DAY GUARANTEE
We now accept all major credit cards - Visit our NEW Web Site

MISCELLANEOUS

Fluke 45 Dual Display Multimeter.....	£350.00
Fluke 77 Multimeter.....	£55.00
Fluke 79 Multimeter + Capacitance.....	£88.00
HP B157A Optical Attenuator 1300/1550nm HP1B.....	POA
HP 8447F Power Amplifier.....	£600.00
Megger Pat Tester.....	£300.00
Megger B15 Digital Milliohm Meter.....	£500.00
Megger F14 Flash Tester.....	£400.00
Philips PM6303 Automatic RCL Meter.....	£400.00
Philips PM6305 Programmable Automatic RCL Meter.....	£900.00
Philips PM6306 Programmable Automatic RCL Meter.....	£1,800.00
Quartzlock 2A Off Air Frequency Standard 1, 5 & 10MHz.....	£275.00
Tektronix AS5029 Isolator.....	£600.00
Tektronix AM503A Current Probe + A6303 Probe + TMS02A.....	£1,200.00
Tektronix CT4 Current Probe.....	£500.00
Voltech PM100 Single Phase Power Analyzer RS232.....	£650.00
Wayne Kerr 4225 RCL Bndge.....	£400.00

POWER SUPPLIES

EMS 600V 5A DC Power Supply.....	POA
Farnell 30/100 30V 100A.....	£700.00
Farnell 60/25 0-60V 0-25A Metered.....	£400.00
Farnell L30BT 0-30V 0-1A x 2.....	£75.00
Farnell L30DT 0-30V 0-2A x 2.....	£85.00
Farnell TSV70 Mk2 Stabilised Power Supply.....	£180.00
General Radio 1265A DC Power Supply 0-400V 0-5A.....	£475.00
HP 6050A System DC Electronic Load.....	£700.00
HP 6181C DC Current Source 0-100V 0-250mA.....	£300.00
HP 6264B 0-20V 0-20A.....	£250.00
HP 6623A System DC Power Supply.....	£1,400.00
HP 6634A Systems DC Power Supply 0-100V 0-1A 100W.....	£550.00
Philips PE1642 0-20V 0-20A.....	£150.00
Power Ten 0-30V 0-60A.....	£300.00
Powerline LAB10 0-30V 0-10A.....	£300.00
Powerline LAB32 5V-5A, 15V-0.5A, -15V-0.5A, 0-30V-2A.....	£200.00
Powerline Electronics 0-70V 0-10A.....	£175.00
Sorenson 600V 16A DC Power Supply.....	POA
Thurlby Thandar PL3300P 32V 3A x 2 GPIB-RS232 DC Power Supply.....	£350.00
Thurlby Thandar PL3300V/D 32V 3A x 2.....	£150.00
Thurlby Thandar TS15425 15V 4A x 2.....	POA
Thurlby Thandar TS30225 30V 2A x 2.....	£150.00
Thurlby Thandar TSX3510P Programmable DC Power Supply 35V 10A GPIB-RS232.....	£350.00

SIGNAL ANALYZERS

Advantest TR4133 100MHz-20GHz Spectrum Analyzer.....	£5,000.00
Anritsu MSS55A2 Radio Communications Analyzer 25MHz.....	£2,500.00

1GHz.....	£1,200.00
Anritsu MS620 Spectrum Analyzer + Tracking Generator 0-1.7GHz.....	£1,900.00
B&K 2033 Signal Analyzer.....	£2,000.00
B&K 2636 Measuring Amplifier.....	£2,500.00
B&K 5935 Dual Microphone Supply.....	£650.00
HP 16508 Logic Analyzer.....	£900.00
HP 334A Distortion Analyzer.....	£250.00
HP 339A Distortion Measuring Set.....	£1,800.00
HP 3561A Dynamics Signal Analyzer.....	£3,750.00
HP 3580A 25kHz Spectrum Analyzer.....	£600.00
HP 3588A 10Hz-150MHz Spectrum Analyzer.....	POA
HP 4193A Vector Impedance Meter.....	£5,000.00
HP 432A Power Meter + HP478A Sensor.....	£250.00
HP 435B Power Meter + HP481A Sensor.....	£500.00
HP 436A Power Meter.....	£700.00
HP 5370A Universal Counter/Timer.....	£850.00
HP 8756A Scaler/Network Analyzer.....	£950.00
HP 8901A Modulation Analyzer.....	£1,500.00
HP 8903B Audio Analyzer.....	£2,500.00
HP 8980A Vector Analyzer.....	£5,000.00
IFR A7550 1GHz Portable Spectrum Analyzer.....	£1,500.00
Marconi 2305 Modulation Meter.....	£2,000.00
Marconi 2370 110MHz Spectrum Analyzer.....	£600.00
Marconi 2501 True RMS Voltmeter.....	£500.00
Marconi 2950 Radio Comms. Test Set.....	£1,500.00
Marconi 6950 Power Meter + 6910 Sensor up to 20GHz.....	£300.00
R&S URE RMS Voltmeter.....	£250.00
R&S ZPV3E 3-2GHz Vector Analyzer.....	£1,800.00
R&S ZW08E Network Analyzer opt. B2, B5 & B7.....	POA
Schlumberger 9702 Spectrum Analyzer 0.1-100MHz.....	£1,250.00
Schlumberger SI4031 Stabilock Communications Test Set.....	£3,000.00
Smith Myers AR1775 Portable Cellular Tester.....	£1,500.00
Tekneda Rikn TR4172 Spectrum/Network Analyzer 1.8GHz.....	£6,500.00
Tektronix DA4084 Programmable Distortion Analyzer.....	£700.00
Wayne Kerr 3245 Precision Inductance Analyzer.....	£3,000.00
Wayne Kerr AMM2000Q2 Automatic Modulation Meter.....	£1,100.00

SIGNAL GENERATORS

Adret 7100B 300kHz-650MHz.....	£700.00
Cushman CE12 Two Tone Generator.....	£150.00
Finn DG52 0.1MHz-110kHz Synthesized.....	£185.00
Finn 437 1A 12-18GHz.....	£50.00
Fluke 6010A 10Hz-11MHz Synthesized.....	£175.00
HP 11710B Down Converter (HP8640B).....	£275.00
HP 11715A AM/FM Test Source.....	£650.00
HP 214B Pulse Generator 100V 2A.....	£1,200.00
HP 3325A 1Hz-21MHz Synthesized.....	£1,250.00
HP 3326A Two Channel Synthesizer.....	£5,000.00
HP 3335A Synthesizer/Level Generator HP1B.....	£2,500.00

HP 4204A 10Hz-1MHz Oscillator.....	£125.00
HP 654A 10MHz Test Oscillator.....	£225.00
HP 8005B 0.3Hz-10MHz.....	£300.00
HP 8008A 10Hz-200MHz.....	£450.00
HP 8015A 1Hz-50MHz Pulse.....	£450.00
HP 8091A/8092A/8093A (2) 1GHz Pulse Generator.....	£650.00
HP 8111A 20MHz Programmable Pulse Generator.....	£800.00
HP 8116A 50MHz Pulse/Function Generator HP1B.....	£2,500.00
HP 8165A Programmable Signal Source.....	£1,200.00
HP 8175A Digital Signal Generator.....	£2,000.00
HP 8642M 0.1-2100MHz.....	£12,500.00
HP 8657A 0.1-1040MHz.....	£2,800.00
HP 8657B Signal Generator 0.1 to 2060MHz.....	£4,000.00
HP 8660D Synthesized Signal Generator 1 to 1300MHz HP1B.....	£2,250.00
HP 8672A Synthesized Signal Generator 2-18GHz.....	£4,850.00
HP 8694B 5-4-12.5GHz.....	£1,950.00
Marconi 2015 10-520MHz.....	£1,100.00
Marconi 2019A 80kHz-1040MHz.....	£1,000.00
Marconi 2022A 10kHz-1GHz.....	£1,300.00
Marconi 2022D 2GHz Signal Generator.....	£1,650.00
Marconi 8057 5-5-8.5GHz Signal Source.....	£200.00
Marconi 6059A 12-18GHz Signal Source.....	£200.00
Philips PM4150 Arbitrary Waveform Generator 20Ms/s.....	POA
Philips PM5766B Pulse Generator 1Hz-125MHz.....	£1,250.00
R&S AFG Function Generator 20MHz.....	£2,000.00
R&S SMLU Power Signal Generator 25MHz to 1GHz Output: 330bm (2W).....	£1,900.00
R&S SMPD Signal Generator 5kHz-2750MHz.....	£3,750.00
R&S SPF2 Digital Video Test Signal Generator.....	£3,000.00
Racal 9053 Two Tone.....	£120.00
Racal Dana 3083 Two Tone Signal Source.....	£275.00
Systrom Donne 1702 Audio-1GHz.....	£600.00
Systrom Donne 1720 50MHz-18GHz Signal Source GPIB.....	£2,000.00
Tektronix 504 0.001-240MHz.....	£250.00
Tektronix FG501A 2MHz Function.....	£250.00
Tektronix PG506 Time Mark Generator.....	£500.00
Thurby Thand TG230 2MHz Sweep/Function Generator.....	£140.00
Wavetek 1080 1-1000MHz Sweeper.....	£300.00
Wavetek 157 Programmable waveform.....	£150.00
Wavetek 159 Waveform Generator 1Hz-3MHz.....	£300.00
Wavetek 171 Synthesizer.....	£400.00
Wavetek 185 Sweeper/Function 0-5MHz.....	£350.00
Wavetek 2001 1-140MHz.....	£600.00
Wavetek 307A 7-12.4GHz.....	£900.00

OSCILLOSCOPES

Fluke 105B Scopemeter 100MHz.....	£1,000.00
Fluke 96 Scopemeter 50MHz (AS NEW).....	£550.00
Fluke 98 Series 2 Automotive Scope Meter/Lab Scope.....	£700.00
Fluke 99 Scopemeter Series 2 50MHz.....	£500.00
Gould (RTO) 350 50MHz Oscilloscope.....	£200.00
Gould 4072 400Msec 100MHz Digital Storage.....	£750.00
Gould 5110 100MHz Intelligent Oscilloscope system.....	£400.00
Gould OS200 20MHz.....	£720.00
Hitachi V-250F 60MHz Oscilloscope.....	£200.00
Hitachi V352F 35MHz Oscilloscope.....	£175.00
Hitachi VC222 20MHz.....	£225.00
Hitachi VC6015 Digital Storage.....	£300.00
HP 1222A 10MHz Oscilloscope.....	£100.00
HP 1720A 275MHz 2 Channel.....	£500.00
HP 1727A 275MHz Storage Oscilloscope.....	£250.00
HP 1740A 100MHz 2 Channel.....	£200.00
HP 1741A 100MHz Storage 2 Channel.....	£200.00
HP 1741A 100MHz Storage 2 Channel.....	£220.00
Iso-Tech ISR640 40MHz.....	£200.00
Kikusui COS5040 40MHz Oscilloscope.....	£160.00
Kikusui COS5041 40MHz Oscilloscope.....	£160.00
Kikusui COS5100 100MHz Oscilloscope.....	£275.00
Kikusui COS56100 100MHz Oscilloscope.....	£275.00
Philips PM3214 0-25MHz Oscilloscope.....	£100.00
Philips PM3234 0-10MHz Oscilloscope.....	£80.00
Philips PM3262 100MHz.....	£250.00
Philips PM3264 100Hz Oscilloscope.....	£300.00
Philips PM3267 100MHz Oscilloscope.....	£300.00
Philips PM3305 35MHz.....	£250.00
Philips PM3311 0-60MHz.....	£200.00
Philips PM3325A 60MHz Digital Storage.....	£1,000.00
Philips PM 3335 60MHz 20Ms/s Analogue and Digital.....	£500.00
Philips PM 3340 2GHz Oscilloscope.....	£4,000.00
Philips PM3325A 50MHz Storage.....	£300.00
Tektronix 2205 20MHz 2 Channel.....	£175.00
Tektronix 2215 60MHz.....	£300.00
Tektronix 2225 50MHz.....	£350.00
Tektronix 2235 100MHz.....	£500.00
Tektronix 2236 110MHz.....	£500.00
Tektronix 2245A 100MHz 4 Channel on screen cursors.....	£800.00
Tektronix 2336 100MHz.....	£500.00
Tektronix 2465/AB/CT 300MHz (4).....	From £1,500.00
Tektronix 434 Storage.....	£150.00
Tektronix 465 100MHz.....	£250.00
Tektronix 465B DC-100MHz.....	£225.00
Tektronix 468 100MHz Digital Storage.....	£350.00
Tektronix 475 200MHz.....	£350.00
Tektronix 7192 10MHz 2 Channel Storage.....	£1,100.00
Tektronix TA5455 60MHz Dual Channel.....	£700.00
Tektronix TA5475 4 Channel 100MHz.....	£500.00
Tektronix TD5302 2 Channel 100MHz 50Ms/s.....	£900.00
Tektronix TD5460 4 Channel Digitizing Oscilloscope 350MHz 100Ms/s GPIB + VGA.....	£2,250.00
Tektronix TD540 4 Channel 500MHz 1Gs/s VGA + GPIB.....	£3,250.00

MICROWAVE


Digital Microwave Transmitter/Receiver 12GHz.....	£1,200.00
HP 8405 Vector Voltmeter.....	£250.00
HP 8502A Transmission/Reflection Test Set 500kHz-1.3GHz.....	£750.00
HP 8743B Reflection Transmission Test Unit 2-12.4GHz.....	£800.00
HP 11720A Pulse Modulator 2-18GHz.....	£720.00
HP 11722A System Module.....	£600.00
HP 11691D Directional Coupler.....	£600.00
HP 11692D Directional Coupler.....	£700.00
HP 3350 120dB Attenuator DC-16GHz.....	£300.00
HP 11752A Directional Coupler 3dB.....	£150.00
HP 8414A.....	£175.00
HP K3E2A Variable Attenuator 0-50dB 8.2-12.4GHz.....	£120.00
HP 33304A Programmable Attenuator 18GHz 0-11dB.....	£175.00
HP 33305A Programmable Attenuator 18GHz 0-110dB.....	£175.00
HP 33306A Attenuator 11dB.....	£250.00
HP 33308 Attenuator 21dB.....	£250.00
HP 33322A Attenuator 12dB.....	£250.00
HP 532B Frequency Meter.....	£250.00
HP 536A Frequency Meter 3.7-12.4GHz.....	£200.00
HP 54111A 2GHz S/S Test Set.....	£560.00
JFW Stepped Attenuator 0.9dB In. 2dB steps DC-2GHz.....	£65.00
JFW Stepped Attenuator 0.10dB In. 1dB steps DC-2GHz.....	£65.00
Semi-Rigid UT1141A Co-Axial Cable 0-20GHz 3 meter length.....	£10.00

COUNTERS

EIP 575 Source Locking Counter 10Hz to 18GHz.....	£900.00
Fluke 164 Multi-Function Counter 160MHz.....	£600.00
HP 5335A Universal Counter HP1B.....	£600.00
HP 5342A 18GHz Frequency Counter.....	£800.00
HP 5370A Universal Time Interval Counter DC-500MHz.....	£350.00
HP 5384A Frequency Counter 10Hz to 225MHz HP1B.....	£475.00
Philips PM6665 Timer/Counter 120MHz GPIB.....	£350.00
Philips PM6666 Timer/Counter Opt C fitted.....	£650.00

CIRCLE NO.125 ON REPLY CARD

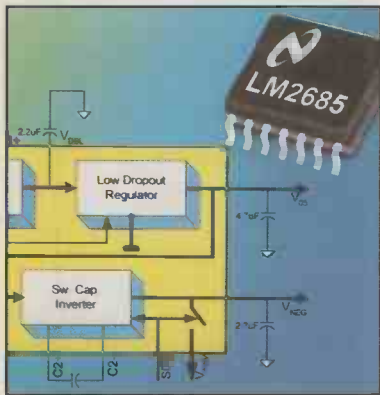Please quote *Electronics World* when seeking further information



inverter in a low profile, TSSOP-14 package. The LM2685 provides a dual output (+5V regulated and -5V unregulated) power supply by using switched capacitor and LDO techniques. The +5V regulated power supply is required for components such as audio codecs, amplifiers and SIMs. The -5V can be used for contrast bias for LCDs, and to increase the dynamic range of operational amplifiers used for analogue inputs.

National Semiconductor
Tel: 01634 863494
Enquiry No 518

Voltage regulator with enable

Low dropout voltage regulators from Semtech, designated the SC1540 and SC1540A are 300mA and 500mA

regulators with the new feature of an enable pin. This allows the user to turn on or turn off the regulator as required. This feature can be used to turn on voltage rails in a determined order to ensure start-up sequences are followed, or to turn a voltage rail off for power saving in perhaps a battery powered application.

Thame Components
Tel: 01844 261188
Enquiry No 519

In-circuit test platform

GenRad has enhanced its GR TestStation in-circuit test platform which can be configured from 256 to 7680 pins. Evolved from GenRad's GR228X technology the TestStation can be populated with any of the current CR228X pin cards or with the company's Ultra 121 all-real pin card. Existing CR228X fixtures and programs are fully compatible. The TestStation can be re-configured by adding modules to increase node count up to 7680 pins, or to populate the system with the Ultra 121 pin card.

Genrad
Tel: 00 49 89 96285 303
Enquiry No 520

Current transducer

Electrically isolated measurements of DC, AC or complex waveforms currents can be accomplished with the HAS series of open-loop current transducers from LEM. There's a choice of nominal currents ranging

from 50A to 600A and a measuring range of up to ±1% with a response time of less than 3µs. Overload currents outside the recommended



measuring range are accepted without damage to the transducer, making the range suitable for current control or protection in many industrial applications.

LEM
Tel: 00695 720777
Enquiry No 521

CMOS IC targets hands-free phone

Austria Mikro Systeme's programmable chip for hands-free speaker phones is a mixed-mode CMOS integrated circuit for analogue telephones incorporating hands free speech circuit, CPU/dialler and tone ringer all in a 44 pin TQFP. The AS2525's software programmable

BACK ISSUES

Back issues of Electronics World are available, priced at £3.00 UK and £3.50 elsewhere, including postage. Please send your order to Electronics World, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Available issues

1994	1996	1998
January	January	February
April	February	March
May	March	April
July	May	May
August	June	June
November	July/August	July
December	September	August
	October	September
	November	December
1995	1997	1999
February		January
April	June	February
May	August	March
June	September	April
August		May
September		June
October		July
December		August

Flash/SRAM on one BGA


STMicroelectronics has introduced a device consisting of 8Mbit flash and 1Mbit SRAM in a single BGA48 chip scale package. The M36W108A's footprint of 12 x 10mm occupies around 60 per cent less space than separate flash and SRAM devices, according to the supplier. The flash memory is functionally identical to the firm's M29W008A device and is organised as 1Mbit x 8 in a boot block configuration and the device is available with Top and Bottom boot block options. Operation is from a single 2.7 - 3.6V supply, with the high voltage required for erasure and programming being generated internally. The flash memory includes a Security Protection area factory-programmed with 256bytes of ID. The SRAM component is a 128k x 8-bit SRAM with fully static operation requiring no external clocks or timing signals and with equal address access and cycle times.

STMicroelectronics
Tel: 01628 890800
Enquiry No 513



FM Embedded Controllers at a ground breaking price!

WEB SITE
<http://www.cms.uk.com>

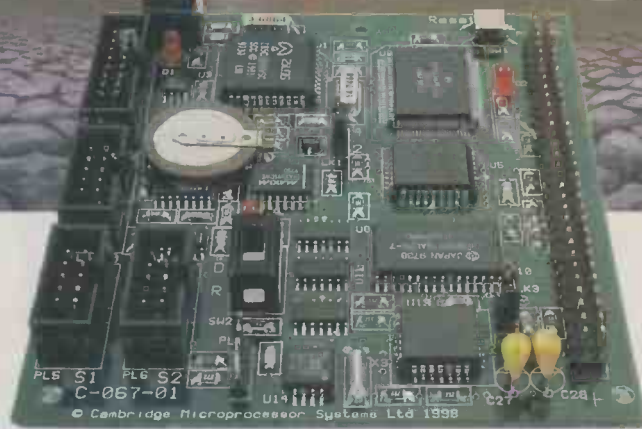

£95 each
PER 100 UNITS

The range of 'FM-Controllers' provide most of the features required for embedded control at a very low cost

FEATURES FM-200 Controller

- ◆ 68K Micro-Controller 14 MHz clock
- ◆ 512 Kbytes Flash EEPROM
- ◆ 512 Kbytes SRAM Battery Backed
- ◆ 2 RS232 Serial Ports
- ◆ 1 RS232/RS485 Serial Port
- ◆ Real Time Calendar Clock (Y2K Compliant)
- ◆ Watchdog & Power fail detect
- ◆ 10 Digital I/O Lines
- ◆ 2-16 bit Counter/Timers
- ◆ I²C Bus or M-Bus
- ◆ Expansion Bus
- ◆ Size 100 x 80 mm

OTHER FEATURES

- ◆ Up/Download removable card for data logging and or re-programming
- ◆ STE I/O Bus, 68000 and PC Interface
- ◆ Designed, Manufactured and supported in the UK

OPTIONAL EXTRAS

Additional extra features to the FM 200

- ◆ LCD Port Graphics or Alphanumeric
- ◆ Key Pad Port 64 Keys 8x8
- ◆ 8 Channels 8 bit analogue in
- ◆ 2 Channels 8 bit analogue out
- ◆ 8 Channels 13 bit analogue in
- ◆ Up to 32 Digital I/O Channels
- ◆ Up to 8 Mbytes of SRAM Battery Backed
- ◆ Up to 512 Kbytes of Flash EEPROM
- ◆ 1 Mbyte EPROM Space

DEVELOPMENT

The PC Starter Pack provides the quickest method to get your application up and running

Operating System

- ◆ Real Time Multi Tasking
- ◆ Unlimited copy licence

Languages

- ◆ 'C', Modula-2 and Assembler
- ◆ Full libraries & device drivers provided

Expansion

- ◆ Easy to expand to a wide range of peripheral and I/O cards

Support

- ◆ Free unlimited telephone, FAX, email and Internet support

Custom Design

- ◆ CMS will design and manufacture to customers requirements



**CAMBRIDGE
MICROPROCESSOR
SYSTEMS LIMITED**

Units 17-18, Zone D Chelmsford Road Industrial Estate, Great Dunmow,
Essex UK CM6 1XG Tel. +44 (0) 1371 875644 Fax: +44 (0) 1371 876077

CIRCLE NO.126 ON REPLY CARD

The Phantom Power Box

48 volt microphone phantom powering unit

Professional portable units operating from an internal PP3 battery or external mains adaptor



- ★ Suitable for converting any microphone amplifier to P48 standard phantom power
- ★ High efficiency DC to DC converter for extended battery life
- ★ Accurate line balance for high common mode rejection
- ★ Low noise and distortion
- ★ Extensive RFI protection

The Balance Box (mic/line amplifier) – The Headphone Amplifier Box – The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW

Information line: 01428 751469 Fax: 751223

E-mail contact@confordelec.co.uk

Web <http://www.confordelec.co.uk/catalogue/>

CIRCLE NO.127 ON REPLY CARD

EMC TESTING

For a Full Comprehensive EMC Test Service

- FULL TESTING TO CE MARK FOR EMC
- COMPETITIVE RATES
- FREE TECHNICAL ADVICE

From Design to Compliance

R. N. Electronics are specialist Wireless Design Consultants, this expertise is available to our clients when undertaking EMC testing, AT NO EXTRA COST.



R.N. Electronics Ltd
EMC TEST FACILITY & R.F. DESIGN SERVICES

Arnolds Court, Arnolds Farm Lane, Mountnessing,
Brentwood, Essex. CM13 1UT
Telephone: 01277 352219 Facsimile: 01277 352968
email: sales@rfdesign.co.uk <http://www.rfdesign.co.uk>

CIRCLE NO.128 ON REPLY CARD

Please quote *Electronics World* when seeking further information

parameters allow adaptation to various standards, such as ETSI (ETS 300 001, TBR21, TBR38) and FCC Part 68. The AS2591 is capable of driving a 7-segment LCD with up to 16 digits and 12 symbols.

Infineon Technologies
Tel: 00 43 3136 500265
Enquiry No 523

Software radio

Harris has announced a digital software-radio chip for cellular base stations. The software-programmable down-converter integrates everything except the baseband processor on one chip. Called the Commlink HSP50216 PDC, it can support up to four cellular protocols simultaneously, including CDMA, TDMA, IS-95, GSM, 3G and legacy protocols such as

Amps. The IC contains four separate channels capable of simultaneous multiple channel processing. It lets cellular operators move between existing radio interface standards.

Microchip
Tel: 01344 350250
Enquiry No 524


CMOS image sensor

Toshiba Electronics claims to have the world's smallest CMOS image sensor with an integral lens measuring 3.6mm. The sensor is fully compatible with the common intermediate format (CIF) for videoconferencing. It is 10mm wide and deep and 6mm high. Available in both colour (TCM5023LU) and black and white (TCM5020LU) versions, samples of the sensor are available immediately, with commercial quantities available from September 1999. The low-power CMOS device is suitable for battery-powered camera and videophone applications. Operation requires a 2.8V single power supply, and consumption is 15mW.

Infineon Technologies
Tel: 0990 550500
Enquiry No 525

Small 1k serial EEPROM

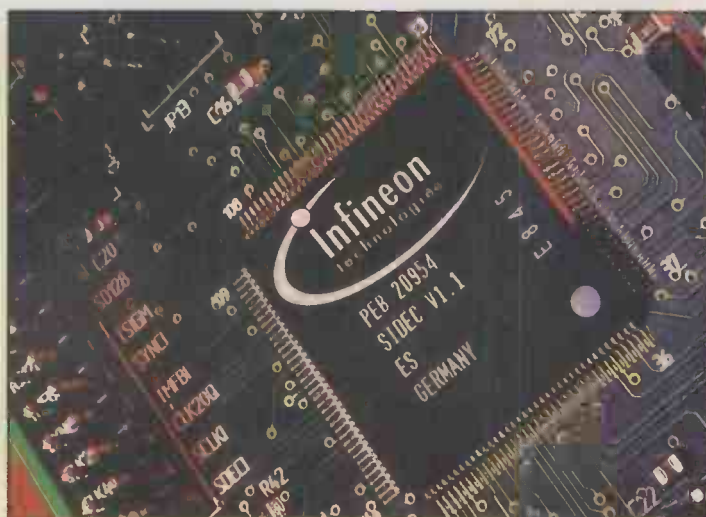Microchip claims to have the world's smallest 1k serial EEPROM in a 5-lead SOT-23 package. This means the 24LC01B offers a 50 per cent reduction in board space compared with a standard 8-lead TSSOP



In-circuit test platform

Infineon Technologies' latest chip for T1/E1 echo cancellation, the SIDE C (Smart Integrated Digital Echo Canceller), PEB20954 suppresses both electrical and acoustic echo and effectively compensates for these unwanted delays. It provides T1/E1 echo cancelling for up to 32 channels in accordance with ITU-T G.165, G.168 and G.168 (2000) standards. It integrates an array of different functional blocks onto a single device. These include: speech control, disabling logic, adaptive echo estimation unit, PCM I/O interface with selectable p- and A-law coding, non-linear processor, subtractor, microprocessor interface and Universal Control and Communication interface for signalling highways with direct hardware control.

Infineon Technologies
Tel: 0990 550500
Enquiry No 522



£10 DISCOUNT

Electronics World is delighted to offer you £10 off Newnes CD-ROM library of Circuits, including simulations, from leading experts around the world.

Please send me a copy of "Newnes Interactive Electronics CD-ROM", normal RRP £49.99 DISCOUNTED PRICE only £39.99 (postage free)
Simply return this order to:
Jackie Lowe, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS.

Name _____

Address (for delivery) _____

Pay by cheque (payable to Reed Business Information)

Visa Access/Mastercard Amex

Card Number: _____

Expiry Date: _____

Signature _____



package, and over 70 per cent compared with an 8-lead SOIC package. The EEPROM supports standard I²C protocol, 5µA typical standby current and 1mA read current, 200-year data retention and 1 000 000 erase/write cycles.

Microchip
Tel: 0118 921 5858
Enquiry No 526

Portable virtual instruments

TiePie has introduced the Handyprobe model HP2, which is claimed to be the world's first combined multimeter, oscilloscope, spectrum analyser and transient recorder for connection directly to a portable computer without an external power supply or battery. Handyprobe is a compact, truly portable instrument sampling at 20MHz with resolution of eight bits and a memory depth of 128 Kbyte. Windows based software is used to implement the Handyprobe's four virtual instruments.

TiePie Engineering
Sneek, The Netherlands
Tel: 00 31 51 541 5416
Fax: 00 31 51 541 8819
Enquiry No 527

http://www.electro
 Cat's Paw
 What's Cool?
 electronicsWEEKLY
HyperACTIVE
 HOME
 DAILY NEWS
 NEWS
 PRODUCTS
 ARCHIVE
 JOBS
 INSIDE VIEW
 TECHNOLOGY
 DISCUSSION
 REGISTRY
 MEETINGS
 TOOLKITS
 MARKET INFO
 TEMAP
 Multiple Users
 TRACK NAVIGATION

over 2,000
 electronics jobs
 updated daily
www.electronicsweekly.co.uk

electronicsWEEKLY
 Smart Recruitment Solutions

REED
 BUSINESS
 INFORMATION
 choice for business information



electronicsWEEKLY
HyperACTIVE

brought to you in conjunction with

recruiter information: **0181 652 4894**
 email: maggie.songer@rbi.co.uk



Jones
 RESOURCING
 017

Portables with a Purpose



Reliable Tools that do the Job

FieldPac uniquely combines the power and expandability of a desktop PC with the mobility, strength and form-factor of a metal attaché case. One truly full-sized ISA or PCI expansion slot allows you the freedom to choose any add-in card on the market

for applications such as: Network Testing & Monitoring, Portable D/A systems, Image Capture & Commissioning/Installation Tools. Trust the FieldPac anywhere you travel and feel confident it will survive the rigors of transport, ready to do the job, every time.

- ISA or PCI Full Sized Slot.
- High Brightness TFT Display.
- Pentium CPU, CD, Multimedia.
- Rugged, All Metal Attaché Case.

- Airline Hand Luggage.
- Universal Autoswitch Integral PSU.
- Removable Full-size Keyboard.
- CardBus / PCMCIA x 2.

Tel: +44 1908 263622

Fax: +44 1908 263220

sales@dolch.co.uk

www.dolch.com



Crystals made clear II

With the theory out of the way, Joe Carr now presents a variety of practical oscillator circuits for use with crystals ranging from 50kHz to 110MHz.

Miller oscillators are analogous to the tuned-input/tuned-output variable-frequency oscillator. This is because they have a crystal at the input of the active device, and an LC tuned circuit at the output.

Figure 1 shows a basic Miller circuit built with a junction field effect transistor, or JFET. Any common RF device can be used for Tr_1 , like for example the MPF102.

Direct-current bias is provided by R_2 , which places the source terminal at a potential above ground due to the channel current flowing in Tr_1 . The source must be kept at ground potential for AC, so a bypass capacitor, C_4 , is provided. The reactance of this capacitor must be less than one-tenth the value of R_2 at the lowest intended frequency of operation.


A parallel-resonant LC tank circuit, L_1/C_1 , tunes the output circuit of the oscillator. The tuned circuit must be adjusted to the resonant frequency of the oscillator, although best performance usually occurs at a frequency slightly removed from the crystal frequency.

If you monitor the output signal level while adjusting either C_1 or L_1 you will note a distinct difference between the high side and low side of the crystal frequency.

Best operation usually occurs at the low side. Whichever is selected though, care must be taken that the oscillator will start up reliably. Output can be taken either from capacitor C_2 as shown, or through a link coupling winding on L_1 .

The Miller oscillator of Fig. 1 has the advantage of being easy to implement, but it suffers from some problems as well. One is that the feedback is highly variable from one transistor to the next because it is created by the gate-drain capacitance of Tr_1 . There are also output level variations noted, as well as frequency pulling, under output load impedance variations. These are not good attributes for an oscillator.

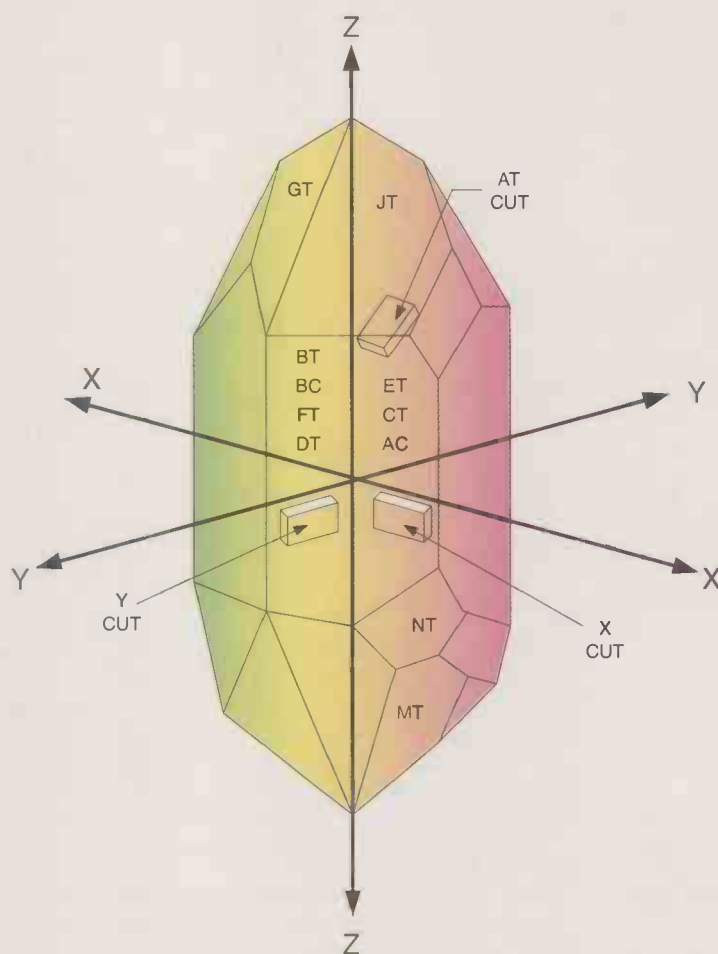Also, there is a large difference in starting ability between JFETs of the same type number, and between different crystals of the same type number from the same manufacturer. I



Surely an equivalent transistor will do?


Be careful when using 'universal' replacement lines of transistors. Crystal oscillators may operate in an unwanted overtone mode - i.e. at a higher frequency. Or because of stray LC components they may parasitically oscillate on a VHF or UHF frequency.

Because of this, you will want to keep the gain-bandwidth product of the active device low. But many replacement lines use a single high-frequency transistor with similar gain, collector current and power dissipation ratings as a 'one-size fits all' replacement for transistors with lower gain-bandwidth products.

I've seen that situation in service replacements on older equipment. The original component may not be available, so a universal service shop replacement line device is selected. It is then discovered that there are parasitic oscillations and other problems because the new replacement has a gain-bandwidth product of, say, 200MHz, whereas the old device was a 50MHz part.

This problem can show up especially severely in RF amplifiers and low-frequency oscillators where LC components naturally exist, or in any circuit where the stray and distributed LC elements provide the required phase shift on some frequency above the unity gain-bandwidth point.

Fig. 1. Basic Miller crystal oscillator using a junction fet – easy to implement but sensitive to gate-drain capacitance differences and load variations.

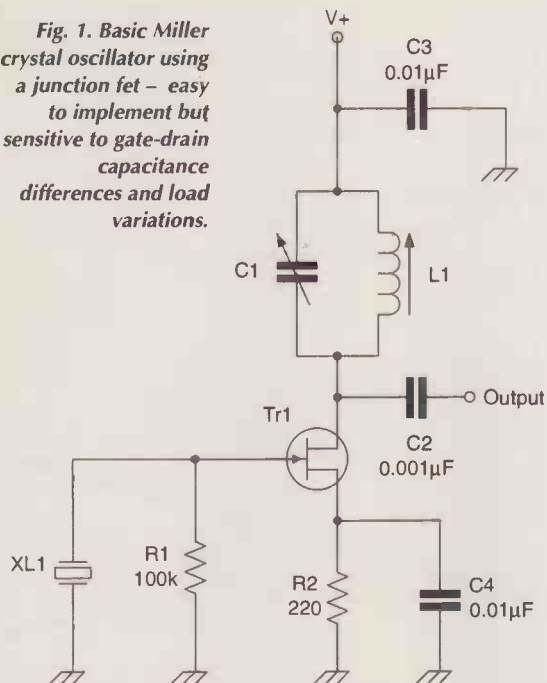

have also noted problems with this circuit when either the JFET or crystal ages.

In the case of the JFET, I've seen oscillators that worked well, and then failed. When the JFET was replaced, it started working again. What surprised me was that the JFET appeared OK when tested.

Figure 2 shows an improved Miller oscillator. This circuit uses a dual-gate MOSFET, such as the 40673, as the active element. It is a fundamental-mode oscillator that uses the parallel-

resonant frequency of the crystal. The crystal circuit is connected to gate 1, while gate 2 is biased to a DC level. This circuit can provide a stability of 15 to 20 ppm if AT-cut or BT-cut crystals are used.

A problem that you might find with this circuit is parasitic oscillation at VHF frequencies. The MOSFETs used typically have substantial gain at VHF, so could oscillate at any frequency where Barkhausen's criteria are met.

There are two approaches to solving this problem. One approach is to insert a ferrite bead on the lead of gate 1 of the MOSFET. The ferrite bead acts like a VHF/UHF RF choke.

The second approach, shown in Fig. 2, is to insert a snubber resistor – R_S in Fig. 2 – between the crystal and gate 1 of the MOSFET. Usually, some value between 10 and 47Ω will provide the necessary protection. Use the highest value that permits sure starting of the oscillator.

One interesting aspect of the Miller oscillator of Fig. 2 is that it can be used as a frequency multiplier – not to be confused with an overtone oscillator – if the tuned network in the drain circuit of Tr_1 is tuned to an integer multiple of the crystal frequency.

Pierce oscillators

The crystal being connected between the output and input of the active device characterises the Pierce oscillator. Figure 3 shows the basic Pierce

crystal oscillator circuit using a bipolar n-p-n transistor such as a 2N2222 or 2N5179.

The crystal connects directly from the collector to the base of Tr_1 . Output is taken through capacitor C_2 connected to the collector. This circuit is used extensively in low-cost receiver circuits, but is not recommended.

An improved Pierce oscillator is shown in Fig. 4. This circuit includes a capacitor, C_1 , for pulling the crystal a small amount in order to tune the frequency precisely. With the capacitance values shown, this circuit operates at frequencies between 10 and 20MHz. If the output is lightly loaded, and C_4 kept small, then the oscillator will provide reasonable output stability at a level of near 0dBm.

Figure 5 is a variation on the theme that works in the 50 to 500kHz region. This circuit is almost the same as Fig. 4, except for increased capacitance values to account for the lower frequency.

In both circuits ordinary n-p-n devices such as the 2N2222 can be used successfully.

Butler oscillators

Superficially, the Butler oscillator looks like the Colpitts in some manifestations, Fig. 6. The difference is that the crystal connects between the tap on the feedback network and the emitter of the transistor.

This particular circuit is a series-mode oscillator. The value of R_1

Fig. 2. Performance of the Miller oscillator is improved if a dual-gate MOSFET is used instead of the junction FET. Stability can be as good as 15ppm.

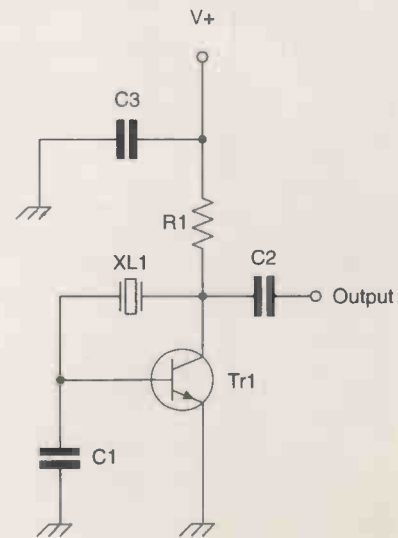
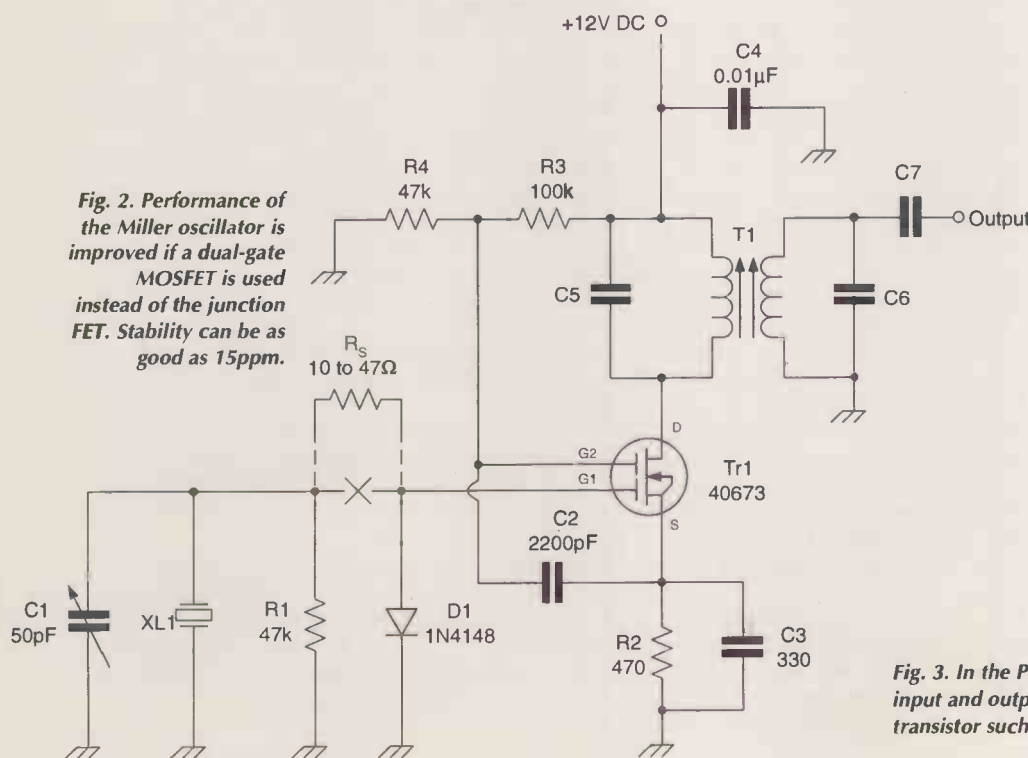



Fig. 3. In the Pierce oscillator, the crystal connects between the input and output of the active device – in this case an n-p-n transistor such as the 2N2222

should be whatever value between 100 and 1000Ω that results in reliable oscillation and starting, while minimising crystal dissipation.

A table of capacitance values for feedback network C_1/C_2 is provided. For the 3 to 10MHz range, use 47pF for C_1 and 390pF for C_2 ; for 10 to 20MHz select 22pF for C_1 and 220pF for C_2 .

The collector circuit is tuned by the combination of C_1 and L_1 . This circuit may well oscillate with the crystal shorted, and care must be taken to ensure that the 'free' oscillation and the crystal oscillation frequencies are the same. The crystal should take over oscillation when it is in the circuit.

The Butler oscillator of Fig. 6 is

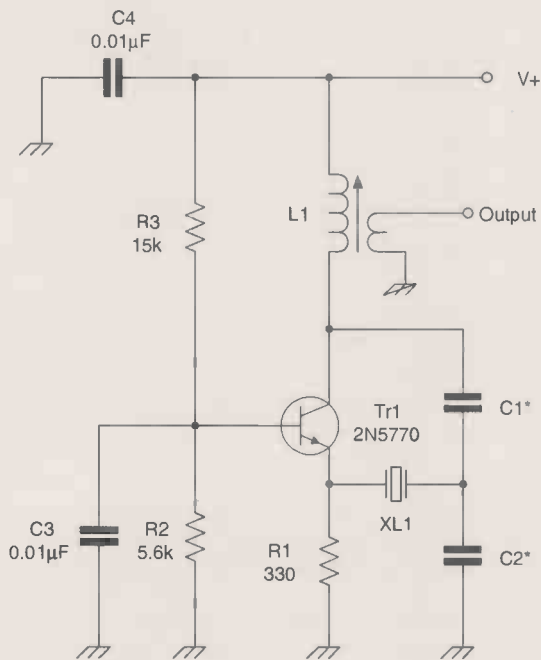

Freq (MHz)	C1 (pF)	C2 (pF)
3 - 10	47	390
10 - 20	22	220

Fig. 6. The Butler oscillator is capable of stability down to 10ppm if an output buffer with good isolation is used.

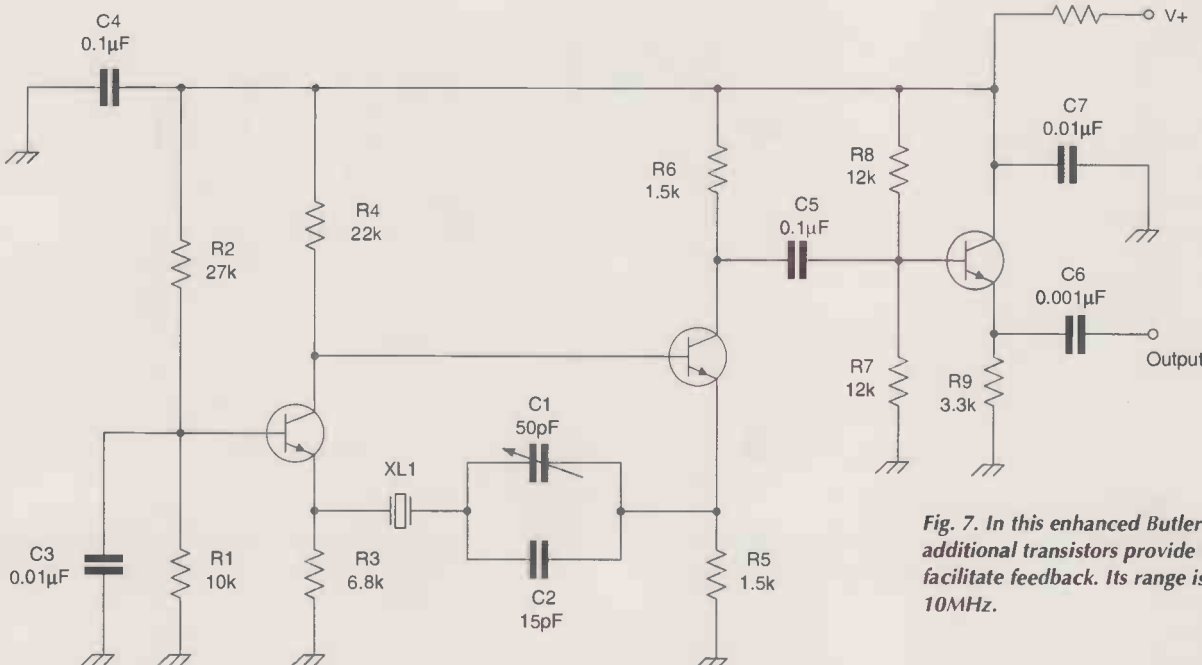


Fig. 7. In this enhanced Butler oscillator, two additional transistors provide buffering and facilitate feedback. Its range is 300kHz to 10MHz.

Fig. 4. In this improved Pierce oscillator, capacitor C_1 pulls the crystal, allowing the circuit to be tuned precisely. Works at 10-20MHz with components shown.

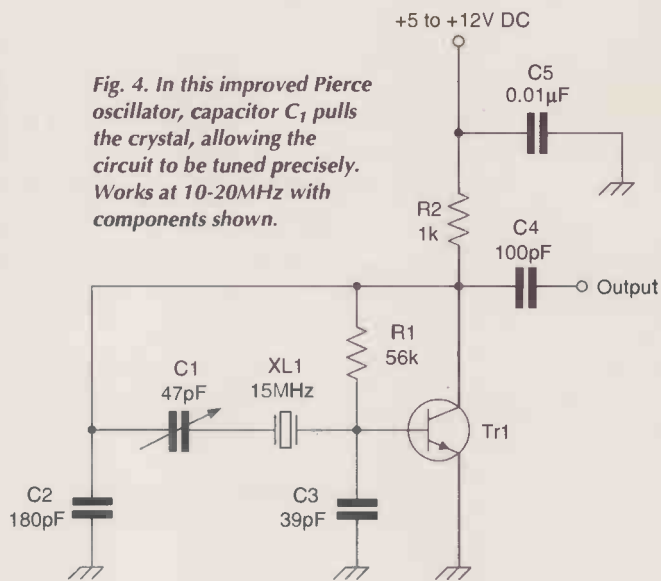


Fig. 5. Pierce oscillator circuit with components modified for operation at 50 to 500kHz.


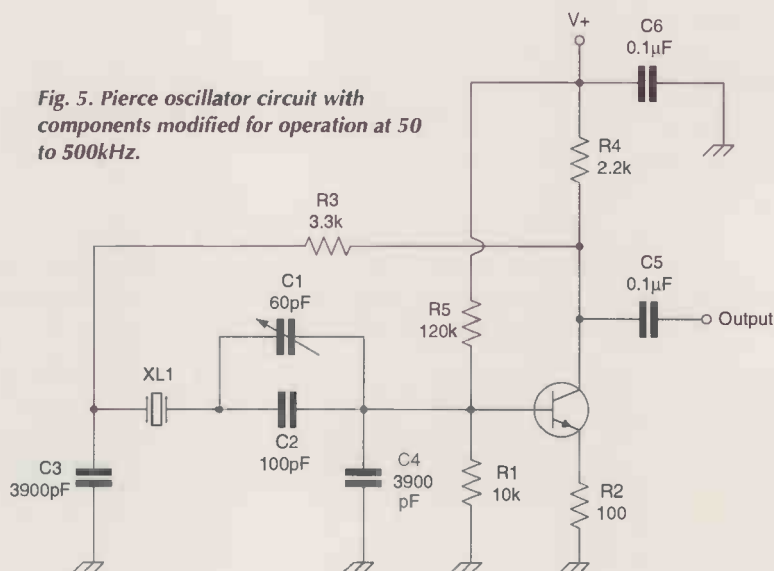


Fig. 8. Butler oscillator configured for reduced sensitivity to supply voltage variations.

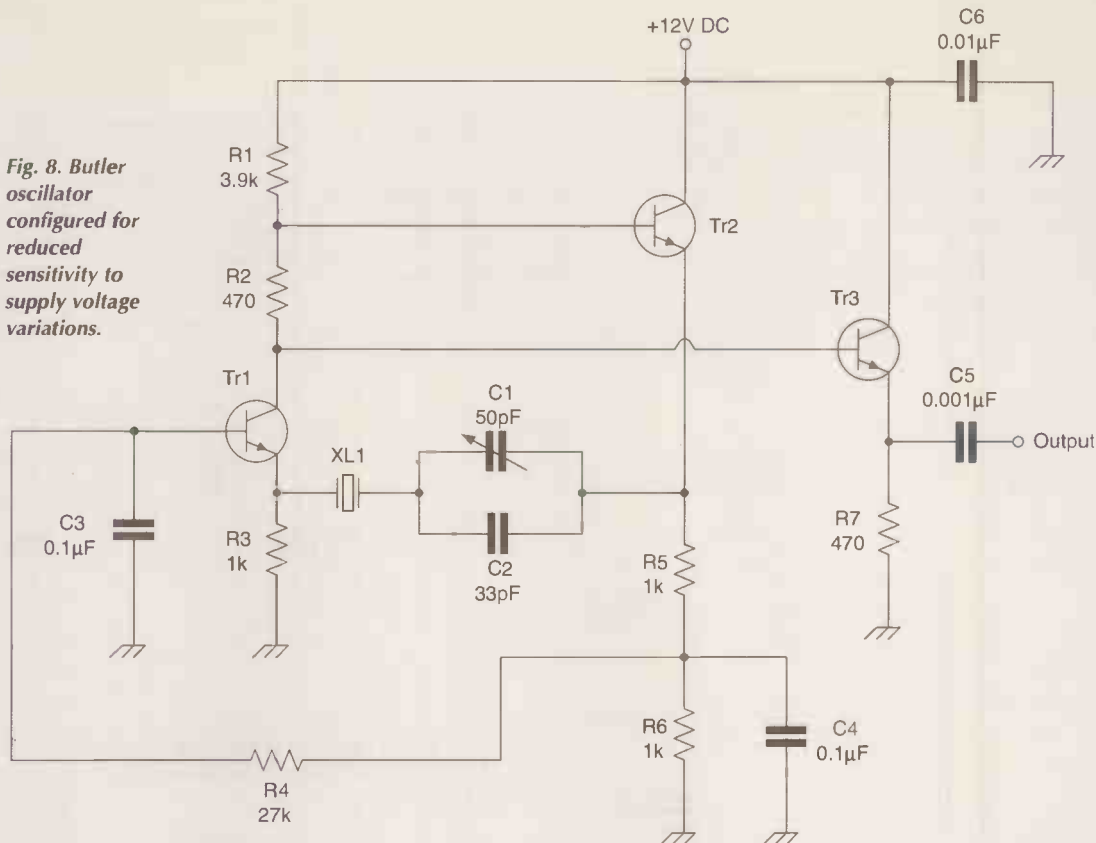

capable of 10 to 20ppm stability if a buffer amplifier with good isolation is provided at the output. Otherwise, some frequency pulling with load variations might be noted.

The output signal is taken from a coupling winding over L_1 . This winding is typically only a few turns of wire on one end of L_1 . Alternatively, a tap on L_1 might be provided, and the tap

connected to a low value capacitor. That approach might change some resonances unless care is taken.

Another alternative output scheme is to connect a small value capacitor to the collector of Tr_1 . Keep the value low so as to reduce loading, and also to reduce the effects of the output capacitor on the resonance of L_1/C_1 .

A somewhat more complex Butler

oscillator is shown in Fig. 7. This circuit is sometimes called an aperiodic oscillator circuit. It uses two additional transistors to provide buffering and also serve as part of the feedback circuit. The circuit will operate from about 300kHz to 10MHz, but the transistor may need to be selected carefully.

Many low-frequency crystals exhibit a lower equivalent series resistance, or

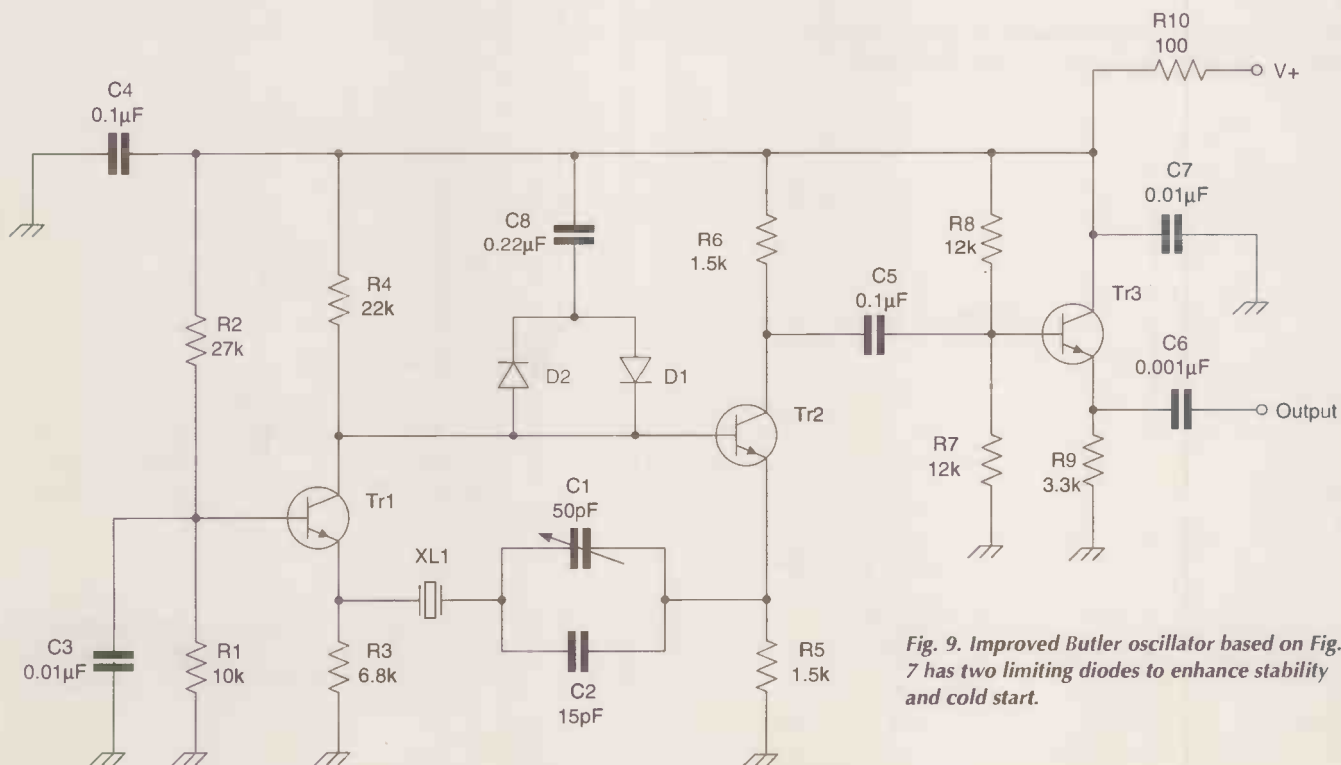


Fig. 9. Improved Butler oscillator based on Fig. 7 has two limiting diodes to enhance stability and cold start.

ESR, in one of the higher-frequency modes of oscillation than in the fundamental mode. As a result, you might find this circuit oscillating at some frequency in the medium wave or HF region, rather than at LF. The key to preventing this problem is to use a transistor with a lower gain-bandwidth product, such as a 2N3565. An explanation is given in the panel entitled, 'Surely an equivalent transistor will do?'

The circuit of Fig. 7 produces a sine wave output, but not without relatively strong harmonic output. The second and third harmonics are particularly evident. However, if harmonics are desired – when the oscillator is used in a frequency multiplier for example – then strong harmonics up to 30MHz can be generated from a 100kHz crystal if R_5 is reduced to about $1k\Omega$.

The output of this oscillator is taken through an emitter-follower buffer. This circuit can be used as a general buffer for a number of oscillator circuits. It is generally a good practice to use a buffer amplifier with any oscillator in order to reduce loading and smooth out load impedance variations.

Another variation on the Butler theme is shown in Fig. 8. This circuit is similar to Fig. 7, but is a bit less sensitive to frequency pulling due to DC power supply voltage variations. It is good engineering practice to use a separate voltage regulator for all oscillator circuits though, in order to prevent such variation. The availability of low cost three-terminal integrated circuit voltage regulators makes this easy.

An improved Butler oscillator is shown in Fig. 9. This circuit is based on Fig. 7. Both circuits can be used at frequencies from LF up to the mid-HF region – about 12 to 15MHz – if appropriate values of R_3 and R_5 are used.

The improvement of Fig. 9 over Fig. 7 stems from the limiting diodes $D_{1,2}$ between the two oscillator transistors, $Tr_{1,2}$. These diodes can be general-purpose 1N4148 small-signal types.


The circuit of Fig. 9 is preferred over Fig. 7 because it is more stable because crystal dissipation is limited, and it offers more reliable cold starting.

The Butler oscillators above are series-mode circuits, but because of the series capacitors, they are able to use parallel-mode crystals. For a strictly series-mode circuit, eliminate the capacitors in series with the crystal and replace them with a short circuit.

Colpitts oscillators


A feedback network consisting of a tapped capacitive voltage divider characterises the Colpitts oscillator. In Fig.

Fig. 10. Colpitts oscillator can be used with parallel-mode crystals. This circuit operates from 3 to 20MHz.

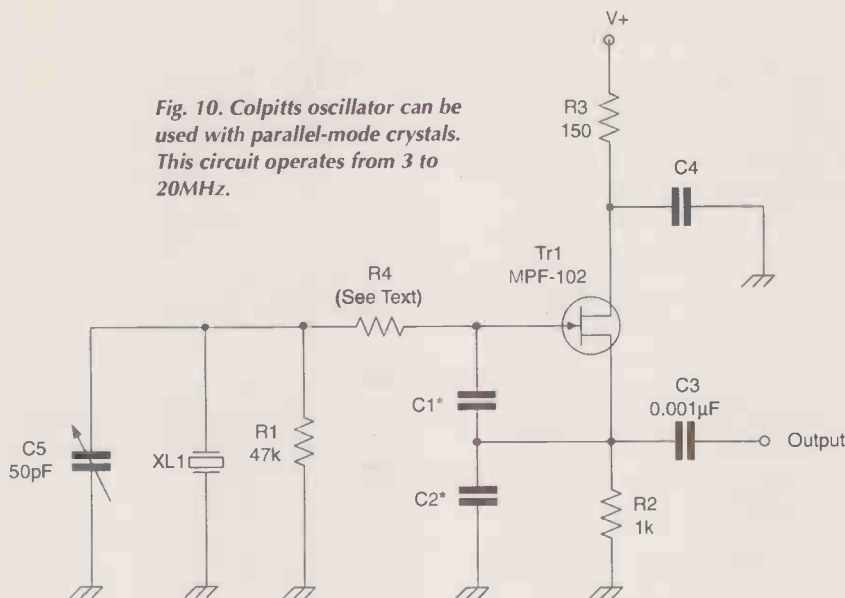

Freq (MHz)	C1 (pF)	C2 (pF)
3 - 10	27	68
10 - 20	10	27

Fig. 11. Similar to the Colpitts oscillator Fig. 10, this variant involves a MOSFET instead of a junction FET and it has a small-signal diode added to provide output amplitude stabilisation.

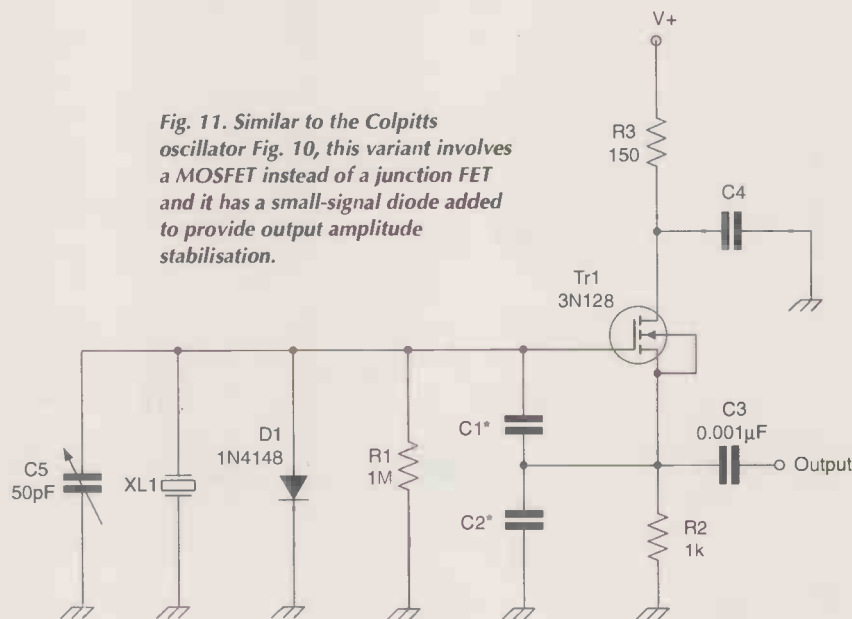

Freq (MHz)	C1 (pF)	C2 (pF)
3 - 10	22	180
10 - 20	10	82

10 the feedback is provided by C_1 and C_2 , although the situation is somewhat modified by the gate capacitances of Tr_1 . This circuit can be used with parallel mode crystals from about 3 to 20MHz with proper values of C_1 and C_2 as in the table in Fig. 10.


Frequency trimming of the oscillator can be done by shunting a small value trimmer capacitor across the crystal. Alternatively, the trimmer can be placed in series with the crystal.

If the oscillator tends to oscillate parasitically in the VHF region, then try

using the snubber resistor method, R_4 in Fig. 10. This could occur because the JFET used at Tr_1 will have sufficient gain at VHF to permit Barkhausen to have his due at some frequency where strays and distributed LC elements produce the correct phase shift.

A value between 10 and 47Ω will usually eliminate the problem. Alternatively, a small ferrite bead can be slipped over the gate terminal of Tr_1 to act as a small value VHF/UHF RF choke.

Fig. 12. Colpitts variant comprising an impedance-inverting oscillator. With the right components, its stability can be 10ppm from 0 to 60°C.

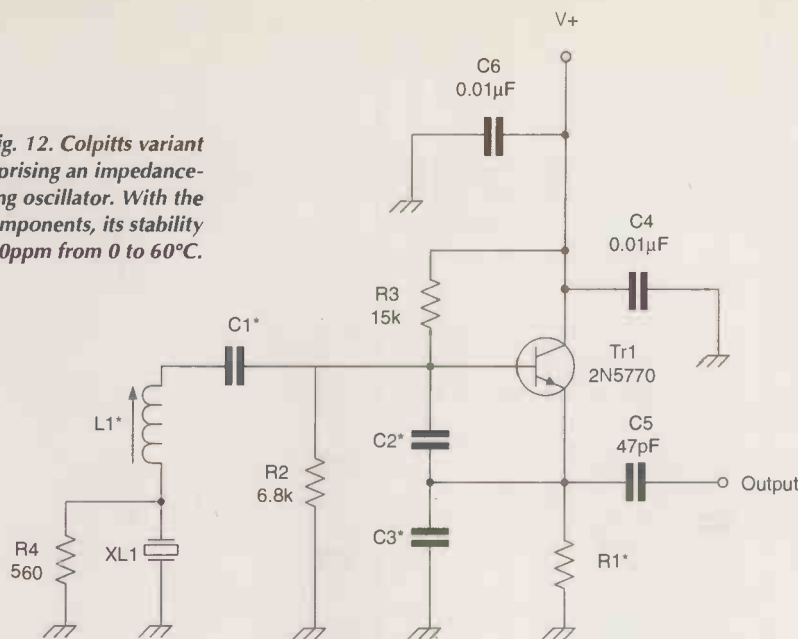

Freq (MHz)	C1 (pF)	C2 (pF)	C3 (pF)	R1	L1 (turns)
2 - 4	1000	270	270	1.5k	60
4 - 6	1000	270	270	1.5k	40
6 - 10	1000	270	270	1.5k	25
10 - 15	100	220	220	680	15
15 - 20	100	100	100	680	10

Figure 11 is the same as Fig. 10, except for two features. First, the active device is an n-channel MOSFET rather than a JFET. Any of the single-gate devices, such as a 3N128, can be used, but remember that such MOSFETs are very sensitive to ESD damage.

The other difference is a 1N4148 small-signal diode that shunts the gate-source path to provide a small amount of automatic gain control action. When the signal appearing across the crystal and feedback network is sufficiently large, the diode rectifies the signal and produces a DC bias on the gate that counters the source bias provided by R₂. This diode helps smooth out amplitude variations, especially when more than one crystal is switched in and out of the circuit.

Another variation on the Colpitts theme is the impedance inverting oscillator circuit of Fig. 12. It provides stability of 10ppm over a wide temperature range of 0°C to 60°C provided that the components are carefully selected. Bear in mind that C_{1,3} and L₁ are particularly troublesome here.

The circuit will also remain within ±0.001% over a DC power supply variation of 2:1 – provided the crystal

Fig. 14. Alternative impedance-inverting third-overtone circuit based on the Colpitts oscillator. Again, this circuit works from 15 to 65MHz.


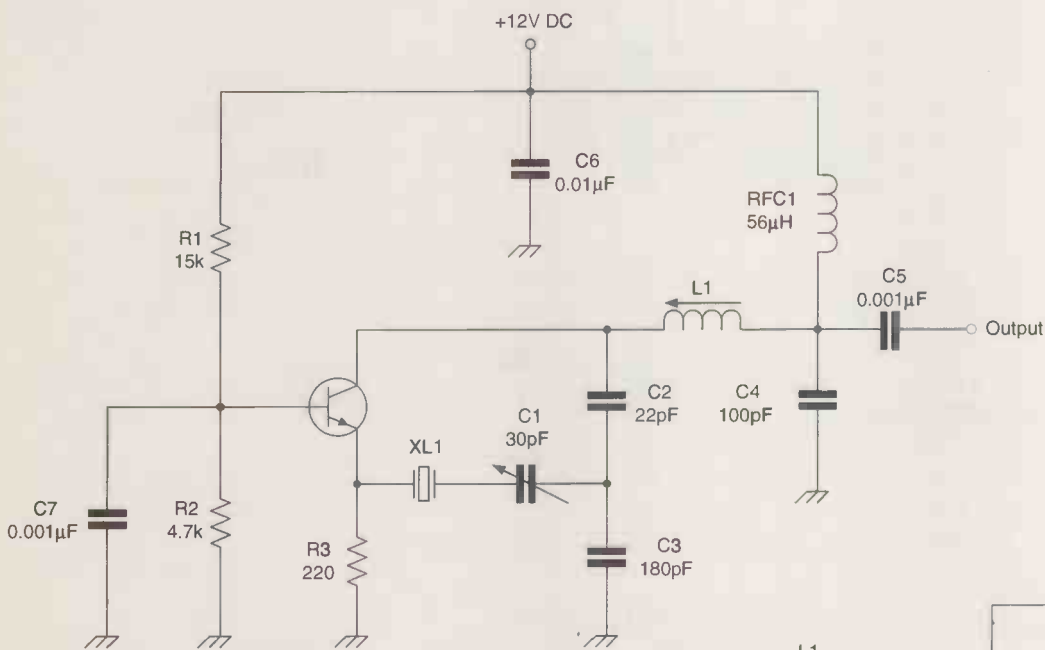


Fig. 13. Third-overtone Butler oscillator for 15 to 65MHz. Tuning inductor L₁ helps ensure that the circuit oscillates at the desired overtone frequency.

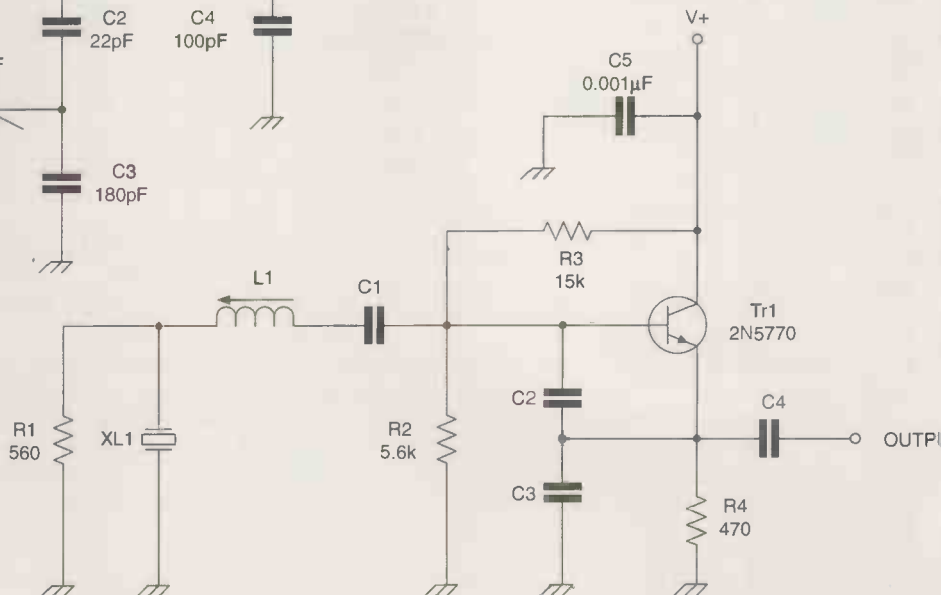

Freq (MHz)	C1 (pF)	C2 (pF)	C3 (pF)	C4 (pF)	L1 (0.25in form)
15 - 25	100	100	68	33	12t, #30, CW
25 - 55	100	68	47	33	8t, #30, CW
50 - 65	68	33	15	22	6t, #22, CW

dissipation is not exceeded. Harmonic output of this configuration is typically low.

Frequency of oscillation is set by adjusting inductor L_1 . The turns counts shown in the table in Fig. 12 assume a 6.5mm slug-tuned coil form designed for use in the frequency range 3 to 20MHz. Some experimentation is needed depending on the particular former used. The idea is to set the resonant frequency of the coil and C_{1-3} combined to something near the crystal frequency.

It is sometimes appealing to add a tuned circuit to the output circuit of oscillators. The harmonics of the oscillator are suppressed when this is done. But in this case, a transistor equivalent of the old-fashioned TGTP oscillator will result because of the action of the output tuned circuit and the L_1/C_{1-3} combination. Don't do it!

Overtone oscillators

So far I have only discussed the fundamental oscillating mode. But crystals oscillate at more than one frequency.

The oscillations of a crystal slab are in the form of bulk acoustic waves, or BAWs. These can occur at any frequency that produces an odd half-wavelength of the crystal's physical dimensions, for example $1\lambda/2, 3\lambda/2, 5\lambda/2, 7\lambda/2, 9\lambda/2$, where the fundamental mode is $1\lambda/2$.

Note that these frequencies are not harmonics of the fundamental mode. They are actually valid oscillation modes for the crystal slab. The frequencies fall close to, but not directly on, some of the harmonics of the fundamental – which often causes confusion.

The overtone frequency will be marked on the crystal, rather than the fundamental. It is rare to find fundamental mode crystals above 20MHz or so, because their thinness makes them more likely to fracture at low values of power dissipation.

The problem to solve in an overtone oscillator is encouraging oscillation on the correct overtone, while squelching oscillations at the fundamental and undesired overtones. Crystal manufacturers can help with correct methods, but there is still a responsibility on the part of the oscillator designer.

Figure 13 shows a third-overtone Butler oscillator that operates at frequencies between 15 and 65MHz. Inductor L_1 is set to resonate close to the crystal frequency, and is used in part to ensure overtone mode oscillation. If moderate DC supply voltages are used – 9 to 12 volts in most cases

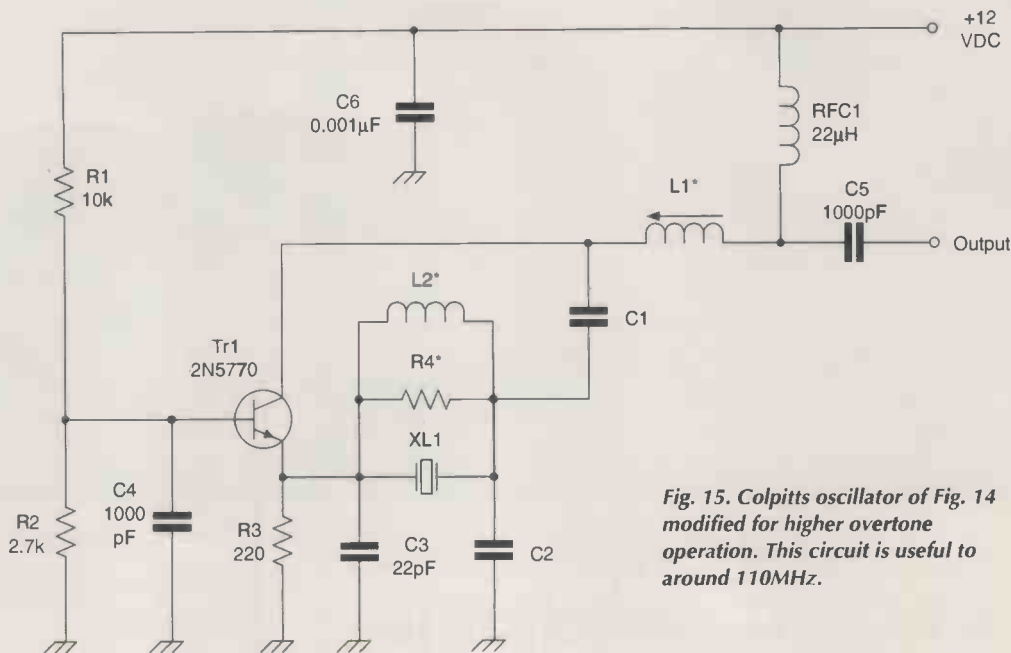


Fig. 15. Colpitts oscillator of Fig. 14 modified for higher overtone operation. This circuit is useful to around 110MHz.

Freq (MHz)	C1 (pF)	C2 (pF)	C3 (pF)	L1	L2
65 - 85	15	150	100	7 t, #24, 3/16in. CW	10t #34 over 10Ω 1/4W
85 - 110	10	100	68	4 t, #24, 3/16in. 1WD	10t #34 over 10Ω 1/4W

CW = close wound
1WD = spaced 1 wire diameter

– the harmonic content is low, at around -40dB. In addition, stability is at least as good as a similar fundamental mode Butler oscillator.

Figure 14 is a third-overtone impedance inverting Colpitts style oscillator that operates over the 15 to 65MHz range. As in similar circuits, inductor L_1 is tuned to the overtone, and is resonated with C_1 , combined with the capacitances of C_2 and C_3 . Values for C_1 through C_3 , and winding instructions for a 6.5mm low-band VHF coil former are shown on the diagram.

Note the resistor across crystal Y_1 . This resistor tends to snub out oscillations in modes other than the overtone, including the fundamental. Take care not to make L_1 too large, otherwise it will resonate at a lower frequency with C_{1-3} , forming an oscillator on a frequency not related to either the crystal's fundamental or overtones. The oscillator may well be perfectly happy to think of itself as a series-tuned Clapp oscillator!

Operation of the circuit of Fig. 14 to 110MHz, with fifth or seventh overtone crystals, can be accomplished by modifying this circuit to the form shown in Fig. 15.

In summary

The crystal oscillator is probably the best way to obtain a single-frequency source. Crystal oscillators are also used to provide accurate references and time base in such applications as frequency counters and frequency synthesizers.

With proper care and component selection, these circuits can be used to provide a stable, accurate signal. ■



**Unique reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive***

*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to Probe Offer, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Readers outside Europe, please add £2.50 to your order.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Cheques should be made payable to Reed Business

Information

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____ Signed _____

Please allow up to 28 days for delivery

Specifications

Switch position 1

Bandwidth	DC to 10MHz
Input resistance	1MΩ – i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC

Switch position 2

Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

Switch position 'Ref'

Probe tip grounded via 9MΩ, scope i/p grounded

More than
25.000
Users

ULTIboard, a leading PC based Windows 98/NT design system, is supplied worldwide via a network of offices & distributors. ULTIboard's success with professional designers is primarily thanks to its superior interactive functionality.

REAL TIME Placement Help, REAL TIME Design Rule Check, Reroute-While-Move and Trace Shoving, are all features which will dramatically reduce your design time.

Integration with ULTIcap guarantees smooth data flow between Schematic and PCB editing. ULTIboard's 1 nanometre resolution ensures that routing errors belong to the past.

Another of ULTIimate Technology's strengths is its flexible growth path. Users may start with a low cost ULTIboard Challenger and grow, step by step, to advanced Autorouting & Placement, Analog/Digital Simulation. ULTIboard offers the best price/performance!

ULTIimate Technology looks after existing users! With valid maintenance they will be upgraded to a new system based on the original investment. For instance, a 1987 ULTIboard-DOS system was upgraded to Windows 95/98/NT with advanced AutoPlacement & AutoRouting and Simulation. Regular User Meetings and Surveys result in 2 major Updates per year.

ULTIimate Technology not only adds value to your investment in an ULTIboard system but backs it up with the highest quality support.

CALL-FREE INTERNATIONAL PHONE:
00-800-ULTIMATE (00-800-85-846283)


SPECIAL OFFER

Order our Challenger 700, a full-feature design system with 700 pin capacity, consisting of ULTIcap schematic capture, ULTIboard PCB Design and ULTIroute GXR Autorouter (designed to route boards with thru-hole components) for the price of £ 249 (until 30.11.99). With the system you also get an evaluation copy of our high-end ULTIroute GT AutoPlacement & AutoRouting targeted at the most complex SMT designs). This way, you know exactly what you will buy, when you decide to upgrade later (based upon the price difference).


Challenger 700 **£ 249** excl. VAT



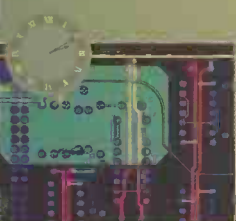
Your design ideas are quickly captured using the ULTIcap schematic design Tool. ULTIcap uses REAL-TIME checks to prevent logic errors. Schematic editing is painless; simply click your start and end points and ULTIcap automatically wires them for you. ULTIcap's auto snap to pin and auto junction features ensure your netlist is complete, thereby relieving you of tedious netlist checking.



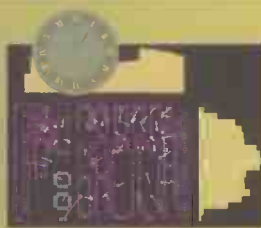
If you need partial ground planes, then you can automatically create copper polygons simply by drawing the outline. The polygon is then filled with copper of the desired net, all correct pins are connected to the polygon with thermal relief connections and user defined gaps are respected around all other pads and tracks.



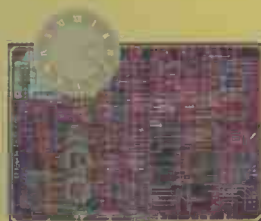
Good manual placement tools are vital to the progress of your design, therefore ULTIboard gives you a powerful suite of REAL-TIME functions such as FORCE VECTORS, RATS NEST RECONNECT and DENSITY HISTOGRAMS. Pin and gate swapping allows you to further optimise your layout. For optimal design automation, consider our fully automatic placement option.



ULTIboard's autorouters allows you to control which parts of your board are autorouted, either selected nets, or a component, or a window of the board, or the whole board. ULTIboard's intelligent router uses copper sharing techniques to minimise route lengths. Automatic via minimisation reduces the number of vias to decrease production costs. The true 45 degree autorouter will handle up to 32 layers. Gridded or Shape based!

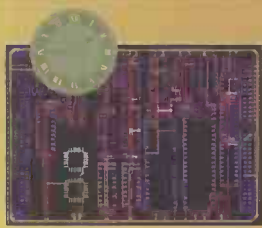

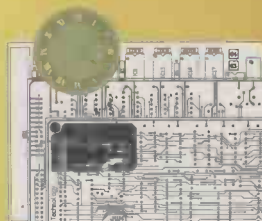Now you can quickly route your critical tracks. ULTIboard's REAL-TIME DESIGN RULE CHECK will not allow you to make illegal connections or violate your design rules. ULTIboard's powerful TRACE SHOVE, and REROUTE-WHILE-MOVE algorithms guarantee that any manual track editing is flawless. Blind and buried vias and surface mount designs are fully supported.



ULTIboard's backannotation automatically updates your ULTIcap schematic with any pin and gate swaps or component renumbering. Finally, your design is post processed to generate pen/ photo plots, dot matrix/laser or postscript prints and custom drill files and Bill of Material.

NOT HAPPY WITH YOUR CURRENT CAD SYSTEM?

Call for a competitive upgrade!

HOW INTERACTIVE IS YOUR BOARD STRATEGY



Your move

YOU want the best placement

YOU use SMD Technology

YOU want 100% design integrity

YOU want 100% automatic routing

YOU don't want Autorouters

ULTIboard's move

In addition to dynamic rats nests, force vectors and density histograms, ULTIboard's **Direct Reconnect** instantly displays the shortest possible connections. **Automatic Gate- & Pin Swap** with full **Backannotation** guarantee the best. Or... select our Auto-Placement option!

ULTIboard understands the different soldering techniques that apply to SMT. Flip your SMD to the other side of the board and ULTIboard **automatically** applies the pad definitions for either wave or reflow soldering.

ULTIboard **Real-Time DRC** does not allow you to accidentally connect wrong pins or violate trace clearances. It always respects your design rules.

The ULTIroute GXR Ripup & Retry Autorouter is able to remove connections that cause a block and automatically reroutes the removed connections. The user can define the Autorouter parameters. Gridded or gridless (shape based): the choice is yours!

ULTIboard's acknowledged powerful interactive features such as Reroute-While-Move and Trace-Shoving under **Real-Time DRC** guarantee flawless designs in the shortest time. After all, this was an important factor to make ULTIboard Europe's #1 choice for Professional Designers!

FROM CONCEPT TO ARTWORK IN 1 DAY

ULTIMATE
TECHNOLOGY

European Headquarters: ULTIimate Technology BV, Energijestr. 36, 1411 AT Naarden NL
phone: 003135-6944444 - fax 003135-6943345 - Freephone: 00-800-85-846283

USA/Canada phone: (416) 977-5550 - fax (416) 977-1818

ULTIBOARD 12 1/2 YEAR

E-mail: sales@ultiboard.com • www.ultiboard.com

857

Save over £80

Reader offer

1GHz spectrum analyser

Easy to connect and use
The adaptor connects to the oscilloscope via two BNC connectors using true 50Ω impedance for minimal vswr. A calibration button allows a standard -30dBm 50MHz marker signal to be superimposed for precise amplitude and frequency checks.



TSA1000 1GHz spectrum analyser

Designated the TSA1000, this spectrum analyser is in the form of an adaptor that converts any standard oscilloscope into a 1GHz spectrum analyser.

The instrument has a dynamic range of 70dB with a typical accuracy of 1.5dB. Its frequency range is from 400kHz to over 1GHz, and its bandwidth – i.e. selectivity – is 250kHz.

A built-in crystal-controlled marker provides a precision means of frequency and amplitude calibration. The centre frequency can be adjusted over the full 0-1GHz range using a ten-turn control, and is displayed on a large 3.5-digit liquid-crystal display.

Scan width is fully variable between 10MHz and 1GHz, and the scan rate can be set anywhere between 10Hz and 200Hz.

The TSA1000 is supplied with an operating manual describing the basics of spectrum analysis and EMC measurements. Its normal price is £581 including VAT in the UK. Electronics World readers can obtain it for just £499 – including VAT and carriage.

TSA1000 key specifications

Frequency range	400kHz to 1000MHz
Centre adjust	0MHz to 1000MHz
Bandwidth	250kHz (-6dB typical)
Meter accuracy	1% of reading +1MHz
Calibration marker	50MHz fundamental, harmonics to 1GHz
Scan width	1MHz to 100MHz/div
Scan speed	0.5ms to 35ms/div
Amplitude	
Input impedance	50Ω
Amplitude range	-70dBm to 0dBm nominal
Amplitude scale	Logarithmic, 10dB/div
Amplitude linearity	Typically ±2dB
Amplitude flatness	Typically ±1.5dB
Max. input level	+10dBm
Calibration marker	-30dBm ±1dB at 50MHz

Oscilloscope requirements

Oscilloscope mode	X-Y mode, DC coupling; bandwidth not critical
X-Input sensitivity	0.5V/div
Y-Input sensitivity	0.5V/div

Designed and manufactured to IEC1010-1 ● +5 to +40°C, 20% to 80% RH operating range ● 260(W) x 88(H) x 235(D)mm, 1.4kg
Runs from 220/240 or 110/120V at 50/60Hz ● Full operating ranges 198–264V or 99–132V ● Power consumption 8VA max

Use this coupon for your order
Please send me:

..... TSA1000 Spectrum analyser(s) at the fully-inclusive price of £499.

Name:

Address:

Tel no

Total £

Cheques payable to REED BUSINESS INFORMATION

Or debit my visa, master, access or switch card

Card type:

Card No:

Expiry date:

Switch iss no

Please post this order to TSA1000, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Overseas readers can still obtain this discount but details vary according to country. For more information, write or e-mail jackie.lowe@rbi.co.uk. We endeavour to dispatch as soon as possible, but please allow 28 days for delivery.

Anti-jitter: new circuits

Neil Downie reveals more details of a brand new building block for removing signal jitter, and presents some example circuits.

The anti-jitter circuit, or AJC, is a simple but novel configuration of circuit elements that has been overlooked until now. It is as fundamental and potentially as useful as time-honoured configurations such as the PLL or the active filter.

Practically all the circuit blocks we use today, from AGCs to PLLs, were developed in the first half of the twentieth century. Pioneers like Alan Blumlein or even Lee de Forest would have little difficulty in recognising most of the basic circuits we use today.

You might be forgiven for thinking that the electronics pioneers in the valve era had tried out every possible combination of fewer than a dozen circuit elements. Not so. Three years ago Professor Mike Underhill of Surrey University was looking for a simple circuit to reduce pulse time jitter or, equivalently, phase noise in communications systems.

New electronics technology such as digital radio and new cellular and satellite radios increasingly needs lower jitter values. Lower jitter would enhance the performance of key elements such as sigma-delta converters and make DSP subsystems better, Mike reasoned.

There were traditional solutions to reduce jitter around. If it is jitter from an oscillator that concerns you, for example, you can use high-Q LC combinations or other low-jitter designs. Alternatively, for externally sourced signals, locking onto the incoming sig-

nal with a phase-locked loop can reduce jitter.

However, Mike was unhappy with these solutions and their limitations and came up with a much simpler and more direct approach – a circuit to directly reduce jitter.

Mike, Mike Blewett, Thomas Bruchert, staff and students at Surrey and myself at Maran & Co have worked for three years developing AJCs. There is now a number of versions of the AJC concept.

Discussions with semiconductor companies have begun, and it seems likely that commercially produced AJC chips will become available within a year.

What is an AJC?

The concept behind the anti-jitter circuit is to generate pulses from an input waveform containing jitter, feed them into an integrator, then pass the result through a comparator. The reconstituted pulses emerge equally spaced, with

jitter sidebands reduced by typically 20dB or more – a factor of 10x reduction in time jitter. The core of circuits adopting the AJC approach is shown in Fig. 1.

Note that there is no oscillator in this circuit. The output signal derives directly from the input, having been governed to the average input frequency by the action of the integrator and comparator.

The output can track the input over wide frequency deviations – around 3:1 to 10:1 with many simple designs. By making the monostable time constants track the input frequency to some extent, even wider ranges of frequency can be followed. The output can even track instantaneous frequency jumps up to a factor of two or so, as well as jitter values up to 150° in phase.

DC removal is required to keep the integrator circuit within the circuit voltage limits such as supply rails. Although this can increase the time needed for the circuit to begin func-


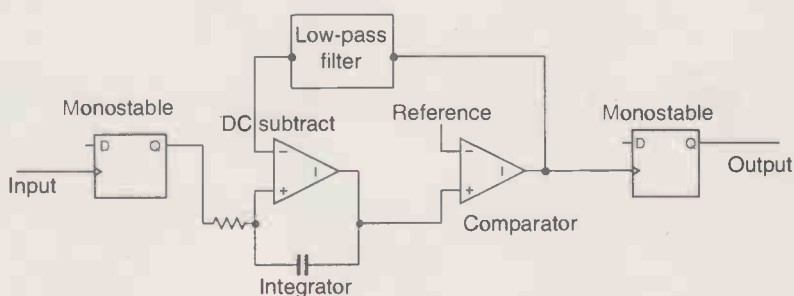


Fig. 1. Basic anti-jitter circuit – note the absence of an oscillator.

Fig. 2. Basic functional blocks of the AJC, a). Waveform b) shows jitter on the output from the input monostable. Sawtooth c) is output from the integrator, op2, and comparator switching level, op3, together.

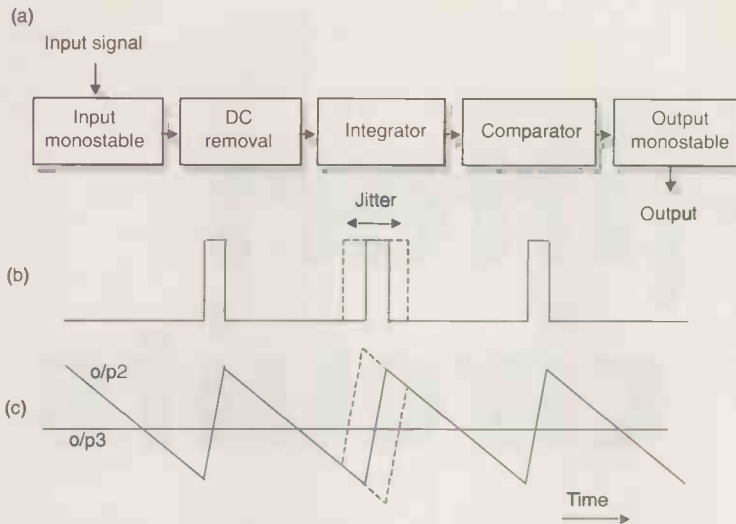

tioning at switch on, there are ways to avoid this, as discussed later.

Note how the circuit can easily be cascaded. If 25dB jitter suppression is insufficient in an application, connecting two AJCs in series will yield about 50dB. In some applications, perhaps, three or more AJCs in series might be used, although there is an ultimate noise floor, below which AJCs will not reduce noise.

Finally, the AJC is also a 'drop-in' separate circuit block which can be added to existing designs in a simple way. In an existing circuit with a jitter problem, an AJC can – conceptually at least – be soldered in across a cut track.

Basic action of the AJC

Figure 2a) reveals the basic operation of the AJC.

In the absence of a pulse, the charge on the integrator capacitor simply leaks away at a constant rate, the waveform sloping gently downward. As the same size pulses come in they push the inte-

grator capacitor up by the same amount.

However, if a pulse arrives early, then that increment in charge builds on a higher base, and pushes the next downward slope to a higher point. Intriguingly though, that new downward slope, although it starts earlier and is longer, is actually coincident with the slope that would have occurred had the pulse arrived at the right time.

Think of the gentle sloping sides of the sawtooth as the sliding tubes of a trombone, and the pulse upward increment as the handle. This should give you an idea of how the waveform changes with different pulses arriving on an oscilloscope display.

Now the fact that the downward slopes are all in the same place means that a comparator placed between the sawtooth waveform and a reference can trigger output pulses at regular time intervals – i.e. without jitter. More picturesquely, the horizontal

reference line always cuts the trombone tubes in the same place, even though the handle has moved.

Simple AJC demonstration circuit

The block diagram of Fig. 1 can be implemented directly to make a practical AJC circuit. The demonstration circuit of Fig. 3 shows the principles of the AJC using only common low-frequency glue logic circuits, and shows clearly the straightforward nature of AJC action.

For simplicity, a 4528 monostable wired to give a 200ns pulse is used for both input and output pulse shaping. The CA3140 single supply CMOS operational amplifier is used for the integrator, with the LM311 comparator comparing the integrator output with a half V_{cc} reference. Voltage V_{cc} is conveniently a 9V battery.


To show the action of the circuit, a jittered input of 100kHz-300kHz is required. An FM signal generator can be used, or a VCO such as a 4046. Alternatively a pair of multivibrator circuits such as 555s could be wired up. The input should be large enough – 5V or so – to trigger the 4528 monostable on the input.

Some elementary considerations apply to viewing the produced waveforms on an oscilloscope. Triggering on the input pulses, as given by the input monostable, and looking at the jitter on the next pulse(s) shows the jitter on the input signal.

Triggering on the output pulses and looking at the jitter on the next pulse(s) on the display shows the jitter on the output signal. Alternatively, the input and output frequency spectra can be compared.

At these low frequencies, no partic-

Fig. 3. Low-speed anti-jitter demonstration circuit. This configuration is useful from 100 to 300kHz.

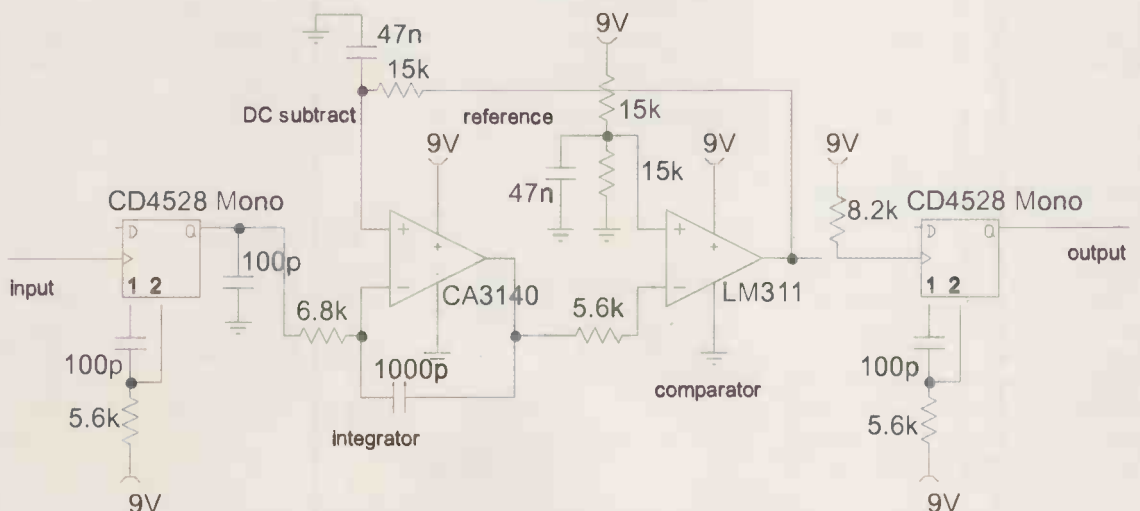

ular care is required over the construction of the circuit. A printed wiring board is not required, and because of the slow rise time of the low speed CMOS logic circuits, no radio-frequency or power supply precautions are necessary other than the decoupling capacitors indicated. Furthermore, standard oscilloscope and spectrum analyser probes can be used without disturbing the action of the circuit too much.

Figure 4 shows oscilloscope measurements of the integrator waveform at the top, with the input, 4a), and output, 4b), pulses below. Measurements were taken using a Tektronix TDS210 storage scope.

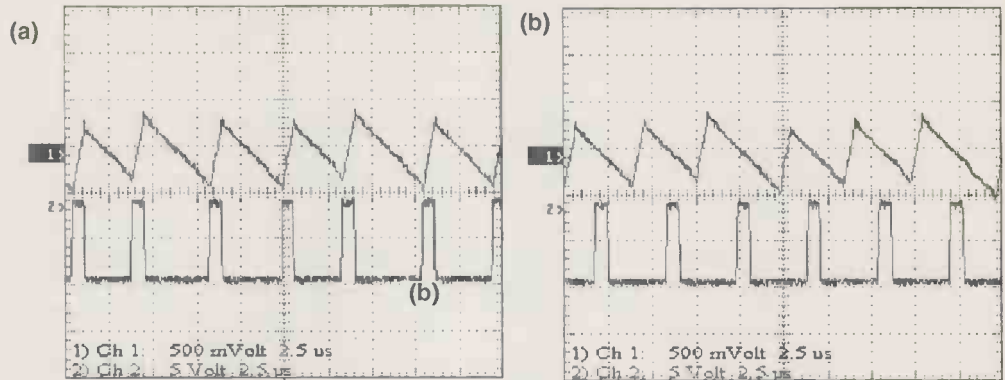


Fig. 4. Actual output from the anti-jitter demonstration circuit of Fig. 3. In each display shot, the upper waveform is integrator output. In the shot on the left, a), the pulses are the input while in the one on the right, b), the pulses represent output.

AJC refinements

For high-frequency operation, a variant called the 'adiabatic AJC' can be used. Here, the AJC integrator block is replaced by a diode/capacitor energy storage circuit, which is entirely passive: all its energy derives from the driving circuit.

The energy-conserving nature of this part of the circuit has led to it being dubbed an 'adiabatic AJC'. In this, a charging circuit pushes pulses of charge an integrator capacitor, while the charge on the capacitor is continuously leaked away.

The cup-and-leaky-bucket integrator. For high-frequency operation, a true integrator operation is difficult to achieve. A circuit that is faster and also simpler is what might be dubbed the 'cup-and bucket' integrator. In this, the input is arranged to transfer 'cups' of a small standard charge to the 'bucket' (integrator capacitor), the charge being leaked away continuously by a constant current source.

The cup part of the circuit could be a diode pump or a grounded-base transistor stage. The constant current source could be a transistor mirror, or,

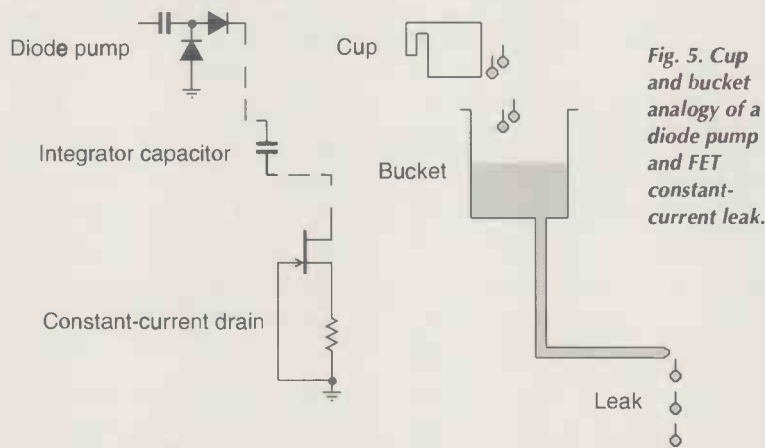


Fig. 5. Cup and bucket analogy of a diode pump and FET constant-current leak.

more simply, a FET with grounded gate, Fig. 5.

In a further refinement, using the FET current leak, a resistor and capacitor connected to the FET gate provide the DC subtract function as well.

Tracking large frequency changes. The 'lock on' time of an AJC – how long it takes to get pulses out – is not limited by the slewing of a voltage-controlled oscillator output frequency, as a phase-locked loop jitter reduction system might be.

In the AJC, signals flow directly through the circuit and thus the 'lock on' time is often just a fraction of an input pulse. However, on power up, and with large changes in frequency, the DC-subtract circuit needs charging up to operational voltage. This can be speeded up by the addition of diodes around the resistor, as shown on the simulation circuit below.

With these additions, it is often found that the AJC will not lose a single pulse during frequency switches – an important advantage in communications sys-

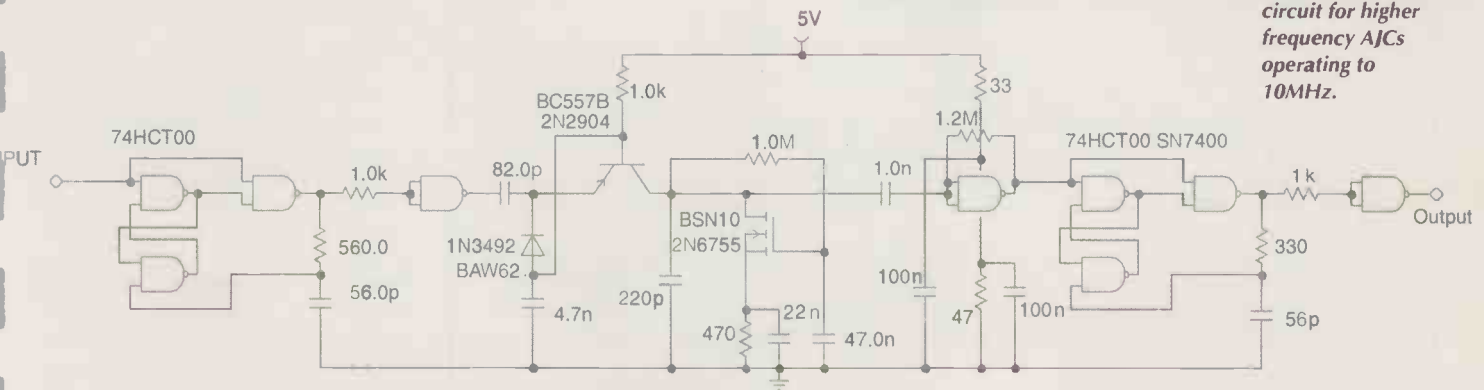


Fig. 6. Simulation circuit for higher frequency AJCs operating to 10MHz.

tems such as cellular radio where rapid switching is an absolute requirement. Be aware though that jitter suppression is reduced during a frequency switch: clearly it is a logical impossibility to reduce jitter to zero during switching unless the circuit had prior knowledge that the switch was coming.

In practice, jitter suppression may be reduced to only 10dB or so, with full 20-30dB jitter suppression reappearing after a time constant set by the circuit's DC subtraction.

The logic-gate AJC. The logic-gate AJC is the latest development, and will allow the widespread adoption of AJCs. As announced at the recent Besancon EFTF/FCS Conference, the new AJC design uses only straightforward logic gates for its active components.

This most recent step in the development of the AJC replaces another part of the block diagram of the conceptual AJC: the comparator output circuit. At high speed, true comparator circuits are relatively unusual on large, otherwise digital chips, and somewhat difficult, being an analogue technology.

In the AJC, the comparator can be replaced by using the preset logic threshold of a standard logic gate as the 'reference input', the logic gate input being the signal input, in the language of the comparator. Note that the AC coupling into the comparator needs to have a time constant longer by a factor of ten or so than the closest-in jitter sideband that needs to be suppressed. At the same time, it should not appreciably load the integrator.

The latest refinement of the AJC makes it simpler to implement, especially in IC technology, and especially when the AJC needs to be incorporated in a larger IC using standard cells, which often do not include a differen-

tial comparator function.

There's a number of other AJC variants for which there is insufficient space in this article. For example, the AJC can be used in a different mode where the input frequency is doubled before the first monostable, and then divided by two on the output. This gives some important facilities, such as the capability to de-jitter both leading and trailing edge of an input waveform, and can give a 'quieter' sawtooth waveform at the integrator.

We expect to uncover yet more versions of the AJC.

Higher-speed demonstration circuits

The discrete higher-speed demonstration circuit is intended for demonstration only. But with a little further tweaking it could find practical application in digital systems at up to around 10MHz.

The AJC is certainly capable of much higher speed than this, however. The simulation described below shows operation up to 50MHz with discrete component values, and 5GHz with micrometre-sized IC components, showing the kind of performance IC implementations of the AJC will have.

1-10MHz logic-gate demonstration circuit. Still under development, this circuit illustrates some of the latest AJC design principles described above. Note that because of its higher operating frequency this circuit is sensitive to layout, can both emit and receive spurious signals, and is somewhat sensitive to oscilloscope probing, Fig. 6.

As explained earlier, the high-speed comparator action needed is supplied by means of a logic gate circuit, which is simpler and faster than a genuine comparator.

Note that the gate is connected to the

power supply rails via by-passed current-limiting resistors. Although these limit the output voltage swing to 2V or so, they avoid any possible excess current flow in the gate. Here, the gate is being used as a quasi-analogue device so it could conduct strongly at certain input voltages and overheat.

As before the integrator is provided by the cup-and-leaky-bucket approach. The p-n-p transistor here forms the 'cup' part of the circuit, while the current source 'leak' is provided by the MOSFET. Finally, note the use of logic gates to form simple short-pulse monostables.

50MHz simulated circuit. This circuit can be easily modelled in any Spice-based analogue circuit simulator. Many AJC circuits can easily be modelled. However, in using simulators, it is important not to use time constants that are too long in DC subtract.

It may also help to preset node voltages to the values to near their final settling values, once you have found out what those are. Although a second may not be long to wait with a real circuit on an oscilloscope, simulating 50 million cycles on the average PC-based simulator will require serious patience, to say the least!

The version below assumes a transistor of beta of 0.5mA/V^2 , gate capacitances around 0.5pF and threshold 0V . Other values of these parameters will work too. The diodes must be high-speed, low-capacitance devices.

In practice, it may be difficult to make the circuit work because of the effects of stray capacitance and inductance and the effect of extended connecting wires in discrete circuits.

Figure 7a) shows the circuit, while diagram 7b) gives the printout from the SPICE-based TINA simulator, showing rapid $0.5\mu\text{s}$ lock-on of this simple circuit.

Removing jitter up to 5GHz. With the components shown, the circuit achieves around 50MHz. However, with components and stray capacitance values of the range normally encountered on submicron high speed IC circuits, the same simulator model can be made to run as high as 5GHz.

We expect that early IC versions of the AJC will not run quite this fast, but IC versions will run faster than the discrete circuits given above – certainly in the hundreds of megahertz. Such circuits could also form functional blocks within a much larger IC, for example,

Need more information?

Contact Dr Neil Downie, Maran & Co Ltd, via fax on +44 (0)1483 302112 or via e-mail using n.downie@maran.co.uk for the latest information. Other sources of AJC information are: 'Jitter Buster,' *Electronics World*, June 1999 p. 516.

'The Adiabatic AJC Circuit,' MJ Underhill, European Frequency Time Forum (EFTF) Frequency Control Symposium (FCS) Conference, Besancon 1999.

'The anti-jitter circuit for low spurious DDS square waves and low cost fractional-N synthesis,' MJ Underhill, S Stavrou, M Blewett, N Downie, European Frequency Time Forum, Warsaw, 1998.

'Performance assessment of a delay compensation phase noise and time jitter reduction method,' MJ Underhill, M Blewett, European Frequency Time Forum, Neuchatel, 1997.

'Spectral improvement of direct digital frequency synthesizers and other frequency sources,' MJ Underhill, M Blewett, European Frequency Time Forum, Brighton, 1996.

one of the ICs in a cellular or broadcast radio chip set.

Who needs an AJC?

Anti-jitter circuits are not merely a laboratory curiosity. At least a dozen applications for the AJC are currently being explored. No doubt, more will occur to people as knowledge of the technology spreads.

The most obvious uses for AJCs involve the reduction of jitter in systems, where it occurs. The output of direct digital synthesisers for example typically contains significant spurious sideband components. Normally these are dealt with by spreading the sideband power over a wider band, the so-called 'noise spreading direct digital synthesiser'. However, an AJC would suppress jitter, eliminating the sidebands entirely, and giving a lower noise overall system.

Similarly, simply adding an AJC to a phase-locked loop may well turn out to be a popular application. A PLL with a wide bandwidth is easy to design and has the desirable properties of rapid lock and a large lock-in range. However, it has the less desirable property of a high jitter output.

The PLL used for locking CRT displays is a potential user of this approach: the AJC may allow very large displays to avoid completely the tendency to have 'crawling lines' down the edge of the screen.

Why not add some jitter?

Although many AJC applications will simply be to reduce jitter in an existing system, others will revolve around the concept of putting jitter deliberately into a system to obtain other advantages, and then using the AJC to get it out again.

The seasoned electronic engineers among you might observe that the noise-spreading algorithm used in direct digital synthesis follows a similar philosophy. An example will illustrate: consider the PLL-based frequency synthesiser of Fig. 8.

If it is a good one, the VCO will produce little output jitter, and the divider chain will further reduce any residual jitter. The relative time jitter is divided by two when a waveform is divided by two in frequency.

The phase comparator compares the reference with the divided waveform and outputs a signal via the loop filter to move the VCO either up or down in frequency. This locks the VCO output to the reference. All this is a standard

PLL frequency synthesiser.

However, now consider the addition of the two blocks marked 'Pulse removal' and 'Fractional rate multiplier'. When it receives a signal from the rate multiplier, the pulse subtractor divides by 10 instead of 11, or simply blocks a single pulse.

Clearly, the new waveform is now just a fraction lower in average frequency. However, it also has a very high degree of jitter. The divide-by- N_p circuit reduces this, but it does not eliminate it.

Jitter penetrates the phase comparator and imposes a small variation on the loop-filter output. This results in the VCO having a small but highly undesirable frequency modulation. The addition of the AJC as shown allows this circuit to perform much better.


There are other circumstances where the ability to use circuits that add jitter can be useful. One example is clock restoration. On noisy lines, where a clock signal must be extracted, extra interference pulses may be present, or pulses may be missing. In this case, a pulse subtractor or pulse inserter may be used to correct the waveform.

Normally, such a situation is impossible, because the added pulses are too late, or the removed pulses are the wrong ones – the ones after the one that should have been removed. These problems raise the average jitter on the clock signal too much. With the AJC though, such circuits are practicable.


Other applications for AJCs

Anti-jitter circuit are likely be used in communications, for the main part. But there could be other significant application areas.

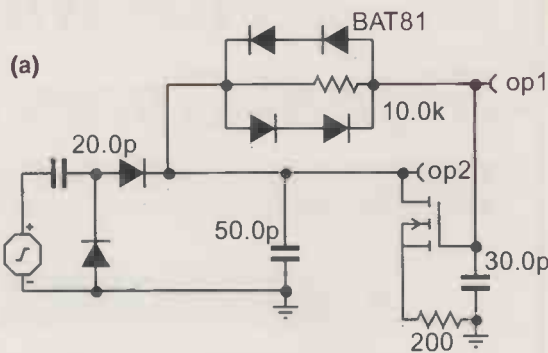In high-quality oversampled digital audio systems for example, there may be a case for using an AJC to de-jitter/retime the data. This would max-



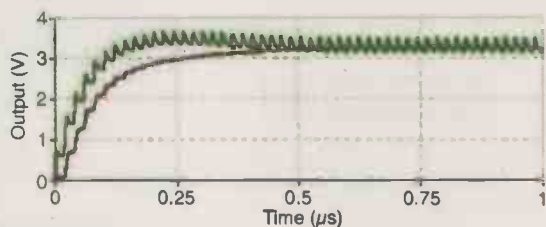FET is 300µA/VV, threshold 0V
op1 and op2 feed a high-speed comparator



(b)

imise the additional quality given by the oversampling and extrapolation circuits.

Similarly, complex multiphase clock circuits used on modern microprocessors could benefit from AJCs. A development of the AJC employs multiple comparators, which generate multiphase signals in a very natural and versatile way.

There may even be applications of the AJC that do not involve jitter. Mike Underhill observes, for example, that the DC subtract loop of the AJC can be modified so that it constitutes an FM/FSK demodulator.

Can you think of other AJC applications? ■

Note that the AJC and variants are covered by a number of patents and patent applications. Manufacture of AJC ICs or other uses of the AJC on a commercial scale may require a licence. Contact Maran & Co for details.

Fig. 7. De-jittering at up to 50MHz. This circuit simulation, a), works well, and locks in rapidly, as the plot in b) shows. This circuit will be difficult to implement though because of wiring inductance and stray capacitance.

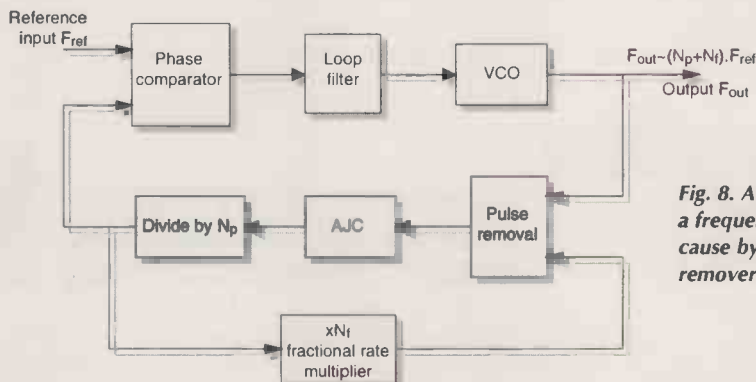


Fig. 8. Adding an anti-jitter circuit to a frequency synthesiser removes jitter cause by the action of the pulse remover removing a pulse.

You Can't Buy Better!

This Month is Anchor's Signal Generator MAYHEM Month

MARCONI 2019A Synthesised Signal Generators

80kHz to 1040Mhz AM-FM-CW LCD Displays
Complete with Lids etc. FULLY TESTED and Warranted

NOW ONLY £495.00

MARCONI 2022E Synthesised Signal Generators

10kHz to 1010Mhz LCD Display Fitted IEEE with covers
Small and Lightweight FULLY TESTED and Warranted

NOW ONLY £595.00

Frequency Counters

Racal Dana 9918
9 segment 560Mhz £75

Signal Generators

Farnell PSG520
10Mhz-520Mhz AM-FM Sinad ONLY £295
Rohde and Schwarz APN62
1hz to 260kHz with LCD display £995
Farnell DSG2
Synthesised 0.1mHz to 110Khz £195
Wavetek 155
Programmable VCG 0.01hz to 1Mhz sine,
square, triangle £195
Schlumberger FSD120M
Remote Synthesiser to 120Mhz in 0.01hz
steps
Was £175 . . . Reduced, Now ONLY £125

Oscilloscopes

TEK 2445

150Mhz Four Trace/2 Time base
with Cursors, etc. Now Only £495

TEK 2445A 150Mhz Four Trace/2 Time bases
with Cursors, etc. Now Only £995

TEK 2465 300Mhz Four Trace/2 Timebases
Now Only £1250

GOULD OS3500 with
DM3010 DMM fitted, 60Mhz
Dual trace, Dual Timebase

Was £350 . . . Reduced, Now ONLY £250

HP 1741A 100Mhz Storage. Dual Time base
Was £350 . . . Reduced, Now ONLY £250

TEK 465B 100Mhz Dual Trace/
Timebase Now Only £295

TEK 465M scope as 465B but built only
for Military. Only £350

TEK 475 200Mhz Dual Trace/Timebase
Now Only £395

Studio Quality AUDIO Equipment

Studer A710
Cassette desk with Dolby C. 1 ONLY £325
Uher 4000
Report monitor portable. To 9.5ips
1 ONLY £75

THIS MONTH'S SPECIALS

Philips PM3217 Scopes
DC-50Mhz 2 Trace/2 Timebase
A REAL Anchor Special ONLY £275



Gould OS300 Scopes
DC-20Mhz 2 Trace
SPECIAL NOW ONLY £150



Regulated Power Supplies

Thorn Automation
Variable power supply giving 0-40 volts at
0-50 amps DC. V and I limiting (advise
calling... these are heavy). 2 ONLY £125

Lambda Labs

LME5V 5V at 40A DC... ONLY £20
LMD12YV 12V at 10A DC... ONLY £20
LMB24V 24V at 1.4A DC... ONLY £7.50
LP523 variable 0-60V at 0.9A... ONLY £45

Farnell B30/10

Regulated + Stabilised Power supply. 0-30V
@10A £60

Miscellaneous

SE labs SE7000 instrumentation recorder
system

42 channel, 8 speeds from 15/16ips to
120ips, 1in tape complete with SE7000
patch panel... 1 ONLY £500

GIGA Pulse internal counter
2-8Ghz ONLY £150

Fluke 80-40K

High Voltage probe for DMM's 40kv. Cased.
NEW £45

Beckman Industrial HD110
LCD Multimeters in Leather case,
1000V, 10A
ONLY £50

ANCHOR SUPPLIES LTD

All prices are EX VAT and Carriage

MAIL ORDER A PLEASURE

The Cattle Market Depot, Nottingham NG2 3GY, UK

Tel: (0115) 986 4902 Fax: (0115) 986 4667

Also at Ripley, Derbys (01773) 570137 and Coalville, Leicestershire (01530) 811800

Robinair 14950A
Autobalance Refrigerant Leak Detectors in
Leather case
ONLY £35

Robin 3111V
Insulation/Continuity tester, cased
ONLY £75

ELF
16mm Cine Projectors... Various...
Model RM1... with sound ONLY £75
Model NT1 with Sound ONLY £145

NEW THIS MONTH

High Power RF attenuators
A pair of 10db oil-filled attenuators.
Mounted in a common heat sink assy.
Each rated at 100w 50 Ohms. BNC
connectors. OK well into UHF range.
As new condition ONLY £25

Emerson PL400 UPS
400VA Uninterruptable Power Supplies.
Built in 12v battery to give 230v @ 400VA
AC output to keep your computer running
when the main fail!
Small, modern. Tested working. ONLY £45

AVO Model 8 Mk 5/Mk 6
Multimeters . . . THE Standard
ONLY £85

NEW EQUIPMENT

DTA20 Oscilloscope 20Mhz
Twin trace incl probes ONLY £225

DTA40 Oscilloscope 40Mhz
Twin Trace incl probes ONLY £299

DTS40 Oscilloscope 40Mhz
Digital Storage twin channel
Cursors + readouts Incl. Probes. ONLY £399

AMM255 Automatic Mod Meter
1.5Mhz to 2Ghz, LCD IEEE488 ONLY £275

SCG50 Synth Clock Gen.
To 50Mhz, LED display ONLY £125

NEW SCOPE PROBES

X1/X10 switchable to 100Mhz
Complete with adaptors
Limit 2 sets per customer
ONLY £9.95

Visit our Web Site: www.anchor-supplies.ltd.uk email: sales@anchor-supplies.ltd.uk



All-pass filters, instrumentation amplifiers, simulated inductors and single-wire bidirectional communications links are among applications that benefit from transconductance op-amps, as Cyril Bateman has been finding out.

In the last issue of *Electronics World*, I mentioned a slightly unusual circuit function, the Norton current input amplifier, introduced by National in 1972. This month I take a look at circuits using an even earlier unusual technique – the transconductance op-amp, introduced in 1969.

I recall eagerly buying a CA3080, one of the first commercially available transconductance amplifiers, which I still have kept for posterity.

This early version was soon followed by improved versions. The most notable of these were the CA3094, which increased peak output current capacity to 300mA, and the LM13600, a dual transconductance amplifier.

What is an OTA?

A transconductance amplifier converts its input voltage into an output current proportional to the voltage difference at its differential input terminals, Fig. 1.

Traditionally, transconductance amplifiers have been used in gain-control circuits, modulators, multiplexers, multipliers, voltage-controlled oscillators and sampling circuits. These applications and many more for the CA3080, can be found in AN6668 from Harris Semiconductor, which is available for downloading.²

Two other Harris notes concentrate on applications that make use of the increased current output available from the CA3094. Note AN6077 details how

to use the CA3094, together with three transistors to build a complete 12W audio amplifier. This design is provided with bass and treble tone controls located in the amplifier's feedback loops. A companion RIAA preamplifier based on the CA3080 amplifier is also detailed.²

Class-A instrumentation amplifier

One especially useful aspect of the transconductance amplifier is its ability to produce a class-A instrumentation amplifier. Its differential voltage-input signal is converted to a single-ended output.

Obviously this can also be done using an off the shelf instrument amplifier, or the usual discrete three op-amp circuits.

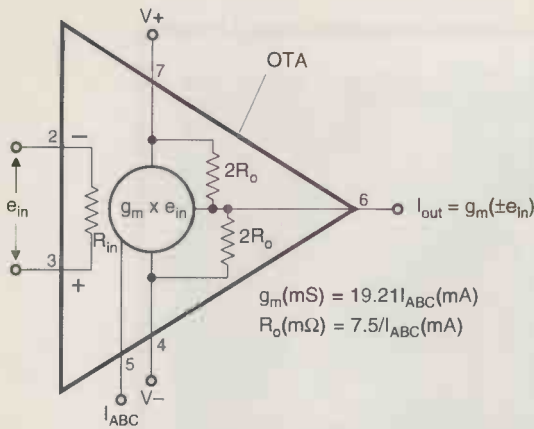


Fig. 1. Basic structure of the CA3080 transconductance amplifier. Differential input voltage results in an output current that can be scaled as needed.

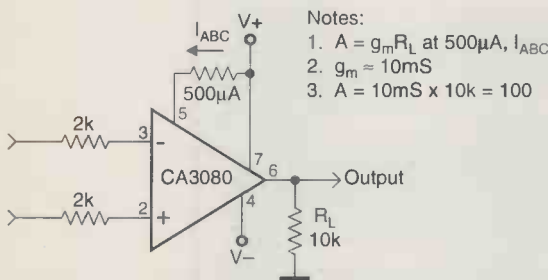


Fig. 2. Classical three amplifier in-amp requires precision matched resistors. A transconductance amplifier provides similar differential to single ended conversion but without needing precision resistors.

But these designs involving three op-amps need accurately matched feedback resistor networks to provide acceptable common-mode rejection.

Gain of the transconductance amplifier's preamplifier section can be changed by altering its transconductance and load resistance. As a result, no matched resistor networks are needed, Fig. 2. It was this particular attribute that I choose to investigate using Internet. I was searching for a circuit that I could use in a balanced input probe for my oscilloscope. In the process, I found several other interesting transconductance applications.

OTA fast enough for a 100MHz scope probe?

Many commercial instrument amplifiers provide excellent performance at low frequencies, but I wanted to avoid restricting my scope's 100MHz capability.

Prior to searching the Internet, I already had one particular integrated circuit in mind. Analog Devices produces a high-speed video difference amplifier. Known as the AD830, it has a unity-gain bandwidth of 100MHz.³ It combines a common mode rejection of 60dB at 4MHz with minimal video differential gain and phase errors.

This chip performs excellently as a high-speed differential amplifier up to

10MHz, Fig. 3. Could this limit be bettered without too much design effort?

During my searches I came across two other especially intriguing integrated circuits. One was from Maxim,⁴ the other from Burr-Brown.⁵ These opened up many new design possibilities.

Maxim provides two similar wide-band transconductance amplifiers, both having true-differential and fully-symmetrical inputs with relatively high impedance. Their unique architecture provides accurate gain without needing feedback, eliminating closed-loop phase shifts. Closed-loop phase shift is a primary cause of circuit oscillation in conventional high-speed amplifiers.

Unity gain bandwidth of 275MHz

The MAX435 has a unity gain bandwidth of 275MHz and provides both differential inputs and outputs. Its companion, the MAX436, has single ended output and a 200MHz unity-gain bandwidth.

Both offer 800V/µs slew rates and a 1% settling time of 18ns to a 0.5V step input. This performance is accompanied by a common mode rejection of 53dB at 10MHz and a 300µV DC offset voltage.

While these characteristics indicate an excellent high frequency perfor-

Y2K_Bugs

The recent conflict in Kosovo demonstrated the important role played by the US military Global Positioning System. On 22 August a very different GPS civil role was also tested, perhaps the very first

world wide trial in the countdown to the Millennium Bug, will have commenced.

The GPS navigation system relies on a precision clock which is used to calculate your position. This clock introduces its own particular version of the Millennium Bug consequently the GPS system

has to survive a double whammy, 21 August and 31 December.

For technical reasons, the GPS system time counts in weeks from 6 May 1980, the 1023rd week ends on 21 August. On 22 August the week count 'rolls-over' from 1023 to restart at 0. As with the year 2000 date change, some receivers and ground equipment will exhibit roll-over problems in August, with consequent positional errors.

This End of Week roll-over has a second perhaps more significant bearing on everyone. You may not need or use a GPS system yourself, but many commercial

institutions make use of its extremely precise global clock.

Some US banks use this clock to control their time locks, and to calculate the interest payable on international money transactions. Very fast digital networks, including Internet, can use this external clock to synchronise data transmissions. In the US, considerable fears have also been expressed concerning its use in electricity supply, switching control and power distribution.

Considerable data on the EOW roll over and its possible US implications can be found on Internet, but my searches revealed almost no details for other countries.

The US military performed its largest ever Y2K trial in April. This included all military uses for the GPS systems.¹ While these systems now claim compliance, the detailed test results are not yet publicly available, Fig. A.

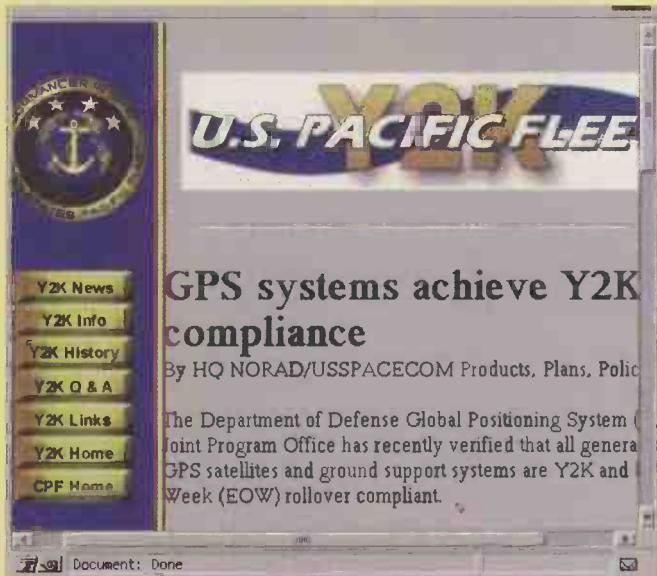


Fig. A. The Global Positioning System provides its own unique Y2K date bug, called End of Week roll-over, which repeats every 20 years. Many non-military time clocks depend on the GPS atomic reference for time stamping, but will they be affected ?

mance, both designs have a unique gain-control characteristic, which is even more interesting. Their gain is set by the ratio of two impedances and an internally set current gain factor, K.

The gain of many conventional instrument-amplifiers is set via the value of a resistor between two gain setting inputs. Gain of the MAX435 and MAX436 can also be set using a similar resistor. Amazingly though, both integrated amplifiers can also accept a complex impedance, rather than just a simple gain setting resistor. This is possible because their transconductance network's impedance has no interaction with output load impedance.

This complex impedance can be a series resistor and capacitor between the gain setting inputs. In this case the amplifier has a high-pass characteristic. The low corner frequency depends on the resistor and capacitor values. Adding a parallel capacitor resistor combination to ground at the amplifier's output then produces a band-pass amplifier.

Since no overall feedback is needed to control gain and ensure stability, these amplifiers can safely drive a high-capacitance load. Having no feedback network, the usual feedback phase shifts cannot occur, so the circuit remains stable.

The main effect of capacitive loading is a reduction in slew rate and output bandwidth, hence the low-pass amplifier characteristic.

Changing the OTA's characteristics

In similar fashion a series capacitor/inductor combination can be used between the gain setting inputs. This provides a sharply tuned amplifier

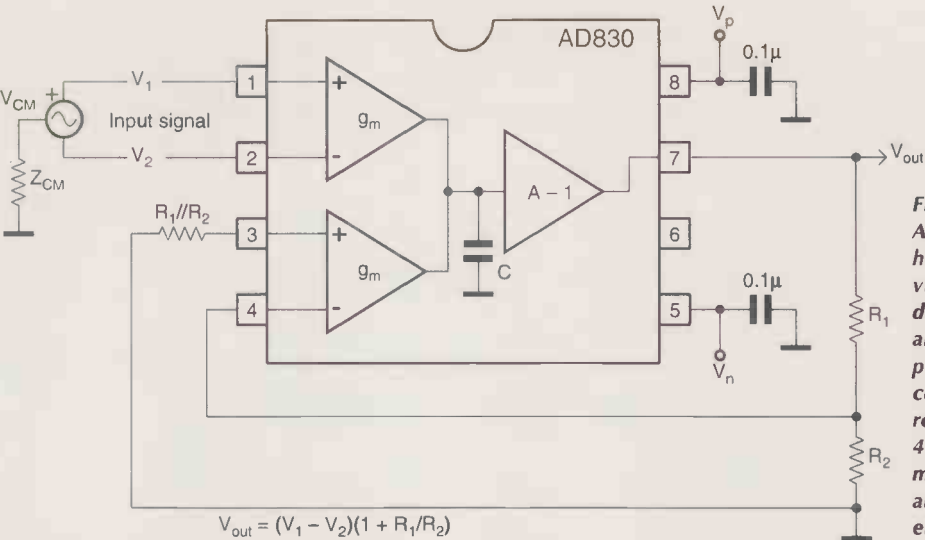


Fig. 3. The AD830, is a high-speed video differencing amplifier providing 60dB common mode rejection at 4MHz with minimal gain and phase errors.

$$V_{out} = (V_1 - V_2)(1 + R_1/R_2)$$

Where to surf

- | | |
|---------------------------------------|---|
| 1. GPS systems achieve Y2K compliance | http://www.cpf.navy.mil/y2k/y2knews/y2kgps.htm |
| 2. Harris Corporation | http://www.harris.com |
| 3. Analog Devices Inc | http://www.analog.com |
| 4. Maxim Integrated Products | http://www.maxim-ic.com |
| 5. Burr-Brown Corporation | http://www.burr-brown.com |

whose resonant frequency is determined by the capacitor and inductor values.



Such an arrangement is especially useful in a differential input, tuned selective amplifier. The tuned circuit is placed as near as possible to the amplifier inputs, rejecting unwanted signals and noise. Using a conventional instrument-amplifier, several stages of broadband amplification precede any tuning circuits, reducing circuit performance

when subject to out of band signals.

Most surprising of all, to increase the Q of a tuned amplifier, the MAX 435 and 436 can even be used with a crystal connected between their gain setting inputs. The data sheet shows the measured performance of a MAX436 tuned amplifier with a 25MHz crystal. The circuit produced a narrow gain peak of more than 40dB, while driving a 25Ω load. This load can be a doubly terminated 50Ω coaxial cable.

Video over a 5km twisted pair

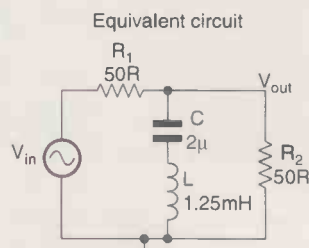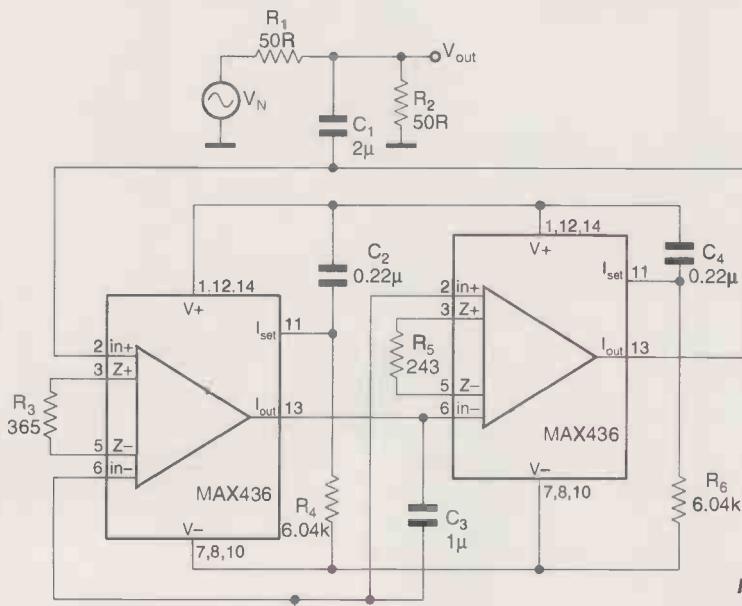The final data-sheet application shows a 435 and 436 being used to transmit a single baseband video channel over a



$$\frac{V_{out}}{V_{in}} = \left(\frac{R_1}{R_1 + R_2} \right) \left(\frac{S^2 + 1/LC}{S^2 + S(1/R_1 // R_2/L + 1/LC)} \right)$$

$f_o = \text{corner frequency} = 1/(2\pi\sqrt{LC})$

$Q = \sqrt{LC} = 1/(R_1 // R_2)$

Fig. 4. Using two MAX436 transconductance amplifiers to synthesise a 1.25mH inductor provides a DC accurate 3.2kHz notch filter.

twisted-pair wire. Using these two amplifiers, good quality video can be transmitted up to 5km with a considerable cost saving compared to using coaxial cables.

Maxim application notes, available from the company's web page, provide a further five applications which use the unique properties of these chips. Three of these applications use

MAX436 amplifiers to simulate inductors, providing freedom from EMI and improved circuit performance. These can all be quickly downloaded as small PDF files.


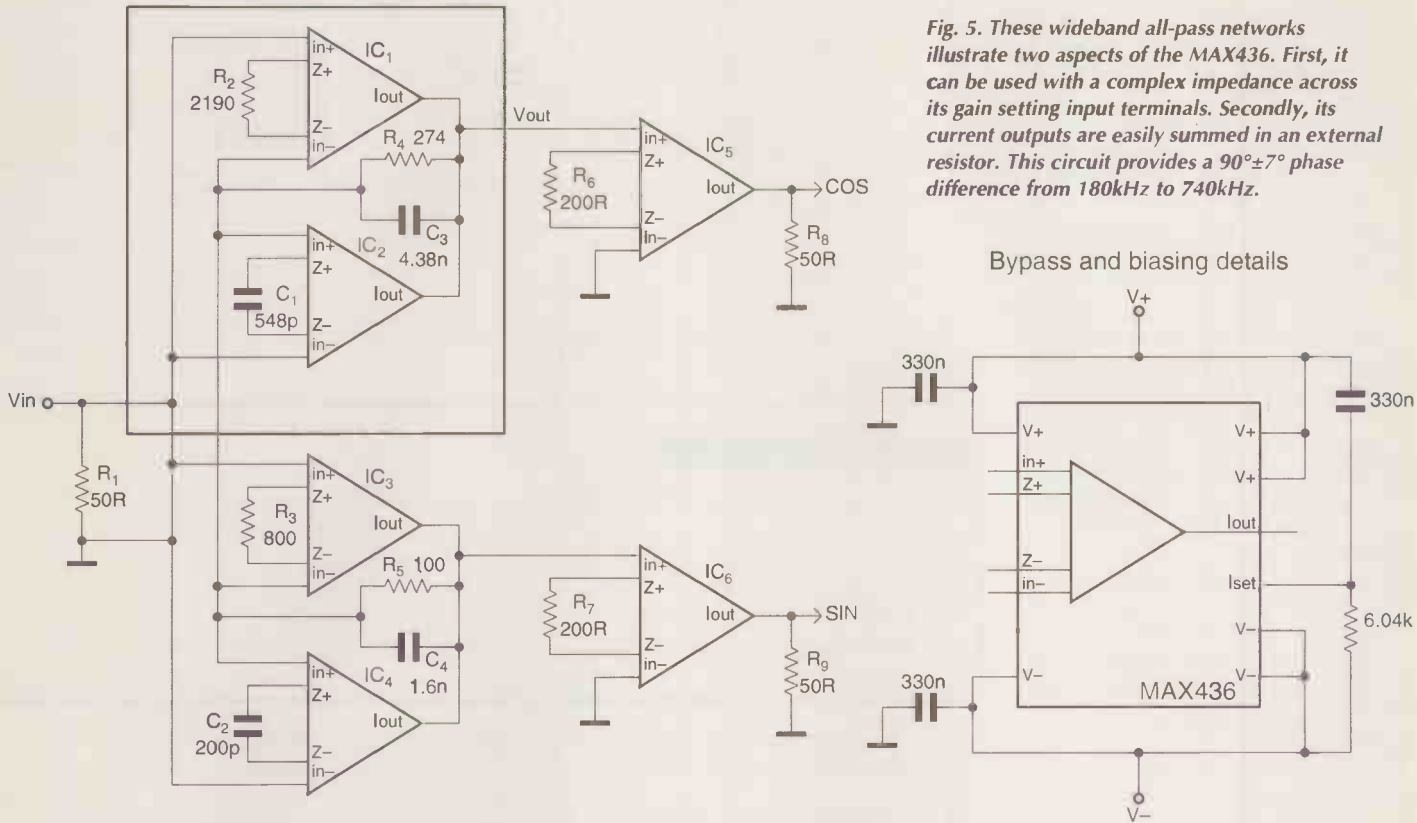



Fig. 5. These wideband all-pass networks illustrate two aspects of the MAX436. First, it can be used with a complex impedance across its gain setting input terminals. Secondly, its current outputs are easily summed in an external resistor. This circuit provides a $90^\circ \pm 7^\circ$ phase difference from 180kHz to 740kHz.

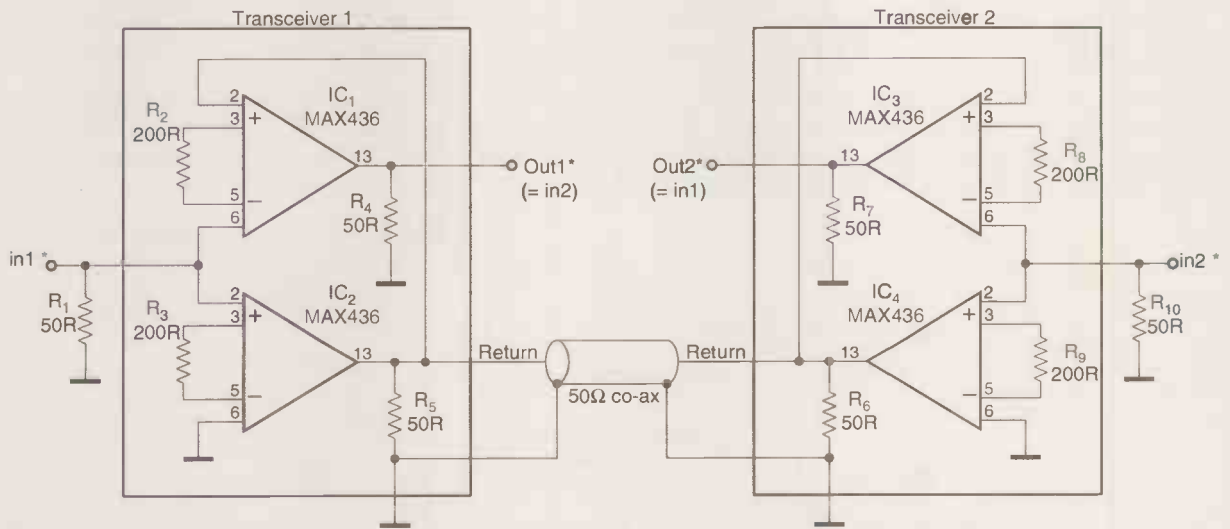

* Note: to maintain 0dB gain as required the inputs must see 50Ω sources. The outputs must also see 50Ω loads. You can also configure 0dB gain by substituting 75Ω cables, 75W terminations and 300Ω for the gm setting resistors R_2, R_3, R_9 and R_6

Fig. 6. Simple and cost effective method for transmitting bi-directional signals along coaxial cables. This method provides for megahertz bandwidths with 30dB discrimination between forward and reverse signals.

MAX436 connections
4 places

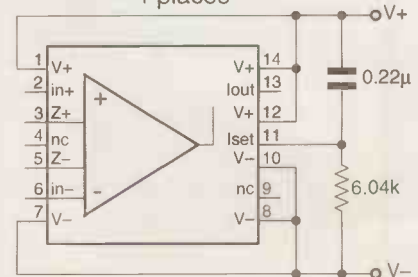

A DC accurate notch filter circuit is described in application note A2013.PDF. By separating the DC and AC paths, this circuit avoids using op-amps in the DC path, making it free from DC offsets and gain errors.

The AC path uses a capacitor in series with a simulated inductor to ground. This simulated inductor is formed using two transconductance amplifiers, Fig. 4.

Simulating inductance

A 3.2kHz third-order high pass filter using two 436 op-amps to simulate a 1.25mH inductor is detailed in A1315.PDF. This filter attains a slope of 58.6dB per decade – very close to the theoretical 60dB slope of a perfect filter.

Achieving similar performance in a passive filter could prove difficult. A practical inductor of this value has significant ESR and its inductance falls at low frequencies.

Application note A1616.PDF describes a 50Ω output 9.3MHz sinewave LC oscillator with 1% distortion, produced using a single 436.

While these are interesting application circuits, two others particularly caught my eye. Some time ago a reader asked for a circuit that could generate a 90° phase shift at moderate audio frequencies. Providing this phase shift at a discrete frequency is easy, but much more difficult with dynamic and mixed frequencies.

Application note A1610.PDF illustrates such a circuit. As presented it is intended for higher frequencies, but it can be re-scaled for audio frequencies. These transconductance amplifiers provide a current output. As a result, simply tying their output terminals together into a single resistor, Fig. 5, can sum the outputs from two or more amplifiers.

This application uses two transconductance amplifier pairs to form an all-pass network. Each pair comprises one amplifier with a resistor between its gain setting terminals, the second having a capacitor between these terminals. Both amplifier outputs are then summed using a common output resistor.

By choosing appropriate corner fre-

quencies, one amplifier pair generates the cosine of the input waveform while the second pair generates the sine of the input, producing the desired 90° phase shift. It can be used with dynamic signals covering three octaves.

Bidirectional drive over coaxial cable

The last application note was the most interesting. Entitled 'WTAs provide wideband, bidirectional drive for coaxial cable', it describes four 436s in a circuit arrangement similar to that used in telephone systems. It is able to send signals in two directions simultaneously on the one cable, Fig. 6.

In this case the cable is coaxial. Signals from audio up to RF can be transmitted in both directions at the same time. Using these high-speed transconductance amplifiers with 1% resistors produces around 30dB of cancellation of the unwanted signals on either output.

In my next piece, I will be looking at the versatile and interesting high speed 'diamond' transistor circuit from Burr-Brown.

**WATCH SLIDES ON TV
MAKE VIDEOS OF YOUR SLIDES
DIGITISE YOUR SLIDES**
(Using a video capture card)



"Llesgang diatv" automatic slide viewer with built-in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use £91.91 + VAT = £108.00
Board cameras all with 512 x 582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts.
They all require a power supply of between 10 and 12v DC 150mA.
47MIR size 60 x 36 x 27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye)..... £50.00 + VAT = £58.75
40MP size 39 x 38 x 28mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole..... £50.00 + VAT = £58.75
40MC size 39 x 38 x 27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses..... £38.79 + VAT = £45.58
Economy C mount lenses all fixed focus and fixed Irls.
VSL1220F 12mm F1.6 12 x 15 degrees viewing angle..... £15.97 + VAT = £18.76
VSL4022F 4mm F1.22 63 x 47 degrees viewing angle..... £17.65 + VAT = £20.74
VSL6022F 6mm F1.22 42 x 32 degrees viewing angle..... £19.05 + VAT = £22.38
VSL8020F 8mm F1.22 32 x 24 degrees viewing angle..... £19.90 + VAT = £23.38
Better quality C Mount lenses
VSL1614F 16mm F1.6 30 x 24 degrees viewing angle..... £26.43 + VAT £31.06
VWL813M 8mm F1.3 with Iris 56 x 42 degrees viewing angle..... £77.45 + VAT = £91.00
Blue and silver recordable CD ROM bulk..... £0.766 + VAT = £0.90
With jewel case..... £1.00 + VAT = £1.18
P6KE103A 130v diode..... £0.98p + VAT = £1.15 20 for £13.00 + VAT = £15.28
RC300 Philips universal remote control.5 for £24.45 + VAT (£4.69 + VAT each) = £27.55
Konig Ultrasonic remote control clearout, limited quantities. Quantity left in brackets:
US8207 (15), US8209 (5), US8220 (4), US8224 (5), US8225 (2), US8232 (3),
US8233 (2),US8239 (8), US8260 (1), US8264 (124), US8265 (116), US8302 (2),
US8306 (1), US8309 (1), US8406 (1), US8513 (21), US8514 (40), US8516 (19),
US8519 (2), US8535 (82), US8578 (182).....
..... £5.50 + VAT each, £22.00 + VAT for 5, £85.00 + VAT for 25.
1206 surface mount resistors E12 values 10 ohm to 1m ohm
..... 100 of 1 value £1.00 + VAT, 1,000 of 1 value £5.00 + VAT
Please add £1.66 + VAT = £1.95 postage & packing per order

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield S40 2BH
Tel: 01246 211202 Fax: 01246 550905
Callers welcome 9.30am to 5.30pm Monday to Saturday

CIRCLE NO.134 ON REPLY CARD

PPM5
20 PIN DUAL IN LINE

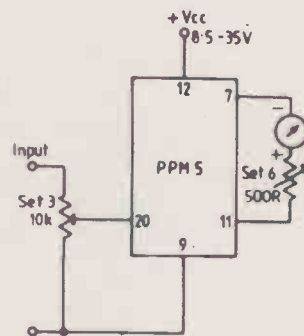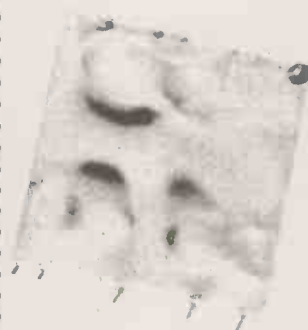

Mother Board MB1

Consumption 3mA.

Fully meets BS5428-9

- ★ PPM10 In-Vision PPM and Chart Recorder
- ★ Advanced Active Aerial 4kHz-30MHz
- ★ Stabiliser frequency shift units for howl reduction
- ★ Stereo Variable Emphasis Limiter
- ★ PPM9, PPM5 hybrid and PPM8 IEC/DIN -50/+6dB drives and movements
- ★ Broadcast Monitor Receiver 150kHz-30MHz
- ★

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh GU6 7BG
Telephone: 01483 275997 Fax: 01483 276477

SVGA GENERATOR

Roy Harding's VGA and SVGA test generator uses a PIC variant that's so fast that it is capable of producing the test signal without any external timing circuitry, making the hardware side easy to implement.

As an electronics design engineer in the computer industry, I often get asked by friends and relatives to check or repair computers and monitors. If someone arrives with just a monitor for checking this involves wiring up a PC with a keyboard and mouse, then loading software and waiting while the whole thing boots-up.

The addition of a computer also takes up valuable workspace if one is working in a confined area. There are a few SVGA generators already available on the market, but the cost of these can only be justified if you are doing servicing or repairs full time, rather than as a favour.

Last year I was introduced to a new microcontroller from Scenix. This micro uses a combination of PIC code with additional instructions to enhance performance.

The device can operate up to 50MHz. It has a turbo setting to cancel the clock's internal divide-by-four, as found in PICs. This gives you 50MIPS performance, coupled with 2048 bytes of E2 flash memory, an eight-level stack and easy page switching. There's also 30mA source/sink capability on the I/O pins, which makes the device very useful.

As this micro works so fast, I thought of the idea of using it to create a video

generator that could work up to high resolutions. The generator described will generate standard VGA signals at 640 by 480 pixels and popular SVGA displays of 800 by 600 and 1024 by 768, all at 60Hz frame rate.

How it works

As already mentioned, the micro is the basic building block for the complete design, only a handful of additional parts being required to complete the implementation. All timings are created in software by the microprocessor

using an external 40MHz-oscillator clock IC.

Although a crystal and capacitors can be used for the oscillator circuit I have found crystals over 30MHz difficult to obtain. A voltage regulator and a few LEDs are the only additional semiconductors.

My PCB has two buttons, a power connector, a 15-way video connector and a few resistors and capacitors to complete the component count.

The LEDs indicate the display resolution setting, as it is not obvious from

VGA waveform, 640 by 480

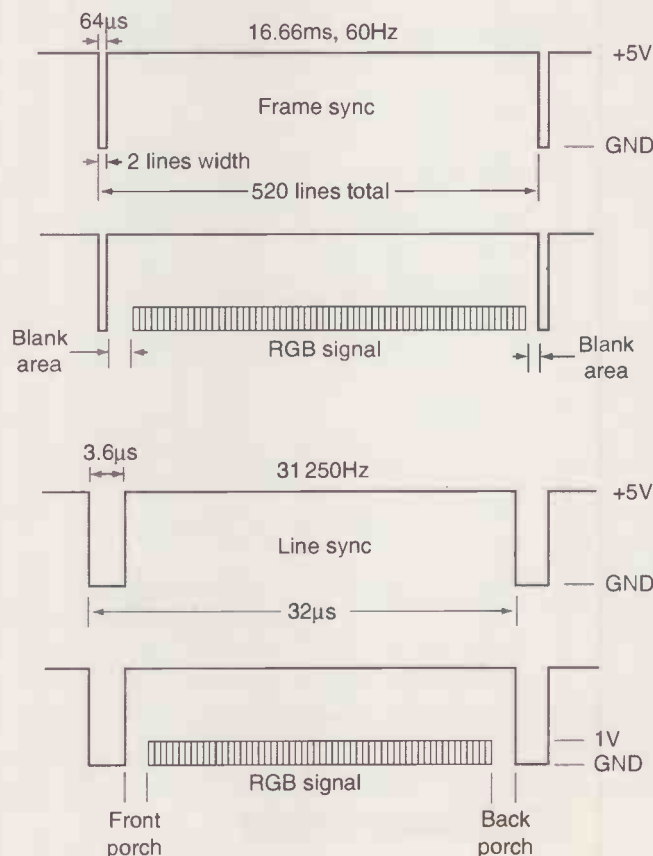


Fig. 1. Timings for a VGA signal's frame and line sync pulses.

Table 1. Forms of the signals needed to drive an SVGA monitor.

Vertical sync	5V TTL, negative going
Horizontal sync	5V TTL, negative going
Red	1V analogue signal, positive going
Green	1V analogue signal, positive going
Blue	1V analogue signal, positive going

the monitor display which resolution is being used. Also, if the monitor is not capable of displaying SVGA you will possibly be looking at a black screen.

Although the design can run on batteries and tags are provided on my PCB, I use a ready available 9V mains adapter. After all, you need the mains to power the monitor anyway and batteries have a habit of going flat just when you need them.

There are five signal lines used to drive a standard video monitor, as in Table 1. There are also ground returns for all these signals at the connector.

An example of the timings for a VGA signal is shown in Fig 1. Vertical and horizontal sync signals are driven directly from the microprocessor. The RGB analogue signals are attenuated by a resistor divider network to give a maximum of 1V output into a 75Ω load.

Software

The whole design revolves around software running on the Scenix microprocessor.

Timings for the functions are critical. Each scan line must be balanced to

within a couple of instructions or tearing of the image will result.

Button presses are checked at the beginning of each frame and a software trap waits for the button to be released for the changes to take place.

The first button changes the displayed output and the second button changes the resolution. Each button press changes the parameters of the main loop which are present in a software table.

The complete code is shown in List 1. Note that a special Parallax serial programming adapter is required to program the Scenix parts.

On my PCB, the programmer plugs directly onto the four-way connector next to the micro and the crystal oscillator link removed while programming, Fig 2.

Implementing the design

The unit can be housed in a two-piece plastic moulding with built-in mounting posts for the PCB. All parts can be mounted directly on the board and no wiring needs to be involved in the construction.

As the unit is based on a crystal

clock, no set-up procedure or calibration is required. I estimate only a two to three hour construction time if all parts are available. This will of course be extended if you decide to produce your own printed circuit board.

You may socket the microprocessor, but it can be reprogrammed on board making removal unnecessary.

The mains adapter can be regulated or unregulated, 9-12V at 300-500mA. Test the unit by connecting a VGA or SVGA monitor to the output and switching on the unit. The generator will default to colour bars in standard VGA mode of 640*480. Pressing the buttons should change patterns and resolutions.


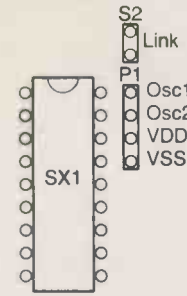


Fig. 2. On my prototype PCB, the programmer plugs directly on to a four-way connector next to the microcontroller. The crystal oscillator link is removed while programming.

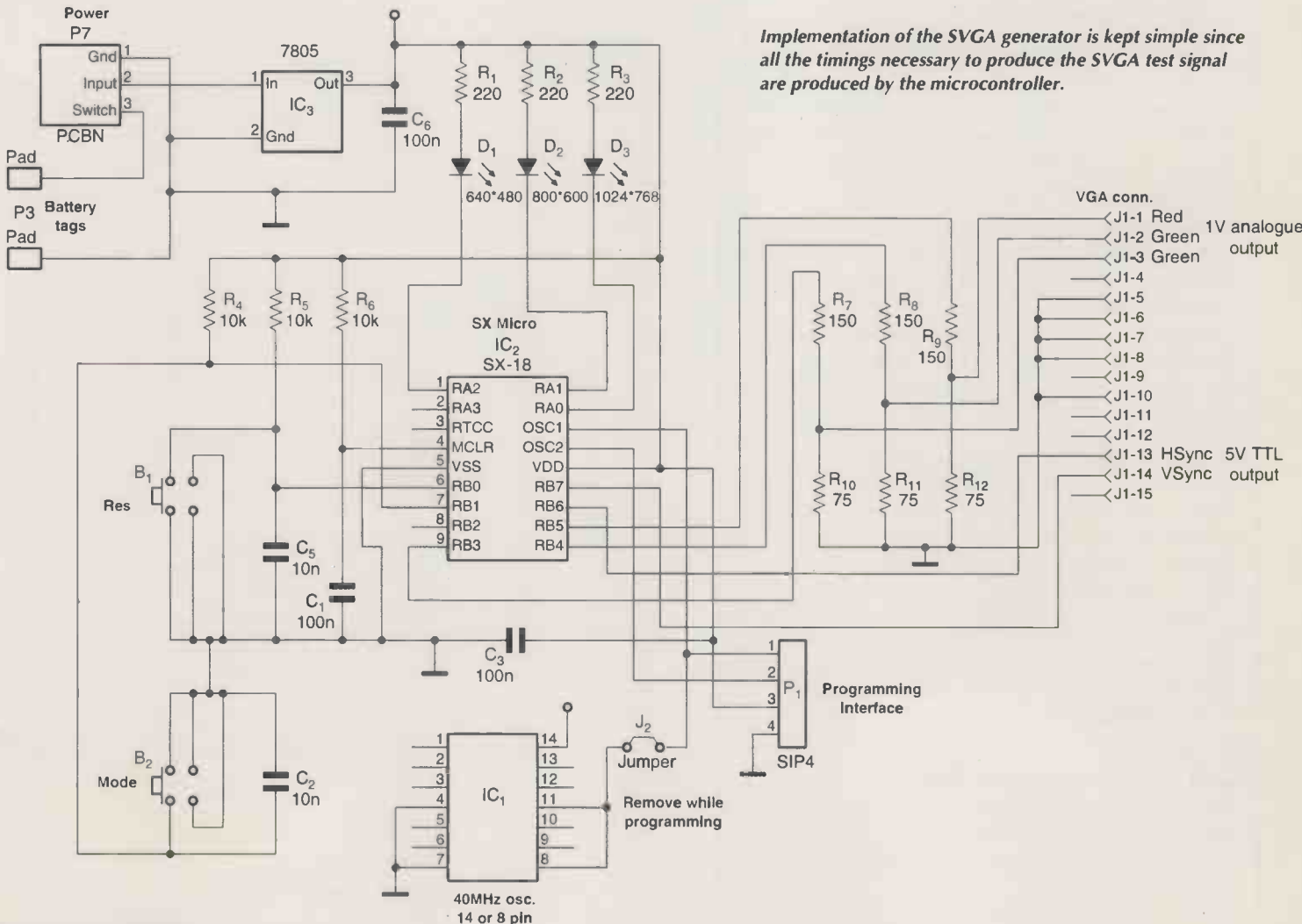Implementation of the SVGA generator is kept simple since all the timings necessary to produce the SVGA test signal are produced by the microcontroller.



Components

Resistors 1/8 watt 5% carbon film:

- R_{1,2,3} 220
- R_{4,5,6} 10k
- R_{7,8,9} 150
- R_{10,11,12} 75

Capacitors 50V polyester or ceramic:

- C_{1,3,4} 0.1µF
- C_{2,5} 0.01µF

- D_{1,2,3} 3mm red leds
- B_{1,2} vertical push switch
- P₁ 4 way 0.1 pitch pins
- J₂ 2 way 0.1 pitch pins + jumper

J₁ is 15-way min D-type 90°, Maplin part JW85G.

Connector P₇ is a 3.5mm power connector from Farnell, part 224-959.

IC₁ is a 40MHz CMOS or universal oscillator 8-pin or 14-pin, Farnell 704-738 for example

IC₂ is the Scenix SX18/AC/DP processor, 18-pin version

IC₃ is a 7805 5V positive regulator

Suggested case, Farnell part 250-030. Mains adapter, 9-12V 300mA from CPC.

Approximate build cost £20 plus mains adapter.

New circuit board service from Quickroute

Electronics CAD specialist Quickroute, in conjunction *Electronics World*, is offering a new printed circuit board service to readers of *Electronics World*.

You can obtain single-sided boards based on Roy's original design direct from Quickroute for a fully inclusive price of £14.69. To order, fax your credit card number and expiry date together with the cardholder's address to 0161 4760505. Alternatively, ring Quickroute on 0161 4760202. If you wish to order by post, write to Quickroute at Regent House, Heaton Lane, Stockport SK4 1BS and send a postal order or cheque payable to Quickroute Systems Ltd.

Overseas readers should contact Quickroute before ordering for details of postage.

Alternatively, you can obtain a disk of the PCB layout in Quickroute form by sending £12.50 via postal order or cheque payable to Reed Business Information to SVGA, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Need a programmed controller?

All parts, pre-programmed chips and software on disk can be obtained from the author by sending an SAE marked 'SVGA software' to the Quadrant House address above for details.

A word of warning

If you try to run a monitor on a resolution that it is not capable of displaying, it is possible to cause damage to its internal circuitry. Therefore, if the display fails to appear on an increased resolution within a few seconds, switch back

immediately to a lower resolution.

I used a self-adhesive label on the front panel to make the unit more professional. The artwork was done on a PC and printed out on a colour ink jet printer using glossy self-adhesive paper. ■

List 1. Complete software listing for the SVGA generator.

```

; VGA & SVGA Display
; colour bar and crosshatch screen displays, by C R Harding
; Parameters for 40MHz crystal. Finished version 1.01
;port bit 7 frame sync
;port bit 6 hsync
;port bit 5 RED
;port bit 4 GREEN
;port bit 3 BLUE
;port bit 1 Button1
;port bit 0 Button2

device pins18,pages2,banks1,oschs,turbo
device stackx,optionx,protect
id 'CRH SVGA'
reset start
org 8

count ds 1
port ds 1
temp ds 1
temp1 ds 1
temp2 ds 1
temp3 ds 1
pattern ds 1
flag ds 1 ;10h
res ds 1
colour ds 1
T1 ds 1
T2 ds 1
T3 ds 1
T4 ds 1
T5 ds 1
T6 ds 1 ;18h
T7 ds 1
T8 ds 1
T9 ds 1
T10 ds 1
T11 ds 1
T12 ds 1
T13 ds 1
T14 ds 1
org 100h

start ;setup ports
mov !rb,#%00000011 ;port B 6 out 2 in
mov !ra,#%00000000 ;port A all out
mov port,#255
mov pattern,#0 ;colour bars
mov res,#0 ;vga

mainloop
mov flag,#0 ;reset interrupt flag
cje res,#0,vga ;vga
cje res,#1,svga1 ;svga1
cje res,#2,svga2 ;svga2

vga ;640*480 31250Hz
mov T1,#5 ;Front porch delay
mov T2,#26 ;Line sync width 3.6uS
mov T3,#30 ;Frame blank lines start
mov T4,#12 ;Frame blank lines end
mov T5,#32 ;Colour bar width delay 26
mov T6,#160 ;Number of lines(*3)
mov T7,#2 ;number of lines in fsync
mov T8,#97 ;line delay length 28uS
mov T9,#30 ;chequer lines
mov T10,#8 ;chequer squares
mov T11,#59 ;crosshatch lines
mov T12,#9 ;chequer delay
mov T13,#16
mov T14,#10
mov ra,#%00000011 ;led 3
jmp frameloop

svga1 ;800*600 37880hz
mov T1,#4 ;Front porch delay
mov T2,#23 ;Line sync width 3.2us
mov T3,#24 ;Blank lines start
mov T4,#8 ;Blank lines end
    
```

Continued on page 875

WEB DIRECTIONS

To reserve your web site space contact Joannah Cox

Tel: 020 8652 3620 Fax: 020 8652 8938

AQUILA VISION

<http://www.aquila-vision.co.uk>

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general Interest CD-ROM's.



ALCATEL COMPONENTS

<http://www.components.alcatel.com>

ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

ARCOM

<http://www.arcomcontrols.com/ew/>



A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

BROADCASTING COMMUNICATIONS SYSTEMS

www.broadercasting.co.uk

WINRADIO now brings you a complete choice in personnel computer controlled radio scanning and reception solutions ● Broadcast ● Media ● Monitoring ● Professional Amateur Radlo communications

BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseefa optocouplers tubular and surfacemount, panel mount LED assemblies.

CAMBRIDGE MICRO PROCESSOR SYSTEMS LTD

<http://www.cms.uk.com>

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are speciallsts in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

CONTROL SOLUTIONS

www.controlsolutions.co.uk

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: info@controlsolutions.co.uk.

COOKE INTERNATIONAL

<http://www.cooke-int.com>
e-mail: info@cooke-int.com



Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

CROWN HILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.



DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/k/eng.html>


Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

DISPLAY ELECTRONICS

<http://www.distel.co.uk>

EQUINOX TECHNOLOGIES UK LTD


<http://www.equinox-tech.com>

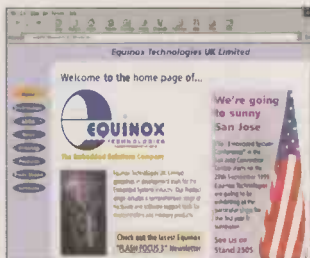

Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

ELECTRONICS WEEKLY HYPERACTIVE

<http://www.electronicweekly.co.uk/>

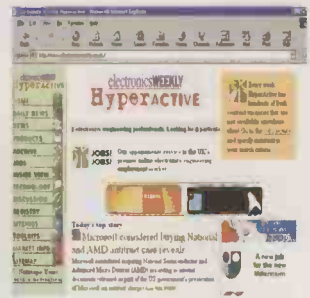

ECM SELECTION

<http://www.ecmsel.co.uk>

For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager -- £22,000 - £70,000



EPT EDUCATIONAL SOFTWARE

<http://www.eptsoft.demon.co.uk>

Electronics, Electrical and Mathematics Principles V6. Over 700 colourful interactive topics from Ohm's Law to PIC microcontrollers. Email sales@eptsoft.demon.co.uk for full details.

FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FLASH DESIGNS LTD

<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (€39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMELE AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now. Watch out for Special Offers'. ARE YOU developing code in a Flash?

HSPS LTD

<http://dSPACE.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

LOW POWER RADIO SOLUTIONS


<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>

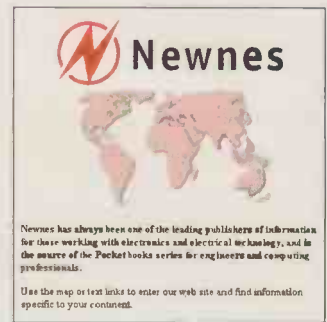Over 300 books and information packages for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads



OMEG POTENTIOMETERS

<http://www.omeg.co.uk>

Omeg 16mm and 20mm potentiometers and switched potentiometers with conductive polymer tracks. Web site has full product details, latest news, company contacts, stockists and distributors.

PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RADIOMETRIX


<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

RD RESEARCH

<http://www.looking.co.uk/spice>

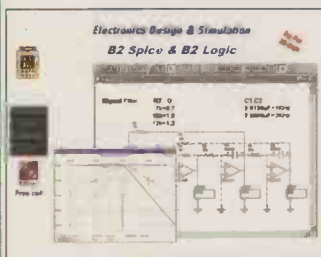Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.



RALFE ELECTRONICS

professional test & measurement
www.ralfe-electronics.co.uk



RS COMPONENTS LTD

<http://rswww.com>

The award winning on-line service from RS

- 110,000+ products available
- Technical data library
- Stock availability check
- Integrated on-line purchasing
- Order by 8pm - with you tomorrow.



SUPRA AUDIO CABLES

<http://www.jenving.se>

Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.



SOFTCOPY


<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

SESCOM, INC.

<http://www.sescom.com>

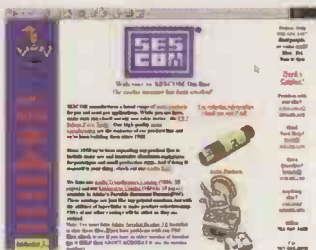SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.



SWIFT EUROTECH

<http://www.swiftdesigns.co.uk>

EDWin NC - Professional EDA software at 90% discount! Integrated schematics, PCB layout and simulation. Plus CAMtastic! CAM software and netlist translators for most EDA systems.

THOSE ENGINEERS LTD

<http://www.spiceage.com>


Working evaluations of SpiceAge mixed-mode simulator, Spicycycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

THERMOSPEED

<http://www.thermospeed.co.uk>

Temperature and pressure, control and instrumentation. Full on-line purchasing.

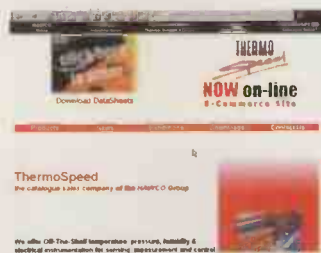- * Overnight ex-stock delivery
- * Create your own hotlist
- * Download datasheets
- * Full technical support



TRIDENT MICROSYSTEMS LTD

<http://www.trident-uk.co.uk>

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TRUMETER

<http://www.truemeter.com>

TRANSONICS

<http://www.transonic.com>

VANN DRAPER ELECTRONICS LTD

<http://www.vanndraper.co.uk>

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>

VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

WOOD & DOUGLAS

<http://www.woodanddouglas.co.uk>

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

To reserve your
web site space
contact
Joannah Cox

Tel:
020 8652 3620
Fax:
020 8652 8938

WEB DIRECTIONS

Put your web address in front of 21,000 Electronics fanatics. Electronics World acknowledges your company's need to promote your web site, which is why we are now dedicating pages in every issue to WEB ADDRESSES. This gives our readers the opportunity to look up your company's name, to find your web

address and to browse the magazine page to find new sites. We also understand that cost is an important factor, as web sites are an added drain on budgets. I am sure you will agree these rates make all the difference.

FOR 12 ISSUES:
Lineage only will cost £150 for a full year just £12.50 per month. This includes your company's name, web address and a 25 word description.

Lineage with colour screen shot will cost £350 for a full year just £29.17 per month. This will include the above plus a 3cm screen shot of your site, which we can produce if required. To take up this offer or for more information ring Joannah Cox on 020 8652 3620 or fax on 020 8652 8938. E-mail: joannah.cox@rbi.co.uk

Company name	Web address

	mov	T5,#25	;Colour bar width delay 20		nop	
	mov	T6,#200	;Lines*3		jmp	frameloop
	mov	T7,#4	;92.8us	redscreen		
	mov	T8,#79	;line delay length 23.2us		mov	temp,T3 ;frame blank1
	mov	T9,#25	;chequer lines	r1	call	blackline
	mov	T10,#12	;chequer squares		djnz	temp,r1
	mov	T11,#49	;crosshatch lines		mov	temp2,T6 ;160 vga 200 svga
	mov	T12,#4	;chequer delay	r2		
	mov	T13,#5			call	redline
	mov	T14,#13			djnz	temp2,r2
	mov	ra,#%00000101	;led 2		mov	temp2,T6 ;160 vga 200 svga
svga2	jmp	frameloop		r3		
	mov	T1,#7	;Front porch delay		call	redline
	mov	T2,#13	;line sync width 2us		djnz	temp2,r3
	mov	T3,#24	;Blank lines start	r4	mov	temp2,T6 ;160 vga 200 svga
	mov	T4,#4	;Blank lines end			
	mov	T5,#19	;Colour bar width delay 15		call	redline
	mov	T6,#256	;Lines*3		djnz	temp2,r4
	mov	T7,#6	;120us	r6	mov	temp,T4 ;frame blank2
	mov	T8,#59	;line delay length 19us		call	blackline
	mov	T9,#24	;chequer lines		djnz	temp,r6
	mov	T10,#16	;chequer squares		jmp	frameloop
	mov	T11,#47	;crosshatch lines			
	mov	T12,#1	;chequer delay			
	mov	T13,#9		linesync		;3.8us
	mov	T14,#7			and	port,#%10111111
	mov	ra,#%00000110	;led 0		mov	rb,port
frameloop					mov	count,T2 ;delay loop
	mov	temp,rb	;buttons check		call	dly
	and	temp,#3			or	port,#%1000000
	cje	temp,#3,exit	;exit if buttons not pressed		mov	rb,port
	call	button			call	linedly
	cje	flag,#1,mainloop	;jump to mainloop if set		call	linedly
exit				bars		;7 bars red to white
fsync						
	and	port,#%01111111	;bit 7 low vertical sync		cjne	res,#2,bv3
	mov	rb,port	;write value to port		nop	
	mov	temp,T7			nop	
floop					call	linesync
	call	blackline	;complete horizontal sync line		jmp	bv4
	djnz	temp,floop		bv3	nop	
	or	port,#%10000000	;bit 7 high	bv4	call	linesync
	mov	rb,port				
					or	port,#%00100000 ;red
					mov	rb,port
					call	bardly
					and	port,#%11011111
					or	port,#%00010000 ;green
					mov	rb,port
					call	bardly
					or	port,#%00110000 ;yellow
					mov	rb,port
					call	bardly
					and	port,#%11001111
					or	port,#%00001000 ;blue
					mov	rb,port
					call	bardly
					or	port,#%00101000 ;magenta
					mov	rb,port
					call	bardly
					and	port,#%11010111
					or	port,#%00011000 ;cyan
					mov	rb,port
					call	bardly
					or	port,#%00111000 ;white
					mov	rb,port
					call	bardly
					and	port,#%11000111
					mov	rb,port
					mov	count,T14 ;trim end
				trim		
					djnz	count,trim
					ret	
				bardly		
				boop		
					mov	count,T5 ;width delay
					djnz	count,boop
					retp	
				dly		
				loop2		
					nop	;delay set in count
					djnz	count,loop2
					retp	
				linedly		
					mov	count,T1 ;porch delay
b4				loop3		
					djnz	count,loop3

hatch	retp			call	linedly
	cje	res,#1,hv2		retp	
	cje	res,#2,hv3		button	
	call	linesync		mov	w,rb ;buttons check
	mov	temp,#10 ;vertical bars		and	w,#2
hl				test	w
	or	port,##%00111000 ;white	patchange	jz	reschange
	mov	rb,port		add	pattern,#1 ;next pattern
	and	rb,##%11000111 ;black		cjbe	pattern,#3,bexit
	mov	count,#22 ;delay between bars		mov	pattern,#0 ;back to start
h1lp				jmp	bexit
	djnz	count,h1lp	reschange		
	djnz	temp,h1		add	res,#1 ;next resolution
hloop				mov	flag,#1 ;set res change flag
	or	port,##%00111000 ;white		cjbe	res,#2,bexit
	mov	rb,port		mov	res,#0 ;back to start
	and	rb,##%11000111 ;black	bexit		
	call	linedly		mov	temp,rb ;buttons check
	and	port,##%11000111 ;black		and	temp,#3
	ret			cjne	temp,#3,bexit ;wait release
hv2				retp	
	call	linesync		org	200h
	mov	temp,#6	cheqboard		
h2				mov	temp,T3 ;frame blank 1
	or	port,##%00111000 ;white	b5	call	@blackline
	mov	rb,port		djnz	temp,b5
	and	rb,##%11000111 ;black		mov	temp2,T10 ;vertical squares
	mov	count,#14 ;delay loop	cheq		
h2lp				mov	temp1,T9 ;chequer lines
	djnz	count,h2lp	chb		
	djnz	temp,h2	cheque1		
	mov	temp,#6		nop	
h2a				nop	
	or	port,##%00111000 ;white		call	@linesync
	mov	rb,port		mov	temp3,T10
	and	rb,##%11000111 ;black	ch1		
	nop			or	port,##%00111000 ;white
	mov	count,#14 ;delay loop		mov	rb,port
h2lpa				mov	count,T12 ;delay loop
	djnz	count,h2lpa		call	@dly
	djnz	temp,h2a		and	port,##%11000111 ;black
	jmp	hloop		mov	rb,port
hv3				mov	count,T12 ;delay loop
	nop			call	@dly
	call	linesync		djnz	temp3,ch1
	mov	temp,#7		and	port,##%11000111 ;black
h3				mov	rb,port
	or	port,##%00111000 ;white		call	@linedly
	mov	rb,port		nop	
	and	rb,##%11000111 ;black		nop	
	nop			mov	count,T13 ;trim end
	mov	count,#8 ;delay loop	trim1		
h3lp				djnz	count,trim1
	djnz	count,h3lp		djnz	temp1,chb
	djnz	temp,h3		mov	temp1,T9
	mov	temp,#7	cha		
h3a			cheque2		
	or	port,##%00111000 ;white		nop	
	mov	rb,port		nop	
	and	rb,##%11000111 ;black		call	@linesync
	mov	count,#8 ;delay loop		mov	temp3,T10
h3lpa				nop	
	djnz	count,h3lpa	ch2		
	djnz	temp,h3a		and	port,##%11000111 ;black
	nop			mov	rb,port
blackline	mov	hloop		mov	count,T12 ;delay loop
	mov	colour,##%00000000		call	@dly
	jmp	line		or	port,##%00111000 ;white
whiteline	mov	colour,##%00111000		mov	rb,port
	jmp	line		mov	count,T12 ;delay loop
redline	mov	colour,##%00100000		call	@dly
	nop			djnz	temp3,ch2
	nop			and	port,##%11000111 ;black
	nop			mov	rb,port
line				call	@linedly
	call	linesync		nop	
	nop			mov	count,T13 ;trim end
	or	port,colour	trim2		
	mov	rb,port		djnz	count,trim2
	mov	count,T8 ;delay loop		djnz	temp1,cha
	call	dly		djnz	temp2,cheq
	mov	count,T8 ;delay loop	b6	mov	temp,T4 ;frame blank2
	call	dly		call	@blackline
	and	port,##%11000111		djnz	temp,b6
	mov	rb,port		jmp	@frameloop

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable TV service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture + full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L. 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D. 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg. (for IBM pc's) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03 U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop(12.5 mm H) New £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) New £89.50
 - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
 - 2 1/2" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) New £190.00
 - 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £14.95
 - 3 1/2" FUJI FK-309-26 20mb MFM I/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
 - 3 1/2" QUANTUM 40S ProdrI ve 42mb SCSI I/F, New RFE £49.00
 - 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
 - 5 1/4" CDC 94205-51 40mb HH RFE I/F RFE tested £69.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2392K 160Mb SMD I/F RFE tested £195.00
 - 8" FUJITSU M2322K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1KW to 400 kW - 400 Hz 3 phase power sources - ex stock £POA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360.11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(ZM) 64 i/o £POA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £1995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector £POA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set £POA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP A1, A0 8 pin HPGL high speed drum plotters - from HP DRAFTMASTER 1 8 pin high speed plotter £550
- EG+G Brookdeal 95035C Precision lock in amp £750
- View Eng. Mod 1200 computerised inspection system £1800
- Sony DXC-3000A High quality CCD colour TV camera £995
- Kelthley 590 CV capacitor / voltage analyser £POA
- Fiscal ICR40 dual 40 channel voice recorder system £3750
- Fiskers 45KVA 3 ph On Line UPS - New batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system, 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS
One of the highest specification
monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little

used condition.
Tilt & Swivel Base £4.75
VGA cable for IBM PC included.
Only £119 (E) Order as MITS-SVGA

External cables for other types of computers available - CALL

Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.
Full 90 day guarantee. Only £199.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 1/4" x 15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 kHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

- HP6030A 0-200V DC @ 17 Amps bench power supply £1950
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
- Nikon HF-11 (Ephiphot) exposure control unit £1450
- PHILIPS PM5518 pro. TV signal generator £1250
- Motorola VME Bus Boards & Components List. SAE / CALL £POA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM high speed band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- VG Electronics 1035 TELETEXT Decoding Margin Meter £3250
- LightBand 60 output high spec 2u rack mount Video VDA's £495
- Sekonic SD 150H 18 channel digital Hybrid chart recorder £1995
- B&K 2633 Microphone pre amp £300
- Taylor Hobson Tallysurf amplifier / recorder £750
- ADC SS200 Carbon dioxide gas detector / monitor £1450
- BBC AM20/3 PPM Meter (Ernest Turner) + drive electronics £75
- ANRITSU 9654A Optical DC-2.5Gb/s waveform monitor £5650
- ANRITSU MS9001B1 0.6-1.7 uM optical spectrum analyser £POA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characteristic test set £POA
- R&S FTDZ Dual sound unit £650
- R&S SBUF-E1 Vision modulator £775
- WILTRON 6630B 12.4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955
- TEK TD5380 400MHz digital real time + disk drive, FFT etc £2900
- TEK TD5524A 500MHz digital real time + colour display etc £5100
- PH3585A Opt 907 20Hz to 40 MHz spectrum analyser £3950
- PHILIPS PW1700 10 60KV XRAY generator & accessories £POA
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900



19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting + plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603W. (64" H x 25" D x 23 3/4" W)
Sold at LESS than a third of makers price !!



A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £20 each
Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.

Overall dimensions 66 mm wide x 117 mm deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.

Web ref = LK33 ONLY £99.00 or 2 for £180.00 (E)

SOFTWARE SPECIALS

- NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
 - ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
 - DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
 - Windows for Workgroups 3.11+ Dos 6.22 on 3 1/2" disks £55.00
 - Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
- shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL TO
Dept ww, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

LONDON SHOP
Open Mon - Sat 9.00 - 5:30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
W. Thornton Heath &
Selhurst Park SR Rail Stations


NEW
DISTEL ©
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (C1)=£12.50, (D)=£16.00, (E)=£18.00, (F)=£20.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1999. E & O 07/99.



OPERATING & SERVICE MANUALS

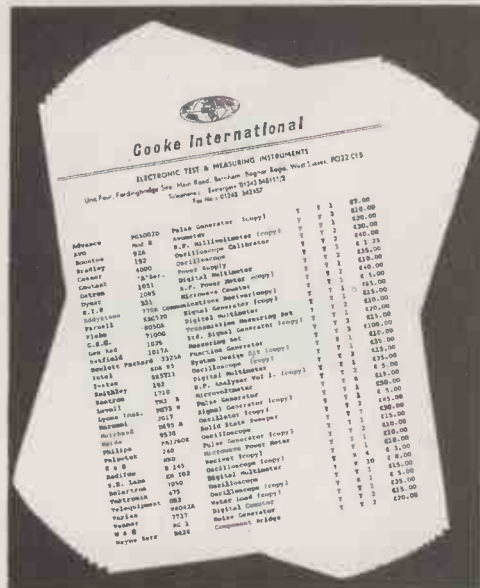

Cooke International

Unit Four, Fordingbridge Site, Barnham, Bognor Regis, West Sussex, PO22 0HD, U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>


E-mail: info@cooke-int.com

catalogue available

CIRCLE NO.136 ON REPLY CARD



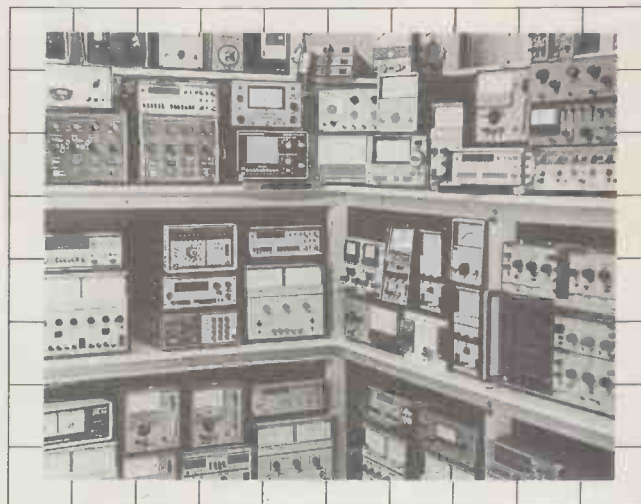SUPPLIER OF QUALITY USED TEST INSTRUMENTS



Cooke International

Unit Four, Fordingbridge Site, Barnham, Bognor Regis, West Sussex, PO22 0HD, U.K.

Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>

E-mail: info@cooke-int.com

catalogue available

CIRCLE NO.137 ON REPLY CARD

ADVERTISERS' INDEX

ANCHOR SUPPLIES.....	864	QUICKROUTE.....	825
CMS.....	845	RADIOTECH.....	839
CONFORD ELECTRONICS.....	845	RALFE ELECTRONICS.....	880
CROWNHILL.....	794, 829 and 839	RAMCO.....	
DATAMAN.....	OBC	RD RESEARCH.....	796
DISPLAY ELECTRONICS.....	877	SEETRAX.....	835
ECC.....	827	SIGHTMAGIC.....	796
HITEX UK.....	794	STEWART OF READING.....	835
ICE TECHNOLOGY.....	823	SURREY ELECTRONICS.....	869
INTERNATIONAL RECTIFIER.....	IFC	SWIFT EUROTECH.....	821
JPG ELECTRONICS.....	869	TELFORD ELECTRONICS.....	843
LABCENTER ELECTRONICS.....	IBC	TELNET.....	817
LANGREX.....	829	TIE PIE.....	799
MILFORD INSTRUMENTS.....	829	THOSE ENGINEERS.....	843
PICO.....	825	TTI.....	839
PS CONSULTANTS.....	801	ULTIMATE TECHNOLOGY.....	
		797, 798, 800 and 857

ARTICLES WANTED**TOP PRICES PAID**

For all your valves,
tubes, semi conductors
and IC's.

**Langrex
Supplies
Limited**

1 Mayo Road, Croydon
Surrey CR0 2QP
TEL: 0181 684 1166
FAX: 0181 684 3056

WANTED

Valves & Semiconductors
All types e.g. Discrete & IC's
Good Rates Paid
CHELMER VALVE CO.
130 New London Road
Chelmsford, Essex
Tel: 01245 265865
Fax: 01245 490064

WANTED. Gemstar Video+ Plus+ programmer
model VIP-185 (preferably). Must be in good
working order. Instructions not required. 01736
367100.

WANTED TO BUY. Used Neutrik chart
recorder system. Fax USA 702/565-4828
Franklin Miller. Email fjm@anv.net

VALVES WANTED

All types considered
Ask for a free copy of our
wanted list.
eg ECC83, KT88, PX4
Avo Valve Tester VCM163

ONE MILLION VALVES IN STOCK
As for our free catalogue, eg 4CX250B,
4CX1000A, 6C33CB, 300B, 6156,
6550B, CV2131

BILLINGTON EXPORT LTD
Billingshurst, Sussex
Tel: 01403 784961 Fax: 01403 783519
VISITORS PLEASE PHONE FOR
APPOINTMENT

Wanted to Buy. Component Data, books/sheets,
any age. Email list to: info@sentienc-
systems.co.uk. Fax list to: 01202 884420.

WANTED Sony model CDP-K1 CD player. This
has variable speed and microphone facility.
Equivalent considered. - Reading 9428986.

WANTED USED COPY of PSPICE Dos or
Windows. Phone: 01458 210881.

WANTED: Brüel & Kjaer type 2606 or later
measuring amplifier in good working condition.
Manuals etc not necessary. All reasonable offers
considered. M. Edinger, Bjaelkevangen 10B, dk-
2800, Lyngby, Denmark. Contact: Email:
Musiklab@image.dk, phone +45 45 874977, fax
+45 45 874976.

ARTICLES FOR SALE**RF DESIGN
SERVICES**

All aspects of RF
hardware development
considered from
concept to production.

WATERBEACH ELECTRONICS

TEL: 01223 862550
FAX: 01223 440853

HP54111D Colour DSO

500MHz BW, 1G S/sec, 2+2Ch,
4 Ch logic trigger,
2 x HP10430A 6pF probes, full
set of manuals, £2,000 + VAT

HP1630D Logic Analyser

43 Ch, 100MHz, £450 + VAT
steve@csys.demon.co.uk

SHORTWAVE BROADCASTERS

Monitor reception from within your
target area

GOVERNMENT AGENCIES

Control radio receivers/transceivers
worldwide

Radpoint 2000DX from

www.pca.cc

Intel+61-2-98889777

Fax+61-2-98050253

DYNAMIC Sciences Tempest RX, £1,695;
HP141T > 18GHz, £950; Icom IC-M800 TSVR,
£695; Racal RA1795, £995; Advantest TR4131
Spectrum Analyser, £2,750. - Tel: 01908 365726.

ELECTRONICS WORLD incorporating
Wireless World 1971-1996 free to a good home.
Tel: Graham on 0118 973 2119.

500,000+ GP10Y glass passivated 1A diode.
Offers - 01233 750481.

100MHz OSCILLOSCOPE with 60MHz probe
set, £580, unused (OS5100); TG230 Function
generator, £200, unused; 10MHz Oscilloscope,
£50. Evenings 01264 391165.

FISCHER 5 PIN CABLE PLUGS type
S103A054-120 with cable clamp E3 103.6/5.2
£4. Quantity available. Tel: 01476 550826.

Quad II. Valve Power - Amplifier, good as new,
unused. Only the one, unfortunately never found
another to make pair £300. Tel: 01795 585378.

ELECTRONIC circuit analysis program for PC.
Provides graphical output to screen and printer.
Many circuit examples. £10. - Tel. 01753
643384.

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
Inverter

Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk
Lomond Electronic Services

Rack Enclosures

New and Used most sizes
16U to 50U side and rear panels
mains distribution 19" Panel mounts
optima eurocraft. Prices from £45 +vat

M&B Radio

86 Bishopsgate Street Leeds LS1 4BB
Tel. 0113 2702114 Fax. 0113 2426881

Racal RA1795 rx £995, Dynamic Sciences
Tempest rx, £995, HP 5352B 40GHz Counter,
£2,995, Thomson-CSF TRC 350H HF M11
TSVR, £1,995, Icom IC-M800 HF Marine,
£495. Tel/Fax: 01908 365726 or E-mail:
Phil@g4zow.freemove.co.uk

TEKTRONIX 7313 mainframe type oscillo-
scope with 7A13 dual trace module and 7B53A
dual time base module fitted (one slot free).
Limited cal due to non-functional storage facility,
£150. Also Tequipment S54A single trace
general purpose suitable for audio and TV use,
£45. Also Nashua 3916 A3 and A4 photocopier
enlarges/reduces, sale includes an unfitted new
drum. Working but could do with a service, £95.
01963 362143 evenings and weekends.

Wave Analysers Marconi type 2330 and 2330A.
£20 ono. Tel: 01727 859653.

SERVICES

From
**Concept
To
Production**

European leader
in matrix-control
PC based systems

Designer Systems has over a decade of
experience designing innovative products for
client companies and individuals. If you have a
product idea, need to develop a new product
or sub-assembly from scratch, want to re-
develop an old product or need professionally
written documentation or software, contact us
for more information or see our web site.

Tel/Fax: 01872 223306
Email: designer.systems
@btinternet.com
Web: [http://
designersystems.co.uk](http://designersystems.co.uk)

**DESIGNER
SYSTEMS**
Bespoke electronic solutions

PRINTED CIRCUIT BOARD SERVICE.
Phone Mr Belt for details (01673 842338).

P&P Electronics Analogue and digital design
services. Tel: 01924 402931.

Printed Circuits manufacturing service.
Production from artwork out of Magazine or
CAD design. Single- or double-sided boards.
Quantities and one-offs. For details telephone Mr.
Belt on 01673 842338.

ADVERTISERS PLEASE

**NOTE FOR ALL
YOUR ENQUIRIES ON
ADVERTISING RATES
PLEASE CONTACT
JOANNAH COX ON
TEL: 0181 652 3620
FAX: 0181 652 8938**

T & M EQUIPMENT




- AVANTEST TR9407 fft spectrum analyser to 1MHz £2000
- ANRITSU ML93A optical power meter with MA96A power sensor (0.75-1.8uM) £1000
- CHASE LFR1000 interference measuring receiver 9KHz-150KHz £200
- ORANETZ 626-PA-6006 ac neutral monitor, c/w TR2018 clamp £250
- FLANN MICROWAVE 27072 frequency meter 73-1136Hz £275
- MARCONI 2019A signal generator 10KHz-1GHz INCLUDING FREE CALIBRATION £1500
- RACAL OANA 1991 frequency counter, GPIB opt £550
- SCHLUMBERGER 4922 radio code analyser £250
- SCHLUMBERGER SRTG-GA62 selective call test set £150
- SYSTRON OONNER 6041A 100MHz 8-digit frequency counter IEEE £100
- TEKTRONIX 2432A 100MHz 250M Sa/sec digital storage oscilloscope £1000
- TEKTRONIX 2236 100MHz analogue oscilloscope £500
- TAU-TRON MN302/MB302N bert transmitter/receiver £250
- WANDEL & GOLTERMANN PCM4 test sets ... call for details & options call
- WANDEL & GOLTERMANN PCM4 pcm measuring set version 985/01, IEEE opt £7500
- WANDEL & GOLTERMANN PF2 error ratio measuring set £400
- WANDEL & GOLTERMANN OLM-20 data circuit test set £250
- WANDEL & GOLTERMANN SPM31 level meter £500
- WANDEL & GOLTERMANN WM30 level tracer £500
- WANDEL & GOLTERMANN PF4 bit error rate tester (BN911/01, Opt 00.01) £2000
- WAVETEK 23 synthesized function generator 0.01Hz-12MHz £500
- WAVETEK 1080 sweep generator 1-1000MHz £750
- WAYNE KERR 3220 20A bias unit (for 3245 inductance analyser) £1000

• ralfe electronics • *exclusively professional T&M ©*

• 36 Eastcote Lane • South Harrow • Middx HA2 8DB • England •
TEL (+44) 0181-422 3593 • FAX (+44) 0181-423 4009

EST
45
YRS

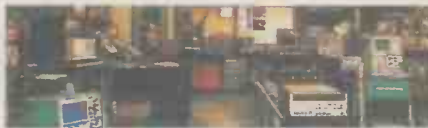

- WAYNE KERR SR268 source and detector £250
- WILTRON 6637 sweeper generator 2-18GHz (option 03) £2000
- WILTRON 6659A sweep generator 10MHz-26.5GHz (options 01/10/13) £3000
- WILTRON 6640B sweep generator 26.5-40GHz (option 03) £3500

THIS MONTH'S SPECIALS

SYNTHESIZED SIGNAL GENERATORS:

- HP 8657B 2GHz £4000
- HP 3325B function £2250
- MARCONI 2030 1.35GHz £2250

SPECTRUM ANALYSERS:

- HP 8591E 1.8GHz £4000
- HP 8590A 1.5GHz £2000 (B, £3000)
- IFR A-7550 1GHz £1500

D.E.C.T. TEST SET:

- HP 8923B currently £19000.
- Asking Half list price. Just cal'd.

HEWLETT PACKARD



- 214B pulse generator £2000
- 3336A level generator £1000
- 1640B serial data generator £500
- 10715A digital interferometer £1000
- 4274A multi-frequency icr meter £3000
- 3314A function generator £1500
- 33320G/33322G programmable attenuators 4GHz each £350
- 3561A dynamics signal analyser £5000
- 3586A selective level meter £1250
- 4093B protocol tester base (PT300) £3000
- 4142B OC source/monitor (with 41421B, 41420A, 41424A) £8500
- 8018A serial data generator £1000
- 5334B frequency counter, option 060 £1000
- 5461C oscilloscope £2000
- 83411C lightwave receiver 100/1550nm £1750
- 83440C lightwave detector 20GHz 1300nm/1550nm £2000
- 8350B sweep generator mainframe £2000
- 83572B sweeper plug-in unit (for 8350B) 26.5-40GHz £7500
- 85046A S-parameter test set £2000
- 85053B 3.5mm verification kit £2000
- 85640A tracking generator to 2.9GHz £2000
- 8672A synthesized signal generator 2-18GHz £6000
- 8671A synthesised signal generator 2-6.2GHz £3000
- 86222A 10MHz-2.4GHz sweep generator plug-in unit £1000
- 86290B 2-18GHz sweep generator plug-in unit £1500
- 8684B signal generator 5.4GHz-12.5GHz £1000
- 8903B audio analyser with opts 10 and 051 £2500
- 8904A/001/002 multifunction synthesizer DC-600kHz £2000
- E5200A broadband service analyser (STM1 options) £9500
- J3458A fast ethernet Lanprobe £1500
- J2215A FDOI portable multimode test set £1500

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.

CALLERS WELCOME BY APPOINTMENT ONLY.

FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE

www.ralfe-electronics.co.uk



**ISO9002 ACCREDITED STOCKIST
MEASUREMENT & TEST EQUIPMENT**

CIRCLE NO.138 ON REPLY CARD

ELECTRONICUPDATE

A regular advertising feature enabling readers to obtain more information on companies' products or services.

Contact Joannah Cox on
0181 652 3620



PROGRAMMERS

- Hand held and bench top
- Single socket to 16 gang
- Stand alone and PC based
- DOS and Windows 3.1/95/NT
- Fast algorithms
- Vast range of adaptors:-
-PLCC, QFP, SOIC,
-SSOP, BGA, etc...

Tel: +44(0) 181 953 9292
Email: sales@smartcom.co.uk
Web: www.smartcom.co.uk

CIRCLE NO.139 ON REPLY CARD




Unique PCB Test Tool

- handheld connectivity tester
- quickly locates shorts & opens
- ideal for SMT-based PCBs
- cost just £93.50 including p&p

**Circuit Trace
PO Box 70
Retford DN22 0SY
Tel/Fax: 01777 248993
www.toneohm.com**

CIRCLE NO.141 ON REPLY CARD

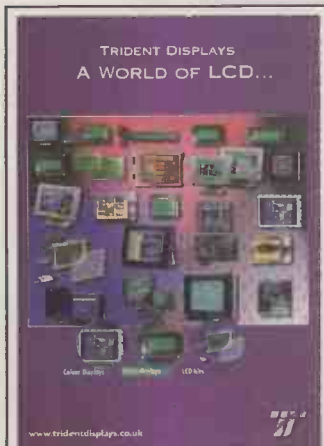

The widest range of colour LCDs, LCD monitors and plug and play kits available in the UK, all in one easy to use brochure, is now available FREE!

It includes information on products ranging from 2.9" monitors to 16.1" colour LCD screens, mono/colour STN TFTs and touch screen technology from the world's leading manufacturers.

Phone TRIDENT today for your free copy.

**TEL: 01737 780790
FAX: 01737 771908**

OR VISIT OUR WEBSITE:
www.tridentdisplays.co.uk

CIRCLE NO.140 ON REPLY CARD



**FREE VISION
EVALUATION CD**

The IMAQ™ Vision Evaluation CD, from National Instruments, is a free evaluation package for its machine vision and image processing software, IMAQ Vision. With the IMAQ Vision Evaluation CD, users can go through tutorials and build actual programs, learning how to create custom imaging applications for factory and laboratory automation applications.

Call National Instruments now for your FREE copy on 01635 523545.

E-mail: info@natinst.com
Website: www.natinst.com/uk

CIRCLE NO.142 ON REPLY CARD


PROTEUS

including **NEW SIMULATOR**

PRO SPICE 3F5

NEW

NOW WITH
Interactive Circuit
Animation

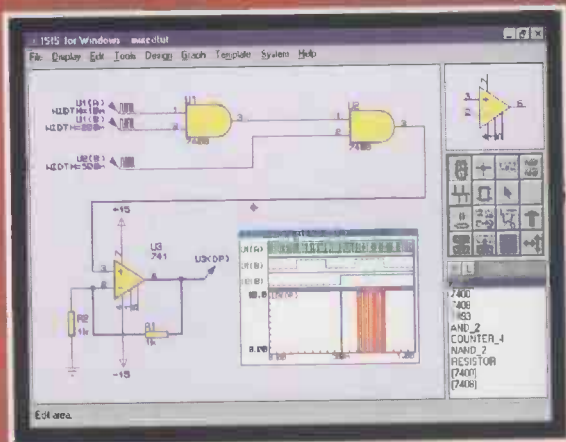

Simulation

- Berkeley SPICE3F5 analogue simulation kernel.
- True mixed mode simulation.
- New analysis types include multi-plot sweeps, transfer curves, distortion and impedance plots.
- Active Components: Switches, Pots etc.
- Over 1000 new library parts with SPICE models.
- Greater ease of use.

**“a constant high level
of capability throughout”**

EWV CAD Review Round Up September 1998


Schematic Capture

- Produces attractive schematics like in the magazines.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Full support for buses including bus pins.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.

PCB Design

- Automatic Component Placement.
- Rip-Up & Retry Autorouter with tidy pass.
- Pinswap/Gateswap Optimizer & Back-Annotation.
- 32 bit high resolution database.
- Full DRC and Connectivity Checking.
- Shape based gridless power planes.
- Gerber and DXF Import capability.

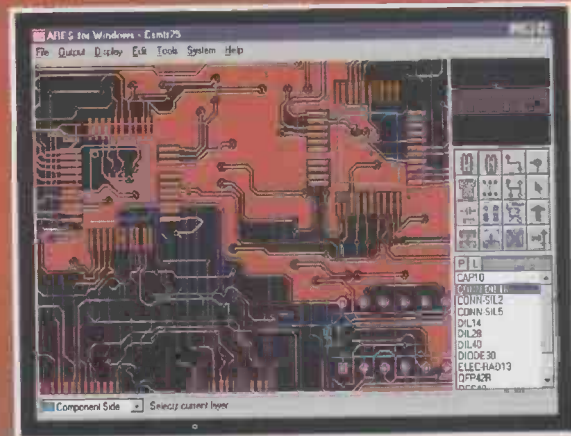Available in 5 levels - prices from £295 to £1625 + VAT.
Call now for further information & upgrade prices.



SHAREWARE VERSIONS

NOW WITH INTERACTIVE CIRCUIT ANIMATION
DOWNLOAD YOUR COPY NOW

<http://www.labcenter.co.uk>

**“the
BEST all-round
PROGRAM”**

EWV CAD Review Round Up September 1998

labcenter
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857. EMAIL: info@labcenter.co.uk
53-55 Main St, Grassington. BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

[TRUTH
OR
ILLUSION?]

the world's most powerful portable programmers

CE



£495
PLUS VAT

Dataman S4

[Analysis]

- Programs 8 and 16-bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 Microcontrollers and more.
- EPROM emulation as standard!
- Rechargeable battery power for total portability.
- All-in price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual.
- Supplied fully charged and ready to use.

S4 GAL Module

[Analysis]

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors.
- Supports JEDEC files from all popular compilers.

Dataman-48LV

[Analysis]

- Plugs straight into your parallel port of PC or laptop.
- Programs and verifies at 2, 2.7, 3, 3.3 and 5 V
- True no-adaptor programming right up to 48-pin DIL devices.
- Free universal 44-pin PLCC adaptor.
- Built-in world standard PSU – for go-anywhere programming.
- Package adaptors for TSOP, PSOP, QFP, SOIC and PLCC.
- Optional EPROM emulator.

Support


[Analysis]

- 3 year parts and labour guarantee.
- Windows/DOS software included.
- Free software updates via BBS/Internet.
- Free technical support for life.
- Next day delivery – always in stock.
- Dedicated UK supplier, established 1978.

Truth — Claim Verified

[Recommended Action]

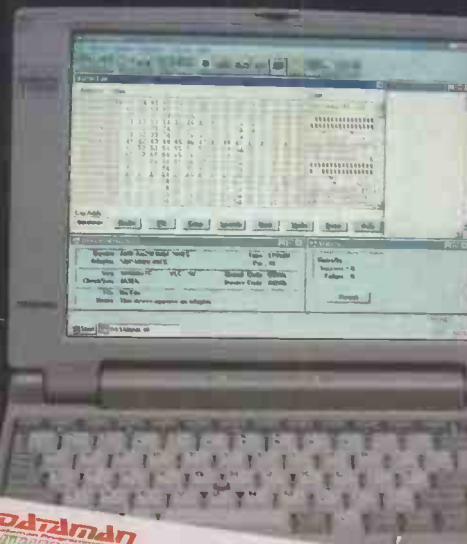Secure for own use without delay. Order via credit card hotline – phone today, use tomorrow. Alternatively, request more detailed information on these and other market-leading programming solutions.



NEW MODEL



£795
PLUS VAT

3
YEAR

GUARANTEE

DATAMAN

Dataman Programmers Ltd, Station Road,
Maiden Newton, Dorchester, Dorset, DT2 0AE, UK
Telephone +44/0 1300 320719 Fax +44/0 1300 321012
BBS +44/0 1300 321095 (24hr) Modem V.34/V.FCN.32k
Home page: <http://www.dataman.com>
FTP: <ftp://ftp.dataman.com> Email: sales@dataman.com

hotline
01300 320719



Orders received by 4pm will normally be despatched same day.
Order today, get it tomorrow!

Money-back 30-day Trial

Try the Dataman S4 or Dataman-48LV without obligation for 30 days. If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund.

CIRCLE NO. 103 ON REPLY CARD

iv