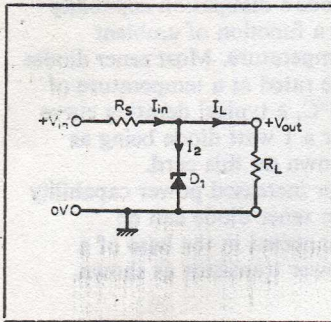


Zener diode shunt regulator



Typical performance
 I_L constant, V_{IN} variable
 D_1 BZY96C9V, I_L 50mA
 $V_{IN(min)}$ 12V, $V_{IN(max)}$ 18V
 R_s 54 Ω (39 Ω +15 Ω)
 R_L 195 Ω (3 \times 56 Ω +27 Ω) to set I_L at 50mA

Measured results

$V_{IN}(V)$	$V_{OUT}(V)$	$I_L(mA)$	$I_z(mA)$	$Pz(W)$
12	9.16	48	1	0.0092
15	9.49	49	48	0.46
18	9.72	50.5	106.5	1.035

Description

A voltage regulator should ideally provide a form of buffer action which makes its output voltage independent of changes that occur in its input voltage or its load current. The extent to which a particular regulator circuit approaches this ideal usually depends on the complexity of the electronic regulation element used. The

simplest form of electronic shunt regulation element is the zener diode which may be considered to consist of an internal reference voltage source (V_z) in series with an internal resistance (R_s), both of which have values that depend on the operating point and junction temperature. The basic form of a zener diode shunt regulator is shown

Typical performance
 V_{IN} constant, I_L variable
 D_1 BZY96C9V, V_{IN} 15V
 $I_{L(max)}$ 100mA, $I_{L(min)}$ 80mA
 R_s 54 Ω 39 Ω +15 Ω
 R_L 95 Ω to set I_L at 100mA
 R_L 124 Ω to set I_L at 80mA


Measured results

$I_L(mA)$	$V_{OUT}(V)$	$I_z(mA)$	$Pz(mW)$
102	9.27	7	64.9
80	9.56	26	248.6

above where the input voltage must be larger than the required regulated output voltage. The input voltage will often be derived from the a.c. mains by rectification and will have a value that varies with mains input voltage and with load current, due to imperfect power supply regulation. The current in R_s is the sum of the load current (I_L) and the zener

diode current (I_z). If V_{IN} increases, the current in the zener diode and the load increases. But at the same time, a shift occurs in the zener diode operating point causing its internal resistance to fall. Thus the combined effects of the increase in I_z and the decrease in R_s tends to maintain the output voltage at its former value. Similar but opposite effects occur if V_{IN} decreases. Ability of the circuit to maintain the output voltage depends on the zener resistance and on the temperature coefficient of the zener voltage. The output voltage will not, in general, be equal to the nominal zener voltage because V_z and R_s have values that depend on I_z and junction temperature. In some applications the load current may be virtually constant and in others it may

Simple transistor regulators

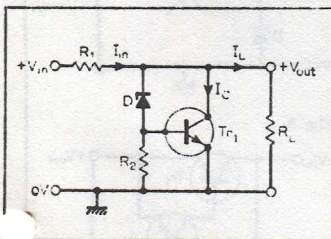


Typical performance
 Tr_1 BFR41, D_1 ESM18
 R_1 330 Ω , 3W; R_2 100 Ω
 R_L 1k Ω , 1/2W
 V_{IN} 32.5 \pm 7.5V
 V_{OUT} see graphs opposite

Description

Although less efficient than series regulators, the shunt regulator is normally a simpler circuit and is useful where an existing supply is to be used to provide a lower-value regulated output voltage. A simple regulator is shown above which includes a zener diode reference-voltage element and a transistor, in shunt with the load, acting as the regulator element. Note that the circuit is simply a common-emitter d.c. amplifier. The value of R_2 is


chosen to provide a current in D_1 that is greater than the minimum value required to maintain the zener diode in its breakdown region without exceeding the rated dissipation. Output voltage remains essentially constant because the transistor collector current changes as the input voltage and/or the load current changes, causing a corresponding change in the p.d. across R_1 . Transistor Tr_1 must be chosen to accommodate the maximum dissipation that

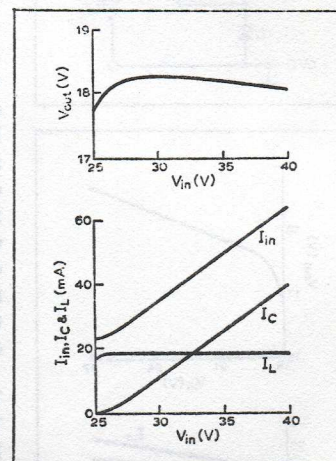


can occur under specified input voltage and load current variations, including open-circuit load if this is a possibility.

Circuit modifications

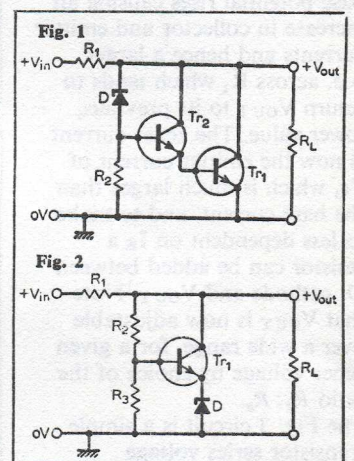To reduce changes in zener diode current, due to Tr_1 base current, cascaded transistors



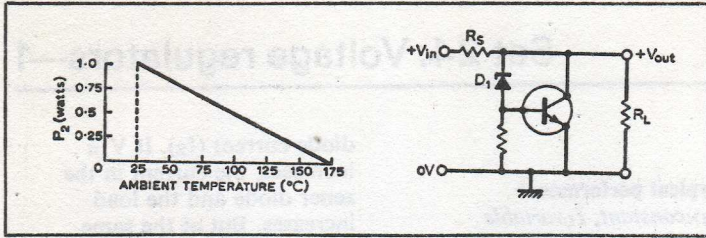may be used to increase the current gain of the regulating element, as Fig. 1. The base current of Tr_2 is then only $\approx I_{B1}/h_{FE2}$ which can be made much smaller than the zener diode current by choice of R_2 . An alternative form of simple shunt regulator is Fig. 2 where the zener diode is in



vary over a wide range. If the load current decreases, the current shunted by the zener diode will increase, and vice versa, resulting in a substantially constant output voltage. Protection against excessive load current can be obtained with a fuse, but protection of the zener diode under light loading or open-circuit load conditions must be catered for by choosing a diode that can safely dissipate the power generated when $I_L \rightarrow 0$, if there is any possibility of the load being removed. The design of this shunt regulator therefore becomes a matter of determining the value of R_S and the maximum power dissipated in the zener

diode under specified conditions of variable V_{IN} and/or variable I_L . Although more precise results can be obtained by measuring and plotting the zener diode characteristics, for all practical purposes the nominal value of V_Z can be used to approximate the value of V_{OUT} in order to determine the component values. The Kirchhoff voltage equation for the circuit is

$$V_{IN} = I_{IN} \cdot R_S + V_Z$$

$$\therefore R_S = (V_{IN} - V_Z) / (I_Z + I_L)$$

as $I_{IN} = I_Z + I_L$
and $I_Z = (V_{IN} - V_Z) / R_S - I_L$
and the diode dissipation is

$$P_Z = I_Z \cdot V_Z$$

$$= [(V_{IN} - V_Z) / R_S - I_L] V_Z$$

Determination of suitable values for R_S and $P_{Z(max)}$

depends on the specification. The value of R_S must be such that the zener current will not fall below some minimum value, $I_{Z(min)}$, required to keep the diode in the breakdown region so that V_Z is maintained. Minimum zener current occurs when V_{IN} is a minimum, V_Z is a maximum and I_L is a maximum, so that

$$R_S = \frac{V_{IN(min)} - V_{Z(max)}}{I_{Z(min)} + I_{L(max)}}$$

Using the nominal zener voltage V_Z and an empirical factor of 10% of $I_{L(max)}$, for $I_{Z(min)}$ gives

$$R_S = \frac{V_{IN(min)} - V_Z}{1.1 I_{L(max)}}$$

for the condition where either V_{IN} or both V_{IN} and I_L are variable. When only I_L is variable

$$R_S = \frac{V_{IN} - V_Z}{1.1 I_{L(max)}}$$

Having determined R_S , $P_{Z(max)}$ can be found from

$$\left[\left(\frac{V_{IN(max)} - V_Z}{R_S} \right) - I_{L(min)} \right] - V_Z$$

for I_L and V_{IN} variable.

A zener diode is then chosen

having the desired nominal voltage and capable of safely dissipating this maximum power. It may be necessary to design a heat sink of suitable area and/or to derate the diode's dissipation capability as a function of ambient temperature. Most zener diodes are rated at a temperature of 25°C, a typical derating curve for a 1 watt diode being as shown on this card. For increased power capability the zener diode can be connected in the base of a power transistor as shown.

Further reading



Zener Diode Handbook, Motorola 1967.
Patchett, G. N. Automatic Voltage Regulators and Stabilizers, chapter 6, Pitman, 1970 (3rd edition).

Cross references

Set 23, card 1.
Set 24, cards 3, 4.

series with Tr_1 emitter. A fraction of the output voltage $V_{OUT} R_3 / (R_2 + R_3)$ is compared with V_Z . If V_{OUT} increases the base potential rises causing an increase in collector and emitter currents and hence a larger p.d. across R_1 which tends to return V_{OUT} to its previous, lower value. The zener current is now the emitter current of Tr_1 which is much larger than the base current, and to make I_Z less dependent on I_E a resistor can be added between D_1 cathode and V_{OUT} . Note that V_{OUT} is now adjustable over a wide range, for a given zener voltage by choice of the ratio $R_2 : R_3$.

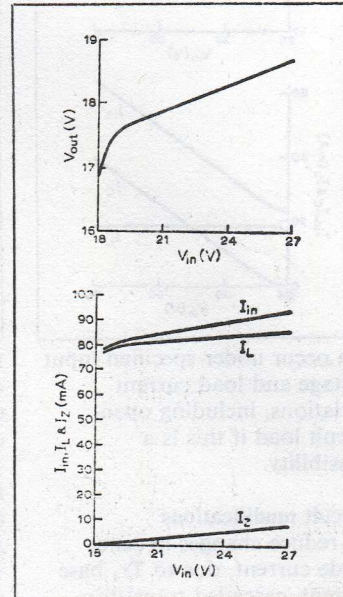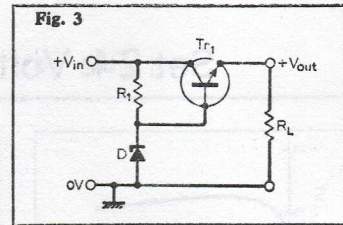The Fig. 3 circuit is a simple transistor series voltage regulator, i.e. the regulating element Tr_1 is in series with the load. Note that the circuit is an emitter follower d.c. amplifier where ideally $V_{OUT} = V_Z$ but in practice $V_{OUT} = (V_Z - V_{BE})$. If the output voltage tends to decrease due to changes in input voltage or load current,




the base-emitter voltage of Tr_1 increases causing the transistor to feed a larger current to the load which will tend to restore V_{OUT} to its previous value. The current in the zener diode can be made much larger than the base current of Tr_1 by choice of R_1 and this current, hence V_Z and V_{OUT} , will be subject to variation as V_{IN} changes. The circuit is inherently safe with open-circuit loads but Tr_1 must be chosen to dissipate the maximum power generated under $V_{IN(max)}$ and $R_{L(min)}$ conditions.

Typical performance

Tr_1 BFR41, D_1 ESM18
 R_1 1k Ω , $\frac{1}{4}$ W; R_L 200 Ω , 3W
 V_{IN} 22.5 \pm 4.5V
 V_{OUT} see graphs above

The variation of current in the zener diode with base current can be reduced by replacing Tr_1 by a Darlington pair as in Fig. 4, where the base current of Tr_2 is then only $I_L / [(1 + h_{FE1})(1 + h_{FE2})]$.

This principle can be extended

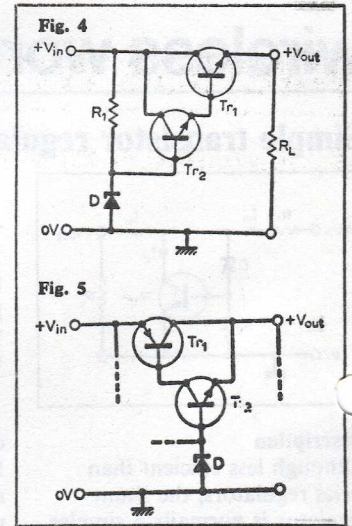


to a number of emitter followers or a complementary pair may be used, Fig. 5, to keep $V_{OUT} = (V_Z - V_{BE})$.

Further reading

Patchett, G. N. Automatic voltage regulators and stabilizers, chapter 6, Pitman, 1970 (3rd edition).
Zener Diode Handbook—Motorola, chapter 6, 1967.

Feedback series regulators

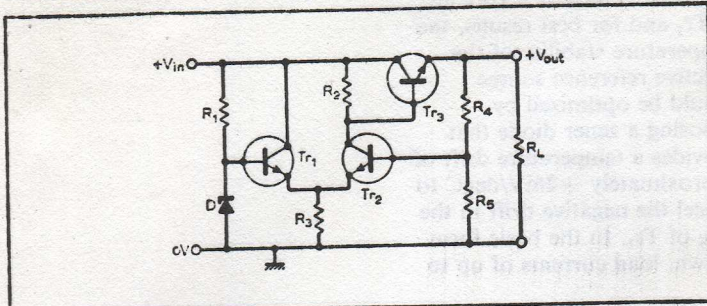

Long-tailed pair regulator

A very common type of feedback voltage regulator is shown above where the control amplifier is in the form of a long-tailed pair, or differential-input amplifier containing transistors Tr_1 and Tr_2 .



Resistor R_1 and D_1 act as a simple voltage reference circuit making Tr_1 base potential V_Z . The base potential of Tr_2 is a fraction of the output voltage, determined by the ratio of the

resistors in the potential divider R_4 and R_5 , so that the output voltage is continuously monitored. The output from the long-tailed pair is taken from Tr_2 collector and controls the base drive to the series transistor Tr_3 (an emitter follower). The differential amplifier attempts to keep its two inputs equal by altering the p.d. across the series transistor in order to hold the regulated output voltage


Typical performance

Tr_1, Tr_2 BC125 Tr_3 BFR41
 D_1 BZY88C5V6
 R_1 560 Ω , R_2 1k Ω
 R_3 220 Ω , $R_4 + R_5$ 1k Ω
 R_L 250 Ω 1W
 V_{IN} 18V \pm 6V
 V_{OUT} see graphs opposite

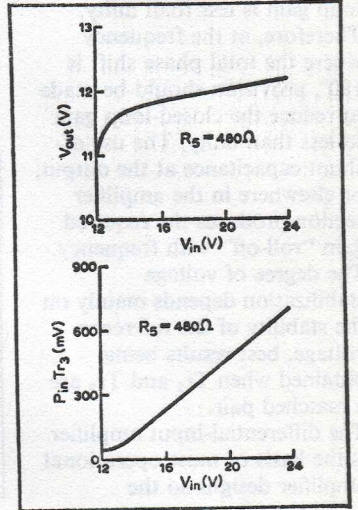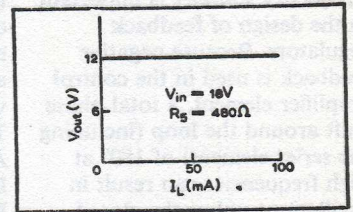constant despite changes that occur in the input voltage or load current. With a load current of 50mA, the circuit shown typically provides a load regulation of about 0.03% and a line regulation of approximately 0.5% for a $\pm 20\%$ change in V_{IN} . For a fixed input voltage the output voltage may be varied conveniently by realizing R_4 and R_5 in the form of a potentiometer e.g. with



Bipolar/c.m.o.s. op-amp regulator

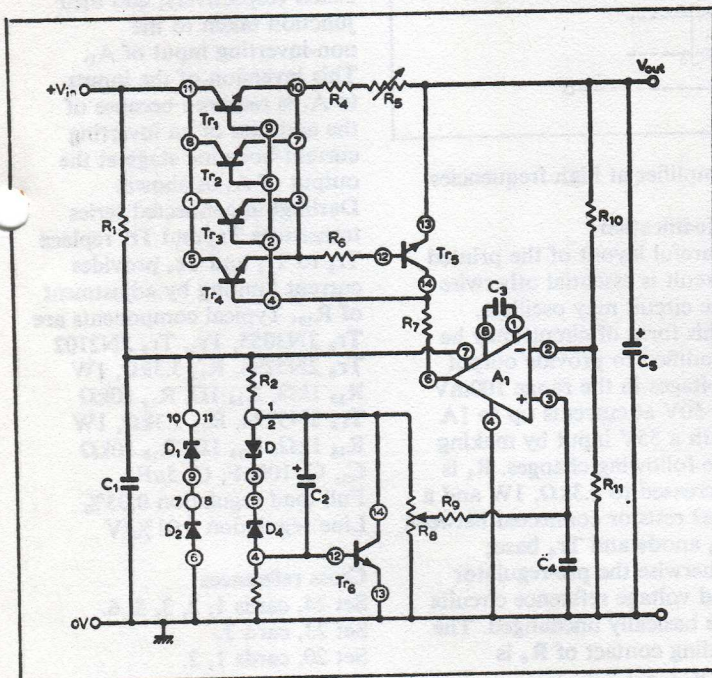

Typical performance

A_1 CA3130
 Tr_1, Tr_2 1/5 \times CA3086
 D_1, D_2 1/5 \times CA3086
 R_1 390 Ω , R_2 2.2k Ω , R_3 62k Ω
 R_4 3 Ω , R_5 , R_6 , R_7 1k Ω
 R_8 50k Ω , R_9 100k Ω
 R_{10} 20k Ω , R_{11} 30k Ω
 C_1, C_4 10nF, C_2 25 μ F, 15V
 C_3 56pF, C_5 5 μ F, 25V
 With V_{IN} 20V, V_{OUT} variable in range 0 to 13.9V at I_L 40mA
 Full load regulation $< 0.01\%$
 Line regulation 0.02%/V
 Standby current 8mA

Circuit description

The voltage regulator shown above uses three monolithic integrated circuits. A_1 is a bipolar-c.m.o.s. hybrid operational amplifier, Tr_1 to Tr_6 are contained within one bipolar array package, and D_1 to D_4 plus Tr_6 are contained in another identical package. Diodes D_1 , D_2 and D_4 are bipolar transistors with


collector and emitter strapped and operating in reverse bias in the breakdown region to serve as zener diodes having a zener voltage of about 7.3V. Diode D_3 is forward-biased and consists of a transistor in the same package with its collector and base strapped. Resistor R_1 and the series-connected zener diodes D_1 and D_2 act as a simple shunt regulator across the input to provide a regulated supply of $2V_Z$ for the CA3130 operational amplifier. The output from this part of the circuit also serves as a pre-regulated input to the low-impedance, temperature-compensated voltage reference source consisting of R_2 , D_3 , D_4 , R_3 and Tr_6 —the diodes and transistor being part of the same monolithic structure. The output from this reference source is taken to the non-inverting input of the

$(R_4 + R_5) = 1k\Omega$ and R_5 varied over the range 100 to 900Ω . V_{OUT} may be varied over the range 16.86 to 6.4V. Frequency stability is important in the design of feedback regulators. Because negative feedback is used in the control amplifier element, a total phase shift around the loop (including the series element) of 180° at high frequencies can result in oscillations unless the closed-loop gain is less than unity. Therefore, at the frequency where the total phase shift is 180° , provision should be made to reduce the closed-loop gain to less than unity. The use of shunt capacitance at the output, or elsewhere in the amplifier section produces the required gain "roll-off" with frequency. The degree of voltage stabilization depends mainly on the stability of the reference voltage, best results being obtained when Tr_1 and Tr_2 are a matched pair. The differential-input amplifier is the basis of most operational amplifier designs so the

long-tailed pair may be replaced by such an amplifier as shown below. In this arrangement the operational amplifier isolates the zener reference from load changes improving the load regulation. Potentiometer R_3 allows the output voltage to vary over a limited range. Typical performance is A_1 741, Tr_1 SE3035, D_1 1N4611, R_1 $12k\Omega$, R_2 , R_4 $1.2k\Omega$, R_3 $2.5k\Omega$. With V_{IN} of +30V, V_{OUT} may be varied over the range 9 to 25V with load currents up to 100mA. Output impedance is

less than 0.1Ω . Useful minimum V_{IN} 20V. Another type of feedback regulator in common use is the d.c. feedback pair shown below. In this circuit the effective reference voltage is $V_Z + V_{BE}$ of Tr_1 and for best results, the temperature stability of the effective reference source should be optimized by choosing a zener diode that provides a temperature drift of approximately $+2mV/degC$ to cancel the negative drift in the V_{BE} of Tr_1 . In the basic form shown, load currents of up to

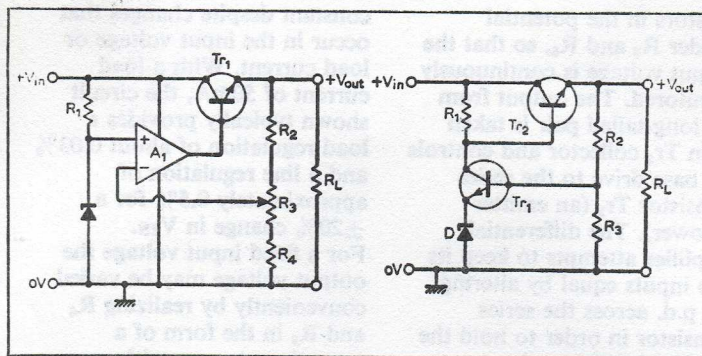about 100mA can be accommodated and for higher output currents Tr_2 can be replaced by a higher-current-gain transistor pair.



© 1975 IPC Business Press Ltd.

Further reading


English, M. Applications for fully compensated op.amp.i.c. *EEE*, January 1969, pp. 63-5. Potted power, *Design Electronics*, January 1971, pp. 34/5.

Cross references

Set 24, cards 1, 4, 5, 6.
Set 23, card 3.
Set 20, cards 1, 2, 4, 10.

error amplifier via potentiometer R_3 which allows the amplifier's reference to be varied continuously over the range 0V to about 8.3V allowing the output voltage to be controlled over the range 0V to about 13.9V. A fraction of the output voltage is fed to the inverting input of the error amplifier by means of the potential divider R_{10} and R_{11} .

Transistors Tr_1 to Tr_4 are contained in a single integrated circuit package and are all connected in parallel to act as an equivalent series transistor (emitter follower) which is capable of handling the full-load current, when driven from the output of the error amplifier. Transistor Tr_5 (in the same package) in conjunction with R_4 , R_5 and R_6 serves as a current limiting device. If the load current increases the p.d. across $R_4 + R_5$ increases and since the base voltage of Tr_5 is held at approximately 600mV above V_{OUT} the base current to Tr_5 through R_6 increases. Hence

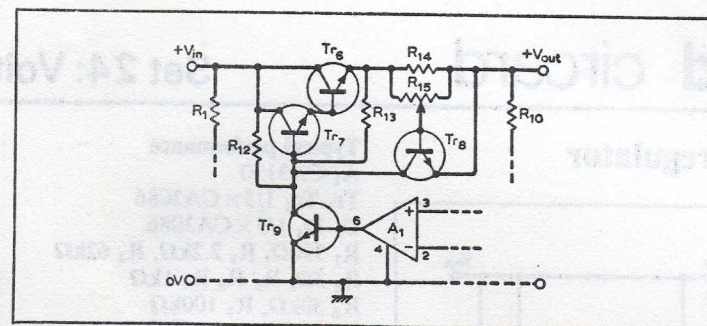

the collector current of Tr_5 increases, diverting the base current from the series pass transistors. Thus the collector currents of these transistors, and hence the load current, falls back to its previous value. The value of load current at which the current limit becomes operative is set by R_6 , the maximum limited current being determined by R_4 , a $3-\Omega$ resistor. Capacitor C_3 provides compensation for the operational amplifier the other capacitors serving to remove residual hum at the input and to control the closed-loop gain of the

amplifier at high frequencies.

Modification

Careful layout of the printed circuit is essential otherwise the circuit may oscillate. This form of circuit may be modified to provide output voltages in the range 100mV to 50V at currents up to 1A with a 55V input by making the following changes. R_1 is increased to $4.3k\Omega$, 1W and a $1k\Omega$ resistor connected between D_4 anode and Tr_6 base; otherwise the pre-regulator and voltage reference circuits are basically unchanged. The sliding contact of R_8 is

connected directly to the inverting input of A_1 . R_9 is omitted along with C_4 and the compensation capacitor C_3 is increased to 1nF. R_{10} and R_{11} are changed to $43k\Omega$ and $8.2k\Omega$ respectively, and their junction taken to the non-inverting input of A_1 . This inversion of the inputs to A_1 is required because of the addition of an inverting current-boosting stage at the output of A_1 as shown.


Darlington-connected series transistors Tr_6 and Tr_7 replace Tr_1 to Tr_4 and Tr_8 provides current limiting by adjustment of R_{15} . Typical components are Tr_6 2N3055, Tr_7 , Tr_8 2N2102, Tr_9 2N5294, R_{15} $3.3k\Omega$, 1W, R_{13} $1k\Omega$, R_{14} 1Ω , R_{15} $10k\Omega$, Tr_9 2N5294, R_{12} $3.3k\Omega$, 1W, R_{13} $1k\Omega$, R_{14} 1Ω , R_{15} $10k\Omega$, C_1 , C_3 $100\mu F$, C_2 $5\mu F$. Full load regulation 0.05%. Line regulation 0.01%/V.

Cross references

Set 24, cards 1, 2, 3, 5, 6.
Set 23, card 3.
Set 20, cards 1, 2.

© 1975 IPC Business Press Ltd.

Monolithic regulators—1

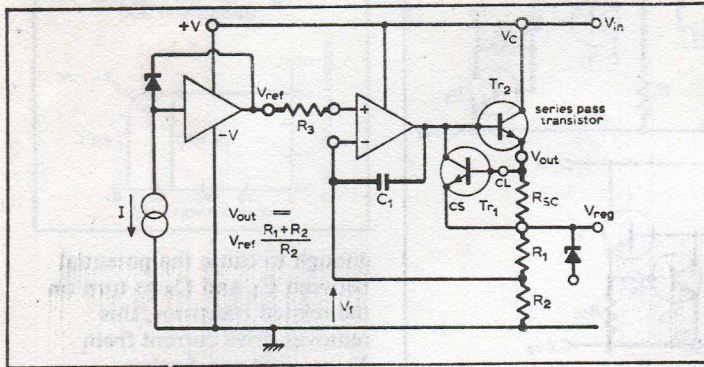

Circuit description


The schematic diagram of this regulator package is shown above, with the external components for a high voltage regulator circuit. The series-pass transistor is connected as an emitter-follower, and the amount of feedback to the internal operational-amplifier is defined by R_1 and R_2 . V_I is

approximately equal to V_{REF} because the differential input to the op-amp is very small, and hence, as $R_{SC} \ll R_1$ or R_2 . $V_{OUT} = V_{REF}(R_1 + R_2)/R_2$ i.e. the emitter of the series-pass transistor is constrained to be a multiple of V_{REF} . Therefore, if the unregulated input V_{IN} increases, this increase must be absorbed by

Typical data


IC $\mu A723C$ or LM723C
 Temperature range 0 to 70°C
 Line regulation for V_{IN} 12 to 40V 0.1%. For 12-15V, 0.01%
 Load regulation 0.03% to 30mA
 R_1 7.87k Ω $\pm 5\%$
 R_2 7.15k Ω $\pm 5\%$
 $V_{REG} + 12V$, C_1 100pF
 Ripple rejection 74dB
 Temp. coeff. of 0.003%/degC
 V_{ref} 7.15V
 Standby current 2.3mA for V_{IN} 30V
 Input voltage range 9.5 to 40V

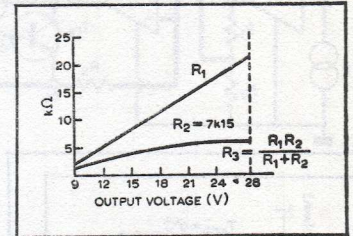an increase in the collector-emitter voltage of series transistor. Conceptually, if the emitter potential tends to increase, then V_I to the inverting input would increase, which would cause a decrease in potential at the base of the series transistor, and due to emitter-follower action, this opposes the assumed increase.



Load regulation. Percentage change in output voltage for a specified load current change.
Line regulation. Percentage change in output voltage for a defined change in input voltage. Note—above are defined for a constant junction temp.
Ripple rejection. Ratio of pk-pk input ripple voltage to pk-pk output ripple voltage.
Input-output differential. Working range of regulator based on difference between supply and regulated voltage.
Standby current. Current drain for no load on output or reference.

Monolithic regulators—2

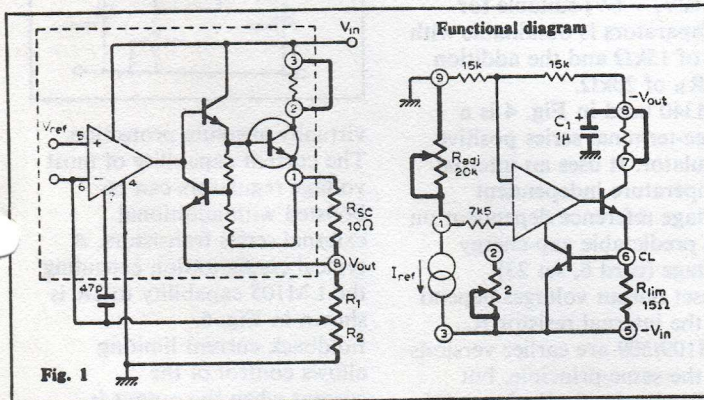

The schematic diagram of the LM105/205/305 group is within the dashed box. External components provide a basic low current positive regulator circuit.

LM305, Fig 1.

Temperature range: 0 to 70°C
 Input voltage range: 8.5 to 40V

Output voltage range: 4.5 to 30V
 Output current: 20mA
 Load regulation: 0.03% for load current 0 to 12mA
 Line regulation: depends on $V_{IN} - V_{OUT}$ differential 0.025%/V
 Parallel combination of R_1 and R_2 should be about 2k Ω
 LM305A can provide 45mA.

Negative voltage regulator

LM104, Fig. 2, Current reference is temperature compensated. Output voltage programmed by value of R_{ADJ} . R_{LIM} provides short-circuit protection. C_1 (tantalum) prevents oscillation.
 Output current: 25mA
 Input range: -50 to -8V
 Output range: -40V to -V15m
 Typical load regulation: 0.05% from 0 to 25mA
 Typical line regulation: better than 0.2% for $\pm 20\%$ input change

$$V_{OUT} = R_{ADJ}/500$$

The LM104/LM105 interconnection, Fig. 2, provides a dual polarity tracking regulator.

Using the LM104 as an inverting amplifier i.e. $+V_{OUT}$ at pin 9 appears as $-V_{OUT}$ at pin 8. $V_{IN} \geq \pm 18V$, $V_{OUT} \pm 15V$ defined by potential divider chain R_1, R_2

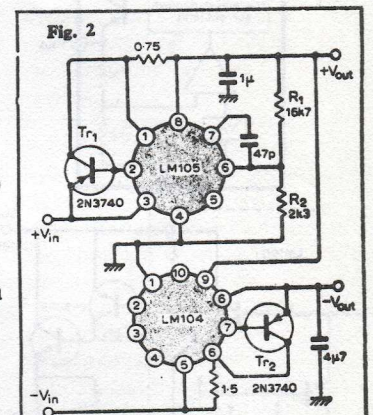


Fig. 2


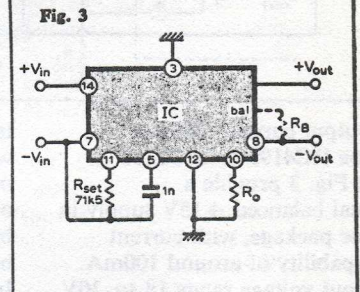
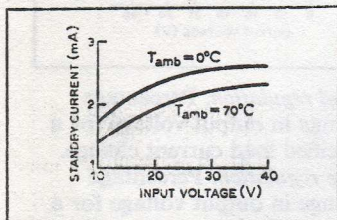




Fig. 3

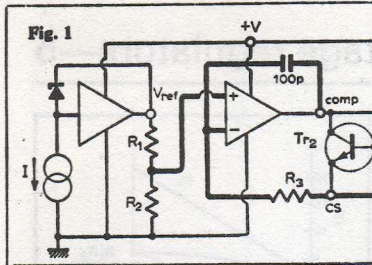

Note—regulation is sometimes defined on basis of a percentage change in input.


Fig. 1 is a low-voltage arrangement suitable for a 2 to 7V output voltage range $V_{OUT} = V_{REF}R_2/(R_1 + R_2)$ For V_{REG} of +5V, R_1 2.15k Ω , R_2 4.99k Ω , R_3 1.5k Ω .

Fig. 2 provides a negative regulated voltage suitable for a -9V to -28V range.

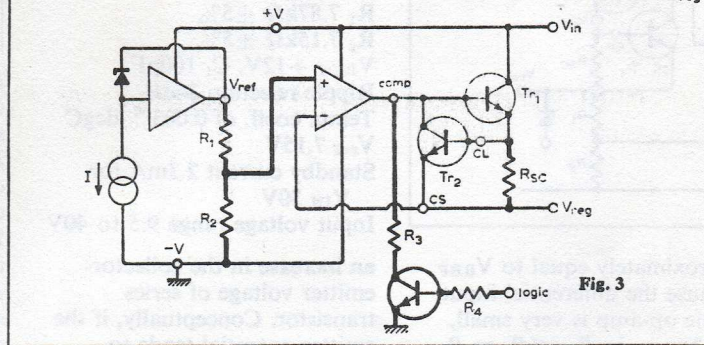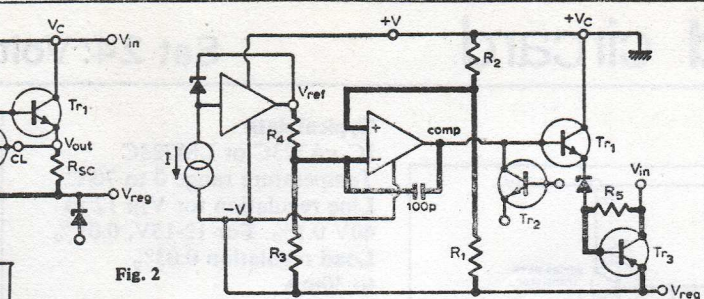


Typically $V_{REG} -15V$, R_1 3.65k Ω , R_2 11.5k Ω , R_3 R_4 3k Ω , R_5 2k Ω , Tr_3 2N4898. An extension down to -6V is possible but V^+ must be at +3V minimum.

Fig. 3 is similar to Fig. 1 but permits a remote shutdown facility via a logic source. Current limiting and sensing depends on the value of R_{SC} . When the load current is large

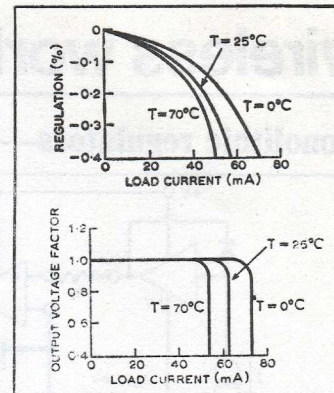

enough to cause the potential between C_L and C_S to turn on the related transistor, this removes drive current from Tr_1 to limit any further increase in output current. Curves above show typical load regulation and current limiting characteristics for V_{OUT} 5V, R_{SC} 10 Ω , V_{IN} +12V.

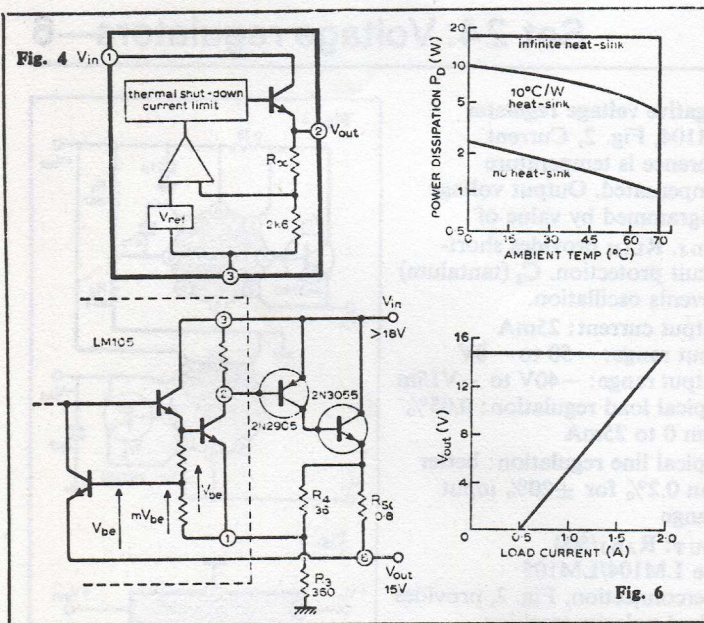Further reading
Hinatek, E. R. Users Handbook of Integrated Circuits, Wiley, 1973.
 $\mu A723$ The Universal Voltage Regulator, Fairchild.




Output current: 200mA
The RC4195 or MC1468 in Fig. 3 provide a dual balanced $\pm 15V$ supply in one package, with current capability of around 100mA. Input voltage range 18 to 30V. The RC4194 is a dual

tracking voltage regulator in which the positive and negative output voltages are adjustable over the range 0.05 to $\pm 32V$ by variation of R_o . This should be 2.5k Ω for each volt required. Input voltage range: 9.5 to 35V Load regulation (1 to 100mA)

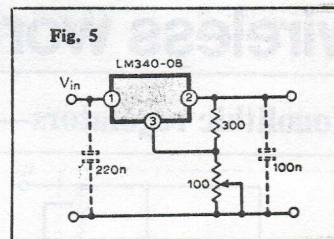
0.001% V_{OUT}/mA
Line regulation: For a 10% change in V_{IN} 0.02% V_{OUT}
Load current: 100mA
An unbalanced output (+12V, -6V) suitable for comparators is obtainable with R_o of 15k Ω and the addition of R_B of 20k Ω .

LM340 used in Fig. 4 is a three-terminal series positive regulator. It uses an internal temperature independent voltage reference dependent on the predictable gap-energy voltage (card 6, set 23). Preset output voltages depend on the internal resistor R_x . LM109/309 are earlier versions on the same principle, but designed specifically for +5V logic levels. Fig. 5 is an adjustable output circuit. Capacitors are optional depending on transient response requirement and distance from supply. Another advantage of this i.c. is the internal circuitry which provides shutdown of the regulator if the die temperature reaches 175°C, thus providing



virtually absolute protection. The current capability of most voltage regulators can be boosted with additional external series transistors. A typical configuration extending the LM105 capability to 2A is shown in Fig. 6. Foldback current limiting allows control of the current when the output is short circuit.

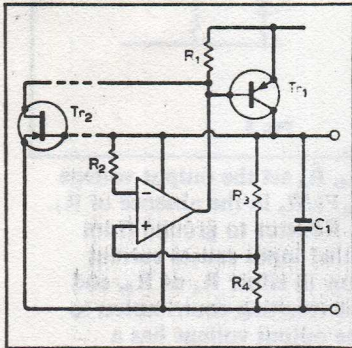Voltage regulation using current-differencing amplifiers



Typical performance


R_1 330 Ω
 R_2 1M Ω
 R_3, R_4 10k Ω potentiometer set for V_o of 5V. Typically
 $R_4=675\Omega$
 Tr_1 BC125
 Tr_2 2N5457
 C 10 μ F tantalum
 V +7V

Circuit description

The basic voltage regulators described previously using a current-differencing amplifier had two distinct limitations. The obvious one is the very limited output current available, and this can be overcome by adding an emitter follower inside the feedback

loop. This actually increases the second problem—that the minimum value of the supply voltage has to be one or more volts above the regulated output. It is possible to solve both problems while simultaneously improving the regulation against supply changes, if the amplifier is


supplied from the regulator output (simultaneously regulating the supply to the three other amplifiers in the package). The trick is to make use of the ability of the output stage to sink current safely even when the output potential is greater than that on the amplifier positive supply terminal (provided the difference does not exceed 5V, breakdown in the internal p-n junctions is avoided). The minimum sink current in this mode is 1.3mA and R_1 is chosen so that Tr_1 is kept out of conduction when minimum output current is required. In the simplest form shown 'n V_{be} ' biasing is used that fixes the output voltage at $(R_3/R_4+1)V_{be}$ where the V_{be} is that of the internal transistor at the amplifier non-inverting input. R_1 provides a small bias current to the inverting input.

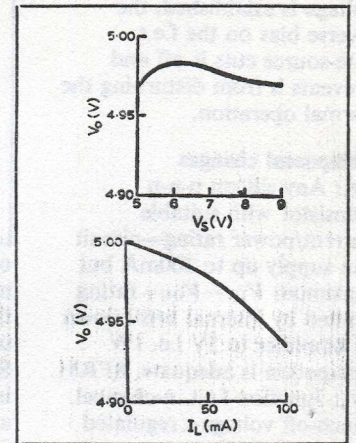

(Improved regulation would follow from the replacement of R_3 by a suitable zener diode.) The main problem remaining is that the circuit is not self-starting since with output temporarily at zero no current flows and the state is held permanently. One solution is to add a junction f.e.t. of low

wireless world circard

Dual-polarity regulator

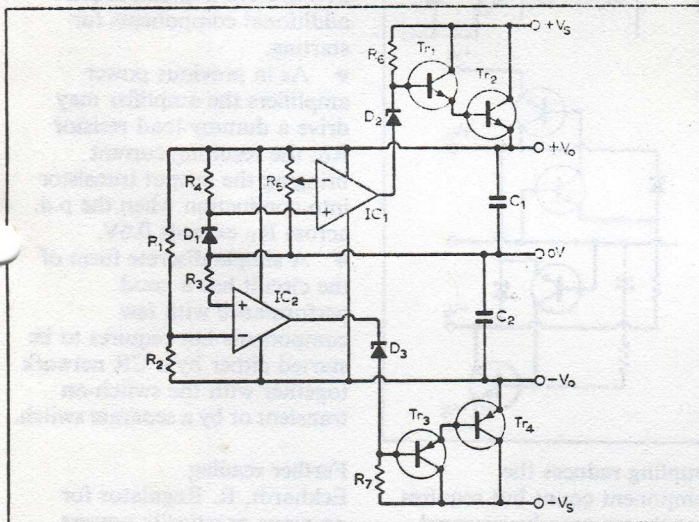

Typical performance

IC_{1-2} 741
 Tr_1 BFR41, Tr_2 2N3055
 Tr_3 BFR81, Tr_4 2N2955
 D_{1-3} 6.8V zener diodes

R_{1-2} 8.2k Ω , R_3 3.9k Ω
 R_4 2.2k Ω ; R_5 10k Ω
 R_{6-7} 22k Ω , C_{1-2} 47 μ F
 V_s \pm 15V
 V_o \pm 10V, I_o 0-1A

Circuit description

In a dual regulator it can be very important that the outputs track well. This can be achieved by having one section dependent on a particular zener diode or other reference element; the other output uses the output of the first as its own reference. Any variation in the zener voltage whether due to supply or temperature changes affects each equally. To maximize the regulation the zener diode and the error amplifiers should if possible be supplied from the regulated outputs. This can complicate the coupling network between each amplifier and the power output stage. The positive regulator compares a variable portion of the output via R_5 with the constant voltage across D_1 . Any difference is amplified by IC_1 , whose output is coupled via D_2 to the

Darlington pair composed of $Tr_1, 2$. The negative output is controlled by IC_2 via $Tr_3, 4$, the amplifier operating in the virtual earth mode with $R_1, 2$ defining the inverting gain. For $R_1=R_2$ the positive and negative output voltages are equal in magnitude. As shown the positive output is restricted to values greater than the zener voltage, but the negative output can take up values from zero to just short of the negative supply. The outputs are highly stabilized against both supply and load current changes (typically to within 1 or 2mV) and the stability is limited by that of the zener diode D_1 .

Component changes

$IC_{1, 2}$. Most compensated op-amps may be directly substituted. The output stage contributes no additional voltage gain and hence no

pinch-off voltage and on-current sufficient to bring Tr_1 into conduction. Once the output voltage is established, the reverse bias on the f.e.t. gate-source cuts it off and prevents it from disturbing the normal operation.

Component changes

Tr_1 : Any silicon p-n-p transistor with suitable current/power rating—circuit can supply up to 200mA but maximum $V_{IN} - V_{OUT}$ rating limited by internal breakdown of amplifier to 5V i.e. 1W dissipation is adequate. BFR81.

Tr_2 : Junction f.e.t. n-channel. Pinch-off voltage < regulated output. Zero-bias on-current must be sufficient to drive Tr_1 into conduction—typically >2mA.

R_1 : 150 to 390 Ω . If resistor is too high the minimum sink current of 1.3mA drives Tr_1 into conduction losing control at light loading. If R_1 is too low, insufficient drive current is available for Tr_1 .

R_3, R_4 : In this mode of

change in compensation is warranted. Tr_{1-4} . The drive transistors are standard silicon medium-power devices and a maximum collector current of a few tens of milliamperes is sufficient for output currents beyond 1A. The power devices may then have to dissipate considerable power under short circuit conditions, i.e. current limiting should be added or adequate heat-sinking provided.

D_1 : Zener diode with low temperature coefficient for minimum drift.


D_{2-3} : Not critical. Included to allow op-amp outputs to remain in linear region while retaining control of output. Diodes can be replaced by resistors typically of same value as R_{6-7} .

$R_{1,2}$: Equal for precise tracking of outputs. 1 to 100k Ω .

R_3 : Minimizes offset if $R_3 = R_1/R_2$. Can be omitted.

R_4 : Sets zener diode current to optimum for low drift.

R_5 : May be padded out with

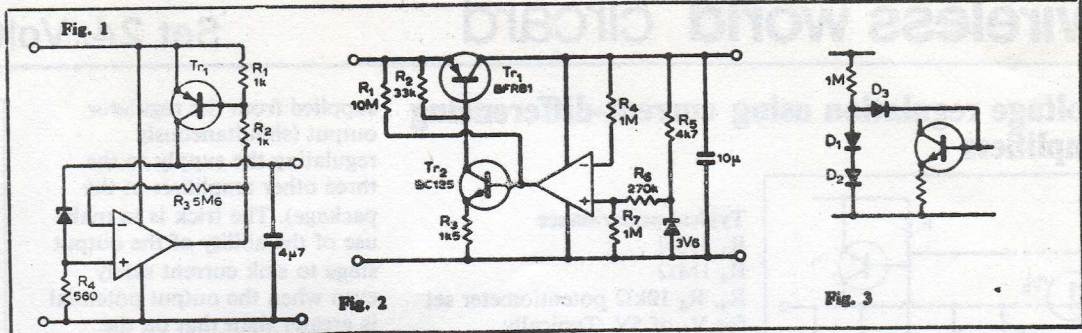

operation, the potential at the non-inverting input is 0.6V and the ratio of $R_3:R_4$ scales this up to $[(R_3/R_4)+1] \cdot 0.6V$. Stability is considerably increased by replacing R_3 with a zener diode when $V_o = V_z + 0.6V$.

R_2 : Not critical. Sets operating currents of input transistors. Suitable values 1 to 10M Ω .

Circuit modifications

- For increased input-output voltage differential the amplifier is supplied directly from $V+$. To allow the amplifier output to be out of saturation the base of Tr_1 is


driven through a potential divider. Without this Tr_1 could not be driven off. The upper voltage limit is then the rating of the i.c. (36V for the LM3900). All other amplifiers in the package are subject to the full supply voltage variations.

- To increase the supply voltage rating further while retaining a low $(V_{IN} - V_{OUT})$ a second transistor is added such that all terminals of the amplifier are operated at a low voltage while Tr_1, Tr_2 must be chosen for a suitable voltage rating. An alternative zener circuit is shown in which

R_6, R_4 set the output voltage $R_4 V_z / R_6$ in the absence of R_7 . A Resistor to ground from either input causes current flow in either R_4 or R_6 , and the resulting contribution to the output voltage has a temperature coefficient which can be used for overall temperature compensation. As shown R_7 contributes $-[1 + (R_4/R_7)] V_{be}$ to the output.

- To remove the effect of supply variations via R_1 a diode network is chosen that ensures self-starting but has D_3 dropping out of conduction after starting has been achieved.

© 1975 IPC Business Press Ltd.

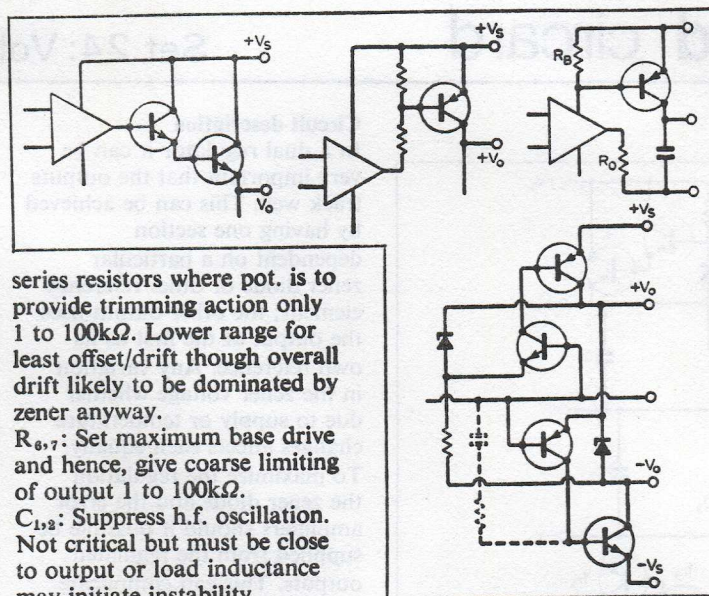

series resistors where pot. is to provide trimming action only 1 to 100k Ω . Lower range for least offset/drift though overall drift likely to be dominated by zener anyway.

$R_{6,7}$: Set maximum base drive and hence, give coarse limiting of output 1 to 100k Ω .

$C_{1,2}$: Suppress h.f. oscillation. Not critical but must be close to output or load inductance may initiate instability.

V_s : Because amplifiers powered from regulated outputs, V_s can be high if transistors have appropriate ratings. Increase $D_{1,2}$ voltages to match.

Circuit modifications

- The error amplifier outputs may be coupled to the power stage in several ways. Direct

coupling reduces the component count but requires that the op-amp be powered from the supply rail. The input-output differential is increased to >3V in many cases.

- To reduce this, the output stage is operated in common

emitter (with or without an intermediate driver). The inversion requires the op-amp inputs to be reversed and the resulting circuits are typically non-self-starting and require additional components for starting.

- As in previous power amplifiers the amplifier may drive a dummy load resistor R_o , the resulting current bringing the output transistor into conduction when the p.d. across R_B exceeds 0.6V.

- A simple discrete form of the circuit has a good performance with few components but requires to be started either by a CR network together with the switch-on transient or by a separate switch.


Further reading

Eckhardt, R. Regulator for op-amps practically powers itself, *Electronics*, Oct. 3, 1974, p. 106.

Holmskov, Ole, Voltage stabilizing a symmetrical power supply, *Wireless World*, May 1975, p. 226.

© 1975 IPC Business Press Ltd.

Switching regulator

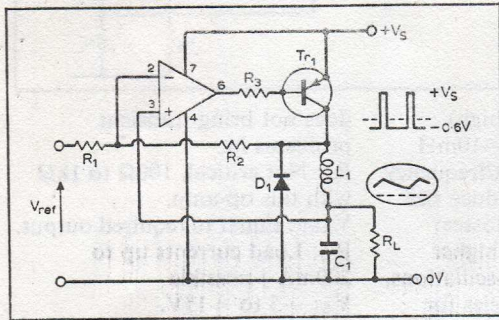


Typical performance

- IC₁ CA3130 (RCA)
- Tr₁ BFR81
- D₁ 1N4148
- L₁ 680μH
- C₁ 15μF
- R₁ 1kΩ
- R₂ 470kΩ
- R₃ 680Ω
- V_{REF} 5V
- R_L 50Ω
- V_S 10V

Circuit description

Switching regulators are related to Class-D switching amplifiers. The power stage Tr₁ conducts for a varying portion of the time. If the switching frequency is high, the current in L₁ varies little throughout

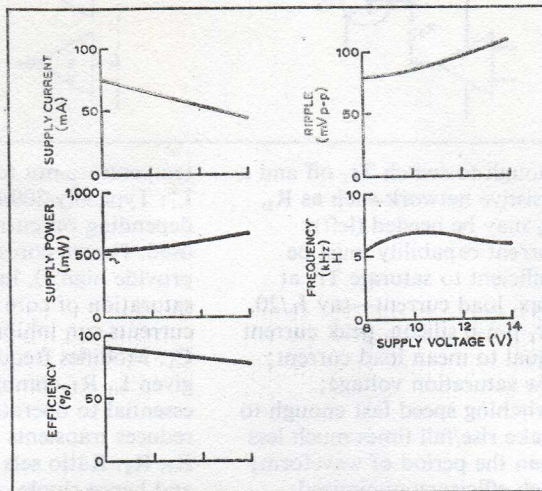the cycle, with D₁ sustaining the current in the load when the transistor is off. The inverting gain provided by Tr₁ reverse the effective polarity of gain at the amplifier inputs; 100% negative feedback is applied from the load to one input




and with L₁ short circuit, a linear regulator would result were V_{REF} to be fed directly to the other input. A small amount of hysteresis via R₂, R₁, combined with the L₁R_L creates an astable—the LR equivalent of the standard op-amp CR astable. The load voltage has a similar exponential waveform with a ripple of the order (R₁/R₂)V_S and a mean value of V_{REF} when the hysteresis is small. Power losses include those due to the speed of switching including core losses in L₁, and the “d.c.” losses such as V_{ce(sat)} for Tr₁ and the on voltage of D₁. For low output voltages the latter limits the efficiency—between 70 and 90% is common even where the output voltage is < V_S/2. As the supply voltage varies the mean current changes in the opposite sense because the

wireless world circard

Set 24: Voltage regulators—10

Self-regulating d.c.-d.c. converter

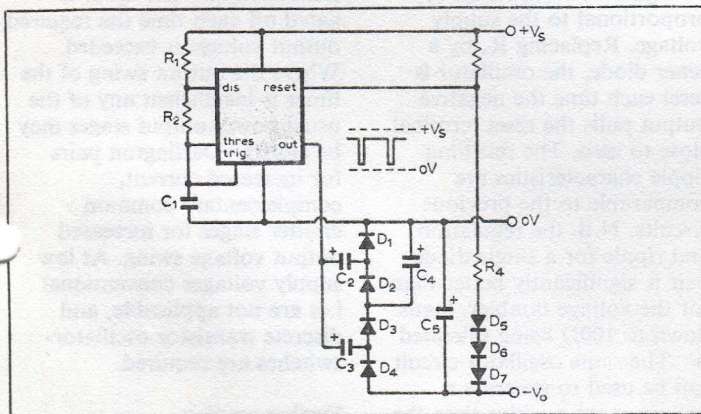

Typical performance


- IC₁ 555 timer
- D₁₋₇ 1N4148
- C₂₋₅ 47μF, C₁ 0.015μF
- R₁ 1.2kΩ, R₂ 10kΩ,
- R_{3,4} 22kΩ
- +V_S +10V
- V_O -10V
- I_O 0 to -20mA

$V_O/V_S \pm 0.5\%$ for V_S 7 to 14V

Circuit description

Dual-polarity supplies are needed in many systems where only a single supply is initially available. The circuit shown achieves this by acting as a free-running astable

oscillator producing an output voltage just less than the supply. This is applied via a diode-capacitor network D₁₋₄, C₂₋₅ to produce a negative output voltage. Assume ideal diodes, D₁ clamps the right hand side of C₂ to zero on positive output swings; similarly D₃ clamps the right hand side of C₃ to C₄. On negative swings, C₂ transfers charge via D₂ into C₄ as does C₃ through C₄. On negative swings, C₂ transfers charge via D₂ into C₄ as does C₃ through D₄ into C₅. Eventually C₂, C₄ each acquire a p.d. equal to the output swing, while C₃, C₅ achieve double that value. Two factors reduce this output voltage: losses across the diodes drop the maximum output by about 2V. The timer has a reset terminal; when the potential on this approaches ground the oscillations are inhibited.

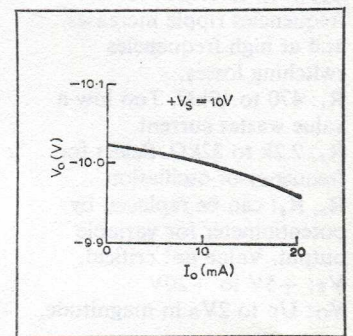

A potential divider composed of R₃, R₄ and D₅₋₇ provides a potential at the RESET terminal such that each time the magnitude of the negative output increases, the oscillation is inhibited and the magnitude decreases. The diodes optimize the tracking for |V_O| = V_S.


Component changes

IC₁: The circuit depends on the particular characteristics of the 555 timer available from

mark-space ratio is adjusted automatically via the astable action. Hence the mean power drawn from the supply depends mainly on the power required by the load.

Component changes

IC₁: This op-amp is particularly suitable for several reasons (i) high input resistance (m.o.s.) allows high R_2 : R_1 ratio without R_1 becoming too low. (ii) input common-mode range includes zero line allowing control of output down to zero. (iii) high slew-rate allows switching speeds to be increased to suit optimum frequency-range of ferrite-cored inductor. (iv) c.m.o.s. output stage allows direct coupling to Tr_1 if needed with rapid switch-off reducing charge-storage problems. Most other un-compensated op-amps and comparators can be used provided following precautions observed: V_{REF} must lie within input common-mode range; the output may not be able to swing high

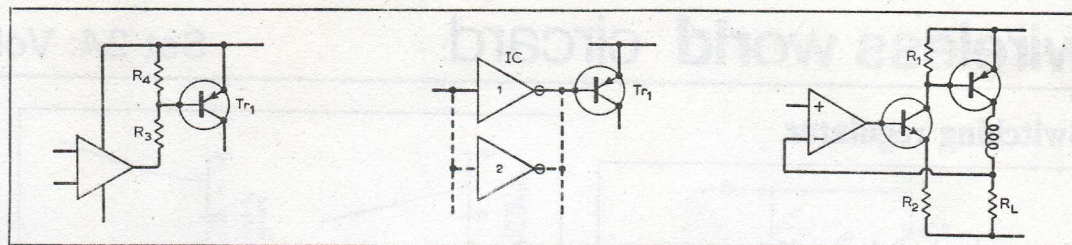

enough to switch Tr_1 off and a resistive network such as R_3 , R_4 may be needed (left); current capability must be sufficient to saturate Tr_1 at max. load current—say $I_L/20$. Tr_1 p-n-p silicon, peak current equal to mean load current; low saturation voltage; switching speed fast enough to make rise/fall times much less than the period of waveform; high efficiency minimized dissipation in transistor if above observed. **D₁:** current rating mean output current; peak inverse voltage rating (p.i.v.) V_S ; efficiency increased at low output voltages by reducing diode on-voltage (Schottky or germanium diodes if

temperature not too high). **L₁:** Typically $200\mu H$ — $10mH$ depending on current/frequency used. Ferrite cores reduce size provide high Q, low losses; saturation of core at higher currents can inhibit oscillations. **C₁:** Modifies frequencies for given L_1 R_L combination. Not essential to operation, but reduces transients in load. **R₁, R₂:** Ratio sets hysteresis and hence ripple. As ripple is reduced, so is time taken for completion of cycle i.e. frequency increases. By keeping R_1 , R_2 as large as possible injection of switching current into V_{REF} is minimized. Ratio R_2/R_1 typ. 100 to 1,000; high value gives low ripple provided increased frequency

does not bring transient problems in. **R₃:** Not critical. 100Ω to $1k\Omega$ with this op-amp. **V_{REF}:** Equal to required output. **R_L:** Load currents up to $200mA$ + possible **V_S:** +5 to +15V. **Circuit modifications** Paralleled c.m.o.s. buffers may be used to boost output drive (centre). See op-amp data sheet. Alternatively use additional transistors (right). Final stage should be common emitter for highest efficiency. **R₁, R₂** 100 to 470Ω . Outputs to 1A. **Cross references** Set 6, card 7. Set 24, card 10. Set 7, card 12.

© 1975 IPC Business Press Ltd.

most i.c. suppliers.

D₁₋₇: Not critical. Any fast silicon diodes.

C₁: 470p to $0.1\mu F$. At low frequencies ripple increases and at high frequencies switching losses.

R₁: 470 to $10k\Omega$. Too low a value wastes current.

R₂: 2.2k to $22k\Omega$. Select for frequency of oscillation.


R₃, R₄: can be replaced by potentiometer for variable output. Value not critical.

V_S: +5V to +20V

V_O: Up to $2V_S$ in magnitude.

Circuit modifications

● For some applications the circuit can be considerably simplified. Where the negative voltage required is less than the positive supply available then the rectifying network can be simplified as shown. If the precise tracking of the two supplies is not important then the compensating diodes D_{5-7} can be omitted. With R_{3-4} replaced by a potentiometer, the result is a convenient circuit for producing, say, $-6V$

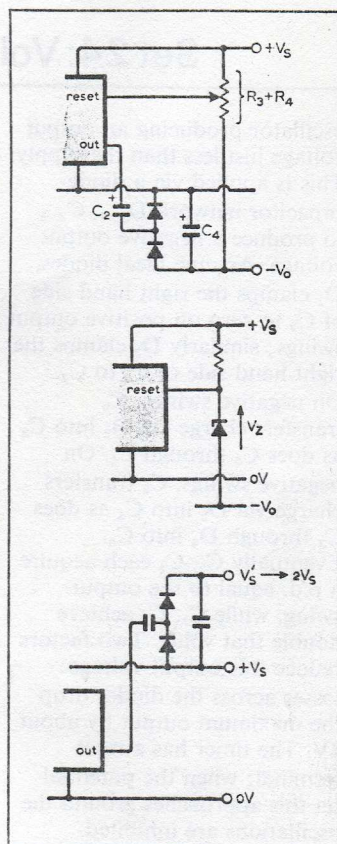

from a +12V supply as required by widely used i.c. comparators.

● A second modification allows the negative output to be regulated rather than be proportional to the supply voltage. Replacing R_4 by a zener diode, the oscillator is reset each time the negative output pulls the reset terminal close to zero. The resulting ripple characteristics are comparable to the previous circuits. N.B. the regulation and ripple for a single diode pair is significantly better than for the voltage doubler, loads down to 100Ω being tolerated

● The same oscillator circuit can be used to generate a voltage more positive than the supply as shown. To regulate the output, a separate sensing circuit would be required since the original depended on using the RESET as a virtual earth. The circuit has affinities with certain re-triggerable monostables, and those based on op-amps in which the switching action is controlled

by positive feedback can be adapted.

The two functions performed by the timer can be separated, with a clock generator driving a monostable. The latter is gated off each time the required output voltage is exceeded. Where the output swing of the timer is insufficient any of the usual power output stages may be added—Darlington pairs for increased current, complementary common emitter stages for increased output voltage swing. At low supply voltages conventional i.c.s are not applicable, and discrete transistor oscillator-switches are required.

Further reading

Gartner, T. IC timer and voltage doubler form a dc-dc converter, *Electronics*, Aug. 22, 1974.

Cross references

Set 21, card 9.
Set 10, card 2.
Set 10, card 10.
Set 24, card 9.

© 1975 IPC Business Press Ltd.