

electronics TODAY

INTERNATIONAL

JANUARY 1976, VOL. 6 No. 1

EDITORIAL

Editorial Director: Collyn Rivers
Engineering Manager: Barry Wilkinson
Technical Editor: Brian Chapman

ADVERTISING

Sydney: Terry Marsden (Manager),
15 Boundary St., Rushcutters
Bay, 2011. Tel 33-4282.
Melbourne: Clarrie Levy, Suite 24,
553 St. Kilda Rd,
Melbourne. Tel 51-9836.
Brisbane: David Wood, 11-14 Buchanan
St, West End. Brisbane.
Tel: 44-3485
Adelaide: Ad Media Group, 12-20
O'Connell St.,
N. Adelaide. Tel 267-1129.
Perth: Aubrey Barker,
38 Mounts Bay Rd.
Tel 22-3184.


PUBLISHER: Max Press

OVERSEAS

London: Electronics Today
International, 36 Ebury St, SW1 WOLW
Tel 01-730 8282. **New York:** A.C.P. 444
Madison Ave, New York, 10022.

GENERAL:

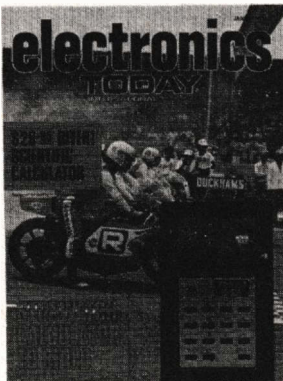Electronics Today International is
published by Modern Magazines
(Holdings) Ltd, 15 Boundary St,
Rushcutters Bay, NSW 2011. It is
printed (in 1975) by Wilke & Co,
Browns Road, Clayton, Vic and
distributed by Australian Consolidated
Press. *Recommended price only.
Copyright.



COVER: This month ETI shows how to
build a digital stopwatch *inside* an
existing calculator case – and still retain
all calculator functions. Cost? Under \$17
– including the calculator!
Background pix – Indonesian Grand
Prix – photo courtesy REVS Motorcycle
News.

PROJECTS

- NOISE GENERATOR**40
Unit generates white or pink noise for audio equipment testing.
- CALCULATOR STOPWATCH**47
Build a stopwatch inside a calculator! Cost – under \$17 all parts.
- RF SIGNAL GENERATOR**55
Simple effective unit for servicing AM receivers
- AUDIO MILLIVOLTMETER**73
Sensitive instrument for 'A' weighted audio noise and signal measurements.

FEATURES

- SCIENTIFIC CALCULATOR OFFER**11
Unitrex 901SR calculator for \$29.95 plus \$2 post and packing!
- LOW-COST 'SCOPES**14
What they do – and how to choose one – also market survey.
- CA 3130 OPERATIONAL AMPLIFIER**28
Versatile new device has input impedance of 1.5×10^{12} ohms.
- DESIGN YOUR OWN FM TUNER Pt. 3**62
How to design a high quality FM-tuner – it's easier than you might think.
- IDEAS FOR EXPERIMENTERS**70
Potpourri of circuits, ideas, hints and tips.
- ELECTRONICS IT'S EASY!**79
Code converters and display systems.
- AUDIO FACTS**91
Regular monthly audio feature – latest news on audio developments.

NEWS & INFORMATION

NEWS 5; NEXT MONTH'S ISSUE 10; ADVERTISING INDEX 94; SERVICE
NOTES 94.



A MODERN MAGAZINES PUBLICATION



It's very gratifying when you start
at the bottom and work your way to the top.

At AKAI, we concentrate on being better. Not bigger. So you'll probably find bigger hi-fi ranges than ours. But you'll have your work cut out finding a better range. For quality. Performance. And reliability. All our equipment is listed below. And each and every piece of hi-fi equipment distributed by AKAI Australia is

covered by the Complete Protection Plan[†]. Which means 12 months full parts and labour warranty, 12 months free insurance and a lifetime guarantee on all GX recording heads. So, whether you're new to hi-fi, or an old hand at it, you'll find something exactly right. We'll stack our reputation on it.

PORTABLE	\$	OPEN REEL RECORDERS		AMPLIFIERS		TURNTABLES	
CT-5	196.00	1730SS*	535.00	AA-5210	215.00	AP-001C	155.00
CASSETTE RECORDERS		GX-1820	785.00	AA-5210DB	299.00	AP-003	235.00
CS-34	280.00	OPEN REEL DECKS		AA-5510	299.00	AP-004	260.00
GXC-39	380.00	202-DSS*	625.00	AA-5810	375.00		
GXC-46	410.00	GX-210D	570.00	RECEIVERS		N.B. All turntables complete with cartridge, stylus, base and lid.	
GXC-65	469.00	GX-230D	620.00	AA-810	245.00	SPEAKERS	(per pair)
CASSETTE DECKS		GX-265D	710.00	AA-810DB	310.00	SW-30	75.00
CS-34D	220.00	GX-270D	685.00	AA-910DB	375.00	SW-35	119.00
GXC-36D	289.00	GX-286D	925.00	AA-930	450.00	SW-42	150.00
GXC-39D	360.00	GX-400D	1445.00	AA-940	565.00	SW-126	245.00
GXC-75D	498.00	GX-400DP	1365.00	AS-960*	495.00	SW-136	310.00
GXC-325D	550.00	GX-400DSS*	1593.00	AS-970*	575.00	SW-156	385.00
GXC-710D	439.00	GX-600D	770.00	AS-980*	850.00	SW-176	580.00
CARTRIDGE RECORDERS		GX-600DP	770.00	TUNER			
GXR-82	395.00	GX-600DB	885.00	AT-550	260.00		
CR-80SS*	528.00	GX-630DSS*	1090.00				
CARTRIDGE DECKS		GX-1820D	715.00				
GXR-82D	345.00	4000DB	435.00				
CR-80DSS*	435.00						

[†] The AKAI Complete Protection Plan warranty does not cover equipment purchased outside Australia.
70608

* 4 channel.
DB in model name signifies Dolby System.
Prices quoted are the recommended retail prices only


AKAI
The name you don't have to
justify to your friends.

PRINCE PHILIP PRIZE FOR AUSTRALIAN DESIGN 1975

Standard Telephones and Cables Electronic Minimat EM 90 Private Automatic Branch Exchange (PABX) has been awarded a Certificate of Merit for winning the Operational Systems Category in the Prince Philip Prize for Australian Design 1975.

The PABX operating mechanism in the Electronic Minimat EM90 departs from the normal cross-bar automatic exchange equipment and substitutes an all solid state equipment. In addition, the system of control from the manual console incorporates a number of excellent features of an innovative nature.

Although utilising some technology based on the work of international affiliates, the whole design, conception and execution has been carried out in Australia by a large development team. Many standard electronic and telephone components have been incorporated, but the resulting system has many unique features in a design of reduced size and weight. These include push button dialling for the operator, busy extension display, extension number and status display, console metering, night service security, operator restriction of access, priority facility, automatic call-back, S.T.D.

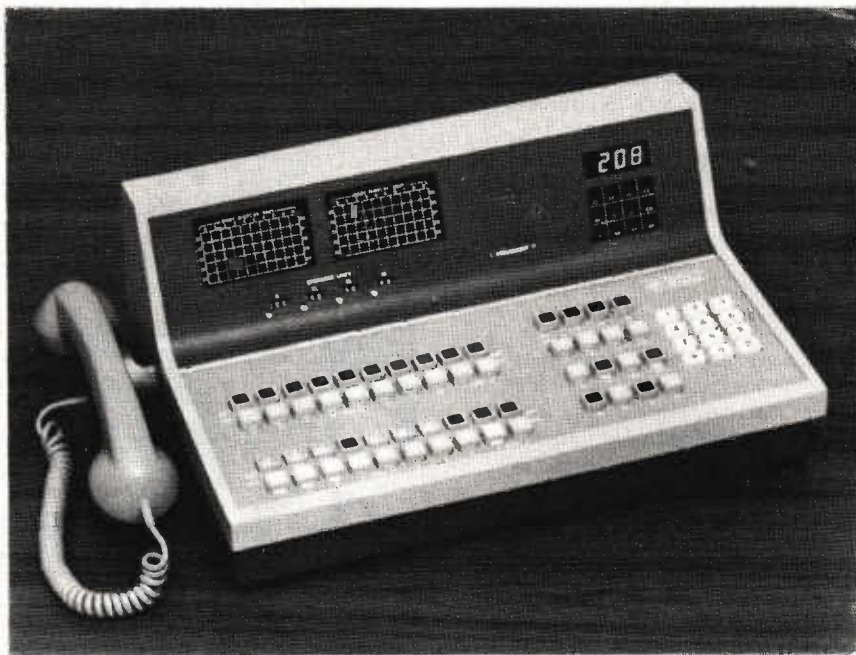

barring and most importantly, both-way exchange lines. The design of the console itself is functional and attractive. In use it is simple to operate.

As a system it provides the maximum of desirable facilities. As equipment, the use of complete solid-state circuitry ensures ease of servicing and substantially trouble free operation. The Judges were most impressed with the system.

AUTOMATIC FOCUSING OF CAMERAS

Honeywell's Photographic Products Division have announced an electronic development that will make automatic focusing of cameras commercially feasible for the first time.

The development, a small solid-state electronic device called the Honeywell Visitronic Auto/Focus, represents a "significant breakthrough in electronic optical technology and is expected to have considerable impact on the photographic industry," said Robert L. Pennock, Vice President and General Manager of the Division.

"Visitronic Auto/Focus can be designed into virtually any type of camera and as a result, the picture-taking process from focusing to exposure can be fully automatic," Pennock said.

Automatic exposure already is widely used in camera design, he pointed out, but automatic electronic focusing has been under intense investigation and experimentation for many years by scientists and engineers throughout the world.

The device which works on electronic and optical principles, was developed by Honeywell's Photographic Products Division with the assistance of the company's Minneapolis-based, Corporate Research Centre and Solid State Electronics Centre.

SARNOFF LEAVES RCA

Robert Sarnoff has announced his resignation as chairman and chief executive officer of RCA.

Sarnoff's resignation came as a total surprise to the industry. RCA decline to comment except to state that 'Mr Sarnoff intends to pursue other interests of a personal nature'.

Mr. Sarnoff recently married Anna Moffo of the Metropolitan Opera.

CONCORDE NOISE PROBLEM NOT SOLVABLE?

During Concorde's visit to Australia in 1972, this magazine asked the then Federal government for permission to publish their officially measured noise figures.

This permission was refused so we consequently commissioned our acoustical consultants to take measurements for us.

As expected we found that the aircraft's noise level was very much higher than its protagonists had claimed and in fact exceeded by a wide margin the noise level standards of most airports.

It now seems that Concorde's noise problems may be unsolvable. A recent editorial in Nature (October 30 1975) states that present noise standards at London Airport require Concorde to generate no more than 107 EPNdB. Modern subsonic planes meet these standards with at least 6 dB in hand. But Concorde exceeds the required level sometimes by as much as 10 dB.

Nature go on to say 'The story has some rather unpleasant implications for the relationship between government and science and technology.

news digest

Those who worked in noise were aware, years ago, that the Concorde problem was essentially insoluble, and that the chances of finding a palliative in a strictly limited time were negligible. And yet this message never got through to, or was ignored by, those who might, given a few years, have found political or administrative solutions which would have alleviated the present situation. "We couldn't write to the papers about it", one engineer told us, "quite apart from the risk of professional suicide, we knew that an immense public relations effort would be mounted to demonstrate how limited the horizons were bound to be of one man in one laboratory."

SOLAR CELL IS 20% EFFICIENT

A 20% efficient solar cell has been developed by Varian Associates. According to the firm, its 8 mm diameter cell produces 10 watts of electricity directly from a focused sunlight beam. Varian makes the cell from a gallium arsenide material developed by IBM. Although the cells are not yet in commercial production, Varian says it plans eventually to build a system of cells that can generate 1 kW.

ASTRONOMERS DETECT INDIVIDUAL PHOTONS

A digital television system for astronomy, developed by University of Arizona astronomers, is sensitive enough to detect individual photons of light coming into a telescope and record them for immediate playback. As a result it is possible to see objects 100 times fainter than previously possible. The system is based on a special television tube — a silicon intensified target tube — that records 64 000 points of light simultaneously. The information then is sent in digital form to a computer, which removes the image's noise. Photographs or a spectrogram can be produced.

ELECTRONIC WATCH HAS CONTINUOUS DISPLAY

A challenge to LED and LCD watches has been launched by America's Optel Corporation (Princeton N.J.). Optel have just released details of a prototype

unit incorporating an 'electro-chromic' display claimed to be capable of showing a continuous readout without constant battery power.

The prototype unit is a three function device which shows hours and minutes continuously and seconds on demand. The corporation say that there are still 'some problems' with the design but claim a two to five year life for the prototype readout which they say has a 200 millisecond response time.

Optel's prototype unit was shown at a recent meeting of the International Society for Hybrid Microelectronics.

In Switzerland, Brown Boveri SA has introduced a new field effect liquid crystal with permanent readout of hours, minutes and seconds.

NOVUS TO MAKE SCIENTIFIC CALCULATORS

National Semiconductor plan to add complex scientific calculators to its Novus range — starting in January 1976. The new calculators are intended to compete with basically similar units from Hewlett Packard and Texas Instruments.

PROGRAMMED TV FROM TOSHIBA

A TV channel preselector is shortly to be produced by Toshiba. The device enables the viewer to pre-programme his selections for the day.

The actuating device is a clocked complementary-MOS chip which automatically switches a varactor tuned colour TV set to the desired channel at the preset time.

The selector can be set for up to 16 programmes. It is battery powered to ensure that programmes are not missed due to power failure during the day.

SIGNETICS DROP CMOS

Our US correspondent advises us that Signetics have just telexed all their US sales staff and distributors advising them that the company will be discontinuing their CMOS logic series as from November 3.

Signetics' sales of CMOS products fell short of their projected target by a considerable margin. We understand that whilst the 1975 target was US\$200 million, actual sales are not expected to exceed US\$120 million.

SIMPLE PROJECTS BOOK

HOW TO BUILD PROJECTS. CRYSTAL RADIOS. ONE-TRANSISTOR RADIO. KILL THAT GHOST. TV MASTHEAD AMPLIFIER. FM ANTENNA. SIMPLE SPEAKER. SIMPLE AMP.

SIMPLE PROJECTS
from electronics today **\$2.00**

... UNIT. SIMPLE
COODHAILER. BASIC POWER SUPPLY. FET DC VOLTMETER. LIGHT DIMMER. DRILL SPEED CONTROLLER. TWO BIREN CIRCUITS. HI-POWER STROBE. LIGHT OPERATED SWITCH. CAR ALARM. AUTO-AMP. FOUR-CHANNEL FOR \$10. BUYING COMPONENTS. TRANSISTOR TESTER. COURTESY LIGHT EXTENDER. BETTER SOUND FOR \$5. ETI UTILIBOARD. SIMPLE INTERCOMS. MONOPHONIC ORGAN.

More than thirty five of the most popular simple projects ever published in Electronics Today have now been published in a single 94 page book.

Called 'Simple Projects' the book is available now from all main newsagents for a recommended retail price of \$2.00. It is also available directly from Electronics Today — see advertisement elsewhere in this issue.

PAL COLOUR CAMERA SYSTEM



A simple, inexpensive, PAL colour camera system has been released by Hagemeyer (Australasia) B.V., sole importers of JVC video and audio equipment in Australia.

The camera has been designed for field or studio use. An ergonomically designed hand grip converts the camera to a portable unit for use with JVC PAL colour portable recorder PV-4800E. Fitted to a tripod and equipped with


a mains adaptor, the camera system provides video and audio signals for use with PAL colour Video U-matic cassette recorder or ½" PAL colour recorders to the EIA-J standard.

For studio use JVC's remote controlled PAL colour U-matic video cassette recorder CR-6000E is remotely controlled in the record function from the stop/start switch on the camera.

Apart from the 4:1 zoom lens together with constantly variable aperture, the camera has only two switches. One for 240 Vac power and the other is a three position colour temperature control.

Error free operation together with low cost makes this colour camera system eminently suitable for users in the fields of education, industry and commerce.

LASER PARTICLE COUNTER

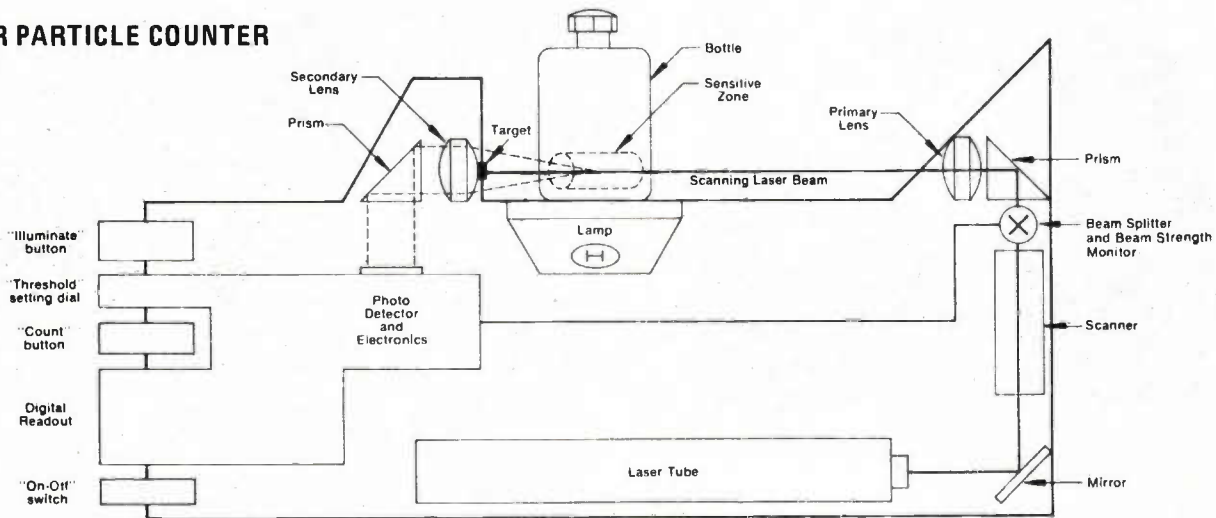

A new American instrument counts micron-sized suspended particles in fluids in 15 seconds. The instrument called the Prototron ILI 1000 is non-destructive and can test fluids in sealed glass or clear plastic containers.

The number of particles in one millimetre of fluid is determined by

counting the pulses of light scattered by the solids in a focussed laser beam. It is claimed that the machine is sensitive to particles in the range 1-100 microns. Variable threshold level enables particles to be counted according to size within the specified range.

One advantage offered is the ability

to test such products as intravenous liquids without breaking the seal on the bottle. Other applications include the testing of photographic liquids, hydraulic fluids and pharmaceuticals.

The Prototron instrument is available through Foss Electric (Aust.) Pty. Ltd, 251 Condamine St, Balgowlah, NSW.

TRUE DUAL BEAM PLUS STORAGE OSCILLOSCOPE


Philips Industries have recently introduced a new 10 MHz 2 mV storage oscilloscope that features true dual beam operation, a technique developed by Philips in order to eliminate the need for chopped or alternate mode displays. This technique ensures that the phase relationship of the signals is always correct and allows the complete waveform to be displayed.

In this new oscilloscope, designated the PM 3234, this technique is combined with that of half tone storage and the result is a very versatile specification that is of particular value for

obtaining true displays and records of single shot phenomena.

When the storage facility is not re-

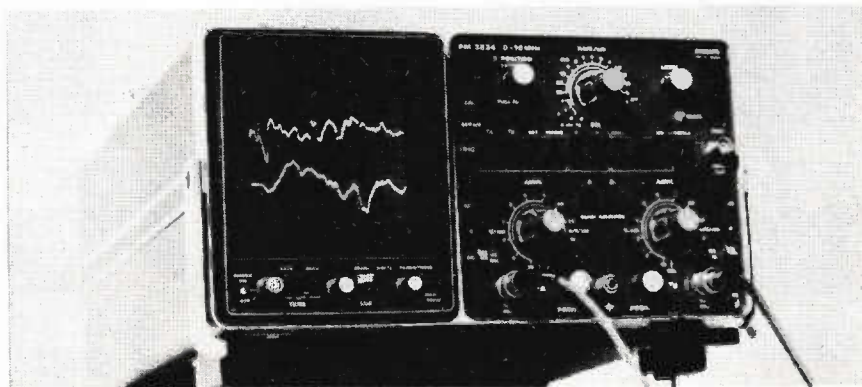quired the PM 3234 operates in the normal manner but with the added benefit of having continuous control




Hand made sound.

With JBL you know you're not just paying for the name. You're paying for a quality of sound that is impossible to mass produce.



JBL's require equipment so specialised we had to design and build our own.

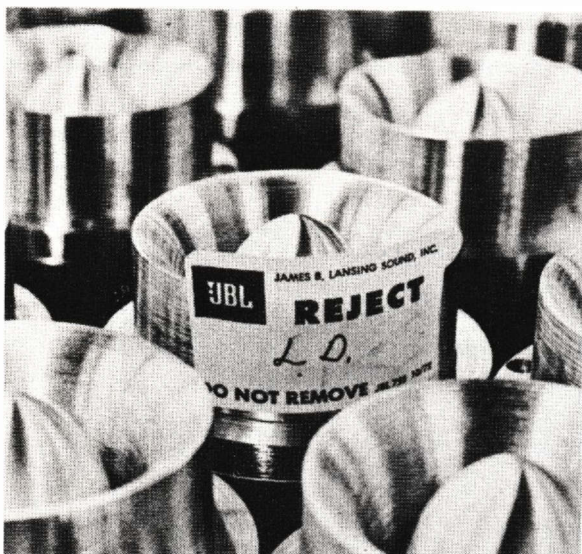If we cut out all the things we do by hand, and the checking double checking and rejecting, we could probably produce a speaker for about 25% less. But then it wouldn't really be a JBL. Our reputation is based on an unchanging commitment to quality. We make no compromises. Never have, never will. The same applies to all the JBL range. Like the JBL Decades.




Near enough is just not good enough.



Cabinet tolerances are typically held to 1/64th of an inch.

Until we developed them just recently, most JBL's were out of the normal person's reach. Now you can own a pair of JBL's for around \$500.

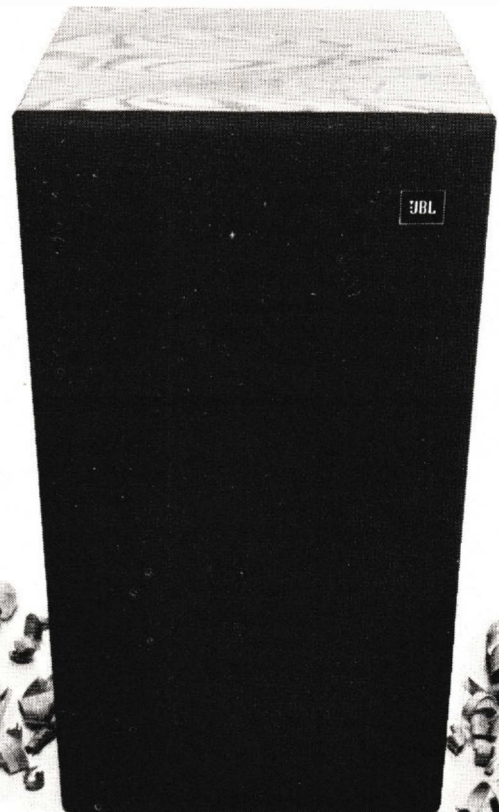They're still more expensive than ordinary speakers, but then they're JBL's aren't they.



harman australia Pty Ltd

271 Harbord Road, Brookvale, Tel 939 2922
PO Box 6, Brookvale NSW 2100

JBL is the registered trademark of James B. Lansing Sound Inc. Los Angeles



of the persistence from 0.3 seconds to 1.5 minutes. This allows difficult-to-see signals like low frequency signals with flicker and high frequency, fast rise time pulses with low repetition rates to be displayed in the optimum manner.

PORTABLE PRECISION TEMPERATURE BRIDGE

Leeds & Northrup Australia Pty. Limited have recently concluded an agreement with the CSIRO, which will permit Leeds & Northrup to develop, manufacture and market (under licence to CSIRO) a new, advanced design, versatile, precise ac resistance thermometer bridge.

The new, low-cost thermometer bridge was designed by Mr. Clive Pickup — a scientist at the National Measurement Laboratory, University Grounds, Chippendale, N.S.W. It was developed to overcome practical measuring problems encountered by scientists, research staff and industrial personnel who traditionally use liquid in glass thermometers, or thermocouples and thermistors plus an assortment of electrical or electronic equipment to make accurate temperature measurements.

The clever application of previously known — but not used — measuring principles, together with the incorporation of modern electronic technology, has produced a bridge design which is believed to be in advance of any known equivalent instrument on the world market. Mr. Pickup's original bread board design has been redeveloped by Leeds & Northrup engineers in Australia and, additionally, new thermometer Ro compensation circuitry has been added, which now makes the temperature bridge truly unique. The result is a simple to use,

small, attractively designed portable instrument, which can measure and record temperature changes as small as 0.001°C, yet can equally well be used by unskilled industrial staff to measure temperatures to the lower levels of precision normally required for routine industrial purposes. The robust construction of the bridge makes it very suitable in such applications.


Additionally a comprehensive range of accessories has been developed in Australia to complement the bridge. Included are two general purpose hand held rugged type miniature resistance thermometer assemblies which have proven to be ideal for typical laboratory, plant and field applications in the temperature range -200 to +500°C.

The instrument, which will be known as the 8078 Portable Precision Temperature Bridge, will be built by Leeds & Northrup Australia Pty. Limited. Two prototype production units have already been built, which have passed rigorous evaluation testing at the National Measurement Laboratory. Production units are expected to be available in February 1976 and a comprehensive world-wide marketing programme is planned by Leeds & Northrup Australia Pty. Limited to ensure the success of the project.

VACUUM/PRESSURE MEASUREMENT SYSTEMS CATALOGUE

Datametrics have produced a new catalogue called "Vacuum/Pressure Measurement Systems" describing instruments for measuring pressure and vacuums.

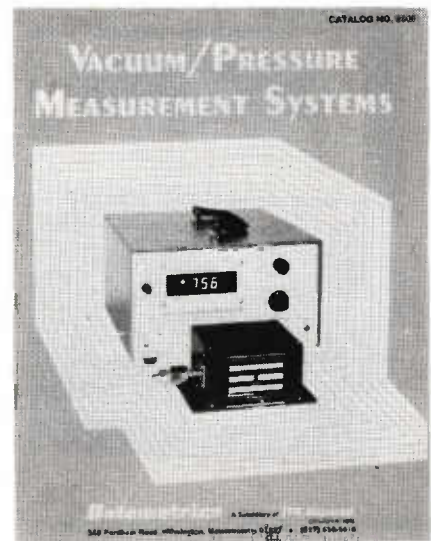The catalogue outlines operating principles of Barocel sensors and also describes and illustrates self-contained



instruments, modular instruments, popular accessories and options.

Datametrics transducers employ capacitance sensing techniques which give them high stability and wide dynamic range. Typical system resolution is claimed to be one part in a million with sensitivity down to one micro-torr. Pressure and vacuum ranges from one torr to 100 psi are available at John Morris Pty. Limited, P.O. Box 80, Chatswood . . . NSW 2067.

PHILIPS DIGITAL MULTIMETER

Philips compact, high quality, digital multimeter is highly competitive with standard analogue service instruments presently on the market. Designated the PM 2513, this new DMM offers a number of outstanding features.

The heart of the PM 2513 is an LSI circuit which performs part of the analogue circuit functions, the A/D conversion and the digital signal evaluation. The integrated circuit drives directly a very bright, 3½ digit, seven segment LED display with automatic decimal point. The display is recessed, so it is eminently readable, even under high ambient light conditions. It also features a polarity indication, plus an indication for range overloading and low battery loading.

Ac and dc voltages are measured in five ranges, from 0.1 to 600 V and 0.1 to 1000 V respectively.

Resolution is 100 μV in the 0.1 V range, and accuracy is ± 0.2% f.s.d ± 0.3% rdg for dc and ± 0.2% f.s.d ± 1% rdg for ac. Errors due to the instrument loading the circuit under



news digest



test are eliminated by the high input impedance of 10 M. Five ac and dc current ranges extend from 100 μ A to 1 A fsd, with a resolution of 100 μ A in the lowest range. Resistance is measured from 0.1 Ω resolution to 1000 k fsd. The accuracy for both

current and resistance measurements is 0.2% fsd \pm 1.5% rdg. The overall accuracy is thus an order of magnitude higher than that of analogue instruments. Response time is also very low, with an average of one second for each measurement.

An unusual feature of the PM 2513 is built-in provision for temperature measurements, which can be made with an optional probe. A function selector button and a range setting are provided for this purpose. Surface temperature measurements can thus be made simply and economically in a range of -50°C to $+200^{\circ}\text{C}$, with a resolution of 0.1 $^{\circ}\text{C}$ and an accuracy of $\pm 1^{\circ}\text{C}$.

CANNIBALS AND MISSIONARIES

Last month we published a constructional project to represent in electrical form the following puzzle:

Three missionaries and three cannibals came to a river they wanted to

cross. A little boat at the bank would carry only two people. All the missionaries could row, but only one of the cannibals could row — he wore a white shirt and had been to Oxford. If at any time, on either side of the river, the cannibals outnumber the missionaries then the cannibals will eat the missionaries, which, understandably, the missionaries didn't want. Problem: how did they cross safely?

For those who made the project and think it can't be solved — and for those still struggling with the problem on bits of paper — here's a solution:

M means any missionary. C means either of the non-rowing cannibals. C2 means the cannibal who can row.

1. C and C2 go over
2. C2 comes back
3. C and C2 go over
4. C2 comes back
5. M and M go over
6. M and C come back
7. M and C2 go over
8. M and C come back
9. M and M go over
10. C2 comes back
11. C and C2 go over
12. C2 comes back
13. C and C2 go over

next month

PROJECTS

- * **TOP QUALITY STEREO FM TUNER**
Simple to construct unit has LED frequency indication, varicap tuning — preset plus manual — auto frequency control.
- * **MAGNAVOX 10-50 LOUDSPEAKER**
The earlier Magnavox 8-30 speaker was a winner! Here's its even better successor.

RADIO AMATEURS

- * **SOLID STATE CONVERTERS**
Converters for 28, 52, and 144 MHz bands.
- * **RF MARKER GENERATOR.**
Accurate RF frequency marker
- * **DIGITAL TEMPERATURE METER**
Full three digit display.

The feature articles listed above are included amongst those currently scheduled for our February issue. However, unforeseeable circumstances, such as highly topical news or developments may affect the final issue content.

electronics
TODAY
INTERNATIONAL

February
Issue
— on sale
mid-January.

Special Readers' Offer

UNITREX 901SR

Scientific Calculator

\$29.95*

* plus \$2 postage and packing.



JUST TWELVE MONTHS ago we offered readers the opportunity to buy a pocket scientific calculator for \$59.50. The response was extraordinary — over 1500 were sold within a week of the offer being published. At the time of the offer, competitive units were priced at \$100 upwards so our special offer was a bargain indeed.

Now, we have an equally attractive offer. Electronics Today International have made arrangements for Unitrex to supply our readers with their excellent 901SR scientific calculator for the very low price of \$29.95 plus two dollars postage and packing. The normal selling price of this unit at the date of publication was \$39.95 plus \$2 postage and packing.

The Unitrex 901SR is an eight-digit scientific calculator offering an easily-readable, green, seven-segment display.

It has a full range of 26 scientific functions including natural and common logarithms and their reciprocals; square root; x to a power; trig functions and their inverse as well as pi and reciprocals.

The calculator has a very flexible 6-key memory together with operations in degrees, radians, or grads mode.

The 901SR does not have scientific notation, but when two eight digit numbers (for example) are multiplied, an answer is obtained with the decimal point positioned eight places to the left of its true position. An overflow sign is now displayed and the calculator locks out. Depressing the clear key, once, deletes the overflow — lockout and symbol and calculation may then continue.

The unit is powered by two AA-sized dry cells.

NOTES

We regret that we cannot arrange to supply these special-offer units against a sales-tax exemption.

The units can only be obtained in the manner outlined below. Electronics Today International cannot supply directly nor can undertake to demonstrate or discuss details of the units offered.

All units will be thoroughly inspected by Unitrex before despatch. The package should be carefully inspected before accepting delivery. Acceptance should be refused if the package is damaged.

Whilst every possible effort will be made to fulfill readers' orders, this offer is subject to stocks being available. So if you want to be sure of receiving this special bargain-price unit send your cheque in soon!

Orders must be addressed exactly as per the coupon below. Please note — due to current postal delays, readers should expect a delay of between three to four weeks between posting an order and obtaining delivery.

Finally — in the improbable event of the unit not working — please return it directly to Unitrex, 414 Collins St, Melbourne, Vic 3000. NOT repeat NOT to ourselves. This offer closes on January 31st 1976.

WARRANTY

The Unitrex 901SR calculators offered carry the same warranty as those sold at full price. That is — "the calculator is warranted (except for batteries) for a period of 12 months from original purchase date — under normal use and service against defective materials or workmanship. Defective parts will be repaired or replaced at our (Unitrex's) option when the calculator is returned prepaid to Unitrex of Australia Pty Ltd., 414 Collins St, Melbourne, Vic 3000. The warranty is void if the calculator has been damaged by accident or misuse. Removal or alteration of serial number or repair by unauthorised personnel also voids warranty."

"The warranty contains the entire obligation of Unitrex of Australia Pty Ltd and no other warranties, expressed, implied or statutory are given — this warranty does not exclude limit restrict or modify any condition or warranty implied by the Trade Practices Act 1974, or other State laws or Acts. . ."

UNITREX CALCULATOR OFFER.


NAME

ADDRESS

Please forward Unitrex Scientific Calculator/s.
My cheque/postal note for \$31.95 (including postage and packing) is enclosed. (Make cheque/postal note payable to 'Unitrex Offer').

SEND TO UNITREX CALCULATOR OFFER.
c/- ELECTRONICS TODAY INTERNATIONAL
15, BOUNDARY ST,
RUSHCUTTERS BAY. NSW 2011.


FROM **Honeywell**

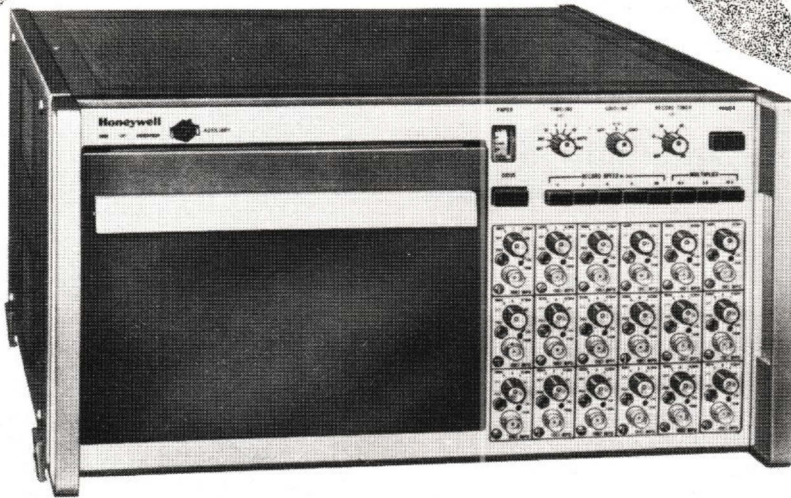

FIBRE OPTIC *Visicorder* OSCILLOGRAPHS

1858 Series: New concept fibre-optic CRT recorder complete with self-contained signal conditioning ... a compact 18-channel Graphic Data Acquisition System.

Since their introduction by Honeywell Visicorder oscillographs have set the standards for high speed graphic recording, Honeywell's Visicorder oscillographs record each channel's data by means of precisely controlled light beams. The art of light beam oscillography has been greatly enhanced by the use of UV-sensitive direct-print paper, which can be used easily in all Visicorder oscillographs. No stylus, ink, powder, chemicals or heaters are required. When exposed by UV light in the oscillograph, the latent image appears as the direct-print paper emerges into visible light. When extremely high writing speed and resolution are required, certain models can be used with wet or dry processed film or paper.

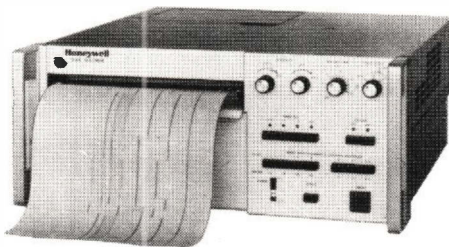

The Model 1508B Visicorder is a direct-writing Oscillographic Recorder designed to provide maximum usefulness, versatility, operator convenience, and exceptionally high accuracy and reliability.

FO RECORDER FEATURES

- ★ Inertialess recording—no moving elements, no styli
- ★ No trace overshoot
- ★ Sharp static traces without high frequency "wipe-out"
- 18-channel system in single 8¾ inch high package
- Front panel plug-in signal conditioning modules
- DC—5000 Hz response at up to 7.2 inch trace amplitude
- 100 μ V-300 input sensitivity, to 300V common mode
- Direct writing, 8 inch record width, 200 ft. record length
- 0.1% accuracy 5 interval timing system with accentuated tenth line
- Time-interval marker
- Auto-linearised for increased data accuracy
- Numbered trace identification
- Wide-range, dc-servo drive system
- 0.1 to 120 ips record speeds
- 42 discrete record speeds with binary addition push-buttons
- Remote drive and speed control
- Internal record takeup
- Automatic record-length control
- 120/240V, 50-400 Hz power, switch selectable
- Lightweight, low power consumption
- Rack or table mounting
- Wide selection of signal-conditioning modules available
- Easy to use as an oscilloscope—just add signal input connections

For full information contact Australian Representatives:

JACOBY 
MITCHELL

Specifications quoted are for general guidance only, are subject to verification and change without notice.

215 North Rocks Rd., North Rocks,
N.S.W. 2151. Phone 630 7400.

OFFICES: Melbourne 44 5021 ● Adelaide 293 6117
● Brisbane 52 8266 ● Perth 81 4144

18/75

Isn't it nice to know that someone still makes Hi-Fi like this?

You'll find that Lux units usually perform rather better than their printed specifications. For instance if we claimed our amplifiers could do 100 mph it wouldn't be downhill with the wind behind us. Our specifications are minimum standards and the goal is always ultimate performance. With Lux you're liable to get a little more than you bargained for.



LUX 309, 308

To Lux, sound is not only a science, but an art. That's why the company conducts tests not only with engineers, but with musicians in different fields to ensure that Lux amplifiers sound best, apart from what looks good in brochures.

Consider: the precise tonal balance with LUX's exclusive, and the world's first, linear equalizer. A dual rail power supply system that ensures a clear,

tight bass response down to 5Hz with absolute control of speakers. A differential input, fully complementary direct coupled power amplifier that offers you a genuine 75W x 2 RMS into 8 ohms. Main amp and preamp distortion below 0.03%, frequency response 10-50,000Hz.

And above all, the Lux 'ultimate fidelity' —the quality of sound that must be heard to be believed!



Hear L 308, L 309, and AM/FM STEREO RECEIVER R800 (40 + 40 watts, 8 ohms) at the addresses below — an experience in living sound that will thrill you!


Distributed in Australia by:

INTERDYN

INTERNATIONAL DYNAMICS
(AGENCIES) PTY. LTD.
23 Elma Rd., North Cheltenham,
Melbourne, Victoria 3192

Available from:

A.C.T.: Duratone Hi Fi, Cnr Botany St & Altree Crt, Phillip 2606. Telephone: 82-1388.
N.S.W.: M & G Hoskins Pty Ltd, 400 Kent St, Sydney 2000. Telephone: 546-1464, 547-1093.
Qld.: Stereo Supplies, 95 Turbot St, Brisbane 4000. Telephone: 21-3623. S.A.: Challenge Hi Fi Stereo, 98 Pirie St, Adelaide 5000. Telephone: 223-3699. TAS.: Audio Services, 9 Wilson St, Burnie 7320. Telephone: 31-4111. VIC.: Encof Electronics Pty Ltd, 431 Bridge Rd, Richmond 3121. Telephone: 42-3762. W.A.: Arena Distributors, 282 Hay St, Perth 6000. Telephone: 25-2899.

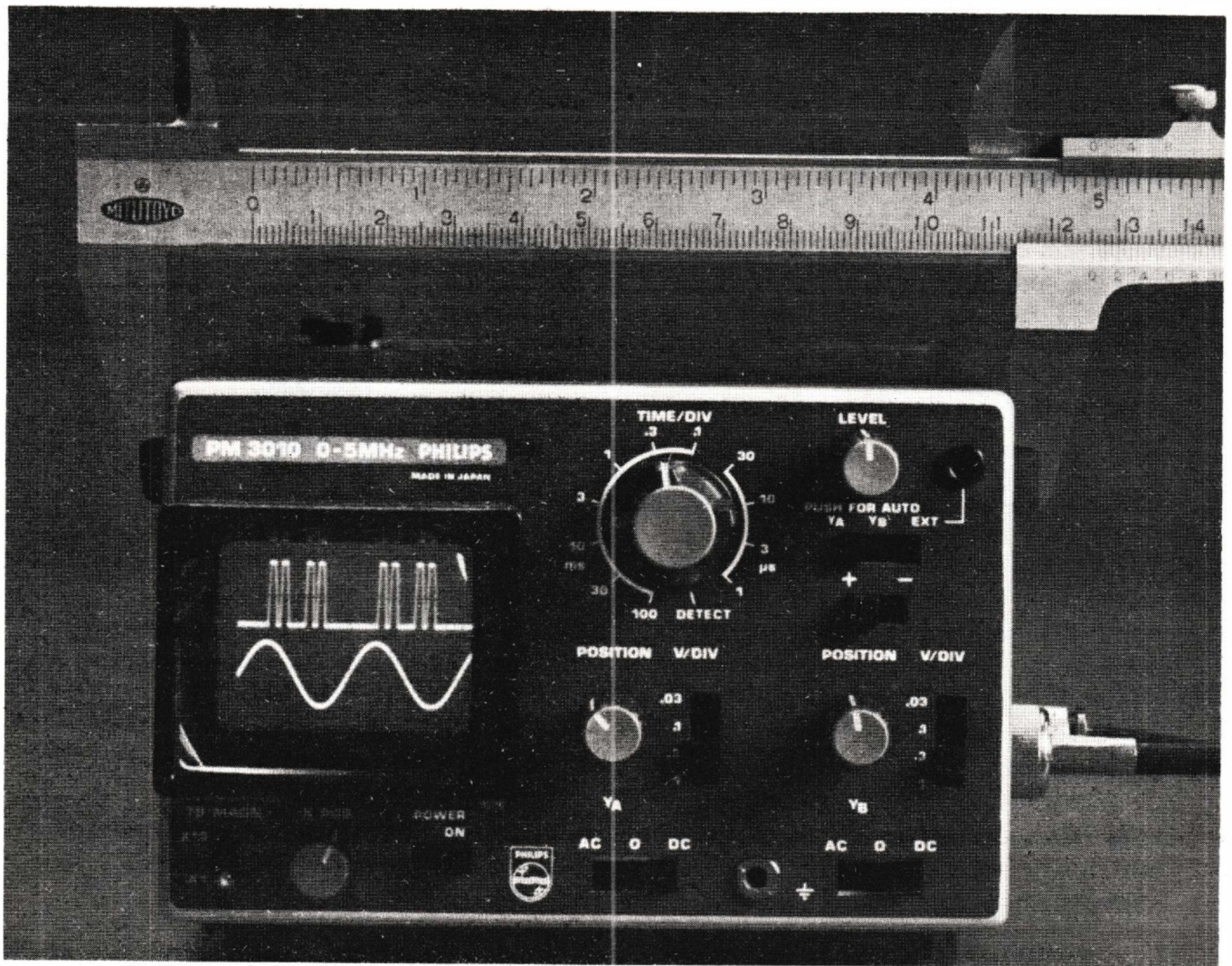

LOW COST 'SCOPES

What they do—and how to choose one

THE EXTENT to which an oscilloscope can be used depends largely on the instrument itself — and the most versatile 'scopes are usually the most expensive.

One can pay as little as about \$100 for a small, general purpose, or service type 'scope and \$2000 or more for a wide-band multi-purpose instrument with a storage c.r.t. facility. However, good secondhand instruments are available, mostly of the older valve type and these are nearly equal in performance, and accuracy to their modern transistorised counterparts, *providing* they are in good condition and one has the means of checking calibration etc.

As a general rule, the choice of a 'scope should be made according to the kind of work one wishes to do. As a guide, instruments costing between \$100 and about \$400 are usually perfectly adequate for audio, radio,

TV and electronics applications of a general nature. A double beam (two separate traces) instrument is a great asset and allows input and output waveforms to be displayed simultaneously for comparison but, whatever type is used, it is important to know its limitations and the calibration accuracy. For example, a 'scope with a Y amplifier bandwidth of up to say, 2 MHz will not show the amplitude of a 5 MHz signal in true relationship to one at 1 MHz. One would not be able accurately to measure the duration of a voltage pulse in terms of microseconds with a fastest timebase of a few milliseconds; to display a 1 μ s pulse opened out to cover one centimetre on a ten centimetre c.r.t. screen would require a timebase speed of 10 μ s. Signal amplitudes can only be measured accurately if the attenuators for input signals and the Y (or X) amplifiers are

in good order. Last but not least comes interpretation of the display itself and here really useful information can only be obtained from intelligent observation made in conjunction with accurate calibration and full knowledge of the performance parameters of the 'scope itself.

CALIBRATION

For the benefit of those unfamiliar with the oscilloscope, a few examples concerned with calibration may not be amiss. The oscillogram in Fig.1 shows a typical timebase waveform (B) beneath the negative-going trace flyback suppression pulse: Now the timebase waveform looks linear, which it is, and the flyback suppression pulse coincides exactly with the return of the timebase waveform from zero to maximum amplitude. A very linear timebase is important otherwise

repetitive waveforms will appear as crowding together toward one side or the other of the display. An example of good linearity is shown in Fig.2 in which (A) is the timebase waveform and (B) an actual display of squarewaves of 1 kHz. The three complete cycles of square-waves are uniform in width and since 1 kHz is a time duration of 1 mS, the timebase is 3 mS. Note that the timebase is synchronised to the square-waves and good synchronisation is also important, particularly when examining coincident waveforms.

Most oscilloscopes have a calibrated graticule over the c.r.t., usually divided into centimetre squares as in Fig.3 against which is displayed a square-wave. If the vertical calibration is say 0.5 V per centimetre, then the amplitude of the square-wave is almost 2 V. The frequency of the square-wave is unknown and only a complete half-cycle is displayed but the horizontal calibration is say 0.1 ms/cm. The duration of the half-cycle is almost $5 \times 0.1 \text{ ms} = 0.5 \text{ ms}$ which gives 1 ms for the full cycle, or a frequency of 1000 Hz.

Finally Fig. 4 shows five complete cycles of a square-wave at a frequency of 1000 Hz (A). What is the duration of the time base? Each complete cycle is 1 ms so the timebase speed is 5 ms, (just over in fact as another quarter-cycle appears at the extreme right). The waveform (B) below, shows marker pips, derived by differentiation of the square-wave. These are more convenient for calibration of a timebase of unknown duration. The square-wave is simply passed through a CR circuit (Fig. 5) and the positive or negative-going pulses can be rectified out.

Having devoted a little space to calibration and to some extent interpretation of displays, let us now look at some typical applications of the oscilloscope. These are relatively few and fairly basic for any attempt to cover *all* the possibilities would require endless editions of ETI.

MISLEADING DISPLAYS

False information can be given by an oscilloscope display because of unwanted signals from circuits under test, defects in the oscilloscope itself and so on. It is also important to make full use of the various timebase speeds when analysing displayed waveforms. A simple case is shown in Fig. 6 where (A) is a 1000 Hz sine wave but appears to be duplicated. Reducing the timebase speed reveals that this is due to modulation by another signal of lower frequency, in this case 50 Hz mains hum which could come from the circuit being tested, unscreened leads, or even the 'scope itself.

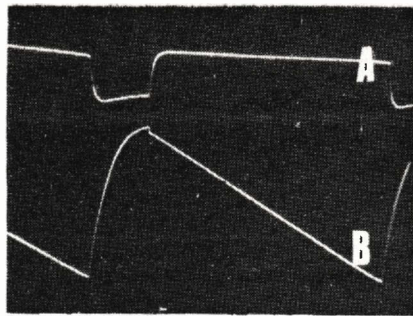


Fig.1. Typical time base waveform (B) with flyback suppression pulse (A) Note excellent linearity of time base waveform.

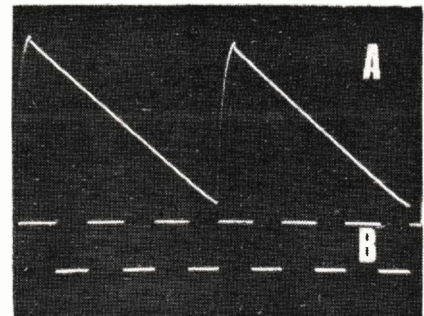


Fig.2. Time base waveform (A) against displayed square-waves (B) to show synchronisation. Text explains time relationship.

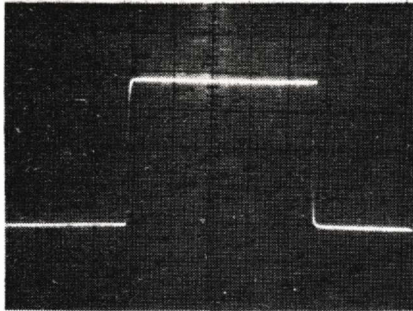


Fig.3. Graticule in centimetre squares provides voltage (Y deflection) against time scale (X deflection) calibration (see text for interpretation).

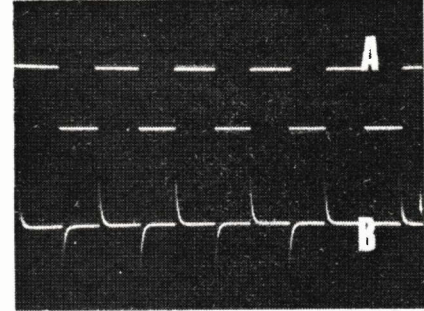


Fig.4. Display of square-waves (A) and marker pips obtained by differentiation. See also Fig.5 and text for further explanation.

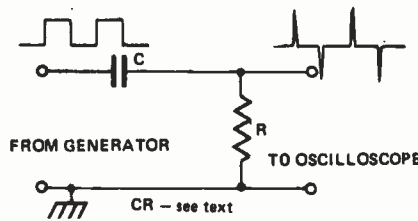


Fig.5. Simple RC network to obtain marker pips from a square-wave signal and which lend themselves for time scale calibration A diode may be connected across R to eliminate positive and/or negative going pulses as desired.


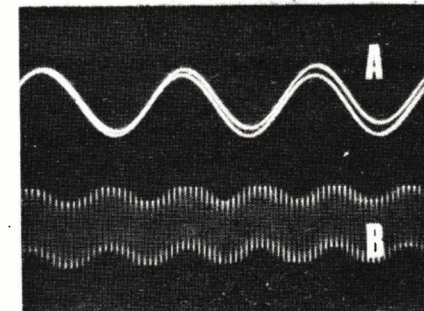


Fig.6. (A) Sine-wave deflected by (B) 50 Hz hum modulation.

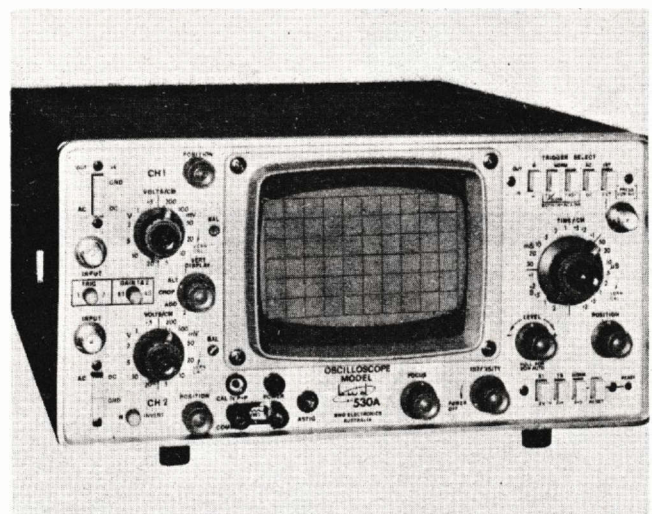BWD is the only Australian manufacturer of oscilloscopes. The 530A is a dual trace 20 MHz instrument featuring 20 nanosecond signal delay, comprehensive triggering and optional battery supply.



4

TOP QUALITY SYSTEMS TO CHOOSE FROM

Leak 600 Speakers
TEAC AS.100 Amplifier
Sansui 525/91ED *Rank Turntable

\$749



Sony SS.7100 Speakers
Sansui 4400 Amplifiers
Apan Bfu. 121 Turntable

\$559



Nikko 500 Amplifier
PHF 3 ways Speakers
Sansui 212 Turntable

\$449




Technics SU.3000 Amplifier
Kenwood 1022 Turntable
PHF 2 ways speakers

\$379



KENT HI-FI

412 KENT STREET, SYDNEY Ph. 29-6973

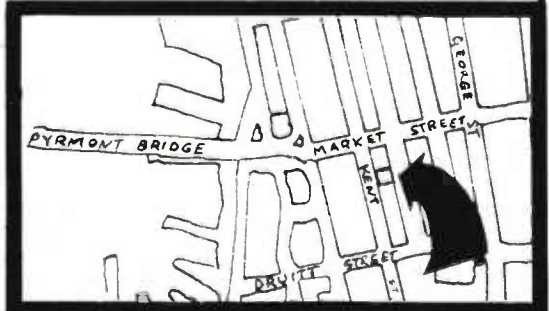

LOW COST 'SCOPES

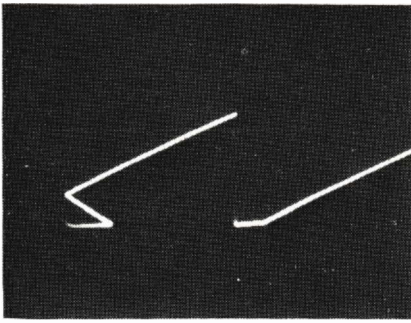


Fig. 7. Distortion of displayed waveform due to crosstalk within 'scope circuitry itself.

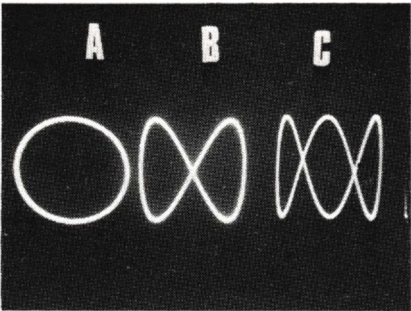


Fig. 9. Typical Lissajous patterns of 1:1, 2:1 and 3:1. See text for interpretation.

In Fig. 7 a ramp voltage waveform is shown but the first cycle is distorted, in this case by crosstalk in the 'scope, so it pays to investigate not only the equipment being tested but also the 'scope itself when things do not appear as they should.

PHASE SHIFT

The oscilloscope can be used to determine phase shift, of signals, through an amplifier for instance, by feeding the input signal to the Y plates and the output signal to the X plates. Some 'scopes have what is called an *XY facility* for this and matched amplifiers but accuracy will be limited by phase shift in the X and Y amplifiers themselves. When there is no phase shift (0°) or reversal to 180° , a diagonal line will appear in one direction or the other, as in Fig. 8A. An ellipse indicates phase shift at angles between 0° and 180° , or 180° and 360° , for example at 45° , 135° , 225° and so on, until the angle is either 90° or 270° at which a full circle is displayed, as in Fig. 8A. The phase angle can be ascertained as per Fig. 8B.

LISSAJOUS PATTERNS

Determination of an unknown frequency with the aid of a known frequency and an oscilloscope can be


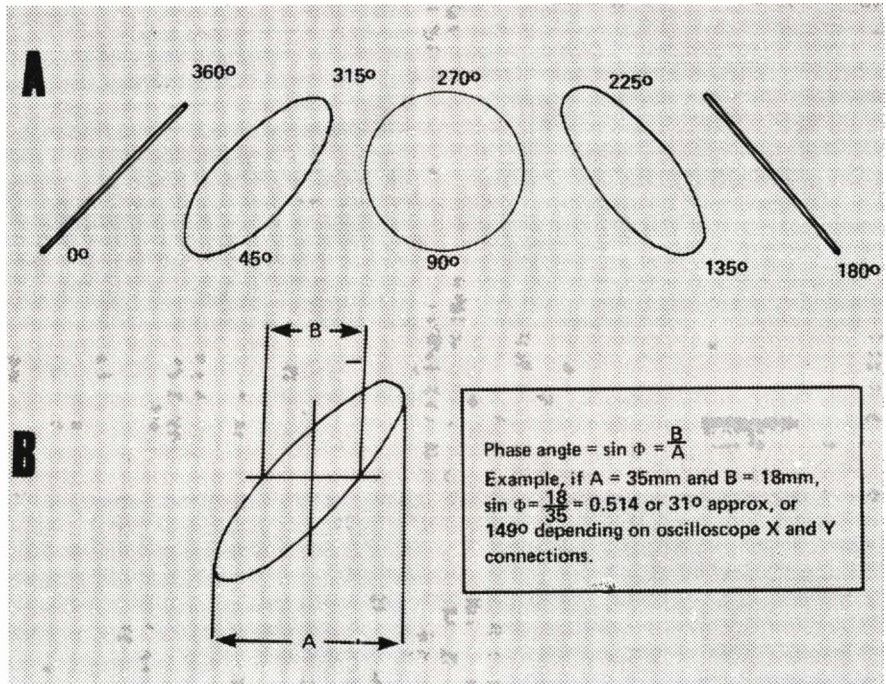


Fig. 8. (A) Phase angles. See text for explanation. (B) Determination of phase angle from an oscilloscope.

made by the Lissajous method (after the French physicist M. Lissajous). The known frequency is connected to say, the Y plates and the unknown to the X plates. When the unknown exactly equals the known then a circle is formed as in Fig. 9A if the signals

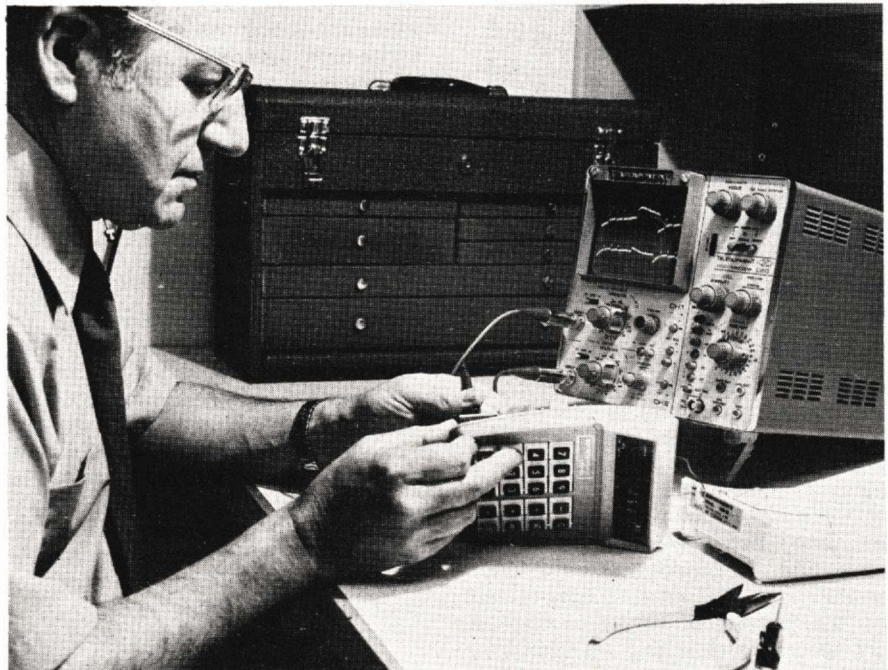are of equal amplitude. If the frequency difference is 2 to 1 then two loops will be formed as Fig. 9 (B and C), and so on. When the loops are above each other (turn the page sideways) the frequency ratios are reversed e.g., $1/2$ or $1/3$ etc.



Dual beam operation is essential in the servicing of digital equipment. Here a Telequipment model D66 is being used to fault find an electronic calculator.

LOW COST 'SCOPES

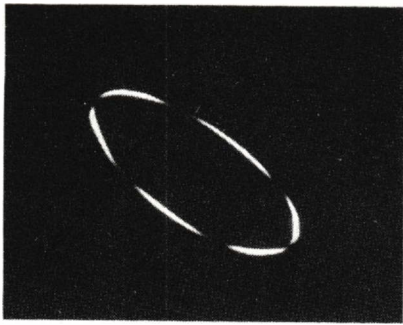


Fig. 10. Frequency comparison by Z modulation is explained in the text.

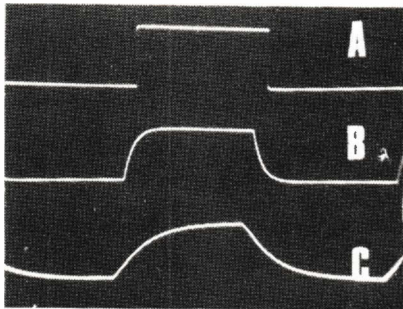


Fig. 13. Amplifier tests with square-waves. (A) 1000 Hz square-wave input signal. (B) indicates fairly good high frequency response falling away about 20 kHz. (C) indicates poor high frequency response falling away badly at probably less than 10 Hz.

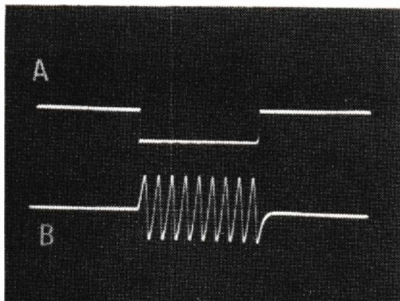


Fig. 16. Coincident pulse waveforms. See text for explanation.

A similar technique is Z modulation (brilliance modulation of the c.r.t.) and many 'scopes have this facility. In Fig. 10, an ellipse has been formed by phase shift (it may be a circle) of a signal of known frequency. Signals of an unknown, and in this case higher, frequency have been applied to the c.r.t. grid to produce the brilliance modulation. The ratio is determined by the number of bright or blacked out spaces which in Fig. 10 is six, i.e., a 6 to 1 ratio.

SOME AUDIO APPLICATIONS

Square-wave testing is popular with

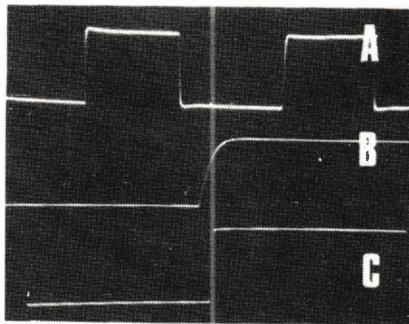


Fig. 11. (A) Appears to be a good square-wave with a fast leading edge. (B) reveals it is not so fast (several μsec) whereas (C) has a rise time of 1 μsec .

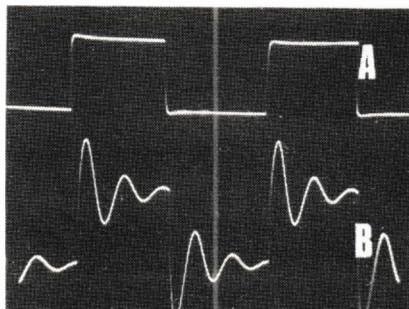


Fig. 14. Square-wave test for ringing. (A) input signal (B) Output from amplifier showing severe ringing due to inductive circuitry. Frequency of ring is about 5 kHz.

audio engineers as a ready means of estimating, among other things, the frequency response performance of amplifiers including tone controls, filters etc. A uniform square-wave with a rise-time over 10% to 90% of the leading edge of about $1\mu\text{s}$ is essential. This can be checked by using the 'scope calibration as already outlined. Don't accept what appears to be a nice looking square-wave as in Fig. 11 (A) because the leading edge *looks* fast. Opened out, it appears as in Fig. 11 (B) and the rise-time is several micro-seconds, whereas (C) has a rise-time of better than $1\mu\text{s}$. We cannot delve too far into the interpretation of square-wave displays as this could warrant a whole article in itself but instead give some general examples, with the aid of oscillograms, of how amplifier performance can be estimated just by looking at the display. These are shown in Figs. 12, 13 and 14. Further information on the subject will be found in the references given at the end of this article.

Figure 15 shows at (A) a good clean sine-wave, but supposing this is passed through an amplifier and appears as either (B) or (C). Both indicate what is called *clipping* and (B) is asymmetrical i.e., positive peak only clipped, whilst

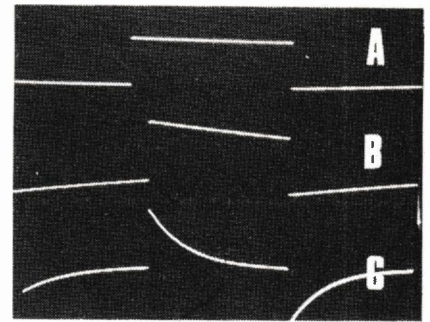


Fig. 12. Amplifier tests with square-wave (A) 1000 Hz square-wave input signal. (B) only slight slope at top indicates good response at low frequencies. (C) Curved and steep slope indicates severe loss of low frequency response.

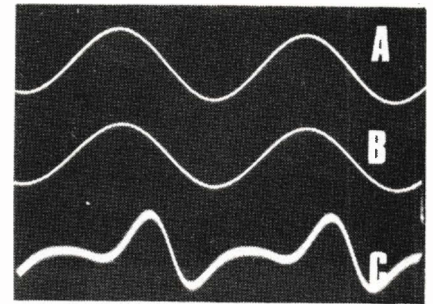


Fig. 15. Deceptive sine-waves (A) and (B) both look good but (A) has less than 0.02% distortion whereas (B) has more than 0.3% and its harmonic content is shown at (C) greatly amplified.

(C) shows symmetrical clipping with both positive and negative peaks clipped. This suggests either too much input signal and therefore overloading at the input stage, or malfunction of the amplifier due to wrong component values causing wrong operating voltages etc.

SOME GENERAL APPLICATIONS

The double beam (two trace oscilloscope) is invaluable for simultaneous display of two events, each time related to the other, and Fig. 16 (A) shows a square pulse (negative going) which has been used to gate a tone burst generator (B). The trace is fast enough to display one pulse so that close examination of time relationship can be made i.e., the tone burst starts its first cycle (positive going) precisely with the leading edge of the gate pulse.

The 'scope has many uses in analysing waveforms of unknown component and Fig. 17 shows a display of the spoken word *SEE*. The timebase was triggered by the beginning of the sound so the whole

Continued on page 21

Play with a loaded deck.



Packed with features from front to back, Pioneer's new CT-F9191 cassette deck stacks all the cards in your favor. A balanced combination of precision and convenience created by Pioneer to beat even the best reel-to-reel decks at their own game.

The CT-F9191 starts out by delivering top performance via access to the front. A newly designed tape carriage employs hexagonal reel shafts plus twin-link stays. The cassette is completely visible for checking tape movement and direction (a Pioneer exclusive). And since there's no rattle-prone ejection mechanism, changing tapes is a "snap."

In the CT-F9191, two motors provide the key to stable tape transport. An electronically controlled DC motor with built-in generator guarantees accurate record/play tape speed. A

second motor for high speed fast-forward and rewind. As a result, wow and flutter is no more than 0.07% and speed deviation is precise within $\pm 1.0\%$.

Next, a high-performance ferrite-solid head and a built-in Dolby* Type-B noise reduction system join to increase the S/N ratio to more than 62dB.

Operating the CT-F9191 is easy. Feather-touch user-oriented controls activate solenoid circuits thereby eliminating inconvenient mechanical linkages. After that, an advanced Memory Rewind device permits quick location and playback from any point on a prerecorded tape automatically. There is an automatic chrome-tape detector plus separate BIAS and EQ selection. And for making music tapes with wide dynamic range, an LED peak level indicator reacts instantly to warn of any distortion +5dB over the

reference level.

Next in the series, the CT-F7171, 6161 and 2121. Created for those who want to play, but with a deck that's loaded slightly less. Of course, the stakes are lower as well.

Pioneer's new front-loading cassette decks. A full house of outstanding features. No matter how you play them, you'll wind up with a winning hand in every suit.

Pioneer Electronics Australia Pty. Ltd.
178-184 Boundary Road, Braeside, Victoria
3195, Phone: 90-9011, Sydney 93-0246,
Brisbane 52-8213, Adelaide 433379,
Perth 76-7776

PIONEER
leads the world in sound.

Roll over, chromium!

New particle: TDK has developed a new particle called Super Avilyn. It's cobalt and ferric-oxide in a single layer. It is **not** the same as so-called 'cobalt-doped' and 'cobalt-energized' tapes.

New performance: The superior high-end saturation of Super Avilyn's high-coercivity formulation (allowing it to take more high frequency energy during recording), combined with its compatibility with the CrO₂ equalization (1EC 70 microsecond time constant) results in a simultaneous suppression of high-end noise (for better S/N) and delivery of a flat response curve with better highs.

SA's performance exceeds even CrO₂, which suffered from reduced output in the middle and low frequencies (SA provides 1.5-2db more output than the best CrO₂ in those ranges, equal output at high frequency).



SA also outperforms the ferric-oxide tapes (regular and cobalt-energized) which are unable to take full advantage of the noise reduction benefits of the CrO₂ equalization because their high-end saturation characteristics are not compatible with this standard.



Ask for TDK SA Cassettes.

Australian Distributor: Convoy International Pty. Ltd.
4 Dowling Street, Woolloomooloo 2011. 358 2088.

PF 648

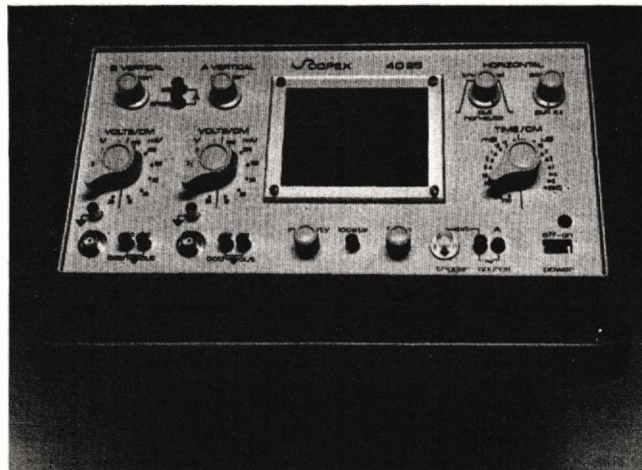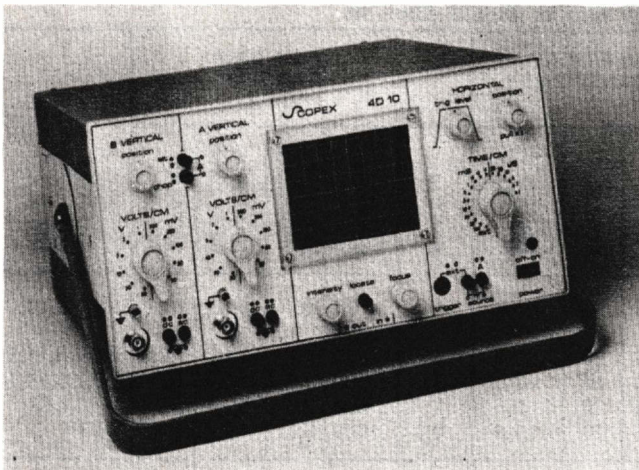

The Scopex 4D-25 features simple triggering, 25 MHz bandwidth and signal delay. The 4D-10 is virtually identical except that bandwidth is 10 MHz and delay is not provided.

waveform of the word is displayed. The S sound is clearly definable followed by the EE waveform. A faster time base would show even more detail of frequency components or formats as they are called.

The trackability of pickup cartridges has become an important performances factor in the world of hi-fi and special laboratory test records are used, with the aid of an oscilloscope, to obtain instant indication of performance. An example is shown in Fig. 18 in which (A) shows a typical test signal and how it should appear on the 'scope if the trackability is good. The lower trace

(B) shows poor trackability by the distortion in the pulse envelope and individual sine-waves.

It would be possible to go on almost *ad infinitum* giving examples of oscilloscope displays and their interpretation and of course literally hundreds of ways in which a 'scope can be used.

FREQUENCY SWEEP TECHNIQUES

The Oscilloscope at Work by A. Haas and R.W. Hallows. Iliffe and Sons. Last published 1959 but should be available from technical libraries. A very comprehensive work.

Servicing with the Oscilloscope by Gordon J. King. Newnes-Butterworth. New edition to be published. Excellent examples covering radio, audio and TV.

Radio and Electronics Laboratory Handbook by M.G. Scroggie. Iliffe Books. Latest edition published 1971. Informative on the use of the oscilloscope and other laboratory instruments.

The book mentioned above by Gordon J. King deals with television very thoroughly and thanks are due to him for the excellent frequency sweep oscillograms of FM tuner responses (26, 27 and 28).



Fig. 17. Spoken voice waveform of the word 'SEE'.


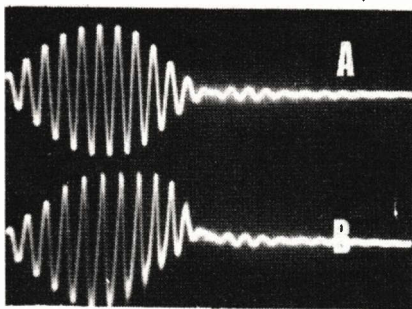


Fig. 18. Pickup cartridge trackability testing. (A) Good trackability. (B) Poor trackability. See text for explanation.

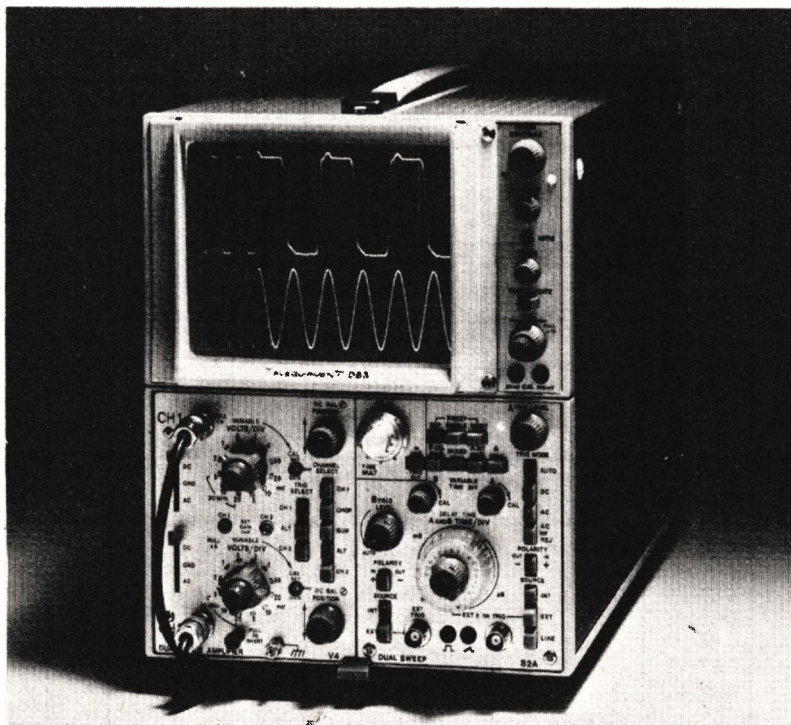

Although not included in the survey chart, plug-in instruments such as this are available for around \$1100 (including plug-ins). This instrument, the Telequipment D83, is shown fitted with a delayed-sweep time base and 50 MHz dual-trace plug-ins.

OSCILLOSCOPE SURVEY

MANUFACTURER	MODEL	DISTRIBUTOR	PRICE NOTE 5	No. OF BEAMS	SCREEN SIZE (cm) NOTE 1	GRATICULE	GRATICULE LIGHT	BANDWIDTH MHz	VERTICAL SENSITIVITY			TIME BASE RANGE NOTE 2					TRIGGER MODES NOTE 3
									HIGH mV	LOW V	RANGE SEQUENCE	FAST / μ s	SLOW ms	VARIABLE REDUCTION	RANGE SEQUENCE	EXPAND TIMES	
Advance	OS140	Jacoby Mitchell	344	1	8x10 (8)	●		10	5	20	1,2,5	1	100	10	1,10	1,2,5	1-5,7,8,13
	OS240		384	2	8x10 (8)	●		10	5	20	1,2,5	1	100	10	1,10	1,2,5	1-5,7,8,11,13
	OS250		500	2	8x10	●		10	5	20	1,2,5	1	500	2.5	1,2,5	10	1-5,7,8,11,13
	OS250TV		556	2	8x10	●		10	5	20	1,2,5	1	500	2.5	1,2,5	10	1-7,11,13
	OS1000A		816	2	8x10	●	●	20	5	20	1,2,5	0.5	1000	2.5	1,2,5	10	1-13
Kikusui	556B	Jacoby Mitchell	261	1	8x10	●		1.5	20	20	1,10	4 ranges 10 Hz—100 kHz					1,2,9
	537		205	1	7.5	●		5	10	20	1,10	4 ranges 10 Hz—100 kHz					1,2,3,4
	558		310	1	8x10	●		7	10	10	1,10	4 ranges 10 Hz—100 kHz					1-4
BWD Note 7	504	BWD	195	1	8x10	●		6	10	50	1,2,5	0.5	100	12	1,10		auto trigger
	506		385	1	8x10	●		15	5	20	1,2,5	0.2	2000	5	1,2,5	1.5	1-6,12,13
	509B		281	1	8x10	●		10	10	50	1,2,5	1	100	12	1,10	1.5	1-4,9,12,13
	511		479	1	8x10	●		10	10	50	1,2,5	0.2	2000	5	1,2,5	1.5	1-4,7,8,9,12-14
	530A		685	2	6x10	●		20	1	20	1,2,5	0.2	2000	5	1,2,5	1.5	1-5,7-14
	539C		399	2	8x10	●		20	10	50	1,2,5	0.5	500	5	1,2,5	1.5	1-9,11-13
Dumont Note 8	5111	Warburton O'Donnell	POA	1	8x10	●		10	10	5	1,2,5	0.5	200	●	1,2,5	5	1-5,7,10,12,13
Hewlett Packard	1220A	Hewlett Packard	870	2	8x10	●		15	2	10	1,2,5	0.1	500	10X	1,2,5		1-11,13
	1221A		746	1	8x10	●		15	2	10	1,2,5	0.1	500	10X	1,2,5		1-10,13
	1222A		1038	2	8x10	●		15	2	10	1,2,5	0.1	500	10X	1,2,5		1-11,13
Leader Note 8	LB0505	Warburton O'Donnell	POA	2	8x10	●	●	10	10	5	1,2,5	1	200		1,2,5	10	1-6,10-13
	LB0301		"	1	8x10 (6)	●		5	10	5	1,2,5	1	200		1,2,5	5	1-6,12
	LB0512		"	1	8x10	●		8	10		1,10	100 kHz to 10 Hz	●	1,10			1,2
	LB0510		"	1	8x10	●		4	20	2	1,10	100 kHz to 10 Hz	●	1,10			1-4,9
	LB0310A		"	1	8x10 (6)	●		4	20	2	1,10	100 kHz to 10 Hz	●	1,10			
National	VP5601A	Scientific Devices	610	1	4x6 (4.5)	●		5	10	30	1,3	0.3	100		1,3		1-4,12,13
	VP5601T		660	1		5	10	30	1,3	0.3	10	10X	1,3		1-6,12,13		
	VP5602A		739	2		30	1			1	100	10X	1,3		1-4,12,13		
	VP5107A		316	1	8x10	●		7	20	10	1,2,5	1	100	5X	1,3		1-4,12,13
	VP5107T		325	1	8x10	●		7	20	10	1,2,5	1	100	5X	1,3		1-6,12,13
	VP5105A		295	1	8x10	●		5	20	10	1,2,5	1	100	5X	1,3		1-4,12,13
Philips	PM3000	Philips	654	1	4x6 (4.5)	●		5	10	5	1,2,5	0.3	100		1,2,5		1-4,10,12,13
	PM3010		725	2	4x6 (4.5)	●		5	30	1	1,3,10	1	100		1,2,5	10	1-4,10,11,12,13
	PM3110		699	2	8x10	●		10	50	50	1,2,5	0.5	50	2.5X	1,2,5	5	1-6,9,11
	PM3200		516	1	8x10 (7.5)	●		15	2	50	1,2,5	0.1	500		1,2,5		1-4,7-10,13
	PM3232		1138	2	8x10	●	●	10	2	10	1,2,5	0.2	500	●	1,2,5	5	1-9,11-13
	PM3233		1164	2	8x10	●	●	10	2	10	1,2,5	0.2	500	●	1,2,5	5	1-9,11-13
	PM3225		581	1		●		15	2								
	PM3226		811	2		●		15	2								
	new releases — no other details available at time of printing																
Scopex	4D-10	Arlunya	349	2	6x8	●		10	10	50	1,2,5	1	100		1,2,5	5	1,2,9,12,13
	4D-25		669	2	6x8	●		25	10	50	1,2,5	0.2	200		1,2,5	5	1,2,9,12,13
Telequipment Note 7	D32	Tektronix	699	2	8x10 (7)	●		10	10	5	1,2,5	0.5	500	5X	1,2,5		1-7,10-13
	D61		349	2	8x10	●		10	10	5	1,2,5	0.5	500	5X	1,2,5		1-7,10-13
	D65		688	2	8x10	●	●	15	10	50	1,2,5	0.1	2000	2.5	1,2,5	5	1-8,11,13,14
	D66		749	2	8x10	●	●	25	10	50	1,2,5	0.1	2000	2.5	1,2,5	5	1-8,11,13,14
	D67		899	2	8x10	●	●	25	10	50	1,2,5	0.2	2000	2.5	1,2,5	5	1-8,10-14
	DM64		949	2	8x10	●	●	10	10	50	1,2,5	0.1	2000	2.5	1,2,5	5	1-8,11-14
Trio	CO1303A	Parameters	167	1	6x6	●		1.5	20	2	1,10	100 kHz—10 Hz			1,10		1
	CS1351		431	1	8x10 (7.5)	●		10	10	20	1,2,5	0.5	500	●	1,2,5	5	1-6,13
	CS1557		295	1	8x10	●		10	10	20	1,2,5	0.5	500	●	1,2,5	5	1-6,13
	CS1560		399	2	8x10	●		15	10	20	1,2,5	0.5	500	●	1,2,5	5	1-6,11-13

DUAL BEAM MODES NOTE 4	MODES DISPLAY NOTE 6	INPUT SOCKET	Z MOD	DELAY	CALIBRATOR	DIMENSIONS (mm)	REMARKS	NOTES
3	1	BNC	●		●	132x270x317		<p>1. SCREEN SIZE If graticule dimensions are not in cms figure in brackets indicates size in mm.</p> <p>2. TIMEBASE RANGE Quoted speeds are calibrated per division. Timebase variable reduction ratio is quoted in VARIABLE REDUCTION column. Where figure is followed by 'X' it is an expansion ratio. Fixed accurate switched expansion ratios are indicated in EXPAND column.</p> <p>3. TRIGGER MODES 1. Internal or Y1 2. External 3. + 4. - 5. TV frame 6. TV Horizontal 7. AC 8. AC fast (HP filter) 9. Line 10. Free run 11. Y2 12. Auto 13. Level control 14. Single sweep</p> <p>4. DUAL BEAM MODES 1. Chopped 2. Alternate 3. Auto select (1 & 2) 4. True dual beam CRT</p> <p>5. PRICES Prices are quoted at time of printing and may vary without notice. They are inclusive of duty but exclude 15% sales tax. Accessories such as probes etc are usually optional extras.</p> <p>6. DISPLAY MODES 1. Y1 2. Y2 3. Y1 + Y2 4. Y1 - Y2 5. XY (Y2 = X) 6. differential input</p> <p>7. EXCLUSIONS Some companies have main frame/plug scopes which fall within ≈\$1000 range. Due to specification complexity these have not been included in survey. Details available from company concerned. Products surveyed are typical of those available in Australia. Not all companies are necessarily included.</p> <p>8. PRICE ON APPLICATION Prices well under \$1000 but not released at time of survey.</p>
3	1,2,5	BNC	●		●	132x270x317	internal sync separator for TV	
3	1,2,5	BNC	●		●	180x290x420		
3	1,2,5	BNC	●		●	180x290x420		
3	1-5	BNC	●	50 ns fixed	●	180x290x420		
	1	Banana			●	167x275x440		
	1	N			●	200x155x155		
	1	N			●	175x260x460		
1,2	1	Banana	●		●	182x198x405	rechargeable battery version available at \$1040 optional battery supply available	
1,2	1	BNC	●		●	235x190x419		
1,2	1,6	Banana	●		●	240x190x420		
1,2	1,4	BNC	●	20 ns	●	230x180x410		
1,2	1,2	BNC	●		●	165x320x430		
	1	BNC			●	228x164x420		
3	1,2,5	BNC				181x312x412	fitted with beam finder	
3	1	BNC		●		181x312x412		
3	1-5	BNC				181x310x412		
1,2	1-5	BNC	●		●	185x250x380		
1,2	1	N			●	120x200x300		
1,2	1	N			●	270x175x422		
1,2	1	BNC			●	250x180x415		
1,2	1	Banana				180x125x300		
3	1	BNC				125x 80x196	built in battery supply optional ac adaptor/charger available	
3	1	BNC				220x150x390		
3	1,2	BNC				220x150x390		
3	1	BNC			●	220x150x390		
3	1	BNC				220x150x390		
3	1					80x125x196	supplied with ac adaptor charger. Rechargeable battery optional extra - X10 vertical sensitivity switch ac only can be operated with external 24 Vdc supply	
3	1,2					80x125x196		
3	1,2	BNC				195x305x455		
4	1	BNC			●	175x210x330		
4	1,2,5	BNC	●	150 ns	●	185x326x503		
4	1,2,5	BNC	●		●	185x326x503		
1,2	1,2	BNC				153x312x350	fitted with beam finder	
1,2	1,2	BNC				153x312x435		
3	1,2				●	105x130x288	built in rechargeable batteries and charger	
3	1,2,5	BNC	●	200 ns	●	160x280x420		
1,2	1-5	BNC	●	200 ns	●	240x210x370		
1,2	1-5	BNC	●	200 ns	●	240x210x370		
1,2	1-4	BNC	●		●	240x210x440		
1,2	1-5	BNC	●		●	240x210x370		
1,2	1-5	BNC	●			240x210x370		
	1	Banana				180x130x350		
	1	N			●	200x135x300		
	1	N			●	225x195x400		
3	1-5	BNC			●	250x200x370		
3	1-5	BNC				250x200x370		

ELECTRONIC HOBBY KITS

To-day's Technology for Your Enjoyment

SPECIAL OFFER!


ETI 534 STOPWATCH/CALCULATOR - A MUST FOR ALL SPORTSMEN

By special arrangement with N.S. Electronics we are pleased to offer this NOVUS 650 calculator together with the complete set of components to build the ETI 534 Stopwatch/Calculator. The kit includes a specially designed fibreglass printed circuit board with a silk screened component overlay. With our unique STEP-BY-STEP ASSEMBLY MANUAL and TECHNICAL SUPPORT virtually anyone can build this exciting and useful project. We thoroughly recommend it for beginner or professional.

\$16.75 Nett, delivered free anywhere in Australia **\$19.75** nett, assembled and tested.



ETI 440 SIMPLE 25 WATT AMPLIFIER

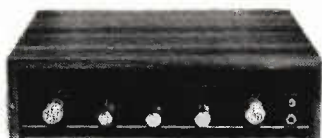

Designed by the ETI Team the International 440 is a remarkable combination of high performance, easy construction and low cost.

We offer our own exclusive step-by-step assembly manual, the choice of buying individual packs or the full kit and a really good looking Walnut Veneered Cabinet that guarantees you a professional finished product anyone would be proud to own. For pack prices, see December ETI.

With our full Technical support and Warranty Service (see below) you just can't fail to build this kit!

\$85.00 nett Delivered Free Anywhere in Australia. Assembled and Tested **\$115** nett

MR 25 SCORPIO CD1

Based on one of the most popular CDI projects in the world, this proven design has been updated and re-engineered to ensure that the kit can be readily assembled by anyone from a novice to an expert design engineer. The kit comes complete in every detail including all components and hardware; screened, etched and drilled PC Board, machined and finished metal work, pre-wound and tested transformer and a unique, easy to follow assembly manual that converts the assembly task to sheer pleasure.

If you have any problems before, during or after assembly - just call on our exclusive Technical support and Warranty Service.

\$28.50 nett

(Assembled and tested \$36.00 nett)



ETI 704 CROSS HATCH/DOT GENERATOR

\$27.50



This incredibly popular project now given the HOBBY KIT treatment.

- Pre drilled/screened front panel.
- Fibreglass PC Board with screened Component Overlay.
- Pre-wound coils.
- Sockets for all IC's.

Complete to last detail including solder and hook up wire. Full warranty support applies. (Doesn't include battery.)

FULL TECHNICAL SUPPORT AND WARRANTY SERVICE

All Applied Technology HOBBY KITS are covered by our exclusive 90 days warranty against faulty components and packaging (full details with each kit).

Yet another exclusive is the full technical support service. If you are unable to make your HOBBY KIT operational, help is just a phone call or a letter away. If you do have to return any KIT for factory attention, it will be repaired for a nominal service fee.

All kits are on display at our Factory Showroom. Personal callers welcome - weekdays by appointment, or anytime Saturday Mornings. Phone 476 4758.



109-111 Hunter Street,
HORNSBY, N.S.W. 2077
Phone (02) 476-4758
Open Saturday morning

Please supply

Delivered FREE anywhere in Australia

Enclosed is my Cheque/Postal Note/Money Order for \$
made out to APPLIED TECHNOLOGY PTY. LTD.
(PLEASE PRINT CLEARLY)

NAME

ADDRESS

..... P/C

ETI 176

- FAST SERVICE – ALL ITEMS DESPATCHED AT TOP SPEED
- ALL NEW ITEMS – UNUSED AND CARRY MANUFACTURER'S GUARANTEE
- SATISFACTION OR MONEY BACK (IF GOODS RETURNED WITHIN 7 DAYS)
- PRICES INCLUDE SALES TAX, CUSTOMS DUTY, POSTAGE & PACKING
- 10% DISCOUNT ON ORDERS OVER \$25.00
- DATA SHEETS AVAILABLE – 20c EXTRA
- FIRST QUALITY BRANDED COMPONENTS FROM THE WORLD'S LEADING SEMICONDUCTOR HOUSES

SPECIALS OF THE MONTH

LM3909 LED FLASHER	\$1.20
CA3130T FET OP AMP	\$1.65
NE555 TIMER	.75
LM339 QUAD COMPARATOR	\$3.00
TCA220 TRIPLE OP AMPLIFIER	\$2.20
SCL5411T OSCILLATOR – 16 STAGE DIVIDER WITH BUFFER	\$3.00

VOLUME BUYS

5023 LEADS	10 for \$2.00
1N914 DIODES	20 for \$1.50
IN4004 DIODES	10 for \$1.00
741 OP AMP	5 for \$3.00
555 TIMERS	5 for \$3.00
IC SOCKETS 8, 14 or 16 PIN	5 for \$2.00

AT LAST !!

The Electronic Mailbox Short Form Semiconductor Catalogue.

A comprehensive listing of our rapidly increasing stock lines including Transistors and diodes
Linear IC's
CMOS TTL
FREE with all orders. Otherwise send 35c to cover Post and Packing.

PROJECT PACKS

The most economical way to build magazine projects. We supply all IC's, transistors, diodes, LED's as well as top quality printed circuit boards and sockets for the IC's. (You add your own resistors, capacitors etc.)

ETI 553 READOUT	\$21.00
ETI 117 OVM MODULE	\$8.50
ETI 118 FREQUENCY METER	\$11.25
ETI 438 VU METER	\$13.75
EA 50 Hz QUARTZ CLOCK DRIVER	\$6.50
ETI 123 CMOS TESTER	\$6.50

CMOS 4000 SERIES

PRODUCT CODE	PRICE \$ c	PRODUCT CODE	PRICE \$ c
4000	.35	4025	.45
4001	.35	4027	1.25
4002	.35	4028	2.50
4006	2.75	4029	2.75
4007	.40	4030	1.00
4009	1.00	4035	2.90
4010	1.00	4040	3.00
4011	.35	4044	2.45
4012	.35	4046	4.80
4013	1.25	4049	1.00
4014	2.75	4050	1.00
4015	2.50	4060	3.00
4016	1.00	4071	.45
4017	2.65	4081	.45
4018	2.80	4416	1.00
4019	1.00	4426	3.50
4020	2.95	4449	.45
4021	2.60	4511	2.65
4022	2.25	4518	2.60
4023	.45	4520	2.60
4024	2.75	14553	7.60

CMOS 74c SERIES


PRODUCT CODE	PRICE \$ c	PRODUCT CODE	PRICE \$ c
74C00	.35	74C76	.85
74C02	.35	74C90	2.35
74C04	.35	74C192	2.90
74C10	.35	74C193	2.90
74C14	1.60	74C221	2.35
74C48	3.30	74C89	14.00
74C73	.85		

FOR OTHER CURRENT STOCK LISTINGS REFER TO ELECTRONICS TODAY NOVEMBER ISSUE, PAGE 47.

Send Cheque/Postal Order to

THE
**ELECTRONIC
MAILBOX ***

P. O. BOX 355,
HORNSBY N.S.W. 2077

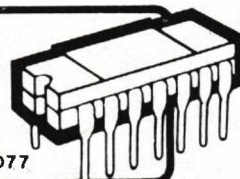

*MAIL ORDER DIVISION OF APPLIED TECHNOLOGY P/L. PHONE 476 3759

Hot talent and hot material need Hot Sound Tape by Ampex

An ordinary tape just won't do these days for most audio recording jobs. You need the hot Ampex 406/407 studio mastering tape, or the hottest, Ampex GRAND MASTER. With 406/407 you'll get 72 dB s/n ratio, high output, low noise and low distortion. If your requirements call for an even hotter tape, then you need Ampex GRAND MASTER. This spectacular mastering tape offers a full 76


dB s/n ratio and as much as 3 dB extra sensitivity on the high end. You can drive GRAND MASTER tape harder than you've ever driven a tape before. From a whisper to a scream, it responds with more undistorted output across the entire audible range than any other mastering tape available. It has high erasability so it is fully reuseable. And there's no need for bias adjustments:

use GRAND MASTER at the same settings you've established for Ampex 406/407 or for 206/207.


Detailed technical specifications and performance curves are available in our free brochure, offered to all audio professionals. Just ask us for literature on the Ampex Hot Sound Tapes, GRAND MASTER and 406/407.

AMPEX

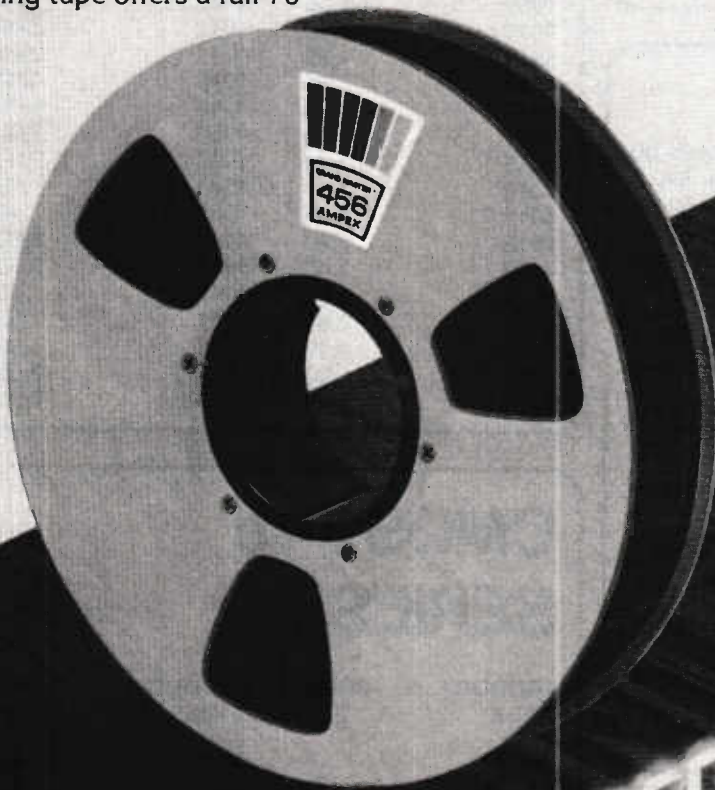Ampex Australia Pty. Ltd.
4 Carlotta St., Artarmon, N.S.W. 2064
TLX 20608, Phone 439-4077
and
292 Victoria Street
North Melbourne, Victoria, 3051
Phone Melbourne 329-5229



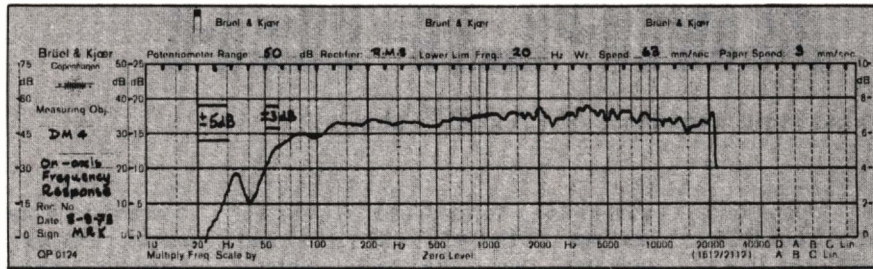Lots of people tell you what their speakers will do.




When you buy a B&W, you get it in writing.

B&W's reputation is based on producing clean natural sound without distortion, even at low volume. Each B&W speaker is tested in an Anechoic Chamber and issued with its own individual pen graph. You know exactly the performance of the speaker you are buying.




**B&W DM70 Monitor
Electrostatic.**

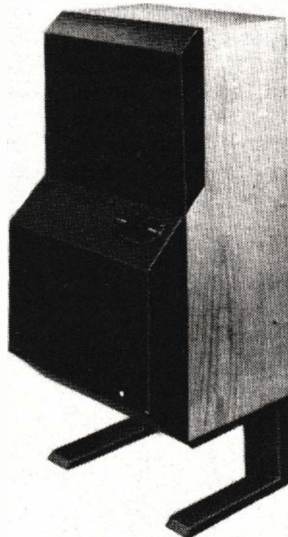A combination of dynamic bass unit and electrostatic mid and high frequency module. One of the best speakers you can buy.



B&W DM6 Monitor.

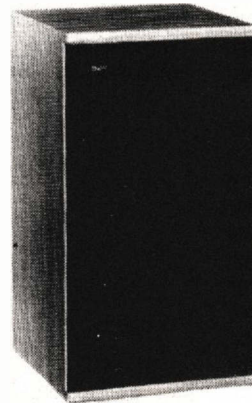A brand new design. A high powered dynamic loudspeaker with low colouration and very high transient performance.




B&W DM2A Monitor.

A more conventional design, utilising B&W research into acoustic line rear loading. Brilliant clarity and lack of distortion.



B&W DM4 Monitor.

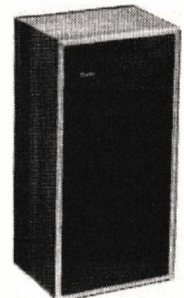A speaker with large B&W Monitor characteristics; its performance surpasses speakers of much greater size.



B&W D5.

A speaker for small living areas. It has above average performance at moderate cost.

B&W



Sole Australian Agents
Convoy International Pty. Ltd.
4 Dowling Street, Woolloomooloo 2011
Sydney. 358 2088

PF693

THE CA3130 OPERATIONAL AMPLIFIER

Versatile new device has input impedance of 1.5×10^{12} ohms.

A NEW COSMOS operational amplifier is now available from RCA. It has several unusual features. It is a device which combines the advantages of both CMOS and bipolar transistors on a single monolithic chip.

The device, the RCA type CA3130, uses gate protected, p-channel MOS/FET (PMOS) transistors in the input circuit to obtain very high input impedance, very low input current, and exceptional speed performance.

The use of PMOS field-effect transistors in the input stage results in common-mode input-voltage capability down to 0.5 volt below the negative-supply terminal, an important attribute in single-supply applications.

The output circuit consists of a complementary-symmetry MOS (COS/MOS) transistor pair, capable of swinging the output voltage to within millivolts of either supply voltage terminal (at very high values of load impedance).

The CA3130 Series circuits operate at supply voltages ranging from 5 to 16 volts, or ± 2.5 to ± 8 volts when using split supplies. They can be phase compensated with a single external capacitor, and have terminals for adjustment of offset voltage for applications requiring offset-null capability. Terminal provisions are also made to permit strobing of the output stage.

The CA3130 Series is supplied in either the standard 8-lead TO-5-style package (T suffix) or in the 8-lead

dual-in-line formed-lead TO-5-style package "DIL-CAN" (S suffix) and operates over the full military-temperature range of -55°C to $+125^{\circ}\text{C}$. The CA3130B is intended for applications requiring premium-grade specifications and with limits established for: input current, temperature coefficient of input-offset voltage, and gain over the range of -55°C to $+125^{\circ}\text{C}$. The CA 3130A offers superior input characteristics over those of the CA3130.

CIRCUIT DESCRIPTION

Fig. 3 is a block diagram of the CA3130 Series COS/MOS Operational Amplifiers. The input terminals may be operated down to 0.5 V below the negative supply rail, and the output can be swung very close to either supply rail in many applications. Consequently, the CA3130 Series circuits are ideal for single supply

operation. Three Class A amplifier stages, having the individual gain capability and current consumption shown in Fig. 3, provide the total gain of the CA3130. A biasing circuit provides two potentials for common use in the first and second stages. Term. 8 can be used both for phase compensation and to strobe the output stage into quiescence. When Term. 8 is tied to the negative supply rail (Term. 4) by mechanical or electrical means, the output potential at Term. 6 essentially rises to the positive supply rail potential at Term. 7. This condition of essentially zero current drain in the output stage under the strobed "OFF" condition can only be achieved when the ohmic load resistance presented to the amplifier is very high (e.g. when the amplifier output is used to drive COS/MOS digital circuits in comparator applications).

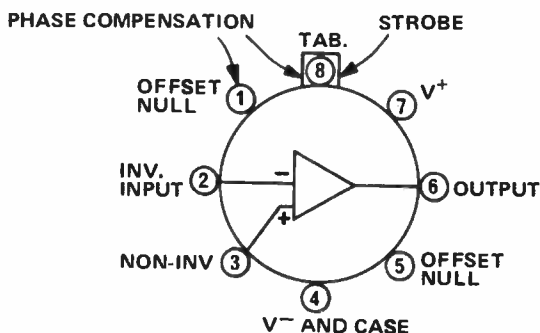


Fig. 1. Functional diagram of the CA3130.

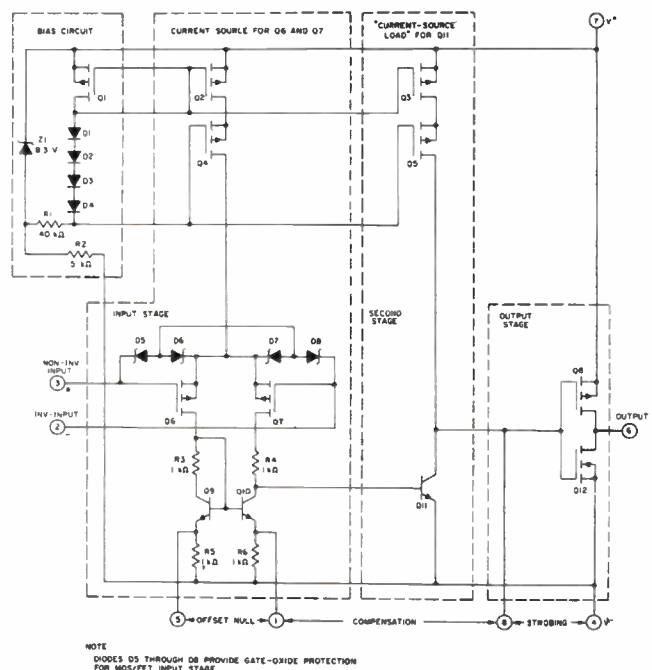


Fig. 2. Schematic diagram of the CA3130.

TABLE 1

MAXIMUM RATINGS, Absolute-Maximum Values

DC Supply Voltage (between V⁺ and V⁻ terminals) . . . 16 V
 Differential-mode input voltage . . . ±8 V
 Common-mode DC input voltage . . . V⁺ to (V⁻ - 0.5 V)
 Input-terminal current 1 mA
 Device Dissipation: without heat sink - up to 55°C 630 mW above 55°C . . . Derate linearly 6.67 mW/°C
 With heat sink - at 125°C 418 mW below 125°C, inc. lin. at 16.7 mW/°C
 Temperature range operating -55 to +125°C
 Output short-circuit duration Infinite

* Short circuit may be applied to ground or to either supply.

CHARACTERISTIC	SYMBOL	TEST CONDITIONS			UNITS	
		CA3130	Min.	Typ.		Max.
Input Offset Voltage	V _{IO}	V ⁺ =±7.5 V V ⁻ =0 V T _A =25°C (Unless Specified Otherwise)	-	8	15	mV
Input Offset Current	I _{IO}	V ⁺ =±7.5 V V ⁻ =0 V T _A =25°C	-	0.5	30	pA
Input Current	I _I	V ⁺ =±7.5 V V ⁻ =0 V T _A =25°C	-	5	50	pA
Large-Signal Voltage Gain	AOL	V _O =10 V _{p-p} R _L =2 kΩ	50 k	320 k	-	V/V
		R _L =∞	94	110	-	dB
Common-Mode Rejection Ratio	CMRR		70	90	-	dB
Common-Mode Input-Voltage Range	V _{ICR}		0	-0.5 to 12	10	V
Power-Supply Rejection Ratio	ΔV _{IO} /ΔV ⁺ ΔV _{IO} /ΔV ⁻	V [±] =±7.5 V	-	32	320	μV/V
			-	32	320	
Maximum Output Voltage	V _{OM} ⁺ V _{OM} ⁻	V _{OM} ⁺ R _L =2 kΩ	12	13.3	-	V
		V _{OM} ⁻ R _L =∞	-	0.002	0.01	
Maximum Output Current: Source	I _{OM} ⁺ I _{OM} ⁻	V _O =0 V	12	22	45	mA
		V _O =15 V	12	20	45	
Supply Current	I ⁺	V _O =7.5 V R _L =∞	-	10	15	mA
		V _O =0 V R _L =∞	-	2	3	
Input Current	I _I		-	Fig. 11	-	nA
Input Offset Voltage Temperature Drift	ΔV _{IO} /ΔT	T _A =-55 to 125°C V [±] =±7.5 V V _O =10 V _{p-p} R _L =2 kΩ	-	10	-	μV/°C
Large-Signal Voltage Gain	AOL		-	320 k	-	V/V
			-	110	-	dB

* Applies only to AOL.
 ▲ Applies only to I_I and ΔV_{IO}/ΔT.

HANDLING

The CA3130 uses MOS field-effect transistors in the input circuit. Because MOS/FET's have extremely high input resistances, they are susceptible to damage when exposed to extremely high static electrical charges. To minimize the possibilities of damaging the input stage transistors, Q6 and Q7, the CA3130 utilizes a protective diode network in the input stage.

TABLE 2

CHARACTERISTIC	SYMBOL	TEST CONDITIONS		
		CA3130	UNITS	
Input Offset Voltage Adjustment Range		10 kΩ across Terms, 4 and 5 or 4 and 1	±22	mV
Input Resistance	R _I		1.5	TΩ
Input Capacitance	C _I	f = 1 MHz	4.3	pF
Equivalent Input Noise	e _n	BW=0.2 MHz R _S =1 MΩ	23	μV
Unity Gain Crossover Frequency	f _T	C _C =0	15	MHz
		C _C =47 pF	4	
Slew Rate: Open Loop	SR	C _C =0	30	V/μs
		C _C =56 pF	10	
Transient Response: Rise Time	t _r	C _C =56 pF C _L =25 pF	0.09	μs
		R _L =2 kΩ	10	%
		(Voltage follower)	1.2	μs

* Although a 1-MΩ source is used for this test, the equivalent input noise remains constant for sources of R_S up to 10 MΩ.

CHARACTERISTIC	SYMBOL	TEST CONDITIONS		
		CA3130	UNITS	
Input Offset Voltage	V _{IO}	V ⁺ =5 V V ⁻ =0 V T _A =25°C	8	mV
Input Offset Current	I _{IO}		0.1	pA
Input Current	I _I		2	pA
Common-Mode Rejection Ratio	CMRR		80	dB
Large Signal Voltage Gain	AOL	V _O =4 V _{p-p} R _L =5 kΩ	100 k	V/V
			100	dB
Common-Mode Input Voltage Range	V _{ICR}		0 to 2.8	V
Supply Current	I ⁺	V _O =5 V, R _L =∞ V _O =2.5 V, R _L =∞	300	μA
Power Supply Rejection Ratio	ΔV _{IO} /ΔV ⁺		200	μV/V

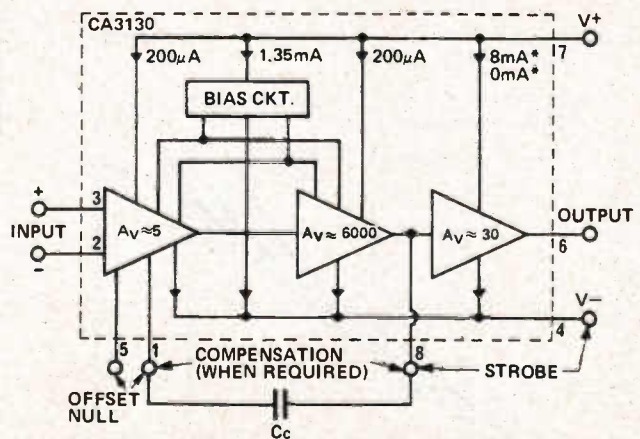


Fig. 3. Block diagram of the CA3130 illustrates how the device is organized.

THE CA3130 OPERATIONAL AMPLIFIER

Nevertheless, it is good practice that the following precautions be observed during handling, testing and actual operation of the CA3130 devices to minimize exposure to damage-inducing hazards:

1. Soldering-iron tips, metal parts of fixtures, tools, and handling facilities should be grounded.
2. Devices should not be inserted into or removed from circuits with the power ON because transient voltages may cause damage.
3. Signals should not be applied to the input (Terms. 2 and 3) when the device power supply is OFF. Input-terminal currents should not exceed 1 mA.
4. After CA3130 devices have been mounted on circuit boards, proper handling precautions should still be observed if the input terminals are unterminated. It is good practice during board-processing operations

to return Terms. 2 and 3 to Term. 4 by jumping the appropriate conductors.

OFFSET NULLING

Offset-voltage nulling is usually accomplished with a 100,000-ohm potentiometer connected across Terms. 1 and 5 and with the potentiometer slider arm connected to Term. 4. A fine offset-null adjustment usually can be effected with the slider arm positioned in the mid-point of the potentiometer's total range.

INPUT-CURRENT VARIATION WITH TEMPERATURE

The input current of the CA3130 Series circuits is typically 5pA at 25°C. The major portion of this input current is due to leakage current through the gate-protective diodes in the input circuit. As with any

semiconductor-junction device, including op amps with a junction-FET input stage, the leakage current approximately doubles for every 10°C increase in temperature. Fig. 7 provides data on the typical variation of input bias current as a function of temperature in the CA3130.

In applications requiring the lowest practical input current and incremental increases in current because of "warm-up" effects, it is suggested that an appropriate heat sink be used with the CA3130. In addition, when "sinking" or "sourcing" significant output current the chip temperature increases, causing an increase in the input current. In such cases, heat-sinking can also very markedly reduce and stabilize input current variations.

INPUT-OFFSET-VOLTAGE (V_{IO})

It is well known that the

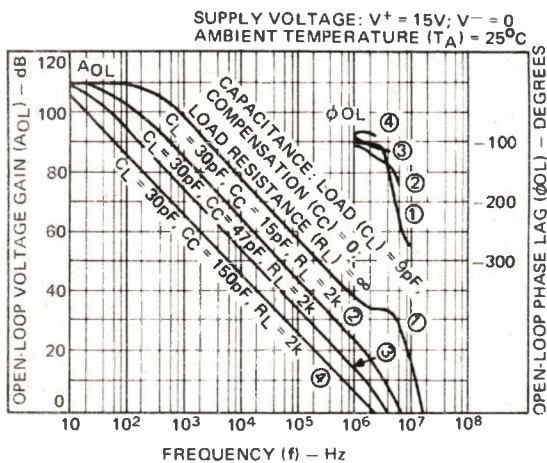


Fig. 4. Open loop voltage gain and phase shift versus frequency for various values of C_L , C_C and R_L .

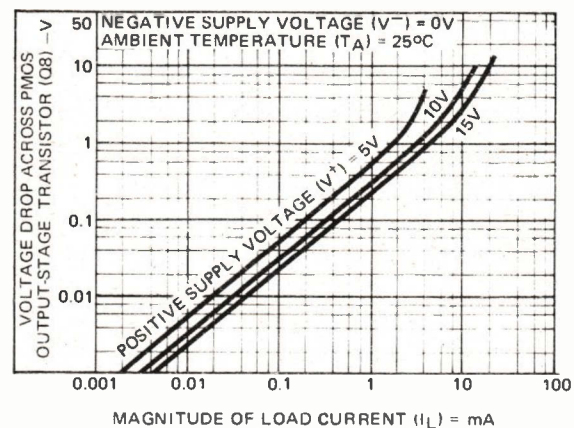


Fig. 5. Voltage across the PMOS output transistor, Q_8 , versus load current.

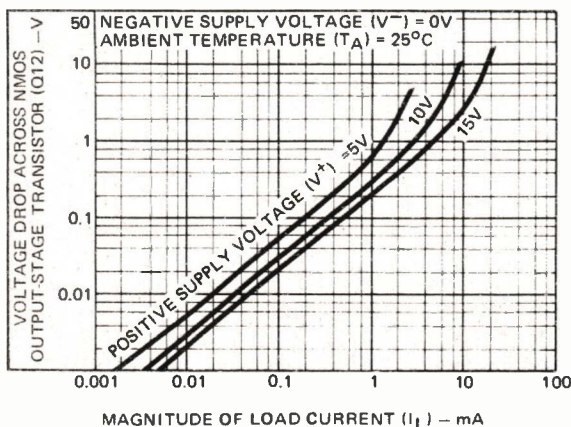


Fig. 6. Voltage across NMOS output transistor, Q_{12} , versus load current.

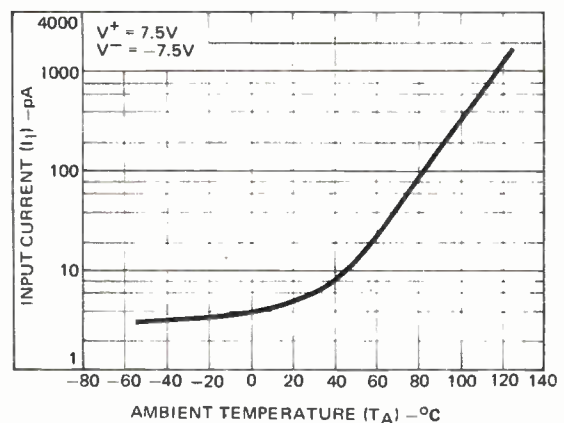


Fig. 7. Input current variation with ambient temperature change.

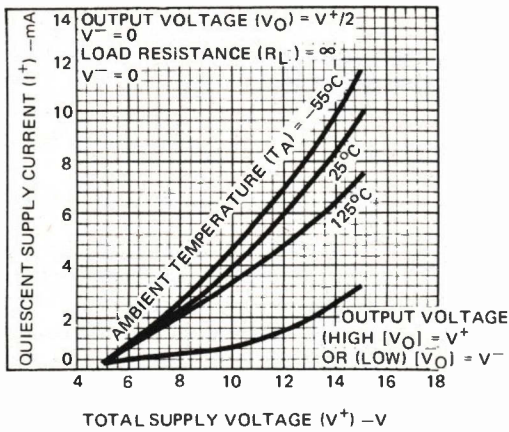


Fig. 8. Quiescent supply current versus supply voltage at several temperatures.

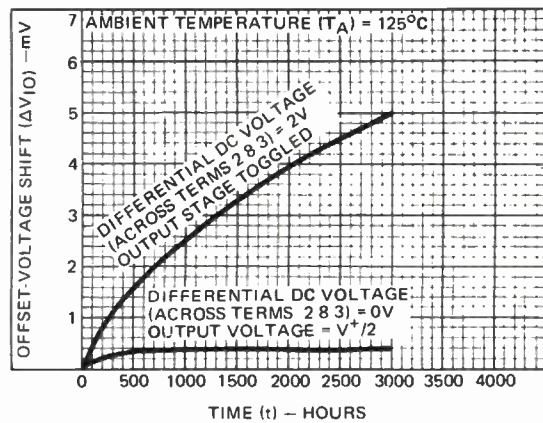


Fig. 9. Typical incremental shift in offset voltage versus operating life.

characteristics of a MOS/FET device can change slightly when a dc gate-source bias potential is applied to the device for extended time periods. The magnitude of the change is increased at high temperatures. Users of the CA3130 should be alert to the possible impacts of this effect if the application of the device involves extended operation at high temperatures with a significant differential dc bias voltage applied across Terms 2 and 3. Fig. 9 shows typical data pertinent to shifts in offset voltage encountered with CA3130 devices during life testing. The two-volt dc differential voltage example represents conditions when the amplifier output stage is "toggled", e.g., as in comparator applications.

WIDEBAND NOISE

For low-noise performance the CA3130 is most advantageous in applications wherein the source resistance of the input signal is 1 megohm or more. In this case, the total input-referred noise voltage is typically only 23 μV when a test-circuit amplifier is operated at a total supply voltage of 15 volts. This value of total input-referred noise remains essentially constant, even though the value of source resistance is raised by an order of magnitude. This characteristic is due to the fact that reactance of the input capacitance becomes a significant factor in shunting the source resistance. It should be noted, however, that for values of source resistance very much greater than 1 megohm, the total noise voltage generated can be dominated by the thermal noise contributions of both the feedback and source resistors.

VOLTAGE FOLLOWERS

Operational amplifiers with very

high input resistances, like the CA3130, are particularly suited to service as voltage followers. Fig. 10a shows the circuit of a classical voltage follower, using the CA3130 in a split-supply configuration.

A voltage follower, operated from a single supply, is shown in Fig. 10b. This follower circuit is linear over a wide dynamic range.

The follower does not lose its input-to-output phase-sense, even though the input is swung 7.5 volts below ground potential. This unique characteristic is an important attribute in both operational amplifier and comparator applications. The COS/MOS output stage also permits the output signal to swing down to the negative supply-rail potential (i.e. ground in the case shown). The digital-to-analog converter (DAC) circuit, described in the following section, illustrates the practical use of the CA3130 in a single-supply voltage-follower application.

9-BIT COS/MOS DAC

The circuit of a 9-bit Digital to

Analog Converter (DAC) is shown in Fig. 11. This system combines the concepts of multiple-switch COS/MOS IC's, a low-cost ladder network of discrete metal-oxide film resistors, a CA3130 op-amp connected as a follower, and an inexpensive monolithic regulator in a simple single power-supply arrangement. An additional feature of the DAC is that it is readily interfaced with COS/MOS input logic, e.g. 10-volt logic levels are used in the circuit of Fig. 11.

The circuit uses an R/2R voltage-ladder network, with the output potential obtained directly by terminating the ladder arms at either the positive or the negative power-supply terminal. Each CD4007A contains three "inverters", each "inverter" functioning as a single-pole double-throw switch to terminate an arm of the R/2R network at either the positive or negative power-supply terminal. The resistor ladder is an assembly of one per cent tolerance metal-oxide film resistors. The five arms requiring the highest accuracy are assembled with series and parallel combinations of 806,000-ohm

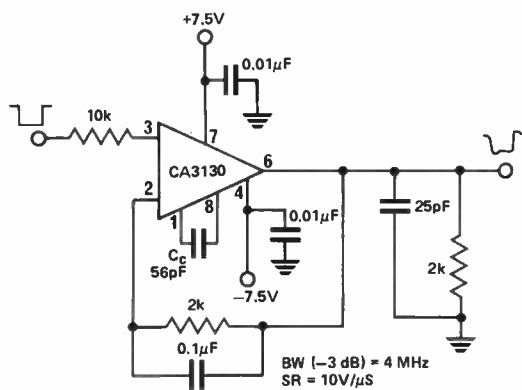


Fig. 10. Voltage follower circuit with split supply of plus and minus 7.5 volts. This circuit allows low impedance loads to be driven from a high impedance source.

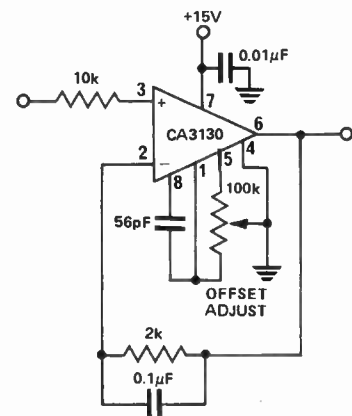


Fig. 10b. Voltage follower operating on single supply rail.

THE CA3130 OPERATIONAL AMPLIFIER

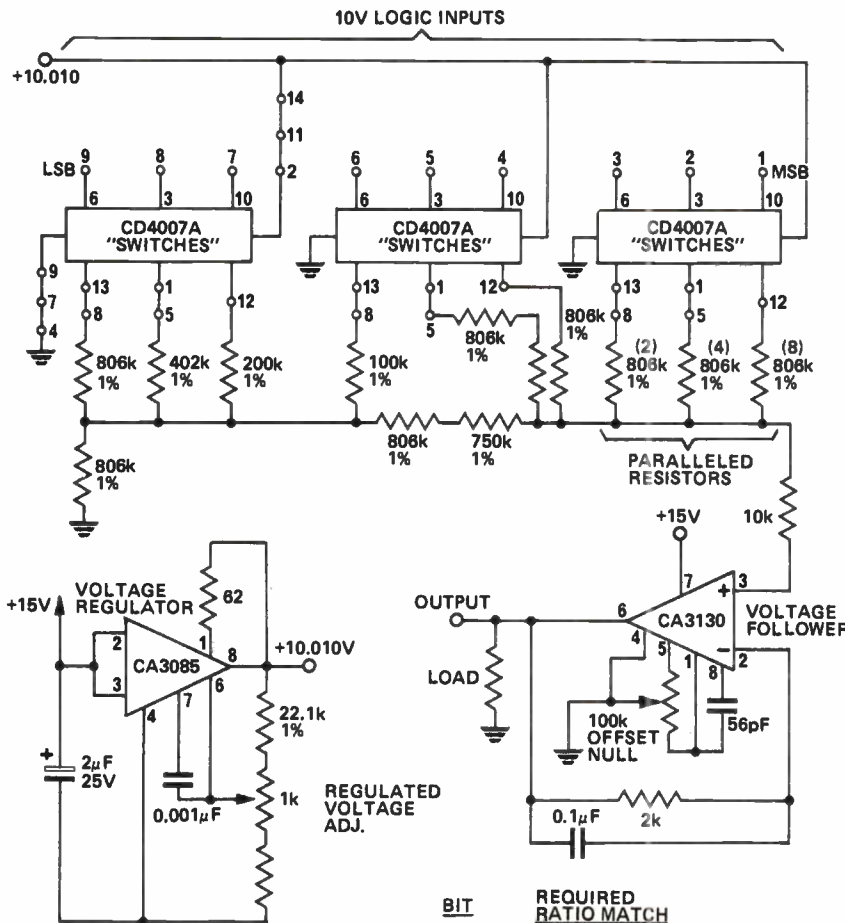


Fig. 11. Nine-bit digital-to-analogue converter uses CMOS digital switches and the CA3130.

BIT	REQUIRED RATIO MATCH
1	STANDARD
2	±0.1%
3	±0.2%
4	±0.4%
5	±0.8%
6-9	±1% ABS

ALL RESISTORS IN OHMS.

resistors from the same manufacturing lot.

A single 15-volt supply provides a positive bus for the CA3130 follower amplifier and feeds the CA3085 voltage regulator. A "scale-adjust" function is provided by the regulator output control, set to a nominal 10-volt level in this system. The line-voltage regulation (approximately 0.2%) permits a 9-bit accuracy to be maintained with variations of several volts in the supply. The flexibility afforded by the COS/MOS building blocks simplifies the design of DAC systems tailored to particular needs.

SINGLE-SUPPLY, ABSOLUTE-VALUE, IDEAL FULL-WAVE RECTIFIER

An absolute-value circuit, using the CA3130 is shown in Fig. 12. During positive excursions, the input signal is fed through the feedback network directly to the output. Simultaneously, the positive excursion of the input signal also drives the output terminal (No.6) of the inverting amplifier negative such that the 1N914 diode effectively disconnects the amplifier from the signal path. During a negative-going excursion of the input signal, the CA3130 functions as a normal inverting amplifier with a gain equal to $-R2/R1$. When the equality of the two equations shown in Fig. 12 is satisfied, the full-wave output is symmetrical.



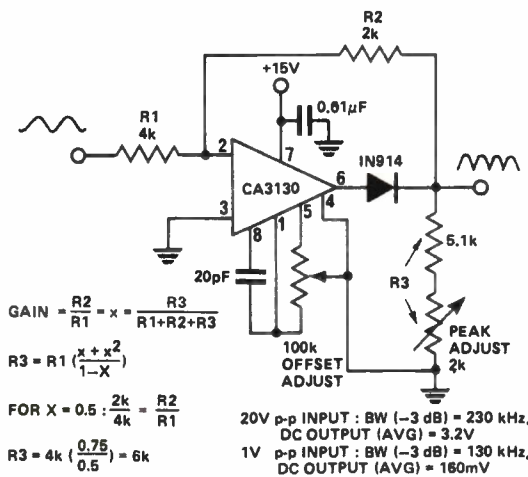


Fig. 12. An absolute value full-wave detector provides the average of the input waveform. This is useful for converting dc meters, eg digital voltmeters to read the average of the ac input signal.

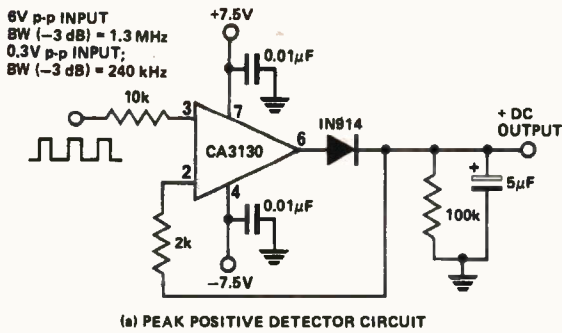

(a) PEAK POSITIVE DETECTOR CIRCUIT

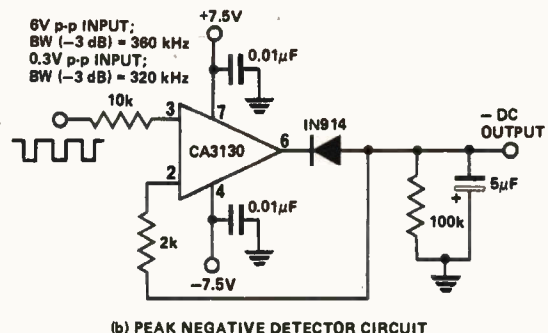

(b) PEAK NEGATIVE DETECTOR CIRCUIT

Fig. 13. Peak positive detector circuit. Detectors such as this are ideal for building accurate ac voltmeters.

Fig. 14. The peak negative detector, although only requiring a reversal of the detector diode gives different bandwidth characteristics.

ERROR-AMPLIFIER IN REGULATED POWER SUPPLIES

The CA3130 is an ideal choice for error-amplifier service in regulated power supplies since it can function as an error-amplifier when the regulated output voltage is required to approach zero. Fig. 15 shows the schematic diagram of a 40 mA power supply capable of providing regulated output voltage by continuous adjustment over the range from 0 to 13 volts. Q3 and Q4 in IC2 (a CA3086 transistor-array IC) function as zeners to provide supply-voltage for the CA3130

comparator (IC1), Q1, Q2, and Q5 in IC2 are configured as a low impedance, temperature-compensated source of adjustable reference voltage for the error amplifier. Transistors Q1, Q2, Q3, and Q4 in IC3 (another CA3086 transistor-array IC) are connected in parallel as the series-pass element. Transistor Q5 in IC3 functions as a current-limiting device by diverting base drive from the series-pass transistors, in accordance with the adjustment of resistor R2.

Fig. 16 contains the schematic diagram of a regulated power-supply

capable of providing regulated output voltage by continuous adjustment over the range from 0.1 to 50 volts and currents up to 1 ampere. The error amplifier (IC1) and circuitry associated with IC2 function as previously described although the output of IC1 is boosted by a discrete transistor (Q4) to provide adequate base drive for the Darlington-connected series-pass transistors Q1, Q2. Transistor Q3 functions in the previously described current-limiting circuit.

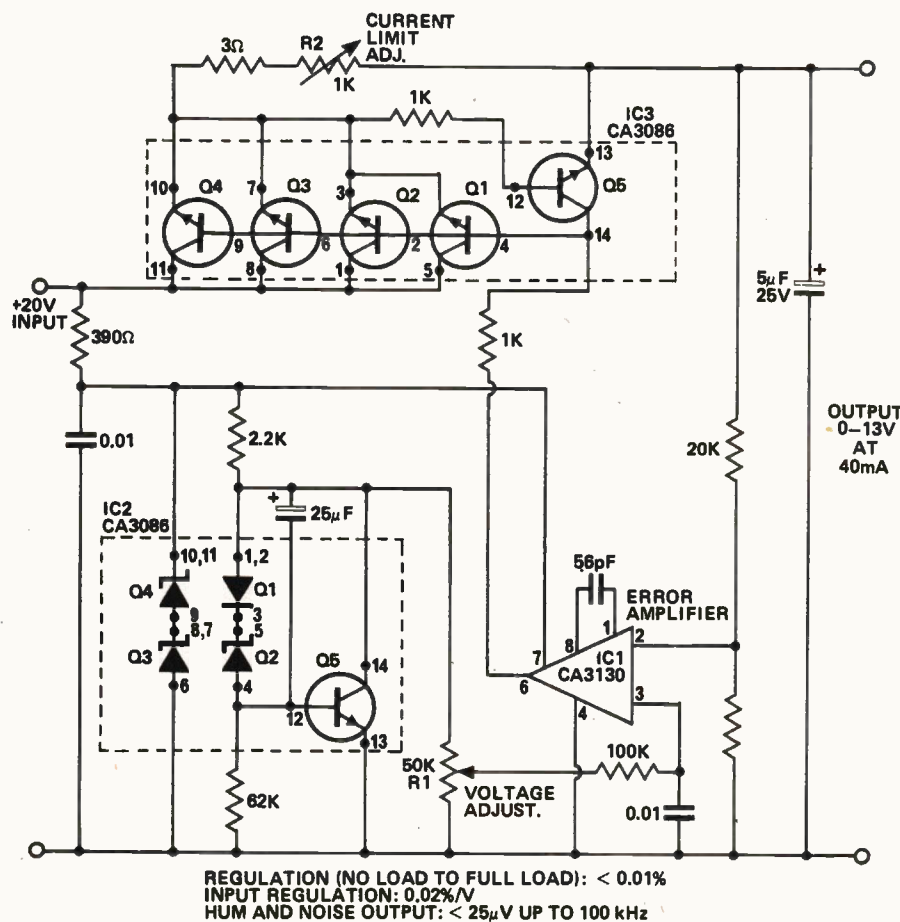


Fig. 15. This voltage regulator circuit provides 0 to 13 volts at up to 40 mA with good regulation and low hum and noise.

MULTIVIBRATORS

The exceptionally high input resistance presented by the CA3130 is an attractive feature for multivibrator circuit design because it permits the use of timing circuits with high R/C ratios. The circuit diagram of a pulse generator (astable multivibrator), with provisions for independent control of the "on" and "off" periods, is shown in Fig. 17. Resistors R1 and R2 are used to bias the CA3130 to the mid-point of the supply-voltage and R3 is the feedback resistor.

FUNCTION GENERATOR

Fig. 18 shows a function generator using the CA3130 in the integrator and threshold detector functions. This circuit generates a triangular or square-wave output that can be swept over a 1,000,000:1 range (0.1 Hz to 100 kHz) by means of a single control, R1. A voltage-control input is also available for remote sweep-control.

The heart of the frequency-determining system is an operational-transconductance-amplifier IC1, operated as a voltage-controlled current-source. The output, I_o is a current applied directly to the integrating capacitor, C1, in the feedback loop of the integrator IC2, using a CA3130, to provide the triangular-wave output. Potentiometer R2 is used to adjust the circuit for slope symmetry of positive-going and negative-going signal excursions.

THE CA3130 OPERATIONAL AMPLIFIER

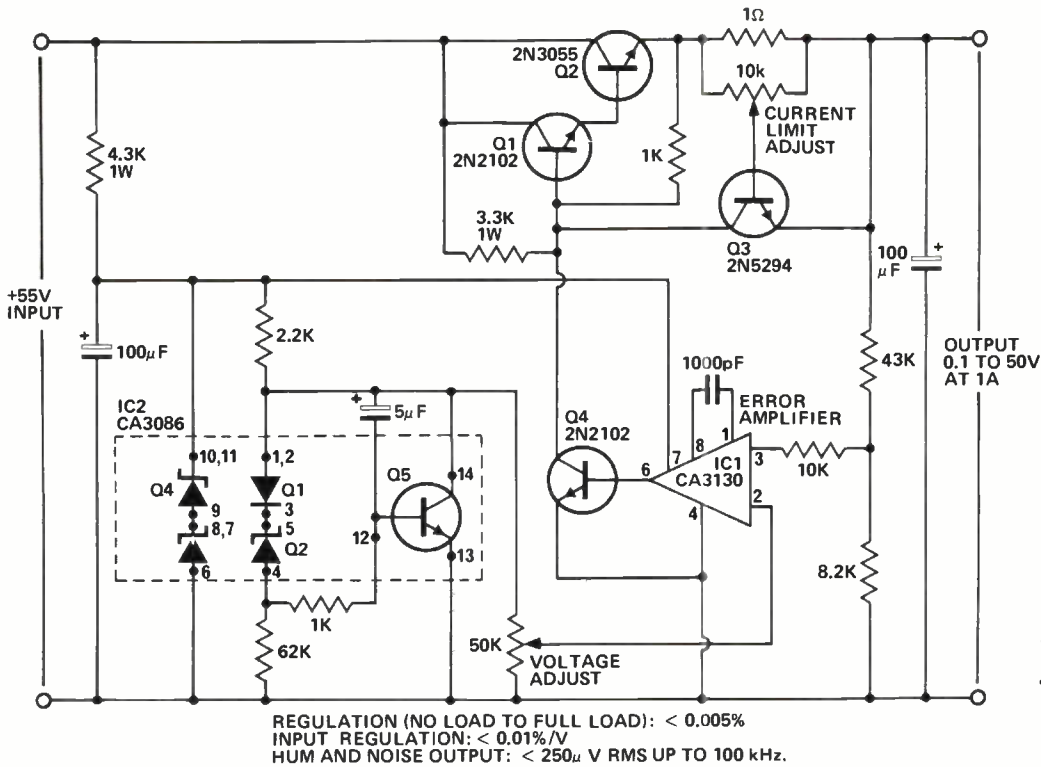


Fig. 16. This regulator provides 0.1 to 50 volts at currents up to 1 amp and has variable current limit.

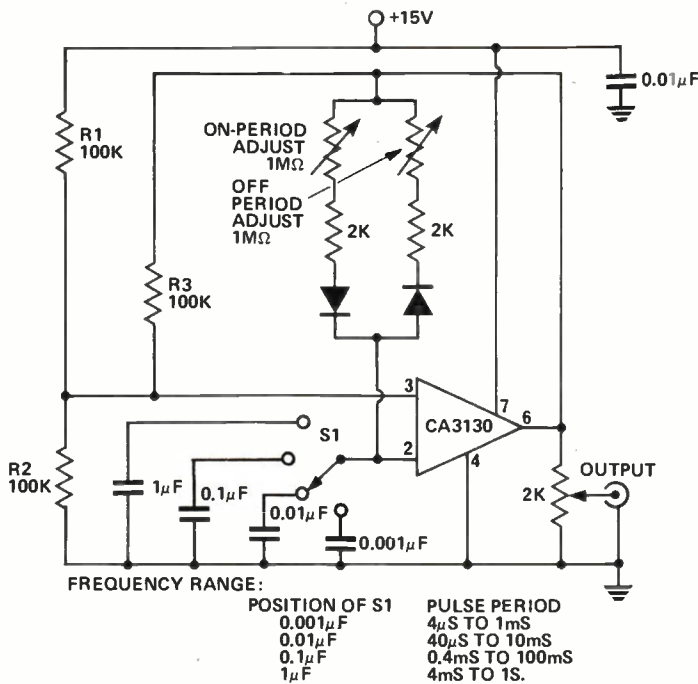


Fig. 17. This pulse generator is basically an astable multivibrator with provision for independent control of ON and OFF periods.

Another CA3130, IC3, is used as a controlled switch to set the excursion limits of the triangular output from the integrator circuit. Capacitor C2 is a "peaking adjustment" to optimize the high-frequency square-wave performance of the circuit.

Potentiometer R3 is adjustable to perfect the "amplitude symmetry" of the square-wave output signals. Output from the threshold detector is fed back via resistor R4 to the input of IC1 so as to toggle the current source from plus to minus in generating the linear triangular wave.

OPERATION WITH OUTPUT-STAGE POWER-BOOSTER

The current-sourcing and sinking capability of the CA3130 output stage is easily supplemented to provide power-boost capability. In the circuit of Fig. 19, three COS/MOS transistor-pairs in a single CA3600E IC array are shown parallel connected with the output stage in the CA3130. In the Class A mode of CA3600E shown, a typical device consumes 20 mA of supply current at 15V operation. This arrangement boosts the current-handling capability of the CA3130 output stage by about 2.5.

The amplifier circuit in Fig. 24 employs feedback to establish a closed-loop gain of 48 dB. The typical large-signal bandwidth (-3 dB) is 50 kHz.

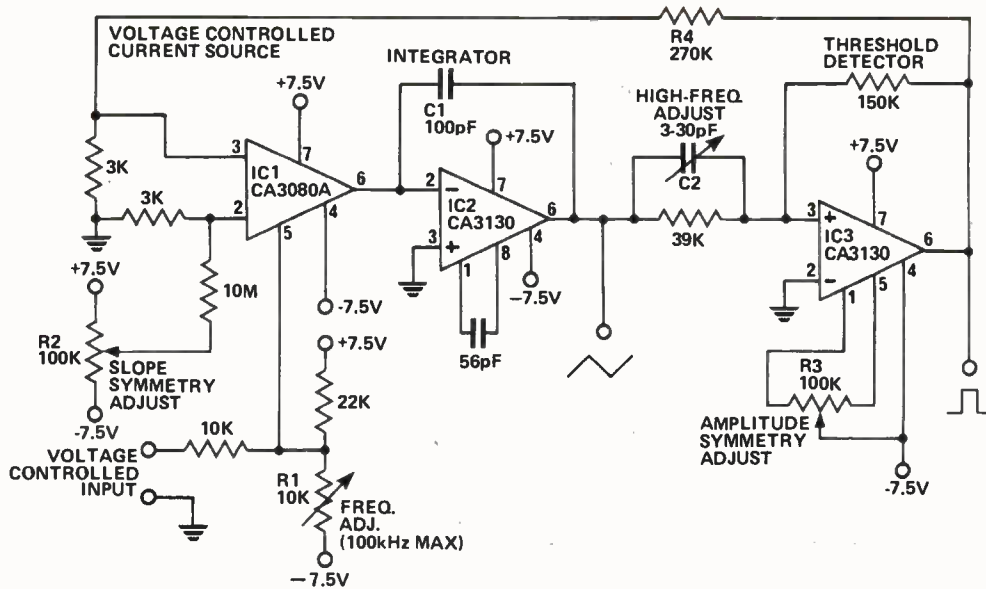


Fig. 18. This function generator provides a frequency variation of 1 000 000/1 with a single control.

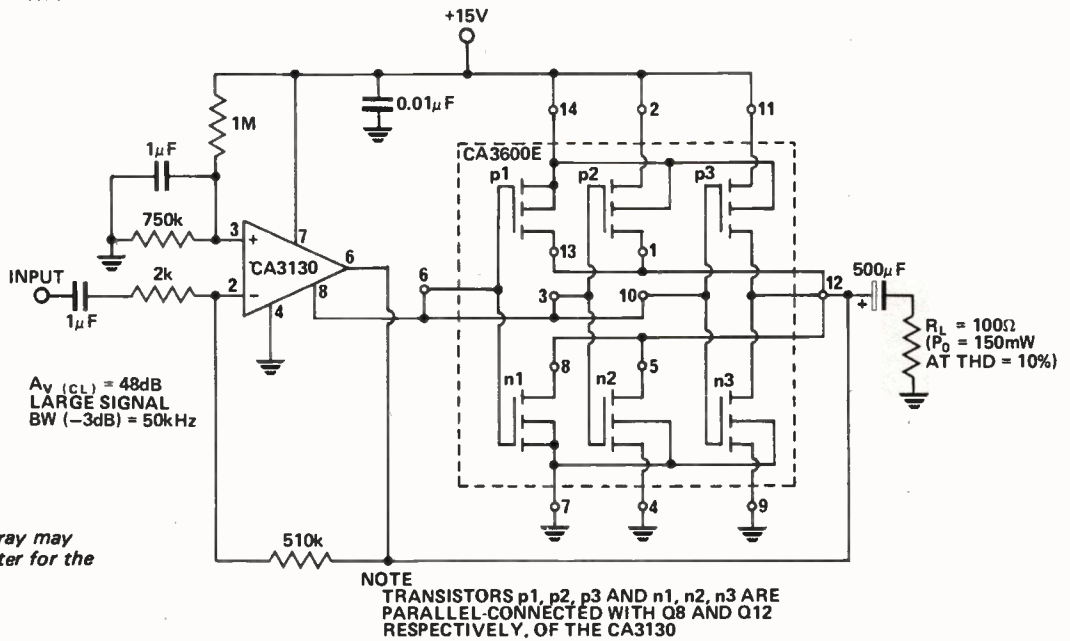


Fig. 19. A CMOS transistor array may be connected as a power booster for the output stage of a CA3130.



18" & 26"

COLOUR MONITORS

Based on the technically advanced Rank Arena colour receiver. Do you want to record TV programmes off-air?

These monitors will also enable you to record with a colour or black and white video camera.


The Video & Hi-Fi Centre

Commercial Concepts

Phone 312-555 — 445 Oxford St., Paddington, N.S.W. A.H. 451-7876

THE NEW '#TWO'

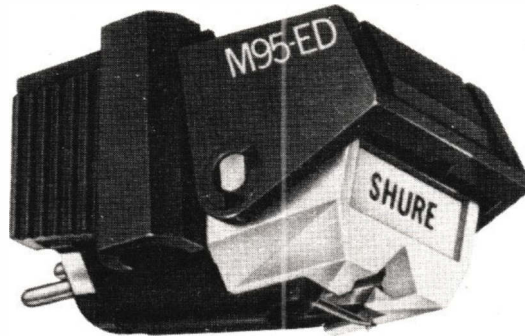BY ANY MEASURE OF PERFORMANCE... THE CARTRIDGE SECOND ONLY TO THE SHURE® V-15 TYPE III



NEW!

M95ED Deluxe High Trackability Cartridge

Second only to one! The Shure M95ED combines several of the high-performance design features of the Shure V-15 Type III to deliver exceptional trackability (at 3/4 to 1 1/2 gram forces). A radically new internal electromagnetic structure insures a level of total performance surpassed only by the Type III. The M95ED incorporates a new, thinner, uninterrupted pole piece developed by Shure design engineers to optimize electromagnetic characteristics—especially at higher frequencies. As a result, magnetic losses have been minimized, and frequency response remains essentially flat across the entire frequency range.

With its nude-mounted, biradial elliptical stylus tip, the M95ED has a very low effective stylus tip mass. This results in higher trackability to maintain perfect groove contact through the "hottest," most heavily modulated passages encountered on modern recordings—all at extremely light tracking forces that reduce record wear and increase stylus tip life. And, as a "plus," its exceptional trackability makes the M95ED an outstanding choice for use in four-channel encoded (matrix) systems.

AE095/FP


M95ED SPECIFICATIONS

Trackability at 1 gram tracking force using a Shure/SME Arm:

24 CM/SEC at 400 Hz
33 CM/SEC at 1,000 Hz
28 CM/SEC at 5,000 Hz
19 CM/SEC at 10,000 Hz

Tracking Force: 3/4 to 1 1/2 grams
Frequency Response: 20 to 20,000 Hz

TRACKABILITY CHART (at 1 Gram)

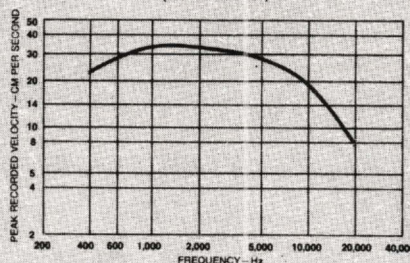

Optimum Load

47,000 ohms resistance in parallel with 400 to 500 picofarads total capacitance per channel. (Load resistance can be as high as 100,000 ohms and total capacitance can be as low as 100 Picofarads with only minor audible change.) Total capacitance includes the capacitances of the tone arm wiring, phono cables, and the amplifier input circuit.

Output Voltage: 4.7 mV per channel at 1,000 Hz at 5 CM/SEC peak velocity

Channel Separation: Minimum 25 dB at 1,000 Hz

Channel Balance: Output from each channel within 2 dB

Stylus: N95ED Biradial elliptical with nude diamond tip

17.8 microns (.0007 inch) frontal radius

5 microns (.0002 inch) side contact radii

25 microns (.001 inch) wide between record contact points

78 rpm Stylus: N95-3 Spherical—63 microns (.0025 inch)

Inductance: 650 millihenries

D.C. Resistance: 1550 ohms

Weight: 6 grams

Mounting: Standard 12.7 mm (1/2 inch) mounting centers

FOR HEAVIER TRACKING TURNTABLES AND TONE ARMS

... Shure designed the M95EJ Custom high trackability cartridge. It uses the same newly developed pole piece as the M95ED and delivers a frequency response virtually identical in its flatness—but at slightly greater tracking forces. The M95EJ features a biradial elliptical stylus tip, and tracks at 1 1/2 to 3 grams. An ideal cartridge choice for audiophiles who want to upgrade their record playback systems at moderate cost!

New Recommended Retail Prices: M95ED \$52 — M95EJ \$33

SHURE


AUDIO ENGINEERS P/L
342 Kent Street,
SYDNEY 2000 N.S.W.

AUDIO ENGINEERS (Vic.)
2A Hill Street,
THORNBURY 3071 Vic.


RON JONES PTY. LTD.
57 Castlemaine Street,
MILTON 4064 Qld.

ATHOL M. HILL P/L
1000 Hay Street,
PERTH 6000 W.A.

ب.و.د. إلكترونيات
-539C

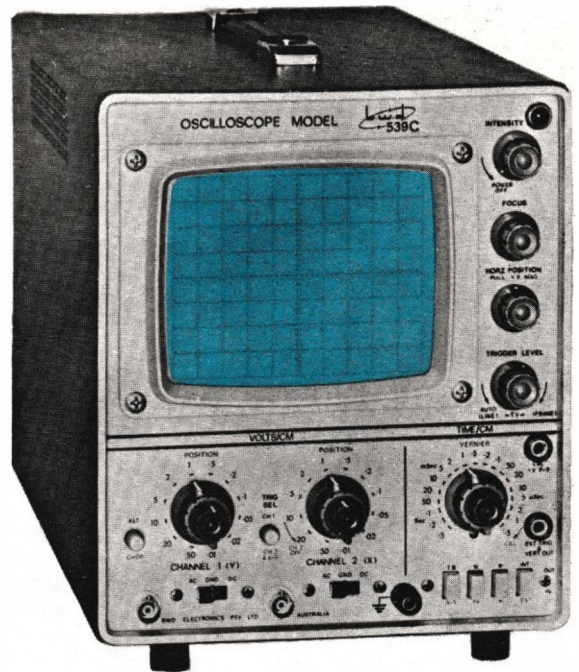

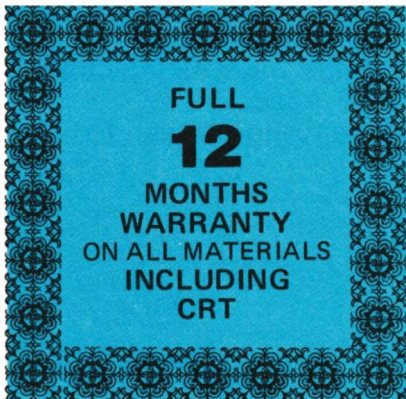At \$399*
the only
DUAL TRACE oscilloscope
with DC to 20MHz bandwidth



The bwd539C stands at the forefront of oscilloscope design and manufacture. Be ready for tomorrow's measurements with an oscilloscope as new as today.

Negligible phase difference between channels over video pass band


and ALL these outstanding features:

- * DC to 20MHz – 3db bandwidth – 17n Sec Rise Time!
- * 10mV to 50V/cm sensitivity – 12 step attenuators.
- * 1mV/cm – 10Hz to 100kHz single channel – for very low level signals.
- * 100nS to 1S/cm time base – 19 steps + 5–1 vernier.
- * <5Hz to 30MHz triggering – bright AUTO base line. TV line & frame selection included.
- * Identical X-Y to 2MHz, phase corrected to 2° from DC to 200kHz – for vector displays & amplifier testing.
- * Precision 1V p-p cal waveform coincident with power line zero cross over – for probe alignment & an ideal trigger source for power line measurements.
- * An 8x10 cm display, 3.3KV EHT – for bright crisp waveforms.
- * Measures signals to beyond 40MHz – sensitivity chart included.
- * 5% calibration including effects of a 10% power line variation – accuracy that doesn't change with the time of the day or from job to job!

* FIS Australian Capital Cities plus sales tax if applicable.

MB7613B

B.W.D. ELECTRONICS PTY. LTD.
MILES STREET, MULGRAVE, VIC., 3170
PHONE: (03) 561 2888
CABLES: 'OSCILLOSCOPE, MELB.
N.S.W. PHONE: (02) 929 7452
DISTRIBUTORS: S.A.: (08) 269 1244
W.A.: (092) 25 3144
QLD.: (072) 52 7255
TAS.: (002) 23 1843

EXPORT AWARD 
Winner of Award for Outstanding Export Achievement

1955/1975 20 YEARS OF AUSTRALIAN DESIGN INNOVATION

B.W.D. Electronics Pty. Ltd.,
P.O. Box 325, Springvale, Vic. 3171.
Please let me have full details on the bwd539C oscilloscope

Name

Company

Address

The FET I/P OP AMP CA3130

Added to the RCA range

Our CA3130 gets many of its winning ways from four very capable relatives. Four RCA op amps that can fill special requirements you may have. If you need programmable linear gain control, check the CA3080. For high crossover frequency plus high slew rate, there's the CA3100T. For high output current and easy programmability, the CA3094E. For low power supply drain, the CA3078T.

The CA3130 is the ideal choice when you're looking for a good measure of all these characteristics in one device. That's what makes the CA3130 so great. Its versatility comes

from the unique combination of MOS/FET, bipolar and COS/MOS on the same chip.

Beyond the table, here's more typical data about the CA3130:

Input Impedance: $1.5 T\Omega$ ($1.5 \times 10^{12} \Omega$).

Input Current: 5 pA.

Input Offset Current: 0.5 pA.

Input Offset Voltage: 0.8 mV (CA3130B).

Settling Time: 1.2 μ sec.

An output voltage swing to within 10 mV of either supply rail.

Strobing terminals.

Package: 10 lead T05.

	CA3080E	CA3100T	CA3094E	CA3078T	CA3130
Gateable plus programmable gain control	> 60 dB				Gateable
Unity gain crossover frequency, MHz		40			15
Slew Rate, V/ μ sec		25			10
Output, mA (peak)			300		22
Power consumption, mW				.0015	2.5
Single supply voltage required, V				1.5	5.0



For further information on the above and other semi-conductor products, please contact:


Amalgamated Wireless Valve Company Pty. Ltd.
(Technical Information)

554 Parramatta Road, Ashfield, NSW 2131.

Telephone: (02) 797 5757. Telex: 24530.

Postal Address: PO Box 24, Ashfield, NSW 2131.

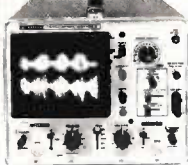TRIO SCOPES (see special reviews this issue)



\$444.13
inc tax
Tax Free \$399.25

CS1560 DUAL TRACE, 15MHz is the ideal scope for servicemen, professionals and advanced hobbyists. Features a full 15MHz bandwidth with 10mV/cm sensitivity and sweep times from 0.5 US/cm to 0.55 0.55/cm. Easy X-Y operation for Lissajous measurements. On dual trace CHOP or ALT is selected automatically. The CS1560 comes with 2 FREE x10 probes worth \$70 and is really outstanding value (p&p Freight on).




\$159.00
inc tax
Tax Free \$144.00

CO1303A 3", 1.5 MHz SCOPE is specially aimed at the advanced hobbyist and is ideal for many applications. Sensitivity is 20mV/cm. Direct input facility allows displays to 150MHz. Dick's huge \$10,000 purchase has brought a \$33.00 saving. Normal trade price is \$192.00. Dick's price is just \$159.00 or Tax Free for just \$144.00. Only while stock lasts. (See review in E.A. June 74) p&p Freight on.

AM-FM MULTIPLEX TUNER YFX-601-IC Specially produced for Australia with 50.5 F.M. de-emphasis (NOT the overseas 75uS) in built ferrite rod for A.M. reception. 25db separation. Provision for stereo indicator. Multiplex IC. Separate tuned R.F. stage. Beaut air spaced tuning gang covers full AM/FM bands. FULLY ASSEMBLED at less than the value of the parts. Highly recommended at \$29.50 (p&p \$1.00)

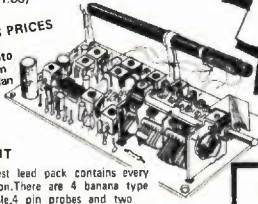COMPARE OUR PRICES WITH TANDY!! You will save upto 10% buying from us - The Australian Company



TEST LEAD KIT

Handy universal test lead pack contains every possible combination. There are 4 banana type terminals, 2 crocodile, 4 pin probes and two spade type. All are nicely plated and attach to the heavy duty red and black leads. They are selling their set of only 11 pieces at \$40. Our price for a 16 piece set is just \$2.90

SIGNAL INJECTOR SPECIAL
The first piece of test gear the serious hobbyist needs. Simply probe into amps radios etc. from speaker back towards front end till the signal dies and you've located the fault! Output extends from audio through to M.F. Fully transistorised. Normally sells at \$8.75 Now under half price at \$4.25. 200 only, so hurry. Requires 1.5V Battery. (p&p \$0.50)

Under Half Price!
\$4.25

CALCULATOR CENTRE NOW OPEN

Up at Gore Hill you'll find Australia's first calculator specialist. The new department has scientific, mathematical, programmable, metric converter, financial, statistical store program... YES every type of calculator is there. Plus Steve Dundrad B.Sc. to advise you. Steve has checked all the calculators for top value from \$10.00 upwards. **FORDS SCIENTIFIC CALCULATOR** the full scientific calculator with memory, fluoro displays etc. 8 digit square roots, trig etc etc. NOW ONLY \$37.50 (tax free) or \$39.75 inc tax (P&P insured \$2.00)

CASSETTE SPECIALS!
We continue our superb Prices on cassettes

BASF	Singles	5	10	20
CB0LHSM	2.50	2.00	1.85	1.55
CB0LHSM	3.00	2.50	2.20	2.00
CB95MC02	3.50	3.00	2.75	2.50

And now HITACHI Cassettes

CB0L N	1.69	1.49	1.39	1.29
CB0L N	2.25	1.99	1.84	1.69
CB0UD	2.50	2.45	2.29	1.99
CB0UD	2.99	2.69	2.49	2.29

For SONY enthusiasts, we have a few Sony HF Tapes left:

CB0	2.75	2.50	2.30
CB9	3.70	3.40	3.10

don't forget P&P

p&p	1 tape	50c
	5	75c
	10	\$1.00
	20	\$1.75

DICK SMITH "DIL" BOARD
Fantastic little plug in printed circuit board measures 100mm x 60mm and takes dual in line IC's or transistors over 400 holes and copper leads, 24 way 1" "plug" etched on board. Will take up to 14, 14pin or 16pin IC's or up to 20 "mini-dip" IC's. Ideal for hobbyists and professional engineers alike. ONLY 75c each or 10 for \$5.00

SALE!
GRAND SLAM JANUARY SUPER SALE!!
We've never had a sale before so the prices here probably been pulled down too far. Every one of our 25,000 regular mail order customers will have received a copy of our special sale bulletin. We won't reveal details here, because we want them to have a chance to place their orders first. It's the only fair way to ensure they don't miss out. You can be in our stores or writing in now. **DON'T MISS OUT ON DICK'S FIRST SALE**

STROBOSCOPE
Check the true speed of your turntable \$1.25

HI-FI NEEDS CARE ... LET DICK SMITH CARE WITH METRO SOUND PRODUCTS

Ioniser—Let velvet remove the dust from discs

Hi-Fi Kit 4 complete care kit with super groove-master ioniser & stylus cleaning kit in permanent storage case.

Discmaster Two free standing arms, one for wet cleaning and one for dry cleaning. Renovate and rejuvenate your records.

8 Track Head & Capstan Cleaners Unique principle for cleaning of tape capstans and replay heads.

Super Groovemaster Efficient removal of dust from your discs while being played—Freestanding.

Hi-Fi Kit 3 Includes ioniser, stylus cleaning brush cleaning fluid in a permanent storage case.

Ioniser	\$2.49
8 Track Clean	\$2.99
Super Groovemaster	\$6.75
Hi-Fi Kit 3	\$5.75
Hi-Fi Kit 4	\$10.95
Discmaster	\$7.95

p&p all items \$1.75

SAVE \$31.00 on this AWA Car Stereo

\$118

CAR STEREO
PU 811C UNDER DASH CASSETTE
From AWA a cassette system incorporating auto reverse with fast forward and rewind system.

SPECS:
Playback system: stereo.
Frequency response: 50-10,000 Hz.
Speaker impedance: 4 ohms.
Output: 5.5W x 2
Power Supply: 10.8V-15.6V Neg ground.
Semiconductors: 4 IC's, 4 trans, 3 diodes
Dimensions 140mm(w)x55mm(h)x150mm(d).

SAVE \$31.00
DICK'S PRICE \$118.00 Bare Unit (No speakers) p&p \$2.50

SAVE \$10.00 **SAVE \$2.96** **SAVE \$21.05**

EXPO CPH145A AC/DC CASSETTE WITH AM/FM RADIO DICK'S PRICE \$69.95	EXPO C1550 HP's The coloured 8Ω Headphone. State Red or Yellow DICK'S PRICE \$12.99	PIANOLA SR2201 Push Button Car AM Radio for 12V Neg or Pos. includes Speaker DICK'S PRICE \$49.95
---	---	---

PLUS FREE 2 C90 Cassettes worth \$2.80

PLUS FREE Convert from 1/4" jack to 3.5mm for cassette worth 85c

PLUS FREE L3 0e Luxe Lock-down Antenna worth \$4.75

SAVE \$31.00
DICK'S PRICE \$118.00 Bare Unit (No speakers) p&p \$2.50

Fed up with not being able to listen to your car radio at the right level when you have passengers with sensitive ears?

Dick has the answer - install an extra speaker front or rear and then put in a TWO SPEAKER SYSTEM FADER. You listen from the front speaker at your level and the passengers from the rear speaker at their level for only \$2.25 p&p 50c (full mounting instructions on box).

AND THAT EXTRA SPEAKER
(All rated at 4 ohms except Bx4 which is 8 or 16 Ω)

7x5	6x9	6x4	6x9	5" round
\$8.00	\$8.00	\$4.50	\$6.99	\$4.50

p&p on all speakers \$1.00

SAVE on Hi-Fi

Pioneer Rando 3000 Complete Tuner/Amp-Turntable and Speakers \$449

SENNHEISER HD414 "The can of the professional"
Save on the old price of \$39.99
NEW PRICE \$33.00 p&p \$2.00

Dick Smith System 1 Expo DX1212 AMP + Expo MX56 Semi Auto Turntable + 2 way Bookshelf System
Save \$64
OUR PRICE \$299

Harmon Kardon Synergy 20+20W RMS Tuner (Amp & Belt Drive Turntable & Bookshelf Speakers
Save \$119 \$499

STOP PRESS: NEW STOP WATCH NOVUS TIMER KIT (E.T. JAN 75) SEE THIS ISSUE
Special kit includes silk screened printed circuit and all components to build this handy timer. YES! including the 650 calculator for only \$16.75 650 Calculator only for \$9.75 (p&p \$1.00)

3 GREAT STEREO CASSETTE DECK OFFERS from

GREAT NAMES GREAT SAVINGS PACKING \$2 FREIGHT ON

WATTMASTER CDS Stereo Cassette Deck with Dolby and chrome switching
\$139.95

NATIONAL PANASONIC RS269 US Including Dolby, Chrome Switching, etc. **\$199**

HITACHI D2500 Calibration of Dolby, chrome memory switch a De Luxe unit. **\$279**

PROFORDS CLOCK NOW IN KIT FORM!

An incredible clock the DCB has everything. Big bright auto charge theory of book minutes and AM just Auto ring on switch or separate push buttons for setting hours and minutes plus hold for accurate setting. Electric alarm to ring the minute on 24 hour operation. Single facility gives a minute cycle. 240V operation. Build it yourself or get one ready made for only \$37.50

KIT VERSION \$27.50 FULLY BUILT & TESTED \$37.50 p&p \$1.00

Posh case for Kit \$3.00 extra

Gore Hill open till 8pm Thurs' for Jan SALE!!

KITS

CAR AERIALS

Lockdown De-Luxe
Heavy duty chrome plate finish. 13" Underhang mounts in 1" hole. Extends 42" Gives maximum performance. Complete with lead and aerial plug. \$4.75

Universal Top Cow!
Mounts in 1" hole 3 sections extending to approx 45" Complete with lead and aerial plug. \$3.75

Roof Aerial
Be a snob and have a centre roof aerial. Spring back gives flexibility. Comes with lead and plug. \$8.95

The SA5100 Electric Aerial
Flick the supplied switch and the aerial will glide up or down. Don't worry about when to stop, the slipping clutch will tell you and save any damage. Operates on 12V reg. or positive. Underhangs 12" mounts in 1" hole. \$21.00

Rear Aerial Head
Want to mount your aerial on the rear of your car - do it properly and use a COMPENSATED AERIAL EXTENSION.
1 Metre length \$2.50
4 Metre (for that extra long car) \$5.95

CAR RADIO NOISE SUPPRESSORS

C1 Cappy for coil. Generator, Alternator etc. 0.5µf 100V. Price .50c

R1 Resistor for inserting in HT leads helps reduce impulse noise. 10Kohm Price .50c

DICK SMITH ELECTRONICS CENTRE 162 Pacific Highway Gore Hill N.S.W 2065 tel:439 5311 telex: AA20036 cables: DIKSMIT Sydney

ALL MAIL ORDERS TO Dept 1 ET P.O. Box 747 Grows Nest N.S.W. 2065


Also at **CITY 125 York St tel: 29126** (Nr Town Hall) and **BANKSTOWN 361 Hume Hwy tel: 709 6600** (Nr Chapel Rd)

bankcard welcome here



PROJECT 441

AUDIO NOISE GENERATOR

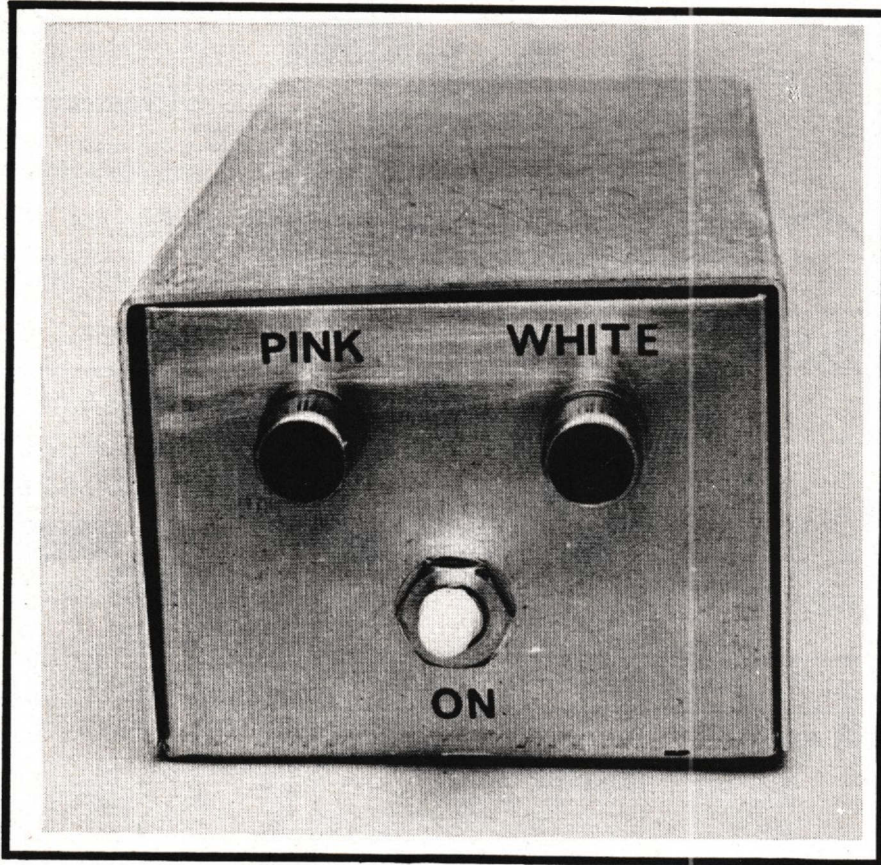

Simple circuit generates both white and pink noise.

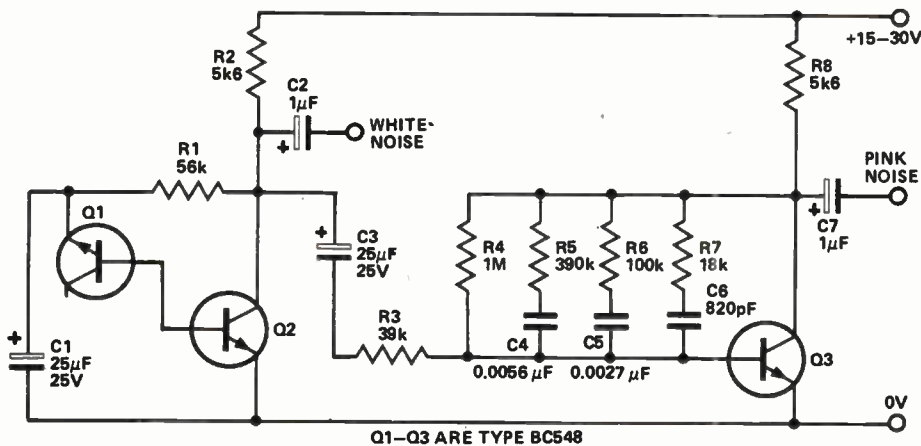


Fig. 1. Circuit diagram of the noise generator.

NOISE is generally an undesirable phenomena that degrades the performance of many measurement and instrumentation systems. It therefore seems strange that anyone should want to generate noise, but this is often the case.

Noise generators are often used to inject noise into radio-frequency amplifiers in order to evaluate their small signal performance. They are also used to test audio systems, and as random signal sources for wind-like effects in electronic music.

There are two commonly used noise source characteristics, 'pink' and 'white'. White noise is so called because it has equal noise energy in equal bandwidths over the total frequency range of interest. Thus, for example, a white noise source would have equal energy in the band 100 to 200 Hz to that in the band 5000 to 5100 Hz.

HOW IT WORKS — ETI 441

In the days when vacuum tubes were in common use the most commonly used form of noise generator was a vacuum-tube diode operated in the current saturation mode. Nowadays noise generators may be very complex indeed. Highly complex digital generators which produce pseudo-random digital noise may cost many thousands of dollars. An example of a simpler type of digital noise source may be found in our synthesizer design (see International Music Synthesizer 4600 ETI December 1973). However for audio work of a general nature the most commonly used, and the simplest, method is to use a zener diode as a noise generator.

Transistor Q1 is in fact used as a zener diode. The normal base-emitter junction is reverse-biased and goes into zener break-down at about 7 to 8 volts. The zener noise current from Q1 flows into the base of Q2 such that an output of about 150 millivolts of white noise is available.

The 'zener', besides being the noise source, also biases Q2 correctly, and the noise output of Q2 is fed directly to the White Noise output.

To convert the white noise to pink a filter is required which provides a 3 dB cut per octave as the frequency increases. A conventional RC network is not suitable as a single RC stage gives a cut of 6 dB per octave. Hence a special network of Rs and Cs is required in order to approximate the 3 dB-per-octave slope required. Since such a filter attenuates the noise considerably an amplifier is used to restore the output level. Transistor Q3 is this amplifier and the pink noise filter is connected as a feedback network between collector and base in order to obtain the required characteristic by controlling the gain-versus-frequency of the transistor. The output of transistor Q3 is thus the pink-noise required and is fed to the relevant output socket.

If white noise is filtered or modified in any way it is referred to as coloured noise or, often more specifically, as 'pink' or 'grey' noise. The term pink noise should be restricted to the noise characteristic that has equal energy per percentage change in bandwidth. For example with true pink noise the energy between 100 Hz and 200 Hz should equal that between 5000 Hz and 10 000 Hz (100% change in both cases).

Pink noise therefore appears to have more bass content than does white noise, and it appears to the ear to have a more uniform output level in audio testing. To change white noise to pink noise a filter is required that reduces the output level by 3 dB per octave (10 dB per decade) as the frequency is increased. The ETI 441 Noise Generator is designed to provide both white and pink noise as required.

PARTS LIST — ETI 441

R1	Resistor	56k	½W	5%
R2	"	5k6	½W	5%
R3	"	39k	½W	5%
R4	"	1M	½W	5%
R5	"	390k	½W	5%
R6	"	100k	½W	5%
R7	"	18k	½W	5%
R8	"	5k6	½W	5%
C1	Capacitor	25µF	25V	electro
C2	"	1µF	25V	electro
C3	"	25µF	25V	electro
C4	"	0.0056µF		polyester
C5	"	0.0027µF		polyester
C6	"	820pF		ceramic
C7	"	1µF	25V	electro

Q1-Q3 Transistor BC548, BC108

or similar

PC board ETI 441

CASE

BATTERIES

OUTPUT SOCKETS


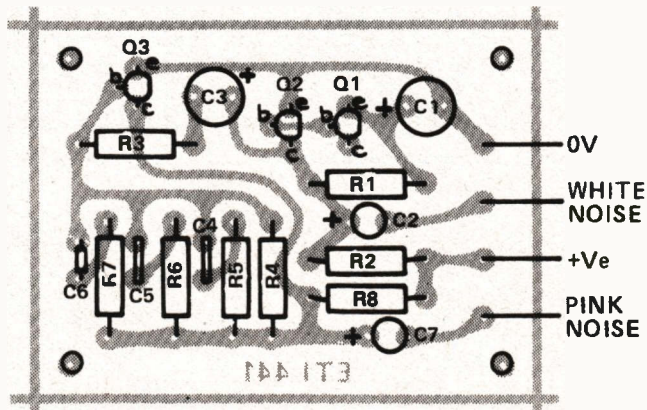


Fig. 2. Component overlay.

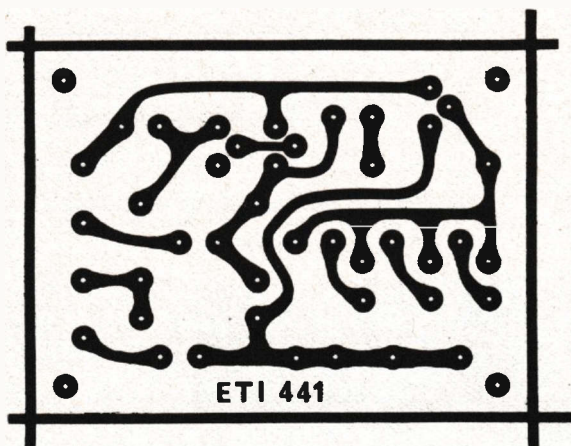

Printed circuit layout. Full size 67 x 49 mm.

CONSTRUCTION


Construction is relatively simple and almost any of the common methods, such as Veroboard or Matrix board, may be used if desired. For neatness and ease of assembly it is hard to beat a proper printed-circuit board and for this reason we have provided details of a suitable board.

Almost any type of NPN transistor will do for the generator provided that the one used for Q3 has a gain of 100 or more. If BC548 type are used watch


out for the two different pin connections used by different manufacturers.

For use as a separate instrument in general experimentation the unit will need to be powered by a pair of nine-volt batteries. However if the unit is to be built into some other piece of equipment, as is often the case, any supply within the equipment which has an output of between 15 and 30 volts dc will be suitable.


AUDIO NOISE GENERATOR

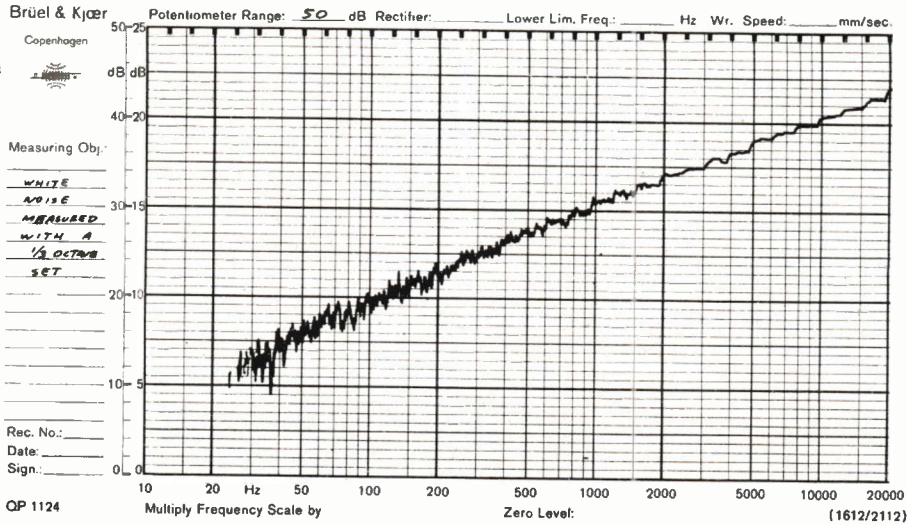

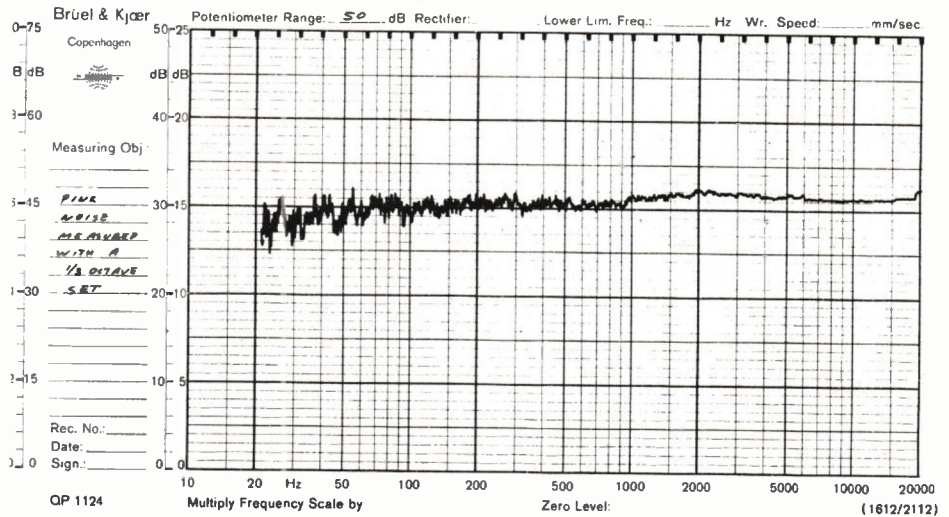Amplitude of white noise versus frequency as measured with a one-third octave filter set.



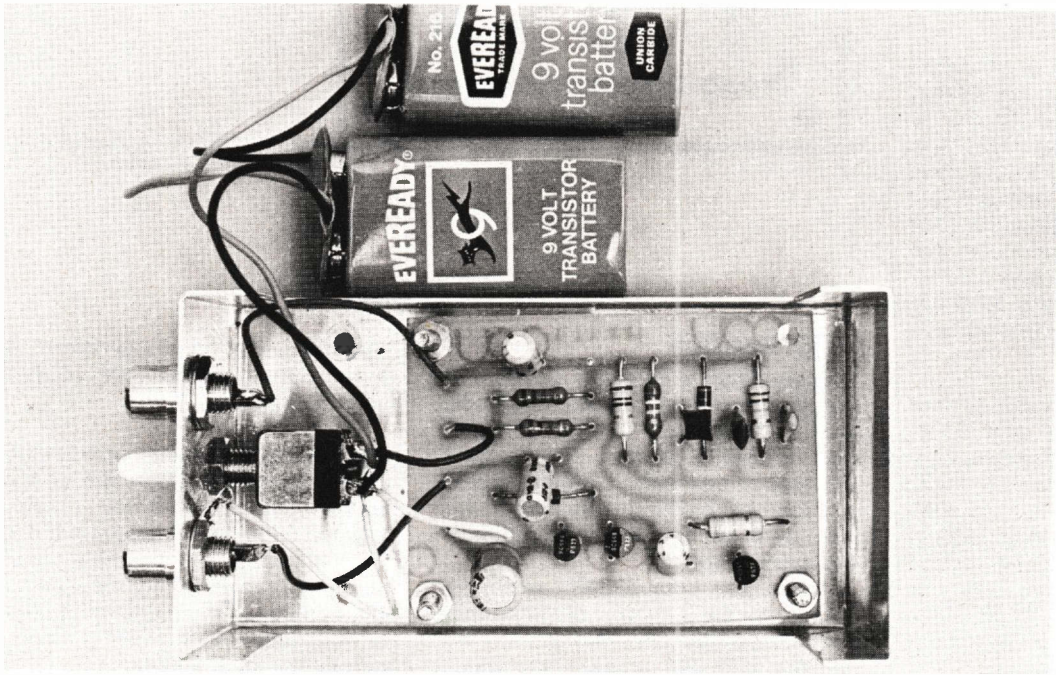Amplitude of pink noise versus frequency as measured with a one-third octave filter set.



Internal layout of the generator.

HAM RADIO SUPPLIES

MAIL ORDER SPECIALISTS

323 Elizabeth Street, Melbourne (2 doors from Little Lonsdale Street) 674286 67-7329
new Richmond branch now at 390 Bridge Rd., Richmond Phone 42-5174

MODEL NC-310 DE LUXE 1 WATT 3 CHANNEL C.B. TRANSCEIVER

● WITH CALL SYSTEM
● EXTERNAL AERIAL CONNECTION
SPECIFICATIONS, NC-310
Transistors: 13
Channel Number: 3, 27.24 OMHZ
Citiz. Band
Transmitter Frequency Tolerance: $\pm 0.005\%$
RF Input Power: 1 Watt
Tone Call Frequency: 2000 Hz
Receiver type: Superheterodyne
Receiver Sensitivity: 0.7 μ V at 10 dB S/N
Selectivity: 45 dB at ± 10 kHz
IF Frequency: 455 kHz
Audio Output: 500 mW to External Speaker Jack
Power Supply: 8 UM-3 (penlite battery)
Current Drain: Transmitter: 120-220mA
Receiver: 20-130mA.



\$49.00 each or \$95 a pair.
Post & pack \$1.50 per unit.

1 watt 2 channel transceiver with call system. 27.240 MHz. 12 transistor. PMG approved type.

SPECIFICATIONS:
Transmitter — Crystal Controlled: 1 Watt input power to RF stage. Operating frequency — Any 2 channels in the 11-meter Citizens Band. Receiver — Crystal-controlled superheterodyne circuit with 455 Kc IF. Antenna — Built-in 60" telescopic whip antenna. Audio Output — 0.8 Watt maximum. Power supply required — 12 volts DC (Eight 1.5 volt DC battery cells). Loudspeaker — 2 1/4" PM type (built-in) function as microphone on transmit.



\$39.00 each or \$75 a pair.
Post & pack \$1.50 each unit.



BARLOW-WADLEY XCR-30

a truly portable communications receiver, based on the WADLEY LOOP principle, the same principle as applied in the

DELTAHET and RACAL receivers. A truly crystal-controlled highly sensitive multiple-heterodyne portable receiver of exceptional stability with continuous, uninterrupted coverage from 500 kHz to 31MHz.

BARLOW-WADLEY XCR-30 features include: Selectable USB/LSB, CW & AM reception, frequency read-out 10kHz throughout the entire range, calibration accuracy within 5kHz, antenna resonator, tuning signal-strength meter, zero-set control, clarifier-vernier tuning, MHz & kHz tuning controls, telescopic antenna. Power source: 6 type D dry cells; provision for external DC power supply. Weight 9 lbs; size 11 1/2 x 7 1/2 x 4in.

All for **\$275 F.O.R.**

When not in use or for carrying, the top meter/megahertz scale flips down flush with the case and clear of the handle.

NEW REDUCED PRICE THIS MONTH ONLY



\$6.95
Post Free.

MODEL C1000M MULTIMETER
Compact, handy and versatile, the C1000M is the ideal low cost pocket meter. Mirror Scale. Specifications: 1,000 Ohm/Volt DC; 1,000 Ohm/Volt AC; DC volts — 10; 50; 250; 1,000; AC volts — 10; 50; 250; 1,000; DC amps — 1 mA; 100 mA; Ohms — 150 K Ω ; Centre scale — 3 K Ω ; Decibel — 10 dB to 22 dB; Dimensions — 3-1/2" x 2-3/8" x 1-1/8" 90 x 60 x 30 mm.



\$27.95
P&P \$1.50.

MODEL C-7077/P MULTIMETER
Specifications: 100,000 ohms/volt DC; 10,000 ohms/volt AC; DC volts — 5; 25; 50; 250; 500; 1,000; AC volts — 10; 50; 250; 500; 1,000; DC amps — 10 μ A; 2.5 mA; 25 mA; 500 mA; Ohms — 10 K Ω ; 1 M Ω ; 10 M Ω ; 100 M Ω ; Centre scale — 150 Ω ; 15 K Ω ; 150 K Ω ; 1.5 M Ω ; Decibel — 20 to +22 dB. Dimensions — 151 x 102 x 48 mm. Diode protected movement. Carrying case available Model C.

MODEL OL64 D/P MULTIMETER.

Very ruggedly constructed this model is particularly suitable for workshops. It features special scales for measurement of capacitance and inductance. Diode protected movement. Specifications: 20,000 Ohm/Volt DC; 8,000 Ohm/Volt AC; DC volts — 0.25; 1; 2.5V; 10; 50; 250; 1,000; 5,000; AC volts — 10; 50; 250; 1,000; DC amps: 50 μ A; 1 mA; 50 mA; 500 mA; 10 A. Ohms — 4 K Ω ; 400 K Ω ; 4 M Ω ; 40 M Ω ; Centre scale — 400 Ω ; 4,000 Ω ; 40,000 Ω ; 400,000 Ω ; Decibel: —20; to +62 dB. Dimensions: 6" x 4-1/5" x 2"; 152 x 107 x 51 mm. Capacitance: 250 pF to 0.02 μ F. Inductance — 0/5000H Carrying case available Model C.

\$22.50 P&P \$1.50.

MODEL AS100 D/P MULTIMETER.

This meter features double zener diode meter protection and 3 1/2" full view easy to read 2 colour scale. It is fitted with polarity reversing switch and housed in a strong moulded case with carrying handle. Specifications: 100,000 ohm/volt DC; 10,000 ohm/volt AC; DC volts — 0.3; 12; 60; 120; 300; 600; 1,200; AC volts — 6; 30; 120; 300; 600; 1,200V; DC amps — 2 K Ω ; 200 K Ω ; 20 M Ω ; 200 M Ω ; Centre scale — 200 Ω ; 2,000 Ω ; 20,000 Ω ; 200,000 Ω ; 20 M Ω ; Decibel — 20; to +57 dB. Dimensions — 7-3/5" x 5-2/5" x 2-3/5" 193 x 137 x 66 mm. Carrying case available model I.

\$37.50
P&P \$1.50.

SCOOP PURCHASE



\$13.50 With FREE leather carry case.
\$1.50 Postage.

200-H, p.p. 75c. 90
quadrant meter. Pocket
size. AC V: 10V, 50V,
100V, 500V, 1000V
(10,000 ohm/V). DC/V:
5V, 25V, 50V, 250V,
500V, 2500V (20,000
ohms/V). DCA/A: 50 μ A;
2.5 mA, 250 mA. OHM:
60k ohm, 6M ohm.
Capacitance: 100pF to 0.1
 μ F, .001 μ F to .1 μ F. dB:
-20 dB to +22 dB. Audio
Output: 10V, 50V, 120V,
1000V AC. Approx. size:
4 1/2" x 3 1/4" x 1-1/8"

THIS MONTHS SPECIAL SOLID STATE 19 TRANSISTOR MULTI- BAND RADIO — 9 RANGES



AM, SW, FM,
VHF, AIR, PB


BATTERY/OPERATED
COLOUR CODED 9 BAND DIAL

1. AM 535 to 1600 kHz, 2. Marine 1-5 to 4 MHz, 3 & 4. combined SW 4 to 12 MHz, 5. 30 to 50 MHz, 6. 88 to 108 MHz, 7, 8 & 9 combined VHF Aircraft 145 MHz-174 MHz Incorporating weather band. Slider controls, Dial light, Fine tuning control, Flip-up Time Zone map, Telescope antennas complete with batteries

SPECIAL PRICE \$59 Post AC-DC
Pack S.E.C. \$3.00 APPROVED

CHRISTMAS SPECIAL

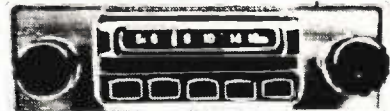8 transistor, push-button car radio, 12 volt neg. earth. With large 7 x 5 inch speaker and lock down aerial.



\$24.95 P&P \$2.00.

Manual tuning model
\$15.50 Post & Pack \$2.00.

A M / F M / V H F / T V . MULTIBAND RADIO. NEW MODEL AC/DC.

Latest military design multi-band radio, 30 transistors and diodes. With exclusive (LED) light emitting diode tuning indicator for positive station selection. Battery and electric covers all popular AM and FM bands.



NEW PRICE \$49.50

P&P \$2.50
APPROVED BY ELECTRIC SUPPLY
DEPT. BEWARE OF MORE EXPENSIVE
IMITATIONS.

BRIGHT STAR CRYSTALS

ESTABLISHED FOR THE PAST 35
YEARS FOR ALL YOUR

★ REQUIREMENTS ★
STILL ON TOP

CRYSTAL FILTERS


- 9 MHz side band with carrier crystals 4 & 8 pole type
- Specialised monolithic filters, 10-100 MHz
- Front end filters to 190 MHz

ELECTRONIC UNITS

- Decade Counting units to .1 Hz
- Wide band amplifier for your counter, 1 MV sensitivity, band width 1-250 MHz

DEVOTED EXCLUSIVELY TO
THE MANUFACTURE OF
PIEZO ELECTRIC
CRYSTALS

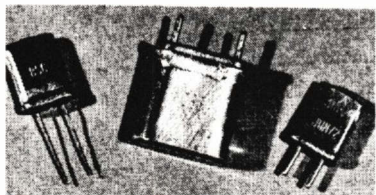Contractors to Federal & State
Government Departments.



"All Types of Mountings"

REPRESENTATIVES —

S.A. Rogers Electronics
P.O. Box 3,
Modbury North, S.A.
Phone: 264-3296

N.S.W. Paris Radio Electronics,
7A Burton Street,
Darlinghurst, N.S.W.
Phone: 31-3273

QLD Fred Hoe & Sons Pty Ltd,
246 Evans Road,
Salisbury North, Brisbane,
Phone: 47-4311

W.A. W.J. Moncrieff Pty Ltd.,
176 Wittenoom Street,
East Perth, 6000
Phone: 25-5722

TAS. Dilmond Instruments,
P.O. Box 219,
Bellerive, Hobart, Tas.
Phone: 479-077.

Send stamped addressed
envelope for new catalogue or
quote for your requirements.

BRIGHT STAR CRYSTALS P/L.
35 EILEEN ROAD, CLAYTON,
VICTORIA, 546-5076



-that's where the money is!

Stott's course is totally comprehensive — and includes both sophisticated electronic equipment and project materials you need to gain a thorough understanding of servicing techniques.

Divided into three self-contained sections, the course covers:

Part 1 — Introduction to Electronics (theory and practice)

Part 2 — Monochrome Television Receivers

Part 3 — Colour Television, including processing circuitry, service techniques, fault tracing and trouble shooting techniques.

Like all Stott's courses, you work with your own instructor who is an expert in this exciting and rewarding field, at your own pace, in your own home.

If you are a beginner, Stott's will teach you everything you need to know concerning television principles and receiver circuitry.

If you are already working in the field, or have completed some studies in electronics, you may be eligible to enter the course at an advanced stage. Whether your aim is to enter the TV service industry or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course which will help you make it!

Other electronics courses offered by Stott's include:

Radio for Amateurs — Amateur Operator's Certificate

For full information mail this coupon today:

Stotts

TECHNICAL CORRESPONDENCE COLLEGE
The name to trust in correspondence education
Please send me, without obligation, full details of the following courses:

Stott's undertake that no sales counsellor will call

Mr. Mrs. Miss Age

Address Postcode


159 Flinders Lane Melbourne 66 King William St Kent Town, S A
383 George Street Sydney 89 St George's Terrace, Perth
290 Adelaide Street, Brisbane P O Box 3396 Singapore 1

ET1/76



A TELEDYNE COMPANY

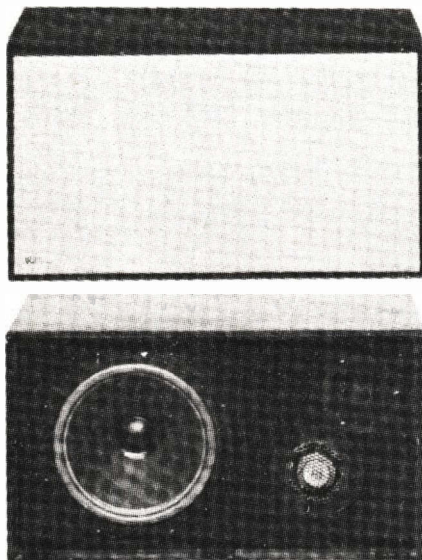THE AR 3a / IMPROVED an evolutionary new SPEAKER SYSTEM




The AR-3a/Improved is the best home speaker system we know how to make. It has been designed to reproduce music as accurately as present-day knowledge of acoustics and electronics permits.

In addition to incorporating the 305mm (12in) bass driver with which AR introduced acoustic suspension to home listeners, the AR-3a/Improved also uses the two miniature hemispherical dome speakers developed for the AR-3a to offer an unprecedented degree of accuracy at middle and high frequencies.


Concepts and techniques developed for the AR-LST and other AR speaker systems have now enabled AR engineers to improve the spectral energy characteristics of the AR-3a and further reduce its already small degree of coloration, while retaining all the virtues of the original design. These improvements have been accomplished by means of significant changes in the design of the crossover: all other components, including driver units and cabinet, are exactly the same as those of the AR-3a.

The AR-3a/Improved is capable of a more linear spectral energy output than was the AR-3a. A two-position switch makes it possible to tailor this characteristic for maximum realism under either reverberant or relatively damped listening conditions.


On-axis response

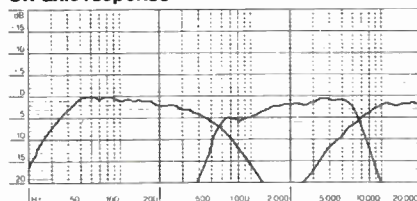

Acoustic power output

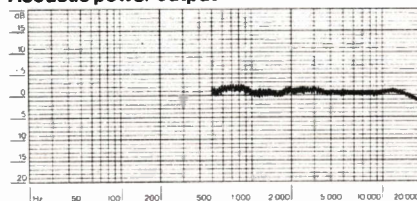

Woofer harmonic distortion

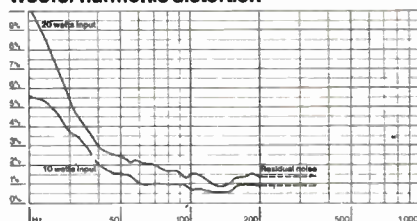

Drive units: 305 mm (12 in) acoustic suspension woofer, 38 mm (1½ in) midrange hemispherical dome, 19 mm (¾ in) high-frequency hemispherical dome

Crossover: 575 Hz, 5000 Hz
Impedance: 4 ohms nominal

Controls: Midrange and high-frequency driver level controls

Amplifier: Up to 100 watts per channel
Size: 356 x 636 x 289 mm deep (14 x 25 x 11½ in)
Weight: 24 kg (53 lb)
Woofer resonance: Free air 18 Hz, in enclosure 42 Hz
Volume of enclosure: 48.2 litres (1.7 cu ft)

'... the best speaker frequency response curve we have ever measured using our present test set-up... virtually perfect dispersion at all frequencies... AR speakers set new standards for low-distortion, low-frequency reproduction, and in our view have never been surpassed in this respect'. *Stereo Review*

'On any material we fed to them, our pair of AR-3a's responded neutrally, lending no coloration of their own to the sound... the speakers sounded magnificent, filling the place with a lot of clean, musical sound and an excellent stereo image... Our tests of the AR-3a simply confirm the manufacturer's design aims and claims for this system'. *High Fidelity*

'The harmonic distortion at bass frequencies was outstandingly low... The high-frequency dispersion is the widest of any speaker we have tested... a new high standard of performance at what must be considered a bargain price'. *Audio*

'Acoustic Research have achieved what they set out to do - a first class loudspeaker by any standard'. *Hi-Fi News*

'Finest bass performance I have heard or measured'. E J Jordan, *Wireless World*

The AR guarantee
The workmanship and performance in normal use of AR speakers are guaranteed for 5 years from the date of purchase. This guarantee covers parts, repair labour, and freight costs to and from the factory or nearest authorized service station. New packaging if needed is also free.

The acoustic research 3A improved is now on demonstration at these franchised dealers:

Sydney
Sydney Hi-Fi Centre
Instrol Hi-Fi
Electronic Enterprises
Mastertone Electronics
Hi-Fi House
Apollo Hi-Fi
Autel Systems
Kent Hi-Fi
Adelaide
Blackwood
Sound Centre

Melbourne
Brash's
Denman Hi-Fi
Douglas Trading
Instrol Hi-Fi
Pantiles Hi-Fi
Mordialloc Electrical
Geelong
Sound Spectrum
(E & B Wholesale)

Perth
Alberts Hi-Fi
Leslie Leonard
The Audio Centre
Canberra
Douglas Hi-Fi
Wollongong
Hi-Fi House
Newcastle
Ron Chapman & Assoc.,

Brisbane
Reg Mills Stereo
Stereo Supplies
Darwin
Pfitzners Music House
Hobart
Quantum Hi-Fi
Launceston
Wills & Co.


Australian Distributors
W.C. Wedderspoon Pty Ltd.,
3 Ford St., Greenacre (P.O. Box 21)
Phone 642-2595, 642-3993

IMPORTED DUTCH

PHILIPS

speaker
kits . . .

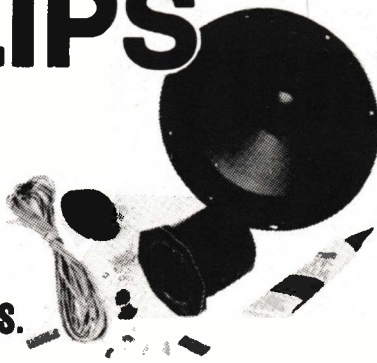POPULAR (7B)
KIT OPTIMISES
AMPLIFIERS FROM
15-40 WATTS R.M.S.
FOR NON-COLORED
30-20,000 HZ RESPONSE. KIT - \$129 PR.



Kit includes plans, all hardware and features the Philips 1265 W8 woofers, sealed back midranges AD5060, ADO160/T8 tweeters and the exclusive G.H.E. crossover.

16 KITS \$28-\$398 PR.

	Power W.	Frequency Range	Kit Price Pr.
7A1	15-50	25,20,000 Hz	\$229.00
7A	15-60	25-20,000 Hz	\$198.00
7B1	15-40	28-20,000 Hz	\$153.00
7B	12-38	28-20,000 Hz	\$129.00
7C	8-28	25-20,000 Hz	\$122.40
7D	6-25	25-20,000 Hz	\$89.96
6A	15-50	40-20,000 Hz	\$193.30
6C	4-16	25-20,000 Hz	\$69.00
5A	6-30	30-20,000 Hz	\$140.00
4A	8-30	40-20,000 Hz	\$140.00
3A	8-20	50-20,000 Hz	\$84.14
AD 8K40	15-40	55-20,000 Hz	\$87.84
ET1 400	15-40	30-20,000 Hz	\$87.98
3B	6-15	45-17,000 Hz	\$28.00
21	20-60	40-20,000 Hz	\$263.50
22	20-60	38-20,000 Hz	\$398.00

- ALL KITS COMPLETE ALL HARDWARE
- UNCONDITIONAL GUARANTEE 1 YEAR
- ENCLOSURE DESIGN SERVICE

HITACHI UDC 90 TAPE 12 PACK PRICE OF \$29

Voted by HI-FI review June 1975 as best performance/value for money tape available. 36 pack \$78.00, 60 pack \$125.00. UDC60/120 available at special savings too!



**USE OUR RAPID MAIL ORDER
SERVICE - Despatch same day!**

G.H.E.
GEORGE HAWTHORN ELECTRONICS

ADD 5% FOR P&P
966 HIGH STREET,
ARMADALE VIC.
TELEPHONE
509 0374, 509 9725

A FANTASTIC OFFER FROM THE U.S.

6 DIGIT L.E.D. CLOCK KITS

12/24 HOUR

50/60 HZ.

BRIGHT
LED's



SLOW SET

FAST SET

TIME HOLD

\$13-75

Postpaid via airmail

To introduce Sabtronics International to readers of E.T.I. Australia, we are offering this top quality clock kit at this low price. All components are brand new factory tested. SATISFACTION GUARANTEED!

COMPONENTS INCLUDE:

- National MM14 Clock Chip, 12/24 hour, 50/60 Hz. option.
- 6 Bright red L.E.D. readouts (0.27" digit height).
- 7 Segment driver transistors.
- 6 Cathode driver transistors.
- 4 1N4001 Rectifier diodes.
- 1 1N914 Diode.
- 9 Carbon resistors.
- 1 1000 μ F/25 V electro. capacitor.
- 2 0.01 μ F Disc capacitors.
- 2 Push button switches for slow and fast time settings.
- 1 Slide switch for time hold function.
- 2 Etched and drilled fibreglass p.c. boards.
- 1 Illustrated assembly instructions manual.

All you need add is a 9-12 Vac/200 mA transformer and a suitable case of your choice. No electronics knowledge required to construct this kit.

ORDERING INFORMATION: The price as listed is in Australian dollars. Remittance by Bank (cashiers) Cheque or International Money Order (send receipt with order).

SABTRONICS INTERNATIONAL P.O. BOX 64683,
DALLAS, Tx. 75206, U.S.A.

CARDIAC

Computer Learning System.

- A device developed by Bell Telephone Laboratories U.S.A. for illustrating the basic working concepts of computers.
- An excellent teaching aid suitable for children or adults.
- Compares with plastic or metal versions at many times the price.
- Contains ten op codes. Memory cells may be entered and erased manually.

IDEAL AS XMAS GIFTS

Available now at \$5.95 plus 40c. postage from:

ELECTRO TECHNICS PTY. LTD.

G.P.O. Box 1210K, Melbourne 3001.
Telephone 699-2716.

CALCULATOR STOPWATCH

An inexpensive calculator modified to provide one-hundredth of a second timing.


FOUR-FUNCTION calculators are now available for as little as \$9.95. At those prices, it is cheaper to buy a calculator and throw away the parts that you don't need, than it is to buy a keyboard, display, or calculator chip separately.

Having this in mind we were very interested to receive an application note from National Semiconductor which detailed how to modify one of their calculators for use as a stopwatch. We therefore decided to develop this idea to a full project for a calculator/stopwatch which provides timing with one-hundredth of a second resolution for a cost as low as \$17 (including the calculator).

The NOVUS 650 calculator is a simple four-function machine which has a fixed decimal point between the second and third (RH) digits. The calculator does not have floating point, and only works in whole numbers, the decimal point being an indicator only. These features however, whilst detracting from the usefulness of the machine as a calculator, make it ideal for modification, without difficulty, for use as a stopwatch.

Stopwatch operation is made possible by the fact that if '1' is entered into the calculator and the '+' key is continually pressed, the calculator will add '1' to the number displayed each time the '+' key is pressed. Thus, as a stopwatch, the '+' key must be 'pressed' electronically 100 times per second. (If a floating-point calculator were to be used, 0.01 would have to be added each time the key was pressed and this of course is much more difficult to do).

The 100 Hz timebase, required for the key-pressing function, needs to be supplied by means of a crystal and a divider chain or, by some other simple but stable oscillator such as a PUT. For most applications the PUT (programmable unijunction transistor) is quite accurate enough and this, coupled with the fact that the crystal and its dividers are bulky and relatively expensive, led to us choosing the PUT oscillator.

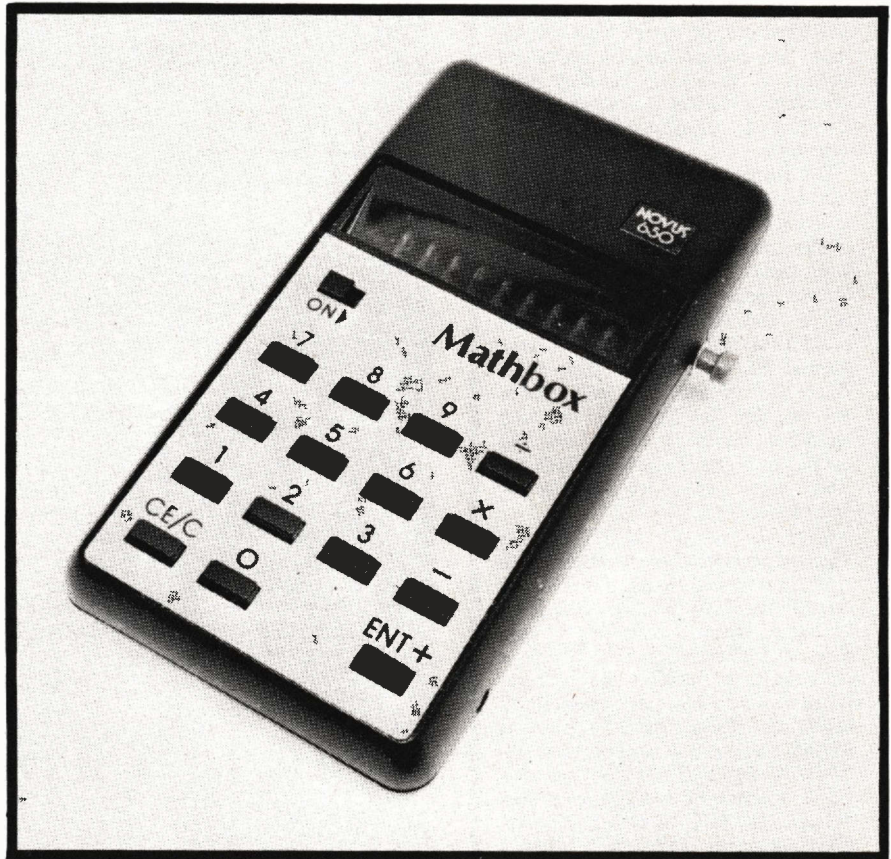

The additional electronics for the stopwatch is all mounted on a separate printed-circuit board which is a very tight fit in the calculator. Soldering to the pins of the calculator IC is also required and unless you have previous constructional experience, especially with soldering, do not attempt this project.

CONSTRUCTION

Due to the unusual nature of this

project the constructional procedure given is much more detailed than usual. The constructor is well advised to follow the following steps carefully.

(a) Disassemble the calculator by removing the battery and the four screws that hold the case together.

(b) Remove the external power socket and disconnect the leads from it to printed-circuit board. Take note

(Text continued on page 50)

SPECIFICATION

Maximum Reading 9999.99 sec (2 hours 46 mins 39.99 secs)
Resolution 0.01 secs
Accuracy (typ) $\pm 0.2\%$
Mode — accumulating type, single button start/stop, separate button for clear.
Calculator.
Six digits, four functions, reverse Polish fixed point.

CALCULATOR STOPWATCH

HOW IT WORKS.

With the standard calculator the keyboard controls a three-line by six-line matrix, that is, a calculator key when pressed joins one of three pins, of IC3, to one of six other pins. This gives a maximum of 18 possible combinations of which only 15 are used. The 6 lines are both input and output of the IC, that is they drive the display via IC4 as well as passing keyboard commands to the calculator.

The stopwatch is controlled by an additional push button, which in effect stops and starts the calculator, whilst reset is performed by the front-panel 'clear' key. The push button operates a flip flop formed by IC1/1 and IC1/2. The capacitors around the flip flop change it from a normal RS type to a toggle type. Diode D3, capacitor C4 and resistor R5 set the flip flop into the stop condition on initial switch on. The output of IC1/1 is at zero volts in the 'stop' state and at +9 volts in the 'run' state.

When the output of IC 1/1 goes high capacitor C8, together with R12, provides a 10 ms pulse to the control input of IC 2/1. This is an analogue switch across the '1' key. Thus the closure of this switch is equivalent to pressing the '1' key. When the switch closes capacitor C5 begins to charge via R7. When it reaches about 6 volts (set by R9/R10) the PUT switches on, and C5 is discharged rapidly to a low voltage, the PUT turns off, allowing C5 to recharge. This action takes at place at 100 Hz. The diode D4 is used for temperature compensation. When the PUT fires, terminal 'ag' drops to a low voltage which discharges C6 via D4 and D6. And, although the PUT is on for only a short time, diode D6 isolates C6 allowing it to charge slowly (5 ms) via R11.

The pulse from the PUT is squared by IC 1/3 and is then used to control IC 2/2, which is across the '+' key. The pulse thus causes one to be added to the displayed number 100 times per second.

To operate the calculator, at the rate of 100 pulses per second, it is necessary to disable the calculator debounce circuitry. This is done by IC 2/3, IC 2/4, IC 1/4 and D7. The debounce is disabled only in the 'run' mode, and is still functional in normal calculator operation.

Diode D5 and capacitor C7 decouple the control circuitry from the calculator, as the high peak currents drawn can result in a two-volt ripple, on the nine-volt supply, which otherwise would upset the timing.


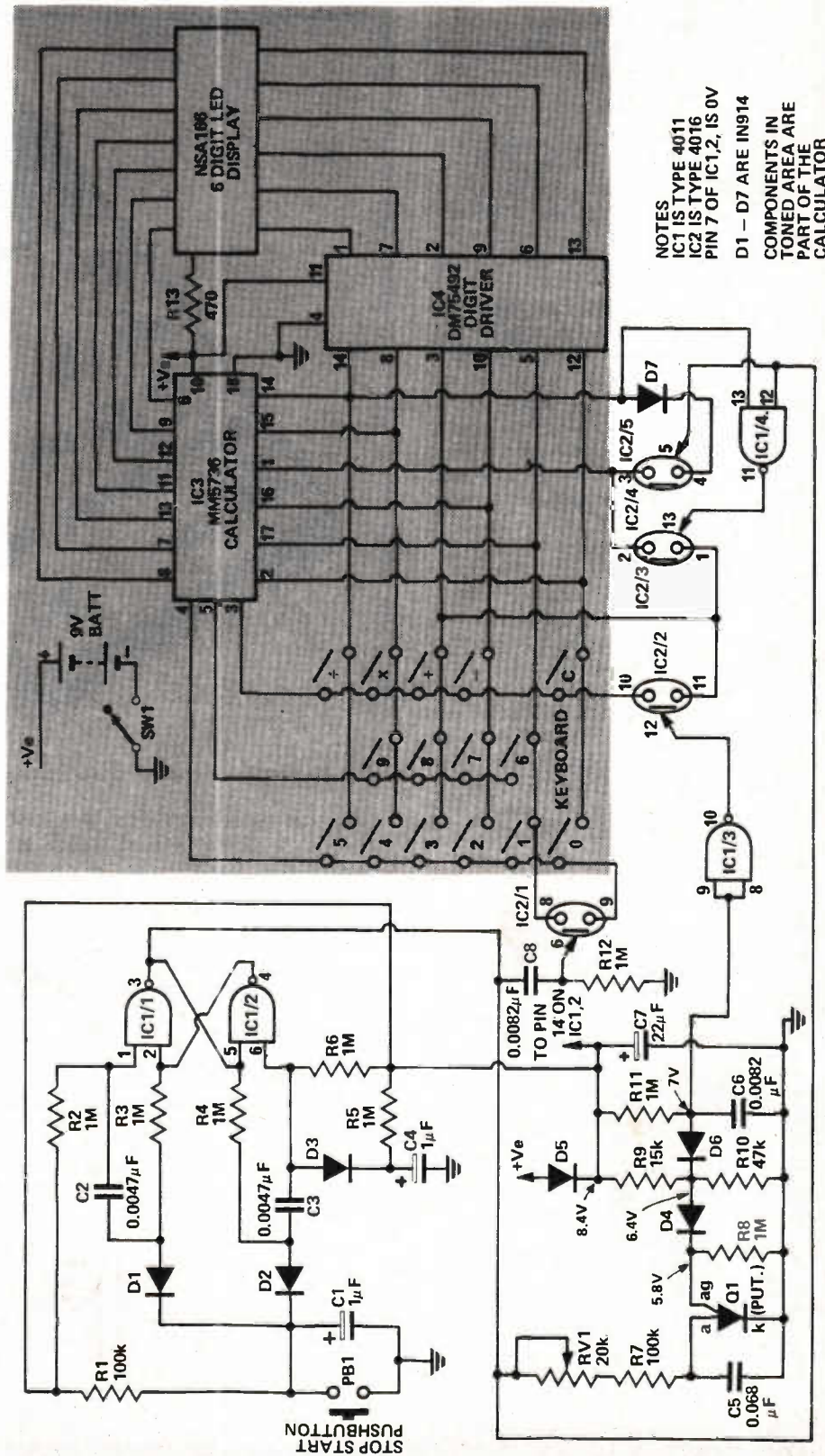


Fig. 1. Circuit diagram of the complete stopwatch. Calculator parts are shown in the shaded area.

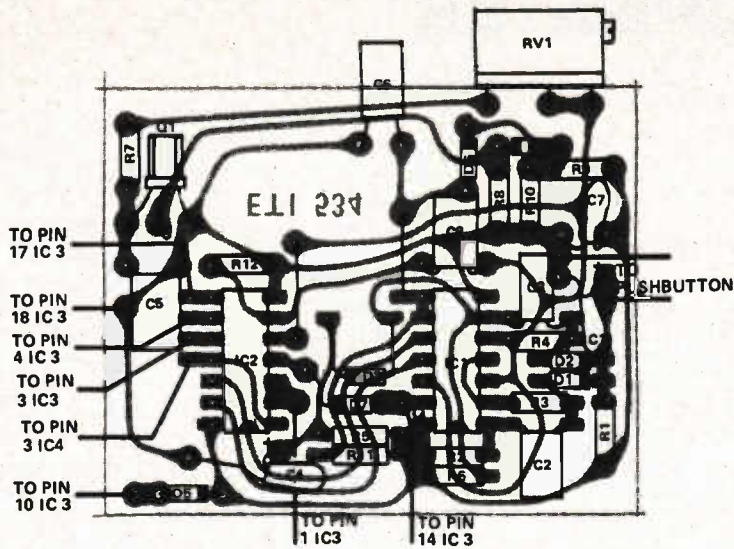

PARTS LIST — ETI 534

- R9 Resistor 15 k ¼ W 5%
- R10 " 47 k " "
- R1,7 " 100 k " "
- R2,3,4,5 " 1M " "
- R6,8,11,12 " 1M " "
- R13* part of calculator

RV1 Trim potentiometer 20 k 20 Turn type 84 (Morganite)

- C2,3 Capacitor 0.0047 µF polyester
- C6,8 " 0.0082 µF " "
- C5 " 0.068 µF " "
- C1,4 " 1 µF Tag tantalum
- C7 " 22 µF 16 V Tag tantalum


D1-D7 Diode IN914 BA318 or similar

Q1 Transistor 2N6027 or similar

IC1 Integrated Circuit 4011 (CMOS)
IC2 " 4016 (CMOS)


Small push button
PC Board ETI 534
Calculator NOVUS 650

Fig. 3. Component overlay.

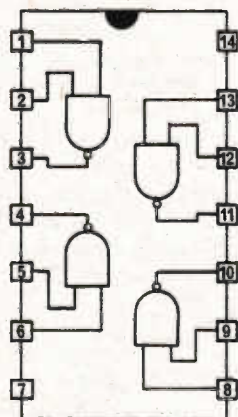

**4011
QUAD 2 INPUT
NOR GATE**


INPUTS		OUTPUTS
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

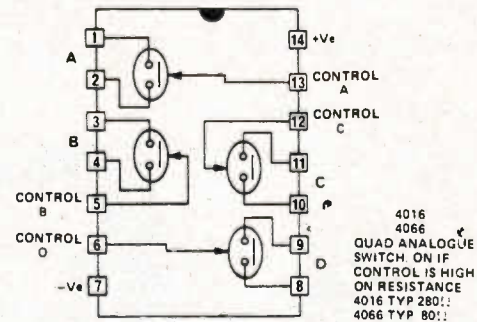

4016
4066
QUAD ANALOGUE
SWITCH ON IF
CONTROL IS HIGH
ON RESISTANCE
4016 TYP 280Ω
4066 TYP 80Ω




2N 6027

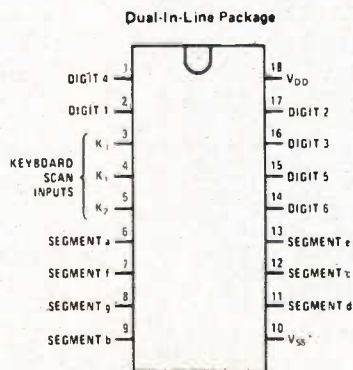


*V_{SS} always must positive supply

MM5736N

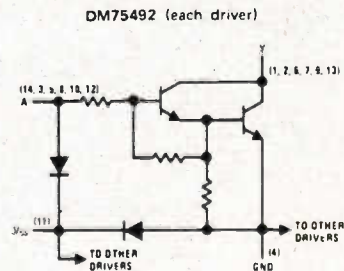

DM75492 (each driver)

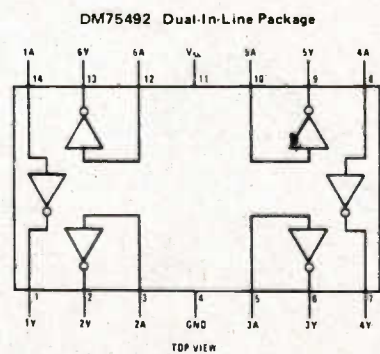

DM75492 Dual-In-Line Package

Fig. 2. Component connections.

CALCULATOR STOPWATCH

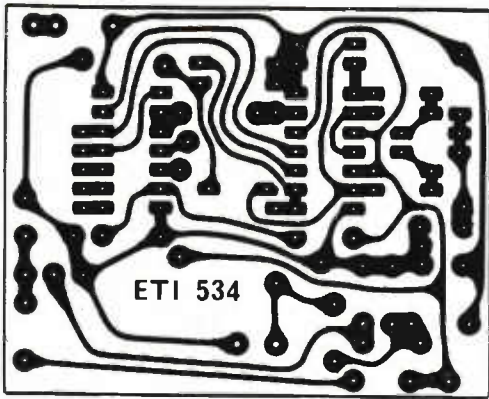


Fig. 4. Printed circuit board layout. Full size 64 x 52 mm.

of the position of these leads as they must be replaced later.

(c) The new pushbutton for the stopwatch must now be mounted into the back cover. The photograph shows the approximate location of this button. Note that the web of plastic, between the battery compartment and the calculator housing, must be cut away on the right-hand side so that the

push button may be fitted. To determine the correct position, temporarily reassemble the calculator, without screws. The correct location can now be determined as the button goes between the display board, the calculator board and the battery (yes there is space!)

(d) Due to the curved case of the calculator we did not use the normal

mounting method for the push button, but just drilled and filed a hole just large enough to allow the push button to cut its own thread in the plastic. It may also be necessary, however, to epoxy the button into position.

(e) Assemble the printed-circuit board, ETI 534, as shown in the component overlay. The components must be positioned as shown, as the board fits between the calculator board and the keyboard and space is very limited

(f) Attach thin insulated wires to the points shown on the overlay and leave them about 75 mm long.

(g) To obtain a little more space, trim all component leads on the back of the calculator board, including those of the calculator IC, as close to the board as possible. Now cut the printed-circuit track on both sides of pin 1 of the MM5736 calculator IC (pin 1 is the pin next to the ● mark) Using a single strand of flexible wire rejoin the tracks on both sides of pin 1, leaving pin 1 isolated.

(h) Position the control board, ETI 534, alongside the calculator board (see photo). Due to space limitations the wires from the control board have to soldered directly onto the pins of the calculator ICs.

(j) Check very carefully the point to which each wire must be connected, cut it to length (not too long), and solder it directly to the specified pin. The ICs are numbered anticlockwise from the '●' mark.

(k) Reconnect the power wiring from the external socket.

(l) Connect the push-button switch.

(m) Check the calculator before final assembly as follows:-

Connect the battery and switch on.

Clear the display and check all keys and calculator functions.

Clear the display

Press the push button once. The calculator should now count up by ones at 100 times per second.


(n) If a frequency counter or an oscilloscope is available connect to the junction of R11 and C6 and adjust for 100 Hz. If an oscilloscope is used sync the cro from the mains and beat the 100 Hz against that.

(p) Fold the control board on top of the calculator board making sure that none of the leads is on top of any of the ICs thus preventing the board from going right down.

(q) Cut a small hole in the side of the case to allow access to RV1.

(r) Assemble the calculator completely again making sure that the leads do not foul anything and that the calculator fits together without

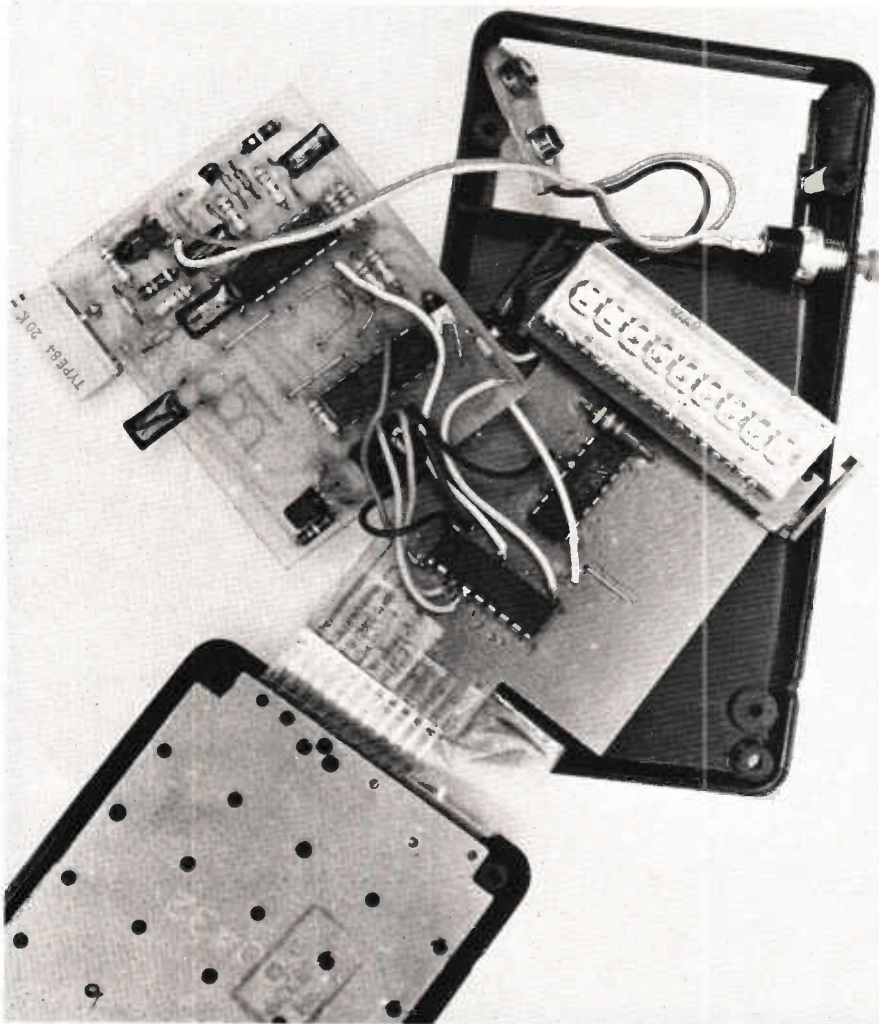The calculator as modified and before final assembly.



needing to be forced.

(s) Check the accuracy of the stopwatch by timing, over a long period, using a known accurate source (eg telephone time service) and make successive adjustments of RV1 to give correct results.

USING THE STOPWATCH

The conventional stopwatch has a single button which starts, stops, and resets, the timing. The ET1 stopwatch, on the other hand, uses the side button for start/stop and the existing CE/C key for reset.

This configuration allows the stopwatch to be used for applications where accumulative timing is required. For example where three separate runs must be timed for a total time, the stopwatch is not reset between runs but merely started and stopped for each run.

A further advantage is that timing may be commenced from a reading preset by the keyboard. This is done by first clearing the display and then entering the starting time in one-hundredths of a second. If the '+' button is now pressed before starting, the stopwatch will count up from the entered time, whereas if the '-' button

Special Offer

STOPWATCH

National Semiconductor, Applied Technology, and Dick Smith Electronics have jointly arranged to supply a complete kits of parts for this project at the extremely low price of \$16.75 (including postage and packing).

This price includes the Novus calculator itself, a special thin printed circuit board and all components.

The kits are available from: —
Applied Technology Pty Ltd,
109-111 Hunter St, Hornsby, NSW. 2077.

Dick Smith Electronics
182 Pacific Highway, Gore Hill, NSW 2065.

is pressed the stopwatch will count down from the previously entered time to zero.

When using the stopwatch be careful

to hold it in such a way that accidental pressing of keys is avoided, as spurious keyboard entries will result in an erroneous reading.

Ideal Xmas Gift:—

BUILD YOUR OWN 2-IN-1 CALCULATOR



It's fun!

Build this Heathkit battery-operated portable calculator. Comes with separate battery charger plus tailored executive desk set with built-in charger, note pad and Schaeffer pen. Complete assembly instructions included.

SPECIAL OFFER \$32.40
complete kit. Normal price \$89.95.
Plus \$3.60 tax if applicable.

Check the functions. Nickel-cadmium batteries give five to eight hours' use between charges. Unit can be left connected to desk set charge for indefinite operation. 8 digit capacity. 4 arithmetic functions. Full floating decimal. Constant key. Negative answer indicator. Battery saver circuitry. Low battery indicator.
And best of all — the calculator you build yourself. is the calculator you service yourself!

**ORDER BY COUPON OR COME
TO OUR SHOWROOM NOW!**

300 other kits: call & collect your free 80 page catalogue.

PLEASE SEND ME:

Heathkit electronic calculator kit IC-2009.
Cheque/money order for \$ enclosed.

NAME

ADDRESS

P/CODE



HEATHKIT KIT
CENTRE

119 Oenmark St., Kew, Vic. 3101. Phone 862 1166

DESOLDERING



**FAST
SAFE
EASY**

with **Soder-Wick**

Soder-Wick is a specially treated copper braid which soaks up molten solder like a sponge. Desolders a P.C. pad in a second or so: acts as a heat sink to protect circuits and components.

1. Hold Soder-Wick on termination with hot soldering tip. Wicking action soaks up solder.

2. Remove tip and braid. Termination is left clean and free of solder.



In a range of sizes from your wholesaler or

**ROYSTON
ELECTRONICS**

02-709 5293
03-848 3777

RE475

IMPORTERS OF ELECTRONICS! ARE YOU PAYING CUSTOMS DUTY UNNECESSARILY?

If you are not aware of the intricacies of the Australian Tariff, the Customs By-Laws and Customs requirements you could well be paying duty unnecessarily on your products.

We offer you expert advice in all Tariff matters including —

- Tariff Classification
- By-Law submissions
- Valuation and Dumping
- Invoice and Documentation requirements
- Industries Assistance and Temporary Assistance Inquiries
- Customs Clearances


For further information contact:

**TREVOR WALLIN,
WALLIN MERRELL
ASSOCIATES PTY LTD,
TEL: (02) 212-4133.**

COLOR BUYING TV RENTING GUIDE

- Why Pal?
- What size?
- Buy or rent?
- Local or import?
- Installing your set
- Problems — problems

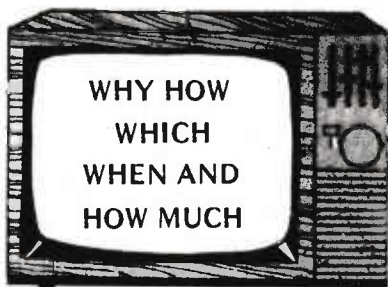PLUS — chance to win magnificent HMV colour TV.



All in COLOR TV GUIDE — ON SALE NOW —
ALL MAIN NEWSAGENTS \$1.00
(recommended retail price).

AT LAST!

THIRTY FIVE SIMPLE PROJECTS IN ONE GREAT VOLUME! PLUS A COMPLETE BEGINNER'S GUIDE TO PROJECT CONSTRUCTION.



ON SALE NOW AT ALL NEWSAGENTS OR DIRECT FROM ELECTRONICS TODAY INTERNATIONAL, 15 BOUNOARY STREET, RUSHCUTTERS BAY, NSW 2011. \$2.00 (plus 40c POSTAGE)

All Prices slashed for Christmas & New Year

MS COMPONENTS

(ELECTRONICS) PTY. LTD.

95-97 REGENT ST., REDFERN N.S.W. 2016
P.O. Box 156 REDFERN 69-5922

HOURS OF TRADING:
MON - TUE - WED & FRI: 9am-5:30pm. THURS: 9am-7pm. SAT: 9am-1pm. SUN: 10am-1pm.
C.O.D.'s: Please add \$2.40 to posting fee. NO ORDERS UNDER \$3.00 accepted. For replies please send S.A.E. Post and Packing 50c where not included in price. PLEASE PRINT YOUR NAME & ADDRESS ON ALL ORDERS AND CORRESPONDENCE.

THE GREAT NAME FOR ELECTRONIC COMPONENTS IN AUSTRALIA



NEW
TRIO
DIGITAL MULTIMETER
MODEL - 703

The latest piece of famous TRIO-KENWOOD GROUP - Housed in handsome case. DC voltage range: 2v-20v - 200v-1Kv. AC voltage range: 2v-20v - 200v-350v. D.C. current range: 200 mA. Resistance range: 200 2K - 20K - 200K - 2M - 20M. Input circuit fully protected against damage due to excessively high DC voltage (up to 100v RMS) & AC voltage (up to 400v RMS) (FULLY GUARANTEED). ~~SLASHED FROM \$136.00~~ to \$135.00 P&P \$3.00. All States.

THE WATTMASTER STEREO CASSETTE DECK WITH DOLBY SYSTEM.

15 transistors 10 diodes. A really handsome addition for your stereo system. Power source: AC 240v 50Hz. Max. power consumption: 5W. Output power: 750 mV RMS per channel. Frequency response: 60-14 kHz (chrome type), 60-10 kHz (normal type). Must be heard to be believed.

NEW
M.S.C. price only ~~\$152.95~~
NOW ONLY \$138.95
P&P \$5.00 all States.

THE FAMOUS "ETONE" HIGH PERFORMANCE SPEAKERS



NOW AVAILABLE

15" Model 451 100W rms 40-5 kHz	\$92.00
15" Model 467 160W rms 50-4 kHz	\$138.00
15" Model 474 160W rms 30-4 kHz	\$135.00
15" Model 475 200W rms 30-3.5 kHz	\$144.00
12" Model 225 Hi-Fi woofer 80W rms	
20-4 kHz	\$43.00
12" Model 231 60W rms 40-7 kHz	\$41.00
12" Model 511 40W rms 40-8 kHz	\$28.00
12" Model 518 Hi-Fi woofer 5W	
20-4 kHz	\$31.00
12" Model 246 twin cone 80W rms	
40-12.5 kHz	\$54.00
12" Model 365 130W rms 30-6 kHz	\$114.00
12" Model 366 twin cone 130W rms	
30-12.5 kHz	\$129.00
12" Model 367 130W rms 40-10 kHz	\$125.00

All the above speakers carry a 5 year warranty: please add \$8.00 for P/P. Refund will be given if P&P is less than this amount.
5% off for quantities of 10 and over.

SPECIAL OFFER CONDUCT-O-TAPE
Twin invisible wire. Paper-thin, pressure sensitive invisible flat tape conductor for low voltage use. Eliminates ugly cord. Can be covered with paint or wallpaper without affecting efficiency. For bells, intercoms, alarms, loudspeakers.
100 Feet for only ~~\$2.50~~ **\$2.25** P/P 50c

NEW
'INTERNATIONAL TIME' DIGITAL CLOCK KIT.

A new kit with extraordinary efficiency. Easy to build, and complete with all necessary components, including: 4 1/2" Digit fluorescent readout (blue), Texas TS3834 chip, speaker, ready etched P.C. board, switches, wire and screws etc. Also has snooze alarm and seconds readout. Supplied with handsome moulded ready-to-fit case.



M.S.C. PRICE ONLY \$36.00 P&P \$2.00.

SPECIAL

AN IDEAL GIFT. The EXPO DX-2020 TRANSISTOR STEREO AMPLIFIER. Specifications: 20 Watts RMS per Channel. FREQUENCY RANGE: 20-30 kHz. Channel Separation better than 45 dB. **NORMAL PRICE \$145.00 NOW FROM M.S.C. \$110.00. P&P \$5.00.**
SPECIAL PACKAGE DEAL: The above PLUS the Wattmaster (as shown alongside) ONLY FOR \$245.00 the pair. (Freight COMET C/F).

SCOOP PURCHASE OF DIGITAL CLOCK MECHANISM'S

All new and unused... fully imported. Complete with Time-setting control, denoting HOURS, MINUTES & SECONDS. Clearly visible figures of 5/16" Ht. Also incorporated are two remote micro-switches for setting Alarms, Radio's or Television etc. With 240V 50Hz Motor.
AMAZING VALUE AT \$10.25 each
For 1 month only **\$9.85 P&P \$1.25**

7 TRANSISTOR BY BENDIX + 2 DIODE RADIO

Completely ready wired with volume control and switch. Large tuning dial and complete with 3 1/2" 8 ohms .6 watt speaker. Battery container included. (Batteries not included) - **READY TO GO!!**
\$3.85 EA
M.S.C.'s CRAZY PRICE!! PLUS P&P \$1.00

2 FOR \$6.50 P&P \$1.50

NEW
SCOPE

The SCOPE CORDLESS 60 WATT SOLDERING IRON. The GO ANYWHERE soldering pistol that heats in 6 seconds and cools rapidly when trigger released. Runs on 2 Nickel Cadmium batteries - delivers an amazing 60 watts of soldering power - capacity is around 100 typical electrical connections - 200 to 400 joints have been achieved with light gauge wire while heavier joints mean proportionately less capacity - overnight recharge from car or power point. **DESIGNED FOR TRADESMEN, HOBBYISTS and HANDYMEN** who can't always bring the job to the workbench.
ONLY \$36.00 each P&P \$2.50.


Accessories to suit:
Auto cigarette lighter adaptor \$5.95 P&P 75c; 240 volt Power adaptor \$9.75 P&P \$1; Stepdown transformer \$13. P&P \$2.

ANNOUNCING OUR NEW QUEENSLAND AGENT:

We have pleasure in appointing the following, to represent us in Queensland, with effect from early February 1976.
R.F. & L.D. HOWE,
P.O. Box 186,
Wynnum Central, Qld. 4178

NEW

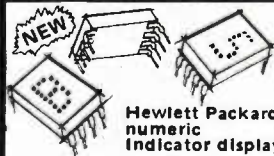10 position B.C.D. THUMB WHEEL SWITCH Size: 1 1/10" x 1 1/2" x 3/10". Moulded grey. Fixing centres approx 35mm. Normally \$4.50 each **M.S.C.'s SPECIAL OFFER \$2.25 each or 10 for \$21.00 P&P single 30c, 10 for 75c.**



DESCRIPTION
The HP 5082-7300 series solid state numeric indicators with on-board decoder/ driver and memory provide a reliable, low-cost method for displaying digital information. The 5082-7300 numeric indicator decodes positive 8421 BCD logic inputs into characters 0-9, a "." sign, a test pattern, and four blanks in the invalid BCD states. The unit employs a right-hand decimal point. Typical applications include point-of-sale terminals, instrumentation, and computer systems. Supply Voltage 4.5 - 5.5V. Size: 2 1/4" x 2 9/16".
M.S.C. SPECIAL PRICE \$12.00 ea. Post Free.


SCOOPACS

MS 1	25 Assorted NPN & PNP SILICON TRANSISTORS. All marked and unused. Not rejects. Very useful assortment. \$2.00 P&P 25c.
MS 2	GOLDRING DC-DC Car converter. High current at 800 mA. Output 6V - 7.5V - 9V. Complete with 4 way output plug. Only \$4.95 P&P 50c.
MS 6	200 ASSORTED 1/4 - 1/2 - 1 & 2 watt resistors 10 & 20%. 200 for \$2.00 P&P 50c.

WIGO ACUSTIC HI-FI LOUDSPEAKERS FROM GERMANY

A top-quality range of respected loudspeakers from Germany, Wigo (pronounced "Vee-go") are now available in Australia as separate component speakers or as complete speaker systems in walnut finish cabinets.

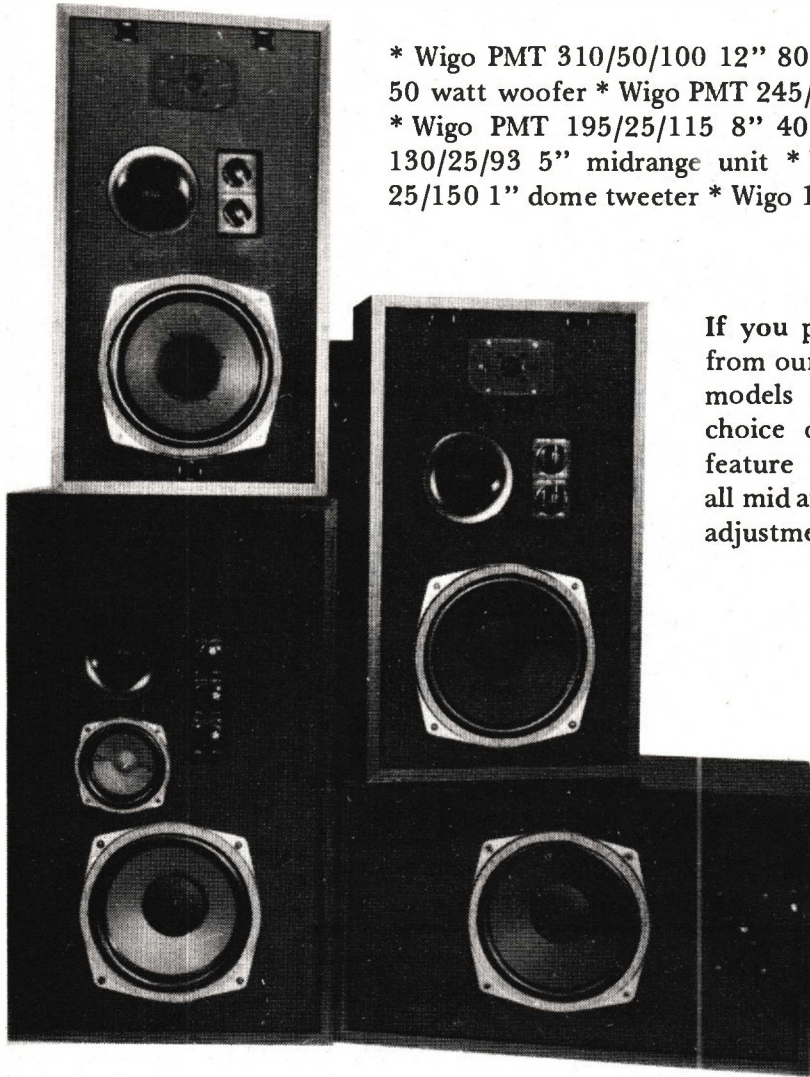If you're a handyman, choose from this large range of loudspeaker units and build your own loudspeaker system.



* Wigo PMT 310/50/100 12" 80 watt woofer * Wigo PMT 245/37/100 10" 50 watt woofer * Wigo PMT 245/25/115 10" 40 watt bass/midrange speaker * Wigo PMT 195/25/115 8" 40 watt bass/midrange speaker * Wigo PMM 130/25/93 5" midrange unit * Wigo 37/110 1½" dome midrange * Wigo 25/150 1" dome tweeter * Wigo 19/135 ¾" super tweeter.

If you prefer to buy ready made systems Choose from our new range with walnut finish cabinets. All models have removable front grille cloths with a choice of patterns. Three and four-way systems feature constant impedance volume controls on all mid and high range loudspeakers to allow suitable adjustment to suit listening area acoustics.

Wigo M102 2-way 40 watt. 8" Bass/mid-2" tweeter. 19" (H) x 10¼" (W) x 9¼" (D)

Wigo M132 2-way 40 watt 10" Bass/mid - 1" dome 25" (H) x 14½" (W) x 9¼" (D); Wigo M133 3-way 40 watt 10" Bass - 1½" dome - ¾" dome 25" (H) x 14½" (W) x 9¼" (D); Wigo M203 3-way 50 watt 10" Bass - 1½" dome - ¾" dome 25" (H) x 14½" (W) x 12½" (D); Wigo M254 4-way 50 watt 10" Bass - 5" mid - 1½" dome - ¾" dome 29" (H) x 17" (W) x 12" (D).

Wigo M504 4-way 80 watt. 12" Bass - 8" mid - 1½" dome - ¾" dome. 37" (H) x 19¼" (W) x 15¼" (D).

Challenge

HI-FI STEREO PTY LTD

96 PIRIE ST.
ADELAIDE

STH. AUST. 5000

PHONE: 223 3599

RF SIGNAL GENERATOR

simple unit for servicing AM receivers



ETI PROJECT
129

AN RF SIGNAL generator is an invaluable instrument for AM radio servicing and alignment — it greatly simplifies alignment and allows each stage to be checked for gain and frequency response.

Three types of signal are required for these purposes. Firstly, we require an audio signal to check that part of the receiver from the volume control (after the detector) to the speaker. Secondly, we need a modulated RF signal at 455 kHz (430 to 480 kHz available for non-standard receivers) for checking and aligning IF stages, and lastly, we need a modulated RF signal in the range 500 to 1600 kHz to check out the RF amplifier and converter.

In addition the level of the generator output should be adjustable so that AGC action may be checked out, and so that optimum levels may be chosen for servicing and gain checks. All the

above requirements are met by the ETI 129 generator and, since only one of the available signals is used at any one time, a common level control is used for all these outputs.

In our generator the provision of IF frequencies from 430 to 480 kHz, as well as catering for non-standard receivers, allows receiver IF selectivity to be checked.

CONSTRUCTION

The prototype instrument was mounted in an aluminium box having external dimensions of 145 x 115 x 90 mm. Layout of the circuitry is important and for this reason the printed-circuit board layout provided should definitely be used. Take care when assembling components to the printed-circuit board to correctly orientate capacitors C9, C11 and C15, transistors Q1 to Q4 and diode D1.


The variable capacitor is mounted onto the component side of the printed-circuit board but spaced from it by about 2 mm (an oversized nut may be used). The mounting of the board and variable capacitor assembly to the front panel and reduction-drive assembly may best be understood by referring to Fig. 3. Note that the board is mounted by four standoffs and that rubber grommets are used to allow the board to move slightly — for this reason the screws should not be tightened too much. This method is used to avoid the expense of using a flexible drive to the variable capacitor.

The six-to-one slow-motion drive is mounted to the front panel by two 15 mm long bolts. The drive is spaced back from the front panel by 4 mm long spacers.

The remaining controls are mounted straight onto the front panel as shown in the photograph.

RF SIGNAL GENERATOR

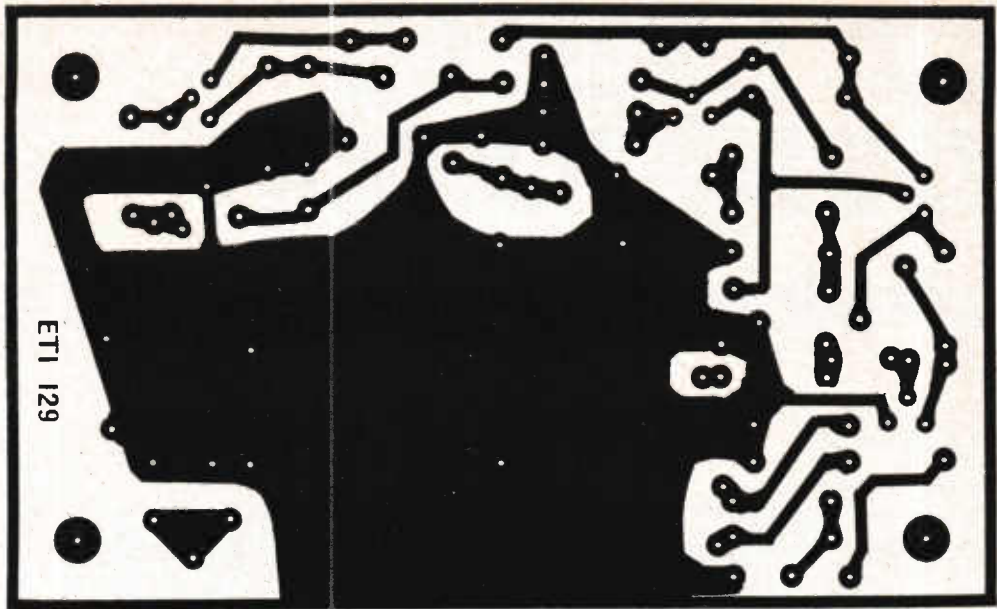Scotchcal front panels, ready to stick on are available from Electronics Today at \$3.00 each. Send stamped addressed envelope — size at least 150 x 120mm. Address to Scotchcal Offer, Electronics Today, 15 Boundary St, Rushcutters Bay, NSW 2011.



Printed-circuit board layout. Full size 129 x 80 mm.

CALIBRATION

High Range. Using a conventional AM receiver tune to a station at the top end of the frequency band. Set the pointer of the RF generator to indicate the frequency of the station being received and couple the

generator to the receiver. Adjust capacitor C3 until the signal from the generator can be heard interfering with the station. This will take the form of a whistle which, as C3 is tuned, will go from a high frequency to a low frequency and then

back to a high frequency again. The correct tuning point is where the frequency is at its lowest, i.e. in the middle. The level of the generator signal may have to be increased to obtain the correct point with accuracy. This procedure is called

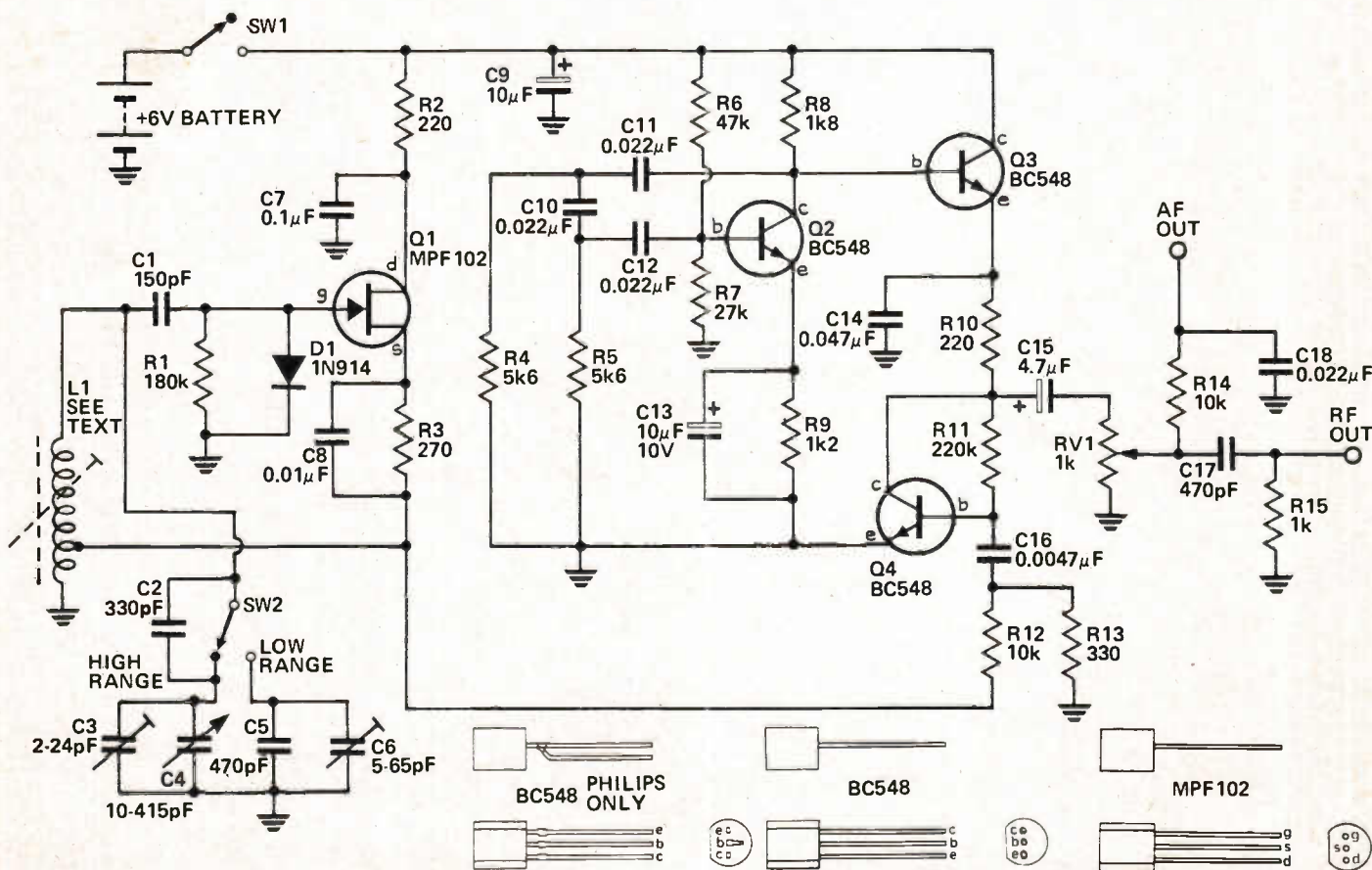


Fig. 1. Circuit diagram of the modulated RF generator.

EDGE ELECTRIX YOUR ELECTRONIC WORLD

31 BURWOOD ROAD, BURWOOD, N.S.W. 2134 TEL: 747 2931


ELECTRONIC KITS ★
CRYSTAL RADIO KIT **4.50**

No soldering — easy to construct. Ideal for Junior to learn about crystal radio.




SUPER
2 TRANSISTOR RADIO KIT

\$6.60

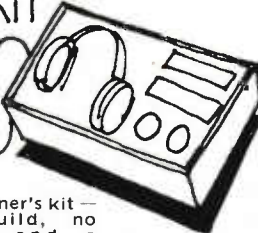

A great beginner's kit — fun to build, no soldering and a practical gift.


20 SIMPLE PROJECTS IN ONE KIT

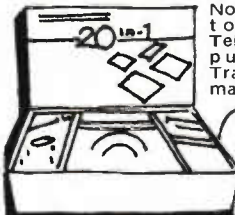

No soldering — no tools • Morse Telegraph set • Water purity tester • Transistor radio and many many more.

\$12.40


65 IN ONE KIT ONLY \$19.50

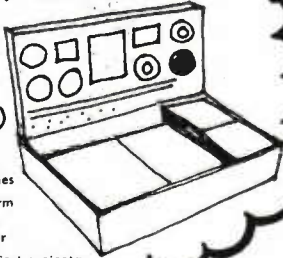

- Transistor Radio
- Harpsicord Chimes
- Burglar Alarm
- Water Level Alarm
- Fire Alarm
- Electric Siren
- Solar Light Meter

Plus 58 other practical projects.

150 IN ONE KIT

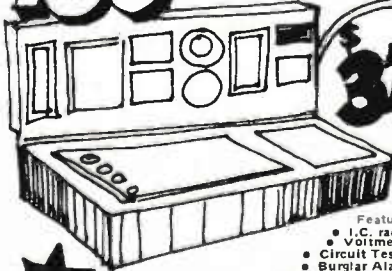


\$37.50

- Features
- I.C. radio
 - Voltmeter
 - Circuit Tester
 - Burglar Alarm
 - Liquid Purity Tester
 - IC Record Player Amp
 - Morse Code Light Signal

Plus 143 more great projects.

Coral
SPEAKER KITS

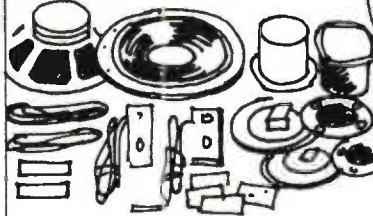

Why pay \$200 to \$300 for a 4 or 3-way pair of top class speakers? Here's what to do — buy the kit (pair) complete with all bits and make or buy your own cabinets. They really sound good.


8" 3 way **\$33.00**
10" 3 way **\$55.00**
12" 4 way **\$77.00**

PHILIPS GREAT KITS

KIT NO 4A
2 x AD 8066 W8
2 x AD 5060 SQ8
2 x AD 130T8
2 x 3 way Cross Over


\$120.00

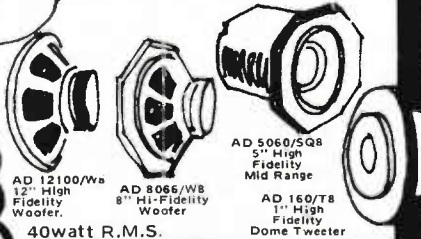KIT NO 7A
2 x AD 12100 W8
2 x AD 5060 SQ8
2 AD 160 T8
2 x 3 way Cross Over



AD 12100/W8 12" High Fidelity Woofer.
AD 8066/W8 8" Hi-Fidelity Woofer.
AD 5060/SQ8 5" High Fidelity Mid Range.
AD 160/T8 1" High Fidelity Dome Tweeter.
40watt R.M.S.

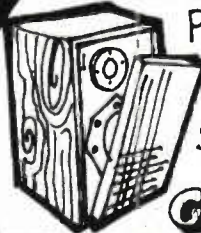PHILIPS 8" 2WAY SPEAKER SYSTEM WITH CABINETS AD8K40



\$109.00 GREAT

All you need is a screwdriver to assemble this pair of Philips Speakers, 12" x 18" cabinets (supplied — 40 watts RMS a side, 8" Woofer and a Philips dome for each. The sound? everyone knows how good Philips speakers are!

MAIL ORDER SPECIAL

E.A. & ETI KITS
E.A. FM & AM TUNER \$135.00. With front panel but less case.

ETI KIT 440
\$99.00. Including metal work.

CROSS HATCH GENERATOR
\$22.00. Without front panel.

SPEAKER SPECIAL
Magnavox 830 \$13.95.

INNERBOND \$1.80 yd.

SEMI CONDUCTOR SPECIALS

2N3055
1 OFF \$1.10 each
10 to 99 .95c each
100 .80c each.

NE555 .70 each
MW 741 DILI 72c ea.
LM309 \$1.20 ea.

MILUX CAR RADIO
Manual 6 Transistor with inbuilt speaker — lock aerial \$21.50.

MICROPHONE SPECIAL
DM17 DYNAMIC
Suits most tape recorders. \$3.80.

PLEASE RUSH ME

I ENCLOSE A CHEQUE FOR +\$5. P&P
(BALANCE OF P&P TO BE RETURNED)

PLEASE FORWARD INFORMATION ON

NAME

ADDRESS

RF SIGNAL GENERATOR

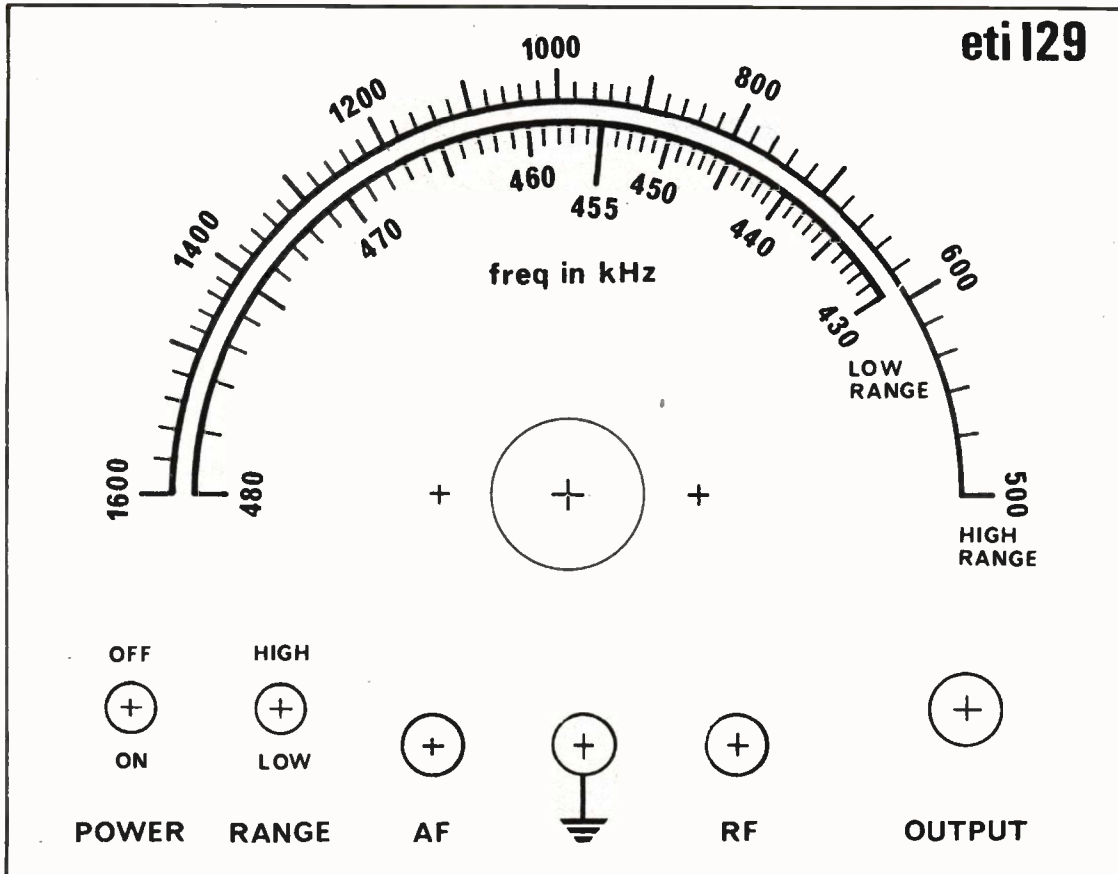


Fig. 4. Front panel artwork. Full size 148 x 116 mm.

COUPLING TO RECEIVER

Method 1. To ferrite rod coil. Connect one end of a length of ordinary hook-up wire to the RF OUT jack and then wrap about two turns of the other end of the wire around and over the aerial coil on the ferrite rod.

Method 2. To an IF amplifier. Connect a wire to the RF OUT jack and to its other end connect a 0.001 capacitor and a 1 k resistor in series. To inject the signal into the IF stage just connect the free end of the resistor to the base of the IF stage transistor.

In both the above methods if insufficient signal level is available an earth connection may also have to be made between the generator and the receiver.

Method 3. Audio testing. Use a length of wire as before but with a series capacitor of about $0.47\mu\text{F}$. Note that an earth connection will definitely be required in this case. Once again the best place to inject a signal is straight into the base of the transistor. ●

Internal view of the generator.

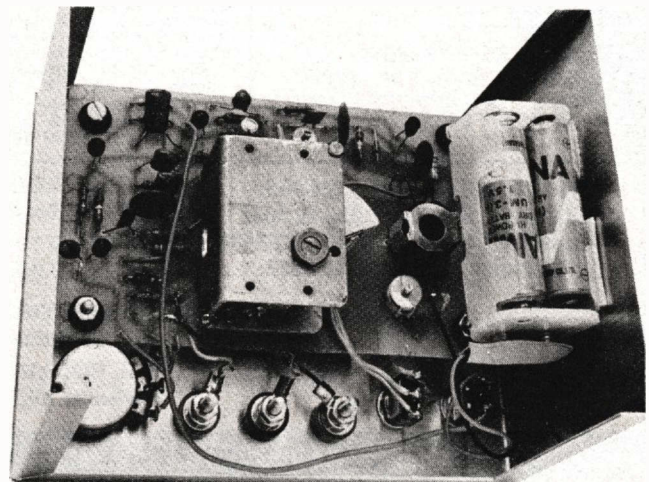



TABLE 1

L1	20 turns 0.5 mm enamelled copper wire tapped at four turns from grounded end.
CORE	Philip potcore P18 series, material 3B7 or 3H1, $\mu_e = 220$. Part No 4322-022 - 24280 or 4322-022-24080
FORMER	4322-021-30270
ADJUSTOR	4322-021-31080
CLIP	4307-021-20000
One each of core, former, adjustor and clip required to assemble one complete coil.	

ELECTRONICS PRICES SLASHED!

- * Top quality components from leading manufacturers
- * Mail orders supplied immediately, ex-stock
- * Available from selected retail outlets (see below).

"ECSTASY" COLOUR ORGANS

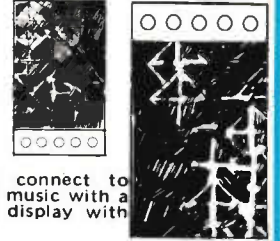

Just plug into mains, connect to speakers and watch your music with a 4 colour multiple light display with control of each channel.

SMALL \$49.50, LARGE \$69.50, P&P \$5.00.

STEREO AMPLIFIERS

	KIT	P&P
5W RMS per channel PM142	\$39.00	\$3.00
15W RMS per channel PM143	\$69.00	\$4.00
25W RMS per channel ETI 440	\$85.00	\$4.00
50W RMS per channel ETI 422	\$115.00	\$5.00

SPECIAL OF THE MONTH
DT1307 - FETVOM
ONLY \$45.00 P&P \$2.50
 Limited stock only

COUNTER-DISPLAY, ETI 533

Runs off 5-15 volts, 1 MHz. maximum counting speed. Three digits.



KIT \$24.00, P&P \$1.50.

CROSSHATCH GENERATOR, ETI 704. # :

Operates from a standard 9V battery, has 75 ohm output,

KIT \$25.00, P&P \$2.50.

DIGITAL DICE

- LIMITED STOCK ONLY

Built and tested, runs off 9v battery

\$7.95 P&P 60c.

LOGIC PROBE, ETI 120

Kit including case, \$13.95. P&P \$1.00.

LOGIC PULSER, ETI 121

Kit including case, \$12.95. P&P \$1.00.

Frequency Counter ETI 118.

As featured in the August issue of this magazine. The ETI 533 is required to be purchased for this unit. Kit includes case and power supply, KIT \$49.50., P&P \$2.00.



DIGITAL I.C.'s

Part No.	Bulk Disc. price	Qty. in pack	Part No.	Bulk Disc. price	Qty. in packs
SD7400	\$3.40	10	SD7483	\$2.50	2
SD7401	\$3.40	10	SD7489	\$2.40	1
SD7402	\$3.40	10	SD7490	\$6.00	10
SD7403	\$3.40	10	SD7491	\$2.25	2
SD7404	\$3.40	10	SD7492	\$3.40	5
SD7405	\$3.40	10	SD7493	\$6.00	10
SD7408	\$3.40	10	SD7495	\$2.50	2
SD7409	\$3.40	10	SD7496	\$3.00	2
SD7410	\$3.40	10	SD74107	\$3.00	5
SD7413	\$4.90	10	SD74121	\$3.40	5
SD7416	\$4.90	10	SD74123	\$4.00	5
SD7420	\$3.40	10	SD74141	\$4.30	5
SD7430	\$3.40	10	SD74151	\$4.30	5
SD7438	\$3.40	10	SD74153	\$4.30	5
SD7440	\$3.40	10	SD74160	\$5.70	5
SD7441	\$3.70	5	SD74161	\$5.70	5
SD7442	\$3.40	5	SD74162	\$5.70	5
SD7446	\$2.75	2	SD74613	\$5.70	5
SD7451	\$3.40	10	SD74164	\$5.70	5
SD7473	\$5.90	10	SD74165	\$2.50	5
SD7474	\$5.90	10	SD74175	\$5.00	5
SD7475	\$4.00	5	SD74192	\$5.00	5
SD7476	\$3.00	5	SD74193	\$5.00	5

FOUR INPUT MIXER

Two 2 mV inputs, two 100 mV inputs with active mixing, built and tested unit. \$35.00 plus P&P \$2.50.

FOUR CHANNEL AUDIO TO LIGHT DRIVER

Just plug into mains, connect to speaker and plug in 4 external coloured lights (not supplied) - Gives you your own Disco show! Built and tested \$49.50 plus P&P \$2.50.

SEMICONDUCTORS

Part No.	Bulk Dis. Price	Qty in Pack
IN914 Small signal diode	\$2.00	25
EM404 400V, 1A	\$3.25	25
EM410 1000V, 1A	\$5.00	25
A15A 100V, 3A	\$6.00	10
NL 5023 Red LED with mounting	\$5.00	25
MB4 400V, 1A bridge	\$4.60	4
MB10 1000V, 1A bridge	\$5.80	4
PA40 400V, 10A, bridge	\$5.60	1
PB40 400V, 25A, bridge	\$6.30	1
DL727 .3" 7 segment read-out	\$2.30	1
DL747 .6" 7 segment read-out	\$2.90	1
2N2646 Unijunction	\$5.60	4
2N6027 Programmable Unijunction	\$4.40	4
C106D1 400V, 4A. Thyristor	\$5.60	4
C122D 400V, 8A. Thyristor	\$7.80	4
C122E 500V, 8A. Thyristor	\$4.80	2
SC141D 400V, 6A. Triac	\$5.20	4
SC146D 400V, 10A. Triac	\$4.40	2
ST2 Diac	\$3.60	5
ST4 Assymetrical Diac	\$4.00	5

Equivalent may be supplied, but in all cases they will have the same specifications and similar style cases. Prices may be slightly higher interstate.

HI-POWER STROBE



Built and tested, simply plug in and use. \$25.50 plus P&P \$2.00

DIGITAL DC VOLTMETER, ETI 117.



Requires ETI 533 display, few resistors, switch and power supply to measure from 1-1000V KIT \$16.00 P&P \$1.

RESISTORS

Value	Bulk Discout price	Quantity in pack
1/2 Watt E12 values, 10 ohm-10 megohm (Code RFH)	\$2.00	100
1 Watt E12 values, 10 ohm-10 megohm (Code RFI)	\$4.75	100
5 Watt wire-wound, .33, .47, .51, E6 values from 1 ohm-4.7 kohm. (Code RFF)	\$2.00	10

NOTE: Mixed value packs of 1/2W, 1W, resistors, ceramics and greencaps are not available. Packs contain one value only. Other components available in any quantity subject to 20% surcharge on quantity not in standard pack. EXAMPLE: 7 double-gang slide pots: Pack of 5 = \$6.00 plus 2 = \$2.40. 20% surcharge on 2 = 48c. Sub-total = \$8.88 plus 10% P&P (88c) TOTAL \$9.76.

THE ELECTRONICS SHOPS:
 9 Young St., Southport, Qld. 32-3632
 23 Russell St., Toowoomba, Qld. 32-6944
 36 Station St., Booval. 82-2322

HI-TEL RECORD BAR:
 Shop 4 Skipton's Arcade, Penrith, NSW
 Shop C Nepean Arcade, Penrith, NSW
 Phone 21-0850

THE ELECTRONIC AND HOBBY CENTRE:
 1168 Gold Coast Highway, Palm Beach, 34 2835

R. LITTLE COMMUNICATIONS:
 20 Bogan St., Parkes, 62 3455

S&P PHOTOGRAPHICS & ELECTRONICS
 26 Queen St., Nambour, 41-1014

A. E. COOLING RADIO & T.V. SERVICE
 6 Trimmer Rd., Elizabeth South, S.A. 255 2249

MAIL ORDER

Add 10% for post and packing, unless otherwise stated.

MOD-AMP

P.O. Box 180, AVALON 2107

RETAIL OUTLETS IN METROPOLITAN AND COUNTRY AREAS NOW BEING APPOINTED - ENQUIRIES WELCOME

Which man are you?



Today's electronic equipment varies widely in its sophistication, and in the demands it makes . . . on soldering equipment, and the man who uses it. Which man are you?

■ Involved with **COMPLEX OR SENSITIVE CIRCUITRY?**

Sophisticated solid state components, multi-layer and high density circuitry as found in colour TV, industrial instrumentation etc. need the controlled temperature, slim profile and high power of the mains voltage **THERMATIC**.



THERMATIC
In-handle temperature control and selection. weight, less cord, 40g (T30)

■ Handle **GENERAL ELECTRONIC EQUIPMENT?**

Radio, stereo, black and white TV service, and general commercial electronics work require fast heat-up and maximum versatility. The **DUOTEMP** idles at soldering temperature, and doubles its power for heavy or sequence soldering.



DUOTEMP
Push button control doubles thermal power weight, less cord, 40g (D30)

■ Keen on **HOBBIES & HANDYMAN JOBS?**


For broken toys, appliances, automotive wiring, door chimes, jewellery, and a hundred jobs around the home, a soldering tool is a must. The inexpensive, single-temperature **STANDARD** tool handles these jobs with ease.



STANDARD
weight, less cord, 36g (S30)

■ Responsible for **HIGH RELIABILITY EQUIPMENT?**

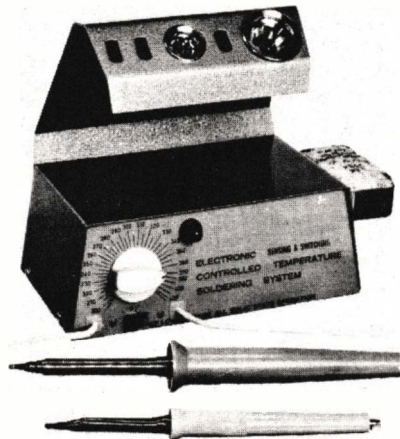Life support, communication, aero-space, weapons etc. make critical demands on solder joints. **ECT SOLDERING STATIONS** provide extremely accurate temperature from direct reading control: low voltage for safety: zero tip potential. Elements, about 4 times normal power, give fast heat up and recovery. The ultimate in accuracy, speed, thermal capacity and component protection.



ECT 6724 SOLDERING STATION

CT7 tool: weight less cord 50g
CT6 tool: weight less cord 23g

Whichever man you are, Adcola equips you better for faster, easier, more reliable soldering . . . and there's an Adcola consultant in each capital city to lend a professional hand.

ADCOLA VIC: 848-3777
N.S.W.: 709-5293
S.A.: 42-6655
QLD: 52-3166
W.A.: 81-5500
MA 752

DESIGN YOUR OWN FM RECEIVER

PART 3

Brian Dance explains . . .

PHASE LOCKED LOOPS are very attractive for use in FM receivers, since they can replace a complete IF circuit and they require no coils. Unfortunately the phase locked loops available until recently have been suitable for communications receivers but not for high fidelity work. However, the recent development of the NE563 device by Signetics has greatly changed the position. The 563 is a new device containing about 180 transistors which can be used in the circuit shown in Fig. 16.

The incoming 10.7 MHz signal from the front-end unit is fed to pin 7 of the NE563. It is then amplified by up to 60 dB in a high gain amplifier/limiter circuit which has a bandwidth of 22 MHz. The output of the limiter at pin 5 has an impedance of about 270 ohms, so the additional series resistor R2 increases this to the value required by the ceramic filter F for correct matching. On the output side of this filter, R1 in parallel with the input resistance at pin 2 (about

1250 ohms) makes a suitable impedance match for the filter.

The 9.8 MHz quartz crystal connected between pins 1 and 16 forms part of a 9.8 MHz local oscillator circuit. The signal from the latter is mixed with the incoming 10.7 MHz and the resulting difference frequency of 900 kHz is fed by an internal connection to the phase locked loop section of the device.

The voltage controlled oscillator of the phase locked loop will free run at a frequency determined by the value of C12. If this free running frequency is reasonably close to the 900 kHz input frequency, the loop will lock onto the frequency of the input signal. The error voltage which keeps the loop in lock will vary with the frequency of the incoming signal. Thus this error signal is the required audio voltage when the incoming signal is a frequency modulated one.

The audio output appears at pin 10 superimposed on a steady voltage. The filter R9-C13 provides the normal

de-emphasis of 50 μ s time constant, whilst R10 and C14 provide some attenuation of RF frequencies. A series capacitor must be employed in both the stereo and monaural output circuits to block the steady voltage at pin 10.

The loop filter connected to pins 13 and 14 controls the bandwidth of the demodulator circuit. The impedance at these pins is typically 6.2 k. If R8 is reduced in value the bandwidth — and hence the noise level at the output — will be reduced, but the centre frequency must then be more carefully matched to the input frequency.

The limiter circuit feeds the stage which provides AGC at pin 4. The variation of the pin 4 voltage with the input signal level is shown in Fig. 17. The limiter also provides muting current to pin 8 where the output impedance is about 20 k. When the potential at this pin falls below about 1.1 V, the circuit is muted. The muting level is set by VR1. The writer has found the action of this muting

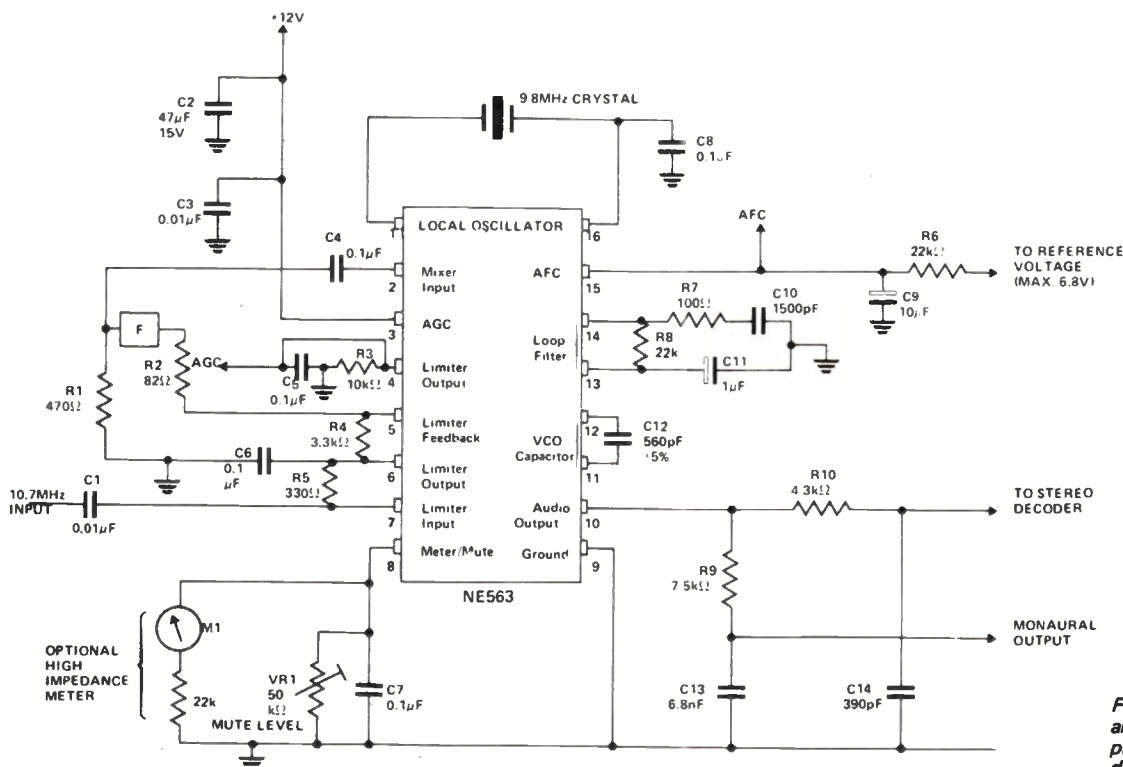


Fig. 16. A typical NE563 amplifier, mixer and phase locked loop demodulator circuit.

AGC OUTPUT VOLTAGE VS SIGNAL INPUT

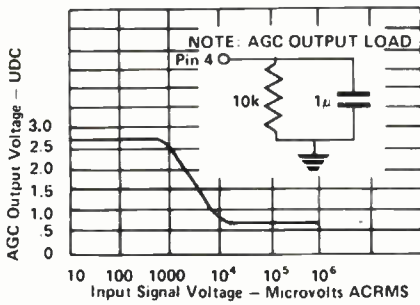


Fig. 17. Typical NE563 AGC characteristic.

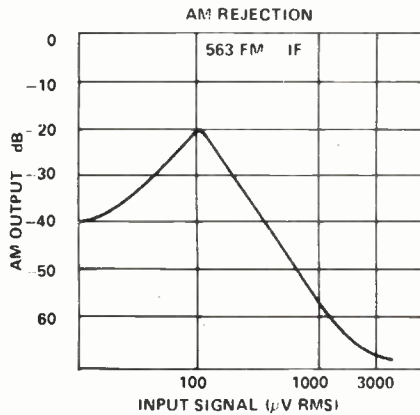


Fig. 18. NE563 AM rejection plotted against input voltage.

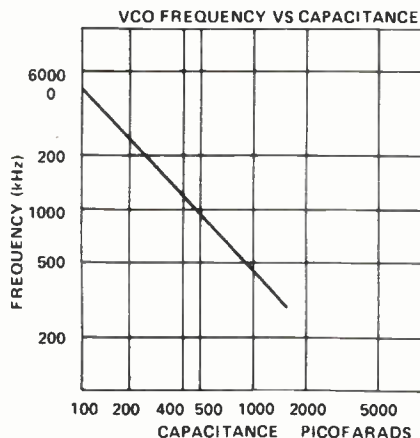


Fig. 19. VCO free running frequency plotted against the capacitance connected between pins 11 and 12.

circuit to be extremely good. Any signal of reasonable strength will raise the potential of pin 8 above 1.1 V when VR1 is suitably adjusted, but inter-station noise is eliminated. If muting is not required, pin 8 may be left unconnected.

A signal strength meter, M1, may be used if desired, but it must have a reasonably high impedance. The readings of this meter vary with the setting of VR1. A meter with a full scale deflection of about 5 V is suitable. The meter deflection is a logarithmic function of the input

voltage over a very wide range (from 10 μ V to at least 0.5 V).

The NE563 requires a power supply voltage in the range + 10 to + 15 V, the current required being typically 38 mA (maximum 42 mA). The power dissipated in this complex device renders it warm to the touch and results in some drift of the centre frequency for the first minute or so after power is first applied; however, this has no effect except when one wishes to receive very weak signals. The internal circuit of the NE563 provides a typical hum rejection of about 33 dB.

PERFORMANCE

The total harmonic distortion at the NE563 output is quoted as 0.4 per cent, this value having been measured at a modulating frequency of 1 kHz when the deviation was the normal maximum of \pm 75 kHz. The audio output voltage is about 0.4 V rms. The AM rejection is shown in Fig. 18 for various input signal levels. This rejection is excellent and input levels exceeding a few millivolts and is probably better than that offered by other well known circuits at such levels.

The input sensitivity is about 9 μ V for a 30 dB signal to noise ratio at 10.7 MHz (allowing for a 6 dB loss in the ceramic filter), whilst the corresponding level at the mixer input is about 1 mV. The capture and lock ranges are about 250 kHz and 290 kHz respectively for the circuit of Fig. 16 at input levels exceeding 1 mV. They fall with decreasing input levels, reaching about 80 kHz and 140 kHz at an input of 10 μ V.

The NE563 device can, of course, be used at other frequencies than those suggested in the circuit of Fig. 16. The phase locked loop section can be operated at frequencies of less than 1 kHz up to several megahertz. The VCO capacitor required for various phase locked loop operating frequencies can be obtained from Fig. 19.

The writer has used 9.8 MHz crystals made by several different manufacturers (in the circuit of Fig. 16) with satisfactory results.

An economical Taiyo ceramic resonator type CR-9.8 has also been used instead of a 9.8 MHz crystal, but a few circuit modifications are required. The capacitor C8 can be omitted and the resonator connected in parallel with a 2.2 k resistor and a 5 pF capacitor between pins 1 and 16. The NE563 will oscillate if one merely connects a capacitor between pins 1 and 16, but the frequency will drift considerably. A 22 pF capacitor will produce oscillation at about 9.8 MHz.

A crystal oscillator is less likely to produce spurious oscillations than the ceramic resonator. Although one has the additional cost of the crystal, the circuit is very simple and ideal for the amateur constructor. Problems may occur with this type of circuit if the input contains spurious frequencies.

The demodulated signal is a multiplex one containing a number of separate parts as shown in Fig. 20. They are:

- (1) The normal audio signal which has a waveform representing the sum of the signals in the left and right hand channels. If monaural reception is being employed, this sum signal is used as the audio output. As shown in Fig. 20, the maximum frequency of this signal is 5 kHz.
- (2) A low level 19 kHz pilot tone which is synchronised with a 38 kHz sub-carrier. This pilot tone is required for the operation of the stereo decoder circuit.
- (3) A left minus right signal which is modulated onto a 38 kHz sub-carrier. This signal is proportional to the sound amplitude in the left channel minus that in the right channel, the maximum frequency in each channel being 15 kHz. Thus the modulated left minus right signal occupies a frequency band of 38 + 15 kHz — that is from 23 kHz to 53 kHz as shown in Fig. 20. There is a small gap in this signal at 38 kHz, since no audio frequencies below about 30 Hz are transmitted.
- (4) The 38 kHz sub-carrier itself is suppressed at the transmitter to a level of not more than 1% of the total signal.

It can be seen from Fig. 20 that a

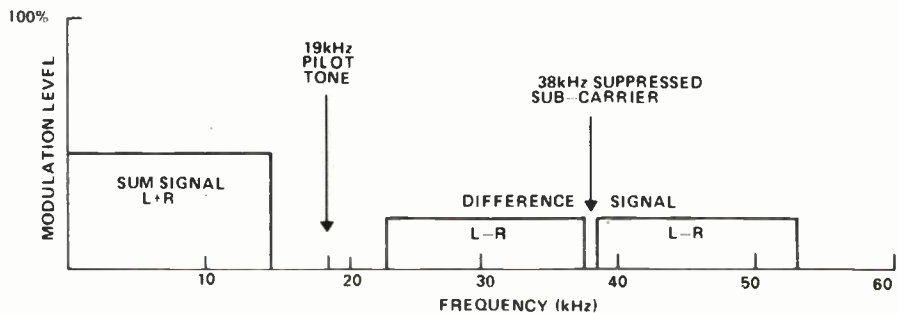


Fig. 20. The frequency spectrum of a stereo multiplex signal.

DESIGN YOUR OWN FM RECEIVER

stereo signal requires a much greater bandwidth than a simple monaural signal. This inevitably means that at a given input level from the aerial the signal to noise ratio will be worse for stereo reception than for monaural reception — actually about 30 dB worse.

The pilot tone is normally switched off at the transmitter when a monaural signal of more than a few minutes duration is being transmitted. This automatically ensures that the stereo decoder in the receiver is switched to the monaural state for the optimum signal to noise ratio.

A number of types of stereo decoder circuit have been published. For example, in the switching type the 19 kHz pilot tone is obtained from the multiplex signal by means of a tuned circuit and is doubled in frequency to re-generate the 38 kHz suppressed sub-carrier; the latter is used to switch the multiplexed input signal. Apart from the necessity of setting up the tuned circuit, such systems have the disadvantage that they do not provide the best channel separation.

In this article, only modern phase locked loop decoding circuits will be

discussed, since they provide optimum performance with circuit simplicity and ease of adjustment. The frequency of the loop automatically locks onto a harmonic of the pilot tone and any normal changes of the component values with time or temperature will not affect the performance. Circuits of this type provide excellent channel separation (typically better than 40 dB) and employ an integrated circuit designed especially for the application.

The CA3090 is a unique stereo decoder integrated circuit first introduced by RCA in mid-1971 as the CA3090Q. An improved version was made available in 1973 under the coding CA 309AQ. Both devices are encapsulated in 16 pin quad-in-line packages which require a supply of about 22 mA at 12V.

Unlike other phase locked loop decoders, these devices have voltage controlled oscillators which are tuned by a 2 mH inductance. The use of an inductance tuned oscillator is said to result in better stability at extremes of temperature (which may be useful in car radios) and better stability as the circuit ages.

The CA3090AQ has the following advantages over the CA3090Q:

(i) It can drive directly a stereo indicator lamp, which requires a current of up to 100 mA. (This indicator lamp is illuminated when the 19 kHz pilot tone causes the loop to lock, showing the circuit is switched to the 'stereo' mode).

(ii) The steady voltage level at the stereo defeat/enable contact (pin 4) controls the operating mode, this voltage level being independent of the pilot tone level, provided that the latter is above a certain minimum level.

(iii) The CA3090AQ is capable of providing rather lower distortion than the CA3090Q.

CIRCUIT

The fairly complex internal circuit of the CA3090AQ is shown in block form in Fig. 21 together with a typical external circuit. The demodulated multiplex signal from the receiver detector is applied to pin 1 of the CA3090AQ where the input impedance is about 50 k. The low distortion pre-amplifier stage feeds the signal to

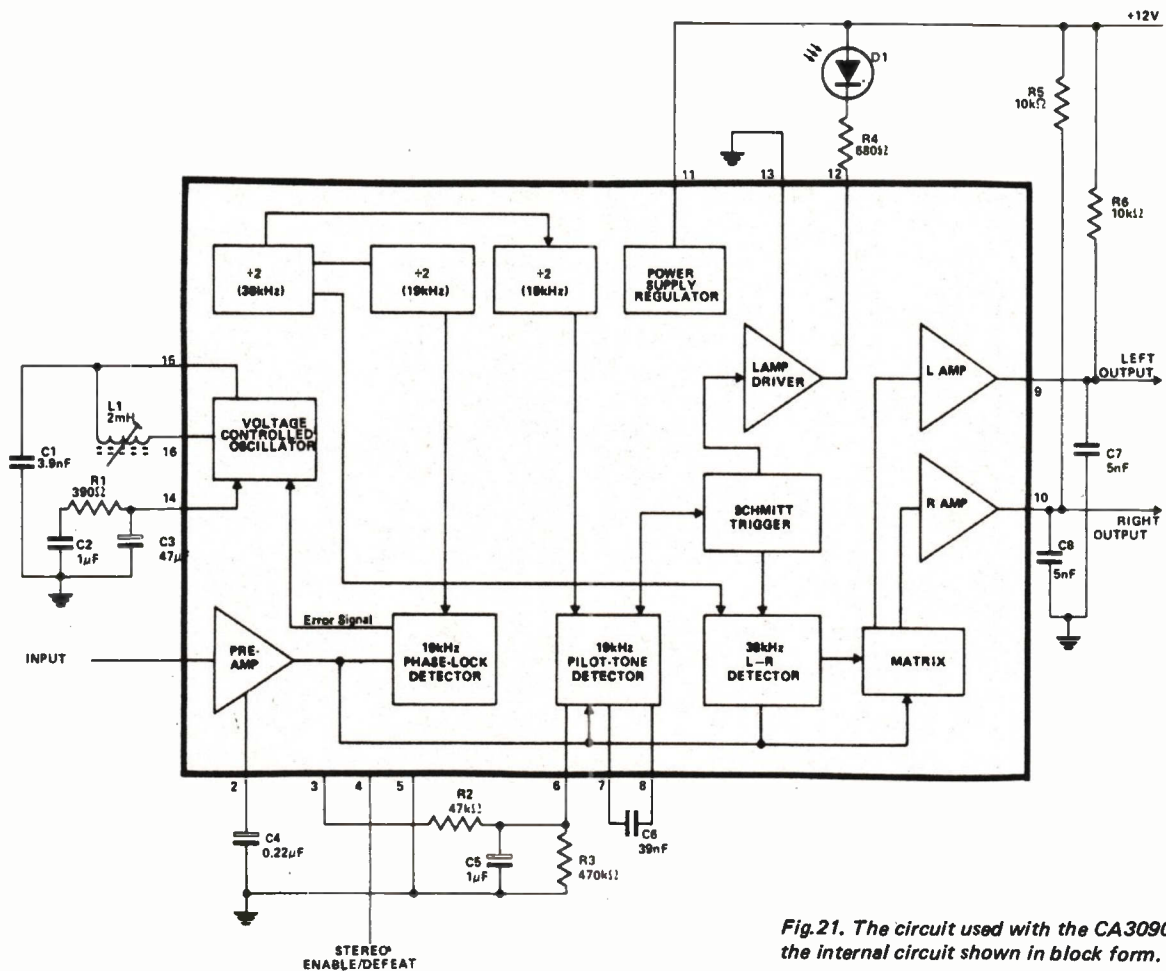


Fig.21. The circuit used with the CA3090AQ with the internal circuit shown in block form.

both the 19 kHz and the 38 kHz synchronous detectors.

The voltage controlled oscillator generates a 76 kHz signal which is divided in frequency to produce a 38 kHz signal and two 19 kHz signals in phase quadrature. The 19 kHz pilot tone from the demodulator circuit is compared with the locally generated 19 kHz signal. An error signal is generated which is used to control the voltage controlled oscillator frequency so that it remains locked with the harmonic of the pilot tone.

A second synchronous detector compares the locally generated 10 kHz signal with the 19 kHz pilot tone. If the amplitude of the latter exceeds a certain value set by an externally adjustable threshold voltage, a Schmitt trigger circuit is energised. The signal from the Schmitt trigger operates the lamp driver circuit which switches the stereo indicator lamp on or off. It also switches the circuit from monaural to stereo operation.

The output signal from the 38 kHz detector and the multiplex signal from the pre-amplifier are applied to a matrix circuit which produces the left and right hand audio signals; the latter are applied to their respective internal amplifiers. The external capacitors C7 and C8 provide the normal 50 μ s de-emphasis.

A light emitting diode, D1, in series with the resistor R4 is shown in Fig. 21. LEDs consume much less current than tungsten filament lamps and are more reliable. However, D1 and R4 may be replaced by a small lamp, consuming not more than 100 mA, if desired.

The core of the inductance L1 should be set half way between the points at which the indicator lamp just switches as the core adjustment is changed. The centre frequency of the voltage controlled oscillator is then very close to 76 kHz. The capture range of the loop is typically $\pm 10\%$ of the centre frequency.

A 2mH coil especially designed for use with the CA3090 device is the Toko type YXNS 30450NK which has its adjuster colour coded blue. It employs 270 turns on a ferrite core which provides a Q factor of about 118. The connections are made to the two pins on the opposite side to the row of three pins on the base of this coil.

If the voltage applied to pin 4 of the CA3090AQ exceeds about 1.2 V, the device is switched to the stereo mode. At lower voltages it is switched to the monaural mode. The tolerance range of the pin 4 voltage is 0.9 V and 1.6 V. The CA3090AQ may be used without the stereo defeat and enable function if a suitable control voltage is

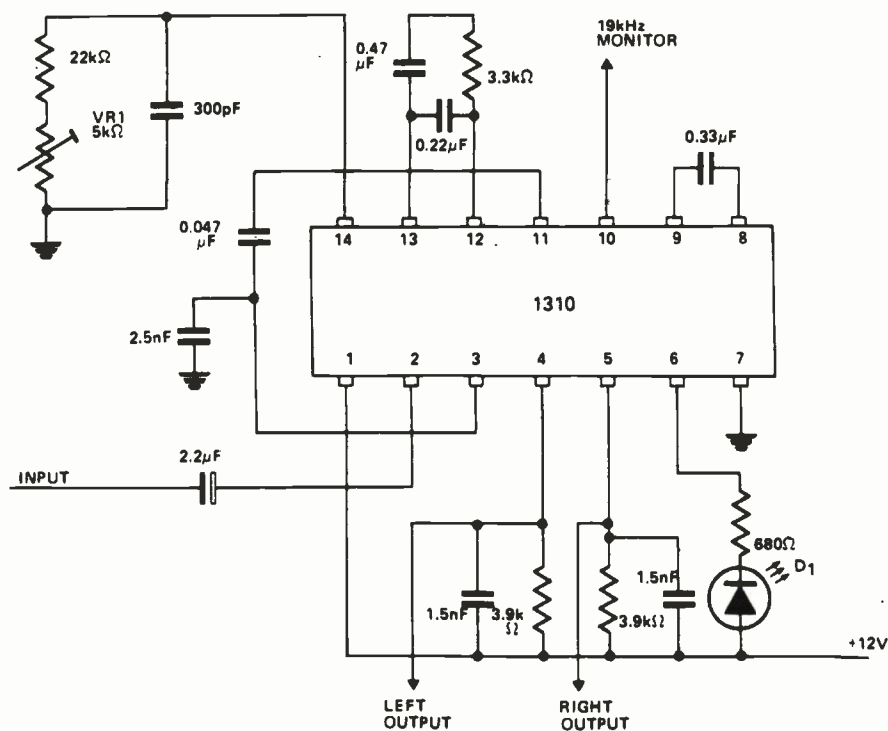


Fig.22. A stereo decoder circuit using the LM1310 type of device.

not readily available; in this case pin 14 should be directly grounded.

The CA3090AQ provides a typical 2nd harmonic distortion level at the outputs of 0.2%, whilst the 3rd, 4th and 5th harmonic distortion is typically less than 0.1%. The channel separation is typically 40 dB (minimum 25 dB).

OTHER DECODER ICs

Another type of stereo decoder which requires no external inductance first appeared in 1972 as the Motorola MC1310P. This is a phase locked loop device operating on similar principles to the CA3090AQ. The frequency is set by a preset resistor rather than an inductance.

The LM1310 (National Semiconductor) device is a 14 pin dual-in-line circuit equivalent to the Signetics MC1310. Other equivalents are the RCA CA1310E and the Texas Instruments SN76115N. These devices can be used in the type of circuit shown in Fig.22.

Rather similar devices are available in 16 pin dual-in-line cases in which an emitter follower is included in each output circuit. The type of circuit which can be used with these devices is shown in Fig. 23. The de-emphasis components are in the pin 3 and pin 6 circuits, whilst the emitter follower outputs appear at pins 4 and 5. Devices of this type include the LM1301E from National Semiconductor, the MC1310E from Signetics, etc.

The National Semiconductor

LM1800 device can also be used in the same circuit as that shown in Fig. 23, but has the additional advantage that it contains a built-in circuit for providing 45 dB power supply ripple rejection. The RCA type CA758E and the Motorola MC1311P are similar devices.

The only adjustment which must be made to the circuits of Fig. 22 and 23 (before use) is the setting of the free running frequency of the phase locked loop by means of VR1. If a frequency counter is available, pin 10 of Fig. 22 or pin 11 of Fig. 23 may be connected to the input of the counter and VR1 adjusted until the signal from the device has a frequency of 19 kHz. (The amplitude of the signal is about 3 V peak).

Most readers will find it easier to adjust VR1 until the stereo indicator lamp remains illuminated at the lowest possible signal level. This adjustment is very easy and causes no problems whatsoever.

The capture range is typically 3%. It can be increased by reducing the capacitance from pin 14 of Fig. 22 or pin 15 of Fig. 23 to ground and increasing the resistors (in parallel with this capacitor) in proportion. However, these alterations are likely to cause increased beat note distortion at high signal levels due to oscillator phase jitter.

The capacitor between pins 8 and 9 of Fig. 22 (or between pins 9 and 10 of Fig. 23) controls the stereo-monaural switching delay. The switching time constant is equal to its value multiplied by about 53 k. If pin

DESIGN YOUR OWN FM RECEIVER

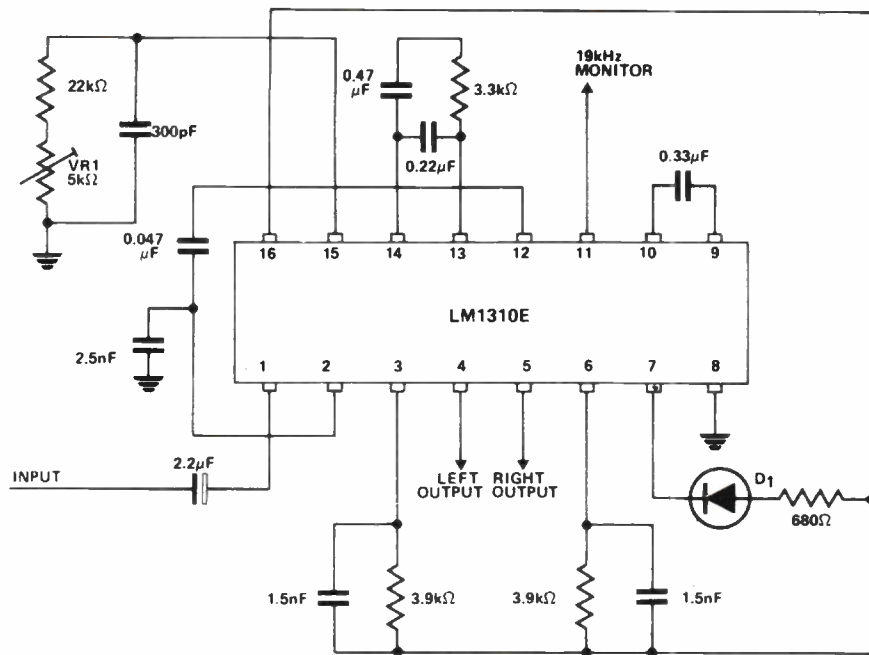


Fig. 23. A stereo decoder circuit using the LM1310E type of device.

8 of Fig. 22 or pin 9 of Fig. 23 is earthed, the circuit operates only in the monaural mode.

There is some variation in the power supply ratings of the devices offered by various manufacturers. For example, the National Semiconductor devices are specified as operating over the range 10 to 24 V and the Signetics devices 8 to 16 V, whilst the RCA 1310E has a supply voltage rating of 8 to 14 V and the CA758 of 10 to 16 V. These ratings should be strictly observed for the particular device employed. The current drawn is of the order of 30 mA.

The audio output voltage is typically 485 mV rms from both the circuit of Fig. 22 and that of Fig. 23. The minimum value of the load resistors in Fig. 22 is affected somewhat by the power supply voltage. The circuit of Fig. 23 does not suffer from this limitation, since the emitter follower outputs provide a low output impedance.

Readers requiring further information on this topic are advised to consult individual device data-sheets and also to study the report by T. D. Isbell and D. S. Mishler "LM1800 phase locked loop FM stereo demodulator". National Semiconductor Application Note AN-81, June 1973.

STEREO OUTPUT FILTERS

The stereo decoder circuits discussed

generate 19 kHz, 38 kHz and 76 kHz waveforms. Although the decoder circuits incorporate about 25 dB and 45 dB rejection of these frequencies, they can still cause trouble when one wishes to feed the output to a tape recorder. Harmonics of these signals may beat with a harmonic of the tape recorder bias oscillator.

This problem can be solved by the addition of a suitable filter to the stereo decoder output. The Toko Company make a number of suitable filters which provide considerable rejection at 19 kHz and 38 kHz.

The Toko BLR-2011-N filter provides a maximum attenuation of 1 dB at frequencies up to 15 kHz and a minimum attenuation of 30 dB at 19 kHz and 38 kHz. This filter is about 42 mm x 34 mm x 20 mm in size. The two inputs from the stereo decoder are connected to the filter, an earth connection made to it and the two outputs taken from the appropriate pins.

The Toko BLR-2007-N is a rather similar filter which provides an attenuation not exceeding 3 dB at frequencies up to 15 kHz and minimum attenuations of 20 dB and 55 dB at frequencies of 19 kHz and 38 kHz respectively. A third Toko low pass filter is the 170 BLR-3107N which has a maximum attenuation of 1.2 dB at frequencies up to 15 kHz and minimum attenuations of 26 dB and 50 dB at 19 kHz and 38 kHz

respectively. The crosstalk does not exceed -45 dB between 50 Hz and 10 kHz, whilst the ripple in the pass band has a maximum value of ± 0.5 dB.

Another type of stereo decoder which requires no external inductance first appeared in 1972 as the Motorola MC1310P. This is a phase locked loop device operating on similar principles to the CA3090AQ. The frequency is set by a preset resistor rather than an inductance.

The LM1310 (National Semiconductor) device is a 14 pin dual-in-line circuit equivalent to the Signetics MC1310. Other equivalents are the RCA CA1310E and the Texas Instruments SN76115N. These devices can be used in the type of circuit shown in Fig. 22.

Rather similar devices are available in 16 pin dual-in-line cases in which an emitter follower is included in each output circuit. The type of circuit which can be used with these devices is shown in Fig. 23. The de-emphasis components are in the pin 3 and pin 6 circuits, whilst the emitter follower outputs appear at pins 4 and 5. Devices of this type include the LM1301E from National Semiconductor, the MC1310E from Signetics, etc.

The National Semiconductor LM1800 device can also be used in the same circuit as that shown in Fig. 23, but has the additional advantage that it contains a built-in circuit for providing 45 dB power supply ripple rejection. The RCA type CA758E and the Motorola MC1311P are similar devices.

The only adjustment which must be made to the circuits of Fig. 22 and 23 before use is the setting of the free running frequency of the phase locked loop by means of VR1. If a frequency counter is available, pin 10 of Fig. 22 or pin 11 of Fig. 23 may be connected to the input of the counter and VR1 adjusted until the signal from the device has a frequency of 19 kHz (The amplitude of the signal is about 3 V peak).

Most readers will find it easier to adjust VR1 until the stereo indicator lamp remains illuminated at the lowest possible signal level. This adjustment is very easy and causes no problems whatsoever.

The capture range is typically 3%. It can be increased by reducing the capacitance from pin 14 of Fig. 22 or pin 15 of Fig. 23 to ground and increasing the resistors in parallel with

this capacitor in proportion. However, these alterations are likely to cause increased beat note distortion at high signal levels due to oscillator phase jitter.

The capacitor between pins 8 and 9 of Fig. 22 (or between pins 9 and 10 of Fig. 23) controls the stereo-monaural switching delay. The switching time constant is equal to its value multiplied by about 53 k. If pin 8 of Fig. 22 or pin 9 of Fig. 23 is earthed, the circuit operates only in the monaural mode.

There is some variation in the power supply ratings of the devices offered by various manufacturers. For example, the National Semiconductor devices are specified as operating over the range 10 to 24 V, and the Signetics devices 8 to 16 V, whilst the RCA 1310E has a supply voltage rating of 8 to 14 V and the CA758 of 10 to 16 V. These ratings should be strictly observed for the particular device employed. The current drawn is of the order of 30 mA.

The audio output voltage is typically 485 mV rms from both the circuit of Fig. 22 and that of Fig. 23. The minimum value of the load resistors in

Fig. 22 is affected somewhat by the power supply voltage. The circuit of Fig. 23 does not suffer from this limitation, since the emitter follower outputs provide a low output impedance.

Readers requiring further information on this topic are advised to consult individual device data-sheets and also to study the report by T. D. Isbell and D. S. Mishler "LM1800 phase locked loop FM stereo demodulator", National Semiconductor Application Note AN-81, June 1973.

STEREO OUTPUT FILTERS

The stereo decoder circuits discussed generate 19 kHz, 38 kHz and 76 kHz waveforms. Although the decoder circuits incorporate about 25 dB to 45 dB rejection of these frequencies, they can still cause trouble when one wishes to feed the output to a tape recorder. Harmonics of these signals may beat with a harmonic of the tape recorder bias oscillator.

This problem can be solved by the addition of a suitable filter to the stereo decoder output. The Toko


Company make a number of suitable filters which provide considerable rejection at 19 kHz and 38 kHz.

The Toko BLR-2011-N filter provides a maximum attenuation of 1 dB at frequencies up to 15 kHz and a minimum attenuation of 30 dB at 19 kHz and 38 kHz. This filter is about 41 x 34 x 20 mm in size. The two inputs from the stereo decoder are connected to the filter, an earth connection made to it and the two outputs taken from the appropriate pins.

The Toki BLR-2007-N is a rather similar filter which provides an attenuation not exceeding 3 dB at frequencies up to 15 kHz and minimum attenuations of 20 dB and 55 dB at frequencies of 19 kHz and 38 kHz respectively. A third Toki low pass filter is the 170 BLR-3107N which has a maximum attenuation of 1.2 dB at frequencies up to 15 kHz and minimum attenuations of 26 dB and 50 dB at 19 kHz and 38 kHz respectively. The crosstalk does not exceed -45 dB between 50 Hz and 10 kHz, whilst the ripple in the pass band has a maximum value of ± 0.5 dB.

6 EASY STEPS TO GOOD AUDIO!

TYPE	min.Watts		SUPPLY volts	Printed Bd. numbers
	4 Ω	8 Ω		
TA3C	3	-	13.2	370105
TA5B	8	5	25	339250
TA10B	13	10	32	339250
TA15B	18	15	38	339250
TA20C	30	20	± 22	339771
TA25C	35	25	± 24	339771
Preamp	-	-	-	339251

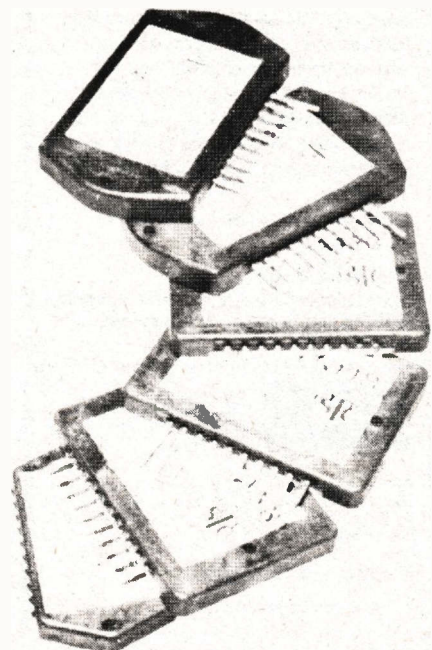

Semiconductor Division

STC-CANNON COMPONENTS PTY. LIMITED

Moorebank ave. Liverpool NSW 2170

6020333
SYDNEY

951566
MELB.

PUT YOUR HANDS TO WORK MAKING MONEY AS A COLOUR TV TECHNICIAN



Do you like to find out why things work, or not work? And do you find electronics an interesting field? Because there is a demand for trained and skilled people to service the millions of pieces of electronic equipment used every day in Australia. Think how many colour TV sets have already been sold in Australia. These will need servicing. And there are millions of older Black and White sets that will also require the services of a good, trained Technician.

If you are interested in electronics, then you should find out more about the ICS training for Electronic and Colour TV Technicians. Send the coupon now, and ICS will return you a complete Career Program guide that tells you how the ICS method works and what the training program teaches you. You study at home, at your own pace. Almost from the first lesson, you can start putting your new knowledge to work. And the study program only asks for about an hour a day.

Would you spend an hour a day to earn more money?

Mail the coupon — today!
International Correspondence Schools,
400 Pacific Highway, Crows Nest,
N.S.W. 2065.

ICS

International
Correspondence Schools
400 Pacific Highway,
Crows Nest, N.S.W. 2065

Yes, I would like to make money. Please ticked below.

put my hands to work to send me, without cost or obligation, the Career Program guide I have

- () Colour TV Technician
() Electronics Technician

Mr./Mrs./Miss

Address

Postcode

Occupation

Age

130126VX

PXB 54382

BUSINESS FOR SALE

A radio, television and record business, established 29 years. Asking price — \$10,000, plus S.A.V. established at \$20,000. Total \$30,000. Selling for health reasons only.

Thompson Radio Service,
Scone, N.S.W. — 065-45-1483

PROTECT YOUR MAGAZINES

ETI BINDERS hold 12 copies

electronics
TODAY
INTERNATIONAL

Send \$4.50 plus 80c postage
NSW & A.C.T., \$1.50 postage
elsewhere with order to

Subscription Department,
Modern Magazines (Holdings) Ltd.,
15 Boundary Street,
Rushcutters Bay, 2011.

Logan Brae Audio Sales

BLANK TAPES BY MAIL ORDER

HITACHI	less than 2	12 off	36 off
C90	\$2.00 ea.	\$1.85 ea.	\$1.75 ea.
C120	\$2.65	\$2.45	\$2.30
UD C90	\$2.55	\$2.35	\$2.20
UD C120	\$3.40	\$3.20	\$2.90
UD R60	\$2.55	\$2.35	\$2.20
UD R90	\$3.40	\$3.20	\$2.90

BASF CrO2			
C90SM	\$2.90	\$2.80	\$2.65

Genac Ultra High Fidelity
UHF 60 \$1.70 ea. \$1.60 ea. \$1.50 ea.

POSTAGE: Up to 6, 60c or \$1.20 airmail or N.S.W. \$1.20 plus 10c per doz. Vic., S.A., Qld., \$1.75 plus 25c per doz. W.A., Tas., N.T., \$1.90 plus 40c per doz.

POST FREE SPECIALS*

Watts Dust Bug	\$5.75
Decca Record Brush	\$11.95
Head Demagnetizer Model 220	\$5.75


*add 20c for airmail



EXPO PORTABLE RECEIVER

AM/FM AC/DC with telescopic aerial and batteries, 9 transistors and 6 diodes. \$22 NSW — \$23 interstate incl. postage. 7 days trial Money back less postage if not fully satisfied.

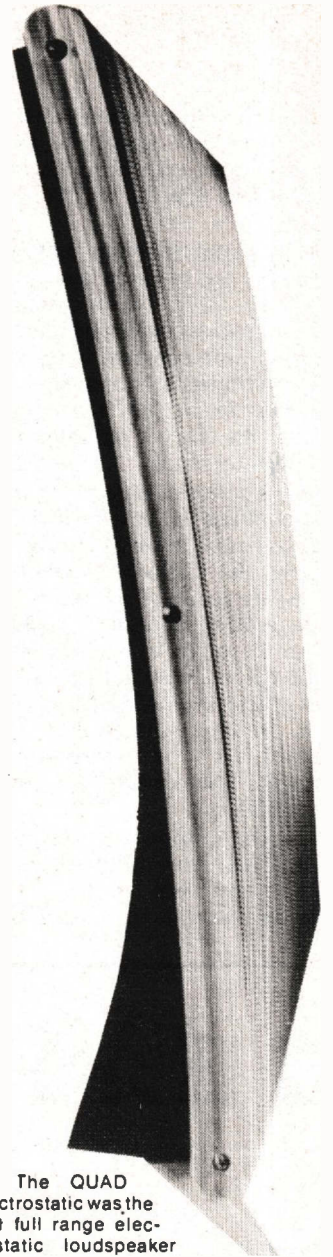P.O. Box 24, Carlton, NSW 2218
Please send SAE with enquiries
Telephone (02) 587-3475



The QUAD Electrostatic was the first full range electrostatic loudspeaker produced commercially and is still the standard by which all others are judged. Using closely coupled moving elements some two hundred times lighter than the diaphragms of moving coil loudspeakers and being entirely free of cabinet resonances and colouration, this loudspeaker overcomes the usual major problems of loudspeaker design and provides remarkably natural reproduction of sound. This explains why the QUAD electrostatic loudspeaker is used by broadcasting and recording organisations all over the world, in applications where quality is of prime importance, and as a standard of reference by the majority of loudspeaker manufacturers.


QUAD for the closest approach to the original sound.

QUAD

is a registered trade mark

For details of your nearest dealer write to British Merchandising Pty Ltd, 49-51 York St, Sydney 2000. Or telephone 29-1571.


CEMA

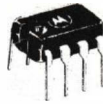

CEMA AND MOTOROLA COME TOGETHER



IT'S OFFICIAL

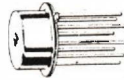


Cema Distributors are now a franchised distributor of Motorola Semiconductors — Australia wide.

It all starts on November 1st and we are ready to go. Stocks are on the shelf there's more coming in and for openers we have an offer you will find hard to refuse.


Our stock will be broad and deep — covering all the product groups you are familiar with — but just to up-date you, we will list them . . .

- SMALL SIGNAL-INC.FET'S
- SILICON POWER
- SILICON RECTIFIERS
- ZENER DIODES
- R.F.
- THYRISTORS
- OPTOELECTRONICS
- LINEAR CIRCUITS: Op. amps
Volt Regs
Interface
Communication
- DIGITAL CIRCUITS: CMOS
HTL
and M6800 MPU

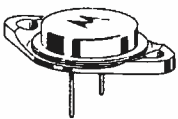So — we have the product — we also have the people and the outlets. If you still have to be convinced, why not call your nearest office or agent and ask about that super opening offer.



COME TO MOTOROLA COME TO CEMA

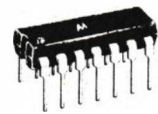

CEMA (DISTRIBUTORS) PTY. LTD.


A FRANCHISED **MOTOROLA** 
SEMICONDUCTOR DISTRIBUTOR

OFFICES: SYDNEY 439-4655 MELBOURNE 329-7144

AGENTS:	Adelaide	Brisbane	Canberra	Wollongong
NAME:	Woollard & Crabbe	Electronic Components (Q'ld)	Custom Scientific	Macelec
PHONE:	51-4713	371-5677	47-6179	29-1276

IDEAS FOR EXPERIMENTERS

IC DIRECT CONVERSION RECEIVER FRONT-END

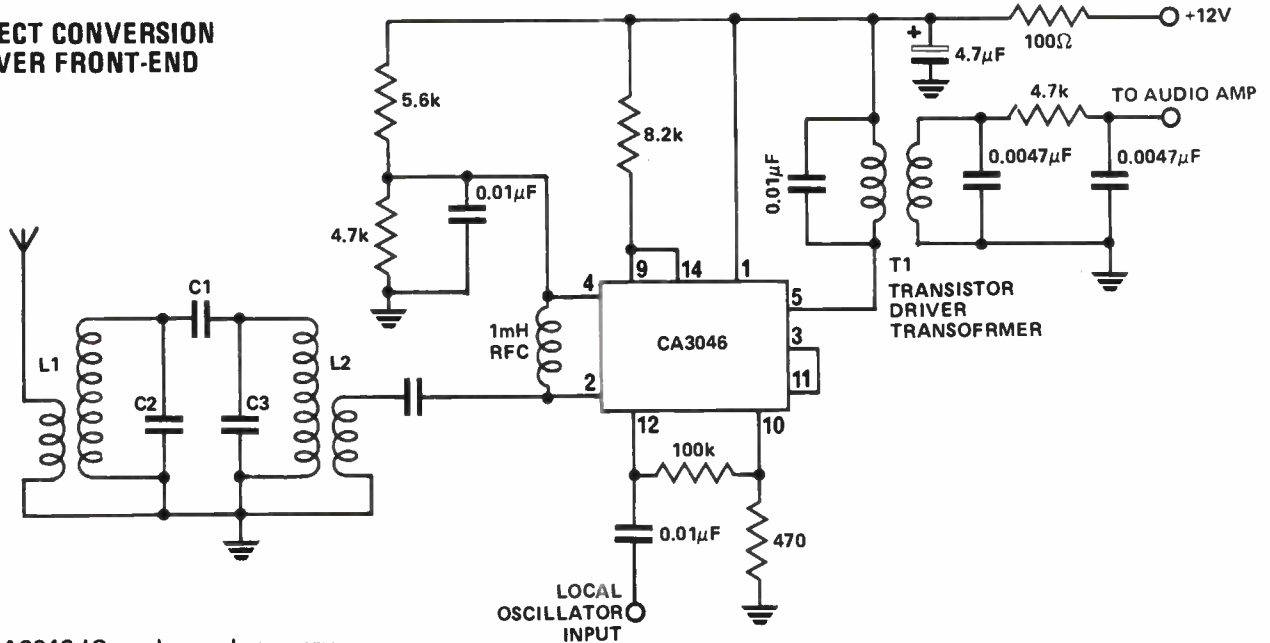

The CA3046 IC can be used as a very efficient mixer in a direct conversion receiver front-end. Some buffering and amplification of the local oscillator is provided and the mixer has a small amount of conversion gain.

The input tuned circuit can be made to suit the desired range. C1 is a coupling capacitor that determines front-end selectivity. For 3.5 to 4 MHz, L1 and L2 are 13 turns of #26

B&S enamel wire wound around 2/3 of a Philips toroid type 020-91010. C2 and C3 are 33 pF capacitors paralleled by 3-30 pF trimmers. C1 is 15 pF or larger for more bandwidth.


JAPANESE COMPONENT CODES

Japanese and some other imported components are marked with codes giving value, tolerance etc. as shown above. Colour coded RF chokes use the same colour code as resistors but the value is in microhenries — similar to the Philips RFC coding.




As the name of this section implies, these pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory.

Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.

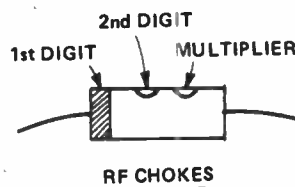
Electronics Today is always seeking material for these pages. All published material is paid for — generally at a rate of \$5 to \$7 per item.



(27nF, 0.027µF) (15nF, 0.015µF)

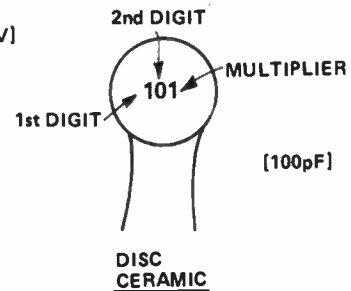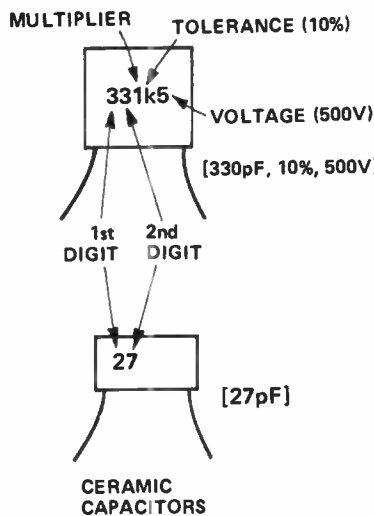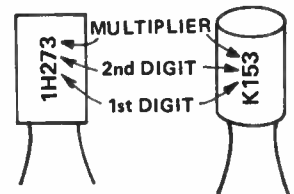


LASH-UP PC BOARD

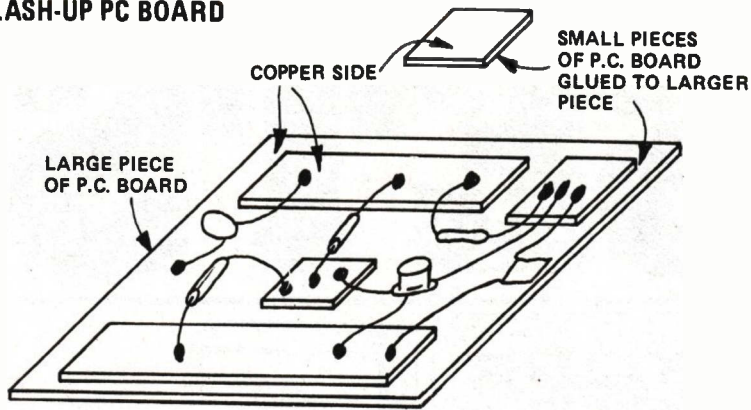

Quick breadboards, or circuit lash-ups can be made with a large piece of p.c. board of suitable size with small, variously shaped, scraps or pieces cemented to it. Single or double-sided p.c. board can be used. Quick drying or 'instant' drying glues that can withstand heat are best, e.g. 'Super


500' or equivalent. It is an excellent form of construction for RF circuitry, particularly VHF-UHF circuitry. Small capacitors can be made in this fashion also. A 5 mm x 5 mm square of 2 mm thick fibreglass p.c. board stuck on a larger piece has a capacitance close to 5 pF.

SIMPLE RLC BRIDGE

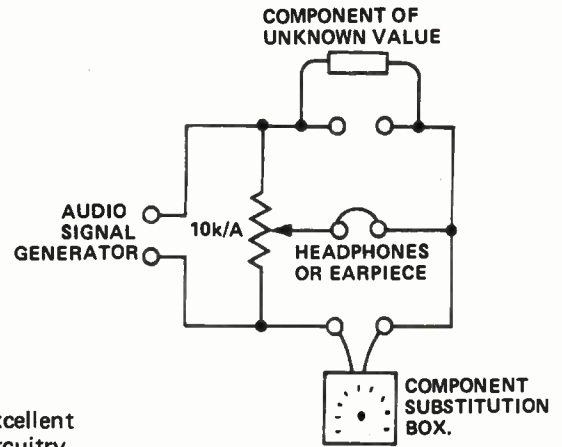

A simple RLC bridge can be made from a few components as shown above. The audio generator provides a signal to a bridge network formed by the potentiometer, the component substitution box and the unknown value component. The headphones or earpiece serve as a null detector — alternatively a CRO can be used.

HIGH PERFORMANCE RF OSCILLATOR

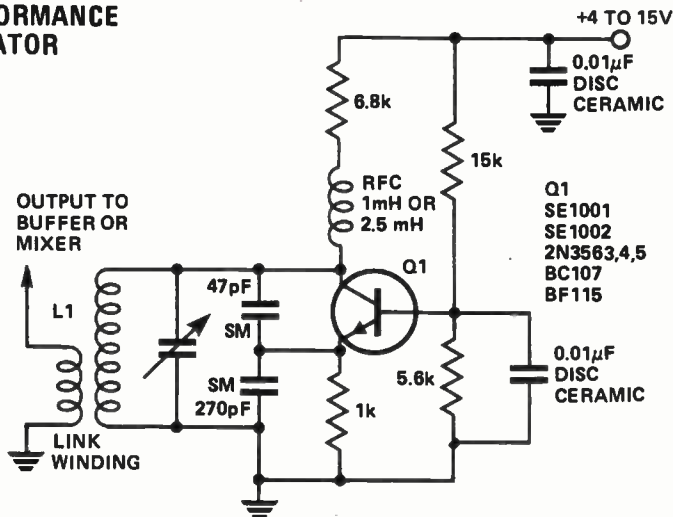


This high performance RF oscillator will produce an output that is level to within ± 10 mV over approximately a 2:1 frequency range. Stability is quite good following warm-up provided the usual precautions are taken. Single point earthing is an advantage.

With the component shown the oscillator will work from 2 MHz to about 25 MHz. L1/C1 should be selected according to the desired range.


Actual output depends on the link winding. The turns ratio of the link winding to L1 should be about 10:1. Couple the link winding to the 'earthy' end of L1. Tight coupling degrades stability. About 300 mV to 500 mV is readily obtained with only loose coupling.

BROADBAND HF DIPOLE

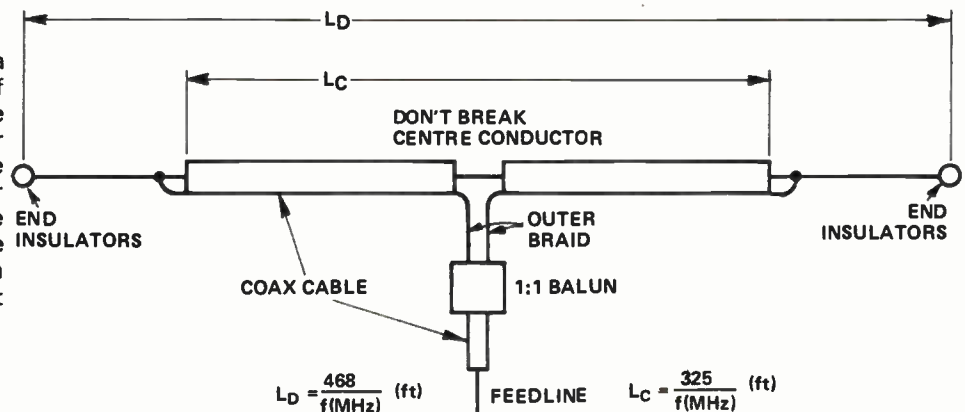A wire dipole at HF typically has a bandwidth of 4% to 5% for an SWR of 2:1 either side of resonance. The bandwidth can be increased to greater than 17% by constructing the dipole with a portion of it of small diameter (1/4" or 1/8") coaxial cable. Tape the coax to a nylon bearer line, either rope or heavy fishing line to give it strength and support. This is an old tip but not well remembered.



KITSETS

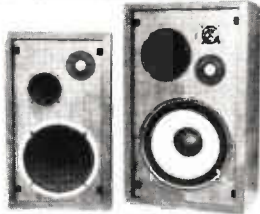

STEINTRON AGAIN!

Our direct import—back again at last. Beautiful timber cabinets with louvred fronts. Absolutely superb performance.

V120: 12" woofer, 6½" middle; 1½ dome tweeter; 2" super tweeter. Crossover rolloff 12dB per octave; handles 45W RMS; 20-22000Hz. Has tone control. 25½" x 15" x 11½". P&P each \$5. Price each \$129.


V100: 10" woofer; 5" middle; 1½" dome tweeter. Handles 35W RMS, 20-20,000Hz. 22½" x 13" x 11½". P&P each \$5. Price each \$99.

DUE TO THE POPULARITY OF THESE FINE QUALITY, HIGH PERFORMANCE SPEAKERS, WE HAVE EXPANDED THE RANGE.

V150 15" woofer, 2 x 5" midrange, 2 x 1½" dome tweeter and 2 x 2" super tweeter. Handles 55 Watt, range from 20-22,000 Hz. Price each \$179. P&P \$5 each.

V80 8" woofer, 1½" tweeter and 2" super tweeter. Handles 25 Watt, 30 to 22,000 Hz. Price each \$69.

NEW ETI 440 KIT

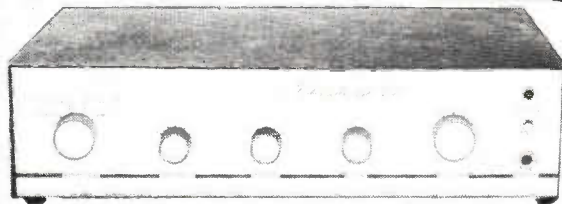

ETI 440. Simple 25 Watt amplifier kit as featured in Electronics Today, July 1975.



25 Watt R.M.S. per channel, distortion round 0.1% 6 Hz to 80 kHz., at -3dB. A full list of specifications and building instructions are in the July issue of Electronics Today. This is a magnificent amplifier which is not hard to assemble. It will suit those people who want a good amplifier at an economical price.

\$95 per kit of parts \$5 P&P

SEE WHAT COLOUR YOUR MUSIC IS

NOT a kit. These are the spectacular SECO colour organs. Connect to any speaker and the colour lamps flicker and glow with varying brightness in relation to volume, pitch, and rhythm. Why put up with colour TV? Works even with small transistor radios. Leaves fibre-optic lamps for dead. **V3050:** Domestic unit. 30 lamps, 3 channels, 5 colours. Diamond pattern. 18½" x 11½" x 7 3/8". 3.5kg. P&P \$5. **\$49-50**

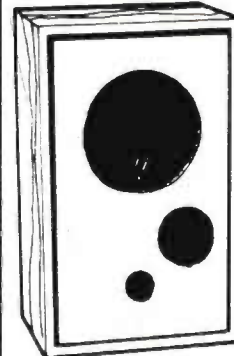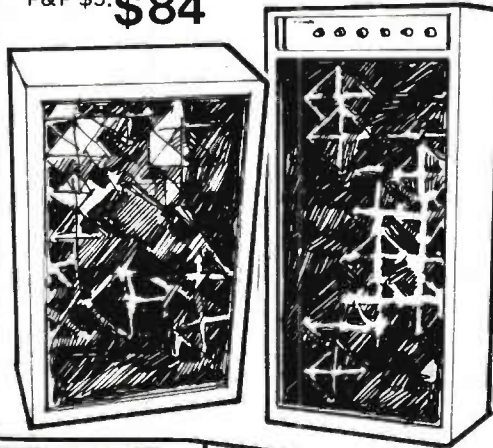4050X: Professional monster. 32 lamps, 4 channels, 4 colours, individual colour mixing controls and a host of other features. Ideal groups. About 30½" x 15½" x 9 1/8". P&P \$5. **\$84**



TOP QUALITY SPEAKER KITS

Pre-assembled & pre-veneered speaker boxes —

ET1400	\$22.50 per kit	\$3 P&P
1.6 c.f.	\$22.50 per kit	\$3 P&P
2.5 c.f.	\$26.50 per kit	\$3 P&P
2.7 c.f.	\$32.00 per kit	\$4 P&P

Speakers available for all these kits.

ETI 422 50 WATT PER CHANNEL AMP KIT.



SPECIAL KIT OF THE MONTH. Electronics Today ETI 422 50 Watt stereo amplifier. This high power, high quality, economical kit gives a genuine 50 Watt per channel into 8 ohms at typically less than 0.2% distortion. Complete with teak cabinet.

\$115 P&P \$5.

KIT SPECIALS

PM 143 15 WT per ch. amp. \$75. P&P \$5. PM 144 cassette Deck \$99. P&P \$5. ETI 422 50W per ch. amp. \$115. P&P \$5. ETI 440 25 W per ch. amp. \$95. P&P \$5. ET Spring Reverb Unit \$59. P&P \$5. Musiccolour II 3 ch. light and colour unit \$59. P&P \$4. Mood Colour IV 4 ch. light and colour unit \$85. P&P \$4. Drill speed control E/A \$17.50 P&P \$2. Transistor Tester E/A \$19.50 P&P \$2. Glide Tone Generator \$9.75. P&P \$1.00. 5 State Logic Probe \$15. P&P \$1.00. Warble Double \$25. P&P \$1.50. E/A C.D.I. \$25. P&P \$2.00.

PLESSEY LOUDSPEAKER

Improve your existing loudspeakers by replacing them with these high-performance, quality units from Plessey:

X 30 1" Dome Tweeter \$9.65 P&P 75c. C6MR 6" sealed back mid-range \$8.50 P&P \$1.20. C100x10" wide

range twin cone \$16.25 P&P \$1.50. C12Px12" wide range twin cone \$25.00 P&P \$2.00.

PARTS SPECIAL

Stock up now on these common types at our special low prices:

¼ W. Resistor Packs, mixed value, approx 200 per pack — \$3.50. P&P 50c. ½ W. Resistor Packs, mixed value, approx 200 per pack — \$3.50 P&P 50c. Mixed value & voltage electro packs, 24 per pack — \$5.50. P&P 50c. Ceramic Cap. Packs, Mixed value and voltage, 40 per pack — \$8.00 P&P 50c. Semiconductor packs containing 20 trans, 10 diodes 5 1/2 C's — \$13.00 P&P 50c. Poly packs, 40 per pack — \$7.00. P&P 50c. Audio Leads, Assortment — \$3.95. P&P 75c. Goldring Cartridges, ES70E (\$21.50) ES70S (\$11.50) P&P 75c. Crystal Ear Pieces — \$0.65 P&P 50c. Magnetic Ear Pieces — \$0.65. P&P 50c. Valves 6 CM5 (\$1.50) 52Am, 12AU7, 6BL8, 6AL3, (\$1.00) P&P 50c.

HOW TO ORDER:

MAIL ORDERS: PRINT all details clearly. Include phone no. for quick checking if any problems. Send cheque or postal order (NOT cash) to Kitsets (Aust) Pty. Limited, P.O. Box 176 Dee Why, NSW 2099. For urgent queries or PMG/COD ring us on 982-7500. Area code 02 (24 hours open line service).

SPECIAL NOTICE: — Due to economy, we have consolidated both our Melbourne showrooms in our Box Hill location, and no longer trade in Adelaide. Adelaide customers are advised to use our Mail Order service.

SYDNEY: 400 Kent St., Sydney, 29-1005. 657 Pittwater Rd., Dee Why, 982-9790. BRISBANE: 293 St. Paul's Tce., Fortitude Valley, 52-8391. MELBOURNE: 985 Whitehorse Rd., Box Hill, 89-8371. PERTH: 557 Wellington St., Perth (opp. new bus terminal), 21-3047.



PROJECT 128

AUDIO MILLIVOLTMETER

Sensitive instrument for 'A' weighted audio noise and signal measurements.

AN ACCURATE and sensitive ac voltmeter is needed for many audio equipment measurements.

Whilst for example, maximum power output is readily measurable with a conventional multimeter, more complex instrumentation is required for measuring noise output (a measurement required when checking signal/noise ratio).

Even signal levels as high as 100 mV, typical output of most pre-amplifiers, are not readily measured with accuracy on a conventional multimeter.


The ETI 128 Millivoltmeter is specifically designed for such measurements whilst also being useful as a general purpose ac/dc voltmeter. The lowest range, of 300 microvolts FSD, allows measurements to 80 dB below one volt, whilst other ranges allow measurements up to 30 volts ac or dc. These ranges cover most of the measurement requirements of audio work.

When measuring noise levels account must be taken of the non-linear characteristics of the ear. For this reason a network has been incorporated which tailors the meter response-versus-frequency to match the subjective response of the ear. Such a network is known as an 'A weighting network' and its use provides a measurement which is realistically related to what is heard. When measurements are made using this network the results must be quoted as being 'A weighted'. Typically this is done by quoting dBA rather than just plain dB.

CONSTRUCTION

The meter is a highly sensitive instrument and for this reason the constructional method given should be followed closely if noise and hum pickup are to be minimized.

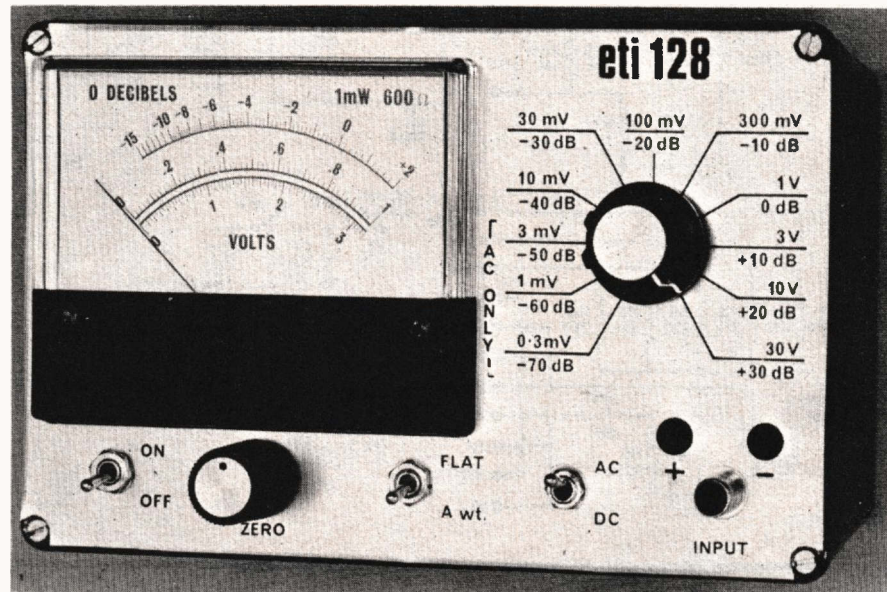A diecast box is used to house the meter as this provides excellent shielding against external signals. The front panel label is made from 'Scotchcal'. This is a specially prepared



sheet of thin aluminium which is coated with a photo-sensitive emulsion on one side. The reverse side has a self-adhesive coating, protected by waxed paper, which is peeled off when the material is to be stuck down. As Scotchcal is only available in bulk, ETI is making available ready-to-use front panel labels made from this material. Should you require one of these labels send \$3.00 and a stamped,

self-addressed envelope (minimum size envelope 190 x 127 mm).

The meter used in the prototype was from Dick Smith Electronics. It measures 100 x 82 mm but requires to be rescaled. The scale as published on page 77 should be cut out and glued over the existing scale taking care not to let glue or dirt enter the meter movement. Any similar meter may be

SPECIFICATION

RANGES	
dc (FSD)	10, 30, 100, 300 mV, 1, 3, 30 V. auto-polarity, LED indication.
ac (FSD)	0.3, 1, 3, 10, 30, 100, 300 mV, 1, 3, 10, 30 V 0 dB = 1 mW into 600 ohms (0.775 V) weighting curves, ac only, flat, 'A' weight ± 3% nominal
ACCURACY	
MINIMUM READING	
Open circuit	-76 dB
Terminated 47 k	-85 dB
POWER SUPPLY	
Voltage	+6 and -6 volt (batteries)
Current	approximately 12.5 mA
Battery life	approx 100 hours (8 x 1015 cells)

AUDIO MILLIVOLTMETER

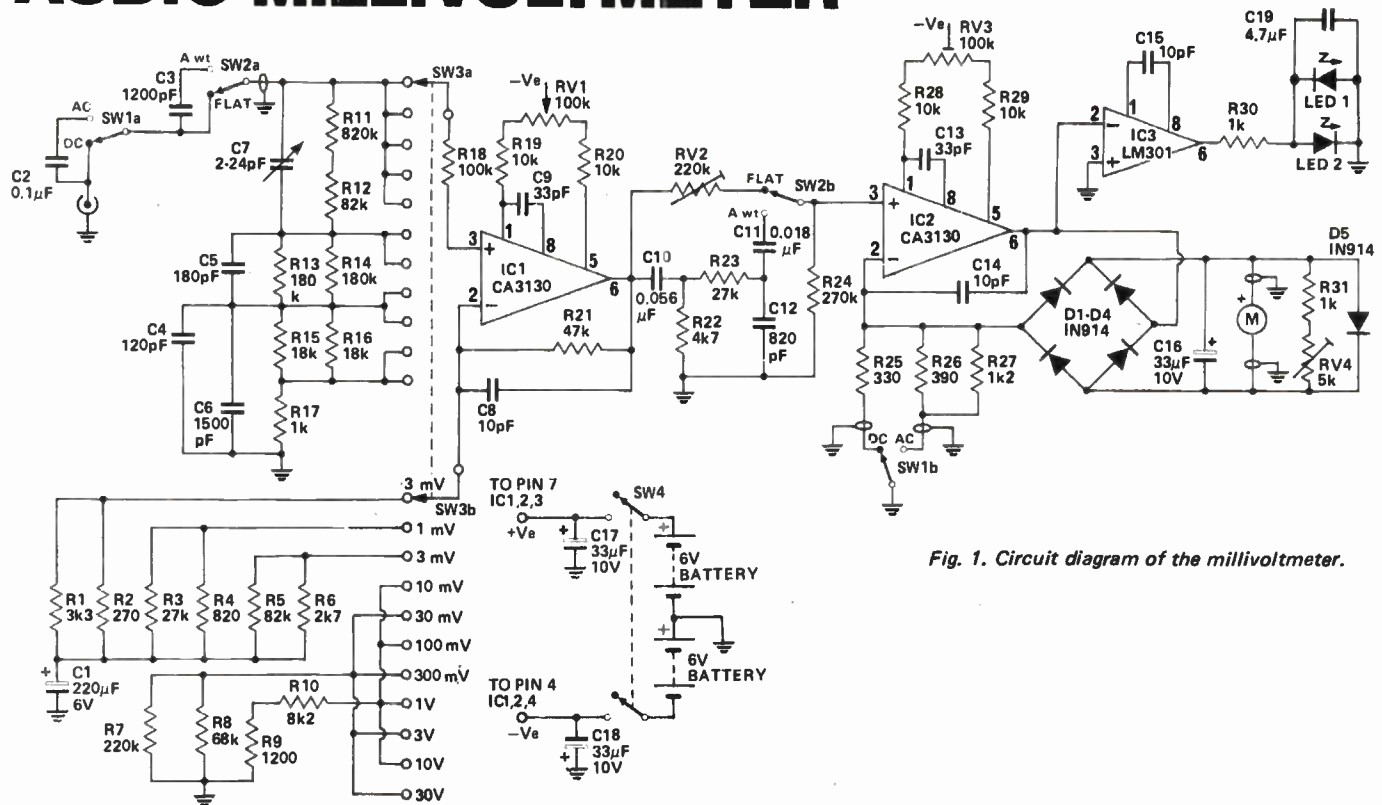


Fig. 1. Circuit diagram of the millivoltmeter.

HOW IT WORKS – ETI 128

The millivoltmeter may be separated into several sections in order to simplify the explanation of its mode of operation. These are:—

- Input attenuator.
- Input amplifier.
- 'A'-weight network.
- Meter drive circuitry.
- Polarity detector.

The input attenuator consists of resistors R11 to 17 and capacitors C4 to 7, and gives division ratios of 1, 10, 100 and 1000. The capacitors are required to ensure that the division remains accurate at high frequencies.

The input amplifier is a CA3130 operational amplifier where the gain is selected by SW3b. Gains of 190, 60, 19, 6 and 1.9 are available which together with the input divider ratios provide the 11 ranges required. The high gain ranges of 190, 60 and 19 are ac coupled, as the temperature stability of the CA3130 will not allow voltages of less than 10 mV dc to be used. The output of this amplifier is 60 mV when the meter is indicating full scale on any range. A potentiometer, RV1, is provided to

adjust the offset voltage on the CA3130 and thus acts as a zero-set control. Since the offset voltage is affected by temperature this control is available externally.

When measuring noise in audio systems a weighting network is often used to give a measurement which is related to the non-linear response of the ear. The most commonly used weighting is known as 'A' weight and this facility is built into the meter. The 'A' weight curve is produced by a network that has a three-pole, high-pass filter and a single-pole, low-pass filter. The main section of this filter is formed by C10, C11, C12 and R22, 23, and R24 (two poles). The third pole is due to C3 and the one megohm combined resistance of R11 to R17. This later section prevents saturation of the input amplifier at low frequencies. Since this filter introduces some loss at 1 kHz, RV2 is incorporated to provide the same loss in the 'flat' mode.

The second IC acts as a meter amplifier. The input signal is rectified by the diode bridge D1 to D4 whilst

the amplifier effectively compensates for the diode drops. A preset for offset adjustment, RV3, is provided for this IC. Calibration is performed by adjustment of the shunting resistance, R31 and RV4, across the meter. Due to the full-wave action of the rectifier the meter when on the dc ranges reads uni-directionally regardless of dc polarity. The output of IC2 will however will either be at over one volt positive or one volt negative (voltage drops across the diodes) depending on whether the input voltage is positive or negative. This is compared by IC3 against zero volts and, depending on polarity, either LED 1 or LED 2 will be illuminated. With an ac input both LEDs will be on. These LEDs are therefore the polarity indicators. Capacitor C19 removes any high frequency components which could be coupled into the input, as the LEDs are located next to the input socket.

Due to the difference between the average and the RMS values of a sine-wave a slight change in gain is necessary in the ac mode and, this change is made by SW1b.

used as long as it has 100 microamp sensitivity.

The ac/dc and Flat/'A' weight switches are four-pole types although only the outer two poles are used. The centre two poles are earthed in order to reduce the capacitance between the

two outer poles. Such precautions are necessary to prevent any possibility of instability on the most sensitive ranges. The metal bracket which supports the printed-circuit board also acts as a shield between the meter circuitry and the input stages.

Commence construction by assembling components to the printed-circuit board, making absolutely sure that all are mounted in the correct position and with the correct polarity. This should be carefully done — once the meter is

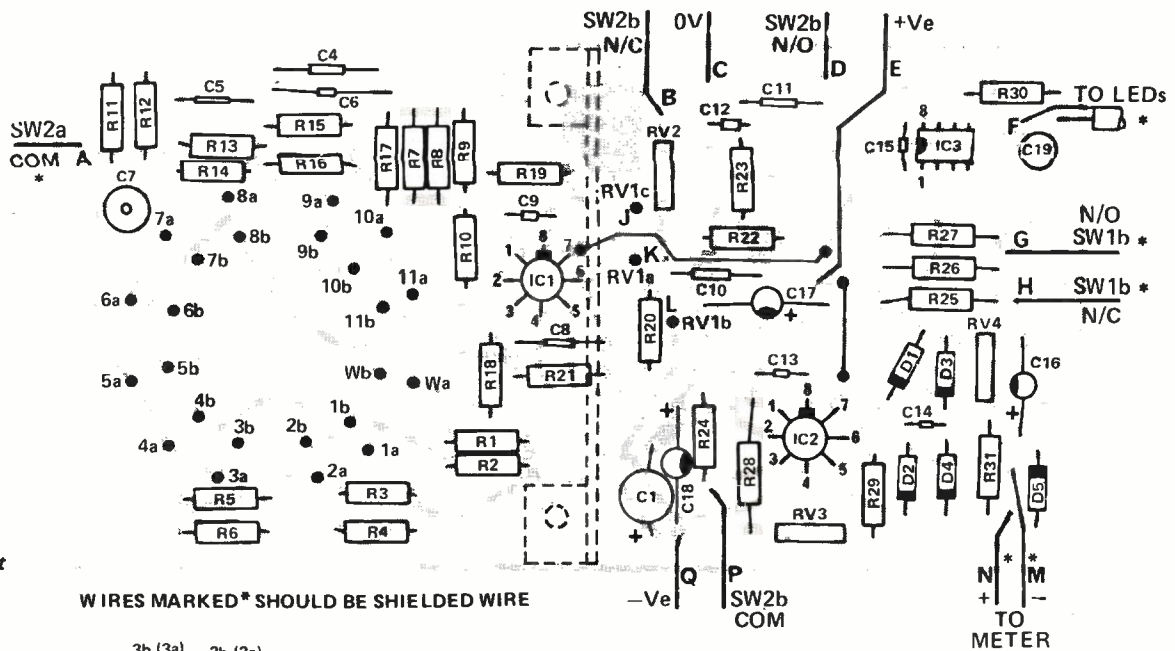


Fig. 2. Component overlay.

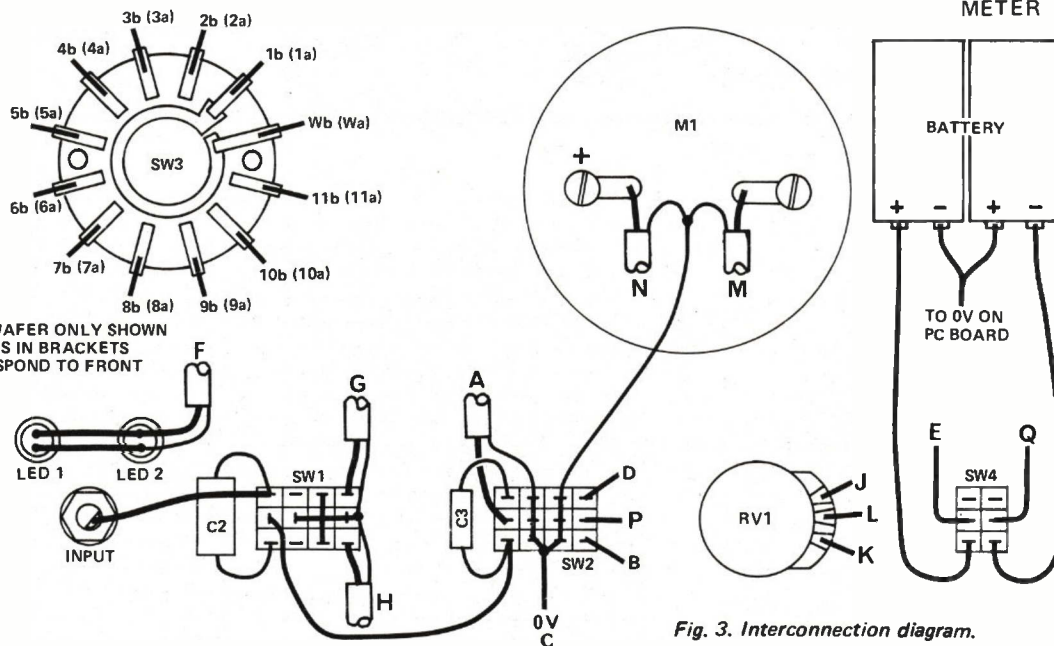


Fig. 3. Interconnection diagram.

fully assembled, it is very difficult to change components.

Assemble the front panel, fitting all switches with the exception of SW3, LEDs, potentiometer, input socket, meter, and the shield. The shield passes between the centre two contacts of the 'A'-weighted switch.

Solder a tinned copper lead to each of the 12 contacts on the rear wafer of switch SW3 (about 25 mm long). Feed these wires through the holes provided in the printed-circuit board (1b to 11b and Wb) making sure that the wiper contact on the switch goes to Wb and that the other wires are inserted in sequence. Do not solder as yet.

Assemble the printed-circuit board onto the shield and the rotary switch to the front panel. We used a 3 mm stack of washers to space the switch back from the front panel so the

PARTS LIST — ETI 128			
R2	Resistor	270 ohm	2% 1/4W
R25	"	330 ohm	2% 1/4W
R26	"	390 ohm	2% 1/4W
R4	"	820 ohm	2% 1/4W
R17	"	1k	2% 1/4W
R6	"	2k7	2% 1/4W
R10	"	8k2	2% 1/4W
R15,16	"	18k	2% 1/4W
R21	"	47k	2% 1/4W
R8	"	68k	2% 1/4W
R13,R14	"	180k	2% 1/4W
R11	"	820k	2% 1/4W
R30,31	Resistor	1k	5% 1/4W
R9,27	"	1k2	5% 1/4W
R1	"	3k3	5% 1/4W
R22	"	4k7	5% 1/4W
R19,20	"	10k	5% 1/4W
R25,29	"	10k	5% 1/4W
R3,23	"	27k	5% 1/4W
R5,12	"	82k	5% 1/4W
R18	"	100k	5% 1/4W
R7	"	200k	5% 1/4W
R24	"	270k	5% 1/4W
RV1	Potentiometer	100k lin rotary	
RV2	"	220k Trim	
RV3	"	100k Trim	
RV4	"	5k Trim	
C7	Capacitor	2-24 pF	Philips 2222 808 00006
C8,14,15	"	10 pF	Ceramic
C9,13	"	33 pF	Ceramic
C4	"	120 pF	Ceramic
C5	"	180 pF	Ceramic
C12	"	820 pF	Ceramic
C3	"	1200 pF	polyester
C6	"	1500 pF	polyester
C11	"	0.018 μF	polyester
C10	"	0.056 μF	polyester
C2	"	0.1 μF	polyester
C19	"	4.7 μF	non polarised electro
C16,17,18	"	33 μF	10V electro
C1	"	220 μF	6V electro
IC1,2	Integrated Circuit		CA3130
IC3	"		LM301
D1-D5	Diode	IN914, BA318 or similar	
LED 1,2	LED	5023 or similar with panel mounting	
SW1,2	Toggle switch	4 pole 2 positions	
SW3	Rotary switch	2 pole 11 positions	
SW4	Toggle switch	2 pole 2 positions	
M1	Meter	100 μA FSD * see text	
		PC Board ETI 128	
		Die cast Box 6357p	
		Two knobs*	
		One RCA socket	
		Eight AA size batteries	
		Two-4xAA size battery holders	
		Shield to Fig. 7	

AUDIO MILLIVOLTMETER

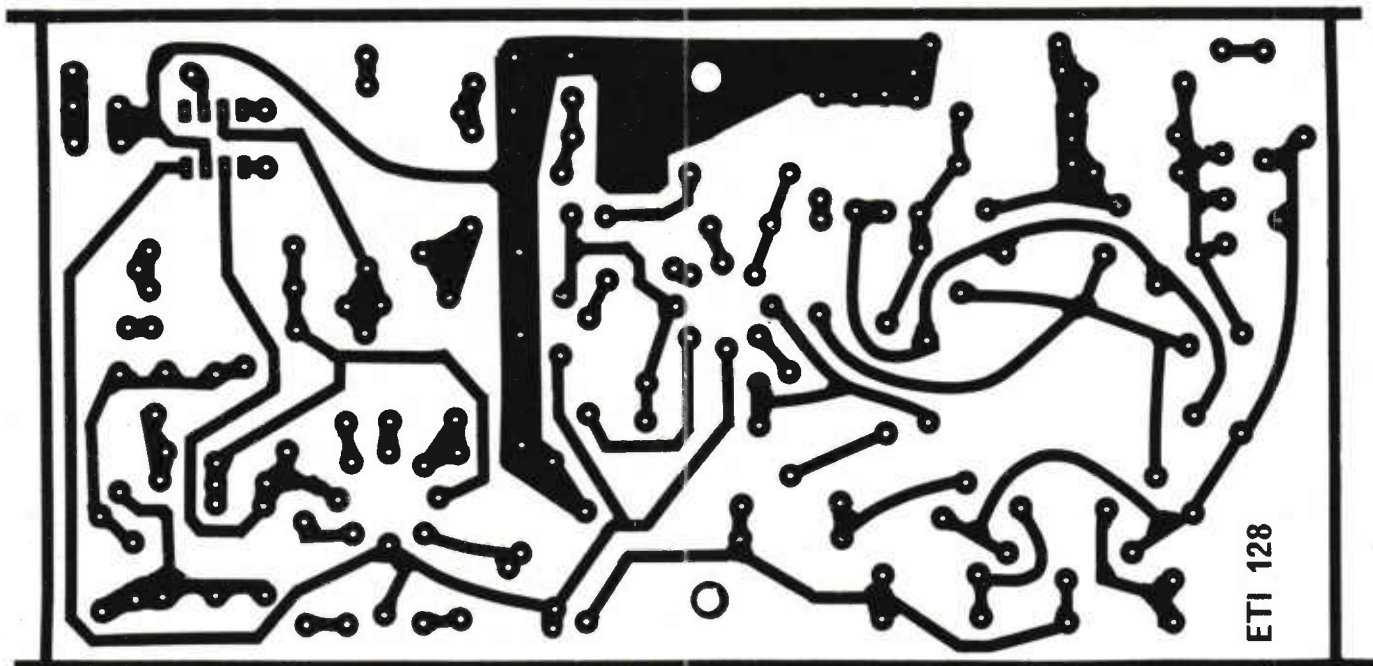


Fig. 5. Printed circuit layout. Full size 170 x 87 mm.

control knob would sit down closer to the front panel. Remove any slack in the tinned-copper wires, connecting the switch to the printed-circuit board and then solder them to the board. Now remove the printed-circuit board and switch assembly from the front panel. The switch will now be rigidly held onto the board, and the front wafer can now be wired to the board via further tinned-copper links. Make sure that none of these wires is touching.

Add leads to the printed-circuit in the locations shown on the overlay and reassemble the board and switch assembly to the front panel. The components on the front may now be connected to the board by these leads which should be kept as short as possible without placing undue strain on the wires. The only exception to this rule is the wire from SW1a to SW2a which should be kept reasonably well clear of the second pole of SW10. This is best done by running the lead down the front panel along the bottom and then back up to SW2a. Shielded wire should be used where designated on the overlay and wiring diagrams, and this should preferably be of the low capacitance variety.

The LEDs are connected in parallel but in anti-phase, the actual polarities

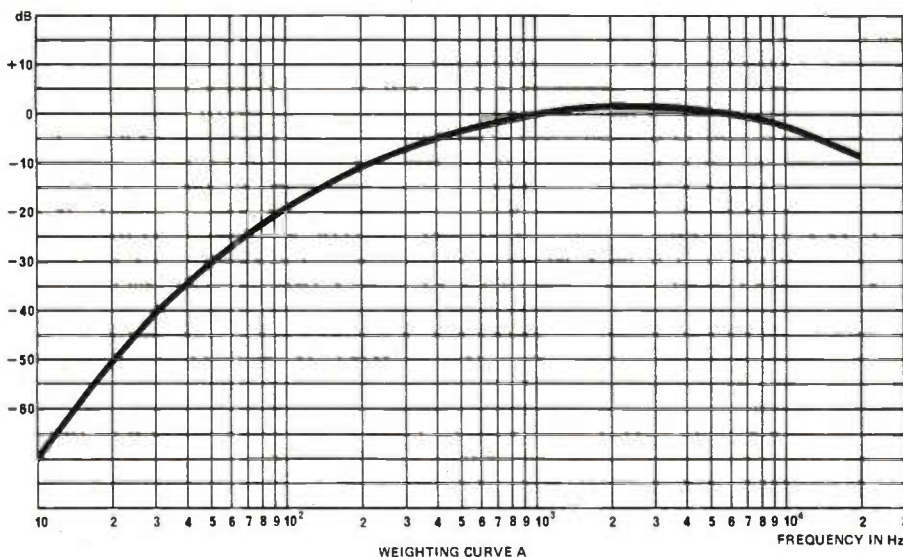


Fig. 4. Curve of 'A' weight response.

may be determined later if necessary during the calibration procedure.

CALIBRATION

Before commencing calibration, check that the meter performs as it should on all ranges by applying known voltages and checking that a deflection of roughly corresponding magnitude is obtained. Also check that the 'A'-weighted switch appears to work as it should.

1. Short the input, select the 3 mV range and switch on.
2. Allow about 5 minutes for the instrument to stabilize thermally and

then adjust RV3 to zero the meter.

3. Select the 10 mV range, dc, and 'flat', and adjust the front panel control RV1 to zero the meter.

4. Remove the short from the input, select the 300 mV range and apply an input having a frequency of less than 500 Hz and a level which gives a convenient indication, eg 0 dB. Change the frequency to somewhere between 10 kHz and 50 kHz making sure that the input level is the same in both cases, and adjust capacitor C7 so that the meter reads the same in both cases.

5. Apply an ac input signal and switch between ac and dc. The reading


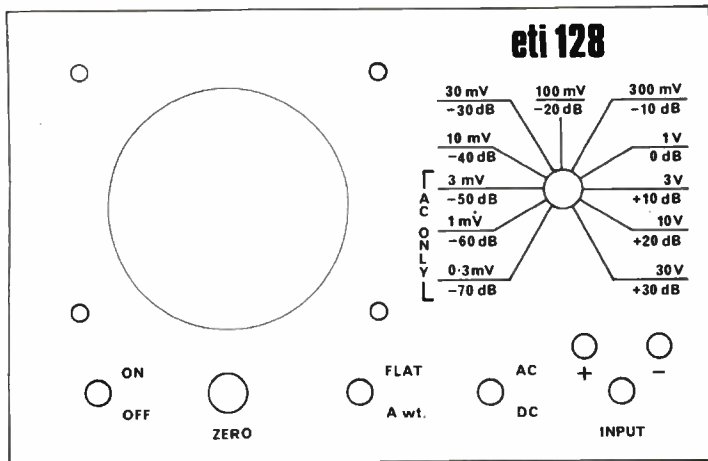


Fig. 6. Front panel artwork. Full size 189 x 121 mm.

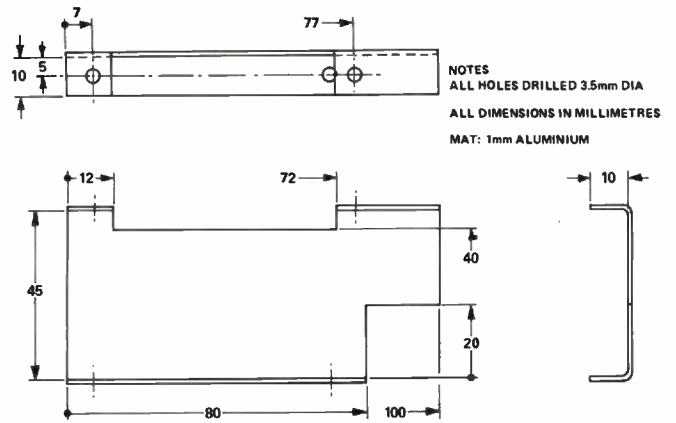

NOTES
ALL HOLES DRILLED 3.5mm DIA
ALL DIMENSIONS IN MILLIMETRES
MAT: 1mm ALUMINIUM

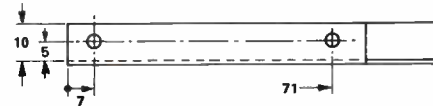


Fig. 7. Details of shield-support bracket.



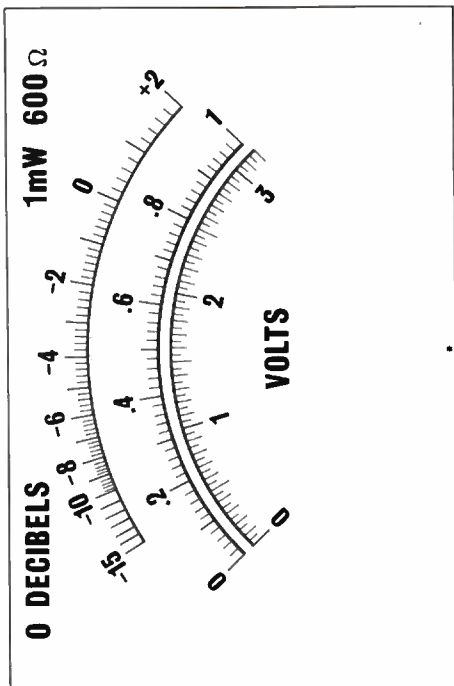


Fig. 8. Artwork for meter (shown full size).

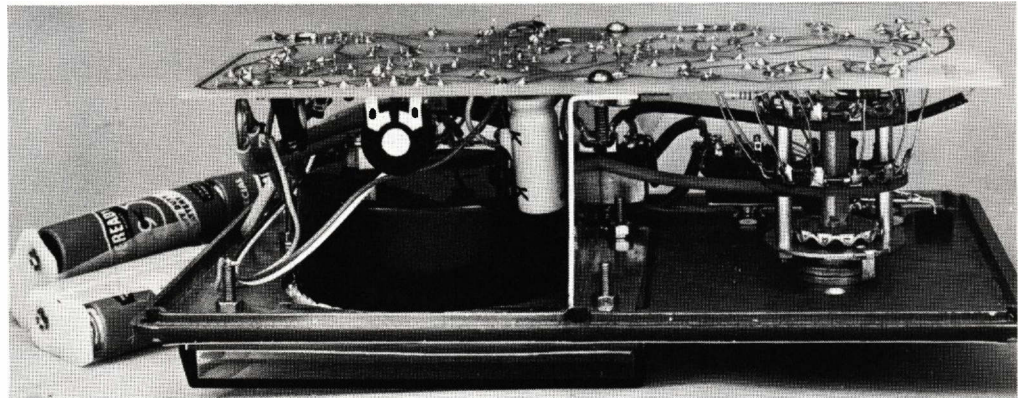

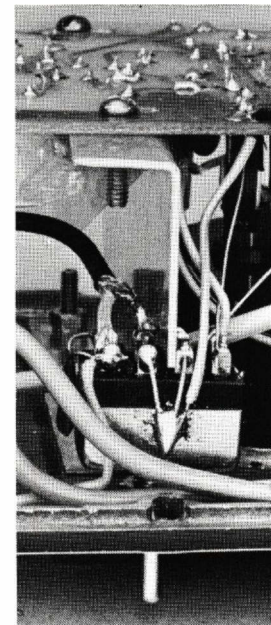This internal view of the meter shows on the right, how the range switch is wired to the printed-circuit board. Note also the shield.



Note how the shield passes between the earthed, centre contacts of the 'A' weight switch.

on ac should be about 10% higher than on dc. If it is 10% lower the leads to switch SW1b should be reversed.

6. In the ac mode select 'A'-weight and apply a 1 kHz signal of sufficient level to obtain a 0 dB indication on the 1 volt range. Vary the frequency over the whole audio range and check that the response as shown in Fig. 4 is obtained.

7. Go back to 1 kHz and check that zero dB is indicated in the 'A'-weight mode. Now select 'flat' and adjust RV2 to obtain the same reading.

8. Apply an accurately known voltage with the instrument set to the


flat and ac modes and adjust RV4 to give the correct reading.

9. Apply a dc input of known polarity and check that the correct LED illuminates. If not, reverse the leads to the LEDs.

This completes the calibration and the instrument should now give accurate readings on all ranges and at all frequencies within the specified range. ●

It's a beauty at just \$399

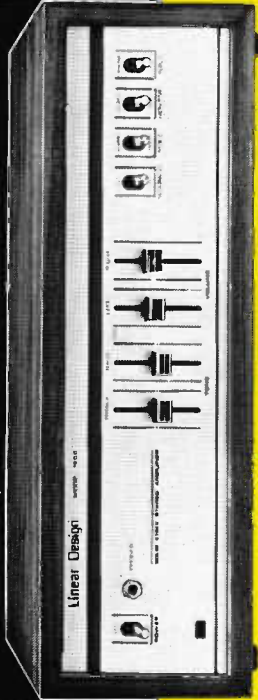A completely integrated and balanced system including turntable, amplifier and famous Jensen speakers. Hand-picked to give you the best sound at the best price.



LINEAR DESIGN GST II

TURNTABLE — DIAMOND STYLUS

A transcription type manual turntable employing a unique suspension system that reduces rumble and acoustic feedback. The transcription tone arm is of the low inertia type and provides excellent tracking characteristics. It is equipped with a patented bias compensation system. Shure MS8C Cartridge with elliptical diamond stylus. See it, you'll believe it.

NEW RELEASE! LINEAR DESIGN 1600

AMPLIFIER

18+18 Watts RMS. Both channels driven. A unique all solid state amp. designed with great care to give you years of hi-fidelity listening. Simply styled, yet it retains features only found in more expensive units. Sensational value at Douglas Hi-Fi.

JENSEN MODEL 2

SPEAKERS.

A magnificent two way two speaker system with a smooth overall frequency and transient response. Midrange is excellent. Aust. Hi-Fi said: "The Jensen Model 2 are highly talented performers with a magnificent midrange. We recommend these systems without any hesitation". So come in an hear these great performers at Douglas Hi-Fi.


SCOOP! QUALITY CASSETTE DECK



\$99

Big bulk purchase, small selling price. Features auto stop on all functions, pause button, chrome and low noise tape equalization. This incredible cassette deck is also available with DOLBY, for just \$129. This is an absolutely RED HOT bargain, and if you've been looking at Dolby prices you'll know just how good it is. Don't delay. Stocks are going like crazy at this unheard of price.

\$129

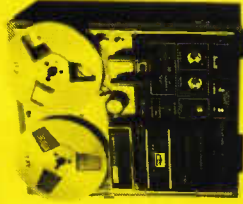

'AKAI' 1900D REEL TO REEL & CASSETTE COMBINATION

\$379

SPOT INC

Two for the price of one! It has both way transfer. Life time guarantee. GX heads, it's another sensational Douglas Hi-Fi discount and it's loaded with features you find on professional recording equipment.



'AKAI' 46D \$289 DOLBY CASSETTE DECK

With auto Dolby noise reduction system to assure clear distortion free sound reproduction. Life time guarantee on GX head, auto stop, high frequency response, tape selector switch, high volume recording level O.L.S. switch 30-18,000Hz. The works, at the craziest discount price.

• CASH
• LAY-BY
• TERMS



NEWS REPORT

A continuous demonstration on a full range of AR and BOSE Hi-Fi speakers.

WARNING:

Douglas Hi-Fi is the city outlet for Linear Design products. Beware of second hand units being passed off as new in other stores.

TAPE SPECIALS

Memorex C90 \$2.50
Memorex C90 Chrome \$3.30
BASF C60 Chrome \$1.30
Agla C90 Super Chrome \$2.50

HI-FI PICK-UP CARTRIDGES

Stanton 681 EEE \$55
Shure 55E \$13

NEW RELEASE...

JENSEN

See the new '76 O. P. C. concept speakers just released by Jensen.

JENSEN O. P. C. SPEAKERS (PAIR) 5 YEAR GUARANTEE!

Jensen model 21 \$229
Jensen model 22 \$319
Jensen model 23 \$419
Jensen model 24 \$549
Jensen model 25 \$699

Douglas·hifi

SELLS SOUND FOR LESS

City Showroom 191 Bourke St., Ph. 639321

Code converters and display systems.

IT IS both necessary and convenient to transfer data between sub units of a digital system, by means of some kind of code. We have seen in the previous section how counting stages are sometimes arranged to count in BCD (Binary Coded Decimal), and how this form of code must then be 'converted' into another form that is suitable for the particular kind of display device used. Thus codes and code converters are of great importance in digital instrumentation.

There are a multitude of digital codes in use for communication, data interchange, and for numerical manipulation and display. Although many of the earlier codes used have now been discarded, there are still dozens in use. In this section we will not discuss codes like ASCII, Baudot, Excess 3 etc, which are computer and communication codes, but restrict ourselves to those codes and converters which are concerned with counting and display.

The main counting codes used in instrumentation are binary and BCD. Octal and Excess 3 are other counting codes used in computers but seldom in instrumentation. Converters are needed to change from any one of these codes to any other, and between any one code and decimal or vice versa. In addition the counting code in use needs to be converted into a form suitable for driving particular kinds of display (seven-segment, dot-matrix and neon tube, etc).

For example we find converters for binary to BCD, binary to decimal, BCD to seven-segment, and BCD to decimal, to mention just a few of the possible combinations.

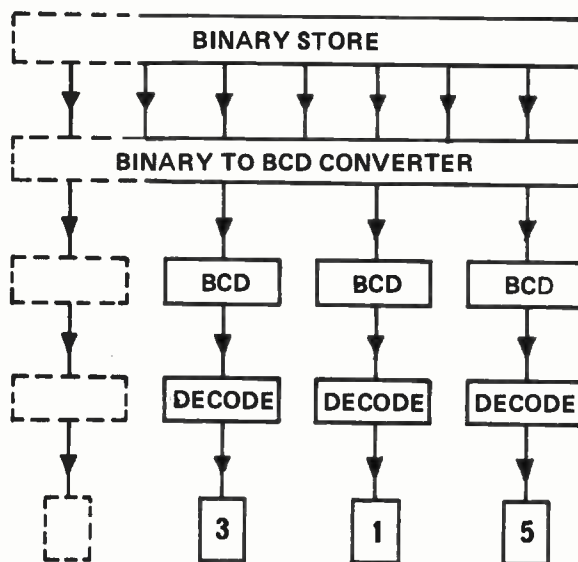


Fig. 1. Basic arrangement of binary to BCD converter and display decoders.

BINARY TO BCD CONVERSION AND VICE VERSA

To convert binary to BCD a common method is to set a binary counter — see Fig. 3 — to the desired number either by direct counting upward from zero, or by transferring the value across from another stage with a parallel converter. Clock pulses are then fed into both this binary counter, now set to count back down to zero, and to an up-counting BCD counter. A detector senses when the binary counter reaches the 0000 state upon which any further changes in the count state of both units are inhibited. The BCD equivalent of the binary number is now held in the BCD counter.

At this point the BCD number is cleared into a store or is available for

any other system need, the binary counter is reloaded and the process repeated to convert the next number from binary to BCD.

The reverse, BCD to binary, is accomplished in the same manner except this time the roles are reversed as shown in Fig. 4. The BCD counter is set to the desired number, the clock, when enabled, clocks the BCD counter down to zero and at the same time the binary counter upward. When the BCD counter reaches zero state its outputs logically inhibit the clock input to both counters. The process is repeated for each new number after clearing and resetting the two counters to the correct starting conditions.

This serial method is fairly slow and a much faster method is to use logic gates in a parallel arrangement. The

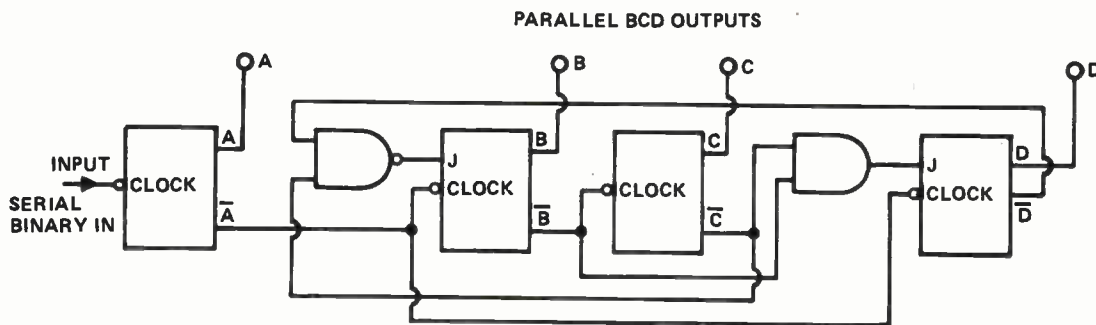


Fig. 2. An asynchronous BCD counter provides a parallel BCD coded output which corresponds to the number of pulses fed to the input.

ELECTRONICS -it's easy!

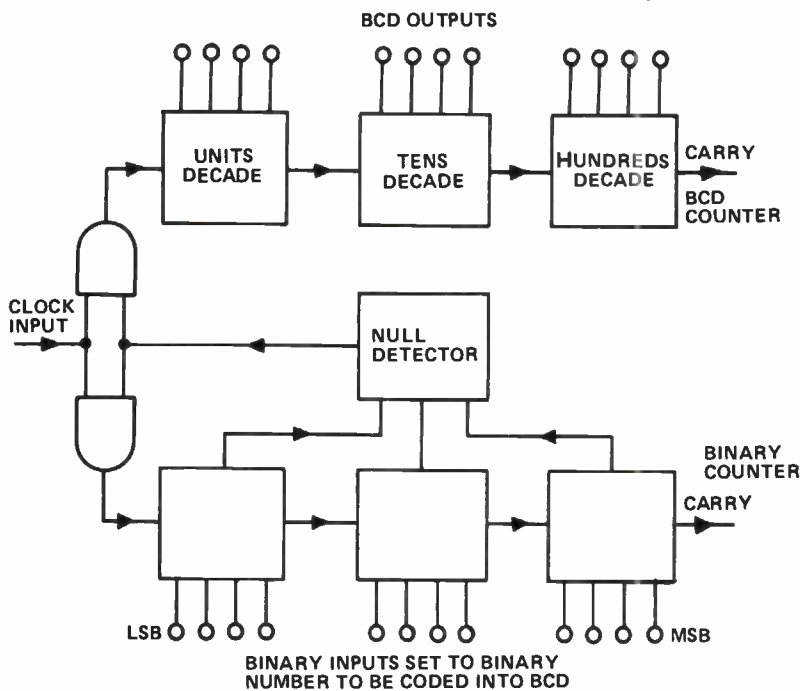


Fig. 3. System required to convert a binary number to its BCD equivalent.

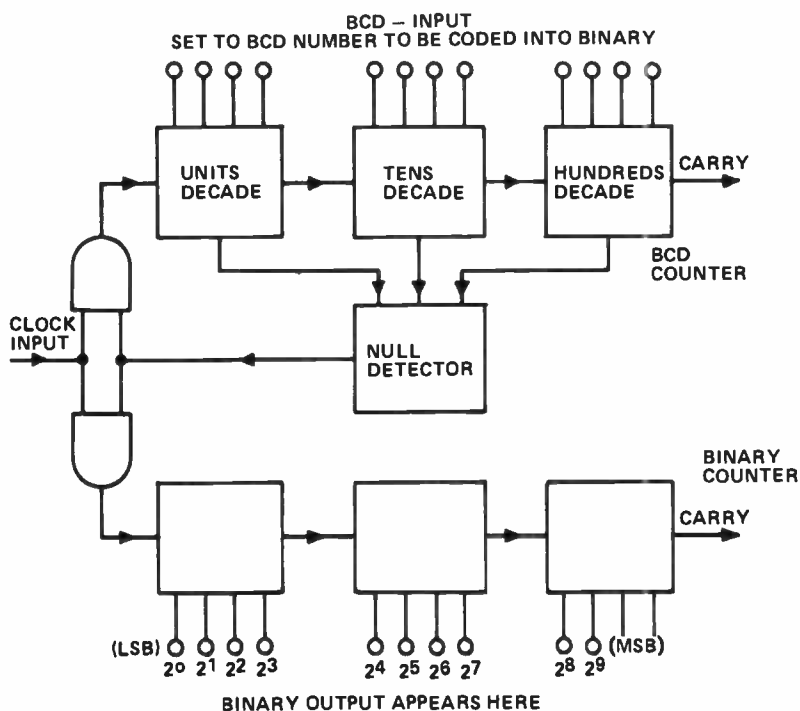


Fig. 4. To convert a BCD number to its binary equivalent the same circuit as Fig. 3 is used but the BCD number is now the one pre-loaded.

parallel method works well for BCD to decimal and other cases but requires innumerable connections when set to convert decimal or BCD back to binary. It is little used in this reverse mode.

BINARY CODED DECIMAL TO DECIMAL AND OTHERS

Each BCD stage stores its decimal number as some form of binary code

using four bits. The 1-2-4-8 weighting is the most usual form used but other codes such as the 'excess three' and the 'Aiken' variations, are also used. Thus, each of the digit values 0 to 9 (in decimal) is represented by four lines, each having a '0' or a '1' state. This is demonstrated by studying the truth table for equivalent BCD and decimal states given in Fig. 5.

When the output must finally appear

as decimal indication, it is necessary to energise the display or character printer segments appropriately. Displays, such as the neon tube or the columnar style — see previous part — require one output for each of the 0 — 9 numbers. From the truth-table of Fig. 5 it can be seen that to energise, say, a decimal '4' output we must set up a logic gate that provides an output when the BCD state is 0100. For '8' we need a BCD state of 1000. It is not possible to totally economise by using only '1', as the logical indications for this leads to ambiguities between numbers. On the other hand there is no need to arrange for all code sequences and bit combinations as that introduces redundancies using up extra unnecessary gates.

By careful design, and the use of inverters to invert '0' to '1's, it is possible to find a minimum number of AND gates and interconnections that will produce the 10 decimal states (0 to 9) as distinct outputs from the four-line (A B C D) outputs of the BCD stage. One such scheme is given in Fig. 6. Thus, by the use of logic gates alone we can provide a parallel code conversion from BCD to decimal.

Getting from BCD to a format suitable to drive a seven-segment display requires more gates, see Fig. 7, but the technique is basically the same. A decoder suited for the BCD to decimal requirement of a neon tube is quite unsuited to drive a seven-segment display. As both these and other conversions are in great demand they are available as simple ICs. Further, in some options the decoding logic is integrated onto the same chip as the BCD counter stage.

In practice the need to understand the internal operation of the decoder arrangement rarely arises, for the ICs are clearly marked with the connections to be made — it is just a case of making correct connections between the counter-stage chip, the decoder chip, and the display.

THE NEED FOR DISPLAY DRIVER STAGES

The power levels available from decoder stages are rarely adequate for direct drive of display units. A buffer stage which raises the power level is normally required. Again, these are generally incorporated into the decoder IC stage. Such integrated units are known as decoder/drivers. Different displays, even of the same format, require differing power needs so it is important to select decoder/driver stages suited to the display being used.

The buffer stage of a decoder/driver obtains current (or voltage gain) by the use of a transistor stage such as a Darlington pair or an emitter-follower

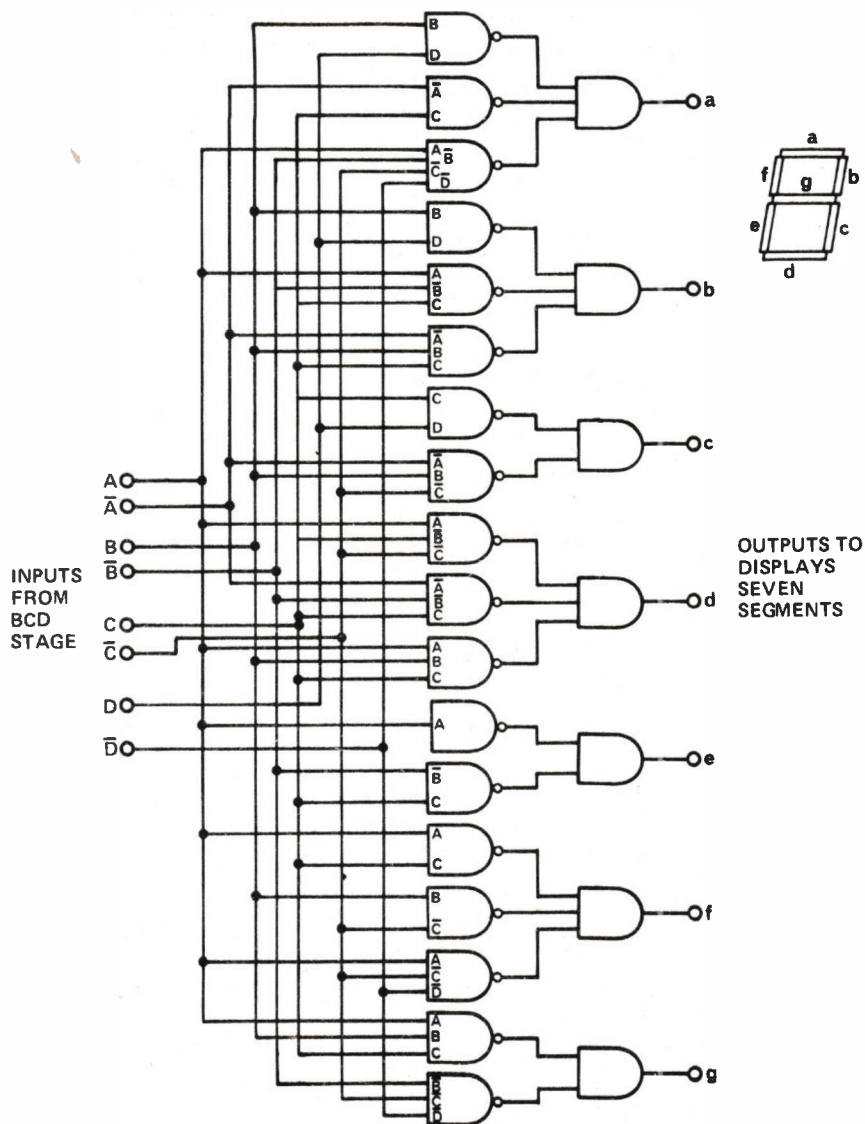


Fig. 7. Logic for converting BCD to seven-segment display format.

write the '0's that appear at either end of a number, for example, 0001357.0 as could be held in an eight digit display, is better presented as 1357 or as 1357.0. A facility is sometimes provided in display-counter systems that blanks unnecessary zeros. Leading zero suppression is performed within the decoder stages of Fairchild seven-segment decoders by connection of the ripple blank output RBO (ripple because each stage connects to the next) of the decoder stage to the ripple blank input RBI of the next lower decoder stage. Blanking of least-significant zeros is not usually included. The actual arrangement for blanking control varies from maker to maker. Fig. 12 shows a method using ripple blanking.

The blanking facility can also serve other purposes. It can, in certain applications, be used to blank-out illegal display values resulting from incorrect codes. The RBO output also provides a detection output indicating when the decoder stage is at the BCD zero state.

Blanking is also valuable as a way to save display power for it can be used to hold all displays off until there is something to display.

When no blanking input is provided it is also possible to blank the system by applying the spare BCD code states that result in no drive to the display. Yet another procedure is to disconnect the supply from the display itself.

INTENSITY CONTROL

Displays are usually manufactured to supply one value of output brightness. When brightness is to be tailored to

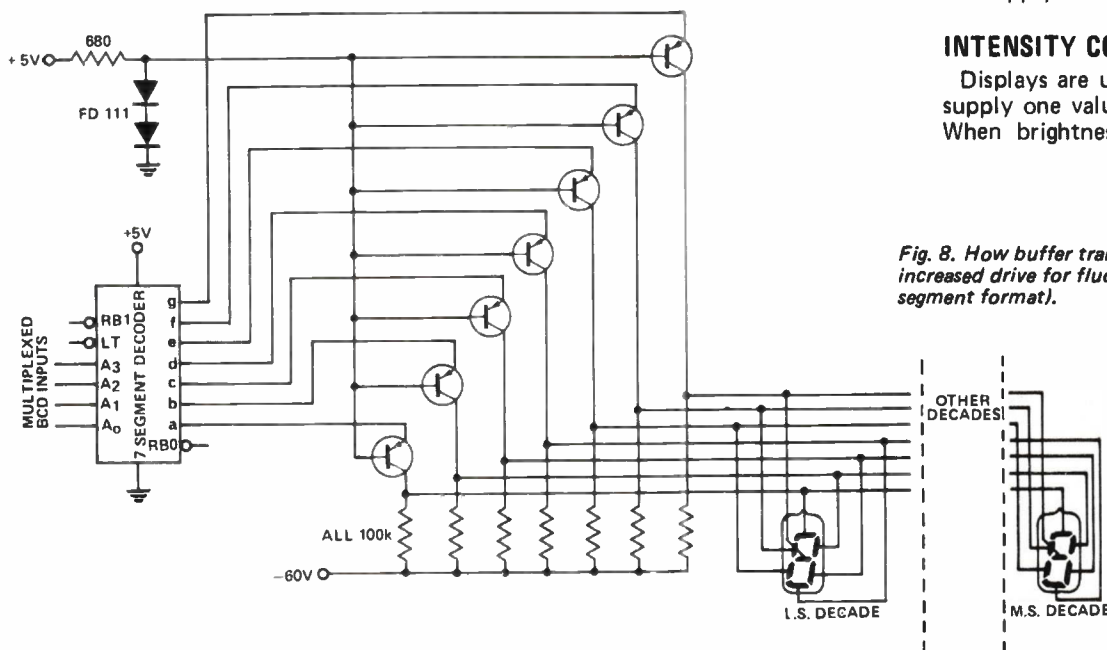


Fig. 8. How buffer transistors are used to obtain increased drive for fluorescent displays (seven-segment format).


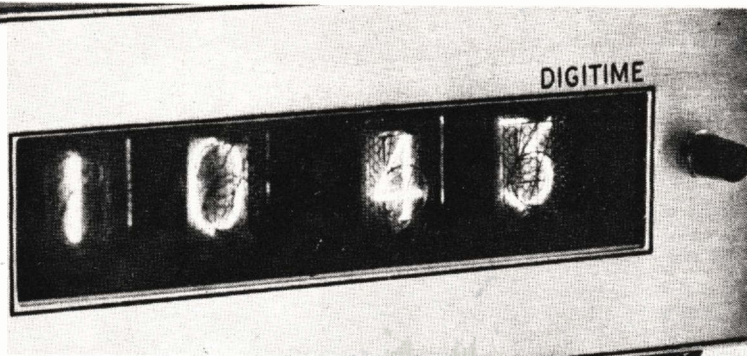
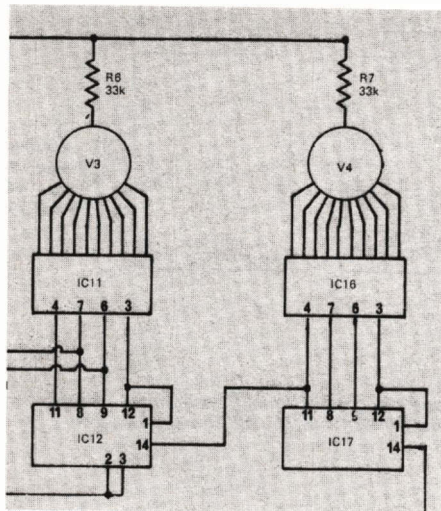


Fig.9. This digital clock illustrates use of counter stage subsystems.
 (a) The frontal appearance of the Nixie display.
 (b) Top view of component assembly.
 (c) Circuit diagram of counter to display section.
 (d) Component overlay. The V1 to V4 positions are the sockets for the Nixie tubes, behind are the decoder/drivers which have the dividers behind those again.

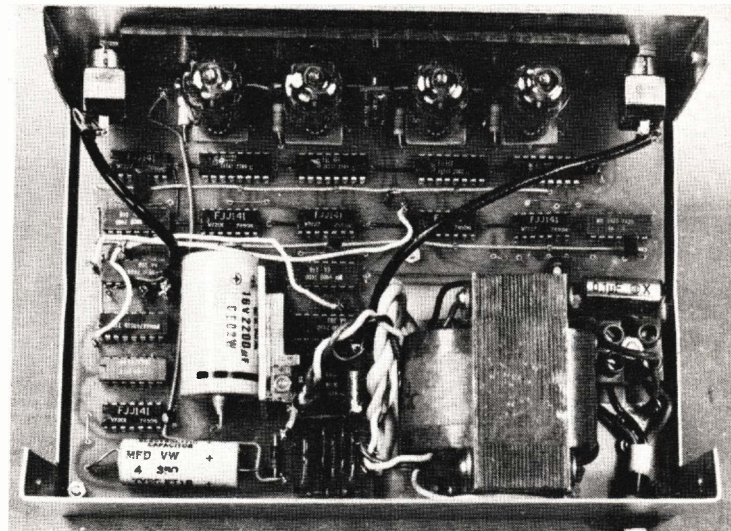


(c)

DISPLAY TUBES

DECODER/DRIVERS

DIVIDERS

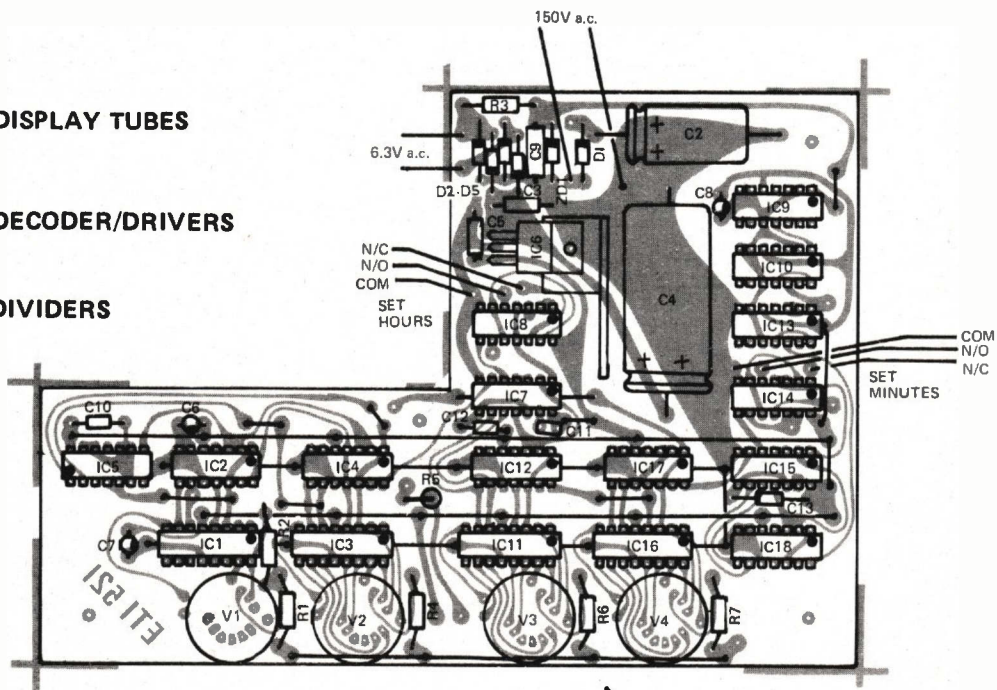

(d) CIRCUIT SHOWN IN (C)

particular ambient light conditions an appropriate kind of display can be selected that provides the desired luminance level. This however, does not always lead to a satisfactory choice when other considerations are taken into account.

Intensity of any display, however, can be controlled in a digital manner (that most desirable in digital systems) by turning the display on and off with an appropriate duty cycle (ratio on to off period). This is called pulse-duration intensity modulation. Provided the repetition rate exceeds 100 Hz the eye cannot detect that the radiation source is being modulated. Modulation may be achieved with any of the blanking methods given above.

The schematic of Fig. 12 includes an intensity modulation facility.

With LED displays, intensity modulation can actually increase the apparent brightness. The human eye has a characteristic response to radiation that has greater sensitivity to the peak value of modulated light, rather the average or rms power. LEDs can be pulsed at high frequency with high peak currents because of their nanosecond response time. The net result is apparently higher brightness for a given amount of power.

STROBING OR SCANNING

Displays which generate characters in the 7 x 5 dot matrix or seven-segment formats require decoding logic which

energises the correct dots or segments. If each character has its own decoder we would need 7 lines for each digit of a seven-segment display. And 35 lines for each digit of a 7 x 5 dot-matrix display!

Obviously a method is needed to reduce the number of lines and circuitry required for multi-digit displays.

One such method is called strobing where lines of dots or segments are illuminated sequentially. The 7 x 5 array can be either strobed as lines horizontally or as rows vertically as illustrated in Fig. 13. Each row is selected one by one in sequence and the appropriate diodes in the row energised. Provided each row is

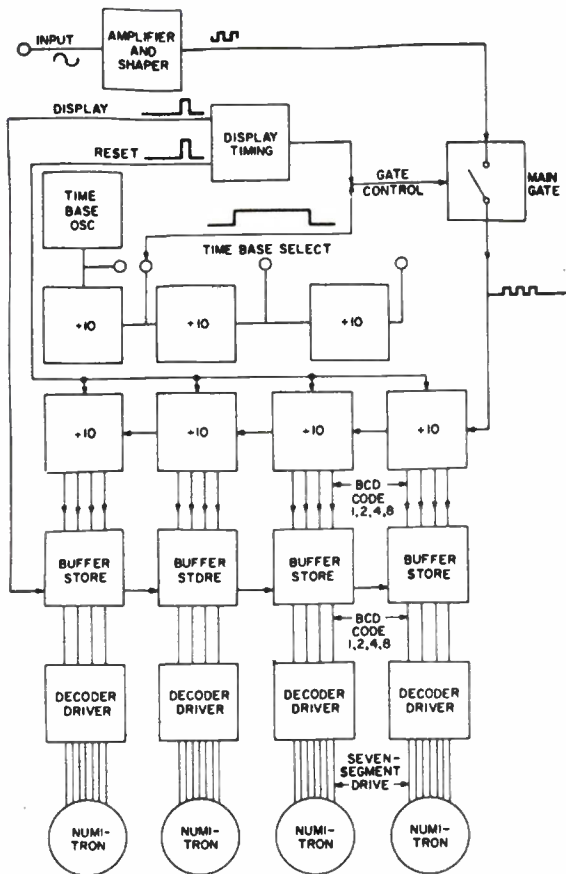


Fig. 10. Buffer stores are used to latch the display causing it to remain steady for selected periods. (circuit shown is a counter/timer using RCA incandescent displays).

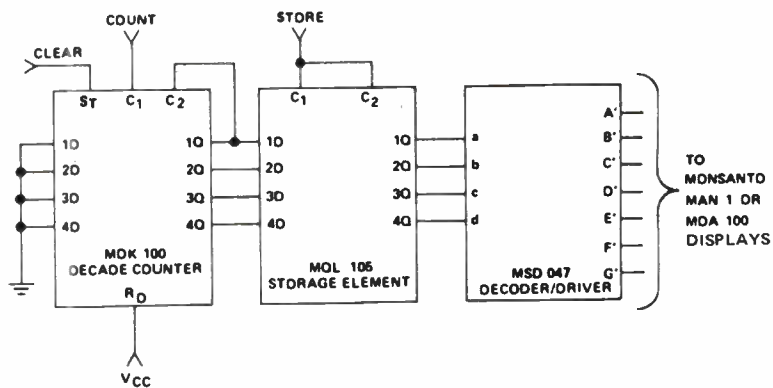
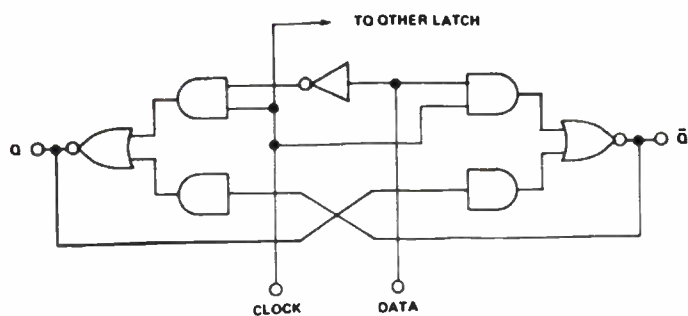


Fig. 11. Schematic (a) and pin connections (b) of counter, latch decoder system using the Monsanto MQL 105 four-bit bistable latch.

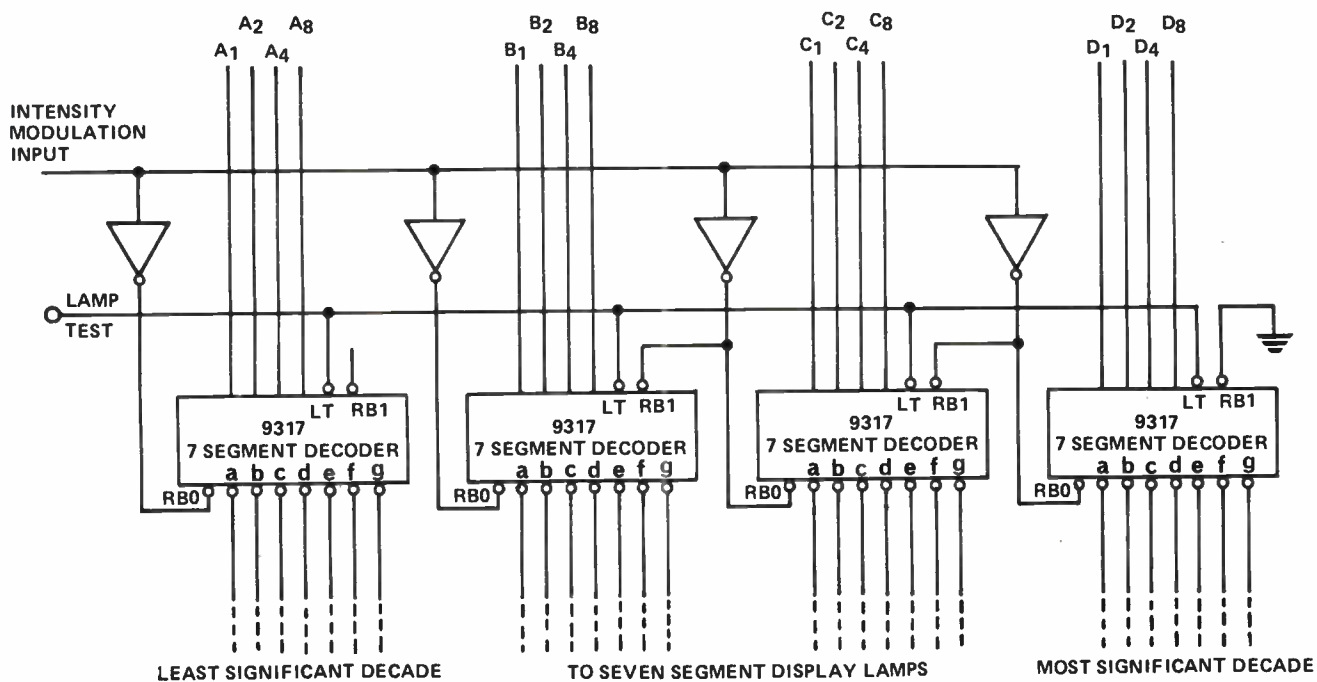


Fig. 12. Connections for ripple blanking in a four-decade display system. (RBD ripple blank output, RBI ripple blank input).

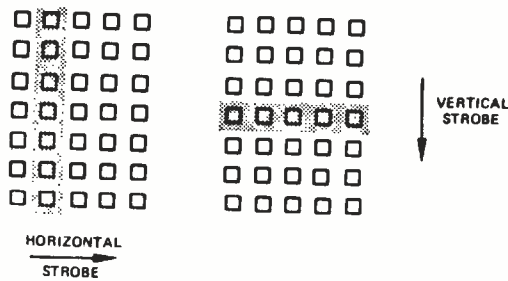


Fig. 13. Horizontal and vertical strobing of a 7 x 5 dot matrix display.

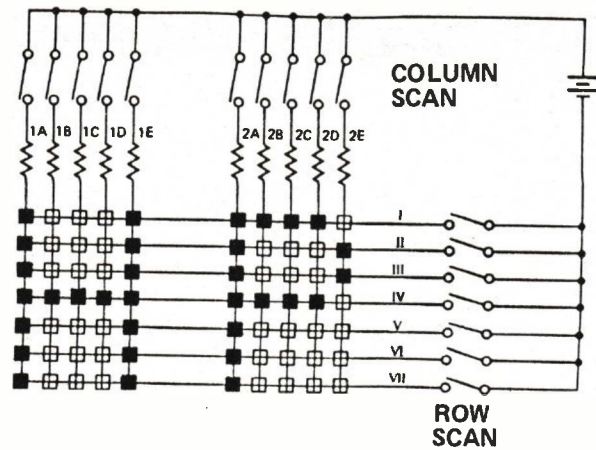


Fig. 14. Schematic of switches needed to address a 7 x 5 dot matrix.

returned to at no greater than 10 ms intervals the characters will be flicker free.

A diagrammatic illustration of how specific diodes are selected in a row is given in Fig. 14. The row switches are scanned in turn to cause a vertical scan. Simultaneous excitation of the other switch sets decides which diodes in the row are to be illuminated.

A strobing system requires a procedure to sequence the scanning action and a method of setting the selection switches that corresponds to the characters needed. The whole is controlled by a clock and timing generator. Storage buffers are also required to store the sequentially generated information. The task of creating the appropriate character timing codes is performed by a read-only-memory ROM. Clearly this method adds up to a complex system... really beyond this course's purpose. A schematic block diagram of a vertically-strobed five-digit LED display is given in Fig. 15. Although of apparently great complication this method is less expensive to employ than direct actuation through fixed gates. (Considerably more detail is to be found in the suggested reading list).

Another scanning method scans the matrix as a raster — across a row, one by one, and then to the next row. Strobing obtains its advantages by time-sharing common elements in a time-multiplexed manner.

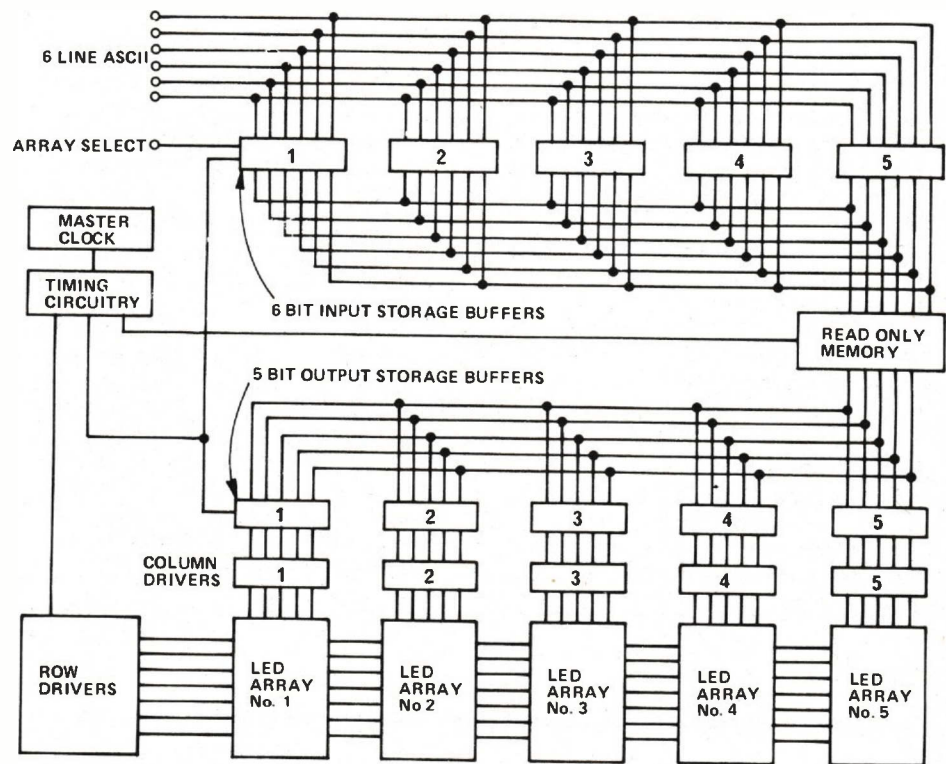


Fig. 15. Basic block diagram of a vertically strobed display using 7 x 5 dot-matrix devices.

MULTIPLEXING

When the input data to be displayed appears in serial form or when large numbers of displays (over four digits) are involved, multiplexing (selection of complete digits sequentially) becomes advantageous for driving seven segment and one-of-ten displays. The basic multiplexing system requires the main system units shown in Fig. 16. An upper limit to the number of digits is around 12 and higher for LEDs. There are disadvantages; namely, a higher voltage is required in the

display to achieve the same brightness (LEDs are not so critical as other forms of display); the scan frequency must be at least 100 Hz to prevent flicker; transients must be carefully decoupled; and a clock failure (which stops the scan) may produce partial display failure because of excessive dissipation brought about by the increased voltage applied. (It is usual to include a failsafe protection circuit).

Again, the complexity appears great but in practice the multiplexed system

ELECTRONICS —it's easy!

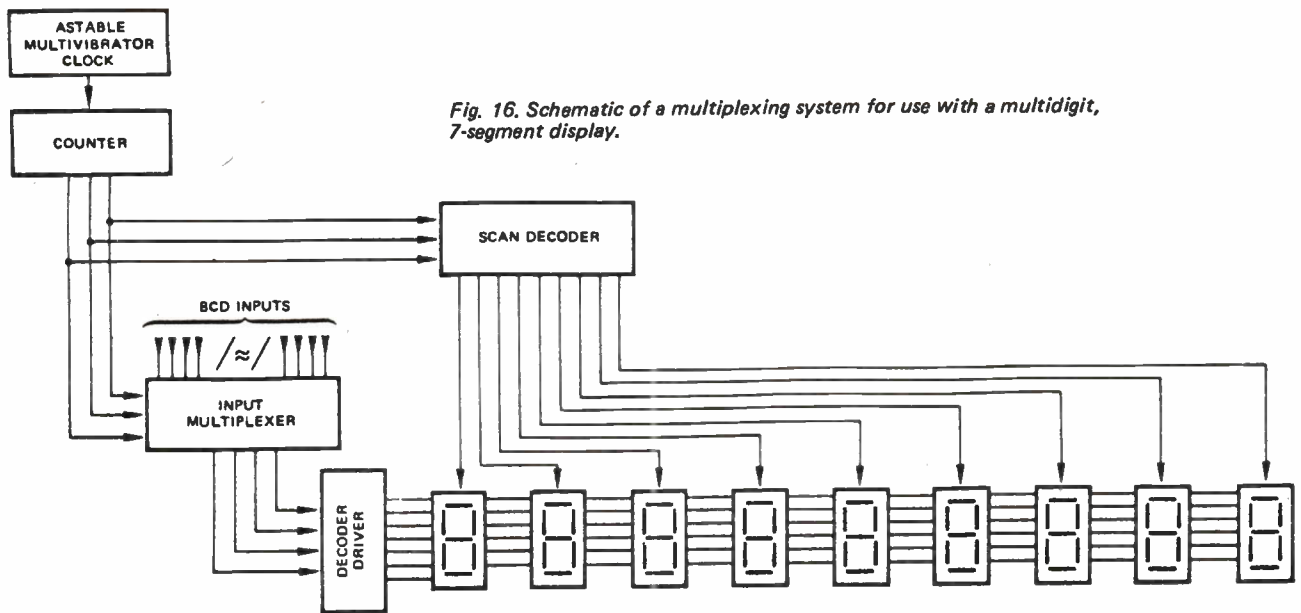


Fig. 16. Schematic of a multiplexing system for use with a multidigit, 7-segment display.

is simpler to build. For example, a multiplexed, seven-segment display, with storage for eight digits, involves around 10 dual-in-line packages and a few discretes which compares with about 16 ICs for a non-time shared system.

To further reduce the connections that must be made upon assembly, manufacturers offer multi-digit displays in which the anodes and cathodes of the LEDs are internally connected ready for multiplexed operation.

OTHER CONVERTERS

Apart from digital-code converters other converters are required in instrumentation: for example, when interfacing different systems of logic,

eg TTL to CMOS, it is necessary to alter the dc levels of signals so that the output of one system provides the logic levels required by that following. This may require amplification or attenuation or shifting of a level. However specific ICs are marketed to suit various interfacing requirements. Other converters are needed for sending digital signals through standard transmission lines in communication links, for receiving signals from lines, for increasing the logic level differences to increase noise immunity (again for transmission), and units that drive peripheral devices such as relays and indicators. Signal inversion may also be necessary — we have already dealt with the inverter block earlier in the course.

Another class of converter is needed for converting digital signals to analogue voltages (D to A) and analogue voltages (and currents) into digital form (A to D). Such converters will be dealt with in the next section.

Further Reading:

"Digital Display Systems" referred to in the previous part deals with blanking and multiplexing.

"Solid State Alphanumeric Display Decoder/Driver Circuitry" — Hewlett Packard application note 931 gives details of scanning methods used with 7 x 5 displays.

"Mullard TTL Integrated Circuits — Applications" includes a chapter devoted to various kinds of code converter gating layouts. ●

IMPORTERS OF ELECTRONICS! ARE YOU PAYING CUSTOMS DUTY UNNECESSARILY?

If you are not aware of the intricacies of the Australian Tariff, the Customs By-Laws and Customs requirements you could well be paying duty unnecessarily on your products.

We offer you expert advice in all Tariff matters including —

- Tariff Classification
- By-Law submissions
- Valuation and Dumping
- Invoice and Documentation requirements
- Industries Assistance and Temporary Assistance Inquiries
- Customs Clearances

For further information contact: TREVOR WALLIN,,
WALLIN MERRELL ASSOCIATES PTY LTD,
TEL: (02) 212-4133.

ADVERTISERS


More than 30,000 people buy ETI each month.

You can reach these people for less than a quarter of a cent* each via an advertisement this size.

*Casual rate (1/8 page) lower rates apply to contracts.

ASTRONOMY

AN EXCITING AND
FASCINATING HOBBY

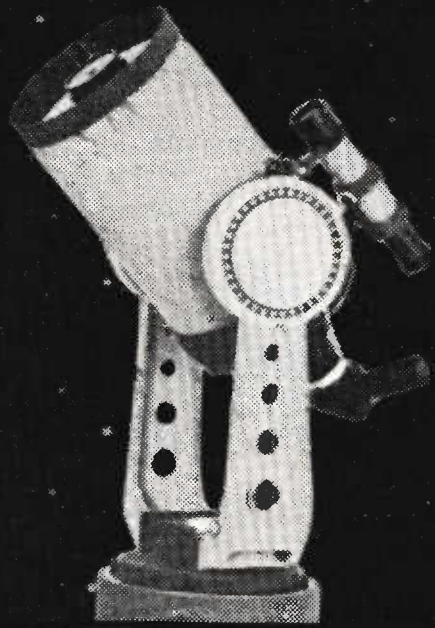

Drop in and take a look at the revolutionary Celestron Schmidt Cassegrains, the precision Unitron refractors, and the big build-it-yourself reflectors. Browse through our range of books, charts and atlases especially selected for the Southern Observer — or send 45c for informative catalogue.

ASTRO OPTICAL SUPPLIES PTY LTD

11 Clarke St.,
Crows Nest,
Sydney. Ph. 43-4360

Mid City Arcade,
200 Bourke St.,
Melbourne. Ph. 663-2761

MARINE CB, and NOVICE 27 MHz ANTENNAE

- Base Station 5/8, 1/2 and 1/4-Wave Ground Planes.
- Yagi & Quad Beams, multi-element.
- Marine & Vehicle Mobile Whips, 1/4-wave, Helical & Centre-loaded.
- Transceivers for Marine, Novice, 27 MHz, Amateur HF, VHF & UHF.
- Station Accessories, HF & VHF Antennae, Ant. Tuning Units, SWR Meters, Digital Clocks, SSTV, Baluns, Dummy Loads, Freq. Counters, Monitorscopes, Monitor Receivers, etc.

Write for details
Sole Authorised Australian Agent for
Yaesu Musen Co. (Japan). Reps in
most States.

**BAIL ELECTRONIC
SERVICES,**

60 Shannon Street, Box Hill North,
Victoria, 3129. Ph: 89-2213.

 **TRIO**

NEW Trio CS-1560


**The 15MHz dual trace with a
10MHz price tag**

Trio certainly know how to pack value into their scopes. Not only are you getting a 15 MHz bandwidth but Trio give you two x 10 probes completely free. And they're worth around \$35.00 each.

The CS-1560 is a highly reliable and stable dual trace triggered sweep oscilloscope with all solid state circuits and a 130mm screen. With its high vertical sensitivity of 10mV/cm, bandwidth of DC to 15MHz, and sweep time of 0.5µsec/cm to 0.5sec/cm, it is ideal for a wide range of applications from analyzing and adjusting television sets to various research, development and production processes, and also for educational purposes.

Check these features:

- Extremely wide bandwidth of DC to 15MHz with its high vertical sensitivity of 10mV/cm.
 - Sweep time extends from 0.5µsec/cm to 0.5sec/cm in 19 ranges. Further, as TV-V and TV-H Syncs are available for measuring video signals and x5 magnified sweep, its range of application is extremely wide.
 - Very easy X-Y operation with high input sensitivity for Lissajous measurements.
 - For dual trace operation, either CHOP or ALT is automatically selected by the sweep time.
 - With "AUTO FREE RUN" function, a sweep is generated even without an input signal.
 - Thanks to newly developed blanking circuitry, starting of waveform display is clear and sharp.
 - Stabilized accelerating high voltage DC power supply (with DC-DC converter) makes the sensitivity and intensity free from effects of line voltage fluctuations.
- You get all this plus FREE x10 probes for \$399.00 (plus Sales Tax).

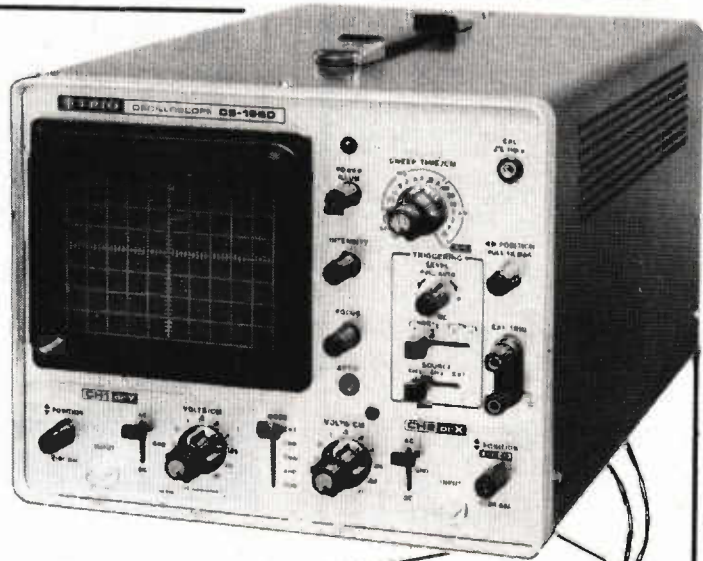

**complete with
FREE x10 probes**

\$399
* Plus Sales Tax if applicable.

Check these too!!

10MHz single beam triggering scope CS-1557
This is the single beam companion to the 1560. Specification similar to the 1560. This instrument also has a 5" rectangular display. Used for T.V. service work or as general Lab. instrument, the 1557 represents outstanding value for money.

1.5MHz low cost scope CO1303A
Although primarily intended for the hobbyist and educational use, the Trio 1303A is suitable for many other applications. Vertical sensitivity is 20mV/cm with a bandwidth from DC to 1.5MHz. A direct input facility permits displays up to 150 MHz.

 **bankcard**

welcome here

Sydney: 68 Alexander Street, Crows Nest
Tel: 439 3288


Melbourne: 53 Governor Road, Mordialloc
Tel: 90 7444

PARAMETERS PTY LTD

ELECTRONIC DISPOSALS

297 Lt. Lonsdale St.,
Melbourne. 3000
Phone: 663-1785

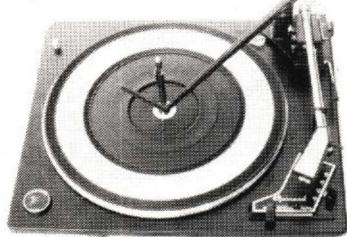GARRARD S.L. 65B Automatic Stereo Turntable



with laboratory balanced synchronous motor. Adjustable balance — anti-skate — lift and heavy platter including Shure magnetic cartridge. Less than 1/2 price at only \$47.50ea. P&P \$4.00

Stereo Amplifier and R.F. Board 4 watts RMS per channel including circuit diagram. Boards are complete with all transistors, capacitors — resistors, etc. and are brand new — famous make. Only \$6 set P/P 60c.

Healing 1280 — 1290 T.V. circuit assembly. Sound output IF, AFC video amp Sync. Separator. Brand new with all components inc. I.C. and 17 transistors — normally approx. \$30 as Spare Part. Our price only \$4 each P/P 60c.

Transistors — AY 9150 PNP 60v 150w — AY 8110 NPN 60v 115 80c ea. AY 8139 NPN — AY 9139 PNP 40v 10w 45c ea. AY 6120 NPN — AY 6121 PNP 50v 1A 40c ea. 2N5088 NPN PN 3694 NPN 10c ea. BF 198 — BF 199 NPN 20c ea. P&P 30c.

A.3065 TV/FM Sound System, I.C. Silicone Dual In Line suitable for a wide variety of applications including T.V. sound channels — line operated and car F.M. radios and mobile communication equipment — brand new. Only \$1 ea. P/P 40c.

Balance Meters 1 1/2" x 7/8" x 1 1/4" Deep 200 UA \$2.25 ea. P/P 40c.

M.S.P. 250V A.C. 3 AMP D.P. Toggle switches 50c ea. P/P 25c.

10 1/2" 3 Watt. Wire wound pots 75c ea. P/P 25c.

7" Dia. Alum. Fans 240V A.C. \$6 ea. P/P \$1.

Multiple Electrolytics. 200 μF — 50 μF — 25 μF at 300V Plus 100 μF at 325V. V.W.I. \$1 ea. P/P 30c.

LEVEL METERS 200 micro amp sensitivity size 1" x 1" x 3/4" \$1.50

SOLENOIDS — tape recorder type. 12V D.C. 5Ω coils. 1 1/2" x 1 1/2" x 3/4" \$2 ea. P/P 30c.

TRANSISTOR RADIO. 5k miniature switched pots. 30c ea. P/P 15c. Miniature 2 gang variable capacitors 30c ea. P/P 15c.

Slide Pots. Single gang. 500ΩA, 20KA, 25KA, 100KC, 200KA, 200KB, 500KA, 500KB, 1 meg.D, 35c ea. P&P 35c. Dual gang — 50KA, 250KB 1 meg.C, 2 meg.C, 60c ea. P&P 35c.

Skeleton Preset Pots. 100Ω — 220Ω 470Ω, 2.2K, 10K, 22K, 47K 10c ea. P&P 20c.

Philips 8Ω dual cone 6" x 4" speakers \$2 ea. P&P 60c.

LARGE RANGE OF COMPONENTS — GOVERNMENT AND MANUFACTURERS DISPOSAL EQUIPMENT, ALSO STEREO AND HAM GEAR ALWAYS IN STOCK.

a priceless GIFT idea —

flexible, cold fibre-optic



treasured by all who work
with electronics and electricals

available from
Department Stores
Electronics and Electrical Stores

ESALIN PTY. LTD

P.O. Box 268,
Croydon, Vic. 3136

NEW RELEASE!

Electronic digital clock kit P 107

12 cm
x
8 cm

\$36.50
Complete
P&P \$2



with alarm and seconds readout

*Digital clock builders special
Flourescent digital clock display.



\$9.90
P&P \$1

AM PM with spec sheets

TRANSISTORS: BC 107, 108, 147, 148,
149, 157, 158, 159.

12 for \$2 P&P 45c

AC 187, 188, 127, 128, 70c ea. P&P 45c

L.E.D.'s 6 for \$2 P&P 45c

DIODES 1N4002

25 for \$2 P&P 45c

Primo Electret. microphones EMU 522
\$24.50 P&P \$2

LINEAR TECHNICS

P.O. Box 180,
WAVERLEY, NSW. 2024.

ETI by jaycar

PROFESSIONAL SOUND
EQUIPMENT FOR THEATRE
AND ROCK BANDS

427-R Two channel graphic equaliser. Features Cannon inputs and outputs and standard 19" rack mounting. R.R.P. \$195.00. Standard kit still available at \$110.00.

433-R ETI's new 3 way electronic crossover. Features selectable crossover points, buffered outputs, Cannon in and out and 19" rack mounting. R.R.P. \$155.00.

414 8 Channel master mixer; Now features Cannon inputs and outputs, robust vinyl cabinet facilities for use with stage mixer, new look front panel. R.R.P. \$547. Standard kit still available for \$254.00.

413 100W Power Slave. 1/2 rack mounting. Cannon inputs and outputs. R.R.P. \$135.00. Standard kit still available for \$75.00.

413-2R 2 x 413 mounted on rack panel. R.R.P. \$281.00.

413-BR 2 x 413 bridged to give 200W RMS into 8Ω. R.R.P. \$281.00.

414-16 16 channel sub mixer. Designed for use with 414 mixer. R.R.P. \$487.00. Standard kit still available at \$206.00.

Please send stamped self-addressed envelope for specification sheets and ordering information.

jaycar

PTY. LTD.

Telephone 211-5077
P.O. BOX K39, HAYMARKET
N.S.W. AUSTRALIA 2000
405 Sussex St. Sydney
ENTRANCE OFF LITTLE HAY ST.

Career Opportunities for COLOUR TECHNICIANS

Large international marketing organisation with offices in all states invites applications from experienced Television Technicians with some knowledge of colour.

Company specialises in colour television only and is building a large comprehensive national sales and service network.

Opportunities will exist in each capital city but immediate requirement is for cities of Sydney, Melbourne and Brisbane.

For Sydney, workshop technicians will be required to work at area service centres located at Pagewood, Rydalmere and Greenwich.

For Brisbane area location will be Albion, and Melbourne location, Richmond.

Field Technicians will be required to operate from area service centres and will be provided with suitable vehicles.

- Training will be provided.
- Colour work only
- Best salaries in industry.
- Immediate life cover and superannuation after qualifying period.
- Successful applicants will be brought to Sydney for training.
- Within reason candidates may choose location.

For interesting career opportunity apply:

Mr. "Berry" Beresford,
TRIDENT TELEVISION PTY. LTD.
152 Bunnerong Road,
Pagewood 2035. (Phone: 349-8888)

***trident colour
television*** 

LAFAYETTE

"GUARDIAN 6600"
Direction Finder 6 Band Radio
Beacon - Broadcast - Marine
FM - Aircraft - VHF



\$179-50

6 BANDS

(1) 160-390 kHz Beacon (2) 550-1600 kHz Broadcast (3) 1.6-4.6 MHz Marine (4) 88-108 MHz FM (5) 108-136 MHz Aircraft (6) 147-174 MHz FM VHF

BATTERY OR 240V AC OPERATION (with external adaptor - optional extra).

FEATURES

- Rotatable Antenna for Direction finding and reception on beacon, broadcast and marine bands.
- Telescopic Whip Antenna plus external antenna jack for reception on FM, Aircraft and VHF bands.
- Signal strength, tuning/battery meter.
- Adjustable squelch control.

The "Guardian 6600" is Lafayette's most advanced Portable Radio for top reception plus Direction Finding. 19 Transistors, 15 Diodes and two Thermistors. Individually tuned circuits for best performance on each band. Adjustable RF gain control varies sensitivity and tuning meter for direction finding purposes. Supplied complete with comprehensive operating manual.

SIZE: 11½" W x 10½" H x 3¼" D. Shipping weight 6lbs.

LAFAYETTE

ELECTRONICS

div. of Electron Tube Distributors P/L
94 St. KILDA RD., ST. KILDA,
VIC. 3182 Phone 94-6036

Also available from
RADIO HOUSE PTY LTD,
306 Pitt Street, and 760 George Street,
Sydney, N.S.W.

DICK SMITH ELECTRONICS CENTRE,
160 Pacific Hwy, Gore Hill, N.S.W.

"OXFORD"

RADIO CHASSIS
INSTRUMENT CASES
ENGRAVED & PRINTED PANELS
"MINI BOXES" (Aluminium)
Speaker Cases
Rack & Panels (To Order)
Stainless Steel Work (To Order)

Wardrop and Carroll
Fabrications Pty. Ltd.
Box 330 Caringbah 2229
Phone 525 5222

FERGUSON

Manufacturers of: Electrical/
electronic equipment, wound
components and lighting
control equipment.

BRANCHES IN ALL STATES

FERGUSON TRANSFORMERS
PTY. LTD.

HEAD OFFICE:
331 High St., Chatswood. 2067
P.O. Box 301,
Chatswood, NSW, Australia 2067
Phone: 02 407 0261

Japan's Leading Manufacturer



- Hybrid Circuits
- Power Transistors
- Rectifier Diodes
- H.V. Diodes
- Fast Recovery Diodes
- G.P. Diodes

AUTOTRONICS PTY LTD

P.O. Box 71, Engadine, 2233

HAM RADIO ELECTRONICS BARGAIN CENTRE

390 Bridge Road, Richmond, Vic.
42-5174

Please allow for postage & packing
when ordering by mail

Plenty of BARGAINS for the
Radio Amateur or the Hobbyist.

15 kHz CRYSTAL FILTERS 10.7 MHz
M.E.W. \$5 each P&P 75c
2N3055 TRANSISTORS \$1 each
58 ohm COAX CABLE 100 yd Rolls,
1/8" diam. \$12 roll P&P \$1.75
52 ohm COAX CABLE ¼" diam. 45c
yd, 50c metre.
DOW KEY COAXIAL RELAYS 48 volt
D.C. operation \$15 P&P 75c.
3 "N" TYPE CONNECTORS to suit
above \$5
SPLIT STATOR CAPACITORS with
screwdriver slot drive, 9 pF, 17 pF or
25 pF. Brand new Eddystone type \$3
each P&P 75c
3ft TWIN CABLE AUDIO LEADS with
3.5 mm plug fitted 10 for \$2 P&P
30c.
2" SQUARE FACE 0-1 mA METERS
calibrated 0-60 \$3 P&P 75c.

THIS MONTH'S SPECIAL

NEW 10 transistor AM/FM circuit
boards suitable for modification to
FM tuner \$2.75 each or 3 for \$7.
Thousands of transistors, radios and
circuit boards. Many to choose from,
AM, AM/FM, etc.

NEW 4 TRACK STEREO CARTRIDGE
PLAYERS. 5 watts output 12V D.C.
operation. In sealed carton. \$15. P&P
\$2.50.

"CAPITOL" 8 TRACK RECORDING
CARTRIDGES \$2 each or 3 for
\$5.25.

"B.A.S.F." C90 CR02
CHROMDIOXIDE CASSETTES \$3
each P&P 30c

6ft 240V AC POWER CORDS with
moulded 3 pin plug 75c each or 10
for \$6.50

STEREO TONE ARMS complete with
ceramic cartridge \$5.90 each P&P
30c.

EDGEWISE 0-1 mA METERS 2½" x ½"
face 3" deep calibrated 0-5 \$3 P&P
75c

PANEL METERS 57/8" x 4¼" face
with 0-1 mA movement. Various
scales on meters (gas analyser, etc) \$5.
P&P 75c

NEW QEO 6/40 CERAMIC VALVE
SOCKETS \$2 P&P 40c.

MORSE CODE PRACTICE KEYS \$1.50
P&P 30c

BATTERY ELIMINATORS to suit
transistor radios and cassette
recorders AC-DC 6 volt 300 mA.
PS6300 \$7.50 P&P 75c

SPEAKER CABLE, colour codes twin
flex 20c yd.


CAR RADIO ANTENNA, 5 section lock
down \$2.50 each P&P 75c

CAR EXTENSION SPEAKER
CONTROLS. Use both speakers
together or separately. \$1.50 P&P
30c.

JACKSON SLOW MOTION DRIVES
6:1 ratio \$2.30 P&P 30c.



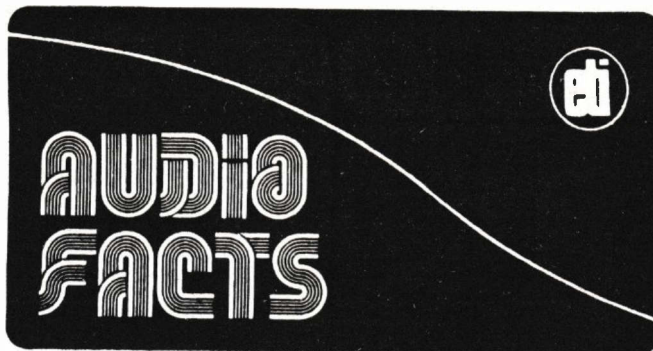MAIL ORDERS WELCOMED.
Please allow pack and post items
listed on this page, if further
information required send a
stamped S.A.E. for immediate reply
from the above address.



SUB WOOFERS

There is a growing trend towards the use of sub-woofers to augment the very low end of the audio spectrum.

Because low bass is essentially non-directional only one speaker enclosure is required. This is connected to the existing system via its own amplifier and active crossover network together with circuitry which actively sums the bass output from the normal two stereo channels.

Our editor reminds us that Electronics Today International published full constructional details of precisely such a system way back in December 1971. He says that it was not then a popular project despite its extraordinary effectiveness — it may have been ahead of its time.

MOVING COIL CARTRIDGES

Most hi-fi enthusiasts have mixed feelings about moving coil cartridges. Some claim that they outperform all other types. But the general feeling has been that their inherently low output and corresponding tendency to pick up hum and other forms of noise outweighs any possible advantages.

Now however several amplifier manufacturers have included very high sensitivity inputs to cater for the inherently low output moving coil cartridges. Sony and Yamaha have included such inputs on their latest products and Dynaco's new PAT-5 kitset amplifier can be alternatively wired to provide the required 6 dB or so more gain.

Current manufacturers of moving coil cartridges include Ortofon, Supex, Fidelity Research and Denon.

REEL TO REEL RECORDER USES DOLBY AT ALL SPEEDS


Dolby noise reduction circuitry has become a standard feature on almost all high performance cassette recorders.

However Dolby have until recently refused to grant licences to allow their circuitry to be incorporated in reel-to-reel machines capable of running at 15 inches per second. Even Revox were we understand unable to persuade Dolby to relax their attitude.

Tandberg must be more persuasive or something for the company has just released their new model 10XD semi-professional machine which incorporates Dolby circuitry usable at all tape speeds *including 15 ips*.

Tandberg's 10XD machine accepts 10½" NAB centred spools. It has three motors and four heads and incorporates most of the features of previous Tandberg machines including remote control. An additional feature though is an external control device which enables tape speed to be varied over a small range (i.e. between the major steps).

NEW AKAI EQUIPMENT

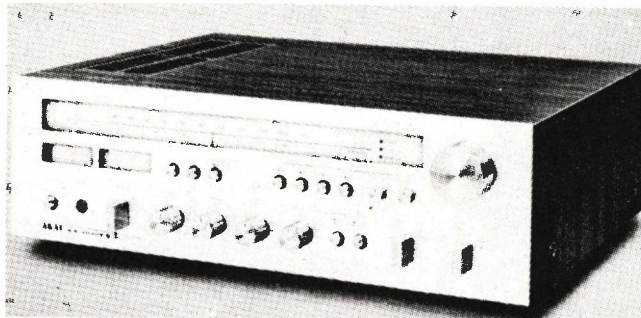

This model 1020 DB Am/Fm receiver is part of AKAI's extensive new range of equipment.

AKAI Australia have just released details of a wide range of new equipment.

The range includes eight new AM/FM receivers varying in price from \$320 to \$945. Several of the models are of particular technical interest in that they incorporate Dolby noise reduction circuitry anticipating the probable use of Dolbized FM radio transmissions.

Also in the new range is a medium-low priced turntable Model AP 001 (without cartridge) AP 002 (with cartridge) which features an interesting non-mechanical auto-stop mechanism. The belt drive machine is equipped with an oil damped tone arm lifting mechanism.

HI-FI AT LOWER COST

An Australian hi-fi equipment manufacturer has developed a speaker system which employs many features normally only available in more expensive units.

Researched and developed by acoustic engineers of the components division of Plessey Australia Pty. Ltd., the company's C12PW Woofer incorporates a roll surround, CFL cone, heavy duty magnetic assembly and an epoxy voice coil with aluminium former.

Combining high compliance and high efficiency with adequate power handling capabilities, the speaker is ideally suited for use in fully sealed enclosures. Coupled with the roll surround, the sealed system creates an air cushion which supports the speaker cone, enriching the quality of bass reproduction, according to Plessey.

Based on this concept, Plessey have developed a four-way/four-speaker system designated the PE 1200.

A departure from the traditional range of Plessey loudspeakers, the C12PW and the PE 1200 are the results of increasing interest in the field of high-fidelity systems for home entertainment.

With a fundamental resonance of 30 Hz and a conservative power handling capacity of 30 watts rms, Plessey claims that the locally produced speaker compares more than favourably in quality and performance with its imported competitors.

5% OFF ON ORDERS OVER \$50.00
10% OFF ON ORDERS OVER \$100.00
15% OFF ON ORDERS OVER \$250.00

JANUARY SPECIALS

TTL			
7400	\$.14	7451	.17
7401	.16	7453	.17
7402	.15	7454	.17
7403	.16	7460	.17
7404	.19	7466	.35
7405	.19	7470	.30
7406	.35	7472	.30
7407	.35	7473	.35
7408	.18	7474	.35
7409	.19	7475	.57
7410	.16	7476	.39
7411	.25	7483	.79
7413	.55	7485	1.10
7416	.35	7486	.40
7417	.35	7489	2.48
7420	.16	7490	.59
7422	.26	7491	.97
7423	.29	7492	.71
7425	.27	7493	.60
7426	.26	7494	.94
7427	.29	7495	.79
7430	.20	7496	.79
7432	.23	74100	1.30
7437	.35	74105	.44
7438	.35	74107	.40
7440	.17	74121	.42
7441	.98	74122	.45
7442	.77	74123	.85
7443	.87	74125	.54
7444	.87	74126	.63
7445	.89	74141	1.04
7446	.93	74145	1.04
7447	.89	74150	.97
7448	1.04	74151	.79
7450	.17	74153	.99

LOW POWER TTL

74L00	\$.25	74L51	\$.29
74L02	.25	74L55	.33
74L03	.25	74L71	.25
74L04	.25	74L72	.39
74L06	.25	74L73	.49
74L10	.25	74L74	.49
74L20	.33	74L78	.79
74L30	.33	74L85	1.25
74L42	1.49	74L86	.69

HIGH SPEED TTL

74H00	\$.25	74H21	.25
74H01	.25	74H22	.25
74H04	.25	74H30	.25
74H08	.25	74H40	.25
74H10	.25	74H50	.25
74H11	.25	74H52	.25
74H20	.25	74H53	.25

8000 SERIES

8091	\$.53	8214	\$1.49
8092	.53	8220	1.49
8095	1.25	8230	2.19
8121	.80	8520	1.16
8123	1.43	8551	1.39
8130	1.97	8552	2.19
8200	2.33	8554	2.19
8210	2.79	8810	.69
		8267	2.59

9000 SERIES

9002	\$.35	9309	\$.79
9301	1.03	9312	.79
		9601	\$.89
		9602	.79

CMOS

4000A	\$.26	4016A	.56
4001A	.25	4017A	1.19
4002A	.25	4020A	1.39
4006A	1.35	4021A	1.39
4007A	.26	4022A	1.10
4008A	1.79	4023A	.25
4009A	.57	4024A	.89
4010A	.54	4025A	.25
4011A	.29	4027A	.59
4012A	.25	4028A	.98
4013A	.45	4029A	.26
4014A	1.49	4030A	.44
4015A	1.49	4035A	1.27
		4042A	1.47
		4049A	.59

74C00	\$.22	74C74	\$1.04
74C02	.26	74C76	1.34
74C04	.44	74C107	1.13
74C08	.68	74C151	2.61
74C10	.35	74C154	3.15
74C20	.35	74C157	1.76
74C42	1.61	74C160	2.48
74C73	1.04	74C161	2.93
		74C162	\$2.93
		74C163	2.66
		74C164	2.66
		74C173	2.61
		74C195	2.66
		80C95	1.35
		80C97	1.13

DIGITAL

7447	BCD to 7 seg. decoder drv.	\$.69
7483	4 bit binary full adder	.59
7490	Decade counter	.45
74151	8 channel multiplexer	.59
74153	Dual 4 input multiplexer	.79
74180	Parity generator checker	.79
74193	Binary up/down counter	.99
9602	Dual one shot.69	
75C00	Quad 2 input NAND gate (CMOS)	.12

LINEAR

301	Hi perf op amp	mDIP	.25
339	Quad comparator	DIP	1.29
320T	5V neg. V reg.	5V	1.39
320T	12V neg. V reg.	12V	1.39
340T	12V neg. V reg.	5V	1.39
340T	15V pos. V reg.	15V	1.39

MEMORIES

2102	\$2.65	5311	\$3.95
2102-1	2.75	5312	2.95
2102-2	2.75	5314	3.95
82S23	3.25	5316	4.15
F93410			
256 bit RAM	2.19		

CLOCK CHIPS

5005	\$1.69
------	--------

8038 FUNCTION GENERATOR

Voltage controlled oscillator — sine, square, triangular output. 16 pin DIP with data **\$3.95**

7001 CLOCK CHIP

4-6 digit, 12-24 hr. alarm, timer and date circuits — with data **\$6.95**

DVM CHIP 4 1/2 DIGIT

MM5330 — P channel device provides all logic for 4 1/2 digit volt meter. 16 pin DIP with data **\$14.95**

Data sheets on request. With order add \$.30 for items less than \$1.00 ea.

PULTRON V.I.P. QUARTZ REGULATED LED WATCH

MEN's 5 function — hours, minutes, month, day and seconds.

Latest slim-line design (prox. 3/8" thick)
Four year calendar — requires setting only on February 29th.

One year warranty against all defects in material and workmanship.

Built-in phototransistor adjusts intensity of display.

Gold tone — with adjustable mesh strap.



\$99.50
+\$1.50 Shipping & Handling
Usual 10% Discount Applies

LED's

MV108	Red TO 18	\$.22
MV50	Axial leads	.18
MV5020	Jumbo Vis. Red (Red Dome)	.22
	Jumbo Vis. Red (Clear Dome)	.22
ME4	Infra red diff. dome	.54
MAN1	Red 7 seg. .270"	2.19
MAN2	Red alpha num. .32"	4.39
MAN4	Red 7 seg. .190"	1.95
MAN5	Green 7 seg. .270"	3.45
MAN6	.6" high solid seg.	4.25
MAN7	Red 7 seg. .270"	1.19
MAN3	Red 7 seg. .127"	
	straight pins	.29
MAN8	Yellow 7 seg. .270"	3.45
MAN66	.6" high spaced seg.	3.75
MCT2	Opto-iso transistor	.61

MEMORIES

1101	256 bit RAM MOS	\$ 1.50
1103	1024 bit RAM MOS	3.95
I702A	2048 bit static PROM	
	UV eras.	17.95
2102-2	1024 bit static RAM	4.25
5203	2048 bit UV eras PROM	17.95
5260	1024 bit RAM	2.49
5261	1024 bit RAM	2.69
5262	2048 bit RAM	5.95
7489	64 bit ROM TTL	2.48
8223	Programmable ROM	3.69
74200	256 bit RAM tri-state	5.90

CALCULATOR & CLOCK CHIPS

5001	12 DIG 4 funct fix dec	\$2.49
5002	Same as 5001 exc btry power	2.79
5005	12 DIG 4 funct w/mem	2.99
MM5725	8 DIG 4 funct chain & dec	1.98
MM5736	18 pin 6 DIG 4 funct	4.45
MM5738	8 DIG 5 funct K & mem	5.35
MM5739	9 DIG 4 funct (biry sur)	5.35
MM5311	28 pin BCD 6 dig mux	4.45
MM5312	24 pin 1 pps BCD 4 dig mux	3.95
MM5313	28 pin 1 pps BCD 6 dig mux	4.45
MM5314	24 pin 6 dig mux	4.45
MM5316	40 pin alarm 4 dig	5.39

MULTIPLE DISPLAYS

NSN33	3 digit .12" red led 12 pin lits IC skt.	\$1.79
HP45082	5 digit .11 led magn. lens com. cath	3.49
HP5082	4 digit .11 LED magn. lens comm. cath.	3.25
FNA37	9 digit 7 seg led RH dec clr. magn. lens	4.95
SP-425-09	9 digit .25" neon direct interface with MOS/LSI, 180 VDC. 7 seg.	1.79

SHIFT REGISTERS

MM5013	1024 bit accum. dynamic mDIP	\$1.75
MM5016	500/512 bit dynamic mDIP	1.59
SL5-4025	QUAD 25 bit	1.29

DTL

930	\$.15	937	.15	949	.15
932	.15	944	.15	962	.15
936	.15	946	.15	963	.15

The prices as listed are in Australian dollars. Send back cheque with order. If international postal money order is used send receipt with order. Shipment will be made via air mail — postage paid — within three days from receipt. Minimum order — \$5.00.

INTERNATIONAL ELECTRONICS UNLIMITED

P.O. BOX 1708/ MONTEREY, CA. 93940 USA

PHONE (408) 659-3171

AT LAST!

THIRTY FIVE SIMPLE PROJECTS IN ONE GREAT VOLUME!
PLUS A COMPLETE BEGINNER'S
GUIDE TO PROJECT
CONSTRUCTION.

VOLUME 1

SIMPLE PROJECTS

from **electronics today** INTERNATIONAL

CONSTRUCTING ELECTRONIC PROJECTS	5	DRILL SPEED CONTROLLER	58
CONSTRUCTIONAL METHODS	6	ELECTRONIC WINDICATOR	61
CRYSTAL RADIO	11	HI-POWER STROBE	62
THREE SIMPLE RECEIVERS	12	LIGHT OPERATED SWITCH	66
ONE-TRANSISTOR RADIO	16	CAR ALARM	68
KILL THAT GHOST!	18	ELECTRONIC FLASH TRIGGER	70
TV MASTHEAD AMPLIFIER	20	CODE PRACTICE OSCILLATOR	72
FM ANTENNA	25	ETI UTILIBOARD	75
SIMPLE SPEAKER	26	TRANSISTOR TESTER	77
SIMPLE AMPLIFIER	28	CANNIBALS AND MISSIONARIES	78
SIMPLE STEREO AMPLIFIER	30	WHY DOESN'T IT WORK?	81
BETTER SOUND FOR S5	32	POOL ALARM	82
AUTO-AMP	34	COURTESY LIGHT EXTENDER	85
SURROUND SOUND	37	RESISTOR COLOUR CODE	86
SIMPLE INTERCOMS	40	STANDARD VALUES	86
MONOPHONIC ORGAN	45	POTENTIOMETERS	87
TWO SIREN CIRCUITS	46	TAG TANTALUM CAPACITORS	87
SPRING REVERBERATION UNIT	51	CERAMIC CAPACITORS	88
SIMPLE LOUDHAILER	52	POLY-CARBONATE CAPACITORS	88
BASIC POWER SUPPLY	53	HOW TO SOLDER	89
RESISTORS IN PARALLEL	54	BUYING COMPONENTS	89
FET DC VOLTMETER	57	TRANSISTOR CONNECTIONS	90
THINGS WORTH KEEPING	57		

ON SALE NOW AT ALL NEWSAGENTS OR DIRECT FROM ELECTRONICS TODAY
INTERNATIONAL, 15 BOUNDARY STREET, RUSHCUTTERS BAY, NSW 2011. \$2.00.

(PLUS 40c POSTAGE)

ADVERTISERS INDEX

Adcola	61
Akai	4
Amateur Astronomer	87
Ampex	26
Applied Technology	24
Audio Engineers	36
Autotronics	90
AWV	38
Bail Electronics	87
Bright Star	44
British Merchandising	68
BWD	37
Cema Dist.	69
Challenge Hi-Fi	54
Convoy	20,27
Dick Smith	39
Douglas Hi-Fi	78
Edge Electrix	58
Electro Technics	46
Electronic Disposals	88
Electronic Mailbox	25
Esalin	88
Ferguson Transformers	90
George Hawthorn	46
Haco	1FC
Hani Radio	43,90
Harmon	8
ICS	68
International Dynamics	13,95
International Electronics Unlimited	92
Jacoby Mitchell	12
John Carr	88
Kent Hi-Fi	16
Kitsets Aust	72
Lafayette	90
Linear Technics	88
Logan Brae	68
Mod-amp	60
MS Components	53
Parameters	87
Pioneer	19
Rank	OBC
Royston	52
Sabtronics	46
STC	67
Stotts Technical College	44
Thomson Radio Service	68
Trident TV	89
Video Hi-Fi	35
Warburton Franki	51
Wardrope & Carrol	90
Wedderspoon, W.C.	45
Wallin & Merrell	52,86

electronics TODAY

SERVICES

READERS' LETTERS

We make no charge for replying to readers' letters, however readers must enclose a foolscap-size stamped addressed envelope if a reply is required. Queries concerning projects can only be answered if the queries relate to the project as published. We cannot assist readers who have modified or wish to modify a project in any way, nor those who have used components other than those specified.

TELEPHONE QUERIES

We regret that we cannot answer readers' queries by telephone.

BACK ISSUES

Our subscriptions dept can supply most back issues of ETI for the twelve months preceding the date of this current issue. Some earlier issues are also available.

The price of back copies is currently 75 cents, plus 40 cents postage and packing. Please address orders to Subscriptions Dept, Electronics Today, 15 Boundary St, Rushcutters Bay, NSW 2011.

PHOTOSTATS

Photostats of any article ever published in ETI can be obtained from our subscription dept (address above). The price is currently 45 cents per page including postage.

CONTRIBUTORS

Material is accepted from time to time from outside contributors. Payment is based on quality and is paid 30 days after the date of publication. Constructional projects will be considered for publication but the standard of design must be to fully professional level. All material must be typed using double spacing and wide margins. Drawings, circuit diagrams etc need not be to professional standards as they will be redrawn by our staff. It is advisable to contact the Editor before submitting copy.

A large stamped addressed envelope must be included if unsolicited material is required to be returned.

ADVERTISING QUERIES

Queries concerning goods advertised in ETI should be addressed directly to the advertiser — not to ourselves.

NEWS DIGEST

News Digest items are published free of charge. Manufacturers and importers should send material at least four weeks before the date of publication. Photographs should be of high contrast and preferably at least 100 by 150 mm. Press releases must be of a factual nature — these pages are not free advertising. The Editor reserves the right to accept or reject material at his discretion. Preference will be given to components and equipment of an essentially practical nature.

BINDERS

Binders to hold 12 issues of ETI are available from our subscription dept (address above). Price is \$4.50 (plus 80 cents postage NSW & ACT — or \$1.50 all other States)

COPYRIGHT

The contents of Electronics Today International and associated publications is fully protected by international copyright under the terms of the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards reproduced in our various publications. Although any form of reproduction is technically a breach of copyright, in practice we are not concerned about private individuals constructing one or more projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note however that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd.