



**ELECTRONICS
TODAY
INTERNATIONAL**

HI-FI
Marantz SC-6/SM-6 amp and preamp ..bordering on perfection

POLYPHONIC 'TOUCH ORGAN' TO BUILD

*two octave range
two voices
speaker output*

60W Amp. module

*very low distortion
using two nested
differentiating
feedback loops*

**Points controller
for model railways**

**Fault-finding your
'660 Learner's Micro**




**SPECIAL
OFFER!**

**LCD
Multimeter
for under
\$100**



Introducing the MicroBee column!



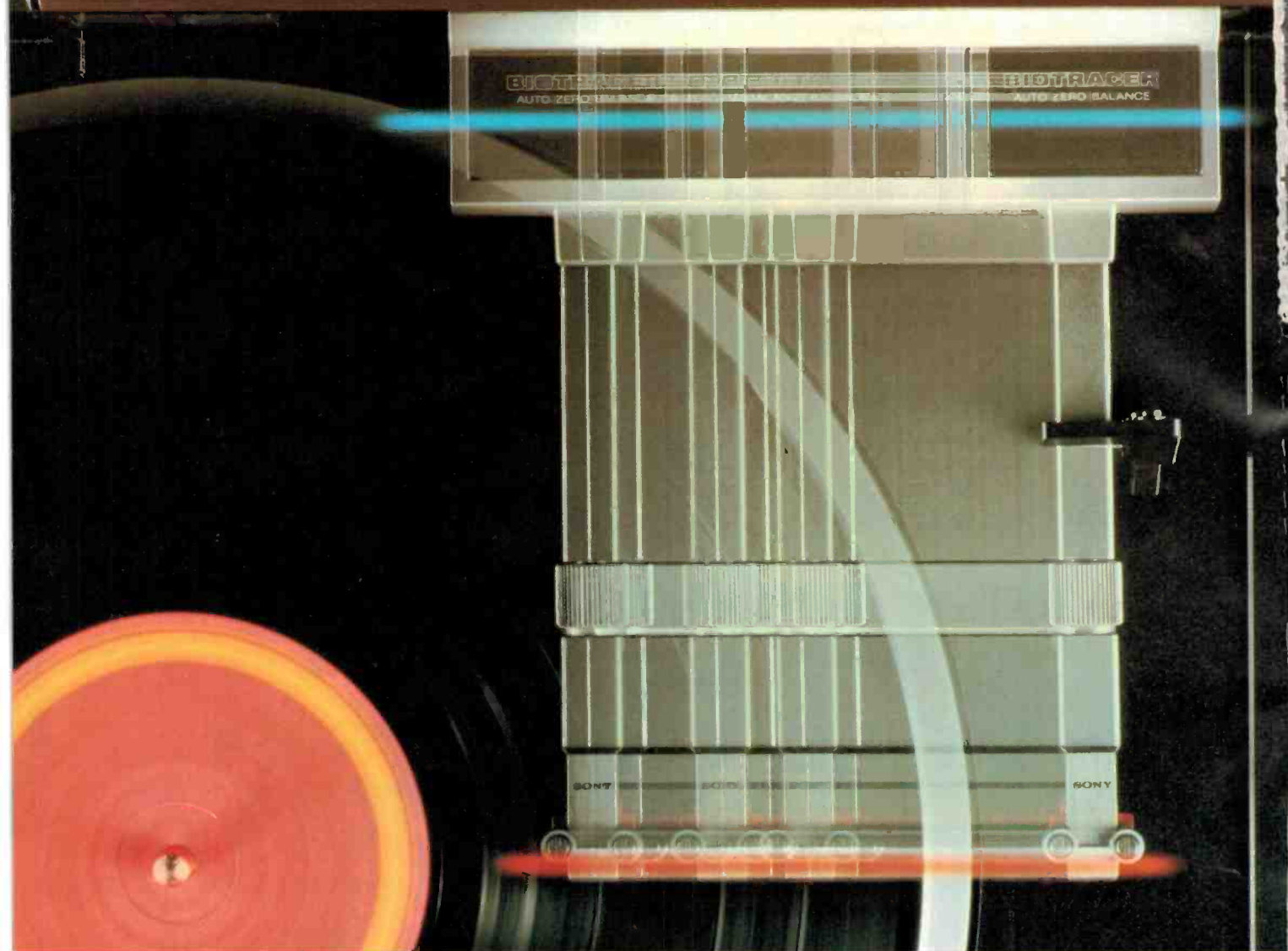

Off on a tangent with Sony.

We didn't jump into tangential tracking turntables right off the bat. And Sony hopes you didn't either. Because while most lateral tonearms don't exactly shift gears as they travel down their path, they do run into some rough spots. A hang-up called "cogging" that inhibits totally free flowing movement, and hampers left and right stereo separation.

Sony has alleviated cogging and out of phase problems with an invention called Tangential Tracking Biotracer.

Controlled by two microcomputers and four sensors, the motion of the Biotracer tonearm is continuously fluid for precise phase alignment of the stylus.

To the average person these differences may sound slight. But if your standards are as high as Sony's, you'll understand the angle we're driving at.



SONY
THE ONE AND ONLY

SON 0116

Applied Technology 81,
82,83,84
Altronics 4,28,29,38,
39,68,69
Audio Engineers 97
A & R Soanar 21
Billco 64
Cooper Tools 14
Delsound 103
Dick Smith 92,93,94
Daneva Control 85
Energy Control 66
Emona 70
Ferguson 103
G.F.S. 66
Hewlett-Packard 10
Imark 66
Inca Data 85
Jaycar 6,7,18,19,
30,40,46,47,62,63
John Cawsey 79
K-Nar 89
Kalex 14
Magraths 72
Moss 14
Magnetic Media 91
Micro Computer House . . 80
Marantz IBC
Melbourne Machinery . . . 74
Parameters 44
Rose Music OBC
Rod Irving 13,25,45,61
Scientific Devices 21
Software Source 66
Sheridan 88
Sony IFC
Truscotts 14
Vendale 75

16 **The HP-15C Scientific Calculator** Perfectly suited to the scientist/engineer

projects and technical

- 22 **488: 60 W Amplifier Module with Two NDFLs** Distortion in parts/million!
31 **905: Polyphonic 'Touch Sensor' Organ** Serenade your sweetie
41 **334: The Auto Tester** For checking vehicle electricals
48 **1510: Model Train Points Controller/Indicators** Sophisticate your system!
59 **Ideas For Experimenters** Automatic car aerial, Humbucker's lament
64 **Shoparound** Where to buy kits, components, pc boards & panels for projects

computing today

- 71 **Hewlett-Packard Release Portable Micro** Powerful notebook-sized computer
76 **Fault-Finding the ETI-660** Sorting out problems in your '660
86 **Hints for CHIP 8 Programmers, Part 2** Making music, 5-digit scoring, Fun routines
90 **Microbee Column — 'Bee-O-Rhythms'** Biorhythm calculator with plot output

electronic lifestyle

- 95 **Philips Demonstrate Compact Disc** AWA-Thorn's new VCR
98 **Marantz SC6 Preamp/SM6 Power amp** Bordering on perfection

news

- 8 **News Digest**
11 **Equipment News**
12 **Component News**
67 **Communications News**
73 **Printout**
96 **Sight & Sound News**

contests and special offers

- 15 **Special Offer — LCD Multimeter**
Super new Univolt DMM—under \$100!
60 **Idea of the Month Contest**
New prize — \$90 'Work Centre' from Scope

general

- 51 **Eight Pages of Mail Order Books**
104 **Mini-Mart**
105 **Subscriptions, Back Issues Order Form**
106 **Dregs**

52 21st 1/2 82 75 JAN 1983

eti ELECTRONICS TODAY INTERNATIONAL

HIFI

POLYPHONIC 'TOUCH ORGAN' TO BUILD
two octave range
two channels
speaker output

60W Amp. module
very low cost for input
using new matched
components making
feedback loops

Points controller for model railways
Fault-finding your 660 Learner's Micro

SPECIAL OFFER!
LCD Multimeter for under \$100

Introducing the MicroBee column!


A graphics montage of parts of the pc board and circuit from our Polyphonic Organ project adorns the cover this month.

Cover design: All White

Registered by Australia Post —
Publication No. NBP0407
ISSN No. 0013-5216

WILL YOUR BUDGET PROBABLY WON'T STRETCH TO AFFORD OUR PROFESSIONAL SERIES ALL ALUMINIUM RACK CABINETS

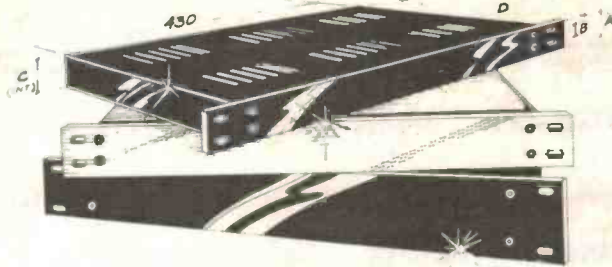NOW YOUR PREAMPS, AMPS, CONTROL MODULES MONITOR PANELS ETC. CAN LOOK EVERY BIT AS GOOD AS TECHNICS, NAKAMICHI AND OTHER TOP MANUFACTURERS



Cat No.	Finish	A	B	C	PRICE	5 or More
H 0401	Natural	44	34	38	\$39.50	\$38.00
H 0402	Natural	88	57	82	45.00	42.50
H 0403	Natural	132	89	126	49.50	45.00
H 0411	Black	44	34	38	39.50	38.00
H 0412	Black	88	57	82	45.00	42.50
H 0413	Black	132	89	126	49.50	45.00

Beware of other rack boxes that do not conform to international rack sizing.

THE BRILLIANT MARC NR 82 FI

FEATURING: Digital frequency Display, SSB/CW, FM/AM reception, B.F.O., Double Conversion, Double Super-het, crystal controlled (VHF) Local Oscillator, 4 inbuilt antennas and good looks, you will spend hours just learning how to drive it!

FREE DELIVERY ANYWHERE IN AUSTRALIA

See Review in Electronics Australia August 1982

- 3 Way Power
- * Digital Tuning
- * HI FI SOUND
- * 4 Inbuilt Antennae



only \$349 C9482

SPECIFICATIONS:

Semi-conductors: 1-LSI, 4 - IC's, 7 - FET, 34 - Transistors, 42 - Diodes

Frequency range:

LW	145-360 KHz	SW3	9-22 MHz	VHF3	88-108 MHz
MW	525-1600 KHz	SW4	22-30 MHz	VHF4	108-136 MHz
SW1	1.6-3.8 MHz	VHF1	30-50 MHz	VHF5	144-176 MHz
SW2	3.8-9 MHz	VHF2	68-86 MHz	UHF	430-470 MHz

Power supply: AC 240V 50Hz. DC 12V (8 x "D" cells). Ext. DC 12V Car/Boat.

Speaker: 12.5cm Permanent Dynamic Speaker (3.2 ohm)

Antenna: Ferrite Bar Antenna for LW, MW and SW1
3 x Telescopic Antenna for SW, VHF and UHF

Controls: Power ON-OFF switch - Digital display ON-OFF switch - Tape-Radio switch, Wide-Narrow band selector switch, AM band selector (LW/MW/SW1/SW2/SW3/SW4), VHF band selector (VHF1/VHF2/VHF3/VHF4/VHF5/UHF), Ant. Selector (Telescopic ANT./EXT. ANT.), Tuning control (direct gear drive), volume control, Bass control, Treble control, Squelch control, BFO pitch control, RF gain control, Antenna adjustor control, Mode switch (USB-NOR-LSB/CW)

Terminals: Ext. Speaker/Headphone Jack, Tape IN-OUT jack, VHF/UHF ANT. connector (coaxial), SW EXT. ANT. terminal (Screw), Ext. battery jack

Meter: Tuning Meter

Digital Frequency Counter Section:

Display:	LW/MW/SW-1	KHz	SW2-4/VHF1-5	MHz
----------	------------	-----	--------------	-----

Control: SW Calibrator Dimensions: 452mm (W) x 288mm (H) x 130mm (D)

ALTRONICS RESELLERS

Please note that resellers may not have all the items advertised in stock, and as resellers have to bear the cost of freight, prices may be slightly higher than advertised. ALTRONICS reseller prices should however represent a considerable saving over our competitors' prices.

SOUTH AUSTRALIA	QUEENSLAND
CITY ADN Electronics 212 5505 Pratronics 212 3111	CITY Deisound P/L 229 6155
SUBURBAN PROSPECT Janice Electronics 269 4744	SUBURBAN SALISBURY Colourways Wholesale 275 3188
ELIZABETH GROVE A.E. Cooling 255 2249	FORTITUDE VALLEY St Lucia Electronics 52 3547
CHRISTIES BEACH Force Electronics 382 3366	BIRKDALE Wholesale Sound Accessories 207 2502
KESWICK Freeway Electric Wholesalers 297 2033	COUNTRY CAIRNS Thompson Instrument Services 51 2404
VICTORIA CITY All Electronic Components 662 3506 Electronics 602 3499	TOWNSVILLE Solex 72 2015
SUBURBAN FOOTSCRAY Acron Electronics 680 1911	ROCKHAMPTON Purely Electronics 21058
CHELTENHAM Talking Electronics 550 2386	GLADSTONE Purely Electronics 72 4321
HUNTINGDALE Stewart Electronics 543 3733	GYMPIE TV and Appliance Services 82 1671
SOUTH CROYDON Trussart Electronics 723 3860	IPSWICH P & P Electronics 281 8001
COUNTRY SHEPPARTON GV Electronics 21 8866	TOWDOOMBA Hunts Electronics 32 9677
MILDURA Electronic and Digital Services 23 3380	Down's Radio and TV 32 1044
NEW SOUTH WALES CITY Radio Dispatch 211 0191 Electronic Agencies 29 2098 Jaxca 264 6888	NAMBOUR Nambour Electronics 41 1604
SUBURBAN LEWISHAM PrePak Electronics 569 9770	NT DARWIN Radio Parks Darwin 81 8508 Kent Electronics 81 4749 Ventronics 81 3491
CONCORD Electronic Agencies 745 3077	ALICE SPRINGS Farmer Electronics 52 2967 Ascum Electronics 52 1713
DEE WHY David Ryall Electronics 982 7500	TASMANIA HOBART Beta Electronics 34 8232
WAITARA Applied Technology 487 2711	KINGSTON Kingston Electronics 29 6802
MATTRAVILLE Creative Electronics 666 4000	AVOCA Freemans TV 84 2166
COUNTRY BROKEN HILL Crystal TV 4803	WEST AUSTRALIA ALBANY BP Electronics 41 2681
COFFS HARBOUR Colts Harbour Electronics 52 5684	GERALDTON Generalion TV and Radio 21 2777
PENRITH Acron Electronics 21 2409	WYALKATCHAM D & J Passer 81 1132
NEWCASTLE D.G.E. Systems 69 1625	MANDURAH Kentrionics 35 3227
WINDANG Medronic Electronics 96 5066	KALGOORLIE Today's Electronics 21 5212
GOSFORD Tomorrow's Electronics 24 7246	ACT SCIENTONS Electronic Components 54 8334 80 4654
KURRI KURRI Kurri Electronics 37 2141	

RESELLERS WANTED IN ALL AREAS (including WA)

Phone: STEVE WRUBLEWSKI (09) 381 7233 for details

LABORATORY MULTIMETER

100K OHMS/VOLT CHECKS TRANSISTORS AND MEASURES CAPACITANCE

Q 1040 Multimeter \$72.50

Q 1041 Carry Case \$14.50



From Tokyo Laboratories, Japan

Remember the days when high grade precision laboratory multimeters were available only from UK and then they cost a King's Ransom? - Well, that's history - The new Q 1040 is everything a high quality meter should be PLUS it checks transistor HFE and ICO and measures capacitors from 50 pf-50 uF.

- * 100K OHMS/Volt DC ranges
- * 8.5 uA movement
- * Fuse and diode movement protected
- * Inbuilt oscillator for capacitance measurement.

RANGES: DCV 250MV, 2.5V, 10V, 50V, 250V, 250V, 1000V. ACV 5V, 10V, 50V, 250V, 1000V (10K/V) DCA 10UA, 2.5MA, 25MA, 500MA, 10A ACA 10A Resistance x1, x10, x1K, x10K Transistors NPN/PNP HFE 0-1000 ICO 0-50UA Capacitors 50PF-3UF. .01UF-50UF.

eti

Editor

Roger Harrison VK2ZTB

Technical Editor

David Tilbrook VK2YMI

Assistant Editor

Jennifer Whyte B. App. Sc.

Editorial Staff

Geoff Nicholls B.Sc./B.E.

Jonathan Scott

B.Sc./B.E. (Hons) VK2YBN

Jan Vernon B.A.

Draughting

David Currie

Advertising Production

John Gerrie

Advertising Sales

Bob Taylor (Group Manager)

John Whalen (National)

Art Staff

Ali White B.A.

Bill Crump

Githa Pilbrow

Typesetting

Julie Hewlett

Reader Services

Jane Nicholls

Managing Editor

Collyn Rivers

Acoustical Consultants

Louis Challis & Associates

Editorial and Sales Office

4th Floor, 15 Boundary St,

Rushcutters Bay NSW 2011

Ph: (02)268-9015; Tlx: 27243

Melbourne: Virginia Salmon and Mel Godfrey,
150 Lonsdale St, Melbourne Vic. 3000.
Ph: 662-1222; Tlx AA34340.

Adelaide: Admedia Group, 24 Kensington Rd,
Rose Park SA 5067. Ph: 332-8144;
Tlx AA82182.

Brisbane: Geoff Horne Agencies, 16 Bellbowrie
Centre, Bellbowrie Qld 4070. Ph: 202-6813.

Perth: C. Thomas, Adrep Advertising
WA 6000. Ph: 325-6395; Tlx ADREP PERTH.

New Zealand: Frank Hargreaves, Circulation
Marketing Manager, c/- ACP, 4th Floor, Sun
Alliance House, 42-44 Shortland St, Auckland.
Ph: (9)30311.

United Kingdom: Australian Consolidated
Press, Ludgate House, 107 Fleet St, London
EC4A 2AL. Ph: 353-1040; Tlx: 267163.

Japan: Genzo Uchida, Bancho Media
Services, 15 Sanyocho, Shinjuku-Ku, Tokyo
160. Ph: 359-8866; Cable: Elbanchorito;
Tlx: BMSINC J25472 Tokyo.

USA: Australian Consolidated Press, 21 East
40th Street, (Floor 23), New York NY 10016.
Phone: (212)685-9570.

Electronics Today International is published by Murray Publishers Pty Ltd, 15 Boundary St, Rushcutters Bay NSW 2011. This issue was printed by Offset Alpine, cnr Wetherill and Derby Sts, Silverwater NSW, and distributed by Network.

* Recommended retail price only

A NEW YEAR and a new look! As this is the time of year for self examination and 'turning over a new leaf', we thought it appropriate to introduce a new 'style' for the pages of ETI, both in form and in content. The broad field of electronics never remains static, and neither should we.


Over the past six months we've examined trends and activity in a wide variety of fields that could be seen as falling under the general umbrella of electronics and looked at what we, as a magazine, have been doing too.

Apart from style, layout and typeface etc, you'll notice a few changes in the magazine this month. We will be introducing new features during the coming year, as a result of our researches. We trust they not only reflect what various reader groups are interested in, but will be informative to a broad section as well. Existing popular features, like Circuit File and equipment reviews etc, will continue. We have carefully examined the trends in project interest and purchasing over the past year, both from reader feedback and in discussions with kit suppliers — and have learned a surprising amount. This is an exercise we go through at regular intervals to see what we should be doing, and when. Sometimes our predictions are off-target, more often though, we're right on target. We aim to improve our on-target to off-target ratio this year.

Our aims in changing the style within the magazine are to 'modernize' the layout, to improve 'readability' and to prevent atrophy. Anything that atrophies, dies — and we don't aim to do that! We have retained the 'magazines within magazine' format as this seems to be thoroughly accepted by readers and advertisers alike, making the contents of particular interest easy to locate in each issue, whether it be articles, projects, reviews or advertisements. What happened to the 'Electronic Lifestyle' section? That's become a publication in its own right and we've reverted to the 'Sight and Sound' section we had previously. Electronic Lifestyle went on sale in December. Your non-technical family, friends and associates will doubtless find it informative.

Despite the doom and gloom promulgated almost everywhere these days, we here at ETI look forward to 1983 with interest and excitement. We trust you have had an enjoyable festive season and that the coming year brings more prosperity than the last.

Roger Harrison
Editor

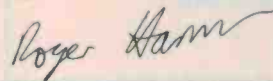

services

Technical enquiries: We can only answer readers' technical enquiries by telephone after 4.30 pm Mondays to Thursdays. The technical enquiry number is: (02)33-5669. Technical enquiries by mail must be accompanied by a stamped, self-addressed envelope. There is no charge. We can only answer queries relating to projects and articles as published. We cannot advise on modifications, other than errata or addenda. We try to answer letters as soon as possible. Difficult questions may take some time to answer.

General enquiries: For enquiries about back issues, photostats of articles, artwork or submitting articles, call (02)268-9015 or write to the address on this page.

The publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

COPYRIGHT: The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Murray Publishers Pty Ltd, or from the copyright holders.

LIABILITY: Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid. The Publisher accepts no responsibility for unsolicited manuscripts, illustrations or photographic material.

next month

IMMERSION-TYPE TEMPERATURE CONTROLLER

This project is built around an ordinary fish tank heater and the CA3059 zero-crossing switch controller. It can be used in a wide variety of applications, from aquarium heating to home brewing. Although our prototype was built into a fish tank heater, the pc board is 'universal' enough to provide zero-crossing switch control of almost any heating element.

'CAMP LAMP'

This project powers a small fluorescent tube and has been designed to be portable, operating from a 10 V to 16 V supply — just the thing for campers! The whole unit can be fitted inside a plexiglass tube, making it convenient to use and very compact. A very efficient dc-dc inverter using MOSFET technology is employed.

MICROBEE EPROM BURNER

This is the first in a series of projects supporting the popular MicroBee personal computer. It is a simple design using low cost off-the-shelf components. The MicroBee was made to take EPROM-based software and this allows you to produce your own.

CIRCUIT FILE: ANALOGUE DELAY LINES

Held over from this issue owing to lack of space, Ray Marston goes into the subject of analogue delay lines in depth and follows up with some practical circuits.

DIGITAL DISC PLAYER REVIEWED!

We review one of the first digital audio disc players released here — the Sony CDP-101. How does this new technology really sound! Find out next month.

COLOUR CLOCK FOR TANDY'S "COCO"

Here's a couple of clock programs for the Tandy TRS-80 Colour Computer — now affectionately known as the "CoCo". They make good use of the machine's graphics and powerful extended colour BASIC. Your grandfather never saw clocks like these!

'660 PROGRAM POTPOURRI NO. 2

More whizz-bang programs for the ETI-660 Learner's Microcomputer. Try your hand at 'IAGO for two', 'Patches', 'Asteroid Shower', etc.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.

HEAT WAVE

WE'VE ASSEMBLED A GREAT BUNCH OF SPECIALS AT "RED HOT" PRICES!!

FUEL SENSOR

GENUINE MORAY UNIT SACRIFICED!!

This is the original unit as used in the EA Car Computer (Ref: EA July/August 1982).

They were very scarce (and expensive!) – until now!! If you are assembling this project from parts you will need this unit. Remember! The Jaycar unit is the LATEST MODEL fresh from the U.K.



GREAT SAVINGS!!

ALMOST
30%
OFF

The Moray fuel flow sensor normally sells for up to \$69.50

You can buy the SAME ITEM from us for – wait for it \$49.50

THAT'S UP TO \$20 SAVING!!

Hurry! Quantities strictly limited

LCD panelmeters



\$49.50

DPM-200

\$39.50

DPM-05

We have been unable to keep up with demand for these, that is why you have not seen them in our ads for the last few months.

DPM-200 – 3½ digit display with annunciators (pictured). 0.6" high. 200mV full scale. Each unit supplied with data sheet.

DPM-05 (Not illustrated). 3½ digit display with "plus", "minus" and "low batt". Annunciators with 0.5" readout. Both units sample at 3/second.

If you want to express any physical measurement in a bright easy to read display these are for you. They contain all analogue-to-digital electronics and LCD drive circuitry. Send SAE for more information.

"PANBRAKE"

SHEET METAL FOLDER

\$69.50



- Handles up to 16 gauge aluminium!
 - Slotted upper clamping bar allows complex corner bends etc.
 - Handles material up to 445mm wide!
- Save a fortune building metalwork yourself!!!
ONLY \$69.50

Now you can afford one in your own workshop. Make your own chassis, boxes, brackets etc. (Please allow \$8 for freight as it is very heavy!)



ELECTRET MIC INSERTS

CRAZY PRICE!!

JANUARY ONLY – 2 FOR \$2.00

Each unit supplied with data sheet. 1000's of uses

SUPER SPECIAL!
URGENT

We have a quantity of 240 V Disco Strobes. Not a kit. Built in Woodgrain cabinet. 0-12 flashes per second. Brand new but re-worked warranty stock. Almost less than 1/3 normal price!

Only \$12.50 each
Were \$36.50

\$2
for
\$2



IF YOU THOUGHT MUFFS WERE SCARCE AT THE KLONDIKE...

you should see our stores!!

Yes, we have the Sennheiser HD414 earmuffs back in stock – for a while anyway.

Grab a muff now (you will get either blue or yellow – no choice) for \$5.95 per pair. (The high price reflects their quality Teutonic origin).



★ ONLY ★

\$5.95

per pair

Green Screen

MONITOR – NEW LOW PRICE!!

A BREAKTHROUGH!!!

Now you can enjoy the benefits of high quality for less than the cost of some B/W monitors!

- 18MHz Bandwidth!!
- Direct Video Connection
- High Resolution



only \$199


SPECIALS

WE'VE ASSEMBLED A GREAT BUNCH OF SPECIALS AT "RED HOT" PRICES!!

final runout of GE Consumer Products

WE HAVE SOLD OVER 1000 OF EACH OF THESE ITEMS. ONLY A FEW ARE LEFT NOW.

Smoke Detector

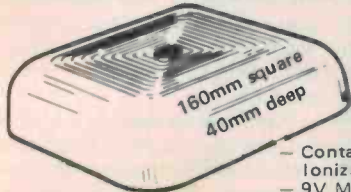


FROM \$12.50

- Contains Americium 241 Ionization Chamber
- 9V Mallory Duracell Included
- Contains very loud solid state buzzer
- 12 month factory warranty.

One of the greatest consumer flops of the last decade was the Ionization Chamber Smoke Detector. Even though it is a brilliant product (reliable compact, easy installation, fall-safe etc) it just did not sell. Human nature being what it is finds safety-oriented products just not worth the investment. We all know that accidents and fires never happen to US!! As smoke is the greatest killer in a fire, the market research gurus thought that such a product would have a wide appeal. When they were \$49.50 no-one wanted them. The price fell to a very reasonable \$29.50 and still they stayed on the shelf. We have now been instructed to clear them for less than 1/2 of \$29.50.

Burglar Alarm

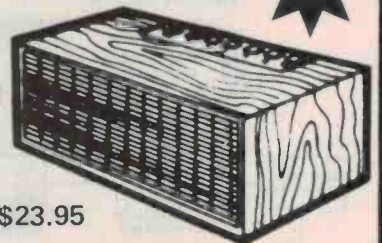

FROM \$23.95

GENERAL ELECTRIC

BURGLAR ALARM SLASHED!!!
HUGE SCOOP PURCHASE -
ONCE SOLD FOR OVER \$100

Amazingly low price for a full feature ultrasonic proximity/burglar alarm. + Completely self contained + 12 month manufacturer guarantee + Instant or delayed alarm + Handsome imitation woodgrain + Cabinet measures 180(w)x85(h)x100(d)mm + Programmable multi-code disable switch + Single 9V Alkaline battery* lasts one year + unit beeps when battery gets low + Contains receiver element designed for greater sensitivity without false triggering + Uses state-of-the-art LSI circuitry + Worth the money in parts alone + Comprehensive 24 page manual included + Comes complete with 4 window deterrent stickers + Absolutely no installation needed * Battery extra.

QUANTITY PRICES

1-\$14.50: 2-5 \$13.50ea: 6-10 \$13.00ea: 10 up \$12.50ea

1-\$29.50: 2-5 \$25ea: 6-10 \$24.50ea: 10up \$23.95ea

4116 RAMs 150nS - GOING CHEAP

We have secured a quantity of 4116 (150nS) RAMs at a price which means great savings to you. Why are they cheap? Well they don't actually have '4116' branded on them. They have '9016 FPC' on their little backs. They are used in a well known TV game computer and this is the 'Mouse Number' for their 4116. If you have ever had to buy a non-standard replacement part you will know that the 'Mouse Number' part can be VERY expensive. We don't want to sell them as 9016 FPC's we want to sell them as 4116's - and at a great price. The normal (i.e. lower than most) price for our 250nS 4116 is \$2.50 You can grab a 9016 FPC (150nS) 1 off for only \$1.95!!! For larger quantities see below.

This price includes sales tax!!



1-9 pcs \$1.95
10-24 pcs \$1.85
25-99 pcs \$1.75
100+ \$1.65

Edgeconnectors

1-9 \$3.50 ea
10+ \$2.95 ea

Collectors special. Made by UECL of England. Sold in quantity for over \$10 each. Each Olally Phthalate moulded connector contains 170 heavily gold plated bifurcated contacts (2x 85 way). Each contact is solder eyelet terminated. The connector is 217mm long but you can cut it down to any length you wish. Outstanding quality.

AM/FM STEREO CAR CASSETTE

Unbelievably low priced (Pre Budget tax) That's right! An AM/FM Stereo Radio and Cassette!

Features:

- * 2 x 7 watts * One lever operation (fast forward and eject) * Tape run indicator
- * FM Stereo indicator * Auto stop * Adjustable pitch controls * Mounting hardware included.



STAGGERING VALUE ONLY **\$69.50**

LOW COST WALKIE TALKIES

What can we say?

Both voice and morse transmission

ONLY

12.50

ea



POWERTRAN TRANSCENDENT 2000

This is the famous UK designed single-board synthesiser from the UK kit experts POWERTRAN. Jaycar imported a kit and had it professionally built for evaluation. It works beautifully and is very well put together. We estimate that it cost us over \$700 including airfreight, duty, cost, customs and labour. We decided not to go ahead with an Australian version but we still have this beautiful prototype.

You can have it for \$500 - No deals. Ring first to check to see if it has already been sold.

Ref: March 1982. NEW LOW PRICE

This P.A. Module is chock full of high quality Jaycar goodies like, extruded jig drilled heatsink bracket, Beryllium Oxide washers etc. Were selling at \$79.50 but, despite inflation, despite sales tax now only \$69.50.

ETI 499 150W MOSFET AMP ONLY \$69.50 SAVE \$10!!



SAVE OVER \$200!!

S0-239

UHF PANEL SOCKET

1/2 Normal Price

\$1.20

1-9 75c

10+ 59c



Jaycar NUMBER 1 FOR KITS

125 York Street, Sydney 2000
Phone: 264 6688 Telex: 72293
"Nevilles Corner"
Cnr. Carlingford & Pennant Hills Road,
Carlingford
Phone: 872 4422
Mail Orders To: Box K-39 Haymarket
Sydney 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.50)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm


MAIL ORDER BY BANKCARD VIA YOUR PHONE



YOU CAN PHONE CARLINGFORD ON 872 4444 AS WELL!

Radio pioneer passes on

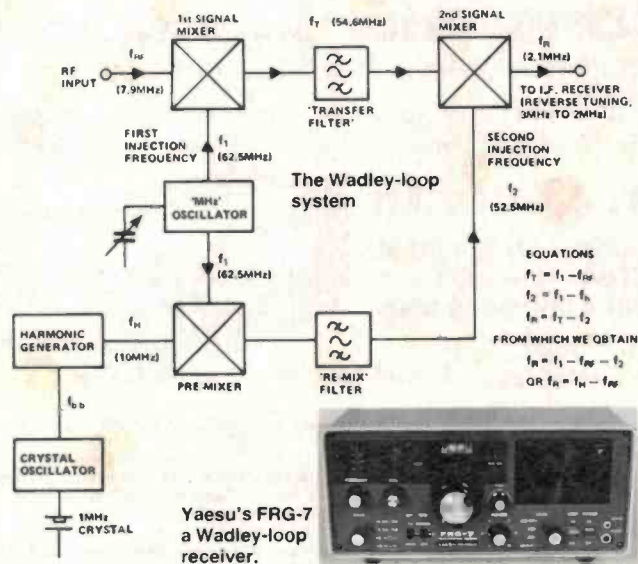Dr. Trevor Wadley, who devised the 'Wadley Loop' method of receiver tuning based on three stages of mixing that automatically cancelled oscillator drift, died recently in South Africa.



The success of Racal Electronics was founded on Dr. Wadley's invention. When they were just a new and little-known English firm, Racal decided to back the then radical ideas of Dr. Wadley when he took the scheme to Britain in the early 1950s. He had offered it to a number of well-known British firms: all regarded it with scepticism. Only Racal were prepared to take the risk and so was born the RA17.

It is said that even Racal almost despaired at one stage in development until somebody found that by making a saw cut in the chassis the performance of the complex filters could be vastly improved. Such was the worldwide success of the RA17 that it rapidly took Racal to the top and made them a real force in all branches of RF communications.

Racal Electronics, now a major electronics and communications group, recently announced that

it has made a net profit (before taxation) of over £73 million on a turnover that has reached a staggering £536 million.

The Wadley-loop system is widely used in shortwave and communications receivers today, made by many famous manufacturers. Receivers are made by Yaesu Musen (FRG-7 and FRG-7000 are very well-known), Drake and Standard. A South African firm associated with Dr. Wadley, Barlow-Wadley, made and sold a portable shortwave receiver around the world using the Wadley-loop tuning scheme.

The tuning scheme employs a system of additive and subtractive pre-mixing of the local oscillator so that any drift is cancelled. Receivers covering 100 kHz to over 30 MHz in 1 MHz segments, with readout to better than 1 kHz in the days before digital dials, were made and the scheme gave better performance than synthesiser systems employed at that time. Mass production and solid state circuitry brought down the cost of employing the scheme and 'consumer' shortwave receivers with Wadley-loop front ends appeared in the early 1970s.

Dr. Wadley, an engineer of brilliance and achievement, died recently in South Africa at the age of 61 years.

Electronics courses at Newcastle Tech.

Newcastle Technical College has scheduled a range of trade, post-trade and special courses in electronics for 1983.

A part time Electronics trade course covering all aspects of digital and analogue techniques is offered. Attendance is one day per week or two nights per week for three years. This trade course is also available in a block release attendance pattern of three days every third week for country students.

Post trade courses are available in Television Receiver Principles, Industrial Electronics and Semiconductor Electronics. Special courses include Microprocessor Evaluation, Microprocessor Circuits and Applications, Film and Television Production for Education and Industry, Principles of Two Way Radio and Two Way Radio Users Courses.

Enquiries should be made to the Senior Head Teacher, School of Electronics, Newcastle Technical College, Maitland Rd, Tighes Hill NSW 2297. (049)61-0461 Ext 367. Enrolments will be accepted on February 3, 4, 7 and 8, 1983 from 10am to 7pm.

New address for Zephyr Products

Zephyr Products, after 16 years in their old premises have moved into a new building which has showroom, office, factory and warehouse facilities.

Zephyr Products have recently been appointed as Victorian distributor for the Ralmar range of hi-fi car sound and accessory products. This range, together with RCF speakers, Primo microphones, MM mixers, Etone and Novic speakers, Motorola piezo electric tweeters and the new ZPE Series II power MOSFET professional amplifiers will be on display.

An expanded stock of Plessey Components and L M Ericsson Telecom approved isolation and audi transformers will be available for trade sales.

Zephyr Products' new address is 421 Warrigal Road, Moorabbin Vic. 3189. (03) 553-3266.

Free energy from the sun

Tandy Electronics is using solar cells which are suitable for battery charging and powering small devices like transistor radios or small electric motors.

The Tandy solar panel generates approximately half a watt of power in full sunlight and includes two mirror panels to help concentrate the sun's rays. It has a switchable output of 6 V at 80 mA or 12 V at 40 mA which can be used to charge batteries (like Tandy's 9 V Nickel Cadmium transistor radio cell), or to directly power radios, calculators, toys and many other small devices.

Tandy sells several solar cells and panels, ranging in price from

\$6.59 for a single 25 x 51 mm cell to \$31.95 for a solar panel (a pre-wired bank of 32 solar cells with lenses and reflectors).

Tandy will also be selling a 120-project Solar Energy kit which, at \$29.95, makes a highly entertaining and educational children's gift. The projects include experiments like a sundial, sun-powered transistor radio and a perpetual-motion pendulum. They also have a \$16.95 Solar Motor kit consisting of an efficient solar cell pre-wired



to a small dc motor. It can be used for powering small model boats, windmills, colour wheels and similar educational projects.



Chloride has maintenance-free systems battery

One year after the release of their maintenance-free auto battery, the Exide Torquestarter, Chloride announced their first industrial battery series.

The Exide RE Systems Battery Series is a range of sealed recombination electrolyte lead batteries.

One feature of the Exide RE Systems battery is that after accidental discharge to zero potential it will recharge with little or no loss of capacity, an ability Chloride believe is totally out of the reach of gell or cylindrical sealed battery types. It has high tolerance to over-charge and will hold its charge in storage for 18 months or more at 25°C ambient. It will give up to 1200 charge/discharge cycles and five to six years float service life. Thus the user has, in the one battery, the ability to give both standby and charge/discharge cycling duty.

It works just as well on its side or even upside-down, as it does the right way up. Neither acid nor gas escapes from its sealed case so there's no corrosion of the terminals and no risk of explosion. In fact, there is no way into the battery.

The design uses special felted fibreglass separators highly absorbent to carry the electrolyte

in close contact with the plates. There is no free electrolyte whatever sloshing loose within the battery. This last feature has won the Exide RE Systems battery its unqualified approval by the Department of Transport for carriage upon aircraft, important to makers and users of battery powered equipment such as wheelchairs. The design produces no hydrogen by electrolysis and oxygen produced during charging is recombined within the battery virtually as it is formed.

The new Exide RE Systems range of batteries comes in a great many shapes, sizes and performance categories. In 6 V, there are models offering from 1.2 to 10 ampere-hours. The 12 V models offer 1.2-24 ampere-hours. Chloride are expected to announce extensions to this range of models quite soon.

Chloride Batteries can be found at 147-149 Woodpark Rd, Smithfield NSW 2164.

What a nerve. Now there's a bionic ear.

The bionic ear will soon be a reality for millions of nerve-deaf people throughout the world. It was developed by the University of Melbourne in conjunction with a Sydney based firm, Telectronics Pty Ltd, part of the Nucleus group of companies, which is well known for its expertise in implantable prosthesis.

The Department of Science and Technology has agreed to fund further research and development for the nine year old project and it is now expected that the device will be available by the mid 1980s.

The device is based on the principle of electronically receiving, processing and coding sounds in a similar manner to that which occurs naturally in the nerve fibres of people with normal hearing. A coded signal is sent by an externally worn transmitter to a miniature receiver-stimulator implanted behind the ear. The receiver-stimulator converts the signals to electrical impulses which are conducted to the inner ear where the nerve fibres are stimulated electrically to enable the nerve-deaf to recognise speech and other sounds.

During the first phase of the project, Melbourne University implanted a prototype receiver into several patients, conducted clinical tests and evaluated the effectiveness of the device.

The second phase saw the University complete a portable prototype of a speech processor unit and a basic rehabilitation package suitable for immediate use and later development.

A biological test programme provided preliminary results which can be used as a basis for agreeing to a full clinical trial programme with health authorities.

The next phase of the project involves the full commercial development of the 'ear' which is being undertaken by the Nucleus group of companies.

This companion will never let you down

Companion is a close relative of Vitalcall, the personal medical emergency system which has given elderly and disabled people all over Australia a chance to enjoy a new sense of independence in their homes.

Like Vitalcall, Companion can quickly summon help in an emergency, simply by squeezing a lightweight plastic pendant. But Companion offers aid at a much lower cost and there are no ongoing payments (except for an occasional battery change).

Companion is a simple alarm system which, unlike Vitalcall, does not operate through the telephone system and therefore can be used in homes where there is no telephone at all. For this reason, it cannot provide the same back up features as Vitalcall. But because the function of Companion is less comprehensive it provides a cheaper alternative to the Vitalcall system.

Companion has 2 components, a lightweight plastic pendant and a small box containing a transmitter activated alarm. When the button on the pendant

is squeezed by the user a signal is sent out to the Companion box which is kept in the home of a neighbour or friend situated within a range of 200 metres. This signal will cause the alarm siren within the box to sound loudly and intermittently and will continue doing so until whoever is in charge of the unit cancels the alarm.


Each Companion is separately coded so that if a neighbour is also using the device the risk of interference is minimised. It retails for approximately \$195 and is covered by a money back guarantee so that if the device fails to operate because the chosen friend or neighbour is out of range, it can be returned in good order within 14 days for a full refund.

Contact the Vitalcall centre in your state for more information.

NOTES & ERRATA

Series 5000 Graphic Equaliser; November '82: In the circuit diagram on page 32, power supply section, diodes D2 and D3 are shown back to front. The pc board overlay is correct. In the parts list, R5 and R6 are shown as 15k, but 10k on the circuit. 10k is the correct value, though not critical.

Three-Channel Light Chaser, Ideas For Experimenters; October '82: Colin Burns of Mawson ACT wrote in to advise us of an error in this circuit. Both flip-flops should be cleared (reset) when their Q outputs (B and C) are high simultaneously. This is to produce a high output (A) from the NOR gate IC3a. The modification required to achieve this is shown below. Only when both Q outputs are low will the flip-flops be cleared. This arrangement also uses one less NOR gate.

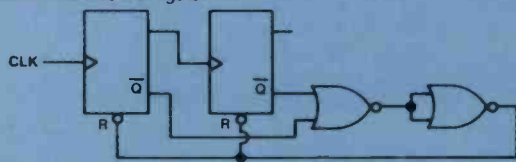


Audio Amplifiers Using Nested Differentiating Feedback Loops, Part 2; November '82: Equation (10) on the bottom of page 123 is missing the 'tau'. It should read $\tau_F = \mu_1 \beta \tau_x$. In Figure 11, the pictures for (a) and (c) have been swapped inadvertently.

$$\frac{d}{dx} \left(\frac{u}{v} \right) = \frac{v (du/dx) - u (dv/dx)}{v^2}$$

$$i^2 = -1$$

$$\int e^x dx = e^x$$
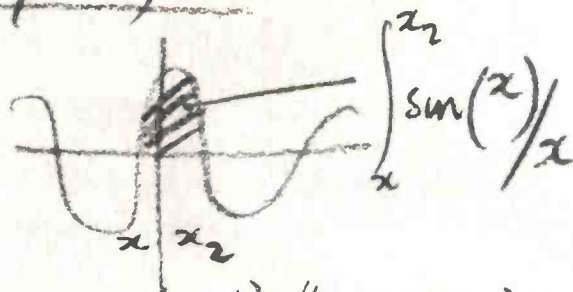
$$y = \frac{\tan^4 52.67}{(4 \times 7.83)}$$



$$(3.14159 + 7.32i)(c + 100i) = (3.14159c - (7.32 \times 100)) + ((3.14159 \times 100) + 7.32c)i$$

$$F(t) = \frac{1}{2\pi i} \int_{c-i\infty}^{c+i\infty} e^{st} / (s) ds$$

$$[r(\cos \theta + i \sin \theta)]^p = r^p (\cos p\theta + i \sin p\theta)$$

$$\hat{A} \cdot \hat{B} = \hat{A} \hat{B} \cos \theta$$

....or get a new Hewlett-Packard HP-15C.

They're the options. You can spend hours with a pencil working out a seven-equation problem or you can spend around 28 seconds with the HP-15C.

It's possible because of the two new sets of functions, never before built into a Hewlett-Packard calculator: Matrix and Complex number operations.

Once matrix elements are defined, matrix arithmetic inversions and transpositions are keystroke-easy.

Up to 64 matrix elements can be stored in the calculator's memory and these can be distributed among five different matrices, this model also has solve and integrate keys.

In addition, the HP-15C's arithmetic and transcendental functions (exponential, logarithmic, trigonometric and hyperbolic



operate on complex and real numbers.

And to make your decision even easier, the HP-15C programming features include up to 448 lines of dynamic continuous memory, five user-definable keys, 25 program labels,

insert/delete editing, 10 flags, 12 conditional tests and indirect-programming control.

Do you really have any choice?


To see the new HP-15C calculator, call Hewlett-Packard Personal Computation Group for dealer locations.

Sydney: 887 1611; Melbourne: 890 6351; Adelaide: 272 5911; Perth: 383 2188; Brisbane: 304 133; Canberra: 80 4244.



HP78R/2

Is nothing sacred?

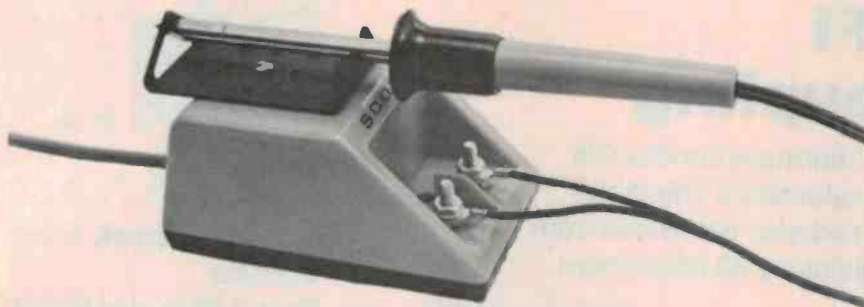

Yet another of the trusted and familiar objects of our youth has gone, the sober black shape of the Scope iron has been replaced with a glossy orange and black 1983 model which fortunately retains most of the working parts of the previous model.

The 'Superscope', first released in 1949 as Australia's earliest temperature controlled iron, had a traditional shape and black or grey handles. Changes to the iron include a more comfortable and impact resistant temperature switch and handle in bright orange and black. Scope advise that apart from the new handle and switch mouldings all other parts are interchangeable with previous models.

The new 'solder system' also includes a 240 V — 4 V power supply unit with electrostatic shield. This is in a matching orange/black housing with iron rest for conventional on-or-under the bench mounting. The thumb switch allows control of the tip temperature in the range 200°C — 500°C and also modulates the effective wattage 20 W — 140 W to suit the unpredictable nature of service and repair soldering.

A 10 W — 70 W 'miniscope' is

also offered using the same PSU. A 12 V version of the 'Superscope' delivering 20 W — 180 W is widely used by Telecom technicians, auto electricians and farmers who are beyond 240 V reticulated power. Prices of the new models are unchanged and supplies are available through a wide range of trade and retail outlets.

For more information contact Scope Laboratories, 3 Walton St, Airport West Vic. 3042. (03)338-1566.

13.8 Volt power supplies

Benelec Pty Ltd distribute a range of 13.8 V power supplies suitable for powering equipment designed to operate from a nominal 12 Vdc battery supply.

The 'Panther' power supply, catalogue no. 9-102, is rated to supply 2 A continuously and 4 A peak. It features a LED 'on' indicator and short circuit protection. It is housed in a sturdy plastic case and is ideal for powering CB or marine transceivers. The Panther is SEC approved.



The 'Transwest Model MK III' is rated to deliver 4 A continuous output, up to 7.5 A on peaks. It features a neon 'on' indicator and short circuit protection. This supply is housed in a sturdy metal case with output terminals at the rear. An on/off switch is mounted on the front panel, along with the primary circuit fuse. Overvoltage protection is also included.

The 'Transwest Model MK IV' has the same features as the Model MK III but is rated to deliver 6 A continuously, up to 10 A on peaks.

Further information can be obtained from Benelec Pty Ltd, P.O. Box 21, Bondi Beach NSW 2026. (02)665-8211.

Sennheiser impedance measurer

Sennheiser has released a compact, battery-driven impedance measurer called the ZP3. It will measure impedances in loudspeakers and loudspeaker systems, in line transformers, deflection coils and audio transformers.

Fitted with six switchable measuring ranges, the ZP3 enables one to accurately determine whether the test object is of an inductive or capacitive nature.

The impedance value obtained is always accurate and easy-to-read on the 3½-digit LCD read-out and a six-part subdivision of the measuring range from 20 R to 2 M, say Sennheiser. The maximum measuring error is smaller than 5%. There is no need to calibrate the ZP3 either before or after carrying out the measuring process.

The load placed upon the test object in each of the six measuring ranges is so slight that even sensitive components such as recorder heads, sound pickups and microphones can be measured without fear of damage Sennheiser claim. In addition to measuring impedances in the inductive range, the ZP3 is also suitable for determining capacitances and purely ohmic resistances.

For more information contact R.H. Cunningham, 146 Roden St, West Melbourne Vic. 3003. (03)329-9633.

UV printed circuit exposure box

The latest Mentrion UV exposure box is suitable for exposure of photosensitive materials such as the Dupont Riston 3000 series and 3M Scotchcal materials.

Designated as the 300NSUV, this unit exposes artwork down to approximately 0.55 mm track separations.

The 300NSUV has a number of features including an exposure timing switch, non-skid rubber feet and foam clamping.

Full details are available from the Australian distributors, Royston Electronics, 27 Normanby Road, Notting Hill Vic. 3168. (03)543-5122 or 15/59 Moxon Road, Punchbowl NSW 2196. (02)709-5293.



FANTASTIC OFFER!

8-Function, 23-Range
LCD digital multimeter
UNDER \$100!

SEE PAGE 15

Heatsink insulators provide EMI/RFI shielding-decoupling

Sil-Pad, who make a wide range of thermally conductive insulators for semiconductors, has released a shielding-decoupling type claimed to reduce radiated emissions from semiconductors mounted on a heatsink by 60 dB or more.

Dubbed the Sil-Pad Shield, the product is a physically tough pad available in a variety of shapes claimed to have low thermal resistance and high dielectric strength.

The shield consists of a one mil. copper sandwich bonded between two layers of calendared nine mil. Sil-Pad material. Part of the copper is exposed for attachment of an earth lead to 'drain off' the signal and reduce radiation from the case of the device. A reduction of 60 dB or greater, generally considered to be excellent, can be achieved at fre-



quencies above 10 kHz, Sil-Pad claim. For lower frequency applications, thicker copper in the sandwich can be specified.

Components that can utilise Sil-Pad Shields include: high speed switching transistors, relays, oscillators, DIP packages, chips etc. In a lot of instances, attenuation at component level will prevent the radiated signal from penetrating and interfering with other components and will also, in some cases, preclude total case shielding.

Shapes currently available are TO-3 and TO-220. Non standard shapes can be produced on request with a lead time of about eight weeks.

For further information contact Mr. Peter Lloyd, Scientific Electronics, 6 Holloway Drive, Bayswater Vic. 3153. (03)762-5777.

Combined digital/analogue meter

A panel meter which combines the readout precision of a digital display with a trend indication similar to that of an analogue meter has been developed by Sifam Ltd, England, and is available from C & K Electronics.

In addition to its dual display, the new meter also constitutes what is claimed to be the first 'off-the-shelf' digital meter capable of being programmed to read in any engineering unit, including non-linear quantities. It can also be programmed to function as a meter relay, initiating alarm or control signals at fixed or variable set points.


Called 'Harmony', the meter incorporates LCDs and micro-

processing. The result is a compact, rectangular display resembling a conventional digital meter, but incorporating a horizontal trend-bar, the length of which fluctuates in proportion to the reading.

Essentially a millivoltmeter with a range of 0—50 mV dc and optional current ranges of 100 μ A and 1 mA, the digital readout is in four digits with a maximum

display of 9999. The trend-bar, made up of 31 segments, grows or falls alongside a printed scale located just beneath the digital display.

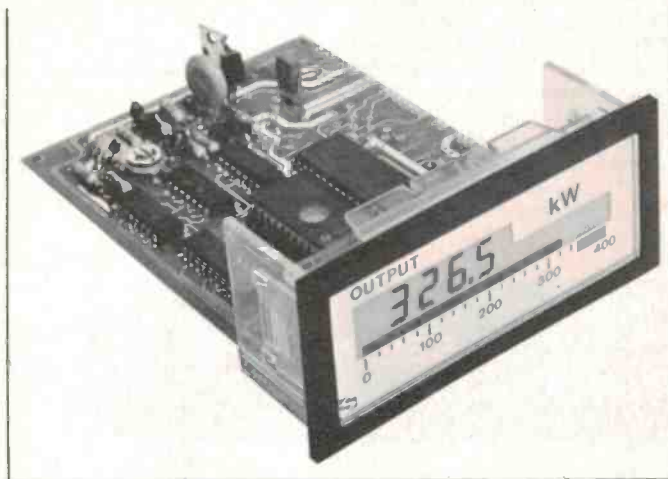For further information contact C & K Electronics (Aust.) Pty Ltd, 15 Cowper St, Parramatta NSW 2150. (02)635-0799.



Comprehensive fuse range

Fuses may seem like mundane items, but they're often worth their cost 10 000 times over for the protection they afford.

Benelec Pty Ltd stock a wide range of fuses in fast blow, slow blow and general purpose types.


They stock 5 x 20 mm glass cartridge instrument fuses in both fast and slow blow types with ratings from as low as 50 mA right up to 15 A. The fast blow types are designated catalogue no. 14-100xx, the slow blow types, catalogue no. 14-400xx. The catalogue number suffix indicates the rating. e.g. 14-10050 is a 50 mA type, 14-11100 is a 1 A type, 14-12100 a 10 A type.

In the 6.35 x 32 mm (3AG) models, Benelec carry general

purpose and slow blow 250 V types as well as 32 V automotive types. The 14-300xx range are general purpose wire fuses available in ratings from 100 mA to 25 A. The 14-500xx slow blow range can be obtained in ratings from 100 mA to 20 A, while the 14-200xx automotive range can be obtained in ratings from 1 A to 30 A.

All fuses are available in packets of 10 pieces, boxes of 200 pieces or cartons up to 20 000.

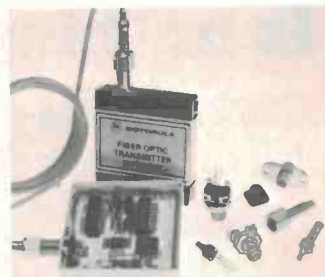Contact Benelec Pty Ltd for more information at P.O. Box 21, Bondi Beach NSW 2026. (02)665-8211.



Soanar stock fibre optics

Soanar Electronics Pty Ltd have announced that they now stock fibre optic components and accessories at all Soanar Branches throughout Australia.

Optical fibre cable is available in continuous lengths in multiples of one metre to a maximum of one kilometre. The 125 micron fibre in 2.7 mm diameter cable is designed for high flexibility and tensile strength and can be supplied plain or prefitted with connectors at the factory.

For those people wishing to fit connectors themselves Soanar have cutting and stripping tools that remove the covering from the optical fibre and then cut the fibre squarely for a mirror-like surface. Two types of connector are stocked by Soanar. One type enables fibre optic cables to be joined together and the other type couples the fibre to active components.

Further information on these products is available from the Soanar Branch in your State or by contacting Head Office at Soanar Electronics Pty Ltd, 30 Lexton Road, Box Hill Vic. 3128. (03)840-1222.

ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA. Ph (03) 489 8131. Telex No. 38897

THIS MONTHS KITS

ETI-488 60 W AMP USING TWO NDFLs



Very low distortion amplifier module can be used to replace modules in existing systems or as the basis of a new amplifier system.

ETI-905 POLYPHONIC TOUCH SENSOR ORGAN



Organ features touch sensor keyboard, 25-note range, two voices and loudspeaker output.

ETI-334 AUTO TESTER



Just the thing to keep in the glovebox or toolkit to find those nasty electrical bugaboos that occur at awkward times. Simple to build, simple use.

ETI-1510 MODEL TRAIN POINTS CONTROLLER AND INDICATORS



This kit comprises a capacitive discharge power supply for operating the points solenoids and remote indicators that show which way the points have been set.

Electric fence **\$17.50**



SEPTEMBER EA 1982

Check our prices

Ultrasonic Rule



AUGUST EA 1982

\$49.00

Car Computer



AUGUST EA 1982

\$109

Tacho/dwell meter with digital display



MAY EA 1982

\$62

12/240 volt Inverter



MAY EA 1982

\$55

\$35

Universal preamplifier for MM/MC cartridges

MAY EA 1982



DIGITAL ENGINE ANALYSER



Engine Analyser Kit

\$48.50



JANUARY EA 1982

Eprom Programmer

\$55.00



Analogue and Digital Storage CRO Kit

\$189.00

\$79.50 Function Generator




APRIL EA 1982



SEPTEMBER EA 1982

\$55.00

Dual Tracking Power Supply

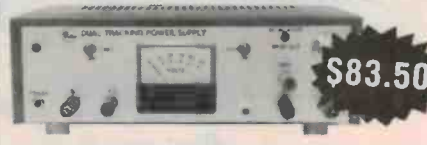

\$83.50

Power Monitor

JULY EA 1982



\$18

Portable 3 1/2 Digit Heart Rate Monitor

JULY EA 1982



\$79.00

100w Sub-Woofer Amplifier



JULY EA 1982

\$85.00

ETI-1508 TRAIN CONTROLLER



This dual-circuit unit provides throttle and brake controls that work in the same manner as on a 'real' train. The circuitry gives the driver the feel of inertia as well as loading. It can run anything from micro-gauge to twin 'O' gauge engines and cost is far lower than 'commercial' equivalents. Tentative parts list attached.

ETI-162 30 V/1 A FULLY PROTECTED POWER SUPPLY



The last power supply we did was the phenomenally popular ETI-131. This low cost supply features full protection, output variation from 0 V to 30 V and selectable current limit. Both voltage and current metering is provided. Tentative parts list attached.

EA ELECTRONIC STARTER

FOR FLUORESCENT LAMPS **\$5**




OCTOBER EA 1982

EA DIGITAL READOUT FOR SW RECIEVERS **P.O.A.**
OCTOBER EA 1982



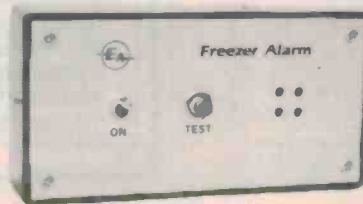EA EASY-TO-BUILD FREEZER ALARM **\$21**
OCTOBER EA 1982



OVER 200 NOW SOLD **\$189**
EA INVERTER INCLUDING TRANSFORMER



P & P \$10.00

JUNE EA 1982

Minimum P & P \$3.00 for kits



Weller



Weller

The Tools. from Cooper The Toolmaker.

Weller industrial SPI non-temperature controlled line voltage soldering irons, with iron plated copper tips, stainless steel barrels. Impact and heat resistant handles are lightweight.

Available as SPI25D 25 watt or SPI40D 40 watt irons.

The Weller WTCPN soldering station is temperature controlled and combines high volume capability with precision performance. The low voltage TC201 soldering pencil employs the exclusive "closed" loop method to control maximum temperature and protect sensitive components.



Lufkin
Official Supplier of
Measuring Tapes to the
XII Commonwealth Games
in Australia 1982.

The Cooper Group
CRESCENT LUFKIN NICHOLSON PLUMB
WELLER WISS XCELITE

The Cooper Tool Group Limited
P.O. Box 366, Nungong Street
Albury NSW 2640, Australia
Tel: 215511, Telex: 56995



COMPUTER CLUBS

**MEMBERS
INTERESTED IN
DIRECT-CONNECT
MODEMS?**

You can bulk-purchase ETI-644 Direct-Connect Modem pc boards at a saving of 15% if you purchase 10 or more in one order, then resell to your members for a slight profit to swell club funds as well as passing on a saving to your members.

Place your orders now. For 10 or more boards, the price is \$43.50 each. Send cheque with order to:

**ETI-644 Modem pc boards
ETI Magazine
15 Boundary St
RUSHCUTTERS BAY NSW 2011**

Back issues of the October 1982 issue, featuring the modem, can be purchased at the same time for \$1.50 each for 10 or more.

COMDEC

**FREE
OFFER**

BUSINESS TECHNOLOGY

A wonderful opportunity to receive a one year's subscription to Australia's leading BUSINESS TECHNOLOGY magazine. Exclusively for business people who have the power to purchase or influence the purchase of office technology equipment or services.

This offer applies in Australia only

Yes! I will take advantage of this opportunity to receive a free subscription to Comdec Business Technology

Name

Title

Company

Address

Postcode

My company's main activity is

and it employs people. *

Please attach your business card or letterhead, fill in the above form and return to:-


**Comdec Business Technology
4th Floor, 15 Boundary Street, Rushcutters Bay NSW 2011.**

* This Information will be kept strictly confidential

SPECIAL ETI READER OFFER

UNIVOLT DT-860 LCD DIGITAL MULTIMETER

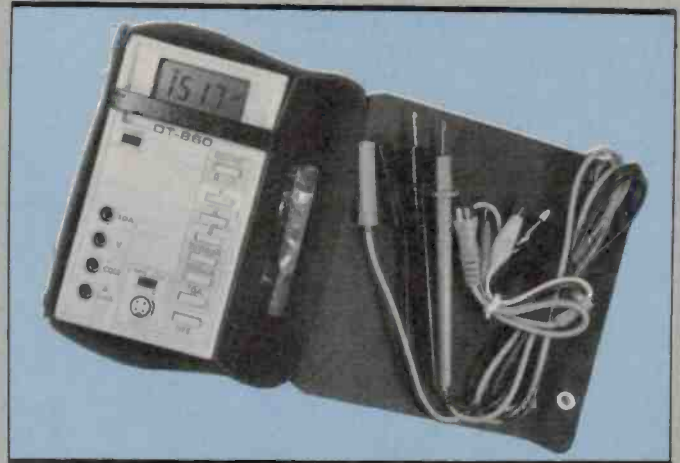- 3½ DIGITS
- 8 FUNCTIONS
- 23 RANGES
- PUSHBUTTON OPERATION
- DC VOLTS TO 1 kV, AC VOLTS TO 750 V
- RESISTANCE FROM 200 OHMS TO 20M
- AUTO-RANGING ON AC/DC VOLTS & RESISTANCE
- AC & DC CURRENT TO TEN AMPS
- FINGER-GUARDS ON PROBES & SHROUDED PLUGS FOR MAXIMUM SAFETY
- TRANSISTOR GAIN MEASUREMENT
- TRANSISTOR CLIP LEAD INCLUDED
- PROTECTIVE CARRY CASE INCLUDED



Here is an opportunity to buy a versatile eight-function, 23-range LCD digital multimeter at a very good price, complete with carry case, special probes and leads.

SPECIAL OFFER PRICE \$97.50 tax paid \$84.38 tax exempt

This instrument would normally sell for about \$130 retail.

This is an entirely new multimeter from Univolt and this offer is being made as a special promotion for the Model DT-860 which has only just been released here.

The DT-860 is a 3½-digit liquid crystal display instrument featuring 23 ranges in eight functions, three functions being auto-ranging. It is a handheld instrument but comes with a tilt stand if you don't need it sitting flat on a bench. The liquid crystal display features 12 mm high digits plus value and function indicators (volts, ohms, ac, dc etc). Range and function selection is by pushbuttons down the right hand side of the instrument. Four recessed probe sockets (which avoid accidental finger contact — a safety feature) are placed down the left hand side while a socket for the h_{FE} clip lead probe is located in the bottom centre of the panel. It's a functional, well laid out front panel.

The test probes have shrouded plugs which prevents accidental finger contact, providing an added measure of safety when using the instrument on high voltage circuits, and the probes have finger guards, further adding to the safety features of this instrument. A strong, synthetic leather carry case is included and this has provision for strapping-in the instrument and a section for storing probes and the spare fuse. The instrument is powered by two 1.5 V 'AA' cells. Input impedance is 10 M Ω ; input capacitance is less than 50 pF.

We have tested a sample DT-860 in the ETI lab and found it met specifications, functioned well and was generally easy to use. The DT-860 appears to be a robust, well-made device. Any serviceman, technician, engineer or hobbyist would find it a very useful instrument.

INSPECTION

You can inspect one of these multimeters during office hours at ETI's Sydney and Melbourne offices:

Sydney: 4th Floor, 15 Boundary St
Rushcutters Bay

Melbourne: 22nd Floor, 150 Lonsdale St
Melbourne

HOW TO ORDER YOUR MULTIMETER

Fill out the coupon and enclose a cheque, bank cheque or money order for the amount required made out to BENELEC PTY LTD.

If you are not paying sales tax, please quote your sales tax number on the coupon, where indicated, or for schools, colleges or other educational institutions, enclose a sales tax declaration on your letterhead.

This offer is made by Benelec Pty Ltd. ETI is acting as a clearing house for orders. All mail orders will be despatched by certified post. Please allow up to four weeks for delivery.

Send the completed coupon (below) with cheque or money order to:

UNIVOLT MULTIMETER OFFER, c/o ETI, 15 Boundary St, Rushcutters Bay NSW 2011.

This offer is made by Benelec Pty Ltd, (Incorporated in NSW).

PLEASE SEND ME Univolt Model DT-860 multimeter(s) @ \$84.38 each, excl. tax or \$97.50 each, inc. tax.

Sales Tax No (If applicable)


Post and handling \$2.50

I enclose \$ total

Name

Address Postcode

Cheque or Money Order No. Signature

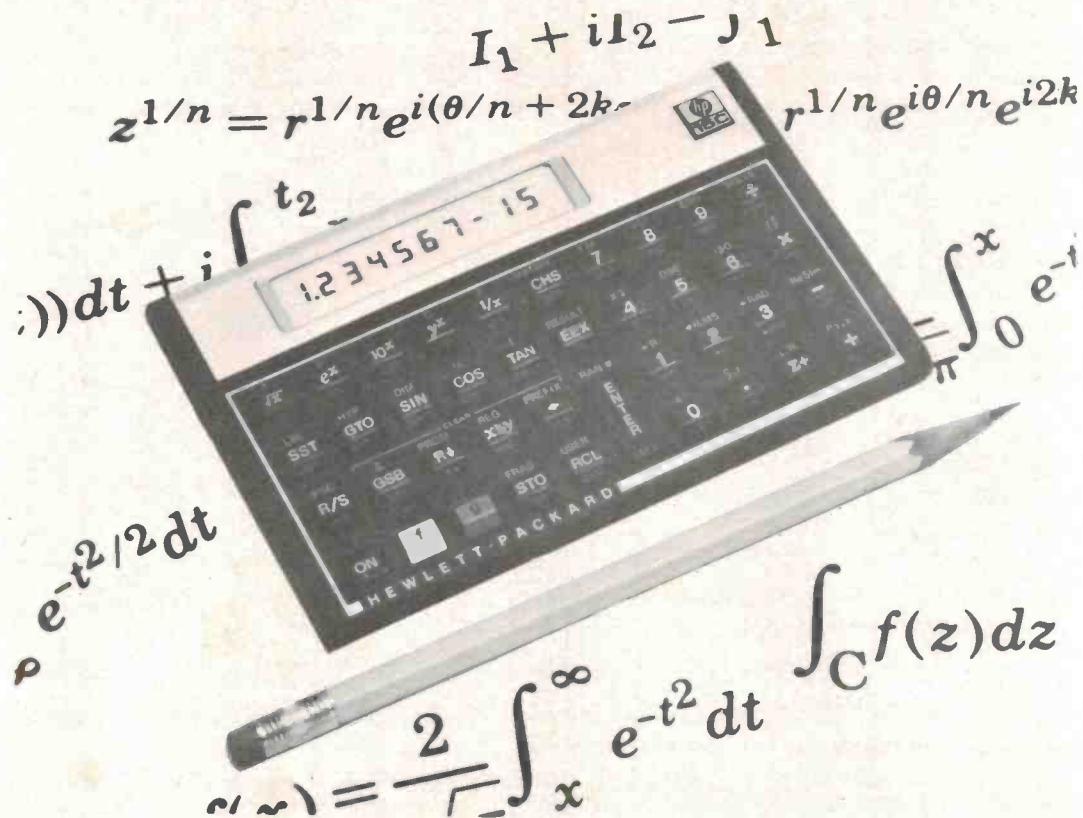

The HP-15C scientific calculator

The HP-15C is the perfect choice for the electrical or electronic engineer. Powerful and ingenious, it can operate in complex and matrix modes (it can even handle complex numbers forming matrices), solve for zeros and integrate functions.

What more could you want?

Jonathan Scott

IT IS POSSIBLE that you have noticed recent press releases for two new pocket calculators from Hewlett-Packard, the 15C and 16C. Why then is this article here, consuming a seemingly large space describing something you have seen outlined before? Simply because the HP-15C is so perfectly suited to the electrical or electronic engineer and is so powerful, ingenious and advanced in its design that we feel it demands special mention. If you need a calculator which is capable of solving problems in the fields of electronics or general science, then this machine is tailored to your requirements. If you have been thinking of purchasing a programmable calculator, updating your current one, converting to a small 'pocket' computer to tackle your numerical tasks or just want to get your hands on one of the finest examples of hardware and software

engineering in the marketplace today, then this is the time and the 15C is the machine. Interested? Then read on.

Features

The 15C follows two earlier machines in format, in that it is a low power consumption device with an LCD display and a soft off/on function. It has a number of features; some are standard for HP machines, some have appeared on only a few selected calculators before and some are completely new and unique. It is these last, coupled with the inclusion of *all* the features developed on HP scientific calculators to date (despite some of these features not being on some later models) which makes this little gem the one

to sit up and take notice of. If you are already familiar with HP machines you can skip to the section marked 'Classier functions'; if not the following is designed to give you a brief introduction to the Rolls Royce series of pocket calculators.

The first and most perpetually pleasing feature which has been the trademark of all HP calculators from the 35 onwards is Reverse Polish Notation. This means that the calculator is stack orientated, or in short, it has no '=' button. It also has no '(or)' buttons, as these are all unnecessary. Other calculators have stacks as, of course, do computers, but they are not visible to the user. In the HP, the function you select is executed as soon as you touch the button identifying it. Thus of course, the numbers upon which you wish to act must be already present in the machine. At first this seems as

if it is a cumbersome and illogical method of doing it, but it is recognised in the scientific community as the best way, once you are accustomed to it.

There is a learning period associated with an HP calculator if it is your first, but the time spent will be paid back tenfold in short order. The more involved and vinculum-nested the problem, the greater the gain over the bracket-and-equals method. For the simplest two numbers-to-be-added problem the number of keystrokes is the same, but the thinking is easier. There are a lot of ways of trying to describe to one not initiated in the technique why it is better, but it can be explained simply by saying that the calculator tackles the problem in the way you think about it. So it is not necessary to try to write the problem out in single line, vinculumless form before entering it into the machine.

All HPs have a four-deep stack, as does the 15C which handles pretty stiff problems without access to other memory. A further benefit of stack accessibility is the retention and availability of the last operand put into the stack in the 'last X' register. This allows correction of your last keystroke if it was wrong.

Next is the almost standard facility (these days) of continuous memory. The 15C keeps not only all programs, all memory contents and all stack contents, but even the place in the program where it left off. It also remembers its mode etc, which means that it can leave one of its advanced functions mid way through and expect to resume later.

It provides all logarithmic functions, trigonometric and hyperbolic trigonometric functions and their inverses, as well as all the simple functions such as square and square root etc, which I shall not list here. It also supports statistical functions with the HP complete Sigma and inverse Sigma data-acquiring function, mean, standard deviation and linear regression (line of best fit) with correlation coefficient. It will round off and also generate pseudorandom numbers.

Like most low power calculators the 15C is not fast, but then you couldn't call it slow either as it will loop 100 times in just over 30 seconds. This is half the speed of the HP-41, two-thirds the speed of the 30-series LED display (not low power) HPs, and is comparable to the low power pocket BASIC machines. It is sufficiently fast that you are not required to pause after a trig function before pressing the next button, as is the case on some calculators. Note here that the LCD display does take a moment to come up, but the machine finishes what it is doing and handles the next key press quickly, so you can keep punching the buttons without waiting to see the answer reappear.

Functions with class — emphasise 'ass'!

In addition to the usual functions, the 15C has a number of pleasing incorporations which are not really advanced, but are very nice to have. Firstly it can address indirectly using a dedicated register. It will go to a calculated line number, program label or fetch data from a calculated register. It will also display a computed number of decimal

places or significant figures and truncate to the set significance if required.

It has five alphabetic labels which may be used to reference subroutine special functions in a single keystroke with the 'user' mode set. This is handy if there are a few complex jobs you must do again and again on a lot of different numbers. These also identify certain routines to the advanced functions which we will describe shortly.

The machine will nest seven levels deep in subroutines and registers an error if you try to overshoot, too.

It has a memory pool, which is all the unused memory kept in a state where it can be converted into data registers or program steps or be used by an advanced function when required. Any surplus memory is returned to the pool when it is no longer required and memory is taken automatically when needed. There is no need to stipulate what the boundaries are, except that the data registers must be numbered, presumably to allow out-of-range errors to be trapped when indirectly addressing. Up to 443 lines of program or 64 registers can be held.

It also has permutation and combination functions which add a little extra convenience for statisticians. Factorial now calculates the Gamma function too!

By means of a cunning command ('test' and a digit following) all possible conditional tests between the first two stack registers and the lowest stack register ('X') and zero have been included. That is, you can see if the X register is less than (<), less than or equal to (≤), greater than (>), greater than or equal to (≥), equal to (=) or not equal to (≠) either Y or 0, without any additional fuss.

Finally, there is a new pair of looping commands which act like the BASIC 'For-Next' loop command. Each one can be called to act on any particular register, incrementing or decrementing its contents by one or any integer up to 99 and testing with respect to an integer up to 999. That is quite a mouthful, and takes a little getting used to in practice, but effectively greatly expands the looping capability of each loop, consuming only one register to hold the count, the increment and the comparison value!

Here ends the *excellent* and begins the *extraordinary*:

Advanced functions

x+iy, ∫, solve . . .

There are four advanced functions: the 15C will operate in a 'complex' mode which is when its stack and functions have real and imaginary parts; it will operate on matrices, placing descriptors of these in the stack or executing a choice of functions on them; it will 'solve' for the zeros of a function identified by a label and executed as a subroutine; and it will numerically integrate such a function. (These last two appeared on the HP-34C, but can be made more powerful in conjunction with the first two).

Starting with the complex-mode, as this no doubt caught the eye of all students in the electrical/electronic fields, let us look in detail at these four facilities. When the complex flag is set (it is flag 8) a 'C' annunciator appears in the display. Also, five registers disappear

from the free memory pool. These are used to create an imaginary stack parallel to the real one. From now on, all applicable functions operate as complex. If you hit multiply a full complex multiplication is performed, using real and imaginary X and Y registers. The same goes for square root, the trigonometrics, powering, logarithms, etc! So taking a complex number to a real or complex power is as easy as doing it for reals. The calculator is organised such that you may ignore the imaginary part and the results will be purely real, if the inputs were purely reals. The imaginary stack takes care of itself, not letting previously input or computed values from the imaginary side drop into the next calculations. Any time a number with a non-zero imaginary component becomes involved, the result is the true complex one. There are functions for viewing the imaginary component temporarily or entering the imaginary part of a number, but apart from these there is no hint of additional keystrokes or complexity required. Computations, particularly of trigonometrics, take a noticeable period of time which is hardly surprising, but for all other intents and purposes the machine is just as it was, but complex not purely real. At any time you can clear flag 8 and the imaginary facility goes away, freeing the five registers. (Last X is the fifth, so that the same error correction facility as has been on all HPs is available for complex results as well.)

Matrix mode is similar in that it is absent until invoked. When a matrix is created (dimensioned) the required memory disappears from the pool and the operator can then act on that matrix. Up to five matrices can be used, one for each of the five alpha labels, A through to E. A matrix may be dimensioned, re-dimensioned to a different size without loss of numbers in registers, dissolved, initialised to all elements of the same specified value, multiplied by a scalar or another matrix, inverted, have its determinant found or have a number of special matrix functions applied to it.

When called, the descriptor of a matrix appears in the X register. Instead of seeing a number, as is the case normally, the letter identifier of the matrix appears, along with two numbers telling you the current matrix size. This descriptor may be moved as usual in the stack. When you touch the multiply key, say, the matrix or scalar in the X register is multiplied with the matrix or scalar in the Y register. Touching the divide key gets you the inverse of one multiplied by the other, so again you can see that the calculator acts just as if it were dealing with purely real scalar numbers. Occasionally a matrix result cannot be placed in the same memory as one of the source matrices. Rather than the result becoming the matrix whose descriptor was in X, another matrix is defined as the result matrix. It receives the computed set of elements and its descriptor replaces the one which was in X. For example, if I wish to multiply $A_{2,3}$ (this means matrix A which has dimensions 2x3) by $C_{7,3}$, I call up A and C. Then I tell the calculator that I want E to hold the result. When I press multiply the display blinks and I finish up seeing the descriptor $E_{2,3}$ which has replaced the A and ▶

GREAT NEW PRODU

HOPE YOU HAD A GREAT NEW YEAR. WE LOOK FORWARD TO BEING OF SERVICE TO YOU IN '83

magnificent! *NEW EA Wide-band AM Tuner* ☆

Ref: EA Dec-Jan 82-83



Australia is one of the few countries in the world where wideband AM is transmitted. In fact a good quality AM signal can be much better than its FM counterpart!! Anyone who has suffered from FM multipath distortion will know what we mean. The Playmaster AM tuner is a true broad-bandwidth superhet design. See the frequency response graph. Once again, the Jaycar kit is a high quality approach. The cover illustration shows the high quality front panel supplied EXCLUSIVELY in our kit. (Note that the standard EA front panel artwork is different). The Jaycar kit provides all components to complete the project INCLUDING a completely pre-punched cabinet.

FANTASTIC VALUE
AT ONLY

\$249



BOGGLE GOGGLES! crazy \$9.50

You've wired your head for sound, now you can wire your head for light!! Great for parties or discos. Simply connect to your spectacles or sunglasses. CRAZY!!!

Ref: December 1982

JUMBO car vacuum cleaner

What next? Whitegoods? No! Jaycar has made a scoop purchase of what is in our opinion the best car vacuum cleaner around. Not a toy - It sold for \$29.95. We have less than 100 of these units (all accessories included) for only \$19.95. That's right \$19.95.
* 12V cig. lighter power * Powerful suction capability * Huge dust compartment for very dirty cars * Good for workbenches (12V reqd) * Inbuilt light.

ONLY **\$19⁹⁵** SAVE \$10!!



GREAT NEW KITS FROM DECEMBER ETI GREAT NEW KITS FROM DECEMBER ETI GREAT NEW KITS FROM DECEMBER ETI
GREAT NEW KITS FROM DECEMBER ETI GREAT NEW KITS FROM DECEMBER ETI GREAT NEW KITS FROM DECEMBER ETI

train controller

New project that features simulated inertia and loading.
- Throttle and brake controls like a 'real' train
- Will run Micro-gauge to twin 'O' gauge
- Complete with control panel
Ref: ETI December 1982

\$69
for single track



polyphonic organ ☆

- "Touch Sensitive" PCB board
- Fully Polyphonic
- Two voices
- 25 note, 2 octave keyboard
- Can run from battery or plugpack
Unbelievable performance for the price.
(Case not included)
Ref: ETI January 1983

\$49.50



0-30V 1amp power supply ☆

- Fully protected
- Output variable from 0-30V DC
- Selectable current limit
- Both voltage and current metering
- After a multimeter & soldering iron an absolute must for the enthusiast.
You will never own a more useful piece of gear.
Ref: ETI December 1982

\$49.50
complete



CTS & KITS FOR '83!

HOPE YOU HAD A GREAT NEW YEAR. WE LOOK FORWARD TO BEING OF SERVICE TO YOU IN '83


Video Enhancer

Unbelievable but true. This unit enables you to actually IMPROVE a copy of a recorded video tape. How? By amplifying the top end of the video signal by a small amount. This sharpens up the detail of the picture. Dubs can actually look better than the original. Works as a video distribution amplifier as well. Will drive up to 4 VCR's from one VCR Input.

value for money

NOT A KIT
BUILT &
TESTED

\$89

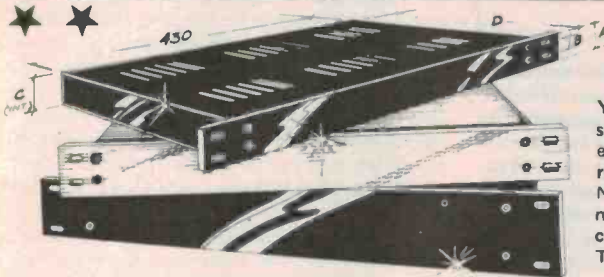

GREAT RACK CABINETS IN STOCK!!

Your Budget probably will stretch to afford our professional series all aluminium rack cabinets.

Now your Pre-amps, control modules, monitor panels etc can look every bit as good as Technics, Nakamichi etc.

Finish	A	B	C	Price	5 or more	Finish	A	B	C	Price	5 or more
Natural	44	34	38	\$39.50	\$38.00	Natural	88	57	82	\$45.00	\$42.50
Natural	132	89	126	\$49.50	\$45.00	Black	44	34	38	\$39.50	\$38.00
Black	88	57	82	\$45.00	\$42.50	Black	132	89	126	\$49.50	\$45.00

PRO-GRADE SOLDER SUCKER

SEE REVIEW EA DECEMBER 1982
Our claim. The best solder sucker for its price in Australia!

- Unique double diaphragm design
- O-ring seal
- Spare O-rings supplied
- Teflon tip
- Self-cleaning plunger
- One hand operation
- Non slip body
- Pro-grade for heavy usage.
- 225(l) x 28(d)mm
- Spare Teflon tip \$1.95




ONLY \$11.95

QUALITY FM ANTENNA "JABBER GRABBER"

\$29.50

Ground Plane Whips \$7.95ea

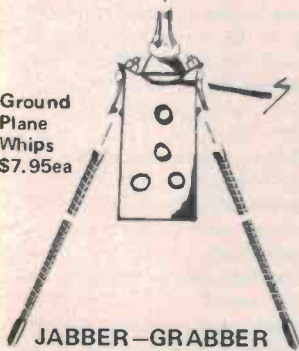

OK. So you have spent a fortune on your Hi Fi system. The FM is great. Almost. You are in a area where the FM fades badly or is affected by multipath distortion. Not all stations but only the ones that you want to listen to!! We may have the answer to your problem!! Jaycar has had a helical FM antenna SPECIALLY MADE for vertically polarised transmissions (i.e most FM stations). The unit is supplied with a vertical whip, heavy duty stainless steel bracket, pre-terminated coax lead (environmentally sealed), U-clamp. It will mount on top of your TV mast and give about 3dB of gain over isotropic. The bracket is designed to fit any flat surface & will even lock into a window sill!! If you cannot mast mount you will need the two ground plane radials as shown in the illustration. The "Jabber-Grabber" may be the FM antenna to solve your problems!!

low cost IC inserters extractors

Up until now these have cost a fortune!!

Features:

- CMOS SAFE conductive plastic
- Exclusive bent pin alignment guides in handle . 8 to 40 pins.
- Ground strap can be connected.
- One hand operation.

INSERTERS

CIT820	8-20 pin	ONLY \$5.95
CIT2428	24-28 pin	ONLY \$6.95
CIT3640	36-40 pin	ONLY \$8.95
CIT22	22 pin	\$6.50



from \$2.95


EXTRACTOR

Deceptively simple looking device. One piece metal construction. 8-40 pins ET-840 ONLY \$2.95 **IMPORTANT!!** Don't be conned into buying a non conductive inserter/extractor. The possible static damage to your MOS I.C.'s could cost you a fortune!!

'T-REX'

Our wirestripper, nicknamed 'Tyranosaurus-Rex' is far from extinct!! It's a great way to strip all sorts of cable without damaging the conductors. It's also a price breakthrough!!

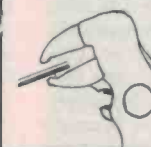- Automatically adjusts to insulation diameter.
- One hand operation.
- New low price for an automatic wirestripper



top ONLY buy \$9.95

HIGH SPEED LOGIC PROBE

- DTL/TTL/HTL/CMOS/MOS compatible!!
 - Pulse memory
 - 10MHz input frequency (tested to 12MHz)
 - ±50V input overload
 - Complete with leads.
- ONLY \$29.95**



Jaycar NUMBER 1 FOR KITS

125 York Street, Sydney 2000
Phone: 264 6688 Telex: 72293

"Nevilles Corner"
Cnr. Carlingford & Pennant Hills Road,
Carlingford
Phone: 872 4422

Mail Orders To: Box K-39 Haymarket
Sydney 2000


POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 8.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

MAIL ORDER BY
BANKCARD VIA
YOUR
PHONE



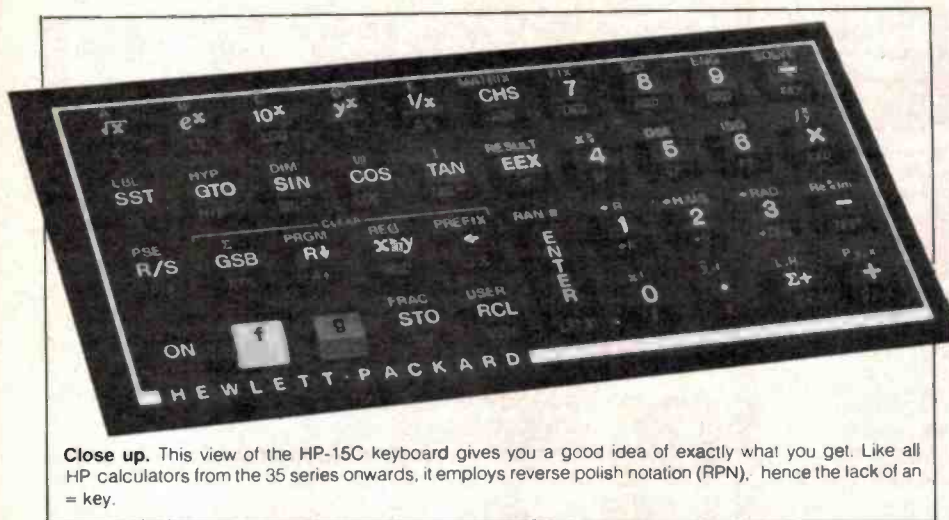YOU CAN PHONE CARLINGFORD ON 872 4444 AS WELL!



Close up. This view of the HP-15C keyboard gives you a good idea of exactly what you get. Like all HP calculators from the 35 series onwards, it employs reverse polish notation (RPN), hence the lack of an = key.

C descriptors in the stack. (The C descriptor is incidentally in 'last X'.) If I had not previously dimensioned E, or if E was the wrong size to receive the result, it is automatically set right by the function being called.

Complex numbers forming matrices can be handled using LU partitioned methods which are supported by the group of special matrix functions. These are invoked with a command similar to the one which allows the conditional tests to be implemented, namely the 'MATRIX n' command, where n is a digit. The rear of the 15C is printed with a list of errors, tests and matrix commands which correspond to the numbers 0-9.

The Solve and Integrate keys cause the numerical equivalent of the analytical processes of solution for zeros and integration to be performed. The command takes the form 'Solve A', where A is the program label which heads the function you wish solved. For instance, say you want to look for zeros of 'sinX + e^X'. This function is keyed in after the A label just as if you were evaluating it. Next you put in a point about which you wish to search for zeros, hit 'Solve A' and in a moment the result is returned. Similarly, integration occurs for the selected function between the limits set by the contents of the X and Y registers.

There is of course no special trickery in any of these four advanced functions. Newton's method is the basis of Solve, Simpson's of Integrate, while the Complex and Matrix functions are standard mathematical processes.

Why are those so powerful here? Firstly, these functions are always there. No need to use up RAM loading them and no need to carry them on cards or paper. Secondly, they are fast as they are ROM-based and machine code written. Much faster than you could implement them yourself. Thirdly, they are superbly integrated with the other functions in the machine. This brings us to the discussion of our earlier statement that the 15C is a superb piece of engineering.

Why, once you speak Reverse Polish, is it so easy to adapt to a new HP and why is it so quick to enter and solve a function? Fundamentally the HP-15C, like all previous HPs, but to a greater extent, has a degree of polish (not Polish) in its software and hardware

which is quite unequalled in other machines. All the keystroke combinations are sensible; all unambiguous commands are accepted and quite often you'll find that some facility you decided you might like is already there. This feeling stems from the fact that each machine in the HP lineup has been extensively used by people like yourself before release. So all the little annoyances have been removed and all the extra conveniences and keystroke economies have been incorporated.

Polishes up well

I will give some examples from HPs in general, and the 15C in particular. When you are adding up a string of numbers with the Sigma function with a view to getting mean and standard deviations, you may wish to see what the total is. You could look in the memory which, according to the book, the machine is using for the running total, but there is no need. By hitting Recall Sigma, using the recall key for ordinary memories and the Sigma key you are using for storing, the X and Y totals are placed in the X and Y registers immediately. This is only sensible, is it not? In the 15C there is a pseudo-random number generator. Such functions, of course, have seeds. I did not have to look up in the book how to get at the seed — can you guess? — of course, just hit Recall Random#. Store Random# also puts away a new seed, should you wish to regenerate a sequence. (That is very useful indeed!)

Another sensibility is the method HP use for coding keystrokes in a program. If you look at the program you have written and you see '24, 57', this means that this command is the one you get by pressing the key fourth along on the second row, followed by the key seventh along on the fifth row. Obvious, isn't it? When you wish to run through a program step by step, you can press the SST key. When you depress it, the display shows you the next line to be executed. When released, the instruction is then executed. Simple, informative and sensible.

There are certain Matrix Functions on the 15C which would be destructive to some data. If you are entering or inspecting a matrix, pressing the appropriate key will cause the element's identity to be displayed, and

releasing it executes the change. What if you press the key and — ERK! — it is the wrong element? Just hold the key down. After about three seconds the little beast figures out that you have probably made a boo boo and the word 'null' appears in place of the element descriptor. Now releasing the key leaves the value undisturbed... *phew!* A nice feature is the ability to see first a description of what is about to happen. Then once you realise what its effect will be it's nice to have the ability to recover from a destructive stroke.

Certain keys on the 15C are multifunctional, depending on what exactly you are doing at the time. For instance, the '=' key. When you are in the process of keying in a number like 27 988.63 and you hit a seven, instead of a six, the arrow key removes only the last digit. When you have computed a result or effectively terminated digit entry, the key clears the whole register. Still more clever, when you are in program mode, the key deletes the current line altogether from the program, shifting up all the following instructions to close the gap. So the delete key, if we may call it that, is convenient and sensible in that it 'knows' what you want to delete.

In certain keystroke combinations, particularly involving the indirect addressing facility, it seems that the prefix keys f and g might need to be pressed more than once, because the second function part of a multikey command is a super or subscripted mark on its key. Inevitably, these extra prefix keys are unnecessary. The keys of HPs, and the 15C in particular because of its relative density of functions, are laid out in a careful manner so as to allow the ambiguous key sequence to be separated by the calculator's operating system.


Hewlett-Packard have a reputation for excellence and 'friendliness' in their machines which will be solidly reinforced by the 15C. But now you have begun to think "this little beggar is going to be expensive!" Not so, really. The 15C sells for \$190, or thereabouts, without sales tax which, for what it does, is probably the best value calculator on the market. Consider the HP-41, which starts around the \$400 mark before peripherals. It is a much higher level machine, but because it does not have the advanced functions built in, it is not as fast or as convenient for tackling the short term problems encountered in the classroom and the laboratory. Anything the 15C can do the 41 can do also, but you will spend a lot longer fooling around getting there and will have more keystrokes in the execution, so it is, in our opinion, not as well suited for tasks below the level where mass storage is needed.

One further note concerning the 15C: It is, significantly, built in the USA, rather than Singapore or Taiwan or whatever. The reliability of HP calculators has always been very high, with the exception of the 30-series units which have established a reputation for being plagued with bad connection problems. It would seem that the return to assembly within the watchful eye of HP engineers is a move to guarantee that there will be a return to the high standard of reliability for which HP strive and which their original 35/45 calculators set. ●



National

A NEW WAVE IS ON THE HORIZON

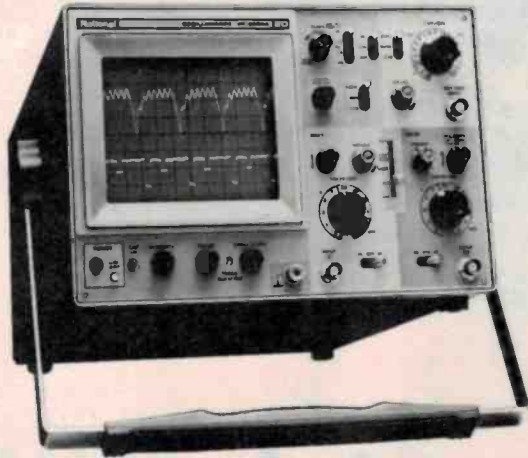

Available in four models these low cost oscilloscopes feature:

- 15-20-30 MHz.
- 1mV/Div sensitivity
- Stable automatic trigger 'AUTO FIX'
- Full range of triggering mode
- Bright and sharp CRT with Auto Fix
- TV(V) and TV(H) sync separator circuit
- Rectangular tube, illuminated internal graticule (VP-5220A and VP-5231A)
- Built-in delay line for observation of pulse transient (VP-5231A only)
- High reliability—MTBF 15,000 hours

National have a wide range of scopes—to 300 MHz. Please call or write for further information

...FROM \$399.00 (NOT INC. S.T.)


Probes supplied as standard accessory



SCIENTIFIC DEVICES AUSTRALIA PTY. LTD.
 2 JACKS ROAD, SOUTH OAKLEIGH, VICTORIA, 3167.
 TELEPHONE: 579 3622
 P.O. BOX 63, SOUTH OAKLEIGH, VICTORIA, 3167. TELEX: AA32742
 CABLES: DEVICES MELBOURNE
 31 HALSEY ROAD, ELIZABETH EAST, S.A., 5112.
 TELEPHONE: (08) 255 6575
 35-37 HUME STREET, CROWS NEST, N.S.W., 2065.
 TELEPHONE: (02) 43 5015

AUSTRALIAN AMP

LOW-PROFILE DIP SOCKETS

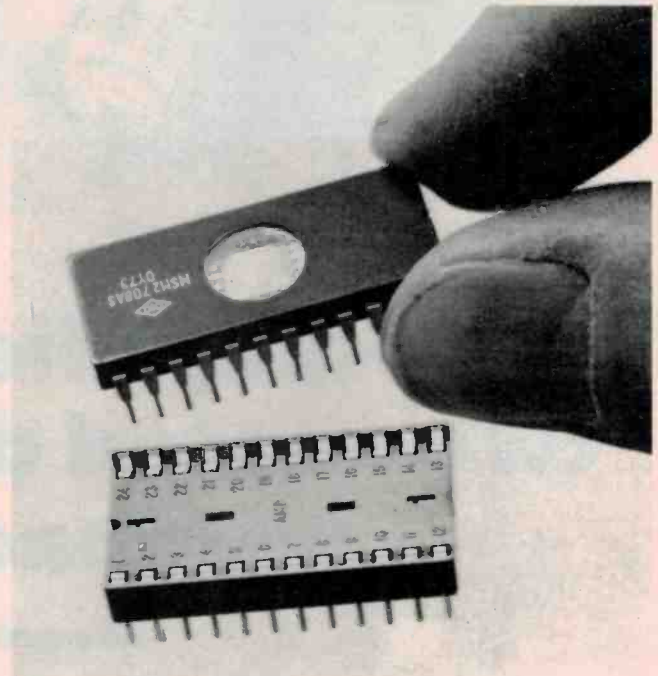

DIPLOMATE

Features

- Low Profile
- Dual wiping contacts
- Large target area, with tapered lead-in ramps
- Designed for automatic machine insertion—
- Tin or gold plated phosphor bronze or beryllium copper contacts
- Closed bottom
- Visual polarization
- Designed to meet EIA RS-415
- Stackable end-to-end and side-to-side for high board density.

Technical information available on request.

SOANAR

Soanar Electronics Pty Ltd

30-32 Lexton Road, Box Hill, Vic., 3128, Australia.

VICTORIA: 840 1222


QUEENSLAND: 52 1131

N.S.W. 789 6733

WEST. AUST. 381 9522

STH. AUST. 42 8918

TASMANIA: 31 6533

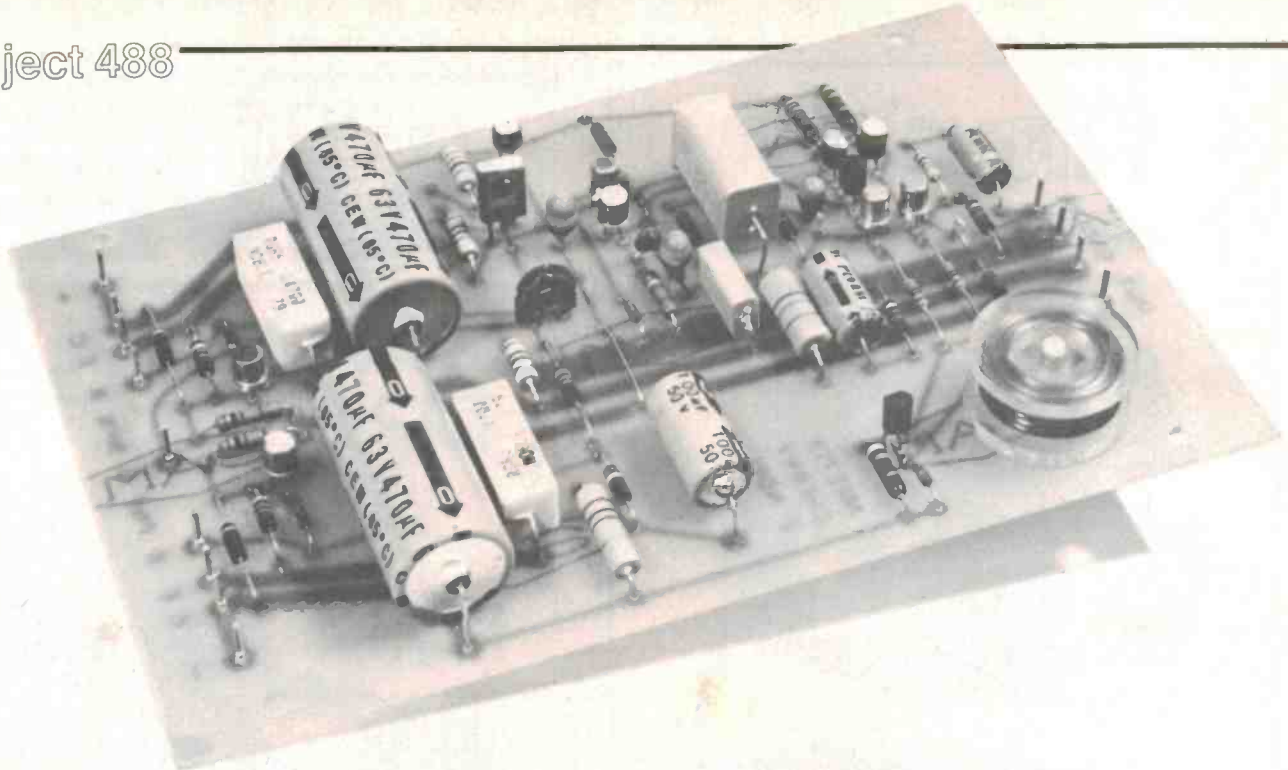

60 W amplifier module with two nested differentiating feedback loops

Edward M. Cherry

Associate Professor, Department of Electrical Engineering, Monash University

This is the third, and concluding, part of Professor Cherry's series on Audio Amplifiers Using Nested Differentiating Feedback Loops. Here is a practical amplifier design, presented as a module, that can be incorporated into a new system or used to replace power amp modules in an existing system. As the feedback technique promises, distortion is very low.

THIS AMPLIFIER will perhaps be of most interest to home constructors who want to re-build an existing system and upgrade its performance without the expense of new major components. The power output transistors employed are the well-known types MJ802 and MJ4502 which have been around for several years and have proved their reliability. Indeed, the whole design is mature and home constructors should have no difficulty in making it work. Total harmonic distortion in this amplifier is only a few parts per million at low outputs at 1 kHz — stacks better than some well-known marks of class-A amplifiers!

The two previous parts of this series appeared in the October and November 1982 issues of ETI.

Circuit description

Figure 15 is the complete circuit of one channel of the amplifier. The circuit is clearly based on Figure 10 (November '82 ETI), with major parameters

$$\begin{aligned} 1/\beta &= 32.9 \\ \tau_x &= 800 \text{ ns} \end{aligned}$$

The value of β is set by the overall feedback resistors R11 and R12 (470R and 15k — see Equation 1, Oct. '82). τ_x is set by:

- a) R4 and R5 (330R) plus C6 and C8 (68p) in conjunction with the chosen value of β (see Equation 13, Nov. '82);
- b) R15 and C7 (1k8 and 470p — see Equation 14, Nov. '82);
- c) R33 and C14 (8R2 and 100n) plus the 8 ohm nominal load and L3 (6u8 H);

- d) R12 and C4 (15k and 33p) via the other constants in Equation 15 (Nov. '82).

The first stage requires little comment. Q1 and Q2 operate at 1.5 mA each, Q3 is a current source, Q4 is a common-base stage to equalise the quiescent voltages on Q1 and Q2; Q5 and Q6 constitute a current mirror. R1 and C2 form a 200 kHz low-pass filter against RF interference.

The Rush current amplifier operates at 3 mA, set by R18, and it incorporates a catching diode (D1) to accelerate recovery from overdrive. Almost any small-signal diode would do — 1S44, 1N914, etc.

Q1 and Q2 should be high gain, low noise types: BC109 and BC549 are among the cheapest available. The others could be almost any small-signal types: BC107 and

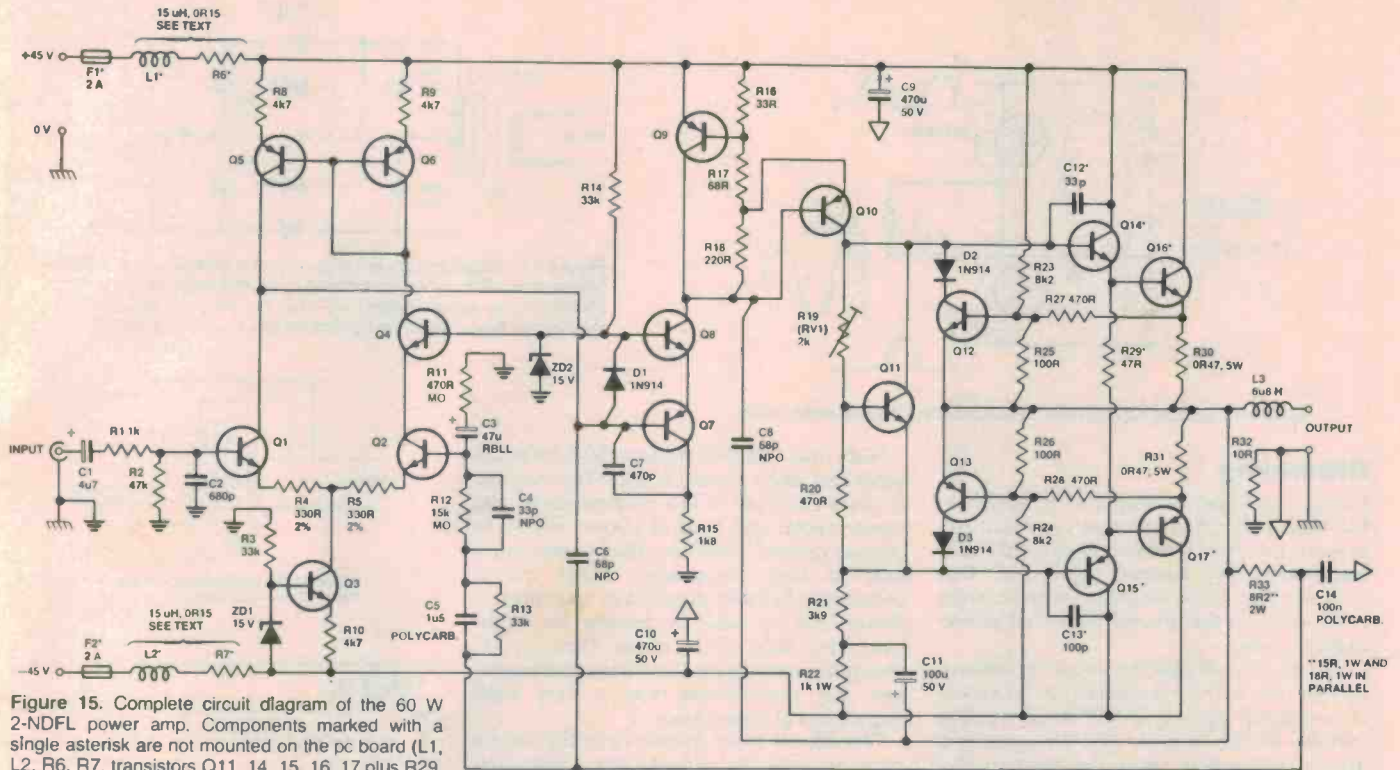


Figure 15. Complete circuit diagram of the 60 W 2-NDFL power amp. Components marked with a single asterisk are not mounted on the pc board (L1, L2, R6, R7, transistors Q11, 14, 15, 16, 17 plus R29, C12 and C13 — see Figure 20).

BC547 are readily available npn types, the BC177 and BC557 are suitable pnps.

The pre-driver, Q10, operates at 8 mA, and should be the preferred type BD140. Q9 protects the stage against damagingly large currents under fault conditions.

The driver and output transistors should be the types shown: BD139 and BD140 for the drivers, MJ802 and MJ4502 for the power transistors. Driver quiescent current is 25 mA, set by R29. The biasing transistor, Q11, could be any npn in a TO-126 pack that can be mounted on the heatsink; types BD135 and BD139 are readily available types that would suit. Quiescent current in the power transistors should be set to 40-60 mA by R19. *Be warned* that this quiescent current is almost zero until R19 is about three-quarters of its maximum resistance, after which the current increases very rapidly; be sure that R19 is set to *minimum resistance* when the amplifier is turned on for the first time.

A convenient way to check the quiescent current is by means of the voltage drop across R30 and R31; this should be 40-60 mV (total) for zero signal input to the amplifier.

Transistors Q12 and Q13 provide short-term protection for the power transistors. Short-circuit current is limited to about 4 A, and peak signal current is limited to 7 A. Long-term protection is provided by 2 A fuses in each supply rail; these should be 'ordinary' types, rather than delay or quick-blow. In the unlikely event of transistor failure, these fuses limit the loudspeaker current to 2 A, corresponding to 32 W into 8 ohms.

The common alternative of a single fuse in the loudspeaker lead is less satisfactory: it provides less protection for the amplifier; it provides less protection for the loudspeaker

as the fuse must be rated to carry the full signal current, and it introduces distortion on large-amplitude, low-frequency signals.

Critical components

The majority of components in the amplifier are not at all critical. As already stated, almost any small-signal transistors and diodes can be used. Unless the contrary is indicated on the circuit, resistors can be standard 1/2 W types and capacitors can be the lowest available working voltage. A few components, however, do require special mention.

A feedback amplifier cannot be more linear than its feedback network, so the various components that constitute the feedback network should have small voltage coefficients. Specifically:

- Overall feedback resistors R11 and R12 should be high-stability types, such as metal oxide or metal film;
- C6 and C8 should be NPO ceramics, not hi-K types;
- C5 and C14 should be polycarbonate, polystyrene or polypropylene types, but not polyester (for example mylar 'greencaps');
- C3 should be an ordinary cheap aluminium electrolytic, definitely *not* one of the relatively expensive resin-dipped tantalum types (this is not a misprint!).

The 6u8 H inductor (L3) needs to be home-made. Winding data are given in the accompanying table, Table 1.

The bobbin should be mounted on the circuit board with a nylon screw; brass or steel must not be used, because of nonlinear eddy-current losses.

HARMONIC ANALYSIS AT 1 kHz

harmonic	rated output	
	21.9 V 60 W	-20 dB 2.19 V 0.6 W
2nd	19 ppm	5 ppm
3rd	14	3.5
4th	2.5	2.5
5th	3.0	1.5
6th	<1	<1
7th	1.8	1.8
8th	<1	<1
9th	1.0	<1
10th	1.8	<1

Notice how the harmonics drop away at small signal amplitude. In this regard a class-B NDFL amplifier is more like a conventional class-A amplifier than a class-B amplifier.

1 ppm = 0.0001%

HARMONIC ANALYSIS AT 6 kHz

harmonic	rated output	
	21.9 V 60 W	-20 dB 2.19 V 0.6 W
2nd	115 ppm	40 ppm
3rd	100	25
4th	32	15
5th	40	9

Harmonics higher than the 3rd are ultrasonic and hence inaudible.

TABLE 1.

Winding details, L3.

Former

Turned from 25 mm diameter polystyrene rod to give 12 mm internal bobbin diameter with 7.5 mm winding space between cheeks.

Wire & winding

Take a 1190 mm length of 1.25 mm diameter enamelled copper wire and wind it onto the former. Leave 20 mm or so lead length at start and finish.

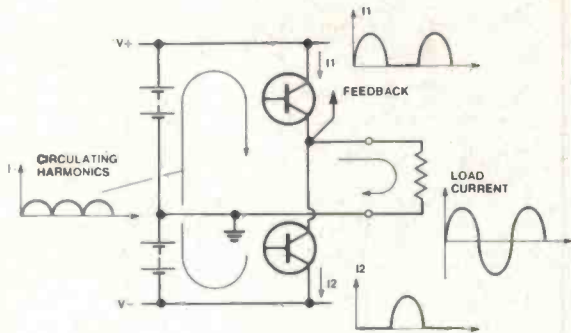


Figure 16. Circulating even-harmonic current in a class-B output stage.

Grounding

In any amplifier where the basic distortion has been reduced to a few parts per million, several distortion mechanisms not ordinarily considered may become significant. One such mechanism is associated with currents circulating in the ground leads and power-supply wiring.

Figure 16 explains the origin of this distortion. The current in each power transistor of a class-B stage is a half-wave rectified version of the output. The two currents, drawn alternately from the positive and negative supplies, are equivalent to a circulating full-wave rectified current and this is basically an even-harmonic distortion of the signal output. If there is any mutual inductance between the power-supply wiring (including the grounds) and the signal wiring (also including the grounds), then an even-harmonic distortion is induced in the amplifier and feedback is powerless to correct it.

The circuit board has been laid out so as to minimise this effect. The areas enclosed by some tracks are critical, and home constructors making their own pc boards are cautioned to follow the layout exactly; you can obtain artwork from ETI (see page 64) or, better still, purchase a ready made board.

Note that the circuit uses three distinct ground symbols:

- a) is the *quiet ground track* on the circuit board (one per channel).
- b) is the *noisy ground track* on the circuit board (one per channel).
- c) is the metal chassis ground (there are six connections to the chassis in total).

Each channel is connected to chassis ground at two points. The input socket is connected to the chassis (rather than insulated from it), the input lead from socket to circuit board is screened, and the quiet ground track is connected to chassis ground at the input socket via the screen. Similarly, the neutral output terminal is screwed into the chassis, the leads from the circuit board to the output terminals are a twisted pair and the noisy ground track is connected to chassis ground at the output terminals via the neutral output lead. The remaining two connections to chassis are in the power supply (Figure 17).

Note that a 10 ohm resistor, R32, links the quiet and noisy ground tracks. This resistor is short circuited at low frequencies by the input screen and neutral output wiring to chassis ground. However, the resistor takes over at high frequencies where wiring inductance becomes significant. (A capacitor should not be used to provide the high-frequency link, as it would form an LC resonant circuit with the wiring inductance and the combination has a very high impedance at resonance.)

The 15 μ H filter inductors in the supply rails are also for suppressing circulating currents (R6 and R7 represent the winding resistances of L1 and L2).

This amplifier employs only two nested differentiating feedback loops and its distortion is not down to the ultimate limit. The benefit of including the filter inductors is therefore marginal. The author is not blessed with 'golden ears' and cannot hear the effect of removing the filters, although the difference is clearly measurable. The filters should certainly be included in amplifiers that use three or more NDFLs. As the inductors must be home made, and therefore cost nothing but time, and as they do make a measurable (if small) improvement, most home constructors will probably wish to include them. Winding data are given in Table 2.

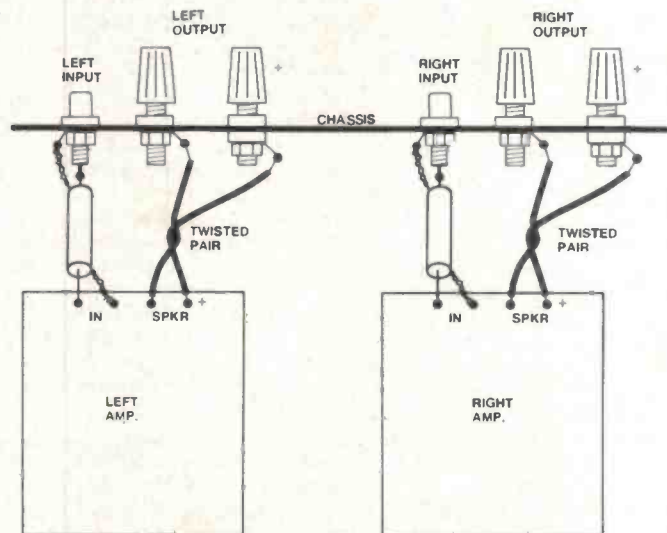


Figure 17. Suggested power supply for the amplifier. The transformer specified is not a common type, but using a Ferguson PF4361/1 as shown below will give the required result. This transformer has a 'flux shorting' strap to give a low external field.

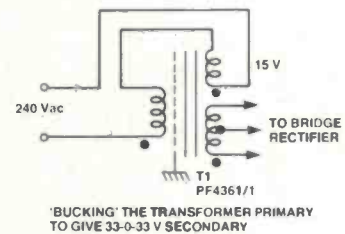


TABLE 2.

Winding details, L1, L2.

Former

Turned from 20 mm diameter polystyrene rod to give 12 mm internal bobbin diameter with 7.5 mm winding space between cheeks. Two are needed.

Wire & winding

Take two 1680 mm lengths of 0.75 mm diameter enamelled copper wire and wind onto each former leaving 20 mm or so lead length at start and finish.

The precise values of inductance and resistance are not important — $\pm 50\%$ is good enough — but do not use the 1.25 mm wire from L3 as something like 0.1 ohm series resistance is essential. For a similar reason, do not parallel the 470 μ F bypass capacitors C9 and C10 with high-frequency types. Brass or steel mounting screws are perfectly satisfactory for the filter inductors, as linearity is not important.

The right connections. Showing the general technique of connecting inputs, outputs and grounds to a stereo pair of ETI-488 modules.



SERIES 5000

As designed by ETI

PREAMPLIFIER



SPECIFICATIONS

Frequency response: High-level input: 15Hz-130 kHz, +0, -1 dB Low-level input — conforms to RIAA equalisation, ± 0.2 dB

Distortion: 1kHz < 0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation).

S/N noise: High-level input, master full, with respect to 300 mV input signal at full output (1.2V): >92 dB flat >100 dB A-weighted.
MM input, master full, with respect to full output (1.2V) at 5 mV input, 50 ohm source resistance connected: >86 dB flat >92 dB A-weighted.
MC input, master full, with respect to full output (1.2V) and 200 μ V input signal: >71 dB flat >75 dB A-weighted.

POWER AMPLIFIER



Please note that the "Superb Quality" Heatsink for the power amp was designed and developed by Rod Irving Electronics and is being supplied to other kit suppliers. This product cost \$1,200 to develop so that your amplifier kit would have a professional finish as well as sound. We also have a new range of rack mounting boxes which will be released soon.

SPECIFICATIONS

Power output: 100W RMS into 8 ohms (± 55 V supply).

Frequency response: 8 Hz to 20 kHz, +0 -0.4 dB 2.8-Hz to 65 kHz, +0 -3 dB. NOTE: These figures are determined solely by passive filters.

Input sensitivity: 1V RMS for 100W output.

Hum: -100dB below full output (flat).

Noise: -116 dB below full output (flat, 20 kHz bandwidth).


2nd harmonic distortion: <0.001% at 1 kHz (0.0007% on prototypes) at 100 W output using a ± 56 V supply rated at 4 A continuous. <0.003% at 10 kHz and 100 W.

3rd harmonic distortion: <0.0003% for all frequencies less than 10 kHz and all powers below clipping.

Total harmonic distortion: Determined by 2nd harmonic distortion (see above).

Intermodulation distortion: <0.003% at 100 W. (50 Hz and 7 kHz mixed 4:1).

Stability: Unconditional

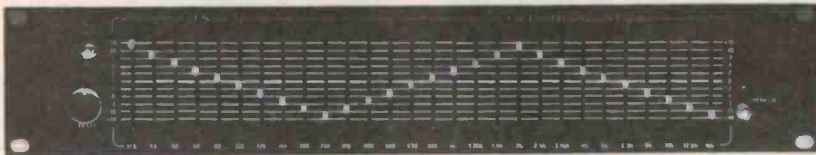

THIRD-OCTAVE GRAPHIC EQUALISER

SPECIFICATIONS

Bands: 28 Bands from 31.5 Hz to 16 kHz

Noise: <0.008 mV, sliders at 0, gain at 0 (-102 dB),

20 kHz bandwidth

Distortion: 0.007% at 300 mV signal, sliders at 0, gain at 0; max. 0.01%, sliders at minimum.

Frequency Response: 12 Hz-105 kHz, +0, -1 dB, all controls flat.

Boost & Cut: 14 dB

1 UNIT \$189
2 UNITS \$359

EXTRA FEATURES OF OUR KITS POWER AMPLIFIER

KIT PRICE \$299 P&P \$8.00

- 1% Metal Film Resistors are used where possible
- Prewound Coils are supplied
- Aluminium case as per the original article
- All components are top quality
- Over 200 Kits now sold
- We have built this unit and so know what needs to go into every kit.
- SUPER FINISH Front panel supplied with every kit at no extra cost to you
- We are so confident of this kit that we can now offer it assembled and tested so that people who do not have the time can appreciate the sound that this amplifier puts out. This is done on a per order basis delivery approx. two weeks after placement.

only \$425

*All parts available separately for both kits.

PREAMPLIFIER

KIT PRICE \$259 P&P \$8.00

- 1% Metal Film Resistors are supplied
- 14 metres of Low Capacitance Shielded are supplied (a bit extra in case of mistakes)
- English "Lorlin" Switches are supplied no substitutes as others supply
- We have built and tested this unit and so know what needs to go into every kit
- Specially imported black anodised aluminium knobs
- Again as with the power amp we are offering this kit A.B.T. at a price which we do not believe there is a commercial unit available that sounds as good. Same delivery as the P.A.

only \$425

ROD IRVING ELECTRONICS

425 HIGH STREET NORTHCOTE 3070 MELBOURNE (03) 489-8131

Low-frequency compensation

A feature of Figure 15 not discussed so far is a low-frequency compensating circuit, R13 and C5.

Amplifiers of the basic circuit topology of Figure 2 (Oct. '82) have a group delay which is different for different signal frequencies. Some frequencies take longer or shorter times than others to pass through the amplifier. High-frequency group delay in NDFL amplifiers can be corrected as described in the last part (Nov. '82), by a small capacitor in the feedback network (see Equation 15). Errors in low-frequency group delay, in both Figures 2 and 10 (Oct. and Nov. '82), are associated with the input coupling capacitor and the capacitor in series with R_{F1} . Low-frequency square-wave inputs are reproduced with a 'tilt' as in Figure 18(a).

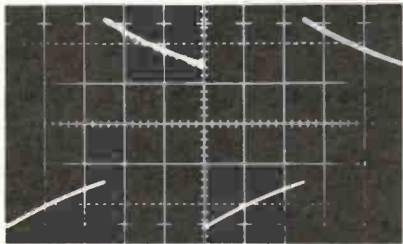


Figure 18a. Square wave response of the amplifier without group-delay compensation.

One approach to this problem is to use a truly direct-coupled amplifier, with no capacitors in series with the signal path; commercial audio power amplifiers of this type appeared in the 1970s. Unfortunately, such amplifiers are prone to drift. A significant dc voltage may appear at the output even when there is no input. Although it is possible to reduce drift in a power amplifier to an acceptable level, it is not possible with today's technology to build a system that is truly direct-coupled from pick-up input, through the RIAA network and the power amplifier.

In the last few years a generation of amplifiers has appeared which include some form of servo amplifier to correct the drift. All circuits known to the author re-introduce the problem of group delay, albeit in a lesser form.

The approach adopted in this design is to retain the coupling capacitors and thereby eliminate drift, but include a group-delay correcting circuit. Figure 19 shows the outline. Group delay is optimally compensated if:

$$R_{F3} = 2 R_{F2} \quad (16)$$

$$R_{F2} C_{F2} = R_{F1} C_{F1} \quad (17)$$

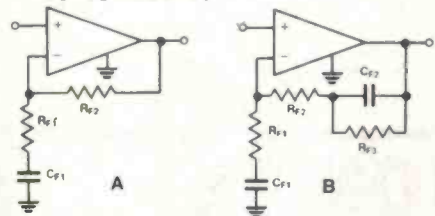


Figure 19. Circuit for compensating low frequency group delay: (a) basic uncompensated circuit; (b) compensated circuit.


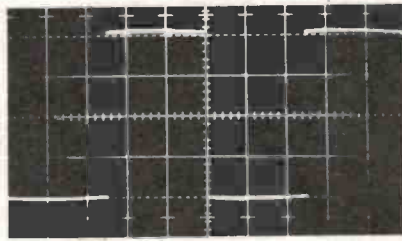


Figure 18b. Square wave response of the amplifier with group-delay compensation — note the improvement over Figure 18a.

Figure 18(b) shows the improvement in square-wave response.

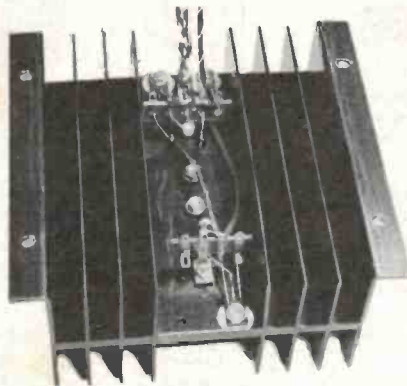Low-frequency group-delay compensation could well be included in audio power amplifiers and preamplifiers other than NDFL types.



Heatsink. Showing components mounted on the heatsink.

Construction

Assembly of the printed circuit board is quite straightforward. It is probably best to commence by soldering all the resistors in place. Note that R33 could be either a 2 W type (not common) or two 1 W resistors (15R and 18R) in parallel. Note that Noble brand resistors have been used for the emitter ballast resistors of Q16 and Q17 (R30 and R31). These have very low inductance and other types may be used and work successfully, but if you have trouble with high frequency instability, these resistors are likely to be the culprit. Mount R30 and R31 a few millimetres above the board. There are several other things to note about the resistors. R4 and R5 should be 1% or 2% tolerance and R11 and R12 should be either metal oxide or metal film types, as mentioned earlier.

Assemble the diodes next, making sure you get them all the right way round. Install the links next. Follow with the capacitors. Note that C5 and C14 must be polycarbonate types and C4, 6 and 8 must be NPO ceramics. None of the other ceramic capacitors should be hi-K types, as mentioned earlier. When mounting C9 and C11, see that there is three or four millimetres between the capacitor body and the adjacent 5 W resistors (R30 and R31) to allow for convection around the latter.

The transistors may be mounted now. See that each is oriented correctly. Wind L3 next and mount it on the board. Details are given in Table 1. It is not necessary to strictly follow the former dimensions given, but the inductance needs to be close to 6u8 H and wound from 1.25 mm wire at least, for low resistance.

To terminate connections leading to and from the board, pc stakes were used, as can be seen in the photograph.

Assembly of the components mounted to the heatsink comes next. The heatsinks in the original were 5" (127 mm) lengths of blackened Philips #56230, each having a thermal resistance to ambient of about 1°C/W at 50°C. Other types could of course be substituted. The specified thermal resistance permits continuous operation at full power. Smaller heatsinks (up to 2°C/W) could be substituted if the amplifier is to be used only for domestic sound reproduction. A 225 mm length of single-sided radial-fin type heat-sink (e.g. D.S.E. No. H-3426 or Electronic Agencies H-2429 would suit). Other suitable similar types are Rod Irving's HS3, which is only 150mm long or a 150 mm length of

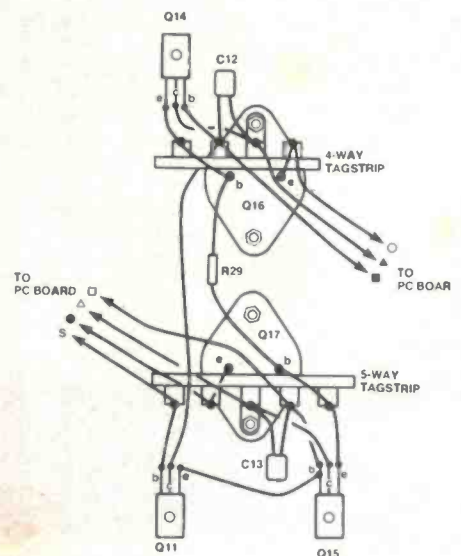


Figure 20. Wiring diagram for the components mounted on the heatsink.

PATENT PROTECTION

The principle of nested differentiating feedback loops, on which this amplifier depends, is patented in Australia and principal overseas countries.

Commercial enquiries should, in the first instance, be directed to the Legal Office, Monash University, Clayton Vic. 3168. Australian manufacturers can expect very favourable licencing terms.

PARTS LIST — ETI-488

Resistors all 5%, 1/2W unless noted

R1 1k
 R2 47k
 R3, 13, 14 33k
 R4, R5 330R, 2%
 R6, R7 see text
 R8, 9, 10 4k7
 R11 470R, MO or MF*
 R12 15k, MO or MF*
 R15 1k8
 R16 33R
 R17 68R
 R18 220R
 R19 (RV1) 2k min. vert. mount
 trimpot.
 R20, 27, 28 470R
 R21 3k9
 R22 1k, 1 W
 R23, R24 8k2
 R25, R26 100R
 R29 47R
 R30, R31 0R47, 5 W
 R32 10R
 R33 8R2, 2 W or 15R and 18R,
 each 1 W

Capacitors

C1 4u7, axial electro.
 C2 680p ceramic
 C3 47u axial electro.
 C4 33p 100 V NPO ceramic
 C5 1u5 polycarbonate
 C6, C8 68p 100 V NPO ceramic
 C7 470p ceramic
 C9, C10 470u/50 V axial electro.
 C11 100u/50 V axial electro.
 C12, C13 33p 100 V ceramic
 C14 100n/100 V polycarbonate

Inductors

L1, L2 15 uH (see text and
 Table 1)
 L3 6u8 H (see Table 2)

Semiconductors

D1, 2, 3 1S44, 1N914, 1N4148 etc
 Q1, Q2 BC109, BC549 etc
 Q3, 4, 8, 12 BC107, BC547 etc
 Q5, 6, 7, 9, 13 BC177, BC557 etc
 Q11, Q14 BD139
 Q10, Q15 BD140
 Q16 MJ802
 Q17 MJ4502
 ZD1, ZD2 15 V zener


Miscellaneous

F1, F2 2 A standard fuse

ETI-488 pc board; one 4-way and one 5-way tagstrip; heatsink to suit (see text); pc stakes; bobbins for inductors, wire, etc.

* metal oxide or metal film.

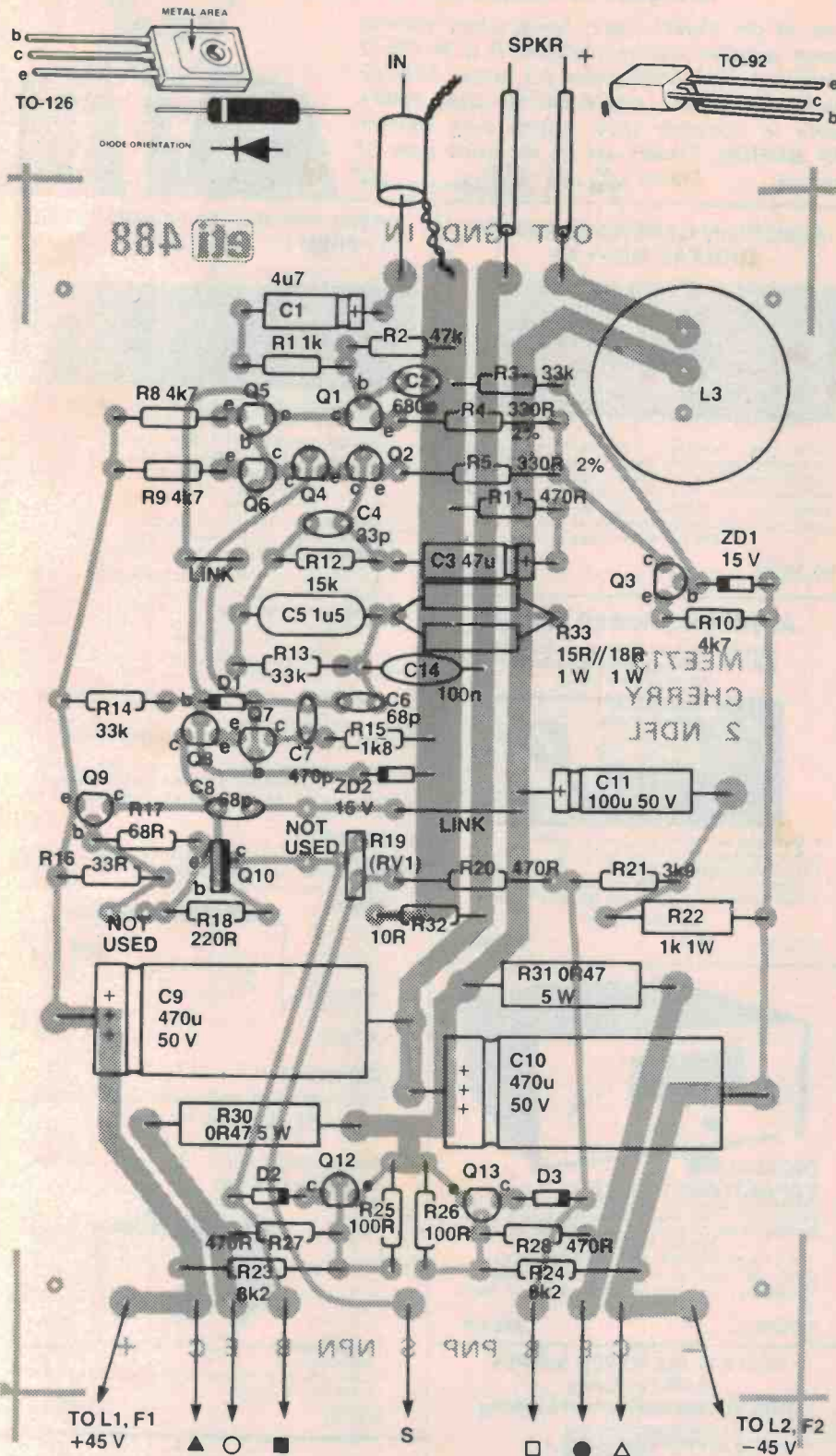Price estimate \$30 — \$35
 (less heatsink)



Autotron 'XA' type heatsink. Use one heat-sink per channel.

Three small components are mounted on the heatsink adjacent to the transistors to keep certain leads short: R29, C12 and C13. Construction is very much simplified if a 4-way tagstrip is installed under one of the collector mounting bolts of Q16 and a 5-way strip under one of Q17's mounting bolts.

Figure 20 shows details.

The collector and emitter leads from each power transistor to the circuit board should be twisted. The base leads to Q14 and Q15 could be twisted in with the corresponding collector and emitter leads (although this is not necessary) and the base lead of Q11 can be kept separate. Note that all transistors must be insulated from the heatsink.

The pc board is a Monash University 'universal' type for NDFL power amplifiers and there is provision on it for two components not used in the present amplifier (both near Q10). Note also that the BD140 specified for Q10 needs its leads dressed to fit the board — the collector and emitter leads should be bent about 0.1" sideways (see the overlay).

I'M BUILDING *have built* THE FIRST TWO

— what am I raving about? Well, having one of the World's finest home stereo systems (the brilliant ETI 5000 series amp and preamp together with my beloved B & W DM II loudspeakers of course!), I couldn't resist building ETI's 5000 series 1/3 octave Graphic Equalizers. I have been pestering ETI for well over a year — and at last the many 1000's of 5000 series owners have the opportunity to complete their system with another classic, no compromise DAVID TILBROOK DESIGN. Details are on the other page of this ad. Cheers *Jack O'Donnell*



DIGITAL FREQUENCY METER

See Electronics Aust. Mag. Dec. 81-Feb. '82
500 MHZ, 7 DIGIT RESOLUTION PLUS PERIOD MEASUREMENT FEATURE



IMPORTANT NOTES:
(1) This project is well within the scope of the "not so experienced" as virtually all components are contained on a single PCB.
(2) ALTRONICS USE ONLY THE SPECIFIED INTERSCIL LSI — BEWARE OF INFERIOR KITS THAT DO NOT CONFORM TO THE ORIGINAL DESIGN.

- * Screened front panel
- * Bright high efficiency 7 segment display
- * Frequency ranges 0-10MHz, 0-50MHz, 10-50MHz (with optional pre-scaler)
- * 4 gating times — 0.1, 1, 10 seconds
- * 4 period measuring ranges 1, 10, 100 and 1000 input cycles give 0.1µs resolution.
- * High input sensitivity — 10mV to 30MHz, 100mV at 50MHz @ 1M input impedance, 200mV at 500MHz @ 75 ohms input impedance.
- * High accuracy — typically better than .005% count uncalibrated.

Costs a fraction of commercial counters.
EXCLUSIVE ALTRONICS KIT FEATURES:

- * IC sockets provided throughout.
- * Low aging 10,000 MHZ XTAL.
- * Thermalloy heatsink for 5V regulator.
- * Quality Pactec Instrument Case

K 2500 (50 MHZ version) \$119.50
K 2501 Pre-scaler \$ 26.00
(add for 500 MHZ version)

FUNCTION GENERATOR WITH DIGITAL DISPLAY



EA's new Function Generator covers the frequency range from 15Hz to 170kHz in three ranges with coarse and fine frequency controls. An economical 4-digit display has been incorporated to eliminate dial calibration. Sine wave distortion can be trimmed to around 0.5%.
See EA April, 1982

K 2505 \$85.00

ALTRONICS POWER SUPPLY

BASED ON EA LM 317K PROJECT
Every workshop, school and hobbyist should get one now!



- * Overload and short circuit protected.
- * Full voltage and current metering.
- * 3.32 volt output at 1 AMP.
- * Uses LM 317K variable regulator.
- * Full instructions and every last part included.

VALUE PLUS!

K 3200 \$39.95



DIGITAL CAPACITANCE METER

Electronics Australia Project. Measures 1PF — 99.99 UF. 240V Mains Powered. Bright LED Display. Easy to build. Complete kit of parts and full instructions.

*** EXCLUSIVE TO ALTRONICS ***
Each kit now includes precision measured capacitors for accurate calibration of each range.

K 2520 \$45.00

NEW ETI 162 POWER SUPPLY

0-30V at 1 amp
With Voltage and Current Limiting



- * Overload and Short Circuit Protected.
- * Full Voltage and Current Metering.
- * Fully variable voltage and adjustable current limiting.

Exclusive — Fully S.E.C. Certified Mains Transformer supplied.

If you're considering buying this kit from your local supplier or one of our competitors — first ring and ask them if the mains transformer is S.E.C. certified to ASC126 — chances are that it won't be.
So why not give us your order? An Altronics Quality Kit speaks for itself and with our overnight JetService we guarantee to deliver to your door faster than your local supplier.

K3205 \$49.50

GREAT NEW MOSFET PA AMPLIFIER KIT FROM ETI

150 watts power output.

See June '82



UNCONDITIONALLY STABLE SOUND STUDIO SPECIFICATIONS

OUTPUT IMPEDANCE Selectable to low Z voice coil or 100V or 70V line out.
INPUTS 2 mic inputs HI or low Z with speech filter.
1 Aux. Input.

- * Low noise 5534 op amps used.
- * Noble W/wound power resistors used in output stage for guaranteed stability.

*** ALTRONICS EXCLUSIVE ***
All due respects to ETI, but we felt the original case was lousie — So we've brought out ours utilising our snazzy H 0400 Black Rack Cabinet.

It looks terrific!! And for this month only, it's the same price as the original version.
K 5035 ONLY \$239.00

GO ANYWHERE 240V PWR. KITS

See EA May and June 82. These great new inverter kits enable you to power 240V appliances for your car, caravan or boat. (From Standard 12V car battery.)

40 WATT

Suits small appliances, i.e. turntable, tape deck, shaver etc. Variable frequency adjustment enables accurate speed control of turntable motors.



IC Sockets Provided

K6700 \$55.00

300 WATT

Fully regulated and overload protected XTAL locked frequency.

Use to power hi-fi, TV sets and for emergency lighting.



- * Gold plating on both PCB edge and edge connector.
- * Low age rate parallel resonant XTAL used.
- * Sockets for all IC's.

K6750 \$199.50

ELECTRONIC FLOURO STARTER

See EA October 1982



Save a fortune on Fluoro Tubes

- * Extends the life of your fluoro tubes by 1,000's of hours.
- * Instant "ON" — no more flickering at switch on.

K3210 \$4.95

* THE EVER POPULAR * MUSICOLOUR IV EA PROJECT



Combination Colour Organ and Light Chaser. Four channel colour organ. Internal microphone or connect to speakers for colour organ operation. (The lights connected to each channel pulse in beat to the music proportional to portion of frequency spectrum concerned.) Four chaser modes forward and reverse. Output lamp load capacity a massive 2400 watts — that's 100 party globes. Full instructions and every last nut and bolt included. Great for parties, shop signs, display windows etc.
K 1004 \$89.50

HIGH FIDELITY AM

Sounds every bit as good as FM
With this absolutely brilliant
EA Project

Project 82 AR12 — See December EA



Frankly, we felt AM was dead and buried for the serious audio buff — when EA told us their new wide band AM tuner had 16KHz bandwidth and made AM sound like as never before — we were still not convinced. But on hearing the New EA AM Tuner, I for one was astonished — AM Broadcasts now sound incredible, there is no other word for it. And the 9KHz whistle filter really works! The result is clear smooth sound reproduction that will be a joy to every constructor on this fantastic tuner project.

The Altronics Kit includes rack box and every last nut and bolt — even solder. Full instructions included.

K5200 \$249.00

NEW! NEW! JAYCAR★

COOLING FANS 240VAC

Quality Ball Race construction, now you pay no more for quieter, much longer lasting and more efficient ball-bearing fans from Jaycar!

TWO POPULAR SIZES:
12 WATTS - 80x80x42(d)

\$24.95

13.5 WATTS - 119x119x25(d)

\$27.50



AT LAST!! INTERNATIONAL STANDARD (IEC 320) 240V APPLIANCE CONNECTOR

You asked for it and here it is. Fully approved 240V mains inlet to International Standard IEC 320.

- Front or rear panel mount
- 240V AC 6A rating
- Accepts IEC 320 International power cords
- Simplifies 240V wiring.
- Quick-connect/solder on terminals.


We also have the IEC 320 line plug assembly for ONLY \$4.95.

6,4 mm dia. Beware of non-approved units!



NEW! INSULATION DISPLACEMENT CONNECTORS & RIBBON CABLE!!

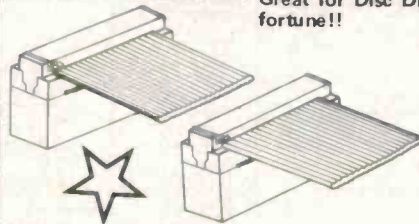I.D. Insulation displacement. The quick and reliable way of making multiple connections to computer peripheral connectors. Great for Disc Drives, Printers etc. Crimp them yourself and save a fortune!!



CONNECTORS;

- 16 pin DIP HEADER \$1.99
- 24 pin DIP HEADER \$2.50
- P.C. Edge Connector 34 way (Suits 5 1/4" Disc Drives) \$8.50
- 25 Pin Cannon 'D' Male \$8.95
- 25 Pin Cannon 'D' Female \$8.95

CABLE:

- 16 way \$1.50/metre
- 25 way (suit DB25's & 24 way DIP) \$2.50/metre
- 34 way for Disc Drives \$3.45/metre

low cost balanced mic transformer

Sensational price for a completely MU-metal shielded unit!!

Until now you had to pay a fortune for a shielded balanced tranny!

- 2-600 ohm (CT) input/output
- 50k output/input
- Can be used either way round
- Standard 9mm bushing mount
- Colour coded leads.

Don't pay over \$30!!!

17⁵⁰



MAGAZINE BINDER

Keep your precious (and expensive) magazines in order for easy reference. Smart blue colour with gold lettering. Heavy gauge and richly chromed metal fittings.

LOW IMPORT PRICE ONLY \$4.95
4 up \$4.50 each



LOW CAPACITANCE SCREENED CABLE

You asked for it! This is the same high-quality screened cable that we use in the 5000 Blueprint preamp. We have had dozens of requests from people who wish to upgrade their preamp etc. As we have said before it's not cheap. But it is good.

1-99m 99c/metre
100m+ 80c/metre

Capacitance is about half cheap screened cable.



EXPERIMENTER BREADBOARDS

Ample stocks of these boards plus the range has been extended.

- WBDN 100 holes \$2.95
- WBTN 640 holes \$9.45
- WB2N 840 holes \$13.95
- WB4N 1680 holes \$26.50
- WB6N 2420 holes \$39.95



Cannon XL connectors~great new range

5 pin and right angle types now in stock.

DESCRIPTION	PRICE
3 pin male line	\$3.50
3 pin female line	\$3.95
3 pin male chassis	\$3.25
3 pin female chassis	\$3.95
5 pin male line	\$6.95
5 pin female line	\$7.95
5 pin male chassis	\$3.95
5 pin female chassis	\$6.95
240V Mains line	\$6.50
240V mains chassis	\$5.25
3 pin male right angle line (Neutrik)	\$4.95
3 pin female right angle line	\$5.95
3 pin female line (Neutrik)	\$4.95
3 pin male line (Neutrik)	\$3.95

superbright LED

The average 15 cent LED has a light output of 0.8mCd (milli Candelas) at 20mA.

Can you imagine a 200mCd LED? (at 20mA)? Well if you can't - buy one and find out. They are ideal for panel illumination or very low current work. (They will still give useful light at 1mA!).

Red with clear lens - 69c each
10 up only 62c each. . . .

SUPER SPECIAL! URGENT

We have a quantity of 240 V Disco Strobes. Not a kit. Built in Woodgrain cabinet. 0-12 flashes per second. Brand new but re-worked warranty stock. Almost less than 1/3 normal price!

Only \$12.50 each

Were \$36.50

Now you can draw PCB patterns, component overlays, block diagrams etc., professionally with the "Linex" design template. Each template is precision die-cut & designed for use with a 0.5mm pen. The template has clearance pads to avoid smudging. Dozens of symbols are provided including:- *IC pads * Edge connectors (.1, .125, .15, .156 & .2") * TO-3 & TO-66 outlines * all TO-6 round IC's * Multiturn pots * TO-92, TO-22D etc * Most capacitors & resistors.

LINEX electronic lay-out

NEW

New! PCB Drafting aids from Denmark!!

2 sizes available

1:1 (same size art) \$18.95
2:1 (2x size art) \$29.95

Both complete with plastic protective wallet.

SEE OTHER JAYCAR ADS FOR ADDRESSES AND PHONE NUMBERS

Polyphonic organ features 'touch sensor' keyboard

Barry Wilkinson
Roger Harrison

Featuring a 'touch sensor' keyboard constructed right on the printed circuit board, this polyphonic organ project covers a two-octave range, has loudspeaker output plus two 'voices' and can be operated from a battery or plug pack.



BACK IN August 1976 we published the "ETI Mini Organ", Project 602. This featured a 'touch sensor' keyboard utilising tracks on the printed circuit board which, when bridged by a finger, turned on a CMOS switch. The switch turned on an RC oscillator and set the pitch of the note produced. The technique was novel and effective. An added tremolo circuit could also be switched in and out using the same technique. However, the technique had one drawback. Moisture from the fingers would sometimes build up on the keyboard and bridge the key tracks for one note or another, and the note would hold on. Wiping the keyboard with a tissue or cloth would solve that, but it proved an occasional problem nevertheless.

The ETI 602 Mini-Organ was only monophonic, that is, could only play one note at a time, a limitation that did not escape many readers and constructors. In defence, one might point out that the entire brass and woodwind family of traditional acoustic instruments are also monophonic, but an 'organ' is traditionally polyphonic, which means any number of notes in its compass can be played simultaneously. Hence, this project is a polyphonic organ.

Many notes

There are two basic ways to generate many notes that can be sounded simultaneously. You can commence with a 'master' oscillator at some suitably high frequency and have a series of frequency dividers that divide this

down stage by stage to produce the required range of notes. This has the advantage that only a single tuning control is required to set all the notes on frequency. That's fine and dandy, but the pitch interval between notes in the chromatic scale (i.e. the ratio of a note to the note above or below) is based on the twelfth root of two. This means that, to produce a scale based around middle C, at least, the lowest frequency you can start off with is around 2 MHz. A string of dividers constructed from discrete ICs would consist of many devices and be quite expensive. However, there is a device called a 'top octave synthesiser' which performs this task — but further dividers are required to produce the 'usual' range of notes. The drawback is the cost — the crystal and top octave synthesiser will set you back around \$30 to start with!

For cost reasons, we've chosen the second method. Twenty five oscillators have been used to generate each of the notes in a two octave-plus-one range from F below middle C to F" above middle C.

Each oscillator is implemented using a single two-input gate — and that includes the touch sensor keying! Hence all the oscillators require only seven quad-gate ICs — leaving two spare gates which have been used in the tremolo circuitry. This project uses even fewer ICs than the ETI-602 Mini Organ! In addition, Schmitt-input CMOS gates have been employed (4093s) as they have two distinct threshold points on the


inputs which means they can be driven on or off with certainty, unlike conventional CMOS gates, such as the 4011s used in the ETI-602 which have only one threshold point. Using this, the problem with moisture on the keyboard holding notes on has been largely overcome. The action of each oscillator and how they are keyed is explained in detail in the *How It Works* panel.

This project has tremolo circuitry and two 'voices', just like the ETI-602, but the circuitry has been arranged differently this time.

Loudspeaker output is provided by an LM380 audio power output amplifier IC. This is capable of driving 1 W into a four ohm load from a 9 V supply and for this reason we have specified the use of two small speakers. The common 50 — 75 mm diameter loudspeakers generally have an eight ohm voice coil. Connecting two in parallel gives a four ohm load and considerably more output. You can add a jack socket to take the organ's output to an external amplifier if you wish, in which case you'll get a much richer sound.

Construction

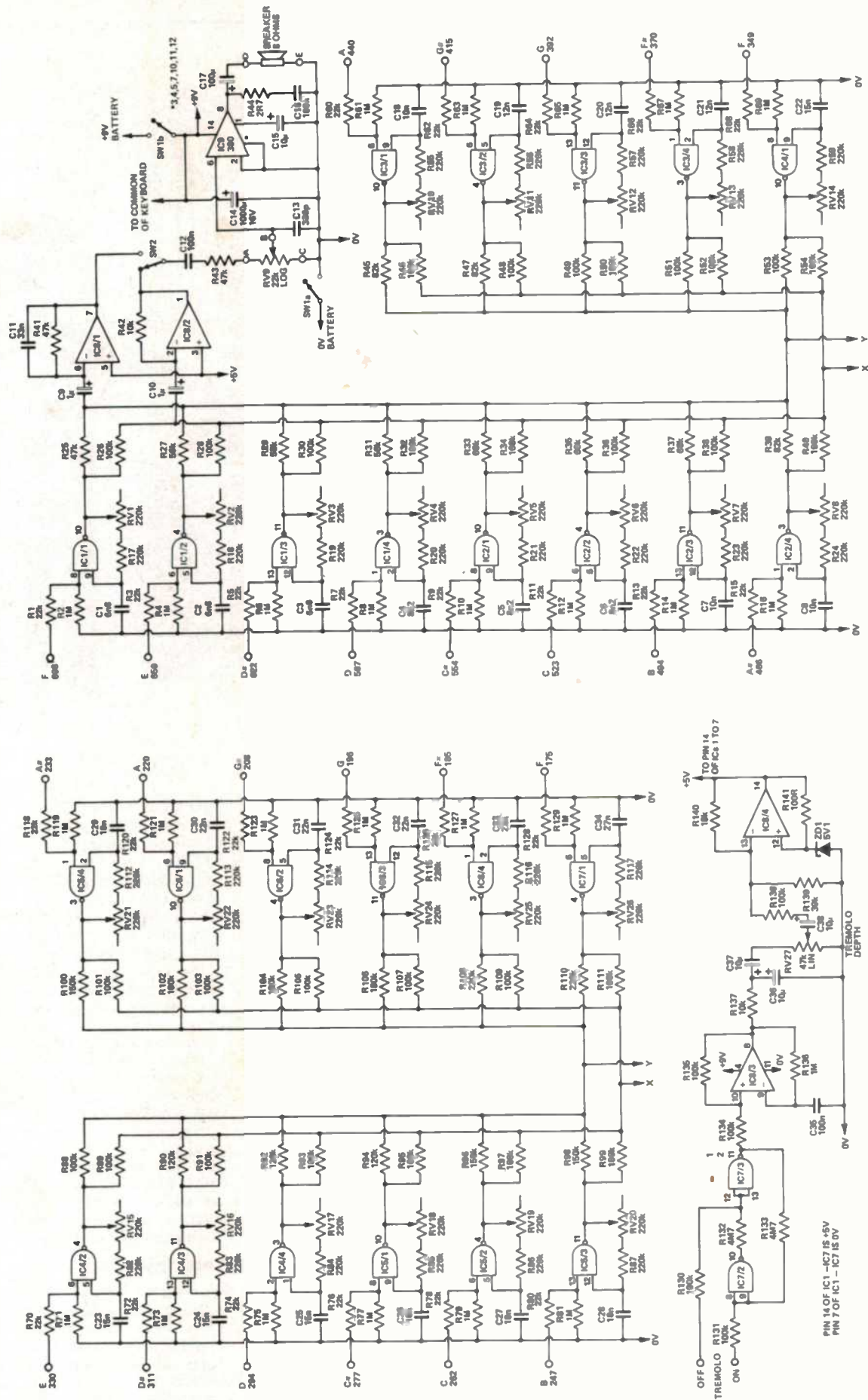For clearly obvious reasons, you'll get best results using our pc board design. However, if you intend making your own pc board, we should point out that tarnishing of the copper on the keyboard area can be a problem. We solved that on the prototype by coating it with solder. It's a fair solution, but not all that pretty! However, we have recom-



A total of 25 separate oscillators are used to provide polyphonic output covering two octaves. Each oscillator is individually adjustable so that they can be accurately tuned to the required note. Apart from the set of note oscillators, there are three other sections to the circuitry: the tremolo circuitry, the voice selection/mixing and the audio output stage.

THE NOTE OSCILLATORS

All the note oscillators have identical circuitry, only the frequency determining components are varied to provide the individual frequencies for the notes. The note oscillators are based on one gate from a 4093 CMOS two-input Schmitt trigger NAND gate. The basic circuit is shown in Figure 1.

The one gate combines both an oscillator and the keying action. What makes the gate oscillate is the feedback loop from the gate output to input 2 via the trimpot and resistor in series and involving the capacitor C.


A NAND gate is a digital IC and it operates according to certain 'rules', spelled out in a 'truth table'. Voltage levels on the gate's inputs or output are either 'high' or '1', which means they're at the positive supply voltage, or they're 'low' or '0', which means they are at the 0 V rail. With a two-input AND gate, the output will be high if input 1 AND input 2 are high, otherwise the output is low. Hence the name, AND. The NAND gate is a NOT AND gate which simply means that its output is inverted to that of the AND gate. Thus, if input 1 and input 2 are both high, the output will be low, not high. The truth table for a NAND gate is given in Table 1.

TABLE 1.

Input A	Input B	Output
'0' (low)	'0' (low)	'1' (high)
'1' (high)	'0' (low)	'1' (high)
'0' (low)	'1' (high)	'1' (high)
'1' (high)	'1' (high)	'0' (low)



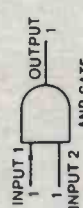INPUT 1(1) NOT AND INPUT 2(1) = OUTPUT (0)



INPUT 1(1) AND INPUT 2(1) = OUTPUT (1)

While we said that a '1' or high normally means the supply voltage and '0' or low the 0 V rail, the inputs of a NAND gate are generally

resistance of the trimpot RV, the frequency of the note oscillator can be varied. The circuit will oscillate so long as input 1 is held high by placing a finger on the key pad.

Note that each oscillator has been given a frequency variation range of 2:1 because of the values assigned to RV and R in each oscillator. The major frequency determining component in the actual circuit is thus the capacitor (C). Only standard value (E12 series) components have been specified so that components are easy to obtain and inexpensive as these are the most common values available.

VOICE SELECTION, MIXING

The output waveform of the oscillator described is a square wave, as you would no doubt have already realised. The output signals from each of the 25 oscillators are mixed together via a resistor network to the inputs of IC8/1 and IC8/2, two op-amps from an LM324 quad op-amp package. Apart from performing the mixing, this stage provides the 'voicing' as well. IC8/1 has a capacitor (C11) across the feedback resistor (R41) which changes the wave shape into a triangular form. This removes most of the harsh odd-order harmonics of the square wave, producing a 'sweeter' sound. As this type of circuit is frequency dependent, the mixing resistors from the oscillator output have different values so as to keep the amplitude constant across the frequency range. The desired voice is selected by switching between the outputs of IC8/1 and IC8/2 using SW2.

AUDIO OUTPUT STAGE

Final amplification of the signal, to drive a loudspeaker, is done by an LM380 IC power output amplifier (IC9). This can drive low impedance speakers and will deliver over one watt into a four ohm load. One or two miniature 8 ohm loudspeakers can be used for audio output. We used two 8 ohm speakers in parallel to give four ohms so that the LM380 will deliver maximum output. However, the output can be coupled to an external loudspeaker mounted in a proper enclosure (i.e. a hi-fi speaker), better sound being obtained in this way. The larger speakers are generally more efficient, which is opposite to what most people first think, and the LM380 generally clips when several notes are played together while driving the very inefficient miniature loudspeaker(s).

Capacitor C12 and resistor R43 provide some low frequency roll-off, reducing 'thump' when you touch a keypad. Volume control is

provided by RV9. C13 rolls off the high frequencies, reducing the harshness of the sound. The RC network across the speaker outputs from IC9 (R44-C16) helps stabilise the LM380 at high frequencies. C17 provides dc isolation for the speaker.

TREMOLO CIRCUITRY

This part of the circuitry involves two gates from IC7 and the remaining two op-amps from IC8. Tremolo is started and stopped by touching the appropriate key pads. IC7/2 and IC7/3 are arranged as a RESET/SET (R/S) flip-flop. If pins 12-13 of IC7/3 are high, pin 11 will be low and thus pin 8-9 will be low, pulled down via R133. This is the 'tremolo off' condition. If pins 8-9 of IC7/2 are pulled high by touching the ON key pad, pin 10 of IC7/2, which would have initially been high, will go low, as will pins 12-13 of IC7/3. Thus, pin 11 of IC7/3 will go high. This is the 'tremolo on' condition.

Now, IC8/3 is arranged as a low frequency oscillator. When pin 10 of IC8/3, the non-inverting input, is low, pin 8 is held low, and so will pin 9 because of the feedback via R136. C35 will be discharged. When pin 10 of IC8/3 is driven high, pin 8 will go high too and C35 will begin to charge via R136. The voltage on pin 9 of IC8/3, the inverting input, will begin to rise at a rate determined by the RC combination of C35-R136. As the voltage on pin 9 rises, the voltage on the output of IC8/3, pin 8, will begin to fall — and so will the voltage on pin 10, the non-inverting input, because of feedback via R135. At a certain level, the op-amp output will be rapidly driven low by the feedback action, C35 will discharge and the whole cycle will start again. Thus, IC8/3 oscillates. It will do so at a rate of about 10 Hz, determined by the component values chosen.

The output is filtered to more or less a triangular shape by the RC network of R137-C36. Capacitor C37 provides dc blocking, the output being applied to the tremolo depth control, RV27. The signal is applied to the inverting input of IC8/4 which is a dc amplifier. The output of this stage is set to an average of about 5V as the non-inverting input is 'clamped' at about 5V by the zener ZD1. When the modulating signal from the 10 Hz oscillator is applied to the inverting input of IC8/4, the output voltage will swing about a 5V mean, modulating the supply voltage to all the oscillators. The amplitude of the swing is determined by the tremolo depth control. Varying the supply voltage to the oscillators causes a small frequency variation, producing the tremolo effect.

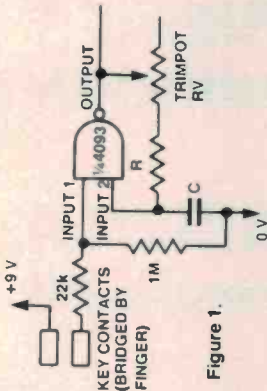



Figure 1.

specified to operate for voltages between these extremes. With a normal CMOS gate there is an input level threshold of about 50%. This means that if the input is at a level above 50% of the supply voltage it is high, if it is at less than 50% of the supply voltage it is low. The actual percentage (threshold) can vary from device to device (the limits are 30% to 70%). However, there is a point above which it is definitely high and a point below which it is definitely low. This is the 'normal' input characteristic of CMOS gates. They only have one threshold point.

With a gate having Schmitt inputs, there are two distinct thresholds: there is a low threshold which, if the input level is below that limit, the input is low and there is a high threshold which, if the input level is above that limit, the input is high. Between the two thresholds, the inputs do nothing. The low threshold may be at 40% of the supply rail, the high threshold at 60% of the supply rail.

Referring to Figure 1, in order for this circuit to oscillate, input 1 must be driven high. Initially, it will be held low by the 1M resistor. If you look at the truth table, if either input is low, the output must remain high. Input 1 is taken high by the action of placing a finger across the key pads. Just before input 1 goes high, the output of the gate must be high and, owing to the trimpot RV and the resistor R, input 2 will also be high and capacitor C will be charged. Thus, when input 1 goes high the output will immediately go low as both inputs will then be high. Input 2, however, now starts to go low due to the feedback via RV-R, but this action is slowed down by the capacitor having to discharge via RV-R. When the voltage on input 2 reaches the low threshold, the output will suddenly go high. Thus, C will begin to charge again via RV-R. When input 2 reaches the high threshold, the output will revert to the low condition once more and the whole cycle will be repeated.

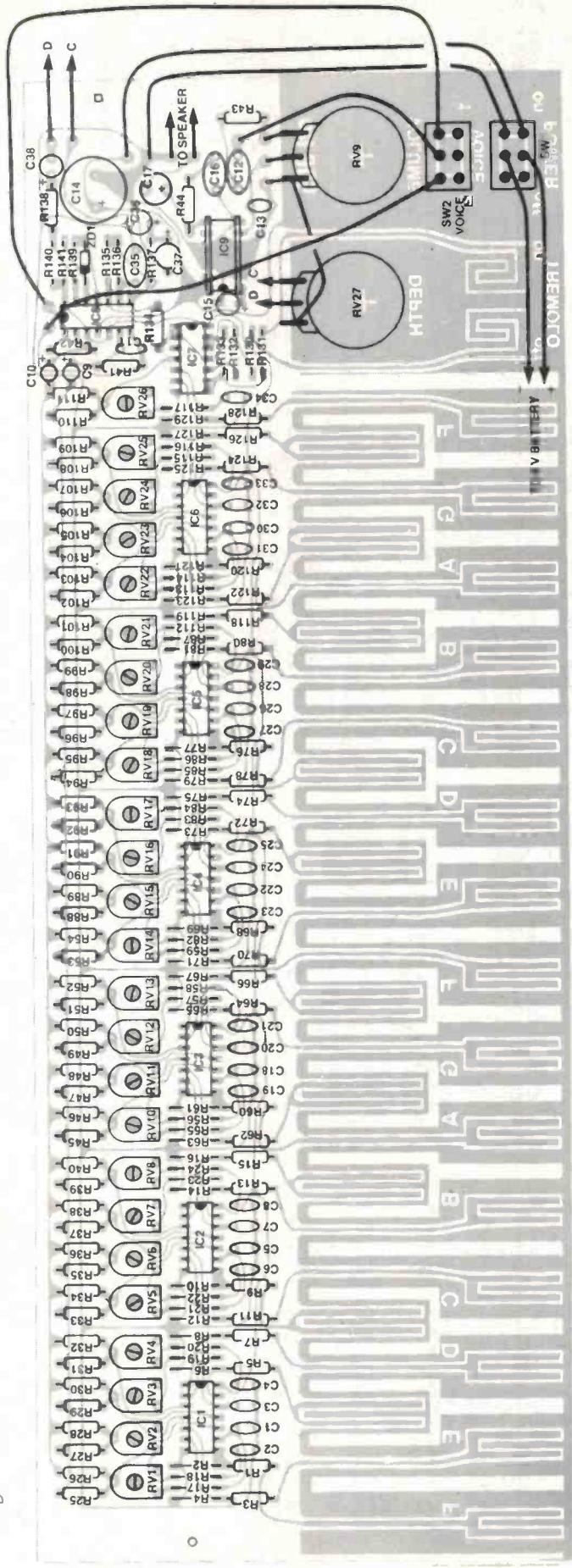This continues with the output going high/low/high at a rate largely determined by the RC network formed by RV, R and C. (The difference between the low and high thresholds, the hysteresis, affects it too.) By varying the



ETI-905 POLYPHONIC ORGAN PARTS LIST

Part	Value	Part	Value	Part	Value	Part	Value
R1	22k	R119	100k	RV1-8	220k miniature trimpot, horizontal mounting.	C22-25	15n greencap
R2	1M	R120	120k	RV9	22k log. pot. (or 20k)	C26-29	18n greencap
R3	22k	R121	100k	RV10-26	220k miniature trimpot, horizontal mounting.	C30-33	22n greencap
R4	1M	R122	120k	RV27	47k lin. pot (or 50k)	C34	27n greencap
R5	1M	R123	100k			C35	100n greencap
R6	22k	R124	150k			C36-38	10u/16 V RB electro.
R7	1M	R125	100k				
R8	22k	R126	150k				
R9	1M	R127	100k				
R10	1M	R128	150k				
R11	22k	R129	100k				
R12	1M	R130-131	180k				
R13	22k	R132-133	100k				
R14	1M	R134-135	180k				
R15	22k	R136	100k				
R16	1M	R137	10k				
R17-24	220k	R138	100k				
R25	47k	R139	39k				
R26	100k	R140	10k				
R27	56k	R141	100R				
R28	100k	R112-117	220k				
R29	56k	R118	120k				
R30	22k	R91	22k				
R31	1M	R92	1M				
R32	22k	R93	22k				
R33	1M	R94	1M				
R34	22k	R95	22k				
R35	1M	R96	1M				
R36	22k	R97	22k				
R37	1M	R98	1M				
R38	22k	R99	22k				
R39	1M	R100	1M				
R40	22k	R101	22k				
R41	1M	R102	1M				
R42	22k	R103	22k				
R43	1M	R104	1M				
R44	22k	R105	22k				
R45	1M	R106	1M				
R46	22k	R107	22k				
R47	1M	R108	1M				
R48	22k	R109	22k				
R49-54	220k	R110	1M				
R55-59	100k	R111	220k				
R60	56k	R112-117	220k				
R61	56k	R118	120k				
R62	100k	R63	56k				
R64	100k	R65	68k				
R66	100k	R67	68k				
R68	100k	R69	68k				
R70	100k	R71	82k				
R72	100k	R73	47k				
R74	10k	R75	47k				
R76	27k	R77	82k				
R78	100k	R79	82k				
R80	100k	R81	100k				
R82	220k	R83	220k				
R84	22k	R85	22k				
R86	1M	R87	1M				
R88-89	1M	R90	1M				

Part	Value	Part	Value
RV1-8	220k miniature trimpot, horizontal mounting.	RV27	47k lin. pot (or 50k)
RV9	22k log. pot. (or 20k)		
RV10-26	220k miniature trimpot, horizontal mounting.		
RV27	47k lin. pot (or 50k)		

Part	Value
C1-3	6n8 greencap
C4-6	8n2 greencap
C7,8,18	1u/16 V tant.
C9-10	33n greencap
C11	100n greencap
C12	330p ceramic
C13	1000u/16 V RB electro.
C14	10u/16 V RB electro.
C15	100n greencap
C16	100u/16 V RB electro.
C17	12n greencap
C19-21	15n greencap
C22-25	18n greencap
C26-29	22n greencap
C30-33	27n greencap
C34	100n greencap
C35	10u/16 V RB electro.
C36-38	10u/16 V RB electro.

Part	Value
IC1-IC7	4093B
IC8	LM324N, uA324PC
IC9	LM390N
ZD1	5V1 zener

Semiconductors

ETI-905 pc board; SW1 — DPST slide switch; SW2 — SPDT slide switch; one or two 50 mm diameter 8 ohm speakers; battery holder to take 6 x AA cells; two small knobs; 30 x 30 mm square of triplate or copper shim; hookup wire; case, etc.

Miscellaneous

Price estimate
\$50 — \$55

ARTWORK.


The pc board is too large to reproduce in the magazine. You can obtain a reproduction by sending a stamped, self-addressed foolscap-sized envelope to:

ETI-905 ARTWORK

ETI Magazine

15 Boundary St

Rushcutters Bay NSW 2011

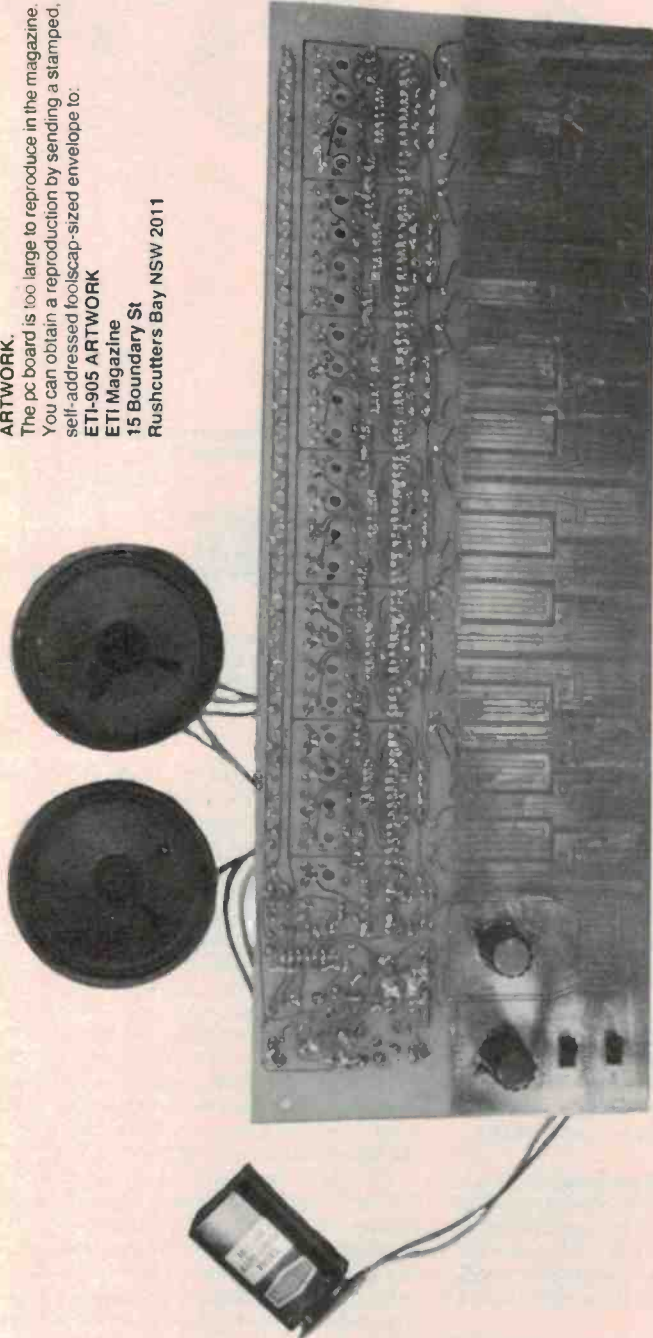

RESISTOR SHOPPING LIST

As there are so many resistors used, here is a 'shopping list' to assist you. The Parts List can be referred to in conjunction with the component overlay when assembling the pc board.

2R7	x1	82k	x3
100R	x1	100k	x34
10k	x3	120k	x3
22k	x25	150k	x3
39k	x1	180k	x3
7k	x3	220k	x27
56k	x3	1M	x26
68k	x3	4M7	x2

POTS & TRIMPOTS			
22k	(or 20k) log pot.		x1
47k	(or 50k) lin pot.		x1
220k	min. horizontal mount trim pots		x25


mended to all the pc board manufacturers making boards for this project that the keyboard area either be nickel plated or gold flashed over nickel plating. The choice of homemade board versus a bought one is up to you.

No matter whether you buy one or make your own, make a careful check of the pc board before commencing construction. Check that all the holes are drilled to the correct size. This is particularly important with the row of trimpots. You may need to drill holes near the two ends of the board, above the keyboard area, so that mounting pillars can be screwed to the board. Exactly where and what size will depend on how you're going to mount the board, and that we'll have to leave up to you. Some suggestions are given later. Check that the two slide switches fit in the slots in the pc board. Enlarge the slots with a small flat file if necessary.

Having satisfied yourself that the board's all OK, all the trimpots can be fitted first. All the resistors can be soldered in place next, mounting them right down on the pc board.

pins. You'll need an iron capable of supplying quite a bit of heat and having a 'chisel' bit (see ETI, October '81, A Good Joint is Hard to Find . . .). Don't overdo the solder. Then, carefully tin pins 3-4-5 and 10-11-12 on the LM380. Take one of the flags and orient it as shown in the diagram. Hold the tag with the solder side against the appropriate pins of the LM380 using a pair of pliers. Apply the flat of the iron to the tag until you see the solder flows freely. Remove the iron and *keep the flag steady until the solder sets*. This process is known as 'sweating'. If you hold the flag with your fingers while doing this you'll know exactly what it means! Now sweat the other flag to the other set of pins of the LM380. Do this carefully. While the LM380 is quite rugged, don't overdo it with the soldering iron. If you make a slip and have to resolder it, let it all cool down first.

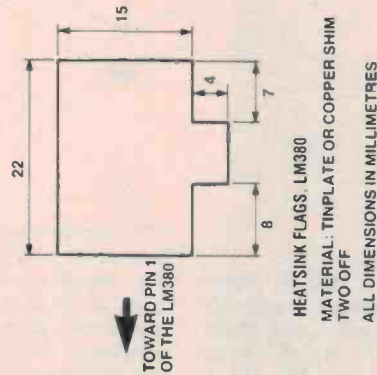Having accomplished that task, insert all the other ICs and solder them in place, making sure — as always — you have them correctly oriented. ICs 1 to 7 are CMOS types. Use either an isolated soldering iron or an iron with an earthed tip. Handle the




The LM380, IC9, should be soldered in place next. Make sure you orient it correctly. Now cut two 'flag' heatsinks, as shown in the accompanying illustration. You can use tinplate or thin copper 'shim'. Both can be obtained in small sheets from hardware stores. Motor spares stores may also stock copper shim. Tin the two tags at the bottom, each on the side that solders to the LM380

ICs by their ends, avoiding touching the pins. Solder the supply pins (7 and 14) first. Now come the capacitors. The only thing you have to watch for here is the polarity of the electrolytics and tantalums. It's probably a good idea at this stage to have a quick check over what you've done so far.

Now attach all the leads that run from the pc board to the two potentiometers, the two switches and the speaker(s). The three wires adjacent to C12 that run to the volume pot RV9 should be tinned copper wire. It makes life easier in a moment.

Now mount the two potentiometers, RV9 and RV27, and wire them up. Follow with SW1 and SW2. We glued our switches in place with quick-setting epoxy, but they could be screwed to the board. Attach the speaker(s) and the battery clip. Put knobs on the two potentiometer shafts.

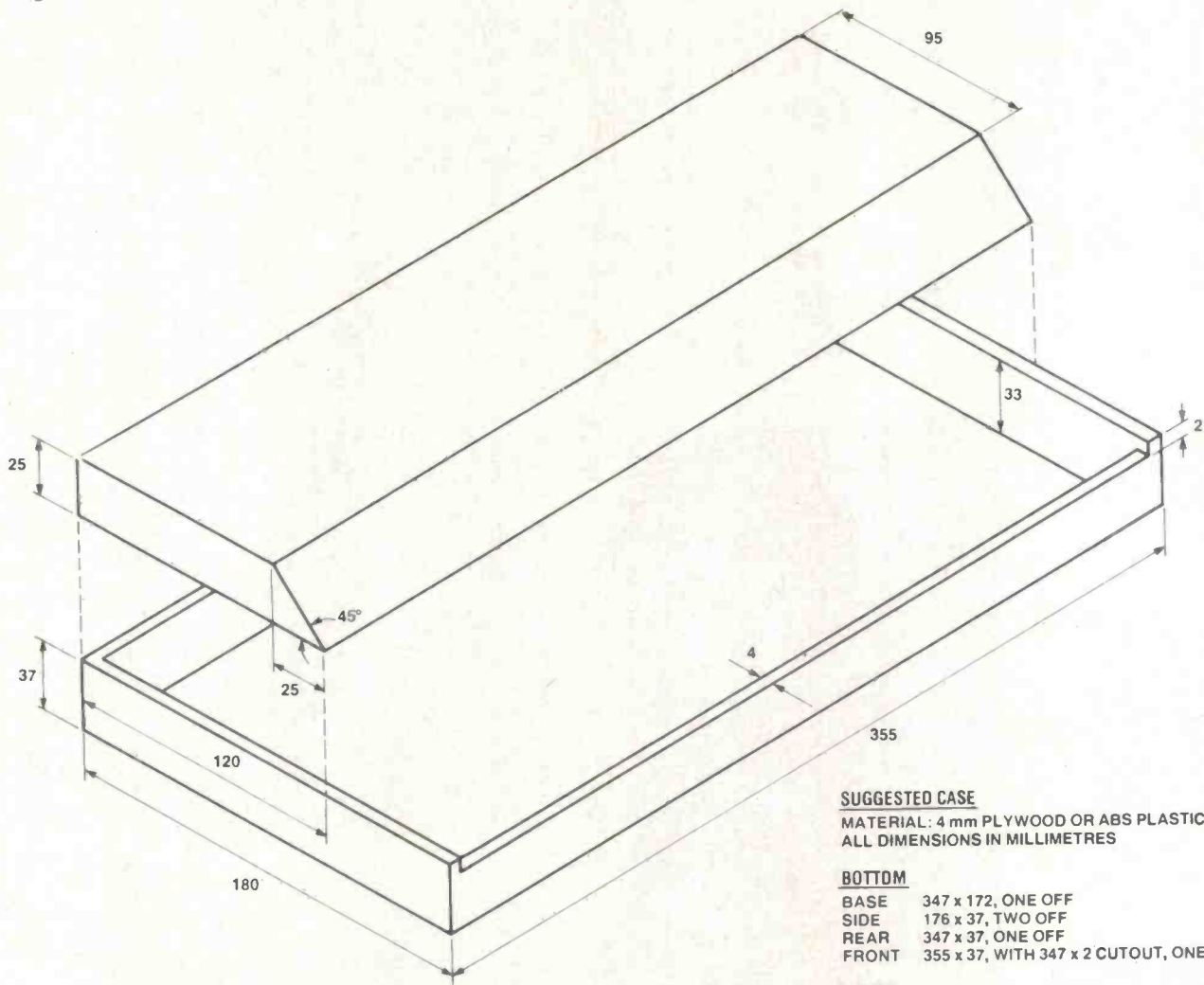Resist the urge to plug in a battery and try it out (it'll be out of tune anyway). First, check everything. Check the IC orientations especially. All OK? Now you're ready for the next bit. ▲



SUGGESTED CASE

MATERIAL: 4 mm PLY WOOD OR ABS PLASTIC SHEET
ALL DIMENSIONS IN MILLIMETRES

BOTTOM

BASE	347 x 172, ONE OFF
SIDE	176 x 37, TWO OFF
REAR	347 x 37, ONE OFF
FRONT	355 x 37, WITH 347 x 2 CUTOUT, ONE OFF

COVER

TOP	355 x 95, ONE OFF
SIDE	120 x 25, 25 x 45° CUTOUT, TWO OFF
FRONT	355 x 35, CHAMFERED EDGES, ONE OFF
REAR	347 x 21, ONE OFF

First try out

Set the VOICE switch to 2, DEPTH control fully anticlockwise (minimum) and the volume control about one-quarter advanced. Set all the trimpots to half travel. Switch on and touch one of the note keys. You should get a sound in the speaker. If not, try several other keys up and down the keyboard. Try VOICE 2 if you still get no response. If nothing happens there either, switch off and check connections and component orientations again. Correct any faults and try again. If you still have problems, check the voltage across pins 2 and 14 (+ve) of IC9 and pins 11 and 4 (+ve) of IC8. There should be 9 V or so on each. Also check that there's about 5 V across ZD1. With the TREMOLO off, check the voltage between the 0 V rail and pin 11 of IC8. There should be 5 V there. Then check the voltage between pins 1 and 14 (+ve) of ICs 1 to 7. There should be 5 V on each IC.

If all this checks out OK, you're going to have to do a bit of signal tracing. All this needs is a high impedance crystal earpiece and a 100nF capacitor in series with one lead.

With one lead on the 0 V rail, put the other lead on pin 2 of IC8 and touch one of the keys. You should get a sound. Try several other keys, or all of them, to see that you get a sound from each group of oscillators. If not, then check the circuitry around ICs 1 to 7. If the oscillators work, check that you're also getting signal across the two outer terminals of the volume control, RV9. If not, the fault is probably in the wiring of SW2 or IC8 is faulty. If you do get signal there, check with the earpiece that you're getting signal at pin 6 of the LM380. If not, RV9 wiring is probably faulty. If signal's there, check to see that it may be on pin 8 of the LM380. If so, then the speaker(s) or speaker wiring is faulty. If no signal there, the LM380 is probably faulty.

When the note oscillators work, try out the tremolo. If it doesn't work, check that IC7/2 and /3 is working correctly. You can do this with a multimeter. If that's OK, see that, with Tremolo ON, the multimeter needle vibrates when looking at the output (pin 11) of IC8/4.

Got it going? Now for that grand old Chinese ceremony "chu ning".

Tuning it up

First of all, put out the cat, tie up the dog and send the rest of the household away. This may be painful to others. If you possibly can, get hold of a digital frequency meter. Using one of these is by far the easiest way to tune each note oscillator to the required frequency. Simply attach the DFM input across the speaker terminals, sound each note in turn and adjust that note's trimpot to the frequency given in the accompanying Table. Looking from the keyboard side of the project, the trimpot for the lowest F is at the extreme left, lowest F# is the next trimpot, lowest G is the third trimpot from the left, and so on. Make sure the Tremolo is OFF. We used a marking pen and wrote the note on the board beside each appropriate trimpot.

The next best method is to tune the ETI-905 against a piano, organ or other fixed-pitch keyboard instrument. This is simple to do by sounding the required note on the piano, or whatever, then sounding the same note on the project and tuning it so that it sounds the same pitch (no 'beats' between them). Be patient and do it carefully, don't swing the trimpot violently one way then

polyphonic organ

the other. Tuning up this way is best done with the organ set to VOICE 2 and Tremolo OFF (turn the DEPTH fully anticlockwise).

There is another way, it's a little more tedious than the other methods, but yields good results, nonetheless. Get hold of a tuning fork (you could even build up and use the ETI-606 Electronic Tuning Fork, in Nov. '79 or Top Projects Vol. 6). Common tuning forks are "A 440" and "C 262" or middle C. You'll need three arms for this or a spare person. Seat yourself at a table or bench. Put a book or piece of sponge under the ETI-905 speakers. Set the VOICE switch to 2. Tremolo should be OFF. Set the tuning fork thrumming and hold the end of its shaft on the table or bench top to get a good, loud, sustained note. Touch the same note on the keyboard and adjust its trimpot so that its pitch is the same as the tuning fork's (i.e. no beats). Put the tuning fork aside and send your friend away, this next bit can be painful.

Say the note you just tuned was middle C (that's the C at the leftmost end of the keyboard). Now sound that C and the C above simultaneously, then tune the C above (C') so that there are no beats. But make sure that C' is above middle C. The trimpots should generally bring each oscillator into tune within a variation of $\pm 30^\circ$ of rotation from centre travel.

Now, count five notes up from middle C — C#, D, D#, E to F. Now sound F and middle C together. Tune F so that you get a pleasant sound with no beats. These two notes are now tuned a 'fifth' apart. Now sound the lowest F (right at the leftmost end of the keyboard) and the F you just tuned together. Tune the lower F so that you get no beats — making sure it's an octave lower. Now sound the topmost F and the F above middle C together and tune the topmost F for no beats. All three Fs should now be in tune. Starting at F above middle C, count up a further five notes — F#, G, G#, A to A# (B flat). Once again, tune for

PLAYING TIPS

The 'keys' should be played with the ball of the finger, not the tip. There is no "touch" to the instruments — hitting the key hard will not alter the sound in any way. This is much like a real organ. Touch the keys smoothly and firmly.

Under extremely humid conditions, or if you have greasy fingers, some trouble may be experienced with notes holding on. Wipe your hands thoroughly and the keyboard, too.

a pleasant sound with no beats. Then tune the A# an octave lower. The next one you will tune is D# (E flat) right up the top end of the keyboard. Tune its partner an octave lower. Where to go from here? Simple. Start down at the lower D#.

Count five notes up from the D# just above middle C — that's the G# to the right. Once again, tune for a pleasant sound with no beats, then tune the companion note an octave lower. Commencing at *that* note, count five notes up — to C#. Tune as before, then tune the octave companion (now to the right, higher in pitch). From C# above middle C, count another five notes up (F#), tune it, then the octave note. Continue — B to E, E to A, A to D, D to G, then check that the Gs are in tune with the Cs — the first notes tuned. They should be. If not, they should only be a little out and you can go back around the loop and make minor adjustments.

All tuned? Now learn to play Bach's Toccata in D minor!

A case

We have not described complete details of a case for this instrument as we would expect constructors to 'customise' a case to suit individual tastes or circumstances. However, we have drawn up the dimensions of a suitable case that may be constructed of 4 mm thick material — such as plastic sheet or plywood. The design has a 'top' and a 'bottom' and each need only be glued together. The board can be mounted in the bottom on standoff pillars. Several standoff pillars screwed onto the board could then support the case top. The accompanying drawings show the rudimentary details. The completed case could be covered in suitably patterned 'Contac', or something similar.

Batteries, supply

The project was designed to be powered by a 9 V battery or other sort of dc supply. It draws around 40 mA at average volume during playing, somewhat over 100 mA at full volume. You can use a No. 216 9 V (transistor radio) battery, but we recommend you get either an extra heavy duty type or an alkaline battery. Alternatively, you could use 6 x AA cells in a 'six pack' battery holder. You can dispense with the battery and use an appropriately rated plugpack if you like. A plugpack rated at 6 V/200 mA will deliver voltages around 8 - 9 V at current loads under 100 mA, and such a plugpack would be the best to use if you want to power the project from the ac mains.

NOTE FREQUENCIES

F	698.5
E	659.3
D#	622.3
D	587.3
C#	554.4
C	523.3
B	493.9
A#	466.2
A	440.0
G#	415.3
G	392.0
F#	370.0
F	349.2
E	329.6
D#	311.1
D	293.7
C#	277.2
C	261.6 (middle C)
B	246.9
A#	233.1
A	220.0
G#	207.7
G	196.0
F#	185.0
F	174.6

PROVIDA

PROFESSIONAL COLOUR VIDEO DISPLAY BOARD

Memory mapped colour video display board has 2K RAM page buffer, 2K RAM function block and separate 2K RAM for 128 programmable characters. The dual character set is generated by an 8K PROM.

- 7 colour RGB output
- 80 x 24 and 16 x 64 page format
- 128 programmable characters or 128 x 256 Hires graphic
- Light pen facility
- S100 standard bus
- Flashing, inverse, ½ intensity, underlining & mirror reverse
- Jitter free video display
- Programmable TV synch. suitable overseas use



QUALITY THRU HOLE PLATED BOARD ASSEMBLED & TESTED

\$220 + 20% Sales Tax

90 day warranty

enquiries to:

TECHNITRON

84 TARGO ST., BUNDABERG
4670 PH (071) 72 5606

NOW READ THIS!



Powerful New 6000 RPM Mini Drill for PC Work

Tons of Torque. Just the shot for PCB work. 12V DC operated from external Power Pack. 1.2mm chuck capacity. Supplied c/w 1mm drill bit.

- T2302 \$12.95
 Drill Bits:
 T2320 (0.8mm) ... \$1.25
 T2325 (1.0mm) ... \$1.25

VELOSTAT



Non-static sheeting for storing CMOS IC's, LSI's etc. 1000 times better than aluminium foil. Will store up to 150 IC's on one 225 x 150mm sheet.

H 0500 ~~\$3.50~~ per sheet
 NOW \$2.00 a sheet — GAD!

MIC INSERT ELECTRET

Great little replacement for tape recorders, etc. Handy for hobby projects. Includes data sheet and application circuit. 50 HZ - 15 KHZ



C 0170 ... ~~\$1.95~~ NOW \$1.00—OUCH!

SOLDER SUCKER

Quality de-solder tool with Teflon tip and nozzle sweeper.

REPLACE- MENT TIP

T 1240 ... ~~\$14.50~~ T 1241 \$2.75
 ½ PRICE\$7.25



BANKCARD PHONE ORDER

FREE DELIVERY THIS MONTH

Bankcard holders may phone your order to us up to 7 pm (Eastern Standard Time) for next day delivery Capital Cities and suburbs. 48 hour delivery to virtually all country centres.

AND WHAT'S MORE ...
 WE'LL PAY THE FREIGHT!

with minimum purchase value of \$25. Why not phone your order in "After Hours" on our Answering Machine? — I know — we all hate those darn tape machines — But tell you what! Tape machine orders are processed first thing in the morning — even before we pick up the mail. Again free Jetservice delivery applies this month for orders over \$25.

AT LAST — SINTERED PLATE NICAD RECHARGEABLE BATTERIES AT A PRICE YOU CAN AFFORD

COLUMN RECHARGEABLE

AA Size 1-2V Genuine Sintered Plate Nicad Construction by Furakawa — arguably the top Nicad designer/manufacture in the world today. Amazing low price.

Cat S3020 ea \$1.95
 10-49 \$1.70, 50+ \$1.60


Incredible!

UNIVERSAL MULTIMETER PORTABLE WITH BENCH STAND

23 ranges at less than \$1 per range.

* 20,000 OHMS/Volt DC * 10,000 OHMS/Volt AC * Mirror backed scale * Overload protected * Unique carry handle doubles as a bench stand * High-impact resistant case * Uses 1 AA Penlight batter (Incl.) * Comes complete with battery, test leads and instructions. RANGES: DC Voltage 0-.25, 1, 2.5, 10, 25, 100, 250, 1000. AC Voltage 0-10, 25, 100, 250, 1000 Decibels 20 to +22db DC Current 0-50, 500 UA, 0-5, 50, 500MA OHM Meter 0-6 megohms in 4 ranges, 30 ohms centre scale. Size 135 x 91 x 39

Q 1002 .. \$22.50 4 or more .. \$21.00

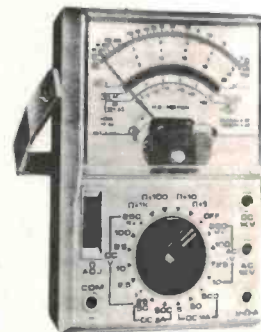


A FREE Carry Case Cat. Q 1012 \$3.50 value with every meter purchased from this advert — YES! that's right — yours for the asking.

CRYSTALS

CRYSTALS	Y 1000	1-000	11.50
	Y 1003	1-8432	9.50
	Y 1006	2-000	7.50
	Y 1010	3-57945	3.00
		Solder Type	
	Y 1012	4-000	5.00
	Y 1015	4-194	5.00
Parallel Resonant	Y 1017	5-000	5.00
	Y 1018	6-000	5.00
Frequencies Quoted in MHZ	Y 1019	8-000	5.00
	Y 1020	10-000	5.00
	Y 1025	12-000	5.00
	Y 1030	16-000	5.00



SOLDERING IRON STAND UNIVERSAL TYPE

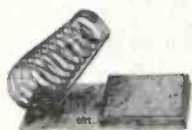

T 1302 ... ~~\$5.95~~ NOW \$4.00 GOSH!

FAMOUS ELECTROLUBE PRODUCTS IN GENEROUS "TRADE SIZE" PACKS



ELECTRO
MECHANICAL
LUBRICANT PEN
T 3062 ... \$3.50

FREEZER
T 3080 ... \$5.50



ELECTRONIC
CLEANING SOLVENT
T 3065 ... \$6.50

CLEAR PROTECTIVE
LAQUER
T 3085 ... \$6.95




YOUR MONEY BACK PLUS \$5

If Altronics Jetservice Delivery is not the Best in Australia

ORDER FROM ALTRONICS WITH COMPLETE CONFIDENCE. Compare this check list with any other Australian Electronics Supplier ... * Delivery Time * Packing * Product Quality * Value for Money * Technical Queries Answered * Prompt Back Order Advice of not in stock items. If after receipt of your Jetservice order you are not convinced Altronics service is superior to any other Australian Electronics Supplier you may return your purchase to us for a full refund plus \$5 for your trouble.

Regards
John & Rosemary

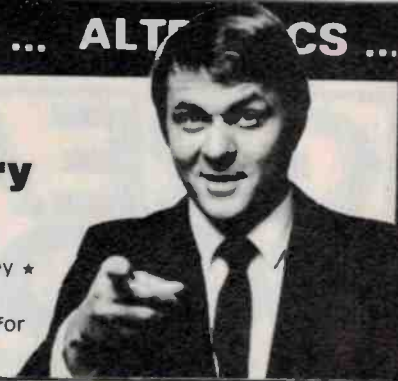

WEATHERPROOF SIREN HORN

12V DC operated — Deafening Siren Wall. Super handy for audio signalling, security systems etc. Current drain 500MA approx. Completely weatherproof. Attractive off-white PVC finish.



S 5058 ... ~~\$19.50~~ NOW \$15.00 ea.

PIEZO ALARM

Similar to "Sonalet" type. Absolutely ear piercing sound. Recommended voltage 5-15V DC. Ideal for almost all audio signalling applications. i.e. fire, water and gas signalling, computer alarms, etc.



S 5066 ... ~~\$4.95~~ NOW \$4.50 each

D25 SERIES CONNECTORS

Universal 25 Pin Computer Series

P 0900 Male 25 Pin ... ~~\$6.50~~ NOW \$3.95
 P 0901 Female 25 Pin ... ~~\$6.50~~ NOW \$4.50
 P 0905 Backcover ... ~~\$3.50~~ NOW \$2.50



SAVE NEARLY 30%

VINYL BINDER

Holds 12 magazines, each on a spring out wire rod. Just the shot for each year's set of Electronics Australia, ETI or any of your favourite magazine.

Suits all A4 size publications (275 x 210). Very smart Royal Blue colour with beautiful gold embossing.

B 9999 ... ~~\$5.50~~

THIS MONTH


\$5.00 each
 4 or more \$4.50 each



TECHNICIAN PARTS CASE

See through acrylic parts tray and see through lid. Ident. label system. Movable compartment dividers. Two lift out compartment trays plus one extra deep tray. Great for screws, semis, passives etc.

H 0450 ...
 ... \$17.50

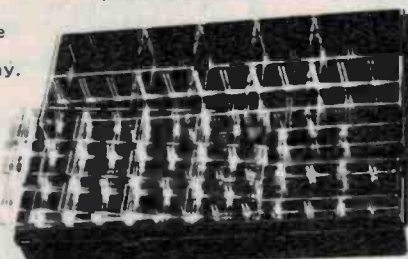

(Clear Lid not illustrated)

Incredible Value Dainichi Loudspeakers

DAINICHI WIDE RANGE 25 Watt



200 mm (8 in.). This superbly smooth high power speaker comes from Dainichi, one of Japan's finest speaker manufacturers (they produce OEM Speakers for Pioneer). Max. input power 25W 8 OHM Z. Resonant to 60 HZ. Huge 10 OZ Magnet frequency response 40 HZ-18 KHZ.

C 2001 ... \$19.50
 4 or more ... \$17.00

DUAL CONE WIDE RANGE



200 mm (8 in.). 10 Watts Max. power input. Public Address, Background Music, Ideal HI FI extension speaker. Includes transformer holes at 51 mm.

Over 30,000 sold in

Australia!

Mounting holes 140 x 140 mm


C 2000 ... \$8.50
 10 Up ... \$7.90

INTERLOCKING PARTS DRAWER

Unique side and top/bottom keying system allows you to use just a few or build a whole wall of drawers as your parts expansion dictates. Quality designed drawer slides will not "stick" or seize. Slide handle also takes ident. cards. Single or double drawers available.

H 0435 Single Way ... \$2.20

H 0436 Double Drawers ... \$2.20

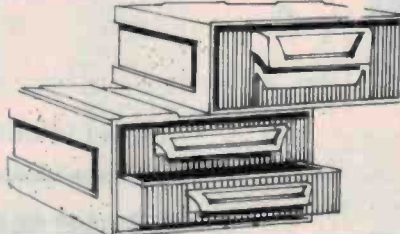

New 10mm Digit LCD Clock Module



Uses the new NEC UPD833G LSI and quality EPSON LCD display.

Size 60 x 38 x 10mm, operates from 1.5V DC. Display selectable to 12 or 24 hour format. AM/PM Display.

Inbuilt control timer selectable to 15, 30, 60 and 120 minute intervals.


Stop watch facility to 24 mins duration. Alarm timer, Snooze timer, Sleep timer.

An incredible diversity of applications. i.e. clock radio, travellers watch, stop watch, digital alarm clock, sleep timer, snooze timer, appliance timer, sequential controller, dual time clock.

And the best news is the low price!

Y 1020 ... \$16.50

MINI TOGGLE SWITCHES

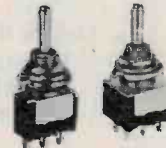

OEM QUALITY
 250V 2 AMP
 RATED

	PRICE	10 UP
S 1010 SPDT	\$1.20	\$1.00
S 1025 SPDT Centre off	1.40	1.20
S 1020 DPDT	1.40	1.20
S 1030 DPDT Centre off	1.95	1.75

DIL Switch Bargains

GOLD PLATE SELF WIPING CONTACTS



S 3050 4 way \$1.25
 S 3060 8 way \$1.75

KEY OPERATED SWITCH



19.5 mm mounting hole required. Supplied with two keys. Hundreds of applications for security type applications.

S 2500 ... ~~\$6.95~~
 NOW ONLY \$5 EACH

ALTRONICS

For Address, Phone No. and Despatch details see our Double Page Advertisement pages 28-29

ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ...


ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ...

GREAT NEW BOOKS

FROM JAYCAR THE ELECTRONIC BOOK SPECIALIST.....



THE CHEAP VIDEO BOOK

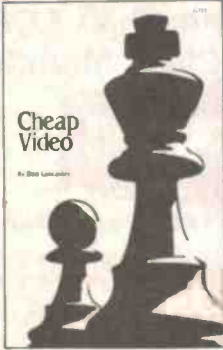

ONLY \$10.95

Complete discussion of a new, low-cost way to get words, pictures, and opcodes out of your computer and onto any ordinary TV set. Don Lancaster outlines an easy to build, seven-IC circuit which you can build for less than \$20. This circuit can be software controlled to provide any alphanumeric or graphics format including high resolution (256x256) and four colour mode. By Don Lancaster. 256 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21524

EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

Conduct interesting and exciting experiments in artificial intelligence with this book, a small computer with extended BASIC, and some knowledge of the BASIC language. The author first introduces you to artificial intelligence - the capability of a device to perform functions normally associated with human intelligence, such as playing, problem solving, reasoning, creativity, and verbal communications. Then game-playing programs, with a checkers-playing game as the main topic, are explained. By John Krutch. 112 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21785

THE BEST FOR \$11.95



ACTIVE FILTER COOKBOOK



GREAT READING - \$19.95

A practical, easy to read discussion of the many types and uses of active filters by popular author Don Lancaster. Learn how to construct filters of all types, including high pass, low pass, and band pass having Bessel, Chebyshev, or Butterworth response characteristics. Easy to understand - no advanced math or obscure theory is used. Active Filter Cookbook can be used as an introduction to active filter circuits or as a reference book for analysis and synthesis techniques for active filter specialists. By Don Lancaster. 240 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21168

DESIGN OF ACTIVE FILTERS WITH EXPERIMENTS



An introduction to the implementation and design of active filter circuits that use the popular 741 op-amp chip. The emphasis is on the use of active filters and their design, without complex maths. Twenty six detailed experiments and many practical examples. By Howard M. Berlin. 240 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21539

FOR THE SHELF - \$14.95

CMOS COOKBOOK

One of the best selling technical books on the market, this cookbook gives you a solid understanding of CMOS technology and its application to real world circuitry. The author explains how CMOS differs from other MOS designs, how it is powered and what its advantages are over other constructions. A mini-catalogue is included which lists over 100 devices, giving their pinouts and application notes. The final chapter shows you how to put all the previous information together to construct a number of large scale, working instruments. By Don Lancaster. 416 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21398

GET COOKING FOR \$17.95

IC OP-AMP COOKBOOK

An informal, easy to read guide covering basic op-amp theory in detail, with 200 practical, illustrated circuit applications to reflect the latest technology. JFET and MOSFET units in both single and multiple formats are featured. Includes manufacturers' data sheets and lists addresses of the companies whose products are featured. By Walter G. Jung. 480 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21695

GREAT BOOK ONLY \$21.95

555 TIMER APPLICATIONS SOURCEBOOK WITH EXPERIMENTS


Describes the construction and use of the 555 timer and gives you numerous, practical examples of its applications in all areas of electrical and computer engineering. Seventeen simple experiments are provided to give you working knowledge. By Howard M. Berlin. 160 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21538

LATE NIGHT READING \$9.95

DESIGN OF OP-AMP CIRCUITS WITH EXPERIMENTS

A series of 35 experiments illustrates the design and operation of linear amplifiers, differentiators and integrators, voltage and current converters, active filters and lots more. By Howard M. Berlin. 224 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21537

EXPERIMENT FOR \$14.95

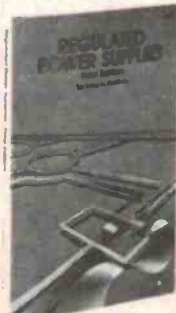

REGULATED POWER SUPPLIES (3rd Edition)

'THE' BOOK ONLY \$25.95



The newest, most comprehensive discussion of internal architecture and operation of the latest solid state regulators. Thoroughly explains when regulated supplies are needed and how to incorporate them into your design projects. Discusses modern, practical circuitry including linear and switching circuits and late ICs. By Irving M. Gottlieb. 424 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21808

ELECTRONIC MUSIC CIRCUITS


Written for the computer and electronics hobbyist with an interest in music, as well as musicians and studio engineers. The author describes how to build a custom electronic music synthesizer, outlines numerous other circuit designs, and then shows you how to modify them to achieve particular responses. Many of the circuits can be used as special effects boxes for guitars and other musical instruments. Approx. 288 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21833

FOR 'MUSO's' - \$23.95

RF CIRCUIT DESIGN

A user-oriented text with a practical approach to the design of RF amplifiers, impedance matching networks, and filters. Can be used in cookbook fashion a catalogue of useful circuits with component values. Utilizes a minimum of complex math. A valuable bridge between the classroom and 'real world' application, and an excellent reference manual. Approx. 352 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21888

FOR DESIGNERS - \$25.95

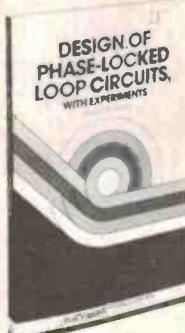

DESIGN OF PHASE-LOCKED LOOP CIRCUITS WITH EXPERIMENTS

'THE' PLL BOOK - \$14.95



DESIGN OF PHASE-LOCKED LOOP Cts WITH EXPERIMENTS

An excellent introduction to the theory, design, and implementation of Phase-Locked Loop circuits using various TTL and CMOS devices. Useful self study course for the experimenter and for inclusion in college courses on control systems or linear ICs. Includes manufacturers' data sheets and describes the use of breadboarding aids in the wide range of laboratory type experiments. 256 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21645

DESIGN OF VMOS Cts WITH EXPERIMENTS

VMOS technology easily surpasses the BJT, FET, and CMOS circuitry in its mimicry of the ideal active circuit element. The authors provide an in-depth look at the technology which makes dramatic advancements possible, and show how these components can easily and effectively be integrated into common circuit designs to enhance their responses. 176 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21686

THE LATEST - \$16.95

HOW TO READ SCHEMATIC DIAGRAMS (3rd Edition)


Learn to successfully read schematics - the roadmaps of electronic circuits. Defines many of the newer symbols including logic gates and provides up-to-date definitions of many electronic symbols. Author Merrington shows you how various components are combined to form circuits, and takes you step by step through a schematic for a radio receiver. 192 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21127

GREAT VALUE - \$9.95

MODERN DICTIONARY OF ELECTRONICS

Join the millions who use this superb reference to the world of electronics. Contains over 20,000 terms, including the latest language used in the fields of communications, reliability, semiconductor, medical electronics, microelectronics, fibre-optics, and computers. For quick and easy reference, separate coverage of schematic symbols, the International System of Units (metric) and a table of the Greek alphabet are provided. By Rudolf F. Graf. 832 pages. 5 1/2 x 8 1/2, hard. Ask for No. 21314

THE GREATEST - \$29.95

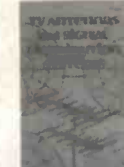

TV ANTENNAS AND SIGNAL DISTRIBUTION SYSTEMS

As reviewed in Sept. EA page 107

WAS \$14.75 NOW \$12.50

An aid in selection and installation of TV antennas and signal distribution systems, and how to implement these systems for high quality TV reception. Includes valuable performance data based on actual measurements made by the author. 256 pages. 5 1/2 x 8 1/2, soft.

LASER TECHNOLOGY (2nd Edition)

Update laser technology from a practical standpoint. Discover applied laser principles, laser holography, and beam capabilities and energies. Other chapters explain laser communications systems, laser systems for the military, and instrumentation in medical surgery and dentistry. 288 pages. 5 1/2 x 8 1/2, hard. Ask for No. 21588

BE A LASER MAN - \$21.95



MODERN RECORDING TECHNIQUES

FOR THE HI FI MAN \$17.95



Explains the equipment, controls and techniques found in the modern recording studio and how to use them creatively as well as properly to produce desired results. Numerous photographs, diagrams, and charts. 368 pages. 5 1/2 x 8 1/2, soft. Ask for No. 21037

73 DIPOLE AND LONG-WIRE ANTENNAS

Experiment with one or more of 73 different wire antennas - from dipole to rhombic. By Edward M. Noll, W3FOJ. 160 pages. 5 1/2 x 8 1/2, soft. Ask for No. 24006

GOOD READING - \$9.95

CMOS DATA '82 FROM NATIONAL ONLY \$8.95 SEMICONDUCTORS

Complete data on National 4000 and 74C series CMOS as well as the CMOS LSI devices produced by N.S. Size: 170w x 230h x 60d.

Jaycar NUMBER 1 FOR KITS


125 York Street, Sydney 2000
Phone: 264 6688 Telex: 72293
"Nevilles Corner"
Cnr. Carlingford & Pennant Hills Road,
Carlingford
Phone: 872 4422
Mail Orders To: Box K-39 Haymarket
Sydney 2000

POST AND PACKING CHARGES \$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40) \$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60) \$100 up (\$6.20)
NEW SHOP HOURS Mon-Fri 8.30 to 5.30pm Sat 8.30 to 12.00pm Thurs night to 8.30pm



MAIL ORDER BY BANKCARD VIA YOUR PHONE

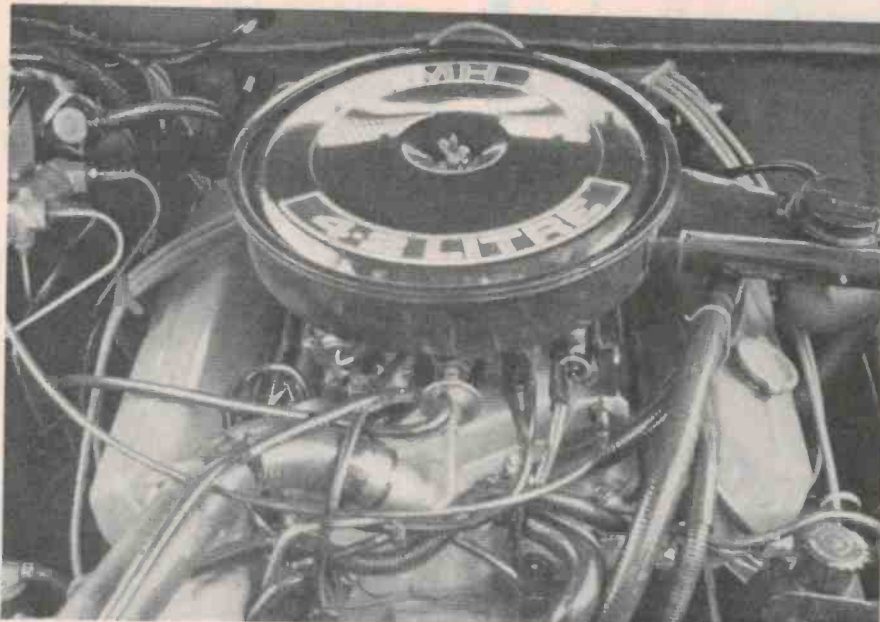YOU CAN PHONE CARLINGFORD ON 872 4444 AS WELL!



The 'Auto Tester'

Graeme Teesdale

This handy little test gadget will help you sort out all those little bugaboos that can go wrong in automotive electrics. With this, you can check voltage drops, on and off charge battery voltages and resistances.

BUDDING MECHANICS are very often bamboozled by the electrics of a modern motor vehicle. An automotive or electronic type multimeter with its combination scales all crammed together simply adds to the confusion. This project was developed to make fault-finding a little easier by providing simple LED indication of 'set' points in voltage or resistance.

In a vehicle, voltage drop in cables of more than 0.5 volt can bring problems. The Auto Tester provides a clear indication of voltage drops less or greater than 0.5 V. The battery system, to perform up to scratch, must deliver at least 12 V on load and the battery should have a terminal voltage of more than 13.5 V when charging.

Resistances encountered in vehicles tend to have fairly well defined limits. Many devices have resistances under 10 ohms, a few range up to 150 ohms. Thus the first resistance 'set' point is at about 150 ohms. Much higher resistances are encountered in HT suppressors, etc. Generally, these are around 10k or 15k. Trouble can occur if they go faulty and exhibit a high resistance, generally greater than 50k. Thus, two other 'set' points for resistance are at 10k and 50k.

The unit was housed in a small, conveniently-sized jiffy box. The pc board designed for this unit will just fit comfortably into several different types on the market. Four indicator LEDs are provided: a



Pragmatic. Simple, but functional. The project was housed in a small jiffy box with a Scotchcal panel added.

POLARITY indicator, followed by one for each of the three set points in voltage and resistance. Two pushbuttons select which 'mode' you wish to use — VOLTS or OHMS.

Where battery polarity is unknown, or in instances where the Auto Tester may be incorrectly connected, the POLARITY LED will light when the red, or positive, input lead is connected to the battery negative.


Protection against input overvoltage damage has been incorporated, so that voltage inputs of greater than 15 V are 'clamped' to avoid damaging the IC.

The Auto Tester, unlike most multimeters, will not be damaged if a dc voltage is applied to the input when it is being used in the resistance mode.

The unit is powered from a No. 216, 9 V battery mounted in the jiffy box. The circuit is based around the commonly available, low cost LM324 or uA324 quad op-amp. The battery will likely last its shelf life (probably a year or more) as consumption is only ever momentary, when you take a reading.

Construction

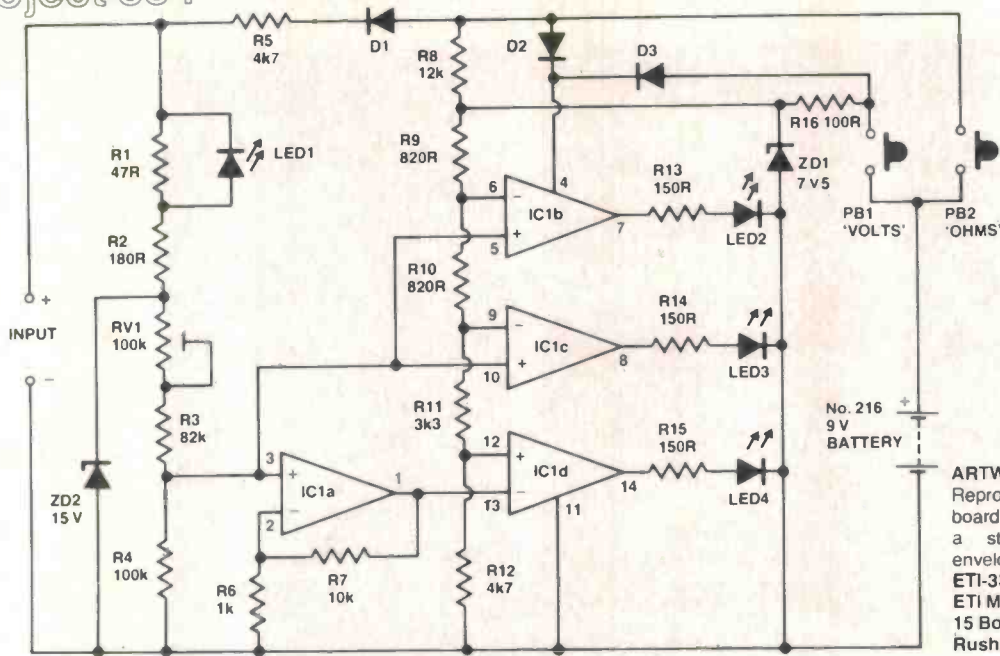The project pc board has been designed to fit into almost any of the small jiffy boxes available. These are generally all-plastic or plastic cases with a light gauge aluminium 'lid'. We designed a Scotchcal front panel which will suit those boxes measuring 52 x 100 mm or a little larger. ▶



ARTWORK.
Reproductions of the front panel and pc board artwork can be obtained by sending a stamped, self-addressed A4-sized envelope to:
ETI-334 ARTWORK
ETI Magazine
15 Boundary St
Rushcutters Bay NSW 2011

Before assembling the components to the board, check that it has no breaks or shorts between tracks, particularly between the IC pins. Also check that components like RV1, the zener diodes and LEDs have the correct lead hole sizes drilled. The board can be mounted by soldering the two pushbutton switches directly to the board and letting the

board hang from their leads — it's quite a robust arrangement. If you're going to do this, see that the holes in the pc board for PB1 and PB2 are drilled the right size.

Next, check that the pc board fits inside the box. Make sure you orient the board correctly when you do this. If the board doesn't fit in without jamming you may have

to carefully trim a little off one or both sides with a file until it fits properly. If it doesn't fit at all, get a bigger box!

Using the front panel artwork, mark out and drill the front panel, or lid, of the box. Fit the four LED mounts.

Once the board is ready to go, commence assembly by soldering all the resistors in

HOW IT WORKS — ETI 334

The clearest way of seeing how this circuit works is to break it down into simplified sections. The Auto Tester performs three main functions: voltage drop measurement, 12/13.8 V measurement and resistance measurement. In addition, an indication of reverse polarity connection is provided along with input overvoltage protection.

The whole circuit is built around an LM324 (or uA324) quad op-amp, IC1. Three op-amps from this are arranged as comparators and one as an amplifier. Let's look at the voltage drop measurement stage first. This portion of the circuit is shown in Figure 1.

Only the relevant components are included. When PB1 is pressed, power is supplied to IC1 via D3. Note that R1, LED1, R2 and ZD2 play no part here. RV1, R3 and R4 form a voltage divider. IC1a is arranged as an amplifier and IC1d as a comparator.

If the input leads are then connected across a cable having a voltage drop of less than half a volt, say 0.2 V, the voltage appearing at the

non-inverting input of IC1a will be about 0.1 V (half the input volts) due to the divider action of RV1, R3 and R4. RV1 is set to provide this division ratio of about two. IC1a provides a gain of 10, and thus the output will be 1 V. This is lower than the 2.6 V on the non-inverting input of IC1d and thus its output will be driven high, lighting LED4.

If the voltage drop on the cable you have connected the input leads across reaches a little over a half a volt, say 0.55 V, the voltage on the non-inverting input of IC1a will be 0.275 V. The voltage on the output of IC1a, and thus the inverting input of IC1d, will be 2.75 V which exceeds the 2.6 V on IC1d's non-inverting input. The output of IC1d will thus go low and LED4 will extinguish, warning you of excessive voltage drop in the cable.

Note that, when performing voltage drop measurements, the positive lead must be connected at the end of the cable closest to the positive terminal of the vehicle battery.

When the input leads are open circuit and

PB1 is pressed, D1 will be forward biased as it is connected to the 7.5 V rail (from ZD1) via R8. Thus, something a little under 7 V will appear at the 'top' of RV1, and about 3.5 V at pins 3, 5 and 10 of IC1. This will drive the output of IC1d low, and LED4 will be unlit. It won't change the condition of either IC1c or IC1d, so LEDs 2 and 3 will also be unlit. Thus, nothing happens if you press PB1 ('VOLTS') when the leads are not connected to anything.

Let us look at the other voltage measurements now. This section of the circuitry is shown in Figure 2. IC1b and IC1c are connected as comparators. Each has their inverting input connected to the voltage divider R9, 10, 11 and 12. This voltage divider is supplied from a regulated 7.5 volts, derived by ZD1 and R16. Thus, battery voltage variations will not affect circuit operation, provided the battery voltage doesn't fall to about 8 V or less. IC1b and IC1c have their non-inverting inputs connected together and these are attached to the input voltage divider.

Figure 1. Voltage drop measurement.


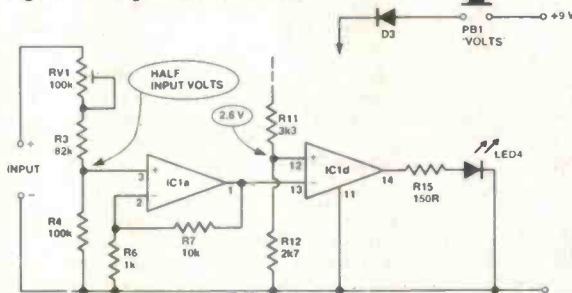


Figure 2. 12 V and 13.8 V measurement.


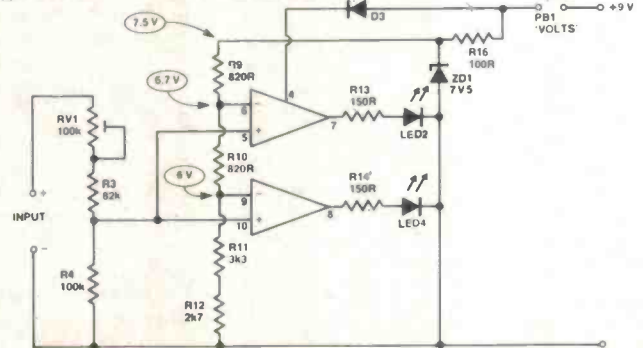


PARTS LIST — ETI-334

Resistors	all 1/4W, 5% unless noted
R1	47R
R2	180R
R3	82k
R4	100k
R5	4k7
R6	1k
R7	10k
R8	12k
R9, R10	820R
R11	3k3
R12	4k7
R13, 14, 15	150R
R16	100R
RV1	100k min. trimpot, horizontal or vertical mount.
Semiconductors	
D1, 2, 3	1N914, 1N4148 etc
IC1	LM324, uA324
LED1, 2, 3, 4	TIL220R red LEDs
ZD1	7V5 zener diode
ZD2	15 V zener diode
Miscellaneous	
PB1, PB2	press-on pushbutton switches

ETI-334 pc board; jifty box 52 x 30 x 100 mm or thereabout; No. 216 battery and battery clip lead; two alligator clips and leads, one red, one black; Scotchcal front panel, etc.

Price estimate \$15 — \$17

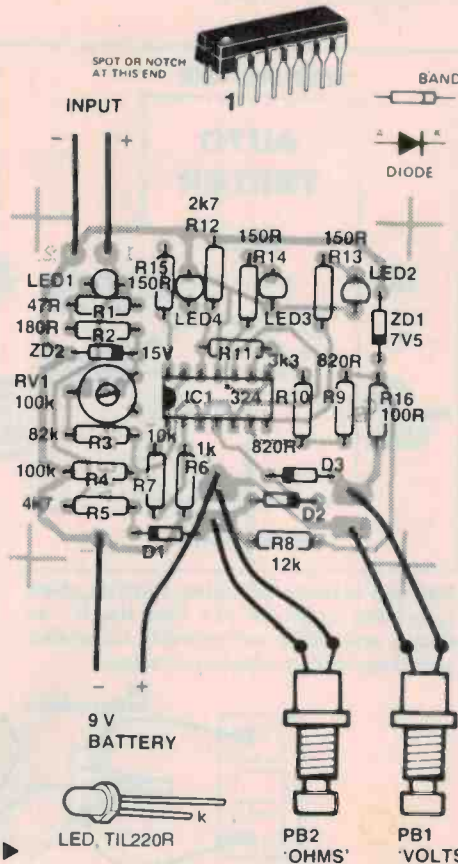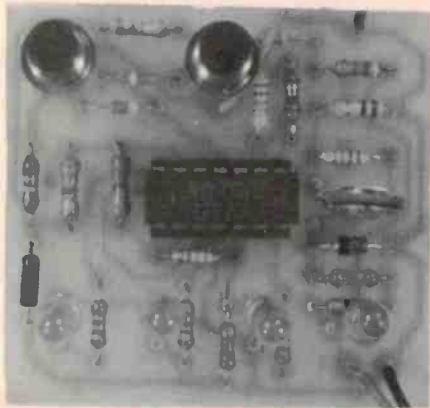

place, then the diodes D1, 2 and 3, followed by the two zener diodes. Make sure you get all the diodes in the correct way round.

If you're mounting the board to PB1 and PB2, solder these in place now, making sure their mounting 'shoulders' are level. Insert the four LEDs next, but don't solder them in place. Make sure you orient them correctly and don't trim off their leads. Temporarily mount the board to the front panel of the case. Push the LEDs into position and then solder and trim their leads. De-mount the board from the panel and fit IC1, RV1, the battery clip lead and the two input leads.

When PB1 is pressed, power is supplied to IC1 via D3, as before. With no input voltage, the outputs of IC1b and c will both be low and LEDs 2 and 3 will be unlit. When the input leads are connected to a voltage a little over 12 V, the voltage on pin 10 of IC1c will be a little over 6 V. This will drive the output of IC1c high, lighting LED3. When the input voltage rises above about 13.5 V, the voltage on the pin 5 of IC1b will be a little over 6.7 V, driving the output of IC1b high, now lighting LED2 also.

Look at resistance measurement now. For this explanation, refer to the complete circuit diagram. As before, R1, LED1, R2 and ZD2 play no part here.

When PB2 is pressed, power is supplied to IC1 via D2. Some current is supplied to the resistive divider network, R9-10-11-12, by R8. This establishes a different set of voltages on the three comparator inputs. Pin 6, IC1b will now have about 3.8 V on it, pin 9, IC1c about 3 V on it and pin 12, IC1d about 1.3 V on it.


When the leads are connected to a resistance, current will be supplied to the resistance via D1 and R5. Say the resistance is 100 ohms. About 1.8 mA will be driven through it because there is about 8.5 V on the cathode of D1 and 8.5 divided by 4800 ohms gives about 1.8 mA. Thus, there will be a voltage drop across the 100 ohms of resistance of about 0.18 V. About 0.09 volts will appear on pin 3, IC1a. The output of IC1a will drive the inverting input of IC1d to about 0.9 V which is less than the 1.2 V on IC1d's non-inverting input. Thus the output of IC1d will be high, lighting LED4. If the resistance across the input is say 180 ohms, the voltage across the input leads will be about 0.32 V. About 0.16 V appears on pin 3, IC1a and 1.5 V on pin 13, IC1d. The output of IC1d will therefore go low, and LED4 will not light.

If the resistance across the input terminals

is between 150 ohms and 10k, say 5000 ohms or so, then the voltage across it will be about 4 V. The voltage on pin 10, IC1c will be about 2 V, which is less than that on pin 9 and the output of IC1c will be low and LED3 will be unlit. If the resistance across the input leads is about 15k, say (such as a spark plug suppressor resistor), then the voltage across the input will be about 6.4 V and the voltage presented to pin 10, IC1c will be about 3.2 V. This is above the 3 V on pin 9 and the output will thus go high, turning on LED3.

If the resistance across the input leads is about 50k, then the voltage across the input will be about 7.8 V. The voltage on pin 5, IC1b will be about 3.9 V and the output of IC1b will therefore be high, turning LED2 on. Note that LED3 will also be on as the voltage on pin 10, IC1c is above that on pin 9 and IC1c's output will be high also. Thus, for all resistances above 50k (including an open circuit) LED2 and LED3 will light.

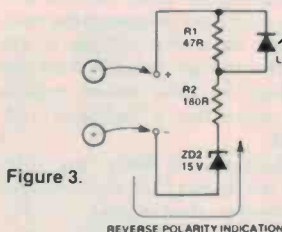
Followed that so far? Alright, let's look at the reverse polarity indication. The relevant portion of the circuit is shown in Figure 3.



If the input leads are transposed while trying to measure voltage, ZD2 will conduct as a diode in the forward direction (as shown by the arrow), passing current through LED1, which

will turn on. It will also pass some current through R1, but that's immaterial. R1 is there so that current can pass to RV1 when the leads are correctly connected, otherwise no current would pass through LED1 as it would appear as a reverse-biased diode.

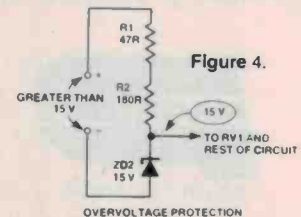If you reverse the input leads while attempting to measure voltage drop, LED1 will only come on if the voltage drop is above about 1.3 V or so. Thus, it is important to watch lead polarity when measuring voltage drop in cables.



Overvoltage protection is provided by ZD2. Why have it? Well, if a battery cable comes adrift and you're attempting to measure voltages while the motor is running the generator/alternator can quite easily deliver outputs of 20 V or so. This can possibly destroy the LM324. In addition, it is not unusual to get inductively-produced voltage 'spikes' on the supply lines in a vehicle, which can also destroy the IC. If a voltage of greater than 15 V appears on the input leads to the Auto Tester, ZD2 will ensure that the voltage delivered to the LM324 does not exceed 15 V.

The various voltages and resistances given here can vary by +/- 10% or so without grossly affecting your interpretation of readings. What you are after, after all, is 'ballpark' measurements which will indicate if all is well, or not.

Beeforth On Oscilloscopes



If you have anything to do with electronics then I bet you can't think of many jobs where an oscilloscope isn't useful. I guess it all comes about from the old adage 'a picture is worth a thousand words'. Now, in less than a thousand words, I'll put you in the picture regarding TRIO's CS-1560All oscilloscope.

The 1560All is a dual trace, 15MHz, honest-to-goodness value for dollar instrument. It is well suited to industrial applications, TV servicing, production line testing, educational or hobby work. It is rugged, reliable, easy to use and very portable. Vertical sensitivity is good without sacrificing large signal input capability. Sweep rates are from a high 0.5 μ S to 0.5S per division and a high persistence P7 Phosphor is now available as an option to make full use of the slowest ranges.

Triggering can be normal or via a video sync separator and has to be the best in any low-cost oscilloscope ever made. How often have you used a big name, high performance oscilloscope for routine work and been driven mad by the constant fiddling needed to maintain a stable triggered display particularly when the input is variable. With one wave of a CS-1560All the problem vanishes. Up to its rated 3db point of 15MHz it will produce a locked display with only 0.2 of a division deflection amplitude. At 20MHz it requires only 0.3 of a division to lock and at 25MHz, 0.7 of a division. That is real triggering!


Along with the rest of TRIO's range, this instrument is slanted toward useability, the kind of convenience and practicability that makes you reach past the 'Gee wizz technoscope' to grab the little TRIO with the sharp, stable, bright blue trace that shows the whole picture quicker than I can tell it.

The best way to see why I'm so keen on the CS-1560All is to check it out for yourself at any Parameters location or stockist right throughout Australia.




Trade Enquiries: Sydney (02) 439 3288
Melbourne (03) 580 7444

Adelaide:	PROTRONICS TRIO ELECTRIX K. D. FISHER & CO.	(08) 212 3111 (08) 51 6718 (08) 277 3288
Brisbane:	ST. LUCIA ELECTRONICS	(07) 52 3547
Canberra:	GEORGE BROWN & CO. ORTEX	(062) 80 4355 (062) 82 4995
Hobart:	IMBROS GEORGE HARVEY ELECTRIC	(002) 34 2233
Launceston:	GEORGE HARVEY ELECTRIC	(003) 31 6533
Melbourne:	RADIO PARTS GROUP GEORGE BROWN & CO. ELLISTRONICS	(03) 329 7888 (03) 419 3355 (03) 602 3282
Newcastle:	D. G. E. SYSTEMS GEORGE BROWN (NEWCASTLE)	(049) 69 6399 (09) 325 5277 (09) 362 1044
Perth:	W. J. MONCREIFF CO. PROTRONICS	(079) 2 1058 (02) 519 5855
Rockhampton:	PURELY ELECTRONICS	(02) 29 6601
Sydney:	GEORGE BROWN & CO. DAVID REID ELECTRONICS	(02) 211 0191 (077) 79 8600
Townsville:	NORTEK	(042) 29 1455
Wollongong:	MACELEC	

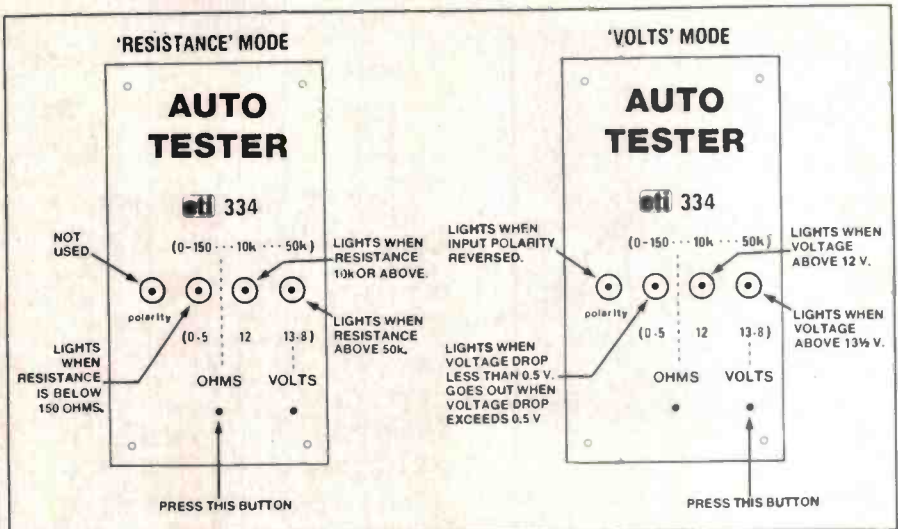

Now you're ready for testing. But first, check *everything* carefully. See that the IC, all diodes and LEDs are correctly orientated, according to the component overlay.

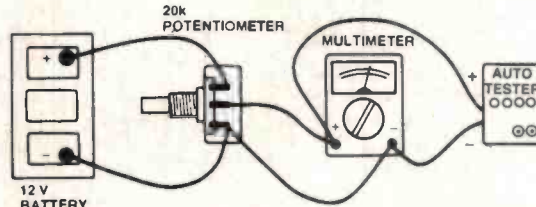Setting 7.5 V (within ± 0.3 V) across ZD1 when you press the VOLTS button. Also check the voltages on pins 6, 9 and 12 of IC1 when you press the VOLTS button and see



Calibration. Test setup for calibrating the Auto Tester.

Testing the unit

Fit a 9 V, No. 216 battery. Short the input clips together and press the VOLTS button. The 0.5 V LED should come on. If not, check component orientations, then resistor values. Fix any faults. Once you have that corrected, try again. When you get the 0.5 V LED to light, unclip the input leads and it should go out.

To calibrate the unit, you'll need to get hold of a multimeter, a well charged 12 V battery and a 20k potentiometer. Hookup the circuit shown here and adjust the potentiometer to give a 12 V reading on the multimeter. Press the VOLTS button and adjust RV1 so that the '12 V' LED just lights. Then, reset the potentiometer to get a 0.5 V reading, or a little more, on the multimeter. The '0.5 V' LED should just light. If it doesn't light, vary the potentiometer slightly until it lights. If the '0.5 V' LED lights when the multimeter reads more than ± 0.1 V from 0.5 V, then you may have to change the value of R12. Increase it if the voltage is low, decrease it if the voltage is high. Just take the next highest or next lowest resistor value, you're only after a 'ballpark' indication, after all.

Set the potentiometer fully 'up' (fully clockwise). If the battery is well charged, then the multimeter should read 13.5 V or above and the '13.8 V' LED should turn on, along with the '12 V' LED. Now, reverse the Auto Tester input leads. The POLARITY LED should come on.

If you can't get the proper indications, check with the multimeter that you are


they are close to those given in the How It Works.

If all is well, proceed with testing the OHMS mode. Disconnect the 12 V battery. Set the multimeter to read resistance (should be the X1 scale). Adjust the potentiometer until the multimeter reads about 100 ohms. Press the OHMS button and the '0-150' LED should come on. Turn the potentiometer until that LED goes out and keep turning till the '10k' LED turns on. It should turn on when the multimeter reads somewhere in the vicinity of 10k.

With the Auto Tester leads open circuit, both the '10k' and '50k' LEDs should turn on.

You are now ready for use. Happy fault-finding!


Full size pc board artwork.

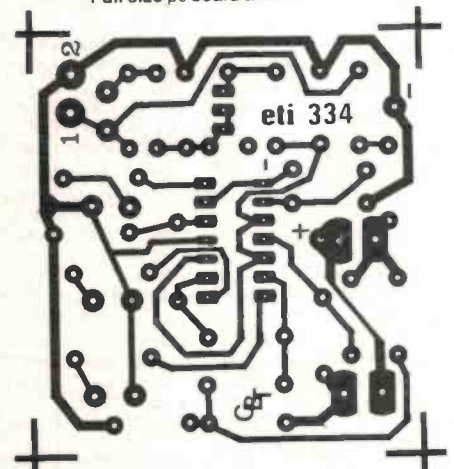

RITRONICS WHOLESALE PTY LTD

425 HIGH ST, NORTHCOTE, VICTORIA 3070
(03) 489 7099 (03) 481 1923

"BIG BOARD II"

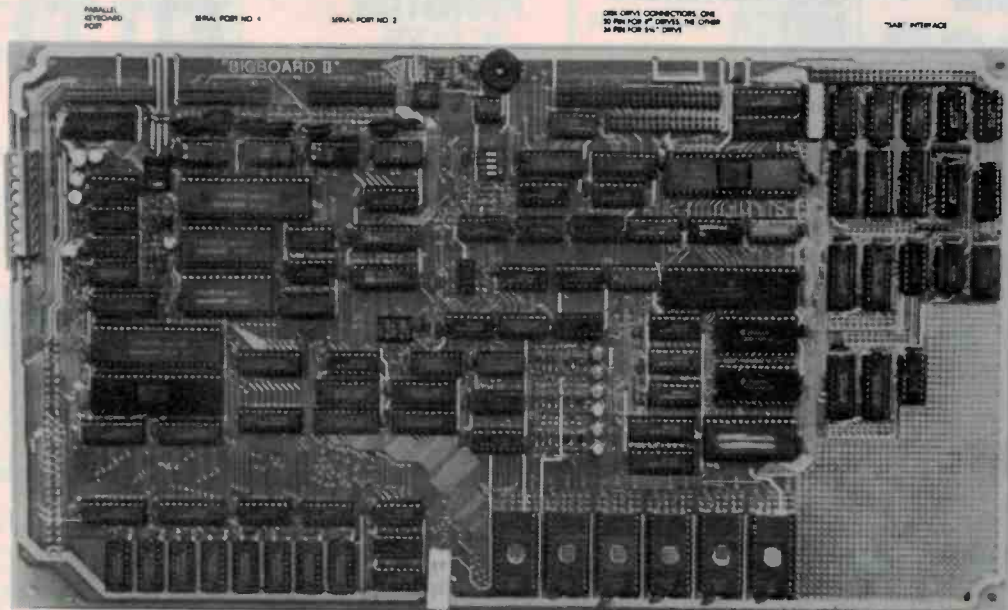

STD
Bus
Connector

Prototyping
Area

Jim Ferguson, the designer of the "Big Board" distributed by Digital Research: Computers, has produced a stunning new computer that we will begin shipping in November called "Big Board II", it has the following features:

4 MHz Z80 — CPU AND PERIPHERAL CHIPS

The Ferguson computer runs at 4 MHz. Its monitor code is lean, uses Mode 2 interrupts, and makes good use of the Z80-A DMA chip.

64K DYNAMIC RAM + 4K STATIC CRT RAM + 24K E(E)PROM OR STATIC RAM

"Big Board II" has the three memory banks. The first memory bank has eight 4164 RAMs that provide 60K of user space and 4K of monitor space. The second memory bank has two 2Kx8 SRAMs for the memory-mapped CRT display and space for six 2732 As, 2Kx8 static RAMs, or pin-compatible E(E)PROMs. The third memory bank is for RAM or ROM added to the board via the STD bus. Whether bought as a bare board, a full kit, or assembled and tested, it comes with a 200 NS2732A EPROM containing the monitor.

MULTIPLE-DENSITY CONTROLLER FOR SS/D5 FLOPPY DISKS

The new Ferguson single-board computer has a multiple-density disk controller. It can use 1793, 1797, or 8877 controller chips since it generated the signal with TTL parts. The board has two connectors for disk signal with 34 pins for 5.25" drives, the other with 50 pins 8" drives.

VASTLY IMPROVED CRT DISPLAY

The new Ferguson SBC uses a 6845s CRT controller and 8002 Video Attributed controller to produce a display that will rival the display of quality terminals. Characters are formed by a 5x7 dot matrix on 15.75 KHz monitors and 7x9 dot matrix on 18.60 KHz monitors. The display is user programmable with the default display 24 lines of 80 characters.

STD BUS CONNECTOR

The Ferguson computer brings its bus signals to a convenient place on the PC board where users can solder an DSTD, bus cards can be plugged directly into it, and it can as well be connected by bus cable to industry-standard card cages.

DMA

The new Ferguson computer has a Z80-A DMA chip that will allow byte-wise data transfers at 500K bytes per second and bit serial transfers via the Z80-A S10 at 880K bytes per second with serial processor overhead, though the monitor for the new computer uses the DMA chip mainly for transferring data to and from disk, the chip can readily be used for other things since its "wait/ready" pin can be connected under software control to some half a dozen signal lines. When a hard-disk subsystem is connected to the "Big Board II" via its "SASI" interface, the DMA chip makes breathtaking disk performance possible.

"SASI" INTERFACE FOR WINCHESTER DISKS

The "Big Board II" implements the Host portion of the "Shugart Associates Systems Interface". Adding a Winchester disk drive is no harder than attaching a floppy-disk drive. A user simply 1: Runs a 50-conductor ribbon cable from a header on the board to any of several inexpensive controller cards for Winchester drives that implement the controller portion of the SASI Interface. 2: Cables the controller to an appropriate drive, and 3: Provides power for the controller-card and drive. Since our CBIOS contains code for communication with hard-disk, that's all a user has to do to add a Winchester to a system!

A Z80-A S10/0 = TWO ASYNCHRONOUS/SYNCHRONOUS SERIAL PORTS

A PARALLEL KEYBOARD PORT = FOUR OTHER PARALLEL PORTS USER I/O

The new Ferguson single-board computer has one parallel port for an ASCII keyboard and four others for user-defined I/O. When the computer is powered-up or reset, the monitor looks for a carriage-return at the keyboard and serial ports. If the first carriage-return the monitor gets comes from the parallel keyboard, the monitor uses the board's video display circuitry to communicate with the user via a CRT. If the first carriage-return is typed at an ASCII terminal attached to a serial port, the monitor autabauds and makes the terminal the system console.

TWO Z80-A CTCs = EIGHT PROGRAMMABLE COUNTERS/TIMERS

The new Ferguson computer has two Z80-A CTCs. One is used to clock data into and out of the Z80-A S10/0, while the other is for systems and application use.

PROM PROGRAMMING CIRCUITRY AND SOFTWARE

The new Ferguson SBC has circuitry and drivers for programming 2716s, 2732(A)s, or pin-compatible (E)EPROMs.

CP/M

CP/M with Russell Smith's CBIOS for the new Ferguson computer is available for \$190. The CBIOS is available separately for \$39.50. Actual board size: 39.6cm x 22.2cm.

Pricing and Availability:

Availability: We should start shipping the second week in November. In single quantities, full kits cost \$750.00 + tax, and A&T'd computers cost \$895. There are attractive discounts that range to 35% for OEM's and dealers. For details about them please call Rod Irving on (03) 489 7099. ie: 3 Ferguson II "Big Board" are less 20% off the one-off price, hard disks disk controllers, boxes and power supply to suit both 8" & 5 1/4" systems will be available.

IT PAYS TO BUY YO

WHY? BECAUSE JAYCAR KITS COST NO MORE & ARE BETTER QUALITY

Digital Thermometer



\$69
EA282

Read the temperature in your room (or outside) from 0 degrees C to 100 degrees C in fact to within 0.1 degree C. Fantastic resolution on a bright easy-to-read display. Includes case.

DIGITAL CAPACITANCE METER

Ref: EA 3/82
This kit once again uses the amazing DPM 200 LCD /driver module. Capable of measuring capacitance from 1pF to 19,99uF. It is a must in every workshop or lab.



\$69

HEART RATE MONITOR

Ref: EA 7/82
WAS \$79 SAVE \$10



Now **\$69**
This unit enables you to measure your own pulse instantly and accurately. It is light enough even for joggers to carry. A must for people who may have heart problems. Complete kit including LCD Display.

MAINS FILTER

250V AC @ 3A.

Includes data sheet. The most economical mains filter available!!



\$14.50

500MHz Digital Frequency Period Meter

REF: EA Dec '81 - Feb '82



ONLY **\$119**

Other people may appear to be selling this kit for less. But you GET less!!! Exclusive Jaycar features:
* Heavy gauge front panel. Pre-punched and silkscreened. (NOT Scotchcal). * Low aging rate 10,000MHz crystal * Quality IC sockets provided (A MUST) * All metal film resistors used (1% 50ppm) * Thermalloy heatsink for +5V reg. Beware of advertised units that do not conform to the original design. They may have inferior performance.

EXCLUSIVE

Gold plated BNC Input Connectors
500MHz option only \$26 extra
50MHz version \$119
Tilting bail to suit ONLY \$4.95

Function Generator

FREE! TILTING BAIL WORTH \$4.95 Included



Ref: EA April 1982

\$99

"Pigeon Pair" companion to the new 500MHz DFM. Low distortion generator of sine, square and triangular waveforms. From below 20Hz to over 160kHz. Inbuilt 4 digit frequency counter in de-luxe Pac-Tec case. Only \$85
JAYCAR EXCLUSIVE - 1% 50ppm metal film resistors used for stability

STEREO STEREO STEREO STEREO

Synthesiser


Creates a very realistic stereo sound from mono sources i.e. AM tuners, TV or video units Very easy to build and comes complete.

ONLY **\$49.50**



COMPLETE

Ref: EA September 1982

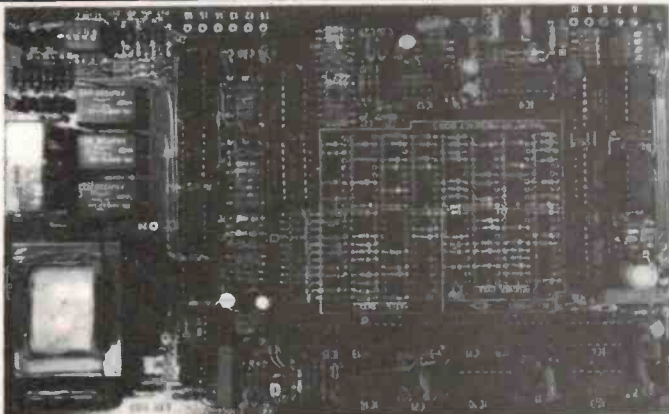

ETI 644 direct connect modem

Ref: ETI October 1982
SHORTFORM KIT

\$169

FULL KIT

\$189 NEW

Two models (i) Short form which contains ALL PCB components as specified by ETI (BEWARE!!). The genuine ETI PCB with plated-thru holes, solder mask and component overlay is supplied. We also supply at NO EXTRA CHARGE a full set of quality I.C. sockets. A must with plated-thru PCB's Remember this when making comparisons. (ii) Full kit. Includes: all of above plus 12V plugpack, case, front panel, switch and LED bezel and Cannon DB-25 RS-232 connector. Makes a complete stand alone modem.

* Capable of a range of Answer/Originate operating modes * Selectable Baud rate * Software controlled * Uses new patented technique * More reliable and faster than most acoustic modems.

ARLEC TRANSFORMER AS USED IN THIS PROJECT \$22.00

Lyrebird Piano Kit NEW LOW PRICE

GREAT NEW FEATURES!!

- FREE! A stand (like the one illustrated but not exactly the same). Worth around \$50 but yours at no extra charge with each 73 or 88 note kit.
- FREE! A soldering iron (worth around \$19). Yours to keep to give years of faithful service after you have completed your Lyrebird. (88 note only)
- FREE! A 200g roll of solder. You will need some to build the Lyrebird but there will be plenty left over for other projects. (73 & 88 note versions).
- FREE! Quality IC sockets provided in both kits.

Ref: EA 11/81-1/82
7 1/2 OCTAVE (88 NOTE) VERSION
\$589

UR KITS FROM US

WHY? BECAUSE JAYCAR KITS COST NO MORE & ARE BETTER QUALITY

NEW

EA FUZZ BOX KIT

Ref: EA January 1981
Economical way to get great guitar sounds! The Jaycar kit contains a heavy duty foot-switch and diecast box. All components only

\$19.50

Staggering value



'Power UP' ONLY \$39.50

Ref: EA 11/82


What will they think of next???? Sensational project that detects the current drawn by one appliance to switch on up to 4 others - AUTOMATICALLY!

Great for computers, component HI Fi etc. when you have to normally switch on several items in a system. Will switch total load of 240V 10A.

Complete kit including outlets, box, mains relay etc. ONLY \$39.50

EA CAR COMPUTER KIT

Ref: August EA 1982

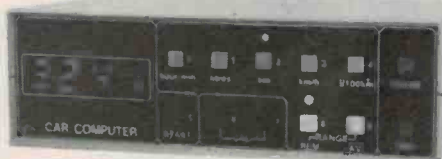

BUY THE WHOLE KIT (inc. Fuel & Speed Sensors) FOR ONLY \$159.00!!

WE TOO have the genuine Moray fuel sensor. We buy it from the same factory as Dick Smith!! We also have an EA APPROVED Speedo Cable Sensor. The speedo cable sensor gives better results at very low speed.

PRICING INFORMATION: ALL ELECTRONICS including both PCB's plated through, programmed EPROM, 1% metal resistors, and other high spec. components. You also get a choice of either tailshaft or speedo cable type speed sensor (please specify) - ONLY \$99.50 Pre-punched genuine American PACTEC case (as used by EA) and not a Hong Kong copy, with special silk-screened front panel and multi-way connector ONLY \$39.50

Tailshaft Speed Sensor ONLY \$14.50

Speedo Cable Sensor ONLY \$29.50

'T' Piece Jaycar exclusive ONLY \$3.95

Genuine Moray Fuel Flow Sensor ONLY \$49.50

NEW KITS NEW KITS NEW KITS NEW KITS TRANSISTOR ASSISTED IGNITION

Ref: EA January 1983. Latest version of this fantastically popular kit!! The Jaycar kit comes with a genuine DIE CAST box - as used in the EA prototype. Beware of others that use flimsy sheet metal boxes!! Ask us about the OPTO option.

ONLY \$35.00 COMPLETE!!!

LED HEAD ☆☆☆☆☆☆☆☆☆

Ref: EA January 1983.



Wire your head for light!! Complete kit (sweatband extra)

ONLY \$9.95

MASSIVE LCD DISPLAY SELLOUT!!! ☆☆☆☆☆

Jaycar has purchased a massive range (probably Australia's largest) of LCD Displays. Clock displays, multi-digit, multi-function, alphanumeric and dot matrix included!! We are liquidating these to pay for new lines. Advertising deadlines prevent us from going into further details. If you want to know more (before our Feb ad) send SAE for a list (with quantities & prices).

LCD DISPLAYS FROM \$1.00 EACH!!!

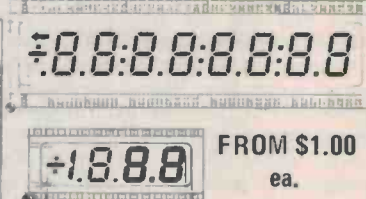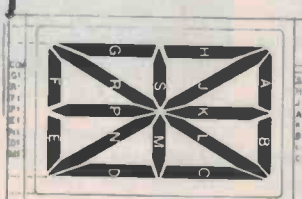

FROM \$1.00 ea.

NEW



DIGITAL pH METER KIT

At last a true scientific instrument for a fraction of the cost of commercial units. Great for checking swimming pools, fish tanks and countless other uses.

The Jaycar kit comes complete with DPM-05 display, ABS case and all components as specified by EA.

'Ionode' probe to suit only \$69

Ref: EA December 1982

ONLY \$69.00

syntom

As used by Warren Cann of 'Ultravox'

Original design from the UK magazine "Electronics and Music Maker" April 1981. Self-contained unit produces a variety of fixed and falling pitch effects. Trigger by tapping the unit itself or by striking a drum to which the unit is attached. The Jaycar "SYNTOM" comes complete with high quality pre-drilled moulded ABS box 152 x 80 x 67mm with professional silk-screened front panel.

FEATURES: Decay from less than 0.1 second to several seconds, pitch control, sweep control and volume on/off.



ONLY \$36.50

\$6 OCTAVE 475



NEW LOW PRICE!! Because we are shipping keyboards and other expensive components in bulk due to high demand, we can pass savings on to YOU.

You can now have a magnificent "Lyrebird" 6 octave touch sensitive piano now for only \$475!! That's a staggering \$50 off the old price. REMEMBER!! THE LYREBIRD OUTPERFORMS READY BUILT PIANOS COSTING UP TO THOUSANDS OF DOLLARS MORE. WHY PAY MORE WHEN YOUR CONSTRUCTION KNOWLEDGE CAN SAVE YOU A FORTUNE?

Jaycar NUMBER 1 FOR KITS

125 York Street, Sydney 2000
Phone: 264 6688 Telex: 72293

"Nevilles Corner"
Cnr. Carlingford & Pennant Hills Road,
Carlingford
Phone: 872 4422

Mail Orders To: Box K-39 Haymarket
Sydney 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40)
\$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60)
\$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm

MAIL ORDER BY BANKCARD VIA YOUR PHONE



YOU CAN PHONE CARLINGFORD ON 872 4444 AS WELL!

Model railway points controller and indicators

This project employs a capacitive discharge type power supply to drive the solenoid actuators in model railway points switchers. An add-on indicator unit can be used in conjunction with it to show which way points are switched at any time.


Jonathan Scott

THE IDEA of using a capacitive discharge supply to drive the solenoids in model railway points switchers is not new. Indeed, you can buy these at hobby shops for \$20 or so, if you are not inclined to build one for yourself. However, this project incorporates refinements you may not have seen, along with a system of indicating the state of the points modelled after the fashion of the 'professional' signal box lighted map.

The capacitive discharge supplies bought 'over the counter' generally charge a capacitor of one to two thousand microfarads via a current limiting resistor from a rectifier and an ac source. This is quite adequate, but can be refined. If you charge the capacitor from a constant current source, it charges somewhat faster and one can provide an 'unready' indication while it's charging. The little extra speed one gains in charging is handy as several points often need to be changed in a short space of time and one's fingers dance from button to button when doing so.

With either system, the current limiting arrangement protects the solenoids against burnout if the supply happens to be accidentally connected indefinitely. The simpler system almost invariably incinerates something if you get a short somewhere.

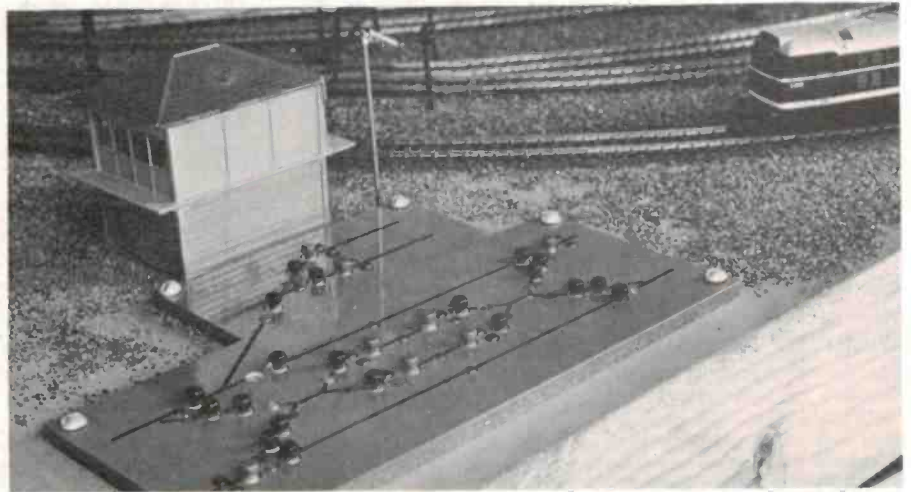The idea behind the capacitive discharge method is simply that the point changes in the first hundred milliseconds or so, any other power delivered is wasted. The high momen-



Signal map. This shows a view of one of my signal maps with the points pushbuttons and indicator LEDs installed.

much less than the current required to actuate the solenoid. Thus, the solenoid remains cool even if connected (by some accident or other) indefinitely, avoiding burnout of the solenoid.

The outline of a capacitive discharge supply is shown in Figure 1, along with the outline of a 'remote point indicator', or 'remoter'.

The remoter is simply a 'memory' circuit which records which way the point was last changed. I used a simple flip-flop for this. Two LEDs or lamps are used to indicate the point's condition. These may be built into a signal map panel. This is basically just a line diagram of a track layout, or part thereof, with lights and switches in the symbolic positions of the actual points on the track layout. Train signal lights are also usually included on the map along with train position sensors, if used.

There is, of course, no need to have remoters. They are purely conveniences, rather than necessary functional items. Remoters are primarily important if you wish to have a layout which is as much like the 'real' thing as possible. However, for the few dollars or so extra cost each, they add a very pleasing touch of realism.

You can have any number of points in your layout and you'll only need one capacitive discharge supply unit. The one described can easily drive three points simultaneously if you need to operate some points together. One remoter is needed for each set of points.

Construction

Construction is relatively brief. The only part we can really cover here is the assembly of the pc boards and with the usual exhortation "assemble the boards according to the overlays", it's nearly all over!

There are two pc boards: ETI-1510a is the capacitive discharge supply, and ETI-1510b is for the remoters. Let us take the supply board first. It is easiest to mount the diodes and resistors first, then Q1 and IC1, followed by the capacitors. Take care with the orientation of the diodes and transistors as well as C1 and C2. Note that Q1 and IC1 should have heatsinks attached. You can make these from a scrap of aluminium; each heatsink should be at least 25 sq. cm in area. They can be bolted straight to the metal face of each device, but don't forget to smear on thermal compound first.

You may or may not wish to mount the 'charging' LED (LED1 on ETI-1510a) off the

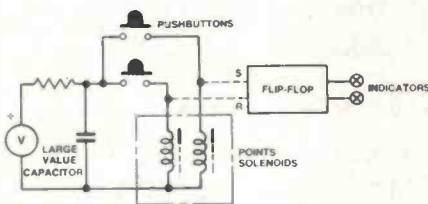


Figure 1. The controller/indicators scheme.

tary current capability of a capacitor means that the solenoid always moves quickly. When you connect the charged capacitor to the points solenoid it will deliver a very high current which rapidly subsides to nothing or, at worst, the charge current which can be

PARTS LIST — ETI-1510a

Resistors all ½ W, 5%
 R1 2R7
 R2 1k2

Capacitors
 C1 1000u/25 V RB electro..
 C2 3300u/25 V axial electro..
 C3 10u/6 V tant.

Semiconductors
 D1-D6 1N4001/2/3/4 etc
 LED1 TIL220R red LED
 IC1 7805
 Q1 BD140

Miscellaneous
 ETI-1510a pc board; hookup wire, etc.

Price estimate \$8 — \$10

PARTS LIST — ETI-1510b


Resistors
 R1, R2 see text, circuit
 R3, R4 see text, circuit
 R5, R6 100k
 R7, 8, 9, 10 47k

Capacitors
 C1, C2 100n greencap

Semiconductors
 LED1 TIL220Y yellow LED
 LED2 TIL220G green LED
 Q1, Q2 BC549

Miscellaneous
 ETI-1510b pc board; hookup wire, etc.

Price estimate \$4 — \$5

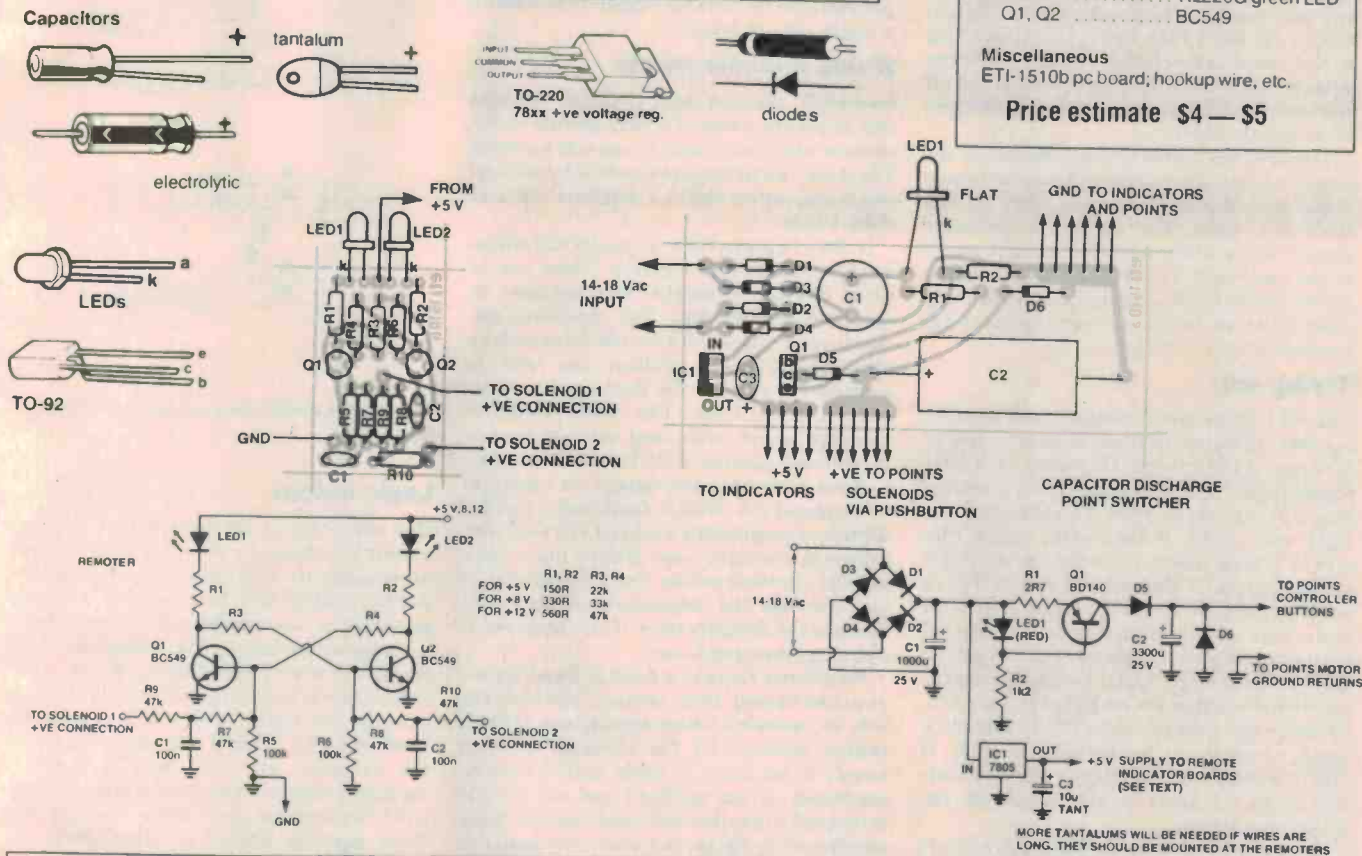

HOW IT WORKS — ETI-1510

There are two distinct parts to the project: the first is a capacitor discharge supply used to operate the point solenoids, the second is a remote indicator unit.

The capacitor discharge supply unit charges a capacitor which is then discharged into the point solenoid, which then operates the points. This unit is capable of changing one point every half second or so, and can power a large number of points together.

The remote indicator unit, or 'remoter', has the job of 'remembering' which way the point set was last switched and indicates the direction with a pair of LEDs mounted as part of a signal map.

Consider the capacitor discharge unit. Diodes D1-D4 rectify the 14-18 volt ac input to provide a dc supply. Capacitor C1 smooths this for IC1 which regulates the voltage supply for the remoters. Up to fifteen remoters can be run off the output of IC1.

Transistor Q1 and surrounding components form a current source which charges C2 via D5. LED1 forms the voltage reference and doubles as an indicator which illuminates for the time when the capacitor is being recharged

after use. Diode D5 prevents reverse biasing of the transistor when C2 is charged and C1 is below the peak input voltage value.

Using a current source for the charging element removes the need for a large series resistor and speeds up recharging as well as making the system short circuit proof.

Diode D6 is a "freewheel" diode which prevents possible reversing of the polarisation of C2 by the flyback voltage of a solenoid.

When a button is pressed, making a connection from the output of the unit to a point solenoid, C2 discharges into the coil, changing the point. After C2 is discharged the only current flowing through the coil is the recharge current of about 375 mA. When the button isolates the point solenoid, the current is free to charge C2, which takes about quarter of a second. When C2 reaches the input voltage, Q1 saturates, LED1 goes out, and the unit is ready to operate again.

The 375 mA charging current is insufficient to harm a solenoid if it is left connected for any reason. As the controller can withstand indefinite shorting itself, the whole system is protected against abuse and failure of

switches, etc.

Each remoter consists of an R/S type flip-flop formed by two transistors. Assume initially that Q1 is on, and Q2 off. The collector current of Q1, via R1, illuminates LED1, and the saturation collector voltage of Q1 ensures that Q2 remains off.

When a solenoid is activated by the discharge of the capacitor, a large voltage spike appears across it. Suppose that the voltage across the coil appears on R10. Capacitor C2 filters out brief induced spikes, so that no signal other than the correct one can affect the circuit. When the longer duration discharge pulse appears on R10 some current reaches the base of Q2, turning it on. This turns on LED2 via R2 and removes the base drive from Q1, and it turns off. Thus LED1 goes out, and the collector voltage on Q1 keeps Q2 turned on via R3. The reverse operation occurs when a pulse appears on R9.

Transistors are used rather than an IC as they have a higher output drive, are less intolerant of supply voltages and ICs normally have more than one flip-flop in each package and you waste the rest.

board; like on the front panel of your controller, for example. This is a good idea if other people are using your layout as it helps them allow for the necessary delay between point switching operations of about half a second or so. Make sure you wire in LED1 the right way round.

The remoter board (ETI-1510b) is quite straightforward. Best way to tackle this one is to mount the resistors and capacitors first. Then mount the two transistors making sure you get them the right way round. Finally, mount the two LEDs. Leave their leads long as the board can actually 'hang' from them. Alternatively, the LEDs may be mounted off the board and the board mounted somewhere conveniently nearby.

I secured my boards to the underside of the model railway baseboard with staples from a staple gun holding down the wires to and from the units. The capacitive discharge supply was actually mounted at right angles to the baseboard. The remoters were held flat on the baseboard by stapling the wires fairly close to the pc board. This arrangement has proved entirely satisfactory.

Trying out

The ETI-1510a board (supply) can be tried out first. Hook up the input to an ac source of between 14 and 18 volts. On switch-on, LED1 should light then extinguish about a second later. If not, check that it's connected the right way round. If that's OK, check that you're getting about 1/2 times the ac input voltage across C1 (between 20 and 25 Vdc or so should appear across it). If not, switch off and check that diodes D1 to D4 are all correctly oriented. Correct any faults as you go. When you've got LED1 to light on switch-on, then check that the output of IC1 is +5 V. Measure the voltage across C2. It should be equal, or nearly so, to the voltage on Q1. If LED1 won't go out, or there's less than one volt across C2, odds-on you've got D6 the wrong way round.

Temporarily hook up the supply to a points solenoid and see that it operates as expected.

You can check out the remoter(s) by temporarily connecting it to the +5 V from the supply board. One or other of the LEDs will light. Say LED2 on the remoter lights. Connect the 'SOLENOID 1' input momentarily to the positive terminal of C2 on the

supply. LED1 should light and LED2 should extinguish. If not, check transistor and LED orientations. If this works, then temporarily connect the 'SOLENOID 2' input to the positive terminal of C2 and the LEDs should swap over.

When wiring in the remoters, it may be necessary to add some extra supply bypassing to prevent random toggling of the LED indicators. Add a tantalum with a value between 4u7 and 10u. You'll need one of these per extra metre of cable length if the cable is a metre long or longer.

Wiring multiple points

Invariably, you will want to install multiple sets of points, some of which operate alone, some of which may need to operate together. There are two wiring options which exist and which may prove useful if you have not seen them before.

It often happens that two points will always need to be switched together. These can be wired directly in parallel and operated by only two pushbuttons. The capacitive discharge supply described should drive such an arrangement easily, without the need to increase the value of the discharge capacitor (C2 on ETI-1510a). The 3300u capacitor specified would easily and reliably operate three parallel points in my layout. If you need to drive more, then the capacitor's value can be increased (try 4700u). Conversely, you can decrease the capacitor's value if you find your solenoids are light ones and/or don't have parallel operated points. Don't forget that, if you increase the capacitor's value, you'll increase the charging time. If you decrease it, charging time speeds up.

Sometimes there is a need to have one set of points 'slaved' from another, but have the first set operated independently also. This is readily achieved by the inclusion of some simple diode logic. A diode with its anode connected to one solenoid and its cathode connected to another will leave the first point unaffected by the second when switched, but will ensure that when the first is switched, the second also operates. This can be implemented with ordinary silicon rectifier diodes such as EM401s, 1N4001s, etc.

The various wiring arrangements are illustrated in Figure 2.

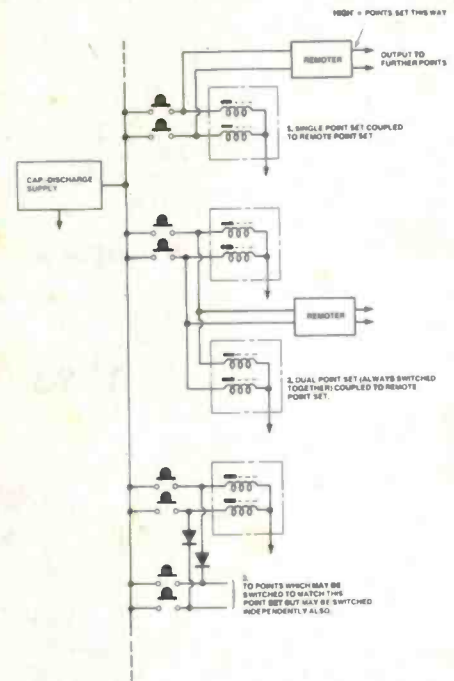




Figure 2. Showing the three fundamental schemes for wiring points.

Logic output

One advantage of remoters is that they can output the state of a point set as logic levels for feeding into a digital system or computer. Astute readers will have noticed a certain provision in these model railway projects for a computer interface. The collectors of the transistors in each remoter circuit give a 'low' voltage when the respective side is that one carrying the traffic. For a 5 V supply, the levels are TTL. This is the main reason that the remoters are run from a carefully regulated supply, apart from a desire to keep LED illumination level fairly constant. For those needing CMOS or other levels the resistor values for 8 V and 12 V supplies are shown on the diagrams. (R1-2 and R3-4 will vary.)

Coupled with position sensing systems, the remoters can allow a simple anticrash logic system to be hardware implemented!

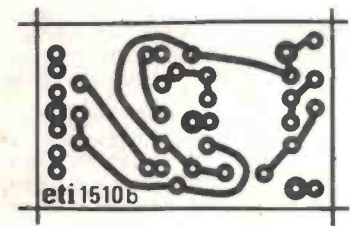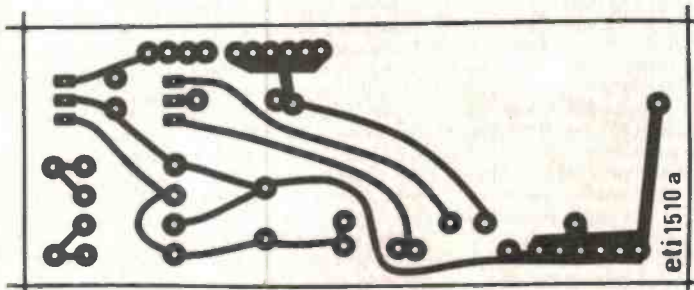Printed circuits. Full size artwork of the two pc boards.



ETI BOOK SALES

Save time and trouble with mail order. Just fill out the coupon on page 58.

electronics textbooks

ELECTRONICS — IT'S EASY VOL. 1 \$5.95
Meters, resistance, capacitance and inductance, emitter followers, op amps, power supplies and electronic filters.

ELECTRONICS — IT'S EASY VOL. 1 \$12.95
Same content in a hard-cover form.

ELECTRONICS — IT'S EASY VOL. 2 \$5.95
Digital sub-systems counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes.

ELECTRONICS — IT'S EASY VOL. 2 \$12.95
Same content in a hard-cover form.

ELEMENTS OF ELECTRONICS

This series is an introduction to modern electronics. All the maths is taught as the reader progresses. The course concentrates on the understanding of concepts central to electronics, rather than digressing over the whole field. The author anticipates where difficulties lie and guides the reader through them.

BOOK 1
BP62 \$7.52
All fundamental theory necessary to full understanding of simple electronic circuits and components.

BOOK 2
BP63 \$7.52
Alternating current theory.

BOOK 3
BP64 \$7.52
Semiconductors technology leading to transistors and ICs.

BOOK 4
BP77 \$9.76
Microprocessing systems and circuits.

BOOK 5
BP89 \$9.76
Communications.

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST
2288 \$4.32
This book supplies the electronics hobbyist with the background knowledge which will exactly suit their specific requirements. Minimum maths.

BEGINNER'S GUIDE TO DIGITAL ELECTRONICS
BP61 \$3.36
Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

A MICROPROCESSOR PRIMER
BP72 \$5.92
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

reference and data handbooks

AUDIO CYCLOPEAIA
20675P \$66.00

A complete, in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. Over 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

REFERENCE DATA FOR RADIO ENGINEERS
21218P \$21.95

The largest and most comprehensive collection of equations, graphs, tables, and other reference data needed in general radio engineering and design. Contains hundreds of charts, monographs, diagrams, curves, tables and illustrations.

TUBE SUBSTITUTION HANDBOOK
21746P \$8.75

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

CONTEMPORARY MATHEMATICS FOR ELECTRONICS
70274P \$29.75

This book is split into three sections. Direct current maths introduces the student to the calculator, fractions and dimensional analysis. Alternating current maths covers phasors, quadratics and RMS in both sine and digital waveforms. Active device maths introduces modern systems and boolean.

AUSTRALIAN MICROCOMPUTER HANDBOOK
72505 NOW \$15.00

Normally \$25.00. A detailed buyer's guide to micro-computer systems and application packages in commercial, industrial, scientific, educational and home/hobby areas.

TRANSISTOR SUBSTITUTION HANDBOOK
21515P \$8.75

17th edition — Accurate transistor substitution in a matter of seconds with this replacement listing of over 19 000 American and foreign bipolar transistors.

THE CP/M HANDBOOK WITH MP/M
88048A \$19.95

Shows you how to use CP/M (control program for microprocessors) and its resources. No prior knowledge of computers is assumed. CP/M is available on nearly all computers using the 8080, 8085 or Z80 microprocessors.

HANDBOOK OF ICS EQUIVALENTS AND SUBSTITUTES
202B \$5.76

Contains full interchangeability data on more than 9500 ICs with possible alternatives and equivalents shown. Covers many types of digital and linear ICs.

HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS
BP2 \$2.25

Equivalents book for amateurs and servicemen. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART
BP7 \$1.60

This large wall chart covers all colour codes in use throughout the world. For all radio and electronic components made in UK, USA, Europe and Japan.

FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

BP1 \$3.36
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in UK, Japan, USA, Germany, France, Europe, Hong Kong and includes types produced by more than 120 different manufacturers.

SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

BP14 \$5.92
Interchangeability data covers semiconductors manufactured all over the world. Immediate equivalents are shown and possible substitutes are included.

GIANT CHART — RADIO, ELECTRONICS, SEMI-CONDUCTORS & LOGIC SYMBOLS

BP27 \$1.92
Identify those symbols at a glance. A must for beginners and advanced enthusiasts alike. Professionals can always hide it in their desks!

RESISTOR SELECTION HANDBOOK

BP28 \$2.24
Shows how to combine two preferred values of resistor to obtain virtually any required value of resistance. Includes information about fixed resistors, standard ranges, colour codes and markings, power ratings and resistor calculations.

ELECTRONIC CALCULATOR USERS' HANDBOOK

BP33 \$5.12
Presents formulae, data, methods of calculation, conversion factors, etc, for use with the simplest or most sophisticated calculators. Includes the way to calculate using only a simple four-function calculator: trigonometric functions, hyperbolic functions, logarithms, square roots and powers.

DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS

BP40 \$12.32
Revised edition showing Japanese, American and European equivalents. Also shows pin connections of a popular user-orientated selection of digital ICs.

LINEAR EQUIVALENTS AND PIN CONNECTIONS

BP41 \$9.12
Shows equivalents and pin connections of a selection of popular linear ICs, with details of families, functions, country of origin and manufacture. Includes devices from Analog Devices, Advance Micro Devices, Fairchild, Harris, ITT, Motorola, Philips, RCA, Raytheon, Signetics, Sescocrem, SGS-ATES, Siemens, AEG-Telefunken, Teledyne, Texas Instruments.

PRACTICAL ELECTRONIC CALCULATIONS & FORMULAE

BP53 \$9.76
For the practical person's workbench. Bridges gap between technical theory and cut-and-dried methods which work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths avoided where possible.

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

BP85 \$9.76
Companion to BP1 and BP14 equivalents books, but contains a huge amount of information on modern transistors produced by over 100 manufacturers. Wherever possible, equivalents are subdivided into European, American and Japanese types. Also shown are the material type, polarity, manufacturer and indication of use or application.

HOW TO IDENTIFY UNMARKED ICS

BP101 \$2.46
This chart shows the reader how, with just a test-meter, to go about recording the particular 'signature' of an unmarked IC which should enable the IC to be identified with reference to manufacturers or other data.

electronics for beginners

BEGINNERS HANDBOOK OF IC PROJECTS

74286P \$19.25
The novice is guided in mastering the fundamentals of building, troubleshooting and testing electronic projects. In addition to many elementary projects, more advanced ones are included concerning bipolar integrated circuits and medium and large-scale integrated circuits.

HI-FI LOUDSPEAKER ENCLOSURES

205B \$3.36
Data for building corner reflex, bass reflex, exponential horn, folded horn, tuned port, Klipschorn labyrinth, tuned column, loaded port and multi speaker panoramics. Clear dimensioned diagrams included.

SOLID STATE NOVELTY PROJECTS

219B \$3.04
A number of novelty projects using modern ICs and transistors. Includes 'Optomin' — a musical instrument played by reflecting a light beam with your hand, water warbler for pot plants, music tone generator, LEDs and ladders game, touch switch, electronic roulette wheel, etc.

SOLID STATE SHORTWAVE RECEIVERS FOR BEGINNERS

222B \$4.32
Design and construction of several solid-state shortwave receivers giving high level of performance yet utilising relatively few inexpensive components.

BEGINNERS' GUIDE TO BUILDING ELECTRONIC PROJECTS

227B \$5.12
Enables total beginners to tackle electronic projects. Includes component identification, tools, soldering, building methods, cases, legends, etc. Practical basic projects are included.

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

228B \$4.32
This book supplies the electronics hobbyist with the background knowledge which will exactly suit their specific requirements. Minimum maths.

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

BP7 \$1.60
This large wall chart covers all colour codes in use throughout the world. For all radio and electronic components made in UK, USA, Europe and Japan.

FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS

BP23 \$2.72
Full constructional data, circuits, components lists for many practical projects including audio distortion meter, superFET receiver, guitar amp, metronome, etc.

RESISTOR SELECTION HANDBOOK

BP28 \$2.24
Shows how to combine two preferred values of resistor to obtain virtually any required value of resistance. Includes information about fixed resistors, standard ranges, colour codes and markings, power ratings and resistor calculations.

HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS

BP32 \$5.92
Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

ELECTRONIC PROJECTS FOR BEGINNERS

BP48 \$4.64
This book gives the newcomer to electronics a wide range of easily built projects. Actual components and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.

POPULAR ELECTRONIC PROJECTS

BP49 \$4.96
A collection of the most popular types of circuits and projects to interest most electronics constructors. The projects cover a wide range and are divided into four basic types: radio, audio, household and test equipment.

BEGINNERS GUIDE TO DIGITAL ELECTRONICS

BP61 \$3.36
Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

ELECTRONIC GAMES

BP69 \$5.92
How to build many interesting electronic games using modern ICs. Covers both simple and complex circuits for beginner and advanced builder alike.

RADIO CONTROL FOR BEGINNERS

BP79 \$5.92
How complete systems work with constructional details of solid state transmitters and receivers. Also included — antennas, field strength meter, crystal controlled superhet, electro-mechanical controls. Section dealing with licensing etc. not applicable to Australia.

EASY ELECTRONICS-CRYSTAL SET CONSTRUCTION

BP92 \$6.56
For those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. The circuits are based on those from earlier publications but have been modified to use modern inexpensive components and home wound coils.

IC PROJECTS FOR BEGINNERS

BP97 \$6.56
Especially written for the less experienced hobbyist, and offers a range of fairly simple projects based around a number of popular and inexpensive linear and digital ICs. Complete layout and in-point-to-point wiring diagrams included.

ELECTRONICS — IT'S EASY VOL. 1

\$5.95
Meters, resistance, capacitance and inductance, emitter followers, op amps, power supplies and electronic filters.

ELECTRONICS — IT'S EASY VOL. 2

\$12.95
Same content in a hard-cover form.

ELECTRONICS — IT'S EASY VOL. 2

\$5.95
Digital sub-systems counters and shift registers, A-D and D-A conversion, digital instruments and test equipment, computers, transmission links and oscilloscopes.

ELECTRONICS — IT'S EASY VOL. 2

\$12.95
Same content in a hard-cover form.

SIMPLE PROJECTS FROM ETI

\$2.95
Two volumes containing easy projects plus chapters on construction techniques and useful information on components.

HOBBY ELECTRONICS PROJECT BOOK

\$4.95
Fifty projects ranging from very simple ones for complete beginners to more elaborate ones for those with more experience. There's a complete guide to soldering and instructions on how to make your own pc boards.

HOW TO BUILD ELECTRONIC GAMES

\$3.95
Alien invaders, electronic die, sound effects, two slot car controllers, electronic poker machine, the family ferry and lots more.

HOW TO BUILD GOLD AND TREASURE DETECTORS

\$3.95
Tells you how metal detectors work and how to construct the different types of detectors: discriminating, BFO, induction balance and a professional deep-seeking unit. How to build a geiger counter.

constructional projects general

DESIGN OF TRANSISTOR CIRCUITS, WITH EXPERIMENTS

21626P \$20.75
A self-teaching course in transistor circuits — seven chapters explore the fundamentals of active semiconductor and their operating principles and procedures. Experiments in design and semiconductor testing provide hands-on experience.

UNIQUE ELECTRONIC WEATHER PROJECTS

21484P \$13.25
Fun and easy-to-build projects include an IC barometer to serve as a tornado warning and a 'thermostat with a brain' to help conserve energy.

BUILD YOUR OWN HI-FI & AUDIO ACCESSORIES

220B \$3.04
Essential for keen hi-fi and audio enthusiasts. Projects include stereo decoder, three-channel mixer, FET preamp for ceramic pick-ups, mic preamp with adj. bass, stereo dynamic noise limiter, loudspeaker protector, voice-operated relay, etc.

28 TESTED TRANSISTOR PROJECTS

221B \$4.32
Some circuits are new, others are familiar designs. Projects can be split and/or combined for specialised needs.

50 CMOS PROJECTS

224B \$4.64
Many interesting and useful projects — multivibrators, amplifiers and oscillators; trigger devices; special devices.

MAJOR SOLID STATE AUDIO HI-FI PROJECTS

BP29 \$3.04
Three projects for the more experienced constructor: 12.5 W/ch stereo amplifier, eight input stereo/mono mixer and 4x14 W quadrasonic amplifier. Full constructional details provided.

HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS

BP32 \$5.92
Electronic and practical details on the simple and inexpensive construction of heterodyne metal locators.

HOW TO MAKE WALKIE-TALKIES

BP43 \$5.12
This treatise on low power transmitter-receivers (walkie-talkies) covers many aspects from licensing requirements and bands, through practical circuitry and construction to the various types of aerials that may be used.

PROJECTS IN OPTO-ELECTRONICS

BP45 \$5.92
Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra red transmitters and detectors, modulated light transmission and also photographic projects etc.

RADIO CIRCUITS USING ICs

BP46 \$4.64
This book describes ICs and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. Also discussed are stereo decoder circuits, quadrophonic circuits and voltage regulator devices.

POPULAR ELECTRONIC PROJECTS

BP49 \$4.96
Includes a collection of the most popular types of circuits and projects which cover radio, audio, household projects and test equipment.

HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE

BP57 \$5.12
Project divided into sections for builder individually to construct and test — then assemble into complete instrument. Includes short section on scope usage.

SINGLE IC PROJECTS

BP65 \$5.12
Simple to build projects based on a single IC. A few projects use one or two transistors as well. A strip board layout is given for each project plus special constructional and setting up info. Contents include low level audio circuits, audio power amps, timers, op-amps and miscellaneous circuits.

ELECTRONIC GAMES

BP69 \$5.92
A number of interesting electronic games projects using ICs for both the beginner and advanced enthusiast.

ELECTRONIC HOUSEHOLD PROJECTS

BP71 \$5.92
Most useful and popular projects for use around the home. Includes two-tone buzzer, intercom, smoke and gas detectors, baby alarm, freezer alarm etc. etc.

REMOTE CONTROL PROJECTS

BP73 \$6.56
Covers radio, infra-red, visible light, ultrasonic controls. Full explanations are provided so that the reader can adapt the projects for domestic and industrial as well as model use.

POWER SUPPLY PROJECTS

BP76 \$5.92
This book gives a number of power supply designs, including simple unregulated types, fixed voltage regulated types and variable voltage stabilised designs. The designs are all low voltage types for semiconductor circuits.

POPULAR ELECTRONIC CIRCUITS — BOOK 1

BP80 \$6.56
Yet more circuits from Mr. Penfold! Includes audio, radio, test gear, music projects, household projects and many more. An extremely useful book for all hobbyists, offering remarkable value for the designs it contains.

ELECTRONIC PROJECTS USING SOLAR CELLS

BP82 \$6.56
Includes a number of projects that benefit from solar power and obviate the problems encountered with batteries, such as weight and bulk, frequency of replacement, and failure when batteries are exhausted.

DIGITAL IC PROJECTS

BP84 \$6.56
Companion to No. 225 Practical Introduction to Digital ICs and BP81 Beginner's Guide to Digital Electronics. The projects included in this book range from simple to more advanced projects — some board layouts and wiring diagrams are included.

AUDIO PROJECTS

BP90 \$6.56
Covers a wide range of audio projects including pre-amplifiers and mixers, power amplifiers, tone controls and matching etc. A number of board layouts and wiring diagrams are included.

LOOK! More books!

Mail order coupon on page 58.

ELECTRONIC TIMER PROJECTS

BP93 \$6.56
These may have a high degree of accuracy with quartz control or they may be quite simple designs, using only a few components. A number of specialist timer projects are car windscreen wiper delay unit, darkroom timer, metronome etc.

ELECTRONIC PROJECTS FOR CARS AND BOATS

BP94 \$6.56
Fifteen fairly simple projects designed for use with 12 V electrical systems but in some cases can also be employed with 6 V and/or positive earth systems as well.

MODEL RAILWAY PROJECTS

BP95 \$6.56
Projects include such things as controllers, signals and sound effects units. Construction stripboard layouts are provided for each project.

CB PROJECTS

BP96 \$6.56
A number of useful designs include a speech processor, interference filters and a simple CB radio receiver. Stripboard layouts, wiring diagrams and notes on construction are provided.

POPULAR ELECTRONICS CIRCUITS — BOOK 2

BP98 \$7.52
A companion for BP80, this book provides a wide range of designs for electronics enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed constructional information.

MINI-MATRIX BOARD PROJECTS

BP99 \$6.56
This book provides a selection of 20 useful circuits which can all be built on a mini-matrix board which is just 24 holes by 10 copper strips in size. Simple and easy for those with not much experience in electronics.

MULTI-CIRCUIT BOARD PROJECTS

BP103 \$6.56
All circuits are based on one specially designed pc board. Recommended to the less experienced hobbyist.

ELECTRONIC SCIENCE PROJECTS

BP104 \$7.52
These projects range in complexity from a simple colour temperature meter to an infra-red laser. There is an electronic clock regulated by a resonating spring and an oscilloscope with a solid-state display. How to build them and use them is fully explained.

AERIAL PROJECTS

BP105 \$6.56
Practical aerial designs including active, loop and ferrite which are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

MODERN OP-AMP CIRCUITS

BP106 \$6.56
A collection of widely varying circuits and projects based on the op-amp ICs.

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

BP110 \$6.56
Helps you to overcome the problems of a circuit that doesn't work by indicating how and where to start looking for many of the common faults that can occur when building up a project.

circuit techniques and design

TTL COOKBOOK

21035P \$17.50
A complete look at TTL logic circuits — what TTL is, how it works, and how to use it. Many kinds of practical TTL are included, such as digital counters, electronic stopwatches, digital voltmeters, etc.

ACTIVE-FILTER COOKBOOK

21168P \$21.95
Learn how to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

ELECTRONIC CIRCUITBOOK 1: PROJECT CONSTRUCTION

21241P \$7.50
Your basic guide to project construction, covering component identification, power supplies, proper tool selection, troubleshooting techniques, oscilloscope use, custom-made enclosures, and more.

CMOS COOKBOOK

21398P \$19.25
This book explains CMOS technology and its application to 'real world' circuitry. A mini-catalogue is included, which lists over 100 devices, giving their pinouts and application notes.

IC TIMER COOKBOOK

21416P \$15.95
Gives you a look at the hundreds of ways IC timers are used in electronic instrumentation.

IC CONVERTER COOKBOOK

21527P \$20.75
Written for the practising engineer, technician, hobbyist or student, this book will be an invaluable working guide to the understanding and use of IC analogue/digital and digital/analogue converters.

DESIGN OF OP-AMP CIRCUITS, WITH EXPERIMENTS

21537P \$16.50
The design of the fundamental circuits that are the basic building blocks of more sophisticated systems. A series of 35 experiments illustrates the design and operation of linear amps, differentiators and integrators, voltage and current converters, active filters, and lots more.

555 TIMER APPLICATIONS SOURCE BOOK, WITH EXPERIMENTS

21538P \$11.25
This book describes the construction of the 555 timer and gives numerous practical examples of its applications in all areas of electrical and computer engineering, including 17 simple experiments.

DESIGN OF ACTIVE FILTERS WITH EXPERIMENTS

21539P \$15.95
Introduction to the theory, implementation and design of active filters using the 741 op-amp.

DESIGN OF PHASE-LOCKED LOOP CIRCUITS, WITH EXPERIMENTS

21545P \$15.95
An excellent introduction to the theory, design and implementation of phase-locked loop circuits using various TTL and CMOS devices. Includes manufacturers' data sheets and describes the use of breadboarding aids in the wide range of laboratory-type experiments.

AUDIO IC OP-AMP APPLICATIONS

21558P \$13.25
This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including small spatial needs, low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

UNDERSTANDING CMOS INTEGRATED CIRCUITS

21598P \$9.95
This book tells you what CMOS ICs are, how they work, and how they can be used in electronic circuit designs. Many practical circuits, complete with parts values, are included.

DESIGN OF TRANSISTOR CIRCUITS WITH EXPERIMENTS

21626P \$20.75
A self-teaching course to provide the background and explanations necessary to teach the reader the art of designing transistor circuits.

GUIDE TO CMOS BASICS, CIRCUITS, AND EXPERIMENTS

21654P \$14.95
If you are already familiar with TTL devices and are ready to examine the benefits of CMOS, this book is your complete source. It tells you what CMOS devices are, their characteristics and design rules. 22 experiments demonstrate the concepts discussed.

PRACTICAL TRANSFORMER DESIGN HANDBOOK

21657P \$35.50
An easy to understand, illustration-filled guide to designing and constructing transformers. Reviews the fundamentals of electricity, magnetism and algebra needed to understand transformer theory, and covers general design considerations, transformer types, power losses and transformer use in converters and inverters.

Z80 MICROCOMPUTER DESIGN PROJECTS

21682P \$20.75
This book provides a complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

DESIGN OF VMOS CIRCUITS, WITH EXPERIMENTS

21686P \$17.50
The authors look at the technology which makes dramatic advancements possible with VMOS, and show how these components can easily and effectively be integrated into common circuit designs to enhance their responses.

IC OP-AMP COOKBOOK

21695P \$23.75
Basic op-amp theory in detail, with 200 practical, illustrated circuit applications. JFET and MOSFET units are featured, plus manufacturers' data sheets and company addresses.

EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS

21785P \$13.25
Artificial Intelligence is the capability of a device to perform functions normally associated with human intelligence. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct interesting and exciting experiments in artificial intelligence.

PRACTICAL SOLID-STATE CIRCUIT DESIGN

21787P \$14.95
An introductory course in practical solid-state circuit design for the experimenter, designer or technician who is interested in constructing tailor-made circuits.

SCRS AND RELATED THYRISTOR DEVICES

21806P \$19.25
Written for experimenters, technicians and engineers, this book is a practical and comprehensive guide to theory, operation, specifications and applications of silicon-controlled rectifiers (SCRs) and related thyristor devices.

REGULATED POWER SUPPLIES

21808P \$29.75
Comprehensive discussion of the internal architecture and operation of the latest solid-state regulators. Explains when regulated supplies are needed and how to incorporate them in your projects, and discusses modern circuitry including linear and switching circuits and late ICs.

ANALOG INSTRUMENTATION FUNDAMENTALS

21835P \$29.75
Numerous practical, hands-on lab experiments and solved problems are included, plus discussions of movements, dc ammeters, voltmeters, ohmmeters, bridges, filters and attenuators. No calculus is required.

RF CIRCUIT DESIGN

21868P \$33.95
A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

SOLAR CELLS

22270P \$37.95
In-depth description of the basic operating principles and design of solar cells. It also covers the techniques currently used to produce solar cells and reviews system applications.

ELECTRONIC DESIGN WITH OFF-THE-SHELF ICs

50274P \$14.70
It contains virtually all the information you need to design and build electronic circuits, systems and subsystems with readily available ICs. Shows how to interface them into highly complex systems.

MODERN FILTER DESIGN

94663P \$49.95
This book details the advances in active RC filters, both from a practical standpoint and from a state-of-the-art point of view. It is the first book that gives detailed analysis and design procedures for switched capacitor filters.

COIL DESIGN AND CONSTRUCTION MANUAL

160B \$6.56
How to make RF, IF, audio and power coils, chokes and transformers. Maths is simplified.

50 PROJECTS USING CA3130 ICs

223B \$4.32
The CA3130 is an advanced operational amplifier capable of higher performance than many others: circuits often need fewer ancillary components. Audio projects, RF projects. Test equipment, Household projects, Misc. projects.

PRACTICAL INTRO TO DIGITAL ICs

225B \$4.32
Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

50 CIRCUITS USING GERMANIUM, SILICON AND ZENER DIODES

BP36 \$3.36
50 interesting and useful circuits and applications using the germanium and silicon signal diodes, silicon rectifier diodes and zener diodes etc.

50 PROJECTS USING RELAYS, SCRS AND TRIACS
BP37 \$5.92
 Practical working circuits using silicon controlled rectifiers, relays and bi-directional triodes. With a minimum of difficulty you can use them in motor control, dimming and heating control, timing and light sensitive circuits, warning devices and many others.

50 FET PROJECTS
BP39 \$5.92
 Projects include amplifiers and converters, test equipment, tuners, receivers and receiver aids, mixers and tone controls etc etc. The FET used is not critical. This book is of interest and value to SW listeners, radio amateurs, hi-fi enthusiasts and general experimenters.

50 SIMPLE LED CIRCUITS
BP42 \$3.36
 50 interesting and useful circuits and applications using the LED. Also includes circuits for the 707 Common Anode Display for the beginner and advanced enthusiast.

IC555 PROJECTS
BP44 \$6.56
 One wonders how life went on before the 555! Included are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus section on subsequent 556, 558 and 559s.

PROJECTS IN OPTO-ELECTRONICS
BP45 \$5.92
 Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and detectors, modulated light transmission and also photographic projects etc.

RADIO CIRCUITS USING ICs
BP46 \$4.64
 This book describes ICs and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. Also discussed are stereo decoder circuits, quadrophonic circuits and voltage regulator devices.

LM 3900 IC PROJECTS
BP50 \$4.64
 Unlike conventional op-amps, the LM 3900 can be used for all the usual applications as well as many new ones. It's one of the most versatile, freely obtainable and inexpensive devices around. This book provides the groundwork for simple and advanced uses — it's much more than a collection of projects. Very thoroughly recommended.

50 CIRCUITS USING 7400 SERIES ICs
BP58 \$5.12
 50 interesting and useful circuits and applications using these inexpensive and versatile devices.

50 CMOS IC PROJECTS
224B \$4.64
 Projects include multivibrators, amplifiers and oscillators, trigger devices and other special devices.

SECOND BOOK OF CMOS IC PROJECTS
BP59 \$5.12
 Leading on from book number 224 '50 CMOS IC PROJECTS', this second book provides a further selection of useful circuits mainly of a fairly simple nature. Contents have been selected to ensure minimum overlap between the two books.

COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS
BP67 \$5.92
 Well-known author F.G. Rayer features applications and projects using various types of numeral displays, popular counter and driver ICs, etc.

VMOS PROJECTS
BP83 \$6.56
 Though primarily concerned with VMOS power FETs and their applications, power MOSFETs are dealt with too, in a chapter on audio circuits. Projects include audio circuits, sound generator circuits, dc control circuits and signal circuits.

DIGITAL IC PROJECTS
BP84 \$6.56
 Helps the reader to develop a knowledge of the workings of digital circuits. Board layouts and wiring diagrams are included.

HOW TO USE OP-AMPS
BP88 \$7.52
 Design notes and applications on many topics including basic theory, amplifiers, power supplies, audio circuits, oscillators, filters, computers and control engineering. It's written around the 741 IC but includes design notes for most of the common op-amps.

ELECTRONIC TIMER PROJECTS
BP93 \$6.56
 These may have a high degree of accuracy with quartz control or they may be quite simple designs, using only a few components. A number of specialist timer projects are car windscreen wiper delay unit, darkroom timer, metronome etc.

ETI CIRCUITS BOOKS 1/2/3 \$2.95 ea
 Many of these circuits have been published in the 'Ideas for Experimenters' section in ETI.

ETI CIRCUIT TECHNIQUES VOLS 1/2 \$4.75 ea
 The how, what, which, where, why and how much anthology of electronic components, circuits and techniques.

test equipment and fault finding

AUTOMOTIVE TUNE-UP AND EMISSION CONTROL SERVICE
21712P \$20.75

Car owners who wish to save money and maintain their cars at peak performance will learn from this book how to adjust, repair and maintain the systems that ensure best operation.

TROUBLESHOOTING WITH THE OSCILLOSCOPE
21738P \$15.95

Excellent for the professional service technician or the serious hobbyist, as it combines step-by-step procedures for using the scope with the specific nuts and bolts of TV receiver troubleshooting.

EFFECTIVELY USING THE OSCILLOSCOPE
21794P \$14.95

Excellent for the professional service technician or the serious do-it-yourself, as it combines the correct step-by-step procedures for using a scope with the specific nuts and bolts of TV receiver troubleshooting.

MICROCOMPUTER DESIGN AND TROUBLESHOOTING
21819P \$26.75

Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. The author also provides a complete description of two popular microprocessors — the 8085 and the 6502.

USE OF THE DUAL-TRACE OSCILLOSCOPE
40023P \$23.75

This programmed text breaks down the process of operating a scope into a series of logical steps starting with the deflection of the electron beam and continuing through proper use of the triggering controls to measure the phase difference between two waveforms.

ELECTRONIC TROUBLESHOOTING HANDBOOK
52585P \$10.50

This workbench guide shows you how to pinpoint transistor troubles in minutes, how to test almost everything electronic and how to get the most out of low cost test equipment.

PRACTICAL REPAIR AND RENOVATION OF COLOUR TVs
BP34 \$4.32

This book shows how to obtain a working colour TV for very little outlay by repairing and renovating a set that has been 'written off' by a dealer. Includes practical details of how to construct your own CRT tester/revivener and cross hatch generator.

HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE
BP57 \$5.12

The oscilloscope is divided into various sections which can be individually constructed and tested and then assembled together to complete the whole instrument. Also tells you how to use the instrument.

TRANSISTOR RADIO FAULT-FINDING CHART
BP70 \$1.92

Used properly, this chart should enable the reader to trace most common faults quickly. Across the top of the chart are four rectangles containing brief descriptions of the faults. Selecting the appropriate fault, the reader simply follows the arrows and carries out the suggested checks in sequence until the fault is cleared.

ELECTRONIC TEST EQUIPMENT CONSTRUCTION
BP75 \$5.92

Describes construction of wide range of test gear including FET amplified voltmeter, resistance bridge, field strength indicator, heterodyne frequency meter etc.

POWER SUPPLY PROJECTS
BP76 \$5.92

Includes simple unregulated types, fixed voltage regulator types and variable voltage stabilised designs. The designs are all low voltage types for semiconductor circuits.

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING
BP110 \$6.56

Helps you to overcome the problems of a circuit that doesn't work by indicating how and where to start looking for many of the common faults that can occur when building up a project.

TEST GEAR — METERING AND POWER SUPPLY PROJECTS \$3.00
 Includes many types of meters, audio noise and signal generators, simple CMOS tester, oscilloscope calibrator etc.

TEST GEAR — VOL. 2 \$3.95
 Projects include audio oscillator, transistor tester, true RMS voltmeter, RF signal generator, versatile logic test probe, microwave oven leak detector etc.

ELECTRONIC PROJECTS FOR YOUNG SCIENTISTS \$3.95
 PH meter, geiger counter, helium-neon laser, sound level meter, solar cells, negative ion generator and much more.

electronic music/audio/video

AUDIO CYCLOPEAIA
20675P \$66.00

A complete in-depth look at the art of audio — from the basic principles of sound to solid-state and integrated circuits. Over 3000 entries and hundreds of illustrations and circuit diagrams cover acoustics, amplifiers, recording, reproduction, test equipment, audio measurements, and much more.

ELECTRONIC MUSIC CIRCUITS
21833P \$24.95

How to build a custom electronic music synthesiser, outlines numerous other circuit designs and then shows you how to modify them to achieve particular responses. Many of the circuits can be used as special-effects boxes for guitars and other musical instruments.

INTRODUCTION TO ELECTRO-ACOUSTIC MUSIC
81515P \$15.95

This book assumes no previous technical knowledge. It discusses the relationship between the technology and the composition of electro-acoustic music.

MODERN RECORDING TECHNIQUES
21037P \$19.25

Explains the equipment controls and techniques found in a modern recording studio and how to use them creatively and correctly to produce a desired result. Numerous photographs, diagrams and charts.

SOUND SYSTEM ENGINEERING
21156P \$32.50

Dealing with audio systems as a whole, it includes installing and equalising the sound system and interfacing the electrical and acoustic systems. Instrumentation, the acoustic environment and designing for acoustic gain are covered.

TUBE SUBSTITUTION HANDBOOK
21746P \$8.75

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

HOW TO BUILD SPEAKER ENCLOSURES
20520P \$8.75

A practical guide to the 'whys' and 'hows' of constructing high-quality top-performance loudspeaker enclosures.

ACTIVE-FILTER COOKBOOK
21168P \$21.95

Learn how to construct filters of all kinds — highpass, lowpass, bandpass. The book is easy to understand — no advanced maths or obscure theory is used.

DESIGN OF ACTIVE FILTERS WITH EXPERIMENTS
21539P \$15.95

Introduction to the theory, implementation and design of active filters using the 741 op-amp.

AUDIO IC OP-AMP APPLICATIONS
21558P \$13.25

This book discusses IC op-amps and their application in audio systems, and describes the numerous advantages of using op-amps, including small spatial needs, low power consumption, reliable performance and low cost. Assumes a basic understanding of op-amp theory.

VIDEO TAPE RECORDERS
21521P \$17.50

In this completely revised second edition, the author tells in simple language how helical VTRs work and how to operate and service them. Includes numerous examples of circuits and mechanical systems.

OOPS! More books!

Mail order coupon on page 58.

CHEAP VIDEO COOKBOOK
21524P \$11.75
Complete discussion of a new, low-cost way to get words, pictures and opcode out of your computer and onto any ordinary TV screen, using a seven-IC easy-to-build circuit which you can build for less than \$20.

AN INTRODUCTION TO VIDEO
BP100 \$6.56
This book is written in layman's language and is for anyone who is thinking about buying or renting or who has just bought or rented a video recorder and wants to get the best out of the machine.

MOBILE DISCO HANDBOOK
BP47 \$4.64
Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.

ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING
BP51 \$5.92
Shows how electronic music can be made at home with the simplest and most inexpensive of equipment. Describes how the sounds are generated and how these may be recorded to build up the final composition.

PRACTICAL CONSTRUCTION OF PREAMPS, TONE CONTROLS, FILTERS, ATTENUATORS
BP60 \$4.96
This book shows the enthusiast how to construct a variety of magnetic tape recording, microphone and disc pre-amplifiers, and also a number of tone control circuits, rumble and scratch filters, attenuators and pads.

ELECTRONIC SYNTHESIZER PROJECTS
BP81 \$5.92
For the electronic music enthusiast, an invaluable reference. This book is full of circuits and information on how to build analogue delay lines, sequencers, VCOs, envelope shapers, etc. etc. The author takes a clear and logical approach to the subject that should enable the average enthusiast to understand and build up what appears to be a quite complex instrument.

AUDIO PROJECTS
BP90 \$6.56
Covers a wide range of audio projects including preamplifiers and mixers, power amplifiers, tone controls and matching etc. A number of board layouts and wiring diagrams are included.

ELECTRONIC MUSIC PROJECTS
BP74 \$5.92
Provides constructors with practical circuits for the less complex music equipment including fuzz box, waa-waa pedal, sustain unit, reverb and phaser, tremolo generator etc. Text covers guitar effects, general effects, sound generators, accessories.

SONICS 1982 YEARBOOK \$5.35
An interview with Kraftwerk, how to cope with recording, lighting, rock acoustics, guitars, equipment reviews and more.

SONICS MAGAZINE \$2.35 ea
The Australian music magazine dedicated to the art and craft of sound. Published April, July, October, Yearbook in December. \$15 for one year subscription. Please indicate starting issue.

computers for beginners

COBOL FOR BEGINNERS
39378P \$21.95
It is a solid text for introductory programming courses in Cobol, using a format that is easy to understand, yet comprehensive enough to make supplementary readings unnecessary.

THE PET PERSONAL COMPUTER FOR BEGINNERS
61827P \$20.95
This handy guide is written for use with all varieties of PET computer, from the original 2001 to the new 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

BIG THINGS FROM LITTLE COMPUTERS
77859P \$19.25
A layperson's guide to personal computing with all the basic information and lots of examples of how personal computers can be used.

BEGINNER'S GUIDE TO DIGITAL ELECTRONICS
BP61 \$3.36
Covers all essential areas including number systems, codes, constructional and sequential logic, analogue/digital/analogue conversion.

BEGINNER'S GUIDE TO MICROPROCESSORS & COMPUTING
BP66 \$5.92
Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

A MICROPROCESSOR PRIMER
BP72 \$5.92
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

AN INTRO TO BASIC PROGRAMMING TECHNIQUES
BP86 \$6.56
Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

BEGINNING BASIC
39806A \$19.95
Intended for beginners with no computing experience, one should be able to intelligently program in BASIC in a short time.

BEGINNING FORTRAN
46011A \$19.95
Starts with simple elementary examples and proceeds to intermediate level programs. Also includes references, tutorials, flow charts, deck set-ups and matrix algebra.

UNDERSTANDING COMPUTERS
39815A \$17.95
This book describes how computers work. For people who use small computers, it starts with the most elementary gates and works up to the complete computer. Gives an understanding of languages and how they operate in the computer.

NAILING JELLY TO A TREE
39842A \$24.95
This guide to software teaches you about machine language, assembly language programming and BASIC. The emphasis is not on learning to write programs but on learning to use the thousands of available programs that have already been written.

PEANUT BUTTER AND JELLY GUIDE TO COMPUTERS
39813A \$14.95
A simple, easy-to-digest source of information on personal computing for the potential buyer who is less than an expert in the field.

INTRODUCTION TO WORD PROCESSING
88076A \$17.95
Written for the non-technical reader, this book tells about the concepts common to all word processing systems, then analyses all features in detail.

YOUR FIRST COMPUTER
88045A \$12.50
An easy-to-understand beginner's book to small computers. Understanding them, buying them and using them for personal and business applications.

FROM CHIPS TO SYSTEMS: AN INTRODUCTION TO MICROPROCESSORS
88063A \$19.95
Explains exactly what a microcomputer system is and how it works. Introduces fundamental concepts and covers all aspects of microprocessors and related components: internal operation, memories, interfacing and system development etc.

COMPUTERS FOR EVERYBODY
39849A \$8.95
In this easy-to-understand book it is explained how a computer can be used at home, in the office or at school. Includes a consumer's guide to computer equipment that will help the reader decide what to buy and who to buy it from.

computers hardware & techniques

USING THE 6800 MICROPROCESSOR
21512P \$13.25
This will guide the reader through the conception, configuration, writing and running of a variety of programs that demonstrate practical use of a 6800 system.

Z80 MICROCOMPUTER DESIGN PROJECTS
21682P \$20.75
This book provides a complete look at the internal architecture of the Z80, the heart of many microcomputers, and even shows how to build a microcomputer, the EX80, using this powerful chip.

MICROPROCESSOR CIRCUITS VOL. 1
21877P \$14.75
Presents basic microprocessor concepts in simple language for beginners and teaches you to construct a useful microcontroller system. Offers 30 demo circuits which take you through assembly, operation and programming of a microcontroller.

INTERFACE PROJECTS FOR THE APPLE II
69387P \$15.95
A series of interface projects that are easily built and enable the user to realise the computer's potential through project construction. Projects are primarily hardware-orientated, with some software supporting the hardware.

PET INTERFACING
21795P \$25.25
Demonstrates how to build numerous interfacing devices for PET hardware. BASIC language programs are used throughout, and the book includes a discussion of the microprocessor's internal architecture and general hardware/software interfacing.

6809 MICROCOMPUTER PROGRAMMING AND INTERFACING, WITH EXPERIMENTS
21798P \$21.95
Gives a solid understanding of how to program and interface the high-performance 6809 microprocessor. The author completely explores internal structure, addressing modes, data movement instructions, registers, arithmetic logic and test instructions for the 6809.

Z80 MICROCOMPUTER HANDBOOK
21500P \$17.50
This thorough handbook covers hardware, software and microcomputers built around the Z80.

THE S100 AND OTHER MICRO BUSES
21810P \$13.25
The key to successful computer expansion is a complete understanding of the bus system, through which the computer communicates with peripherals. This book will give you that understanding.

MICROCOMPUTER DESIGN AND TROUBLESHOOTING
21819P \$26.75
Tells you how to design microcomputer systems and make them work without an expensive commercial development system or the need for costly test instrumentation. The author also provides a complete description of two popular microprocessors—the 8085 and the 6502.

DON LANCASTER'S MICRO COOKBOOK, VOLUME 1
21828P \$20.75
This 'cookbook' starts with the very fundamentals of microprocessors and microcomputers and takes you through number systems, codes, memory, etc, until you can work intelligently with micro.

DON LANCASTER'S MICRO COOKBOOK, VOLUME 2
21829P \$20.75
Carries on where Volume 1 left off.

APPLE INTERFACING
21862P \$15.95
Using this book, you will be able to perform useful experiments which will provide a much clearer understanding of the fundamentals of computer interfacing and computer electronics. A better understanding of interactions between hardware and software will enable you to communicate more effectively with your Apple.

MICROPROCESSOR CIRCUITS VOL. 1
21877P \$14.75
Presents basic microprocessor concepts in straightforward language for beginners. Teaches you to construct a useful microcontroller system through progressive demonstration circuits.

8080 MICROCOMPUTER EXPERIMENTS
39808A \$29.50
This 'hands on' book includes 105 experiments presenting programs and diagrams as required for clarification.

A STEP-BY-STEP INTRODUCTION TO 8080 MICROPROCESSOR SYSTEMS
39804A \$16.95
Doesn't require any electronics or computer background. This book describes the 8080 architecture and instruction set through simple examples. Some basic software is introduced.

DIGITAL CIRCUITS WITH MICROPROCESSOR APPLICATIONS

46032A \$39.50
An introductory text, this book provides readers with the basic ideas and tools needed to analyse and design digital circuits and computer systems. Discusses microprocessor computer organisation, machine language number systems and gate circuits.

MICROPROCESSOR INTERFACING TECHNIQUES

88029A \$24.95
Teaches you how to interconnect a complete microprocessor system and interface it to the usual peripherals. The hardware and software skills needed to effectively interface peripheral devices are covered along with various buss standards and A/D conversion.

PRACTICAL INTRO TO DIGITAL ICs

225B \$4.32
Introduction to digital ICs (mainly TTL 7400). Besides simple projects, includes logic test set to identify and test digital ICs. Also includes digital counter-timer.

BEGINNER'S GUIDE TO MICROPROCESSORS & COMPUTING

BP66 \$5.92
Introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. Only prior knowledge assumed is very basic arithmetic and an understanding of indices.

A MICROPROCESSOR PRIMER

BP72 \$5.92
Learning about microprocessors is easy with this book, written in a style that is easy to follow. The shortcomings of this basic machine are discussed and the reader is shown how these are overcome by changes to the instruction set. Relative addressing, index registers follow as logical progressions.

PRACTICAL COMPUTER EXPERIMENTS

BP78 \$5.92
How to build typical computer circuits using discrete logic. This book is a useful intro to devices such as adders and storers as well as a general source book of logic circuits.

THE 6809 COMPANION

BP102 \$6.56
It is not a beginners introduction to microprocessors in general but a discussion of the features of the 6809 and a reference work for the 6809 programmer in particular.

COMPUTERS & COMPUTING YEARBOOK 1980

\$4.95
Includes beginners buying guide, the Apple, Tandy's TRS-80, the Vector MZ, introducing BASIC, S100 VDU, EPROM programmer, microcomputer power supply and lots more.

COMPUTERS & COMPUTING YEARBOOK 1982

\$4.95
Includes disks, CP/M and your computer, learners microcomputer, programming in CHIP-8, alphsort, fast plotter, PET talk, the System 80 etc.

computing software

CP/M PRIMER

21791P \$21.95
A complete one-stop course on CP/M, the very popular operating system for 8080, 8085 and Z80-based microcomputers. Complete terminology, hardware and software concepts, startup of a CP/M system, and a complete list of CP/M-compatible software.

THE CP/M HANDBOOK (WITH MP/M)

88048A \$19.95
Contains a step-by-step description of all the CP/M command features. Designed for the beginner, the book progresses to detailed explanations of the file transfer program, the debugging program and CP/M's text editing program.

HOW TO GET STARTED WITH CP/M

39832A \$19.95
This practical book eases the reader into the essentials of the system, giving an overview of the operating system, an idea of what it will be like to use and what it can do for the reader.

AUSTRALIAN MICROCOMPUTER HANDBOOK

72505 NOW \$15.00
Normally \$25.00. A detailed buyer's guide to micro-computer systems and application packages in commercial, industrial, scientific, educational and home/hobby areas.

THE C PROGRAMMING LANGUAGE

10163P \$21.95
C is a general purpose 'low-level' programming language. It is not specialised to any particular area of application, but its absence of restrictions make it convenient and effective for many tasks.

THE 68000: PRINCIPLES AND PROGRAMMING

21853P \$19.95
An easy-to-read, systematic approach to the 68000 advanced 16-bit microprocessor. The book guides you through the complex architecture, instruction set, pinouts and interfacing techniques. Written for design engineers, programmers and students.

PROGRAMMING IN BASIC FOR PERSONAL COMPUTERS

30739P \$14.75
Simple instructions show how to give BASIC commands and statements a wide range of applications, from programming video games to developing business or scientific programs.

PROGRAMMABLE CALCULATORS

46008A \$24.95
This book suggests which calculators to buy, their possibilities and limitations, and the how-tos of programming them.

TAKE A CHANCE WITH YOUR CALCULATOR

39807A \$14.95
An introduction to modern mathematics, this book deals with programming of programmable calculators and includes probability problems.

AN INTRO TO BASIC PROGRAMMING TECHNIQUES

BP86 \$6.56
Ideal for beginners seeking to understand and program in BASIC. Book includes program library for biorhythms, graphing Y against X, standard deviations, regressions, generating musical note sequences, and a card game.

BASIC FOR EVERYONE

61481P \$19.75
349 pages of BASIC information for all purposes.

BEGINNING BASIC

39806A \$19.95
Intended for beginners, this book discusses how a programmer and a basic computer interact with the computer. Problems likely to be met by the beginner, the need for and uses of documentation etc.

FIFTY BASIC EXERCISES

88056A \$17.95
Designed to teach BASIC through actual practice, this book contains graduated exercises in math, business, operations research, games and statistics. The programs were designed to run directly on a TRS-80 and will run with minor or no changes on any system with Microsoft BASIC.

INSIDE BASIC GAMES

88055A \$19.95
The medium of games teaches readers how to design error-free, interactive BASIC programs. Rules, algorithms and coding differences for the PET, APPLE II and TRS-80 are also included

MICROSOFT BASIC

39823A \$19.95
Includes branching and loops, arithmetic in BASIC, strings, editing, arrays and files, the disk and a description of the Radio Shack Level II BASIC.

INTRODUCTION TO FORTH

21842P \$14.95
The most complete book available on the MMS FORTH version of FORTH, but also a fundamental approach to programming in all versions of FORTH. Many programming examples are provided, with direct comparisons to the Microsoft Level II BASIC version of these programs.

STARTING FORTH

42922P \$23.75
A clear and complete guide to FORTH, this book covers fundamental principles and then a full set of high-level FORTH commands. It concludes with advanced techniques and style.

A FORTRAN PRIMER

80454P \$6.95
Assumes no previous knowledge of program writing. It covers the fundamentals of the FORTRAN language, enables extensive program writing and concentrates on programming style.

INTRODUCTION TO STRUCTURED FORTRAN

46007A \$19.95
Written for the beginner, the text incorporates the new FORTRAN 77 with a discussion of structural programming. Includes a discussion of time-sharing, pseudo language programming and WATFIV statements

MICROSOFT FORTRAN

39846A \$24.95
An introductory text on FORTRAN in general and Microsoft FORTRAN in particular. The latter is exceptionally well suited for use on microcomputers using CP/M and others of the 8080/8075/Z-80 family

BEGINNING FORTRAN

46011A \$19.95
Introduces readers to FORTRAN. Included are references for further study, brief tutorials on key punching, flow charting, deck set-ups and matrix algebra.

QWIKTRAN

39824A \$19.95
Quick FORTRAN for Micros, Minis and Main Frames. Starts with the basic concepts of computing and Qwiktran, a fundamental subset of FORTRAN IV. Lots of examples to increase the reader's proficiency.

THE UCSD PASCAL HANDBOOK

35536P \$23.75
Language descriptions organised in a quick and easy reference are given in this book for readers with no prior experience of Pascal programming.

INTRODUCTION TO PASCAL

91522P \$19.95
The second edition of this popular book has been updated to conform to the new international standard of Pascal. The contents illustrate the design and construction of Pascal programs, involving a wide range of basic computer algorithms in a practical context.

PASCAL

46028A \$19.95
For people with little or no programming experience, this book gives lots of examples that clearly explain proper usage of language features. Discusses top-down programming, debugging, self-documentation etc

THE PASCAL HANDBOOK

88053A \$23.50
This book summarises the entire Pascal vocabulary, including the variations introduced by different commercial versions of Pascal. All in dictionary format.

PASCAL PROGRAMS FOR SCIENTISTS AND ENGINEERS

88058A \$23.50
Over 60 of the most frequently used scientific algorithms, along with their program implementation in Pascal, are in this book.

COBOL FOR BEGINNERS

39378P \$21.95
It is a solid text for introductory programming courses in Cobol, using a format that is easy to understand, yet comprehensive enough to make supplementary readings unnecessary.

STARSHIP SIMULATION

39810A \$11.95
This book offers both a specific simulation which can be implemented, modified and played, and a complete look at how to put together a simulation on almost any subject.

BASIC PROGRAMS FOR SCIENTISTS AND ENGINEERS

88073A \$19.95
This book contains scientific and engineering application programs written in BASIC.

COMPUTER GRAPHICS PRIMER

21650P \$21.95
Almost every page has a colour drawing, photograph, picture or a schematic to help you learn computer graphics quickly and easily. Programming concepts apply to all microcomputers, and examples are given in BASIC for the Apple II.

INTRODUCTION TO TRS-80 GRAPHICS

39818A \$17.95
It begins with the basic concepts of line drawing and leads the reader on to geometric shapes, moving figure animation and other more advanced topics.

CIRCUIT DESIGN PROGRAMS FOR THE TRS-80

21741P \$21.75
A number of programs written to aid you in using your TRS-80 and Level II BASIC for the design and analysis of many electronic circuits. The programs analyse information on ms values, periodic waveforms, integrated circuit timers and bipolar transistor circuits.

MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80

— BOOK 1
21788P \$19.25
28 ready-to-use BASIC programs which have been completely tested and debugged. Programs include a telephone dialer, digital stop-watch, spelling test, house buying guide, gas mileage calculator, and others. Complete with explanations of each program, sample runs, and complete program listing.

MOSTLY BASIC: APPLICATIONS FOR YOUR TRS-80

— BOOK 2
21865P \$19.25
32 ready-to-run BASIC programs, including two to test your ability in history and maths, a Dungeon of Danger that's strictly for fun, eleven household programs, seven on money and investment, two to test your ESP level, and more. Complete with explanations, sample run and listing for each program

INTERMEDIATE PROGRAMMING FOR THE TRS-80 MODEL I

21809P \$14.95
Step-by-step instructions for the TRS-80 user who wants to progress from BASIC to machine and assembly language programming with the TRS-80 Model I system. A complete how-to guide with numerous examples.

...and for good measure...

computing for business

TRS-80 — MORE THAN BASIC

21813P \$15.95
Learn to program in Z80 mnemonics by using the book's error-tolerant interactive monitor program. Over 26 commands available, with total documentation that helps you change the commands to meet specific applications.

TRS-80 ASSEMBLY LANGUAGE MADE SIMPLE

21851P \$19.25
If you have an understanding of BASIC programming, this book will help you learn to plan, write and hand-assemble your own assembly language programs in memory, using the T-bug and Level II BASIC ROM subroutines.

PROGRAMMING THE TRS-80 POCKET COMPUTER

30531P \$13.25
This book explains all aspects of problem-solving in BASIC, and covers cassette machine interfacing and how to make the best use of the system's keyboard and display.

TRS-80 ASSEMBLY LANGUAGE SUBROUTINES

31188P \$19.25
A wide spectrum of applications is discussed in this book, which provides easy-to-use routines that can be used as they stand or modified.

32 BASIC PROGRAMS FOR THE TRS-80 COMPUTER

39827A \$29.50
Programs for the TRS-80 Level II or Model III BASIC (with 16K or more user memory).

APPLE BASIC

39099P \$19.25
This book gives the beginner a thorough introduction to BASIC programming on an Apple computer, and covers all areas of programming, including graphics, games, mathematical programs, and a great deal more.

CIRCUIT DESIGN PROGRAMS FOR THE APPLE II

21863P \$23.75
A series of ready-to-run Apple II programs ideal for electronics design engineers and others faced with solving problems related to plotting and verification of experimental data. The programs may be used as sub-routines in larger programs, and many can be translated to run on other microcomputer systems.

APPLESOFT LANGUAGE

21811P \$13.95
Written for Apple II micros that use the Microsoft language, this introduction covers each aspect of programming in non-technical language, from elementary concepts to advanced techniques.

APPLE MACHINE LANGUAGE

90230P \$21.95
This straightforward book teaches machine language programming through BASIC, the transition being made step-by-step. Many sketches of video displays are provided, as well as exercises with answers.

APPLE PASCAL GAMES

88074A \$19.95
Explore all the essential elements of UCSD Pascal and learn the important Apple Pascal extensions.

PASCAL PROGRAMMING FOR THE APPLE

95454P \$18.95
This book teaches UCSD Pascal on the Apple II. Many examples, programs for financial applications, graphics, file structures and sound reproduction are supplied.

32 BASIC PROGRAMS FOR THE APPLE COMPUTER

38834A \$29.50
Full of programs with practical applications, educational uses, games and graphics.

PET/CBM BASIC

61751P \$19.25
This book provides a thorough introduction to BASIC programming on a PET computer, explaining programming concepts for graphics, including three-dimensional letters, bar graphs and the use of sound effects in PET programs.

THE PET PERSONAL COMPUTER FOR BEGINNERS

61827P \$20.95
This handy guide is written for use with all varieties of PET computer, from the original 2001 to the new 8032 Super PET. It is suited to novices with no practical experience and provides advice and practical examples.

PET BASIC 1

95524P \$19.25
For users of the PET computer, this book covers such topics as creative graphics, humour and interesting small programs.

PET GAMES AND RECREATIONS

95529P \$18.85
Presenting an interesting mixture of diversions guaranteed to entertain and educate. Ideal for beginners, yet also challenging to computer veterans, the book features progressive levels of difficulty and five different types of games.

32 BASIC PROGRAMS FOR THE PET COMPUTER

39825A \$29.50
Each chapter fully documents a different bug-free program. If readers have a good working knowledge of BASIC, they can devise and implement their own program changes.

THE ATARI ASSEMBLER

90236P \$19.25
This practical book gives detailed instructions for using the Atari Assembler cartridge for novices with some knowledge of BASIC programming. Fundamental information programming in assembly language is given.

ATARI GAMES AND RECREATIONS

90242P \$19.25
Beginners and advanced users can use the pre-programmed games in this book to improve their skill. Charts, flash cards, an error dictionary and graph paper designs are among the features.

EXPLORE COMPUTING WITH THE TRS-80 (AND COMMON SENSE)

96137P \$17.95
This introduction to microcomputers and the BASIC language is suitable for novices and users of the TRS-80. Among the topics covered are creating tables, arts and graphics, games and simulation.

32 BASIC GAMES FOR THE EXIDY SORCERER

39835A \$29.50
Full of programs with practical applications, educational uses, games and graphics. Each chapter documents a different bug-free program.

THE ART OF PROGRAMMING THE 1K ZX81

BP109 \$6.56
This book explains how to use the features of the ZX81 including its random number generator, graphics and timer. PEEK and POKE are explained and you should learn enough to develop programs of your own.

PROGRAMMING THE 6502

88046A \$18.95
Principles of assembly language programming for the 6502 microprocessor are taught in this introductory text. Includes a discussion of trade-offs between hardware and software and detailed explanations of the 6502's internal registers and buss operation.

6502 APPLICATIONS BOOK

88015A \$17.95
Use this book and a few low-cost components to build a complete home alarm system, an electric piano, a motor speed-regulator, a time-of-day clock, a simulated traffic control system and a Morse code generator, etc.

6502 GAMES

88023A \$17.95
You learn how to play ten sophisticated games and also learn assembly language programming. Also learn the techniques of algorithm design and data structures.

8080 MACHINE LANGUAGE PROGRAMMING FOR BEGINNERS

39814A \$12.95
The book will take the reader step-by-step through the most common 8080 op codes and it will do so at a level anyone can understand.

PROGRAMMING THE Z80

88047A \$19.95
This book will enable every reader to write complete application programs for Z80-based computer systems. Includes exercises to measure progress and comprehension at each level of programming.

PROGRAMMING THE Z8000

88072A \$19.95
A complete introduction to programming concepts and techniques for use with the 16-bit, Z8000 microprocessor. Presents detailed descriptions of the architecture and functions of this 'super chip'.

START WITH BASIC ON THE COMMODORE VIC 20

97070P \$14.75
Helpful exercises and step-by-step instructions show you how to program in BASIC utilising all the graphic functions on the Vic 20.

BASIC FOR ACCOUNTANTS

80088P \$9.95
Shows accountancy students and accountants how to use a computer to perform the repetitive tasks associated with record keeping, calculating and report writing. Using the BASIC language attention is concentrated on debtors, inventory and general ledger systems.

COMPUTER BASED BUSINESS SYSTEMS

80192P \$10.95
A short introduction to the sorts of systems used by a typical business to handle its typical activities. The book aims at providing a general understanding and therefore avoids technological detail.

THE COMPUTER SOLUTION

80195P \$13.50
It should be of interest to business people contemplating, implementing or already using computer data processing or to any non-technical person curious to know why and how computers are used in Australian businesses and organisations.

SMALL BUSINESS COMPUTERS: A GUIDE TO EVALUATION AND SELECTION

81134P \$14.95
Ideal for the inexperienced user, this text emphasises management considerations in determining the feasibility, economics, evaluation, selection, contracts and practicality of installing a computer.

SMALL BUSINESS COMPUTER SYSTEMS

81136P \$14.95
This book provides a bridge between the accountant and the DP professional by explaining every step of the trading and reporting process in DP terms. It is especially useful to people engaged in the specification process or in auditing DP accounting systems.

THE VISICALC BOOK — APPLE EDITION

98397P \$22.25
If you are using Visicalc on your Apple II and want to learn more about its expanded uses then this book will show you how to build a model, enter your data and solve problems about profit/loss projections, pricing/costing estimates etc.

THE CP/M HANDBOOK (WITH MP/M)

88048A \$19.95
Containing a step-by-step description of all the CP/M command and features, the book progresses to detailed explanations of the file transfer program, the debugging program and CP/M's text editing program.

YOUR FIRST COMPUTER

88045A \$12.50
A beginner's guide to small computers, understanding them, buying them and using them for personal and business applications. Includes peripherals, languages and application packages.

DON'T (OR HOW TO CARE FOR YOUR COMPUTER)

88065A \$16.95
A guide to computer and peripheral preservation. Specific advice for the computer, floppy disks, hard disks, the CRT terminal, the printer, tape units, the computer room, software and documentation are included.

INTRODUCTION TO WORD PROCESSING

88076A \$17.95
Written for the non-technical reader, this book tells about concepts common to all word processing systems, then analyses all features in detail, from screens to scrolling and formatting.

SMALL COMPUTERS FOR THE SMALL BUSINESSMAN

39831A \$24.95
The book tells readers how and where to shop for a computer successfully; what to expect their computer to do for them; how to select software; whether or not to use a consultant; how to introduce the computer to the staff and how much computer is necessary.

INVENTORY MANAGEMENT FOR SMALL COMPUTERS

39848A \$24.95
Owners of retail businesses and their employees need this book. The program provides an inventory control system so that you know what stock is on hand, where it is located, what price was paid for it and the selling price.

BASIC FOR BUSINESS FOR THE TRS-80

90352P \$22.25
This book covers the application of BASIC language to business uses on the TRS-80 models II and III.

FROM THE COUNTER TO THE BOTTOM LINE

39811A \$24.95
A demystifying guide to basic accounting needs and computer use. Includes inventory and purchasing, billing, accounts receivable, accounts payable and general ledger.

amateur radio, DX, communications

INTRODUCTION TO RADIO ASTRONOMY
21246P \$8.75

It gives background information on the structure of the universe, classification of galaxies and radio-wave propagation. It covers in detail reception of extraterrestrial radio signals and their sources and the types of antennas. It also explains how to construct several practical, low-cost radio telescopes.

TUBE SUBSTITUTION HANDBOOK
21746P \$8.75

Complete, accurate, up-to-date guide to direct substitutes for receiving and picture tubes. Contains over 6000 receiving tube substitutes, over 4000 monochrome and colour picture tube substitutes, and 600 communications substitutes. Also includes pinouts for quick operational checks.

RF CIRCUIT DESIGN
21868P \$33.95

A practical approach to the design of RF amplifiers, impedance-matching networks and filters. Uses a minimum of complex maths.

COMPUTERS AND THE RADIO AMATEUR
66306P \$28.00

For the radio operator who wants to know how computers function and how they can be used with other equipment.

SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS
222B \$4.32

Design and construction of several solid-state shortwave receivers giving high level of performance yet utilising relatively few inexpensive components. See also 226.

HANDBOOK OF RADIO, TV, INDUSTRIAL & TRANSMITTING TUBE & VALVE EQUIVALENTS
BP2 \$2.25

Equivalents book for amateurs and servicemen. More than 18 000 old and new valves from UK, USA, Europe, Japan et al. CV (military) listings with commercial equivalents included.

RADIO CIRCUITS USING ICs
BP46 \$4.64

Describes how ICs can be employed in receivers for the reception of either amplitude or frequency modulated signals. Stereo decoder circuits and the devices available at present for quadrophonic circuits are discussed.

LONG DISTANCE TV RECEPTION (TV-DX)
BP52 \$6.56

Written by UK authority, the book includes many units and devices made by active enthusiasts. A practical and authoritative intro to this unusual aspect of electronics.

RADIO STATIONS GUIDE
BP55 \$5.92

This is an aid for all those who have a radio receiver. Shows the station site, country, frequency and/or wavelength, as well as Effective Radiation Power of the transmitter and in some cases, the station's call sign as well.

AN INTRODUCTION TO RADIO DXING
BP91 \$6.56

One section is devoted to amateur band reception and the other section covers broadcast band reception, with advice on suitable equipment and the techniques employed when using that equipment. The construction of a number of useful accessories is described.

AERIAL PROJECTS
BP105 \$6.56

Practical aerial designs including active, loop and ferrite which are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

INTRODUCTION TO AUTOMOTIVE SOLID-STATE ELECTRONICS
21825P \$14.95

For the professional as well as the home mechanic — explains the functions of most on-board automotive black boxes and logic systems, including anti-skid braking, electronic spark control, diagnostic systems and trip computers.

SECURITY ELECTRONICS
21419P \$11.25

The principles of operation of the electronic devices used in the various types of security systems are described. Intrusion detection and alarms, object detectors, burgling and debugging devices, computer protection, as well as the planning of systems.

ELECTRONIC SECURITY DEVICES
BP56 \$5.92

Besides including both simple and more sophisticated burglar alarm circuits using light, infrared and ultra-sonics, this book also gives circuits for gas and smoke detectors, flood alarms, fire alarms, doorphones, baby alarms, etc.

EXPERIMENTS IN ARTIFICIAL INTELLIGENCE FOR SMALL COMPUTERS
21785P \$13.25

Artificial intelligence is the capability of a device to perform functions normally associated with human intelligence. With this book, a small computer with extended BASIC and some knowledge of BASIC language, you can conduct interesting and exciting experiments in artificial intelligence.

TELEMATIC SOCIETY
02460P \$17.50

An extensive update of 'The Wired Society'; this book demonstrates how developments in telecommunications will affect the way we live.

ELECTRONIC CALCULATOR USERS' HANDBOOK
BP33 \$5.12

Presents formulae, data, methods of calculation, conversion factors, etc. for use with the simplest or most sophisticated calculators. Includes the way to calculate using only a simple four-function calculator: trigonometric functions; hyperbolic functions; logarithms; square roots and powers.

YOUR ELECTRONIC CALCULATOR AND YOUR MONEY
BP54 \$4.64

Starts with a basic revision of percentages and decimals, then deals with mortgages, cars, insurance, fuel, shopping, tax etc. There's a section on investment and the last section deals with the calculator in a small business.

general

AUTOMOTIVE TUNE-UP AND EMISSION CONTROL SERVICE
21712P \$20.75

Car owners who wish to save money and maintain their cars at peak performance will learn from this book how to adjust, repair and maintain the systems that ensure best operation.

ORDER FORM

Send to ETI Book Sales, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011.
Allow 4-5 weeks for delivery. Post & Handling \$1 per book. Effective until April 30, 1983.

Please supply:

BOOK TITLE	BOOK NO.	QTY	TOTAL PRICE
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....

Post and handling

I enclose TOTAL \$

Name:

Please debit my Bankcard

Expiry Date

Address:


American Express Card

Number

Postcode

Signature

These pages are intended primarily as a source of ideas. As far as reasonably possible all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.

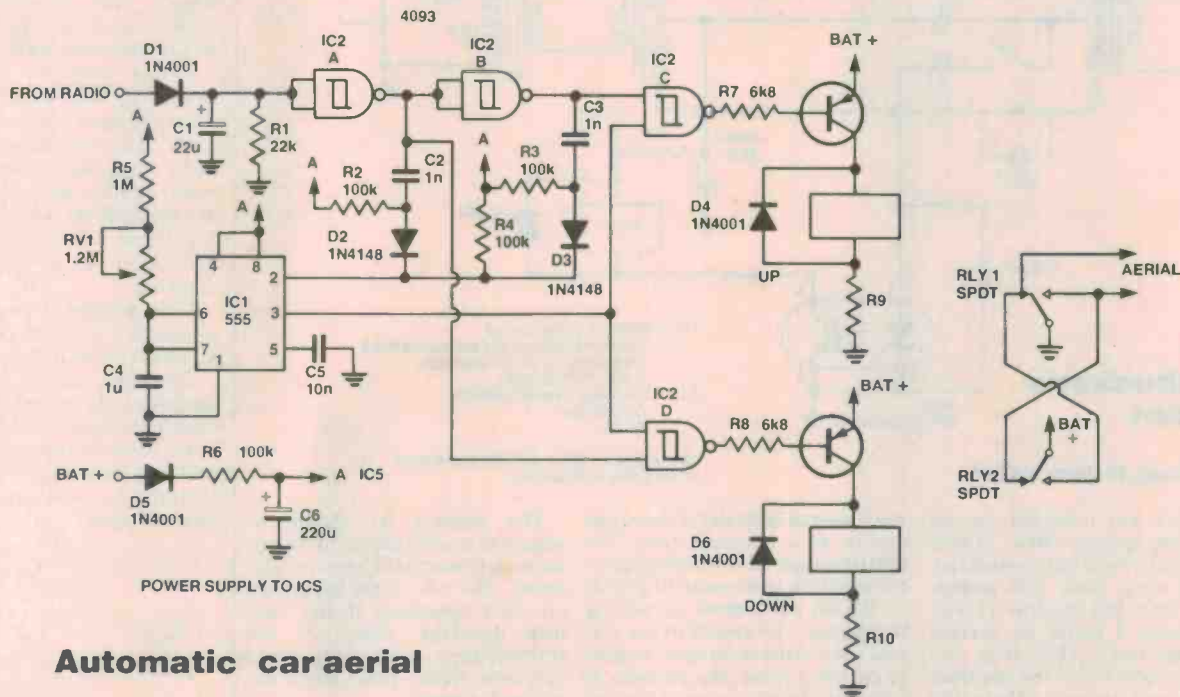

Automatic car aerial

This circuit will impress your friends and deter those dastardly vandals who seem determined to make us drive around with bent coat-hangers for radio aerials, says Steve Gagen of North Balwyn Victoria.

Electric car aerials can be bought quite cheaply, but they require a switch to make the aerial go up and down. You don't always remember to retract the

aerial when leaving your car, and that's when the vandals strike.

The circuit takes its signal directly from the on/off switch of the car radio. When the radio is turned on, C1 rapidly charges up, and a negative going pulse from IC2a triggers the 555. The positive signal from the radio gates the 555 to the 'up' relay, turning it on for a time determined by R5,


RV1 and C4 (adjustable between 1.1 and 2.4 seconds).

When the radio is turned off, R1 and C1 allow about a five second delay before the aerial retracts. This stops the aerial going up and down as you operate the self starter which cuts power to all accessories in most cars.

The diode-resistor-capacitor network in the IC power supply is to remove transients which may cause false triggering. It should

be left connected to the battery at all times, and not wired through the ignition switch. Since the ICs will draw less than 10 mA, battery drain is insignificant. The rating of the relays should be at least 5 A, preferably 10 A, since electric car aerials start with a tremendous current surge.

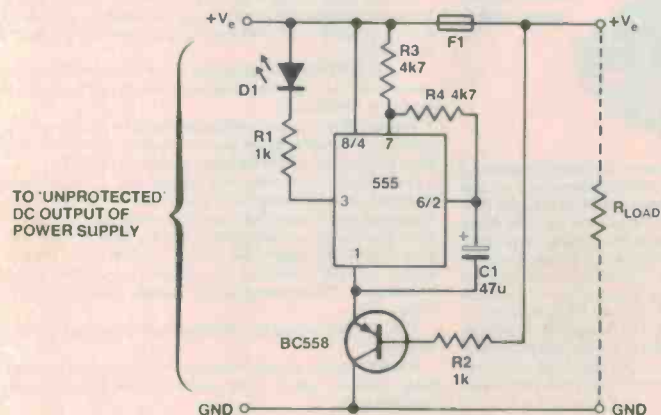R9 and R10 should be chosen to suit the relay. I have chosen the wiring for SPDT contacts, but DPST relays could also be used.



Fuse fail indicator


R.N. Sinclair of Coogee NSW sent in this circuit which indicates an open circuit fuse by flashing the LED D1.

The circuit is based around the popular 555 timer IC which is arranged as a multivibrator with its frequency/period determined by C1, R3 and R4. R1 is the current limiter for D1.

When the fuse is intact, the BC558 is off but when the fuse fails and there is an open circuit the BC558 switches on, supplying power to the input of the 555 (pin 1). A load must be present to switch the transistor on and consequently the LED.

The fuse fail indicator must not be used when the power supply is greater than 15 V.

IDEA OF THE MONTH

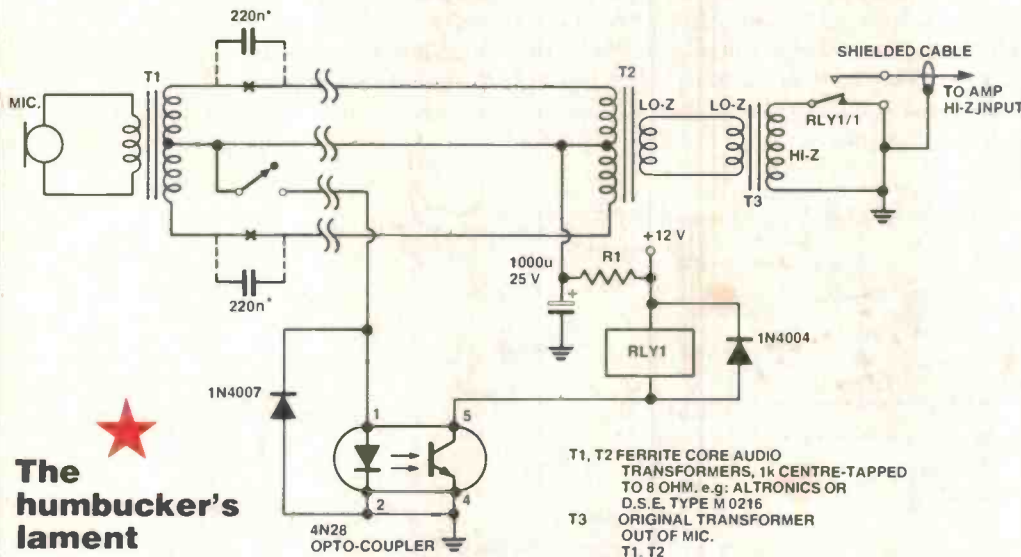

The humbucker's lament

W.C. Gregg, St. Mary's NSW

This idea was invented 'on the spot' when doing a labour of love at a school. A mic was needed in a remote area, some 200 metres distant from the amplifier. Looking around I found an unused telephone-type cable that ran from the room where the amplifier was located to near where the mic needed to be.

The circuit is pretty well self-explanatory. Two low-to-high impedance audio transformers

were used at each end of the cable, driven as a balanced line. The centre-tapped hi-Z windings gave me a dc link to do switching with — it's an old remote signalling technique. The switch in the mic was used to drive an opto-coupler to switch a relay, the contacts of which provided mic switching at the amplifier input. Using a relay switched directly via the line causes hum problems from pickup by the relay coil.

The resistor R1 should be adjusted to give about 10-15 mA current through the opto-coupler input. The two 220n capacitors are only necessary if any hum loop develops. Keep all the transformers away from stray magnetic fields. Don't earth the centre-tap wire.

This system has been used at distances up to 1 km. To the naked ear, there is no degradation in frequency response.

*CAPACITORS ONLY NECESSARY IF HUM LOOPS ARE A PROBLEM.

T1, T2 FERRITE CORE AUDIO TRANSFORMERS, 1k CENTRE-TAPPED TO 8 OHM, e.g. ALTRONICS OR D.S.E. TYPE M 0216
T3 ORIGINAL TRANSFORMER OUT OF MIC.
T1, T2


Etching tank

A discarded cordial bottle is a simple, but effective, etching tank as discovered by N.F. Bush of Canterbury NSW.

I was recently making up several pc boards and found that I did not have a suitable etching tank. The containers which I have used on other occasions were flimsy and etchant was always spilt all over the place. So I grabbed an old cordial bottle and cut it out as shown on the diagram.

I was amazed at how successful it was as I could move it around and didn't spill a drop.

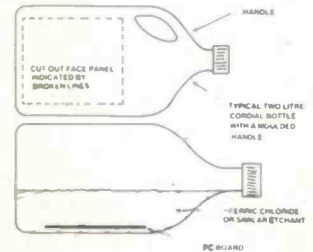The used etchant can be discarded easily by unscrewing the lid and pouring it out. There's not much mess to clean up afterwards and the bottle can be washed thoroughly and stored until needed again.



'IDEA OF THE MONTH' CONTEST

COUPON

Cut out and send to: Scope/ETI 'Idea of the Month' Contest, ETI Magazine, 15 Boundary St, Rushcutters Bay NSW 2011.

"I agree to the above terms and grant Electronics Today International all rights to publish my idea in ETI Magazine or other publications produced by them. I declare that the attached idea is my own original material, that it has not previously been published and that its publication does not violate any other copyright".
* Breach of copyright is now a criminal offence.

Title of idea
Signature
Name
Date
Address
Postcode



Scope Panavise Multi-purpose Work Centre.

Scope Laboratories, who manufacture and distribute soldering irons and accessory tools, have offered to sponsor a contest with a prize to be given away every month for the best item submitted for publication in the 'Ideas for Experimenters' column — one of the most consistently popular features in ETI. Each month we will be giving away a Scope Panavise Multi-purpose Work Centre, Model 376/300/312, comprising a self-centering head (376), standard base (300) and tray base mount (312), all worth about \$90! Selections will be made at the sole discretion of the editorial staff of ETI Magazine. Apart from the prize, each winner will be paid \$10 for the item published. You must submit original ideas of circuits which have not previously been published. You may send as many entries as you wish.

RULES

This contest is open to all persons normally resident in Australia with the exception of members of the staff of Scope Laboratories, Murray Publishing, Offset Alpine, Australian Consolidated Press and/or associated companies.

Closing date for each issue is the last day of the month. Entries received within seven days of that date will be accepted if postmarked prior to and including the date of the last day of the month.

The winning entry will be judged by the Editor of ETI, whose decision will be final. No correspondence can be entered into regarding the decision.

Winner will be advised by telegram the same day the result is declared. The name of the winner, together with the winning idea, will be published in the next possible issue of ETI.

Contestants must enter their names and address where indicated on each entry form. Photostats or clearly written copies will be accepted but if sending copies you must cut out and include with each entry the month and page number from the bottom of the page of the contest. In other words you can send in multiple entries but you will need extra copies of the magazine so that you send an original page number with each entry.

This contest is invalid in states where local laws prohibit entries.

Entrants must sign the declaration on the coupon that they have read the above rules and agree to abide by their conditions.

NEW PRIZE! WORTH \$90!



**SAVE ON STD PHONE CALLS. GIVE ROD A RING.
UP TO 6.30 PM WEEKNIGHTS TO PLACE YOUR ORDERS**

(Remember this service is for Phone Orders only)

AMDEK VIDEO MONITORS



- Green Phosphor
 - 12MHz B/W
 - Used by Telecom
 - Great Value
- NOT \$229
ONLY \$209**

INGERSOLL GREEN PHOSPHOR MONITORS

Update now, and add a touch of class to your computer.

- Features:
- 12 MHz B/W
 - Green Phosphor
 - Concealed Controls
 - 1 Year Warranty
- \$279**



TERMINAL WITH DETACHED KEYBOARD

Incredible Quality
Unbeatable Value
\$1099 inc. tax




BEAT MAINS INTERFERENCE WITH OUR LINE FILTERS



Easily mounted inside equipment with flying heads. Stop the glitches that destroy valuable data. Manufacturer enquiries welcome. Another High Tech Direct Import by Rod
\$12.25

PRINTER SPECIAL MICROLINE 80

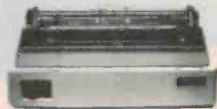An incredible little printer at an unbeatable price.



BUY TWO FOR
CHRISTMAS!
**\$499.00
inc. tax**

DISC DRIVES

- MPI 51 \$275 + 20% ST
- MPI 52 \$385 + 20% ST
- MPI 91 \$415 + 20% ST
- MPI 92 \$515 + 20% ST

MITSUBISHI DRIVES

8" Standard **\$679**

8" Slimline **\$699**

If you want two or more
"GIVE US A YELL!"

2 x 8" Slimline Case with power supply

(can also take 1 standard 8" drive)
Put your S.B.C. in bottom.



Power supply delivers
+5V @ 5A
±12V @ 1A
+24V @ 2A
**\$350.00 inc. fan
Bare case \$95.00**

5" Drive Cases with power supplies

For 1 drive **\$89.00**
For 2 drives **\$109.00**



KEYBOARDS

Clare C70 **\$169.00** Case with cutoff **\$85.00**
RCA **\$99.00**



VERBATIM FLOPPY DISCS

"We won't be beaten on price!"

	1-9	10+
MD525-01	\$3.95	\$3.60
MD525-10	\$3.95	\$3.60
MD525-16	\$3.95	\$3.60
FD34-100	\$3.95	\$3.75

5" UNBELIEVABLE VALUE!

SPEECH SYNTHESISER

	Our Price
DT 1050 National Digitalker and Romset	\$75.00
DT 1057 National Digitalker Second Romset Data Sheets included in chip sets	\$59.00

\$100 EXTENDER CORD

Plug into your S100 system and be able to check your board voltage lines are all fused.

\$49.50

ETI 640 VDU

Bare board \$59.00
Kit Price \$119.00
A + T \$139.00

WHAT ABOUT A STAND FOR YOUR PRINTER

Adjustable and sturdy.
Makes life a
"hell of a lot easier"
\$249.00



**BUY AN 8510P
FOR NEW YEAR
\$795.00 inc. tax**

WE HAVE UNBEATABLE PRICES ON SYSTEMS



Give Rod a ring and discuss what you need

ROD IRVING ELECTRONICS

Min. Pack & Post \$2.50

425 High St, Northcote 3070.
Melbourne (03)489-8131. Now also
at 48-50 A'Becket St, Melbourne.

MAGNIFICENT! NEW 5000

DAVID TILLBROOK HAS DONE IT AGAIN!! 5000 SERIES 1/3

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ 5000 SERIES GRAPHIC EQUALISERS



ALL IC
SOCKETS
PROVIDED



AUSTRALIAN (NOT HONG KONG)
MADE - SPECIAL BUILT RACK
CABINET - QUALITY!!!



SPECIFICATIONS:
Signal-to-Noise: -102dB
with respect to 1 Volt
Frequency Response:
12Hz - 105kHz to -1dB
Boost/Cut: 14dB (28dB
total)
Distortion: 100Hz-0.007%
1kHz-0.007%
10kHz-0.008%
(essentially irrespective of
cut or boost)
Current consumption (DC)
Approx 100mA @ ±15V
(Requires 30V AC CT)
Output short-circuit proof.

Latest addition to the thoroughbred 5000 Series stable! David Tillbrook has once again produced a 'No Compromise' design. This new component, a 1/3 octave equaliser, gives you ABSOLUTE CONTROL over the acoustics of your particular listening environment. You get 3 SEPARATE CONTROLS for every octave of audio bandwidth to virtually eliminate the subtle nuances that are particular to your listening area.

1/3 octave equalisers have been used by professional engineers in Recording Studios and live concerts for over a decade now. It is no accident that the advent of the 1/3 octave equaliser and studio quality live sound have gone hand-in-hand. BUT THERE'S A CATCH. One of these equalisers is not enough. You will have to buy 2 (for stereo). Quite a lot of money - but worth it if you want the best.

For those whose budget does not extend to \$389, may we suggest the 2010MkIIA octave (10 band) equaliser. This unit is rack mounted and in the same format as the 5000 series equaliser. It is stereo (in one 3 1/2" cabinet) with one slider per octave. Basically an upgrade of the ETI 485 graphic, it represents outstanding value for money at only \$139.00.

The Jaycar kit includes a fully prepunched plated chassis, prepunched heavy gauge front panel with silkscreened front panel to match the other 5000 components. It is absolutely original. You can purchase the kits one at a time for \$199 ea. or, for two, \$389 - a \$10 saving. If you are one of the hundreds of happy 5000 users we are convinced that you will be just as delighted with this unit.

BUY 2 AND SAVE \$10 - ONLY \$389

★ only ★
\$199

"BLACK MONOLITH"



ONLY
\$319

Once again, imitation is the sincerest form of flattery. The Black Monolith 5000 Mosfet Power Amp has the following EXCLUSIVE features:
- Beryllium Oxide (Space Age ceramic) TD-3 washers. (Not flimsy mica)
- Jig drilled and extruded heavy gauge, anodised heatsink bracket.
- SUPERFINISH front panel. STILL THE BEST now with blind tapped holes.
- New heavy duty heatsinks for the driver transistors. 100% extra heatsink area and black anodised for greater efficiency. (Not in original design).
- Ventilation holes in metalwork at critical points. (Not in original design).
- Extra 3 pin DIN socket on rear panel (total 2) to power new 5000 components. (1/3rd Octave 5000 series Equaliser coming soon!). Not in original design but now a must with the new additions in the family.

IF YOU THINK THAT YOU CAN SAVE MONEY ON THESE KITS ASK YOUR SUPPLIER IF HE WILL GIVE YOU ALL OF THESE FEATURES AT THE PRICE. MAKE SURE THAT YOU GET IT IN WRITING!!

A PRICE RISE ON BOTH KITS (i.e. SALES TAX AND METALWORK ETC.) IS EXPECTED SOON! BUY THE BEST FOR NO MORE.

Write in (ISAE) for a new glossy leaflet on both amps.

SPECIFICATIONS

POWER OUTPUT FREQUENCY RESPONSE

Around 100W RMS into 8 ohms
8Hz to 20kHz, +0 - 0.4dB
2.8Hz to 65kHz, +0 - 3dB
Note: these figures are determined solely by passive filters

INPUT SENSITIVITY

HUM

NOISE

2nd HARMONIC

DISTORTION

3rd HARMONIC

DISTORTION

TOTAL HARMONIC

DISTORTION

INTERMODULATION

DISTORTION

STABILITY

1V RMS for 100W output
-10dB below full output (flat)
-116dB below full output (flat, 20kHz bandwidth)
<0.001% at 1kHz (0.0007% on prototypes) at 100W output using a +56V supply rated at 4A continuous
<0.003% at 10kHz and 100W
<0.0003% for all frequencies less than 10kHz and all powers below clipping
Determined by 2nd harmonic distortion (see above)
<0.003% at 100W (50Hz and 7kHz mixed 4:1)
Unconditional

"BLUEPRINT"

5000 PREAMPLIFIER



'One Swallow does not make a spring'

- Neither does a few gold RCA sockets!

Several of our competitors are imitating our "Blueprint" preamp by adding a few bits and pieces, notably gold plated RCA sockets to their standard kits. Unfortunately they have missed the point. We supply gold plated sockets in our "Blueprint" preamp but only where it makes sense to do this, i.e. on the inputs - NOT the outputs. 16 gold sockets are provided by us. This, however, does not make a "Blueprint". THIS DOES:

- Low capacitance screened cable - 12 metres of it. NOT Taiwanese cable as supplied in other kits. Our cable costs us NEARLY 5 TIMES MORE than the Taiwanese stuff.
- Original ETI designed front panel. Not an "ADAPTION". Our front panel is by far the nicest.
- Factory pre-tinned PCB's to reduce chances of dry or noisy solder joints.
- Quality LEDs, polished finish, multicoloured display.
- IC sockets on line amp board.
- Special rear panel.
- Special low noise selection LM394H NOT CH device in M.C. preamp.
- Thermalloy (U.S. made) heatsink on 7805 regulator.
- English Lorlin selector switches.
- Apart from the 16 gold RCA's we throw in a pair of gold plated line RCA plugs - worth \$5.
- Special Nylon rear panel grommets.

So don't "Swallow" the facts before they are properly digested!!

You can't make a silk purse out of a sow's ear. Send SAE for full specs.



BLUEPRINT \$299

★ SPECIFICATIONS

Frequency Response

High level input: 15Hz-120kHz, +0 - 1dB
Low level input - conforms to RIAA equalisation
+0.2dB (see detail on Phono spec)

1kHz 0.003% on all inputs (limit of resolution on measuring equipment due to noise limitation)

High level input, master full, with respect to 300mV input signal at full output (1.2V)

92dB flat 100dB A-weighted

12dB input, master full, with respect to full output (1.2V) at 5mV input, 500 ohm source resistance connected

86dB flat 90dB A-weighted

MC input, master full, with respect to full output (1.2V) and 200V input signal

71dB flat 75dB A-weighted

ETI-478MM Moving Magnet input stage

Gain

Frequency Response

Total Harmonic Distortion

Noise

S/N ratio

ETI-478MC Moving coil input stage

Gain

Frequency Response

Total Harmonic Distortion

Noise

Total equivalent input noise

83mV flat, input shorted

62mV 'A', input shorted

56mV flat, after RIAA Eq. input shorted

36mV 'A', after RIAA Eq. input shorted

1, 1kHz, 10mV RMS input

Conforms to RIAA Equalisation +0.2dB

0.001%, 1kHz, 10mV RMS input

28dB with respect to 5mV RMS input signal.

Le. 135mV RMS

Total equivalent input noise, 122mV 'A', input shorted

216mV flat, input shorted

170mV 'A', input shorted

73dB 87dB 93dB

A-weighted 78dB 92dB 98dB

24

7Hz - 135Hz +0 - 1dB

0.003%, 1kHz, 30mV input

Total equivalent input noise

83mV flat, input shorted

62mV 'A', input shorted

56mV flat, after RIAA Eq. input shorted

36mV 'A', after RIAA Eq. input shorted

We regret to advise that we have been forced to increase our prices due to sales tax & component cost increases.

SERIES COMPONENT

OCTAVE GRAPHIC EQUALISER – BRILLIANT!!

FROM \$495



EX-STOCK
CALL IN AND SEE WORKING

JANUARY SPECIAL
If you order in January you will
get the console mount chassis
and power supply FREE! That's
right a \$98 saving! Hurry!!

8 CHANNEL MIXER KIT

The Jaycar 8002 Mixer was originally conceived to be the successor to the very popular ET114 Master Mixer. The 414 was basically configured as a 'stage' mixer and suffered from a number of severe technical limitations – notably poor signal-to-noise figures. Enormous advances in Audio IC's have occurred since the 414 was designed. Jaycar engineers have taken advantage of this. The incredibly low noise and distortion figures of the 8002 are a testimony to the sound basic design of the mixer coupled with the performance capability of these IC's. Whilst the 8002 is the ideal 8 channel compact stage mixer, other applications have been kept in mind. AS A "STUDIO" MIXER. The prime requirement of a studio mixer is that it must be quiet – i.e. have good S/N. Due to the fact that the "miracle" 5534 IC's are used in the 8002 studio applications are entirely feasible. In addition to this, metal film resistors are used in critical signal areas. AS A DISCO MIXER. The balanced input feature of the 8002 is not really necessary for disco use. This section can easily be bypassed with either a moving magnet (Dynamic Cartridge) preamp, or a moving coil preamp. The sensible format of the 8002 and tremendous equalization facilities should make this mixer popular for disco use.

- Balanced (600 Ohm) Mic. Inputs/Line Inputs.
- Cannon Connectors included in the price.
- Bass, Mid & Treble Equalization on each Input.
- "Effects" (i.e. Echo etc.) capability.
- Foldback and Stereo Pan on ALL 8 Inputs.
- 60mm Slide Faders used throughout.
- 19" Rack Mount capability (or Console Mount).
- Professional Black Front Panel with Format borders & multi-coloured knobs to assist function identification.
- VU Metering.

Send SAE for full details + details on use as stage mixer

MASSIVE BREAKTHROUGH! CAR COMPUTER BELOW \$200

COMPLETELY BUILT AND TESTED – NOT A KIT!!

Never before has such a comprehensive car performance computer been offered at such a low price!! Once again miracle microprocessor technology has enabled us to pass enormous savings on to you!! But don't let the low cost fool you. The "Voyager" car computer IS THE MOST COMPREHENSIVE PRODUCT THAT WE HAVE SEEN. No other car computer matches this one AT EVEN TWICE THE PRICE!! You could buy a \$20,000 Holden and not get a better car computer!! Just check the features. We are sure that you will calculate that the "Voyager" represents outstanding value!

IDEAL RALLY COMPUTER!

only \$179 complete

save 20%

FEATURES

- INSTANT FUEL CONSUMPTION IN LITRES/100KM AND MPG!! (MOST OTHERS HAVE ONLY ONE OF THE ABOVE) JUST SWITCH FROM ONE TO THE OTHER AS YOU DRIVE ALONG.
- INSTANT SPEED, TIME AND OTHER FUEL DATA.
- VISUAL AND AUDIBLE EXCESS SPEED ALARM.

INSTALLATION

The "Voyager" comes complete with an unbelievable array of mounting configurations, on dash, under dash or stalk mount. ALL installation hardware is supplied (even a roll of insulation tape!) as well, of course, as the speed and fuel sensors. A lavishly illustrated installation manual is provided as well as a comprehensive operators manual.

JANUARY SPECIAL
Because January is a "slow" month we've slashed \$20 off the very popular "Voyager" Car Computer! Hurry! This month only!

AS REVIEWED IN EA OCT. 1982 and ETI NOV. 1982



CONTAINS EQUIVALENT OF THOUSANDS OF TRANSISTORS – USES MASSIVE CUSTOM LSI CHIP TO ACHIEVE LOW PRICE

'super siren'

Incredible CMOS circuit drives a Motorola piezo horn (KSN 1038A) to achieve extremely high sound pressure levels. Makes a great alarm and only draws – would you believe – 5mA average? Runs for ages on a 9V battery. You can get the electronics including the PCB for only \$5.00. KSN1038A only \$17 extra.

Ref: EA 11/82 FROM \$5.00

Jaycar NUMBER 1 FOR KITS

125 York Street, Sydney 2000
Phone: 264 6688 Telex: 72293
"Nevilles Corner"
Cnr. Carlingford & Pennant Hills Road, Carlingford
Phone: 872 4422

Mail Orders To: Box K-39 Haymarket Sydney 2000

POST AND PACKING CHARGES
\$5-\$9.99 (\$1.20) \$10-\$24.99 (\$2.40) \$25-\$49.99 (\$3.50) \$50-\$99.99 (\$4.60) \$100 up (\$6.20)

NEW SHOP HOURS
Mon-Fri 8.30 to 5.30pm
Sat 8.30 to 12.00pm
Thurs night to 8.30pm



MAIL ORDER BY BANKCARD VIA YOUR PHONE

We will not cut costs by accepting inferior quality components.

YOU CAN PHONE CARLINGFORD ON 872 4444 AS WELL!

SHOPAROUND

This page is to assist readers in the continual search for components, kits, printed circuit boards and other parts for ETI projects and circuits. If you are looking for a particular item or project and it is not mentioned here, check with our advertisers.

ETI-488 60 W amplifier

Professor Cherry's practical realisation of the nested differentiating feedback loop technique he discussed in the October and November issues. This project employs readily available components throughout, even the MJ802 and MJ4502 output transistors are widely available.

At the time of going to press, two firms had indicated they'd be stocking kits. In Sydney, it'll be Jaycar; in Melbourne, Rod Irving Electronics. You might also try All Electronic Components in Melbourne.

If you're hunting up components, most are common stock items in electronics suppliers. The MJ802 and MJ4502 are available from All Electronic Components, Bilco (on order at press time), Magraths (now in A'Beckett St, Melb.), Raycross, Rod Irving Electronics and Ellistronics. Radio Parts have the MJ4502 in stock, but not the MJ802. Artwork for the pc board can be obtained by sending a stamped self-addressed, A4-sized envelope to:

ETI-488 pc board
ETI Magazine
15 Boundary St
Rushcutters Bay NSW 2011.

ETI-905 polyphonic organ

Serenade your sweetie as the sun sets slowly o'er the sea — or somesuch! Kits for this one will be available from Altronics in Perth, Rod Irving Electronics

in Melbourne and Jaycar in Sydney. No special components are used — but take heed of our notes on the pc board if you're contemplating doing the board yourself. Artwork can be obtained by sending a stamped, self-addressed, A4-sized envelope to:

ETI-905 artwork
ETI Magazine
15 Boundary St
Rushcutters Bay NSW 2011

ETI-334 Auto-tester

Just the thing to keep in the glovebox or toolkit. This one uses all standard, off-the-shelf parts so you should experience little trouble shopping around for those bits you don't have in your junkbox. Kits will be stocked by Electronic Agencies in Sydney, Rod Irving Electronics and All Electronic Components in Melbourne.

ETI-1510 points controller and remote indicators

This project is a follow-up to the ETI-1508 Model Railway Controller published in the last issue. It comprises two parts: a points controller capacitor-discharge power supply board and a remote indicator board. There's nothing unusual about any of the parts used, so if you care to make your own boards, the electronic bits should be available from your friendly local electronics shop. However, as a number of kit suppliers are stocking last month's train con-

troller (in one form or another), the same suppliers will be carrying the two ETI-1510 units as kits. These are: Altronics in Perth, Electronic Agencies and Jaycar in Sydney, Rod Irving Electronics and All Electronic Components in Melbourne.

Ritronics moves to city

Ritronics Wholesale, a division of Rod Irving Electronics, now occupies the premises at 48-50 A'Beckett St, Melbourne, just next door to the Oxford Hotel (ah, sweet memories of studentship at the Royal Melbourne Institute of Technology, just across the road. The Oxford provided a much-needed escape from the boring round of lectures and lecturers).

It seems that Melbourne's A'Beckett street, what with Magraths and Ritronics moving in, is starting to become a southern reflection of Sydney's York St, where no less than five electronics retailers are lined up cheek-by-jowl right in the heart of the city. Who next among Melbourne's famed electronics retailers will move into what is obviously a prized address?

Printed circuit board and panel suppliers

Almost every pc board ever published by ETI may be obtained from the following suppliers:

All Electronic Components
118 Lonsdale St
Melbourne Vic. 3000

RCS Radio
651 Forest Rd
Bexley NSW 2207

Panels, meter scales and dial faces may be obtained from:

E.D.C.
17 Elizabeth Ave.
Dulwich Hill NSW 2203

For pc boards produced over the past three to five years, the following suppliers generally keep stocks on hand:

Electronic Agencies
115-117 Parramatta Rd
Concord NSW 2137
and
117 York St
Sydney NSW 2000

Radio Despatch Service
869 George St
Sydney NSW 2000

Rod Irving Electronics
425 High St
Northcote Vic. 3070

James Photonics
522 Grange Rd
Fulham Gardens SA 5024

Jamal Products
P.O. Box 168
Victoria Park WA 6100

Sunbury Printed Circuits
Lot 14, Factory 3,
McDougall Rd
Sunbury Vic. 3429

Mini Tech
P.O. Box 9194
Auckland N.Z.

BILCO ELECTRONICS

SHOP 2, 31 PULTNEY STREET, DANDENONG, VICTORIA, 3175. TELEPHONE (03) 791 8655

FOR ALL YOUR ELECTRONIC COMPONENTS INCLUDING:

Resistors 1/4w 5% 5¢ each \$3 per 100. 4017B 95¢ each 74LS00 40¢ each

Pactec enclosure 145 x 90 x30 with battery compartment \$8.40 each

Lutron Digital Multimeter .5" L.C.D. \$78.50

.71mm Solder—20¢ metre or \$5.60 for 250g.


Rectangular Red Leds 18¢ each. Red—5mm LEDs from 12¢ each

Fujitsu 2716 2K x 8 EPROM \$5.40. 2732 32K ROM 300 N/S \$7.60

8116 16K DYN. RAM 200 N/S \$2.10

ALL PRICES INCLUDE TAX

Jumbo Sale

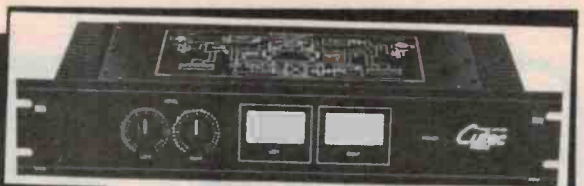

\$49 15W
PAIR 8 inch
2 WAY
speaker systems
at bargain prices!

Famous maker HI-FI SPEAKERS, alightly shop-soiled but otherwise A1, as used on \$400-\$500 HI-FI systems. We were selling these at \$79 PA, but now we need the warehouse space, so, out they go! Overall also 680x 295x230mm deep, weight 20 kgs. MAIL ORDERS: ADD \$25.00 FREIGHT ANYWHERE IN AUSTRALIA

60 WATT HORN TWEETERS

Imported "NOVIK" tweeters 4-20KHz with X'over capacitor
\$8 each
Square or rect.
Worth around \$16.00!

***Jackpot**
100's No 4
SOLD **\$15**
Last few avail now!

Our latest assortment of over 100's of specials, stamps, and off-line clearouts, manufactured over-runs etc. Jackpot No 4 has all new items - contents vary, but contain no less than 3 kpm weight, 460 worth for \$15

FM MIKE
~~\$21~~ **\$17**

Dual purpose, wireless or conventional mike with lead! Omni-directional, with electret

CAPACITORS "GOING CHEAP"

25,000uF .5v. \$2.50	5,500uF .75v. \$5.00
8,000uF .10v. \$2.50	11,000uF .75v. \$8.00
50,000uF .12v. \$4.00	30,000uF .75v. \$11.00
7,000uF .15v. \$3.50	2,500uF 100v. \$3.50
55,000uF .15v. \$7.00	6,800uF 100v. \$6.00
5,000uF .20v. \$3.50	13,000uF 100v. \$11.50
22,000uF .20v. \$7.00	2,200uF 150v. \$7.50
90,000uF .20v. \$9.00	3,500uF 150v. \$7.50
10,000uF .25v. \$4.00	1,800uF 200v. \$6.00
18,000uF .25v. \$6.00	4,800uF 250v. \$11.00
30,000uF .25v. \$7.00	OIL-FILLED PAPER
48,000uF .25v. \$8.00	4uF . . . 660VAC. \$3.00
80,000uF .25v. \$9.50	6uF . . . 600VAC. \$4.00
4,000uF .30v. \$3.50	8uF . . . 330VAC. \$4.00
19,000uF .30v. \$6.00	10uF . . . 660VAC. \$5.00
33,000uF .30v. \$7.50	
56,000uF .30v. \$8.50	
3,000uF .75v. \$3.00	
4,800uF .40v. \$3.50	
12,000uF .40v. \$6.00	
3,500uF .45v. \$4.00	
11,000uF .45v. \$6.50	
24,000uF .45v. \$8.00	
46,000uF .45v. \$10.50	
4,600uF .50v. \$6.00	
12,400uF .50v. \$8.50	
5,000uF .63v. \$6.50	
13,000uF .63v. \$9.00	
18,000uF .63v. \$10.00	

Ex-computer Guaranteed!
BUY 3, LESS 10%
BUY 10, LESS 20%
BUY 25, LESS 33%

**VIDEO IMPROVERS
DETAIL ENHANCER**

Specially designed to rectify loss in detail derived from VCR tapes and picture impairments. Ideal for off-air recording, dubbing from VCR to VCR etc. Outputs for up to 3 separate VCR's for multi-machine recording.
\$84.95

IMAGE STABILIZER
\$74.95

Stability control immediately stabilises picture of pre-recorded tapes, removing the copyguard signal. Also ensures no vertical roll or blackout will occur. Offers 2 video inputs (A or B), output for 1 VCR only. Limited quantity available at these fantastic prices.

RF-VIDEO SWITCHER
Multi-purpose use, very low loss, RF inputs for aerial, home computer, video games, VCR, etc.
\$39.50

Output: 75 ohms to TV set. beautifully styled, timber ends.
VHS VIDEO HEAD CLEANER CASSETTE \$15.99
BETA VIDEO HEAD CLEANER CASSETTE \$16.99

HIGH QUALITY, LOW LOSS VIDEO CONNECTING CABLES-

BNC plug to BNC plug, 75 ohm cable, 1.5m long	\$4.95
BNC plug to PL-259 connector, 75 ohm cable, 1.5m	\$4.95
PL-259 to PL-259 connector, 75 ohm cable, 1.5m	\$4.95
PL-259 connector to RCA plug, 75 ohm cable, 1.5m	\$3.95
RCA plug to RCA plug, 75 ohm cable, 1.5m long	\$2.95
RCA plug to BNC plug, 75 ohm cable, 1.5m long	\$4.35
NEC/SONY to other models, length 1.5m	\$9.55
SANYO to other models, length 1.5m	\$7.90
AKAI to other models, length 1.5m	\$8.85
PANASONIC (TECHNICS) to other models, length 1.5m	\$7.20
JVC to other models, length 1.5m	\$7.85
SABA/PHILLIPS/GRUNDIG to other models, length 1.5m	\$5.50
Camera cable, 10 pin plug to 10 pin socket, 5.0m	\$49.00
6 pin din plug to 6 pin din plug, length 1.5m	\$4.50

5 pin din to 5 pin din, reverse pins for video use	\$3.95
5 pin 180 deg. dubbing adapter, reverses pins	\$5.95
10 pin video camera male plug- suit VHS	\$9.95
10 pin video camera female line socket- suit VHS	\$9.95
14 pin video camera male plug- suit BETA	\$14.50
14 pin video camera female line socket- suit BETA	\$14.50
10 core video cable, for VHS or BETA, max. use to 30 metres, 2x75 ohm video, 2x shielded mike cable, 6 other carriers, grey PVC.	\$3.50 per metre

PROFESSIONAL STEREO PA AMPS
90W x 90W RMS
160W RMS MONO **\$399**

The BEST we've seen! All black, rack-mounted case with Cannon and phone plug inputs, 4mm banana and phone plug outputs, large dual VU meters, speaker output circuit protection and excellent specs for music or speech sound reproduction. Size 483x x 89H x 205D mm.

SPECIFICATIONS:
60 + 60W RMS at 8 ohms, 90 + 90W RMS at 4 ohms, 160W RMS MONO 8 ohms
Frequency Response: 20-50KHz Signal to noise ratio: 100dB
Damping factor: over 45 Total harmonic dist: less than 0.03%
Input sens: 0-0.5dB at 0dB-1V Cross modulation dist: less than 0.03%
Input Imp: 40K ohm (600 ohm line) 240V AC Input.

THE MODERN PHONE DIALER

•EASY INSTAL IN MINS
•ONLY 3 WIRES
•IVORY COLOUR
•FULLY G'TEED
•LED INDICATOR
•LAST NUMBER MEMORY REDIAL
If called number is engaged
Direct replacement for rotary dial.
Not approved by Telecom currently.

NOW ONLY \$25 EA
BUY 5+ \$22 EA.

PACK & POST
\$2.00 PLUS 5% OF ORDER VALUE

VOLUME CONTROL 75¢ ea.
15¢ ea. STEREO CARTRIDGE

ROCKER SWITCH 50¢ ea.
250V SPDT
DPDT MINI ROCKER 15¢ ea.

20¢ MAGNETIC EARPHONE
TUNING GANG 20¢ ea.
Jap. PVC 90/200pf replacement, suit most small radios.

FANS
Ex-computer
5 inch
115v \$8
220v \$10

SCOOP PURCHASE

NO MAIL ORDERS!
VDU WITH KEYBOARD \$60.00
NOT OPERABLE AS IS, BUT IDEAL CABINET, KEYBOARD, DISPLAY FOR HOME BUILDER, LOTS OF USEFUL PARTS ARE YOURS FOR A FRACTION OF THE NORMAL PRICE!
POWER SUPPLY UNIT \$45.00
PROBABLE WORKING ORDER, IN LARGE, ATTRACTIVE DESK-TOP CABINET WITH OVER 100 74 SERIES IC'S AND PLENTY OF EXTRA SPACE. 240V IN.

12V DC ROTARY SOLENOID STEPPING SWITCH
12 POSITION, SINGLE POLE, SHORTING.
\$12.99

Telescopic AERIALS
for TV's and pivots
170 to 875mm POPULAR TYPE
Pack of 10
*\$16
LAST FEW! BUY NOW.

SUPER SPECIAL OFFERS TOO GOOD TO REFUSE!

- 10uF 16vw, 47uF 16vw, 100uF 10vw caps ea. 3c
- 4.7uF 100vw, 22uF 100vw, 47uF 25vw caps ea. 10c
- 50uF 100vw, 220uF 16vw, 1uF 350vw caps ea. 15c
- 2.2uF 350vw, 330uF 35vw, 10uF 315vw ea. 20c
- 220uF 50vw, 400uF 40vw, 640uF 16vw caps ea. 25c
- 220uF 63vw, 330uF 50vw electro caps ea. 30c
- 15uF 500vw, 470uF 50vw electro caps ea. 40c
- 470uF 63vw, 15uF 500vw electro caps ea. 50c
- Transistor Substitute, Jap 1981 \$3.00
- 12v to 6.9, 12vDC 800mA car converter \$6.00
- 240v electronic lamp flasher 300W \$2.95
- Levon power mike with compression \$14.95
- 30MHz CB low pass filter stops TV1 \$2.50
- Quality Ralmar C-60 cassettes 2 for \$1.00
- 100yd rolls multi-strand hook-up wire \$3.00
- GE C37D 400v 35amp SCR's, stud mtg \$2.00
- 560uF + 47uF 160vw can electrolytics \$2.00
- NE-2 neons, 20c ea or 10 for \$1 or 100 @ \$8.00
- Phillips NT3100, NT3101 or NT3122 EHT transformers \$4.00 ea or 5 for \$15.00
- 3AG in-line fuseholders, now only 5 for \$1.00
- 8 ohm magnetic earpieces, 1m cord, 5 for \$1.00
- DPDT slider switches, PCB mtg. 7 for \$1.00
- 6.5mm stereo headphone sockets, 2 for \$1.00
- 3PDT rocker action switch, buy 3 for \$1.00
- uA741 TO-5 case op-amp IC's, 4 for \$1.00
- 25C-515A only \$1.00 ea or 250-198 only \$2.00
- EM-410 1000v lamp rectifiers, 8 for \$2.00
- 0.47uF Greencaps 100v, 10 for \$2.50, 50+ \$9.00

NEW TOROIDAL TRANSFORMERS
40V 1.2AMPS
PLUS 15V 200mA
Made in Sweden by TRANSDUKTOR
\$15

These high-efficiency Toroidal Transformers are only 80mm diam. x 33mm high. Regular price \$42.00

COMPUTER VDU & KEYBOARD
•240V AC MAINS
•GREEN SCREEN MONITOR
•KEYBOARD EASILY ENCODED
•SELF-CONTAINED CABINET WITH MODERN "SWEEP-BACK" STYLE

\$169

5 only ex-computer (from a famous manufacturer) terminals avail. for desk-top mounting. Late model, untested but assumed working. Standard video input to monitor, keyboard output easily interfaced to hobbyist computer. MAIL ORDERS - FREIGHT \$35 ANYWHERE!

PRE-PAK electronics p/l

1a WEST ST, LEWISHAM, NSW

569-9797
24 HR PHONE ORDER SERVICE

SEE THE HUGE RANGE IN-STORE!
IF YOU THINK WE PACK A LOT INTO OUR ADS, YOU SHOULD SEE WHAT'S IN OUR SHOP!

JIL SX-200, A BETTER SCANNING MONITOR RECEIVER.

Covers 26-88 MHZ & 108-180 MHZ
& 380-514 MHZ



Monitors over 33,000 frequencies from 26 to 88 MHz, 108 to 180 MHz and 380 to 514 MHz. Bands included within this range are HF and UHF CB, 27 and 155 MHz MARINE, Australian LOW BAND, AIRCRAFT band, VHF SATELLITE band, 10 Mx, 6 Mx, 2 Mx and 70CMx AMATEUR BANDS, VHF High BAND as well as UHF two-way band.

Mechanically rugged the SX-200 uses high quality double-side Epoxy-Glass printed circuit boards throughout. Some of its other outstanding features include 3 MODE SQUELCH circuitry which allows the lockout of spurious and carrier only signals, extremely low spurious count, AM and FM detection on all bands, FINE TUNING control for off channel stations, 240 VAC on 12 Volt DC operation, Accurate QUARTZ CLOCK, Squelch operated OUTPUT for switching a tape recorder etc, 16 Memory channels, MEMORY BACKUP which lasts up to two years, high SENSITIVITY and SIGNAL-TO-NOISE ratio on all bands, CRYSTAL FILTER for excellent SELECTIVITY and easy serviceability due to component layout as well as a 90 day warranty.

Its high quality and performance is testified by the fact that it is in use by a large number of State government and Federal bodies including most state and federal police departments.

Contact GFS, the Australian Distributors, or our interstate outlets for full technical specifications.

We also market a range of pocket scanning receivers and transceivers. Contact us for full details.

PRICE \$525 INCL S.T. + \$8 P&P
SERVICE MANUAL \$10 + \$1 P&P
SCAN-X BASE ANTENNA \$54 + \$8 P&P

Interstate Dealers:
WA: (09) 387 4966
NSW: (02) 211 0531
QLD: (07) 397 0808
SA: (08) 269 4744


GFS Electronic Imports

15 McKeon Road
Mitcham, 3132 Vic
TLX 38053 GFS
(03) 873 3939

I M A R K for JAPANESE ICs & TRANSISTORS

OEM Quantity prices available

NEC

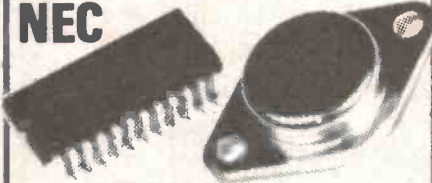

SANKEN



OKI



TOSHIBA



HITACHI



SANYO



MITSUBISHI



MATSUSHITA



FUJITSU

Send for price list

I M A R K

PTY. LTD.

167 Roden St., West Melbourne,
Victoria 3003

Phone: (03) 329 5433 Telex AA37753

SYNERTEK SLASH LS1 PRICES

Check these for real value.

1791-02 Floppy Disc Controller.....	\$28.19
2661-1 Sync/Asyn ComsIF.....	\$12.53
6502 CPU on chip clock.....	\$5.17
6522 Two 8 bit parts, two 16 bit timer counters, 8 bit shift register.....	\$4.54
6532 128 Bytes RAM, two 8 bit Ports interval timer.....	\$6.26
6545-1 CRT controller for Raster Scan Displays.....	\$10.41
6551 ACIA with SW prog. baud rate....	\$6.42

NEW PRODUCTS

EPSON MX 80 TYPE 111.....	\$740
SYM-1 Users group floppy disc controller kit with DOS source & drive cable.....	\$259
KTM 2/KTM 2-80 case.....	\$39
PSI Four output power supply for AIM 65 5V @ 5A adjustable: Ferguson C126 Transformer. +12V @ 1.5A; -12V @ 1.5A; 24V @ 0.5A. Open frame.....	\$109

SPECIAL PACKAGE DEAL

A65-450 AIM65 4K with FORTH. Normally \$106.83.....	NOW \$540.54
--	--------------

**energy
CONTROL**

P.O. BOX 6502,
GOODNA, 4300,
AUSTRALIA.
PH: (07) 288 2757

Prices for prepaid orders plus tax if applicable.

Software Source Pty Ltd.

89 OXFORD ST.,
BONDI JUNCTION
PH: (02) 389 6388 P.O. BOX 364,
EDGECLIFF 2027

SOFTWARE AND PERIPHERALS FOR THE SORCERER

WRITE FOR

FREE

CATALOGUE

New amateur bands gaining ground, but some losses

British amateurs have been granted the use of 18 and 24 MHz, but some have lost the use of 431-432 MHz while US amateurs have at last been granted use of 10 MHz. Also, British Class A licence holders can now use 50-52 MHz.

British amateurs were granted use of the 'new' 18 and 24 MHz bands, established by WARC '79, on 1 October '82 on a non-interference basis. Operation is CW (A1A) only, maximum antenna gain in any direction is limited to 0 dB over a dipole, horizontal polarisation only. Power is limited to 10 W to the antenna. Band limits are 18 068 — 18 168 kHz, and 24 890 — 24 990 kHz.

The sub-band 431-432 MHz has been allocated to private mobile radio services in the London area and UK amateurs have been requested to voluntarily vacate this segment within 100 km of central London.

However, in a surprise move, the British Home Office has released the use of 50-52 MHz to a limited number of Class A licencees for research purposes outside broadcasting hours on a non-interference basis (i.e. night time).

US amateurs were granted use of the 'new' 10 MHz band on 28 October '82. Those holding

General, Advanced or Extra Class licences can use CW and RTTY from 10 100 kHz through 10 150 kHz, except for the segment 10 109-10 115 kHz which is withheld for government services

in the US. Maximum power permitted US amateurs on the band is 250 W input to the final transmitter stage, not including valve filaments.



New frequency counters

A new range of compact, portable, high accuracy solid-state frequency counters, with crystal controlled timebases is now available from Global Specialties Corporation.

Bringing laboratory accuracy to the workshop or field, the three frequency counters consist of:

Max 100 — 100 MHz frequency counter. It measures 5 Hz-100 MHz and features an easy-reading, bright eight-digit LED display, direct reading with 1 Hz resolution. The Max-100 comes complete with clip lead input cable. Take it anywhere, run it on internal rechargeable batteries or from your car cigarette lighter socket or any external 7.2-12 Vdc supply.

Max-550 — a wide range, 1 kHz counter in a calculator-sized case.


The **Max-50** — provides economy and precision in a pocket-sized instrument and measures 100 Hz-50 MHz.

Any frequency counter of 50 MHz can have its range extended up to 500 MHz and above by using the PS-500 prescaler.

It features a BNC input connector, diode protected 50 ohm input, and claimed 250 mV sensitivity from 50 to 500 MHz. Its output is quoted as minimum 400 mV (peak-to-peak) capacitively coupled, available at a phono jack connector. Direct or 10 prescale outputs are switch selectable.

Power is supplied to the PS-500 through a coaxial dc-type power connector.

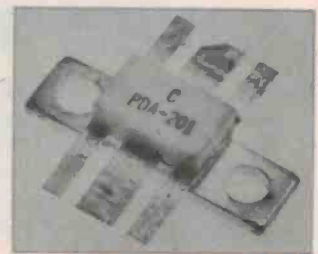Global Specialties Corporation is represented in Australia by **Vicom International Pty Ltd**, 57 City Road, South Melbourne Vic. 3205. (03)62-6931.



Unique 1 GHz hybrid power amp chip

Communications Transistor Corporation has produced a device described as a 'universal building block' for medium power RF circuit operation at frequencies up to 1 GHz and power level to +27 dBm.

Designated PDA 201, the device is a differential amplifier employing three matched 1 W/3 GHz transistor chips housed in a beryllium oxide stripline package for efficient heat dissipation.

Differential amplifiers are used as building blocks for most small-signal linear integrated circuits. But Communications Transistor Corp saw a need for a differential amplifier that could handle large signals at high frequencies and perform many circuit functions that are difficult and costly to implement with discrete components.

The 201 provides tightly matched and thermally coupled active elements for stable operation and excellent common-mode rejection. It can be combined with a few external components to solve many rf design problems, such as:

- Wideband amplifiers covering several octaves.
- Class A linear amplifiers with very low intermodulation distortion.

Minimum gain is specified as 25 dB with a 4 dB noise maximum, though typical figures are 28 and 3.5 dB. Maximum operating voltage is 18 V and source current is 250 mA maximum (the other figures cited here represent operating conditions of 200 mA with a 15 Vdc supply). Output compression of 1 dB does not occur until output reaches 26 dBm, and the third-order intercept is typically at 40 dBm.

The PDA 201 hybrid circuit is available from stock for a price of US\$50 each in 100-piece lots. CTC is a subsidiary of Varian Associates, 301 Industrial Way, San Carlos, Calif. 94070 USA.

UHF-SHF switches

Addington Microwave Components and Semiconductors has available solid-state single-pole multi-throw switches with octave and greater bandwidths operating within the frequency range of 0.5 to 18.0 GHz.

These units are designed to operate under stringent military environmental conditions and are used extensively in EW, ECM, communications, and missile applications.

Integral drivers, which are TTL compatible, are available as an option.

Contact **Eaton Corporation, Addington Microwave Components & Semiconductors**, 680 West Maude Ave, Sunnyvale CA 94086, USA.


YOUR MONEY BACK

PLUS \$5 If Altronics Jetservice Delivery is not the Best in Australia

ORDER FROM ALTRONICS WITH COMPLETE CONFIDENCE. Compare this check list with any other Australian Electronics Supplier ... ★ Delivery Time ★ Packing ★ Product Quality ★ Value for Money ★ Technical Queries Answered ★ Prompt Back Order Advice of not in stock items.
If after receipt of your Jetservice order you are not convinced Altronics service is superior to any other Australian Electronics Supplier you may return your purchase to us for a full refund plus \$5 for your trouble.

Regards

Jack O'Donnell

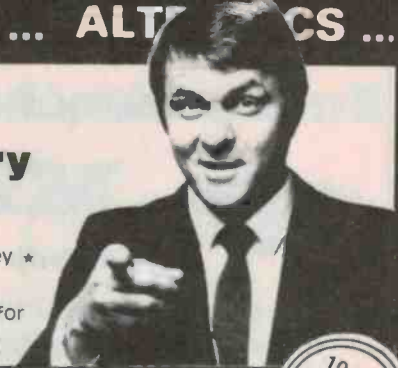


10 Hz - 20 MHz BAND WIDTH

See EA November, 1982

POWER UP

A MUST FOR YOUR COMPUTER SYSTEM

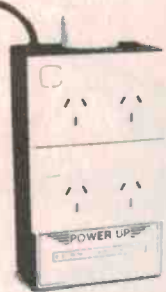

This great new Project from EA is the answer to a Maidens Prayer.

What Does it Do?

A single 240v mains plug and lead feeds one unswitched master 240v outlet plus 4 switched 240v outlets. With say a hi-fi system, plug your main equipment item (e.g. Amp) into the master outlet and whenever you "switch on" your amp - presto - mains power is applied to the other 4 outlets i.e. simply "turning on" your amp turns on your tape cassette, tuner, turntable, graphic equaliser without mains spikes, plops etc.

Just the shot for your Computer System. The Altronics Kit includes case and all outlets.

Cat K600. \$39.50

The Brilliant New MICRON 12 Green Phosphor Monitor

Features 12 inch Screen, Front Controls On/Off, Contrast/Reverse, Brightness, Power 240V/50Hz or 12V DC, Input RCA Type, DC Output Jack 12V/1.1 AMP - power your Micro direct without a power pack, Bandwidth 10Hz to 20MHz the resultant definition is truly amazing for a low cost monitor.


GUARANTEED BY ALTRONICS! Incredible Value

Cat D1112 \$199.50



MICRON D1120

WHY PAY OVER \$80

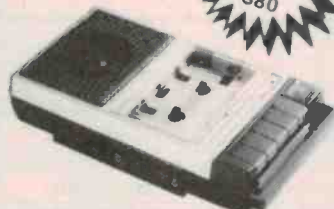

Adjustable Azimuth DATA CASSETTE


At last a Data Cassette Recorder/Player you can afford. The Micron D1120 is fully adjustable azimuth (absolutely essential in our opinion) and incorporates tailored audio frequency response audio stage together with low distortion.

Now you can save and load software in your Micro with confidence.

Micron D1120 Data Cassette Only \$49.50

NEW HITACHI F SERIES SQUARE SCREEN DUAL BEAM CRO

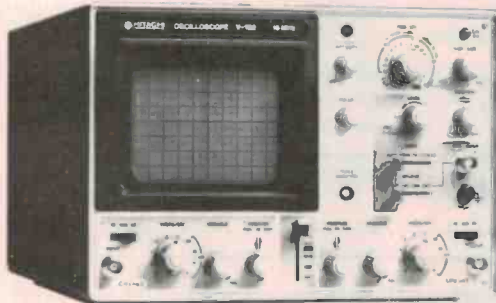SUPERB NEW MODEL V152F DC TO 15 mHz 1mV/DIV DUAL TRACE



FREE DELIVERY ANYWHERE IN AUSTRALIA THIS MONTH

CAT Q0152
PRICE ONLY
\$529⁵⁰ TAX EXEMPT
\$599⁵⁰ TAX PAID

Features ★ X-Y Operation ★ Vertical sensitivity 1mV/div. ★ 10 x Sweeptime magnification with 1-touch operation ★ Convenient CH1 signal DVM output ★ Z-axis Input provided - possible to use as CRT display ★ 0.2us to 0.2s - wide sweep range setting ★ Five modes of vertical operation ★ Panel layout with colour coding of respective functions.

SPECIFICATIONS

• Vertical deflection Sensitivity 5mV/div to 5V/div -5%, 10 calibrated steps 1mV/div to 1V/div -5% (When using x5 amplifier) Uncalibrated continuous control between steps 1 - 25 (provided with click-positioning function)

Bandwidth DC to 15MHz, -3dB (at 4div) DC to 7MHz, -3dB (at 4div) (When using x5 amplifier) 24ns, 1flor x51 20ns typ


Rise time Signal delay time

Max. input voltage 600Vpp or 300V IDC - AC peak, at 1kHz AC, GND, DC Detect 1M ohm, approx 30pF CH1, CH2, DUAL, ADD, DIFF CH1 X axis, CH2 Y axis 5mV/div to 5V/div (when using x5 amplifier, 1mV/div)

Phase difference X bandwidth Dynamic range CH1 output Output voltage Band width Output impedance

• Horizontal deflection	AUTO, NORM, TV (+), TV (-)
Trigger modes	CH1, CH2, LINE, EXT
Trigger source	AC
Trigger coupling	TV sync-separation circuit
TV sync	1div or more IV sync-signal
Internal	1Vpp or more IV sync-signal
External	
Trigger sensitivity	Frequency Internal External
	20MHz to 2MHz 0.5div 200mV
	2 to 15MHz 1.5div 800mV
AUTO low bandwidth	30Hz
Trigger slope	Input impedance approx 1M ohm, 30pF or less
External trigger input	Max. input voltage 100V
Sweep time	IDC - AC peak, at 1kHz) 0.2us/div to 0.2s/div -5%
	19 calibrated steps
	Uncalibrated continuous control between steps 1 - 25 (provided with click-positioning function)
	10 times (-7%)
	100ns/div 120ns/div and 50ns/div, not calibrated
• Sweep time magnifier	
Max. sweep time	
• Amplitude calibrator	Approx 1kHz ±10% (typ), square wave
Waveform	0.5V ±5%
Voltage	
• Power requirements	100/120/220/240V ±10%
	50 to 60Hz approx 40W
• Dimensions	Approx 775(W) x 190(H) x 400(D)mm
• Weight	Approx 8.5kg

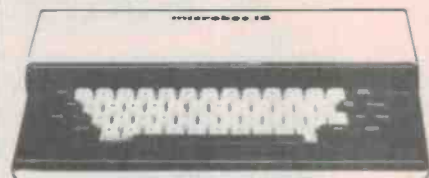The Famous Microbee Microcomputer in stock now at Altronics



★ 16K PLUS PACKAGE ★

Full 16K Microbee including Power Pack, Battery Backup (allows you to store programme "on board" for months at a time), Parallel Port fitted. Fantastic Value!

Cat D1018 \$449.00

★ EDITOR ASSEMBLER OPTION ★ Includes Handbook

Cat D1030 \$59.50

★ WORD PROCESSOR ROM PACK ★

Cat D1035 \$89.50

★ 16-32K UPGRADE PACK ★

Cat D1040 \$125.00

★ 32-64K UPGRADE PACK ★

Cat D1045 \$175.00

Call in for a demo of the fantastic Microbee at Altronics Computer Centre 105 STIRLING STREET, PERTH.

For Address, Phone No. and Despatch details see our Double Page Advertisement pages 28 29

ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ...

ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ... ALTRONICS ...

Emona launches a *NEW...*



Micro-Professor MPF-II

A versatile personal computer for people from the age of 7 to 70

The Micro-Professor MPF-II is the perfect computer for modern homes. All the features that a home/personal computer can have are packaged in the compact, portable MPF-II. Yet, the booksized computer has some other unique features that you cannot find on other computers.



FOR ONLY

\$499

+ Sales Tax

SPECIFICATIONS OF THE MPF-II

CPU	R6502	
ROM	16K Bytes	
RAM	64K Bytes	
BASIC Interpreter	More than 90 Instructions stronger than those for Apple II.	
Video Display	Type	Memory mapped into system RAM.
	Mode	Text low resolution graphics, high-resolution graphics (three modes are mixed).
	Screen Format	960 characters (24 lines, 40 columns).
	Character Type	5 x 7 dot matrix.
	Character Set	Upper case ASCII, 64 characters.
	Graphics Capacity	1920 blocks (low resolution) in a 40 by 48 array. 53760 dots (high resolution) in a 280 by 192 array.
Numbers of Colors	6 colors.	
Keyboard	49 alphanumeric and function keys.	
Cassette Interface	Use various cassette tapes and cartridges as data storage units.	
Software Cartridge Interface		
Printer Interface	Connects to printers with Centronic Interface.	
Display Interface	Connects to color home TVs or video display.	
Remote Control Paddle	Used for education & entertainment.	
Speaker	8Ω, 2¼ inches, 0.25W	
Power	A switching power supply is provided to convert AC power to required power supply.	
Dimensions	9.84 x 7.16 x 1.24 Inches	

- You can use the MPF-II in the home, school, engineering applications or just for fun.
- The MPF-II can be connected to any colour TV and cassette recorder.
- Options include video monitor, thermal printer, full size keyboard remote control pad, RS 232C interface board, Floppy Disk Drive, speech synthesiser board, sound generation board, Chinese character controller and a host of software cassettes and cartridges.

For further information please contact:

Sole Australian Agent



EMONA ENTERPRISES PTY. LTD.

CBC Bank Bldg, 661 George St., Haymarket, Sydney (02) 212 4815 or 211 3038

TRADE ENQUIRIES WELCOME

Also available from:

N.S.W. David Reid Electronics 29 6601 VIC. Radlo Parts 329 7888 S.A. Int. Communication Systems P/L 47 3688 W.A. Henco Engineering P/L 381 4477 A.C.T. Electronic Components P/L 80 4654 TAS D&I Agencies 23 2842

COMPUTING TODAY

New portable computer from Hewlett-Packard

This new personal computer, the first of its kind from HP, is the size of a notebook and features BASIC language programming power and software such as VisiCalc and graphics presentation.

The HP-75C functions as a portable computer by itself, as part of a portable system with compact briefcase peripherals or as a desktop personal system. It measures 254 mm x 127 mm x 32 mm and weighs only 737 grams. It has the ability to run on batteries and retain memory while turned off. It is powered by three rechargeable nickel cadmium batteries which are good for two to three weeks of normal use.

The HP-75C features 16K RAM built-in which can be increased to 24K with the plug-in 8K memory module. Three plug-in ports accept 8K or 16K ROM modules and there's a 48K ROM built-in operating system. The operating system features 169 instructions of which 147 are BASIC commands, statements or functions.

A built-in Interface Loop (HP-IL) allows communications

with instruments, peripherals such as printers or graphics plotters and other computers. Touch-typing is possible on the typewriter-like keyboard. A 32-character, liquid crystal display serves as a movable window on a 96 character line and features character descenders.

The HP-75C has a manually operated mass storage system consisting of long, thin strips of magnetic card which you pull through a magnetic card reader. These cards provide 1.3K of storage each.

Software available is for specific applications such as engineering, math and statistics and general solutions such as electronic spreadsheets and graphics presentations.

For further information contact Peter Delbridge, Hewlett-Packard, 31-41 Joseph St, Blackburn Vic. 3130. (03) 890-6351.

Loan helps build super microcomputer

A \$700 000 loan from a State instrumentality will help a Melbourne company manufacture a locally designed microcomputer which is claimed to be technologically years ahead of international competitors.

The loan from the Victorian Economic Development Corporation is one of the largest it has given and is in accordance with the Government's policy to encourage the development of high technology industries in Victoria.

The computer, known as Unison, will be manufactured by L & L Australia Pty Ltd at its

new Kilsyth plant and was designed by Mr. Bill Hollier, a computer scientist from Melbourne University.



Unison will be available in three basic forms. In its largest and most expensive form it is the size of a suitcase and can accept input from 32 screens and can perform instructions at a speed approaching that of the large

mainframe computers. It is regarded as the start of the next generation of microcomputers in that it takes up the same space as existing micros while its performance is compatible with the larger mini computers.

The company plans to manufacture 5000 units a year and it is aiming to sell to the education and scientific markets, offering

special financial incentives to schools.

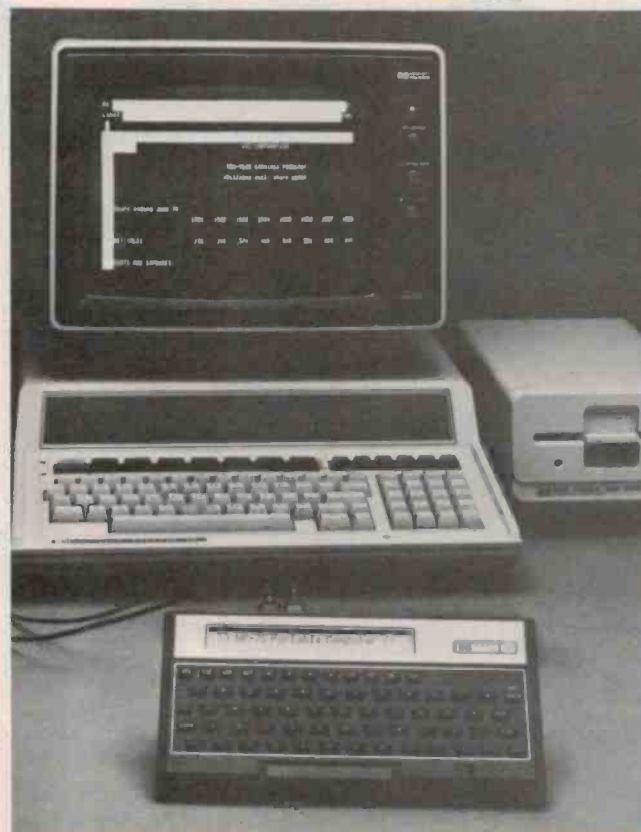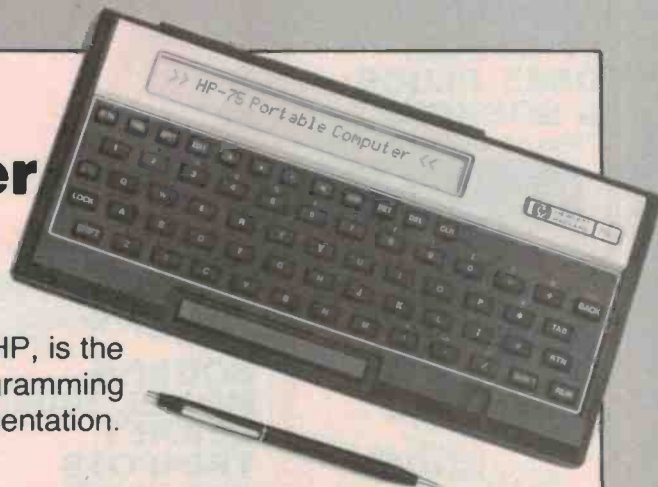As to what the capabilities and features of the computer are, that is left to your imagination, as the Victorian Economic Development Corporation did not give us any information. So we don't know whether it is as good as they claim it to be. ■



SUPER LOW PRICES



**AMPHENOL
17 SERIES
DB25 PLUGS
& SOCKETS**

Plugs \$2.45 Sockets \$1.85



**SPEAK & SPELL
IS HERE**

as featured in

E.T.™

\$110.00
INCLUDES SALES TAX

E.T. PACK INCLUDES

- One Speak & Spell learning aid
- The new E.T. Fantasy Module
- New photo-filled activity book
- Colorful movie poster
- T-shirt decal with E.T. and Elliot

**MEMORY
BARGAINS**

- HM6116P-3 (HITACHI) 2Kx8 CMOSRAM \$7.50
- MB2716 (FUJITSU) 2Kx8 EPROM \$3.00
- MB2764 (FUJITSU) 64K EPROM \$12.00
- MB8118 (FUJITSU) 16K DYNAMIC RAM (Intel 2118) 120ns \$4.00


**INDUSTRY
STANDARD**

**BOURNS
MODEL 3006P
CERMET
TRIMPOTS**

15 TURN 1.25 WATT
ALL POPULAR VALUES

Standard Range ~~Was \$1.60~~
100 OHM-1 MEG **\$1.10 ea.**

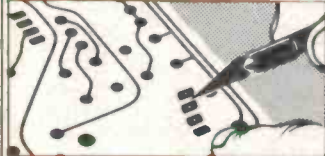**MAGRATH'S —
THE ONLY CITY SOURCE**
Now you can make professional
quality PC artwork and boards



E-Z CIRCUIT™
BY BISHOP GRAPHICS INC.
**PRESSURE SENSITIVE
DRAFTING AIDS**

Ideal for small volume OEM
users, Consultants,
Breadboarders, Experimenters,
Designers, Hobbyists Bishop
quality in small, economical
packages.

CHRISTMAS SPECIAL
**Professional
Video
Monitor**

~~Was \$227~~
\$199

18MHZ Video Bandwidth
BM-12E

- Input Signals: Composite Video Signal Negative SYNC 1.0 P-P 75 ohm
- CRT size: 31 cm diagonal
- Green Phosphor — P31 non glare
- Power input 230V 50Hz
- Display format: 1920 characters max. (80 characters X 24 lines)

**TI PERSONAL HOME
COMPUTER**

TI-99/4A

\$499.00 INCLUDES SALES TAX



**You can buy just a
video game — or you
can get a full colour
Home Computer**

- Typewriter Keyboard
- 16K bytes RAM
- Expandable to 52K bytes RAM
- Easy to follow Instructions
- Extensive range of programmes
- Educational
- Add-on expandability



**HIGH QUALITY,
LOW COST,
DO-IT-YOURSELF
BOOKSHELF
SPEAKER SYSTEM**



RUDAX
The Compact 200

Speakers, Electronics Kit **\$199**
Cabinets (per pair) **\$99.50**

**MAGRATHS MONEY SAVERS
SEMICONDUCTORS**

See 6 pack Specials for super prices. on asterisked products.


4011B	19c	*74LS04	20c	*LM340T.5	51c
*4016B	30c	*74LS14	40c	LM340T.15	60c
4023B	19c	74LS47	72c	LM386N	60c
4028B	55c	*74LS90	42c	LM555	25c
*4066B	44c	74LS161	53c	LM741N DIP	23c
*4511B	69c	81LS95	87c	LM741 DIP	36c
4520B	74c	81LS98	88c	*74C02	20c
7406	20c	LM301A DIP	35c	*74C89	\$1.50
7414	33c	LM308 DIP	49c	*74C107	30c
7416A	48c	*LM324	42c	*JA317UC REG.	\$1.20
74365	37c	LM339 DIP	42c	*KBPC602 6A 200V BR.	\$1.00
*74LS00	20c	*LM340KC.12	\$1.20	*S6006L 6A 600V SCR	80c

**TI CALCULATORS
FROM MAGRATH'S**

- FINANCIAL
- SCIENTIFIC
- STUDENT

TI-35 Student math kit **\$27.00**
TI-54 Engineers & Science **\$45.00**
TI Business Analyst II **\$50.00**

PRICES INCLUDE SALES TAX

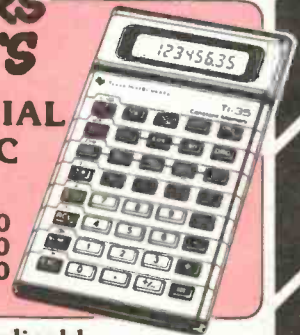

Add Sales Tax if applicable
Prices valid until stock sold.
Prices subject to alteration

Visit us at our new address
**55 A'BECKETT STREET
MELBOURNE, 3000.**
Tel (03) 347 1122



SUPER BARGAINS AT MAGRATHS

Microprocessor design tools and selection seminars

Tektronix has announced a Microprocessor Design Tools seminar which will focus on the hardware and software tools required to develop the microprocessor for a particular application.

The one-day seminar will cover the usage of Universal Development Systems with software tools like PASCAL language directed editors, compilers and debug. The UNIX operating system and hardware tools such as high speed transparent emulators and universal logic analysers will also be discussed.

The seminar will be a full-day event, held in Sydney on February 22, and in Melbourne on February 8, and is intended for engineers and managers engaged in wrestling with the ever-increasing task of developing products or devices using microprocessors. A fee of \$30 per person will cover a luncheon and a set of seminar materials. For further information please contact Sonya Stokell in Sydney (02)888-7066 or Jill Scott in Melbourne (03)813-1455.

Tektronix is also conducting a series of one-day seminars on how to select the right 8- and 16-bit microprocessor for your application. The topics discussed will cover Fabrication Technology, Chip-Architecture, Development Tools and other selection criteria.

The seminars are intended for decision makers who need to know what the microprocessors can do and how to better under-

stand the chip selection process; experienced engineers who need to quickly learn the internals of a micro and how it affects the selection process; less experienced engineers who are suddenly thrust into the task of developing hardware or software and must make the best decision on which microprocessor to use.

Each seminar will be a full-day event and will be held in Adelaide on February 15, Perth on February 17 and Brisbane on March 1. A fee of \$30 per person will cover a luncheon and the seminar materials. For further information and venue details contact Angie Witthaus in Adelaide (08)223-2811, Anna Kudray in Perth (09)325-8433 or Julie Bow in Brisbane (07) 394-1155.

This board won't forget

SME Systems have a new CRC-48 48K CMOS static memory card, a fail safe memory system that retains data when power is removed from the board.

The board is designed for use in high speed 6-8 MHz computer systems. With full S100 buss


compatibility the CRC-48 fits in with other SME Systems S100 products. An on board battery is used to retain power to the CMOS memory devices whenever the system is powered down for any reason.

A major feature of the CRC-48 board is its exceptionally low power consumption. In a power failure situation memory retention to a full complement of 6116 devices is typically around

250 hours on the inbuilt 30 mA/hr battery.

Because CRC-48 uses only 48K of memory, the board can be bank switched in or out completely. Flexibility is offered by the board in its ability to use both EPROM and static memory on the one board.

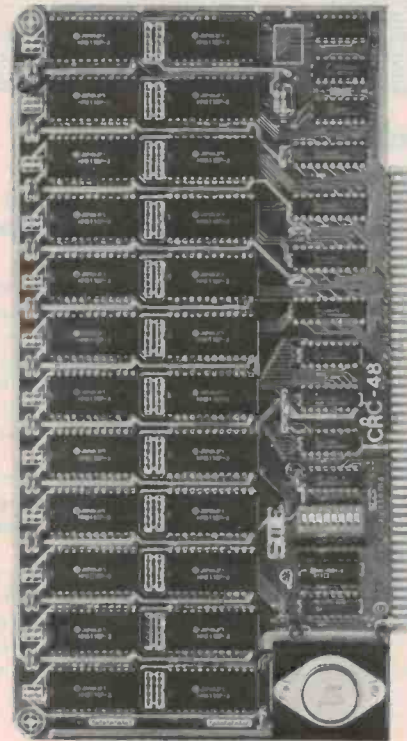SME Systems are at 22 Queen St, Mitcham Vic. 3132. (03)874-3666. ▶





If Athlete's Foot has got your toes in a shocking state...

Try Tinacidin. Pull the plug on the burning, itching, prickly pain of Athlete's Foot... fast!

At pharmacies everywhere.

SCHERING CORPORATION U.S.A., AUSTRALIAN SUBSIDIARY
 — ESSEX LABORATORIES PTY. LTD., BAULKHAM HILLS, N.S.W.
Health Care is our business

PM6067/82 SX 8914/3

Triggerable logic monitor

The LM-3 triggerable logic monitor from Global Specialties Corporation is a new type of logic test instrument.


It combines 40 variable precision-threshold logic-state indicators with a highly flexible triggerable latching circuit in a single benchtop package. The variable-threshold facilities allow the LM-3 to monitor up to 40 logic points simultaneously on any type of circuitry, while the different triggering modes mean that the LM-3 can be used to follow logic states or 'freeze' the display in different ways to examine a particular circuit condition.

The LM-3 is supplied with a 40-conductor ribbon cable term-

inated with 40 coded 'easy-clips' that fit on to the circuit pin, test point, breakpoint or buss-line combination being tested, and 40 discrete light-emitting diodes on the instrument's front panel indicate the logic state of each point.

Input impedance is 500k at 6pF and the instrument works at up to 5 MHz and can capture 100ns events.

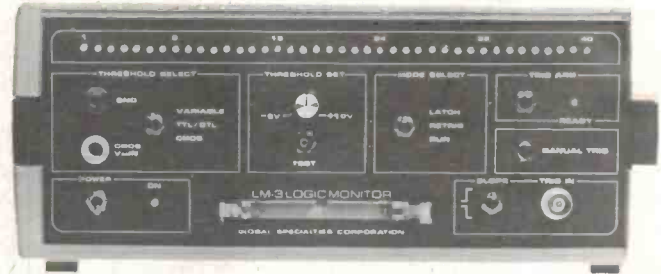Four operating modes are provided on the LM-3. Apart from the normal 'run' mode there is a 'retrig' mode where the display follows the data until a switch-



selectable rising or falling edge appears at the trigger input and then latches until the next selected edge appears. In the 'latch' mode the display follows the data and ignores the trigger input until the instrument's 'arm' button is pressed, when the next trigger input will latch the

display. In addition, both 'retrig' and 'latch' modes can be used with a manual pushbutton.

Global Specialties Corporation is represented in Australia by Vicom International Pty Ltd, 57 City Rd, South Melbourne Vic. 3205. (03)62-6931.



Alfatron has winchester drives

Alfatron has announced that it has the rights to distribute the NCL hard disk drives from Japan.

These Winchester drives are claimed to offer a very low cost entry to the microcomputer user into fast access, high capacity disk drives. The interfaces currently available are the GPIB and Multibus.

The current model is a 10M unit and it is expected to have higher capacity units available soon.

The SA-700 analyser available from Alfatron, features emulation of CPU, EPROM programmer (2716 — 27128) and a standalone computer.

It can accept diskettes from a wide variety of other machines (including MDS) and as it has a hardware control program, is able to emulate user programs in real time. Programs may also be downline loaded via an RS232 serial port.

More information is available from Alfatron Pty Ltd, Industrial Electronics, 1761 Ferntree Gully Rd, Ferntree Gully Vic. 3156. (03)758-9551.


TOYO

PRECISION EQUIPMENT FOR THE ELECTRONICS INDUSTRY

The TOYO mini drills and lathe offer a high level of accuracy comparable with larger machine tools.

The MINI LATHE (as illus) is fitted with a 240 volt motor, speed range from 250-3000 rpm. It has a swing of 100mm and is 250mm between centres. Weighs 15kg.

Basic Price \$435

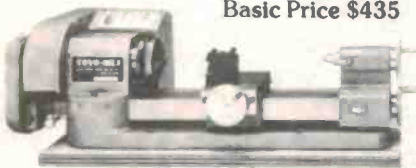

Accessories available
*Prices & Tax

The MINI DRILL comes in two models, MINI DRILL I, a standard speed drill offering 6 speeds from 850-3100 rpm, with a 6.5mm drilling capacity. Weight 5.4kg, ideal for model makers, instrument and repairers, etc. The high speed MINI DRILL IH has 2 speeds 8,000 + 12,000 rpm with a drilling capacity from No. 80 to 6.5mm and weighs 5.4kg, is suited for drilling printed circuit boards etc.

A machine vice is included with both models.

Mini Drill I \$165


Mini Drill IH \$165



For brochures, prices and information contact

MELBOURNE MACHINERY CO. (SALES) PTY LTD

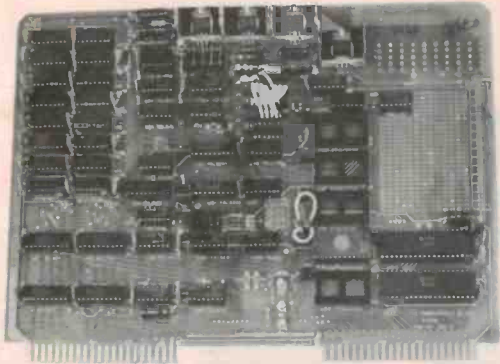51 Queensbridge St, South Melbourne, Vic (03) 61 2911.



The Computerist Inc products

The Computerist Inc US has released a 6809 microcomputer system based on their range of microcomputer boards. Called the 'Focus' system it incorporates Flexi Plus, Dram Plus and Video Plus, together with 640K on dual 5¼-inch DD DS disk drives.

The system features an integral EPROM programmer, RS232 interface and 20 mA ports, six 8-bit parallel I/O ports, up to 132 x 30 display and optional IEEE 488 interface and additional RS232 interface. Available software includes TSC Flex and Extended BASIC. The system is also available in an OEM configuration in an economical three slot card cage.

The Computerist Inc. has also released a 128K RAM version of the 32K Dram Plus. Designed for Rockwell AIM65, Synertek

SYM-1 and Computerist Flexi Plus expansion, it retains the features of four byte wide EPROM/RAM sockets for a maximum of 32K, 16K/32K EPROM programmer, Dual 6522s for four 16-bit timers and 40 programmable I/O lines, quality through plated hole, solder mask, silk screened pcb, and wire wrap area. An improved bank select feature has also been provided. More information is available from Energy Control, P.O. Box 6502, Goodna Qld 4300. (07)288-2757.

Toshiba's personal computer

The T100, now available from Toshiba, is equipped with 64K RAM, 32K ROM for BASIC language and 16K video RAM as standard memory units.

Up to two ROM and RAM packs the size of an audio cassette tape can be installed inside the T100. These options each have 32K of memory. By installing a ROM pack and cutting off the BASIC of the built-in ROM of the CPU, you can use the languages, operating system and applications stored in the ROM pack. The RAM pack can be used as a program file and data file. The RAM pack, even if

removed from the unit, stores programmed data for one year.

The T100 provides very high resolution graphic displays on its eight colour CRT, which presents an array of 640-dot horizontal lines and 200-dot vertical lines.

More information can be obtained from Toshiba (Aust) Pty Ltd, Talavera Rd, Nth Ryde NSW 2113. (02)887-3322.

Club Call

The Zebra-Xray 80 newsletter and the Australasian ZX Users newsletter have merged into what is now known as the Australasian ZX Users Newsletter. The editors are Paul Janson and Tony Mowbray and they can be contacted at P.O. Box 397, Dapto NSW 2530.

This year the cost of subscription to this newsletter is \$15 or \$2 for a single issue. The first four issues of Zebra-Xray 80 are still available for \$7 or \$2 for a single issue.

Subscription price of Vol 3 (82) of this newsletter will be \$10 which covers nine issues and includes all postage costs.


The Melbourne Atari Computer Enthusiasts (MACE) Group is a strictly Atari 400/800 personal computer user group. It has just over 100 members in all states of Australia and New Zealand. A newsletter called the Australian Atari Gazette is sent to members each month.

Meetings are held on the first Sunday of each month at 12 pm at 3M Australia, cnr of Blackburn and Ferntree Gully Roads, Melbourne, where the latest software and hardware from around the world is shown.

32K BYTES FOR THE ZX81

SPECIAL RAM PACK FOR THE ZX81

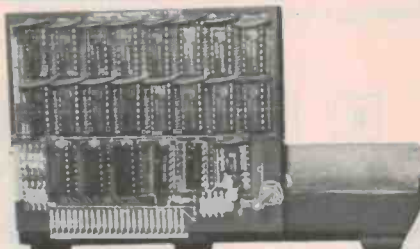This board uses dynamic RAM chips for lower cost and lower power consumption. Simply plugs into the ZX 81 expansion port offering 32K BYTES for basic programmes and data handling. No extra PSU required. Extra memory to help you build your ZX81 into a powerful microprocessor system at an affordable price. Compare the price with other RAM PACKS available on the market!



Price for 32K Ram Pack (RP32) only: \$165.00 incl. P&P (Aust)

Free cases available soon.

Please send order or S A E for further information to:
 VENDALE PTY. LTD., Dept T7, Box 456,
 Glen Waverley, Victoria 3150.
 36 Plymouth St., Glen Waverley,
 (03) 232 0444.

ZX80/81 PROGRAMMABLE CHARACTER GENERATOR

Using simple BASIC programs you can create your own unique character sets and graphic symbols for games, High Res graphs and charts and interesting patterns. Program symbols normally available only on more expensive microprocessors and you are not limited to preprogrammed graphic sets.

Fully assembled price \$95.00 incl. P & P (Australia)
 Uses the 8K ROM from Sinclair (not incl.).

UPGRADE YOUR ZX80 GRAPHICS

Now you can upgrade your ZX80 to the full animated graphics of the ZX81. Your ZX80 will now run in SLOW mode.

Fully assembled price only \$38.50 incl. P & P (Australia)

Works only in conjunction with 8K ROM from Sinclair (not incl.)

VENDALE



VEN 0261

Fault-finding the ETI-660 Learner's Microcomputer

Graeme Teesdale


Having trouble firing up your '660? Has your '660 developed a fault? Or do you just want to learn more about the beast's internal workings? This article illustrates some techniques of fault-finding for this project as well as showing you more about its internal operation.

THIS ARTICLE endeavours to give constructors of the ETI-660 Learner's Microcomputer some fault-finding techniques to narrow down the area where a fault may exist, whether you are attempting to get your project up and running or trying to fix a problem which has developed later.

For many constructors, the ETI-660 is probably the most ambitious project ever undertaken. It would probably be the most difficult to fault-find!

I will have to assume here that you have carried out the tests recommended during assembly. An oscilloscope was the only instrument used in preparing this article. If you possibly can, get hold of one, or access to one. The oscilloscope needs to be a dual beam type and have a vertical amplifier bandwidth of 10 MHz or greater. I used a Hewlett-Packard model 1740A 100 MHz oscilloscope for the tests illustrated here, mainly to obtain good results to photograph. However, you won't need anything as sophisticated or as costly as that! A dual beam 'scope is really a *must* because it allows you to view synchronised data from two sources or trigger the 'scope on one signal while investigating a related signal.

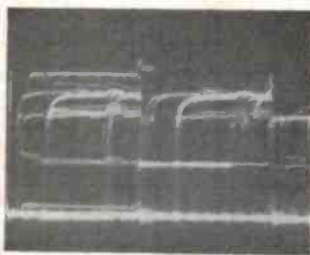As a first example, have a look at what is *not* going to help you!



Looking at a data buss line (D0)

The above waveform was taken from the data buss line D0 and it is very difficult to see exactly what is happening.



SCO (Pin 6, 1802)

D0 (Pin 15, 1802)


Now here's something a bit more useful! This trace is still of the data buss, except that the CRO was triggered from the SC0 state code line pin 6, of the 1802 CPU. When using the 'scope on the '660, *always* have the Y amps switch to *dc*, so that you can see 'high' and 'low' levels immediately.

Flow chart

Fault-finding is a logical procedure where you work from *common* or *general* elements of the circuitry, toward *specific* elements. Fault symptoms will give you a starting point. How does this work? To illustrate the procedure, and to give you a specific guide, I have drawn up a *fault-finding flow chart* for the '660.

Go through it carefully to see how it is structured. You may well have done some of the checks already. This chart won't lead you directly to the component or chip at fault, but it will certainly narrow down the area of the fault. From there you have relatively few things to check, which makes life considerably easier and fault-finding much less frustrating.

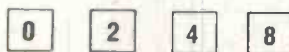Note 1: At this stage we can assume that the initialisation software is running and that the 6821 (IC5) has been initialised also. The CPU is waiting for you to press one of the following keys:



Note 2: If a sound is heard in the speaker, the CPU must have acknowledged that you pressed key 0. Pressing the keys from 0 to F should produce an increasing-length tone with each successive key pressed.

In response to key 0 being pressed, the data in the address field (i.e. on the left of the bar along the bottom of the screen) of the display should be updated each time you press a key between 0 and F.

Note 3: If the keyboard doesn't cause a CPU response, then check the conditions on the 'A' port of the 6821 — I/O lines PA0-PA7. i.e. pins 2 — 9 of IC5.

The keyboard is divided into a 4 x 4 matrix with normally open contacts (note: constructors using the FES-310 pushbuttons should check that pin 1 of each button is aligned to the pin 1 dot indicator on the pc board).

Pins 2 to 5 of the 6821 connect to the 'columns' of the keyboard matrix, while pins 6 to 9 connect to the 'rows'. The column inputs are software programmed to be inputs, the internal pull-up resistors make pins 2-5 at logic 1 (high). Using the CRO, check that pins 2-5 are high. The remaining pins — 6 to 9 — are continually toggled inputs or outputs. Refer to Figure 1 for typical waveform.

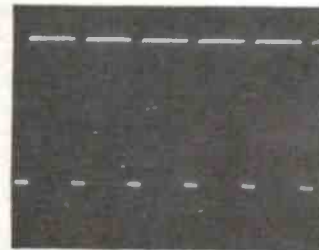


Figure 1.

Timebase set to 0.5 ms/cm

Y amp. set to 1 V/cm

Maintain the same timebase setting but change both Y amp sensitivities to 2 V/cm. Connect them to pins 9 and 5. Press the RESET key followed by the 0 key. Note the change in pulse rate on pin 9 and the changing of pin 5 to a low output. The software is endeavouring to locate the key depressed.

Pressing RESET followed by 8 will cause the CPU to run a CHIP 8 program, hence the keyboard scan subroutine is no longer used. Pins 6 to 9 of the 6821 drop to 0 (low).

The timing signals of the 6821 'read' cycle can be observed by connecting the CRO Y amp inputs to pins 22 (or 24) and 21. A 'chip select' (CS) for the 6821 is generated from the encoded 'N' lines of the 1802 (pins 17, 18, 19). The input code generated by the 1802 is decoded by IC17. (Note: on the circuit diagram, page 36 Nov. '81 ETI, pin 2 of IC17 is connected to pins 22/24 of IC5. Pin 21 of IC5 is the read/write line. When it is high and pins 22/24 high, data is transferred from the keyboard matrix to the data buss.)

Refer to Figure 2. The top trace is the 'select' pulse on pins 22/24 of IC5. The bottom trace is the read/write (R/W) signal generated by A2. With these two pulses going high

together one can assume that the 6821 is being read by the CPU.

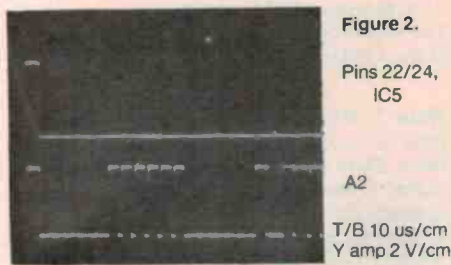


Figure 2.

Pins 22/24, IC5

A2

T/B 10 us/cm
Y amp 2 V/cm

To carry out a comparison, it is essential to trigger the 'scope on the top trace (pin 22/24, IC5) and look at the bottom trace for the condition of address line 2 (A2 — R/W for the 6821). At this stage, the 6821 appears to be working as expected. It is now necessary to check that the 1864 (IC4) is also selected by the decoded N lines. (An error in labelling appears at IC17 on the circuit diagram. Pins 1/14 of IC17 are shown to go to pins 17/19 of IC3 — that should be IC4.)

The tone generator latch in the 1864 is loaded by a '64' output instruction. To obtain any output from the AUDIO pin (pin 39) of the 1864, it is also necessary to activate the AUDIO OUTPUT ENABLE pin (AOE — pin 4). Referring to the circuit diagram you will see that pin 4 of IC4 is connected to pin 4 of IC3 (Q output). To allow the internal counter to toggle freely, pin 4 of the 1864 must be high. The frequency input to the audio generator is the TPB pulse generated by the 1802.

Connect the 'scope to pin 34 of the 1864 and you should observe a short duration positive-going pulse train. The TPA and TPB pulses occur once in each machine cycle and are used by I/O devices to interpret codes and to time interaction with the data buss. Set the CRO timebase to 2 us/cm to observe TPA or TPB.

Connect one Y amp of the 'scope to pin 4 of the 1864 and the other to pin 39. Repeated pressing of the RESET key should result in an audio frequency square wave appearing and should be heard from the speaker. If not, check the value of R20 (390R) and wiring to the speaker. Trace the track from R20 to the speaker. Just adjacent to pin 20 of IC5 is a through-board link. See that it's in place and properly soldered on both sides. If all is OK, replace the speaker with a *known good* one.

Note 4: The 1864 generates both composite and separate horizontal and vertical sync. signals. For monochrome operation, the composite sync. output (CSYNC, pin 30) is combined with the RED video output (pin 29) in a simple resistive network to produce composite video output. Note that this is a high impedance output and cannot be connected directly to the 75 ohm input common to most video monitors. The video refresh cycle of the display section of the 1864 is synchronised with the 1802 using INT (pin 36 on both chips), EF (pin 18, IC4) and EF1 (pin 24, IC3) and the state code lines SC0 and SC1 (pins 5 and 6 of IC3).

Pin 18 on the 1864 pulses at twice the frame frequency, goes low for four horizontal lines prior to the start of display and low again for four horizontal lines prior to the end of display.

Connect one Y amp of the 'scope to pin 18 and the other to pin 36 of the 1864 and observe these pulsing lines. The pulsing lines indicate that the 1864 is requesting a display update. Now connect the 'scope inputs to pins 5 and 6 on the 1864. Your waveform should look something like that in Figure 3.



Figure 3.

SC1

SC0

T/B 10 us/cm
Y amps
2 V/cm

Pin 30 of the 1864 has the composite sync. output on it. Connect the 'scope to this pin and you should get something like Figure 4.

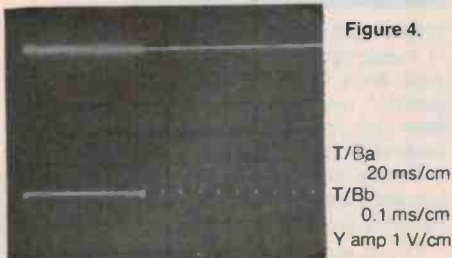


Figure 4.

T/Ba
20 ms/cm
T/Bb
0.1 ms/cm
Y amp
1 V/cm

You should observe little bright-up dots 20 ms apart (50 Hz), the frame frequency sync. pulses (actually, they're 19.8 ms apart — 50.6 Hz). Now speed up the CRO time base to 0.1 ms/cm or faster. You should observe the horizontal sync. pulses. Figure 4 shows both frame and horizontal sync. pulses. This was achieved using the expanded timebase feature of the 'scope I used. Change the input lead over to pin 29 of IC4. Set the timebase back to 5 ms/cm. Figure 5 shows the RED

video output signal, in this case as the luminance output signal.

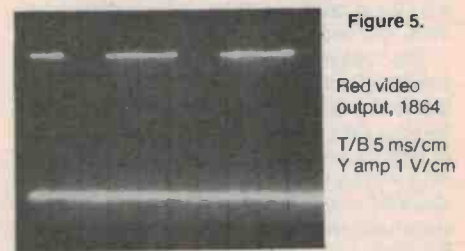


Figure 5.



Red video output, 1864
T/B 5 ms/cm
Y amp 1 V/cm

The signals from pins 29 and 30 are combined in the resistor matrix R11-7-10 to produce a composite video signal of the right sync-to-video levels. Figure 6 shows the resulting combination.



Figure 6.

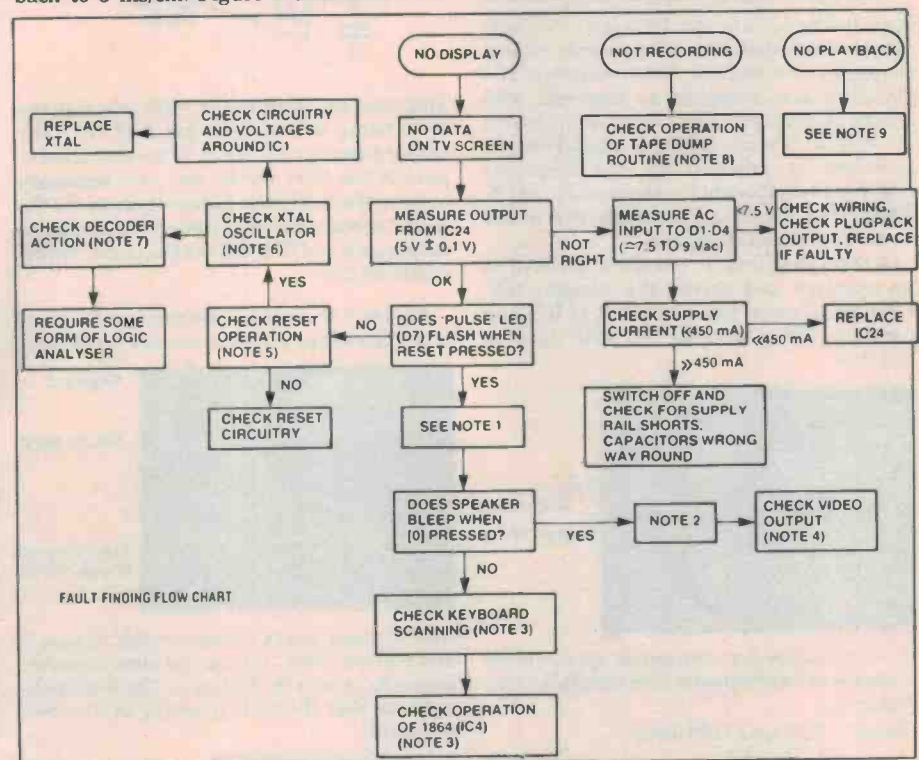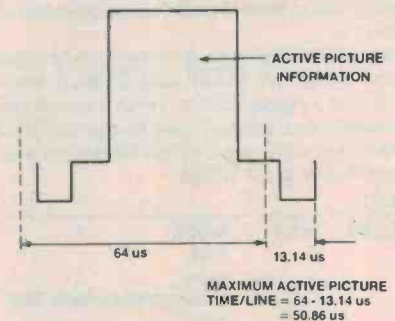Composite video.
T/B 5 ms/cm
Y amp
0.5 V/cm



Connect the 'scope input to the junction of resistors R7, 11 and 10, set the Y amp to 0.5 V/cm and compare your results with ours, shown in Figure 6.

The maximum dc level of the waveform represents *peak white* on the screen and the bottom of the sync pulses represents black level or zero volts dc. This is why an inverter is required in the ETI-760 video modulator (Q2) when a composite video signal is fed into the FET output modulator (Q3). If you are obtaining the same amplitude signal as in Figure 6, but video display is not present on your TV, check your modulator. (Note: R11 is shown on the '660 circuit diagram as 2k2, but in the text it is given as 5k6. A value of 2k2 should be used to give proper sync. levels.)

Note 5: The 1802 receives a reset signal from the 1864 controller chip. On power-up, capacitor C3 pulls pin 38, the CLRIN input of IC4, low (0) for the approximate period of $3 \times R2C3$ time constant. The low level input into the Schmitt trigger on pin 38 of IC4 will cause CLROUT, pin 3, to go low also. CLROUT is connected to the CLEAR input of the 1802, pin 3. The post-Schmitt trigger output provides the 1802 with a clean, clear signal.

Connect one 'scope input to pin 3 of the 1802. There should be a 'high' here. Press RESET and it should go low on depression of the button.

The 1802 is provided with four control modes using the WAIT and CLEAR lines (pin 2 and 3 respectively). Table 1 shows the four modes and the two used by the '660. For correct operation, pin 2 of the 1802 must also be high when pin 3 is high.


TABLE 1.

CLEAR	WAIT	MODE
0	0	load
0	1	reset
1	0	pause
1	1	run

modes used by '660

Note 6: The clock for the 1802 is a 1.773 MHz signal generated from the master crystal frequency of 8.86 MHz. Two sections of IC1 (74LS00) are connected as inverters with inputs biased up by a low value resistor from the output. Positive feedback around the two inverters is provided by the frequency dependant components — the crystal and C5. The latter allows slight adjustment of the crystal's resonant frequency.

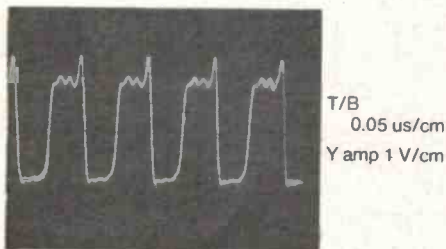A third gate from IC1 is also connected as an inverter and drives the divider, IC2. Connect a 'scope input to pin 3 of IC1 and compare the trace you get with that in Figure 7.




From the 'scope, you can get an approximate measure of the frequency. For example, from Figure 7:

$$\begin{aligned} \text{Period} &= 2.25 \text{ cm} \times 0.05 \text{ us/cm} \\ &= 1.125 \times 10^{-7} \end{aligned}$$

$$\begin{aligned} \text{Frequency} &= \frac{1}{\text{Period}} \\ &= 8.88 \times 10^6 \\ &= 8.88 \text{ MHz} \end{aligned}$$


Which is pretty close to the intended 8.86 MHz, showing you the oscillator's operating in the right ballpark.

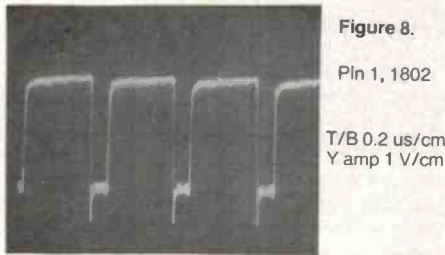The waveform at pin 3 of IC1 is divided by five in IC2. Change the 'scope input now to pin 1 of IC3. Change the timebase to 0.2 us/cm and compare your waveform with that in Figure 8.




It is normal practice to supply the clock input of a microprocessor with a 1:1 mark/space ratio pulse. However, in this case it is not possible because of the odd division ratio from the crystal frequency to generate the necessary 1.773 MHz clock. The 1802 would not accept the output pulse from IC2 directly, but did accept the inverted version, hence the need for IC1d.

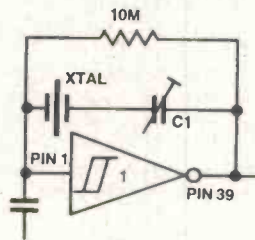The crystal is normally connected between pins 1 and 39 of the 1802 (clock and XTAL), in parallel with a resistance of typically 10 M.



This was not used in the '660, pin 1 of the 1802 being driven from pin 6 of IC1. The output from pin 39 of the 1802 is connected to pin 2 of the 1864. By the way, it is necessary to have the 8.86 MHz base frequency for the colour encoder circuitry (the crystal oscillator output, pin 8 of IC1, goes to the colour multiplexer, IC20).

Figure 9 shows the waveform on pin 39 of IC3. Check that you get a similar waveform.

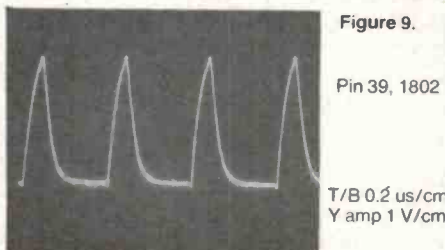

Now connect the two 'scope inputs to pins 5 and 6 of the 1802. You should observe waveforms as shown in Figure 3. These outputs indicate that the CPU is trying to do something like:


- (1) fetch an instruction

- (2) execute an instruction
- (3) acknowledge an interrupt request
- (4) process a DMA request


The latter two are normally used as a result of the 1864 causing a display update.

Note 7: With the 1802, the 16-bit address data is multiplexed onto a common eight lines, MA0-7. i.e. pins 25 to 32 of IC3. The higher order byte of a 16-bit memory address appears on the memory address lines first. Those bits required by the memory system, A8-A11, can be stored into an external address latch (IC6) by the timing pulse TPA.

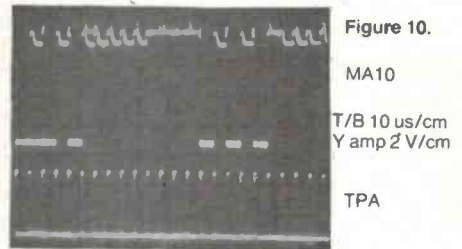Connect the 'scope inputs to pins 4 and 15 (MA10) of IC6 and trigger the 'scope on the TPA pulse. Compare your waveforms with Figure 10.



The data presented to IC6 is latched when the TPA pulse is low. The high address lines A10 and A11, from the latch, are supplied to the address decoder, IC8. While the monitor is running and scanning the keyboard, the chip select lines of IC11 (pin 20) and ICs 9 and 10 (pin 14 on each) should be pulsing. Connect the 'scope inputs to pins 14 and 15 (address decoder outputs) and check your waveforms against those in Figure 11.

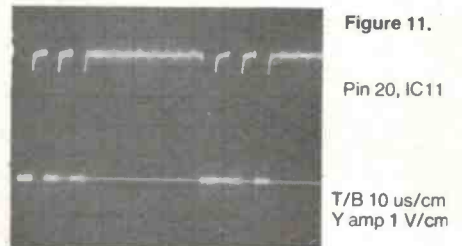

See that you get the chip select signal on IC11 pin 20.

The RAM chips IC9 and IC10 are selected because the display data is stored here, along with monitor 'scratch pad' data, in the memory block 0400 to 07FF. Table 2 shows the chip select logic — which memory block is selected by which output (chip select line) of IC8.

TABLE 2.

A11	A10	CHIP SELECT ACTIVE	MEMORY BLOCK
0	0	pin 15, IC8	0000 — 03FF
0	1	pin 14, IC8	0400 — 07FF
1	0	pin 13, IC8	0800 — 0BFF
1	1	pin 12, IC8	0C00 — 0FFF

Using the 'scope, observe pin 20 of IC11 while you press and hold down the RESET button. Pin 20 should go low and remain low. On reset, the memory address lines are reset to 0000, therefore the address decoder will generate a chip select for the bottom memory block, 0000 — 03FF. Failure to achieve this will indicate a fault in the address latch (IC6) or decoder (IC8).

The monitor EPROM (IC11) must be selected by a RESET otherwise the 1802 will run on some other addressed random data. The decoder chip, IC8, divides the lower memory block into 1K blocks by using A10 as the least significant bit (LSB).

If the problem has not been found by any of the test sequences described here, it is now necessary to locate someone that has a logic analyser. This instrument is connected onto the data buss and several timing pulse outputs. It tracks and stores in its own memory the microprocessor's operation after a certain trigger 'word'. The stored information is displayed on a terminal or 'scope. This then allows the user to determine whether the microprocessor is following the monitor program or where it went to instead.

Note 8: The code for the tape load routine is generated in software and sent out from the 1802 using the Q output, pin 4. Pressing RESET followed by 2 should cause —

- (1) audio tone to be heard from the speaker
- (2) the pulse LED to flash at a high rate.

If you look at pin 4 of the 1802, you should see a waveform as shown in Figure 12.

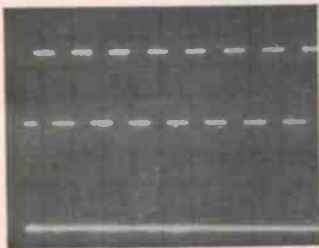


Figure 12.

Pin 4, 1802

After 6 — 10 seconds, the leader tone gives way to the actual data from memory being loaded in 256-byte lumps as a two-tone FSK signal. A 'scope connected to pin 5 of IC7 should produce a signal amplitude of approximately 2.4 V peak-to-peak. If no sound output occurs, refer to note 3 on the operation of the 1864. No Q output pulse (pin 4) will indicate a fault in the EPROM software. Take your EPROM to someone that has a microprocessor system that will allow you to check the listing contained in IC11, the 2716.

Note 9: The signal from the tape recorder is fed into one of the op-amp sections of IC7. Output from this is used to drive the flag input (EF2) of the 1802. For the CMOS input to recognise a change in state, the signal from the op-amp (pin 9) must exceed about 3.5 V. Connect your tape recorder output to the tape input socket of the '660 and start it running (with a tape installed!). Using the 'scope, observe the amplitude of the waveform on pin 23 of IC3. Remember, it must exceed 3.5 V peak for the 1802 flag input to change state. If not, look for insufficient gain from the op-amp or lack of recorder level. Check the values of R31, 32 and 33.

Conclusion

Here's hoping this article has led you along the right path to find faults in your '660 and perhaps shown you a thing or two more about its operation that you didn't know before.

THE EVENING'S JUST BEGUN...



COME HOME TONIGHT TO A BLACK & WHITE





HURRY! HURRY!

WE'VE EXTENDED OUR CRAZY CHRISTMAS SPECIALS!

SPECIAL PACK 1

VIC 20	\$299
C2N Datasette	\$96
2 Cartridges	\$80
6 Tapes (average)	\$85
1 Joystick	\$19
Total	\$579

OUR PRICE \$520

SAVE \$59.00

**LIMITED STOCK
AVAILABLE**

SPECIAL PACK 2

CBM 4000 with 32K RAM* ...	\$1600
C2N Cassette	\$96
Friend 1 Word Processor ...	\$90
The full Microcomputer House exclusive Cursor Collection .	\$350
Sound Unit	\$40

\$2176

OUR PRICE \$1595

SAVE AN UNBELIEVABLE \$581

*4016 updated

SUPER BUSINESS SPECIAL

CBM 8032 — 80 col Screen
CBM 8050 — IMB Disk Drive
CBM 8023 — 132 col Dot Matrix Printer

then plug in and go!

With any two of these packages

- Debtors — Creditors
- Stock Control — Visicalc
- General Ledger.

SAVE \$1491

\$4995



THE MICROCOMPUTER HOUSE PTY. LTD.

116 Abercrombie Street Chippendale NSW 2006

Phone (02) 698 7076 or 698 7866

**LAST CHANCE
CALL NOW**

TRUSCOTT ELECTRONICS

Stockists of:

- ARLEC ● SONAR ● MAGNAVOX
- SCOPE ● PHILLIPS
- FERGUSON ● AWA ● LANKAR
- RALMAR ● SCALAR ● K&W
products

As well as car sound equipment,
CB radio, sky beam antenna.
And a comprehensive range of
electronic components at very
keen prices.

**Ian J. TRUSCOTT
ELECTRONICS**

CNR EASTFIELD
& BAYSWATER ROADS,
SOUTH CROYDON, VIC.
TELEPHONE (03) 723 3860

Riston 3000

Sensitized P.C. Board

(Fibreglass Base)

	SINGLE	DOUBLE
36x24	\$45.00	\$57.00
24x18	\$22.00	\$30.00
18x12	\$12.50	\$16.00
12x12	\$ 7.90	\$10.75
12x 6	\$ 4.50	\$ 5.85

Quantity Discounts

\$100+	10%
\$250+	12½%
\$1000+	15%

All plus sales tax if applicable.

RISTON DEVELOPER PROMOTION SPECIAL

Concentrate (1 = 4) \$4.25 litre
— 5 litre \$19.50—

3M SCOTCHCAL
(Photo sensitive label material)
3M Image 'N' Transfer
(Graphic Transfer Material)
MAJOR STOCKISTS



101 Burgundy St,
Heldelberg 3084
(03) 458 2976
Telex AA37678
MELTON
(03) 743 1011

MOSS COMPONENTS


PO BOX 324, FAIRFIELD, NSW 2165.

- Capacitors & Resistors
- Integrated Circuits
- Wires & Cables
- Semiconductors
- Hirose Connectors
- Ribbon Cable
- Plugs & Sockets

**MAIL ORDER SUPPLY
SPECIALISTS**

**FOR YOUR
ELECTRONIC
NEEDS**

Write for
FREE
Catalogue

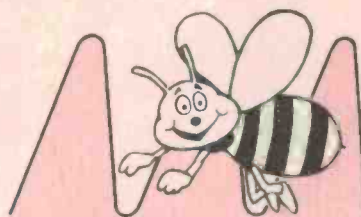

MICRO WORLD

REPORT

Summary Of Commands

Unlimited possibilities for creative graphics are now possible with OZ-LOGO and Your MicroBee.

Study this summary of commands and imagine what you can do.

Turtle Movement Commands:

- nF Move n steps in direction of heading (unless blocked)
- nR Turn clockwise thru 90° n times
- J Jump to Home (leave hidden snap mark at jump off cell). [Note: always valid even if HOME blocked]

Trail Marking Commands

- D Marker DOWN so trail left
- U Marker UP so no trail
- E Erase what is "under" the Turtle
- nD Marker down, trail being snap number D.

Screen

- C Clear Screen
- \$ Make copy of screen into album page given by SNAP character
- * Restore copy to screen
- n* Blow-up onto Turtle territory the current SNAP using SNAP number n as the blow-up character.
- : Restore copy to screen, with [] solid blobs. Used for maze dumping as solid []'s are not penetratable.
- n. Makes n the current SNAP number. Corresponding SNAP now displayed on top RH corner.

Snap

- , Rotate album snap (top LH corner) through 90 degrees.
- : Reflect album snap about vertical axis : unimplemented.



Conditionals

- & BLOCKED = 1 if ahead blocked, else has value 0
- n[Compare accumulator A with number n. If equal, value passed on is 1, else 0. "[]" essentially means Compare.
- n# If n not equal to A has value 1, else value 0.

A and B numbers

- n+ Add a n times to number A.
- n- Subtract 1 n times from A (but stop when A = 0).
- A The value of A.
- B The value of B.
- % Swap A and B.

We're Moving into 1983 with OZ-LOGO

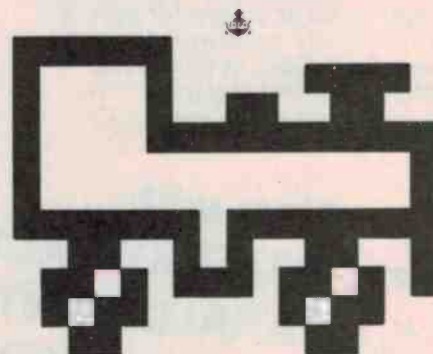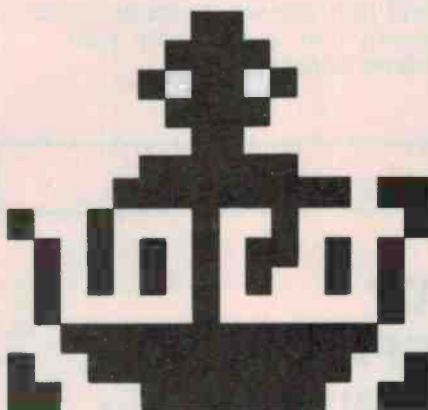

OZ-LOGO — An endless Learning Language for Australian Children.

OZ-LOGO (developed by Dr. Harvey A. Cohen, La Trobe University, Melbourne and consultant member of the original M.I.T. Team in 1973 - 1974) is a derivation of LOGO, a computer language based on a philosophy of education developed over a 12 year period by Professor Seymour Papert and the Staff of the Artificial Intelligence Laboratory at the Massachusetts Institute of Technology (M.I.T.)

OZ-LOGO is a Graphics Language based on LOGO but with many features so as to capitalise on the outstanding graphics capabilities of the MicroBee.

Just as with LOGO, the prime "Drawing" mechanism is via the Turtle, which goes in the forward, in the direction of its heading.

OZ-LOGO will be available in February 1983 as a ROM Based Program for the MicroBee 16 and 32K Plus.

THE PLUS SERIES! More Languages, More Features and More Software.

MicroBee 16K Plus, 32K Plus now with Basic, Pascal S+ CP/M Logo, Pilot, WordBee Wordprocessing ROM Pack, Robot Man, Missile Wars, Editor Assembler, "ESC" Key, Graphic Games, PCG Tutorial and of course the PLUS SERIES from MicroBee has Battery Back-

up, Serial and Parallel Ports as Standard Features.

Watch for new releases of easy-to-use Powerful Educational Software for Your MicroBee.

NEW SOFTWARE

ROBOT MAN is a familiar challenging Arcade Game for the whole family and gives you another reason to enjoy your MicroBee.

PASCAL S+

Developed by Geoffrey Townshend, is a Computer/Interpreter system for substantial sub-set of PASCAL.

PASCAL S+ offers excellent features for structural programming. It is a natural choice for beginners because it was developed as a teaching language. PASCAL S+ will be a ROM Pack based program available in early 1983.

LOOK what the **MicroBee**

NEW 'PLUS' SERIES WITH EXTRA FEATURES

16K PLUS

The 16K PLUS with features such as built in music generation, high and low resolution graphics, with a screen display of 16 lines each containing 64 upper and lower case characters. When you also consider all of the standard extras like continuous memory, built in printer and input/output interfaces and parallel port, 4.5 volt battery back-up and self testing BASIC in ROM, the MicroBee 16K PLUS is unbeatable in its class.

32K PLUS

All of the standard features of the 16K PLUS with twice as much usable RAM. When you add the new Word Bee ROM Pack, you have a powerful word processing capability which does a lot more than play the many games available for the MicroBee. Add a printer and maybe even the Tasman Turtle and just see what you and your family can now do with your home computer.


64K PLUS



The MicroBee 64K is equipped with 56K of user RAM with Battery backed continuous memory and has built-in 80 x 24 screen format as well as 64 x 16 line. All characters are upper and lower case and powerful graphics are readily available. A value packed exclusive feature of the MicroBee 64K PLUS is that it can double as an ADM3A Terminal operating in serial mode at either 300 or 1200 baud (full or half duplex). You can add a modem and use your MicroBee 64 as your personal information window to the world.

A better Bee for '83

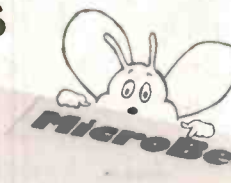- ★ Now with
- ★ BATTERY BACK-UP
- ★ PARALLEL INTERFACE
- ★ SELECTED CONTINUOUS MEMORY



**PLUS
SERIES**



A Happy Bee New Year



Family can do NOW!

**BEE
POWER**

Powerful, affordable Word Processing ? WORD BEE ROM PACK Australia's First!

Everything you'd expect in a fully blown 'Pro' Word Processor. Call at your MicroBee Computer Shop today for a demonstration of the sensational new WORD BEE ROM PACK. A must for every MicroBee owner with a need to write.

Unlike many so called 'Word Processors' on the market today, the Word Bee incorporates many features until now only available on 'megabuck' Word Processors costing many times as much as the mighty Word Bee!

Be early and snap up this powerful, affordable, Word Bee today. You can fit it yourself or your local MicroBee Computer Shop will fit it for you FREE!

Features/Functions

INTERFACE MODE — Allows loading/saving/transferring files, printing your file and so on.

20 Powerful Easy-to-use INTERFACE COMMANDS such as:

? — For general help menu
P — Print the entire file
S — Save file to cassette

EDIT MODE — familiar key functions; Control F (Go to Find/Replace Menu). Control R (Scroll file towards end, with freeze feature).

Control B (Full Block functions).

17 SEPARATE DOT COMMANDS
SAVE AND LOAD TAPE FILES

Other features include verifying tapes, force loading and appending tapes.

MicroBee 64K PLUS

The MicroBee 64K also runs MicroWorld BASIC which is supplied on cassette. You do not need disk drives to use your MicroBee 64. Just load the tape and thanks to the unique CMOS continuous memory, you can run any program available for the 16K or 32K PLUS. With the built-in monitor ROM, with commands to enable you to examine memory, run programs, block move, compare and search through memory, the MicroBee 64 will load and save programs from cassette tape and read and write to disk drives.

"ESC" KEY

A sophisticated single key program for the 16 and 32K Plus. Allows you to enter single letter commands for ease of operation. A must for the serious programmer!

EASY LEARNING LANGUAGE — MicroBee PILOT

Pilot is an easy language to learn and use. Developed in the 70's it allows you to use the MicroBee without having to spend large amounts of time learning the system. MicroBee Pilot has several enhanced features and includes full integer arithmetic support. It is suitable for teaching beginners and young people the essentials of computing and is ideal for Computer Aided Instruction (CAI).

MicroBee EDITOR ASSEMBLER ROM

Consists of a "line oriented" text editor with automatic line numbering and an assembler which will generate Z-80 Machine Codes. Text files may be saved and loaded to tape. Object code may be assembled directly into memory and assembly listings may be sent directly to the printer. A monitor is also available to allow debugging of machine language programs. When fitted your MicroBee has built-in Basic, Editor/Assembler, Machine Code Monitor and Word Processor all in 24K of ROM — another powerful MicroBee feature.

MicroBee PERIPHERALS

Happy Bee
New Year



MicroBee DISK DRIVES (Available in February '83)

An S-100 expansion system, capable of driving two MPI 52 Disk Drives, takes the MicroBee 64K PLUS into a world standard CP/M system, capable of supporting word processing packages, electronic spread sheets, Microsoft BASIC, PASCAL and a world of other programs capable of running under CP/M 2.2.


The MicroWorld CP/M Distribution Disk is supplied with a suite of useful utilities including Disk MicroWorld BASIC, Compare, Config, DTCopy, Format, as well as the normal CP/M support such as ED, ASSM, DDT, STAT, SUBMIT, XSUB and of course, the full documentation package from Digital Research.

MONITORS



You can choose from the low cost B & W monitor (converted B & W TV) or a green phosphorous high resolution monitor with 30 cm non-glare screen.

PRINTERS

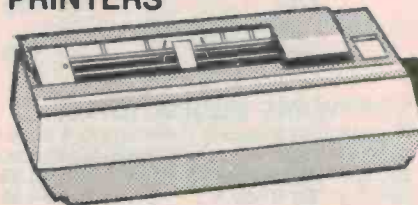


The MX 80 III F/T and MX 100 III F/T are only two of a wide range of low cost powerful printers which can connect to the MicroBee PLUS.

NEW SOFTWARE

In addition to the WordBee ROMPACK a vast quantity of exciting software is continually being prepared for the MicroBee with cassette based programs like EDPACK II for education and entertaining programs with MISSILE WARS, GRAPHIC GAMES and the PCG Tutorial available for the PLUS Series.


MicroBee

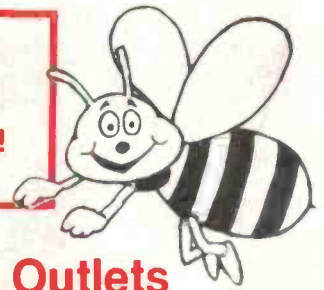Make a BeeLine
for your MicroBee
Computer Shop today!



Price List

CODE	DESCRIPTION	PRICE (inc. S/T) \$	CODE	DESCRIPTION	PRICE (inc. S/T) \$
HARDWARE:					
110.017	MicroBee 16K PLUS	449.00	PRINTERS:		
110.032	MicroBee 32K PLUS	549.00	150.080	Epsom MX 80 111 F/T	1213.00
110.064	MicroBee 64K PLUS	699.00	150.100	Epsom MX 100 111 F/T	1555.00
110.078	S-100 Desk Top Interface	299.00	SOFTWARE:		
110.090	Disk drive with controller & CP/M 2.2	799.00	MicroBee CASSETTES		
110.092	Add on Disk drive	659.00	250.035	Graphic Games	9.95
110.116	16K—16K PLUS Conversion	29.95	250.036	Missile Wars	9.95
110.132	16K—32K PLUS Conversion	125.00	250.037	PCG Tutorials	9.95
110.164	32K—64K PLUS Conversion	175.00	250.020	Space Invaders	14.95
110.025	New MicroBee Moulded Case	25.00	250.021	Concentration	9.95
120.580	S-100 Digitalker	155.00	250.022	Chess	9.95
120.274	S-100 Romblaster	165.00	250.023	Typing / Solitaire	9.95
110.210	Parallel Port inc. DB 15 plug & hood	19.95	250.024	Target	9.95
250.003	MicroBee Editor/ Assembler ROM	59.50	250.025	Lunar Lander/Hurkle	7.95
MONITORS:					
150.020	Kaga Denshi Green Phosphorous 30 cm	299.00	250.026	Star Shoot/Hangman	7.95
150.025	B & W Monitor (converted T.V.)	149.50	250.027	Biorhythm/Calendar	9.95
PERIPHERALS:					
110.011	Printer/Cable Interface Kit	49.95	250.028	Eliza	9.95
150.030	Audio cassette tape I/O drive	39.50	250.029	Kids Game	9.95
110.310	C10 Data Cassette Tape	1.10	250.030	Master Mind/Nim	9.95
110.311	C20 Data Cassette Tape	1.20	250.031	Chase/Wumpus	9.95
110.312	C30 Data Cassette Tape	1.30	250.032	Z Trek	9.95
SOFTWARE EDUCATIONAL:					
We are continuously developing a wide range of educational software cassettes for use at all levels of education.					
250.038	MicroBee PILOT	14.95	250.041	"Esc" Key	9.95
250.033	Ed Pack 1	24.95	250.042	Robot Man	14.95
SOFTWARE IN ROM:					
150.020	Kaga Denshi Green Phosphorous 30 cm	299.00	250.003	MicroBee Editor/ Assembler	59.50
150.025	B & W Monitor (converted T.V.)	149.50	250.040	MicroBee Word Bee ROMPAK	89.50
SOFTWARE DISK SYSTEM:					
110.011	Printer/Cable Interface Kit	49.95	250.007	MicroBee 5.1 Basic Upgrade	20.00
150.030	Audio cassette tape I/O drive	39.50	250.043	Pascal S +	299.00
110.310	C10 Data Cassette Tape	1.10	250.044	Pilot	P.O.A.
110.311	C20 Data Cassette Tape	1.20			
110.312	C30 Data Cassette Tape	1.30			

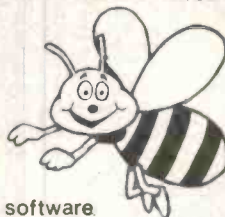

Outlets

See the exciting new MicroBee 16, 32 and 64 K PLUS Series at your nearest MicroBee Computer Shop.

SYDNEY:
Applied Technology,
1a Pattison Ave. Waitara.
Phone: 487 2711.

Electronic Agencies,
117 York St. Sydney.
Phone: 29 2098.

Specialty Enterprises,
6th Floor,
104 Bathurst St. Sydney.
Phone: 267 7747.

GOSFORD:
Applied Technology,
1 Debenham Rd. West Gosford.
Phone: (043) 24 1022.

CANBERRA:
MicroBee Computer Shop,
Level 1, Cooleman Court,
Weston, ACT.

MELBOURNE:
Computerland Sth. Melbourne,
19 - 37 Albert Road,
(Cnr Kingsway & Albert Rd.),
Melbourne.
Phone: 26 6647.

Specialty Enterprises,
1st Floor,
305 Latrobe Street, Melbourne.
Phone: 67 8811.

BRISBANE:
Specialty Enterprises,
6th Floor, 246 Queen Street, Brisbane.
Phone: 229 2450.

PERTH:
Altronics
105 Stirling St, Perth.
Phone 328 1599

NEW ZEALAND
Checkpoint Computers,
36 Main Road, Tawa,
New Zealand.
Phone: (4) 32 6988.

WARRANTY

Applied Technology Pty. Limited warrants that the electrical and mechanical parts of its manufactured products are free from defects in design, materials and workmanship for a period of 3 months from the date of delivery to the buyer.

(Freight must be paid both ways by Sender and is not covered by Warranty.)

MicroBee PHONE ORDERS

Save time and order your MicroBee direct on our Beeline number. Just give your Bankcard Number and Name. We will check stocks and get the goods on the way.



(02) 487 2711

MPI Hi-D Mini Drives

freedom
of choice

Our
way..

.. or theirs

Professional, push-button disk eject, or industry standard flip-front... Either way, MPI builds the quality in. Head load for media protection, 5mSec track-to-track and a choice between 48, 96 and 100TPI, single or double sided 5 1/4" Floppy Drives.

TRUE FREEDOM OF CHOICE

Authorised Dealers:

Sydney: (02) E&M Electronics 51 5880. Applied Technology 487 2711. OT Computers 29 5599. Micro Repair 747 1061. Computer Components 868 3614. **Wollongong:** (042) Macelec 29 1455. **Brisbane:** (07) Baltec 36 5183. **A.C.T.:** (062) Ortex 80 5283. Boulevard 48 5411. **Perth:** (09) Micro Controls 445 2544. Electronic Systems 335 7313. **Adelaide:** (08) DC Electronics 223 6946. Micro '80 211 7244. **Melbourne:** (03) Stewart Electronics 543 3733. Ellistronics 602 3282. Ritronics 489 8131. Pennywise Peripherals 82 2389. Deforest Software 877 6946. Comp Soft 428 5269. **Tasmania:** Coastal Computers (004) 31 3259.

daneva australia pty ltd.

66 Bay Road, Sandringham, Vic., 3191. Ph: 598 5622. Telex: AA34439



LETTER QUALITY PRINTER

and

K.S.R. TERMINAL

and

ELECTRONIC TYPEWRITER

from \$995.00



Call now —
Special ET1
reader offer
on ribbons!

Our printer/terminals use the range of Olivetti daisy wheel electronic typewriters — including the new PRAXIS 41/45 — with twice the life of the PRAXIS 30/35.

Print speeds range from 12 to 25 characters per second. 10, 12 and 15 pitch are standard — proportional spacing models available.

Gain more computer time with printer interface buffers which store as much as 16,000 characters.

RS232c standard, parallel (receive only) option.

All these printer/terminals are maintained throughout Australia. INCA developed the STOL interface for Olivetti's ET221 — we have the experience to understand interfacing problems. Call or write:—

INCA

data systems
pty. ltd.

33 Ryde Road, Pymble,
2073. Phone (02) 498 6933
P.O. Box 200 Pymble 2073

Hints for CHIP 8 programmers

Part 2

IN THIS PART you can learn how to put *big* scores on the screen, explore the operation of the sound generator and learn how to use it in programming and cap it all off with a bunch of fun subroutines from the indefatigable Frank Rees.

Music Maker

Peter Collins, Springvale South, Vic.

While exploring new uses for the '660 I decided to write a 'song' using notes from the *Song In the Key of Yale* program published with the *Programming in CHIP 8* article, November 1981. This was fine, but how could I develop songs in different keys? I then decided to develop the following program to assist. Keys on the keyboard are used to control the program and step through the tones, displaying the hex value of each note on the screen. Here's what each key does:

KEY 0: Tone generator starts at the highest tone and steps *down* in pitch.

KEY 5: Stops the tone at the step it is on.

KEY 1: Repeats the tone of a value displayed on the screen.

KEY 4: Manually *increases* the tone one step for each key press.

KEY 6: Manually *decreases* the tone one step for each key press.

KEY 2: Causes program to jump to song routine.

You can write a song by setting the duration of the tone required using Variable 1 (V1) and setting the tone using Variable 0 (V0). Then follow with a 'do tone' instruction — 27B0 if no space between tones is required, or 'do tone with space' using 278C. If the tone duration and pitch are not changed a further 'do tone' instruction will repeat the tone. If a change in either pitch or duration is required, or both, these are changed before the next 'do tone' instruction by setting the values of V0 and V1 as required.

Spaces are located in routines which can be called as required. A short space is located at 078E and 'special' spaces are located at 0776, 077A, 077E and 0782 by setting V4 then jumping to a timer loop which controls the duration of the space.

Five-digit scoring

Raymond Jones, Eltham Nth, Vic.

This routine extends the counting capability

of the '660. Instead of the normal 0 to 255 count available with the interpreter this counter allows 0 to 99999 count, just the shot for those long duration, high scoring games.

It is intended to be used as a subroutine. All variables used are stacked from 07F8. The value to be added must be variable A, i.e: VA.

Note that VA cannot exceed 245. If a score higher than this is required to be added then the routine will need to be accessed twice, or more (245 = F5).

The coordinates of the score are:

Horizontal — V6

Vertical — V5

Program operation:

0700 — 070E initialisation.

0710 — 074C incrementation & sorting.

074E — 0756 storage and retrieval of variables.

0758 — 0776 display of value.

When used in a program it will be first required to initialise the counter by going to 0700, i.e: a 2700. To erase the present score in preparation for the new score jump to 0754, i.e: a 2754. To display the new score jump to 0710, i.e: a 2710.

To check the operation of the subroutine, use this simple program:

0600 2700 2754 6AXX 2710 1602

where XX is the value to be added (hex).

If all works OK then save it on tape for future use in your extravagant programs (save from 0700 to 0777 to avoid erasing a program you may be working on).

Fun routines

Frank Rees, Boort, Vic.

Here's something to have fun with. Table 4 lists a group of routines which can be incorporated in other programs by themselves, or can have a program written around them. As they stand you can enter and run the complete set and see what it does. It can write a four letter word on screen (oooohh! — Ed.), it can make black white and white black, no argument, then sort the screen out with a routine you may have heard about but not 'seen' — *the bubble sort*.

Each of the routines is 'called' as a subroutine with a 'key wait' separation between each subroutine call.

As I said before, the routines can be used on their own and can be made more effective. For example, try writing out all but the Four Letter Word routine by putting a GOTO, to jump, or replace, unwanted instructions. Have a go at changing one instruction to change word length.

To speed up the bubble sort routine a bit, reset and change the instruction at location 0616 (0216) from 6B19 to 6B01. The Bubble Sort routine is well down memory so you can use it with other ideas you may like to try without needing to relocate it. A very effective display is created by producing a random dot pattern followed by a bubble sort and then repeat without erasing the screen between runs. Leave it running for a *few hours* and watch it. Fascinating!

Both the Screen Invert and Bubble Sort routines demonstrate the need for machine code to speed things up, but in their present form they make observation on working possible without any delay.

The technique used in the Bubble Sort can be slow, even though machine code and more advanced techniques are used in many practical applications. Be sure after a bubble sort to reset and have a look in screen memory, starting from the top, to see what's been going on.

The program runs 'as is' in the ETI-660 with its CHIP 8.D3. For other dialects, the instruction at locations 0638, 0644, 0746 and 076C will need to be changed to A100. In CHIP 8.D2 computers without extra memory, no other changes are required as addresses 0200-03FF and 0600-07FF are the same locations. For other CHIP 8 computers with extra memory at 0600-07FF, you will need to add a 1600 instruction at location 0200. All others will need to have the program relocated to 0200-03FF and this involves changing 1MMM and 2MMM instructions.

References to 16MM, 17MM, 26MM, and 27MM would be changed to 12MM, 13MM, 22MM and 23MM respectively.

The program contains some useful ideas for study. Try the 'complement' function of the inverse screen routine at locations 063E to 0643 on paper, in binary.

You can run the Four Letter Word routine as a game on its own. Change the instruction at 0608 from 2634 to 1600. For random dots to sort, change the instruction at 0640 from 8205 to C2FF.

Have fun!

FIVE DIGIT COUNTER

```

0700 6000 6100 6200 6300 6400 6512 670A 174F
0710 A7P8 P765 80A4 8075 4F00 1720 7101 1716
0720 700A 8175 4F00 172C 7201 1722 /10A 8277
0730 4F00 1738 7301 172E 720A 8375 4F00 1744
0740 7401 173A 730A 8475 3F00 1746 740A A7P8
0750 F755 1758 A7P8 P765 0612 F429 D655 7604
0760 F329 D655 7604 F229 D655 7604 F129 D655
0770 7604 P029 D655 00EE
    
```

MUSIC MAKER

```

0600 6400 E4A1 17AA 6401 E4A1 17A6 6402 E4A1
0610 17A2 6404 E4A1 179C 6406 E4A1 1798 1600
0620 268A 2782 268A 2782 26A0 611A 6021 278C
0630 602A 278C 6021 278C 6130 6025 278C 277E
0640 610C 6021 278C 278C 6025 278C 6120 602A
0650 27B0 277E 610F 602A 27B0 611C 6021 27B0
0660 610C 601C 278C 278C 278C 6120 601F 27B0
0670 277E 26A0 611A 6021 278C 602A 278C 6025
0680 278C 6130 602A 27B0 16B6 610F 602A 27B0
0690 6021 27B0 601F 27B0 6120 601C 27B0 00EE
06A0 610F 602A 27B0 6021 27B0 601F 27B0 611C
06B0 601C 278C 00EE 277A 60BC 6120 27B0 277E
06C0 60FF 610A 27B0 277E 27B0 277E 60E0 6118
06D0 27B0 277E 60FF 27B0 277A 60C4 610E 27B0
06E0 277A 60BC 27B0 1600
    
```


```

0776 64D0 178A 6477 178A 64D0
0780 178A 6433 7401 3400 178A 00EE 27B0 64F0
0790 7401 3400 1790 00EE 7001 179E 70FF 6501
07A0 17AE 6502 1620 6501 17AF 6500 6000 610F
07B0 F000 F115 F118 F207 3200 17B6 4502 00EE
07C0 27D0 6405 E4A1 1600 4501 1600 7001 17B0
07D0 00E0 A7FE F055 6A20 6B15 F029 DAB5 07F0
07E0 A7FF F065 6A1B F029 DAB5 A7FE F065 00EE
07F0 F807 BEF8 FEAE EE72 F6F6 F6F6 73D4
    
```

CONTROL ROUTINE

```

0600 1602 GO TO 0602 universal no operation
0602 00E0 ERASE clear screen
0604 2612 DO SUB 0612 call subroutine 1
0606 F00A V0 = KEY key wait only
0608 2634 DO SUB 0634 call subroutine 2
060A F00A V0 = KEY key wait only
060C 2740 DO SUB 0740 call subroutine 3
060E F00A V0 = KEY key wait only
0610 1600 GO TO 0600 loop back to start
SUBROUTINE 1 - FOUR LETTER WORD GAME
0612 1614 GO TO 0614 universal no operation
0614 6A10 VA = 10 use as X coordinate display
0616 6B19 VB = 19 use as Y coordinate display
0618 620A V2 = 0A use as filter
061A 610F V1 = 0F use as filter
061C COFF V0 = RND.FF L1, random number from 00 to FF
061E 8012 V0 = V0 AND V1 filter out all above 0F
    
```

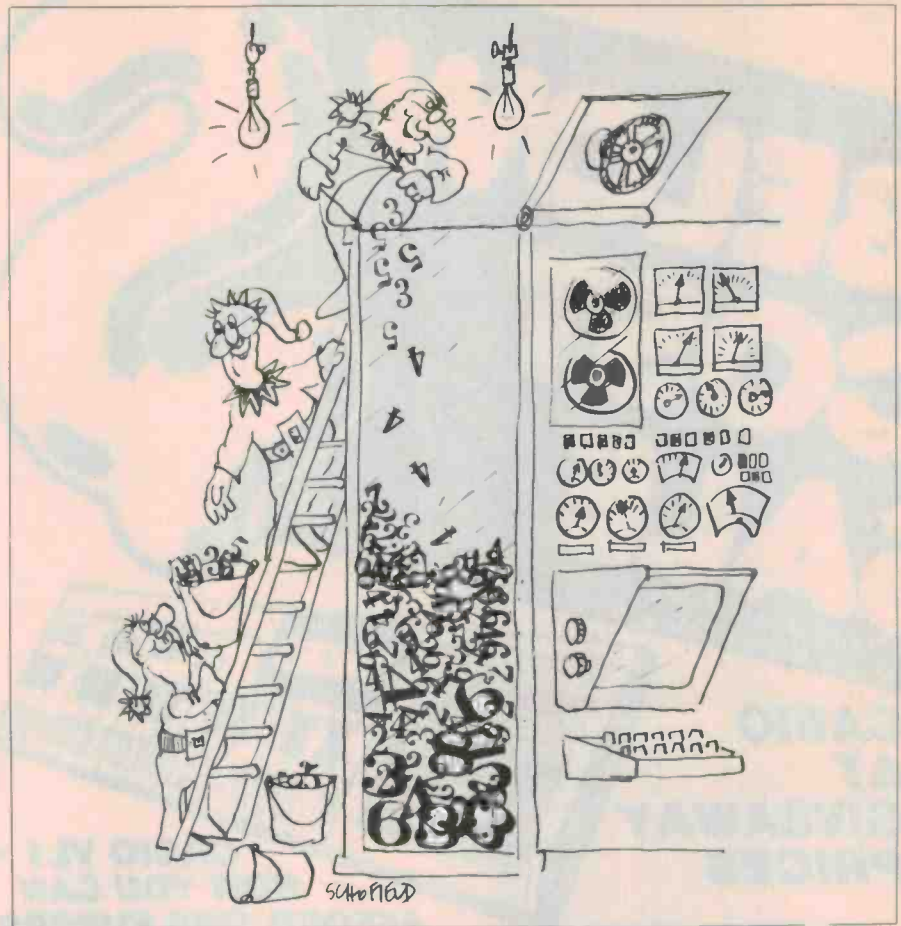

```

0620 8300 V3 = V0 copy V0 in V3 for test
0622 8325 V3 = V3 - V2 equals V0-V2 if V0=Ato F, VF=0
0624 3F01 SKF VF = 01 otherwise go get another number
0626 161C GO TO 061C by looping to L1
0628 F029 I = DISP,V0 prepare V0 for display
062A DAB5 SHOW 58VA,VB display at X=VA,Y=VB, 5 bytes
062C 7A04 VA=VA+04 add to X coordinate to move right
062E 3A20 SKF VA = 20 after four letters
0630 161C GO TO 061C choose another letter
0632 00EE RETURN return to instruction after caller
    
```

SUBROUTINE 2 - INVERT SCREEN

```

0634 1636 GO TO 0636 universal no operation
0636 6100 V1 = 00 use to add to pointer
0638 A480 I = 0480(A100) set pointer to screen start
063A F11E !=I+V1 current pointer calculation
063C F065 V0 TO V0+MI load V0 there
063E 62FF V2 = FF start of complement function
0640 8205 V2=V2-V0 complement FF-M -> M
0642 8020 V0=V2 copy V2 into V0
0644 A480 I=0480(A100) set pointer to screen start
0646 F11E I=I+V1 current pointer calculation
0648 F055 MI=V0 TO V0 store V0 there
064A 7101 V1=V1+01 add to pointer counter
064C 3100 SKF V1=00 finish if 100 done
064E 1638 GO TO 0638 otherwise go do next
0650 00EE RETURN return to instruction after caller
    
```

SUBROUTINE 3 - BUBBLE SORT

```

0740 1742 GO TO 0742 universal no operation
0742 6200 V2=00 use for byte count
0744 6300 V3=00 use for swap flag
0746 A480 I=0480(A100) start of bytes-to-be-sorted pointer
0748 F21E I=I+V2 add byte counter to pointer
074A F165 V0 TO V1=MI get two bytes from calculated location
074C 9010 SKF V0 < V1 if bytes equal
074E 1758 GO TO 0758 skip test for swap
0750 8500 V5=V0 copy V0 in V5 for test
0752 8515 V5=V5-V1 if V0 < V1, then V5-V1
0754 3F00 SKF VF=00 causes flag VF to be = 0
0756 2764 DO SUB 0764 other lse swap subroutine called
0758 7201 V2=V2+01 add one to bytes counter
075A 32FF SKF V2=FF skip if 100 bytes done
075C 1746 GO TO 0746 otherwise go do next bytes
075E 3300 SKF V3=00 skip if swap flag indicates no swap in last 100 bytes
0760 1742 GO TO 0742 otherwise go through 100 bytes again
0762 00EE RETURN return to instruction after caller
SUBROUTINE 3A - SWAP
0764 8410 V4=V1 copy by 1 to V4
0766 8100 V1=V0 copy byte 0 into V1 swap routine
0768 8040 V0=V4 copy byte 1 into V0
076A 6301 V3=01 set swap flag
076C A480 I=0480(A100) set pointer to start of sort
076E F21E I=I+V2 calculate current address
0770 F155 MI=V0 TO V1 store swapped values of V1 and V2
0772 00EE RETURN return to instruction after caller
    
```

BELOW COST SALE

Only items marked ★ are below cost. All others are at our normal low prices.



★ 30 2N3055's PACK

30 below spec 2N3055s at a steal of a price. Great for experiments or where the full spec is not required. We have sold tens of thousands of these transistors with no returns.

\$3.00

for 30!!



★ TAG TANTALUM SELLOUT!!


We all know just how expensive tantalum caps are. So look at our price!! 4 each of the following values (12 in all) 3.3µF 16V, 4.7µF 25V, 100µF 6.3V. Normally you would pay around \$5.50. Look at our price.



12 tantalums \$1.95
Normal cost approx \$5.50!!!

★ 6.5mm STEREO JACK PACK

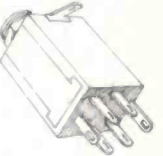Pack of 5 stereo switching jacks sockets, as used on amplifiers for headphone socket. Normally you would pay around \$1.00 each for these. We are selling a pack of 5 for only \$2.50. That's around half price!!



5 for \$2.50

★ THUMBWHEELS 1/3 NORMAL PRICE!!

High quality UK STOLEC 10 position single pole thumbwheel switches slashed for this month only. These precision switches are in grey plastic. Dimensions 57mm (height) x 70mm deep x 15mm wide. Scoop price!!



5 FOR \$10.00!!


★ AUDIO LEAD PACK

We've put together these super audio lead packs at a fraction of normal cost. Pack includes:

PART NO DESCRIPTION

- A 5 pin DIN plug to 5 pin DIN plug
- D 3.5mm plug to 2 alligator clips
- F 5 pin DIN plug to 4x6.5mm plugs
- I 6.5mm plug to 2 x 6.5mm sockets
- K 5 pin DIN plug to 3.5mm plug
- M 5 pin DIN plug to 4 x RCA plugs

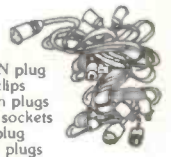Others are charging \$2.00 - \$3.00 each!!




ALL 6 only \$5.00

★ J.B. VARIABLE CAP

Precision made, ceramic insulation, 6-150pF value, this one has got the lot! You would expect to pay over \$10.00 but look at our price!!

\$2.50

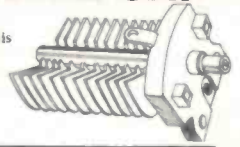

SHERIDAN ELECTRONICS

164-166 Redfern St., Redfern NSW 2016. Phone (02) 699 6912, (02) 699 5922. Mail Orders to Dept ET, PO Box 229 Redfern NSW 1606

Trading Hours	Mail Charges
Mon-Fri ... 9am-5.30pm	\$5.00-\$9.99 ... \$3.50
Thursday ... 9am-7pm	\$10.00-\$24.99 ... \$4.00
Saturday ... 9am-12noon	\$25.00-\$49.99 ... \$6.00
	\$50.00-\$99.99 ... \$7.00
	\$100 or over ... \$8.00



Note: We accept both Bankcard and American Express.

Note: we regret we are unable to offer credit card facilities on quantity purchases and below cost items.

CASIO AT GIVEAWAY PRICES




CASIO VL1 - NOW YOU CAN AFFORD THIS SUPERB LITTLE INSTRUMENT!

Now you can afford a superb musical instrument. Built by Casio - acknowledged as the world's most advanced designer of small keyboards, the VL-1 lets you move into a new world of music. The keyboard incorporates ONE KEY PLAY so you learn quickly without training. With just one finger, you can play a melody. Other features include:

- AUTO PLAY ● 5 sounds (inc. piano, violin, flute and guitar) ● 10 Auto Rhythms ● 2 way power (battery or optional AC adaptor. These superb little keyboards were selling for \$89.00 but look at our super low price!!

only \$69.00

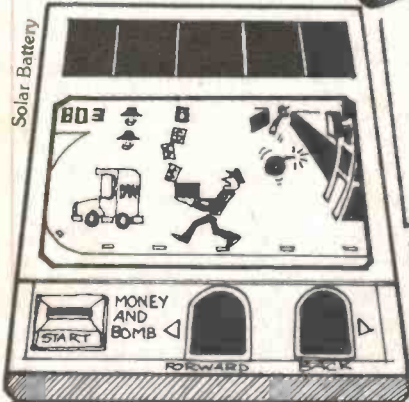

MONEY AND BOMB CLOCK/GAME/CALC

This is a real action game for the true enthusiast. If you've played a lot of games, move up to the best!! The robbers wait to ambush your bankguard, so get him on the move as fast as his legs will carry him. But watch out for the bomb! It's right behind him! Just two keys to press to foil the bankrobbers!! The Money and Bomb uses a built in amorphous solar battery so there are no more battery costs. Normal price for this game is \$34.95, but at Sheridans you save!!

Money and Bomb \$31.95

THREE PUZZLE GAME/CLOCK/CALC

This great little combo gives all you traditional puzzle players a real challenge. The screen converts from a clock/calculator to a puzzle panel.


Three games:

Game 1: Put the same number in all squares.

Game 2: Spin the numbers and test your luck. A real casino delight for all you gamblers!!

Game 3: Hit the '0' whenever it appears then hit the random number. This one will really keep you on your toes!!

\$24.95

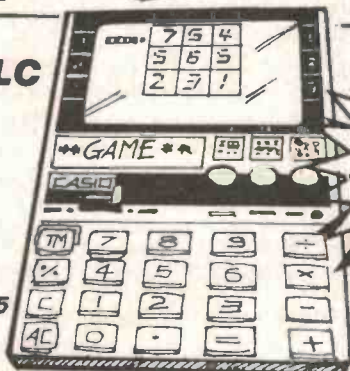

TOP VALUE ON CASIO GAMES

NEW BOXING GAME a knockout!!


Now you can get a calculator, clock, alarm and a great boxing game in one package. This game packs real action: Straights, body blows, counter punches, KO's... A realistic animated boxing game that puts you in the ring against the Casio Champ!! Take the challenge. It will really keep you on your toes.

\$19.95

WERE \$34.95

K-NAR COMPUTER CARDS


S100 Z80 SYSTEM CARD SPECIALISTS

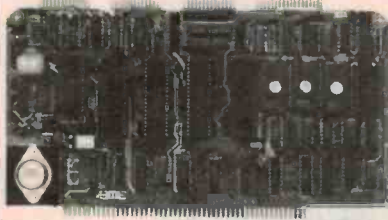

SBC-800



FDC-II

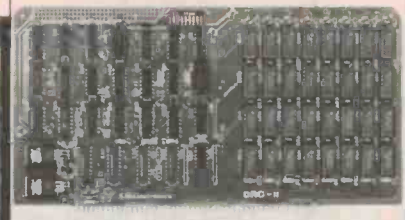

DRC-II

You know the SME Systems boards as the most powerful and technically up-to-the-minute manufactured in Australia today.

Using K-NAR's mail order system can save you dollars. Compare our prices on these high performance cards.

SBC-800

4Mhz Z-80 CPU, two serial RS232 ports, software programmable Baud rate gen., Centronics parallel port, 22 prog. I/O lines, real time clock (battery backed), 2K CMOS RAM, power on reset/power fail detect, battery backed as standard, etc. List Price \$495. Our Price \$395.

FDC-II

Enhanced floppy disk controller, IBM 3740 compatible, operates 5 & 8" and single/d. density drives, handles up to 4 drives, runs multi-density CP/M2.2 & MP/M 2. Vectored interrupt operation optional. List Price \$465. Our Price \$370.

DRC-II

The board for multi-user installations. 64/256K dynamic RAM card, bank select, fast 4Mhz operation, on-board memory prom, dip-switch selectable boundaries, bank mode allows up to 8 boards on bus, hidden refresh, phantom disable. List Price \$600. Our Price \$475.

CRC-48


Fool-proof memory system. State-of-the-art CMOS memory card with memory protection. on board battery back-up, compatible with DRC-II, write protection enable/disable, can be used as complete EPROM card or any combination of EPROM or CMOS ram. List Price \$525. Our Price \$420.

VDC-8024


The low cost alternative to stand-alone terminal. Flexible 80x24 memory mapped video display board with full ASCII, semi graphics, Inverse & half intensity video, flicker free screen updating. Battery backed option offers diagnosis of system shut downs. List Price \$325. Our Price \$265.

SPC-29

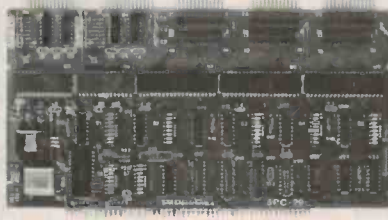
High performance dual serial & 9 parallel port I/O CARD, with full I/O address decoding. Switch selectable baud rates. Link patch area, programmable modes for strobed/latched I/O. List Price \$295. Our Price \$235.




SPC-29

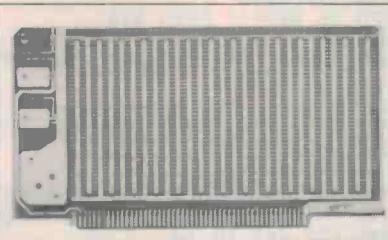

S - 100 WIRE WRAP CARD

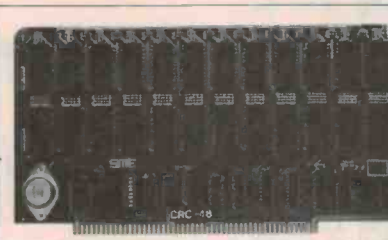

CRC-48

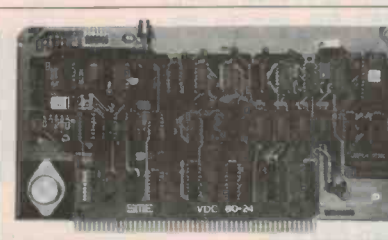

VDC-8024



MINI CARD CAGE

MINI CARD CAGE

Compact card cage frame with 5 - slot motherboard plated through hole. Five edge connectors. Our Price \$125.

S - 100 WIRE WRAP CARD

Gold-plated edge connectors, through hole plating, provisions for four regulators, distributed power rails. I/O connector provision on top of card. Our Price \$33.


PACKAGE SPECIAL

Try this for value

SBC-800 • FDC-II • DRC-II

& 5-slot motherboard with mini-cage. Monitor/BIOS EPROM.

Special package price \$1425*

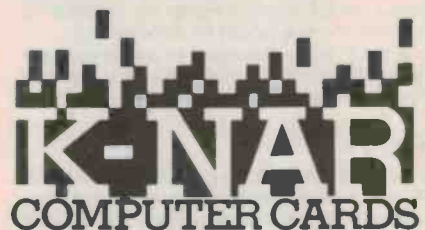

PO Box 412, Dandenong, 3175 Phone (03) 795 5858
Authorized distributor of SME Systems products.

* Prices subject to change without notice. All prices excluding tax. For retail prices add 20%.
All boards fully assembled and tested and backed by 90-day guarantee.

To K-NAR Computer Cards

Please send me product data sheets.
(I enclose 4 stamps).

I wish to order

My cheque/order form is enclosed

Please debit my Bankcard No.

Name

Address

Signature

Please include me on your new product mailing list. I am mainly interested in systems for Hobby, Industrial use Education Business Process control Other

MICROBEE COLUMN

Bee-O-Rhythms

Tom Moffat
Fern Tree, Tasmania

WE'VE ALL HEARD of biorhythms, haven't we? Very popular in the mid-1970s, almost a cult, with many of the attractions of astrology. Today there are still many believers.

We all know that much of life exists in cycles... Lunar cycles, Sunspot cycles, menstrual cycles, economic booms and depressions, the four seasons, day and night, ice ages... all going up and down, or round and round.

Proponents of the biorhythm theory say that the human body experiences cycles that start together at birth and then fluctuate at different but steady rates throughout the rest of life. The way this works is set out in the program listing, so we won't repeat it here.

There is an organisation in Basel, Switzerland, called 'Biorhythmik Centre' that seems to take a very serious view of biorhythms. They claim that a study at the Swiss Federal School of Technology in Zurich has confirmed that biorhythms do indeed exist.

Here are some quotes from their report, reproduced without comment:

"It has been repeatedly proved and confirmed that the tendency to physical or intellectual failure is particularly pronounced on critical days.

"If a businessman uses regeneration (negative) days for making preparations, he establishes all conditions for successful conferences, executive measures, and decisions in the positive phase.

"Medical treatments, inoculations, dental operations, etc are least likely to cause pain and to be followed by complications during the positive phase.

"Enhanced powers of concentration during the positive phase make it easier for students to assimilate the material that has to be learned.

"Industries that take account of biorhythms have found their accident rate falling by 30%, and their production and sales increasing by 20 to 30%.

The program

This MicroBee version is developed from what is probably one of the earliest biorhythm implementations for computers. It appear to have originated in an article in Byte magazine sometime in the mid-70s. It's been written and re-written for many small computers over the years, and it seems to have made its way into at least one well-known Australian mainframe system.

It's a good program with a clever way of using a non-graphics printer to draw the curves. But the earlier versions had a problem. The biorhythms they churned out were wrong! There was a mathematical problem in the method of calculating how many days old the subject was, such that results during the early months of life came out negative and the figures for later years were offset accordingly.

Users of this new program will be happy to know that it's working with a completely different age calculating algorithm and results will be correct (I hope...). But how many mainframe systems did the original version of the program get written into? How many of these mainframe systems were in businesses that reported 'spectacular' results from biorhythms?

The program print-out was done, as usual (with my system) with an antique Model-15 teletype machine, built before the days of ASCII characters. So, 'X' means multiply, and 'OUT5 ON' and 'OUT5 OFF' should read 'OUT#5 ON' and 'OUT#5 OFF'. One of these days I'll get a decent printer, I promise...

```
00100 REM BIORYTHM PROGRAM BY TOM MOFFAT, 5,9,82
00110 REM TO BE USED WITH OR WITHOUT PRINTER.
00120 DIM T(12),S1(52)
00130 FNO=(SIN(FRACT(A1/4)*X6.28)+1)*X25+3
00140 CLS: INPUT 'WHAT IS YOUR NAME? ',N1$
00150 INPUT 'DO YOU WANT A DESCRIPTION? (Y OR N)',K1$
00160 IF K1$='N' THEN 330
00170 CLS: PRINT 'THE THEORY OF BIORYTHM STATES THAT LIFE EXISTS IN'
00180 PRINT 'THREE CYCLES, ALL STARTING AT BIRTH. THE PHYSICAL CYCLE'
00190 PRINT 'HAS A PERIOD OF 23 DAYS, THE EMOTIONAL CYCLE IS 28 DAYS,'
00200 PRINT 'AND THE INTELLECTUAL CYCLE IS 33 DAYS.'
00210 PRINT '      WHEN A CYCLE IS UP, THE FUNCTION IS OPERATING AT'
00220 PRINT 'PEAK EFFICIENCY. WHEN IT IS DOWN, THE FUNCTION IS'
00230 PRINT 'RESTING, AND AT ZERO CROSSING, THE CYCLE IS SAID TO BE'
00240 PRINT 'CRITICAL, A TIME WHEN CAUTION IS INDICATED. WHEN TWO'
00250 PRINT 'CYCLES COINCIDE AT CRITICAL THE DAY IS SAID TO BE'
00260 PRINT 'DOUBLE-CRITICAL. WHEN ALL THREE COINCIDE AT CRITICAL,'
00270 PRINT 'THE DAY WILL BE A TOTAL DISASTER.'
00280 PRINT '      NOW, 'N1$', YOU MAY SAY THAT THIS WHOLE CONCEPT IS'
00290 PRINT 'A LOAD OF OLD CODSWALLOP. IF SO, PRESS ANY KEY TO EXIT.'
00300 PRINT 'BUT IF YOU'RE GAME, PRESS ANY OTHER KEY TO CONTINUE.'
00310 K1$=KEY$
00320 IF K1$='' THEN 310
00330 CLS
00340 INPUT 'PLEASE ENTER YOUR BIRTHDAY (DD,MM,YY):' D,M,Y
00350 GOSUB 780
00360 A=Z
00370 INPUT 'WHEN DO YOU WANT YOUR CHART TO BEGIN (DD,MM,YY)?' D,M,Y
00380 GOSUB 780
00390 A=Z-A
00400 INPUT 'AND FOR HOW MANY DAYS?';L
00410 DATA 31,28,31,30,31,30,11,31,30,31,30,31
00420 FOR I=1 TO 12
00430 READ T(I)
00440 NEXT I
00450 OUT5 ON
00460 CLS
00470 PRINT TAB(10);'XXX PERSONAL BIORYTHM CHART FOR ';N1$;' XXX'
00480 PRINT TAB(10);'PHYSICAL = P; EMOTIONAL = E; INTELLECTUAL = I'
00490 PRINT
00500 PRINT ' '; 'DATE'
00510 PRINT TAB(13) 'DOWN';
00520 PRINT TAB(35) 'CRITICAL';
00530 PRINT TAB(62) 'UP'
00540 PRINT ' ',(A62 45)
00550 A1= FLT(A)
00560 P=INT(FNO(23))
00570 E=INT(FNO(28))
00580 I=INT(FNO(33))
00590 FOR X=0 TO 52
00600 S1$(X)=' '
00610 NEXT X
00620 S1$(28)='.'
00630 S1$(P)='P'
00640 S1$(E)='E'
00650 S1$(I)='I'
00660 PRINT STR(D); STR(M); STR(Y); TAB(10);
00670 FOR X=0 TO 51
00680 PRINT S1$(X);
00690 NEXT X
00700 PRINT S1$(52)
00710 IF L=1 THEN OUT5 OFF: END
00720 L=L-1
00730 A=A+1
00740 D=D+1
00750 IF M=2 AND D=29 AND Y=(Y/4)*4 THEN 550
00760 IF D=(T(M)) THEN 550 ELSE LET M=M+1: D=1
00770 IF M=12 THEN 550 ELSE LET M=1: Y=Y+1: GOTO 550
00780 M1=FLT(M): Y1=FLT(Y)
00790 Z=INT(30.57XM1)+INT(365.25XY-1-32537.25)+D
00800 IF M<3 THEN RETURN
00810 IF Y=(Y/4)*4 THEN LET Z=Z-1 ELSE LET Z=Z-2
00820 RETURN
```

XXX PERSONAL BIORYTHM CHART FOR BABY NEW YEAR XXX
 PHYSICAL = P, EMOTIONAL = E, INTELLECTUAL = I

DATE	DOWN	CRITICAL	UP
1 1 83		I	
2 1 83		IEP	
3 1 83		IE P	
4 1 83		IE P	
5 1 83		IE P	
6 1 83		IE P	
7 1 83		IE P	
8 1 83		IE P	
9 1 83		IE P	
10 1 83		IE P	
11 1 83		IE P	
12 1 83		IE P	
13 1 83		IE P	
14 1 83		IE P	
15 1 83		IE P	
16 1 83		IE P	
17 1 83		IE P	
18 1 83		IE P	
19 1 83		IE P	
20 1 83		IE P	
21 1 83		IE P	
22 1 83		IE P	
23 1 83		IE P	
24 1 83		IE P	
25 1 83		IE P	
26 1 83		IE P	
27 1 83		IE P	
28 1 83		IE P	
29 1 83		IE P	
30 1 83		IE P	
31 1 83		IE P	
1 2 83		IE P	
2 2 83		IE P	
3 2 83		IE P	
4 2 83		IE P	
5 2 83		IE P	
6 2 83		IE P	
7 2 83		IE P	
8 2 83		IE P	
9 2 83		IE P	
10 2 83		IE P	
11 2 83		IE P	
12 2 83		IE P	
13 2 83		IE P	
14 2 83		IE P	

Classifieds : Classifieds

CLASSIFIED RATES

15¢ per character

Minimum of 32 characters

CHARGES: Cash with order only

COMPUTER CLINIC repairs & services Sorcerer, Pet, Apple, System 80, Super 80, Tandy & others. (07)269 8573, P.O. Box 68, Aspley, Qld.

PCB's and SCREEN PRINTING at the best prices. Short runs, long runs from your own artwork. Contact Peninsula Circuits, 7 Portrush Gr., Mornington 3931. (059) 75 5568.

REPAIRS to all home, hobby and small business microcomputer systems and peripherals, also all EA & ETI projects. CAE Electronics, 1/27 Forge St, Blacktown 2148. (02)621 4242.

COMPUTERS: call us for the best price on full range of Commodore & Osborne computers. Inc. software and component parts. See our add this issue. Data Parts, Shepparton. Phone (058) 21 7155, 21 0240.

SORCERER Disk Upgrade Kit with manual. Many Pro features. MICRO-POLIS \$44.95. EXIDY FDS \$39.95. A must! Also free Soft. catalogues. PJB Box 252, Forestville 2087.

COMPUTER Clinic repairs and services Sorcerer, Pet, Apple, System 80, Super 80, Tandy and others. (07) 269 8573, P.O. Box 68, Aspley, Qld.

magmedia magmedia magmedia

Here's to longer life with Datalife from Verbatim.



Verbatim is committed to offering customers the very best removable magnetic storage media. Our line of highest quality magnetic storage products extends to virtually all removable media forms and includes Datalife TM flexible disks and minidisks, data cartridges, data cassettes and Datalife TM head cleaning diskettes. Verbatim is intent on keeping their products at the forefront of technology, going above industry standards, setting a new standard for excellence.



magmedia

MAGMEDIA SERVICE PUTS THE CUSTOMER FIRST

SYDNEY
(02) 428 1100
CANBERRA
(062) 48 6751

BRISBANE
(07) 229 1600
HOBART
(002) 34 4522

MELBOURNE
(03) 699 9688
PERTH
(09) 328 3311

ADELAIDE
(08) 223 6261

magmedia magmedia magmedia

**"OUR AIM:
TO KEEP
ELECTRONICS
PRICES
DOWN IN '83"** Dick Smith

**SAVE
ON QUALITY
DICK SMITH TAPE**

Top quality cassette tapes at a low economical price. They're as good as imported cassettes you'd pay \$\$\$ more for!


C60 Low Noise Cat C-3350	C90 Low Noise Cat C-3352	C90 EDR Cat C-3354
WAS \$1.50 pay only	WAS \$2.00 pay only	WAS \$2.75 pay only
\$1.00 ea.	\$1.20 ea.	\$1.90 ea.

THIS MONTH ONLY!

THAT'S UP TO 40% OFF!

**PROJECT BUILDERS SAVE
ON PRO FINISH
PLASTIC CASES**

**INSTRUMENT CASE
WITH HANDLE**

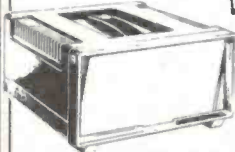

Top quality design for larger projects. Size 200x200x100mm. Cat H-2500

WAS \$21 NOW **\$17.50**

**SUPERB
PROJECT CASE**



For all 'instrument' type projects. Split apart design. Size 200x160x65mm. Cat H-2505

WAS \$19.95 NOW ONLY **\$9.95**

NEW QUALITY CASE

Stylish new case for smaller projects. Split apart design. Size 130x125x38mm. Cat H-2506

ONLY **\$12.50**

THIS MONTH ONLY!

**The Affordable
DFM**



**600MHz 7 Digit
Frequency Meter**

No hobbyist can afford to be without this incredibly accurate piece of test equipment. Fits easily into the palm of your hand. Variable gating times and 3 ranges- 6MHz, 60MHz and 600MHz. Battery operated...take it anywhere! Cat D-3000

WAS \$205 NOW ONLY **\$199**
Why Pay More?

**LISTEN TO
AIRCRAFT**



**AIR BAND
(VHF) AND
AM RADIO**

Listen to pilots and air traffic controllers. Has normal AM band too. Battery operated. Cat O-2836

ONLY **\$29.50**

YOU'LL HEAR
CHOPPERS
TOO!



**STOCK CLEARANCE
SAVE 25%**

NYLON NUTS & BOLTS

Precision white nylon. Fully insulated and heat resistant.

Description	Qty. Pack	Cat. No.	PACK WAS	NOW ONLY
12mm x 4BA cheese head	10	H-1012	95c	70c
25mm x 4BA cheese head	10	H-1022	95c	70c
4BA hex nut	12	H-1302	\$1.95	\$1.45
4BA washer	12	H-1452	95c	70c
12mm x 6BA cheese head	10	H-1032	95c	70c
25mm x 6BA cheese head	10	H-1042	80c	60c
6BA hex nut	10	H-1312	\$1.95	\$1.45
6BA washer	10	H-1462	95c	70c

STEEL NUTS & BOLTS

1/8" round head zinc plated.

Description	Qty.	Cat. No.	WAS	NOW ONLY
9mm long	25	H-1052	75c	55c
12mm long	25	H-1062	75c	55c
25mm long	20	H-1072	75c	55c
3mm hex nut	30	H-1322	90c	70c
3mm shake proof washer	50	H-1472	80c	60c
3mm metal washer	50	H-1482	80c	60c


SELF TAPPING SCREWS

Cadmium plated steel. Ideal for projects.

Description	Qty.	Cat. No.	WAS	NOW ONLY
No. 4 x 12mm: Size 40	25	H-1612	80c	60c
No. 4 x 6mm: Size 40	25	H-1611	80c	60c
No. 8 x 12mm: Size 30	25	H-1632	95c	70c

THIS MONTH ONLY!

\$100 OFF!

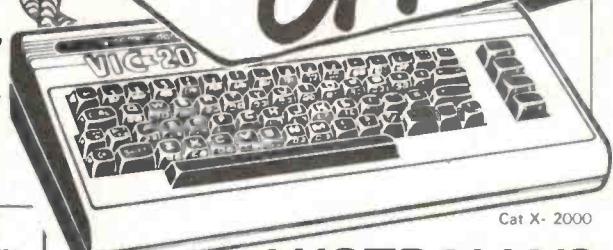

Cat X-2000

**AUSTRALIA'S
MOST POPULAR
COLOUR COMPUTER-
THE VIC 20**

Sensational price cut on the amazing VIC 20 colour computer. Buy NOW and save a massive \$100...yes 25% off!!! Australia's best value colour computer with superb graphics display in up to 8 colours.

WAS INCREDIBLE
VALUE AT \$399
NOW ONLY **\$299**



GREAT VIC 20 MANUALS

PROGRAMMERS REFERENCE GUIDE
Reference manual on VIC BASIC, Programming and much more. Cat B-2004 **ONLY \$25**

LEARN COMPUTER PROGRAMMING
How to write, develop & test Basic programs on the VIC. Cat B-2005 **ONLY \$8.95**

VIC REVEALED
How and why VIC works and how to write better programs. Cat B-2006 **ONLY \$17.50**

INNOVATIVE COMPUTING
Program your own exciting arcade games as well as many new ones. Cat B-2007 **ONLY \$17.50**

YOU JUST BOUGHT A PERSONAL WHAT?
Microsoft and Level II basic creative programs. Cat B-2331 **WAS \$15.95 NOW \$12.95 ONLY**



Terms available to approved applicants through... **HFC**

DSE/A403/HCE

\$50,000 IN PRIZES TO BE WON IN THE MIGHTY MATCH-UP COMPETITION. SEE YOUR NEAREST DICK SMITH STORE.

SCOOP BUY CAR SPEAKERS
AMAZING VALUE
 A Big sound with a small price
 Flush mounted with black cover
 Sins, Swait, 5ohms
 Cat. A-6986 **\$4.95 each**

**EXPERIMENTERS
 LOOK AT THIS
 PROTO BOARD**

Designing your own circuits? then Proto board is a must.

- No soldering
- No desoldering
- No heat damaged components
- No wasted time

Accepts IC's, LSI's, resistors, capacitors, LED's, transistors, relays, etc.
 Box board with two clip on extensions, 390 holes in all and you can add more for even bigger projects - Cat P-4614


SAVE \$2.00
\$7.20

**SAVE \$56
 THIS MONTH ONLY**
 Model V-152B
HITACHI CRO
**QUALITY AT A
 LOW LOW PRICE**

This is a top of the line CRO but with a very low price. Why pay more elsewhere and do no better?

**WAS \$655.00
 NOW \$599.00**

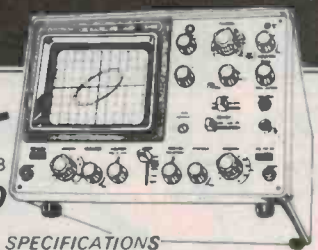**DETAILED TECHNICAL
 BROCHURE AVAILABLE -
 JUST ASK!**



SPECIFICATIONS
 Vertical Sensitivity: 5mV/div - 5V/div
 Bandwidth: DC - 15MHz, -3dB
 Rise Time: 24ns
 Non-dist. max amplitude: More than 4 div @ 15MHz
 Input R and C, Direct 1M ohm, approx. 30pF
 Maximum input voltage: 600V P-P (300V AC + DC peak)
 Display Modes: CH1, CH2, DUAL, ADD, OFF
 Sweep Time: 0.2us-0.2s/div, 19 calibrated steps
 Internal Trigger Sensitivity: 20Hz-2MHz 0.5 div 2:1
 External Trigger Sensitivity: 20Hz-2MHz 800mV 1.5 div
 2-15MHz 800mV
 Power Requirements: 120-240V, 40W
 Dimensions: 275(H) x 190(W) x 400(D)mm
 Weight: approx 8kg Cat Q-1242

**BIG SAVINGS
 ON DICK'S
 ZIPPIES**

THIS MONTH ONLY

The original and the best. The ONLY one with all round ribbing. Don't be fooled by inferior copies. Quick easy all purpose Zippy Box for all projects. Strong and simple PCB's mount without screws.

SAVE 25c
 Small UB1 **\$1.50**
 (28x54x83mm)
 Cat. H-2755

SAVE 35c
 Medium UB3 **\$1.85**
 (41x68x130mm)
 Cat. H-2753

SAVE 45c
 Large UB1 **\$2.30**
 (50x90x150mm)
 Cat. H-2751

SAVE 45c
 Giant UB2 **\$3.30**
 (60x113x196mm)
 Cat. H-2752

SAVE PANEL METER SALE

Accurate high quality meter easy to read with zero adjustment and secure four bolt mounting, ideal for all projects.

SAVE \$1.00
\$7.95

0-50uA (2400 ohms) Cat Q-2020
 0-5A Cat. Q-2030

0-20V (100 ohms) Cat Q-2040
 -20 -+3 VU (1000 ohms)
 (0dB 1mW into 600 ohms) Cat. Q-2050

Dimensions:
 Scale area - 58x31mm
 Overall - 58x52mm

AMAZING QUALITY

**STOCK UP NOW
 SPECIAL PRICE THIS
 MONTH ONLY**

**LARGE PANEL
 METER \$11.95**

Large style easy reading **SAVE**
 0-100uA (1100ohms) cat. Q-2070
 0-1 mA (1200 ohms) cat. Q-2060 **\$1.00**
 Scale size 100 x 50mm Size 100 x 82mm

TERMINAL STRIP

SAVE 31c

99c

Cat. H-6700

This ever popular "chocolate" block in nylon can be used from one to twelve way terminal. Mains use 240V AC Rating

**SAVE ON
 MOVING IRON METERS**

Rugged and accurate AC/DC meter, ideal for power supplies
 Size approx. 55mm wide
 58mm high

0-20V (AC/DC) Cat. Q-2080
 0-10A (AC/DC) Cat. Q-2090

SAVE \$1.00
\$6.95

**ACROSS
 THE BOARD
 PRICE CUTS
 YOU REAP THE
 BENEFIT**

LEVEL METER

Elegant styling with straw coloured face, looks superb when back lit.

Signal Strength Meter
 250uA FSD scale 1-10 Cat. Q-2100
 Center Zero (tuning)
 sensitivity is 250uA half FSD
 (In either direction) Cat. Q-2095 **SAVE \$1.00**
\$4.95

**MAKE YOUR
 OWN IC SOCKETS**

MOLEX PINS

The do-it-yourself IC socket! Ideal for all types of IC's - supplied in strips; you simply solder required number of pins in place, insert IC and break off carrier strip! Even suits round IC's!
 Pack of 100 pins. **\$2.25**
 Cat. P-4504

**EDGE LEVEL
 METER**

Scale calibrated from 1-10 with battery check strip. Ideal for a fine level adjustment meter, audio or battery.
 scale size 32 x 10mm

SAVE \$1.00
\$4.95 Cat. Q-2110

**THREE WAY
 TV/VIDEO/GAME
 COMPUTER SWITCH
 BALUN**

Handy neat switch with antenna and game inputs
 300 ohms and 75 ohms (antenna inputs) output to TV
 Fully shielded in strong metal box

VALUE
\$3.95
 Cat. L-4500

**BIG KNOB SALE
 SAVE ON IMPERIAL KNOBS**

These knobs fit standard 1/4 in. shafts ideal for replacing those worn or missing ones

Very large plastic knob
 Size 40mm dia x 16mm.
 Cat. H-3760 **.75c**

Large flute with silver insert
 24mm dia x 14mm
 Cat. H-3772 **.75c**

Calibrated wide skirt
 37mm dia x 16mm
 Cat. H-3770 **.90c**

Small knob with small skirt
 19mm dia x 13mm
 Cat. H-3762 **.65c**

Positive grip and wide skirt.
 32mm dia x 16mm
 Cat. H-3766 **.55c**

Heavily fluted, small skirt.
 24mm dia x 15mm
 Cat. H-3768 **.55c**

YOU REAP THE BENEFIT

DICK SMITH ELECTRONICS

33 STORES THROUGHOUT AUSTRALASIA

- NSW** Parramatta Rd & Melton St
 T55 Terrace Level
 613 Princes Hwy
 Oxford & Adelaide Sts
 B18 George St.
 531 Pittwater Rd
 147 Hume Hwy
 162 Pacific Hwy
 Elizabeth Dr & Bathurst St
 Lane Cove & Waterloo Rds
 George & Smith Sts
 6 Bridge St
 125 York St
 Tamworth Arc & Kable Ave
 173 Maitland Rd
 263 Keira St
- ACT** 96 Gladstone St

- AUBURN** 648 0558 **VIC** 260 Sydney Rd
BANKST. SQ 707 4888 Nepean Hwy & Ross Smith Ave
BLAKEHURST 546 7744 205 Melbourne Rd
BONDI JCT 387 1444 399 Lonsdale St
BROADWAY 211 3777 Bridge Rd & The Boulevard
BROOKVALE 93 0441 Springvale & Dandenong Rds
CHULLORA 642 8922 **QLD** 293 Adelaide St
GORE HILL 439 5311 166 Logan Rd
LIVERPOOL 600 9888 Gympie & Hamilton Rds
NORTH RYDE 888 3200 **SA** Wright & Market Sts
PARRAMATTA 689 2188 Main South & Flagstaff Rds
SYDNEY 27 5051 Main North Rd & Darlingtong St
SYDNEY 290 3377 **WA** Wharf St & Albany Hwy
TAMWORTH 66 1961 William St & Robinson Ave
TIGHE HILL 61 1896 Centerway Arcade, Hay St
WOLLONGONG 28 3800 **TAS** 25 Barrack St
FYSHWICK 80 4944 Also in Auckland, New Zealand. Re-sellers across Aust. & NZ.

- COBURG** 383 4455
FRANKSTON 783 9144
GEELONG 78 6766
MELBOURNE 67 9834
RICHMOND 428 1614
SPRINGVALE 547 0522
BRISBANE 229 9377
BURANDA 391 6233
CHERMSIDE 59 6255
ADELAIDE 212 1962
DARLINGTON 298 8977
ENFIELD 260 6088
CANNINGTON 451 8666
PERTH 328 6944
PERTH 321 4357
HOBART 31 0800


**SEE
 OVER PAGE
 FOR MAIL
 ORDERS,
 SPEEDY
 BANKCARD
 SERVICE &
 ADDRESSES
 OF MAJOR
 RESELLERS**

DES/A403/RW

The affordable CRO!

OVER 2000 SOLD!

DICK SMITH 6.5MHz 75mm

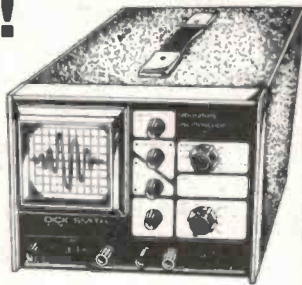

LABORATORY CRO Cat Q-1280

This oscilloscope is ideal for the laboratory, the classroom, in field service, in bench service in assembly centres and, of course, in hobby applications. Solid state electronics (apart from the tube!) ensures extremely low drift and fast warm-up.

Features: Retrace blanking; gives a much clearer display; Lower threshold triggering; less than 1/2 division at 5MHz; Sharper focus - especially at high frequencies; Fibreglass PCB; Colour coded input terminals; AND A USEABLE RESPONSE TO BEYOND 6.5MHz!

STILL ONLY \$199

FIND OUT MORE ABOUT ELECTRONICS THE FUN WAY!

Fun Way Vol. 1

4th printing of this amazing book, 72 pages packed with exciting projects, all safe as they are battery operated. AND all projects are illustrated so mistakes are virtually impossible. Cat B-2600

ONLY \$4.95

Fun Way Vol. 2

After mastering Funway Vol. 1 why not go further? Learn about PCB's and soldering. 130 pages packed with more projects. Cat B-2605

ONLY \$6.95

TRANSISTOR SPECIALS

POWER TRANSISTOR BARGAINS

Quality power transistors at bargain prices: buy now for the junk box - you'll never know when you might need one!

TYPE	DESCRIPTION	Cat No	WAS	NOW
MJ2955	115W 60V PNP Output	Z-1800	\$1.50	\$1.25
MJ3055	115W 60V NPN Output	Z-1804	\$1.50	\$1.25
MJ15003	250W 120V NPN Output	Z-1808	\$5.20	\$4.20
MJ15004	250W 120V PNP Output	Z-1810	\$5.20	\$4.20
2SK133	50W 40V Power Mosfet	Z-1815	\$7.90	\$3.95
2SJ48	50W 40V Power Mosfet	Z-1816	\$7.90	\$3.95

SAVE \$8.50!

DICK SMITH VARIABLE POWER SUPPLY



This popular power supply features a continuously variable voltage range from 5V to 15V DC. The current ratings are 2 amps continuous, 3 amps short term or 4 amps peak pulse. Fuse protection and current limit protection are also featured. Ideal for work bench situation. Cat M-9546

~~\$67.50~~
NOW \$59

SAVE WITH HIWATT BATTERIES

Quality Hi-Watt batteries, low Dick Smith price!



Cat No	Description	each	10up
Cat S-3001	D size metal jacket	35c	30c
Cat S-3002	D size metal jacket	30c	25c
Cat S-3003	AA penlight	25c	22c
Cat S-3004	AAA size	30c	25c
Cat S-3005	UM 5 (R 11)	20c	15c
Cat S-3006	216 9V transistor	50c	45c

'CHARGE' in for these battery bargains!

SAVE ON QUALITY NI-CADS

Don't throw these away - they recharge time and time again!

Cat No	Description	WAS	NOW	STOCK UP NOW!
Cat S-3300	1.2V Ni-cad Pencil	\$2.45	\$2.20	
Cat S-3302	C size cells (pk 2)	\$12.40	\$11.80	
Cat S-3304	D size cells (pk 2)	\$13.20	\$12.50	
Cat S-3306	7.2V (size 216)	\$11.00	\$10.25	

NI-CAD CHARGING CARTRIDGE

To suit the above batteries \$19.95
Charges virtually any size rechargeable battery. Includes test meter and 5 separate LED indicators to show the strength of batteries being charged.

CHEAP RECORD CARE

Push velvet pad with special groove cleaning fluid to keep your records sparkling clean, plus soft stylus brush to remove dust. Cat C-7092

~~\$3.50~~ ~~\$4.50~~

HOOK A BARGAIN!

Miyama Hook Probe Syringe action probe for easy connection to light corners. Knurled grip screw for instant lead attachment. RED W-4589 \$2.50 EA BLACK W-4590

FLASHING LEDS - WHY PAY MORE?

How do we do it? Quality flashing LEDS, normally 45c now an amazing 15c each! They won't last at this price! Cat Z-4000

15c ea

SAVE \$4.50

QUALITY AUTO RANGING DIGITAL MULTIMETER

Portable, 3 1/2 digit, compact sized tester ideally suited for field, lab, shop bench and home application. Features include Overload Protection; Battery Operated (2 AA sized 1.5V) Cat Q-1446

~~\$48.50~~
GREAT VALUE!
\$45



\$2.25 PC RESIST PEN

Essential for precision marking of boards prior to etching. Unique press-to-mark feature ensures adequate dye when marking the board. Cat T-5170

\$1.75

PCB MARKING KIT

Contains two colour pens for easy identification of circuits and an eraser. The pens are for direct use on PC board copper foil. Cat T-5175

\$4.25

YOU REAP THE BENEFIT!

RELAY SPECIALS

- Ultra miniature PC mounting 320 ohm 5V coil. SPDT. Ideal for TTL interface. Cat S-7105 ~~\$2.85~~ \$2.95
- Ultra miniature PC mounting 320 ohm 12V coil. SPDT contacts with 0.5A rating. Cat S-7112 ~~\$3.85~~ \$2.95
- Robust heavy duty PC mounting. 200 ohm 12V coil. DPDT contacts with massive 5A rating. Cat S-7130 ~~\$7.95~~ \$5.50
- Economy heavy duty PC mounting. 160 ohm 9-12V coil. DPDT with huge 10A rating. Cat S-7140 \$3.50

MAJOR RESELLERS

Atherton QLD: Jue Sue's Radio Service, 55 Main St. 91 1208 ● Bendigo VIC: Sumner Electronics, 7 Edward St. 43 1977 ● Ballina NSW: A. Cummings & Co. 91-93 River St. 86 2285 ● Cairns QLD: Thompson Instrument Services, 79-81 McLeod St. 51 2404 ● Coffs Harbour NSW: Coffs Harbour Electronics, 3 Coffs Plaza, Park Ave. 52 5684 ● Darwin NT: Kent Electronics, 42 Stuart Hwy. 81 4749 ● Darwin NT: Ventronics, 24-26 Kavanagh St. ● Deniliquin NSW: Deni Electronics, 220 Cressy St. 81 3672 ● East Maitland NSW: East Maitland Electronics, cnr Laws & High Sts. 33 7327 ● Echuca VIC: Webster Electronics, 220 Packenham St. ● Geraldton WA: KB Electronics & Manne, 361 Main Terrace. 21 2176 ● Gladstone QLD: Purely Electronics, Shop 2, cnr Herbert & Auckland Sts. 72 4321 ● Gosford NSW: Tomorrow's Electronics & Hi-Fi, 68 William St. 24 7246 ● Kingston TAS: Kingston Electronics, Channel Court. 29 6802 ● Launceston TAS: Advanced Electronics, 5a The Quadrant. 31 7075 ● Lismore NSW: Decro Electric 3a/6-18 Camington St. ● Mackay QLD: Stevens Electronics, 42 Victoria St. 51 1723 ● Maryborough QLD: Keller Electronics, 218 Adelaide St. 21 4559 ● Mt. Gambier SA: Hutcheson's Communications, 5 Elizabeth St. 25 6404 ● Mildura VIC: McWilliam Electronics, 40 Lemon Ave. 23 6410 ● Morwell VIC: Morwell Electronics, 128 George St. 34 6133 ● Nambour QLD: Nambour Electronics, Shop 4, Lowan House, Ann St. 41 1804 ● Orange NSW: M&W Electronics, 173 Sumner St. 62 6491 ● Penrith NSW: Acom Electronics, Shop 12, 541 High St. 36 1466 ● Port Macquarie NSW: Hall Of Electronics, 113 Horton St. 83 7440 ● Rockhampton QLD: Purely Electronics, 15 East St. 21 058 ● Shepparton VIC: G.V. Electronics Centre, 189b Corio St. 21 8866 ● Southport QLD: Amateurs Paradise, 121 Nerang St. 32 644 ● Toowoomba QLD: Hunt's Electronics 18 Nell St. 32 9677 ● Townsville QLD: Tropical TV, 49 Fulham Rd, Vincent Village. 79 1421 ● Wagga NSW: Wagga Wholesale Electronics, 82 Forsyth St. ● Wodonga VIC: A&M Electronics, 78a High St. 24 4588 ● Whyalla SA: Mellor Enterprises, Shop 2, Forsythe St. 45 4764 ● Warrambool VIC: Western Districts Recordings, 192 Fairy St. 62 6667

MAIL ORDER CENTRE: PO Box 321 North Ryde, NSW 2113
Phone: (02) 888 3200

STORES THROUGHOUT AUSTRALIA

POST & PACKING CHARGES

ORDER VALUE	CHARGE
\$5.00-\$9.99	\$1.40
\$10.00-\$24.99	\$2.40
\$25.00-\$49.99	\$3.50
\$50.00-\$99.00	\$4.60
\$100 or more	\$6.20

Charges are for goods sent by post in Australia only - not airmail, overseas or road freight.

SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone through your order and Bankcard details - it's so simple! (02) 888 3200

STORE HOURS


All Dick Smith stores are open from 9am to 5.30pm (Sat. 9am to 12 noon)* except Queensland stores which open and close half hour earlier. Many stores are open for late night trading. Phone your nearest store for details.
*North Ryde not open Saturday.



Prices correct and stock available at press time.

Philips demonstrate Compact Disc

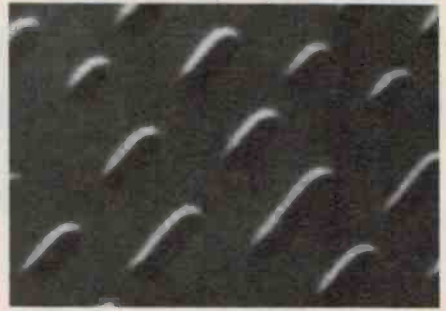With the digital bits still ringing in our ears from the Sony Compact Disc Player demonstration, we heard the Philips system reveal the wonders of digital recording. The demonstration was not without a few minor technical problems but they didn't detract from the clarity and brilliance of the live performance, reproduced through the medium of the digital disc.



The compact disc pit structure, magnified 12 500 times.



The disc is 'read' by focussing the laser light through the underside of the disc and optically reading the reflections.

The standard compact disc developed by Sony Corp. and Philips, and licensed along with the player technology to other makers, is only 12 cm in diameter, allowing for much smaller players than at present. The plastic-sheathed discs never wear out or scratch.

The compact Sony-Philips format won out in industry competition over alternative designs developed by West Germany's AEG-Telefunken and Victor Co. of Japan. A total of 34 companies now hold licences to manufacture and market Compact Disc players and nine record companies in Japan, Korea and Europe have licences for record production.

US companies are conspicuously absent, waiting until the market is established before they follow suit.

Initially the Compact Disc players will cost \$660 to \$1000, but experts expect prices to plunge within a year or two to less than \$200 as makers reach mass-production levels. More important, it appears that digitally recorded discs, the program material essential to the sale of the players, will be available in greater quantity and at lower prices than originally expected. PolyGram of West Germany, Philips' associate company, plans to offer about 600 long-playing albums by the end of 1983. And Japanese-based

software ventures such as CBS/Sony, Toshiba-EMI and Pioneer will be marketing several hundred titles during the coming year. The discs will be priced at up to \$18 and play for up to 60 minutes.

The Compact Disc digital audio system had to happen, but the fact that it happened now is because Philips had all the right technologies and resources. In the late 1960s Philips made strategic, long-term investments in three optical electronics systems, the Compact Disc, Digital Optical Recording and Video Long Play or Laservision. Philips also had at its disposal technologies in the areas of glass, studio recording, mastering, semiconductors, computers, telecommunications and record manufacture.

Few experts doubt the Compact Disc player's potential for success, but no one expects them to replace conventional turntables entirely. People will still want to play their conventional analogue records. But the introduction of the Compact Disc player may inspire consumers to upgrade their stereo systems and it foreshadows a time when music will be stored in computers, available by phone lines for home listening.

AWA-Thorn's new VCR

AWA-Thorn's new 'top of the range' VHS video cassette recorder, the ATV-20 is now on sale in Australia, superseding the ATV-5.

The new compact design incorporates the five motor drive system, having a separate motor for each function. It has an infra-red, 14-function remote control which can be stored out of sight in the unit when not in use. New features are a time elapsed indicator, Dolby noise reduction system and a picture control to sharpen or soften the picture you view. The timer section now has a battery back-up which retains all selected programmes and time settings for up to one hour in the event of a power failure or accidental power disconnection.

It is expected to retail at \$1199. More information can be obtained from AWA-Thorn, 348 Victoria Rd, Rydalmere NSW 2116. (02) 638-9022.

AWA-Thorn's new ATV-20



National's 'super video'

National's 'super video', their new NV777A VTR will replace the NV-7200A, released 12 months ago.

Included in the features of the NV777A are a three-head system for super still/super still-advance and super fine slow playback, noiseless reverse play and one touch timer recording. National claim that the one touch timer recording is unique and has recently been introduced on their new model NV300A.

The NV777A also has insert editing, tape remaining indicator, double-safety tape mechanism, three-day memory back-up system, one-button channel tuning, 16 channel capacity, 31 mode infra-red remote control and all the other functions on the NV7200A (excluding double speed playback).

Like the other products in National's range of home video equipment, the NV777A comes with a three year conditional warranty and home demonstration and installation policy.

National Panasonic is located at 95-99 Epping Rd, Nth Ryde NSW 2113. (02)887-5333.



Yamaha K-500 cassette deck

Yamaha's new cassette deck, the K-500, has a pure Sendust head and two-motor transport system.

The Sendust head coil windings have half the number of turns used in conventional designs and Yamaha claim that this results in improved linearity, wider dynamic range and improved channel separation. In the two-motor design the takeup reel is driven by an independent motor for both fast-wind and record/play operations. Yamaha say that this system completely relieves the capstan motor of excess load, resulting in a wow and flutter of 0.05%.

The signal-to-noise ratio, using Cr₂ tape, is better than 60 dB with Dolby off, 68 dB with Dolby B on and better than 76 dB with Dolby C on. The frequency response, with Cr₂ tape, is 40 Hz to 18 kHz and with metal tape it is 40 Hz to 20 kHz. Total distortion is less than 1%.

If you would like to find out more about the Yamaha range of hi-fi equipment you can do so at **Rose Music, 17-33 Market St, South Melbourne Vic. 3205** or **18 Kent Rd, Belmore NSW 2192. (02)750-8999.**

New video package from Atari

Atari has started shipping its new video package, the 5200 Home Entertainment System. Retailing at around US\$270, the 5200 is in the high end of the home systems market and nearly twice the price of its predecessor, Atari's 2600 Video Computer System.

A feature of the new system is the graphics of the ten game cartridges which make some of the 5200 games closely resemble the arcade versions, an improvement over the corresponding cartridge used on the 2600, observers said.

The 5200 is similar in appearance to Atari's 400 home computer but it doesn't have a keyboard. In 1983 Atari plans to bring out an adapter that will allow cartridges for the 2600 to be played on the 5200.

At the presentation for the 5200 system and the new 'E.T.' game cartridge, the president of Atari's Consumer Electronics division admitted to being a little concerned about competitors. Mattel's M-Network game cartridges are being marketed and have been designed to be used in Atari's 2600 VCS. Colevision, the newest entry in the home systems market, is challenging Atari and Mattel with the quality of its graphics.

The Remx 'Stereo XPander'

This little gadget is an 'interface' unit that goes between your magnetic cartridge and your preamp input. It is claimed to enhance your stereo imaging performance of your record playing system and give greater sonic detail.

In the limited blurb provided with the unit submitted for test, the makers say: "The optimum loading establishes an ideal resistive termination for maximum signal transfer and good damping to maintain control under dynamic signal conditions."

Remx say that the input resistance of the unit is matched to any magnetic cartridge and the output resistance is matched to any phono input. Clearly, the unit is designed to provide optimum, or as near optimum as can be achieved, matching for the cartridge and to reduce 'cartridge impedance interaction'.

Until quite recent times, many preamps in hi-fi amplifiers returned the feedback to the input stage, right at the input. This is quite valid, providing the load on the input has constant characteristics under signal conditions. If not, the impedance of the driving source interacts with the feedback network, changing the dynamic response of the



amplifier — cartridge impedance interaction. The most telling effects are on frequency response during playing and stereo image.

While modern design techniques have, to greater and lesser degrees, obviated this problem, there are still many amplifiers around, and being sold, that will exhibit the fault.

Interposing an 'interface' unit between the cartridge and the preamp input can be an effective cure. This is the purpose of the Remx Stereo XPander.

Remx claim the unit has very high linearity, THD less than 0.001%, crosstalk better than 80 dB, a bandwidth from 20 kHz to 100 kHz, maximum output of 12 mV and gain better than 3 dB.

It is powered by a small plugpack of any convenient voltage between 6 and 12 Vdc. When the unit is off an internal relay bypasses the unit. An LED on one end indicates when the unit is on. Four gold-plated RCA sockets provide input and output connection.

We had the chance to evaluate the unit here at ETI, both on the bench and in a stereo system. Well, what did we find?


At the time we had the unit, we couldn't find a preamp amongst staff that suffered from cartridge impedance interaction, so its effect on that problem is a little hard to report on. It would have to be tried on a 'suck it and see' basis. However, we were able to measure its characteristics.

As the chart shows, the frequency response is almost 'ruler flat'. Input

noise was measured at -62 dB in a 20 Hz to 20 kHz, flat, bandwidth with respect to 10 mV input and the input terminated with a 330 ohm resistance. Distortion (THD) was much higher than anticipated, second harmonic predominating. This measured 0.22% at 100 Hz, 1 kHz and 10 kHz with a 10 mV input. Gain was measured at 5 dB and maximum output before distortion became unacceptable, 1 V RMS. Clipping was non-symmetrical, and 'soft'.

Overall, performance could only be regarded as mediocre, but if cartridge impedance interaction in your system is a problem, you might like to try the Remx Xpander as a solution if you don't want to go to the expense of buying a new preamp or integrated receiver/amplifier.

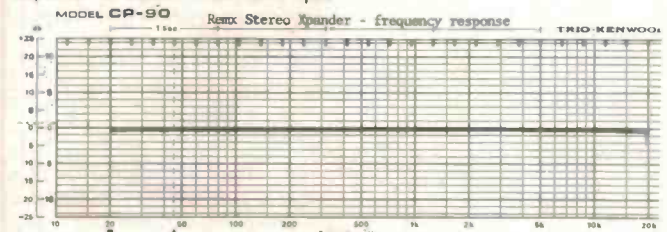The unit should be available in selected hi-fi stores in January. For further information, contact Remx at P.O. Box 417, Woollahra NSW 2025.



One unique instrument deserves another



PE75.(Left) The perfect choice for the lead vocalist. Superb projection and low end power. High sensitivity for rich warm sound at lower levels. Superb internal shockmounting, silent on/off switch, ultra tight cardioid pattern.

PE47.(Below) Tone control in the palm of your hand. Frequency tailoring for vocal and instrumental use. Bass and treble controls. Mellow sibilant vocals or harsh brass. Excellent for unexpected stage problems. **Uses:** All vocals, piano, drums, guitar, cymbals.



PE65.(Left) Handles the highest levels with extreme accuracy. Wide response, tight pattern. Internal shockmount. Silent on/off switch. **Primary use:** Toms, bass drum, snare, cymbals, guitar, piano. **Secondary uses:** Brass, acoustic bass, vocals.

PE85.(Right) Superb vocal system mike. All the qualities of the PE75 plus a more rugged grill and wind filter. Includes impedance matching transformer and Shock Stopper™ swivel mount to eliminate stage vibration. **Uses:** All vocalists.



PE35.(Left) Presence and clarity helps vocals cut through. Bass lift and top end lift give the vocalist more projection and top end power. Internal filter and shock mount for handling and pop rejection. **Uses:** Hard working vocalists.

PE9.(Right) Low cost, high quality. Cardioid pattern. Locking on/off switch. **Primary uses:** Brass, flute, reeds, harmonica. **Secondary uses:** Guitar, vocals (with windshield).



PE45.(Above) Crisp top end to cut through. Wide dynamic range and tight cardioid pattern. Internal shockmount. Brings instruments up in the mix. **Primary uses:** Guitar amp, bass drum, snare, electric bass, electric piano. **Secondary uses:** Cymbals, brass, piano, vocals.

PE15.(Right) Best low cost vocals mike available. Smooth wide range sound, cardioid pattern. On/off switch, pop filter.



SHURE

AUDIO ENGINEERS P/L
342 Kent Street
Sydney NSW 2000
(02)29 6731

NOMIS ELECTRONICS
689 South Road
BLACK FOREST SA 5035
(08)293 4896

AUDIO ENGINEERS (Qld)
47 Castlemaine Street
MILTON QLD 4064
(07)369 9670

AUDIO ENGINEERS (Vic)
2A Hill Street
THORNBURY Vic 3071
(03)44 3295

MARKETEC P/L
18 King William Street
Stn Fremantle WA 6162
(09) 335 8275



Please send me information on the following Shure mikes: PE9
 PE65 PE45 PE47 PE15 PE35 PE75
 PE85. Name:
Address:

Marantz SC6 preamplifier and SM6 power amplifier

This review contains the first set of published data relating to the new IEC test method for evaluating high frequency distortion.

The results are quite outstanding. The SC6 and SM6 are an exceptionally good combination, says Louis, with a performance bordering on perfection.

Louis Challis

THIS REVIEW HAS been written twice because of the need to provide technical data and adequate documentation of what is fast becoming one of the hottest topics in the professional audio field in Australia today. The reasons for this extend beyond Australia to the august International Electro-Technical Commission and to a new draft test method for evaluating odd order and even order high frequency distortion. This draft test method will be described by us as the 'IEC High Frequency Total Difference Frequency Distortion'. The technique was developed in Australia and presented by the Australian Committee to the IEC as a preferred alternative to the Finnish transient intermodulation distortion method of rating and analysis.

Obviously there are good reasons for moving for a suitable alternative to the Finnish proposed method of analysis, one of them being the complexity and cost of that method. The Australian Committee are firmly resolved in their support of the Australian proposal which I also believe is the best method currently available for the evaluation of dynamic distortion analysis, not only for amplifiers, but more significantly for tape recorders, communication circuits and all associated situations.

We have conducted a series of evaluations of the Australian method and over the last few months we have also been evaluating the Japanese method, as embodied by the Italian version of the circuit published in 'Wireless World'.

There is a reasonably good correlation between the results provided by the two methods, although the frequencies at which the Japanese technique is used are only

MARANTZ SC6 PREAMPLIFIER AND SM6 POWER AMPLIFIER

SC6	
<i>Dimensions:</i>	416 mm wide x 146 mm high x 244 mm deep
<i>Weight:</i>	6.5 kg
<i>Price:</i>	\$489 recommended retail
SM6	
<i>Dimensions:</i>	416 mm wide x 146 mm high x 332 mm deep
<i>Weight:</i>	14.5 kg
<i>Price:</i>	\$689 recommended retail
<i>Manufactured:</i>	In Japan for Marantz USA
<i>Distributor:</i>	Marantz (Aust) Pty Ltd, 19 Chard Rd, Brookvale NSW 2100. (02)939-1900.

suitable for amplifiers and not for other electro-acoustic systems. For this reason we believe the Australian draft proposal which operates at frequencies of 10 kHz and 14.97 kHz mixed on a one to one basis is the correct choice. Commercial versions of the Australian system are likely to operate at slightly lower frequencies in order to render them even more suitable for the wide range of possible applications.

This review contains the first set of published data relating to this test method and presents results that are quite outstanding.


The SC6 and SM6 stereo console preamplifier and stereo power amplifier are two of the Marantz 'Esotec' range which we had seen in the trade literature but apart from that had not previously seen or heard them. Their major feature, and in fact the main talking point of this review, is that the

stereo power amplifier output stages offer the option of both a true Class A operation and the more conventional Class AB operation which the units describe as Class B operation. This is done to satisfy the 'Electronic Purists' in our consumer society who firmly believe that only Class A operation can achieve perfection with the total removal of crossover distortion and the lowest possible level of harmonic distortion. Like all the other units in the Marantz Esotec range, the SC6 and SM6 are expensive and have an appearance which I consider to be a little too conservative, especially when compared with the latest generation of consumer electronics from America, Japan and Europe.

SC6 features

The SC6 stereo control console features a golden hued brushed satin aluminium fascia with three main groupings of controls. On the left hand side are the two separate treble controls and two separate base controls. On the right hand side of the console are four rotary controls. The first control is for phono selection which provides a choice of a moving coil cartridge or 27k, 47k, and 100k input impedances for moving magnet cartridges and a second moving magnet cartridge input for phono 2. The second control is the volume control, the third control is the mode switch for stereo, reverse and left plus right channels combined, whilst the fourth control is a balance control with centre indent.

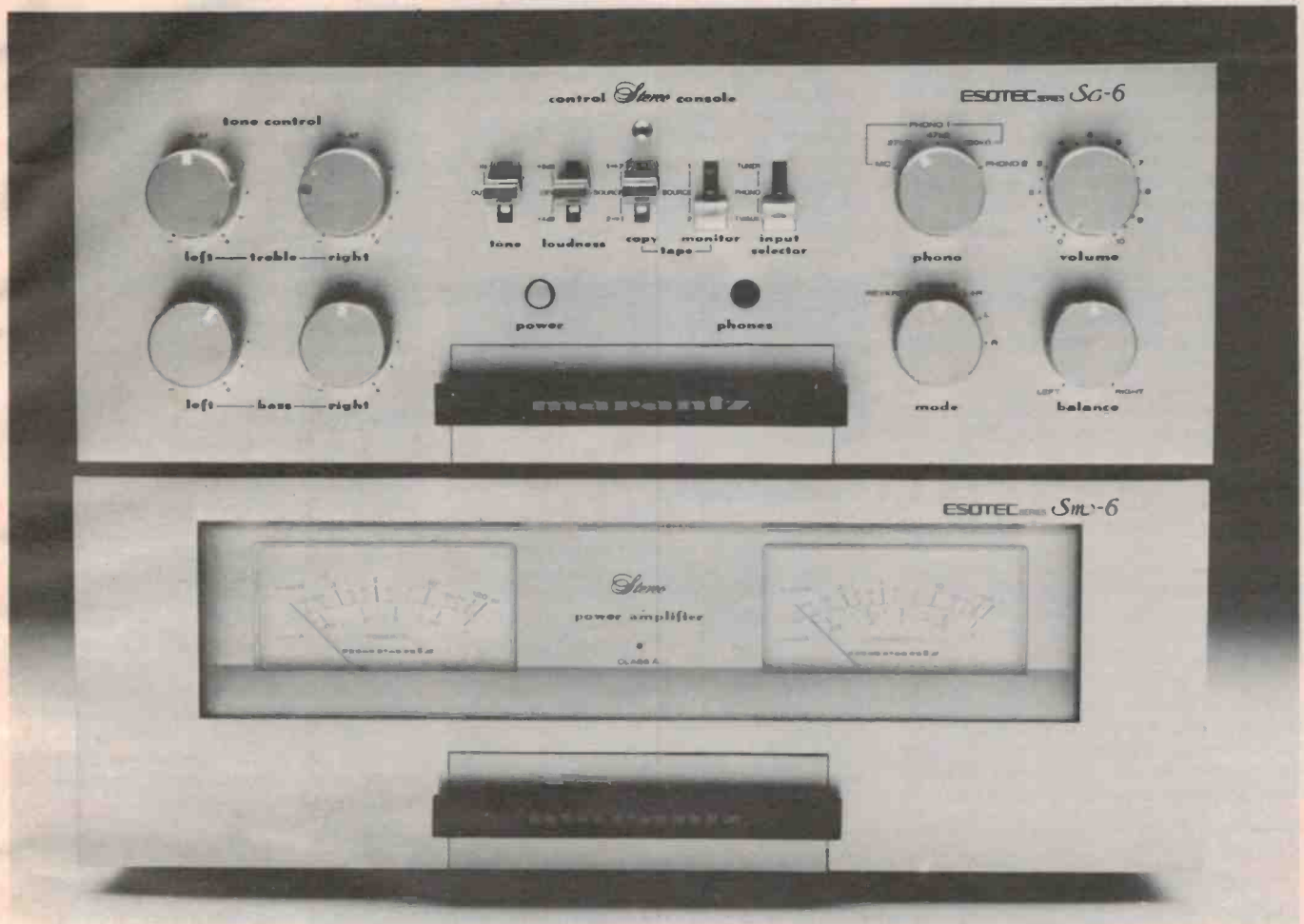In the top centre of the deck are five large toggle switches which, from left to right, are a tone control in or defeat function and next to this is a loudness control setting with centre off and +8 dB at the top and +4 dB



Conservatism. Some brilliant 'avante garde' technology is hidden beneath the conservative shells of the SC6 and SM6.

at the bottom. Adjacent to this switch are two tape control switches for copying and monitoring from or into two separate tape recorders. The last control on the right is the input selector for phono, tuner or TV auxiliary. Below these switches are the power on/off switch and a headphone socket. Behind the bottom fascia panel are two push buttons for selecting output 1 or output 2, a 'high out' filter and a subsonic equaliser filter. This subsonic equaliser filter is intended to reduce the impact of rumble generated either by the turntable or from warped records and it is poorly described in the technical handbook.

The back of the control console features a series of gold plated RCA type coaxial sockets with a pair of shorting plugs in the phono 1 input. These plugs are supplemented by a strict labelled warning that when these terminals are not being used, the shorting plugs should be left in position. This unit is provided with a mains voltage selector.

The switched and unswitched sockets on the back panel, which are normally provided for American and Japanese-type markets, have been deliberately disconnected to meet Australian design requirements. The chassis

and the cabinet are strongly fabricated from heavy weight steel. The unit is well ventilated to allow for its location in semi-enclosed situations, such as in furniture, where this type of unit could be expected to be used.

SM6 features

The SM6 power amplifier presents a somewhat simpler, yet considerably more attractive appearance than the SC6 stereo control console. The front panel features a large glass display window panel behind which are located the two separate power output meters separately calibrated for 'Class A' and 'Class B' operation. The Class B metering range covers more than a 50 dB dynamic range with calibrations from less than 10 mW at one end to greater than 120 W at the other. The Class A meter covers a range from 10 mW to 30 W. When the Class A operation is selected, a red light is activated and if one was not aware of the pull out panel on the front lower section of the fascia one would not even be aware of the additional controls provided. These controls are a power on/off switch and the Class A selection button on the left. And on the right is a switch for selecting speaker system

1 or 2, or 1 and 2 by the use of two push buttons.

The rear of the amplifier features two independent gain controls for the left and right channels and two sets of inputs labelled 'Direct' and 'Subsonic'. The Direct input allows dc coupling to the input stage of the amplifier while the subsonic input provides very low frequency roll-off. The speaker connections are by means of four sets of black and white universal terminals which are well insulated, large and practical. The switched and unswitched parallel pin power outlets on this unit have been internally disconnected to meet the Australian design rules. At the bottom right hand corner is a mains fuse.

The unit is also fitted with a mains voltage selector on the rear panel and arrived already connected for 240 V. The cabinet is very strongly made with hammer tone finished steel featuring a very large expanse of perforated linear slots covering more than 80% of the top of the cabinet and more than 50% of each side of the cabinet. The bottom of the chassis is also extensively perforated and the amplifier features a much greater open area for ventilation than the majority of amplifiers we have reviewed.


Inside the SM6

The output stage of the amplifier features the heat pipe thermal dissipation system, developed by NASA in the mid 70's, which was discussed in the review of the Sony TA-F80 amplifier (ETI, May 1981). This radiator device is claimed to be many hundreds of times more effective than conventional heat sinks and is supplemented by a speaker protection circuit which is intended to switch off the output stage in the presence of either excessive current or overload conditions which might otherwise damage or destroy the output stage. This is particularly important when the amplifier is operating in the Class A mode which generates the maximum possible thermal energy. This mode calls for the maximum amount of heat dissipation and obviously a very fast response time, if the unit is to protect the output stage. The power amplifier features an unusual layout with the heat pipe's thermal output stage at the extreme right hand of the rear of the amplifier. The heat pipe is connected through the centre of an array of eight output transistors. These extend beyond the transistor block right across the rear of the amplifier with the finned heat radiator providing the effective heat dissipation for both Class A and Class B operation.

The front of the amplifier features a large encapsulated mains transformer on the left hand side, two large electrolytic capacitors in the middle, the control circuitry and protection circuitry on the right hand side at the front. The main protection circuits and fuses

are also located on a terminal block at the top of the main control amplifier circuit.

At the extreme front of the chassis are the power output meters and their associated electronic metering amplifiers. The chassis construction is unusually strong and although much of the wiring is conventional twisted pairs, it is neatly laid out and the unit is obviously well designed. Although the amplifier looks relatively simple in appearance, it is nonetheless a complex and unusual piece of electronics.

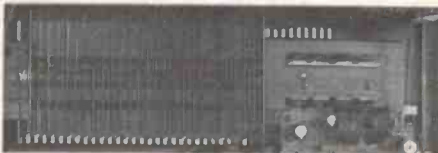

Heatsink. Heat pipe in the SM6.

Testing, testing

The evaluation of the Marantz control console and power output amplifier stages were initially carried out as separate tests and then the results combined to provide an overall picture. When the control console and power amplifier are interconnected the frequency response is excellent, extending from less than 10 Hz to beyond 100 kHz with both the tone controls centred, as well as with the tone controls defeated. Over the frequency region 10 Hz to 20 kHz the response is basically ruler flat, particularly when the

subsonic and associated high pass filters are de-activated. The sensitivity of the auxiliary tuner and tape inputs are, respectively, 12 mV and 12.5 mV for a one watt output into eight ohms.

The moving coil cartridge input required only 21 uV and the moving magnet cartridge input required 210 uV. The overload level for the moving coil cartridge input is 22 mV while the overload point for the moving magnet cartridge is 270 mV, both providing a particularly healthy safety margin. The moving coil cartridge provides input impedances of 75 ohms while the measured moving magnet cartridge impedances are 27k, 47k and 100k which are exactly as specified by the manufacturer.

The harmonic distortion of the preamplifier operating alone is less than 0.005% at its maximum output and under most normal operating conditions is less than 0.002%. The main power amplifier is essentially flat from 0 Hz to beyond 100 kHz in the direct mode, and is typically 2 Hz to beyond 100 kHz in the subsonic mode.


I was intrigued that the designers should want to provide both Class A and AB operation in the one unit as very few people could reasonably be expected to desire such a feature. In the Class AB mode the power output, although specified as 120 watts, actually has a maximum value at clipping of 182 watts. This output is 1.8 dB re the 120 watt level and is more than adequate for the general applications in which the amplifier could be expected to be used.

IEC HIGH FREQUENCY TOTAL DIFFERENCE FREQUENCY DISTORTION


MARANTZ ESOTEC SM-6 SIN.14E060014

10.00 kHz & 14.97 kHz 1:1 INPUT


TOTAL EVEN & ODD ORDER DISTORTION

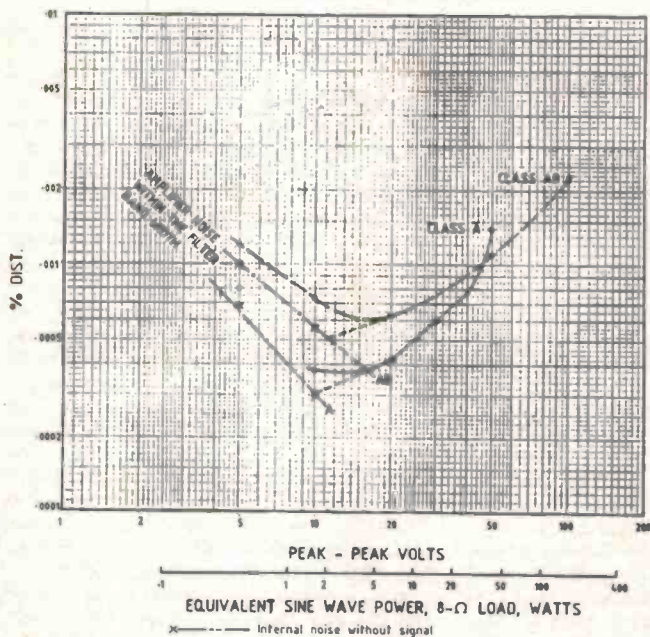

LOUIS A. CHALLIS
& Associates Pty Ltd

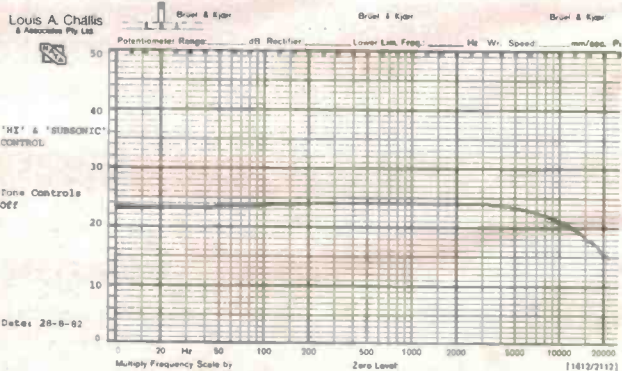

LOUIS A. CHALLIS
& Associates Pty Ltd

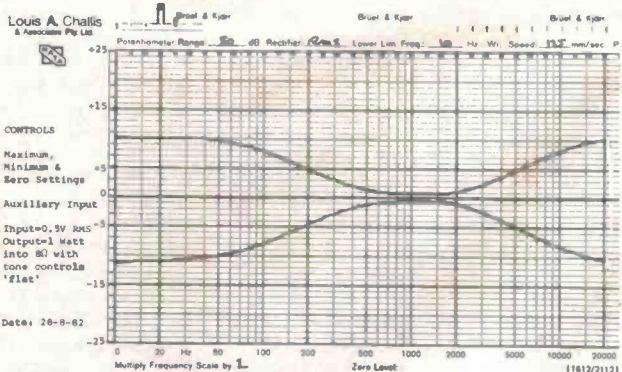

Obviously the parameters that I was most interested in evaluating are the levels of the individual harmonic components and the total harmonic distortion. These were not what we thought they would be for either mode of operation. At 120 W output (in the Class AB mode of operation) the total harmonic distortion with a 100 Hz signal is 0.0047%, at 1 kHz it is 0.0014% and at 6.3 kHz it is 0.0017%. These are exceptionally good performances and there are only a few amplifiers around that are able to better these figures. At 30 W output the distortion in both the Class A and Class AB modes is not greatly different. At 100 Hz they are respectively 0.01% and 0.009%. At 1 kHz the distortion is 0.002% and 0.0009% and at 6.3 kHz it is 0.0013% and 0.0018%. Obviously with differences that are so small the reviewer and the designer are only really playing a numbers game.

Subjectively, the important test is of course, neither determined at 30 W nor at 120 W. What happens at the 1 W level is probably more important for most people listening under reasonable sound levels and classical music is usually listened to at this level. At 1 W output with a 100 Hz signal there is not a significant difference between the A and AB modes which are both 0.006% (being controlled by flux leakage), but at 1 kHz there is a significant numerical difference with 0.0009% and 0.0018%. At 6.3 kHz the levels are 0.0007% and 0.0024%. These are exceptionally low distortions, with the best being only slightly higher than a few

parts per million. A significant portion of the lowest distortion measured is actually being produced in our test oscillator rather than in the power amplifier (0.0001% to 0.00015%). The differences are measurable but anybody who claims that he can hear the difference is "a better man than I am".

The IEC high frequency total difference frequency distortion parameters also proved to be exceptionally good and in fact, the lowest we have yet seen from any amplifier tested. It is interesting to note that in the Class A mode the distortion levels are less than those produced in the Class AB mode at power levels up to approximately 25 W output. Class A distortion was greater than that of Class AB at high levels. Equally significant, the amplifier background noise measured within the filter band width is significantly lower in the Class A mode than it is in the Class AB mode. This characteristic further justifies some of the other claims presented for the use of the Class A option.

The slew rate test of the amplifier (utilizing the Japanese method) showed it to have impeccable performance and the transient intermodulation distortion measured by the archaic SMPTE method proved to be exceptionally low and much less than 0.01%.


The hum levels proved to be primarily 50 Hz leakage hum pickup from the moving coil cartridge input and 50 Hz and 150 Hz from the moving magnet cartridge input. These were measured relative to the 1 W level and still proved to be extremely low, although admittedly, not the lowest we have seen. The

subsonic filter not only cut out the low frequency components but also inexplicably rolled over at the top end by 3 dB and 10 kHz and 9 dB at 20 kHz. The tone controls provided useful and effective adjustment amounting to ± 10 dB at 50 Hz and ± 10 dB at 20 kHz. The loudness control is slightly better than most, providing two contour level slopes to cater for low and moderate listening levels. All of the manufacturer's claims for the signal-to-noise ratio, distortion, crosstalk and sensitivity were equalled or bettered in every single case. The most notable performance being in terms of the harmonic distortion generated by the amplifier which is as close to perfection as one could reasonably expect (more importantly, it is right on the limits of our measurement system).




Subjectively

To evaluate the SC6 and SM6 I took them home and connected them up to three different sets of speakers, a record player and a cassette player. The records that I decided to evaluate included two new ones, one of which is undoubtedly one of the most unusual conventional records ever made and released for sale to the public.

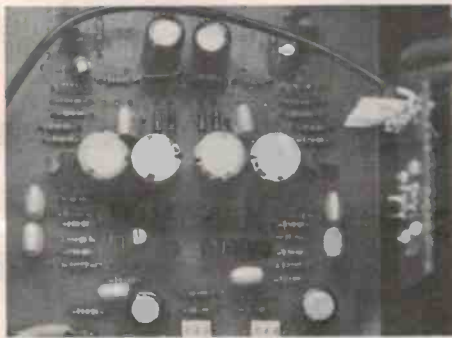This record, called the 'Sheffield Track Record' (lab 20) is produced by Sheffield Laboratories in Los Angeles by the Direct Recording Method. It was released at the CES in America earlier this year and became available to dealers in the USA and Australia



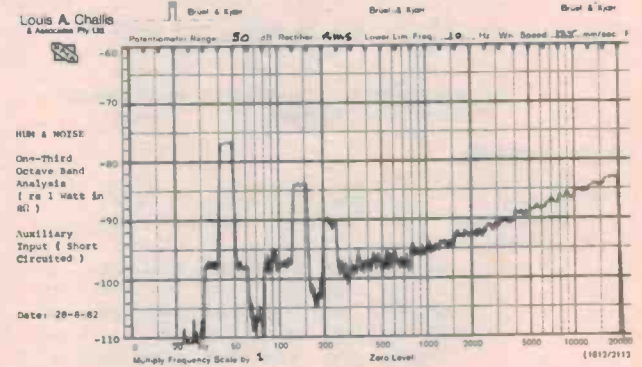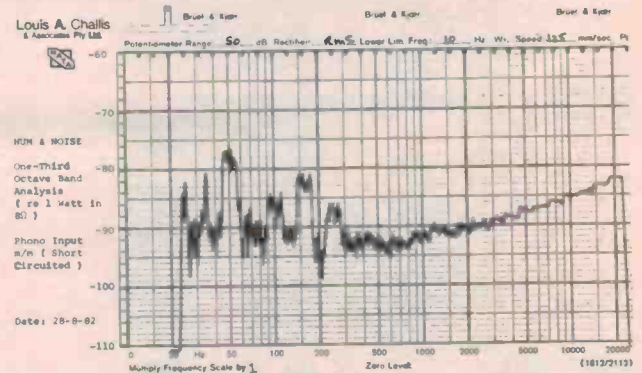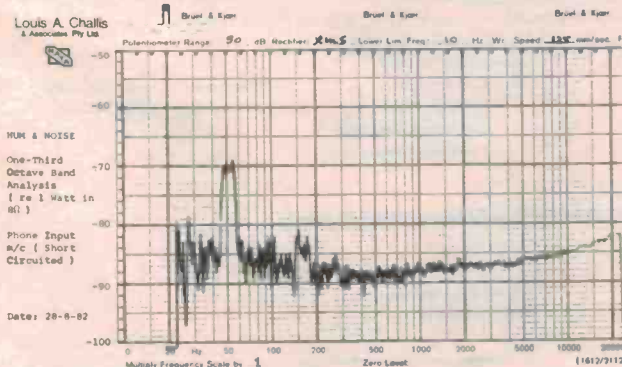MC preamp. Constructors of the ETI-473 MC headamp will recognise the topology of the SC6's moving coil preamp. Their circuits are near equivalent.



SOUND REVIEW

at the beginning of September. The record is unusual in that the recording engineers have cut the tracks on the Neumann lathe with the maximum possible groove spacing so that the full energy of the low frequencies and base transients was recorded without any compression. Because of this, the total playing time of the record is somewhat shorter than usual, being only about 16 minutes. They claim to have done everything possible to make the record perfect. This particular record contains more peak transient energy, higher resolution and more dynamic range than has previously been recorded by any other analogue record. This probably makes it one of the best test records ever produced for evaluating amplifiers, loud speakers and, in particular, record player cartridges.

The amplifier is capable of handling continuous peaks of up to 180 W output into the speakers with normal programme levels averaging between 5 and 20 W. I tried to play this record in the Class A mode and found

that the power output of the amplifier in this mode was just not up to the task. So then I played one of the latest original master recordings from Mobile Fidelity (George Solti conducting the Chicago Symphony Orchestra and Chorus on Mobile Fidelity Sound Labs records MFSL2.516.). This is an exceptional record and better suited to Class A operation.

I was unable to detect any trace of difference between the amplifier when operating in either the Class A or the Class AB modes. This, of course, is not the amplifier's fault for when you have distortion components that range between 2 parts per million and 20 parts per million it would take a better set of ears than mine (or those of anybody else whom I brought in to listen) to detect the difference.

The Marantz SC6 stereo control console and SM6 stereo power amplifier are an exceptionally good combination. The performance that they are able to produce borders on perfection. The amplifier offers

both Class A and Class AB modes of operation with distortion products that are just about at the extreme limit of our measurement ability. The performance is so good that it appears to me that the inclusion of the Class A mode is not strictly warranted. However, for somebody who wants perfection this control console and power amplifier comes near to the best level that one could hope to achieve. The only improvements I could commend to Marantz would be to fix the subsonic filter response at the top end and to improve the design of the front panel of the SC6 to make it a little more 'avant garde' and a little less conservative.

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.

MEASURED PERFORMANCE OF: MARANTZ MODEL SM-6 POWER AMPLIFIER		SERIAL NUMBER:	
FREQUENCY RESPONSE:			
Tone Controls Defeated			
(-3dB re 1 watt, 0.5V Input to Aux.)	Left	< 1 Hz to >100 kHz	
	Right	< 40 Hz to >100 kHz	
Tone Controls Centred			
	Left	10 Hz to 100 kHz	
	Right	10 Hz to 100 kHz	
SENSITIVITY: (for 1 Watt in 8)			
(control-console connected to amplifier)			
	Left	Right	
AUX	12.5 mV	12.0 mV	
TUNER	12.5 mV	12.0 mV	
TAPE	12.5 mV	12.0 mV	
PHONO M/M	210 μV	210 μV	
PHONO M/C	21 μV	21 μV	
OVERLOAD M/M	270 mV	280 mV	
OVERLOAD M/C	22 mV	23 mV	
INPUT IMPEDANCE:			
	Left	Right	
AUX	40 kohm	40 kohm	
TUNER	40 kohm	40 kohm	
TAPE	40 kohm	40 kohm	
PHONO M/M	27k, 47k, 100k,	27k, 47k, 100kohm,	
PHONO M/C	75ohm	75ohm	
HARMONIC DISTORTION:			
(A) (At rated power of 30 Watts (A) into 8 = 15.5 Volts)	100Hz	1kHz	6.3kHz
	A AB	A AB	A AB
2nd	-88.0 -87.7	-107.9 -104.1	-103.4 -96.5
3rd	-80.9 -92.2	-94.2 -104.9	-99.4 -102.9
4th	-113.3 -112.6	-120.8 -113.9	-110.8 -101.6
5th	-97.6 -97.2	-111.4 -107.9	-- --
THD	0.01 0.009	0.002 0.0009	0.0013 0.0018 %
(B) (At 1 Watt into 8)	100Hz	1kHz	6.3kHz
	A AB	A AB	A AB
2nd	-96.3 -110.5	-102.3 -102.3	-102.7 -102.1
3rd	-85.2 -84.4	-108.0 -97	-- -105.9
4th	-114.9 -113.5	-- -106.4	-- -105.1
5th	-116.1 -115.1	-- --	-- --
THD	0.006 0.006	0.0009 0.0018	0.0007 0.0024 %
(C) (At Rated Power of 120 Watts (AB) into 80 = 31 Volts)	100Hz	1kHz	6.3kHz
	AB	AB	AB
2nd	-84.5	-93.5	-97.3
3rd	-82.0	-93.4	-93
4th	-101.7	-103.5	-96
5th	-98.3	-112.3	--
THD	0.01	0.0031	0.003 %
TRANSIENT INTERMODULATION DISTORTION:			
Less than 0.1 % (3.15kHz square wave and 1.5kHz sine wave mixed 4:1)			
I.E.C., High Frequency total difference Frequency Distortion	CLASS A	CLASS AB	
10 volts P.P.	.00038	.0008	
20	.00042	.00063	
30	.0006	.00076	
40	.00078	.00082	
50	.0014	.0011	
100	--	.0022	
Mode	"odd harmonics"		
NOISE & HUM LEVELS: (re 1 Watt into 8)			
	AUX	-73dB (Lin)	-79dB(A)
(with volume control set for 1 watt output with, 0.5V input (Aux) 5mV input (Phono M/M) 0.5mV input (Phono M/C)	PHONO M/M	-72dB (Lin)	-77dB(A)
	PHONO M/C	-68dB (Lin)	-75dB(A)
MAXIMUM OUTPUT POWER AT CLIPPING POINT:			
(IHF -A - 202)	=	182 Watts	
(20ms burst repeated at 500ms intervals)	therefore Dynamic Headroom	=	1.8 dB (re 120 Watts)


WE'RE YOUR RELIABLE SOURCE FOR COMPONENTS

And our prices are
most competitive!

Whenever you're looking for quality components — capacitors, switches, connectors, ICs, resistors, speakers, volume controls, and displays — we offer you your best selection, your best quality, and your lowest prices. And we keep large stocks on hand to ensure prompt delivery.

Delsound PRICE — QUALITY SERVICE

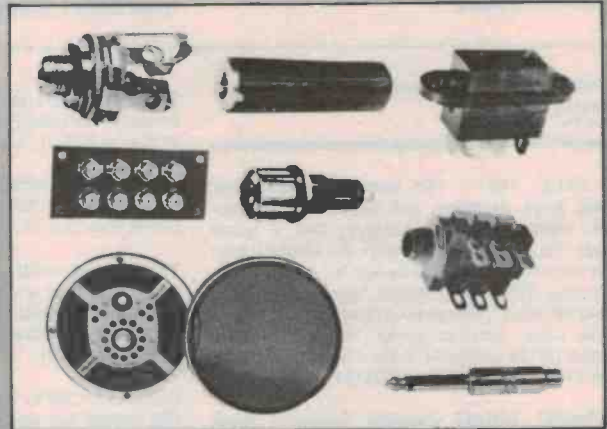1 WICKHAM TERRACE, BRISBANE 4000 — PH (07) 229 6155 TELEX AA44442
QLD. DISTRIBUTORS OF
● SWANN (MCMURDO) PRODUCTS ● SWITCHES & ELECTRONIC HARDWARE
● AUDITEC AUDIO MODULES ● CLIFF KNOBS, PLUGS & SOCKETS ● R.C.A. SEMICONDUCTORS ● NATIONAL SEMICONDUCTORS.



From P.C. Mounting Transformers to Line Conditioners FERGUSON MEETS YOUR MICROPROCESSOR NEEDS

P.C. MOUNTING

The PL161/5VA is ideal for on-board microprocessor use. Provides 200mA at 8V and 150mA at 12-0-12V. Suits standard 0.1" grid.



LOW PROFILE

The popular Ferguson range includes 3 types for microprocessor use rated at 15, 40 and 60VA. Provided with triple secondaries —
PL158/15VA dual 14V at 400mA and 9V at 500mA
PL30-9/40VA dual 15V at 500mA and 9V at 3A
PL30-9/60VA dual 15V at 500mA and 9V at 5A



CONVENTIONAL

For larger system use — PF4405 provides dual 15V at 1A and 9V at 10A
PF4354 provides dual 15V at 1A and dual 9V at 10A



CONSTANT VOLTAGE

Ideal for building in to equipment the ACV137/A172 provides 8V at 25A and 16V at 5A with 1% output variation for a 15% change in the input. One of a range of ferroresonant transformers rated from 150VA to 7.5kVA (single phase) providing constant voltages.



FERGUSON

FERGUSON TRANSFORMERS PTY LTD

331 High Street, Chatswood N.S.W. 2067. Tel: (02) 407 0261. Telex: AA25728
Branch Office: 181-183 Hawke Street, West Melbourne Vic. 3003.
Tel: (03) 328 2843 Telex: AA33510

MINI-MART

Where readers can advertise —
For Sale/Wanted/Swap/Join

● We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — please — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received; however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

● Conditions: Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:
ETI Mini-Mart,
4th Floor, 15 Boundary St,
Rushcutters Bay NSW 2011.

AUDIO

FOR SALE: 100 + 100 comprehensive amp, Auditec Aust. modules, suit band, speaker protector; Musicolour with astable; 240 V globe flasher; Proximity switch with 6" electric bell; 500 W auto transformer; 2-speed 3/8" electric drill, stand, vice, drill grinder attach., speed control, set drills 1/16" to 1/2"; bongo drums with 4 auto drums in one case; electric pump 1.4 L/s unused; Thorens TD125 turntable, Rabco 8L/SE tone arm; Shure V15 cartridge. Ronell (02)331-3547.

MORDAUNT SHORT Pageant Series II loudspeakers for sale, one pair, \$300. Enquire Tim Jewell, 18 Alexander Ave, Campbelltown SA or phone (08)336-6952.

3M WOLLENSAK, set of six high-speed cassette copiers, model 2760AV. 2 ch, 1/2 track. Very good condition, \$850. Butt, Box 503, Glen Innes NSW 2370.

SELL: GUITAR amplifier, as new, Elfa 5 W hardly used, excellent condition. \$85. Phone (02)449-9130.

HARMON KARDON integrated valve amplifier. 30 WRMS/ch using EL34s. This superb sounding amplifier has just recently been modified throughout. Extra brand new tubes, \$390. (02)46-5451.

FOR SALE: SPEAKERS, Goodmans 15 inch woofers. These speakers have only been used once. Less than one year old. Half price at \$195. (02)46-5451.

DISC CUTTING lathe: Presto with spare cutter head and styl. Also power amp limiter and Rola 66 tape recorder level meters and patch panel. \$400 ono. Phone (02)651-2214.

MISCELLANEOUS

FOR SALE: MAGAZINES. 74 EA, April 66-July 80. 63 ETI, April 71-June 82. 23 Electronics International. 32 others. 70¢ each, \$100 the lot. Phone (02)387-3097.

FOR SALE: 4 1/4 inch 240 V Muffin fans, \$7.50 ea. (02)452-3925 ah.

VALVE WANTED, 6U5 (magic eye). Equivalents are 6G5, 6H5, 6M2, 6T5. Write to Martin Smith, 21 Ashburton St, East Victoria Park WA 6101. (09)361-6764 (reverse charges).

WANTED: K901 (EDISON) delay relay (115 Vac heater). Has octal base and glass envelope similar in size to 6V6GT. D. Bruce (03)583-1638.

DUAL BEAM CRO, Leader LB0514, 10 MHz. As new, NZ\$450. Graeme Teesdale, 13 Glendale Drive, Hamilton N.Z.

TEKTRONIX 465B oscilloscope, as new, dc to 100 MHz. Dual channel, dual timebase, delayed sweep, fully calibrated. Three months warranty, manual and probe included, \$3500. Phone Dom (02)546-2463 ah.

OSCILLOSCOPE: Five inch dual-beam Cossar. Old model but excellent condition, \$100. Phone (02)387-3097.

SELL: SIEMENS M100 teleprinters, 240 Vac, internal supply, serial TTL I/O, all good order. \$250. Delivery by arrangement. W. Watkins, P.O. Box 1117, Orange NSW 2800.

TI-59 CALCULATOR and PC-100C printer for sale with all literature, charger etc. As new condition, \$350 ono. C. Daltz, 9 Dine St, Randwick NSW 2031. (02)398-6961.

TELEQUIPMENT D55A 10 MHz true dual beam oscilloscope with delay timebase, \$300. Phillips PM6503 transistor analyser (solid-state), \$100. Tesla 25 MHz single trace oscilloscope, \$200. TI58 calculator, \$60. Sharp PC1211 computer, \$100. (02)527-2873.

RADIO CONTROLLED garage door openers, one demo set \$285. Three new sets \$365 each, with warranty (new price \$485). Easily installed. (02)93-3630.

FOR SALE: Electric train setup, HO gauge, locos and rolling stock, 150 m of track. Phone Tony after 4pm, Adelaide (08)42-2037.

SELL: Lens, wide angle 'Cosmicar' 8 mm focal length. Suitable for surveillance video camera. Sell \$85. Purchased in error, paid \$130. Phone David (03)211-1934.

COMPONENTS: 2N3771 Si. npn. 30 A Vceo 40 V, 60¢ ea. RCA Si Triac 40430 400 V 6 A, 60¢ ea. Spague Electrolytics 2500 µF 75 V, \$1.00 ea. Fuse holder M205, 40¢ ea. Edge connector 35 way 0.156 inch spacing, double sided, \$1.00 ea. Ask for Ron (03)209-8410 bh or (03)795-9413 ah.

WANTED: COPY of Radio Electronics Nov 78. Will pay \$2.00. A photocopy of Part 1 Tank game acceptable. Send to 'Killmarnock', Nullamalma, via Inverell NSW 2360.

COMMUNICATIONS

FOR SALE: ICF-2001 receiver, two months old, not suitable for my use, \$150 ono. G. Willson, 15 Hirt Ave, Murray Bridge SA 5253. (085)32-0259 bh or (085)32-4597 ah.

SWAP: COMMODORE 8K with sound, software and full documentation for telereader CWR-670E or FR6-7700 or equivalents. Phone David (07)246-1474.

COMPUTERS

FOR SALE: Dream 6802 computer with power supply, cassette, some programs and full documentation, \$120 ono. (069)22-5335 after 5pm.

FLOPPY DISK drive power supply, 5 V at 3 A, -5 V at 0.7 A, 24 V at 2.8 A. Open frame, compact, with harness for 2 x SA800. \$100. (07)376-3323.

RCA VP-111 micro, power supply, cassette drive, I/O port, 4K RAM, connect to TV or monitor, software, cables, manuals, carry-case, \$150. (02)692-9174.

PADDLES for VIC 20, \$25 + \$2 p&p. To order or for further information write to BIP Hardware, 34 Knights Rd, Galston NSW 2159.

SORCERER 32K, Devpac, manuals, cables, WP and other programs, \$750 ono. Godbout XX S100 32K static RAM, \$250. Hazeltine terminal, \$100. Terry (02)682-4649 ah.

SELL: Exorciser buss to SS-30 I/O card adaptor board, allows use of SS-30 I/O cards on Exorciser buss, \$150. Ken (03)873-3903.

ETI-660, case, colour components, amplifier, modulator, transformer, leads, 24" monitor, \$300. Willli, 9 Malua Cres, Mill Park Vic. 3082. (03)404-2063.

FOR SALE: Control Data tape transport system, complete and to the best of my knowledge in working order. \$800 ono. Will consider separating and selling parts. Phone Ken George (03)878-7574.

SELL: ETI-660 (Monochrome) complete in case with 3K RAM, programs etc. \$90. G. Hunt, 19 Menzies Close, Frankston 3199. (03)787-5876.

FOR SALE: Sinclair ZX-80 with manual, leads, PSU, dust cover, cassette recorder, loads programs. Cost \$150, sell \$60 ono. Complete 1981 ETI & EA, \$10. (02)84-6564.

FOR SALE: CALIGRAF program for ZX80/8K ROM, ZX81 (6K RAM plus printer). Produces upper and lower case, proportionately spaced printout, \$11.95. R. Morgan, 61 Rathowen Pde, Killarney Heights NSW 2087.

SELL: 'The last one' program generator on 8" diskette with license, manual. Requires CP/M and MBASIC interpreter 5.03 or later, \$495. (03) 598-8129 ah.

SOUTHWEST Technical 6800 CPU card SS50 buss, SWTBUG ROM, baud rates to 9600. Works fine, \$75. Also MPA2 bare board. (051)56-8291.

SELL: TRS-80 games — Nova, Galaxy, Cosmic, Attack, EDTASM+, Advent, Crowley, ATC, etc. Half cost ono. David Brighton, Franklin Rd, Huonville 7109.

BRAND NEW VIC-20: Not even opened, only \$380. K. Fong, 6/46 Mitre St, St. Lucia Qld 4067.

FOR SALE: ETI-660, plug pack, 3K, colour, in wood case, modulator. No reasonable offer refused. J. Higgs, "Galliers", North St, Thirlmere NSW 2572. (046)81-8583.

BBC Model A (16K), brand new, in carton. Complete with 'welcome' package and users guide. Cost over \$1400, will sell \$1150 ono. Phone (03)789-3226.

SELL: APPLE II europlus with sculptured keyboard, green phosphor monitor, 16K RAM card, Microsoft softcard, disk drive and tape archiving. \$3000. Phone (03)20-2150 ah.

SIGNETICS INSTRUCTOR-50 2650 based education board. Has \$100 buss for expansion, all manuals, \$150. (062)51-5848 ah.

CROMEMCO 8-PIO S100 I/O card. Eight x 8-bit parallel ports, two relay outputs, hand-shake, fully buffered, LED outputs, switch inputs. Worth \$400, sell \$300. Phone (02)387-3097.

FOR SALE: SHARP PC1211 pocket computer and printer with manuals, application programs. \$120. Phone (062)72-3711.

FOR SALE: SYSTEM 80 business MKII, excellent condition, only five months old. Suit new buyer, lots of software, \$700 ono. Phone Len (02)569-6271.

FOR SALE: SYSTEM 80 (late model), 16K with sound switch. \$200 of programs with magazine, the lot \$700. W. Pfeffer, 22 Burns St, Capalaba Qld 4157. (07)390-2326.

SUPER 80 in woodgrain and metal case with 48K RAM, ROM BASIC, S100 expansion, lower case generator, separate keyboard in case, technical and basic manuals. \$350. (03)543-5451.

SCHNAPPENDER SPRIGEN WERK: Gadgets for the Apple II. Essential for any serious user. See us at A.U.G. or Computerland. All around \$15. Call Tim (02)36-6710 after 5pm.

ATTENTION! Does anybody have a 'spare' keyboard encoder or cassette interface for the old DGS100 systems? (Desperation: severe.) Ring after 5pm, Ben (02)848-8141.

MICROBEE DOCUMENT editor: a word processing program. 15 page instruction manual and complete listing, \$10. Manual, listing, plus tape \$15. H. Proctor, 27 Roberts Avenue, Mortdale NSW 2223.

SELL: Two XMX80 printers, \$700. Apple interface, \$39. One APF disk drive, \$175. APF colour monitor, \$580. 400 x Verbatim disks, \$3 ea + st, all new. Greg (03)578-6108 ah.

FOR SALE: MICROBEE 32K, ED/ASS, monitor, cass/rec, software, all manuals, cost approx. \$800. Sell \$650. (043)28-4442.

SUPER-80: EPROM BASIC, power supply, 16K RAM expandable to 48K on-board, all IC sockets, manuals provided. \$295. R. Sandland, 9 Downes St, Epping NSW. (02)86-6731.

FOR SALE: HOMEMADE 2650 computer, software, junkbox, \$850. 16K Z81, excellent condition, printer not working, \$450. David Wheatley, 4 Martin Cres, Milperra NSW 2214.

ZX81 PROGRAMS: 15 programs, set \$10. Catalog \$2. Cheque/postal order to Poseidon Software, 72 May Street, West Preston, Melbourne Vic. 3072.

SELL: DUMB TERMINAL, IE Model 33, 72 char/line, 24 lines. 110-500 baud plus service manual, working. \$130. Adrian 398-7224 or 331-6333.

FOR SALE: S100 TCT 16K memory board using prime LP chips. \$105 each or two for \$200. (047)36-3698.

FOR FREE: CHIP 8 User Group programs. Send S.A.E. with details of which CHIP 8 machine to Frank Rees, 27 King St, Boort Vic. 3537.

FOR SALE: 2 MPI B52 disk drives, power supply and case, all \$800 ono. Phone John (02)36-5170 ah.

FOR SALE: TRS-80 Model I Level II + monitor + over 40 games. The lot for only \$700. (03)560-8629 after 7pm.

SUBSCRIPTIONS BACK ISSUES BINDERS PHOTOCOPIES BINDERS

ORDER FORM

I enclose \$..... for (tick appropriate box/es). All prices include postage.
Send orders to: ETI, 4th Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Phone: (02)268-9015

		NAME (Please print)	
<input type="checkbox"/>	Subscriptions	\$28.15 per year within Australia \$41.40 overseas (surface mail)	\$..... \$.....
		Airmail rates on application	
<input type="checkbox"/>	Back issues	\$2.50, available from November 1978.	
<input type="checkbox"/>	or photocopies	\$2.50 per article per issue	
	Project No.	Month Year	\$.....
	Project No.	Month Year	\$.....
	Project No.	Month Year	\$.....
	Project No.	Month Year	\$.....
Please attach a list if more than four required.			
<input type="checkbox"/>	Binders	No..... @ \$6.10 in NSW	\$.....
		No..... @ \$7.50 in other states	\$.....
			Number:
			Signature
		Please debit my <input type="checkbox"/> Bankcard <input type="checkbox"/> American Express card	



drege

The hacks who write for drege have taken their first holiday.



A penny for your thoughts, my dear

Rack off, randy RAM!

Exclusive to Marantz.
 Very sophisticated. Very superior. Very expensive.



Very high fi indeed.

These Marantz Gold components represent the world's most advanced, most inspired, most stringently tested and sophisticatedly engineered audio equipment.

For the wealthy—exclusive toys.

For the connoisseur—the finest hi-fi money can buy.

The Marantz TT1000 (around \$2500), with its precision-made high density glass and golden aluminium sandwich structure, is justifiably described as one of the most beautiful turntables ever.

'Playing a series of direct-recorded discs, warped discs, discs with nasty low frequency content and discs requiring unusual track-ability performance, showed clearly that this system borders on the superlative in areas where even most good turntables only provide good to above average performance.'

'...the resonance characteristics of the TT1000 are the lowest we have yet seen from any turntable irrespective of its selling price.'

'This is top-of-the-line equipment for people who rate hi-fi as their greatest pleasure in life'.
 — Louis Challis, *Electronics Today International*, April 1981.

Similarly, the Marantz SM1000 Stereo Amplifier (around \$5000) is designed to be the ultimate in luxury and performance.

When it was bench-tested by ETI Magazine in an exhaustive lab study, Louis Challis stated 'The Marantz SM1000 Amplifier has the capability to provide superlative performance at home, in a laboratory, in a studio, or in a rock band with the ease and panache of a professional.'

'The power output claims are modest for the unit is readily capable of producing 625 watts into an 8 ohm load with both channels driven...'

And when the Marantz ST8 FM/AM Tuner (around \$700) was

put through its paces so technically surprising was its performance that a second series of tests was devised to check the first results.

'As a result... the Marantz ST8... far ahead of any tuner we have ever measured and better than any tuner we have ever seen

reviewed in any other magazine, either local or overseas.' — Paul de Noskowski, *Electronics Australia*, April 1981.



The TT1000's adjustable, high-absorption air suspension audio insulator feet.

Marantz Gold. The New Audio Standard.



ST8

Detailed specifications of these exclusive Marantz Gold components are available on request by writing to:

Marantz (Australia) Pty. Limited,
 19 Chard Road, Brookvale, NSW 2100
 Phone (02) 939 1900 Telex AA24121
 Melbourne (03) 544 2011
 Brisbane (07) 44 6477
 Adelaide (08) 223 2699
 Perth (09) 276 3706
 Townsville (077) 72 2011

marantz®



SM1000

The range of Hi-Fi equipment you thought was beyond your means is now within your grasp.

RECEIVERS

SEPARATE AMPS

CASSETTE DECKS

INTEGRATED AMPS
TUNERS
CASSETTE DECKS
TURNTABLES
RECEIVERS
SEPARATE AMPS
SPEAKERS
CARTRIDGES
HEADPHONES
SYSTEM COMPONENTS

A Hundred Years of Musical Experience

YAMAHA
HI-FI



Please send me the latest
Yamaha Hi-Fi catalogue.

Name _____

Address _____

Postcode _____



Yamaha Hi-Fi Division, Rose Music Pty. Ltd.,
17-33 Market St., South Melbourne. Victoria. 3205.

MCR/RM3861E/R