

73

May 1965
It may be 40c.

Amateur Radio

**RM-499
Released!**




**Log Periodics 432 Converter Versatile Scope
Beer Can Converter 1215'er 5000 Watt Linear!**



"S" SERIES

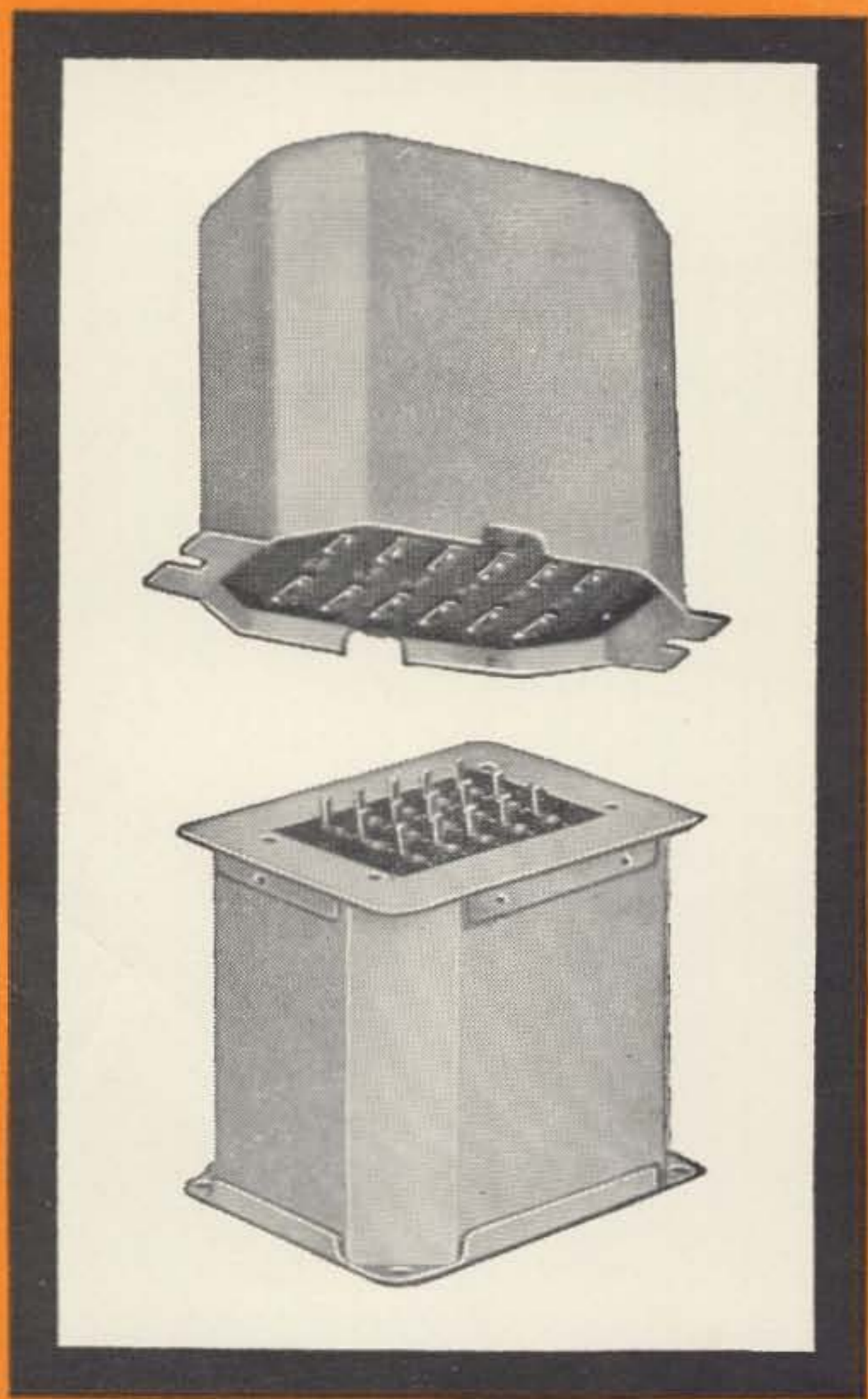AUDIO & POWER TRANSFORMERS & REACTORS For Complete Ham Systems



**Popular Priced
Matched Components
for
Power Supplies
Modulation
Pre-Amp &
Power Amplifiers
... for entire ham rigs**

Thirty years of attention to ham requirements have resulted in a complete line of reliable, high quality components geared especially to your needs. The "S" series of audio and power transformers and reactors, designed specifically for ham and PA service, are completely matched for compatibility in constructing a rig. These are popular priced units which afford the ham the full benefits of UTC's established excellence for quality components coupled with high reliability.

Write for catalog of over
1,000 STOCK ITEMS

UNITED TRANSFORMER CORP.

150 VARICK STREET, NEW YORK 13, N. Y.

PACIFIC MFG. DIVISION, 3630 EASTHAM DRIVE, CULVER CITY, CALIF.

73

Magazine

Wayne Green W2NSD/1

Editor & Publisher

Paul Franson WA1CCH

Assistant Editor

May, 1965

Vol. XXXI, No. 1

Cover by Barry Ober K2YDD

ADVERTISING RATES

	1X	6X	12X
1 p	\$268	\$252	\$236
1/2 p	138	130	122
1/4 p	71	67	63
2"	37	35	33
1"	20	19	18

Roughly, these are our rates. You would do very well, if you are interested in advertising, to get our official rates and all of the details. You'll never get rich selling to hams, but you won't be quite as poor if you advertise in 73.

432 mc Converter	K6MIO	6
Easy-to-build converter to get you on 70 cm.		
A New Approach to Phasing	W8HXA	12
Not <i>all</i> SSB transmitters use filters, you know.		
The Big Bomb	WØSYK	18
Runs a gentleman's gallon.		
Two for Two	W6TKA	22
Some antennas for our western hams.		
The Trouble with Fred	Margolis	26
A fetching tale illustrated by K3SUK.		
A Versatile Oscilloscope	WØOPA	30
Every ham needs a scope. This one does a lot, but doesn't cost it.		
Constant Gain Audio System	Pullman	36
Pretty clever. Take a look.		
A Cool KW	K5YWJ	38
Another approach to the inexpensive power supply.		
Beer Can Cavities	WA2INM/1	40
For use on two. Low noise transistor converter included.		
Four Element Rhombus	K2IRK	44
Yeah, that's right.		
Power Decade Resistor	Lyman	48
Or is it, "Decade Power Resistor?"		
Improve Your GDO	K5JKX	50
If it suffers from the common GDO maladies.		
Six Meter Junk Box Station	K3VLQ	54
The title sounds vaguely familiar.		
Design of Log Periodic Antennas	VE3AHU	62
A 73 technical scoop.		
Gus: Part I	W4BPD	66
This is it: The beginning of Gus' life and DXpeditions.		
73-A-Phone	K5JKX	70
Yeah, it's a stupid title, but what do you expect from an editor of S-9?		
The 1215'er	K1CLL	72
Hoisington sure makes 1200 mc easy to reach.		
Total Boredom	W7IDF	80
But not to read.		
Oscar III Highlights	KØCER	82
What happened.		
Dayco DR-30	WA1CCH	86
Review of a remarkable new receiver.		
Litts Code Snitcher	WA6UVS	90
Code monitor-oscillator. Good to at least 16 wpm.		

De W2NSD/1	2	New Books	92
Letter from Gus	84	New Products	94
VHF	84	Letters	96
Economy TR Switch	88	Caveat Emptor	106
Semiconductors	88	Propagation	112

73 Magazine is published monthly (thank heavens it's not weekly) by 73, Inc., Peterborough, N. H. Zip 03458 (terrible number). The phone is 603-924-3873. Subscription rates \$4.00 per year, \$7.00 two years, \$10 three years world wide. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in New Hampshire, U.S.A. Entire contents copyright 1965 by 73, Inc. Postmasters, please send form 3579 to Good Old 73 Magazine, Peterborough, New Hampshire. You are coming up for our July 4th hamfest, aren't you?



de W2NSD/1

never say die

They Laughed

Yet, they laughed and sneered when I said, "FCC Docket Due in March." On March 31st the FCC dropped the bomb. I laughed back. Here is the FCC synopsis of the proposal . . . you can read the whole dreary text in QST, if you want, it won't get you anything over this:

FEDERAL COMMUNICATIONS COMMISSION

65821
PUBLIC NOTICE-S
March 31, 1965

WASHINGTON, D. C. 20554
Report No. 1851

NONBROADCAST AND GENERAL ACTION

The Commission en banc, by Commissioners Henry (Chairman), Hyde, Bartley, Lee and Cox took the following action on March 31:

INCENTIVE LICENSING AND DISTINCTIVE CALL SIGNS PROPOSED FOR AMATEUR RADIO SERVICE

The Commission proposed amending the Amateur Radio Service rules to provide a new "Amateur First Class" operator license with reservation of the lower half of the 3.8, 7.2, 14.2 and 21.25 Mc telephony sub-bands, and 50.00-50.25, 144-145 Mc to Extra and First Class operators only. Reservation of the lower 50 kilocycles of the 3.5, 7, 14 and 21 Mc bands for Extra Class telegraphy operation is also proposed. The lower half of each segment would become reserved in 12 months, with full reservation 2 years after adoption of the proposed rules.

The First Class examination would require a 16-word-per-minute code test and a written examination intermediate in level between the General and Extra Class examinations. Eligibility would be limited to applicants who have held an Advanced, General or Conditional Class license for at least a year.

Except for a proposed elimination of Novice telephony privileges in the 145-147 Mc band, all classes of licensees would continue to have telegraphy and telephony operating privileges in a portion of each band in which they now have such privileges. Because a valid distinction between them no longer exists, Advanced Class licenses would be changed to General Class upon any renewal.

A distinctive call sign assignment procedure is proposed. The stations of Extra and First Class licensees would be assigned "two-letter" calls (two letters following the number). Unassigned two-letter calls with a single letter prefix would go to the old timers of these classes who were licensed prior to July 1, 1932. Conditional and Technician licensees would be assigned a distinctive two-letter prefix as has been the case for Novice Class licensees. The "one-by-three" combination would be reserved for the Advanced/General Class group.

This action constitutes the Commission's proposed action on petitions RM-378, 455, 470, 474, 480, 481, 499, 516, 517, 538 and 577.

Comments of interested parties may be filed by July 15 and replies by July 30.

Riot, eh?

When I first read it I was surprised at how closely this proposal follows RM-577, my own entry in the incentive licensing derby. You can go back and research my submission if you like and see the strong parallel, I won't belabor you with it. After looking over all of the ideas brought up on the incentive licensing deal I sorted out those that seemed most practical to me and presented them in a package to the FCC.

The resulting plan, Docket 15928 (they could have given us a lot better number than *that*), successfully answers most of the criticisms leveled against ARRL's RM-499. Most important of all it does not throw anyone off any bands.

My first reaction to 15298 was one of relief . . . it wasn't as bad as it could have been. Then I got thinking about what this was supposed to accomplish . . . and what it might accomplish. Rather than my carrying on at length this month with my views, why don't you talk this one over . . . and even more important . . . think it over and see what you decide about the thing. Carefully consider what value the three wpm code speed increase will have . . . and what drawbacks there are to it. Also consider the pros and cons of the First Class license. Ponder too the impact on ham radio as we know it of the splitting of the bands . . . the new call signs . . . consider each band separately . . . the effect on contests, DXing, rag chewing, six meters, two meters, etc. Will these changes be beneficial enough to be worth the immense cost to the FCC in assigning us all new call signs and stepping up their monitoring program to keep up without further divided up bands, not to mention the one to two million dollars in new license fees we will have to pay . . . the effect on older hams who are leading busy professional lives and may be discouraged at having to learn a new license test all over again to keep in touch with

their old buddies . . . the great problems thousands of us have in merely getting to an FCC licensing point now that the Conditional license is virtually a memory.

Think it all over and send your thoughts in as soon as you can so I can run them in the June issue. I'll try to sort out the most well thought out letters. Letters received here before April 30th will be considered for June and those up to May 30th for our July VHF issue.

Perhaps, in view of the 16 wpm bit, it is time to discuss the value of CW ability today . . . 1965.

July 4th

Ever since our open house back in August 1962 I've been wanting to get more of you up here for a personal visit and to get you to see New Hampshire. The big day is July 4th. If you can manage it please come on up and join us for a New England Hamfest. We're trying to think of everything possible to make this an outstanding time.

Bring any ham gear you want to sell . . . we'll have a big auction going all day long . . . at least as long as the gear holds out. We'll be renting the local armory here so we'll have lots of space for exhibits by manufacturers and dealers. Bring a picnic lunch or plan on packing at any of the nearby restaurants . . . there is one right across the street from the armory.

We'll be set up for field strength measurements on both 144 mc and 432 mc, so bring the best antenna you can hold by yourself and see if you can win the prize for the best field strength. We will have a real professional setup to test the antennas . . . here's your chance to see how good yours really is.

Since 73 is largely devoted to homebrewing gear we'll have prizes for the best home constructed equipment . . . bring as many entries as you want.

We'll also have tours of the 37 room headquarters building and the 73 Mountain VHF shack. We want you to see as much of New Hampshire as possible too so we'll have special maps available which show the major places of interest in the state. And, as I may have mentioned before, New Hampshire is one of the most beautiful states in the union . . . and it is small enough so you can easily drive over much of it in one day. If you drive up from New York, New Jersey, Pennsylvania, etc., on Saturday you will be able to visit lower New Hampshire that same day. Sunday is our hamfest. On Monday (a holiday) you can go up through the White Mountains, up

the Tramway, the Flume, and Mt. Washington, and back home again that night or the next morning. We're only a little over four hours by car from New York City here.

If you think you are coming you might drop us a card and let us know so we can plan things for the size group we'll have. Also, if you will be wanting reservations to stay overnight in the area we can help with that too . . . but please don't wait too long for New Hampshire is buzzing at this time of year and reservations can be hard to come by.

If you have mobile VHF gear you can give it a good workout from nearby Pack Monadnock . . . you can drive right to the top. Mt. Monadnock (73 Mountain) is available for easy climbing if you dig that stuff.

Do figure on coming up for a hello and a good time on the 4th.

Hamfest?

Paul and I took in the IEEE show and SSB Hamfest this year. Though I was disappointed that they made room for CQ to have a booth, while having no room for 73 . . . it was all for the good. CQ did a rousing business in engraved badges and I got to talk to about 1000 friends. Peggy Browning was there, fresh from her visit to Bhutan. Dannals was there, but didn't notice me. Huntoon waved hello. A couple of the manufacturers who have been pointedly not advertising in 73 smiled cryptically. And quite a few fellows bent my ear, filling me in on recent ARRL misdemeanors and other trivia of ham life.

We also took the opportunity to stuff on interesting foods: Japanese, Chinese, Lebanese, and Viennese. Say, if you are ever looking for one of the nicest, friendliest restaurants in New York, you might visit the Konditorei, 33 Irving Place . . . regards from Wayne. Stop in for some coffee and Viennese pastry some night, at least.


Ham Stamp Wins Award

"Sour Grapes," they said . . . accusing me of being critical of the ham stamp just because it was designed by the ARRL. Well 30,249 votes were counted in the 17th Annual Design Derby for the best and worst design of U. S. commemorative stamps. Of the 18 different commemoratives issued in 1964 our blessed ham stamp got the fewest votes for "Best Design." Not content with giving us the booby prize, the poll also asked for votes for the worst design of the year. We only won second prize in that category . . . being displaced by the Fine Arts stamp. Perhaps we

Continued on p. 100



NEW FROM

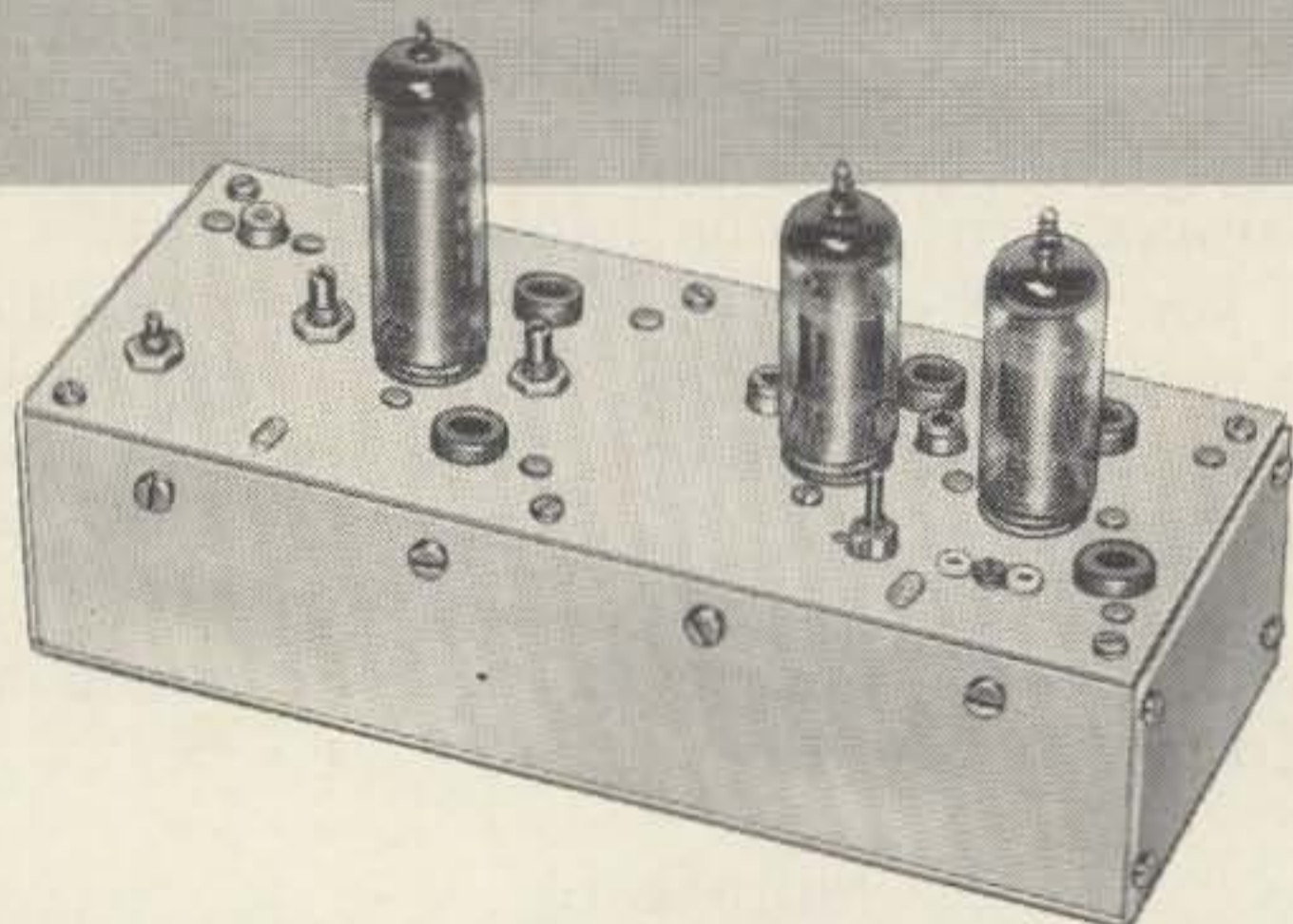VHF/UHF UNITIZED TRANSMITTERS 50 mc — 420 mc





AOD - 57
DRIVER/TRANSMITTER FOR 50 OR 70 mc
 The AOD-57 completely wired with one 6360 tube, two 12BY7 tubes and crystal (specify frequency). Heater power: 6.3 volts @ 1.2 amps. Plate power: 250 vdc @ 50 ma.
AOD-57 complete\$69.50

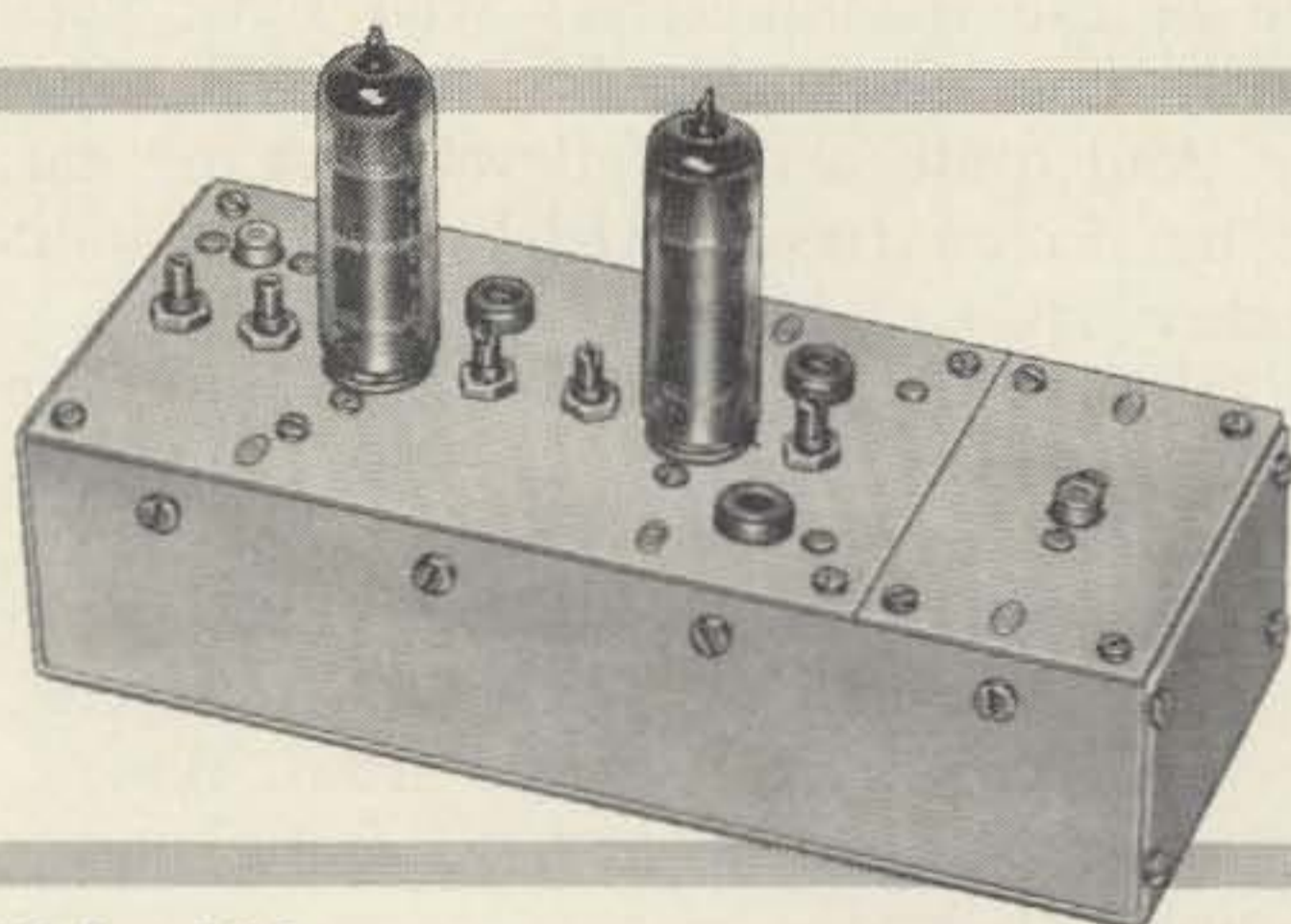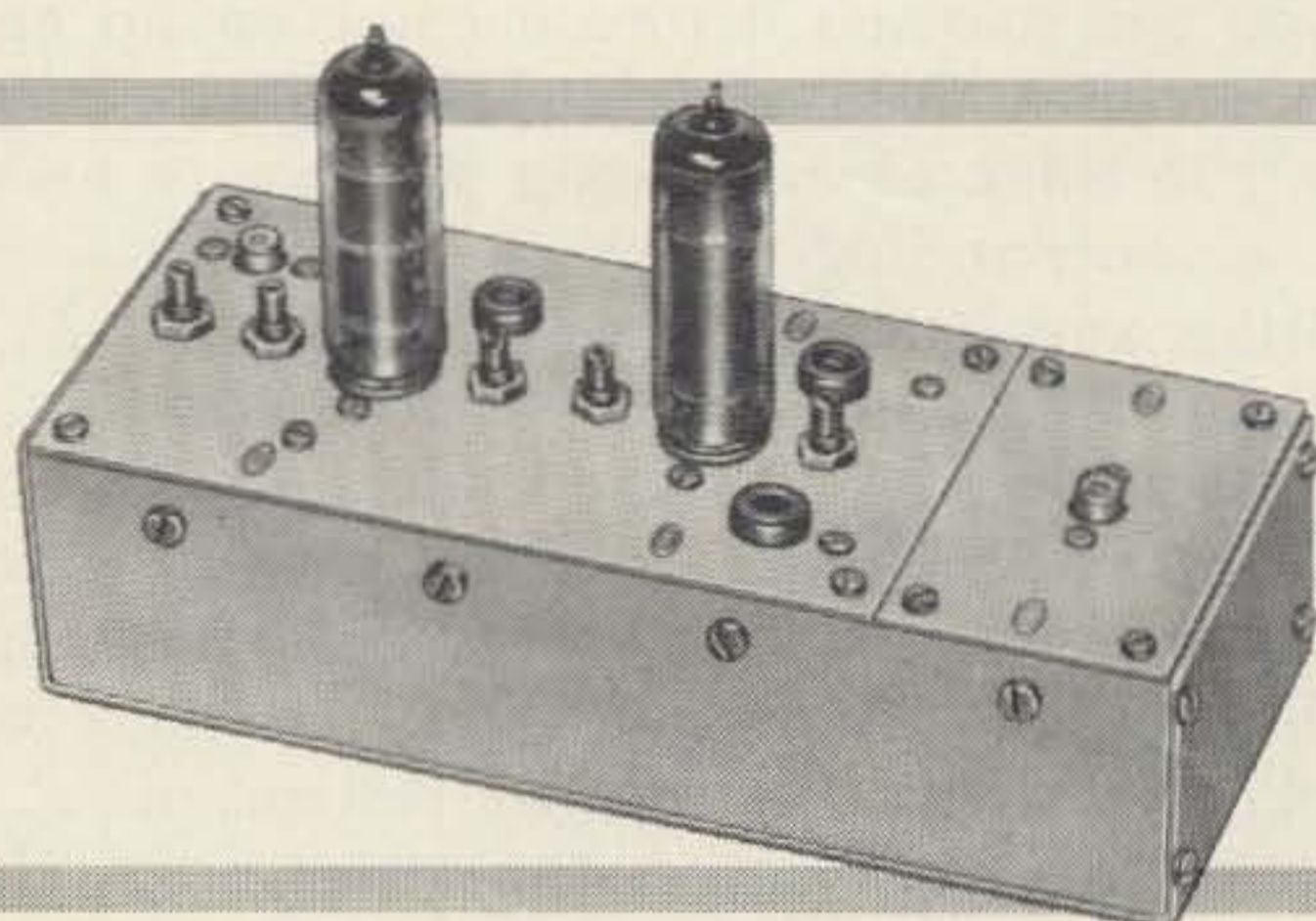AOA - 144
MULTIPLIER / AMPLIFIER FOR 144 mc
 The AOA-144 uses two 6360 tubes providing 6 to 10 watts output. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate power: 250 vdc @ 180 ma.
AOA-144 complete\$39.50



AOA - 220
MULTIPLIER / AMPLIFIER FOR 220 mc
 The AOA multiplier / amplifier uses two 6360 tubes providing 6 to 8 watts output on 220 mc. Requires AOD-57 for driver. Heater power: 6.3 volts @ 1.64 amps. Plate: 250 vdc @ 150 ma.
AOA-220 complete\$39.50

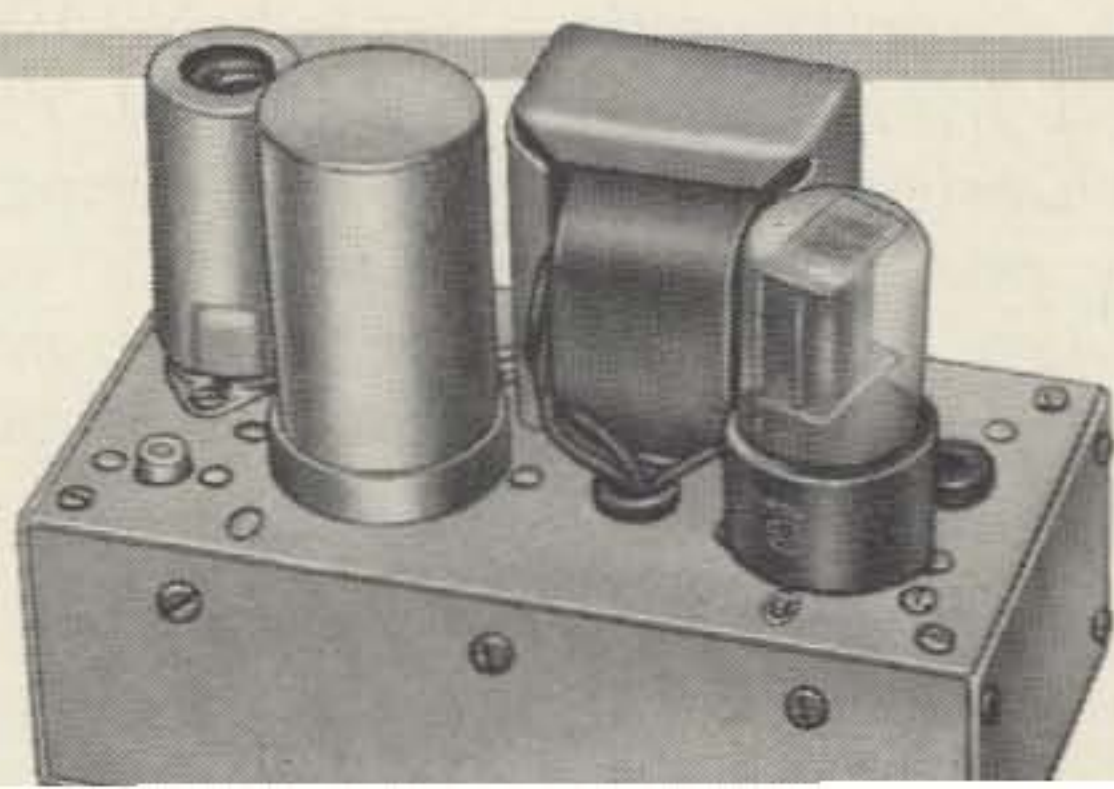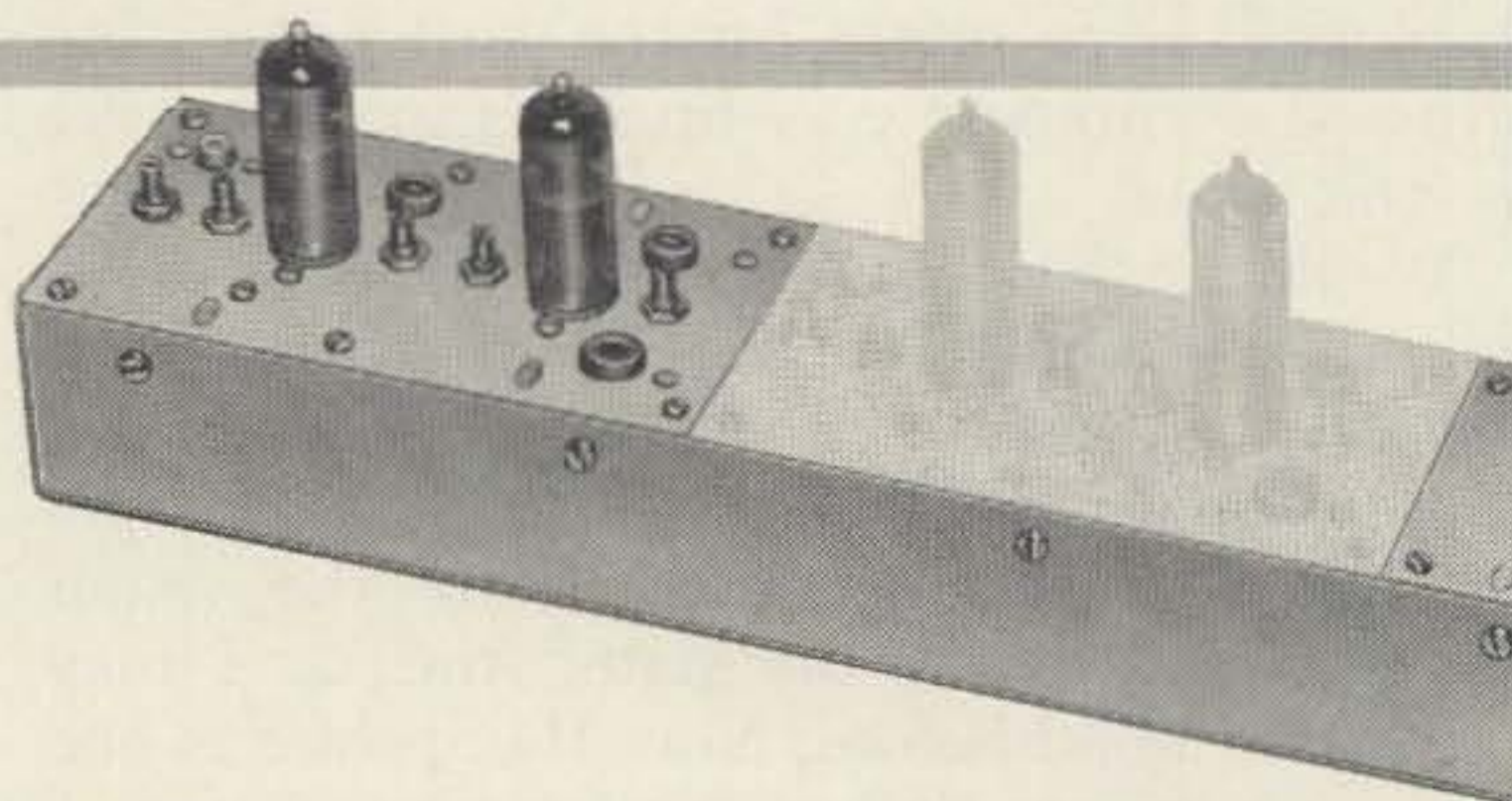AOA - 420
MULTIPLIER / AMPLIFIER FOR 420 mc
 The AOA-420 multiplier / amplifier uses two 6939 tubes providing 4 to 8 watts output on 420 mc. Requires AOA-57 plus AOA-144 for drive. Heater: 6.3 volts @ 1.2 amps. Plate: 220 vdc @ 130 ma.
AOA-420 complete\$69.50



AMD - 10 MODULATOR:
 The AMD-10 modulator is designed as a companion unit to the AOA series of transmitters. Uses 6AN8 speech amplifier and driver, 1635 modulator. Output: 10 watts. Input: crystal microphone (High Impedance). Requires 300 vdc 20 ma, no signal, 70 ma peak: 6.3 vac @ 1.05 amps.
AMD-10 Modulator complete\$24.50

INTERNATIONAL

International's new unitized VHF/UHF transmitters make it extremely easy to get on the air in the 50-420 mc range with a solid signal. Start with the basic 50 or 70 mc driver. For higher frequencies add a multiplier-amplifier. All units are completely wired. Plug-in cables are used to interconnect the driver and amplifier.



ARY - 4 RELAY BOX

Four circuit double throw. Includes coil rectifier for 6.3 vac operation.

ARY-4 Relay Box complete.....\$12.50

APD - 610 FILAMENT SUPPLY

The APD-610 provides 6.3 vac @ 10 amperes.
APD-610 complete.....\$9.50




COMPLETE TRANSMITTER

6 METERS

50 mc


AOD-57

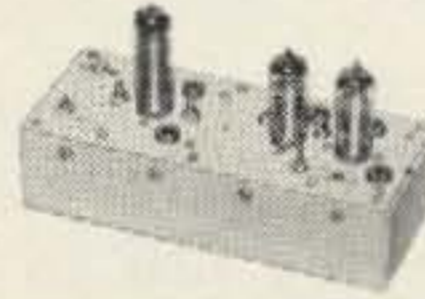

2 METERS


144 mc

AOD-57 PLUS
AOA-144

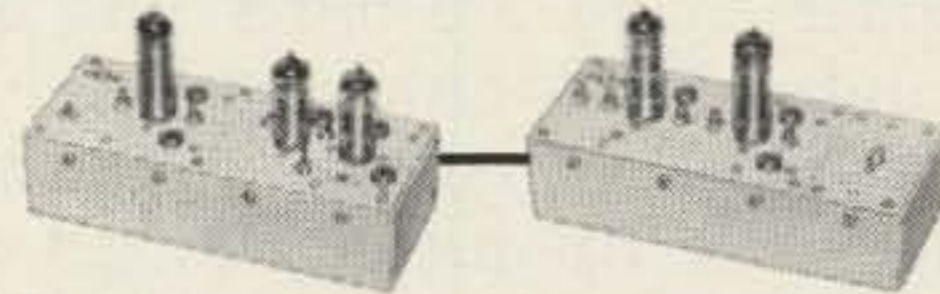


220 mc

AOD-57 PLUS
AOA-220

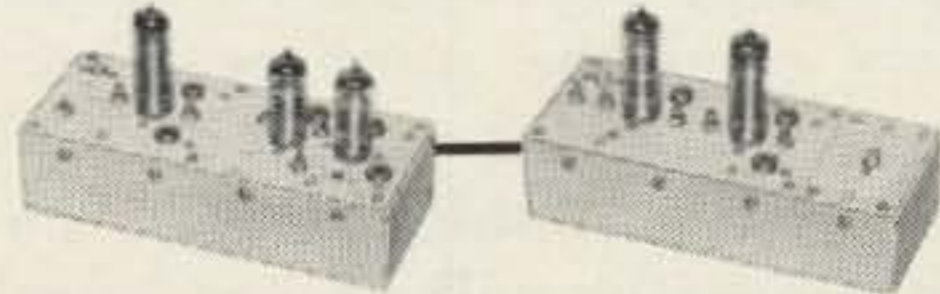

420 mc


AOD-57 PLUS
AOA-144 PLUS
AOA-420

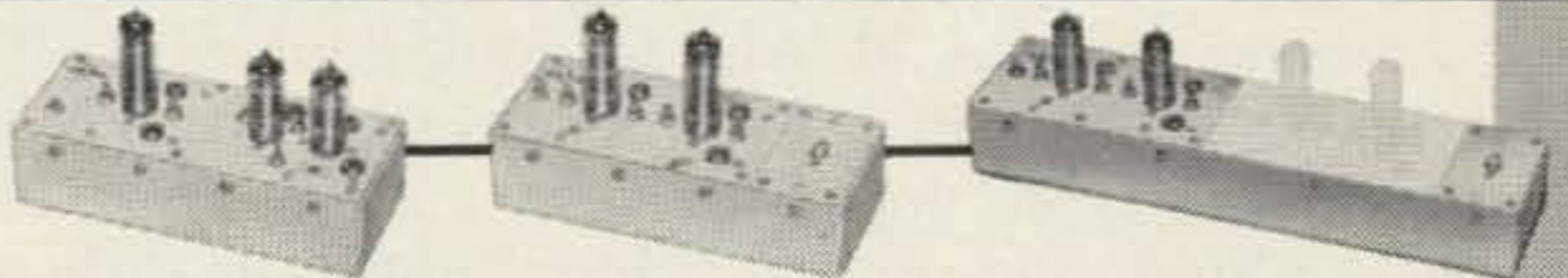

**INTERNATIONAL
CRYSTAL MFG. CO. INC.**

18 NORTH LEE — OKLA. CITY, OKLA.

*Order Direct
from International*

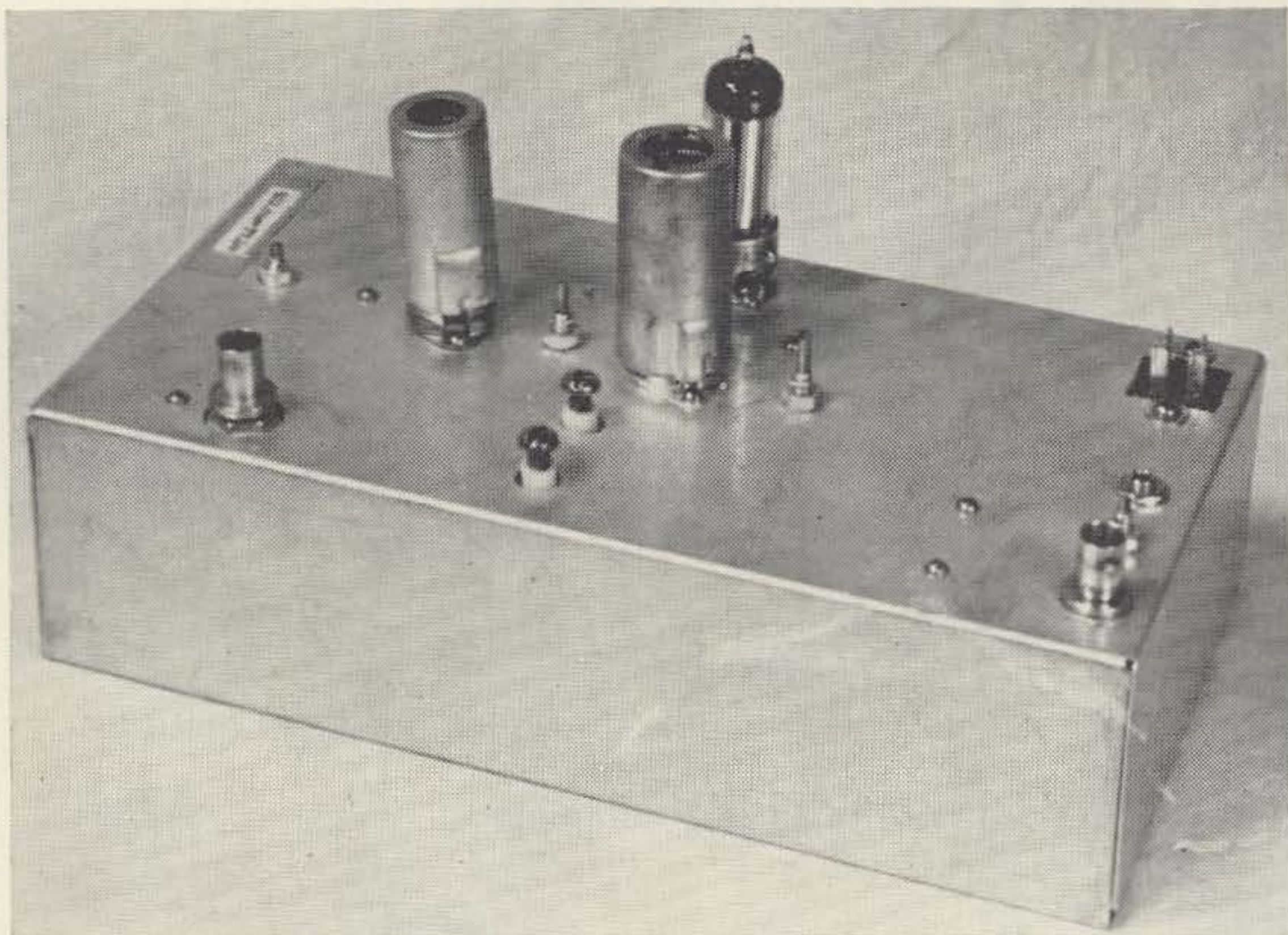

Jim Kennedy K6MI
2816 E. Norwich
Fresno, California

432 mc Converter

The recent increase in interest in 432 mc has sent many a budding UHF enthusiast scurrying to the various handbooks in search of a good converter circuit.

A number of such circuits will be found. However most suffer from circuit complexity. Tube mixers are expensive if they are to be effective. Multiplier chains are often long and somewhat ungainly. In addition, when you have finally built your basic converter, you will still have to add a hot RF preamp to get the most from your receiving system. All these factors can cause even the most enthusiastic ham to pause and count his pennies.

One approach to the problem would be to assume that the converter will be used with a good preamp, at least for long haul work. This will give a much greater latitude to the design of the basic converter.

Noise figure is, within limits, of little importance. In fact, in the interest of economy, no special effort should be made to make the noise figure any lower than that maximum value which the preamp has sufficient gain to cover comfortably. There is no point in paying out good money and time to build an 8 db converter if you intend to put a 5.5 db preamp with 15 db plus gain in front of it. At the same

time there is not too much point in building an 8 db converter and no preamp, when a 5.5 db or better preamp can be had for about the same extra cost.

This relaxation of the noise figure requirement makes an inexpensive crystal mixer look very attractive.

The injection chain can be simplified by starting off with an overtone crystal in the 4 mc region. This is a fairly common practice in VHF converters. A crystal in the 60 mc region would eliminate an additional stage of multiplication and reduce the tube compliment by one, but the crystals in this region are more expensive and the frequency stability of the converter may suffer.

The number of tube stages can be further reduced by making use of a simple diode multiplier for the final multiplication.

This leaves three tube multiplier stages required. They can easily be accommodated in two tube envelopes.

The choice of *if* frequency often depends on the receiving frequencies available, but in the interests of image response an rf to *if* ratio of about 10 to 1 is recommended. This makes 6 meters a logical choice.

Using 6 meters as an *if* has an added div

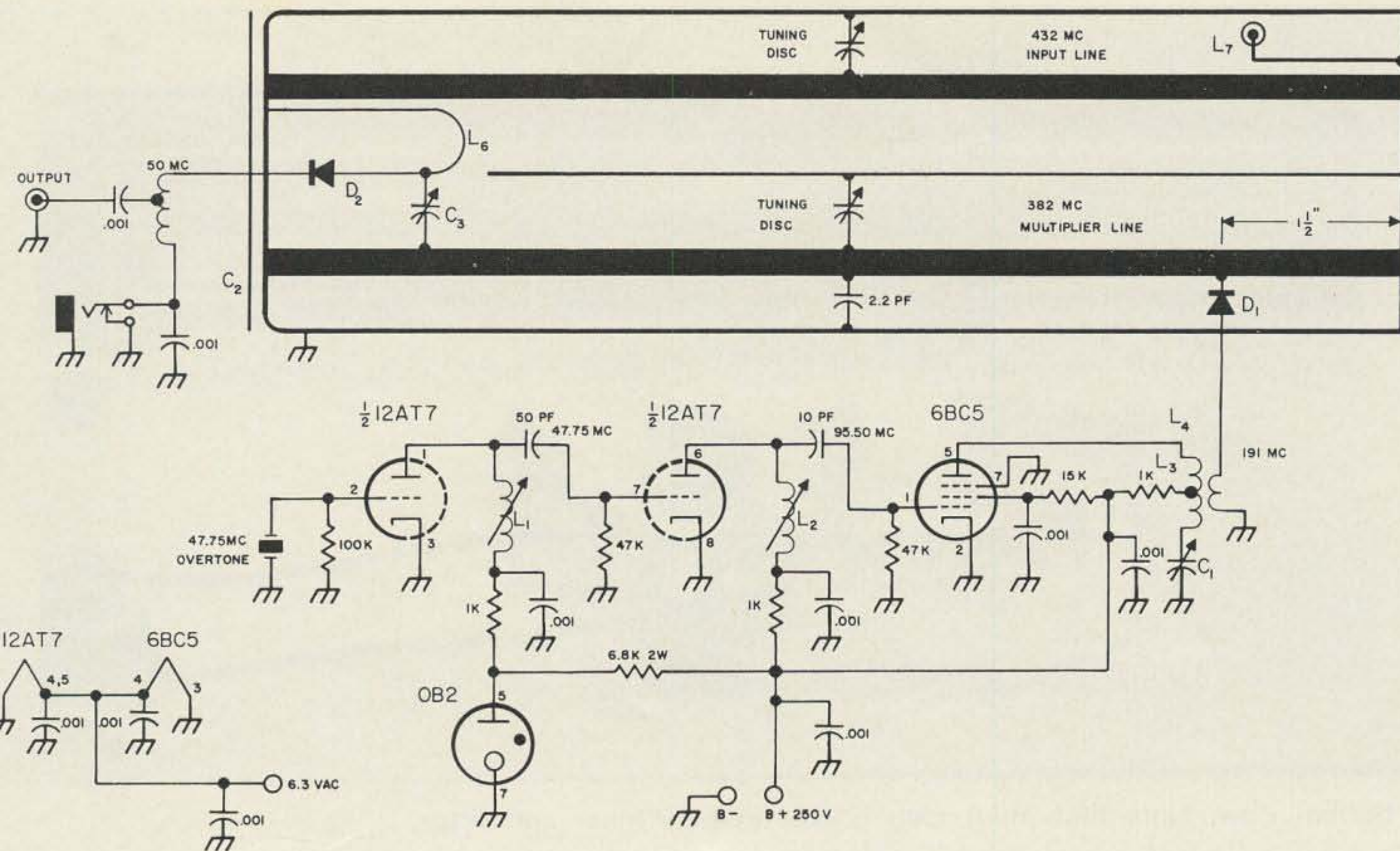


Fig. 1. 432 mc converter.

- 1-5 pf plastic trimmer.
- UHF bypass. See text.
- Injection coupling. See text.
- L2. Slug tuned to frequency.
- 10 turns #19 enameled $\frac{1}{4}$ in. dia., CT.
- 3 turns #18 enameled, $\frac{1}{4}$ in. dia.

- L5. Slug tuned to *if* frequency. Tapped fairly high.
- L6. Mixer coupling. $2\frac{1}{2}$ in. total length, $\frac{1}{4}$ in. wide.
- L7. Input coupling. $1\frac{1}{2}$ in. total length, $\frac{1}{4}$ in. wide.
- D1. 1N72 or 1N82.
- D2. 1N21C.

and. Most 6 meter converters are equipped with a high gain low noise rf amplifier. This abundance of gain will make the *if* amplifier unnecessary in conjunction with most diode mixers. In most cases this eliminates another stage from the 432 mc converter.

Construction

The diode mixer and multiplier circuits are on adjacent trough lines. The multiplier line is to be lengthened somewhat by additional capacitive loading to fit the chassis size used. The lines were made from 16 gauge brass sheet stock and $\frac{1}{4}$ inch brass tubing. The various coupling loops are made of strips of .003 inch brass shim stock about $\frac{1}{4}$ inch wide. The various dimensions of the lines are given in Figs. 1 and 2.


Both lines are tuned with variable capacitors constructed of brass discs about $\frac{5}{8}$ inches diameter. The discs are soldered to the inner center of each line. The other capacitor plates are soldered to the ends of 10-32 screws which are mounted through tapped holes in the trough box or by a 10-32 nut soldered to the box.

The mixer diode is mounted on a $\frac{3}{4}$ inch by $1\frac{3}{4}$ inch plate of brass shim stock. A hole is drilled in the center of the stock to just clear the ceramic and brass portion of the diode body (but not the brass lip on the large end). Then a $\frac{3}{16}$ inch piece of $\frac{9}{32}$ inch diameter brass tubing is soldered over the hole. The end of the tubing can be deformed slightly or you may cut slots in it to form fingers which will hold the diode firmly in place.

The mounting plate for the crystal is insulated from the line box for dc by a thin sheet of teflon or mylar tape. This is held in place by two nylon screws or insulated metal screws. This assembly acts as a bypass capacitor for the UHF signals but acts as part of the tuned circuit for the 50 mc signal and has no ill effect on it.

The clip for the small end of the crystal is made by bending the end of the $\frac{1}{4}$ inch wide diode coupling loop into a triangular shape with a pair of pliers. The small tip on the diode then fits into the clip.

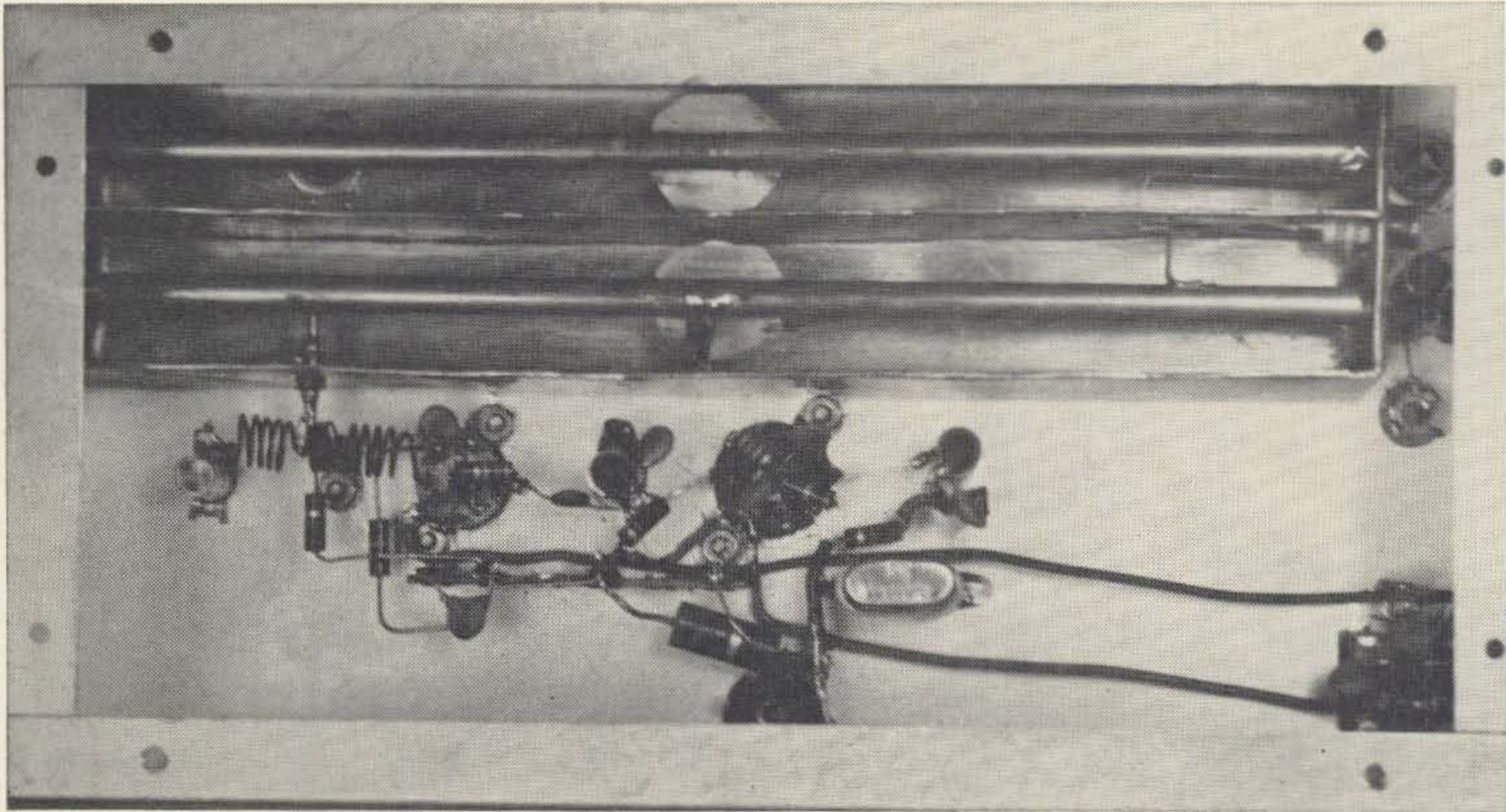The injection coupling capacitor is a shim stock tab attached to the multiplier line and



Bottom view. Note that input loop is obscured by inner conductor.

brought near the mixer diode loop. Varying the spacing between the tab and the loop will vary the injection coupling.

I have found it convenient when working with such circuits to build the trough lines as a complete sub-assembly, that is, with BNC fittings and other protrusions attached to the trough directly rather than to the trough *through* the chassis. The chassis holes are then drilled out to pass the entire fitting. In this way, the entire unit may be assembled and tested free of the confines of the chassis itself.

Parts layout for the injection chain is not too critical, though it would be well to remember that frequencies up to about 200 mc are involved. Bypass capacitors should be used liberally on B+ and filament circuits. A symmetrical layout which will end with the multiplier diode near the appropriate point on the trough line should be used.

Some experiments were performed in an effort to see if the diode could provide enough mixer drive quadrupling rather than doubling. This would eliminate the need for the last tube multiplier. It was found that the diodes used would provide only enough mixer current to provide marginal operation of the converter, even with the 12AT7 going full blast on 250 vdc.

On the other hand, the circuit should in Fig. 1, which uses the additional tube multiplier, develops more than sufficient drive even at low supply voltages (over 900 microamps with 90 vdc).

As a result, this configuration seems more adequate. If a more exotic diode had been used in the multiplier, the quadrupling arrangement could probably be made to work out. A varactor like the DR-303 would undoubtedly outperform the 1N82's and 1N72's in such a configuration.

The use of the VR tube on the oscillator is not mandatory, but it is highly recommended to maintain the stability of the converter when confronted by line voltage variations. Mounting the crystal below the chassis also improves the stability by protecting the crystal from drafts and other such sudden temperature changes.

Tune up

Preliminary peaking of injection chain can be easily accomplished with an absorption meter. An alternate method would be to tune for maximum multiplier diode current. Remember that it is sometimes possible to buy out 1N72's and 1N82's with the rf available from the injection string if they are coupled too tightly.

Once the tube stages are peaked, couple the diode multiplier line output tightly into the mixer diode. The mixer diode current should then be peaked by tuning the diode multiplier line. It should be possible to obtain up to 2 ma of mixer current depending on mixer coupling and diode multiplier input coupling.


Some care should be exercised in the choice of meter used in measuring mixer current.

any of the VOM's on the market today employ a 500 ua or less basic meter. It will be found that, in most cases, the internal resistance of such meters is rather high. If this is so, it will produce some very confusing readings when used to measure the diode current. The impedance of the 1N21 series diodes is in the general neighborhood of 300 ohms. If the meter has, for instance, an internal resistance of 300 ohms, then the measured current will be only one half the true current when the meter is removed, because the meter and diode are in series.

Rather than use the VOM, a better choice would be to use a low internal resistance 0-1 A meter. Many such meters with internal resistances of about 50 ohms, are available on the surplus market for reasonable prices.

In normal operation only about 500 microamps of mixer current will be required. Once the proper operation of the diode multiplier has been confirmed, the multiplier input and output couplings should be reduced until a mixer current of perhaps 600 or 700 microamps is realized. The final adjustment of the crystal current can be made conveniently by tuning one of the tube multiplier slugs (not the oscillator) or by adding a screen pot on 6CB6.

The diode multiplier coupling reduction is governed by three considerations. First, the multiplier diode current should be kept below the burnout point, so a reduction of input coupling will provide extra safety margin in this respect. Second, it is desirable that the coupling between the input cavity and the multiplier cavity should be kept at a minimum to avoid signal loss to the multiplier line. If the 50 mc *if* is used this problem is minimized because of the separation of the resonant frequencies of the two cavities. However, if some lower *if* is used this becomes increasingly more important.

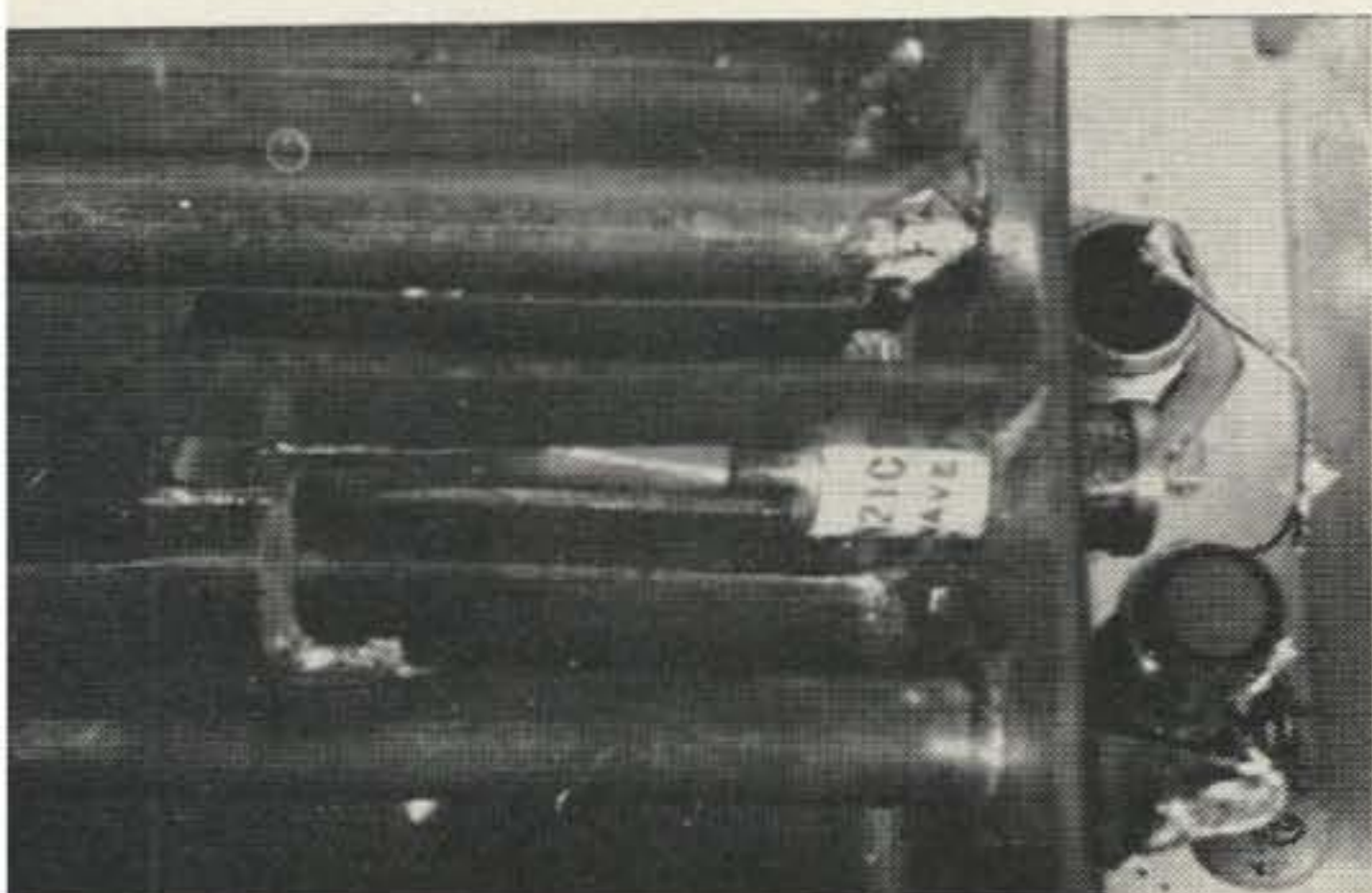

Mixer assembly. Note coupling loop and injection capacitor tab.

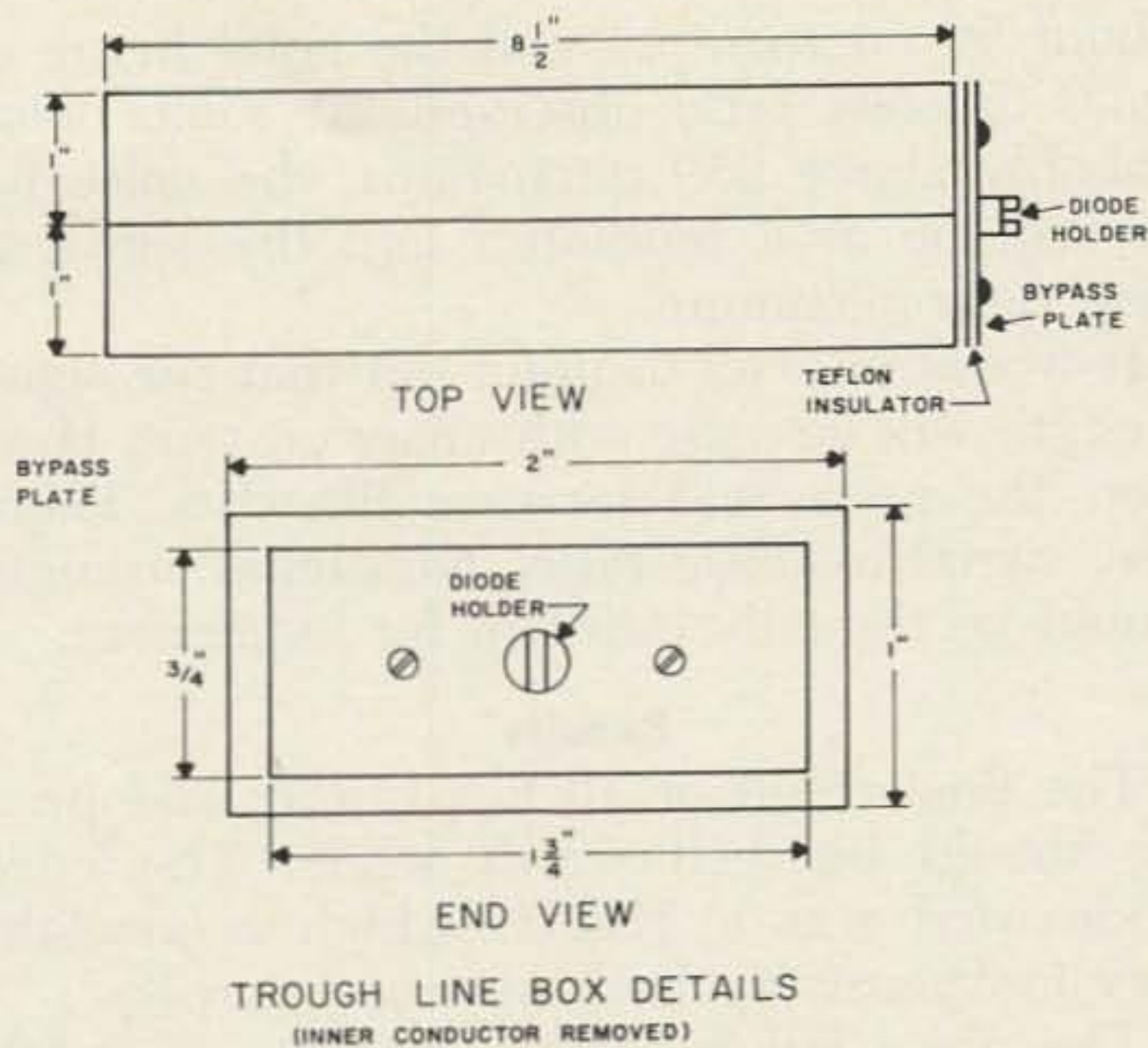


Fig. 2

The two above considerations should be balanced against the importance of delivering sufficient excitation to the mixer diode.

As noted, if the *if* is low enough, some signal will be lost because energy is coupled into the multiplier line. This same effect will also occur in the reverse: injection energy can be lost by coupling into the signal line (and then into the antenna) when the signal line is tuned through the injection frequency. This effect will be indicated by a severe dip in mixer current.

This phenomenon can provide a convenient frequency reference. If your injection is below the desired signal frequency then you should tune your signal line to the high frequency side of the mixer current dip.

The final tune up requires a weak signal source. Either a test signal generator or an on the air signal will do. Connect the converter output to the input of the 50 mc converter. The signal line should be tuned for maximum output. Then tune the *if* output coil for maximum.

You should find that when the signal is removed, the mixer noise can be peaked with the *if* coil. If not, then the *if* coil may not be resonate or the output tap may require adjustment. It may also mean your *if* amplifier (50 mc rf amp) is not sufficient, though the average six meter converter should do quite well.

Every mixer diode has some value of mixer current at which it will produce the best noise figure and hence the best results.

If a noise generator is available it can be used for the adjustments. If not, the signal to noise ratio check should be used.

The procedure is simple. Starting with a mixer current around 700 microamps the current should be reduced in small increments

(about 50 microamps) and the noise figure or signal to noise ratio observed. At some point, probably above 250 microamps, the noise figure will be at a minimum and the signal to noise ratio maximum.

It would be well to point out that the signal strength will increase with mixer current. However, the noise will increase likewise. Therefore, signal to noise ratio, *not* signal strength, should be the only criterion for judgement.

Results

The final result of all this tuning and pruning should be well worth while. The mixer diode used was a 1N21C which is available very inexpensively both new and surplus.

The noise figure of this converter is in the neighborhood of 14 db. This is not outstanding, but is in keeping with the original premise that the noise figure of the basic converter is of only secondary importance.

This noise figure is low enough to cover quite easily with any of the better rf preamps.

The 416 B preamp described in an earlier article¹ does an excellent job, as do some of the better nuvistor and transistor preamps. Needless to say, a good paramp will outperform them all.


For those who feel they need a low noise figure in the basic converter, a more expensive mixer crystal would be a good start. The 1N21E sells for about \$5.00 and the 1N21F for about \$15.00.

Experimenting with the mixer loop size or the loop size on the input line would also be likely to produce some improvement. As previously stated, however the extra money and effort would probably be better spent on a hot front end preamp.

. . . K6MIO

Pictures by Joe De Young WA6CQL

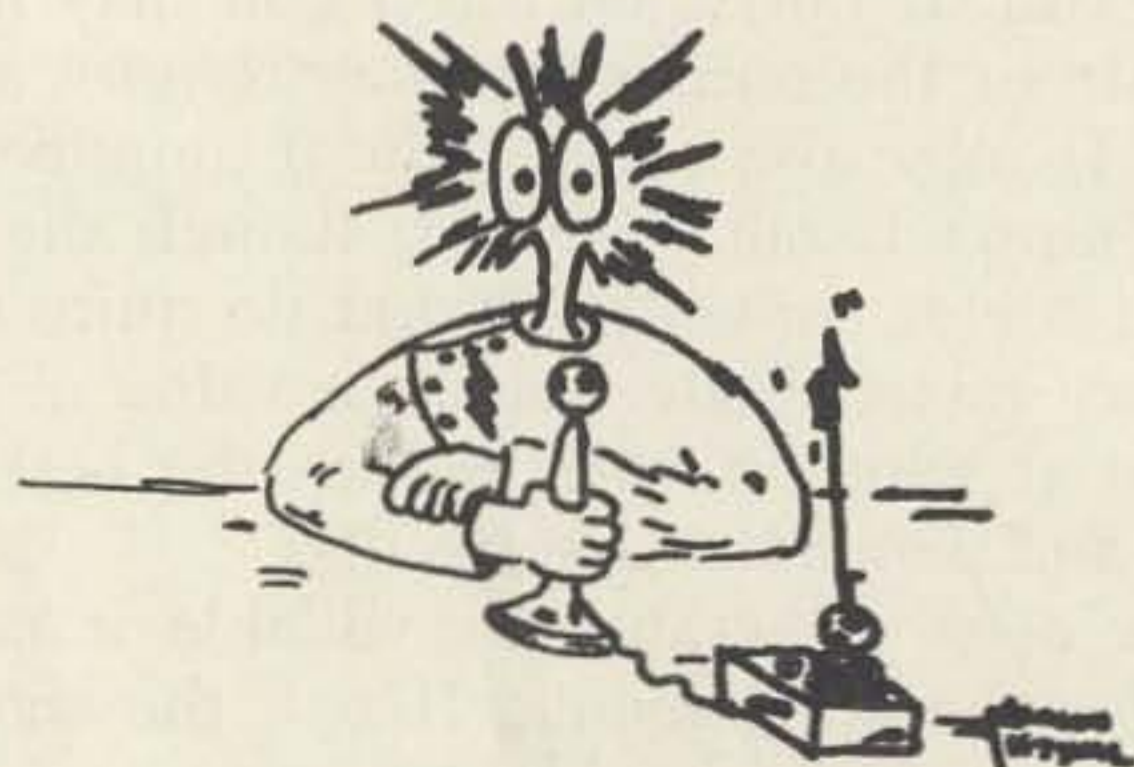1. 432 mc Preamplifier, Low Noise. 73 October 1964.



"Of course I'm interested in earth-bounce, Torfl. . . . But what can I hope to accomplish with this dinky lil' ole homebrew mega-watt rig?"

ROHN

sets the standard

for CRANK-UP TOWERS

Why settle for less than the best



K7ASK

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in Heights of 37 - 54 - 88 - 105 and 122 feet

Heavy Duty Self Supporting and Guyed in Heights of 37 - 54 feet (SS) 71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at all heights. **Versatility**—designed to support the largest antennae with complete safety and assurance **at any height desired!** **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the **right** size and properly rated tower for **your** antenna. The ROHN line of towers is **complete**. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—**ONLY \$100** postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:

ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest EXCLUSIVE Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

ATTENTION: GOVERNMENT, AIRLINES, POLICE, FORESTERS, INDUSTRIES AND OTHERS OPERATING IN THE 2 TO 30 MCS HIGH FREQUENCY BANDS



LEFT: CSB100TR.
RIGHT: CSB125C



YES

SINGLE SIDEBAND SETS BY HAMMARLUND ARE EIGHT TIMES MORE EFFECTIVE.

Who? Says Hammarlund who makes these remarkable long-range transmitter/receivers (see above). Each will deliver signal eight times more effective than an AM set drawing same power. (In regular AM equipment the carrier wave absorbs most of the power and carries no message. So Hammarlund SSB sets transmit the message signal along narrow sideband with no carrier wave.)

IT WORKS

How it works. Hammarlund's SSB sets free themselves from conventional AM interference because they use only half frequency space. They cut distortion because they depend on rigid relations between phase and amplitude. Talk is private because Hammarlund SSB sets can't usually be picked up by home-style shortwave receivers.

IDEAL FOR GOVERNMENT AND INDUSTRIAL OFFICES

When normal telephone lines aren't available or wanted, Hammarlund SSB takes over. The CSB100TR works on mountains, in spots remote from its antenna, in installations where several dispatchers are working separately and can use the 10A Telephone Remote Control units providing up to 20 control points. The CSB125C, less expensive, works when dispatcher, antenna and set are in one location.

This means Hammarlund SSB sets work beautifully in out-of-the-way locations for government, maritime, forestry, airline, police and offshore oil installations.

FITS THE NEED

One antenna serves all six channels. Use handset, speaker or remote line. Phone or code. All simple controls on front panel. Just connect antenna, ground and plug in.

GO AHEAD AND WRITE

Mail this coupon for details on the 8-times more effective Hammarlund SSB sets.

HAMMARLUND MANUFACTURING COMPANY
A GIANNINI SCIENTIFIC COMPANY,
73-88 Hammarlund Dr., Mars Hill, North Carolina, 28754
Cable Address: ARLAB, New York, N.Y.

YES—We want to know about Hammarlund SSB.

NAME _____

WITH _____

AT _____

HAMMARLUND

SUPERPRO ENGINEERING IN EVERY SET

From 1910 to Tomorrow: Hammarlund Builds Commercial Communications Equipment
Variable Air Capacitors, Amateur Radio Equipment and the Outercom 2-Way Radio.

A New Approach to Phasing

This is not a blueprint for an exciter but rather, a collection of design ideas about phasing type SSB. You CAN design and build your own sideband equipment which will produce every bit as high quality signals as the store-bought kind. It may take a little time, but it saves cash and creates pride.

Glancing quickly at the basics of SSB, you will see that a balanced modulator is the heart of all single and double sideband exciters. The filter approach to SSB requires only a single balanced modulator, while the phasing method requires a dual arrangement.

The balanced modulator is the stage of the exciter in which an rf carrier (preferably not operating on the transmitted frequency) combines with the audio signal to produce sidebands minus carrier. It should be kept in mind that sideband is a type of AM, so don't be too rough on your Ancient Modulation friends. AM is referred to as A3 emission; SSB is A3j.

Have a look at the filter type exciters. They generate SSB on one frequency, usually crystal controlled, and heterodyne up or down to the operating frequency. This calls for a mixer stage following the balanced modulator. This is also good practice for the phasing exciters. A separate injection frequency provides much greater long-term stability to the rf phasing and the carrier nulling.



Top view of transmitter.

In building any exciter, filter or phasing type, there must be incorporated some special component. In the filter rig it's a mechanical or piezo crystal filter; in the phasing rig there is an R-C ninety-degree audio phase shift network.

The 90° audio phasing system about to be described was designed around the concept of using only standard off-the-shelf components. The results are extremely gratifying. Unwanted sideband rejection is ideal. Audio quality is good, comparable to the best on the market. The balanced modulator stays tuned up and nulled out for months of operation.

Before describing the phasing system, I would like to discuss the balanced modulator used with it. Fig. 1 illustrates a phasing type dual balanced modulator. Instead of using the expensive sheet beam tubes, this application calls for two economical dual pentode 6BU8's. The transformer windings L₁ and L₂ consist of pruned primary and secondary of an air core 455-kc *if* transformer, rewired as shown, and operating at 900 kc. The secondary, L₃, is about 150 turns

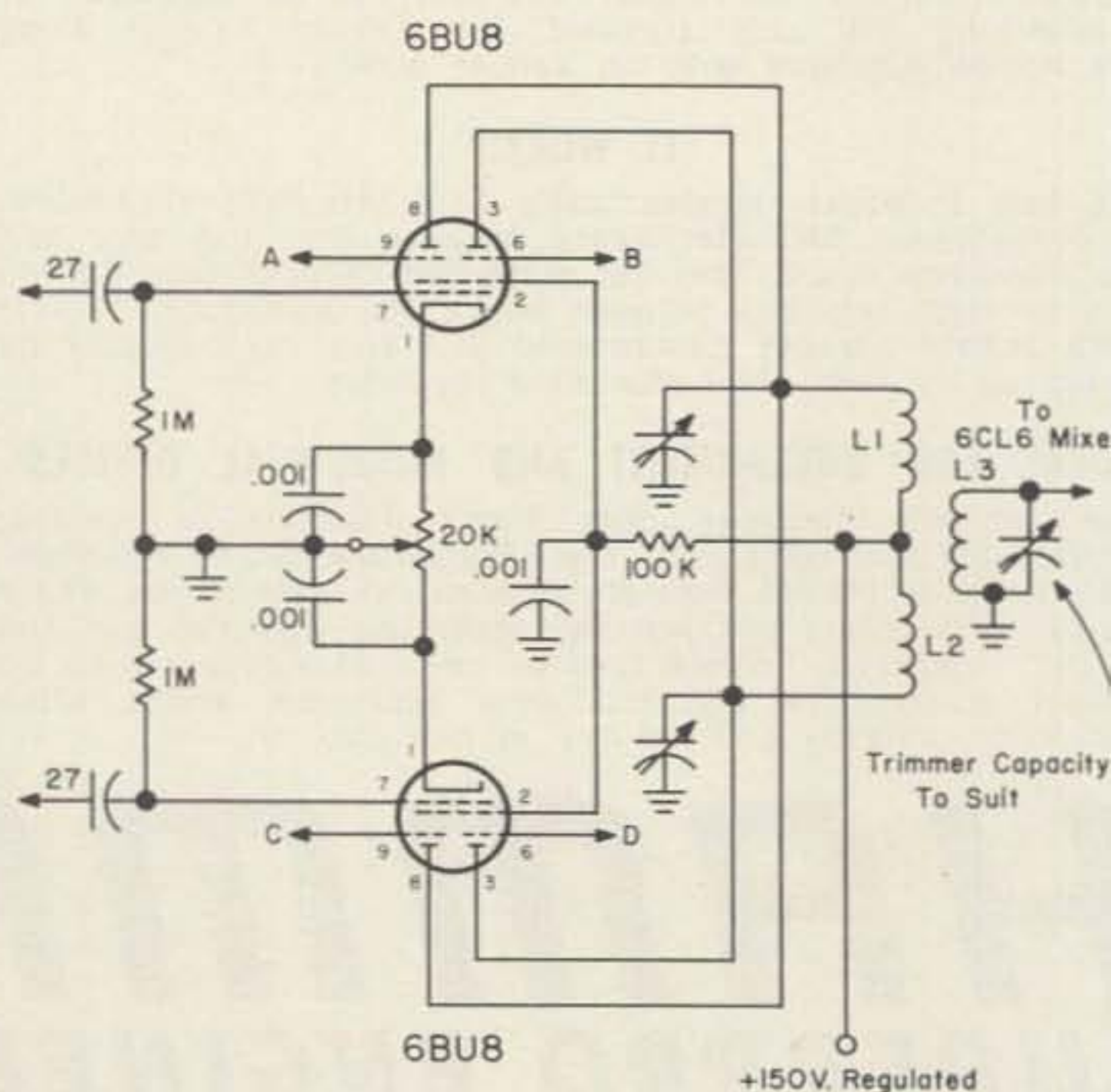


Fig. 1. 6BU8 dual balanced modulator

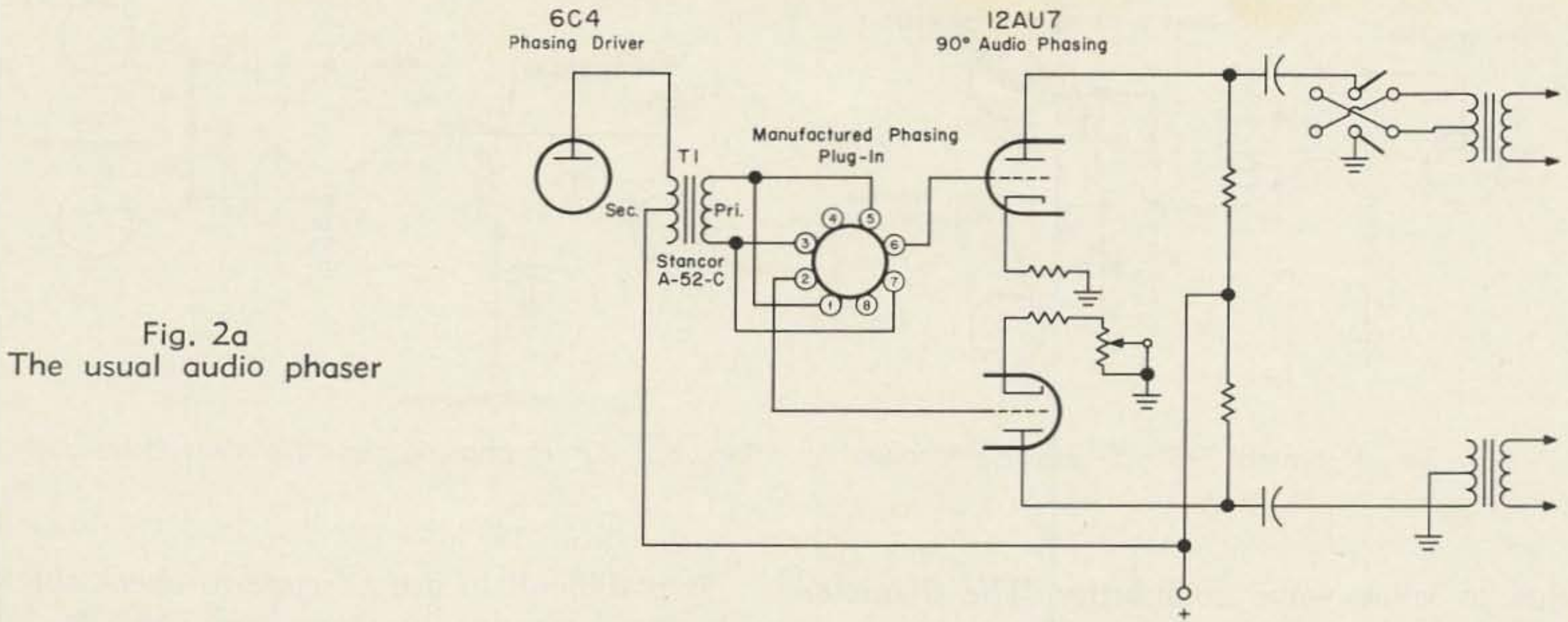


Fig. 2a
The usual audio phaser

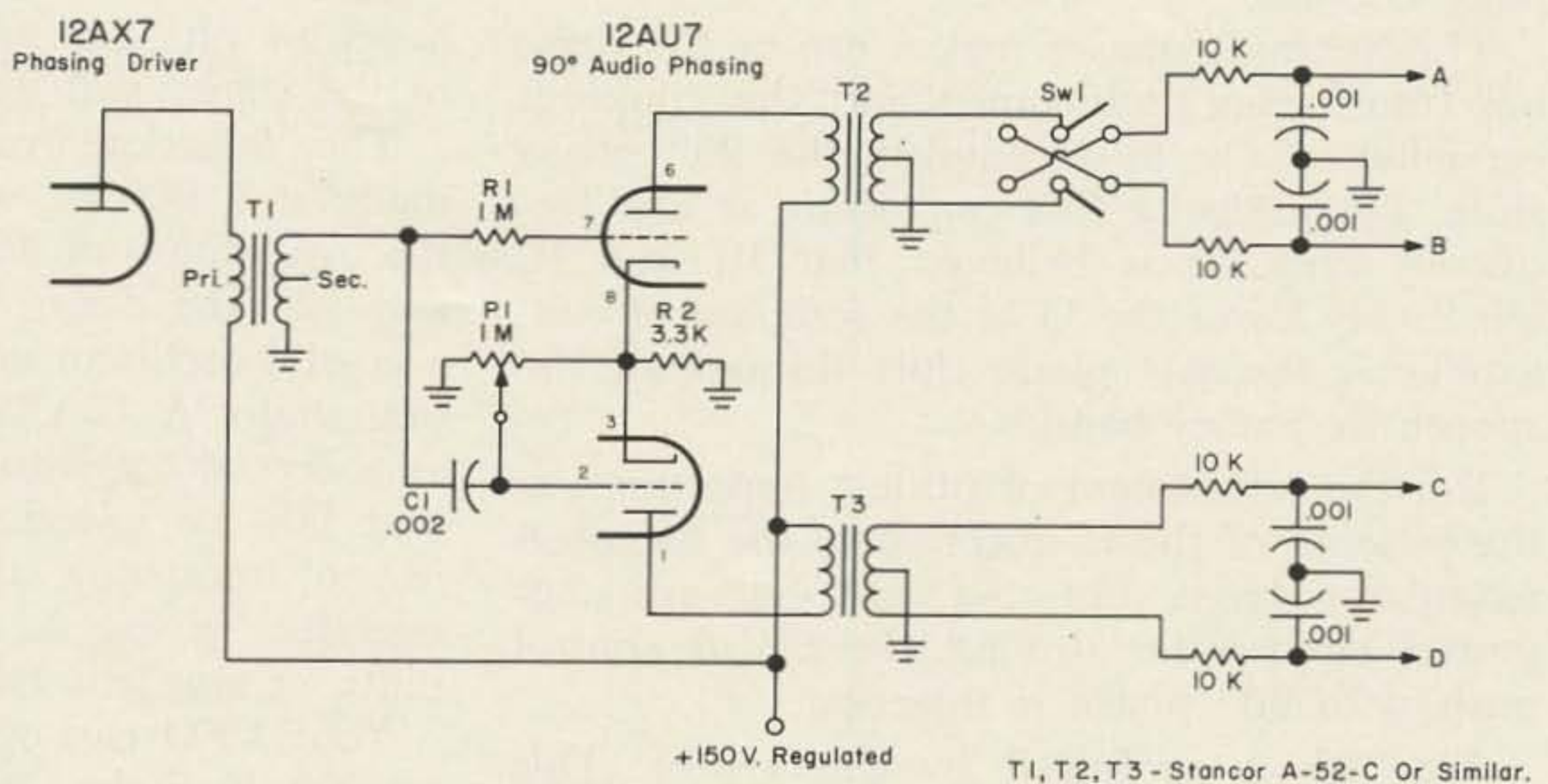


Fig. 2b
The Schmidt phaser


cramble wound Litz wire on the $\frac{1}{2}$ " diameter form between L_1 and L_2 . Ninety-degree phased audio is brought to the suppressor grids through leads A, B, C, and D.

Fig. 2-a is an audio phase shifter for driving a type of dual balanced modulator.* It uses a manufactured plug-in R-C 90° audio phase shift network. Fig. 2-b is the author's original 90° audio phase shifter for driving the balanced modulator of Fig. 1. It is called the Schmidt phaser (with due respect to the originator of the Schmitt trigger). Note that both phase shifters are triode driven and employ transformer coupling in and out. In both phase shifters T_2 and T_3 should be the same type, but do not have to be a matched pair. Any single plate to push-pull grid type transformers should work. T_1 , the Schmidt phaser input transformer should be a single plate to single or push-pull grid interstage type. The mic. preamp and phaser driver stages should pass little above 3,000 cycles.

The Schmidt phaser should be aligned with

a 'scope (sweep disabled). Referring to Fig. 2-b, vertical deflection plates connected to the plate of V_{1a} or V_{1b} and horizontal plates connected to the opposite triode plate. Or, if your 'scope is dc coupled, then connect one set of deflection plates to A or B and the other pair to C or D.

Drive the phaser with a sine wave signal of 800 to 1500 cycles, and adjust P_1 for the best circle throughout the audio band. Maintain the input below the distortion level. Try voice input. The pattern should resemble a lace doily

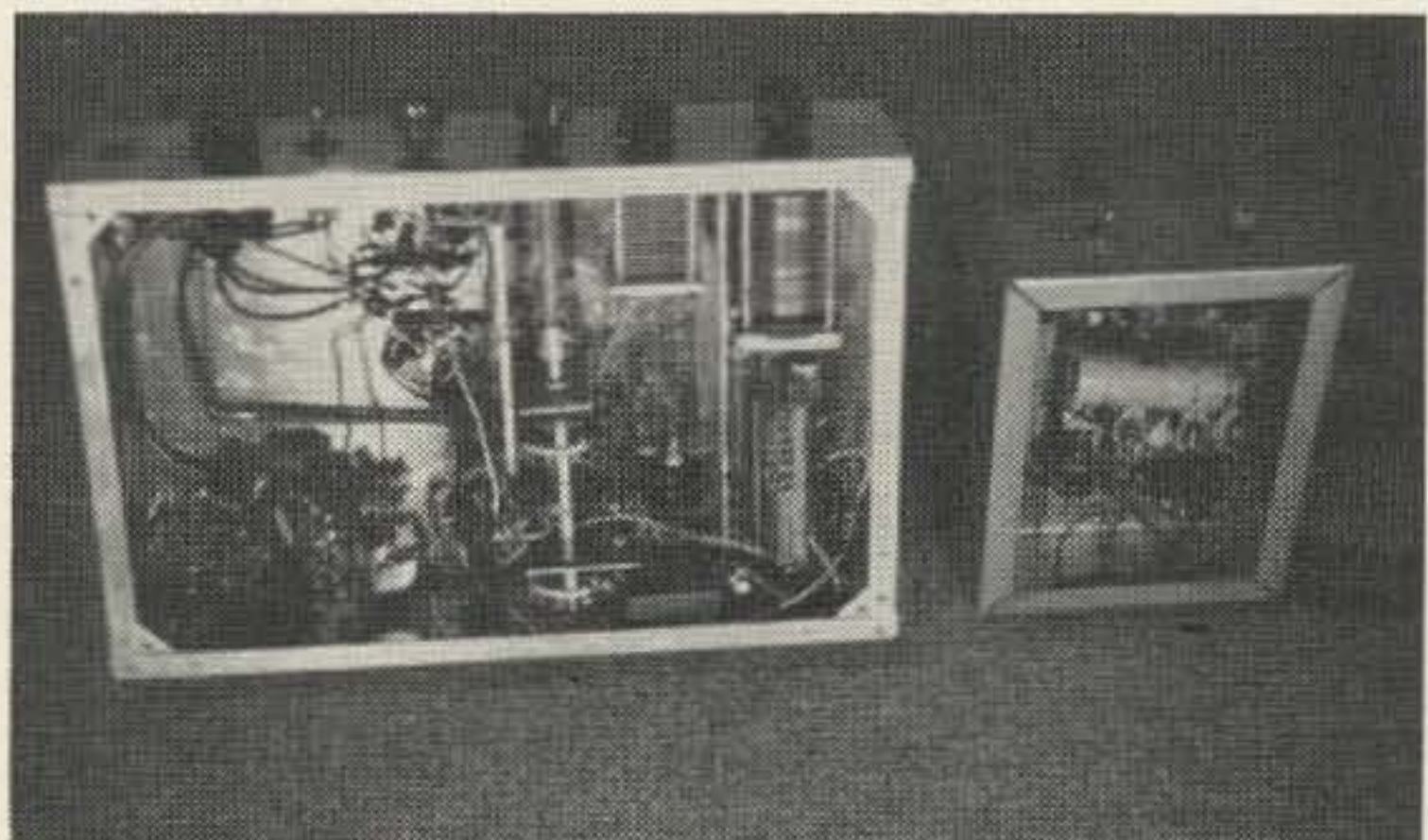

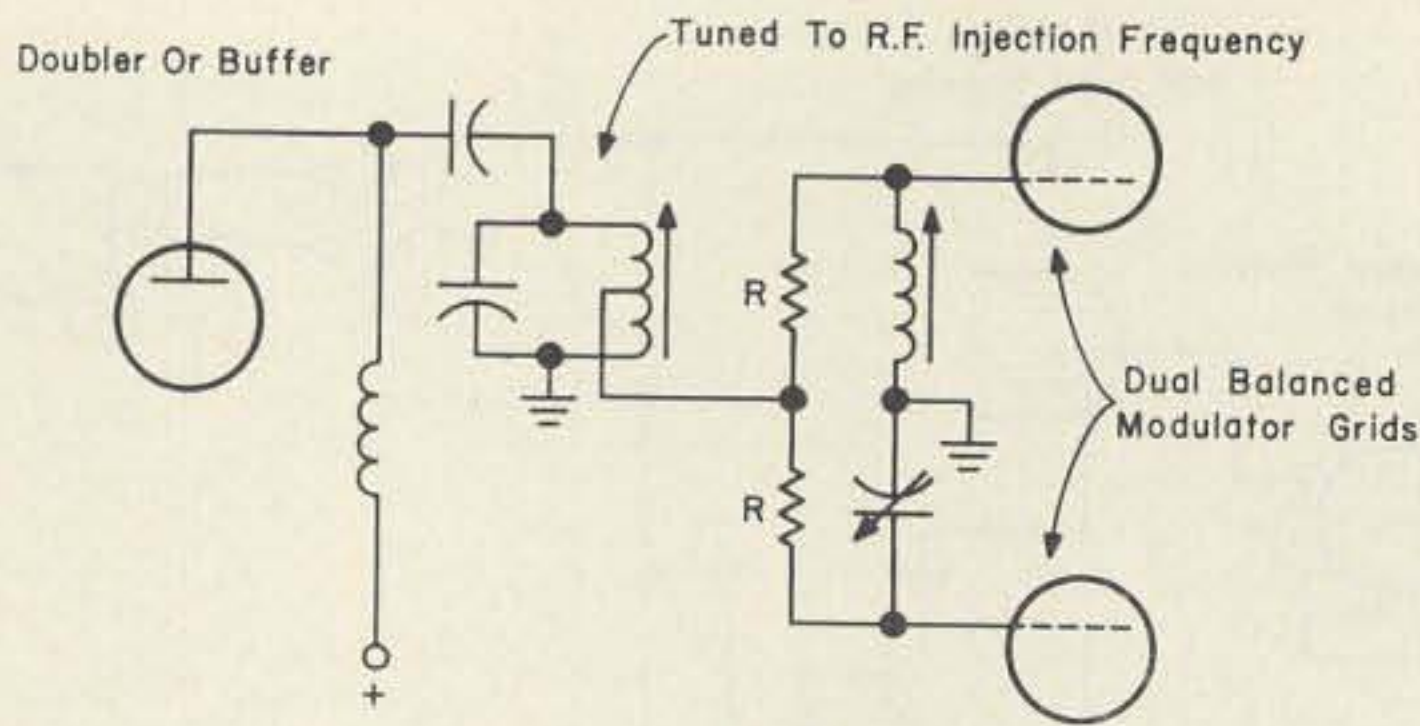


Fig. 3a. A typical 90° rf phasing circuit

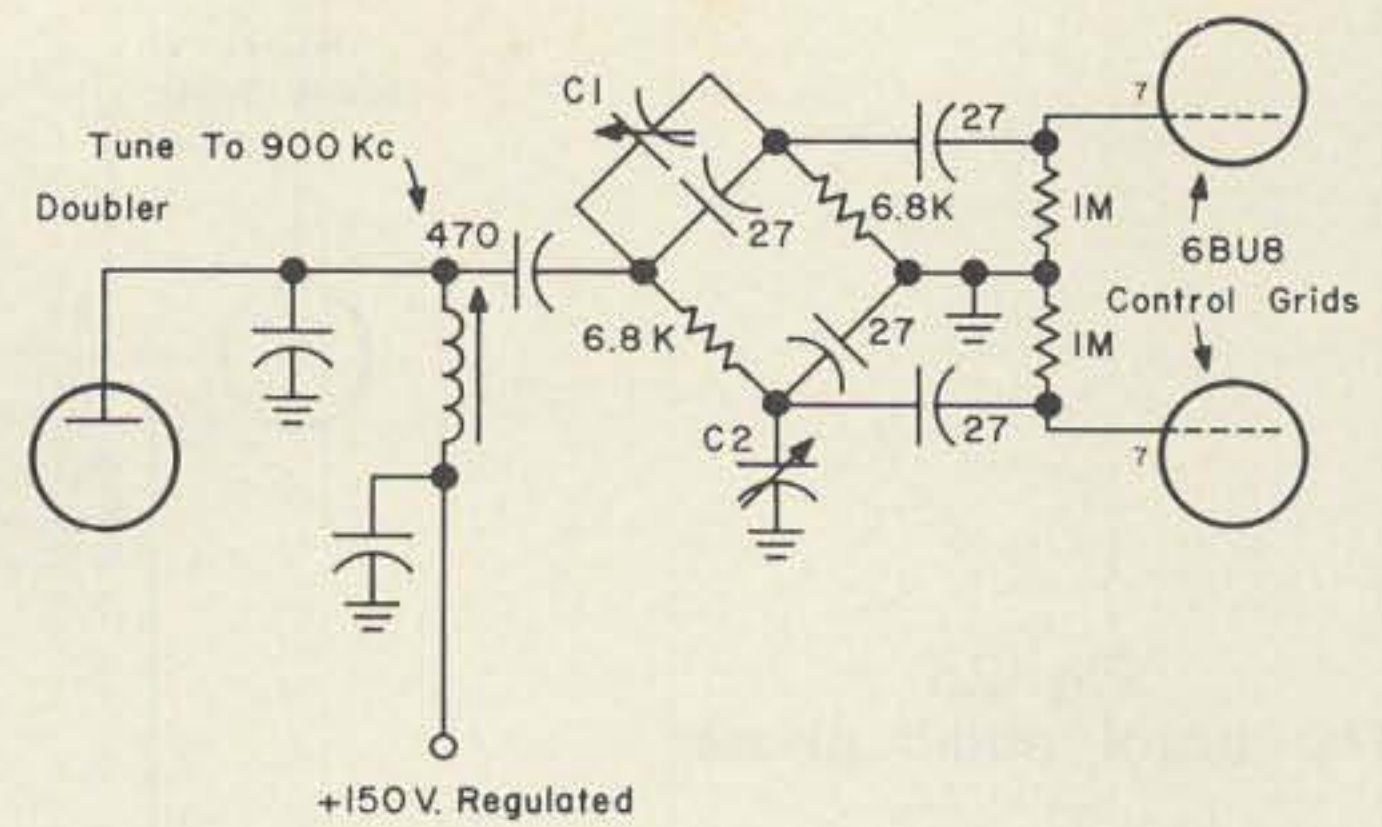


Fig. 3b. 90° rf phasing circuit preferred by author

due to voice wave complexity. The diameter will vary, but the pattern will remain essentially circular.

The Schmidt phaser makes use of the driving transformer inductance and the coupling capacitance, C_1 , to accomplish the 90° phase shift. Theoretically this can occur at one frequency only. It is believed that R_1 and P_1 effectively lower the Q of the resonant circuit, extending the 90° phase shift throughout the speech frequency band.

But the adjustment of utmost importance is the phasing of the rf injection to the balanced modulator stage. Fig. 3-a and 3-b are suggested circuits for driving the 6BU8 control grids with 90° phase rf injection.

Fig. 3-b is preferred by this writer. This is an R-C bridge used by Heath and others. C was chosen at 27 mmfd. Its capacitive reactance at 900 kc is close to 6700 ohms. Resistors, R , were 6800-ohm composition type. Two small ceramic trimmers, C_1 and C_2 , are in parallel with the phasing capacitors. Their purpose is to compensate for inequalities in resistance, stray capacity due to lead dress, etc. Coupling capacitors to the 6BU8 control grids are 27 mmfd. Grid leak values are 1 megohm.

It is difficult to use a 'scope to check the rf phasing here due to stray lead capacity between the exciter and the 'scope. But the rf injection phasing *must* be very close to 90° or the signal will not be clean.

The injection frequency to the balanced modulator, 900 kc, was chosen because of (1) the availability of 450 kc crystals at 10c each, and (2) the desire to use one dual triode as a crystal oscillator and an un-neutralized isolation stage. A 12AX7 fills the bill by working as a crystal oscillator and doubler. It happens that 900 kc injection also produces a higher image frequency after mixing than 450 kc injection, giving an added bonus of less possibility of spurious emissions being transmitted.

Your VFO can operate either 900 kc above or 900 kc below the desired operating frequency. Sidebands are switched by Sw_1 , Fig. 2-b.

On the subject of mixing, it was desired to select a mixer tube which would render some conversion gain. (See Fig. 4.) A 6CL6 was chosen for this purpose. Its control grid receives the balanced modulator output, while the screen grid is driven from the VFO output (about 10 to 15 volts rf) superimposed on the normal screen grid dc potential. The mixer output then drives a 2E26 output Class-A amplifier directly without the use of any buffer stage.

In operating the exciter the microphone preamplifier and phaser driver 12AX7, the oscillator-doubler 12AX7, the Schmidt phaser 12AU7, and the balanced modulator 6BU8's all operate continuously from a 150-volt regulated supply. The 6CL6 mixer and the 2E26 output stage are supplied with 365 volts unregulated, continuously supplied also.

The two stages receiving the 365 volts are blocked-grid keyed. Blocking bias is obtained from a voltage divider to ground from either hot side of the power transformer. A point of the voltage divider feeds a single silicon diode

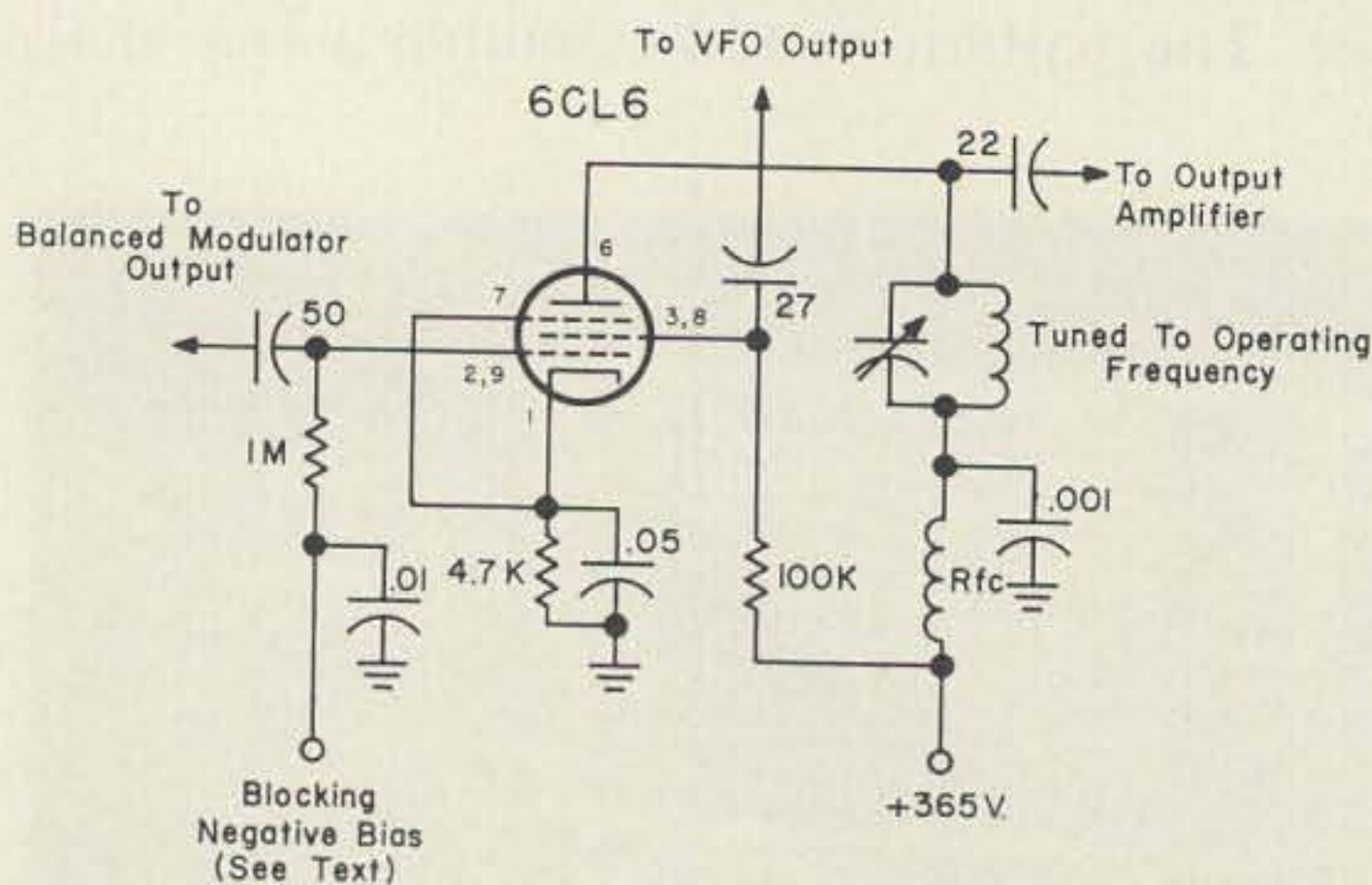


Fig. 4. Mixer with conversion gain

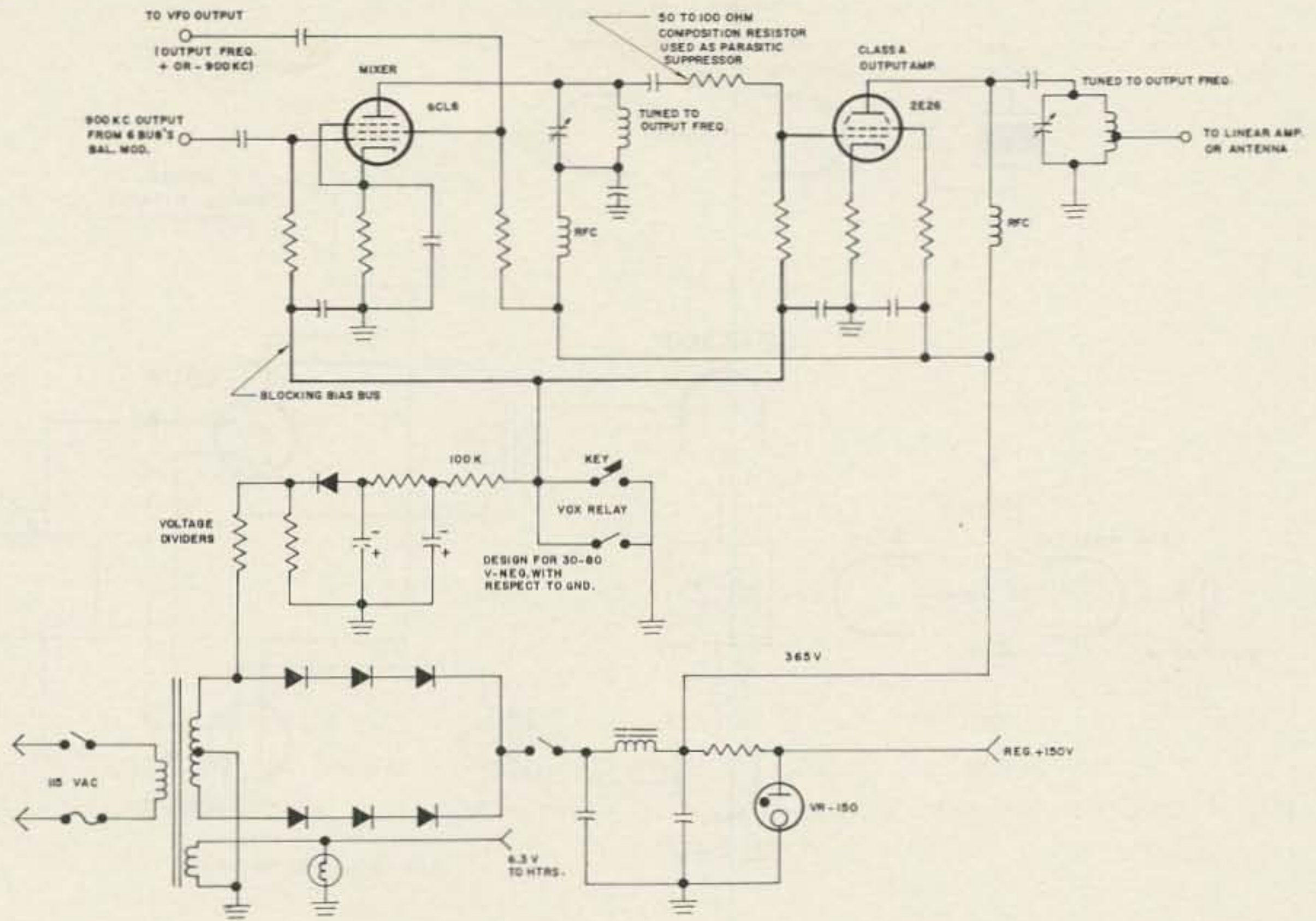


Fig. 5.
Blocked-grid
control system

and an R-C filter to produce 80 volts dc negative with respect to ground. (See Fig. 5.) This blocking bias voltage is fed to the grids of the stages to be blocked through a 100-K series resistor and thence through their respective grid resistors. The keyed stage grid leak resistors terminate in a common bus rf bypassed to ground.

Closing the key or VOX relay connected between the blocking bias bus and ground effectively short circuits the control grid's portion of the blocking bias, allowing normal grid leak bias to control tube emission. At the same time the bias supply is only grounded

through a 100-K resistor, so the supply feels only a very light load. As soon as the ground is removed from the keyed grid circuit bus, the negative bias on the grids skyrockets and blocks plate current flow. Some of the best modern factory-built equipment employs this ancient trick.

Block-grid keying is extremely fast and relatively clickless. Using this method, the key becomes a "push-to-talk" switch on sideband and a key on CW (with carrier re-inserted). If you already have VOX and prefer it, simply wire the VOX relay across the key contacts for the dual function. All of this control jazz

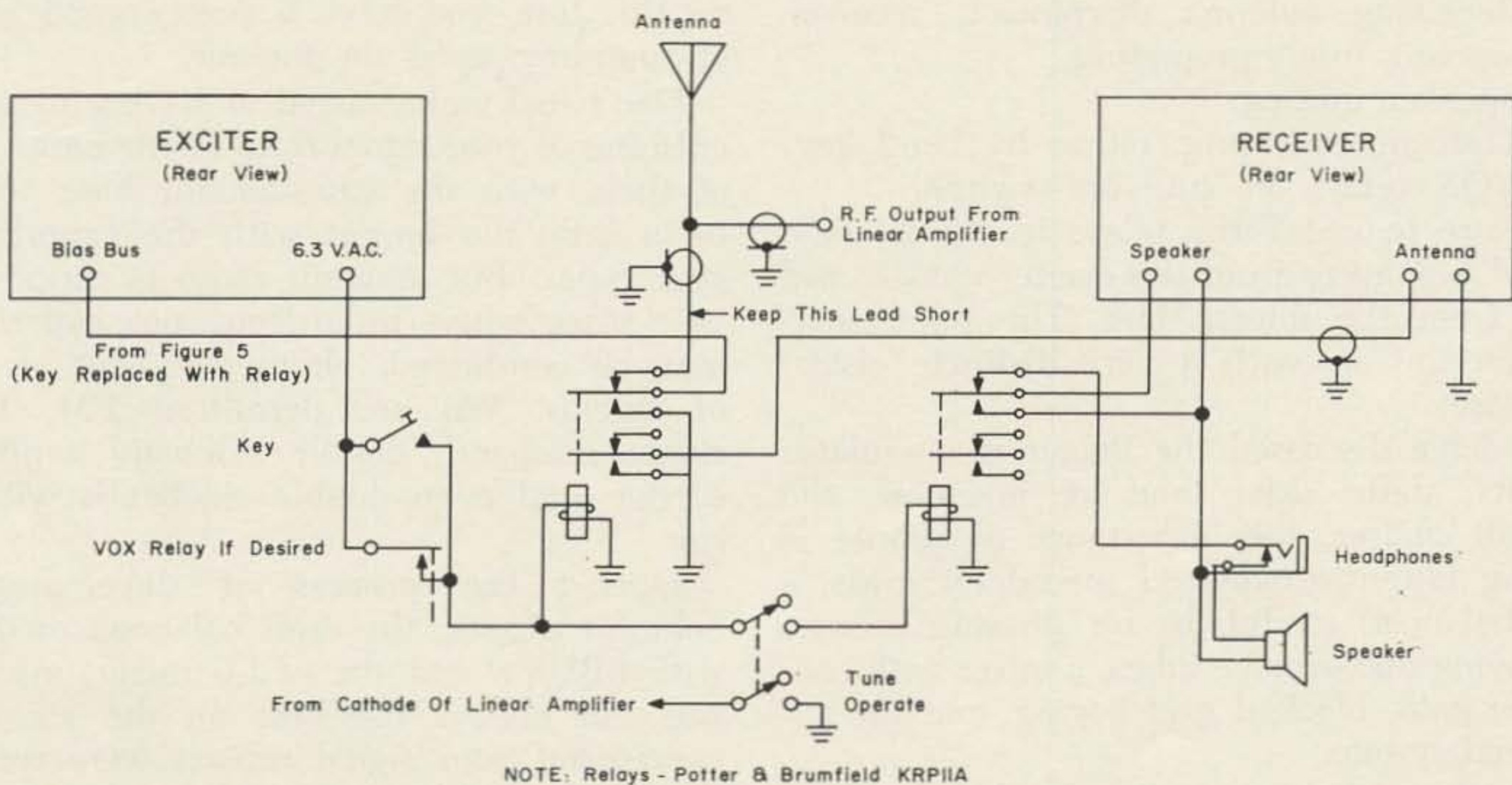


Fig. 6. The engineered system. The "tune-up-operate" switch allows you to talk yourself on frequency

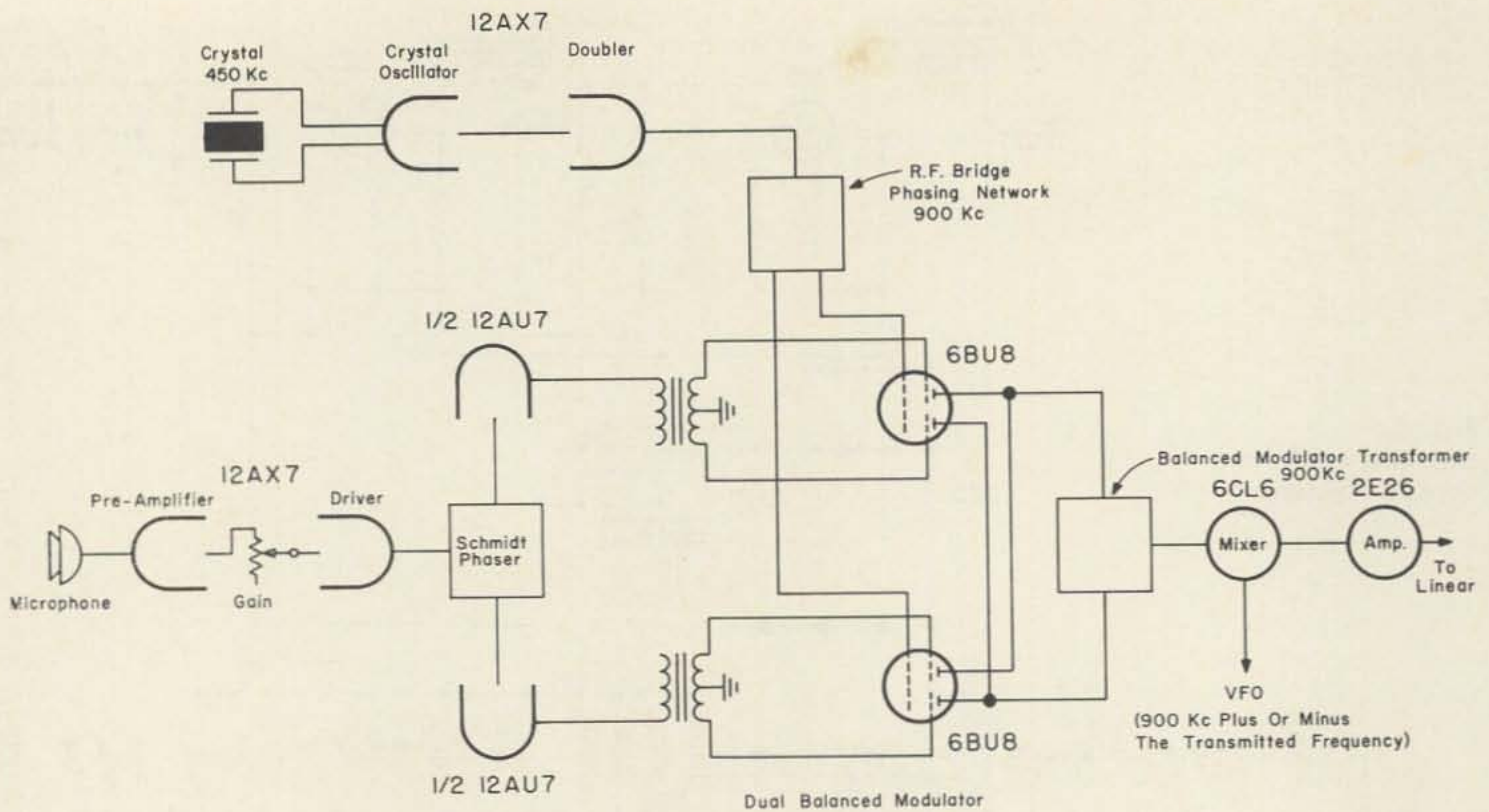


Fig. 7. Block diagram of W9IDP SSB exciter

is really what is referred to as "systems engineering," which means making the components in your station into an integrated "system."

In order to complete the systems engineering of the station layout, and some hams do encounter trouble in this department, the arrangement of Fig. 6 is suggested. A 6.3 volt filament lead is brought out from the power transformer to operate a pair of good quality 6-volt ac relays. These will key well up beyond 25 wpm, so have no fears about CW unless you operate 50 to 60 wpm.

The control functions to be accomplished by the relays are:

1. Receiving antenna disconnect; receiver antenna input grounding.
2. Speaker muting.
3. Transmitter keying, either by hand key, VOX relay, or "tune-up" switch.

Be sure to install the relays inside of some kind of box away from the exciter chassis and away from the microphone. The relay snap goes on the air with a very distinct "clack" otherwise.

We have discussed the balanced modulator and its audio drive and rf injection, the Schmidt phaser, the importance of proper rf phasing into the balanced modulator grids, a dual balanced modulator for phasing exciters employing inexpensive tubes, a mixer with conversion gain, blocked grid keying, and the engineered system.

If nothing else is remembered, let one thing sink in. That is this. The rf injection to the

balanced modulator must have as good 90° separation as it is possible to attain.

Use a good SSB receiver to adjust your transmitter before going on the air. A well shielded receiver with antenna input grounded can tell you a whole lot about your signal. First give a listen on the frequency. (Some hams are sensitive about people who test before listening.) Then ground the receiver antenna input with a very short wire, and make a short transmission with the rf gain of the receiver backed all the way down and the antenna trimmer rotated for minimum signal. Use the cans for this test. If the quality of your signal sounds good on this test, you have a pretty good chance of sounding good on the air.

Don't feel embarrassed at having to ask for criticism of your signal from fellow hams. Some of them with the store-bought kind tend to be a little too honest with the experimental gear types. But amateur radio is supposed to be a place where radio frequency experiments may be conducted. Hams can emit all types of signals. We are permitted FM, RTTY, single sideband, double sideband suppressed carrier, and even double sidebands with carrier.

During the process of developing the Schmidt phaser, the dual balanced modulator with 6BU8's, and the 6CL6 mixer, my signal was not always the best on the air. When concurring poor signal reports were received, though, I tried to do something about it. This is it, and I think you'll like it. . . . W9IDP

IT'S THE SAME LITTLE OLD BOX



1962 SWAN SINGLE BANDER —
1 BAND — 180 WATTS — \$275



1963 SWAN 240 — 3 BANDS — 240 WATTS — \$320

but we've put a **LOT MORE** *in it!*



NOW THE **SWAN-350** TRANSCEIVER 5 BANDS — 400 WATTS AND ONLY \$395

- 3.5 - 4.0 mc, 7.0 - 7.5 mc, 13.85 - 14.35 mc, 21.0 - 21.5 mc, 28.5 - 29.0 mc (10 meter full coverage kit available.)
- Transistorized VFO, temperature and voltage stabilized.
- Precision dual-ratio tuning.
- Crystal lattice filter.
- ALC . . . AGC . . . S-Meter.
- 5½ in. high, 13 in. wide, 11 in. deep.
- 400 watts SSB input
320 watts CW input
125 watts AM input
- Sideband suppression: 40 db
Carrier suppression: 50 db
Third order distortion: 30 db
- Lower sideband on 80M and 40M.
Upper sideband on 20M, 15M, and 10M.
(Opposite sideband kit available.)

WITH THE SAME RELIABILITY AND PERFORMANCE
WE'VE PUT IN ALL OUR LITTLE BOXES

ACCESSORIES:

- AC power supply, matching cabinet with speaker. Model 117-C.....\$ 85
- 12 Volt DC Power supply. Model 412.....\$130
- Plug-in VOX. Model VX-1.....\$ 35

SEE THE NEW SWAN 350
AT YOUR DEALER'S NOW!



ELECTRONICS CORP.
Oceanside, California

Bill Brown WØSYK
 28 Marine Lane
 Hazelwood, Mo.




The Big Bomb

The final of this transmitter started back in 1957. After running a kw with TW150, T200 and 250TH's I went out and bought a new 4-1000A and tried to put it in class C. After a year of confusion I gave up and put the final under the work bench. However, at the National Convention the following year a talk by Rex Bassett W4QS on the ground grided 4-1000A fired me up and once home I started changing my final from class C to class B.

I knew little about driving this tube so with 3000 volts on the plate could not load

up to a kw input. Several months later after building a final using four 811's, and doing very nicely, I thought of using the same match with the 4-1000A as with the 811's. Dividing the 100 ohm impedance of the 4-1000A would give me 50 ohms output to 50 ohm input. For those who are thinking this final would exceed the legal power, let me remind you that any grounded grid linear's output is directly proportional to the drive so without a buffer stage this final will run the same output as a single 4-1000A.

The Big Bomb

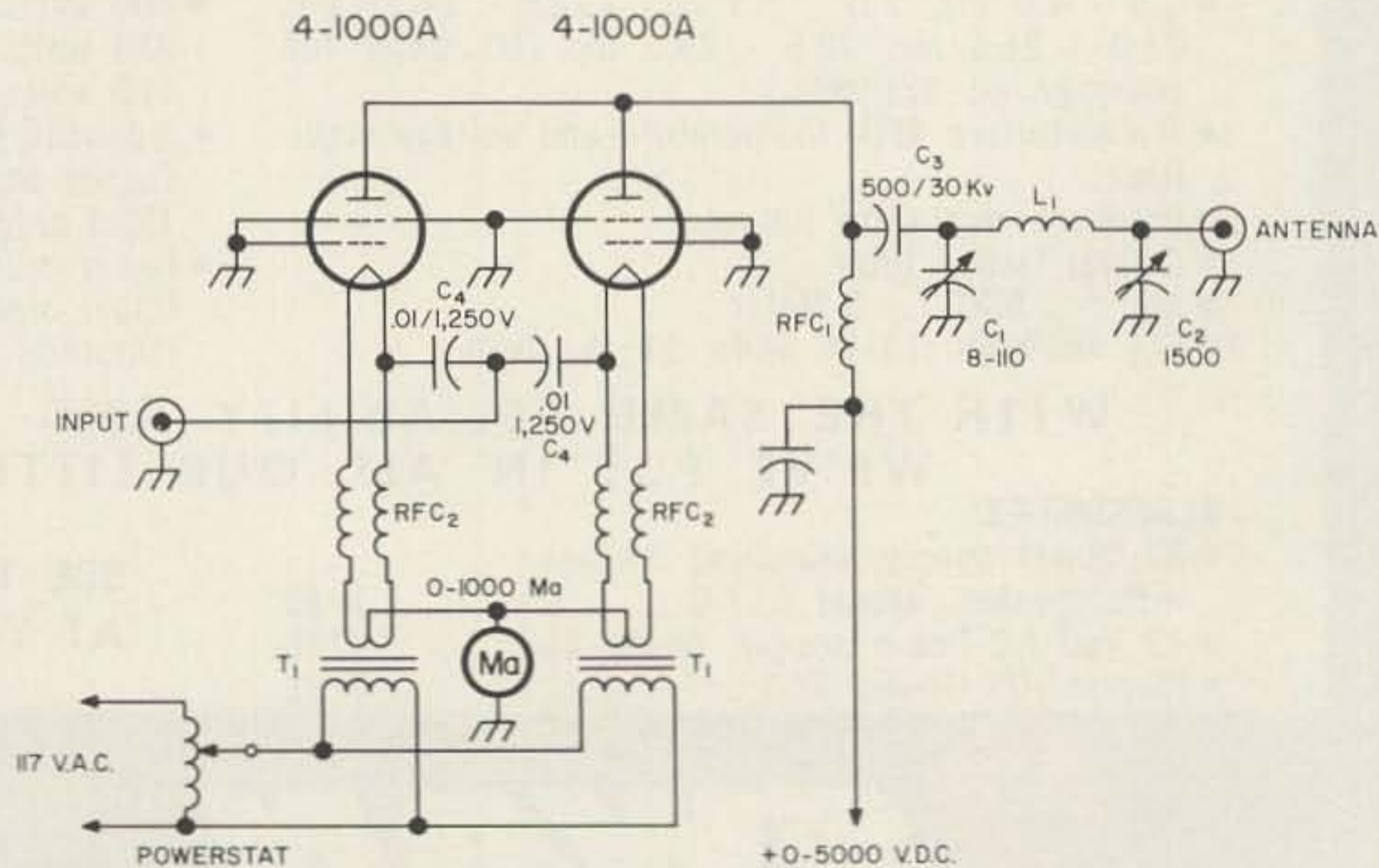

Two tubes will permit the operator to coast along at low voltage without any tuning of the grid and without a matching transformer to get the desired kw input. Who knows how many years these tubes will rest at this voltage and current. As the photo shows there is a Powerstat which changes the dc voltage and my checks show it is not necessary to run these tubes (one or two) at 5000 volts to get maximum efficiency. With a plate voltage of 3000 volts, an efficiency of 70% has been checked. Other advantages include the following; no grid circuit, no neutralization, rapid band change (plate circuit only), no relay as plate voltage on at all times, making more desirable for remote operation since no screen and grid voltage are required. No danger of overloading capability of tubes with excellent linearity and stability. Photo also shows Powerstat on filaments which used with care can prolong the life of tubes. (Play radio engineer: bring the filament voltage up slowly and maintain the required filament voltage. Let the tubes cool off slowly after use.) The driving requirement matches perfectly the exciters now on the market; HT32, HT37, 32S3, 200V etc.

The circuit is very basic. Just parallel the plate and filament leads. Five meters are used reading from left to right; Grid & Screen 0-500 ma, High voltage 0-5000 vdc, RF output 0-8 amp., Filament voltage 0-15 vac., Plate current 0-1000 ma.

I desired maximum efficiency so I chose single band operation. Changing bands can be accomplished in seconds with separate coils. The power supply is a standard bridge using 4 872's. Since completion of the rig I have also tried solid state rectifiers using the Westinghouse silicon rectifier Oz-Pak for the past five months with fine results. The plate transformer is a 5 kva pole pig (7200 vac) bought through the power company most reasonably. It is controlled by a Superior Powerstat with a rating of 28 amps. The cabinet is by Par-Metal using 30" panels. Filter condensers are 2 GE 120 μ f @ 3000 volts. In series they give 60 μ f at 6000 vdc. Chokes are in the negative lead and improved regulation is achieved by using swinging and smoothing chokes in series. Without parasitic chokes in plates leads the final was stable with voltage up to 6000 without any signs of taking off. My driver is a 32S1. I run 3500 volts for legal input knowing that I should be in business for many many years without tube failure or other types of breakdowns.

. . . WØSYK

LATEST "HOW-TO-BUILD" DATA



You get it in the world-famous RADIO HANDBOOK

- New Amplifier Designs
- New Transmitter Designs
- New Receivers & Transceivers

For Builders & Designers of Practical Equipment—The best source book available. Gives you a complete understanding of the theory and construction of all circuitry, transistors & semiconductors, antennas, power supplies; full data on workshop practice, test equipment, radio math and calculations. Provides latest design and construction data for building a wide range of advanced Ham equipment, including 10 amplifiers, 4 transmitters, 5 receivers and transceivers. Broadest "how-to-build" coverage available. Completely revised and up-to-date. Fully indexed. 805 pages; illustrated; hardbound. Invaluable for amateurs, builders, engineers, and designers.

Book No. 166 At your distributor **\$9.50**
(foreign \$10.50)



RADIOTELEPHONE LICENSE MANUAL

*easiest way to prepare
for the license exams*

Here is the complete help you need to prepare for and pass all U.S.A. commercial radiotelephone operators' license exams. Includes comprehensive study-guide questions and answers in a single, easy-to-understand volume. Helps you grasp and master every subject you are required to understand and know in order to obtain an operator's license.

Book No. 030 At your distributor **\$5.75**
(foreign \$6.25)

ORDER FROM YOUR ELECTRONIC PARTS DISTRIBUTOR

If he cannot supply, send us his name and your remittance and we will ship.



EDITORS and ENGINEERS, Ltd.

New Augusta, Indiana

Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers, order from Baker & Taylor Co., Hillside, N.J. or Momence, Ill. Export (except Canada), order from H. M. Snyder Co., 440 Park Ave. South, New York 10016.

...and for twice the power from Mobile Communications Equipment,
without radical design changes, there's the new AmpereX 8458



If the world renowned Amperex 6360 is—as virtually all designers of mobile communications equipment agree—a truly great tube, its new derivative, the Amperex 8458 is an even greater one! For in addition to the great performance, great low-profile convenience, and great reliability of the earlier twin tetrode, the new 8458 can be counted on to deliver 30 watts of useful power at 175 Mc from less than 1.2 watts of drive power.

To drive the 8458, Amperex has developed a second new twin tetrode, the 8457, a 13.5 volt heater version of the 6360. It is ideally suited for use as a cascaded doubler-multiplier, driving the 8458 as a straight-through amplifier in the 150-175 Mc band. This combination of new Amperex tubes provides extremely stable power output under low voltage conditions, since more than sufficient drive is available. Because the profile heights of these two new tubes are identical with the older 6360, modification of existing circuit designs can be made with resulting improved power and performance.

Both tubes incorporate a 13.5 volt center-tapped heater; are internally neutralized and have indirectly heated oxide-coated cathodes.

8458

SIGNIFICANT CHARACTERISTICS CLASS C RF AMPLIFIER AT 175 Mc

	CCS	ICAS
DC Plate Voltage	400	450 volts
DC Grid No. 2 Voltage	155	200 volts
DC Grid No. 1 Voltage	-59	-50 volts
DC Plate Current	85	110 ma
Useful Power Output	20	30 watts
Drive Power	1.0	1.2 watts

Both the 8457 and 8458 are immediately available in production quantities from stock. For complete data on these and other Amperex tubes for mobile communications applications, write: Amperex Electronic Corp., Tube Division, Hicksville, L. I., New York 11802.

Amperex®

IN CANADA: PHILIPS ELECTRON DEVICES LTD., TORONTO 17, ONT.

Two for Two

Here are two easy-to-build antennas for two meters. Either can be used for fixed or mobile operation, but I prefer the 'J' on the car, and the coaxial (or sleeve) antenna on the house.

The J is popular for mobile operation here in California. One drawback to the antenna is that it can sometimes be difficult to construct and cumbersome in appearance. The W6TKA-J eliminates those problems. The mounting for the J consists simply of an aluminum bracket bent in the shape shown in the drawing and photograph, with a UHF-type coaxial panel connector mounted on the bracket. The bracket is held in place just inside the trunk lid by two sheet metal screws. A single hole through the lip of the trunk opening takes care of the RG-59/U cable running to the transmitter. Thus, no noticeable holes have to be drilled in the car to mount the antenna. Also, please note that this J is fed directly at the base with coax, and not at a 300-ohm point through a bulky balun.

It might be well to explain that the J is nothing more than a half-wave antenna fed with a quarter-wave matching section, consisting of the lower 19-inch section with the longer element spaced something less than



W6TKA-J Mounted on Car

two inches away. The J is *not* a three-quarter wave antenna, as I have occasionally heard it described. The lower 19 inches of the element that becomes the antenna and the second, grounded 19-inch section, do not radiate. As a matter of fact, if the long radiating portion of the antenna were bent at a 90° angle to the matching section, you'd have the old-fashioned "end-fed Zepp."


The antenna is built around a PL-259 UHF-type coaxial connector. Both elements are 1/8 inch half-hard brass rod, available from almost any metal supply house. Dimensions for the two elements are given in Table I.

The long piece of rod must be carefully filed until it will slip into the pin of the coaxial connector. The filed end of the rod and the inside of the connector pin are then tinned, and the rod "sweated" into place. Do not force the rod into the connector or the connector insulation may fracture.


Next, the shorter element is prepared. Make a 90° bend 2 1/4 inches from one end of the rod.

TABLE I
 "J" Antenna Dimensions


Frequency, Mcs	Length, In., Short Section after bending	Length, In., Long Section above connector
144	19 1/4	38 1/2
145	19 1/8	38 1/8
146	19	38
147	18 3/4	37 3/4
148	18 5/8	37 1/2

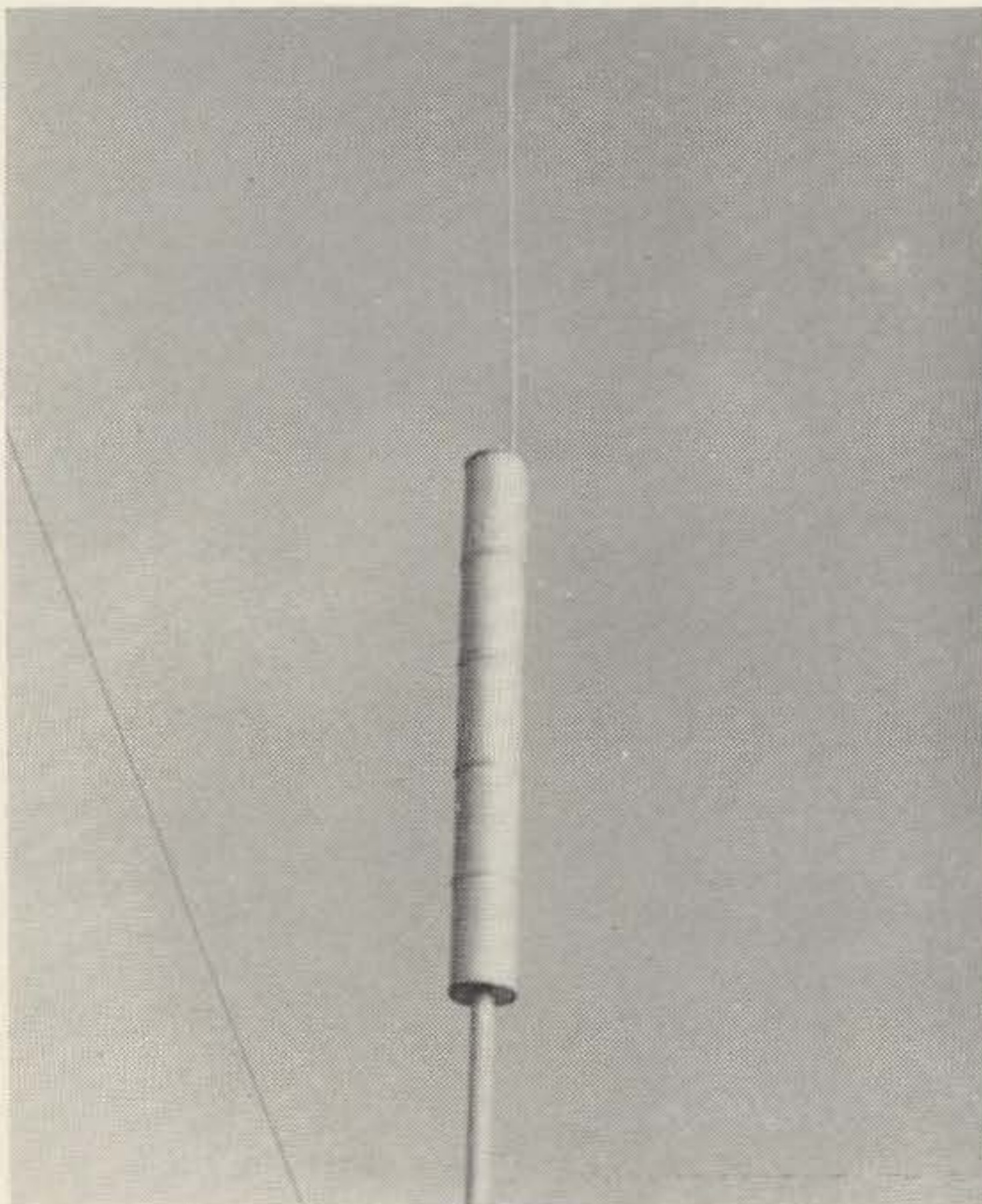

Completed Coaxial Antenna

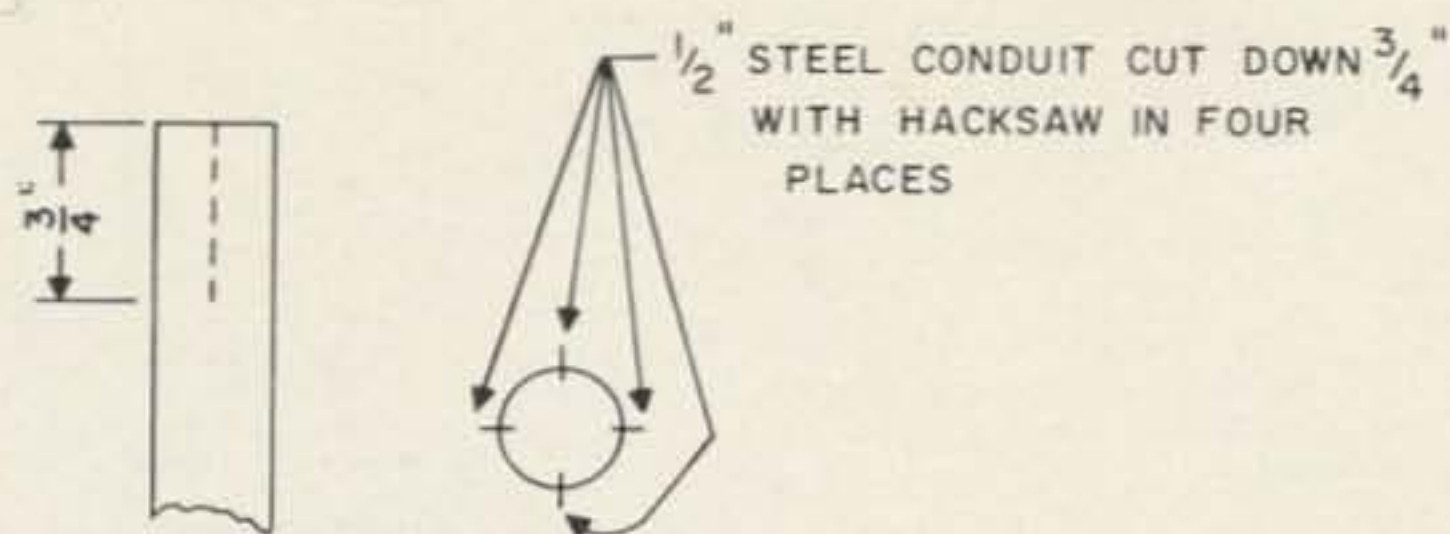

FOLD OUT AND HAMMER
FOLDED PORTIONS FLAT

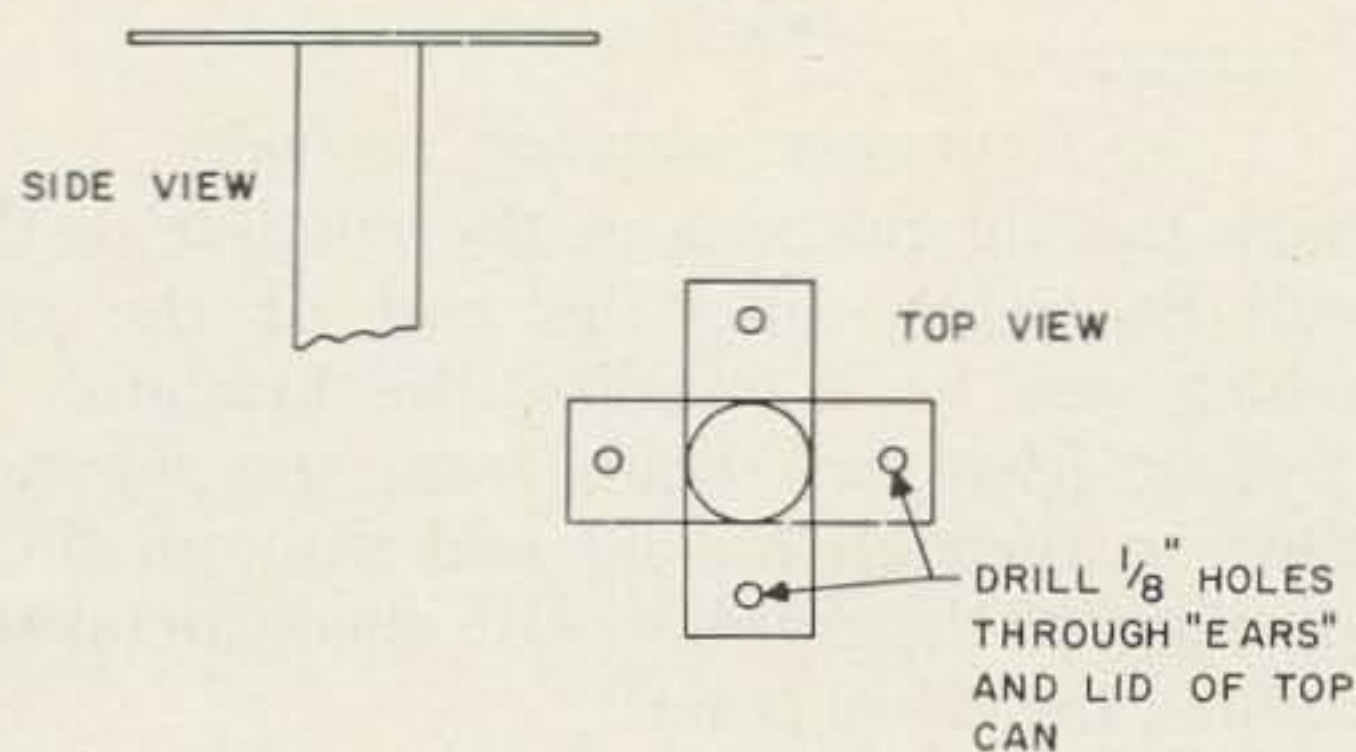

DETAIL OF END OF CONDUIT PREPARATION
FOR MOUNTING COAXIAL SLEEVE. REFER
TO TEXT.

See Table I for the correct rod length. Then bend the last $1\frac{1}{4}$ inches of the $2\frac{1}{2}$ inch section into a semi-circle of the same inside diameter as the outside diameter of the upper portion of the connector. Tin both the upper part of the connector and the loop that you have formed, and solder into place. At this point the shorter element will be spaced between $1\frac{1}{2}$ and $1\frac{3}{4}$ inches from the longer element.

The upper part of the connector is now packed with small pieces of polystyrene foam, taking care to keep the antenna centered within the plug. Then, when the foam has been tightly tamped into place, use polystyrene cement to dissolve the plastic. When dried, you will have a low-loss insulator which will keep the antenna centered in the plug.

To maintain the correct spacing between the elements over the entire length of the shorter element, a piece of plastic rod the same length as the spacing between the elements (as measured just above the connector) is placed near the top of the shorter element. In our case we used a plastic spreader taken from 450-ohm TV open-wire line. About $\frac{3}{4}$ inch of the TV wire was left extending on both sides of the insulator, and the wires twisted around the two antenna elements, and then held in place with plastic electrical tape. As a finishing touch, the entire antenna (except for the insulator and the connector, which were masked with masking tape) was spray painted aluminum, and the plastic tips

TABLE II
Coaxial Antenna Dimensions
(Same dimensions apply to both sleeve
and radiator)

Frequency, Mcs	Length, In.
144	$19\frac{1}{4}$
145	$19\frac{1}{8}$
146	19
147	$18\frac{3}{4}$
148	$18\frac{5}{8}$


from an old "rabbit ears" indoor TV antenna were placed on the ends of the two elements.

The antenna is easily removed when garaging the car, and has little wind resistance. Best DX to date—with one watt output from the transmitter—was a station in San Diego, California, contacted while driving through downtown Los Angeles—a distance of some 100 miles.

Now for the coaxial vertical antenna. There we used frozen orange juice cans (yes, other flavors will work!), and soldered them together. Five cans, each $3\frac{3}{4}$ inches long, with both ends removed (except for the top can, which has one end left in) were used to make up the sleeve. Using tin shears, the lower can is trimmed so that the overall sleeve length corresponds to the dimensions given in Table II. One word of caution: not all frozen juice cans are steel. Some are aluminum—even within the same brand we found both metals being used—so choose the cans with care. If a can won't solder, chances are it is not steel.

A small ceramic feed-through insulator (E. F. Johnson No. 135-44) was installed in a hole drilled in the top can lid, and the center conductor of RG-59/u coaxial cable connected to the insulator stud. The braid of the coaxial cable is soldered to the inside of the top can.

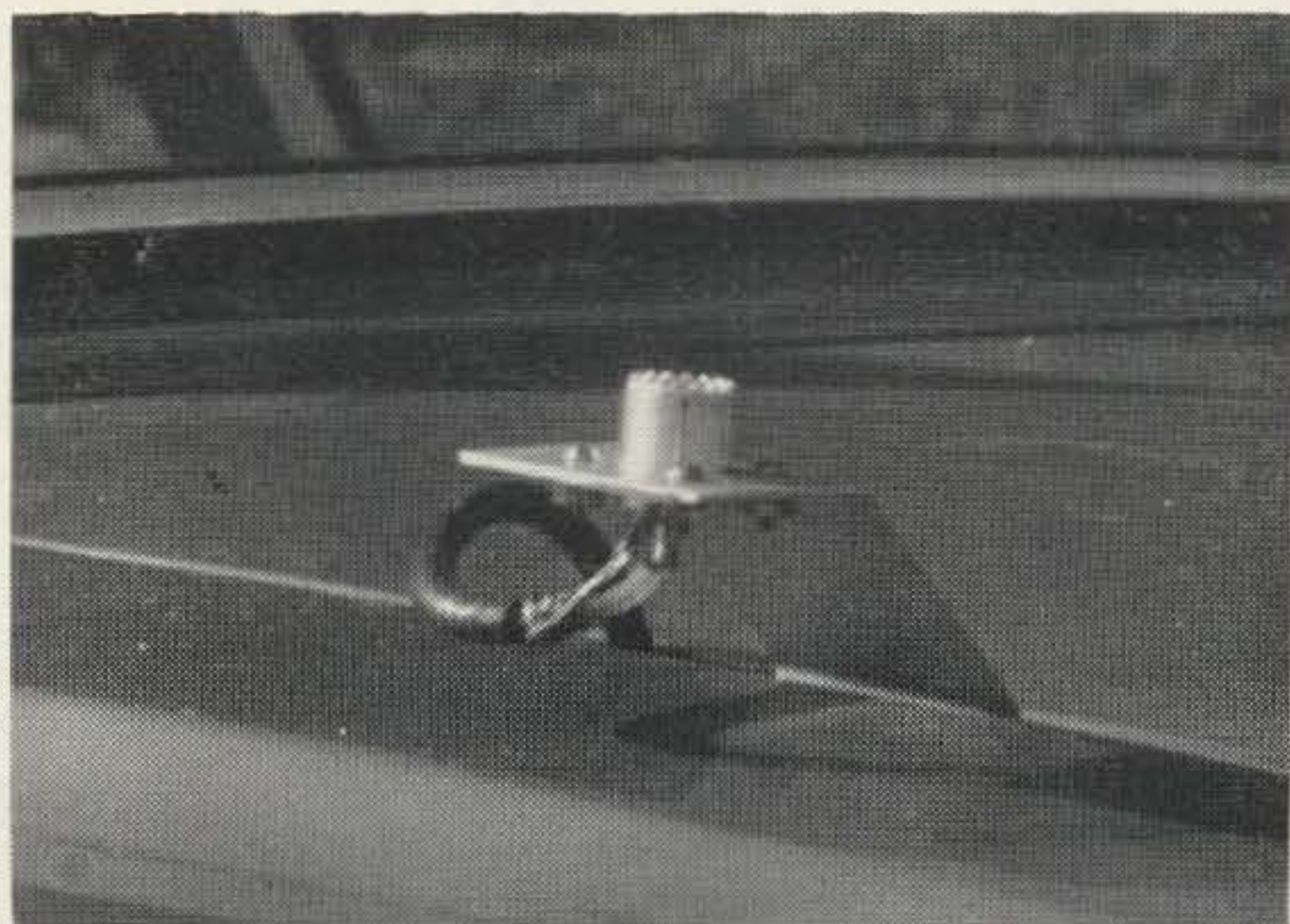Next, take a ten-foot length of one-half inch steel "thin-wall" steel conduit, available at hardware or electrical supply stores. Split one end using a hacksaw as shown in the sketch. Feed the coaxial cable down through the conduit and out the other end. Then fold




Mobile J Antenna Mounting Bracket

**These Distributors Have INSTANT LETTERING®
Dry Transfer Marking Kits in Stock**

- ALASKA**
Juneau Electronics
Juneau
- CALIFORNIA**
Yale Radio Electric Co.
Hollywood
Newark Electronics Co., Inc.
Inglewood
- ***Scott Radio Supply Inc.**
Long Beach
Alcom Electronics Supply
Mountain View
Brill Electronics
Mountain View
Brill Electronics
Oakland
Pencor Electronics
Palo Alto
Zack Electronics
Palo Alto
Electronic Components of
Pasadena
Pasadena
- ***R. V. Weatherford Co.**
Pomona
Zackit Corp.
Sacramento
Zack Electronics
San Francisco
Channel Radio Supply Co.
Santa Barbara
Midway Electronic Supply
Santa Monica
Sunnyvale Electronics
Sunnyvale
California Electronics Corp.
West Los Angeles
- CONNECTICUT**
Westconn Electronics, Inc.
Bridgeport
J. V. Electronics Co., Inc.
East Haven
Lafayette Radio Electronics
Groton
Radio Shack Corp.
New Haven
Bond Radio Electronics
Waterbury
- DELAWARE**
Delaware Electronics Supply Co.
Wilmington
Wholesale Electronics, Inc.
Wilmington
- DISTRICT OF COLUMBIA**
Capital Radio Wholesalers
Washington
Electronic Wholesalers Inc.
Washington
- FLORIDA**
Art & Engineering Supply Co.
Cocoa Beach
- HAWAII**
Pacific Electronics &
AIEA Electronics
Honolulu
- ILLINOIS**
Allied Radio Corp.
Chicago
***Newark Electronics Corp.**
Chicago
J & M Electronics Inc.
Rockford
- KENTUCKY**
Peerless Electric Equipment Co.
Louisville
- LOUISIANA**
EPCOR (Electronic Products
Corp.)
New Orleans
- MAINE**
Down-East Ham Shack
Lewistown
- MARYLAND**
Radio Electric Service
of Baltimore Inc.
Baltimore
***Wholesale Radio Parts**
Baltimore
- MASSACHUSETTS**
***Gerber Radio Supply Corp.**
Boston
***Radio Shack Corp.**
Boston
Doric Electronics, Inc.
Cambridge
Alco Electronics
Lawrence
- MISSOURI**
***Olive Industrial Electronics**
University City
- NEW HAMPSHIRE**
Evans Radio, Inc.
Concord
- NEW JERSEY**
Midstate Radio Supply
Berling
General Radio Supply Co., Inc.
Camden
State Electronics Parts Corp.
Hanover
- ***Federated Purchaser Inc.**
Springfield
Jackson Distributors
Trenton
- NEW MEXICO**
Electronic Parts Co., Inc.
Albuquerque
- NEW YORK**
***Arrow Electronics**
Farmingdale
Standard Parts Corp.
Hempstead
***Harrison Radio**
New York
Lafayette Radio Electronics Corp.
Syosset
Adelphi Electronics, Inc.
Westbury
- NORTH CAROLINA**
Southeastern Radio
Supply Co., Inc.
Raleigh
- OHIO**
***Hughes-Peters Inc.**
Cincinnati
***Pioneer Electronic**
Cleveland
***Thompson Radio**
Columbus
Whitehead Radio Co.
Columbus
The John A. Becker Co.
Dayton
Lima Radio Parts Co.
Lima
Hillebrand Electronic Supply
Toledo
Electronic Supplies Inc.
Toledo
Armies Electronics
Youngstown
- OREGON**
***H. & R. Radio Supply**
Portland
United Radio Supply
Portland
- PENNSYLVANIA**
A. A. Peters, Inc.
Allentown
Radio Electronic Service Co.
of Lehigh Valley Inc.
Allentown
Cumberland Electronics Inc.
Carlisle
***Commercial Blue Print**
& Supply Co.
Erie
***J. V. Duncombe Electronic Corp.**
Erie
Kass Electronics Dist. Inc.
Havertown
A. C. Radio Supply Co.
Philadelphia
Penn Electronic Parts Co.
Philadelphia
Simco Electronics, Inc.
Philadelphia
Techni-Tool, Inc.
Philadelphia
Cameradio Co.
Pittsburgh
The Tydings Co.
Pittsburgh
George O. Darbey Co., Inc.
Reading
- RHODE ISLAND**
W. H. Edwards Co., Inc.
Providence
- SOUTH CAROLINA**
Dixie Radio Supply Co.
Columbia
- TEXAS**
***All-State**
Dallas
McNicol Inc.
El Paso
***Sterling Electronics Inc.**
Houston
- UTAH**
Ballard Supply Corp.
Ogden
- VIRGINIA**
Womack Radio Supply Co.
Danville
Radio Supply Co., Inc.
Norfolk
Peoples Radio & TV Supply Co.
Roanoke
- WASHINGTON**
Skagit-Whatcom Electronics
Supply, Inc.
Mount Vernon
G & I Electronics, Inc.
Tacoma
- WEST VIRGINIA**
Meyers Electronics Inc.
Blue
- WISCONSIN**
Amateur Electronic Supply
Milwaukee

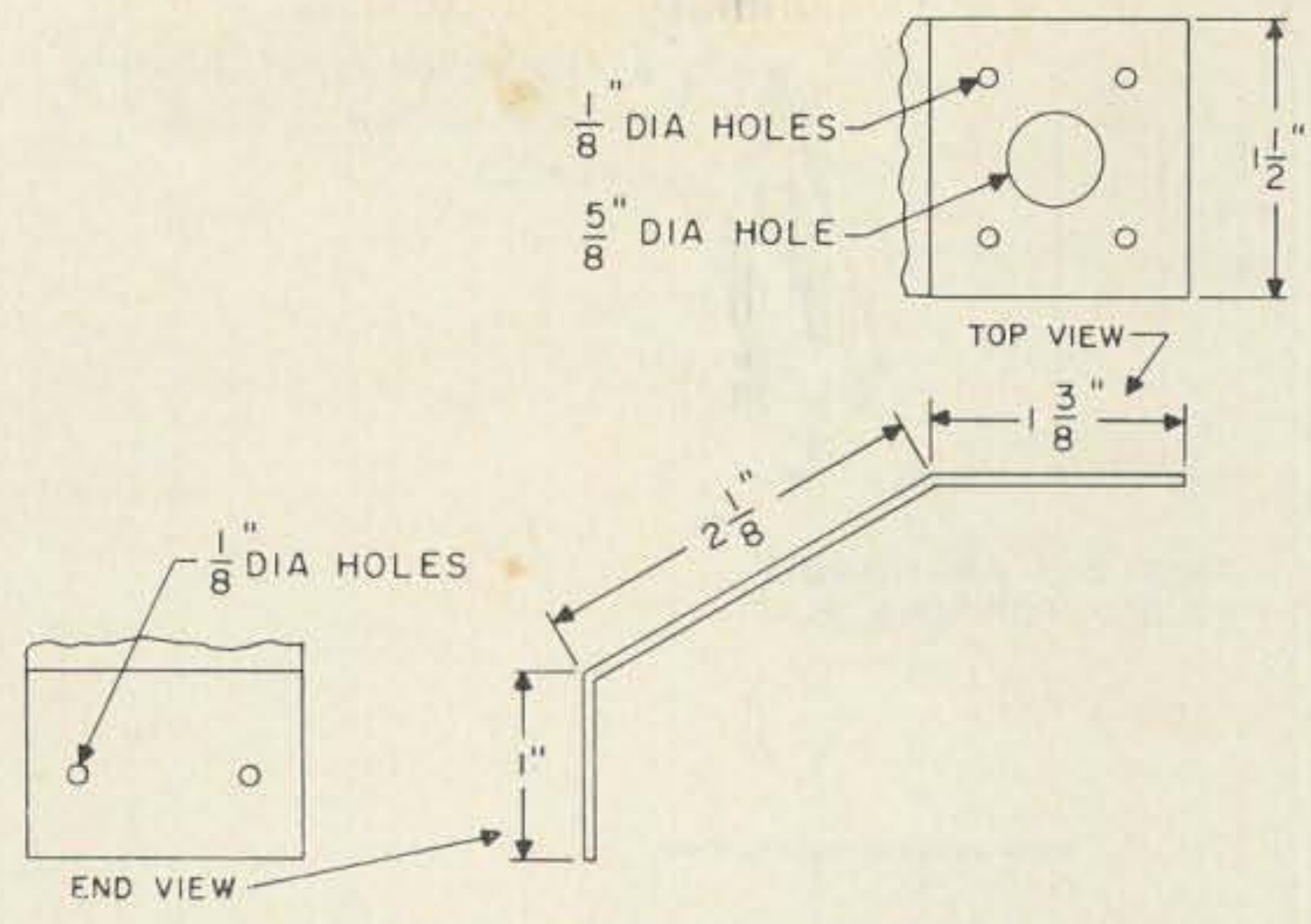*These distributors carry the entire line of INSTANT LETTERING dry transfer products including the complete range of over 1000 standard sheets—50 different type faces in sizes ranging from 8 pt. to 3" display letters in black, white, red, yellow, blue and gold. There's a specific sheet to fill your every marking or lettering requirement.



J ANTENNA MOUNTING BRACKET

back the slit portions of the conduit so that it will fit tightly into the end of the can in which you have installed the insulator. Then drill at least two holes from the lid side of the can through the lid and through the split portions of the conduit. Use sheet metal screws to hold the lid in place.

The next problem is soldering the cans together—which really isn't much of a problem if you have a good 100 watt iron, *non-corrosive* soldering flux, and resin core solder. First, "tack" each can in place with solder at about four places around the periphery of the can. Then go back and solder heavily all the way around. I laid the assembled portion of the antenna flat and held the cans between stacks of old books.

When you finish, you should have something that looks like the antenna shown in the photograph—except, of course, for the radiator itself, which we have not yet installed. Now take a piece of polystyrene foam and cut it circularly the size of the inside diameter of the lower can. Make the foam just a little oversize, so it will fit tightly. Then, cut the piece of foam in two, cut a semi-circle in each half for the conduit, and put the two pieces in place to hold the end of the assembled sleeve equidistant from the conduit.

Now cut a piece of aluminum clothesline wire (see Table II for correct length). Make a 90° bend in the wire at a point one-half inch from one end. Then bend the one-half inch portion into a semi-circle so it can be attached to the insulator. It will probably be necessary to use two 1/4-inch washers on the insulator to attach the antenna securely.

And that's the coaxial antenna. Just mount it where you want it, by means of clamps to a mast or the side of the house, run the coax where you want it, and you're on the air.


With the J on the car and the coaxial on the house, you can drive around the block talking to yourself!

... W6TKA

TRY IT . . . you'll be amazed!

instant lettering[®] dry transfer MARKING KITS

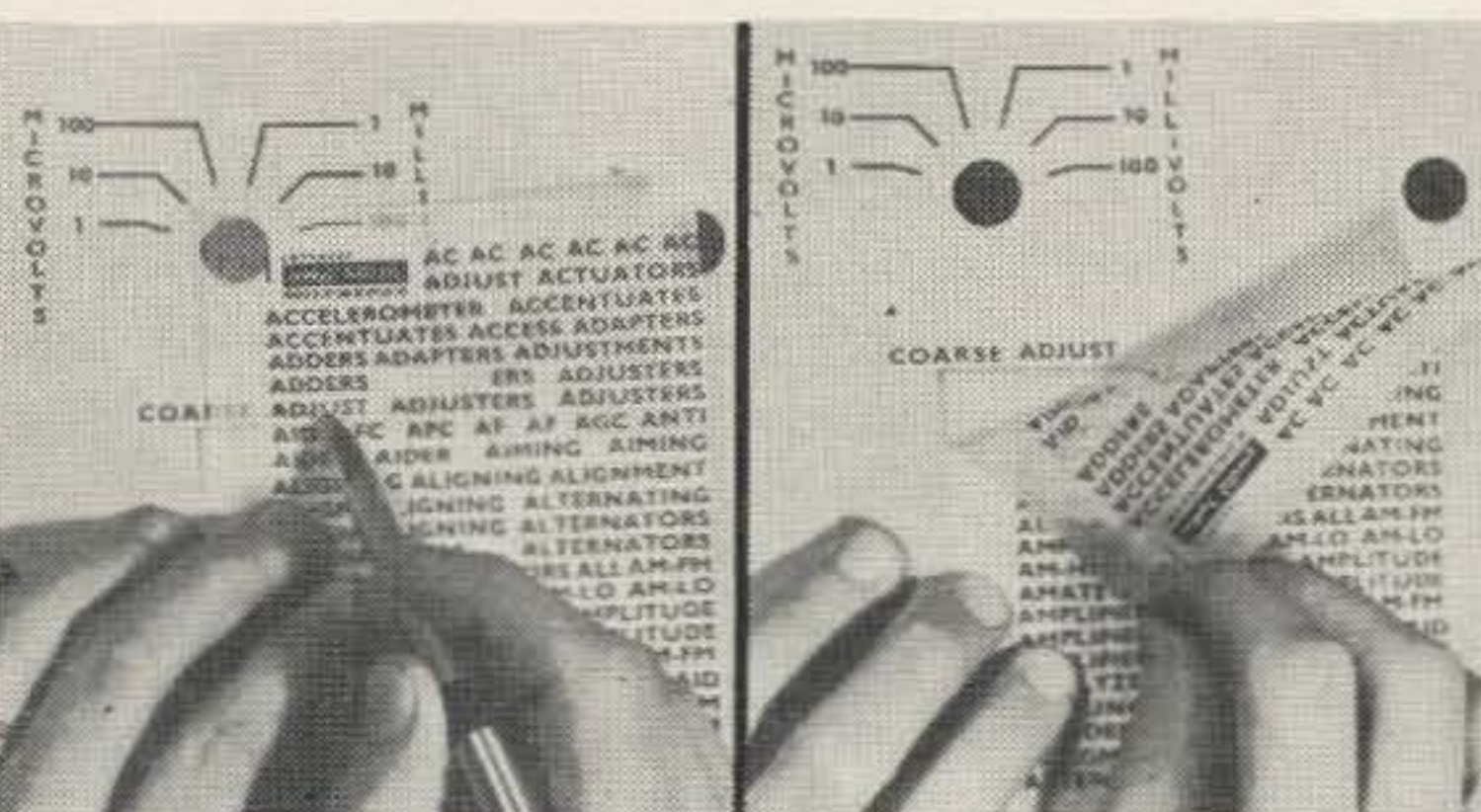Ask your local parts distributor for your free sample . . . then try it. All you do is rub over a word or symbol and it's transferred. What could be easier?



INSTANT LETTERING[®] marking kits bring you all the necessary elements for completely marking electronic equipment, prototypes, drawings, etc. in this fast new easy-to-use form. There's even a new drafting symbol kit for better more readable schematics.

Words, letters, numerals, switch patterns, arcs, drafting symbols, etc. are printed on a special transparent carrier film. Rubbing over one of these elements with a ballpoint pen releases it from the carrier film and adheres it to your working surface. **INSTANT LETTERING[®]** words and symbols transfer to almost any surface including glass, plastic, even painted and bare metals. Now you can quickly mark all panels, even especially calibrated two-color nomenclatures, pilot light jewels, sub-assemblies, circuit boards, etc. Reproduction quality **INSTANT LETTERING[®]** transfers are clean and sharp, leave no background haze or film, make prototypes look like finished production equipment and give all equipment and drawings a professional look.

NEW!
dry transfer
**ELECTRONIC SYMBOL
DRAFTING SET**

instant lettering[®] dry transfer ELECTRONIC SYMBOL drafting set

THE MODERN WAY TO BETTER, MORE READABLE DRAWINGS! WITH THE AMAZING INSTANT LETTERING[®] DRY TRANSFER PROCESS YOU JUST RUB AND THE SYMBOL IS TRANSFERRED.

Contains 40 sheets of INSTANT LETTERING[®] dry transfer electronic symbols including letters and numerals. These sheets are made with a new diazo-proof adhesive that adheres perfectly to all vellum, paper and polyester tracing films. Also included is a complete guide to drawing with dry transfer symbols. Designed to conform with MIL-STD-15-1.

Drawn by MIL-STD-15-1

The quicker way to more readable schematics. Contains 40 sheets of electronic symbols including letters and numerals. These sheets are made with a new diazo-proof adhesive that adheres perfectly to all vellum, paper and polyester tracing films. Also included is a complete guide to drawing with dry transfer symbols. Designed to conform with MIL-STD-15-1.

No. 970—Electronic Symbol Drafting Set\$15.95

LETRASET instant lettering
dry transfer TITLES for ELECTRONIC EQUIPMENT

LABELING, MARKING, TITLING ALL ELECTRONIC CONTROL PANELS and DRAWINGS, ETC.

NO WATER
NO TAPES
NO SCRIBING
NO ENGRAVING

Costs minimally
Starts in processing
Leads the printing!

TITLES FOR ELECTRONIC EQUIPMENT
Hundreds of preprinted titles researched to give up to 95% of all electronic marking. For labeling, marking, titling all electronic control panels, drawings, prototypes, etc.

No. 958—Black\$4.95
No. 959—White\$4.95

instant lettering[®] dry transfer TERMINAL & CHASSIS MARKING KIT

ELECTRONIC PANELS, PROTOTYPES, CHASSIS, ENGINEERS DRAWINGS, PRINTED CIRCUIT & TERMINAL BOARDS, SCHEMATICAL, ROTATING COMPONENTS, ETC.

TERMINAL & CHASSIS MARKING KIT
All the necessary letters, letter combinations and numerals for marking chassis, printed circuit and terminal boards, rotating components, etc.

No. 966—Black\$4.95
No. 967—White\$4.95

DATAKOAT PROTECTIVE COATING
Specially designed for all INSTANT LETTERING dry transfer products. Water-clear, dries quickly and protects against abrasion and weathering. Particularly effective on metal and other non-porous surfaces. Protective Coating Kit contains 1 oz. bottle of DATAKOAT with applicator brush cap and 1 oz. bottle of thinner. No. 04176.....\$1 00 • Quick drying Spray Coating in handy 16 oz aerosol can. No. 04177.....\$2.95



instant lettering[®] dry transfer METER & DIAL marking kit

METER & DIAL MARKING KIT
Arcs, dial patterns, lines, wedges, graduation lines, switch symbols, alphabets and numerals in black, white and red for marking standard and special rotary tap switches, potentiometers and prototype and especially calibrated meter dials. Colors provide contrast on scales and switches simplifying usage of complex instruments.

No. 968—Meter & Dial Marking Kit\$4.95

Ask your local parts distributor for your free sample or write direct.
THE DATAK CORPORATION • GUTTENBERG, NEW JERSEY

The Trouble

With Fred . . .

You couldn't call amateur radio a sexy hobby—like amateur dramatics, for instance, where a Romeo and Juliet might find themselves truly wedded and bedded before you could say Wherefore; or Siamese cats—“Why doesn't your queen get together with my tom . . . ?”; or veteran cars—“Come up to my apartment for a quiet evening, honey, and I'll show you my rally route . . .”

No, radio amateurs are a pretty stolid lot as a rule. Never let it be said, though, that their chemistry doesn't work in the orthodox manner. The science of electronics is so won-

derful that the time may very well come when other arrangements might be possible. Until then radio amateurs are apt to come to heel eventually, no matter how great their resistance. That was the trouble with Fred.

There are nine amateurs in our town and we stick together for mutual protection as much as for personal friendship. It's far easier to hunt the DX in an organised pack than to have everybody QRM'ing everybody else. TVI sorts itself out more easily when friends rally round to help. The wives can get together, too, to air their mutual grievances. That was our downfall.

For Fred and I were true friends, besides having the hobby in common. We had gone to the same school and the same college—he to study accountancy, me to learn engineering. We were the best of buddies.

The trouble with Fred began when his mother, after ten decorous years as a widow, threw her heels over her head and married a guy out on the West Coast. She signed the old house over to Fred and off she went, leaving the poor boy to fend for himself. I guess she thought he should be O.K., pushing 40 as he was. He had the house he had grown up in and Myrtle, who came in twice a week to clean. What more did he need?

He needed plenty. The old lady had spent her lonely years spoiling him like the big baby he resembled. For Fred, with his round face, big cuddlesome frame and helpless expression, had the sort of little-boy-lost look that sets the hormones buzzing in any woman, from nine to ninety. They all wanted to mother him. He had been efficiently mothered for forty years and suddenly had to look after



You couldn't call ham radio a sexy hobby—like dramatics or vintage cars, or Siamese cats . . .

himself. The result was chaos.


His shirts, for instance; he came to our house one night with one button obviously missing. Later that week I noticed two buttons adrift. He seemed blissfully unaware that anything was wrong but, when he came the third time with more buttons missing than present, Janet, my wife, offered to do a little mending for him. He came next day with a grip full of perforated socks and buttonless shirts. It took Janet a week to get him mended again.

Food was an even greater problem. His own catering experience was rudimentary and that chubby body took a lot of stoking to keep it comfortable. He ate occasional meals in a road-side joint, where he got nothing but heartburn. Myrtle fixed him something now and again, but a man has to eat more than twice a week. So Fred got to dropping in at our house just before meal-times. What could Janet do but offer him lunch—or dinner—or breakfast—or a midnight snack when there was a contest on? No housewife could bear to dish up good food with a lonesome man watching, drooling and eyeing the apple pie wistfully and with affection, especially when the man was someone as appealing as Fred and the housewife as tender-hearted as Janet.

As I say, Fred was a regular visitor. Sometimes, though, Janet would have arranged a dinner party, with all the best china, glass and silver, with linen napkins instead of paper and an equal number of men and women. It might be an important client of mine we were entertaining, or some old friend from Janet's schooldays for whom she wanted to put on the style. There we'd be sitting, all dressed up, with me mixing martinis as if we had them every night, and the conversation going nicely easy and sophisticated and plenty of status symbols showing. And in would lumber Fred to tell me that a ZD9 was on. Fred would be wearing sneakers and an old sweat shirt but who would have the heart to send him away?

We weren't the only victims of course. Fred was engaged for weeks helping Bert to build a sideband rig—takes time and care to do a job like that. And a man can build up a hearty appetite. So Bert sat Fred down and very appreciative he was, for he loved home-baking and it had been his mother's boast that no store-cake ever crossed her threshold.

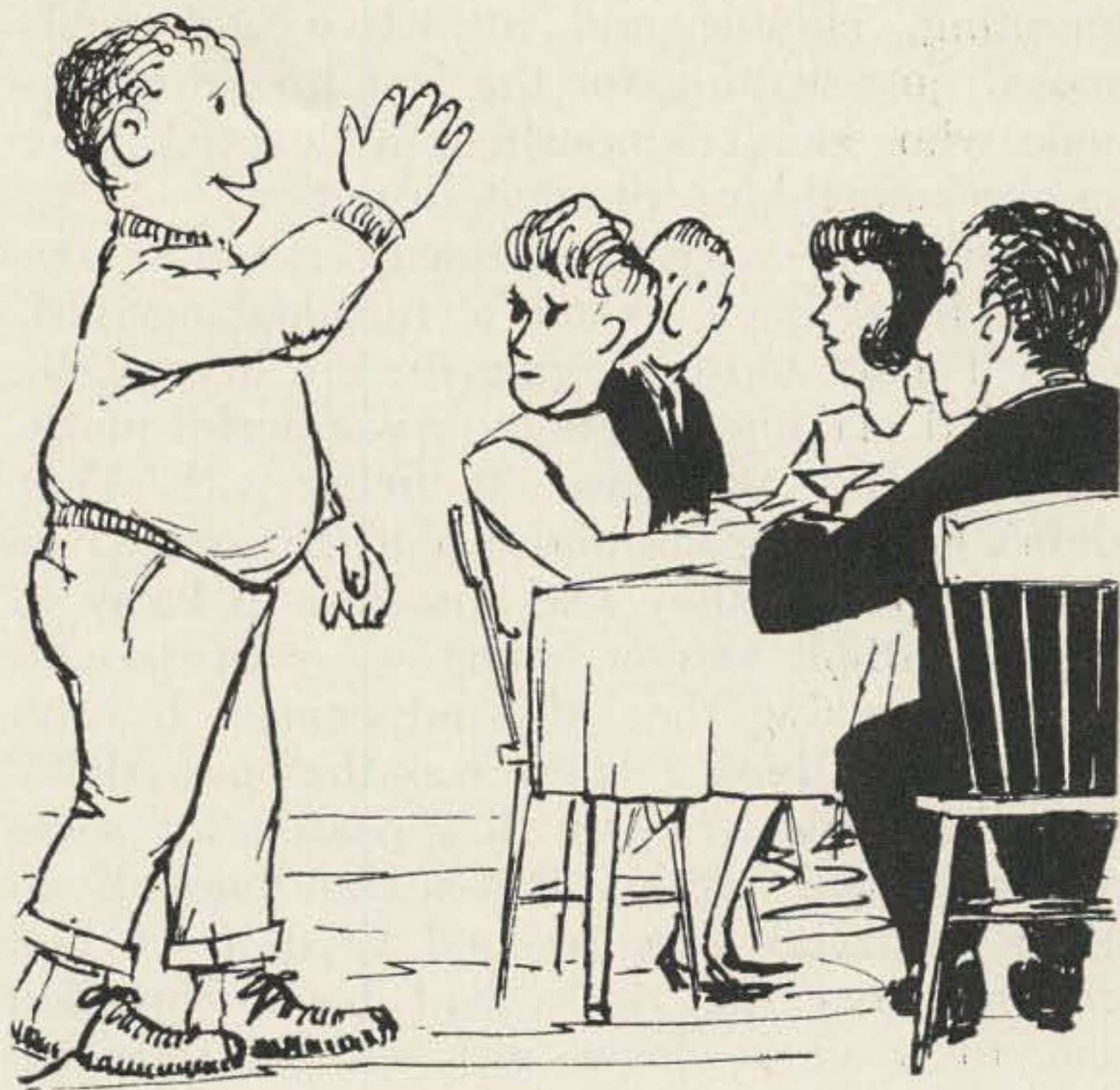One weekend George put up a log periodic, the first in our area. It was just like Field Day, with people driving in from miles around on the Saturday to help or to admire. Doris



Fred would drop in on a dinner party dressed in sneakers and a sweat shirt . . .

fed them all coffee and pie but, when everyone had gone home, there was Fred still helping George, so Doris had to invite him to supper and to stay the night, so that he and George could make an early start on Sunday morning—after a huge breakfast.

So there it was. We all genuinely loved the big lug and enjoyed his company. It was the wives who ganged up on us—they decided it was time Fred got married.

George and Bert and I did our very best to protect him. We argued, pleaded, threatened but Fred's fate was sealed. It was just a question of finding the girl. This presented the wives with a serious obstacle which delayed their plans for a while. We thought it might render our friend safe, for we knew our Fred. He was terrified of women. Married women, particularly those who fed him, were OK but if a single girl so much as breathed on Fred, he would hang his head, his baby-soft skin would flush the prettiest and most appealing shade of pink and he wouldn't say a word. Fred's conversation was limited entirely to radio. He lived radio. Jayne Mansfield might be the answer to my prayer, or Bert's or George's. All Fred would ask was did she work AM or SSB?

This, you understand, had considerably hampered his sex life so far but Fred didn't seem to mind. There was always food as consolation.

So the girls had themselves a problem. And the girls solved it and in the most cunning, dirty, under-handed way . . . after all, Fred was a sitting target, plump and ripe and


tempting, eligible and attractive and well-heeled, just waiting for the first predatory female who could demonstrate a devoted, nay, an obsessional love for amateur radio.

Doris' niece arrived in town. I suppose she could have been called a nice-looking girl, even if a bit too managing for my liking. She intended making somebody a wonderful mother, even if it was Fred, to begin with. That didn't justify the iniquitous plot that our wives concocted . . . they sold the idea to Patsy in one marathon session, when we were too involved working the sideband contest to stop them. Next thing I knew was that my ARRL Handbook mysteriously disappeared for some weeks. So did George's RSGB Handbook. Even then we could have rescued Fred if we had realised that the books had been smuggled out to a very clever girl with a retentive brain, determination and desire for a husband.

The trouble with Fred came to a head at Christmas, when all the local amateurs and their wives got together for a party—there being no contests to work that weekend.

Doris brought her over to us—I remember so clearly, in the same way that a picture of a fatal disaster remains clearly etched on the victims' memories. There were George, Bert and I, happily discussing the possibility of fitting mobile sideband transceivers, when up slithers Doris. You could almost hear the rattle at the end of her tail. Beaming at her side was this dame, Patsy.

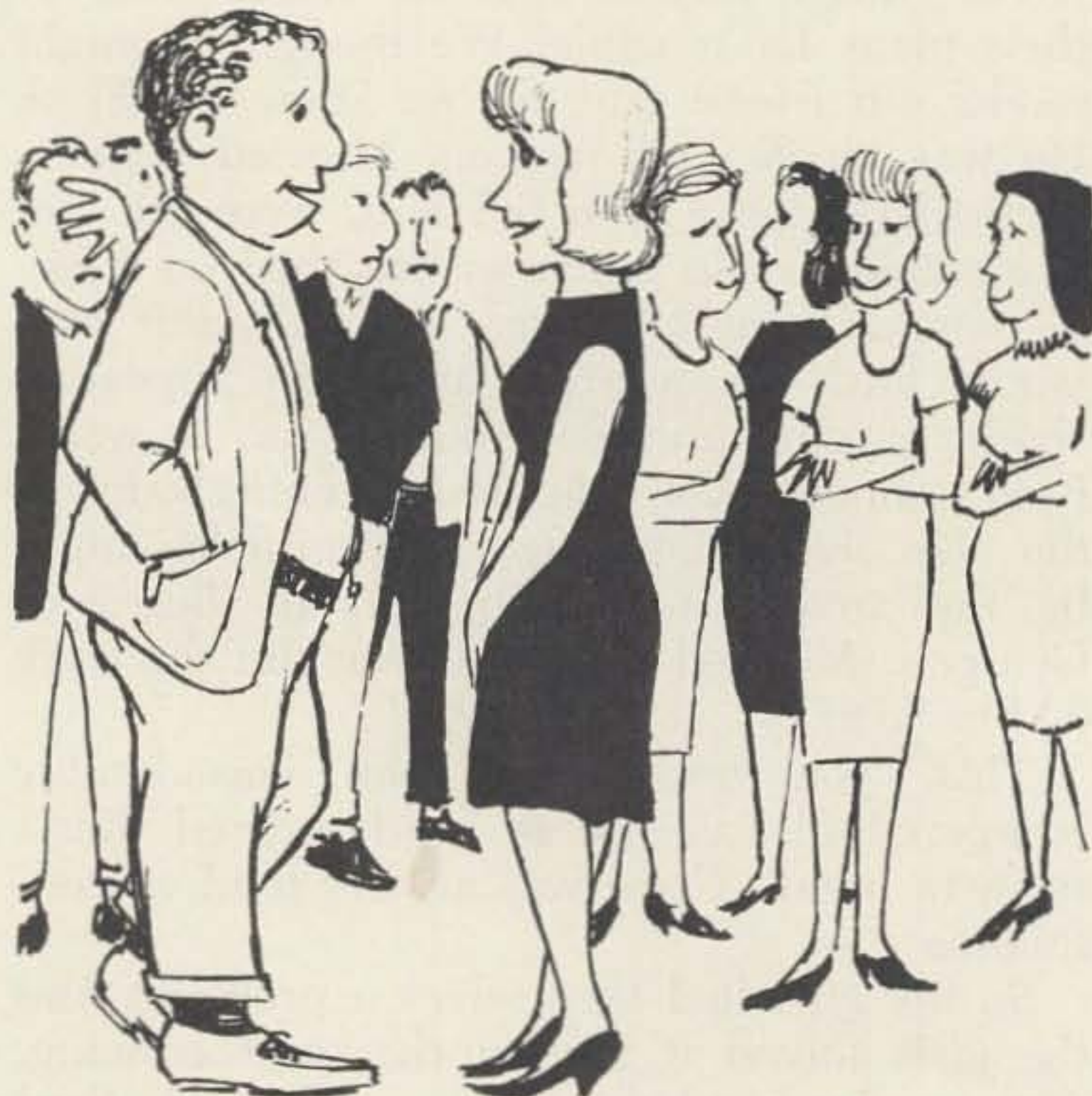"Hello, Fred," hissed Doris. "Do you know my niece, Patsy?" And off she coiled, leaving Fred to go into the mumbling and blushing



Fred was left alone with Patsy . . .

routine. Never will I forget what happened next. It was cruel, heartless. It wasn't cricket. Nor was it baseball, football, handball or tennis.

"I heard you men discussing sideband transceivers," said Patsy brightly, "Tell me—what kind of sideband generation do you use—crystal filter, phasing or mechanical filter?"

It was horrible to see. Fred raised his head. *This* he had never seen. Then he proceeded to tell her, in very great detail, exactly which kind of SSB generation he did prefer—and why. Our Fred, roped and bridled, trotted meekly into the corral, waiting for his saddle.

They were married within weeks. There was nothing to delay them. Patsy moved into Fred's house and shared not only Fred's bed but his cubical quad too.

Of course they were happy. And Patsy had learned just enough amateur radio to trap Fred, but her interest was aroused and those first blissful, honeymoon weeks must have been interspersed with passionate lessons on circuit diagrams and regulations, for soon Patsy had a call of her own.

A year went by and, for the first wedding anniversary Patsy had Fred buy her not diamonds, not mink, but a genuine 5-carat furrier-designed linear, which must have set him back a helluva lot but that's what a guy will do for love. Theirs was now the biggest signal in the town and you could see this in Patsy's attitude to the rest of us—a kind of patronage which we began to resent.

I should have known it was to be big trouble when, some weeks after Fred and Patsy had gone up into the linear class, Bert mentioned to me casually that Fred had visited them the previous evening and stayed for supper. It seemed that Patsy had a sked she just couldn't miss and there was no time to cook supper. Then one day he arrived at our house just before lunch. He plainly had all the time in the world to spare, for Janet called me twice for lunch. Then she came into the shack to find me.

"Hurry and wash," she said, "Lunch has been ready for ten minutes already. I guess Patsy has your lunch waiting for you, too, Fred."

"Well, Janet," said Fred—and it was quite like old times—"you see—Patsy has been kinda busy this morning. There's a ZD7 coming up on 20 and she needs him to make her century—so she just didn't get around to cooking . . ."

It was while Fred was tackling a king-sized portion of Janet's pot-roast that I noticed there were two buttons missing off his shirt

. . . Sylvia

Super-combination for transceiving...

The new Receiver-controlled Exciter...

DRAKE
T-4
RECITER

+

DRAKE
R-4
RECEIVER

=

The Transceiver with the MOST!!



Model T-4 **\$269⁹⁵** Amateur Net

T-4 Features

- Covers all Ham Bands 160 thru 10 meters.
- Covers MARS and Other Frequencies between ham bands.
- Upper and Lower Sideband on all frequencies.
- Automatic Transmit Receive Switching on CW (semi break-in).
- Controlled Carrier Modulation for AM is completely compatible with SSB linear amplifiers
- VOX or PTT on SSB and AM built-in.
- Adjustable Pi-Network Output.
- Two Crystal Lattice Filters for sideband selection, 2.4 Kc bandwidth.
- Transmitting AGC prevents flat topping.
- Shaped Grid Block Keying with side tone output.
- 200 Watts PEP Input on SSB—180 watts input CW.
- Meter indicates plate current and relative output.
- Compact size; rugged construction.

Model R-4 **\$379⁹⁵** Amateur Net

R-4 Features

- Linear permeability tuned VFO with 1 Kc dial divisions. VFO and crystal frequencies pre-mixed for all-band stability.
- Covers ham bands 80, 40, 20, 15 meters completely and 28.5 to 29.0 Mc of 10 meters with crystals furnished.
- Any ten 500 Kc ranges between 1.5 and 30 Mc can be covered with accessory crystals... (160 meters, MARS, etc 5.0-6.0 Mc not recommended).
- Four bandwidths of selectivity, 0.4 Kc, 1.2 Kc, 2.4 Kc and 4.8 Kc.
- Passband tuning gives sideband selection without retuning.
- Noise blanker that works on CW, SSB, and AM is built-in.
- Notch filter is built-in.
- 100 Kc crystal calibrator is built-in.
- Product detector for SSB/CW, diode detector for AM.
- Crystal Lattice Filter gives superior cross modulation and overload characteristics.
- Compact size; rugged construction.

Complete Transmitter

DRAKE
T-4X

- All T-4 features plus
- Solid State VFO and
 - XTAL Oscillators...

Give:

- Separate control of receive and transmit frequencies
- Transceiver operation with frequency control by either Rcvr or Xmtr
- Coverage on 80, 40, 20, 15 meters completely and 28.5 to 29.0 Mc of 10 meters with crystals furnished
- Four extra 500 Kc ranges can be covered with accessory crystals (160 meters, other 10 meter ranges, MARS, etc.)

Model T-4X **\$369⁹⁵**
Amateur Net



R. L. DRAKE COMPANY MIAMISBURG, OHIO 45342



A Versatile Oscilloscope

Harvey R. Pierce WØOPA
5372 E. Bald Eagle Blvd.
White Bear Lake 10, Minnesota

In my previous articles in 73 Magazine I described the "Simplescope" monitor and then a more advanced design in "Complicating the Simplescope." Both of these were excellent monitors, but the Simplescope was limited to monitoring high-level AM, and the improved version merely added a wide-band vertical amplifier so it could be hooked to a receiver.


I felt there was a need for a more advanced design: something that could be used with low-level modulators as well as high-level, for SSB and DSB, and with receivers, provided this could be done without at the same time being too expensive or too complicated for the ham builder. A sort of minimum oscilloscope for all-around monitor use, but not necessarily for other scope purposes.

With the above in mind, specifications were drawn up. For low-level work, wide-range amplifiers for both horizontal and vertical deflection would be necessary, and these amplifiers should have fairly high gain and no phase-shift to blur the pattern. The scope should have direct input to both vertical and horizontal plates for high-level work, and for frequencies above the range of the amplifiers. Construction should not require expensive or hard-to-get parts. The circuit should be as simple and fool-proof as possible. Centering controls should be used, and a 60-cycle linear sweep would be nice if the circuit was simple.

The diagrams and pictures show what was done. The 6CL6 video amplifier circuit used in "Complicating the Simplescope" had proved satisfactory so it was used again, with minor changes. (See Fig. 1) A small (1/10th mhy) rf choke was added in series with the 6CL6 plate load resistors to improve the response at the high-frequency limits. The 6CL6 plates connect directly to the deflection plates to avoid phase shift. A bias supply for the 6CL6 grids was added to prevent any low frequency degeneration from cathode bias. Identical amplifiers were used for vertical and horizontal deflection.

The amplifiers connect to only one of each set of deflection plates, and direct input is available to the other two plates. The direct input plates also connect to the two centering controls. Of these two, the vertical plate is isolated (decoupled) from the vertical centering control by a 2½ mhy rf choke, allowing high-level rf to be fed to it, while the horizontal plate is decoupled from the horizontal centering control by a 270k ohm resistor, allowing either high-level af or rf to be fed to it. Both plates are connected to the direct input connectors by capacitors, and if direct input is not used, the connectors may be grounded, thereby bypassing these unused plates to ground.

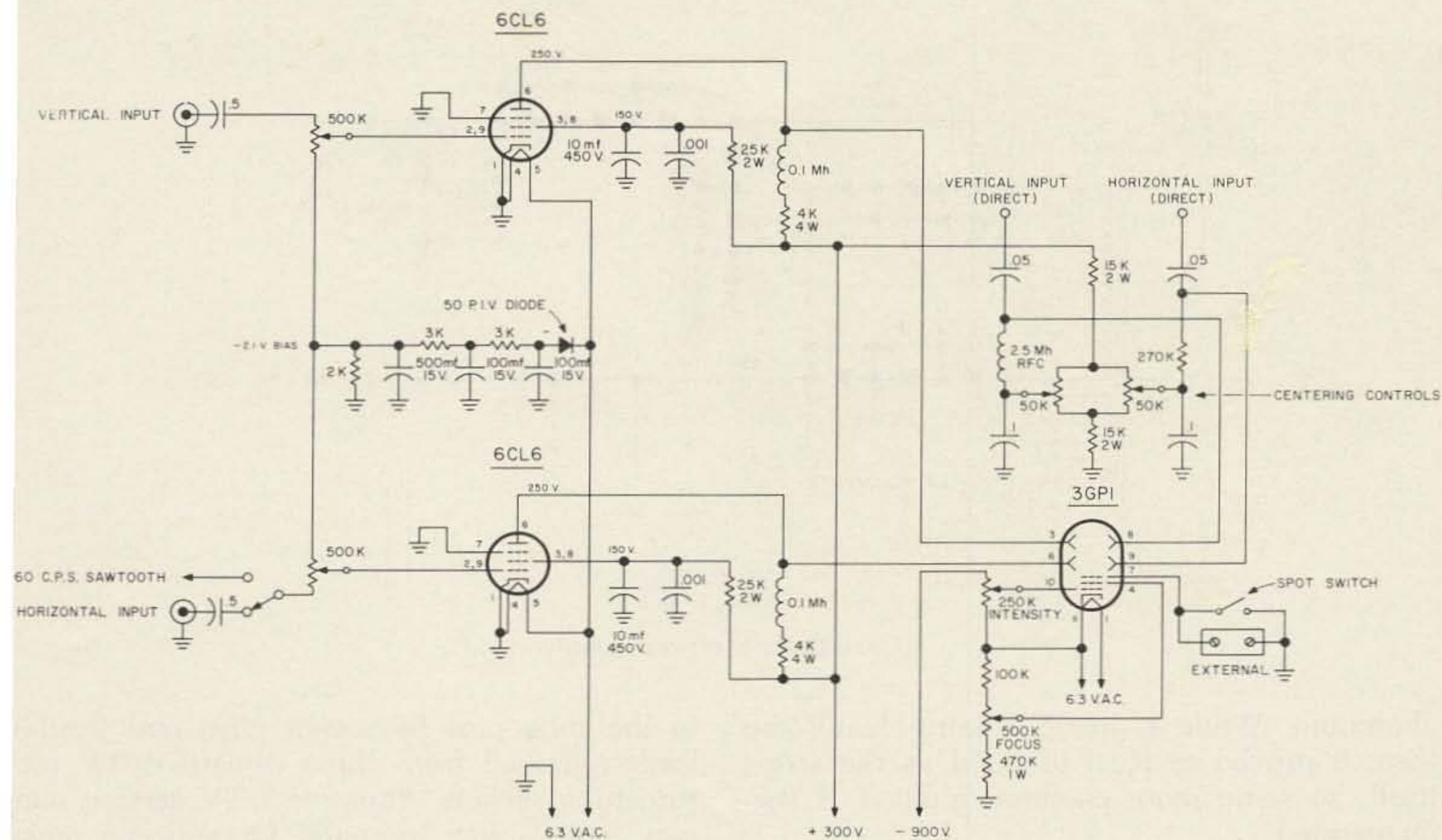When the amplifiers are not in use, the low



Versatile oscilloscope

impedance of their plate circuits (less than 3,000 ohms) keeps them from having much effect on the direct deflection.

The power supply (see Fig. 2) uses a TV power transformer and low-cost silicon diodes in series as rectifiers. The diodes save space and heat. Resistors equalize the voltages for the diodes. A conventional full-wave rectifier supplies a positive 300-volts for the amplifiers, while a voltage doubling circuit supplies about 900 volts negative. Together they supply about 1200 volts for the cathode ray tube (crt). The voltage doubler produces about 6 volts of beautiful 60-cycle sawtooth ripple, which is used for the linear sweep voltage.

Provision is made for blanking the spot by opening the lead to the last crt anode, either by a front-panel switch ("Spot Switch") or remote relay. This blanking is desirable during standby periods to prevent burning of the phosphor screen by an unmoving spot. Other methods of blanking can be used, but this seemed the simplest and involved nothing but ground potential.


In building this instrument, primary consideration was given to short grid and plate leads because of the high frequencies involved. (See Fig. 3). Second came ease of construction, then cost and size. Last came cabinet or enclosure. The basic design, as shown in the pictures, consists of two aluminum plates, one at each end of the crt. A third plate forms the rear, on which is mounted the power trans-

former, fuse, and all connectors. The three plates are held together by four threaded rods, one at each corner.

The cabinet shown in the pictures was an experiment. It is made of one eighth inch tempered hardboard covered on the smooth side by self-adhesive vinyl film and on the inside by thin sheet aluminum. It is held together by outside-corner molding for wall tiles (from Sears, Roebuck) and the four tie bolts. The ventilation holes are backed by perforated



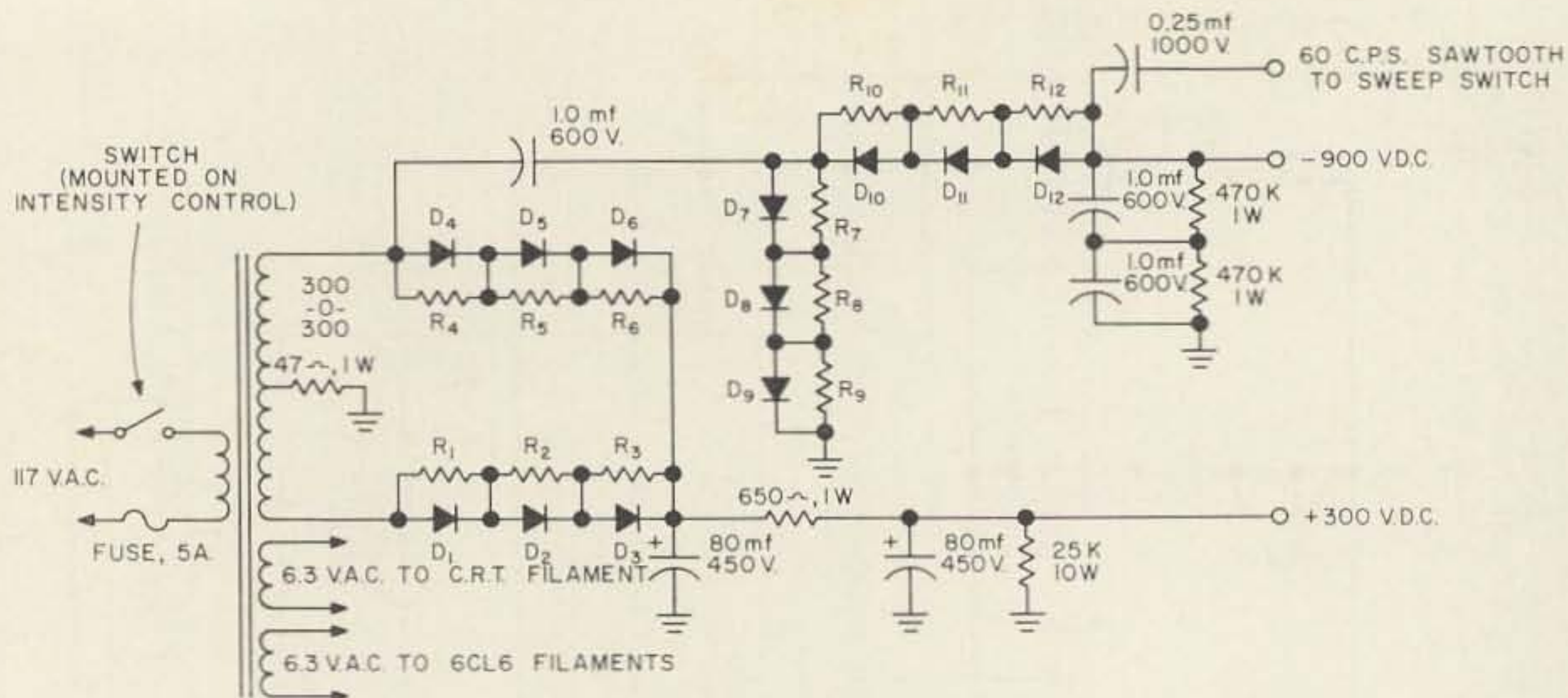Rear view. Connections for remote control of spot to the right of transformer, fuse and ac connector on left. Input connections (3-way binding posts) across the top. Handle at rear top for balance.



D₁ - D₁₂ - 500 Ma, 400 P.I.V.
 R₁ - R₁₂ - 820 K, 1/4 W

Oscilloscope power supply

aluminum. While it made a fairly handsome case, it proved as hard to build as the scope itself, so some more common method is recommended.

The aluminum plate at the rear of the crt is the main "chassis" and its layout (Fig. 3) should be followed closely in the interest of short leads and maximum high frequency amplification. With a little care, the 6CL6 sockets can be positioned so their grid lugs can be soldered directly to the center lug of the adjacent gain control, and their plate lugs a minimum distance from the crt deflection plate pins. Position the 60-cycle/audio sweep switch for shortest leads to the horizontal gain control, and keep the lead away from the chassis.


Crt sockets are hard to come by, so in this case a hole was cut in the chassis to clear the crt base, and a clamp devised to hold the tube firmly in position. Connections were made

to the tube pins by socket clips and flexible leads obtained from three discarded TV picture tube sockets. Your local TV service man may have a few to spare. Or you can make your own leads using clips from old octal sockets. Use insulation tubing over the clip lugs to avoid shorts and allow enough slack in the leads to permit rotating the crt 30 degrees or so later to level the horizontal trace. The keyway ridge of the crt base should be on the bottom.

Vertical and horizontal centering (positioning) controls are mounted directly below the gain controls. Between them, below the tubes, tie-points are placed as needed to support the amplifier and bias supply components, and a long, multi-point strip is placed along the bottom edge of the chassis plate for the connections to the other units. (Transformer, front panel, rectifier/filter sub chassis.) The shaft extensions shown in the pictures are birch dowel (cheap) but metal is best.

To conserve space, the large electrolytic capacitors for bypassing the 6CL6 screens and for the bias supply were placed on the tube side of the chassis. The screen connections were brought through the metal by feed-thru capacitors, for better bypassing at the high frequencies. If preferred, .001 or .005 mfd disc ceramics connected at the tube socket lugs could be used in place of the feed-thrus.

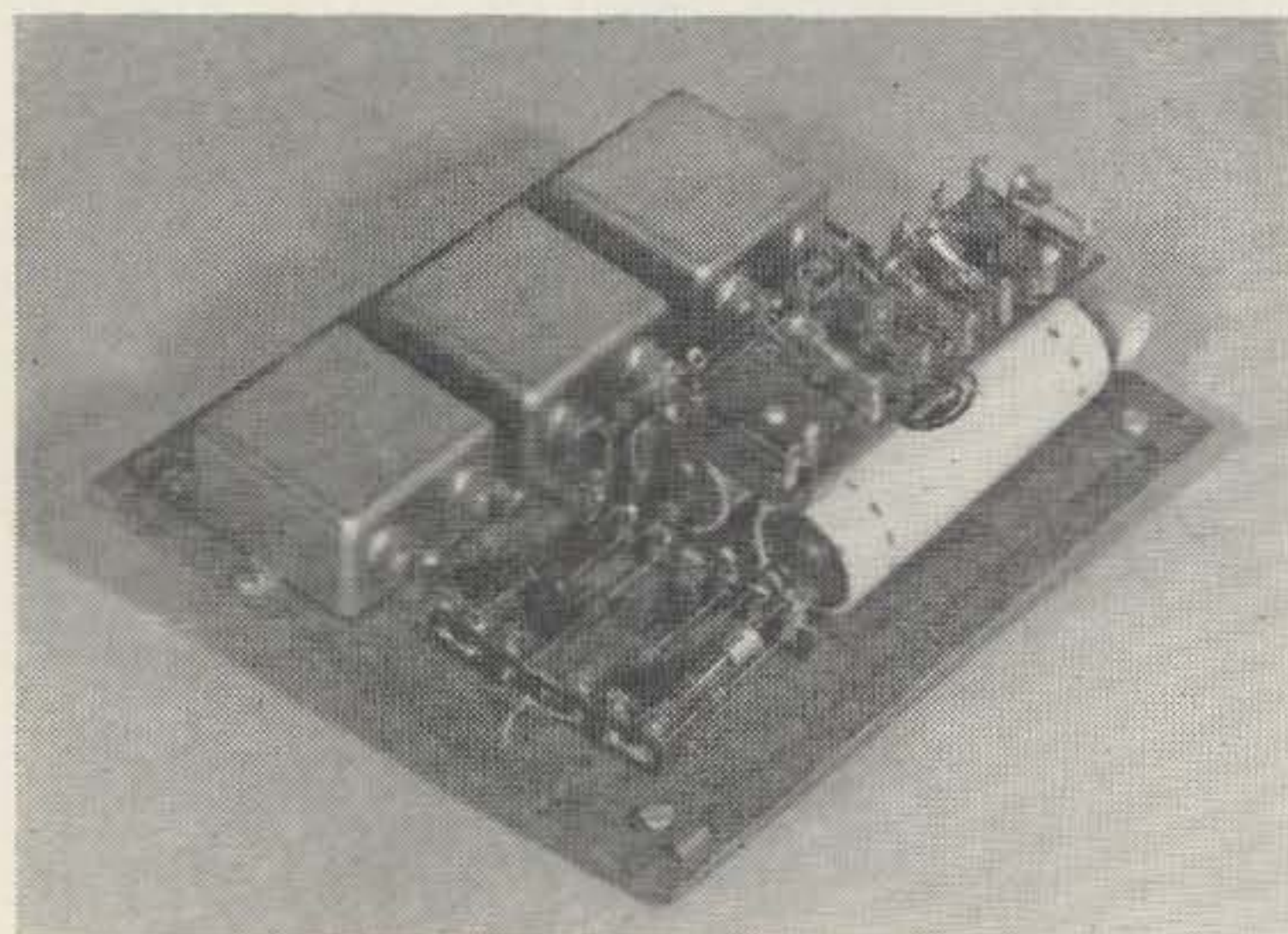A hole is cut in the front panel about 1/4" greater in diameter than the crt face and the tube is cushioned by four soft rubber grommets pushed into slots around the hole. On this panel, below the crt face, are mounted the focus and intensity controls and a pilot light. (The latter may be omitted, if you wish. If



The rectifier/filter sub chassis. High-voltage diodes in foreground,, high voltage capacitors in rear. Low voltage diodes on terminal board above the two 80 mfd capacitors.

used, a light shield must be provided to keep it from shining on the crt face from the back.) The power switch is on the intensity control.

To insure proper alignment of shaft bearings, tube face, and tie bolts, this panel and the main chassis should be clamped together and small centering holes drilled thru both sheets for all holes common to both. These holes may then be enlarged to the sizes needed. In the scope pictured a separate "dress" panel was used to cover the grommets, bolt heads, etc. A hint—it is a big help to use color-coded wires between this panel and the main chassis.


Rectifier/filter/bleeder components are mounted on an insulation board that clamps to the tie bolts, underneath the crt. The placement of parts will depend a great deal on the size and shape of the capacitors used. In the picture the full-wave diodes are mounted on an insulation strip over the two 80 mfd electrolytics, and the voltage-doubling high-voltage diodes on one corner with their metal-cased capacitors along the edge. Bleeder and filter resistors are underneath, as is a tie-point strip for the connections to the transformer and main chassis.

The power transformer is mounted on the rear panel so the crt will be as far from its magnetic field as possible. All connectors are on this rear panel, as well as the input capacitors and the fuse. Be sure to have long enough leads attached to the units on this panel to reach the appropriate points on the main chassis when assembled. I used a cheater cord connector from an old TV set for the power cord because I dislike cords dangling from unused instruments. If you don't have one it may be omitted.

The four units are wired separately, then assembled and wired to each other. Color coding of the wires is a big help. Otherwise, care should be taken to identify each wire as it is hooked up.

No exact dimensions have been given, because I feel that in a project such as this the builder should be free to accommodate his own ideas and parts. Placement of gain controls, amplifier tubes, and crt as shown in Fig. 3, with the rear panel close behind, assures short lead where short leads are important, and the power transformer must be behind the crt. The rest of the construction can be done any way the builder chooses.

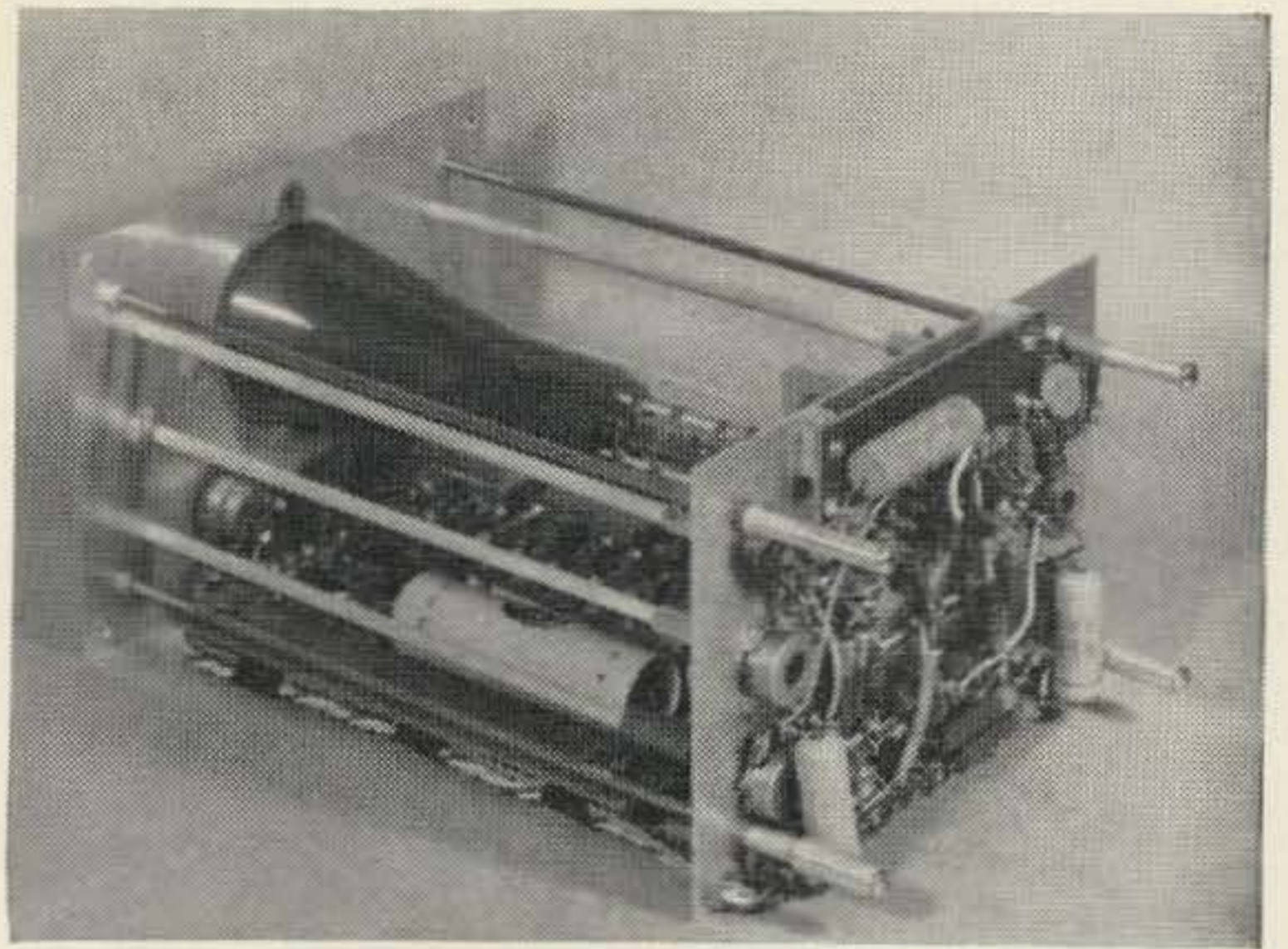There are few critical parts. The amplifier plate load resistors are made by connecting two 8200 ohm, 2-watt carbon resistors in parallel to make the 4,000 ohm, 4-watt resistors required. The screen resistors are 27,000




Interior view, showing rear of main chassis, general construction, placing of rectifier-filter sub chassis, and bolt extensions for rear panel.

ohm 2-watt, 20%, carbon resistors that checked close to 25k on an ohmmeter, but 25k 10-watt wirewound resistors are OK at added cost. The resistors in the bias supply were selected to give 2.1 volts bias at 1 ma. Any other combination that comes out with 2.1 volts will do as well.

The .25 mfd/1000 volt capacitor used to couple the sawtooth ripple of the voltage-doubler supply to the horizontal input (Sweep Switch) must be of very high quality. The permissible leakage is one micro amp, but even this is a bit high. Leakage resistance should be well over 1000 megohms. Too much leakage will over-bias the horizontal amplifier.

The power transformer should have two 6.3 volt heater windings, and its high voltage secondary should be good for at least 100 ma; the actual voltage can be anything from 500 to 750 volts centertapped, with 650 about right. The experimenter can change the value of the filter resistor to obtain not over 300 volts of dc for the 6CL6 plates according to whatever voltage the transformer has.

Once wired and assembled, the first test is the usual "smoke test": plug it in and see if anything overheats. (Note—the 6CL6 plate resistors normally get pretty hot.) Voltages should be checked next. They should be reasonably close to those indicated in the diagram. Be sure the voltage-doubler high voltage is NEGATIVE to the chassis. (This point bothers some builders, they are so used to high voltages being positive to chassis!) Be sure the bias voltage is right, 2.1 volts. Check the .25 mfd/1000 v sweep coupling capacitor for leakage: with the sweep switch set for 60-cy. sweep a vtvm should measure no more than -5 volts to ground from the switch side of the capacitor.

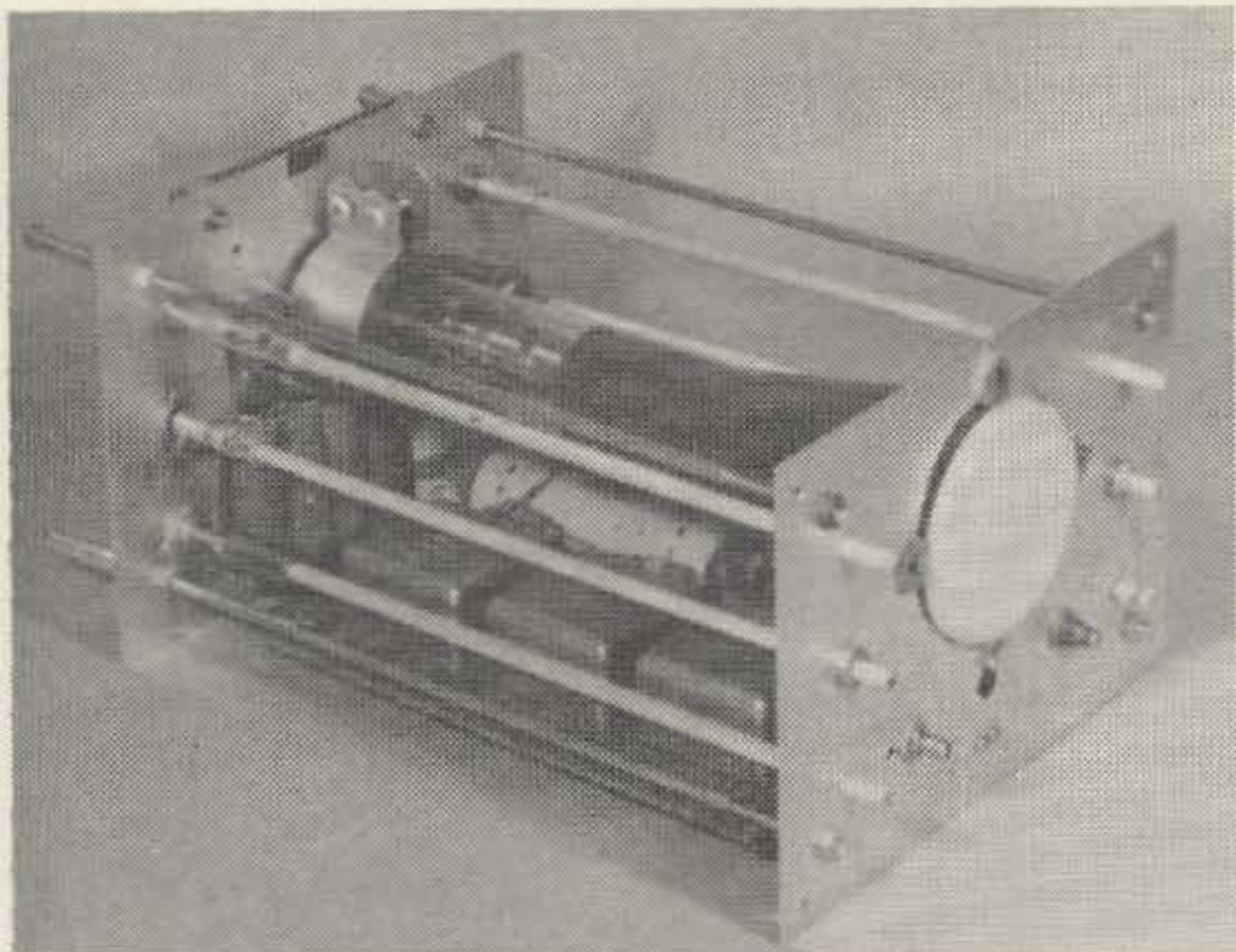

Interior view from the front, showing mounting of the crt. Note clamp for tube base, four grommets around face.

If all voltages are present and reasonably correct turn the spot switch on and advance the intensity control half way. With both gain controls turned full off and the centering controls half advanced, a spot should appear on the screen. It will be noted that the centering controls will move the spot further off center in one direction than the other, and there may be a slight interaction between the focus and intensity controls. If there is leakage in the 60-cycle sweep coupling capacitor, the horizontal gain control adjustment will have an effect on the horizontal centering. None of these irregularities affect the use of the instrument.

A simple operating test is to jumper the vertical and horizontal amplifier input connectors together and set the sweep switch to the audio position. Apply 5 or 6 volts of ac (any frequency to 10kc) from the jumpered inputs to ground. A straight line should appear on the crt face, and by various adjustments of the two gain controls this line can be made to assume any angle over a range of 90 degrees between horizontal and vertical. Try all combinations of control settings. Any curvature, especially at the ends of the line, indicates distortion, and if everything is normal the line should extend $\frac{3}{4}$ ths the width of the tube at any angle before curving. Excessive distortion indicates amplifier trouble, usually improper bias.

Note carefully the areas of the crt face where distortion is evident in this test. In any future use of the instrument these distortion areas cannot be depended upon to give a true picture of things.

By now you should be familiar with the controls. Now is a good time to level the trace by loosening the crt clamp and rotating the tube so the horizontal line formed by the

60-cycle sweep is level with the vertical gain off. The scope is now ready to use. All four inputs—vertical direct, vertical amplified, horizontal direct and horizontal amplified—are independent of each other; they can be mixed in any combination and used simultaneously if desired. Switching from direct operation to amplifier use is thus avoided in many uses.

Amplifier input (sensitivity) for full-screen deflection in this scope is 1.5 volts horizontal (rms) and one volt vertical. Full screen deflection requires about 80 volts (rms) at the horizontal direct connector, 100 volts for vertical. Frequency response of both amplifiers runs from 15 cycles to something over 4.5 megacycles within 3db. The vertical direct (rf only) input range is from about 400 kc to well over 50 megacycles. The horizontal direct input frequency range is from about 20 cps to over 50 mcs. Input sensitivity varies somewhat with the voltage on the crt, so the figures above are not absolute values.

Within the frequency and sensitivity ranges above, this instrument can be used for the usual forms of radio monitoring, and a few not so usual. For instance, with the vertical amplifier input connected to the receiver if and an rf pickup from the transmitter connected to the vertical direct input, and the 60-cycle sweep, you can watch received signals and your transmitted signal without doing any switching of the scope as you go from receive to transmit and back.

The main limit to the versatility of this instrument is that the linear sweep is only 60 cps. This is no great handicap in monitoring, and may be an advantage because it "stops" all 60- and 120-cycle ripple and hum so common in electronics and clearly identifies them. A minor limit is sensitivity, though there will be few times when it is desired to "see" voltages less than the $\frac{1}{4}$ volt (rms) that gives about the smallest usable pattern (about $\frac{1}{2}$ inch) through the amplifiers.

It is beyond the scope of this article to cover the uses of this instrument, because its applications are so varied. Of course, due to simplification and corner-cutting it cannot compare with standard scopes for all-round use, but the cost of parts is moderate compared even with the kit scopes, it is an interesting building project, and the finished instrument will monitor just about any transmitter you have. I put an antenna and a tuned circuit coupled to the vertical amplifier and got a good pattern from a local BC station five miles away. (They had good modulation, too!)

. . . WØOPA

Credit for the pictures goes to Bob Rode WØBRE.



Notice to other receiver manufacturers; Read this and weep

Our formula for receiver design: Take the finest receiver on the market, modernize it, add a noise blanker, reduce it to about QSL size, add six meters and WWV, start building.

The Davco transistorsized receiver is the first receiver available to the amateur at an amateur radio price which is state-of-the-art in quality and performance. None of those hot fragile tubes to break and generate heat, none of those big if transformers for us—our whole if strip is smaller than the usual transformer. The Davco DR-30 has eight plug in micro-miniature circuit modules. The chassis and interstage shielding are all made of 3/16th inch aluminum for extreme rigidity. We use toroids, Cleveite transfilters, a Collins mechanical filter, 14 crystals, 25 transistors, and 15 diodes—The results are spectacular. The Davco DR-30 receiver operates from 13 volts and draws only 40 mils with no input signal which is about half the current a pilot light lamp draws—explaining why there is so little heat generated. One-half watt, mostly expended in the loudspeaker, is not going to make much heat.

So who needs a micro-miniature receiver? Well, there may be a few of you who would like a full-fledged communications receiver that you can use in the car—take on trips—wear as a watch fob—or use at home. Before long we'll have a companion transmitter which will transceive with our receiver—and about the same size (4 inches high, by 7 inches wide).

Available direct from factory; insured shipping included. A time payment plan is available.

Introductory price:

\$337.50

DAVCO ELECTRONICS


Post Office Box 2677
2024 South Monroe St.
Tallahassee, Florida
Phone 305-224-4322

Send for free brochure explaining all of the features of this unique receiver.

- COVERAGE** — Every kc. of 80, 40, 20, 15, 10 meters
plus 50.0 - 50.550 Mc. (6 meters)
plus WWV at 10 Mc.
plus expanded coverage for MARS, etc.
plus two more 550 kc. segments YCU can choose
- SELECTIVITY** — 2.1 kc. Collins Mechanical Filter for SSB
plus 200 cycle ultra-sharp crystal filter for CW
- STABILITY** — **plus** broad IF position for AM crystal first conversion oscillator (10 crystals supplied)
plus transmitter-type tuning VFO
plus crystal BFO-carrier generator
plus a new concept in extruded aluminum chassis design for the most rigid construction available
- SENSITIVITY** — .6 microvolt sensitivity, with tuned RF stage using premium UHF-type transistor (2N2495, with rated noise figure of 3db at 50 Mc.)
- PLUS**
 - tunable rejection-notch filter for eliminating heterodynes
 - and** blanking-type noise limiter (preselectivity)
 - and** built-in 100 kc. crystal calibrator
 - and** split-gear ball-bearing tuning mechanism
 - and** separate AM and product detectors
 - and** plug-in module subassembly construction
 - and** new expanded warranty; designed and manufactured in USA
 - and** transceive compatibility with companion DT-20 200-watt SSB transmitter
 - and** size (1/10 cubic foot) and weight (nine pounds); installs anywhere

*Save your ears with
this interesting circuit.*

Steven Pullman

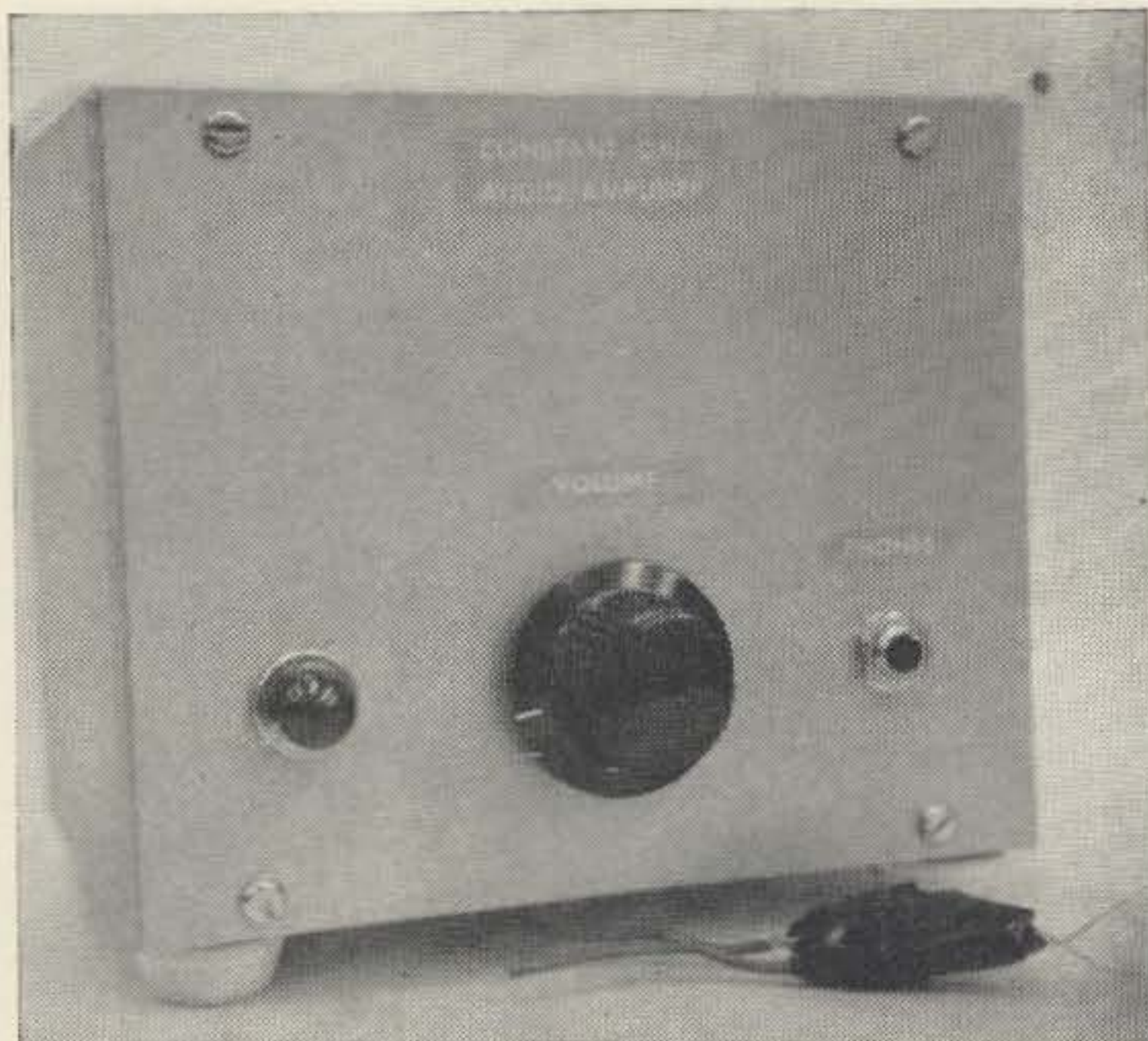

Constant Gain Audio System

Do you go deaf every time a local joins a QSO you are holding with an XZ2? Is he 60 over 9 while the XZ2 is S7, or is that four way QSO keeping you riding the gain control? Here's a solution to your problem—an amplifier that will keep the audio level from shattering your eardrums while you sit back and relax.

Several months ago a company came out with a variable resistor that is controlled by low voltage dc or ac. The information that I received from them had several interesting circuits, one of which was a constant gain audio stage. I rushed out and checked the price of this variable resistor. Upon hearing

that the price was \$11.00, I decided to forget all about it.

This variable resistor is actually a sensitive photocell and a small light bulb sealed together. A photocell will exhibit a very high resistance across its terminals with no light striking its face, and a very low resistance when exposed to a quantity of light. I started experimenting recently, and found that an Amperex ORP63 cadmium sulphide photocell exhibited the resistance characteristics that were needed. This cell is very sensitive and with no light on the cell, it exhibits a resistance of better than 10 megohms. The ORP63 and a number 40 pilot light were taped together with black electrical tape and made light tight. Fig. 1 shows a plot of resistance of the cell versus voltage to the bulb. As can be seen, the resistance varies exponentially from better than 10 megohms to as low as 300 ohms. The total cost of this combination is approximately \$1.60 as compared to the commercial device costing \$11.00.

Fig. 2 shows the first circuit tried. This

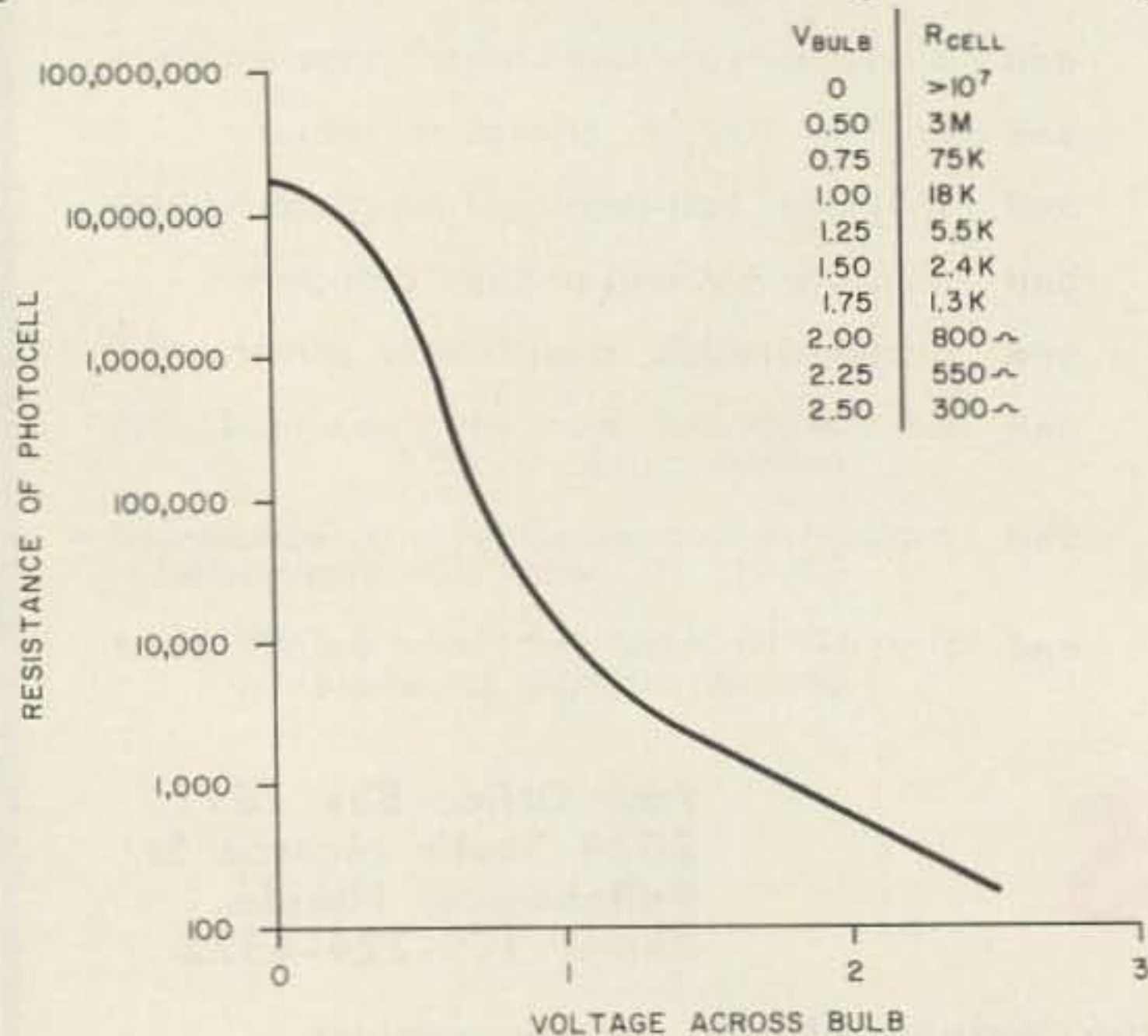


FIGURE 1


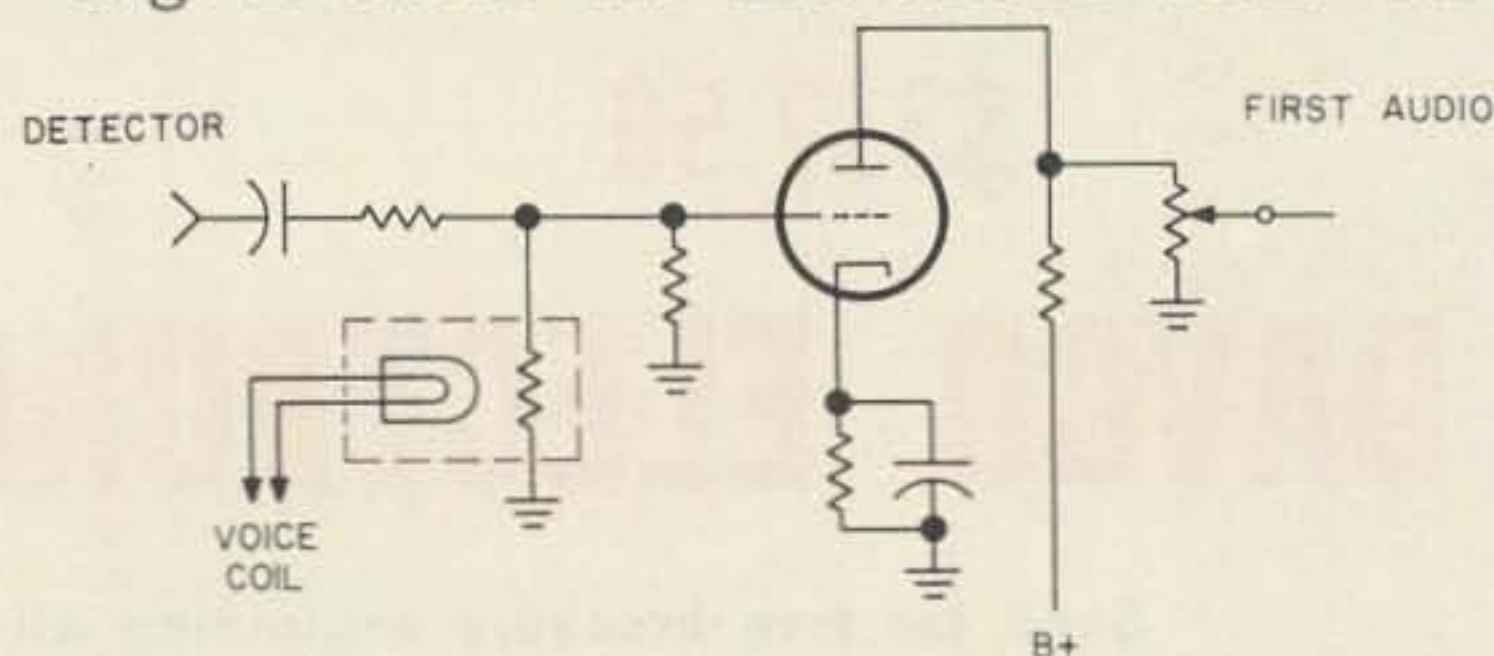


FIGURE 2

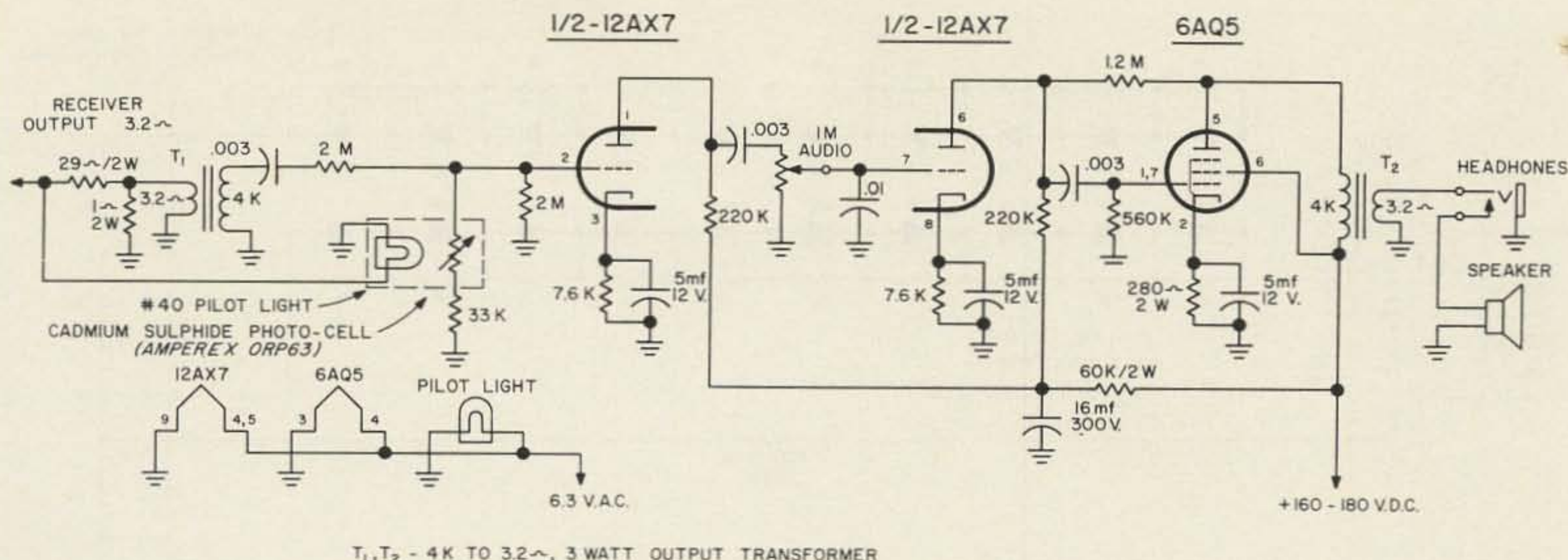

T₁, T₂ - 4K TO 3.2~, 3 WATT OUTPUT TRANSFORMER

FIGURE 3

circuit works well though it necessitates modifications to the receiver and gives only one level of constant gain. Signals below that level will vary widely. After a little thought, I realized that a separate audio system would have to be used. The only modification to the receiver is the disconnection of the speaker. The circuit is shown in Fig. 3. The circuit is a standard audio amplifier except for the first stage. The first stage is controlled by the photocell-bulb combo. The number 40 bulb is connected to the input of T2. A signal is applied and the bulb's intensity varies at almost an audio rate. The decay rate of the filament provides an averaging effect. The averaging effect allows the output to vary with the amplitude rate of the signal instead of the syllabic rate of speech. The resistance of PC1 varies as the audio signal strength varies. PC1 now acts like a volume control shunting more signal to ground as the signal increases and less signal to ground as the signal decreases. This then provides a fairly constant level to the manually variable gain control R1. This constant level can be set to any higher or lower level the operator desires.

The unit is built into a 5 × 6 × 4 aluminum utility case. A chassis was bent from some spare aluminum. T2 and T3 are cheap plate to voice coil transformers with a 4K primary. Standard audio layout is used. A neon bulb pilot light connected to the B plus was used; but a standard 6 volt pilot light connected to the filament may also be used. A B plus voltage of 160 to 180 volts at 30 ma is needed. This can be stolen from the receiver or from an external supply. The photocell is taped so that the sensitive face is parallel to the long side of the bulb's filament. Operation is simple. Set the receiver audio gain so that most signals are limited in gain by the first stage, V_{1A}. This can be checked by placing a VTVM across the output of V_{1A} and checking for a constant voltage as the receiver audio gain is increased. If a VTVM is not available, just listening to the output will suffice. Once the minimum signal is set by the receiver audio gain, this control is no longer used. The volume control, R1, is now used to provide any volume level needed with a fairly constant level at any setting.

... Pullman

The GAIN 'Moonbouncer' Skybeam by J. BEAM

G2 HCG worked KP4BPZ via Moonbouncer on 144.01 MC on 6/14/64 with a stock J Beam antenna . . . which would cost you less than \$60.00.

WIDE SELECTION VHF COMBINATIONS FOR 3/4, 1 1/4, 2 AND 6 METERS


Send for our FREE Catalog

DISTRIBUTORS PLEASE WRITE

GAIN, INC. DEPT. 73S — 27 E. 112th Place, Chicago, Illinois 60628 Phone us anytime at 312-568-1973

The Only Amateur Antenna Offered with Choice of Vertical, Horizontal or Circular Polarization EXCLUSIVE QUADRATIC PHASE FEED

Change polarization at operating position . . . NOT the roof! The point is: If the Gain Skybeam can 'moonbounce' successfully . . . it can do a far better job of day to day VHF communications. The Gain 'Moonbouncer' mounts vertical and horizontal elements on the same boom, separated and fed to give either vertical or horizontal polarization automatically, or by using proper termination, circular polarization in either direction. Horizontal and vertical gain consistent with good engineering practice — circular gain is additive! Rugged — will take 100 mph winds. 144MC 'Moonbouncer', as shown, with balun, \$69.95 Ham Net. Far better transmission for mobiles, too. Your rig deserves the best — get the dope on Gain J Beams!

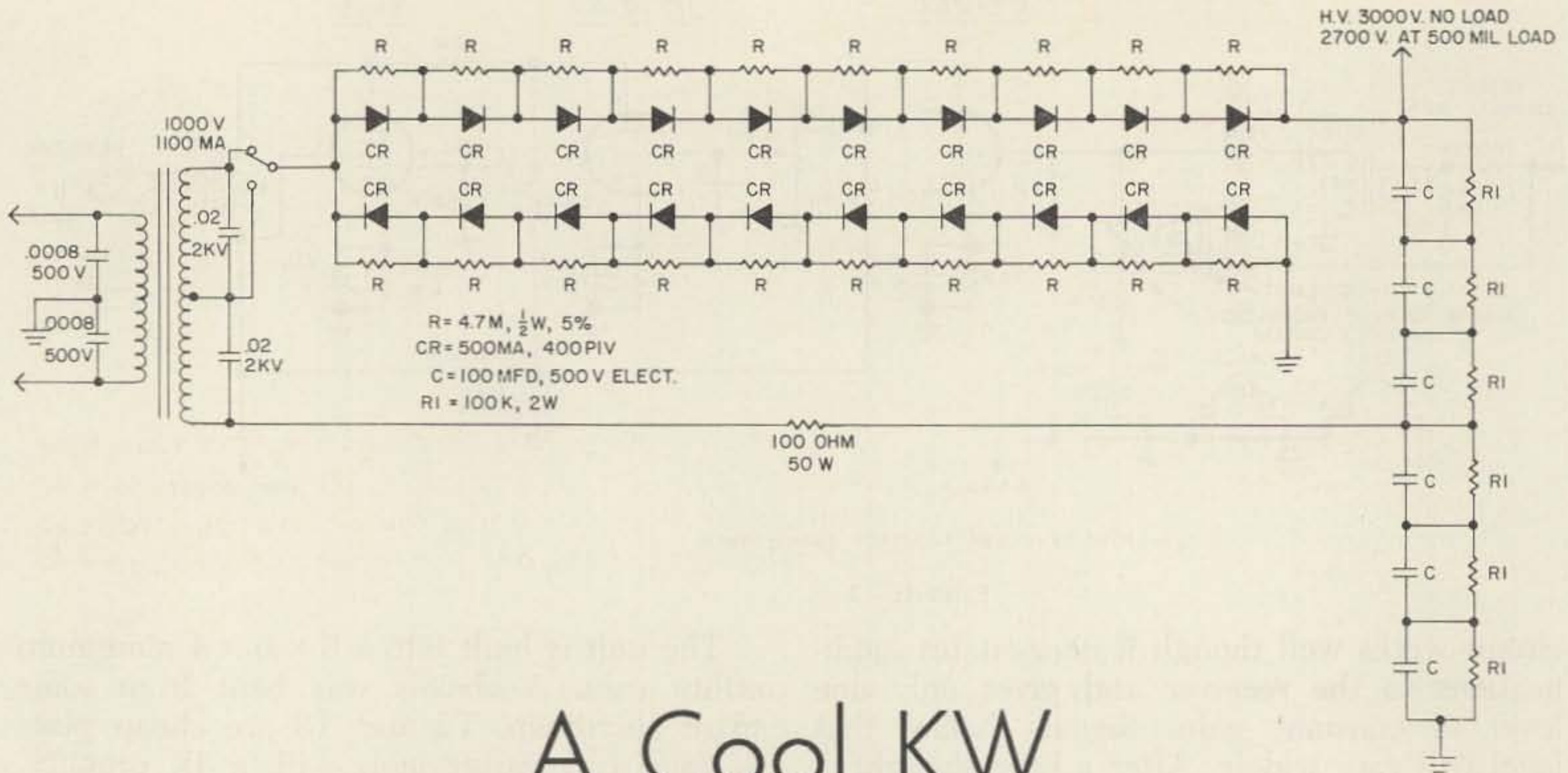

A Cool KW

Perry Thomas K5YWJ
P. O. Box 367
Silverton, Texas

Even a ham does not get "something for nothing" anymore, but this kw power supply is next to it! Compared to the cost of a conventional supply, you can have money left over for a new hat for the XYL, new shoes for the baby and cold 807's for the OM!

The transformer, about 1000 volts, at 500 ma or more, can be easily found on the surplus market. Mine is 1000 volts at 1.1 amps; Pacific Transformers #20046, from a radar power supply. Caution: do not go much above the 1000 volts across the secondary or you will end up with an embarrassingly high voltage and blown filters.

The schematic is a standard voltage doubler circuit using Silicon Diodes and high capacity filter. This shows an odd ripple pattern on a scope, but I have used it on my 813's in grounded grid ala G. E. Ham News for over two years of SSB AM and CW operating, driving it with the Apache-SB10 at first and now with the HT-37, and have had no complaints of hum. Nor have I had a single component failure in the power supply.

The diodes are Sarkes-Trazian M-500's, but 750 mil top hats are cheaper. The shunt re-


sistors on the diodes should be 5% tolerance because they act as a constant load balance on the diodes and keep the diodes from blowing when operated at full rating.

To figure the diodes and capacitors for a transformer of different voltage, since this circuit almost triples the rms of the secondary, each leg of diodes and filter capacitors should be rated 1½ times the secondary voltage, or slightly more for a safety factor; raising the resistance of the surge resistor gives a little better regulation with a corresponding drop in output voltage. My supply delivers 3000 volts with no load and 2750 volts at 500 mil load, which is as good as most conventional supplies.

The center tap is used to give reduced power for tune-up. This really is not necessary on 813's but is an essential for some of the other tubes that may be used. I use a SPDT switch rated at 10A-250 volts here and have no trouble hot-switching it.

I hope you are as satisfied with the supply you build as I am with mine—I will never use 866's again.

. . . K5YWJ

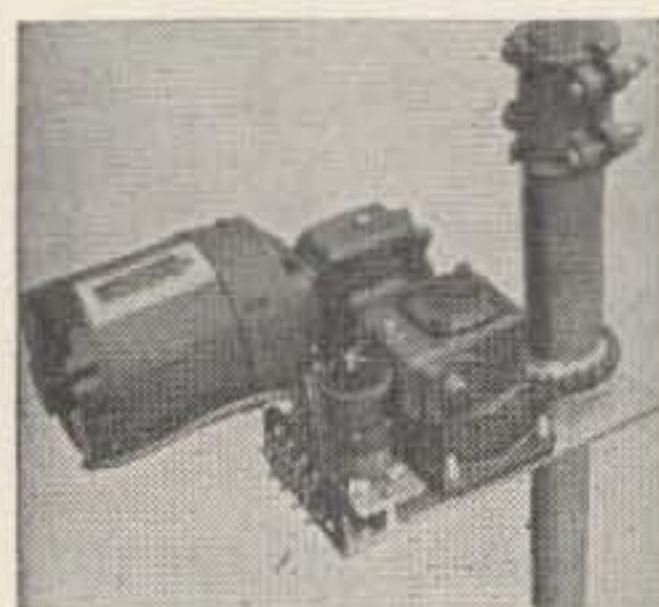

TELREX ROTATOR-INDICATOR SYSTEM MODEL TS250-RIS

Mast Feeds Thru Rotator For Safe, Easier, Installation

- 1300 IN./LBS ROTATION TORQUE
- SELF LOCKING BY STURDY WORM GEARS
- SELSYN AZIMUTH INDICATION
- ACCOMMODATES 2" O.D. MASTING
- MALLEABLE CAST MASTING CLAMP SUPPLIED
- OUTPUT SPEED APPROX. 1 RPM
- WILL FIT INTO OR ONTO A 6" SIDED TOWER

A Really Sturdy
ROTATOR-INDICATOR SYSTEM—
NOT a Modified TV Rotator!
Designed To
Out-Perform, Outlast!


\$25000
F.O.B.

ALSO:

TS325-RIS \$325.00
TS435-RIS \$435.00
TS535-RIS \$535.00
TS585-RIS \$585.00

TELREX LABS.

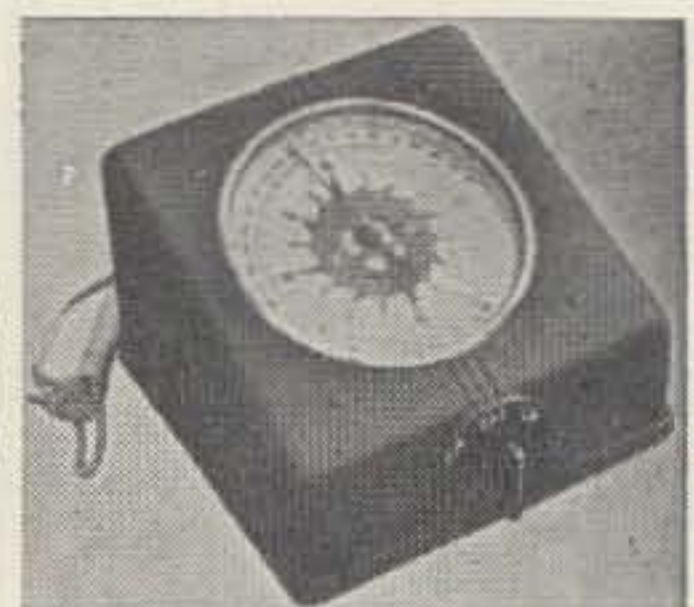Write for FREE PL65 Describing Rotators and Antennas ASBURY PARK, N.J.



TRANSCEIVER HIT PARADE



Use our tailor-made
time payment plan.

COLLINS

KWM 2 Transceiver	1150.00
516 F2 AC Supply	115.00
MP 1 DC Supply	198.00
351 D2 Mobile Mount	120.00

DRAKE

TR 4 Transceiver	585.00
AC 3 AC Supply	79.85
MS 3 Speaker	19.95
DC 3 DC Supply	129.95
Mk III	6.95

HALLICRAFTERS

SR160 Transceiver	349.50
P150 AC Supply/speaker	99.50
P150 DC Supply	109.50
MR 160 Mobile Mount	14.50

NATIONAL

NCX-5 Transceiver	685.00
NCX 3 Transceiver	369.00
NCX-A AC Supply/speaker	110.00
NCX-D DC Supply	119.50

SBE

SB 34	39.00
SB 2LA	249.50
SB 2MB	12.50
SB 2VOX	34.50
SB 2XC	24.50
SBE Mike	14.50

SWAN

Swan 350	395.00
Swan 1117B AC Supply	75.00
Swan 512 DC Supply	145.00

Write for our Special
Transceiver Packet

Hi OM!

Lots of turn over this past month and this new listing includes many new items. Remember these are fully reconditioned and guaranteed complete satisfaction. 73—Stan Burghardt WØBJV

	CASH/NO TRADE
CLEGG INTERCEPTOR 6&2 Meter Receiver	\$249.00
COLLINS 75S-3 Receiver (like new)	449.00
GLOBE CHIEF Deluxe Transmitter	39.00
GLOBE SCOUT 680A Transmitter	44.00
GLOBE PSA-63A AC Supply	25.00
GONSET GSB-100 Transmitter	199.00
HALLICRAFTERS HA-2 & P-262 mtr Transverter	159.00
HALLICRAFTERS S-40 Receiver	44.00
HALLICRAFTERS S-40B Receiver	49.00
HALLICRAFTERS S85 Receiver	65.00
HALLICRAFTERS SR-150 Transceiver	379.00
HALLICRAFTERS SR-160 Transceiver — demonstrator —	249.00
HALLICRAFTERS SX-99 Receiver	79.00
HALLICRAFTERS SX-101A Receiver	189.00
HALLICRAFTERS SX-101 MKIIIA Receiver	159.00
HALLICRAFTERS S-108 — demonstrator — (new)	109.00
HALLICRAFTERS SX-110 — demonstrator — (new)	129.00
HALLICRAFTERS SK-111 Receiver	129.00
HAMMARLUND HQ-110 Receiver	119.00
HAMMARLUND S-100 Speaker	9.00
HEATH APACHE & SB-10	209.00
HEATH DX-100B Transmitter	129.00
HEATH HW-12 & HP-13 Supply	159.00
HEATH HW-32 Transceiver	109.00
HEATH SB-200 Linear	189.00
HUNTER BANDIT 2000A	369.00
HY-GAIN TH-2 (discontinued model) (new)	49.00
JOHNSON 122 VFO	19.00
JOHNSON ADVENTURER	29.00
JOHNSON RANGER	119.00
JOHNSON 6N2 Transmitter	99.00
JOHNSON THUNDERBOLT LINEAR	269.00
KNIGHT R-100 Receiver	59.00
KNIGHT T-60 Transmitter	39.00
KNIGHT V-44 VFO	19.00
LAFAYETTE HE-30 Receiver & Speaker	45.00
MOSLEY CV-160 (new) 160 mtr Converter	9.00
NATIONAL NC88 Receiver	65.00
NATIONAL NC98 Receiver & Speaker	85.00
NATIONAL NC125 Receiver	79.00
NATIONAL NCX-3 and NCXA Transceiver and AC Supply	379.00
RME 4300 Receiver	85.00
SWAN SW175 Transceiver	139.00
SWAN SW240 & AC Supply	299.00
SYLVANIA Model 140 Tube Tester	15.00
TERADO 50173 12v to 110v AC 200 watt	49.00

WRITE FOR LATEST REVISED BULLETIN
ISSUED MONTHLY

Box 37A Watertown, So. Dak. Phone 605 866-5749

Burghardt
RADIO SUPPLY, Inc.

America's Most Reliable Amateur Dealer.

*Especially as
used in a
low-noise
transistor converter*

Larry Levy WA2INM/1
Marlboro, Vermont

2m Beer Can Cavities

(Teetotalers may use soft drink cans)

The subject of resonant cavities seems to be surrounded by an air of mystery and confusion. They are things that are used by people who work UHF and microwaves and seem to have found little use in the VHF field. One reason for this is that few amateurs seem to fully understand what they are, exactly what they do, their construction, and their applications. I will attempt to simplify the subject and show what the practical applications for cavities at the VHF frequencies are.

Cavities are basically an infinite number of shorted quarter-wave tuned stubs in parallel. They take the configuration of a cylinder with a rod in the center, with one end shorted and the other end tuned by a capacitor. If you will try to forget your mental picture of expensive-looking silver-plated plumbing for a moment, try to imagine a shorted quarter wave stub. Now connect another one in parallel. Now add more until you have a circle of them so that the last one added is touching the first. You will have a can with a rod in the center, which is precisely what a cavity is. Proceeding on this assumption, and also the assumption that you

don't want to spend many dollars for the silver plated variety, I will show how they can be made very inexpensively.

The cavity has many advantages over a conventional tuned circuit. It has a very high Q and low loss. By substituting the front end tuned circuits of a converter with a cavity, the selectivity can be improved to the point that no additional selectivity is needed to eliminate images and spurious responses that are less than a megacycle from the desired frequency. Two cavities are needed, not to get a narrow enough bandwidth, but to get a wide enough bandpass to be practical. Image rejection of better than 60 db is easily obtainable for signals removed by 1 mc from a 2 mc bandpass at 2 meters. By adding one or two more cavities, rejection of better than 100 db is possible. This means that it is not necessary to use double conversion or a high *if* to get desired selectivity. With the use of cavities tuned for a 1 mc bandpass, it is possible to use the BC band *if* with few problems. This should make construction of mobile converters easier.

Cavities have a very high Q and low loss, as I mentioned earlier. Aside from the advantage of image rejection, this can noticeably improve the effective sensitivity of many low noise converters. Because of the high voltage gain, the s/n ratio of an amplifier is better. There is a fixed amount of noise at the grid of a tube. The more voltage that is applied to that grid, the more the signal will be out of the noise. The Q of a cavity effectively raises the voltage of a signal. When used to feed an amplifier, this means that a signal is amplified without the addition of any noise, as the same signal is driving the grid of the tube with more voltage compared to the tube noise, in comparison with the voltage that the same signal would deliver with a conventional tuned circuit. On a margin-

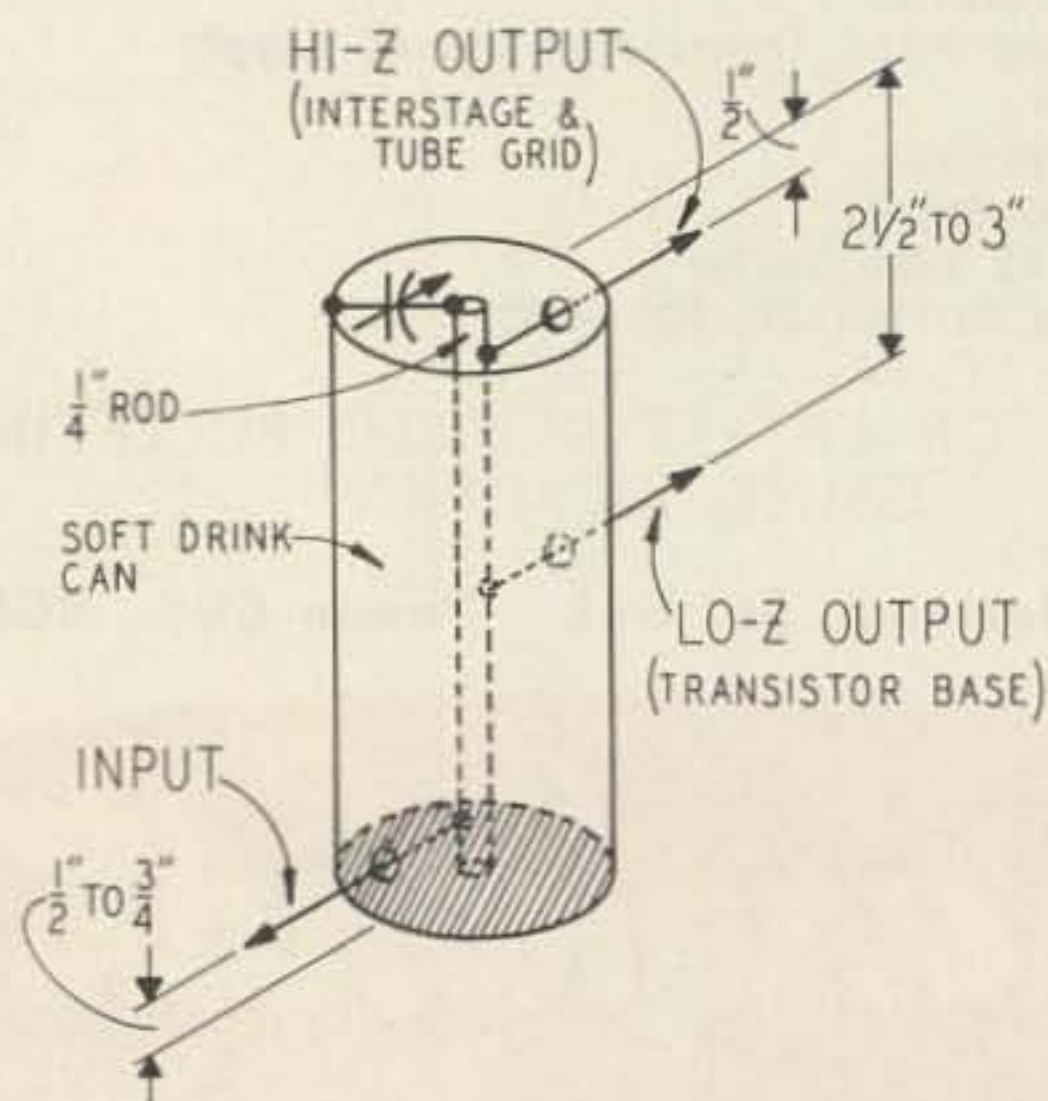


Fig. 1. Basic cavity.

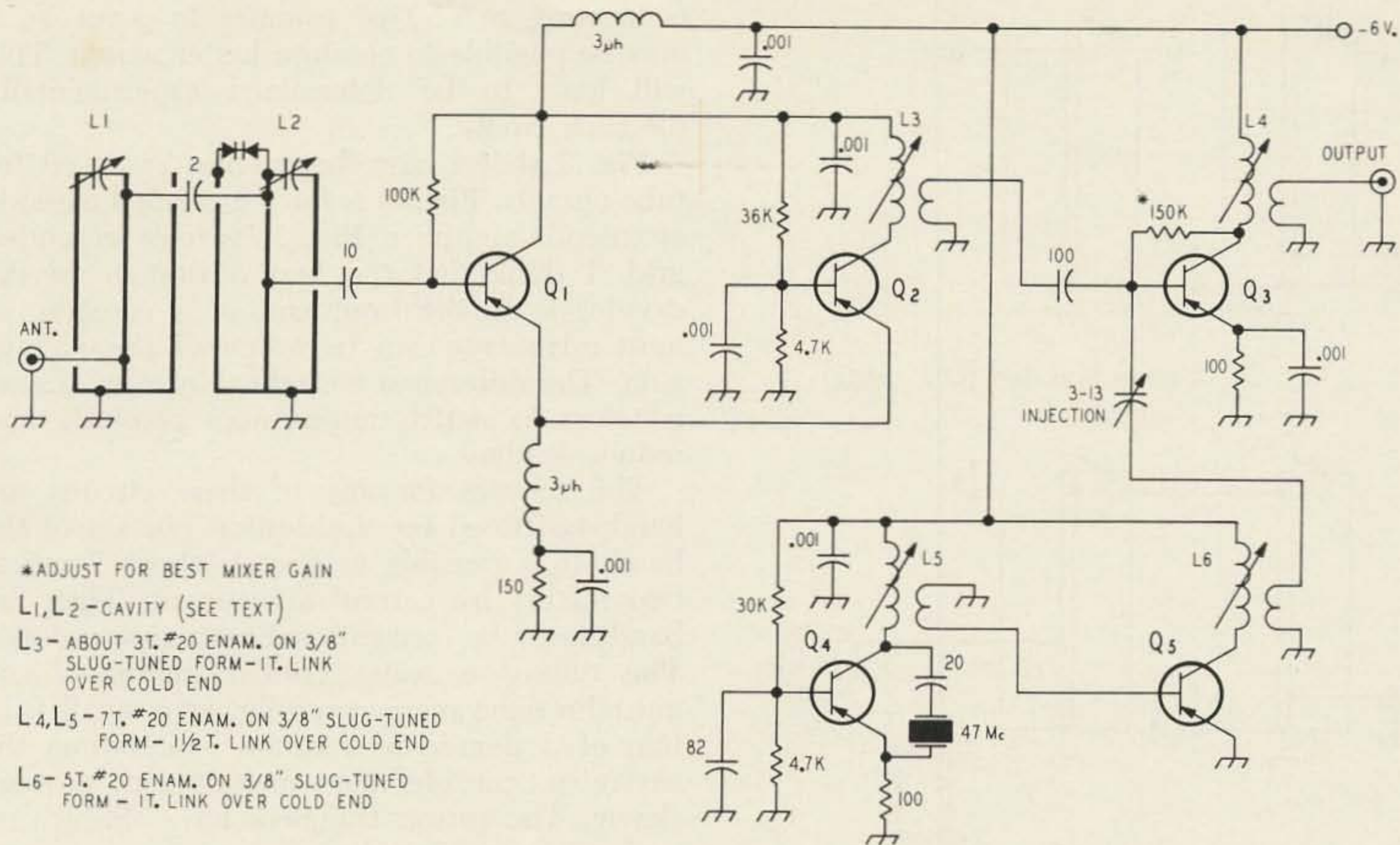


Fig. 2. Low-noise two meter transistor converter. Q1 and Q2 are 2N2360, 2N1742, 2N2495, etc. Q3, Q4 and Q5 are VHF transistors such as 2N2084, 2N1743, etc.

al signal, this means the difference between Q5 copy and no copy.

Getting back to construction of cavities, I mentioned before that a cavity is nothing more than a glorified can with a rod in the center. So why not use a can with a rod in the center? The tin plated soft drink cans (12 oz.) are just about the right size for a two meter cavity. They are easy to solder to and are easily available. The rod can be a length of copper tubing of about $\frac{1}{8}$ " or $\frac{1}{4}$ " diameter, available from auto supply stores. The rod is soldered to the bottom of the can in the center. Holes are drilled for the proper taps in the side of the can. The cavity is tuned with a ceramic trimmer of about 5-20 pf for the two meter version. A six meter cavity can be made by soldering two cans together after removing the bottom of one can, and tuning it with a 7-45 pf trimmer. The taps should be twice the distances given for the two meter cavity as impedance depends on distance relative to overall length. Some experimenting with the taps will produce an optimum point. Average distances are given as a starting point, and will work quite well, but each cavity should be adjusted for best s/n ratio. Fig. 1 shows the basic construction.

As for practical applications, Fig. 2 shows a transistorized two meter converter that can be built using cavity input. Transistor Q1 is an emitter follower and is used to match the impedance to the grounded base amplifier, Q2.

The emitter-coupled circuit has a small amount of loss because of slight impedance mismatch, but it is low enough to be negligible, and the direct coupling makes up for some of the losses found in coupling networks. The circuit shown is capable of a sensitivity of better than .1 microvolt for a readable signal. I have not actually built the converter as shown, but have on separate occasions built both the two transistor preamp and a two meter converter using this basic design and there is no reason why the two combined shouldn't work as well or better than the separate circuits. The cavity preamp was built exactly as shown and the output is taken from point X, in case someone would like to build a preamp alone. The converter is the same as one that I built using conventional tuned circuits, except that the rf amplifier is replaced by the cavity/Q1-Q2 combination. The if output of 50 mc was chosen to work into a six meter converter for mobile use. With the use of cavities, the if could be changed to any frequency from six meters down to the broadcast band by just changing the crystal, and L4, 5, and 6 to the correct frequency. Two diodes, wired back to back are used to protect the transistors from strong signals. Any small general purpose diodes with a very low PIV will work. Don't underestimate the voltage gain of a cavity. The Q can run anywhere from 50 up into the thousands, depending upon the load-

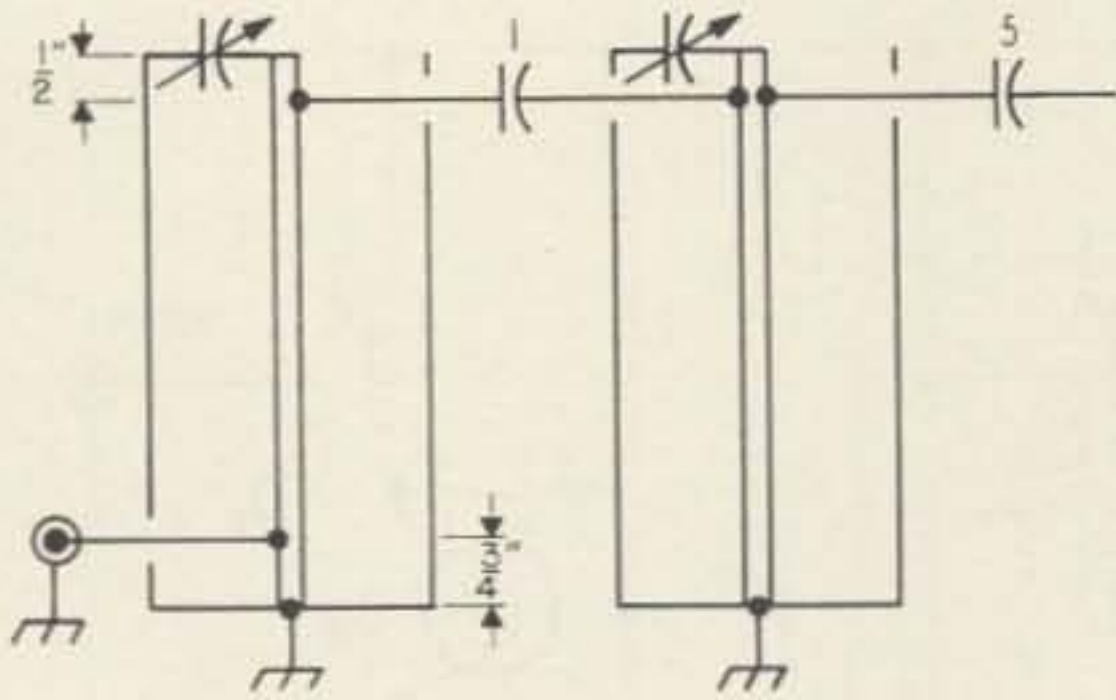


Fig. 3a. Connection for tube grid.

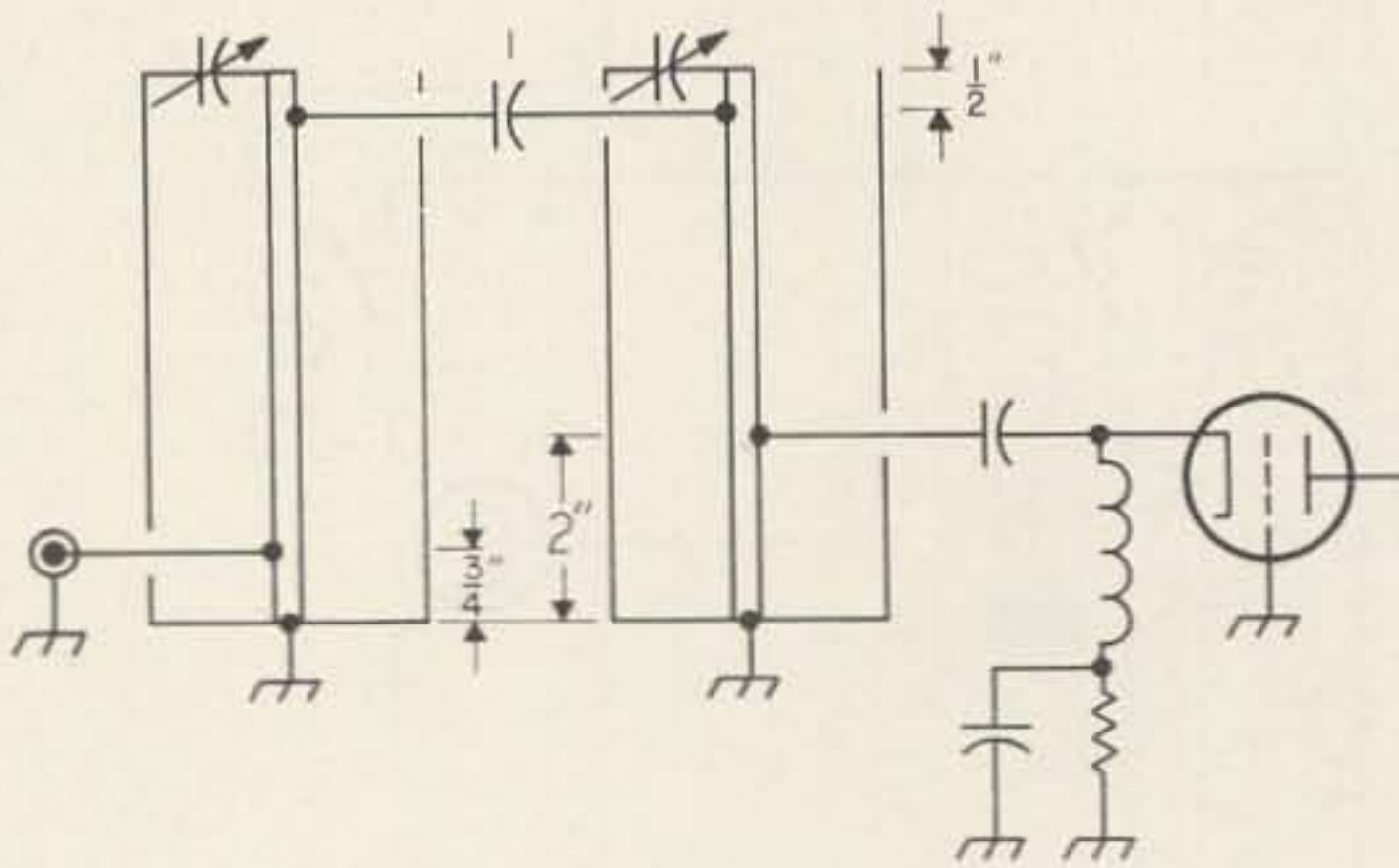


Fig. 3b. Grounded grid input.

ing. With a Q of 1000, 10 millivolts input can give up to 10 volts output, or enough to destroy the base-emitter junction of a transistor. Think about that for a second. 10 millivolts isn't much when you consider the leakage of an antenna relay at this frequency. When the diode breaks down, it loads the cavity so that the Q, and the voltage gain, drops to a very low value. This should happen before the base-emitter junction breaks down as the diodes are at a higher impedance, therefore a higher voltage point.

The loss can be reduced more by using a glass piston trimmed instead of a ceramic trimmer. Just drill a hole by the top of the cavity and mount it. A BNC connector can be mounted on the cavity for the input, if desired. By

connecting a 5-50 pf trimmer to point Y, it may be possible to obtain a better match. This will have to be determined experimentally for each cavity.

Fig. 3 shows how the cavities are used for tube circuits. Fig. 3a is for a grounded cathode or cascode amplifier. Fig. 3b is for a grounded grid. I think that the best advantage of the cavities is in the front end of a cascode, as most advantage can be taken of the voltage gain. The difference is slight, however, if care is taken to match impedances carefully and reduce loading.

The cavities for any of these circuits are bandpass tuned for the desired portion of the band. It is possible to stretch about 2 mc at two meters by careful adjustment. They are bandpassed by conventional tuning procedures. The tuning is quite critical, however, and must be done more carefully, as a small fraction of a degree of rotation can detune the cavity a considerable amount, so proceed slowly. The piston trimmers have the advantage of finer control.

The physical mounting of the cavities are easily accomplished by the use of small copper straps. The outside of the can is cold for rf and can be grounded at almost any point or points. The simplest way is to mount the can on its side and strap it to the chassis at both ends, making doubly sure to make good contact. Mounted this way, they take up little space.

I hope that I have cleared up some of the mystery of cavities for you. It would be nice to see more hams taking advantage of the benefits of cavities, and saving money by not having to buy that gold-plated converter that you were going to mortgage the shack to buy, in order to gain 1/2 db. Spend the money on a better beam instead, and improve your transmitted signal, and you will be better off. Get out your can opener and good luck.

... WA2INM/1

NOW

EXCLUSIVE 66 FOOT **MOR-GAIN** 75 THRU 10 METER DIPOLE

NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS

Fully Air Tested — Thousands Already in Use

NEW MODELS

MULTIBAND SECTIONS FULLY GUARANTEED PAT APPLD FOR

40% Copper Clad wire—Under three lbs. Air Weight—Rated for full legal power—AM/CW or SB—Coaxial or Balanced 50-75 ohm feed—VSWR under 1.5 to 1 at most heights—Rust resistant hardware—Drop-proof insulators. Completely assembled, ready to put up. Model 75/40 Amateur Net **\$23.80**. Terrific Performance—No coils or traps to break down or change under weather conditions—Fully Guaranteed. MODEL 75/40HD (HEAVY DUTY DIPOLE) **\$26.00**—RATED 3KW PEP—66'.

NEW SUPER HEAVY DUTY DIPOLES 66' LONG. RATED 4KW PEP-2000 POUND BREAKING STRENGTH—DELTRIN CENTER & END INSULATORS—OUT PERFORM FULL SIZE DIPOLES;	MODEL 40/20..... \$17.00 • 36 FEET LONG
75/40 SHD \$30.00 ; 75-20 SHD \$34.00 ; 75-10SHD \$45.00	MODEL 80/40CW..... \$25.80 • 69 FEET LONG
	MODEL 75-10..... \$40.00 • 66 FEET LONG


ORDER DIRECT OR WRITE FOR FULL INFORMATION

MOR-GAIN


P.O. Box 6006
Alexandria, Virginia 22306

Phone: 703-768-7766; Nights and Holidays 703-780-2171

OR THRU YOUR FAVORITE DISTRIBUTOR



VHF AMATEUR COMMUNICATION ANTENNAS

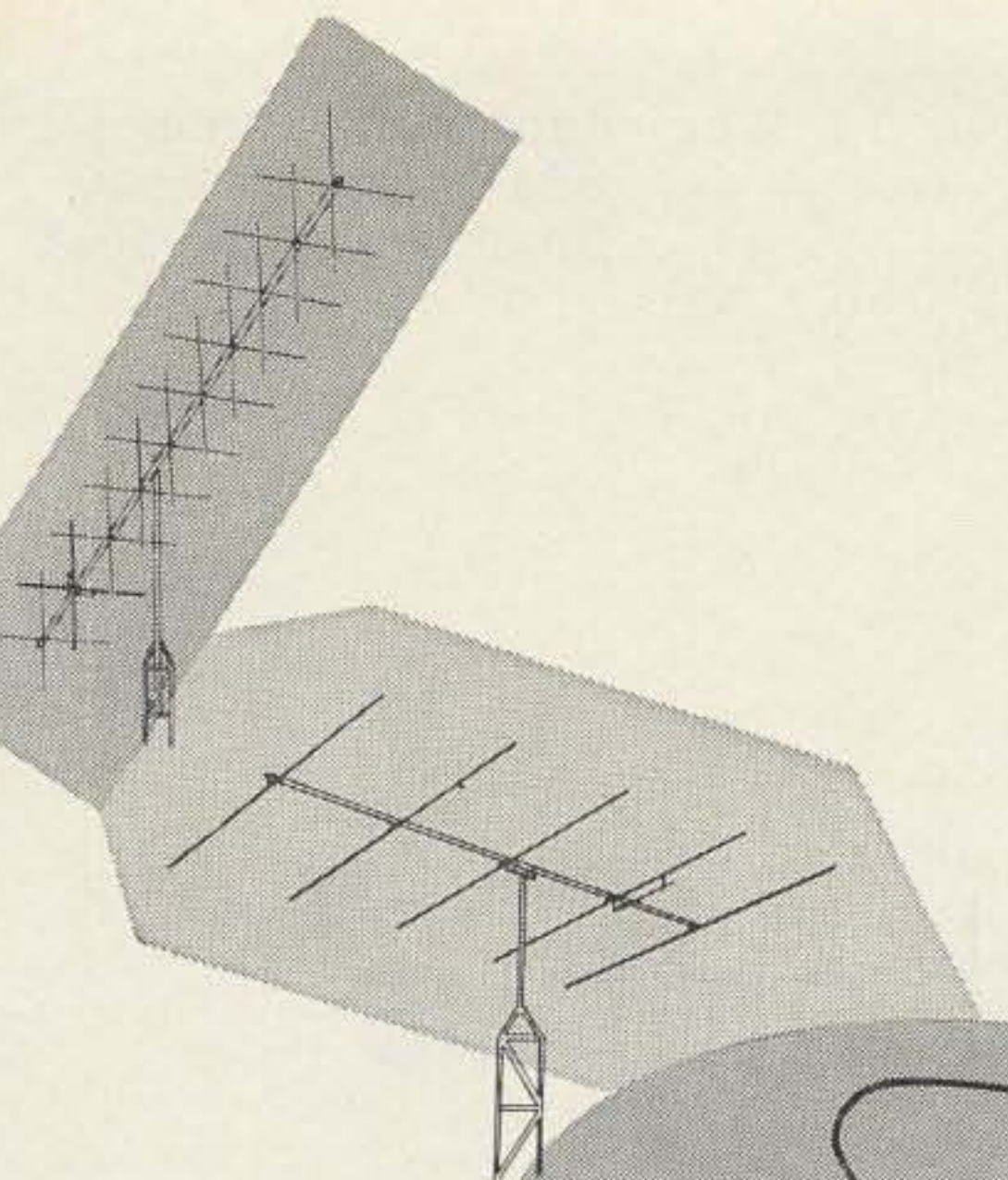

MULTI-POLARIZED TWIST

For tracking, back scatter, Moonbounce
Priced from \$29.50 to \$186.00

PERFORMANCE PROVEN 6 METER BEAMS

3-5-6-10 elements
Priced from \$14.95 to \$49.50

THE BIG WHEEL

Omnidirectional gain antennas
Priced from \$8.95 to \$55.55

COLINEAR ARRAYS

16-32-64 elements
Priced from \$9.85 to \$133.50

MULTI-ELEMENT YAGIS

Single, dual, quad stack arrays
Priced from \$9.75 to \$84.50

SQUALO MOBILE & FIXED ANTENNAS

Omnidirectional, horizontally polarized, square
antenna. For car top or base station mounting.
Priced from \$9.45 to \$66.50

MAKE YOURS A REAL SIGNAL . . . use a CUSH CRAFT ANTENNA!

Whether you are Tracking Satellites, Moon Bouncing, DX-ing, Rag Chewing or Winning Contests — you will do it better, more efficiently, and at a lower cost with a **Cush Craft Antenna**. You will have a signal that really radiates when you buy **Cush Craft . . .** the antennas with a "PATTERN OF FIRSTS" in Amateur Communications.



BUY FROM YOUR DISTRIBUTOR
OR WRITE FOR FREE CATALOG

621 HAYWARD ST., MANCHESTER, N. H.


The 4-element Rhombus

An antenna's gain is determined primarily by its configuration. For example, a two element parasitic beam characteristically exhibits about a 4-5 db gain over the usual dipole standard. It will give only 4-5 db, and no alteration to the feed point or spacing will materially increase the gain. A third element properly spaced will add some gain. However, diminishing returns reduce the amount of gain to a smaller percentage than when the second element was added to the driven dipole. Consequently, a practical point is reached where the yagi array supplies the greatest benefit, and further element additions produce an extremely cumbersome system without corresponding increase in gain. The normal yagi is therefore 3-4 elements on a 16-20' boom with a gain of about 5-8 db.


For increased gain above a well tuned yagi, the amateur must turn to a different array for 9-13 db gain.

The rhombic antenna several wavelengths


long is acknowledged to be a desirable antenna. It has superior radiation and gain qualities. With this in mind, it was decided that a rhombus (one wavelength in periphery) in a vertical plane coupled parasitically to three similar units properly spaced and tuned would produce an outstanding signal. The large area within the closed loop intercepts a greater portion of the radiated magnetic field thereby sampling more signal. Since the antenna's receiving quality is directly proportional to the gain, it follows that the antenna will radiate a great amount of rf energy. For the low vertical angle of radiation, the feed point remains at the lower apex of the rhombic. The normal resistive terminations are deleted. Since the maximum field of radiation is perpendicular

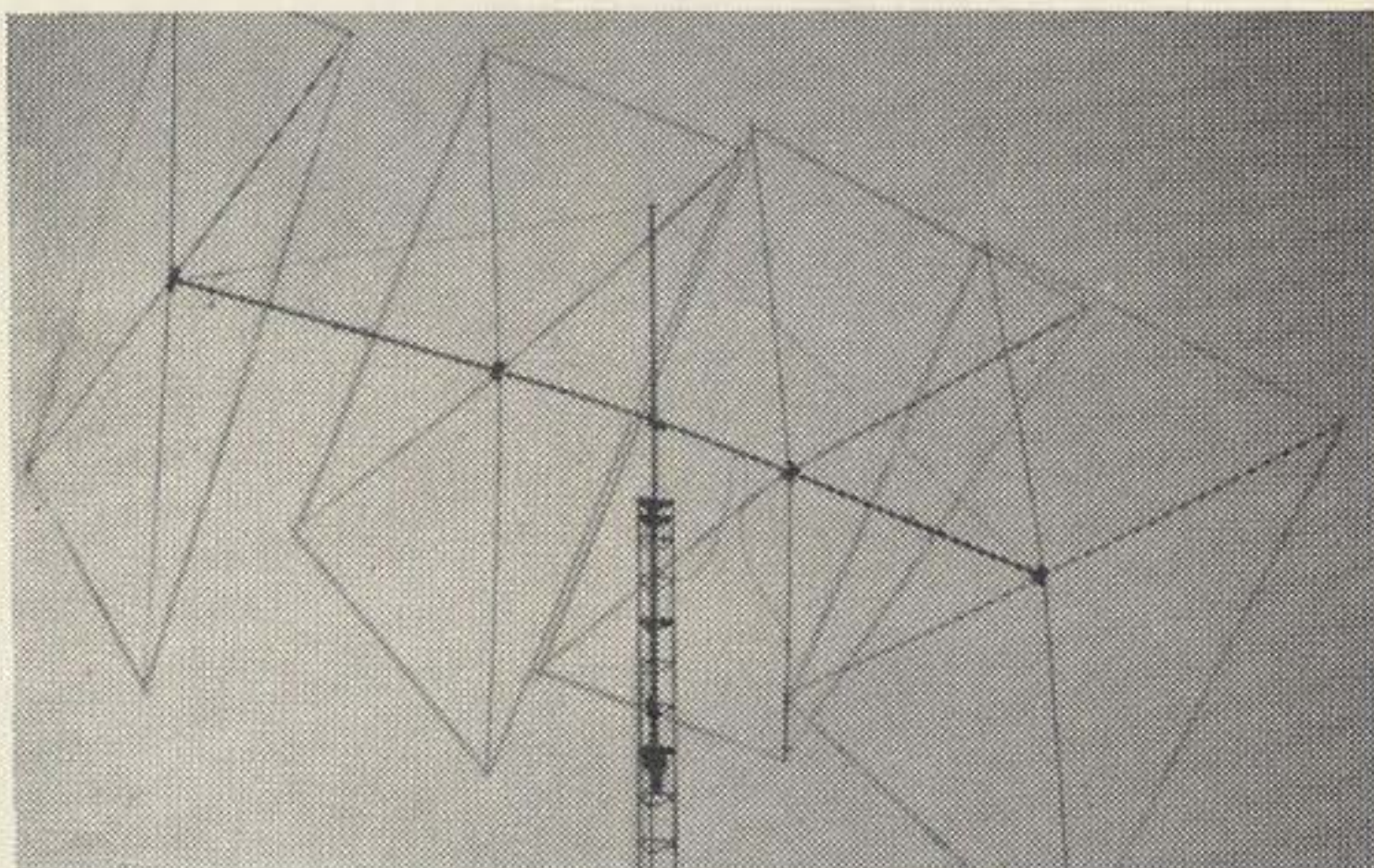


4-element rhombus.

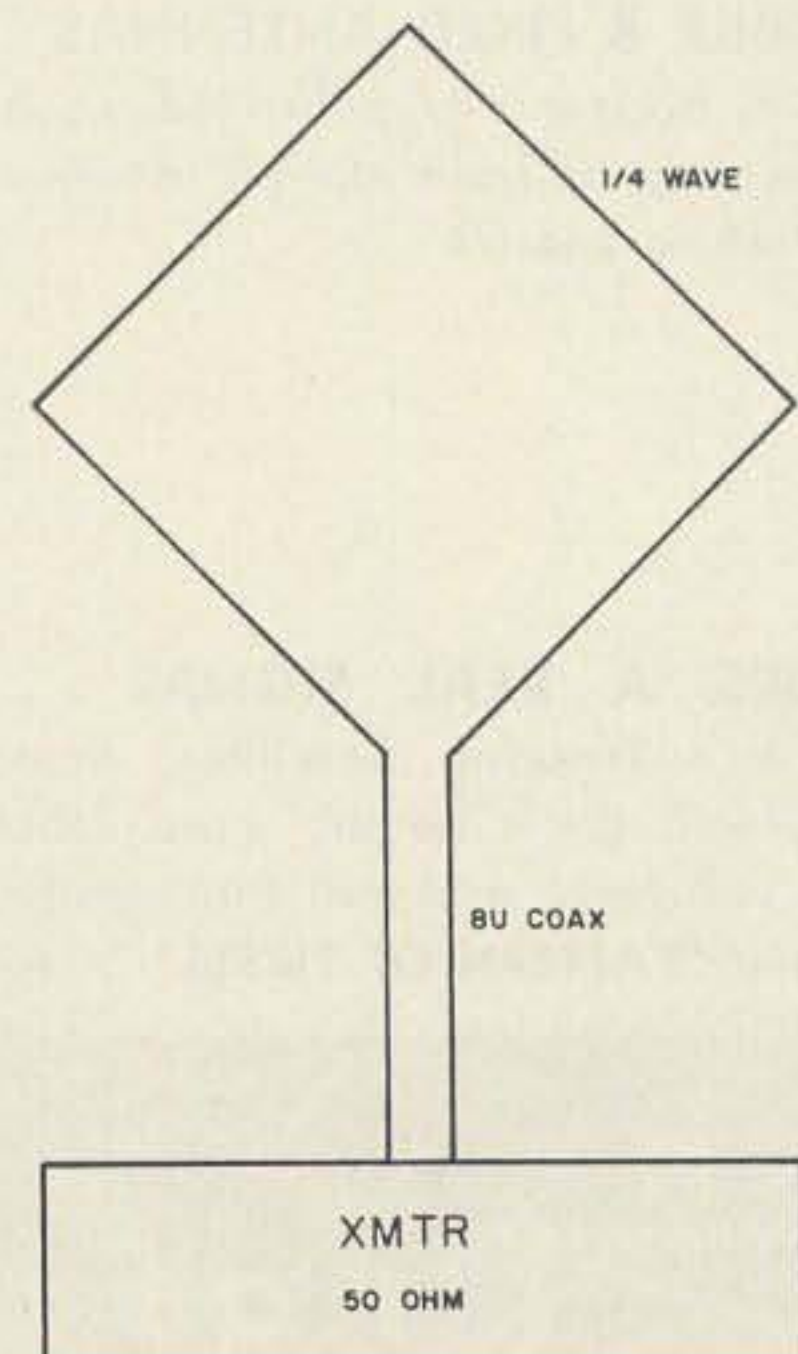


1ST DIRECTOR
61'-11" PERIMETER

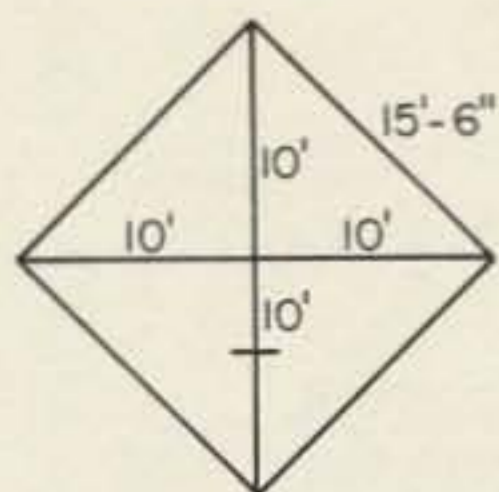


2ND DIRECTOR
64'-10" PERIMETER

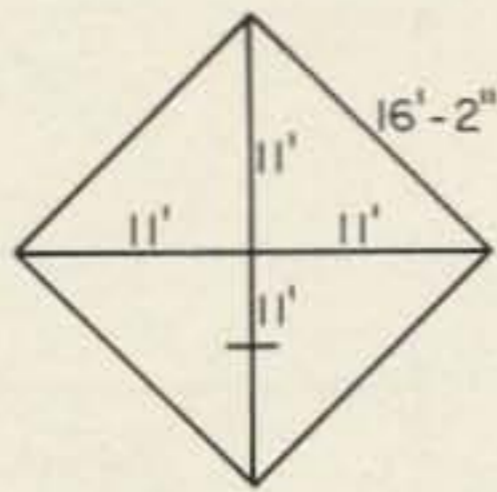

DRIVEN
67'-9" PERIMETER

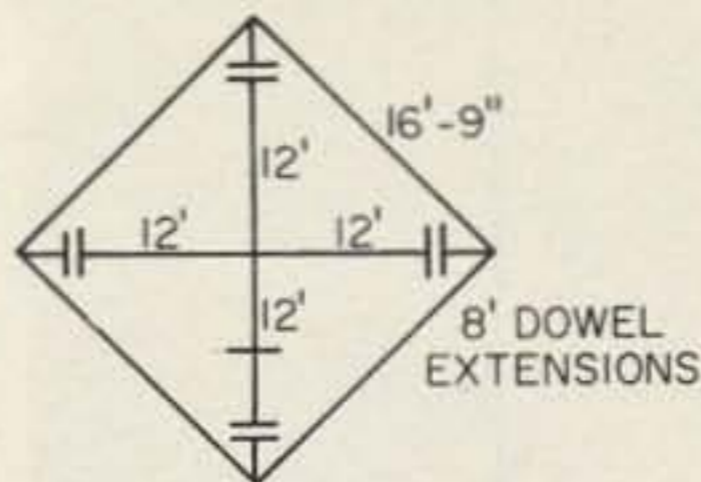

REFLECTOR
72' PERIMETER

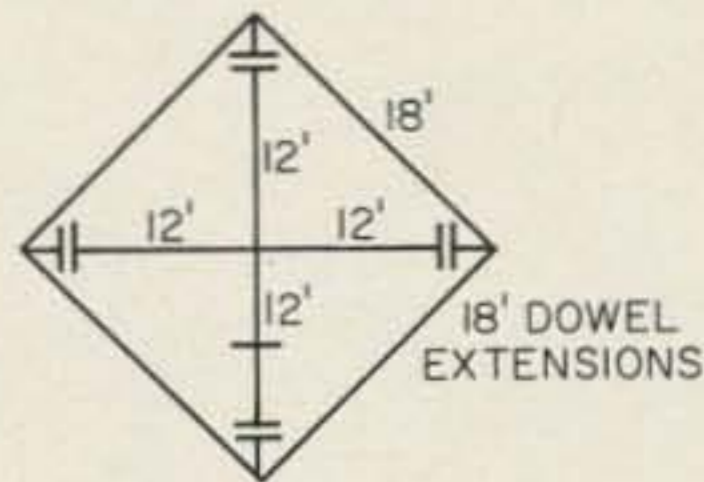

Dimensions of rhombus.

to the plane of the array with insignificant minor lobes, it is ideally suited to the rotatable installation. On the air tests have shown the front-to-side ratio to be 30-40 db.

The entire unit is home-brew and utilizes aluminum spreaders for strength and durability with no detectable sacrifice to antenna input characteristics. Contrary to popular belief, signals were not spuriously radiated or absorbed due to the aluminum cross arms. Tests were made by a local amateur (WA2KQZ) residing several blocks away for harmonic indications (within the range of a 75A4 receiver) and none were detected. The antenna reflected zero reactance when coupled to various measuring devices and exhibited a near perfect resistive termination. Since maximum signal transfer was of prime importance, the unit was designed for one band only. Compromise SWR was not to be tolerated since no multiband antenna performs as well as an antenna designed for one-band operation.


Construction

A boom length of 30' worked well and permitted a spacing of 10'; however, 8' between elements will exhibit properties of similar value with a somewhat lower input impedance and gain factor. Should a perfect 50 ohm terminus outweigh the desire for maximum gain, driven element spacing with respect to the reflector element could be attempted. Anticipate lower gain but receive a better transmission line-antenna match with the smaller spacing due to the closer parasitic element coupling effects.


The spider units were built around four 2x12" squares of 3/4" plywood preserved in creosote solution. Four aluminum 1 1/4" pipe angles with set screws provided spider-boom securement. Holes equal in diameter to the range openings were drilled in two spider units to facilitate placement on the boom. Light tubing clamps were positioned on each plywood square so that the aluminum spreaders would be properly oriented and perpendicular to each other. A 12' length of 3/8" tubing

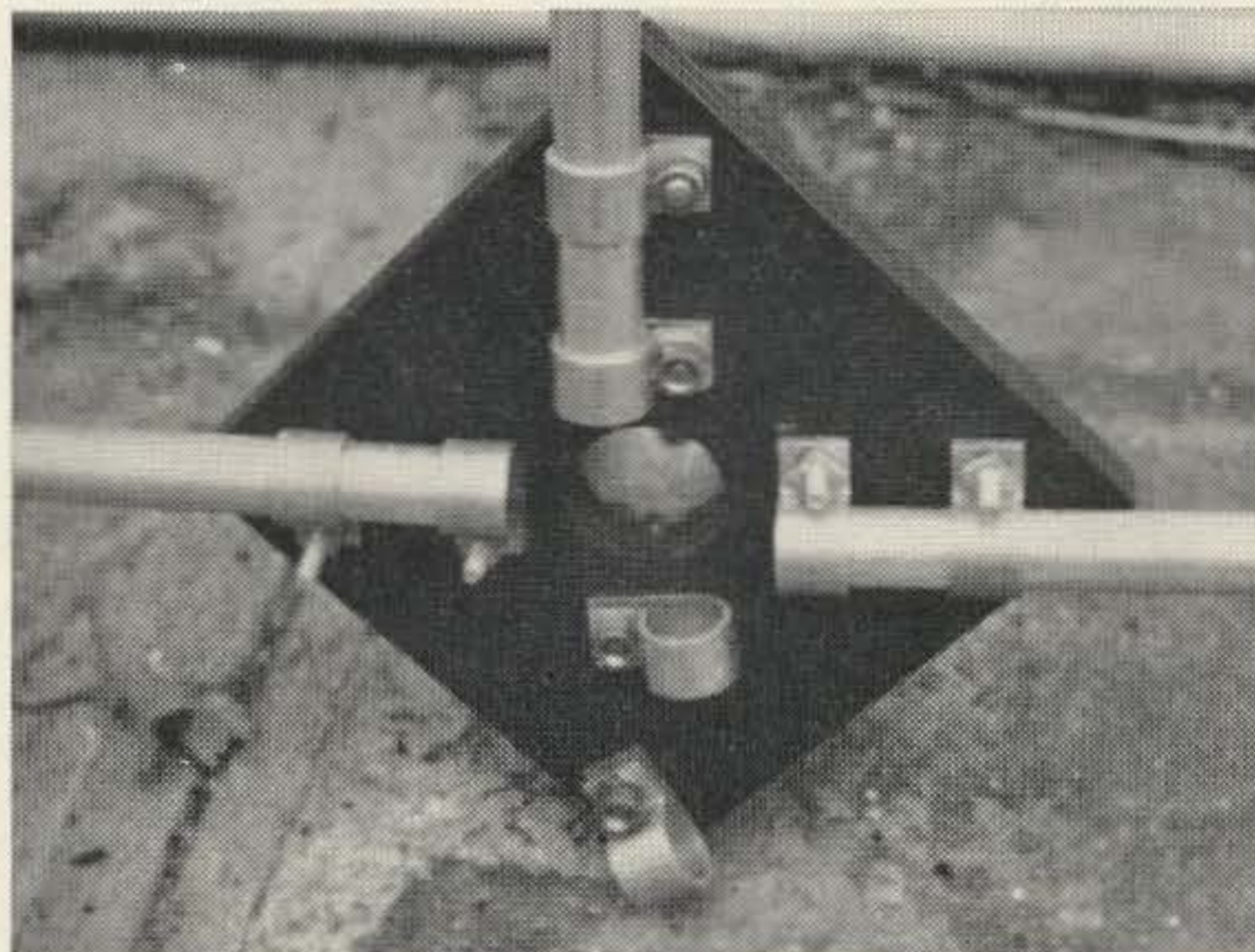0.058" wall was chosen for each upper mast vertical spreader support since the greatest stress was upon this unit. A 6' length of 3/8" tubing was chosen for the lower vertical portion. An additional 6' length of 3/4" tubing 0.058" wall was telescoped several inches into the larger unit for ease of construction. The two horizontal and one vertical (upper) portion of the four systems were assembled at roof level and then raised to 6' with the tower or supporting structure. While still within arm's reach, the 6' length of 3/8" tubing was installed into each spider unit and secured. The antenna was then raised another 6' and the length of 3/4" tubing installed by telescoping into the larger unit. A 1" hose clamp completed the mechanical bond. This telescoping flexibility will be particularly welcomed by those with no tilt-over tower or long extension ladder facilities.

In order to insulate the #14 formvar coated copper wire from the aluminum, dowels were cut, boiled in paraffin to increase their insulating quality, and installed into each spreader end. The 3/8" and 3/4" tubing requires 3/4" and 5/8" dowel respectively. Screw-in TV type insulators were installed in each dowel which not only provided isolation but assisted



Details of center support.

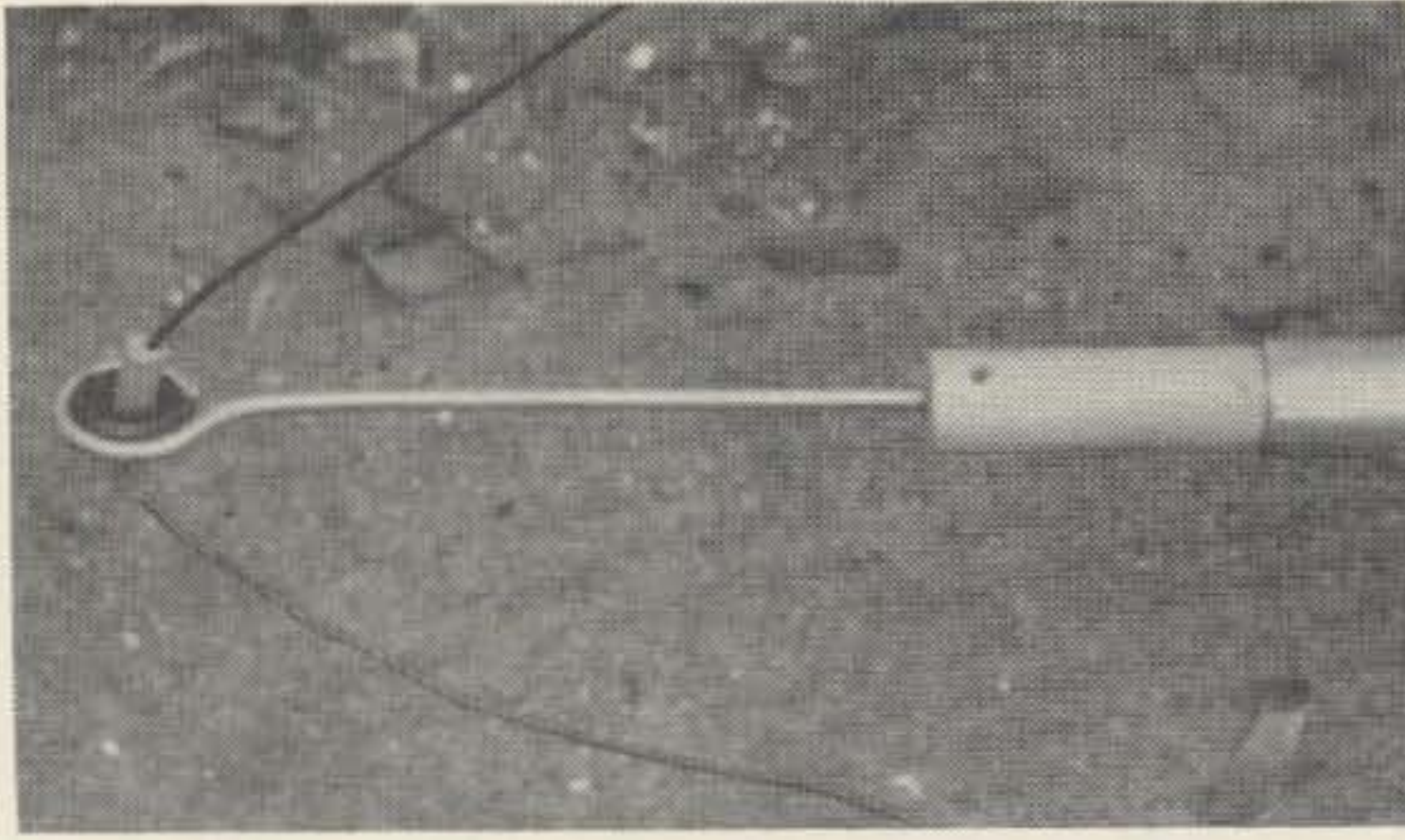

Detail of spreader.


in subsequent adjustments of spreader breadth. Where the formvar wire passed through the standoffs, a length of polystyrene 8U insulator was slipped over the wire. The inner conductor insulator not only provided additional isolation, but tended to soften the corner angles thereby reducing radiation loss due to the otherwise sharp bend angles. After final adjustment, each standoff was squeezed closed with a plier and further movement was prevented.

Rather than measure each rhombus leg individually, four separate lengths of twine were cut which corresponded to one side of the four antenna elements. This aided immeasurably when leg lengths were being determined. One end of the twine was placed at the uppermost vertical support and the other end swung in a pendulum-like motion. Each leg was adjusted and pulled taut using the premeasured string as the reference. Error was kept to a minimum. The screw-in standoffs were adjusted slightly to provide the proper length and tension and insured a true geometric figure. Balance was the key to the proper design and careful attention was given to the symmetry of the array.

The rhombus is a balanced system electrically and the transmission line should also boast balanced properties; however, coaxial cable, inherently unbalanced and not ideally suited to this installation, was used with no negligible loss. Simply solder the center conductor and shield to the two antenna wire terminations at the lower apex angle and coat the connections with liquid polystyrene. Dampness will have less effect on the loading.

The antenna reflected about 60-65 ohms when at roof level and varied slightly when raised to the operating height. This tended to indicate that the array was suitable to installations where height cannot be easily at-

TUBING SIZE LAYOUT

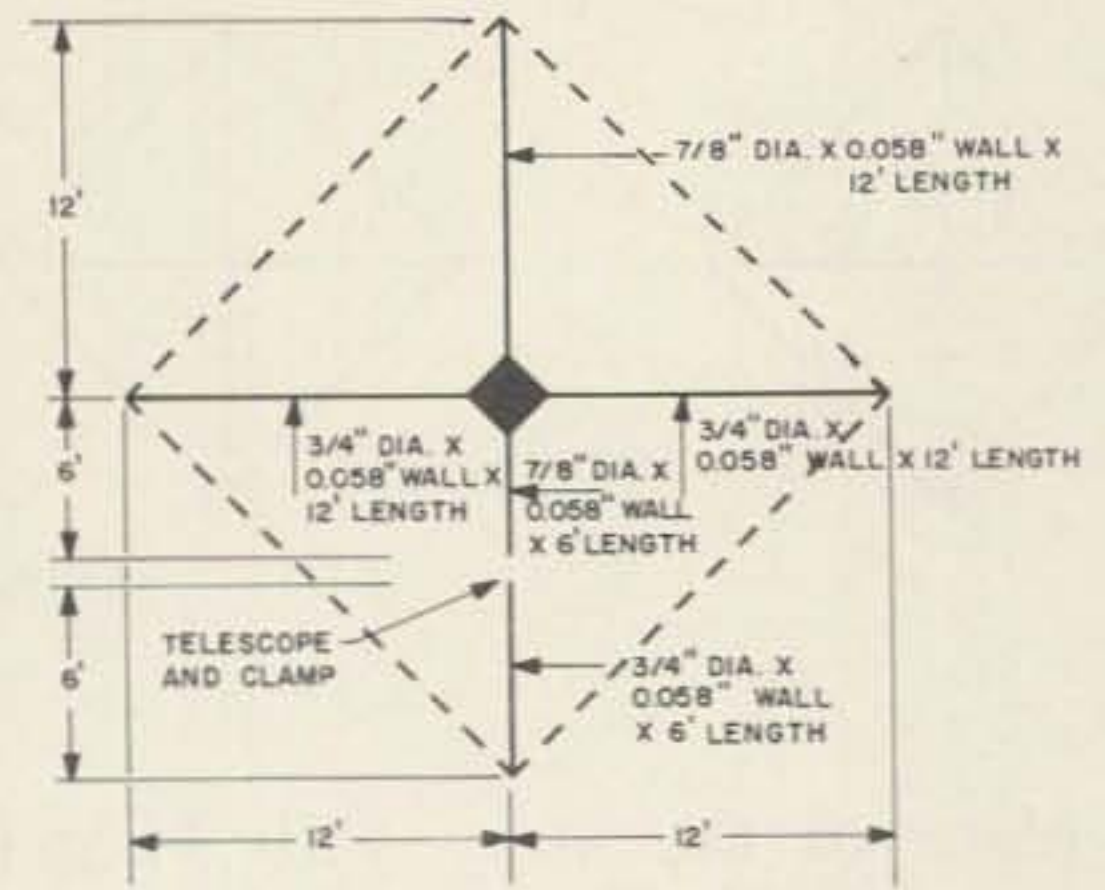

tained. Many apartment house and limited space dwellers could easily rotate the system several feet above the roof level with little sacrifice to radiation input characteristics; however, for the low angle of radiation and maximum signal projection a height of 60' and more is necessary. Although polarization shifts when reflected from the ionized layers, the initial low vertical angle of radiation provides the slight edge over the standard horizontally polarized quad array of comparable design. For line-of-sight transmissions (to a horizontal array) cancellation affects due to cross polarization are evident, but the DX signal losses are infinitesimal and are of no concern.

The dimensions given are to resonate the antenna system at the 14.270 MC mark. For operation in the CW portion of the spectrum, add one foot to the perimeter thereby lowering the resonant frequency. Insure that equal increments are also added to the other elements to maintain inductive and capacitance reactance balances. The "Q" or bandwidth of the system is reasonably low and will allow for operation over the entire amateur portion of 20 meters, but losses can be expected with major movements away from the resonant frequency. An SWR bridge will indicate the tolerances within which one's transmitter will properly perform.

. . . K2IRK

Parts List

- 6 12' lengths 7/8" 0.058" wall tubing
- 10 12' lengths 3/4" 0.058" wall tubing
- 4 1 1/4" pipe flanges (aluminum)
- 16 7/8" aluminum clamps
- 16 3/4" aluminum clamps
- 4 12 x 12" 3/4" plywood (creosote soaked)
- 4 spools #14 magnet wire (heavy formvar insulation)
- 16 7" standoff insulators (screw-in)
- 4 length of 3/4" dowel
- 12 Lengths of 5/8" dowel
- 4 aircraft hose clamps 3/4"
- 32 1/4 x 3" bolts
- 32 1/4" nuts
- 32 lock washers

Now!



for discriminating amateurs
who are satisfied
with nothing less than *THE VERY BEST*

McCoy SINGLE SIDE BAND FILTERS


The GOLDEN GUARDIAN (48B1)

TECHNICAL DATA

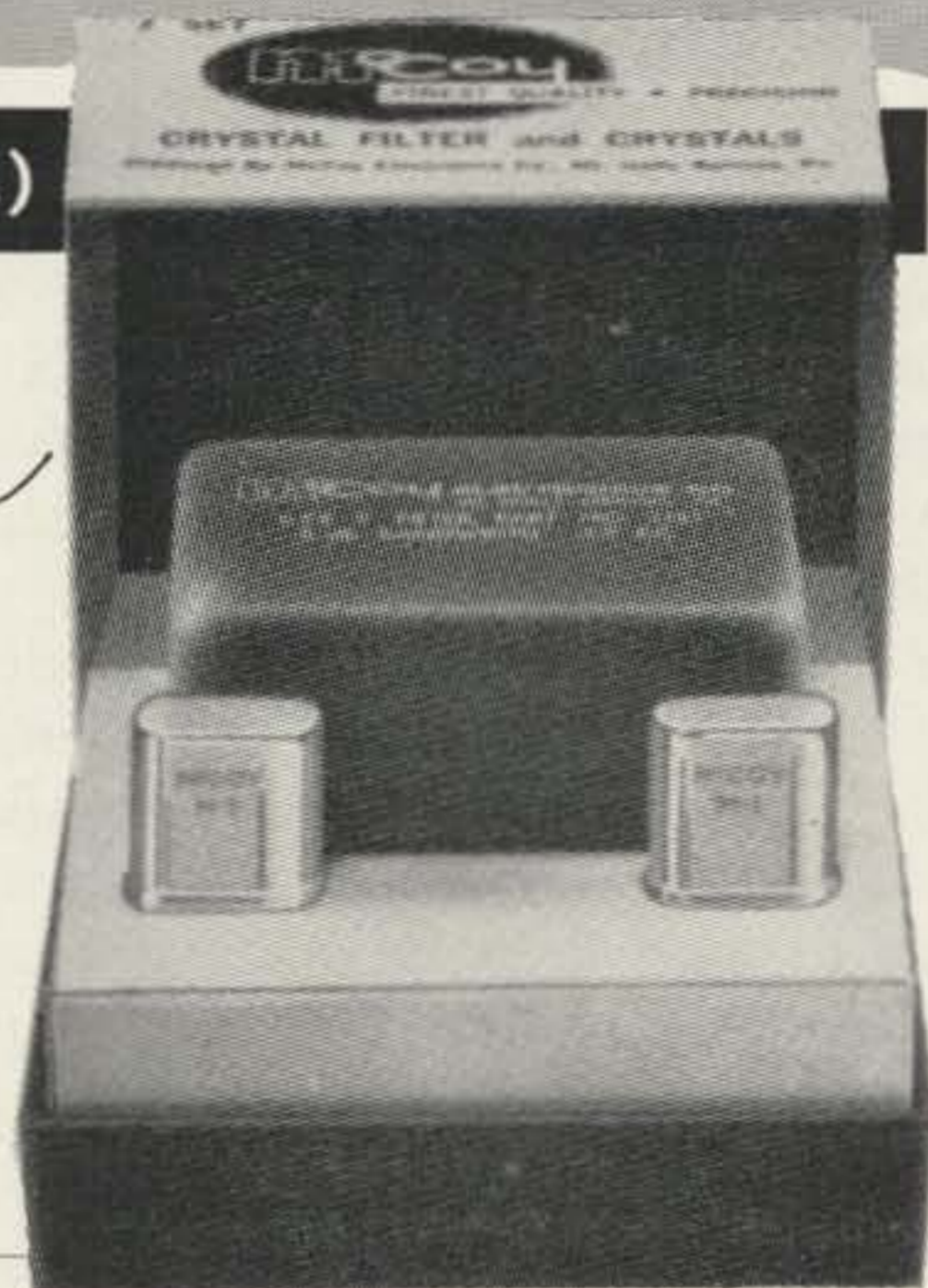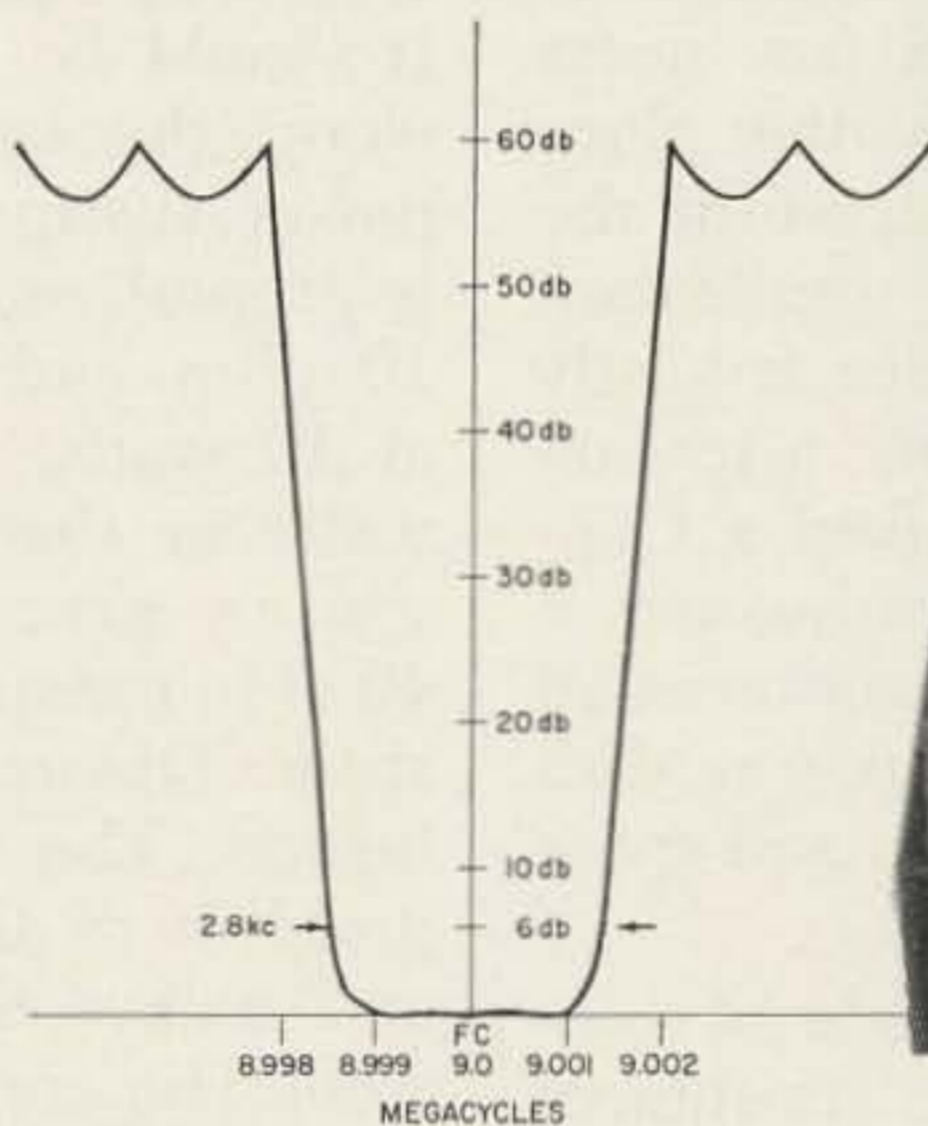Impedance: 640 Ohms in and out (unbalanced to ground)
Unwanted Side Band Rejection: Greater than 55db
Passband Ripple: $\pm .5$ db
Shape factor: 6 to 20db 1.15 to 1
Shape factor: 6 to 50db 1.44 to 1
Package Size: $2\frac{7}{16}$ " x $1\frac{1}{32}$ " x 1"
Price: \$42.95 Each




The SILVER SENTINEL (32B1)

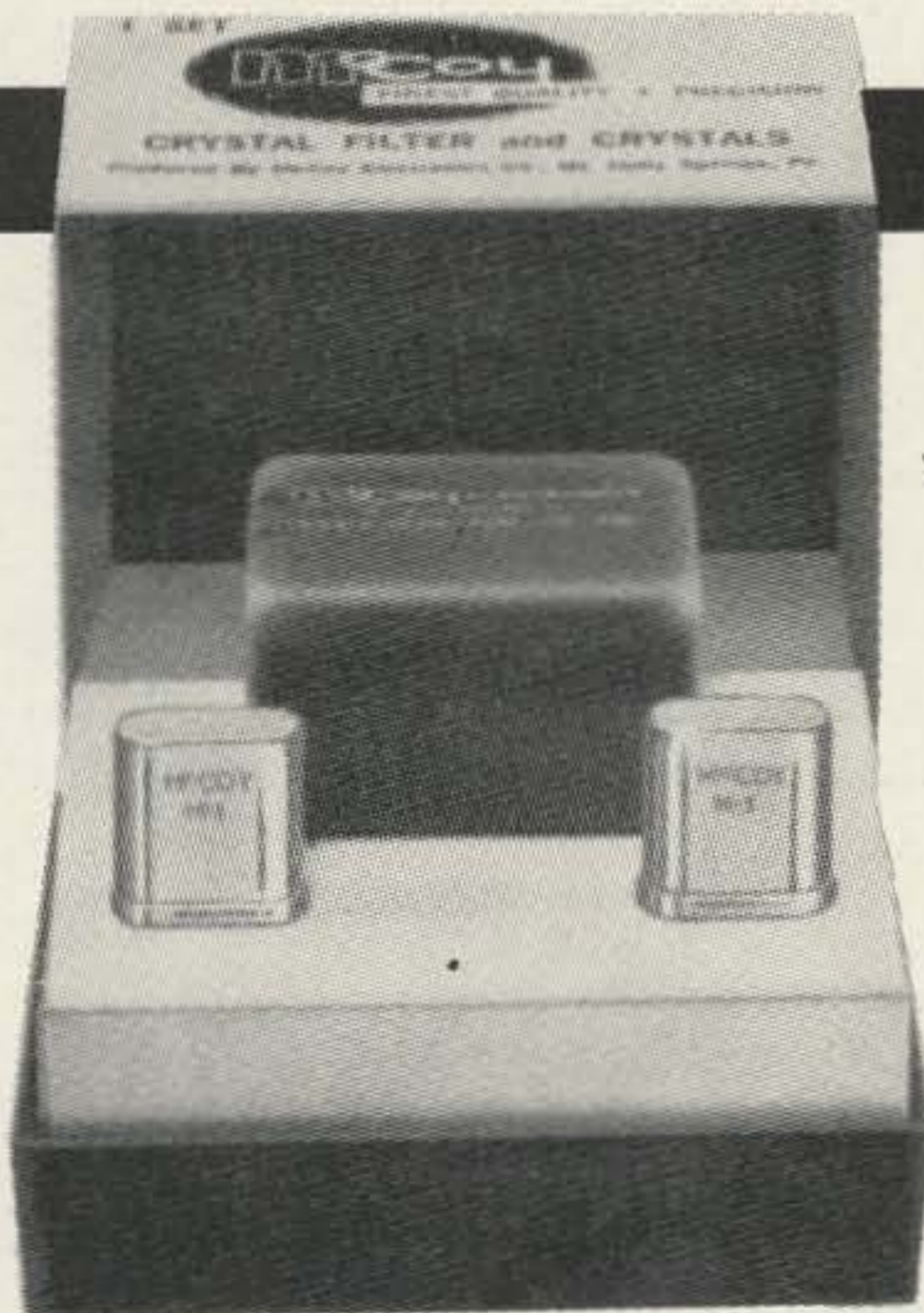

TECHNICAL DATA

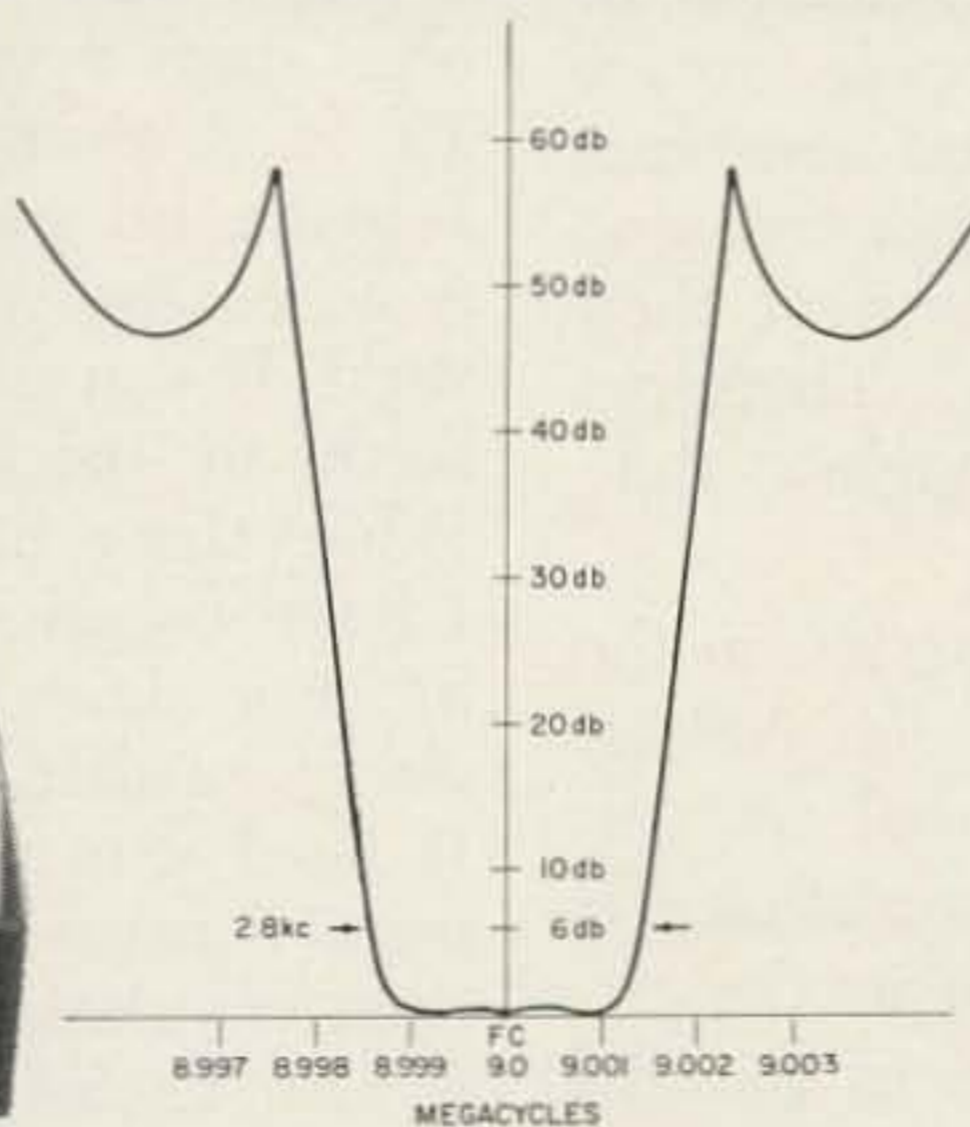Impedance: 560 Ohms in and out
Unwanted Side Band Rejection: Greater than 40db
Passband Ripple: $\pm .5$ db
Shape factor: 6 to 20db 1.21 to 1
Shape factor: 6 to 50db 1.56 to 1
Package Size: $1\frac{3}{4}$ " x $1\frac{1}{4}$ " x 1"
Price: \$32.95 Each



Both the Golden Guardian and the Silver Sentinel contain a precision McCoy filter and two of the famous M-1 McCoy Oscillator crystals. By switching crys-

tals either upper or lower side band operation may be selected. Balanced modulator circuit will be supplied upon request.

Both sets are available through leading distributors. To obtain the name of the distributor nearest you, or for additional specific information, write: Dept. E-11



MCCOY ELECTRONICS COMPANY

Mt. Holly Springs, Pa.

Tel. 717-486-3411 TWX: 717-486-3400

A SUBSIDIARY OF OAK ELECTRO/NETICS CORP

A Power Decade Resistor

As most technicians and hams are all too well aware, the average resistor decade or substitution box is only rated for a few watts power dissipation at most. Usually the place where one needs the adjustable feature of the decade box the most is just the application where the power rating of the device is vastly exceeded. This was brought to my attention one day when a fellow student cooked a General Radio decade resistor while adjusting a voltage divider in a laboratory experiment at school. I decided that I needed a power decade resistor, and since these are rare and quite expensive, I decided to homebrew it.

One of the most common methods of constructing decade resistors is to use resistances of 1, 2, 3 and 4. With these four values, one can obtain any value between 1 and 10. Usually a special rotary switch such as that made by Mallory (or a special connection of a standard 11 position double pole rotary switch) is used to select the desired resistances. Rotary switches, however, are not too well suited for power application, because of their limited current carrying capacity. Therefore the simple circuit in Fig. 1 using toggle switches was put together.

Note that the resistors are all in series, in the natural order 1, 2, 3, 4 and that each resistor has a SPST toggle switch in parallel with it. With all the switches closed, the resistance is zero; to put a particular resistance in the circuit, one merely opens the switch in parallel with that resistor. The desired value of re-

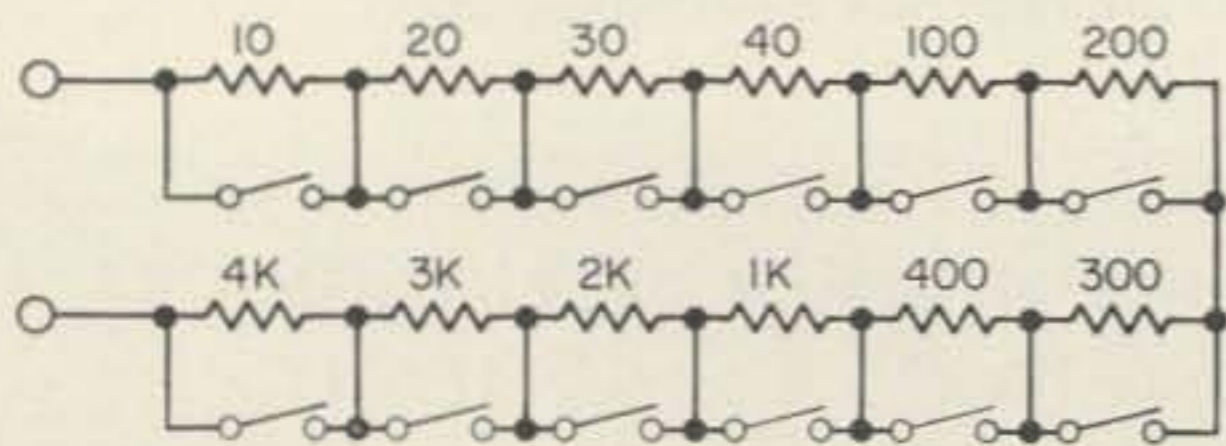


Fig. 1. Schematic diagram of power decade resistor.

sistance is made up by adding the various values up until the desired total is reached. It should be remembered that in a series network, the voltage across (and therefore the power dissipated by) any particular resistor is proportional to its resistance. If you have a 10 ohm and a 20 ohm resistor, each rated at 10 watts, in series and try to dissipate 20 watts in the combination, you will find that you are actually dissipating 13.3 watts in the 20 ohm resistor and 6.7 watts in the 10 ohm resistor. Obviously the 20 ohm resistor is overloaded. The use of toggle switches solves the problem of the switch contact current rating and makes the wiring of the unit simple as well. The cost of the unit using toggle switches is cheaper than that of the unit using rotary switches.

A decade box using three decades and adjustable from 10 ohms to 11,100 ohms in 10 ohm steps was constructed in a standard $5 \times 10 \times 3$ aluminum chassis. The units which I made all used 10 watt resistors, but there is no reason why one cannot use any size desired. If you use 10 watt resistors, the cheapest seem to be the PW series made by IRC. While these have a nominal tolerance of 10%, I have found very few that are off more than 5%. For short term use it was not found necessary to drill ventilation holes in the chassis. If hard use of the box was foreseen, or if it were constructed for a higher wattage rating, then ventilation would be a must. This method is also useful for making standard resistance decades using precision resistors, but it is often cheaper to buy these ready made, unless you have a supply of precision resistors of the proper values. A similar method may be used to make a capacitor decade box, by placing all the capacitors in parallel, and putting the switches in series with the capacitors. In this layout, the switch is closed to select a particular capacitor.

. . . Lyman



Leo I. Meyerson
WØGFQ

LEO SAYS: BUY DIRECT AND SAVE BIG ON THESE WRL HAM EXCLUSIVES

NEW

WVG MARK II ALL BAND VERTICAL ANTENNA

Low cost — self-supporting 10-80 meter antenna. Tunes 3.5 — 30 Mc with manual tap adjustment. Feed with 52 ohm coax. Quick installation. Amazing efficiency for DX or local contacts. Used as portable antenna also.

\$15.95

Postpaid
Continental USA

MECHANICAL SPECS:

Overall ht. — 18'. Tubing diameter — 1 1/4" to 7/16". Max. unguyed wind survival — 50 mph. — Mtg. bracket for 1 5/8" mast. Wt. 5 lbs.

ELECTRICAL SPECS:

Maximum power: 1000 watts AM or CW — 2 KW PEP. Omnidirectional. Vertical polarized.



TECH-CEIVER 6A

Low cost, compact, 6 meter transceiver

Stable superhet receiver. 5 watt transmitter, featuring PTT, using std. (Ft 243) 8 Mc range xtals, non-critical coils, plate modulation, power and modulation indicators, 10 tube performance. Step-by-step manual included. Wt. 9 lbs. 115 VAC Power supply (kit) — 15.95.

- 5 Watt input
- Sensitivity — better than 1 UV

only \$39.95 kit



- Selective — 20KC @ 6DB points
- 49-54 Mc coverage

PSA-63 POWER SUPPLY

Universal Power Supply: Powers most AM rigs up to 100 watts, SSB units — up to 200 watts, PEP. Silicon rectifiers provide both 300 VDC & 600 VDC @ 300 Ma., ICAS (210 watts total), plus 6 VAC @ 10A or 12 VAC @ 5A, plus 95 VAC @ 10 Ma. Size 11 1/4" x 4 3/4" x 6". Wt. 15 lbs. Kit — 24.95, Wired — 39.95. Opt'l cabinet — 4.95.

- Use with 30-200 watt XMTRS—XCVRS
- Dual voltage B + Fil. power-bias
- Customized units available—Extra

only \$24.95 kit



DUO-DOUBLET 84



NEW 80-40 meter diapole using proven parallel diapole principle to resonate on both bands. Requires only one 52 ohm feed line (coax not supplied). Kit includes wire, insulators, center connector & full instructions. Complete formula supplied & quick graph chart for easy adjustment. May be used on 15 meters also. SWR: Better than 2:1 at resonance — 80/40. Max. length — 123 ft.; 140 ft. for lowest CW range. Easy to install. Wt. 4 1/2 lbs. Shipped Parcel Post.


80-40 Meter Diapole
One Feed line

\$7.95

NEW

WRL'S 12R GENERATOR

\$149.95

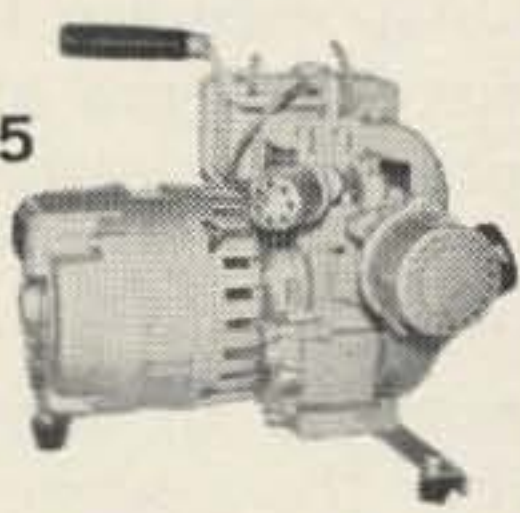

Shielded ignition. 1250 Watts, 115 VAC, 60 cy., 77 lbs. (FOB Milwaukee, Wisconsin)



SS-3 "Q" MULTIPLIER

- Notch and peak
- Self Powered
- One simple receiver connection

Int'l 115 VAC P.S. Plugs into Collins 75S-1, KWM-2 & others. Use with receivers having 455KC-IF: AC or DC powered. Adj. selectivity: 300 cy. to 10 KC. Sharp rejection (50DB) null for heterodynes. 6 1/4" x 4 1/4" x 4 3/4".

\$15.95 kit

ANTENNA TUNER MM-100



\$10.95 kit

Specifically designed to match end-fed long wire which is 1/2 wave, or multiples thereof, to 50 ohm transmitters. Panel lamp indicator. For inputs up to 150 watts SSB, 100 watts CW, 75 watts AM. 4 x 5 x 4 steel case. Reduces TVI.



\$4.98

\$6.37



WRL NUVISTOR PREAMP PRINTED CIRCUITS

PA50-2 Stage preamplifier for 6 meters. Use 2 RCA 6CW4 nuvistors. Highest grade glass epoxy board. Assembled and pre-aligned for 50 ohm input-output. Requires 60-120 VDC @ 10 MA. & 6.3 VAC. Size 2 3/4" x 2 1/4". Wired \$6.37. PA-144 Same as above except only 1 6CW4 nuvistor & for 2 meters. Wired \$4.98 (less 6CW4 tubes).

WRL

WORLD RADIO LABORATORIES, INC.
3415 West Broadway
Council Bluffs, Iowa 51504

Rush me FREE!

WRL 1965 Catalog

Reconditioned Specials!

Please rush me item _____

Enclosed is Cash Charge* COD (25% cash w/order)

*If new customer, send credit info with your charge order

Name _____

Address _____

City _____ State _____ Zip _____

Clip & Mail

Is your GDO too touchy?
Fix it!

Jim Kyle K5JKX
1236 N. E. 44th St.
Oklahoma City, Okla.

Improving The Grid Dip Meter

One of the most useful items in any ham shack is a grid-dip oscillator, usually called either a grid-dip meter or simply a dipper.

Many versions of this handy little device are available in either kit or ready-wired form; all work well, some better than others. However, many of the less expensive ones share one common disadvantage—difficulty in keeping the meter needle on-scale at the lower frequencies.

This comes about because the oscillator must be extremely active to get any kind of meter indication at the UHF end of the range, which results in so much grid current at the lower frequencies that the “sensitivity” control’s effect is greatly magnified.

In my dipper, the result was almost complete inability to keep the needle on-scale when using either the A, B, C, or D coils. It was even a problem with the 42-100 mc coil; the only place I didn’t have this trouble was on the 100-200 mc band!

However, for 15 cents and a few minutes’ time, the problem can be completely removed. The modified dipper can give an off-scale reading still, but the “sensitivity” control moves it smoothly back to the top of the dial. All who have used it agree that the modification is well worth the effort—which is actually so small as to make that statement a sort of left-handed compliment!

Though the description which follows ap-

plies specifically to my dipper, the modification is applicable to any GDO whose meter circuit resembles Fig. 1.

A glance shows the reason for the difficulty. The meter itself is a 500 microamp movement, connected through the phone jack from the bottom of the grid-leak to ground. The “sensitivity” control is simply a variable shunt for the meter. When grid current is 500 microamps or less, the sensitivity control is turned to its full-resistance position and effectively is out of the circuit. But when grid current is higher than this, the 2500 ohm pot must be cranked down to shunt the meter.

The amount of shunt resistance required on the lower ranges is somewhere near 100 ohms in most cases; trying to set a 2500 ohm pot to 100 ohms with any degree of accuracy is almost impossible, since the resistance of the pot changes some 8 ohms for each *degree* of movement, and the hand is unable to move the knob much less than 5 or 10 degrees at a time. The result is the familiar inability to set the needle; the meter jumps from zero to off-scale with almost imperceptible movement of the control.

However, if the arm of the pot is lifted from ground and connected to the negative meter terminal, breaking the connection from the meter to the phone jack in the process, and a low-value resistor is added from the top of the pot to ground as shown in Fig. 2, the circuit becomes somewhat different.

Now the grid current develops a voltage across the new resistor, and the pot-meter combination becomes a variable-scale voltmeter. Sensitivity of the voltmeter varies directly with pot movement.

My dipper develops a maximum of about 2½ ma of grid current on its lowest band. The combination of the 500 microamp meter and the 2500 ohm pot forms a voltmeter which reads full-scale with 1.25 volts input, if the pot is set for maximum resistance. These voltage and current values, in turn, prescribe the maximum value for our added resistor. To

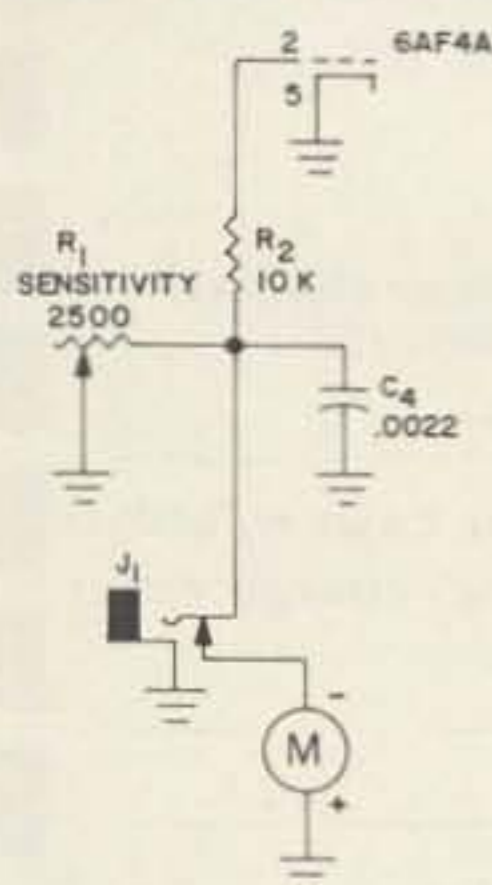


FIG. 1 ORIGINAL CIRCUIT

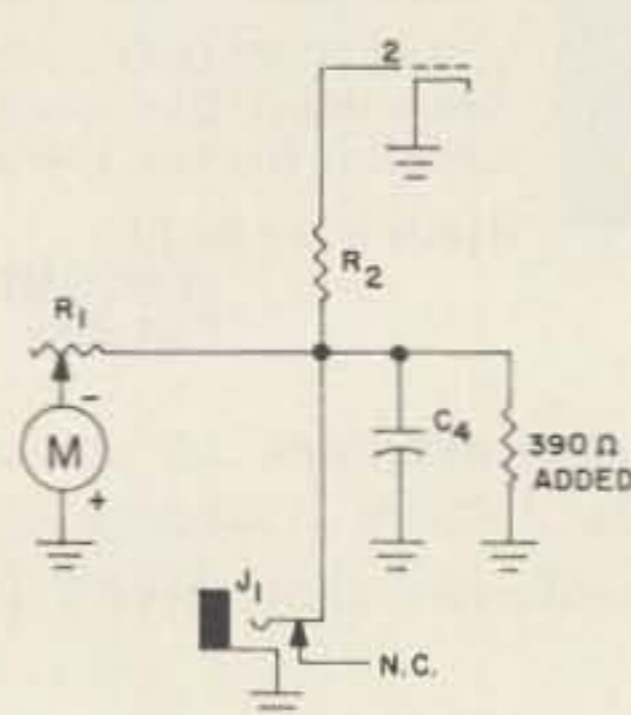


FIG. 2 MODIFIED CIRCUIT

just be capable of full-scale readings, the added resistor cannot exceed 500 ohms in value.

To leave some margin for tube aging, etc., I chose to use a 390 ohm resistor. This will allow a reading of 390 microamps on the meter if the pot is set for maximum resistance, and this will be the *lowest* reading you can get at this point with the modified meter. Reducing the pot resistance to 1,950 ohms gives you an exact full-scale reading.

On the UHF bands, turning the pot to minimum resistance will effectively remove it from the circuit, leaving you simply the 500 microamp meter shunted by a 390 ohm resistor. While 390 ohms is a whale of a lot less than 2500 ohms, the effect turned out to be negligible here; readings were reduced less than 5 scale divisions on the meter, and it was still a cinch to read the unit.

If you'd like to make a second modification while you have the case off, here's one which has nothing at all to do with the operating convenience but can help protect your meter movement if you carry the instrument around a lot.

This change involves replacing the SPST "power" slide switch with a DPDT switch of similar construction and size, and using the added pole to short out the meter when the power is off.

Any D'Arsonval movement will tend to "kick around" quite a bit with vibration, and a sensitive meter such as used in this unit is especially subject to getting knocked off its bearings by any extreme shock.

However, if the meter terminals are shorted together, the movement of the needle with vibration is almost completely damped out. This comes about because if the needle moves, the coil in the meter generates a small voltage (it's just a small generator in reverse). When the terminals are shorted, this voltage is immediately applied back to the meter, freezing it in position at zero.

The change is as simple as the previous one: Remove case, take out power switch, and disconnect both wires. Connect them to new DPDT switch, using corresponding terminals. Connect two new wires to the other pole of the switch, using the terminals toward the opposite end of the switch. Reinstall switch, and connect one of the new wires to each terminal of the meter. To check for proper wiring, turn power switch "off" and shake meter. If needle moves, check your connections—it shouldn't budge a fraction. If it stays put, slide switch to "on" and shake gently again. Meter should now gyrate wildly.

... K5JKX

send for New FREE

CRYSTAL
CATALOG

... with New
TRANSISTOR
OSCILLATOR
CIRCUITS

3 BIG MODERN PLANTS
TO SERVE YOU BETTER

2 in Fort Myers

1 in Los Angeles



HERMETICALLY SEALED
PRECISION GROUND
CUSTOM-MADE
NON-OVEN CRYSTALS

Top performance assured with quality controlled throughout manufacture. Gold or silver plating acts as electrodes. Crystals are spring mounted and sealed under vacuum or filled with inert gas. Very high frequency stability. Max. current capacity is 10 milliwatts—5 for overtone type. Conformity to military specifications guaranteed.

1000KC to 1600KC (Fund. Freq.)	Prices on Request
1601KC to 2000KC (Fund. Freq.)	-----\$5.00 ea.
2001KC to 2500KC (Fund. Freq.)	----- 4.00 ea.
2501KC to 5000KC (Fund. Freq.)	----- 3.50 ea.
5001KC to 7000KC (Fund. Freq.)	----- 3.90 ea.
7001KC to 10,000KC (Fund. Freq.)	----- 3.25 ea.
10,001KC to 15,000KC (Fund. Freq.)	----- 3.75 ea.
15MC to 20MC (Fund. Freq.)	----- 5.00 ea.

OVERTONE CRYSTALS

15MC to 30MC Third Overtone	-----\$3.85 ea.
30MC to 40MC Third Overtone	----- 4.10 ea.
40MC to 65MC Third or Fifth Overtone	----- 4.50 ea.
65MC to 100MC Fifth Overtone	----- 6.00 ea.

DRAKE 2-B Receiver Crystals\$4.00
(All Channels—Order by Freq.)

OVEN-TYPE CRYSTALS

For Motorola, GE, Gonset, Bendix, etc.
Add \$2.00 per crystal to above prices
SUB-MINIATURE PRICES slightly higher

CITIZEN BAND Class "D" Crystals\$2.95
Over 50,000 CB crystals in stock for all sets and channels, both HC6/U and miniature types. To insure proper correlation and correct freq. operation, order by manufacturer model number and channel.

NOW . . . 48 HOUR SHIPMENT

ALL TEXAS CRYSTALS are made to exacting specifications, quality checked, and unconditionally guaranteed!

Send for new Citizen Band Crystal Interchangeability Chart with Texas Crystals Code System.

ORDER FROM CLOSER PLANT

TEXAS CRYSTALS

DEPT. 73-4
1000 Crystal Drive
FORT MYERS, FLORIDA
Phone 813 WE 6-2109

Division of

AND
4117 W. Jefferson Blvd.
LOS ANGELES, CALIF.
Phone 213-731-2258



4 NEW THUNDERBIRD 4 TRIBANDERS FOR 10, 15, 20 M



from **hy-gain**

- New Hy-Q Traps
- Advanced Design Beta Match
- Taper Swaged Seamless Aluminum Elements

1 ALL NEW 6-ELEMENT THUNDERBIRD DX MODEL TH6DX

Superb DX performance. Features wide spaced elements on a 24 ft. boom. New Hy-Q Traps provide true full-sized performance. Feeds with 52 ohm coax—Beta Matched for optimum gain—maximum F/B ratio without compromise. SWR less than 1.5:1 on all bands. Longest element, 32 ft.—weight, 47 lbs. Model TH6DX, \$139.95 Net.

2 NEW, IMPROVED 3-ELEMENT THUNDERBIRD MODEL TH3Mk2

Outstanding performance on 10, 15 and 20 meters. Separate and matched new Hy-Q Traps for each band. Feeds with 52 ohm coax—Beta Matched for optimum gain—maximum F/B ratio without compromise. SWR less than 2:1 on all bands. Boom length, 14 ft. Longest element, 26 ft. Weight, 36 lbs. Rotates with heavy duty TV rotator. Model TH3Mk2, \$99.75 Net.

3 NEW, IMPROVED 2-ELEMENT THUNDERBIRD MODEL TH2Mk2

Compact...installs almost anywhere...delivers excellent performance. Features new Hy-Q Traps. Feeds with 52 ohm coax—Beta Matched for maximum gain. Rugged lightweight construction compatible to rotating with standard TV rotator. Boom length, 6 ft. Longest element, 26 ft. Weight, 21 lbs. Model TH2Mk2, \$69.95 Net.

4 IMPROVED 3-ELEMENT THUNDERBIRD JUNIOR MODEL TH3JR


A compact 3-element beam that delivers outstanding performance. Up to 20db of directivity. SWR less than 2:1 at resonance. Hy-Q Traps—Beta Match—seamless heavy gauge aluminum construction. Rotates with standard TV rotator. 12 ft. boom. Longest element, 27'6". Turning radius, 15'11". Model TH3JR, \$69.95 Net.

Moonbounce or across town...

hy-gain VHF ANTENNAS are best for you!

For optimum performance and maximum mechanical reliability on VHF, you have to look to Hy-Gain. Uniquely staggered optimum spaced beams with exclusive Beta Match...stacked jaypoles...Beta Matched center mount halos...maximum gain 6 & 2 meter duobanders...gain ground planes...mobile halos and whips...and, many, many more. They're all pictured and fully described in Hy-Gain's 16-page Catalog No. 204—available via return mail.

Send for your FREE copy today.

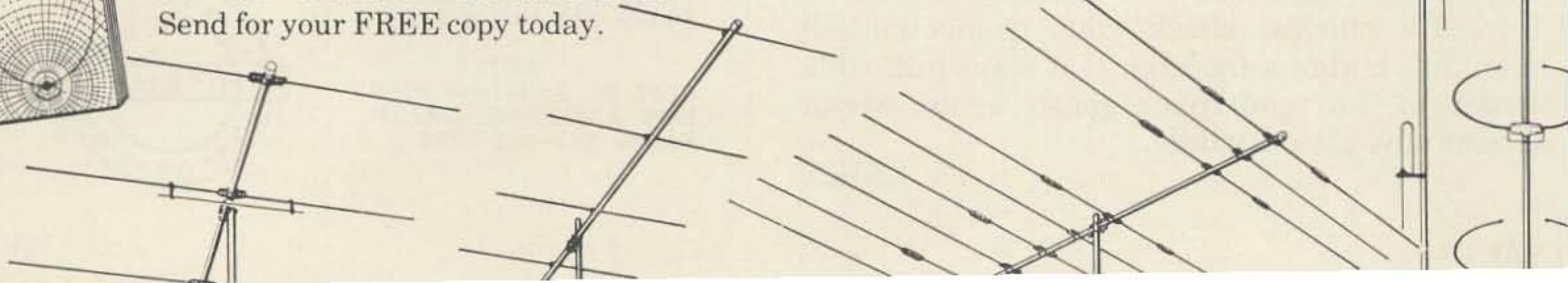

2 NEW MULTI-BAND TRAP VERTICALS

from **Hy-gain**

- New Hy-Q Traps
- New 12" Double-Grip Mast Bracket
- Taper Swaged Seamless Aluminum Construction

1 **HY-GAIN'S MODEL 14AVS**, the world's most popular Ham antenna, has a new, improved successor...the Model 14AVQ. Three separate new Hy-Q Traps...completely factory pre-tuned...provide peaked performance on 10 through 40 meters. Outstanding low angle radiation pattern for DX. New 12" double-grip mast bracket insures maximum rigidity whether roof-top or ground mounted. New total performance construction... heavy gauge taper swaged seamless aluminum radiator—full circumference compression clamps at tubing joints non-conducive to corrosion or wear. Unsurpassed for portability ...outstanding for permanent installations. Overall height, 18 ft. Weight, 10 lbs. Adapts to 80 meter operation using Hy-Gain's Model LC80 loading coil. Model 14AVQ, **\$29.95 Net.**

- Loading Coil for 80 Meter operation—Model LC80.....\$ 7.95 Net
- Roof Mounting Kit—Model 14RMK.....\$11.95 Net
- Decoupling Stub adds 6 Meter operation—Model 6MK.....\$ 4.95 Net

2 **For 10, 15 and 20 Meters...Hy-Gain's New Model 12AVQ.** Companion to the new Model 14AVQ, the Model 12AVQ, for 10-20 meters, incorporates new Hy-Q Traps—a new 12" double-grip mast bracket—taper swaged seamless aluminum construction. It delivers outstanding low angle radiation. SWR is 2:1 or less on all bands. Overall height is 13'6". Weight, 9 lbs. Model 12AVQ, **\$21.95 Net.**

- Roof Mounting Kit—Model 12RMK.....\$11.95 Net
- Decoupling Stub adds 6 Meter operation—Model 6MK.....\$ 4.95 Net


5 NEW HY-GAIN DOUBLET...TAKE MAXIMUM LEGAL POWER



Model 5BDQ for 10 thru 80 Meters



Model 4DBQ for 10 thru 40 Meters

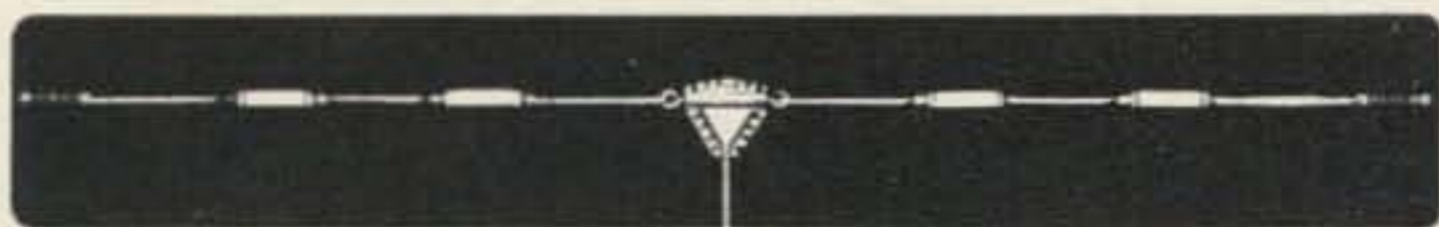

Model 3BDQ for 10 thru 20 Meters



Model 2BDQ for 40 and 80 Meters



Model 248BDQ for 20, 40 & 80 Meters

- New Hy-Q Traps
- Super-Strength Aluminum Clad Steel Wire
- Install Horizontally or as Inverted V
- Weatherproof Center and End Insulators

Installed horizontally or as an Inverted V, new Hy-Gain Doublets with Hy-Q Traps deliver true half wavelength performance on all bands. Completely factory pre-tuned ...SWR less than 1.5:1 on every band. Super-strength aluminum clad single strand steel wire defies deterioration from salt water and smoke ...will not stretch...withstands hurricane-like winds. Easily installed with famous Hy-Gain molded high impact cycolac plastic center and end insulators.

- Model 5BDQ 10 thru 80 M... \$34.95 Net
- Model 4BDQ 10 thru 40 M.....\$24.50 Net
- Model 3BDQ 10 thru 20 M... \$17.50 Net
- Model 248BDQ 20, 40 & 80 M.....\$22.50 Net
- Model 2BDQ 40 and 80 M... \$19.95 Net
- Model 2TQ Matched Trap Kit for building 40 & 80 Meter Doublet.....\$12.95 Net
- Model 2BDP Trapless Fan Doublet for 15, 40 & 80 Meters.....\$19.95 Net

ALL HY-GAIN ANTENNAS IN STOCK FOR IMMEDIATE SHIPMENT



Just off the press...
Hy-Gain's new 16-page
HF Catalog No. 200.
Send for your FREE copy.



Phone
886-5749


One More 6 Meter Junk Box Rig

Perhaps my junk-box is better stocked than some (most of my parts come from junked TV sets and 6 volt auto radios), but this little rig required a cash outlay of under seven dollars for the missing parts. With a little trading I might have cut it down further. The biggest outlay was \$4.50 for the crystal for the receiver converter. The west coast boys are a little more fortunate with their plentiful supply of military surplus gear, but we make do with old TV sets.

The transmitter could be called a "Glorified Sixer", running about 18 watts input into a 6V6. This tube was chosen as a final because most car radios from the junk yards happen to have two of them in the line-up. The 6U8 oscillator and doubler came from a TV set, as did the 12AX7, the slug-tuned coil forms, sockets, resistors, condensers, and the modulation

transformer. A word about the transformer—in the original version of this rig, I tried a push-pull audio transformer as described in several schematics, and had my share of troubles trying to get enough audio to modulate the rig. I finally used the filter choke from a TV set and now have audio gain to spare.

Lay out your parts so that all leads can be kept as short as possible. Another point: isolate the modulator section from the oscillator and final. The rule is "shield until it hurts." This complete rig, less power supply, was built in a box 5x7x6 inches high, starting on a 2x5x7 inch chassis. The modulator was kept away on one end of the chassis, and the underside has an aluminum shield 2x5 inches separating the modulator wiring and sockets from the oscillator and final. If good construction practices are observed you shouldn't have any difficulty.

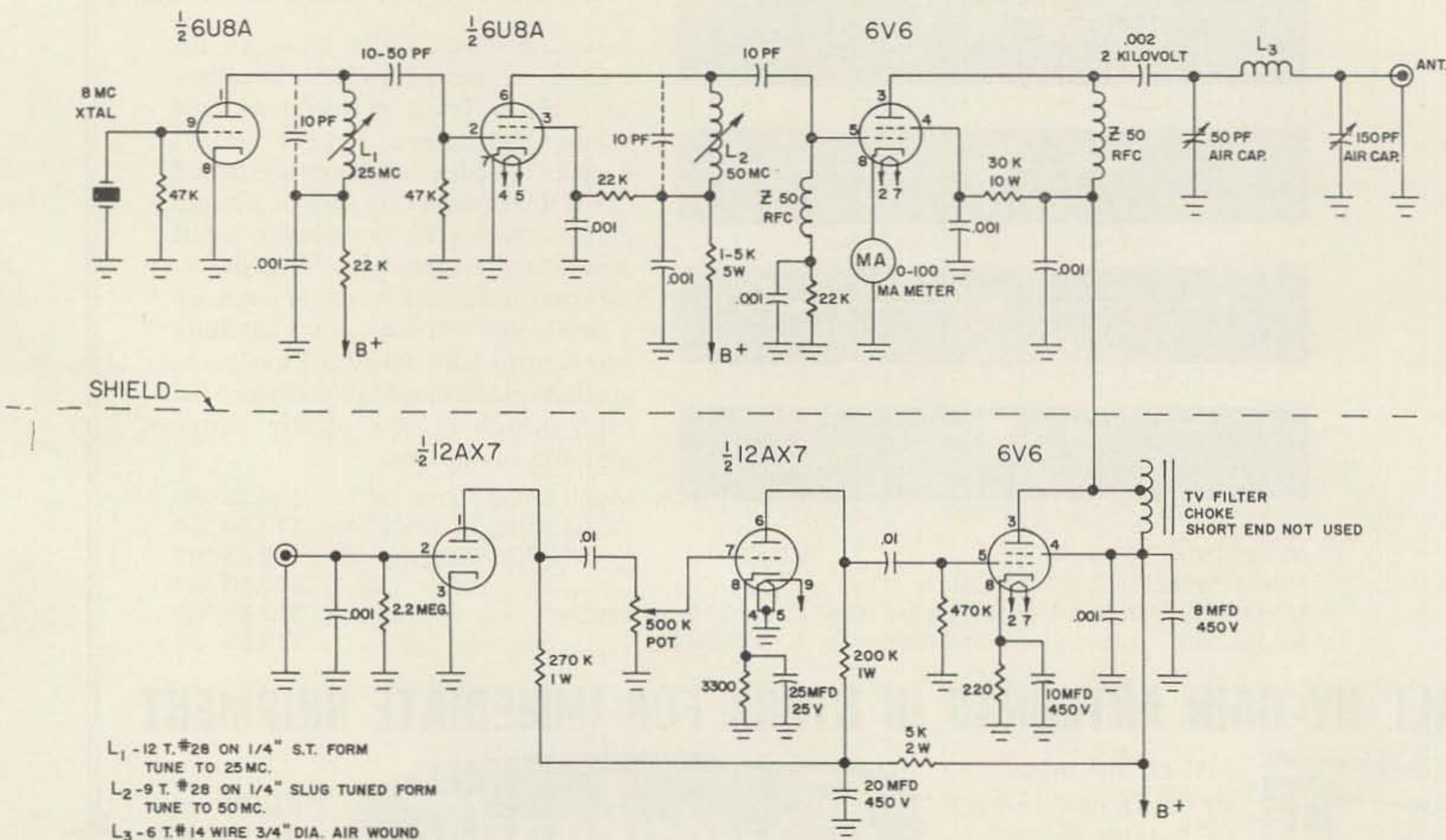

Waters

**AMATEUR
RADIO
EQUIPMENT**

“Convenience Engineered”

Waters amateur radio equipment is “Convenience Engineered” to make correct operating practices easier while assuring superior performance. The Waters trademark is a guarantee of the finest that advanced engineering skill and sound manufacturing principles can produce.

Bob Waters—W1PRI





Waters TEST EQUIPMENT

Good clean signals and maximum efficiency are usually the result of proper adjustment using reliable test equipment. Waters Test Equipment provides the means to get the most out of your equipment.

WATERS DUMMY LOAD/WATTMETER — Model 334

The Dummy Load/Wattmeter is an RF power absorption device and an RF wattmeter for making non-radiating performance tests on radio transmitters.

It combines a structured monolithic 52 ohm load and an integral direct reading RF wattmeter. The load is contained in an hermetically sealed liquid dielectric-filled container providing RF shielding and cooling. It is rated for continuous operation at 50 watts and intermittent use to 1,000 watts over a frequency range of 2 to 230 megacycles. A thermostatically operated warning light indicates when the maximum safe-operating temperature is reached.



DUMMY LOAD/WATTMETER SPECIFICATIONS: Frequency Range: 2 to 230 mc. Load: Non-inductive, oil cooled. Load Impedance: 52 ohms. VSWR: Less than 1.3:1 up to 230 mc. Power Range: 50 watts continuous; 1,000 watts intermittent. (Maximum inner case temperature of 220 F is reached in 5 to 7 minutes at 1,000 watts input. Warning light signals at this point.) Wattmeter Range: 3 calibrated scales: 0-10 w; 0-100 w; 0-1,000 w. Accuracy: 2-30 mc, $\pm 5\%$ of full scale; 30-150 mc, $\pm 10\%$ of full scale; 150-230 mc, $\pm 20\%$ of full scale. Input Connector: Hermetically sealed SO-239 UHF, mates with JAN standard PL-259 (Amphenol 83-1SP). Size: 4 $\frac{3}{4}$ " x 9" x 10 $\frac{1}{4}$ " Weight: 12 lb. Price: \$89.95

WATERS REFLECTOMETER—Model 369

The new Waters REFLECTOMETER is a dual indicator voltage standing wave ratio MEASURING instrument. BOTH the forward and reflected voltages expressed in RF watts are shown at the same time on the unique double meter. Unlike conventional VSWR indicators, the REFLECTOMETER has multiple scales that provide 5 & 10 to 1 increase in sensitivity of Reflected Power, permitting very accurate readings of low reverse power values.

The REFLECTOMETER Indicator is housed separately from its Directional Coupler which may be located remotely on the coaxial line and connected with shielded cable.



REFLECTOMETER SPECIFICATIONS: Scales Forward: 1,000 watts; 200 watts. Scales Reflected: 200 watts; 20 watts.

Impedance: 52 ohms. Frequency Range: 3 to 30 megacycles. Accuracy: (Power) $\pm 10\%$ of full scale (in 52 ohms). Power Loss: Negligible. Size: Indicator—5 $\frac{1}{2}$ " x 3 $\frac{3}{4}$ " x 4 $\frac{1}{4}$ "; Directional Coupler—4" x 2" x 2 $\frac{7}{16}$ ". Weight: Indicator—1 $\frac{1}{2}$ lb; Coupler— $\frac{3}{4}$ lb. Price and Availability: To be announced.

WATERS WIDE RANGE ATTENUATOR—Model 371 & Model 372

The new WIDE RANGE ATTENUATOR is an accessory device designed to provide stepped attenuation of signals in receivers, signal generators and other low-level radio frequency equipment (converters, etc.). The WIDE RANGE ATTENUATOR installs in the coaxial line using either UHF or BNC connectors. Attenuation steps are selected with rocker-type switches marked in decibels. There is 0 dB insertion loss with switches in OUT position.




ATTENUATOR SPECIFICATIONS: Power Level: $\frac{1}{4}$ watt maximum. VSWR: 1.3 maximum DC to 225 mc. Impedance: 50 ohms, nominal. Attenuation Range: 0-61 db in 1 db steps. Attenuation Accuracy: .1 db/db DC-60 mc; .1 db/db ± 5 db DC-150 mc; .1 db/db ± 1.0 db DC-225 mc. (Model 371-1 with SO239 UHF connectors. Model 371-2 with BNC UG-1094/U connectors. Price and Availability: To be announced

WATERS "LITTLE DIPPER"® TRANSISTORIZED RADIO FREQUENCY DIP OSCILLATOR — Model 331

The "LITTLE DIPPER" is a fully transistorized RF dip oscillator which performs all functions of a grid dip oscillator, an absorption wave meter and a signal generator for field use with its built-in audio modulation.

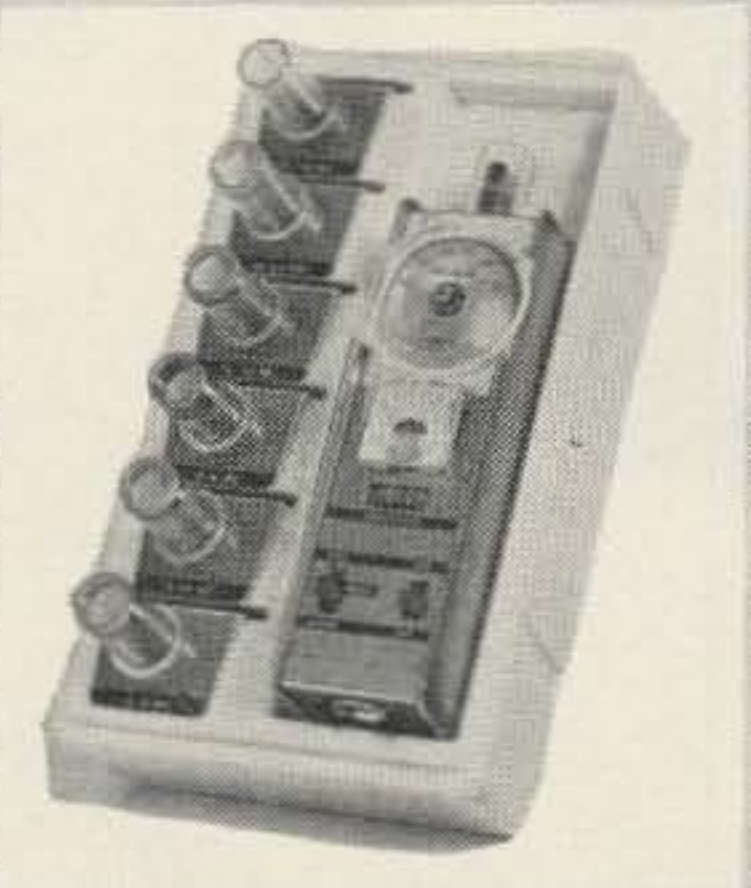The "Little Dipper" consists of: 1) a stabilized MADT transistor RF oscillator covering the frequency range of 2 to 230 mc in 7 overlapping plug-in coil ranges. Each coil carries its own linear calibrated frequency scale. 2) Transistorized 1,000 cycle audio oscillator for modulation. 3) Transistorized DC amplifier and meter for detecting the dip.



"LITTLE DIPPER" SPECIFICATIONS: Frequency Ranges: 2-4 mc, 4-8 mc, 8-16 mc, 16-32 mc, 32-64 mc, 50-110 mc, 100-230 mc. Accuracy: $\pm 3\%$ (full scale value). Modulation Frequency: 1,000 cps nominal. Battery Life: 300 hours. Power: Four AA penlight batteries. Size: 7" x 2 $\frac{1}{4}$ " x 2 $\frac{1}{2}$ " Weight: 1 lb. 6 oz. Case: Stainless steel. Price: \$129.75



Waters **NEW AUTO-MATCH™**

The Stronger Mobile Antenna



Combining stronger structural strength with stronger signal strength Waters new AUTO-MATCH Mobile Antenna is setting new high standards in the mobile operating field! AUTO-MATCH operates with only a coil-change on every ham band to provide more signal strength with its greater radiation efficiency. The tapered radiator tip is of drawn 17-7 PH stainless steel and adjusts to all frequencies. Interchangeable Top-Center loading coils are molded in low-loss Epoxy and are completely sealed

against moisture and water seepage. High Q stable inductance handles 500 watts of RF and at resonance presents an "Auto-Match" of 50 ohms. The lower mast is of aircraft aluminum tubing upper mast of solid tapered-drawn aluminum rod. Pull-up foldover hinge drops AUTO-MATCH to car-top level and AUTO-MATCH fits any standard base or bumper mount. AUTO-MATCH is rugged, very rugged — designed to last for car after car, rig after rig.

PRICES

MAST 370-1	\$12.95	COIL 370-20	\$13.45
RADIATOR TIP 370-2	\$ 9.95	COIL 370-15	\$12.75
COIL 370-75	\$15.95	COIL 370-11	\$11.95
COIL 370-40	\$14.95	COIL 370-10	\$11.95



Waters

CODAX™

Automatic Keyer

MODEL 361

Waters CODAX Automatic Keyer makes "smoothest-ever" CW operating possible with automatic spacing and timing for any speed from 5 to 50 WPM. A built-in double-paddle key (one for dots and one for dashes) adjusts to accommodate any fist and CODAX won't walk at high speed transmissions. CODAX has solid state digital circuitry and an hermetically sealed "Reed" relay for last-

ing reliability. The keyed 1500 cycle audio output is at microphone level permitting use of the VOX circuit on either upper or lower sideband. CODAX permits self-monitoring and interconnects with any transmitter, transceiver or receiver (keying the grid block circuit or operating keying relay in AM/CW rigs). CODAX is self-powered.




CODAX SPECIFICATIONS: Speed Range: 5 to 50 WPM, variable. Dot-Dash Ratio: Fixed 3-to-1. Space-to-Character Ratio: Fixed 1-to-1. Controls: Audio output level/On-Off switch; Speed control. Semiconductors: 10 transistors; 14 diodes. Outputs: #1 Cable—Relay contacts rated at 15 watts total power; 250 volts DC maximum and 1 ampere maximum. (Volts x Amperes not to exceed 15 watts.) #2 Cable—Keyed audio, 1500 CPS nominal, .050 volts @ less than 100 ohms #3 Jack—Sidetone/mixed audio from receiver for headphone operation. Input: #4 Cable and Plug—Audio from receiver output. Power: #6 RM—502R Mallory 1.35 volt batteries (not furnished). Size: 2 3/8" x 3 3/4" x 6 1/8". Price: \$92.50



Improved Operation for COLLINS 75S-1 and KWM-2/2A

WATERS "CHANNELATOR"® — Model 349

The Channelator is a crystal-controlled "external PTO" providing up to six preselected EXACT crystal frequencies. With Channelator operation frequency-problems are eliminated on nets and round tables since BOTH receiving and transmitting frequencies are crystal-controlled. Novel oscillator circuit together with Waters special crystals permits "pulling" of the crystal to an EXACT frequency. The built-in heterodyne frequency meter provides precise measurement of each crystal. A function switch selects normal PTO or Channelator crystal operation as well as "split channel" use.

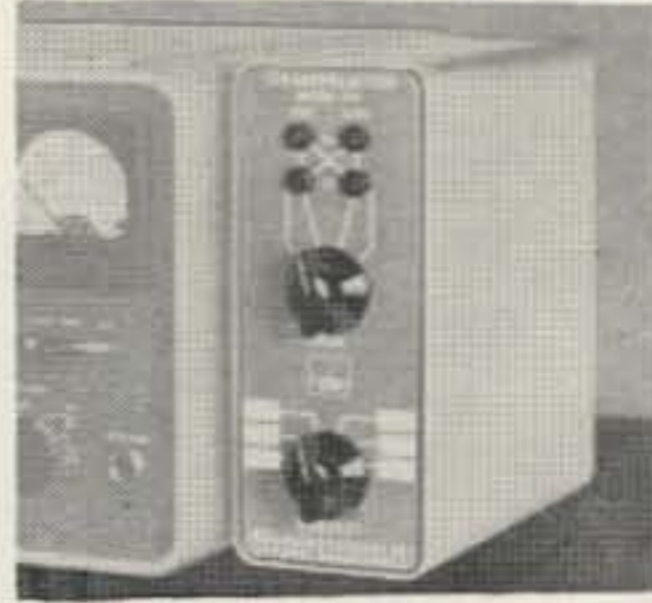


The Waters Channelator connects to the Collins equipment in minutes and may be mounted directly on the 75S series and KWM-2/2A. All cables and plugs are furnished. It operates from any fixed or mobile Collins DC or AC power supply. The front panel is reversible to permit vertical or horizontal mounting.

Price: \$79.95 (less crystals)
Adapter Kit Model 349-27 for "S-line" installation \$15.95
Crystals—any frequency, USB or LSB \$6.00 each.

WATERS Q-MULTIPLIER/NOTCH FILTER

The Waters Q-Multiplier/Notch Filter eliminates heterodynes and other unwanted signals in the IF passband. By combining an isolating amplifier and a tunable LC Bridged-T network with a Q-Multiplier, it provides a deep transmission null or notch of over 40 db, tunable across the entire passband. Operating with only a single tuning control on the front panel, the Q-Multiplier/Notch Filter becomes an integral part of the 75S-1 or KWM-2/2A. Escutcheon plates and knobs are matched to the Collins panel and no drilling of the panel is required. Operates in fixed or mobile service with any standard Collins power supply.

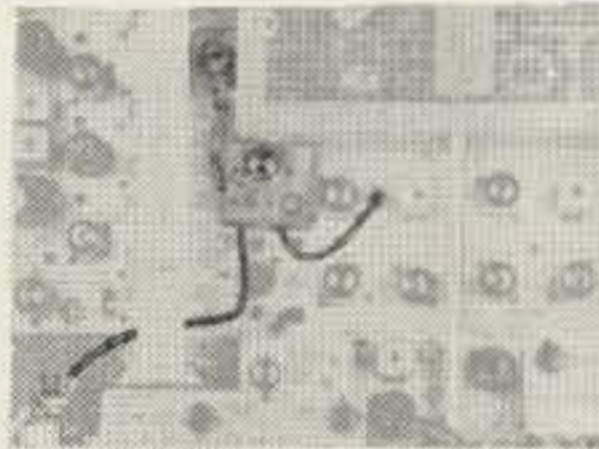

SPECIFICATIONS: 337-S1A (for Collins 75S-1) Center Frequency: 455 KC nominal. Notch Depth: Greater than 40 db. Notch Tuning Range: 2.5 KC. Power: (from 75S-1) .3 a @ 6.3 v, 1.5 ma @ 140 v. Price: \$39.95

340-A (for Collins KWM-2/2A) Center Frequency: 455 KC nominal. Notch Depth: Greater than 40 db. Notch Tuning Range: 2.5 KC. Power: (from KWM-2/2A) .3 a @ 6.3 v, 1.5 ma @ 275 v. Price: \$53.75

WATERS "EVT" ELECTRONIC VERNIER TUNING

The "EVT" provides a 20-to-1 tuning ratio reduction on the KWM-2/2A. A stable, solid state varactor tuning device it attaches to the PTO without wiring change. Tuning range of ± 500 cycles from any PTO setting. Complete with matching escutcheon plate, knobs, hardware, instructions, etc.




Model 354: For KWM-2A without Waters Q-Multiplier/Notch Filter. For KWM-2 when equipped with Q-Multiplier/Notch Filter. (337-M2 or 340-PT) Price: \$23.95

Model 355: For KWM-2 without Waters Q-Multiplier/Notch Filter or with Model 340-A Q-Multiplier/Notch Filter. Price: \$21.95

WATERS UEW 572B HIGH POWER AMPLIFIER TRIODE

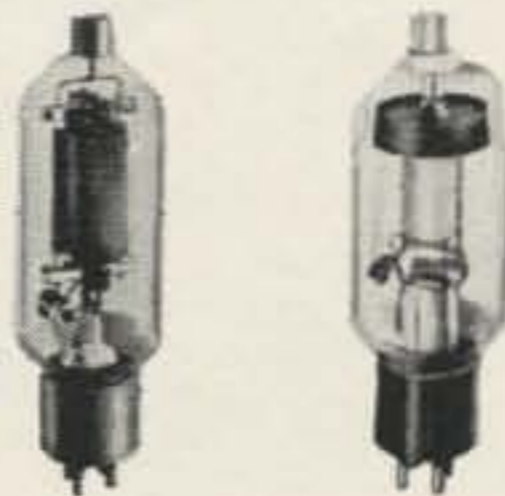The UEW572B is a zero bias power triode ideal for use in grounded grid amplifiers. Built in a hard glass envelope with heavy graphite plate, the UEW572B has a plate dissipation of 160 watts. It is directly interchangeable with 811-A tubes and one 572B is the equivalent of two 811-A's. Complete operating data including ratings and general characteristics will be sent on request. Price: \$13.95



WATERS UEW 3B28 XENON FILLED RECTIFIER

The UEW3B28 is a half wave, hot cathode, Xenon filled rectifier tube directly replacing the 866A. The UEW3B28 operates over a wide temperature range without heating or cooling and does not require prolonged conditioning before application of plate voltage. "Hash filters" are not necessary. Complete operating data will be sent on request. Price: \$6.40



"to give you **BETTER PERFORMANCE**
and **GREATER VERSATILITY"**

Waters "Convenience Engineered" ham equipment helps you to become a better operator with a better station.

WATERS
COMPREAMP™ Model 359

The COMPREAMP Audio Preamplifier/Limiter increases the effective speech power output of a transmitter up to four times. Self-contained and battery powered, the two-stage transistorized COMPREAMP is designed to be used with all types of transmitters.

COMPREAMP connects between the microphone (50,000 ohm dynamic or high impedance ceramic) and the transmitter microphone input connector without any wiring change. Provision is made for switching the Compreamp in and out of the circuit and for adjustment of compression level. Recommended for use with tape recorders and public address system amplifiers.



COMPREAMP SPECIFICATIONS: Input Impedance: 100K ohms, nominal. Input Level: .005 to .020 volts. Gain: (voltage) 10 db, nominal. Output Level: .060 volts. Output Impedance: 50K ohms, nominal. Power: 9-volt Burgess 2U6 or equivalent. (Not supplied.) Size: 2 3/4" x 3" x 4 1/2" .1/2". Price: \$27.95 (less battery.)

WATERS
CLIPREAMP™ Model 372

The new Waters Clipreamp is a solid state, battery operated Preamplifier-Clipper designed for use with voice modulated transmitters to increase "talk power" and intelligibility under adverse band conditions. Frequency response is carefully adjusted for maximum intelligibility and minimum distortion. RF "flat topping" is prevented in SSB operation. Clipreamp is easily installed between high impedance microphone (dynamic, crystal or ceramic) and microphone input of transmitter.



CLIPREAMP SPECIFICATIONS: Voltage Gain: 10-13 db. Frequency Response: 300-3000 cps. Input Level: .020 volts, nominal. Output Level: .060 volts, nominal. Impedance Input: Suitable for high-impedance microphones. Output Impedance: 50,000 ohms. Power: 9-volt burgess 206 or equivalent, (not supplied) Size: 3 1/8" x 2 5/8" x 3 1/4" Weight: 6 1/2 oz. Price: \$21.95 (less battery)

WATERS
"NUVERTER"® — Model 346

The Nuverter adds 2 and 6 meter coverage to any ham superheterodyne receiver that tunes 10 meters. It is easily installed without modifying or drilling and requires no external switches or relays. A single function switch selects wanted frequency band and also transfers antenna connections between HF and VHF. Nuverter has separate all-Nuvisor converters for each band, high-stability crystal oscillators and an integral power supply. The receiver's automatic gain control may be fed into the Nuverter to provide complete AVC performance at VHF. Broad-banded circuitry covers 1.8 megacycles in three 600 KC segments on both 2 and 6 meters.



NUVERTER SPECIFICATIONS: Frequency Range: 50.0 to 51.8 mc; 144.0 to 145.8 mc. Frequency Sub-Bands: 50.0 to 50.6 mc; 50.6 to 51.2 mc; 51.2 mc to 51.8 mc—144.0 to 144.6 mc; 144.6 to 145.2 mc; 145.2 to 145.8 mc. Output IF: 28.5 to 29.1 mc (50 ohms). Input RF: 3 antenna inputs at 50 ohms (2 meter, 6 meter and HF antennas). Power: 115 volts AC or 12 volts DC @ .27 amperes and 125 volts DC @ 25 MA. Sensitivity: .1 microvolt SSB/CW. Noise Figure: 4.0 db maximum at 50 mc; 5.0 db maximum at 144 mc. Size: 2 3/4" x 6 1/2" x 7 1/2". Weight: 4 1/4 lb. Price: \$175.

WATERS
COAXIAL FILTERS — Model 373-2 & 373-6

Waters new Coaxial Filters are double-tuned, resonant cavity band-pass filters for both 2 and 6 meter transmitters and receivers. Installed in 52 ohm coaxial antenna lines, the filter assures an outgoing signal free of the spurious frequencies that cause serious interference problems. (TVI, etc.) The filter provides rejection at the receiver front end of high-level out-of-band signals such as beats between local TV stations. No tuning adjustments required and insertion loss is held to 1.5 db maximum.




FILTER SPECIFICATIONS: 373-2 — Center Frequency: 146 mc. Shape Factor: 40 db—12 max. 3 db
Bandwidth at 3 db: 5 mc. nominal. Insertion Loss: 1.5 db max. Maximum Power Level: 100 watts PEP.
373-6 — Center Frequency: 51 mc. Shape Factor: 40 db—20 max. Bandwidth at 3 db: 3 mc nominal. Insertion Loss: 1.5 db max. Maximum Power Level: 100 watts PEP. Weight: 2 lb. Size: 6 3/4" x 8 3/4" x 3 5/8"
Price and Availability: To be announced



WATERS COAXIAL SWITCHES

Waters Coaxial Switches are designed for panel mounting and feature in-line orientation of the coaxial connectors. They occupy minimum space and are readily accessible for connecting and disconnecting. Waters switches add to the station appearance, are easily installed and provide efficient and convenient switching techniques.

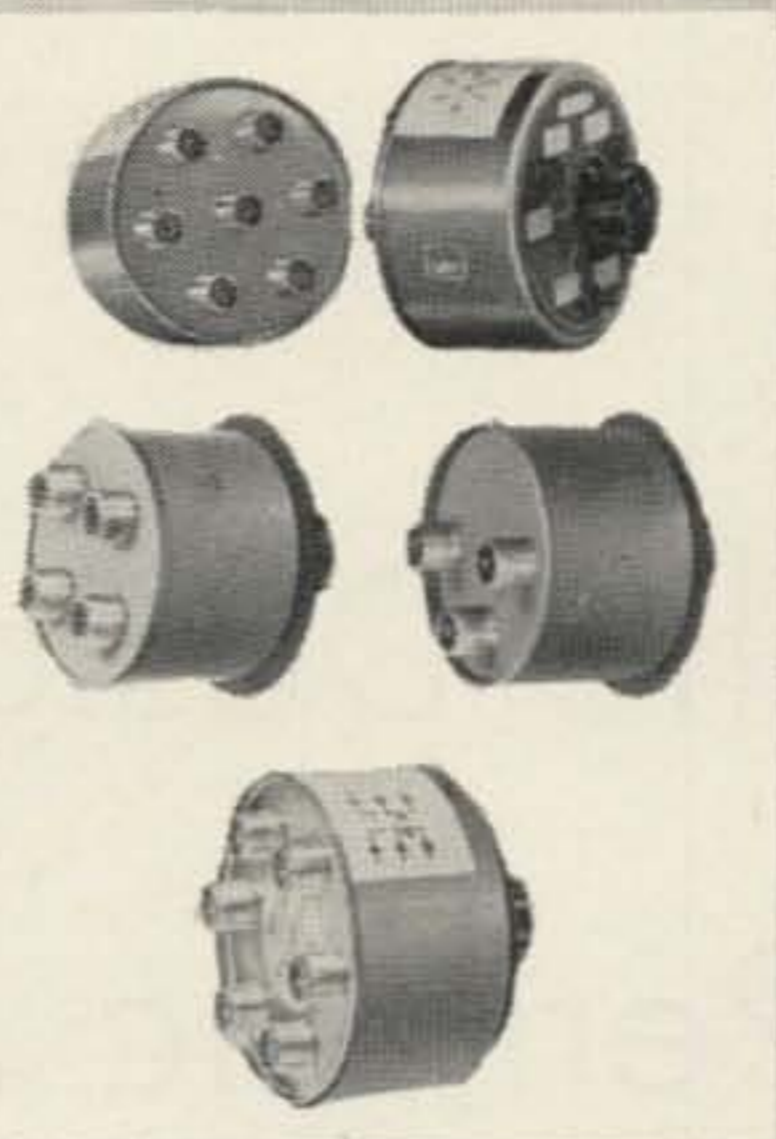SPECIFICATIONS: Internal Construction: Ceramic switch with silver plated conductors. Power Carrying Capacity: 1000 watts. Insertion Loss: Negligible. VSWR: Less than 1.2 up to 150 mc. Mounting: Mounts behind panel with 3 screws. Hardware Supplied: Mounting screws, escutch-plate with provision for erasable marking; knob.



COAXIAL SELECTOR SWITCH — Model 335. Single pole, six-position for switching RF sources, antennas, etc. Has seven UHF (SO-239) connectors. Price: \$12.95

COAXIAL TRANSFER SWITCH—Model 336. Double-pole, double-throw internally strapped for switching amplifier in and out between exciter and antenna. Four UHF (SO-239) connectors. Price: \$11.45


ANTENNA SYSTEM TRANSFER SWITCH—Model 341. Single-pole, double-throw for switching RF device to either of two antennas or two RF devices to single antenna, etc. Three UHF (SO-239) connectors. Price: \$11.45

DUAL COAXIAL TRANSFER SWITCH — Model 351. Double-pole, double-throw for switching converters, filters, etc. in and out of coaxial lines. Six UHF (SO-239) connectors. Price: \$12.95

WATERS ILLUMINATED KNOB — Model 347

Waters Illuminated Knobs serve as pilot lights and position indicators. The Knob projects a light beam on the panel to identify position and has a lighted red pointer as a pilot light. Ideal for applications where the pointer position must be read accurately or identified from a distance or under poor lighting conditions.

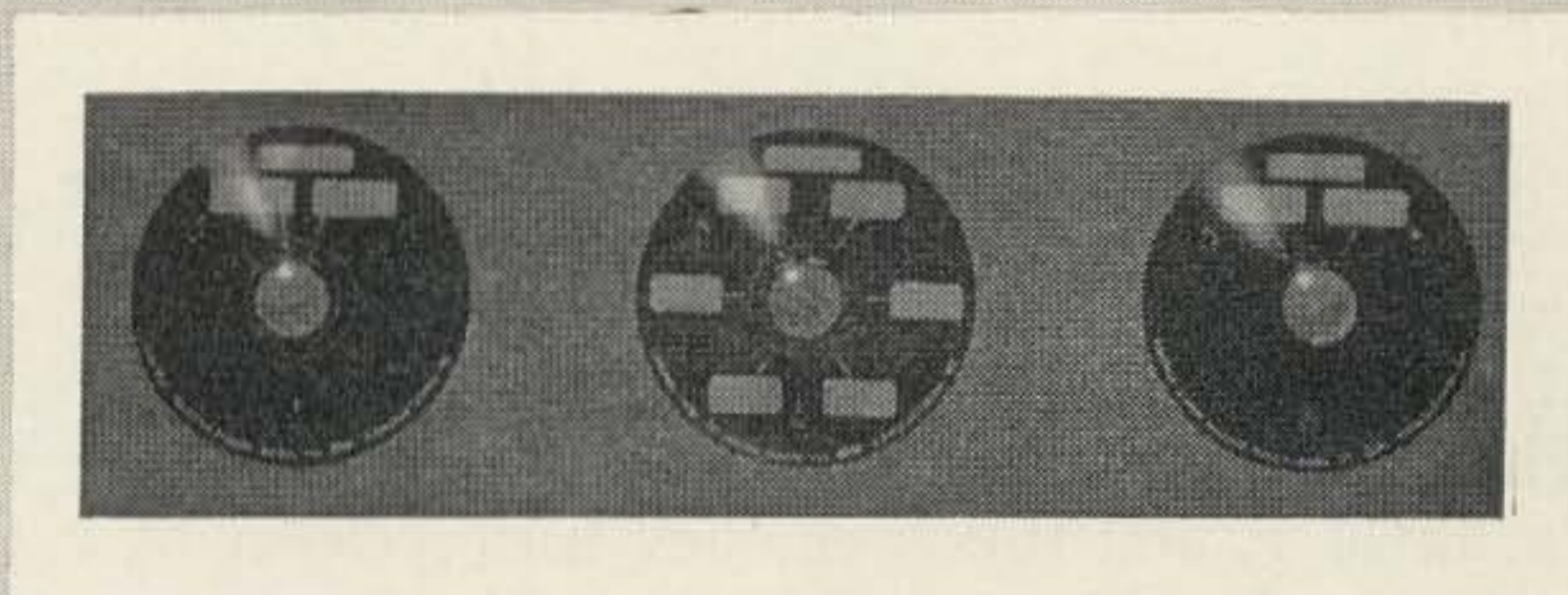Installation is simple. The knob contains the light and mounts on any 1/4" shaft rotary control or switch. No changes required behind the panel. One wire provides the 6 volt source for light with the shaft serving as ground. Price: \$5.00



WATERS UNIVERSAL HYBRID COUPLER and PHONE PATCH — 3001 & 3002

3002 UNIVERSAL HYBRID COUPLER II

The Universal Hybrid Coupler II is an excellent phone patch that connects receiver and transmitter to the phone line for remote voice operation. Provision is also made in the Coupler to connect a tape recorder for both recording and playback of station QSO's and the telephone line. The hybrid circuit provides for effortless VOX operation of the phone patch. A built-in "Compreamp" speech preamplifier/limiter serves to increase the level of weak phone signals and also to avoid over-modulation when the local telephone serves as the station microphone. The "Compreamp" also functions as a preamplifier/limiter with the station microphone, if desired. Front panel is reversible to permit either horizontal or vertical mounting.

3001 UNIVERSAL HYBRID COUPLER

Identical to 3002 but without the "Compreamp"



SPECIFICATIONS: Input Impedances: Line — 600 ohms nominal, RX Output — 4 ohms nominal (varies with receiver output control). Mike—High impedance crystal or dynamic. Tape Recorder, Speaker—4 ohms nominal. Output Impedances: To Tape Recorder — 1/2 meg. ohm. To XMTR — 50K ohms nominal, RX SPKR — 4 ohms nominal.

PRICES: 3002 \$69.95 (less battery)
3001 \$49.50 (less battery)

The Design of Log Periodic Antennas

The performance of a lossless antenna will remain unchanged if all dimensions, in terms of electrical wavelength, are held constant. Thus, if all dimensions are decreased by a factor of τ , and the frequency is decreased by a factor $1/\tau$, the fields about the two antennas will be similar. The dimensions of the log-periodic antenna are such that the electrical properties repeat with the logarithm of the frequency. If the n radiating element is resonant at a frequency f , the next shorter element $n + 1$, is resonant at a frequency of $\tau \times f$, where τ is the design ratio and equals $x_{(N+1)}/x$, x representing the length of the element. The frequency range from f to $\tau \times f$ is called a period of frequency and, if the variation in electrical characteristics is negligible over a period, variations can be assumed to

be also negligible over the entire design range of the antenna.

The log-periodic dipole (LPD) is an adaptation of the basic log-periodic antenna in which the "teeth" of the non-planar, wire, trapezoidal tooth structure are replaced by dipole elements and the angle between the two halves of the structure is reduced to zero. A schematic of the LPD is given in Fig. 1 showing the method of feed.

The symbols used in describing the antenna are:

α (alpha)—half the angle subtended at the vertex.

σ (sigma)—the relative spacing ratio = $d_N/2L_n$

σ' —the mean spacing factor = \sqrt{T}

τ (tau)—design ratio, or scale factor = L_n/L_{n-1}

n (subscript)—any element

$n+1$ (subscript)—next smaller element to "n"

a —radius of element

d_N —distance from any element to next smaller element

x —Boom length between shortest and longest elements.

B —operating bandwidth = (max freq)/(min freq)

B_{ar} —bandwidth of the active region

h —half length of a dipole element

L —full length of a dipole element = $2h$


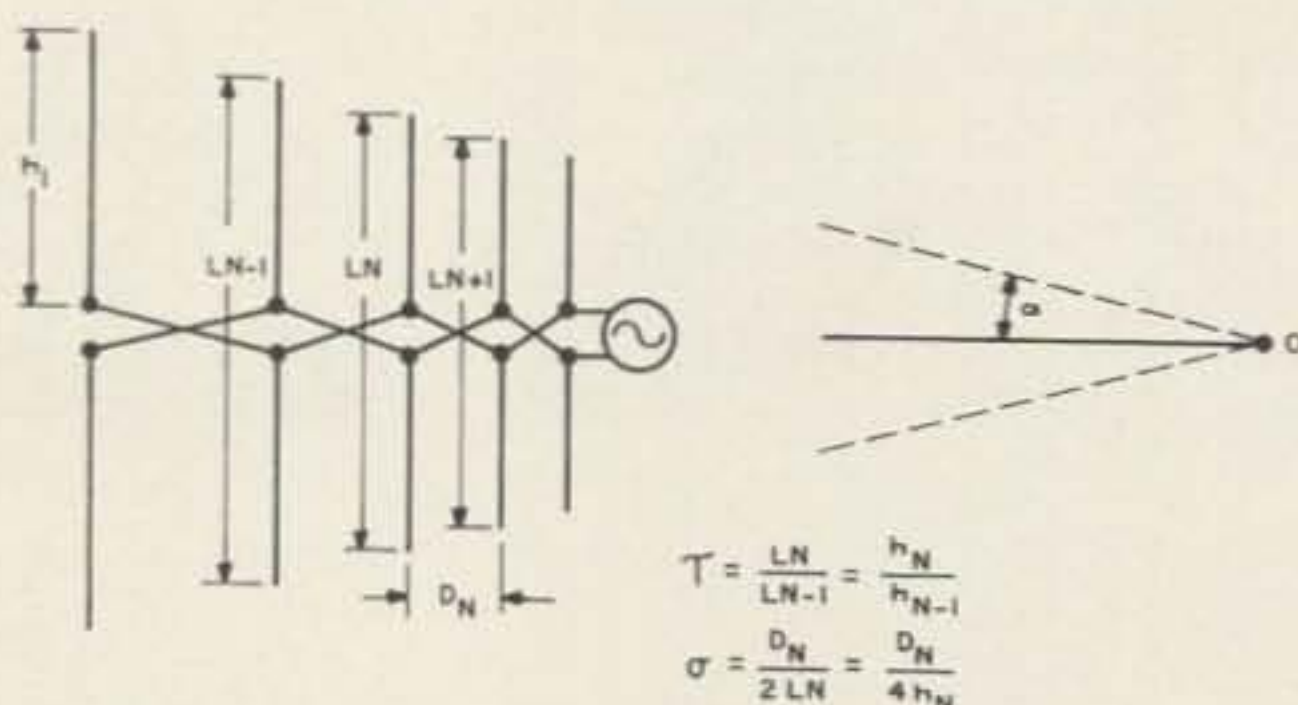


Fig. 1.

Fig. 2.

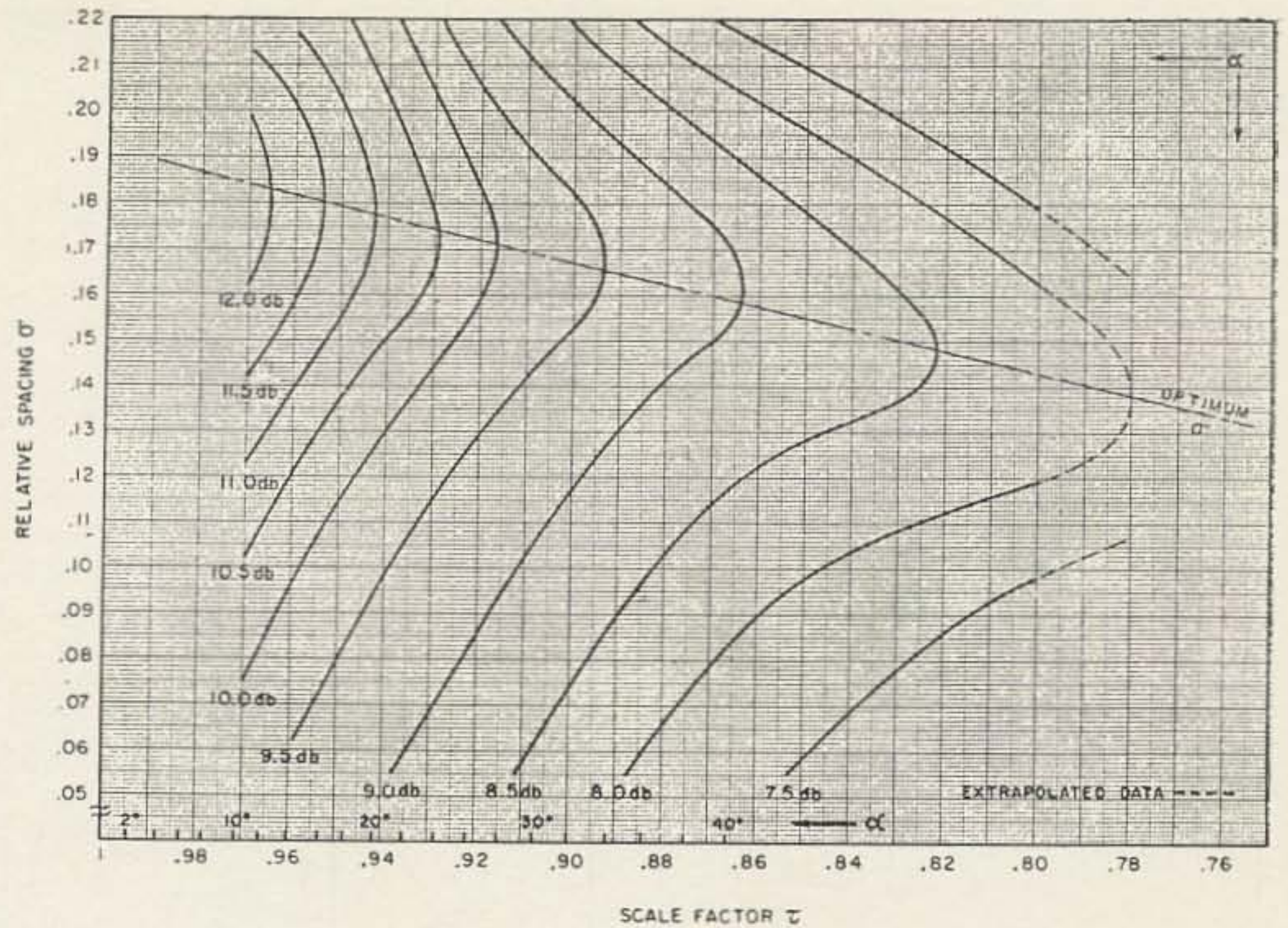

R_o —input impedance at the front of the antenna

Z_a —average characteristic impedance of a dipole element

$$= 120 \left(\log \epsilon \frac{h}{a} = 2.25 \right) \text{ ohms}$$

Z_o —antenna structure feeder impedance (boom impedance)

$$Z_o = 120 \cosh^{-1} \left(\frac{b}{2a} \right) \text{ where } b$$

= center-to-center spacing between the boom elements

It is normal to design an LPD antenna for a given gain and input impedance over a given frequency band. The relative size of the structure and the number of elements is of importance and these two factors will depend on the values of τ (an increase in τ means a greater number of elements) and α (increase in α means a decrease in size). The factors τ and σ are the main determining factors affecting the shape of the radiation pattern and there will be a value of σ , called "optimum σ " that will be an optimum for any desired gain and will give a minimum value of τ and SWR and maximum front-to-back ratio. A chart giving this relationship is shown as Fig. 2. The best design procedure is to start with the optimum value for σ and make a table for lesser values. The values for α , boom length, and number of elements, can be found from the charts given as Figs. 3 to 6.

As an example, let us design an LPD for use on 6 meters, fed by 75 ohm coax cable and giving optimum results for a maximum boom length of 10 feet.

a. Using values for optimum σ from Fig. 2

for a gain of 8.5 db $T = 0.822$; $\sigma = 0.148$.

b. From Fig. 3, $\alpha = 17.8^\circ$

c. From Fig. 4, $B_{ar} = 1.8$; $B = 55/50 = 1.1$; $B_s = 1.98$

d. From Fig. 5, $x/\lambda_{max} = 0.38$; $\lambda_{max} = 984/f = 19.65$ feet. $x = 19.65 \times 0.38 = 7.46$ feet.

e. From Fig. 6, number of elements = 4.

A second run, using a gain of 9 db, gives a boom length of 14.2 feet.

The value of Z_o is now determined to give the required value for R_o . The ratio h/a should be the same for each element, but practically the element diameters can be the same for each element, or scaled in groups and the average h/a used. Let us use $\frac{3}{8}$ " diameter tubing for the elements and, taking the value of h at 52.5 Mc, $h/a = 600$. The values of Z_a and σ' are then calculated and give $Z_a = 500$ and $\sigma' = 0.1725$. The relative feeder impedance Z_o/R_o can be obtained from Fig. 7 which gives, $Z_a/R_o = 500/75 = 6.66$; $Z_o/R_o = 1.1$; $Z_o = 82.5$ ohms.

The length of the longest dipole element is given by $\lambda_{max}/4 = 58.95$ inches. The lengths of the other three elements are given from the relationship $h_{N+1} = h_N \tau$, which results in:

$$\begin{aligned} h_1 &= 58.95'' & h_2 &= 48.4'' \\ h_3 &= 39.8'' & h_4 &= 32.7'' \end{aligned}$$

The distance between the elements is given by: $d_N = \sigma 4h_N$, and this gives the distances as:

$$\begin{aligned} d_1 &= 34.85'' & d_2 &= 28.65'' \\ d_3 &= 23.55'' & & \end{aligned}$$

Ideally, the boom elements should be conical but, in practice, two parallel cylinders can

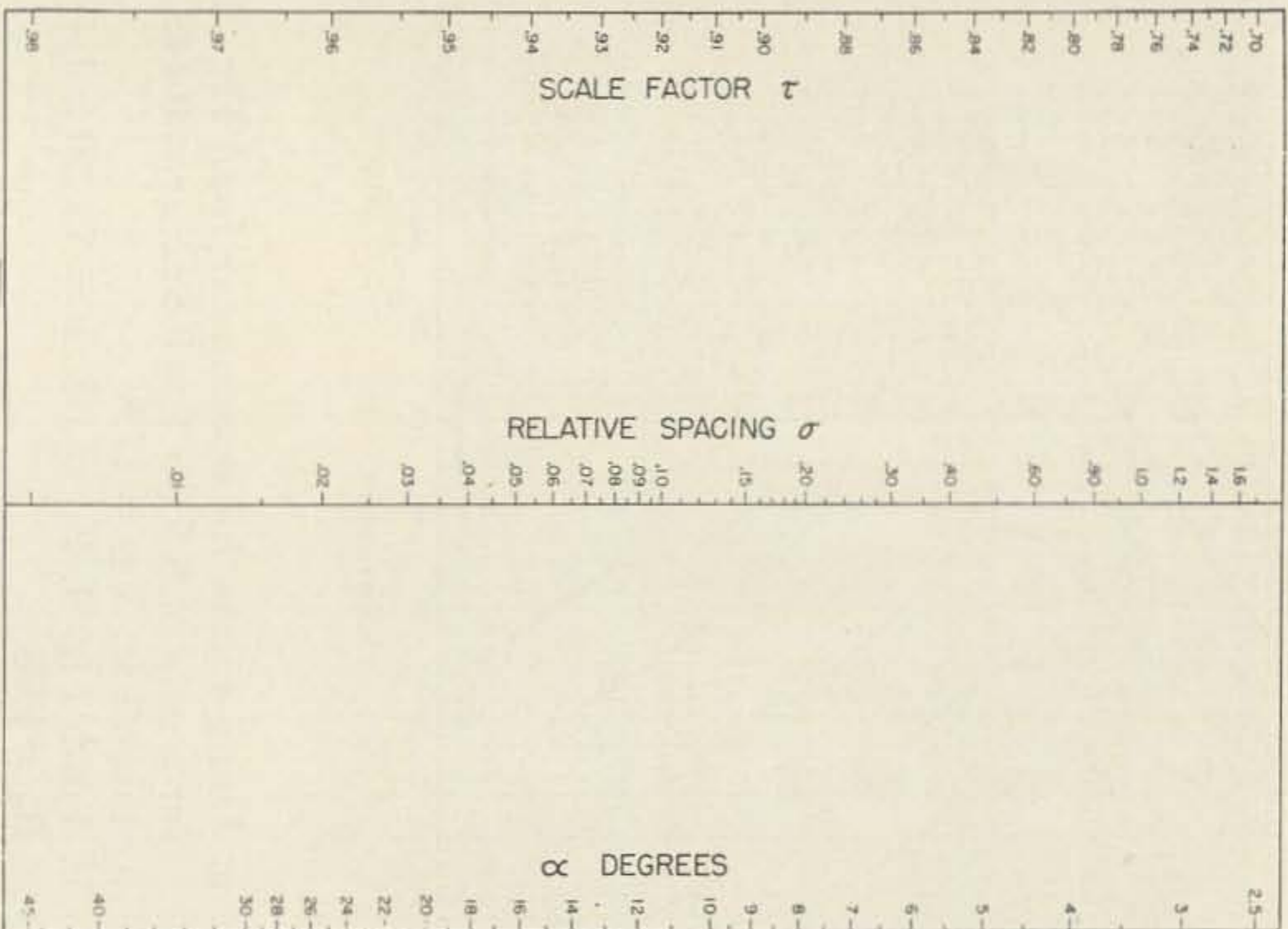


Fig. 3.

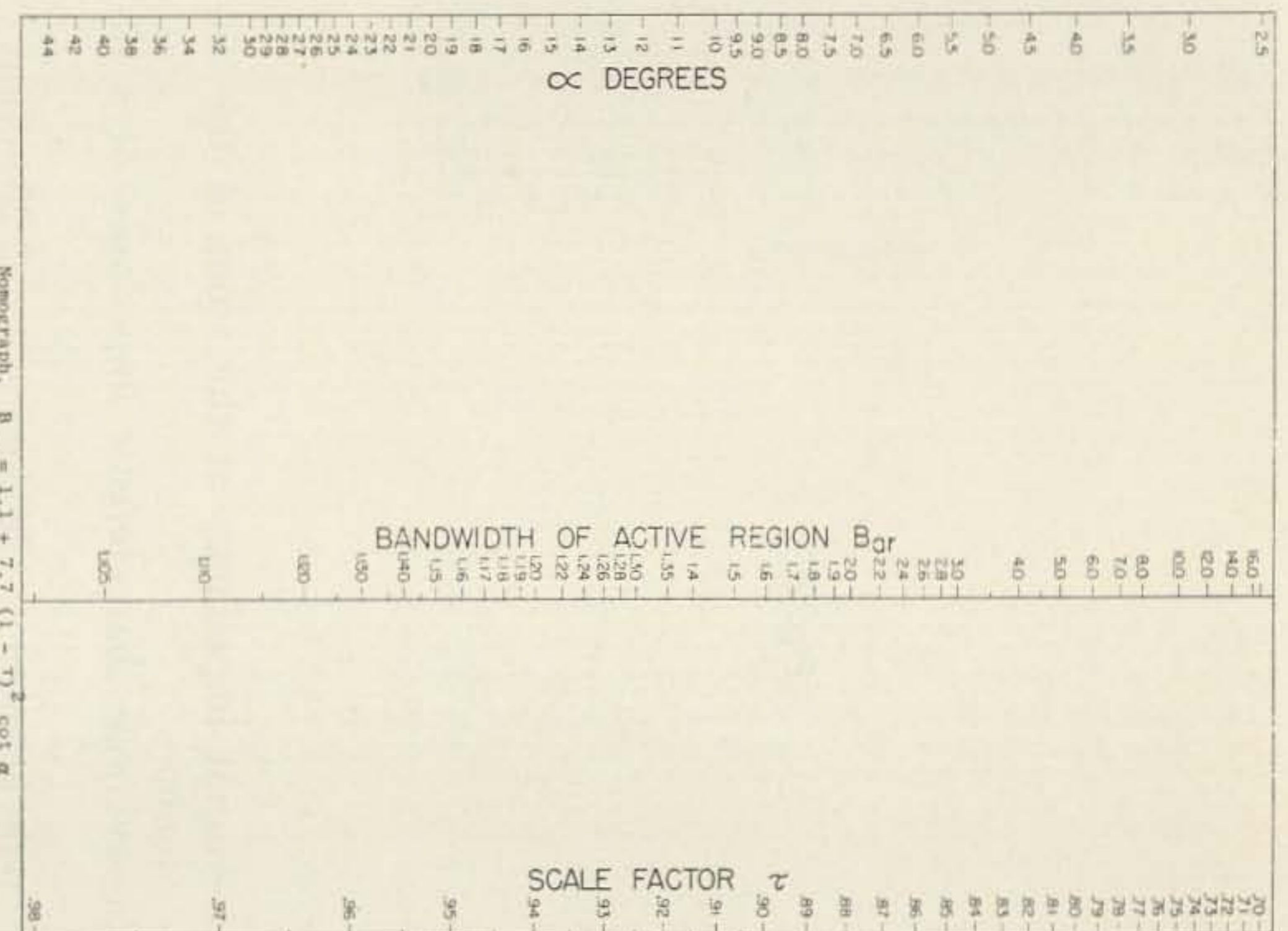


Fig. 4.

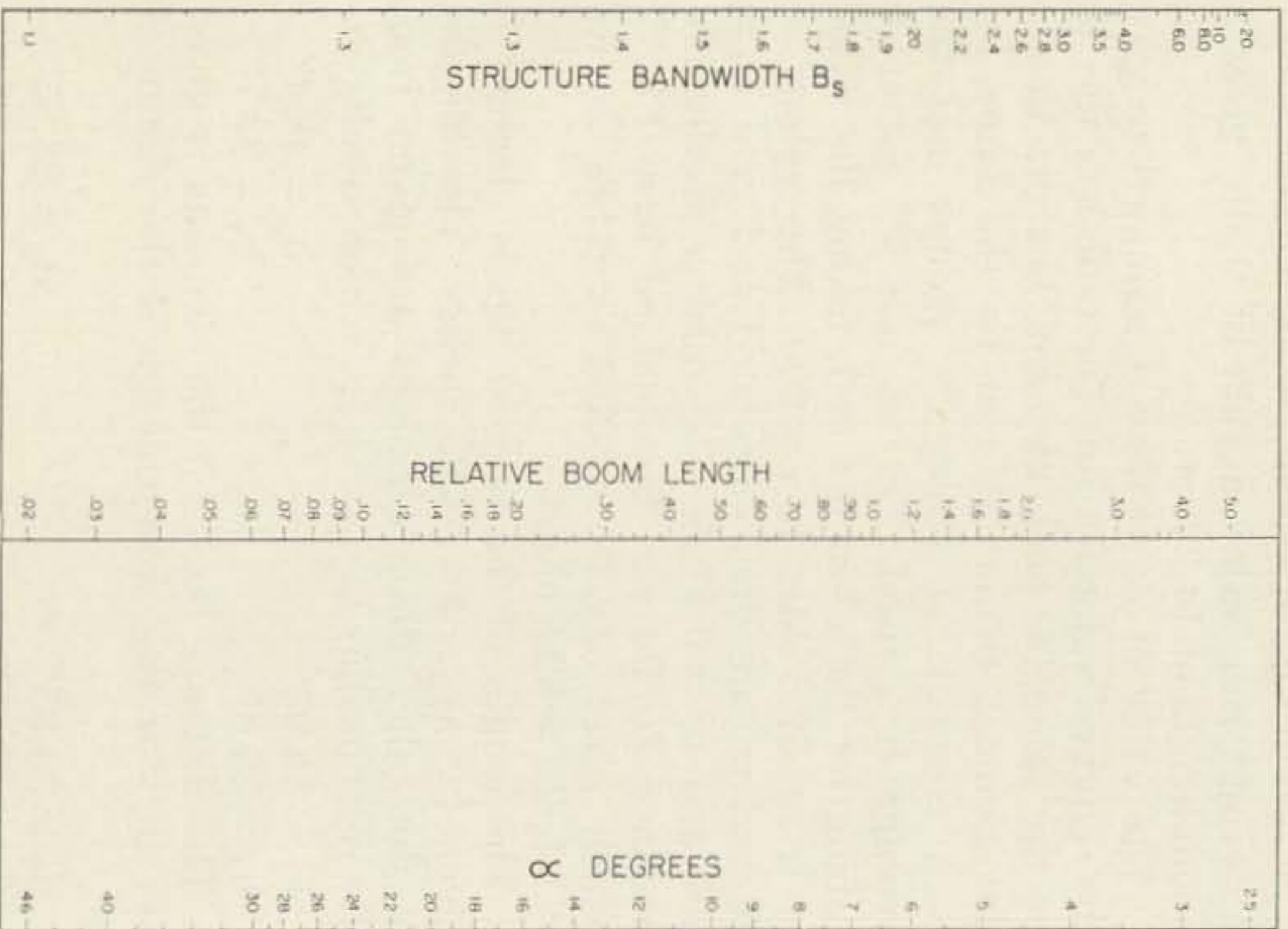


Fig. 5.

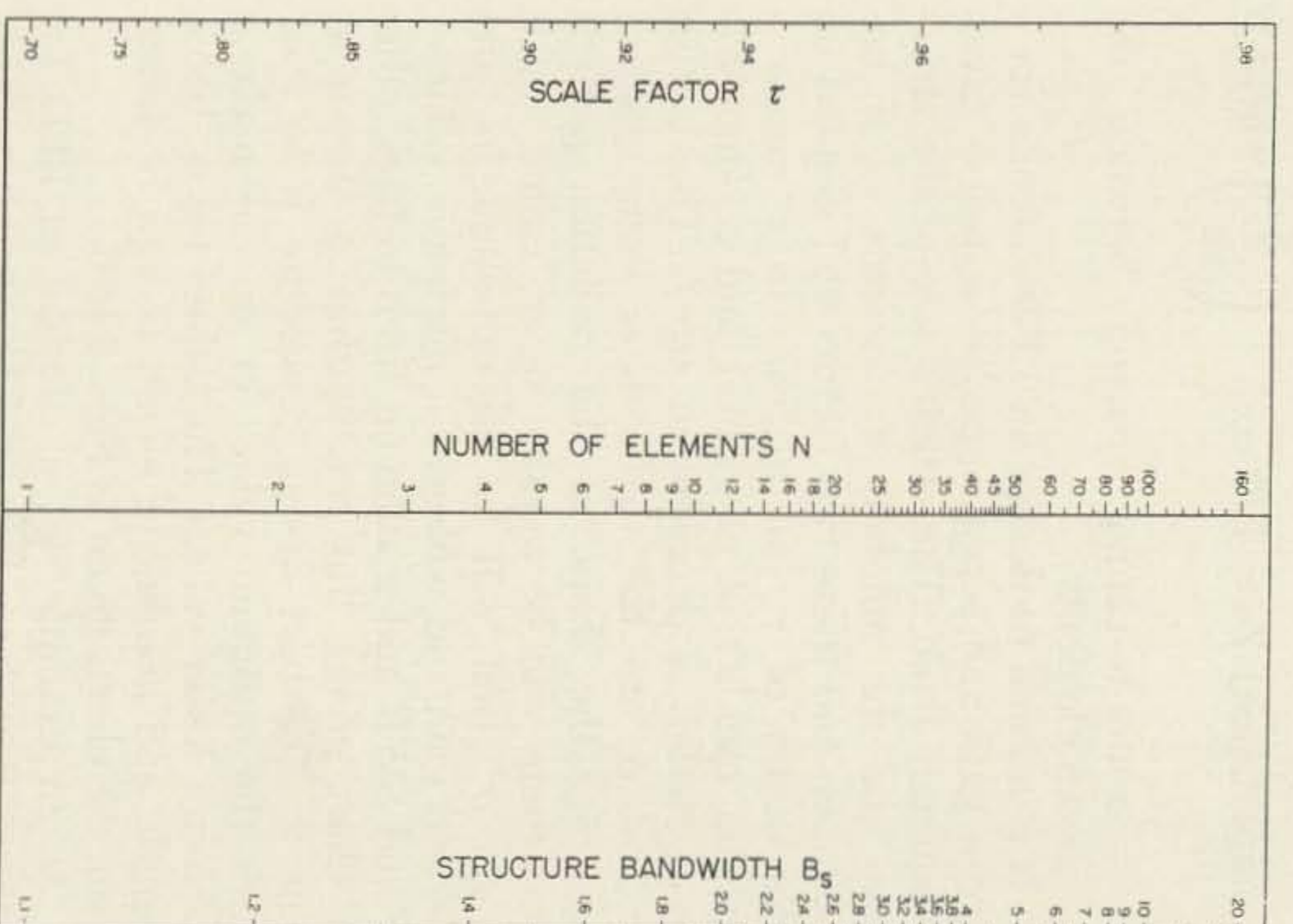


Fig. 6.

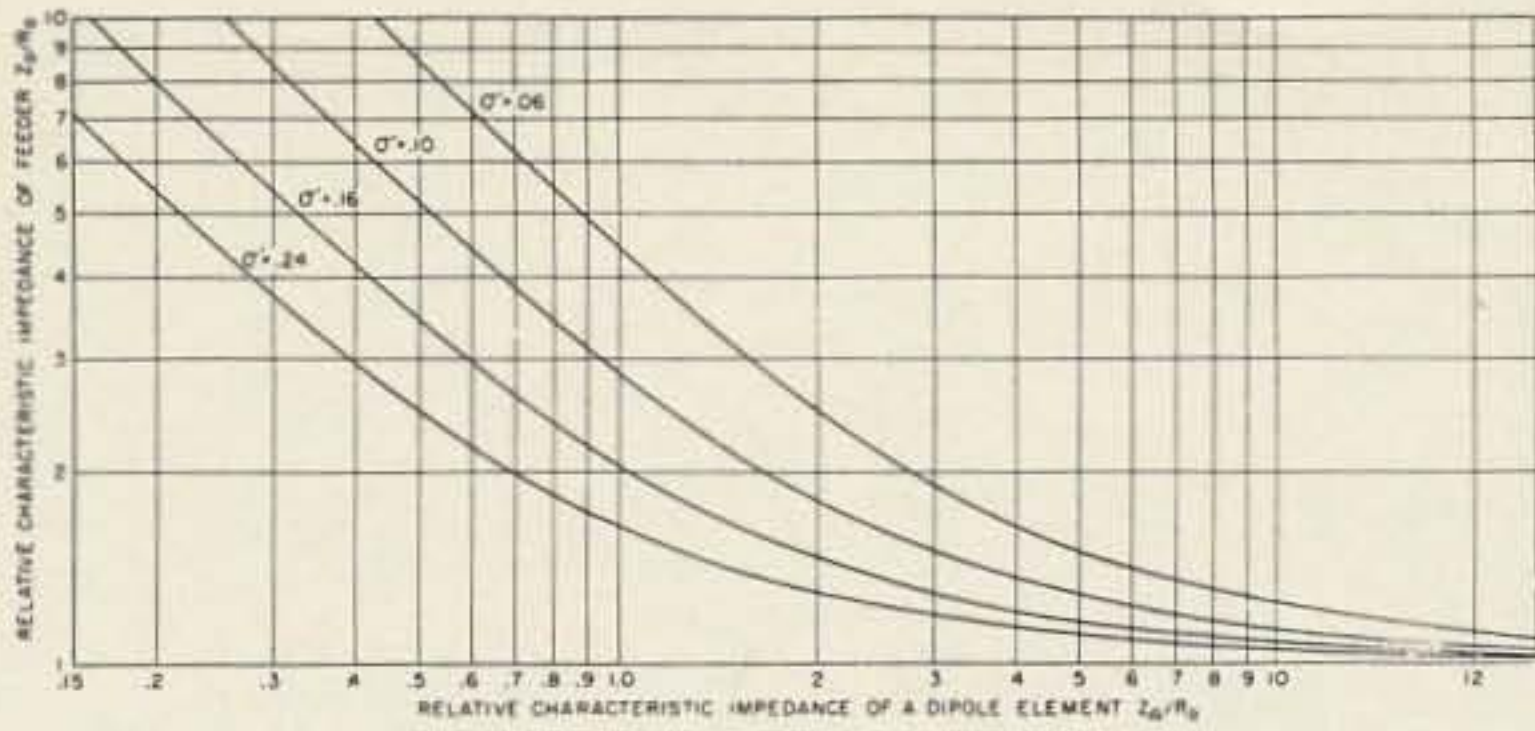


Fig. 7. Relative feeder impedance vs. relative dipole impedance.

satisfactorily replace the cones as long as the cylinder radius is small compared to the wavelength. The spacing between the two boom elements can be calculated from the formula for Z_0 and for our calculated value of $Z_0 = 82.5$ ohms, $b/2a = 1.244$ inches. This means that, using one-inch diameter tubing for the booms, a center-to-center spacing of 1.244 inches is required or the booms will be separated by a quarter inch. To keep reflections from occurring, the antenna should be terminated in its characteristic impedance (Z_0). However a short-circuit across the boom elements at a distance of $h_1/2$, or less, behind the largest element will prove satisfactory. This point can be found experimentally by running a shorting bar between the boom elements until the lowest SWR is obtained on the lowest frequency in the antenna range.

The LPD may be fed in three common ways. (1) By connecting a two-wire, balanced line at the junction of the boom and the smallest element with the characteristic impedance of the line matching the input impedance R_0 . (2) By connecting a balanced, two-wire line at the large end of the structure with the boom elements forming a 4:1 balun transformation. Each boom can be considered to be a coax feeder constructed by inserting a wire in the center of the boom of each structure. For use with 300 ohm line, the formula $D/d = 12.25$ can be used with D the inside diameter of the boom and d the outside diameter of the wire. The two inner wires are cross-connected to the outer booms at the front of the antenna. (3) A coax line, with characteristic impedance equal to the input impedance of the antenna, may be inserted through the back of one of the boom elements. The coax shield is connected to this boom and the center wire to the other boom at the front of the antenna.

Additional details on the construction of the LPD antenna can be found in the article "A Wide-band, high-gain antenna" that appeared in the Nov. '64 issue of 73 magazine.

... VE3AHU

good mobiles STILL

go



HUSTLER

by **NEW-TRONICS**
the home of originals!

HUSTLER is the mobile antenna that has won the widest praise from everyone that has used it. For really reaching out, and for exceptional results on every band, the HUSTLER has no equal. For unbiased opinion of performance, ask any HUSTLER user... there are thousands of them.

See the HUSTLER at your dealer or write us for literature.

NEW-TRONICS CORPORATION

"the home of originals"

3455 Vega Ave., Cleveland, Ohio 44113

Gus

Part 1

I would like to start this story by telling you that at this very moment I am sitting at my typewriter in my bedroom at the home of N. Chhawna, AC5PN, in Dechencholing, Bhutan, in the High Himalyas. At this moment all ham bands are closed. But to do the story up properly I must start at the beginning of my life so that you can understand how all this business of traveling around the world just to put one of these rear countries on the ham bands so that the world's hams could get a chance to contact a "new country" got started.

I was born on Nov. 25, 1908 on a Tuesday (according to an electronic calculator in Schneider-Kreuznach in Bad Kreuznach Germany it was a Tuesday) in a small town in South Carolina. At the age of some few months my family moved to the small town of Elloree, S. C. That's where you might say I got my start—and boy what a start it was!

Ever since I was a young kid down on that poor cotton farm I have wanted to see the world. To be truthful, I never had any hopes of seeing further than maybe Orangeburg, a small city 21 miles from my old home town of Elloree. But you will see that things did happen to change all of this.

I well remember one Sunday when our old cook who had been on a visit to Orangeburg returned home and told us all about the Aero-plane that she saw. She told us that there were some folks sitting in rocking chairs on the wings and that they were rocking while the plane flew over.

Now this set my mind to wondering about the world. Just where would you be if you were to sit in one of those rocking chairs for one whole week, and the plane just kept flying


all that time? I figured you might be in Arabia where all those veiled ladies were with the camel caravans coming in from across the dessert. Maybe you would be in the middle of Tanganyika with all the natives with the big spears and long ornaments hanging from their ears, or again you might be down on one of the palm covered islands in the Indian Ocean looking at the island ladies dancing under the palm trees under a big full moon! Well, I did get to all those places and a lot more, many years later on.

I can truthfully say if there were one thing I was sure of it was never seeing such sights. Even getting to Orangeburg once each year to visit the County Fair was a real adventure that we talked about many days and nights before and after each visit. I didn't think I would ever get to go to those far away places in North Carolina or down in Georgia. Things with us on the farm were very bad; then they got worse. The boll weevil that got in my dad's cotton did not help much either. But I suppose I should thank Mr. Boll Weevil because he assisted my dad in making up his mind to leave his cotton fields in South Carolina and head for that "easy money" down in Florida. He told us that there was plenty of money and oranges in Florida. Now that statement "plenty of oranges" interested us kids because if we got one orange a week in South Carolina we were lucky; of course on Christmas we always got two oranges.

Finally, we sold the farm and my father said we were moving down to Florida. There was a lot of celebrating that night, and we stayed up real late (nine o'clock) and did a lot of talking and planning.

To make this trip my dad bought a third

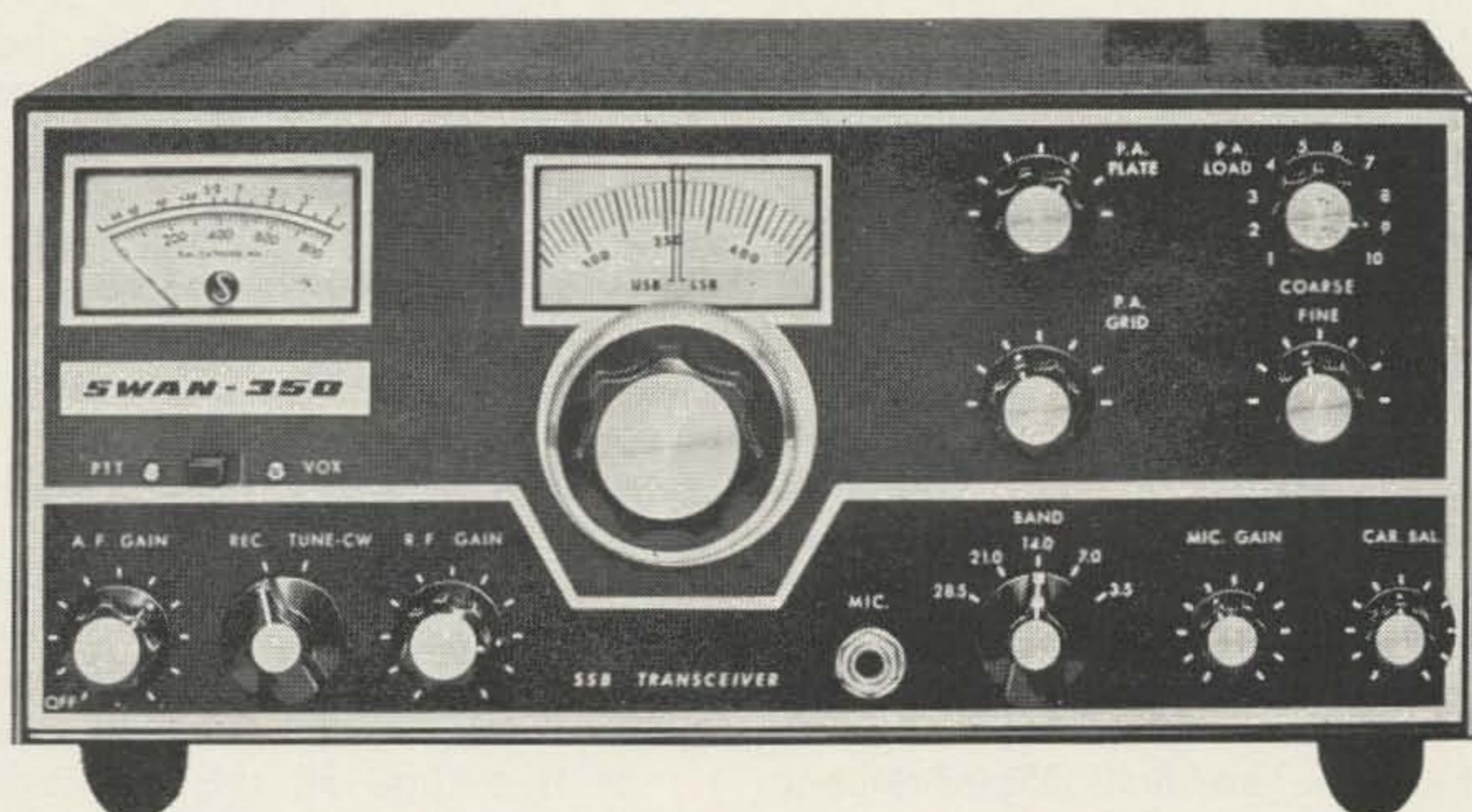Power --- Versatility --- Expensive features
 --- All at a price that defies comparison



the new **SWAN-350** TRANSCEIVER

At only \$395, the Swan 350 transceiver offers features to gladden the heart of the most discriminating. Five bands, 400 watts of power and equally at home as a mobile, portable or home station.

For complete specifications call or write your nearest Henry Radio Store

and — DESIGNED TO SOLVE YOUR FINANCING PROBLEMS . . . HENRY RADIO'S EASY TERMS

6% FINANCE CHARGE • 10% DOWN OR TRADE-IN DOWN
• NO FINANCE CHARGE IF PAID IN 90 DAYS • GOOD RECONDITIONED APPARATUS. Nearly all makes and models. Big savings! 15 day trial — 90 day warranty. 90 day full trade back on new apparatus. Write for bulletin.



CALL DIRECT . . . USE AREA CODE

Butler 1, Missouri	816 679-3127
11240 W. Olympic, Los Angeles, Calif.	213 477-6701
931 N. Euclid, Anaheim, Calif.	714 772-9200
431 E. Green St., Pasadena, Calif.	213 684-0861
6116 N. 27th Ave., Phoenix, Ariz.	602 AM 4-3895

"World's Largest Distributors of Short Wave Receivers"

hand model "T," and you talk about a time! We all wanted to learn to drive that thing; it was one of those arm breaking model "Ts." My dad got it twice and my oldest brother Bud twice, and a few of our friends had an arm or two broken also. None of us had ever driven a car up to the time Dad bought this one. I remember my oldest sister Lorena and what she did to that Model T. We got it going and she drove it OK, but she forgot to put on the brakes and right through the garage she went, right on out in the plowed field, where it stalled.

Now it was my father's turn. He got it going down the road and headed in a country church yard to turn around. Church was in full swing, and somehow he forgot how to stop the thing; up the steps it went and if the church doors had not stopped him, right on in church he would have gone, all the time hollering, "Whoa, whoa, consarn it, I said whoa." After a few months of practicing, Father, Lorena and Bud did learn more or less to control that Fliver. So we started in earnest getting ready for that trip (my first DXpedition) to Florida. (At this time I was not sure whether the world was flat or round, as our school teacher said it was. It was flat to me because there was only flatness everywhere I looked.)

We packed up that fliver with 6 kids, Mom and Pop, a few chickens, Lord knows what all else, and away to Florida, the land of plenty of money and *oranges*.

Back in those days there was not a single inch of paved road between Ellore, S. C. and Orlando, Florida. It was a real American Robinson Crusoe trip all the way: lots of mud which we got stuck in many times and very few bridges. We crossed many rivers on a ferry pulled by a horse on the other side. I suppose this trip made traveling get into my blood. Well, when we got down near Orlando, Florida and started seeing those orange groves, my father, being a regular fellow, stopped any number of times and let us kind of "borrow" a gunny sack full of oranges. Boy, did we eat oranges! Even to this day I love to eat oranges by the sack full and have never got tired of them.

When we got about 5 miles northeast of Orlando, Florida, we just pulled up under a big shade tree and we pitched camp. No one seemed to mind the fact that we did not inquire who owned the land.

My father took his few hundred dollars and went looking for land. He found a nice little tract almost on the shores of Large Lake Fairview and he bought it. But his money was almost all gone, so we went to work with

someone who was wrecking some houses in Orlando. Every night he brought home a big pile of that used lumber and a bucket or two of bent used nails. It was the kids' job to straighten those bent nails and to assort and stack the lumber. This kept up for a number of months until we had enough nails and lumber to build a house. My father quit work for a month and all of us pitched in and built the house. I don't think there was ever a house built in Florida any cheaper.

Well, school time finally arrived and we walked the two miles to meet the school bus to take us all to the Winter Park school. Over in Winter Park I heard about a man who was a radio amateur (at that time I had no idea what one was). His name was W. J. Lee and his call sign was 4XE. I made it my business to meet him, he turned out to be one of the nicest men I have ever met. I remember him trying to explain to me that he was one of the very first people in the world to use quartz crystals to control his transmitting frequency (Mr. Popoff excepted, of course).

At that time all this was miles over my head. In fact my knowledge of radio was zero minus; I had never heard or even seen one yet. But the bug had bitten me and I decided that I must learn more about this radio business. Somehow I got some kind of a radio magazine describing how to build a L. M. Cockiday one tube set (why I picked such a circuit I am still wondering). My problem was to get some money to buy the parts and boy, that \$8.50 tube looked like a gold mine. I sold newspapers on the streets, and mowed lawns every afternoon for months and months before I scraped up enough money to order all the parts except that \$8.50 tube.

I wired the radio on one of my mother's breadboards (they said breadboard and I was very careful to do just exactly what they said). I guess I checked that circuit over hundreds of times and it looked good to me.

After a few more months of scrimping and saving I had my \$8.50 and ordered that tube (I think it was a WD-11). When it arrived I guess I was shaking like a leaf and in the excitement somehow the 45 volts got hooked to the 1.5 volt circuit and that tube went up with a flash. I went running in the house crying my head off saying I had blown up my tube. My father said, "Didn't I tell you not to throw away your money on that radio junk?" Well, my Aunt Polly, who was teaching school was staying with us said, "Gus, I will give you the money so you can get another tube."

Away went the money to some company up North for another tube. This time you can

be assured that those battery wires were wired up right. Of course the set didn't work, and I monkeyed with it for about 6 months before I got a signal from it. To this day I don't remember just what was wrong. But you should have seen the excitement around our house that night. The only signal I could tune in was old KDKA in Pittsburgh, Pennsylvania. My father was the first one who heard it work, and he said, "I knew Gus would make it work."

Then I became a "radio expert" and got a job working in the afternoons in a radio store in Orlando. My job was sweeping out the store every day, dusting off tubes, and later on I was instructed on how to test tubes. My salary was 25 cents per day and 50 cents on Saturdays. But I was in "Radio," that was the main thing. You know how the bug bites, and it had me good and proper.

Along about this time I met NU4ACZ, good ole Tony, and he told me all about ham radio. Now you talk about the Radio Bug nibbling on a fellow! This one really had the hammer lock on me. But old Tony told me that the first thing I had to do was to learn the code before I went any further. I went home and told the folks about this and my sister Lorena said she wanted to learn the code too because she wanted a job at Western Union. I got a door bell buzzer and made a key with an old hack saw blade, and my sister and I learned the code, though it took us six months. But we had learned Land Morse! To make matters even worse my sister had learned Land Morse but on a door buzzer! This really put me in the dog house sure enough. Tony had forgotten to tell me that there were two codes!

My mind was made up. I would learn this darn code or bust. I had by that time built a short wave receiver and by the hour I would sit with a pencil in my hand and write down a stray letter every now and then. I learned it after about a year's practice. Then, after a few more months of study, I felt like I could pass the Ham license test. After three trials I did.

I was now "one of the boys." I got an old Hartley circuit going on 40 meters, operating on a 6 volt battery and 180 volts of "B" battery with an input that was all of 6 watts. After trying out many different aerials I finally got up a $\frac{1}{2}$ wave with a counterpoise and the fun really started.

I had heard Ole Tony working DX, places in Germany, Belgium, England, etc., and I had made up my mind that I could do it too.

For over 6 months I had tried using an aerial and ground with no results at all, as far as working stations out of North America. But boy, when I put a counterpoise in place of the ground, I hit pay dirt! I worked stations in Europe, South America and even Australia. Their prefix was then OA, the letter O standing for Oceania and the letter A for Australia. The prefixes in those days were very simple, nothing like these new prefixes you hear now.

My Pop was an Old Timer and a kerosene lamp was good enough for him. He absolutely refused to have electricity wired to our house. I was stuck on batteries and it looked like that's all I would ever be able to use.

My brother Bud moved up to Philadelphia, Pennsylvania and he wrote me I could get a good job in radio if I came up too. I was not interested in the job; what interested me was that if I went up there I could have a transmitter operating on the ac power mains.

Have you ever tried to go from Orlando, Florida to Philadelphia with \$2.50 in your pockets? Have you ever spent nights in jail while hitch hiking? One jail in North Carolina would not let me out the next morning, as the man who let me in went on vacation that same night. Here I was in a mess boys, and not the only mess I have ever been in. MORE NEXT MONTH. Did I get out of that jail? Did I serve six months on their chain gang? Next month tells about that!

. . . Gus

Envelope stuffers available from 73 for the price of a stamped self addressed envelope. One envelope per stuff.

4. Maxwell Meyers W2BIB Coca-Cola vs ARRL letters. Read for yourself how the League got K2US thrown into the Coca-Cola pavilion attic instead of having a ground floor exhibit . . . thereby losing amateur radio enormous publicity.
53. Synopsis of the K2US/WA2USA story by Dana Griffin W2AOE . . . telling how the ARRL again sabotaged amateur radio for its own gain. This is the disgusting story of the scuttling of WA2USA.

32. An answer to the fantastic distortions in the Washington Amateur Radio Newsletter (mouthpiece for ARRL Hq) June 64 issue. Of slight interest only if you had the misfortune to get a copy of the WARN bulletin.

37. Ditto WARN July 64. More trash . . . lies . . . and mudslinging. Fortunately the Foundation for Amateur Radio in Washington seems to have been able to stop this poisonous publication.

33. Those few of you who read the July 64 issue of CQ and found the wealth of 73 publicity in it may be interested in my reaction. This, my "Cuke Letter," is it.


29-30-31. We still have a few copies of an exchange of letters with Doug DeMaw W8HHS regarding a particularly stupid editorial in his VHF'er, an ad sheet put out by the now defunct Comaire Products. Not worth reading.

All the above are in short supply . . . we'll substitute if we run out of your request. Send SASE's to 73, Peterboro-ugh, New Ham Shire.

The 73-A-Phone

Ever need to shout louder than you can? Perhaps on a DX'pedition when you were on top of the hill and your buddy was just starting up—without the chow?

Here's a device which can help you out in such a situation. We dubbed it the 73-A-Phone not so much because it's appearing in these pages as because (if you use the specified speaker or one of similar characteristics) it will produce a 73 db sound level at a distance of some 90 feet, or the same 73 db sound level inside a room 10 feet high by 15 feet wide by 20 feet deep. This 73 db is twice as much power as average conversational speech levels, so should be clearly heard.

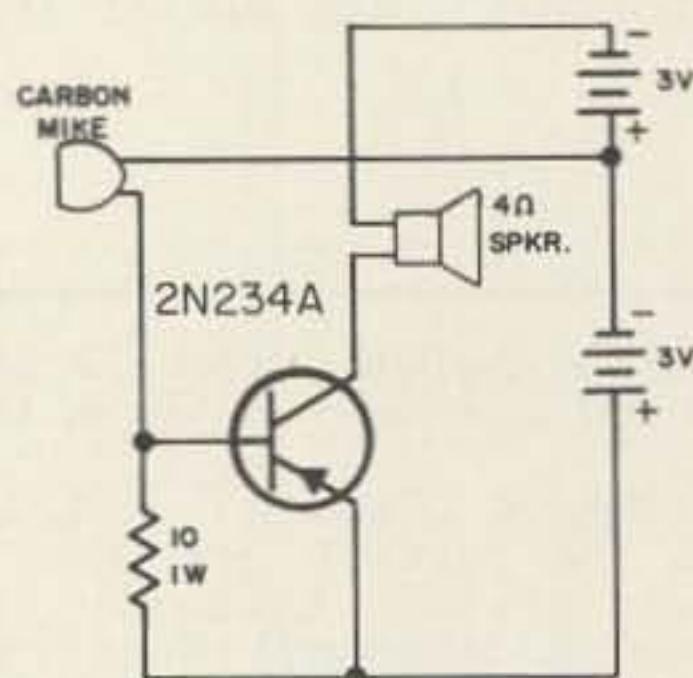

73-A-Phone

As you can see by the schematic, there's not much to the 73-A-Phone. A carbon mike (the Western Electric F-1 button is ideal for the purpose and usually rather inexpensive unless you get caught), a 10 ohm resistor,

the 2N234A transistor, and the speaker are all there is to it except the batteries. For portability these can be flashlight cells, but the larger lantern type are preferred for longer life.

While the University MIL paging speaker is recommended and is the only one I tried, any 4 ohm speaker will work with this circuit. The MIL has a self-contained horn and is a high-efficiency unit, which is why it was chosen, but is admittedly a trifle expensive for such an otherwise simple device.

The transistor delivers approximately 1/3 watt in this hookup. This may not sound like very much, but if it's driving an efficient speaker it's a pretty potent package.

Many variations of this simple circuit are possible, but we don't recommend any drastic increase in supply voltages. Under no circumstances should you increase the base supply voltage above 3 volts; you're free to increase the collector supply as high as 9 volts, though, at the risk of incurring possible distortion. This, naturally, would increase power output somewhat.

With conventional speakers, this can make a most usable portable PA system for hamfest use. The batteries, transistor, and resistor can be placed inside the speaker box, leaving only the wire running to the mike button. Take care to avoid feedback in such use, though—this gadget will surprise you with its sensitivity!

... K5JKX

telrex "BALUN" FED INVERTED "V" ANTENNA KITS

SIMPLE-TO-INSTALL, HI-PERFORMANCE ANTENNA SYSTEMS:

1 KW P.E.P. Mono-Band Kit... 1KMB1V/81K...	\$19.95*
2 KW P.E.P. Mono-Band Kit... 2KMB1V/81K...	\$22.95*

*Kit comprises, encapsulated, "Balun," copperweld, insulators, plus installation and adjustment instructions for any Mono-band 80 thru 10 Meters. Also available 2, 3, 4, 5 Band Models.

Mfd. under Pat. 2,576,929

Write for TELREX PL 65


TELREX LABORATORIES
 ASBURY PARK, NEW JERSEY

DOW-KEY

has a **COAXIAL RELAY**
for most every switching
application . . .

DK60 SERIES

HEAVY DUTY SPDT COAXIAL RELAYS

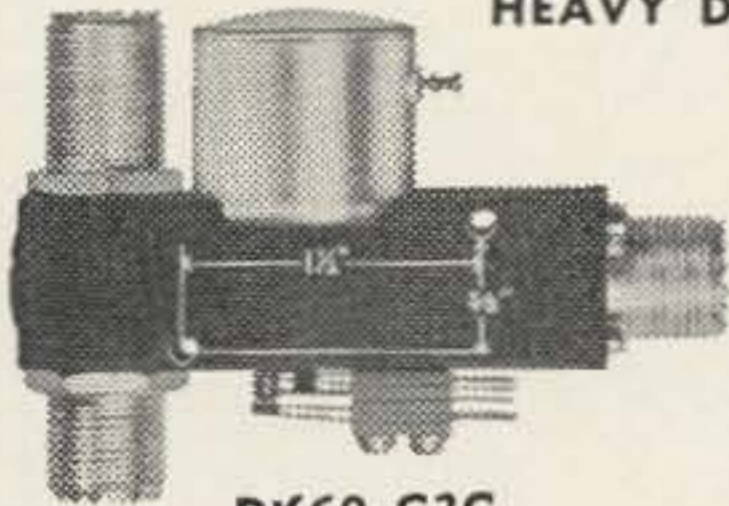

DK60-G2C

Heavy duty SPDT 50 ohm impedance. 1 kw rating. Life expectancy 1,000,000 operations. VSWR less than 1.15:1 from 0 to 500 mc. DK60-G and DK60-G2C feature patented automatic receiver protecting connector for positive isolation of r.f. from receiver greater than 100 db isolation between receiver and transmitter lines from 0 to 500 mc.


DK60-G2C has DPDT external contacts for switching auxiliary circuits. Size: 2 3/4 x 3 3/4 x 1 1/8". Wt. 9 oz.

With UHF Coaxial Connectors, AC or DC

from \$12.45 ea.

DK2-60 SERIES

A DPDT SWITCH for SWITCHING 2 COAXIAL LINES SIMULTANEOUSLY

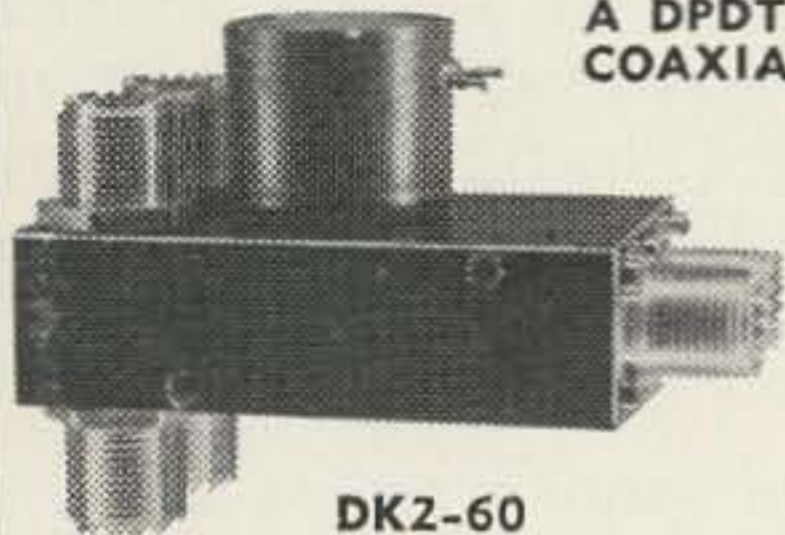

DK2-60


Frequency range 0 to 500 mc. Power rating to 1 kw. VSWR less than 1.15:1 from 0 to 500 mc. Isolation greater than 30 db @ 500 mc. Loss less than 0.03 db @ 30 mc. Life over 1,000,000 operations. 50 ohm impedance. Size: 2 3/4 x 3 3/4 x 1 1/4". Wt. 12 oz.

With UHF COAXIAL CONNECTORS

from \$19.00 ea.

DK2-60B SERIES

A DPDT SWITCH INTERNALLY CONNECTED IN DE-ENERGIZED POSITION

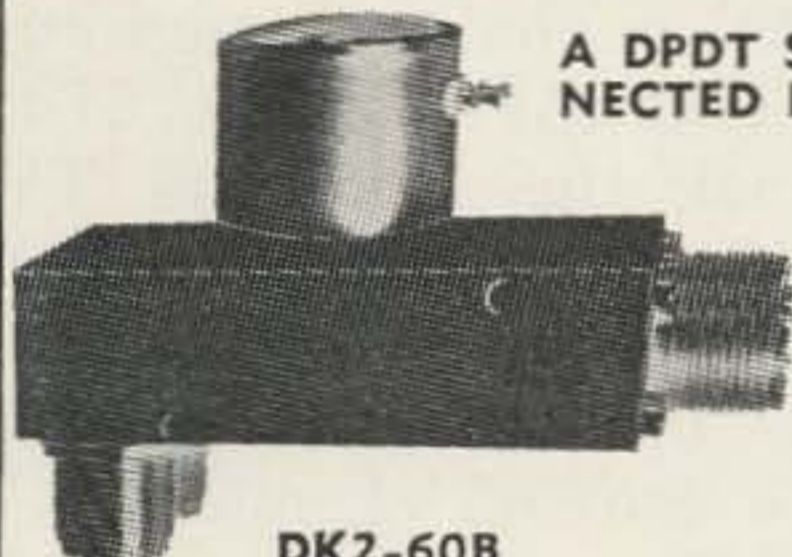

DK2-60B

Ideal for switching in and out a power amplifier between an exciter and antenna. Frequency range 0 to 500 mc. Power rating 1 kw. VSWR less than 1.15:1 from 0 to 500 mc. Isolation greater than 30 db @ 500 mc. Loss less than 0.03 db @ 30 mc. Life over 1,000,000 operations. 50 ohm impedance.

Connectors UHF. Size: 2 3/4 x 3 3/4 x 1 1/4". Wt. 12 oz.

Available in all standard AC, DC voltages

from \$19.00 ea.

DK71 SERIES



DK71

1P6T COAXIAL RELAY FOR SWITCHING OF r.f. SOURCES


Weatherproof. Common connector may be switched directly to any one or combination of six positions. Frequency range 0 to 500 mc. Power rating 1 kw. VSWR less than 1.1:1 at 100 mc. Isolation greater than 40 db at 100 mc. Life expectancy greater than 1,000,000 operations. 50 ohm impedance.

Size 5 3/4 dia. 2 3/4" deep. Wt. 3 lbs. With UHF Coaxial Connectors

\$49.50 ea.

DK72 SERIES

1P3T COAXIAL RELAY FOR REMOTE SWITCHING OF r.f. SOURCES

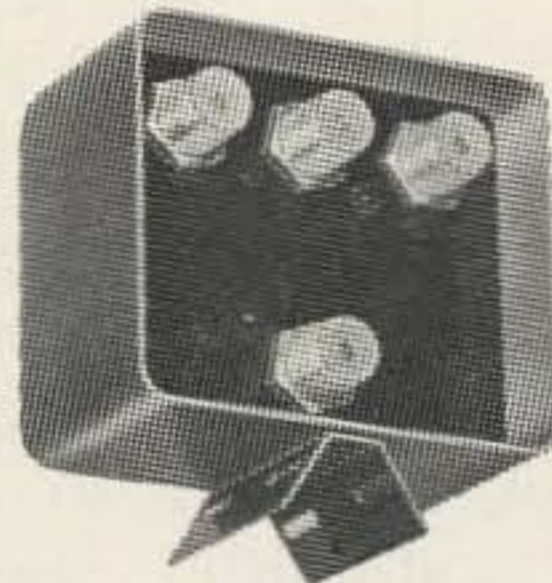

DK72


Weatherproof. Frequency range 0 to 500 mc. Power rating 1 kw. VSWR less than 1.1:1 at 100 mc. Isolation greater than 40 db at 100 mc. Life over 1,000,000 operations. 50 ohm impedance. Size: 4" x 3 1/2" x 2 5/8". Wt. 1 lb., 8 oz.

WITH UHF CONNECTORS

\$22.95 ea.

DK77 SERIES

MINATURE, LOW COST 50 ohm SPDT COAXIAL RELAYS

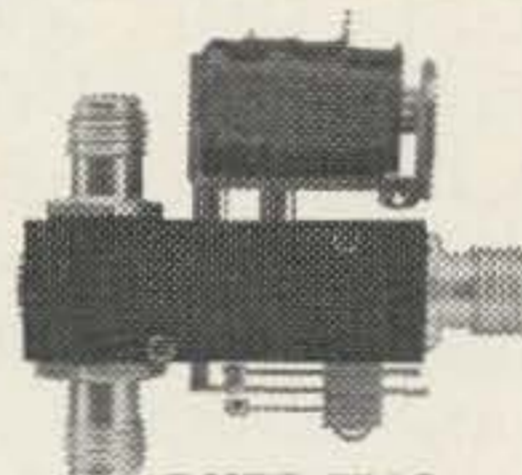

DK77-TNC

Wt. less than 3.5 oz.

from

\$7.90 ea.

DK 77 relays available with phono, TNC and BNC coaxial connectors— with high performance characteristics. Freq. range 0 to 1000 mc. Power rating 250 w. VSWR less than 1.1:1 @ 500 mc. Isolation greater than 30 db @ 500 mc. Insertion loss less than .03 db @ 500 mc. Life expectancy over 1,000,000 operations. Models with 1C in mfgs. type have SPDT auxiliary switches rated at 5 amp @ 110 VAC resistive.

Comply with MIL-5541. AN-C-170 and MIL-S-5002.

AND NOW
DOW-KEY'S


DK78 SERIES



New Manual Coaxial Switches

New manual DK78 series coaxial switches with excellent r.f. characteristics (not wafer switches). r.f. rating, 1 kw. 50 ohm impedance. VSWR less than 1.05:1 at 150 mc. Isolation greater than 50 db @ 500 mc. and greater than 80 db @ 30 mc. With dial plate and knob. Wt. 10 oz. Size: 3" dia. x 1 1/8" deep.

Available: 1P2T, SP3T, 1P6T and crossover switch from \$12.75 ea.

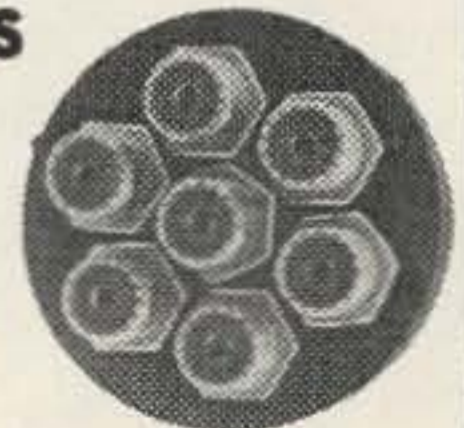

DK78-6

DK60, DK2-60, DK2-60B, DK71, DK72 available in standard AC, DC voltages. Also available with types BNC, TNC, N & C Connectors. DK77 all st. DC voltages. DK78 with BNC, TNC, N & C connectors.

DOW-KEY UHF CONNECTORS



DK201
Panel Mount
Male Connector
\$1.25 ea.



DK202
Double Female
Connector
.85 ea.

DK210
Female UHF to
Male Phono
Connector
\$1.25 ea.



DK211
Male UHF to
Male Phono
Connector
\$1.25 ea.



AVAILABLE TOO: DK61, DK63 and DK67 Series of Relays for Military and special application. Write for complete brochure of Dow-Key Products.

Dow-Key products available at your distributor or write:

Manufactured by **DOW-KEY COMPANY, Thief River Falls, Minnesota**

The 1215'er

How to build (easy) a good super-heterodyne receiver that tunes from 1200 to 1300 mc using a \$1 tube (better make that \$2 if you insist on new brand names) and a store-bought capacitor, a hack-saw, soldering iron, and tin snips. A low cost transmitter, and 12 element yagi are also included.

Introduction

The frequency region known as UHF, 300 to 3,000 megacycles, is a fascinating place for the true experimenter, but *there are problems!* Right away on the first amateur band in it, 420 to 450 mc, techniques begin to get fussy. Circuits are described as, for example; "L1 is a $\frac{3}{4}$ inch brass strap, $\frac{1}{4}$ inch wide, soldered to pin 5"; transmitter circuits feature \$17 tubes; and "a real low noise rf amplifier tube" costs \$10 and up.

With this and lot's more like it in mind what would you say to a \$1 tube used in a good, variable capacity-tuned local oscillator for 1215 mc? There is no mystery about it (except maybe a little in the cathode circuit) but it may sound as though there was before you really study the subject.

A great many electronic problems, defective

operation, unsatisfactory results, etc., are found to be the result of not one but several troubles working together. We have mentioned this in a previous article (73, Feb. 63). In as many as six different items, the absence of any one of them can cause inability to reach the desired goal.

On 1200 mc it's the same way. It takes a number of things together to operate inexpensively.

Details

1. The tube: So far as I know there are only a few low cost tubes that will perform on 1200-1300 mc. A. The 6AF4, B. the 6T4, and C. 6DZ7. As usual, the radio and TV industry has given the amateur a lift. When it is built for those boys you can be sure it doesn't cost much! I'm not kicking. On the contrary, I look for the "82 channel law" to benefit us amateurs like mad. Like maybe with a \$2 low-noise lighthouse tube. And UHF tuning capacitors for 25 cents, maybe.

2. The tuning capacitor: Good old Hammarlund Co. has made these for some time. I do not know of any other capacitor except the Hammarlund type macbf butterfly type that

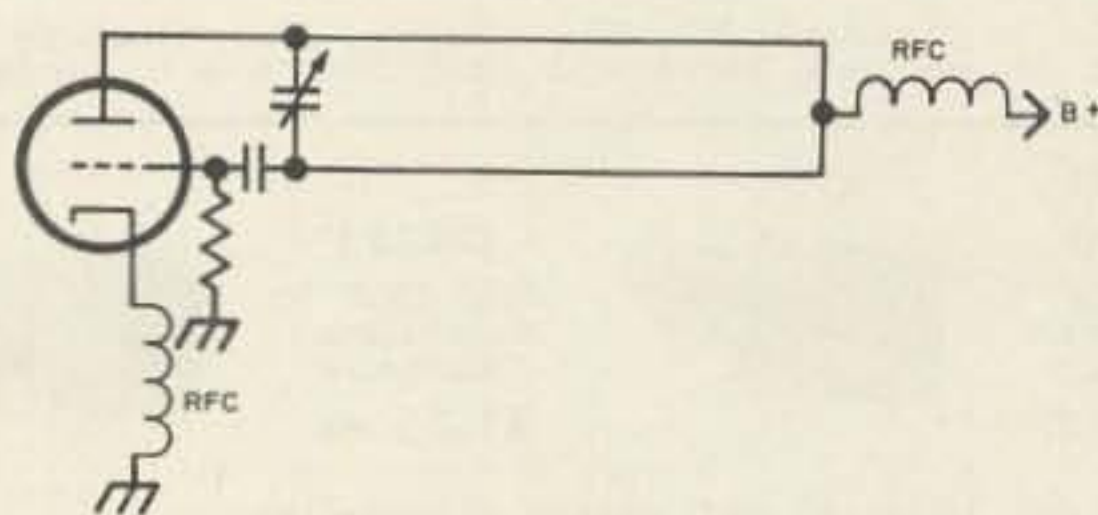


Fig. 1. Quarter wave oscillator.

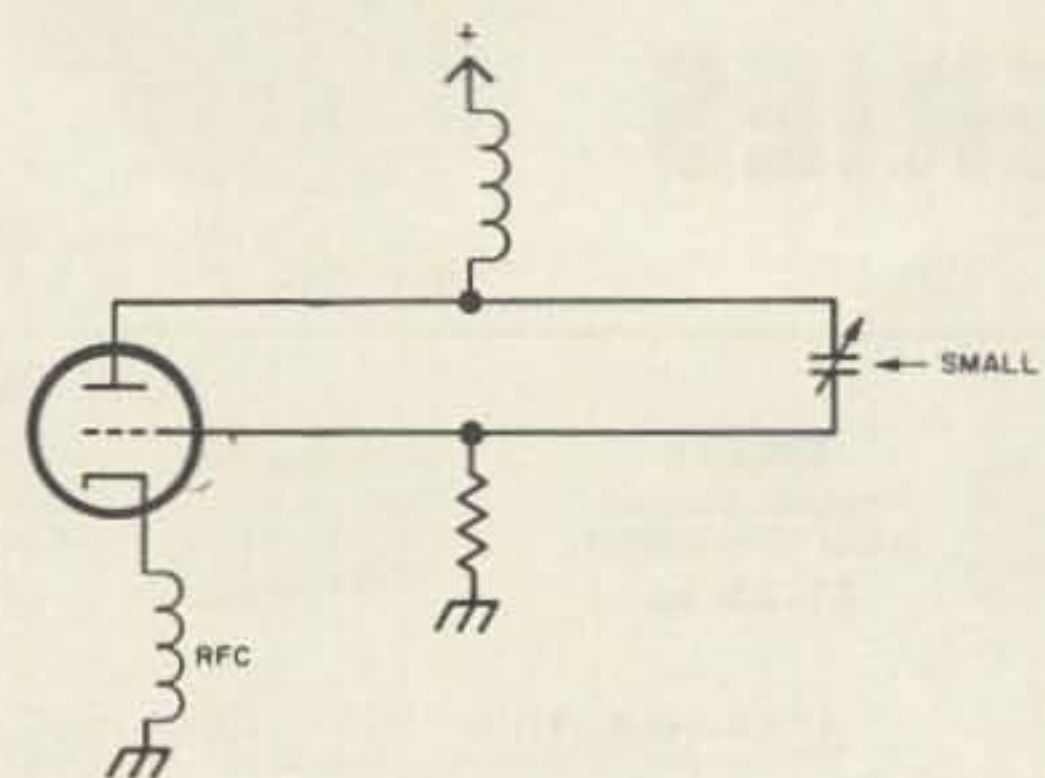


Fig. 2. Half wave oscillator.


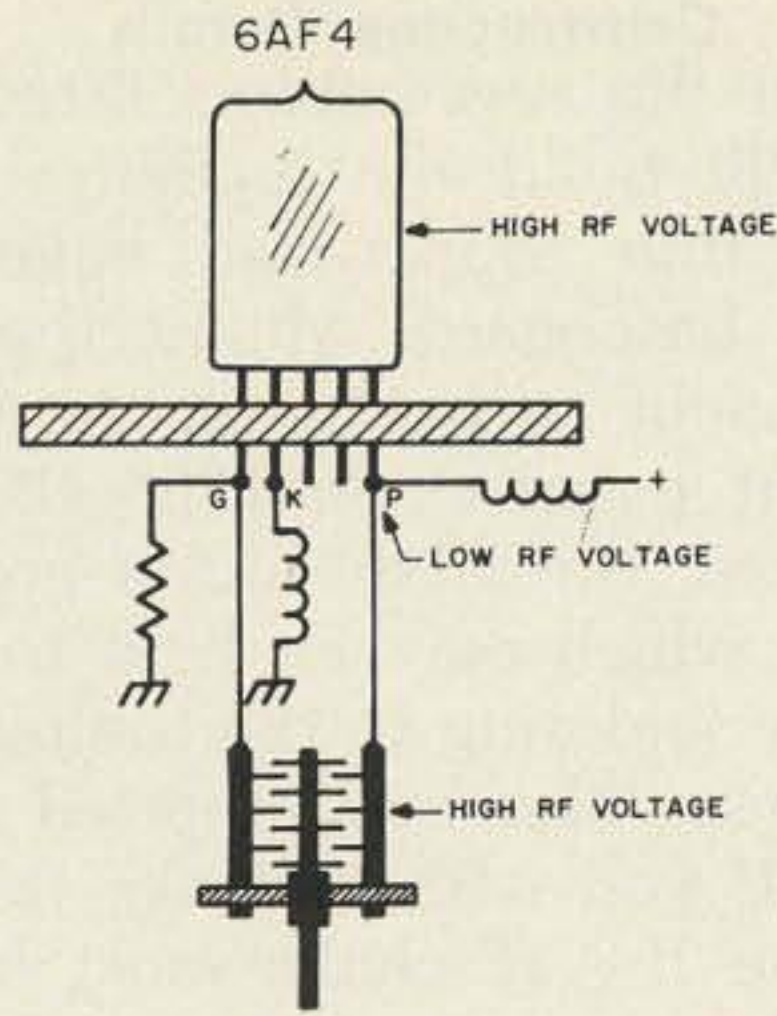


Fig. 3. Practical half wave oscillator.

will do the job. I mean of course, drill a single hole, use a 10 cent shaft extender, an 89 cent slow motion dial, and tune from 1100 to 1300 mc.

3. Half-wave lines: Let's try it this way. Half wave lines are well known but wait and see what happens when you add all together. Fig. 1 shows a simplified circuit of a 200-300 mc quarter wave line oscillator. Note that the "line" is acting like the old familiar pre-war ultra-audion circuit, with the plate on one end and the grid (out of phase, which is of course correct) on the other. This works fine up to a point. This is where the line shorting bar has arrived in the vicinity of the socket and grid capacitor. If you squeeze everything like mad it will go well over 500 mc, but don't use this circuit there! Fig. 2 shows a much better way. Note that now there is a half wave line on *each* line, so that if you consider the phase out and back you could call it a "full-wave oscillator". The trick now is that you can jam the first quarter wave right into the tube and, as in Fig. 3, you can still tune it with an "ordinary" (one that you can buy ready-made) capacitor! Even to 1400 mc! With the smallest Hammarlund butterfly type, 2 stator and 3 rotor plates, it tunes from well below 1100 mc to over 1300.

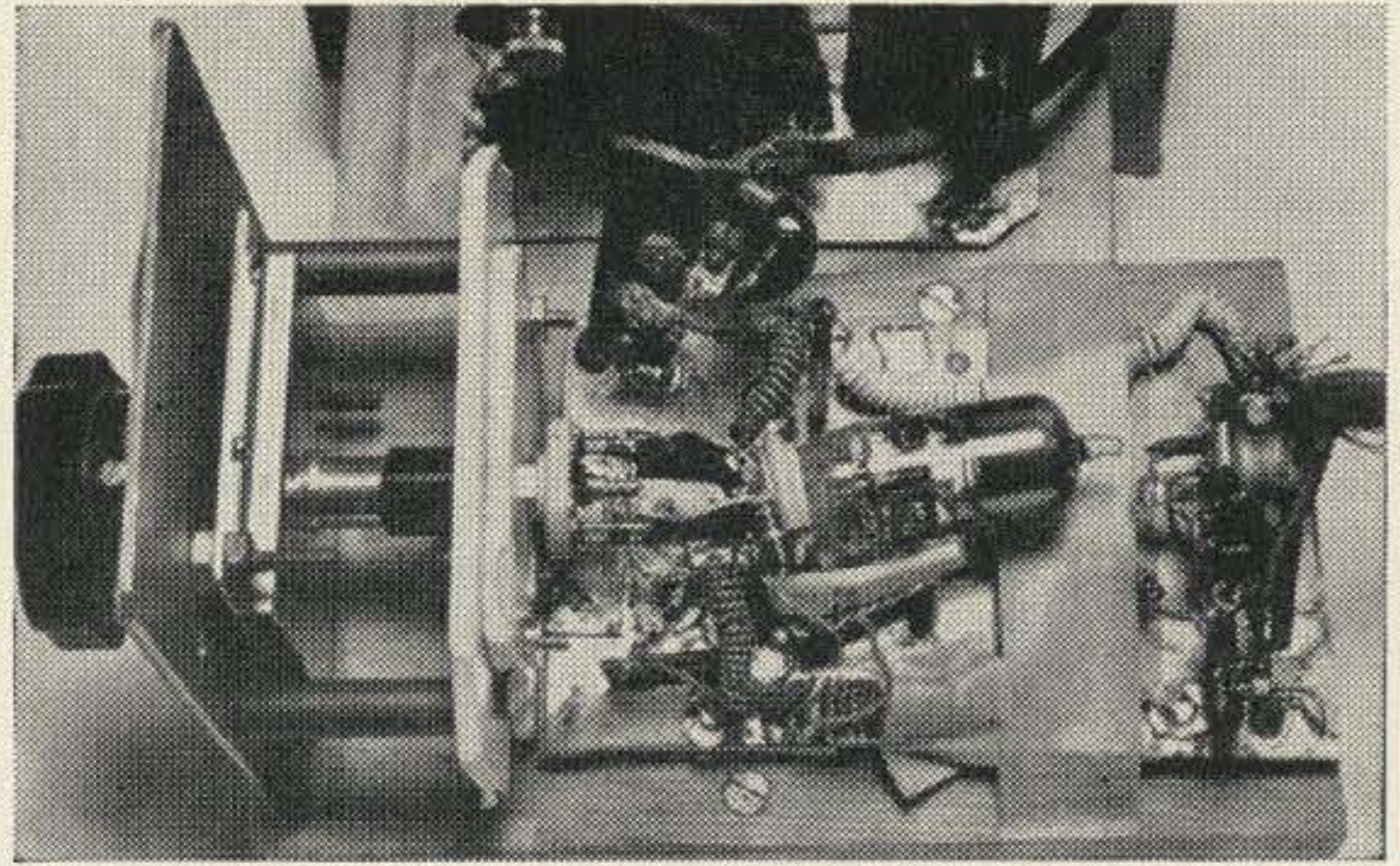4. Don't go away yet. There are still some other ingredients. The shape of the lines next. As you go up in frequency towards microwaves (1400 mc) you will find more and more that the configuration of what you are using becomes of greater and greater importance. This leads eventually to waveguides but these are not in today's lesson. However, the use of flat opposed straps of thin brass (should be silver-plated) for the "lines" in Fig. 3, which is the same as Fig. 2 but going up in frequency, is a must.



Receiver local oscillator/Transmitter

5. Socket: Believe it or not, there is a socket used! It just happens that for UHF TV there is a very thin porcelain socket, which grabs the tube pins right up close to the glass base of the tube and allows you to make connections which are very short. Don't try the usual VHF kind. Believe me, you need everything working for you at 1400 megacycles. You don't have to go to 1400, but if 1300 is the end of the line you won't do very well on 1296.

6. The "ground-plane" chassis: It has been found by trial and error that on positioning both the lines an equal distance, about 1/4 inch, from the base plate on which the oscillator is built, the maintenance of correct phase will be aided. Just one thing in mind, if you make a Chinese copy it will work up to 1400. Most of those I have built are still oscillating at 1500 mc, but that's it. The end of the line. Remember, this is still a \$1 tube plugged into a socket.

7. The cathode circuit: Here there might be a little "magic". A "good" circuit (that is, expensive) on L. band (1200) with a plunger tuned coax cavity between the plate and grid

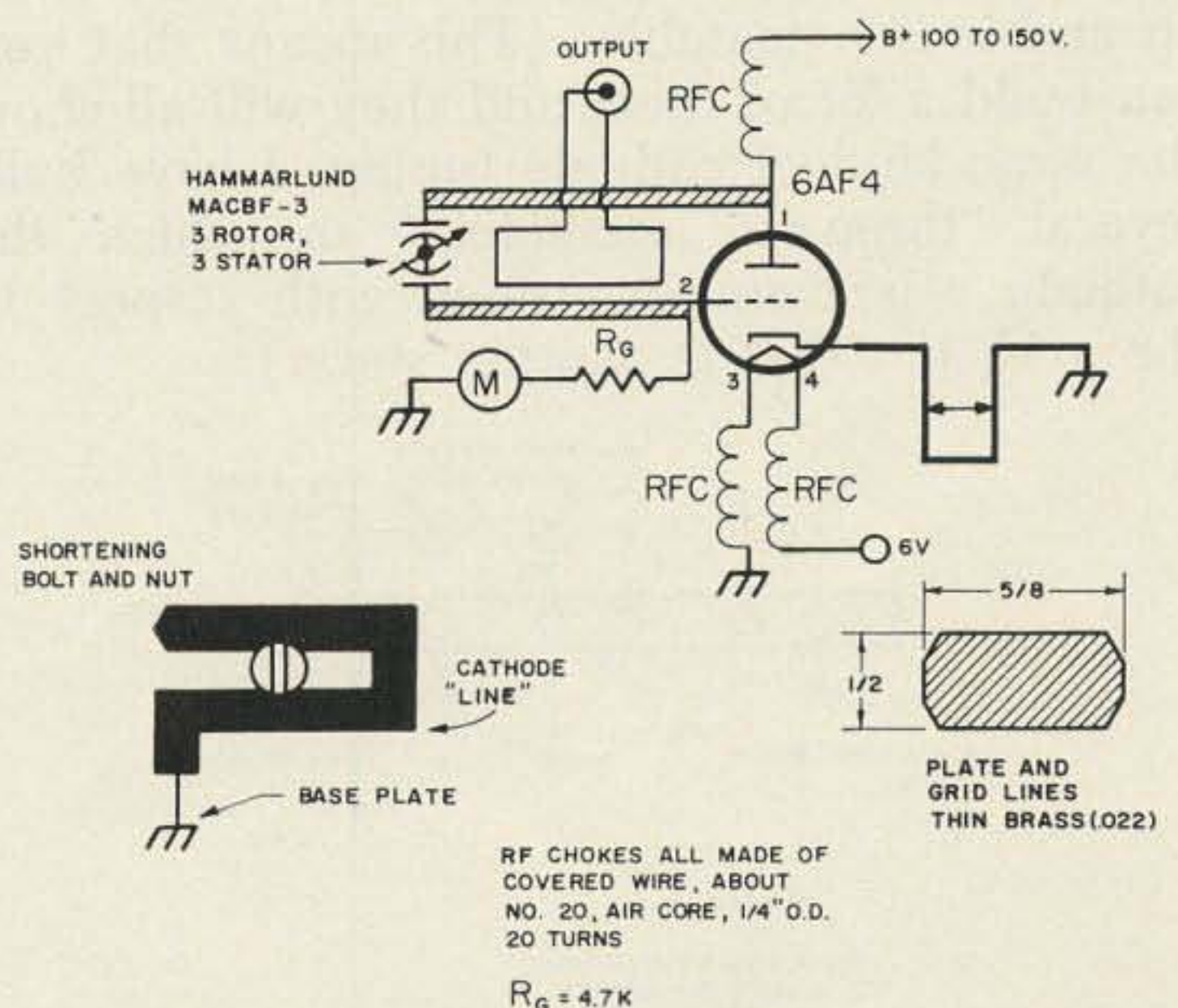


Fig. 4. L.O. and transmitter.

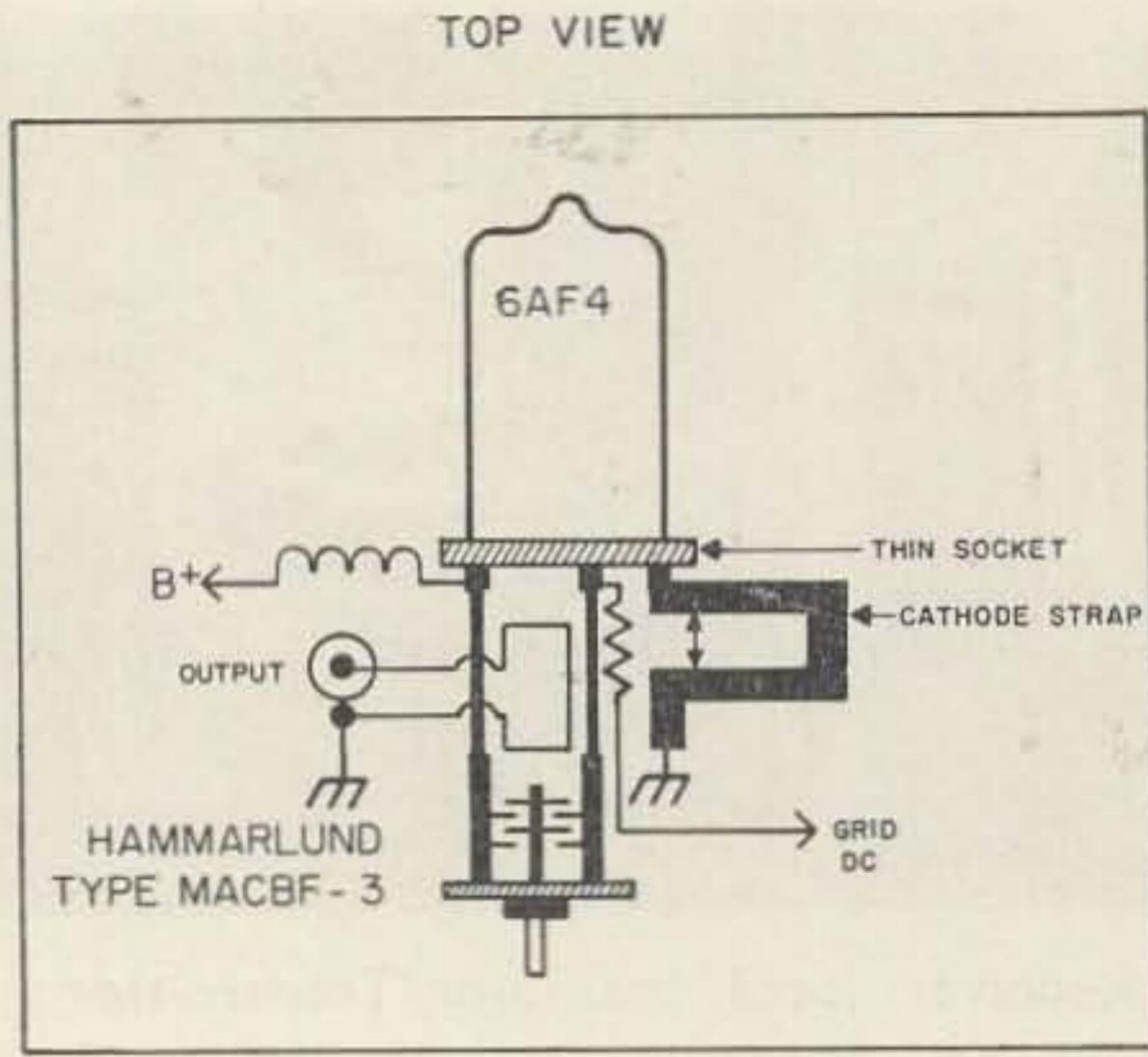


Fig. 5. Top view of oscillator.

of a 2C40, and another between the cathode and grid, will have a relatively easily determinable phase relation between the cathode and the plate. This is known as "in phase", or, as the cathode goes positive, so does the plate. The grid goes negative, "releasing" the plate which goes positive, etc. However, in an inexpensive "TV" triode such as the 6AF4 the plate, grid, and cathode are all in there together. The grid does not separate the plate from the cathode as in the 2C40. The plate-grid capacity of the 6AF4 is 1.9 mmf, which makes the fixed capacity on the tube end of the lines in Fig. 3. Now, what about the cathode? The "bible" says C_{gk} is 2.2 mmf, and C_{kp} is 1.4, but this doesn't help much. So, back to the good old "trial and error" again. After all Faraday didn't do too bad using this method a good portion of the time. After some years of it I have evolved a method of treating the cathode portion of triode oscillators that at least works, even if it isn't exactly obvious just how. A certain small amount of inductance down to the base plate from the cathode does the trick. It tunes quite broadly which is just as well, but it does peak up and it is repeatable. (This means that you can build a lot of them and they will all show the same kind of cathode tuning. I have built several "three-rod oscillators" in which the cathode was definitely tuned with respect to the grid, but that is another story.)

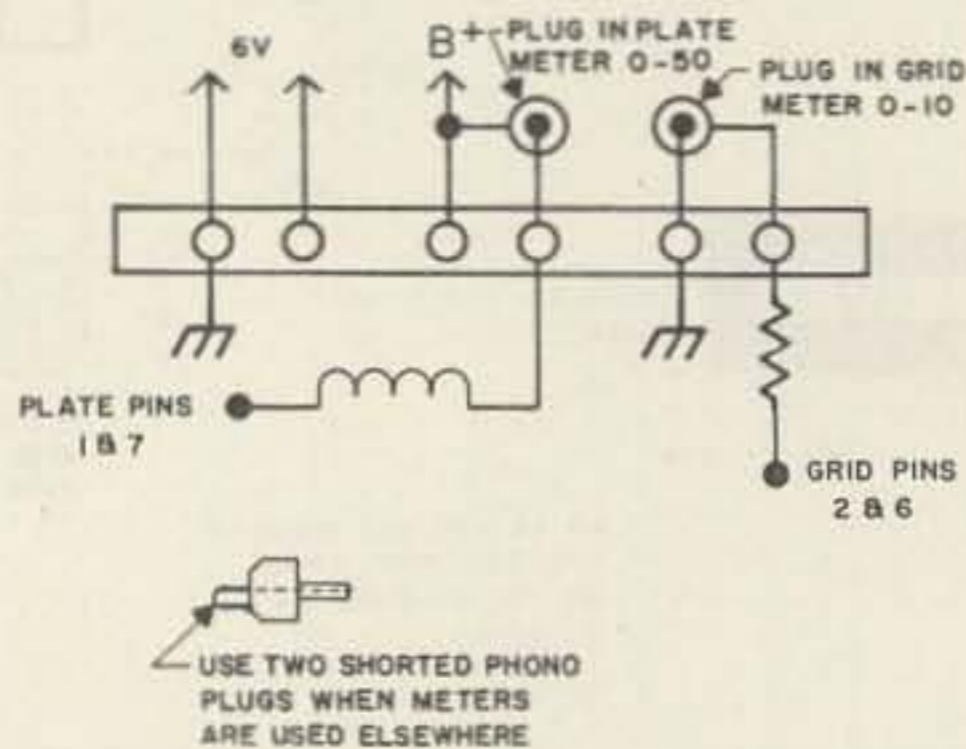


Fig. 6. Metering and power connections.

Construction Details

Now, with the seven items listed above in mind, we will build the oscillator of Fig. 4. Once again thin copper-clad bakelite makes an excellent baseboard. Mount the Hammarlund type macbf capacitor on the vertical insulating front panel as in Fig. 4B. The grid and plate lines, the UHF socket and the tube make a unit which may be held together and supported by soldering to the tuning capacitor. The socket may also be supported by a piece of insulator if you wish to make the assembly stronger. The B+ rf choke must be soldered directly to the plate pin (pin 1) of the socket, and the grid resistor directly to grid pin 2. That is, with the tube mounted as shown, which it must be, use the uppermost pins. Note that the plate pins are 1 and 7, and the grid pins are 2 and 6. Details in Fig. 4. This means that the solder which holds the socket pin to the brass plate line also holds the end of the plate choke. There isn't too much room there but it does work. Ditto for the grid resistor and grid line.

Firing Up

I generally use a couple of phono jacks for meters on the cable strip. See details Fig. 6. This frees your meters for other rigs. With 6 volts ac on, the tube should light up visibly. If everything is ok the plate current should rise as the plate voltage is turned up. It's a good idea to have a variable plate voltage supply for these tests. At somewhere around 15 to 20 ma the tube should start to oscillate and the grid current should begin to rise also. Plate current of some 25 ma may be found

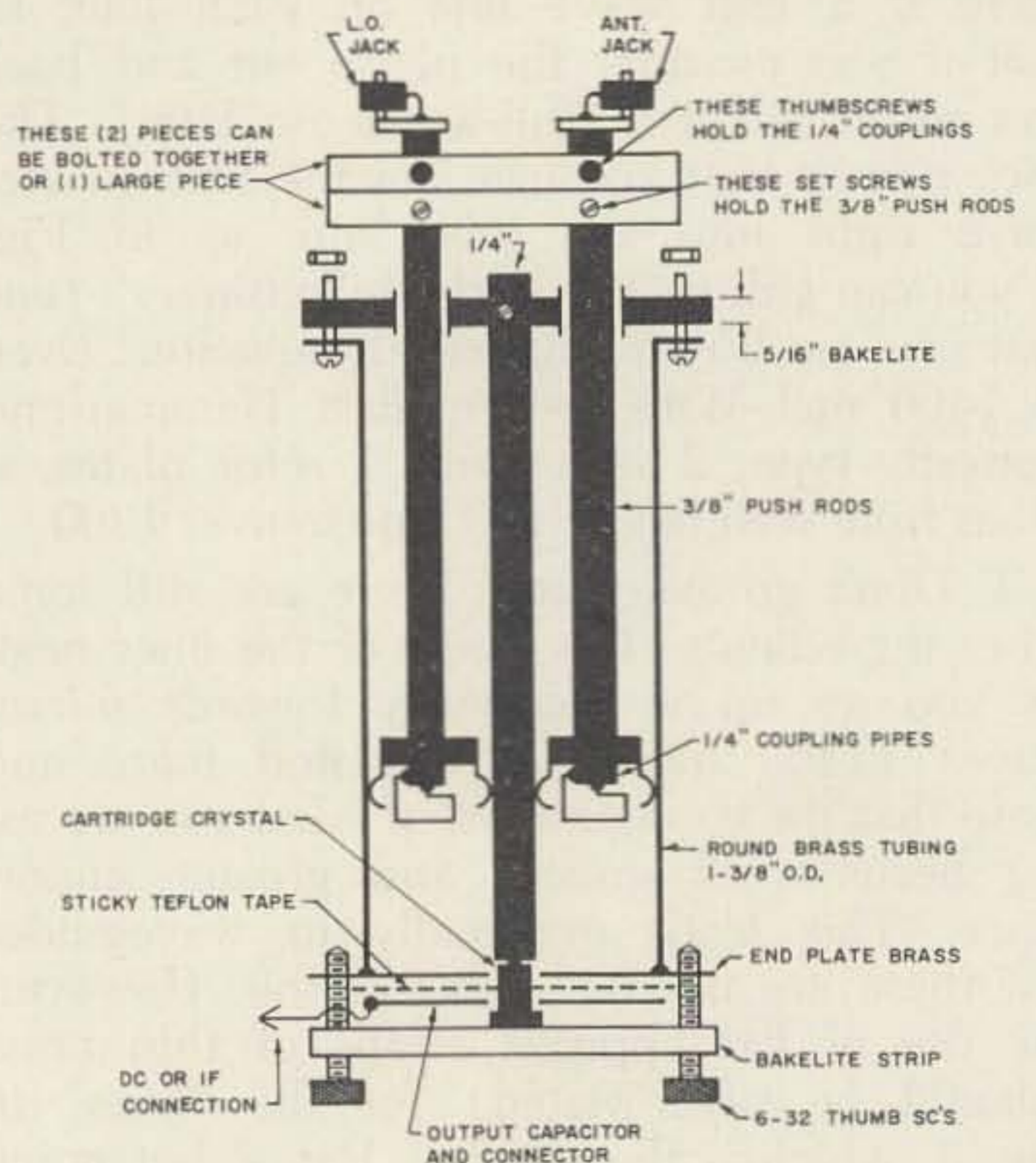


Fig. 7. Cavity mixer for 1215 mc.

SERVICE TESTED EQUIPMENT

ORDERS PREPAID WITH
CASH REMITTANCE
IN CONTINENTAL U. S.



RECEIVERS

Collins 75S1	\$369.00
Elmac M-1070 P/S	49.00
Elmac PMR-6A	39.00
Gonset G66	69.00
Gonset G66B	79.00
Gonset 3 way P/S	15.00
Gonset Super 6 Convertors	19.00
Hallicrafters S-76	85.00
Hallicrafters S-85	65.00
Hallicrafters SX-71	85.00
Hallicrafters SX-99	84.00
Hallicrafters SX-101	189.00
Hallicrafters SX-111	169.00
Hammarlund HQ145	189.00
National HRO-60 (w/5 coils)	239.00
National NC-60	39.00
National NC-183-D	179.00
National NC-270 (like new)	165.00
National NC-300 w/calib.	189.00
National NC-303 w/calib.	259.00
RME 4350A	129.00
RME 6900	169.00
RME VHF-152A	29.00
RME DB-23	27.50

TRANSCEIVERS

Galaxy III (demo)	269.00
Gonset G-76	199.00
Hallicrafters SR-150	459.00
Hallicrafters SR-150 AC P/S	75.00
Hallicrafters SR-160 (demo)	295.00
Heath HW-22 (like new)	125.00
National NCX3 (like new)	275.00
SBE SB-33 (demo)	249.00
Swan SW-120	159.00
Swan SW-140	159.00
Swan SW-175	249.00

TRANSMITTERS

B & W 5100	\$139.00
B & W 5100 w/51SB	269.00
B & W LPA-1 Linear	219.00
Central Electronics 200-V (like new)	495.00
CE Slicer Model "B"	27.00
CE Q-Multiplier #DQ	17.00
Collins 30L-1 Linear (like new)	375.00
Collins 32V-1	129.00
Elmac A-54H	29.00
Elmac AF67	49.00
Globe Scout 680A	49.00
Globe "Sidebander"	49.00
Globe 755 VFO	29.00
Globe 755-A VFO	39.00

MISSION HAM SUPPLIES

3316 Main Street
Riverside, California 92501
Phone 683-0523 (area code 714)

Globe AT-4 Matchbox	34.00
Globe LA-1 Linear	59.00
Gonset GSB-100	199.00
Gonset GSB-101 Linear	189.00
Hallicrafters HT-31 Linear	129.00
Hallicrafters HT-32B (Like new)	525.00
Hallicrafters HT-33 Linear	299.00
Hallicrafters HT-40	65.00
Heath "Apache"	159.00
Heath DX-60	75.00
Heath DX-100	89.00
Heath HA-10 Warrior	209.00
Johnson "Challenger"	49.00
Johnson "Valiant"	179.00
Johnson "Courier" (like new)	199.00
Johnson "Pacemaker"	179.00
Johnson "Navigator"	99.00
Johnson Desk "Kilowatt"	595.00
Johnson Viking II	89.00

VHF EQUIPMENT

Clegg "Venus" (demo)	\$459.00
Clegg "Interceptor" 2 & 6 M Recvr	339.00
Gonset Comm II 2M (clean)	129.00
Gonset Comm II 6M	99.00
Gonset Comm III 6M	159.00
Gonset Comm IV 2M	279.00
Gonset Comm IV 6M	229.00
Gonset Comm 6M Linear	99.00
Johnson 6N2 Xmtr	99.00
Lafayette HE45B	99.00
Poly-Comm 6-2 Transceiver	239.00

NEW EQUIPMENT SPECIALS

	Reg.	Special
GONSET		
Super 12 Conv.	\$94.50	\$39.00
GPP-1 Phone Patch	49.95	39.00
HALLICRAFTERS		
HT32B	725.00	589.00
HT40K Trans. Kit	89.95	69.00
HT41 K.W. Linear	395.00	269.00
NATIONAL		
NC303	449.00	389.00
SWAN		
TCU	115.00	69.00

**ORDER
TODAY**

MISSION HAM SUPPLIES
3316 Main Street, Riverside, Calif. 92501

Attn: Bill Hullquist, K6LOS, Please Ship me the following:

\$ enclosed. (Cash orders shipped FREE in continen-
tal U. S.)

- QUOTE trade allowance and terms.
 Please send latest HAM flyer.
 Put me on your mailing list.

NAME Call
(please print)

Address

City Zone State Zip
(Calif. orders add 4% tax)


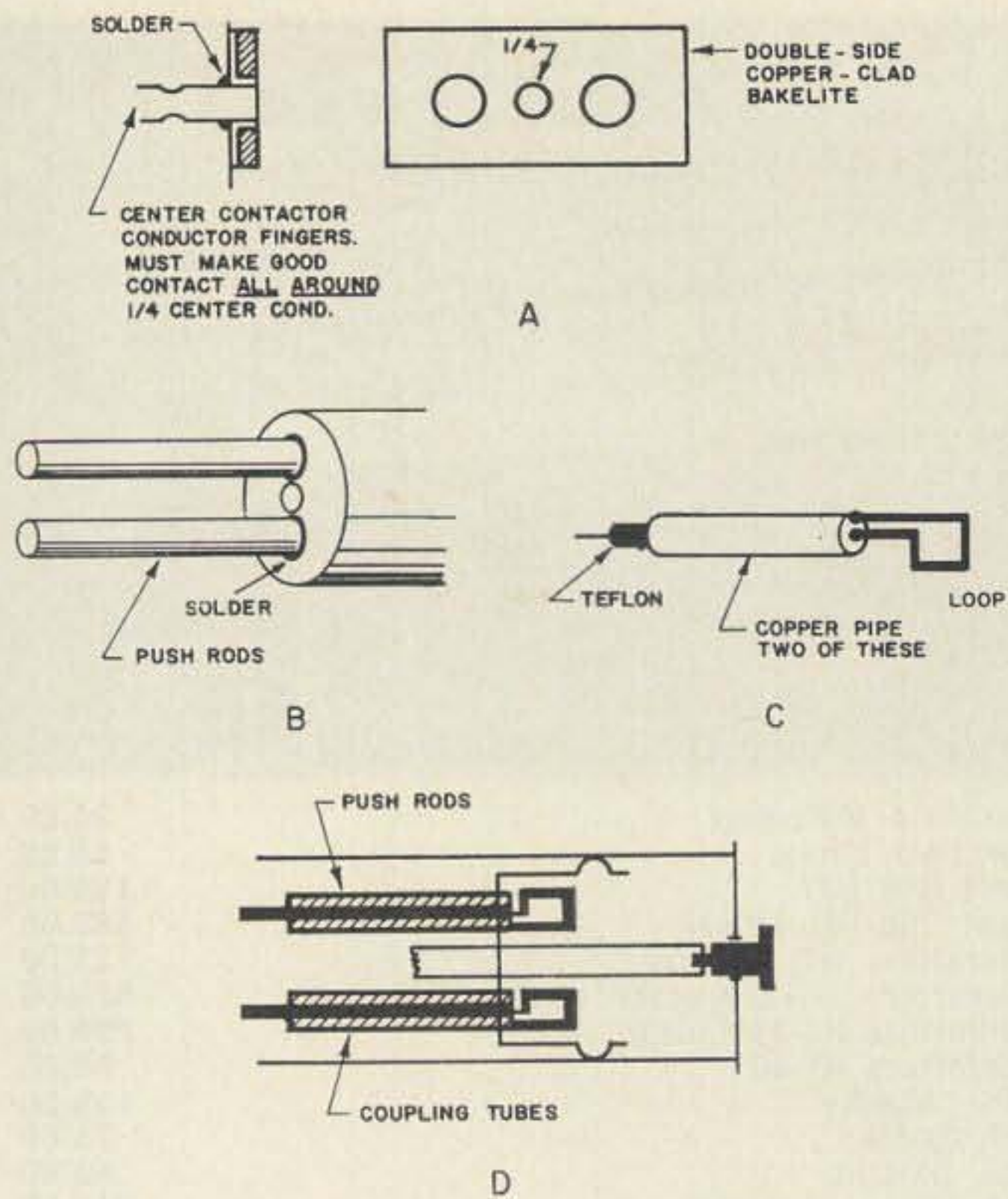


Fig. 8. Details of the cavity.


at 1100 mc rising to over 30, or even 35, near 1300 mc. The frequency of this unit can be adjusted for 1200 to 1300 mc, less the *if* frequency used. This little word "adjustment" actually means unsoldering and cutting the brass strips or making new ones. That's just part of the fun. For an *if* amplifier I have been using a slightly modified ASB-7, double frequency *if*, first stages on 52 mc. A low cost do-it-yourself *if* will be described later, but there really are (or were) loads of surplus wide band *if* strips around! Don't forget that 1215 is the modulated oscillator portion of the band, by general agreement, and this means an *if* bandwidth of several megacycles, not kilocycles. Use whatever dial you wish for the tuning control. Don't forget that the butterfly capacitors tune only 90 degrees.

Good Cavity Mixers for 1215 mc

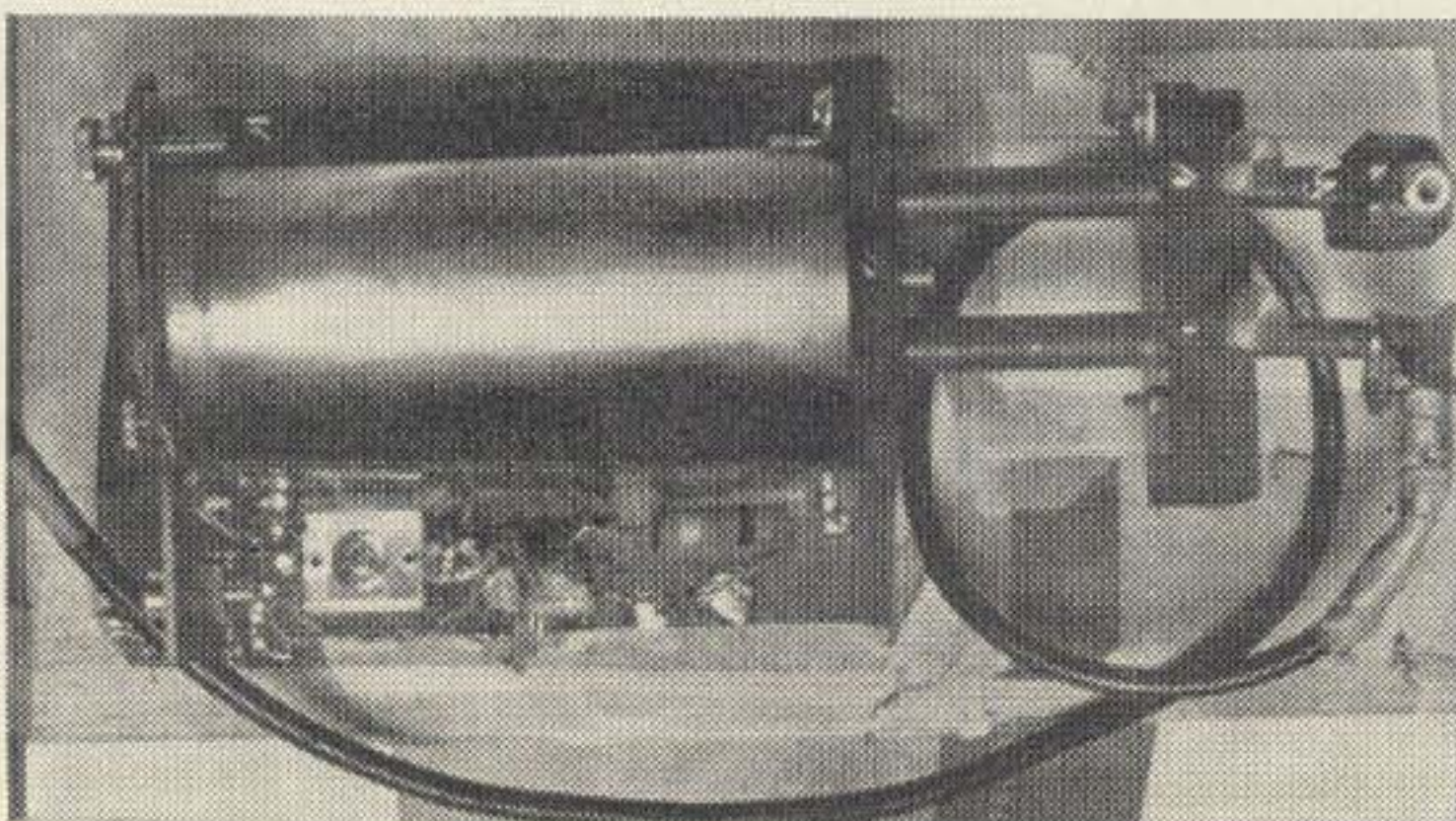By good I mean ones that really tune, putting 1215 into the crystal, the desired *if* out, and nothing else! This is a long story, so settle down. If you do you will learn how to make



Typical cavity.

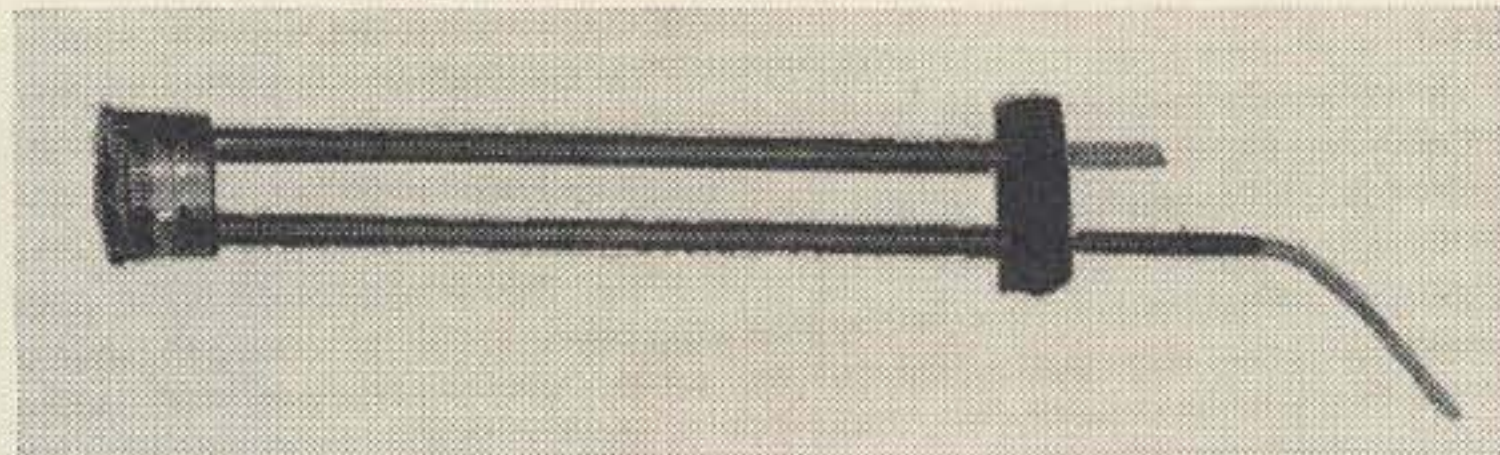


Push rod for inside of cavity.

a good tuneable cavity for 90 cents. I have made several of them and have been using them ever since. They are also easy to take apart and service or modify. You can put tubes, transistors, or diodes in the business end of them.


These cavities also have considerable "growth potential" as they say on Madison Avenue. If you make the *if* output coils plug-in, you can also use the cavity as a basic element for a narrow-band converter later. Plug in a 14 mc (or other, to suit your communications receiver) *if* coil, (see again Fig. 9.) remove the tuneable local oscillator cable, Fig. 7, and plug in a fixed tuned local oscillator chain. That is, later on, when you either make one or get one. This tends to sort itself out automatically. The customers generally fall into two groups. They have quite a lot of time and not too much cash, (usually a youthful group), or they will have more dollars and not near so much time available. And what time they do have they want to spend operating. This more or less describes the "family man." The main body of this article is obviously slanted towards the first group. On the air I have noticed that the amateurs interested in 1200 mc are almost always quite young. Of course there are always a hard core of born experimenters who carry on with this sort of thing till they die, but they are not so numerous.

Cavity

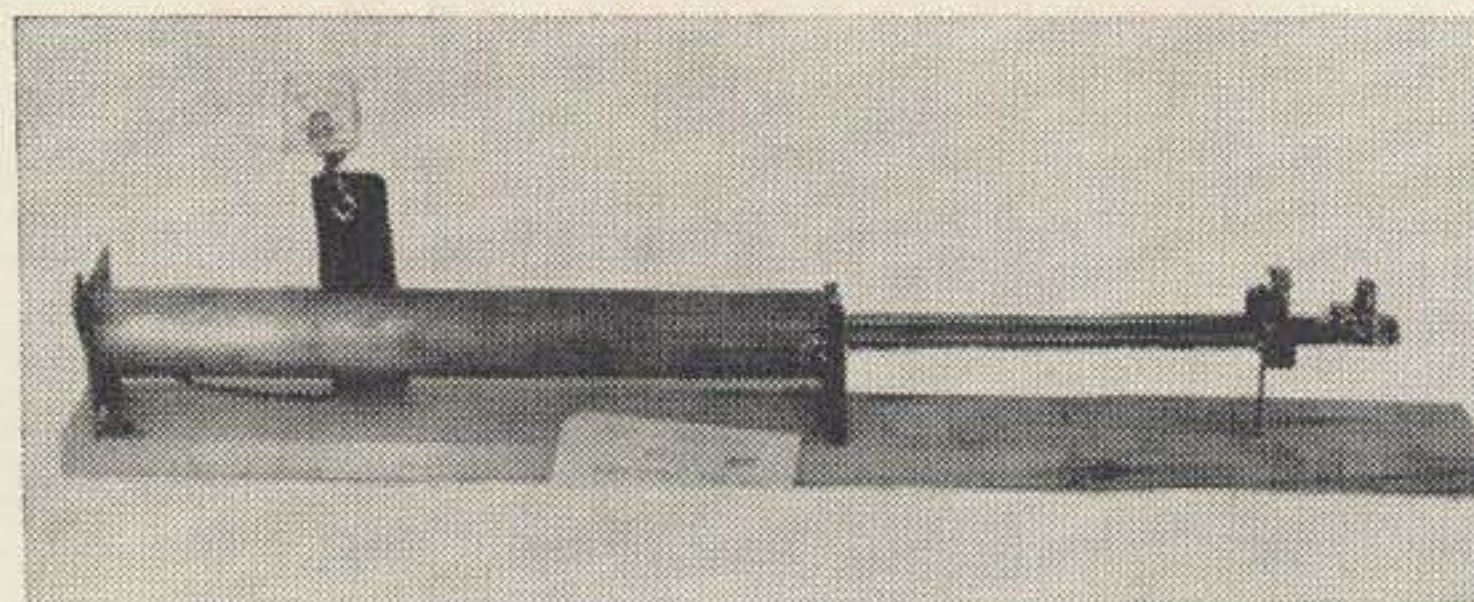While, as I said, some kinds of coil or line circuits can be made to work on 432 mc, and oscillators to 1200, to achieve good repeatable tuning on 1300 takes a little work and understanding. I have tried a large variety of circuits and methods and some of them work after a fashion. That is, a poor fashion. Lines get to be $\frac{3}{4}$ of an inch and do not like to be



Another cavity.

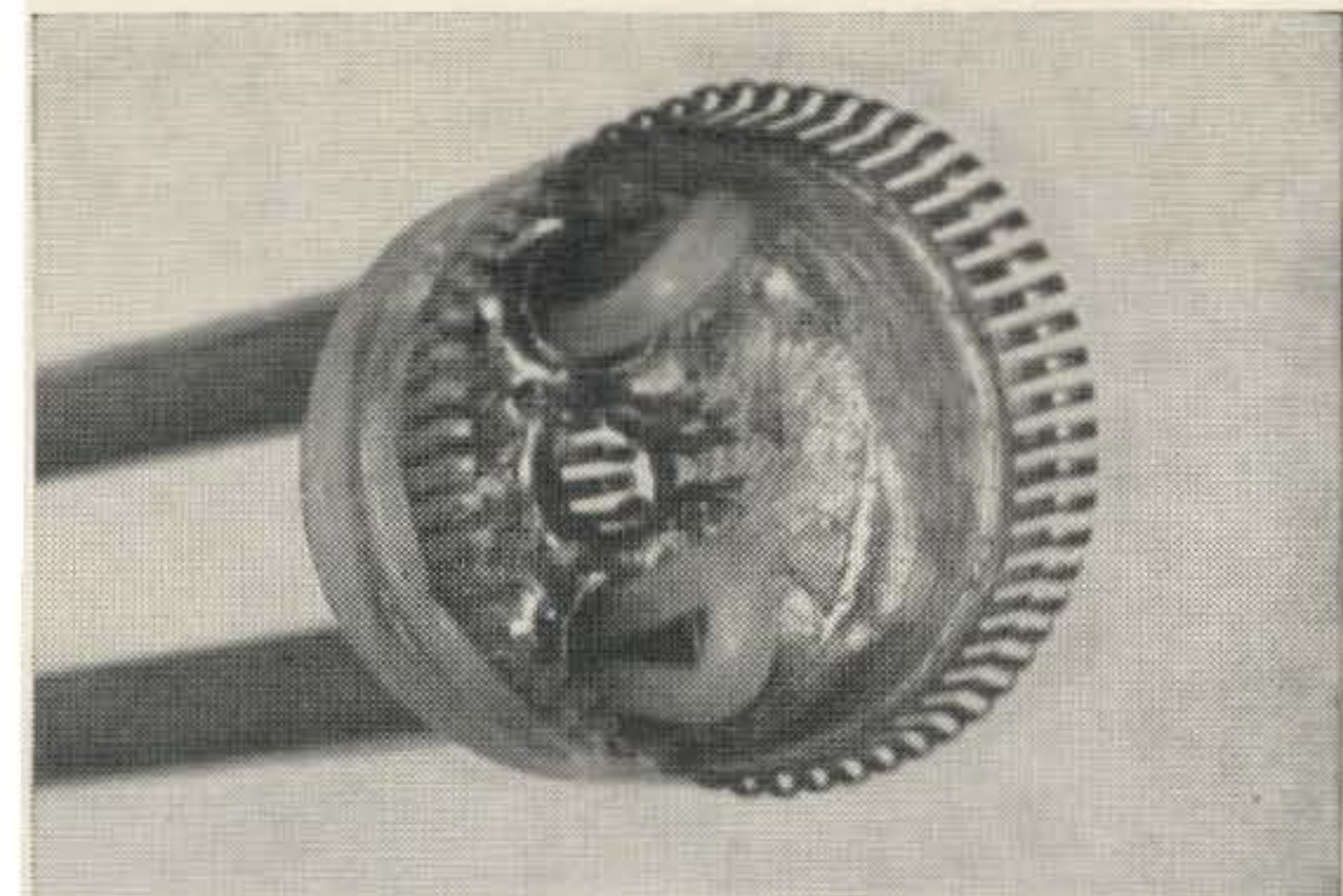

End of push rod.

enclosed. Condenser tuned coax cavities are also about $\frac{1}{4}$ of an inch long. I have made some of them work but they are still nothing like the plunger tuned coax tuner I will describe here. The difference is immediately noticeable. Fig. 7 shows a pictorial diagram. Now don't be scared by it. While this looks similar to previous pictures you have seen, there is no lathe or machine shop work in this one. You understand, I have nothing against lathes personally, it's just that I have never learned to run one, and having obtained my first license in 1923 (2BAV) I'm not likely to learn now.

The following items should be procured at the plumber's shop: thin wall brass tubing of $1\frac{1}{2}$ " and $1\frac{3}{8}$ " O.D. copper tubing, $\frac{3}{8}$ " and $\frac{1}{4}$ " O.D.; clean .022 brass plate. Now, cut a half inch length of the $1\frac{3}{8}$ " O.D. tubing, and solder on the finger stock. A small piece of steel wire, or enamel wire will help hold the finger stock in place while soldering. Or use a small finger-vise or clamp. Now solder the finger ring to a piece of copper clad bakelite, which has first had three holes drilled in it, Fig. 8A. The result should be as in Fig. 8B.

Now strip the outer conductor from two lengths of Teflon insulated RG58/U and slide them into the quarter-inch copper pipe, making small loops sticking out of one end of each pipe, as in Fig. 8C. These "coupling pipes" are then inserted inside the push-rods, see Fig. 8D, and positioned temporarily by the $\frac{6}{32}$ knurled thumbscrews shown in Fig. 7. The loops, Fig. 8E, should turn freely at least 90 degrees inside the cupped (inside) end of the shorting plunger, one on each side of the center conductor (see Fig. 8E) allowing the coupling of the antenna and local oscillator to be varied independently as needed. Some lengthwise variation in the positioning of these loops may be tried, but better keep them well inside the finger ring, as per Fig. 8E.

NEW callbook

HOT OFF
THE
PRESS!



Over 60% of listings
changed in only a year!

PLUS THESE EXTRA FEATURES:

- Great Circle Bearings
- Great Circle Charts
- Prefixes by Countries
- "Q" and "Z" Signals
- World Time Chart
- Int'l. Postal Rates

United States Listings... \$5.00
DX Listings..... 3.00

RADIO AMATEURS REFERENCE LIBRARY OF MAPS ORDER YOUR SET TODAY!



WORLD PREFIX MAP—Full color, 42" x 29", shows prefixes on each country... DX zones, time zones, cities, cross referenced tables.....postpaid \$1.00

POLAR PROJECTION MAP—Azimuthal equidistant projection. Shows prefixes on each country, DX zones, cities, prefix index by countries, 29" x 25".....postpaid \$1.00

UNITED STATES MAP—All 50 States with call areas, prefixes, DX and time zones, FCC frequency allocation chart. Plus interesting information on all 50 States. 29" x 17".....postpaid 50c

WORLD ATLAS—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country... full color, 16 pages.....postpaid \$1.00

Complete reference library of maps—set of 4 as listed above.....postpaid \$2.50

WRITE FOR
FREE
BROCHURE!

RADIO AMATEUR

callbook INC.

Dept. B, 4844 W. Fullerton Ave.

Chicago, Ill. 60639



See your favorite dealer or order direct (add 25¢ for mailing)

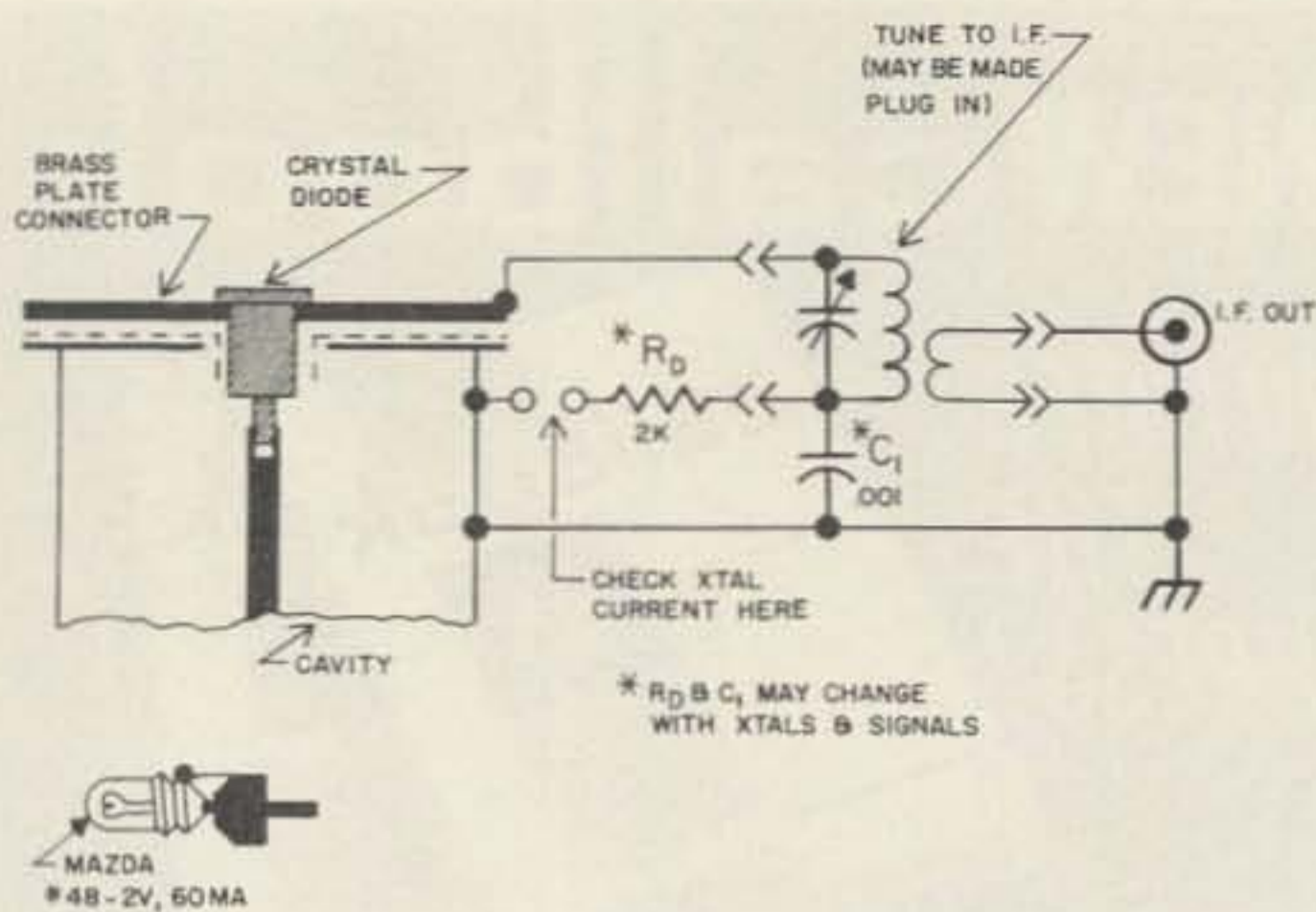


Fig. 9. *if* output.

Fig. 9B. Dummy load.

The other ends of the cables may be brought to jacks as in Fig. 7, or may be left longer and fastened directly elsewhere as needed. The brass end plates, Fig. 7, should be soldered to the outer wall. Sticky Teflon tape, perhaps two sheets of .002, is applied to the end plate from the "output capacitor and connector". See again Fig. 7. This little brass plate (see also Fig. 9.) is quite important. It bypasses the rf (1200 mc) but leaves the DC, in the case of use of the cavity as a wavemeter, or the *if* in the case of a mixer. Fig. 9 shows a simple *if* circuit that has never failed me yet. You can make the brass plate larger for more bypass action, or smaller for use with a higher *if* frequency, such as for a TV channel when using this cavity as an ATV converter. Notice that the brass plate and the outer shell, or "ground" form a fixed capacitor across the *if* output transformer primary, and so will be in parallel across the *if* tuning capacitor. If a slug-tuned *if* is used then it may constitute the fixed tuning of such a circuit.

So far, this type of cavity, with the crystal diode directly across the "hot" end, puts out more DC as a wavemeter, and more *if* as a mixer, than anything else I have encountered yet on 432 and 1296. It is also an excellent filter for the frequency to which it is tuned, as it is very positive in tuning. For example, 1296 stays at one spot on the dial with different antennas and different local oscillators. This is due to an extremely important principle in VHF and UHF work. A large cavity, such as this one, has a terrific "short circuit capability" for any frequency except that to which it is tuned. This shows up like mad in front-end work, where a small-wire coil will pass all kinds of images, harmonics and other junk. The large properly made cavity will not! You can also put your hands all over the out-

side with a signal on the inside and no change in tuning or output will be found.


This about finishes the "1215 Receiver" article except for station operation. As described it tunes nicely with test transmitters and the heavy radar signals which are heard almost anywhere in New England.

Low Power 1215 mc Transmitter

So far I have used the same type of oscillator for transmitting as the one described for use as the local oscillator. About the only difference is that for the local oscillator use about 30 to 35 ma plate current, whereas the xmtr can run 40 ma. (If you have half a dozen 6AF4's on hand, live it up! I still wouldn't go over 50 ma. Anyway, you're on your own there.)

The B+ for the transmitter also goes through a small 5 watt modulation transformer. A single 6AQ5 more than modulates the 6AF4 with a carbon mike and high gain mike transformer (30 ohm to 500K). Be sure to use a gain control on the grid.

It is also handy to make the output coupling loop (Fig. 4) variable, because when the beam is tuned up properly, it can easily overload the oscillator and block it off. When in that condition, putting your hand on the radiator or reflector will detune the beam plenty and bring the oscillator back into action again. This of course shows that the beam is tuned up. Or at least part of it! I mounted a piece of quarter inch bakelite rod through a thick piece of upright bakelite with a locking thumb-screw. With a one foot piece of RG58/U cable soldered to the output loop, which is quite small, about 7/8" long by about 3/16" wide, a no. 48 Mazda bulb lights easily on 35 ma plate current and shows about 200 to 300 milliwatts of 1215 mc rf when using 45 ma on the 6AF4. I mount these 60 ma 2 volt bulbs on a phono plug with coax leads. See Fig. 9B. They are handy rf power output indicators. Don't leave them in circuit though, or you won't have any power left for the antenna. Best for the moment to set the output coupling loop for maximum reading on the distant (10 to 15 feet) detector and beam, and note the grid and plate current.

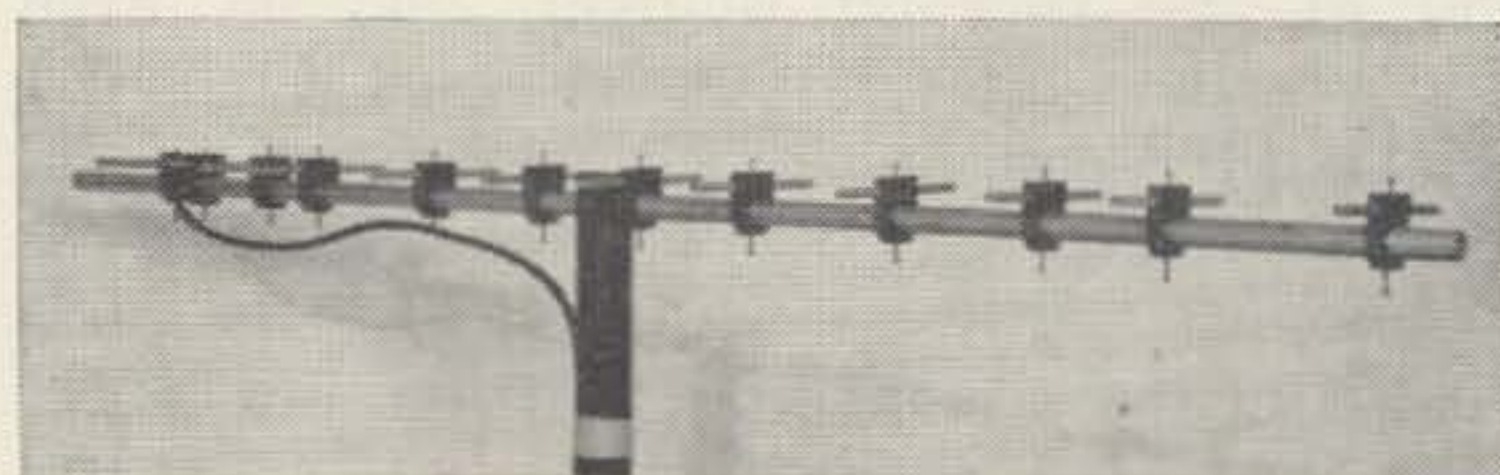

1215 mc yagi

ELEMENT LENGTH CM. (ALL 3/16" AL. TUBING)


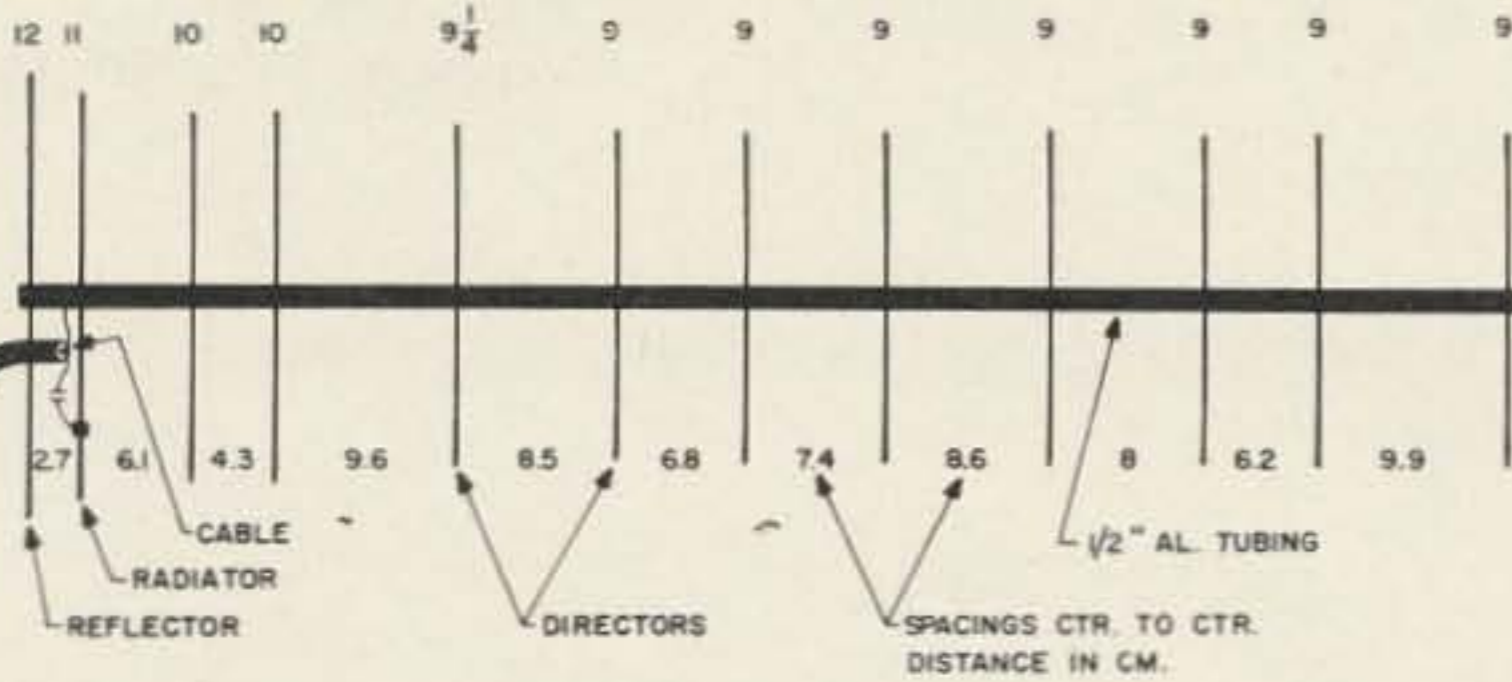


Fig. 10. 1215 mc yagi dimensions.

1215 mc Beams

Two of these will start you off on 1215. With the transmitter on one beam and the mixer cavity used as a power detector on the other beam, by connecting a 0 to 100 microampere meter in the place of the *if* coil (or in series with it) the meter shows full scale with the beams pointing at each other 10 to 15 feet across the room.

Figs. 10 through 14 show details. Again,

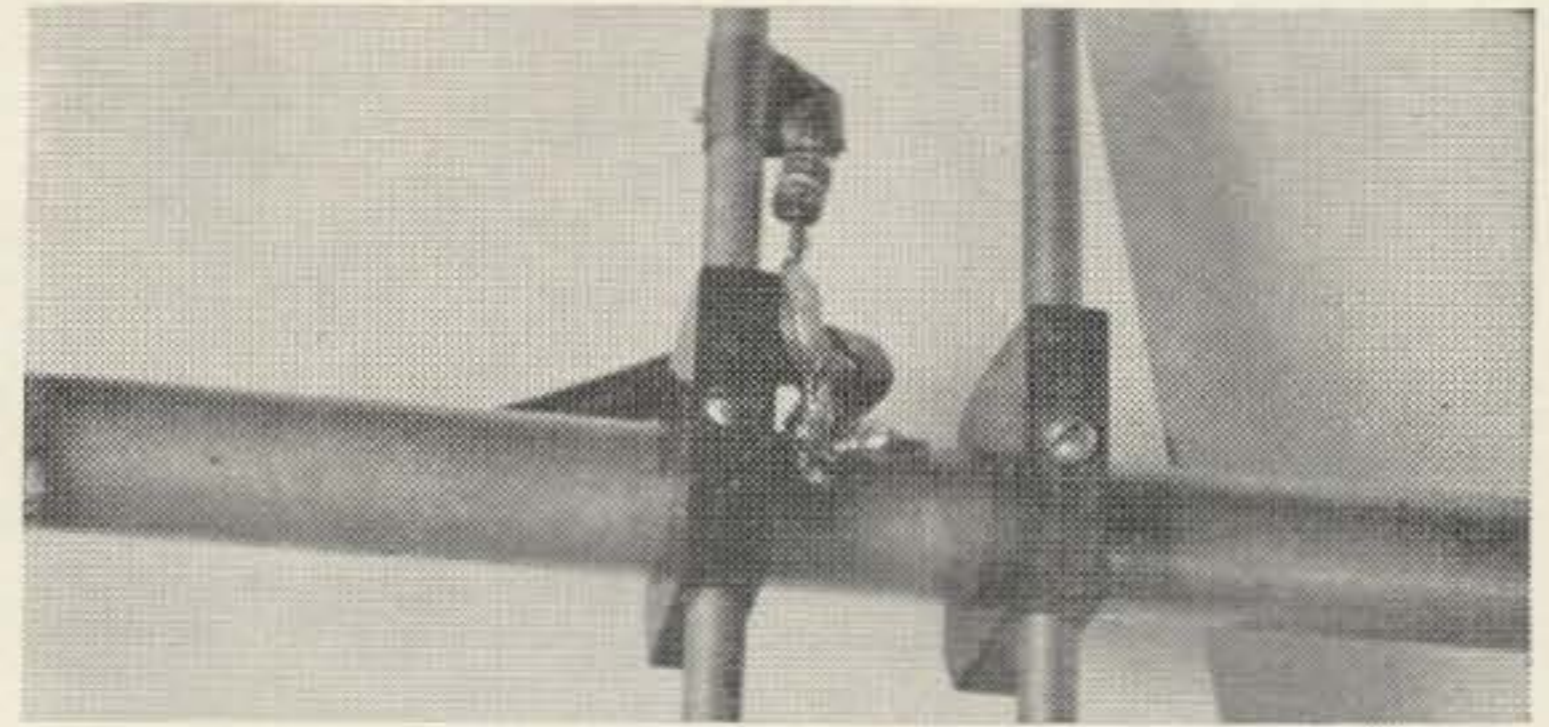

Gamma match.

make Chinese copies and they will work. They are very handy for getting started. Then you can go creative and try anything you wish using these little ones as standards, test antennas, etc.

There is only one adjustment you should make on these beams. Plug in the transmitter (I used about 10 feet of RG58/U to start (probably makes about a 3 db pad, at least)) and, watching the distant (ten feet) receiver (use a DC cable to bring the meter back near you so you can read it) meter tune the gamma match capacitor with a screwdriver made of fiber, with no metal tip. You can also try a few different spacings, for the reflector only, adjusting the gamma capacitor each time, or leaving a sub miniature fixed 4.7 mmf capacitor there. See Fig. 2. Do not change any of the director spacings. Once again, these little firecrackers are just to start with. All kinds of things can be done later. Skeleton parabolas, four corner reflectors vertically stacked, sky's the limit. At least you now have a low cost, test oscillator-signal generator, two good beams, a low cost receiver, a small antenna range, and you can work across town!

K1QNM took one unit to his shack about half a mile away in Melrose, Mass., through trees, houses, etc., and came in very loud using his beam indoors. My beam was just outside the roof about one foot average above a skylight on the third floor.

Of course, a good deal is to have some local lad near you make up a second complete rig along with yours. How far will these go on mountain tops? You think I should already know? Listen, good friend and reader, fellow 1215'ers are scarce enough! In the cold weather I do circuit work!

I use one beam on the receiver and another on the transmitter, without rf switching, so far. I intend to run a series of 1215 mc tests on cables, connectors, switches, and relays, soon, however, and hope to let you know the results, via 73 grapevine.

. . . K1CLL

1215 mc Beams

Two of these will start you off on 1215. With the transmitter on one beam and the mixer cavity used as a power detector on the other beam, by connecting a 0 to 100 microampere meter in the place of the *if* coil (or in series with it) the meter shows full scale with the beams pointing at each other 10 to 15 feet across the room.

Figs. 10 through 14 show details. Again,

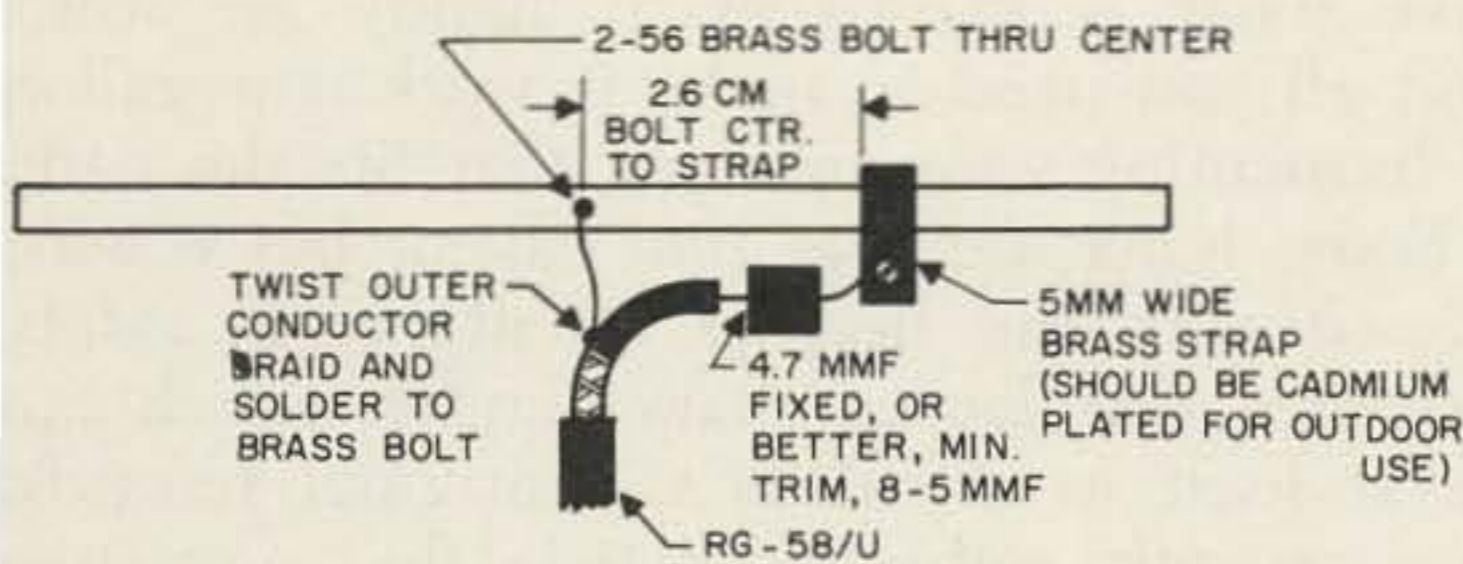


Fig. 11. Driven element of yagi.

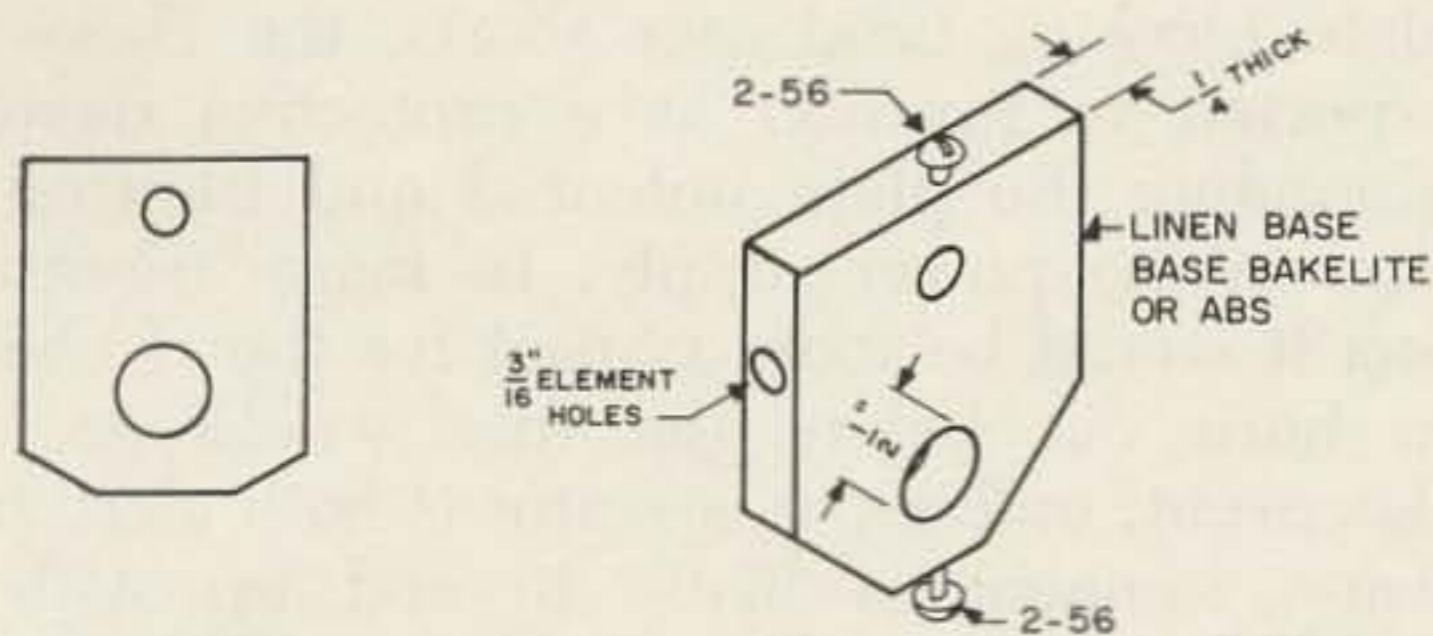


Fig. 12 and 13. Details of yokes.

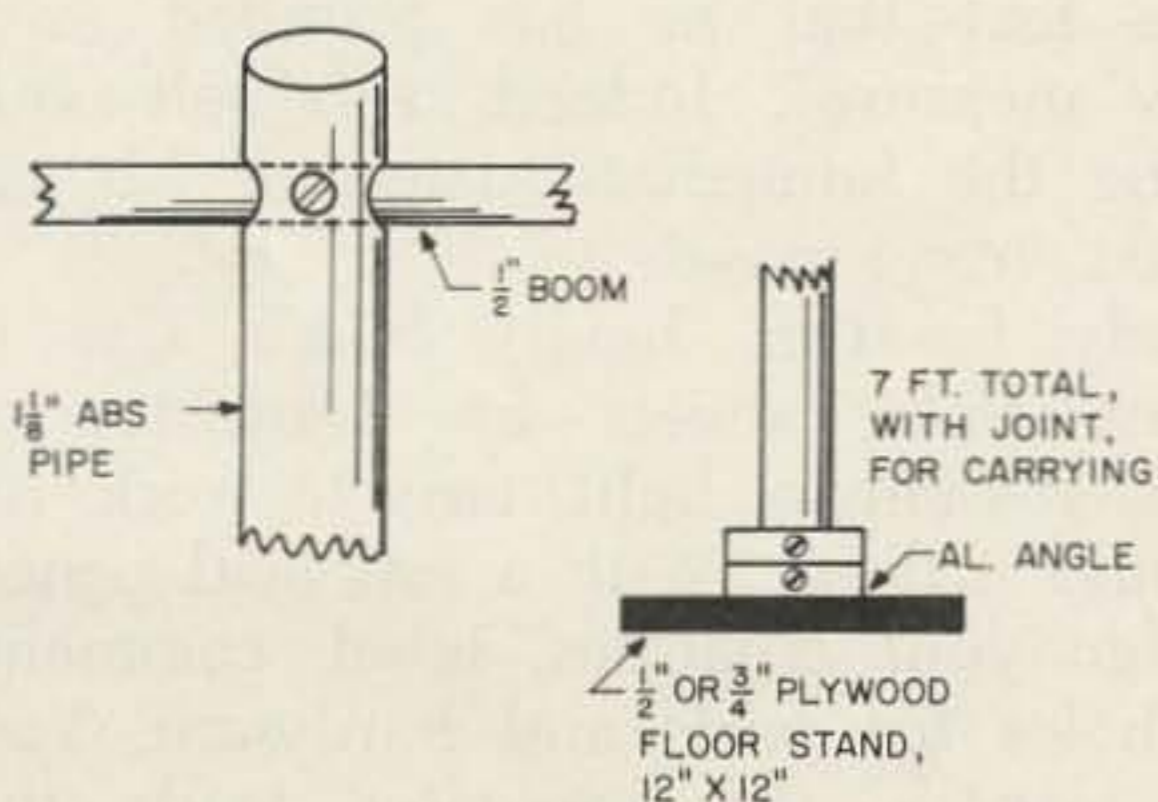



Fig. 14. Antenna mast and support.

Total Boredom

How many times have I read a "handy hint" in a magazine and thought: "Of course! Why didn't I think of that?" And later, when the ingenious suggestion turned out to be less practical than imaginative: "Naturally! Why didn't I think of that?"

Most often I do this mental two-step to my own tunes. The mechanical facts of life kill off a majority of my inspirations with swift mercy, often leaving a legacy of odds and ends best referred to frankly as trash. Like all these nice aluminum cans that came filled with Red Kettle soup mix—a good product but one I didn't need. In the supermarket these "handy parts containers" stacked perfectly. But not after they had been opened.

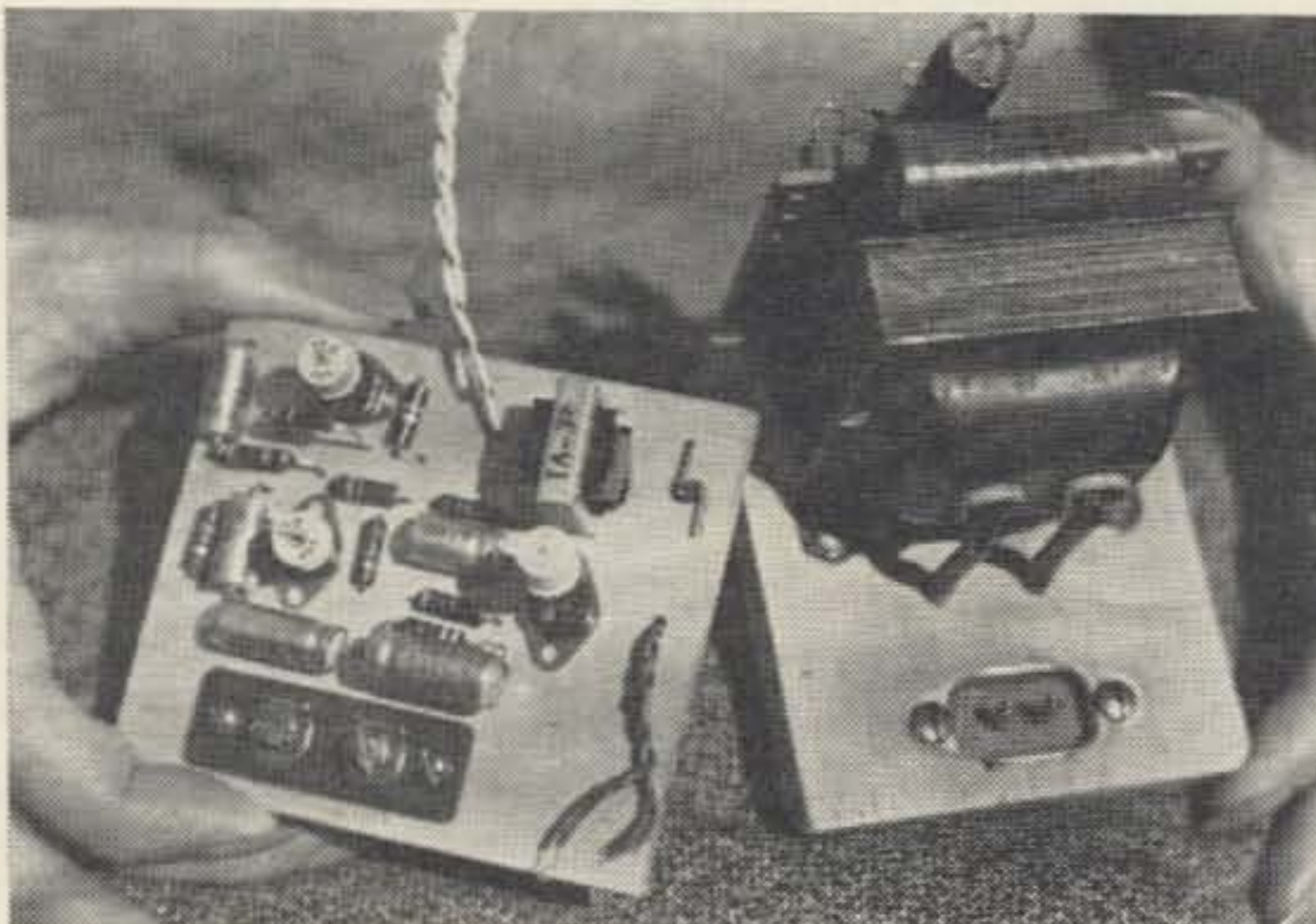On the other hand, some ideas work just fine, but who needs them? And how often? Clip the point from an exhausted ball-point filler and force the empty plastic tube through a hole in a cork. Slip a few inches of spaghetti (our kind) over the other end of the tube.



Chassis. See text.

Put the free end of the spaghetti into a plastic pill bottle filled with water. The bottle cap should have two holes drilled in it—one a tight fit for the spaghetti. Now you have what is known as a "handy air seal." And all you need to make it work is a gallon of fermenting wine in a jug that fits the cork.

Some hints are real time-savers but others, offered with the best of intentions as safety measures, develop corollary dangers which can be at least as lethal as the original hazards. In a recently published article the suggestion was made that a 2.5 mh rf choke in the range of 200 to 300 ma be connected from a transmitter output to ground. In the event the plate blocking condenser shorts, the choke is expected to function as a protective device, grounding the plate potential and blowing a fuse in the power supply. In many transmitters it would be more typical for the rf choke to burn out before the fuse would go. In this event, unless the operator is both alert and wary, someone is likely to end up with a handful of volts. The shock would be psychological as well as physiological for his attitude will have been conditioned by confidence in the fact that he has installed an extra "safety measure". Indeed, this self-assurance may be the immediate cause of his making that last wrong move.

Ready for the "handy hint"? Use model airplane balsa sheets for transistor circuit boards. It's cheap, light, easy to work, ubiquitous, and it floats. With a soft lead pencil you can sign your creations, label, comment and start holes for parts and hardware. You can work resistor and capacitor leads through thicknesses up to a quarter inch with no diffi-

telrex

"BEAMED-POWER" ANTENNAS and ANTENNA SYSTEMS

The Choice of the Discriminating
Communication Engineer . . . the
Man who Never Settles for Any-
thing Less than THE-VERY-BEST!

You too—can enjoy world renowned TELREX performance and value! Send for PL65 condensed data and pricing catalog, describing the lowest priced antennas on the market, in relation to materials and performance! Expanded data sheets—including your favorite band, are also available.

ANTENNAS
SINCE
1921

COMMUNICATION SYSTEMS
telrex LABORATORIES

ASBURY PARK 25, NEW JERSEY, U.S.A.

with a *line*

**MATERIAL DIFFERENCE
—IN USE IN 135 LANDS!**

culty, although it's something like giving a penicillin shot the first time.

I prefer quarter inch because it's strong enough to permit bolting small transformers, chokes and terminal strips. The transformer in the photo is a ten volt doorbell unit used here in a nine volt transistor-experimenting power supply. The completed board was aligned with an identical piece which had been coated with airplane cement, and then it was carefully stepped on. This forced the wiring and other odds and ends into the surface of the lower board, permanently hid the amateur workmanship (no pun) and saved the cost of rubber feet. There are very few surfaces a sheet of balsa will mar.

Splinters and grain are no problem with this wood, and your wife will agree the color of balsa blends nicely with the modern decor she reads about. The light hue provides an effective background for the components in the event photographs are requested by your attorney, 73 or Western Electric, and you will find it gives a certain lift to your circuits. Speaking of lift—when you give up on one of those maddening projects that just will not work, you can hit back by pinning wings to the circuit board and giving it a savage overhand launch into the blue. The natives will wonder for weeks what to make of a glider with an aborted multivibrator piggyback. Lately, to spare a lame right arm, I've been taking my rejects into the tub with me, where they make very avant-garde rafts for my plastic ducks.

NEW FROM TRANSCOM!

SBT-3

Transistor
SSB Transceiver
\$299.50



A completely new SSB transceiver styled and designed for mobile operation. The smallest, most compact transceiver and the biggest dollar-value in the field.

Smallest size: 4 $\frac{3}{8}$ x 11 $\frac{3}{8}$ x 8 $\frac{3}{4}$. Low battery drain: 500 ma in receive. Big voice: 165 watts PEP to 2-8042 instant heating tubes. Solid state switching, solid state circuits. Simple operation. Full phone coverage of 80, 40 and 20 m. Stable: Less than 100 cps drift in any 15 min period. Sensitive receiver: .5 uv for 10 db s/n.

SBD-3 mobile power supply: \$99.50
SBM-3 mobile mounting kit: \$3.50

Bank terms available


Western Radio

1415 India Street

San Diego 1, California

BEI mont 9-0361

2 METER (almost) NON-DIRECTIONAL ANTENNA

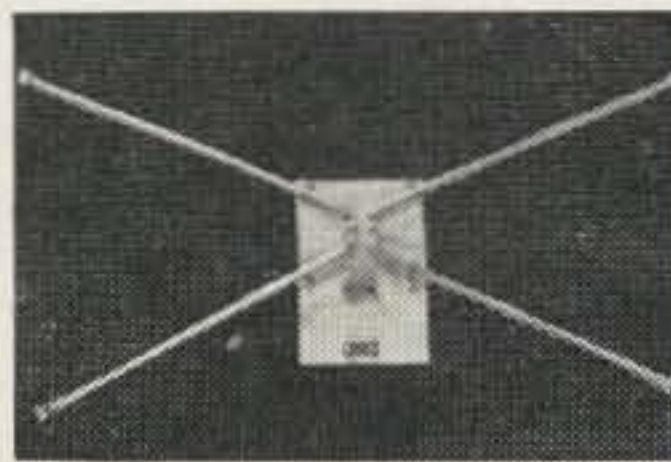

2M Con-ex

A rugged antenna for 2 meters that will give more gain and better coverage than a dipole. The Con-ex will withstand gales in excess of 100 mph. Perfect for local nets. An antenna every VHF ham can afford and should have for local contacts. Mounts for either vertical or horizontal polarizations.

\$8.95ppd in continental USA

ELL-CONN PRODUCTS

Box 83, Ellington, Conn. 06029

Oscar III:

Some observations

"It is up" . . . three words that opened the door to another era of Amateur Radio communications. These are the words that flashed around the world March 9th when OSCAR III completed its first orbit at 1930 GMT.

OSCAR III was launched from Vandenberg Air Force Base and a short time later was reported in a Polar orbit about 500 miles high and circling the Earth once every 103 minutes at a 70 degree inclination.

From my own observations, and those that have been reported to me, the satellite functioned as planned with the exception of the 145.950 megacycle beacon, I did not hear it and I know of no one who did.

However, the well-known, friendly "HI" signal and telemetry beacon on 145.850, plus or minus depending on Doppler shift, was loud and clear.

The transmitting pass-band from 145.875 to 145.925 also functioned well although a few kilocycles lower than planned.

I began tracking on the sixth orbit but did not hear any amateur signals until orbit number 8, although the "HI" beacon was very strong, about 25 db over receiver noise.


The first amateur signal I could identify because of the QRM and QSB was that of K9AAJ . . . the same gentleman, who along with K2IEJ, made the first confirmed two-way QSO via OSCAR on orbit number 13.

Another contact that may be of interest, although the two stations are only some 360 miles apart, was on orbit number 76. K9AAJ worked KØCER when the satellite was off the southeastern tip of Greenland. THAT is a long way around to work a station 360 miles away!

The maximum distance that I was able to hear the "HI" signal was somewhat over 3,000 miles with 2,500 miles being consistent.

Being located in the midwest puts me in a rather favorable position to hear stations throughout most of the United States. Over 20 states were logged with K9AAJ, K4IXC, K5TQP, K2IEJ, K3KEO, K9UIF, WA6MGZ, and K5WXZ having the most consistent signals.

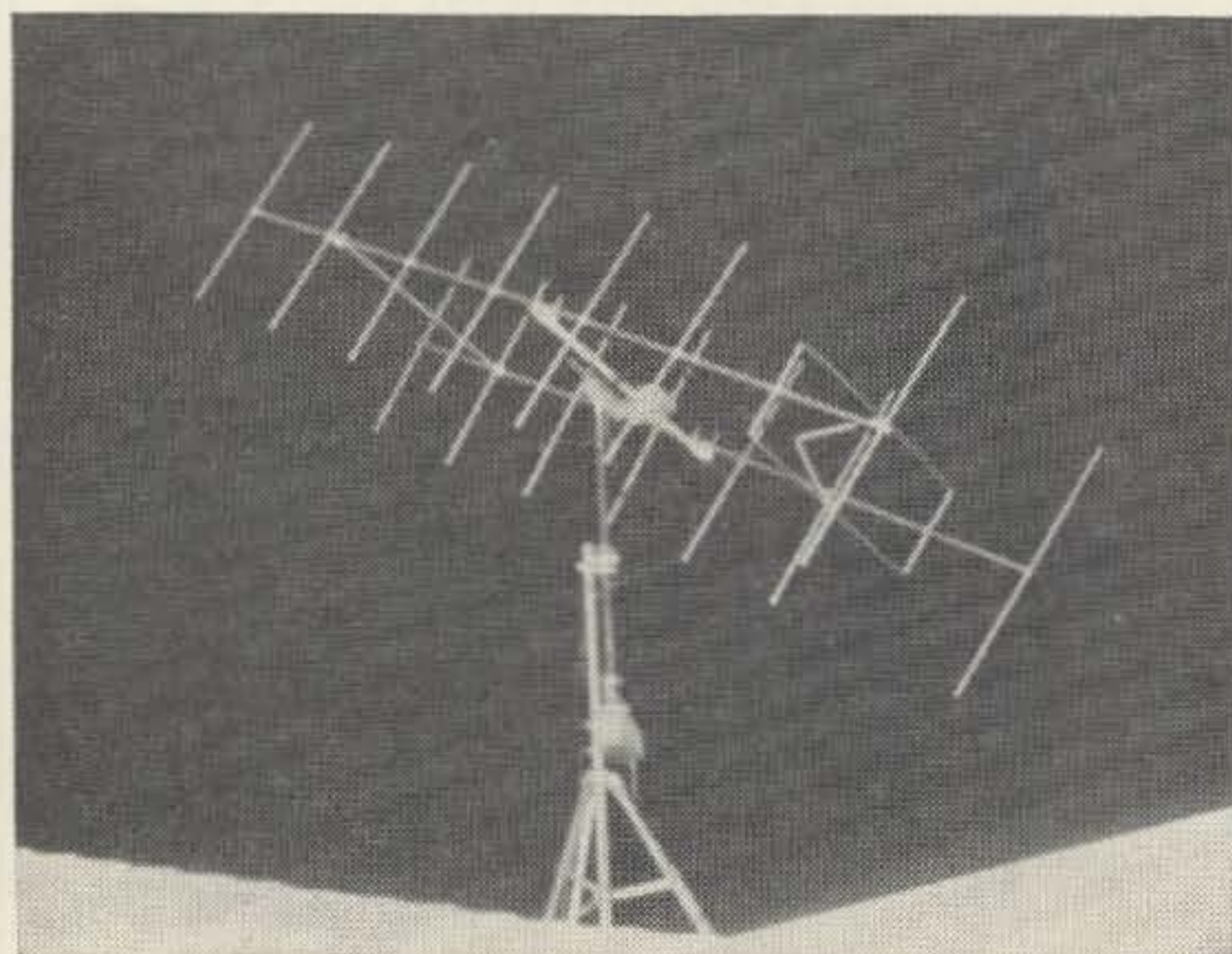Now for some observations. These should prove of interest for comparison and I welcome any comments for a later article where some comparisons can be drawn.



KØCER's Oscar III antenna.

1. There appeared to be no difference in signals between north and southbound passes.
2. The "HI" beacon could be acquired usually about 8 minutes before TCA but the largest number of amateur signals were heard immediately after TCA until the abrupt cut-off as the satellite passed out of range, about 2,500 miles.
3. There was a very marked signal increase just before the satellite dropped over the horizon.
4. Horizontal and vertical polarization worked about equally well except during passes that were nearly, or directly, overhead. Vertical polarization and being able to point the antenna at the satellite showed a marked improvement over horizontal polarization.
5. QSB . . . we all cursed this. The QSB was probably THE limiting factor in preventing more QSO's. A signal would be solid copy for about 10 to 30 seconds and then disappear. This was no doubt due to the pitching of the satellite in space and made meteor scatter techniques for information exchange a must. The QSB and the Doppler shift caused many QSO's to be lost. I probably lost seven due to this and I heard any number of fellows miss out the same way.
6. Slow speed CW (I heard only one AM and four SSB stations) would have been the best way to cope with the rapid signal strength variation, but the short duration of the signals forced keying speeds in general of 20 wpm or more. This hampered the "phone-only" operators.
7. The "HI" beacon could be copied on the simplest of receivers but it took a good, low-noise converter/receiver to pick out the ham signals. The ham signals appeared to be only about one-half as strong as the "HI" beacon. The beacon could be copied continually but not ham signals.
8. Buck-fever. I guess we all suffered from this. During the first 75 or so passes everyone was calling CQ. Later the trend seemed to reverse and everyone was listening. Somewhere along the line we are going to have to adjust ourselves to this kind of communication.
9. I know of no station using the OSCAR Association suggested transmitter power of 100 watts. I used 400 watts. This might have had something to do with all the over-all amateur signal strength being less than the "HI" beacon if the translator power was being "used-up" by the high-power boys. Maybe it takes higher power to work through the satellite than was anticipated.

In summary, it would appear the amateur who was an experienced operator and fairly well equipped had the most success. We all learned the fine techniques of satellite tracking, developed our own ideas of what was the best antenna and which polarization to use, and operating procedure. This experience will be most helpful in future OSCAR's and we should see more contacts being logged.

I am most interested in receiving reports from all participating operators and will put the information together for a future article where we can all gain from each others experiences and observations.

And finally, a salute and a thank-you for all the efforts of the Project OSCAR gang, a job well-done, fellows.

. . . KØCER

AMATEUR TELEVISION is the EXCITING NEW FRONTIER GO ON THE AIR NOW WITH A VANGUARD TV CAMERA



\$149.95

Model 400 for TV channels 2-6 (closed circuit) } Only \$149.95
Model 440 for ATV 436-450 mcs. } less vidicon and lens.

25 mm. F1.9 normal angle lens in focusing "C" mount \$18.95

Other lens available from \$15 to \$250 for our fantastic F1.4 ZOOM lens.

Complete description in our catalog for 10c.

Vidicon tubes:	7038	7735A
Grade A	\$85.00	\$100.00
Grade B+	\$75.00	\$ 90.00
Grade B	\$60.00	\$ 75.00

Grade C Our choice of any type 1" vidicon, new or used—guaranteed to give satisfactory service for amateur use. \$35.00

The VANGUARD Models 400 and 440 are factory assembled with the same precision as our industrial cameras now in continuous duty throughout the U.S. Complete with self-contained synchronizing generators, 4 mc. video amplifiers, power supply, tripod base plate and low power TV transmitter which can easily be increased with simple linear amplifiers. Illumination can be as low as 1 foot-candle when using our vidicon and lens. Picture sharpness is guaranteed to be equal to the best capabilities of any standard 525 line TV receiver. Modular construction and printed circuits permit quick replacement and servicing of major circuits. Weighs 11 lbs.—measures approx. 8" x 6" x 6".

Crystal controlled horizontal scan available on either model for only \$20.00 more. Add the suffix X to model number.

Building your own TV camera? Our complete line of tested circuit modules and deflection yokes will save you much time and money. Fully described in our catalog for 10c coin or stamps.



\$10.95 up

VANGUARD TRANSISTORIZED CONVERTERS

New series 300 with 3 VHF-UHF transistors, crystal-controlled oscillator, tuned R.F. stage and low noise mixer. One microvolt sensitivity. More than 30 high quality parts carefully assembled and tested. Measure only 3" x 2½" x 2". Operate at 12 volts DC 4-5 ma.

Nuvistor converters available from \$10. Circuit modules and government surplus equipment also available. Send 10c coin or stamps for complete catalog. For prompt shipment please include postal money order

Available in the following modules:

	Model	Input mc.	Output mc.	Price
2M	{ 300-D	144-148	50-54	\$12.95 ppd.
	{ 300-E	144-145	.6-1.6	\$12.95 ppd.
	{ 300-F	144-146	28-30	\$12.95 ppd.
	{ 300-Q	144-148	14-18	\$12.95 ppd.
6M	{ 300-B	50-51	.6-1.6	\$10.95 ppd.
	{ 300-C	50-54	14-18	\$10.95 ppd.
	{ 300-J	50-52	28-30	\$10.95 ppd.
20M	300-G	14.0-14.35	1.0-1.35	\$10.95 ppd.
CB	300-A	26.965-27.255	1.0-1.29	\$10.95 ppd.
WWV	300-H	5.0	1.0	\$11.95 ppd.
Int'l.	300-I	9.0-10.0	.6-1.6	\$11.95 ppd.
CHU	300-K	7.3	1.0	\$11.95 ppd.
CHU	300-L	3.35	1.0	\$11.95 ppd.
Marine	300-M	2-3	.6-1.6	\$11.95 ppd.
Aircraft	{ 300-N4	121-122	.6-1.6	\$13.95 ppd.
	{ 300-N5	122-123	.6-1.6	\$13.95 ppd.
Fire, Police etc.	300-P	155-156	.6-1.6	\$13.95 ppd.
CUSTOM MADE	300-X	Choice of 1 input freq. and 1 output freq. between .6 mc. and 160 mc.		\$14.95 ppd.

All above converters are supplied with Motorola type connectors. For two SO-239 connectors instead, add 75c. N.Y.C. residents add 4% sales tax.

or cashier's check. COD's must include 20% deposit. N.Y.C. residents add 4% sales tax. Include sufficient postage for all items except converters and circuit modules which are postpaid.

VANGUARD LABS

Dept. H-5
190-48 99th Avenue
Hollis, N. Y. 11423

Letter from Gus

Calcutta, India
March 8, 1965

At this moment I am setting in a small hotel room here in good old Calcutta, India. I keep thinking about Peggy leaving me all to my lonesome on the 11th when she will leave here for home, ICE COLD COKES, hamburgers, Southern Fried Chicken and rice, and seeing those FB Grandchildren! Boy I kind of wish I were going home along with her, but I have promised her I will be home by Christmas—and I HAPPEN to mean it THIS TIME.

You boys want to see a real Ham license—well here is an exact copy of my Bhutan License:—

RADIO AMATEUR STATION LICENSE

Gus M. Browning of Route 1, Box 161-A, Cordova, S. C., United States of America are hereby issued a license to operate an Amateur Radio Station in Bhutan.

He is permitted to use a call sign of his own choosing provided it begins with the letters AC.

It is understood that he will obey the rules and regulations that pertains to the operation of radio Amateur stations, thru out the World.

This license is good for the life of Mr. Browning, no renewal at any time is necessary, of course it may be cancelled by the Government of Bhutan at any time.

THIRD party traffic may be handled with any radio amateur station. Telephone patch may be used at anytime. Dated this 21st. Day of Jan. 1965.

Signed by the
Chief Signal Officer
for the Government of BHUTAN

Now boys ain't this a dandy Ham license? THAT is the kind of license I LIKE!!!

Peggy and I just arrived here from Bhutan, I plan to go back there on the 13th of March. So far I have operated from AC5 and AC8 (12500 Ft up) and when I go back I plan on going to AC9 after another shot at AC8 and if possible even AC0, when the snows melt and if things are RIGHT and nice and QUIET maybe even even AC4—but you won't hear that prefix ever given—it will just be AC8/ (with NOTHING after the / mark. Of course AC3 is very strong in the plans and this may be the hardest one of the lot to pull off this time. I will be trying and I mean trying VER YHARD, but this one will not be easy. BE ON YOUR TOES BOYS this one may come out of a clear sky without any warning at all. I hope it will be right after the 15th of April.

Conditions have really been stinko. They are the worst I have ever seen. The openings are short and usually weak. My GOOD EQUIPMENT at this moment is still in the INDIAN CUSTOMS here in Calcutta. I have been stuck on Transceive up to now with only 100 watts input. The new rig has 2 VFO's and 300 watts input and getting it thru INDIAN CUSTOMS will be really tricky this time. They want me to get a license from their Ministry of Transport and Communications JUST TO BE ABLE TO TAKE IT THRU THEIR INNER LINE (the Inner line being a strip of land just south of Bhutan, Sikkim and Nepal) I intend to stay here in INDIA until I have exhausted EVERY MEANS of getting this equipment to Bhutan with me. THESE INDIAN CUSTOMS are MEAN—they go by THE BOOK and the book has a lots of very fine print in them—and they are reading EVERY WORD of the fine print this time. I sure hope I get a chance to use this fine lab built gear that Hammarlund built up especially for me. Stick with me boys—I AM A TRYIN' and A SWEAT-IN' THIS ONE OUT.

CAN SOMEONE TELL ME PLEASE WHAT HAS HAPPENED TO THIS RECIPROCAL LICENSING STUFF? It ain't helped me a bit yet. How about you fellows writing your Senators and Congressmen and ASK THEM WHAT'S BEING DONE on that bill! The bands go out in AC5 at 1300 Z and at AC8 about 1400 Z. EXCEPT for Raju-VU2NRA who is still the loudest thing on the bands ALL THE TIME even when the

con't. on next page

VHF

LATE OSCAR FLASH

It would appear the Repeater is beginning to fail on about orbit 210. On orbits 213 and 214 the "Hi" Beacon was peaking 50 DB over noise but no evidence of any repeated signals although "pings" similar to meteor scatter signals were heard faintly. WØENC at Rapid City, South Dakota reports the battery voltage down to about 18 volts. The last amateur signal heard here was from K2GUG on orbit 201 peaking 25 DB over noise. WØENC reported hearing K9AAJ, WB6KAP and K2GUG on orbit 202 but nothing identifiable after that.

With this issue of 73 comes the initiation of a VHF column. Wayne and I hope you will enjoy and support it because only through YOUR support and interest will it thrive.

A short time ago Wayne asked for your comments on whether 73 should carry some columns on selected topics. Forty per cent of you said you wanted a VHF column in 73 so after the exchange of a number of letters between Wayne and myself he gave me the go-ahead.

It is our intention to aim this column at the technical and construction aspects of the field and it is along these lines we shall move. In doing this, I solicit and welcome ideas, your pet circuit, technical and construction projects, suggestions and criticisms. I realize that a great number of VHF/UHF operators just simply do not want to take time away from their projects to write a finished article. This is where I will come into the picture as your editor. I will take your notes and rough drawings, etc. and put them into finished form so each of us can benefit from the work of each other.

Now a short introduction is in order. I was first licensed in 1955 and after two years on the DC bands, moved to six meters operating from Iowa, Arizona (as K7RIA) and South Dakota. In August of last year I switched to two meters and that is where I operate most every night with 400 watts of CW. I am 25 years old, married, have a daughter and am employed as the news editor of a Sioux Falls radio and television station.

Enough of that, and on with the column.

During the past several weeks the eyes of the VHF world have been focused on a small package of transistors circling the globe once every 103 minutes.

OSCAR III is writing new pages into the history of amateur radio in the space age. What are some of these pages of history? Let's look at some "firsts."

K6GSJ heard the first repeated amateur signal from OSCAR, that of K6UQH on the very first orbit. On orbit six, W8PT heard W4WNH for the first "long-distance" repeated signal. The first confirmed two-way contact came on orbit 13 when K9AAJ and K2IEJ contacted with signals of a meteor scatter nature. The first reported two-way QSO outside of the U-S came on orbit 20 between HB9RG and DL6EZ. Leave it to W1BU to come up with another first. On orbit 19 he heard HB9RT for the first Trans-Atlantic reception of a repeated amateur signal. On orbit 51 KH6UK scored a Trans-Pacific first when he heard WA6MGZ. K9AAJ reported hearing KL7CUH on the ninth orbit. W6NLZ and K2GUG scored the first coast-to-coast QSO on orbit 35 but W1BU seems to have outdone them all. On orbit 61 Sam and DL3YBA spanned the Atlantic for a two-way contact. I also have a non-confirmed report that Sam worked HB9RT also. The above information is accurate with the possible exception of when W1BU heard HB9RT, the orbit number might be wrong because of a garble in KØSZJ's teletype copy. I am sure there have been other similar firsts but I have not received reports of them. How about it, you fellows that were involved? I might also comment that the first two-way contact, between K9AAJ and K2IEJ, was copied here from both stations.

Next month, most of the country should be defrosted enough to think about antennas, so we will cover matching harnesses and beam stacking. While you're thinking about that summer antenna project, look at these figures before you buy your new coax feedline.

FANTASTIC SBE CLOSEOUT



Sideband Engineers
SB-33 SF1 Series
4-Band Solid State
Transceivers.

Regularly \$389.50
New boxed

SPECIAL \$250

Also National

H CJ ELECTRONICS

NCX-5 \$585
NCL2000 \$585

E 6904 Sprague Ave., Spokane, Washington
HAM HEADQUARTERS OF THE NORTHWEST

RUSH ME MY:

SB-33 _____

NAME _____

NCX-5 _____

ADDRESS _____

NCL2000 _____

CITY _____ STATE _____

HERE'S MY CHECK FOR \$ _____

DB loss @	VHF				Price/ft.
	30mc	50mc	144mc	432mc	
RG 8 U	1.0	1.4	2.8	5.2	10c
RG 11 U	.9	1.3	2.5	4.7	9c
RG 17 U	.4	.5	1.1	2.3	66c
RG 58 U	2.0	2.7	5.5	10.5	3c

It is false economy to buy inexpensive coax for VHF applications. Even at 2 meters RG 58 U soaks up nearly 75% of the transmitted power before it reaches the antenna.

Also planned in the near future are articles from WØCTM on 432 megacycle transmitters, tropo dx by WØEMS and so forth.

Please do let me hear from YOU.

Bill Smith KØCER
1301 Churchill Ave.
Sioux Falls,
South Dakota 57103

Gus

bands are DEAD for anyone else. They must have the exact perfect skip for AC lands and VU2NRA lands ALL THE TIME. 40 meters—Ha Ha Ha, boy that's a joke with all those commercials there—and I mean ALL OVER THE BAND too, right down to 7,000 kc, once in a while you might find a 1 kc hole near 7,000 kc. I keep trying on 40 but it really looks like it's a losing battle. I keep trying about 0000 Z until 0130 Z and again 1000 to 1200 Z and also at other odd times hoping it may open up accidentally. Don't give up fellows. W8FGX and W8JIN SHOULD COME THRU SOMETIME!!! I did hear a W1 once and one single W6 and that's all as far as the USA is concerned.

COME ON SUN SPOTS I AM AWAITIN' FER YOU—

... Gus

"Your Friendly Supplier"



OFFERS

THE *hallicrafters*
HT-44 TRANSMITTER



Versatile compact amateur band transmitter for independent operation or transceiving with SX-117 receiver. SSB, AM, or CW on 80 through 10 meters. Features Hallicrafters stabilized phasing system. Vox/CW break-in and PTT operation. Exclusive AALC. Same size and style as SX-117. Takes P-150 AC Supply.

IN STOCK: Net \$395.00

P-150 AC SUPPLY for HT-44 \$99.50

ALSO IN STOCK: SX-117 Companion Triple-conversion super-heterodyne communication-type receiver. AM, SSB/CW, T-Notch filter. Net \$379.95

"Used Equipment Special"

HALLICRAFTERS SX-101A \$239.95
HALLICRAFTERS HT-37 \$344.95

WRITE FOR LATEST COMPLETE LIST


Evans **RADIO**

P.O. BOX 312

FONE
603-225-3358

CONCORD, N. H.

Paul Franson WA1CCH

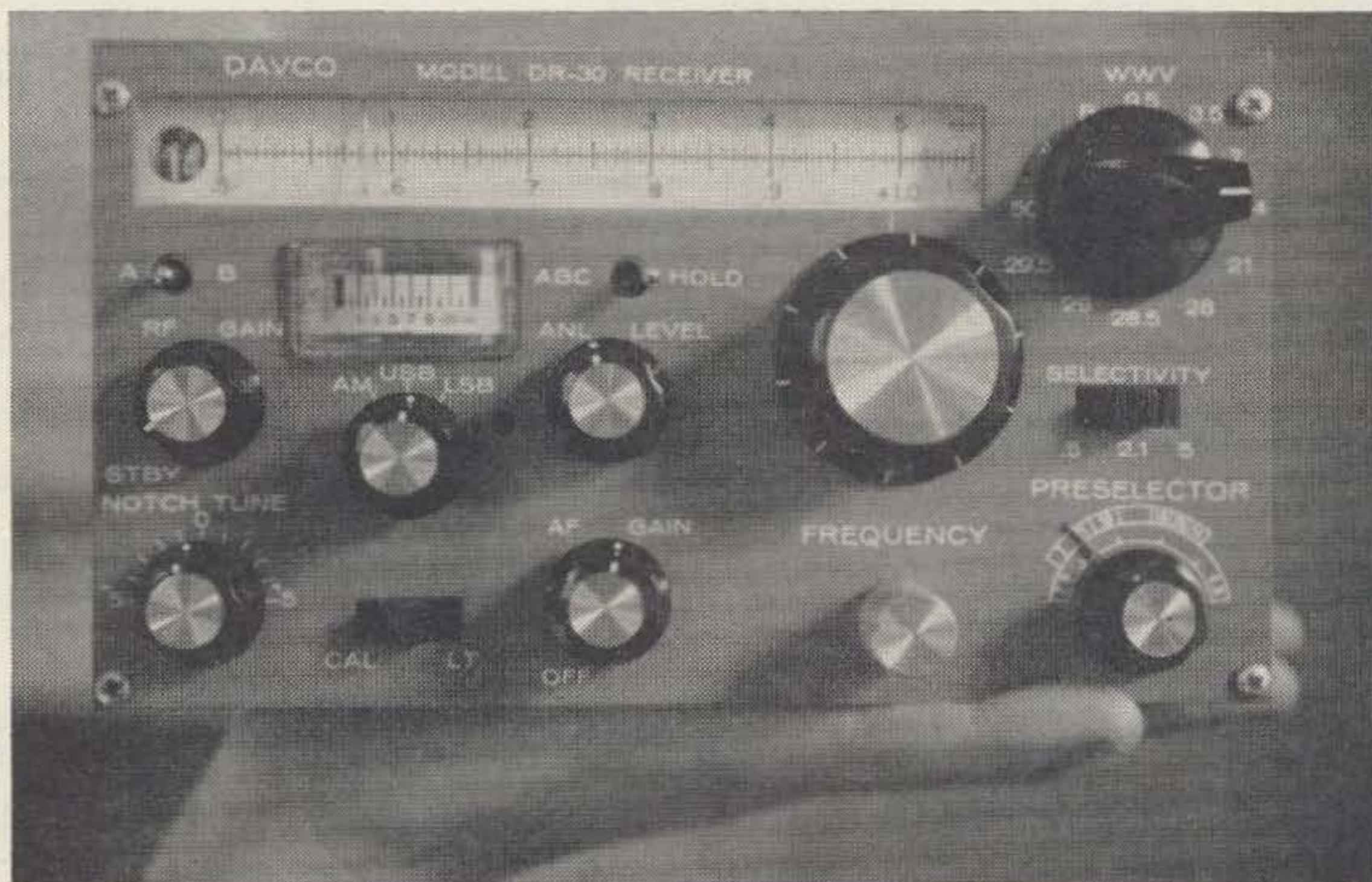

Testing the Davco DR-30

I was skeptical when I read the first Davco ads. You've seen them. The Davco DR-30 is a ham band transistorized communications receiver. That's not much of a surprise. We've all been waiting for one for 10 years. But the DR-30 sounded like a 75A4 crammed into a file card box—and then some! How could they fit all that performance, versatility and reliability into 1/10 cubic foot?

When the Davco arrived, I found out. They threw away the book of old-fashioned conventions on this one. It's the first really up-to-date amateur equipment I've seen. Davco has used modern techniques that are long overdue in ham gear. The DR-30 isn't just an old receiver stuffed into a little box; it's completely new. The first thing you notice about the DR-30 after its small size (4 x 7 x 6) and good looks is how solid it is. It's a heavy handful of high quality parts and state-of-the-art techniques: The "chassis" is a solid extruded aluminum frame with 3/16 inch walls. You couldn't bend it without driving over it. The controls are mounted on cadmium plated steel attached to the extrusion. The circuits mount on eight miniature fiberglass modules that plug into mil spec connectors on the frame. High-Q toroids are used for the rf amplifier and VFO. The *if* transformers are

the size of pencil erasers. A Collins mechanical filter, Clevite transfilters and a crystal filter furnish selectivity. In all, 15 diodes, 14 crystals and 25 transistors are used. All parts are high quality and conservatively rated.

Here is a complete high performance communications receiver that is compact enough to use anywhere: mobile, home, portable. It draws less current than a flashlight bulb, so it's economical to use with small batteries as well as in the car or from the power line. Yet the DR-30 offers exceptional performance. It uses dual conversion with a crystal-controlled front end. It covers every kc of the amateur bands between 3.5 and 50.55 mc (as well as 9.5 to 10.05 mc for WWV and two other 550 kc bands of your choice). The RF amplifier in the DR-30 uses high-Q toroidal coils for excellent image rejection and a UHF premium low noise transistor (2N2495). The noise figure of less than three db—even on six meters—and AM sensitivity of better than $\frac{1}{2}$ μ v means that you can hear those real weak stations when no one else can. It also means that the DR-30 is exceptionally quiet with no signal. None of that annoying hiss. In spite of all the advantages, transistors have one drawback compared to tubes: crossmodulation. Davco avoids this completely with a very clever trick: The RF gain control is an at-

tenuator in the antenna circuit. There is no loss when it's switched out, but the control provides excellent control action and seems to completely eliminate crossmodulation.

The DR-30 has three selectivity positions for optimum performance under all conditions in all modes. For AM, the *if* cans and transfilters provide about five kc bandwidth. SSB uses a Collins mechanical filter for 2.1 kc. For the CW hounds, there is a very sharp (about 500 cycles) crystal filter used in addition to the mechanical filter. There is very little difference in audio level as you switch between the three positions if your signal is tuned in properly. The audio is properly restricted for communications, yet very clean.

The Davco doesn't seem to drift at all. I varied the input voltage from 11 to 15 volts, dropped the receiver on the desk, took it outside (brrr) and couldn't hear any change in the beat note with WWV. This is partly accomplished by the high stability toroidal oscillator coils, partly by the solid construction, partly by the zeners, and partly by very extensive development of the temperature compensating networks.

The tuning mechanism uses a flywheel with extensive spring loaded split gears for very smooth, slow, backlash-free action. The dial is calibrated to five kc, and the tuning knob to one. Tuning sideband is as easy as tuning WCKY.

The notch filter is very effective in taking out QRM and heterodynes. The 100 kc calibrator is included. One of the real bonuses of the DR-30 is the noise blanker. It's not just an audio noise limiter. It picks up the noise pulses before the selectivity of the receiver lengthens them and uses the pulses to turn off the receiver for the minute duration of the noise. It's very effective in getting rid of all types of pulse-type noise.

The case of the Davco is heavy steel with a hard, scuff and scratch proof textured finish. The panel is HP grey with white silk screened lettering. Knobs are professional black with chrome inserts. Very nice.

Davco has also announced the companion transmitter to the DR-30. It's called the DT-20 and has the same front panel size. The two plug together for complete transceive operation, yet each has a VFO, so the receiver and transmitter can be used on separate frequencies if desired. The DT-20 should be available this summer.

One thing that occurred to me before I used the DR-30 was that the small size might make operation difficult. It doesn't. In fact, I'm impressed with the ease of operation of the

receiver. All of the controls are there within easy reach. You don't have to reach all over a huge panel trying to grab the gain control or selectivity. All of the controls have the same solid feel that the receiver itself has. Using the DR-30 is a real pleasure. My first thought was that it would be useful primarily for portable and mobile operation. Well, it's invaluable for that, but it also is the best home station communications receiver I've ever used. It's more convenient, more versatile and works better than those huge old-fashioned heat generators. I compared it to other receivers and converters. It beat them all. On six, the tremendous sensitivity and low noise let me hear many stations I couldn't hear on the well-known converters. And the price! The introductory price of \$337.50 is incredible. I don't see how they can make and sell the DR-30 for that. You can even get two for the price of some other good receivers. One for your car and one for your shack. I bet that the Davco will be more convenient, more versatile and work better than the big one, too.

You can see that I'm sold on the Davco DR-30. Try one out. You will be, too.

... WA1CCH

SUPERSPECIAL! VHF SEASON SALE

BE READY FOR THOSE 6 METER DX
OPENINGS WITH A

HIVERTER • 50

EXTENDS THE RANGE OF YOUR PRESENT
14 MC TRANSMITTER TO 50 MC

SEE OUR 73 ADS AND THE 73
REVIEW OF DECEMBER 1962 OR
SEND FOR FREE INFO.

HIVERTER 50, less TUBES
(1-6146,6CL6,5763) and POWER SUPPLY
was 99.50 NOW \$49.95 PREPAID

HIVERTER 50 Kit,
less TUBES and POWER SUPPLY
was 59.95 NOW \$29.95 PREPAID

Send for free list of etched circuit boards


IRVING ELECTRONICS CO.

P. O. BOX 9222

419 S. MAIN

SAN ANTONIO, TEXAS

Economy TR Switch

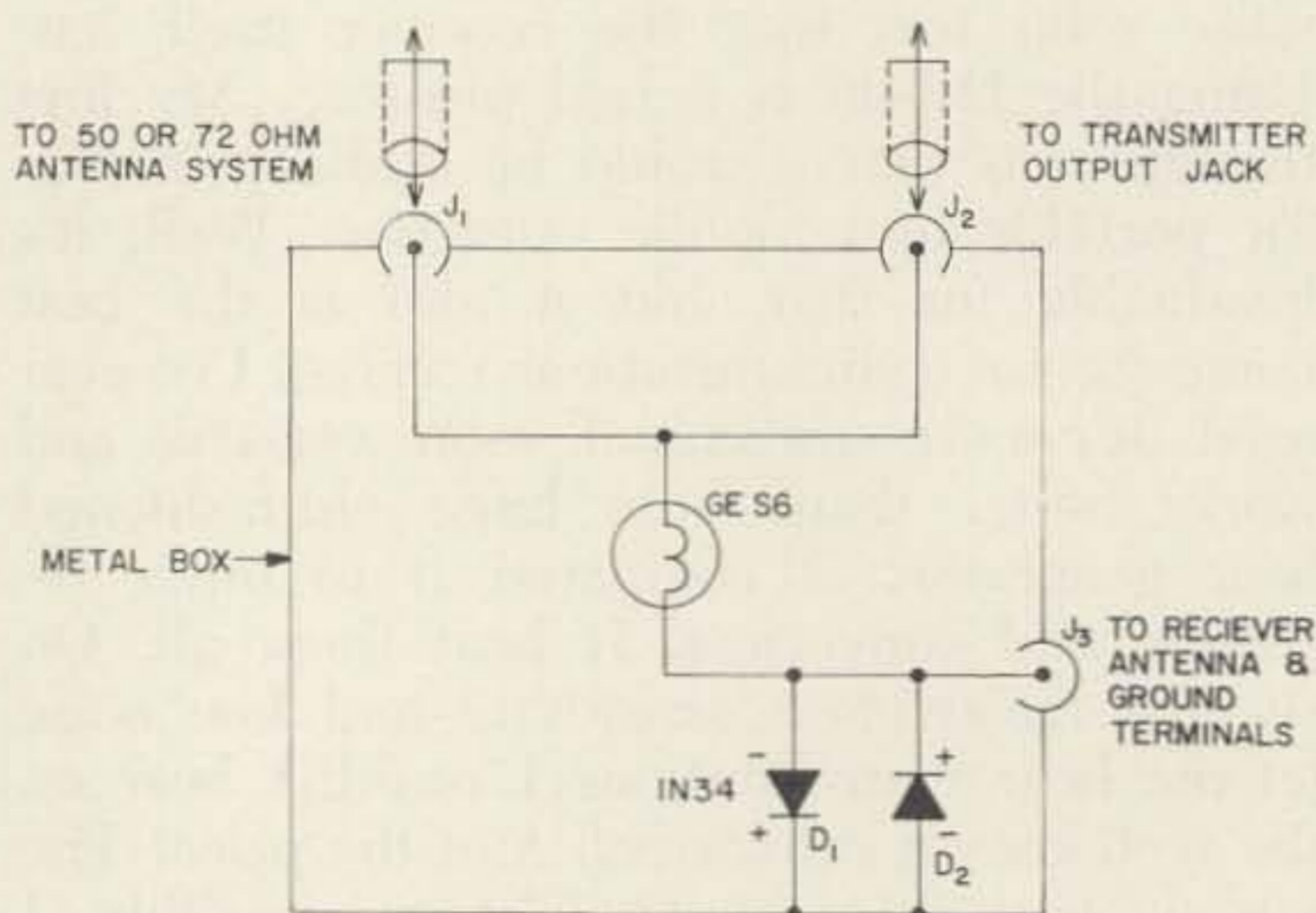

Here is an electronic device that permits instantaneous "switching" of a single antenna from transmitter to receiver. It is simple to build and requires no external power supply. It will handle output up to 500 watts and will also operate on "flea" power such as a Heath Sixer when an outboard converter is used. The only disadvantage found in this unit is that it does attenuate receiver signal slightly.

The unit can be built in a small metal box where all parts can be easily mounted. It should be remembered to use a heat sink when soldering the IN34.

This unit works very well on both CW and SSB and a single relay can be added and used on AM.

... W5ZBC

SEMICONDUCTORS

Paul Franson WA1CCH
73 Magazine

Welcome to the first of the monthly 73 semiconductor columns. I will write this column on the assumption that most types of vacuum tubes are obsolete, so will try to devote a good bit of the column to practical transistors for the average ham. At the same time, I'll try to tell you about the latest developments in semiconductors—even if some are a little beyond the reach of most of us. I'll be happy to hear about what you are doing and what you are interested in. Let me know about the transistors that you use. You may have made a find that none of the rest of us know about. All comments are solicited, but if you ask questions, be sure to include a SASE.

The IEEE show in New York provided the opportunity for visiting a bit with most of the semiconductor manufacturers. They had many new items on display. Many were very sophisticated (and expensive!), but others were quite reasonable and of immediate interest to all hams. One significant trend is to very inexpensive transistors for consumer uses. It's about time; until fairly recently, transistors were used for entertainment only in the ubiquitous portable radio. Hi-Fi equipment was the next field conquered. Now portable TV sets are becoming very popular and the American semiconductor manufacturers are rushing to bring out suitable cheap high performance transistors for TV. Most of these devices are good and inexpensive, but not the ultimate. They'll match a 6BS8 or 6CW4, but not a 416B. The easiest (?) way to make transistors cheap, of course, is to make lots of them. Thank goodness for the broadcast receiver industry. Another way to make transistors cheap is to substitute inexpensive, non-critical, plastic or epoxy cases for the expensive hermetically sealed, environment-proof, mil spec metal cases. Here are some of the interesting new economy transistors:

From GE: Silicon planar economy transistors in a small plastic case about 1/5 x 1/4 inch with three inline leads. Bulletin 45.01 describes the line. A few examples: 2N3663 has an f_t of 1100 mc, a "typical" noise figure of 4 db in TV rf amplifier service, and a price of 83c in large quantity. The 2N3721 has an f_t of 120 mc and only costs 20c in quantity. For transmitters, the 2N3405 has 900 mw dissipation, 50 volts BV_{CBO} and f_t of 150 mc. Price is 52c in quantity, and either \$1.25 or \$2.08 apiece singly depending on where you look.

Texas Instruments has a line of germanium epitaxial planar transistors that promise many ham and commercial applications. Numbers are TIXMO1-08. They are

encased in a new glass and plastic package with standard lead arrangement. Prices go as low as 30c. Among the advantages TI claims for the transistors are very low noise figure, guaranteed forward AGC characteristics, low feedback capacitance to eliminate need for neutralization, minimum detuning with AGC, and the package. Incidentally, extensive tests show that the package is very reliable and long-lasting.

Other manufacturers are also working on these economy transistors. Let's hope that they find their way into ham gear in not too long and replace those old tubes. Incidentally, I've been using the fabulous new Davco DR-30 receiver. It's what receivers have been working up to for these 50(?) years. Make sure that you find out all about it; it's a fantastic piece of gear, and considering its features and quality, should sell for twice its price.

Not all of the new transistors are cheap receiving types. TI has a new one (TIXS12) for microwave use. It oscillates up to 2500 mc (2.5 Gc) and puts out 1/4 watt at 1.5 Gc. Cost is a bargain \$1080! Other new TI transistors are the 2N2876 (\$49.50) for ten watts at 50 mc and three on two, and the 2N2631 in a TO-5 case (\$33) for 7.5 watts on six.

RCA has the 2N3632, 2N3553 and 2N3375 epitaxial silicon planar types for class A, B and C amplifiers, frequency multipliers, and oscillators at VHF and UHF. The 2N3632 will put out about 14 watts on two in unneutralized class C service.

RCA has also come up with some transistors specifically designed for use in 117 vac broadcast sets without low voltage transformer. Since most radios are used in buildings with AC power, why bother with batteries. The 40261-40264 transistors and 40265 rectifier provide excellent service from a four transistor circuit instead of the standard six transistor line-up of low voltage sets. They are also good in phonographs.

Bendix BIG rf silicon planar epitaxial transistors show a rating of up to 20 watts out at 50 mc. Typical numbers are 2N3619 through 2N3630.

TRW's (formerly PSI) new PT4690 puts out six watts from 28 volts at 400 mc with an efficiency of 40%. At 250 mc, output is eight watts with 8 db gain (1.7 honest watts of drive) and 70% efficiency. Cost is about \$38 in 100-quantity.

Write and tell me what you want in the column.

... WA1CCH

Quement

ELECTRONICS

"YOUR COLLINS HEADQUARTERS"

C-O-O-L BARGAINS




ROTRON MUFFIN FANS

110V AC 60 cycle (Like New Used)

4⁸⁸

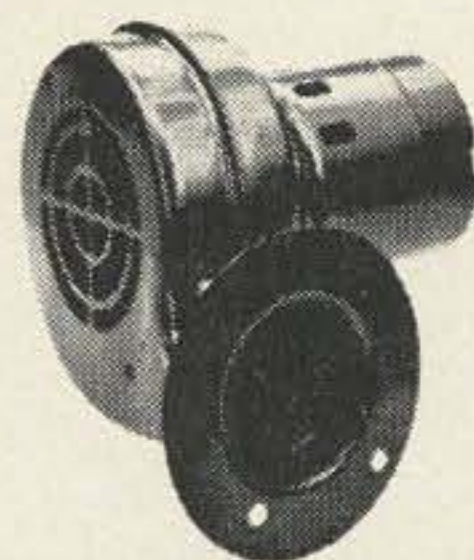EACH
Allow 50c for packing and shipping.
California residents include 4% sales tax.



SQUIRREL CAGE BLOWERS

2 1/4" vent—approx. 100 cfm—220V AC 60 cycle
Simply parallel the two windings for 110V AC
(LIKE NEW USED)

TIMER MOTOR

CLUTCH DRIVE FOR RESET
MAKE CLOCKS OR 10-MINUTE TIMERS



48c
EACH

Hundreds of Uses

BUY SEVERAL

Allow 25c each for shipping

1/60 RPM
110V AC
60 cycle

S.W.R. BRIDGE and FIELD STRENGTH METER

9⁹⁵

Allow 50c for packing and shipping.
California residents include 4% sales tax.



MAY BE LEFT IN LINE, UP TO 2000 WATTS.

GOOD THROUGH 2 METERS

THE BEST VALUE WE HAVE EVER OFFERED!

3⁸⁸

Allow 50c shipping

Collapsible 2 METER GROUND PLANE ANTENNA



Broad Band "N" connector furnished

LOOK!

20,000 OHMS per VOLT DC

1% Precision Resistors

RANGES:

AC volts: 0-10-50-250-1000

DC volts: 0-5-25-125-500-2500


DC current: 0-250 mil, 0-50 microamp

OHMS: 0-10,000 & 1 meg.

Expanded low-ohm scale.

DB: -20 to +22

Test Leads
Leather Carrying Case

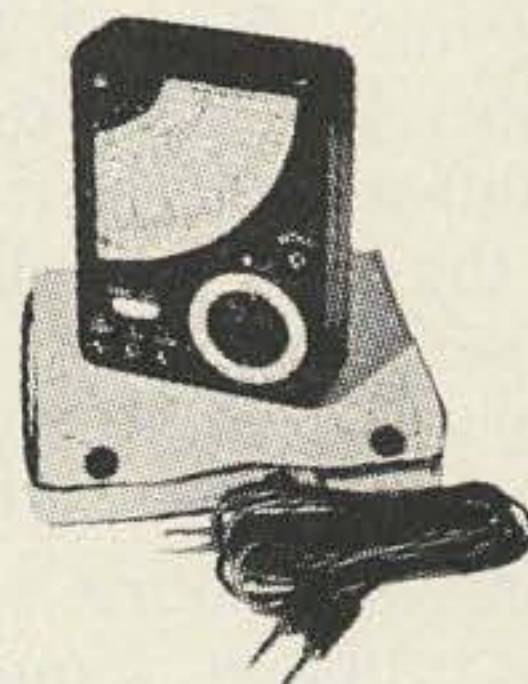

9⁹⁵

Allow 50c for packing & shipping. Calif. residents include 4% sales tax.


THE IDEAL MOBILE MIKE

HIGHEST OUTPUT CERAMIC MICROPHONE AVAILABLE — AVERAGE LEVEL — 48 db. TWICE THE VOLTAGE OUTPUT OF ANY OTHER CERAMIC MIKE. RESPONSE CURVE TAILORED FOR MAXIMUM INTELLIGIBILITY 300 to 4000 CYCLES.

- Rugged Hi-Impact cyclolac, take-apart case.
- Shock-resistant internal construction.
- Extra heavy duty push-to-talk switch can be rewired for special applications.
- Heavy duty rubber covered coil cord. 3 conductor, 1 shielded, 12" retracted, 6' extended.
- Spring retainer hang up clip.

5⁸⁸

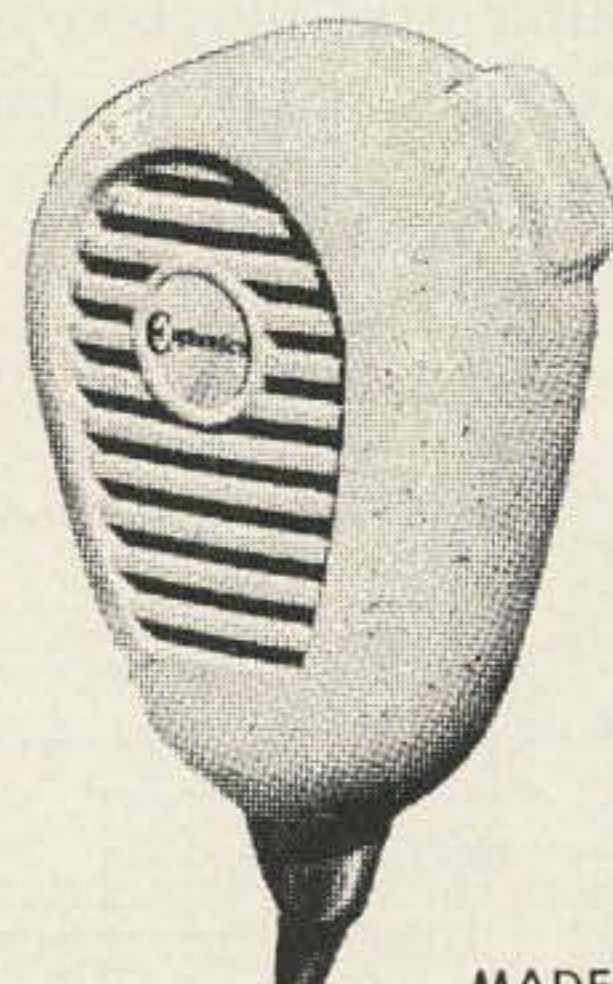Allow 50c for packing & shipping. Calif. residents add 4% sales tax



MADE IN U.S.A.

QUEMENT ELECTRONICS
1000 SOUTH BASCOM AVE. SAN JOSE, CALIF.

"NORTHERN CALIFORNIA'S MOST COMPLETE HAM STORE"

Here is a simple set and forget code monitor for those Novice and General brass pounders who operate the popular grid block keying transmitters

Jack Bruce WA6UVS
Box 259, Route 3
Carmel, Calif.

The Litts Code Snitcher

A few months back, friend and neighbor Dean Litts acquired for himself a new call, WV6YOV, an almost new DX-60, and an old but suddenly active set of nerves. Shortly thereafter on a visit to observe operations at the new shack I found friend Dean groggy, jumpy and determined as he pounded brass, twitched dials and strained to make sense out of the dits and dahs pouring out of the receiver. He had but one specific complaint, however: the necessity for retuning the receiver each time the QSO was "turned over." Most Hams, of course, will immediately recognize this problem. I must confess I didn't. Starting with a "General" and a sidetone transmitter I have always regarded a code monitor as strictly a gadget for tinkerers—until now. Herein, then, is an accounting of fun and education in designing a surefire monitor for the popular grid block keying transmitter.

There are two main problems associated

with designing a good code monitor. First, for a pleasing tone, a good sine wave must be generated; secondly, the sine wave must be keyed correctly and without disturbance to the keying circuits of the transmitter.

I researched the published literature on the subject. One author advocated breaking the grid resistor from ground and inserting the key at this point; this for grid block keying only. This arrangement produced some of the most sickly sounds this side of Doctor Ber Casey. Actually the results are understandable since cut-off of the tube is controlled by the value of the grid resistor through which the blocking voltage must pass; the larger the resistance, the slower the tube is forced into cut-off, and vice versa.

All the other literature concentrated on the principle of rectifying rf from the tank or antenna line and amplifying to either earphone or loudspeaker volume. The trouble with this

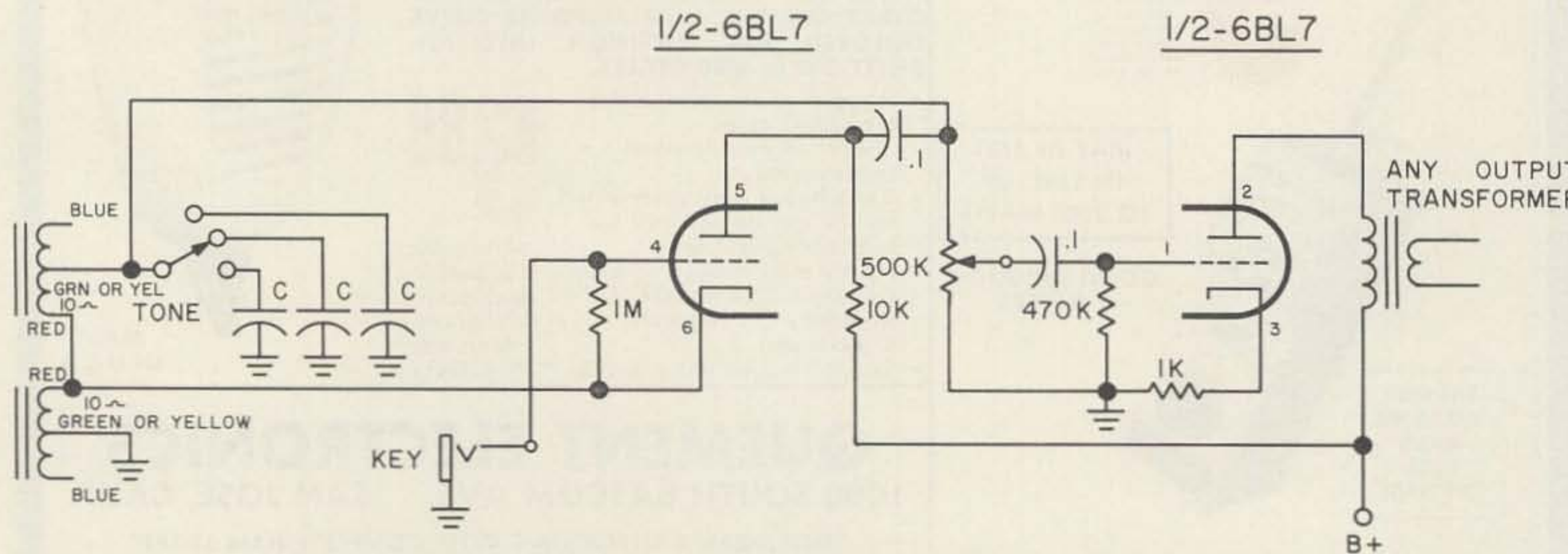


FIGURE 1

atter arrangement is that there are too many loose ends flopping around. For example, closeness of the pick-up coupling loop versus frequency.

Salvation of the situation rested in using a simple LC oscillator circuit in which the grid of the oscillator tube was at ground potential during operation and considerably above ground when in the standby position. This arrangement assured no interference with the transmitter circuits during "key down" and maintained the transmitter final at cut-off with the key up.

Fig. 1 shows the final arrangement of the Snitcher developed after many circuit changes. The final product is as bare of frills as possible. The only difference from a basic oscillator circuit is that the grid is keyed to ground, while the inductance coil feedback tap is connected to cathode and is above ground.

The grid resistor performs two purposes. The first is naturally to bias the tube. The second purpose is to keep the grid block voltage of the transmitter at approximately its original value before attachment to the monitor. Something between 100K and 1 meg will suffice. Actually the best waveform, and consequently the best tone, is obtained with a very low value grid resistor, but unless the monitor is to be used exclusively as a code practice oscillator, anything less than 100K will be impractical. The tank capacitor should be chosen to suit the ear of the user; decrease for a higher tone and increase for a lower one.

The inductance coil (L1) is the chief source of the good waveform. Almost any two coils of approximately the same inductance will work if connected in series. My unit worked quite well using two television vertical output transformers. These are readily available from old receivers. Select those of the auto-transformer type and choose two whose resistance between two of the leads is 10 ohms or less. Connect them as shown in Fig. 1 and wrap off the other two leads. It will be necessary to try a variety of tank capacitors to find the right combination because the inductance of transformers will be unknown.

The nicest thing about these devices is that they almost always work; the fun lies in making them work better.

Dean Litts no longer grumbles amid his bits and dahs; his Snitcher stays with him wherever he moves.

. . . WA6UVS



PEAK?
AVERAGE?
HI LEVEL?
LO LEVEL?
????

Hi Level Plate Modulation **what it means in TALK POWER**

With other low level modulation methods, we could have sold the 621 much cheaper, BUT with plate modulation, the peak power is 240 watts, not 60. This is 4 times the talk power we could obtain with a low level modulator. Discover how it pays off when you make the contact that the 60 watt peak power station, using grid or screen modulation (low level), couldn't quite make. The high efficiency final, 40 watts out on CW, 160 watts peak AM, plus other features such as the 220 mc adapter, make the 621 the best buy for 6 & 2 (& 220).

Write for catalog 1164 for full details on this and all our other VHF-UHF products.



Dept. P

P.S. The 621 is only \$274.50
(\$1.15 per peak watt) . . . — . . .

New Books and Literature

TMC SSB Handbook

In 1962, the Technical Material Corporation began a factory training program for their field engineers and customers. Out of this program grew the *SSB Handbook* by William P. Henneberry. This book covers the field of SSB carefully and completely. It was designed as a textbook, so is ideal for home study by novices and a reference for experienced engineers. Chapters: Introduction to SSB, Review of AM, Elements of SSB, Types of SSB Operation, Nature of SSB Signals, Distortion in SSB Transmitters, Balanced Modulators, Linear Amplifiers, Filters, Frequency Synthesis, SSB Receivers and Converters, The *SSB Handbook* is hardbound with 210 pages and many photos and drawings. Price: \$10. TMC, 700 Fenimore Rd., Mamaroneck, N. Y.

Zeus Catalog

The Zeus Portable Generator Co. has released a new comprehensive general catalog of its alternator-type electric power generators and accessories. A total of 14 different models from 1000 to 300 watts, including two new propane powered items, are listed. The catalog also describes describes 12 new accessories and options. All of Zeus' power plants are built around a permanent magnet alternator with only one moving part. This reduces weight and reliability considerably over conventional generators. Zeus also has available a series of charts showing the power required to operate various tools and appliances. Write to Tom Creighton, Zeus, 12435 Euclid Ave., Cleveland, Ohio.

Charts and Nomographs for Electronics

Solutions to hundreds of electronics math problems the easy way can be found in the new *Charts and Nomographs for Electronics Technicians and Engineers* by Donald Moffat and published by Gernsback. It will save you time and effort in any problem in every field of electronics. All you have to do to find a solution to your problem is turn to the proper page, slide your ruler in place and read the answer. You don't have to mess around with a slide rule or wear out your brain. Examples are even provided for each chart. The book is a large $8\frac{1}{2} \times 11$ and is spiral bound to lie flat. It contains 96 pages and costs a reasonable \$5.95. Gernsback Library, 154 West 14th Street, New York City.

Cush Craft Catalog

Cush Craft has out an attractive new catalog listing all of their amateur antennas and accessories. Included are yagis for 20 through 432, portable beams, collinears, Squalos, Big Wheels, halos, Twists, and ground planes. Make sure that you get this catalog from your distributor or from Cush Craft, 621 Hayward Street, Manchester, N. H.

1965 EICO Catalog

The new 1965 EICO short form catalog features many new EICO kits. EICO has many kits in the Hi-Fi, service and general fields of interest to most 73 readers. Their ham gear is particularly interesting. A new item is the only three band SSB transceiver kit. In all, over 90 items are fully described in the 48 page catalog. You can get your copy at your local distributor or from EICO at 131-01 39th Avenue, Flushing, N. Y.

Sams Transistor Spec Manual


You don't have to work with transistors very much to find an interesting fact: unlike the popular tube manuals put out by manufacturers, transistor manuals usually list only those transistors made by the company. Consequently, it's often very hard to find data about a specific transistor. The new Sams *Transistor Specification Manual* gives complete electrical specs, basings and outlines for over 3500 transistors. A useful section lists older transistors with new type numbers. If you work with semiconductors, you need this book \$2.95. Available from your distributor or from Howard Sams, 4300 W. 62nd St., Indianapolis, Ind.

GE Tube Manual

The eleventh edition of General Electric's *Essential Characteristics*, a digest-sized 320 page manual is now available. It contains a wide range of information on receiving tubes, special-purpose tubes and some other GE products. The manual provides information on virtually any tube you're likely to run into. One of its special features is that the basing diagrams are arranged across the separately hinged bottom portion of the pages so that data on any tube can easily be matched with its base. *Essential Characteristics* is available from distributors or by mail for \$1.50 from GE, Dept. B, 3800 N. Milwaukee Ave., Chicago, Ill.

EDWARDS ELECTRONICS whose personnel includes
**WA5EIY...WA5EDE...W5FYX...W5MZR...
W5KFT...WA5ISW...K5MPA...**

RECOMMENDS

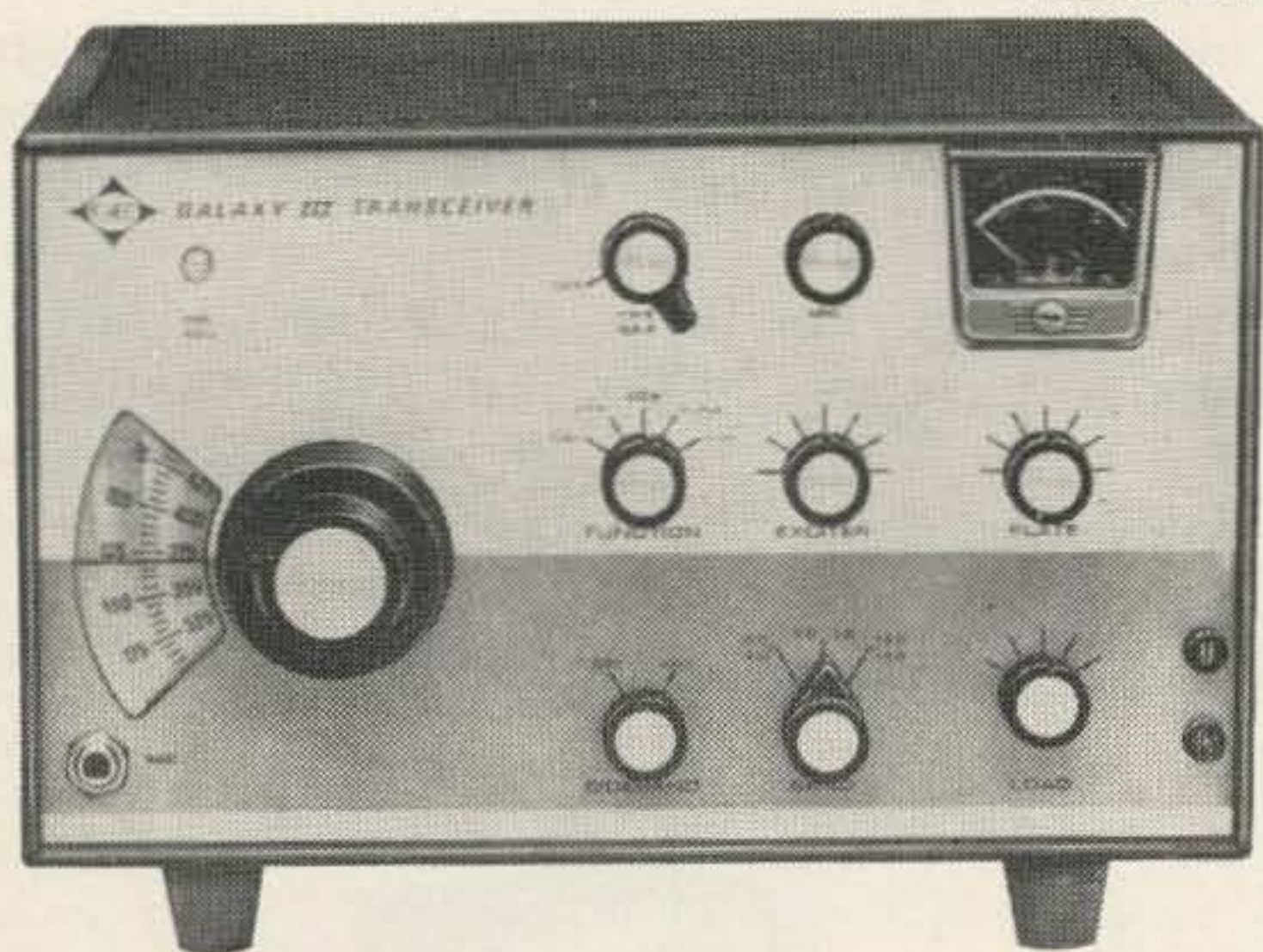

GALAXY III \$349.95

80-40-20 METERS (Illustrated)

GALAXY V \$469.95

80-40-20-15-10 METERS

IMPORTANT FEATURES OF THE
GALAXY III AND GALAXY V . . .

- ✓ 300 Watts SSB/CW Input conservatively rated.
- ✓ "Hottest Receiver" because of advanced design.

- ✓ Best Filter Available: 2.1 kc bandwidth with exceptional 1.8: 1 shape factor. The only 6-crystal filter used in amateur equipment.
- ✓ Most Compact 300-Watt Transceivers: 6" high, 10¼" wide, 11¼" deep; weight —only 13 lbs.

ORDER TODAY!

★ LUBBOCK, TEXAS
THE HOME OF

EDWARDS ELECTRONICS

WHO GIVES TEXAS-SIZE TRADES

P.D.Q. DELIVERY

AND A
TIME PAYMENT
PLAN.

PERSONAL
INDIVIDUAL
SERVICE
GUARANTEED

WE WANT YOUR BUSINESS!

**Edwards
Electronics**

TELEPHONE POrter 2-8759
1320 19TH ST. / LUBBOCK, TEXAS 79401

Edwards Electronics
1320 19th Street
Lubbock, Texas 79401

I'm interested!

- Enter order for equipment listed on attached sheet.
- Send Galaxy III and V literature.
- Send quotations for trade in allowances on equipment listed on attached sheet.

Name _____ Call _____
Address _____
City _____ State _____

New Products



Ham TV Camera Kit

There's no excuse any longer to put off getting on ham TV. ATV Research has done the difficult part of the work for you. Their model 65A Focus-Deflection Coil Kit furnishes all of the special hard-to-make parts for your camera. Included are machine wound focus and deflection coils, shielding materials and a shielded vidicon target connector. Assembly of the coils takes less than one hour. Included with the kit is a 16 page Vidicon Camera Construction Manual with complete instructions for building a straightforward 5 tube TV camera that uses standard, economical parts. Price is \$16.95 ppd. Write to ATV Research at P.O. Box 396 in South Sioux City, Nebraska, for more information.



Design Furniture

Are you tired of having to leave your beautiful ham gear on an old table in the basement because your unesthetic wife thinks it's ugly and won't let you bring it upstairs? Design Industries has come out with the solution to your problem. They make beautiful wood-finished equipment consoles that will soften the hardest wife's heart. The furniture is on casters, the front panels are easily replaceable for new gear, and the doors have locks to keep out sticky fingers. Our photo doesn't do them justice; get an attractive four color brochure from Design Industries, P.O. Box 6825, Dallas, Texas.




Tunaverter

No, there's nothing fishy about this one. It's Tompkins Radio Products' tunable converter for any single ham band (or special frequencies). The Tunaverter uses vernier tuning, tuned antenna circuit, printed circuit board, gimble mount, and an inexpensive nine volt battery. There are a number of different models including BFO's and a choice of 262 kc, 455 kc and 800 kc output, so write to Herbert Salch and Co., Woodsboro, Texas for more information.



New VHF Converters

Scientific Associates has brought out some new VHF transistorized converters. One is crystal-controlled and covers any one-mc segment from 108 to 170 mc. The other is tunable over a band of frequencies in the range. Both models include audio squelch, a tuned rf stage, and a tuned mixer and feature instant switching from regular BC to VHF. Size is only 5 x 3 x 2½". Price is under \$40. Scientific Associates, P.O. Box 1027, Manchester, Connecticut can send you more information.

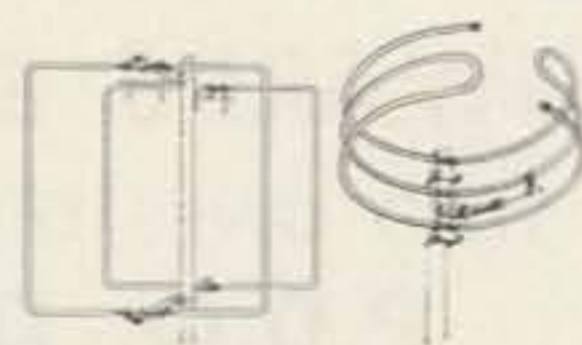

New 2 Meter Antennas

Hi-Par is making some interesting new 2 meter antennas. One is a halo that is three half-wavelengths long. Two of the half wavelengths are in phase and the other provides matching. Use of the extra section provides gain over a single ring halo. The other antenna is a two meter quad. It is completely factory assembled so that you only need to open it up and tighten a few nuts for use. Sounds good for portable operation. Contact WILKQ at Hi-Par, 347 Luenburg St. in Fitchburg, Mass., for more information.

73 Books

Peterborough, N.H.

CARE AND FEEDING OF HAM CLUBS—K9AMD.—Carole did a thorough research job on over a hundred ham clubs to find out what aspects tend to make them successful and what seemed to lead to their demise. This book tells all and will be invaluable to all club officers or anyone interested in forming a successful ham club. **\$1.00**

SIMPLIFIED MATH FOR THE HAM—K8LFI.—This is the simplest and easiest to fathom explanation of ham's Law, squares, roots, powers, frequency/meters, logs, slide rules, etc. If our schools ever got wind of this amazing method of understanding basic math our kids would have a lot less trouble. **50c**

REVISED INDEX TO SURPLUS—W4WKM.—This is a complete list of every article ever published on the conversion of surplus equipment. Gives a brief rundown on the article and source. Complete to date. **\$1.50**

SURPLUS TV SCHEMATICS.—You can save a lot of building time in TV if you take advantage of the real bargains in surplus. This book gives the circuit diagrams and info on the popularly available surplus TV gear. **\$1.00**

7—AN/ARC-2 CONVERSION.—This transceiver sells in the surplus market for from \$40 to \$50 and is easily converted into a fine little ham transceiver. Covers 2-9 mc (160-80-75-40 meters). This booklet gives you the complete schematics and detailed conversion instructions. **\$1.00**

12—CW—W6SFM.—Anyone can learn the code. This book, by an expert, lays in a good foundation for later high speed CW ability. **50c**

14—MICKEY MIKER—WØOPA.—Complete instructions for building a simple precision capacity tester. Illustrated. **50c**

15—FREQUENCY MEASURING—WØHKF.—Ever want to set yourself up to measure frequency right down to the gnat's eyebrow? An expert lets you in on all of the secrets. Join Bob high up on the list of Frequency Measuring Test winners. **\$1.00**

RECEIVERS. K5JKX.—If you want to build a receiver or to really understand your receiver, this is the book for you. It covers every aspect of receiving in author Kyles usual thorough manner. **\$2.00**

ATV ANTHOLOGY. WØKYQ and WA4HWH.—A collection of the construction and technical articles from the ATV Experimenter. Includes a complete, easy to build vidicon camera and 50 other projects. The only book available about ham TV. **\$3.00**

PARAMETRIC AMPLIFIERS. WA6BSO.—Parametric amplifiers are probably the most practical way for hams to get a low noise figure at VHF and UHF. This book is the only one available that covers both theory and practice. **\$2.00**


TEST EQUIPMENT HANDBOOK. W6VAT.—Every ham needs to have and know how to use test equipment. This book tells you how to make valuable ham test gear easily and cheaply. It also covers the use of test equipment. **50c**

HAM-RTTY.—This is the most complete book on the subject. Written for the beginning TT'er as well as the expert. Pictures and descriptions of all popular machines, where to get them, how much, etc. **\$2.00**



Babcock Band Filter

Babcock has announced the new Model 3-3234 Solid-State Band Filter that is used to improve performance of existing transmitters and receivers. It increases the talk-power of SSB transmitters by up to 12 db while reducing the transmitted bandwidth. Speech intelligibility is improved to aid in penetrating heavy QRM. When receiving, a steep-skirted adjustable bandwidth mechanical filtering system removes QRM that a fixed selectivity receiver would pass. T-R switching is automatic. Only three connections to your equipment are necessary: transmitter mike jack, receiver headphone jack and transmitter accessory jack for switching. A 455 kc SSB output jack allows the units to be used as an SSB generator. AC and DC power supplies are provided. \$319. L. E. Babcock and Co., 85 Nob Hill Drive, Framingham, Mass.

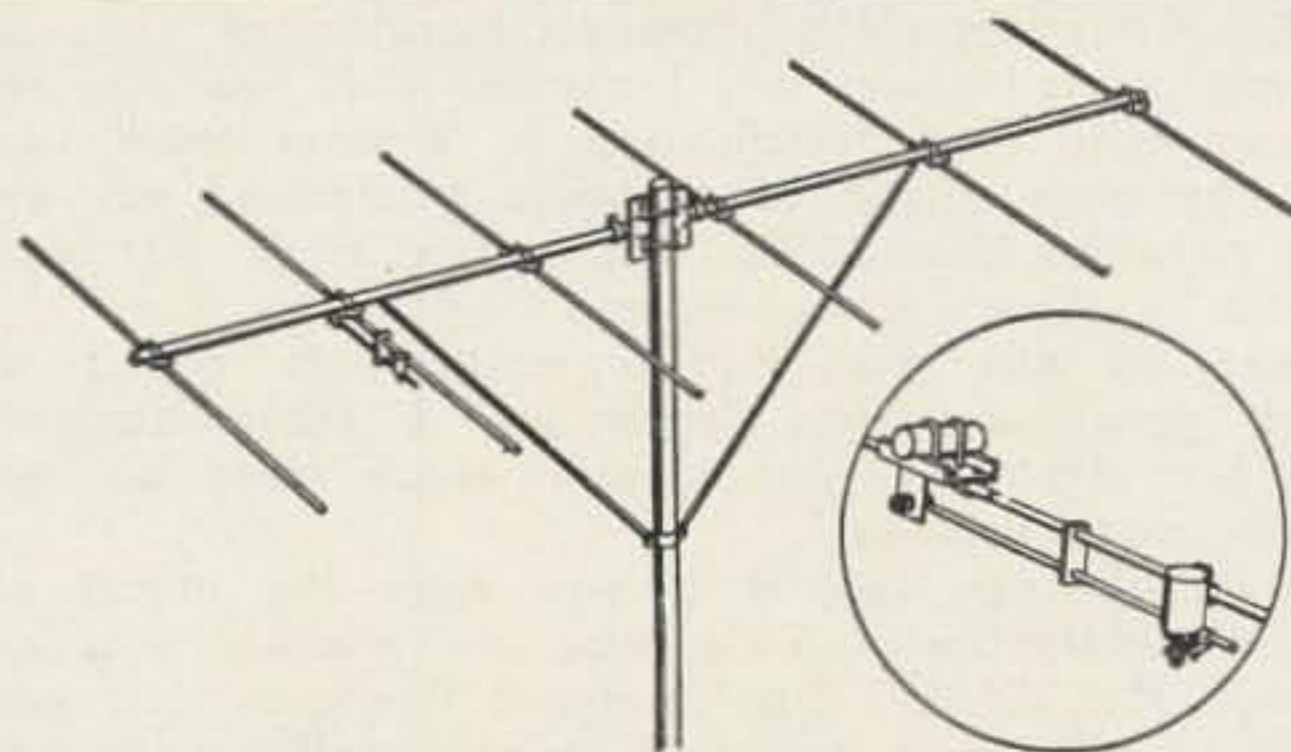

Long John
for Six Meters **\$34⁹⁵**

FEATURES

- Designed for maximum forward gain.
- Gamma Match for co-ax feeder.
- Finest grade aluminum tubing.
- Exceptionally strong since there are no drilled holes.
- All aluminum construction eliminates electrolysis.
- Entire beam and supports can be grounded for lightning protection.

We are proud of this new Long John Antenna. We've tried to put in every feature you could want. The result is a reasonable cost high gain beam which can easily be put up and which will stay there practically forever. It has a wide enough lobe so you don't have to swing it around all the time, yet gives you tremendous gain where you want it.

AT YOUR DISTRIBUTORS OR WRITE DIRECT

HI-PAR Products Co.
FITCHBURG, MASSACHUSETTS

advised by my lawyers that
don't you ever proofread y
are a bunch of crooks and
this is the last straw for
Letters
have no other recourse but
should be tarred and feath.

Sic

Mr. Green Attn.:

In pertaining to your article of November 1964 concerning our Kentucky DXpedition on page 90, I would like to comment that one certain sentence is a low down dirty lie deliberately defaming my character!

The article stating that I was kicked in the slats IS NOT TRUE and is a willful deliberate lie and there are witnesses who can prove this fact!

It was Alan, not I, who instigated that incident on our trip and he was the one who got into a fight and not I!

I don't know how that article got into that editorial but I have a pretty good idea who did it. Alan's picture is on the far right!

In the first place, the Hammarlund Co. put a ***** in charge of the trip by the name of Alan Day K8ITM! And the trip should never have got started!

I hate to do things like this Mr. Green, believe me, but my reputation is at stake here and I am not the troublemaker that Alan is!! Believe me I was in strong debate as to what to do about this and several friends of mine told me I should write you about it! They told me I would be a fool if I didn't!

You don't know half the story about that trip pertaining to the things Alan got away with and tried to get away with! i.e., trying to get me into trouble with the law!! Furthermore he was going to blame it all on me!!

I wanted to back out of the deal since I heard some bad things about Alan but he and his father forced me to go!! They are from Canton, Ohio.

I Demand a retraction and rectification of that false statement printed about me, I demand that you give me a free copy with that rectification in a later issue of 73 within the next couple of months! I Demand my share of the royalties printed in that article since Art and I did most of Alan's dirty work!!

If you do not wish to cooperate with me I shall sue you personally Mr. Green and I mean business!! People just don't like lies printed about them no matter what the cause may be!!

How would you like it if you were the object of a character defamation?? This hurt me whether you know it or not Mr. Green! But anymore it seems that people don't care who gets hurt! I would furthermore advise you to pre edit any further material you print. I also would like to assert that for the most part these people were most congenial, hospitable and much more honest than Alan! In conclusion after doing most of Alan's dirty work Art and I didn't even get to use the rig!!

Paul D. Keller K8EJN

Dear Wayne,

This is an emergency. Popular Electronics sent a petition to the FCC for a codeless ham bands to get the rag chewers etc. off 11 and put them on 2 meters. This would be a Communicators License according to P.E For reference see January and November Popular Electronics. Please let me know how this strikes you. It strikes me sickening. We're losing enough frequencies now without having to lose our VHF frequencies.

Darwin Hansen WAØHAY
Belmond, Iowa

You are absolutely right Darwin, we don't want any codeless hams on our bands. All of us had to suffer through that process and we want everyone else to have to go through the same thing. Sure, I know, half of the active hams never have to know the code once they get their license . . . but just think, suppose we had a war and all the Teletype machines and microphones were destroyed . . . we wouldn't be able to communicate without code. Let's keep that there code.

Hi Wayne—

I have a question for traffic handlers—so wonder if you can throw this one into the mixer and see what comes out?

Before you read this particular question I'll have to say I can't really sign it—if I do I'm a disgruntled so and so—or a rat fink—or disloyal (to who? I mean to whom—or do I?) So, if you don't think anyone can shed any light on it, throw it into the round file (like some of the traffic). By the way, I wrote another leading magazine this same tale of woe and I didn't see it in print—(I guess because I didn't sign that letter either) I'm a subscriber to the two leading magazines—73 (see, I put you first!!!) and QST. (Don't take offense, Macy's mentions Gimbel's) That third mag I let go, it was too wishy washy.

Okay, I'll get down to my state of puzzlement.

That BPL list that comes out in that other magazine? Are they all one operation stations? This is something I can't possibly understand and I wish some one could help me figure it out. I'm the kind of a person who checks the electric co bills and the oil bills to make sure I'm being charged the proper rates. (only about once a year, tho)

For instance, let's start at the top of the list for the month of December—here's a station with a total of 9802 pieces of traffic—originations 544—Rec'd 4669—Rlyd 3797—Delivered 792.

First I figured out the time values (estimated, of course) for delivered traffic. I have delivered traffic—most messages have no phone numbers so you look them up or call information—most of those with phone numbers are wrong anyway, so again you look them up or call information—when you finally get to call them it takes time to dial, half the time there's no answer or its busy—finally you get an answer, explain yourself, deliver the message, accept thanks, sometimes you have to wait and be told what a wonderful thing to do—average 4 minutes per message, total time 52.8 hours for 792 messages. (and if you can't reach them you must write it up and mail it)

Next originated—even a service message takes at least 2 minutes to write up. When someone calls with a message it takes anywhere from 5 to 10 minutes after introductions, finding the correct address, thinking just what to say—let me be generous again and say 4 minutes per—39.3 hrs for 544 originations.

Now, Received & Relayed. Good clear band, lots of power, no QRM, no breakers (who may be in the same town tlc is going to), standard texts (very small percentage and should be counted as 'book' traffic, anyway, and usually isn't), necessary fills, possible discussion about garbled name or address—lets say 3 minutes per, 4669 & 3797 messages total 423.3 hrs. This comes out to an estimate of a possible operation time of a Grand total 515 plus hours per month, broken down to 30 days for the month of December means 17 hours of full operating time (I allowed one day off for Xmas)

As I look at this awesome total I begin to wonder—does one have time for such everyday good health habits as eating and sleeping, etc, or daily necessities like food and family, or a simple little headache, or separating & sorting messages to reroute them in the proper direction to their destination? Then after all that is done, how does one sort time and count them without collapsing from mental and physical exhaustion?

Y'know, if someone gave me 9802 dollars in one dollar bills I'd take their word for it and not count it! How does one count all those Recd & reld, Recd & Delvd, Rcvd & QTA, Orig. Me oh my! It takes hrs. And where does one store these for a whole year?

I checked the call book to see where that station is and I looked on my road map and it isn't even listed altho I finally determined it is near a very large city area. Still, 792 messages are a heck of a lot of messages for delivery from one station in one month. Forget I wrote that—I'm too rotten a typer to rewrite this and my two fingers are about worn out.

So, you see, that's my question????? Using this top station as an example, can this possibly be done by one operator?

Didn't that operator go Xmas shopping or send out Xmas cards?

L. T.
Ann Arbor, Mich.

Dear Wayne:

I have just finished reading "The Amateur and Civil Defense Emergencies," page 58 of the February edition of QST. We need more of this type of article to motivate amateurs toward emergency service. I am in the military and a member of MARS and know only too well what an emergency is and what a backup means of emergency communications can do. I have been in the amateur service the last five years: I am sorry that I didn't think of it sooner. I also have over twenty years in the communications business.

I have a few remarks to make after reading Homer Gaston's (W5CZ) article. I found it very well written, especially concerning RACES, etc. Why can't a frequency within the amateur bands be designated for an emergency? Let's say 10 kc or so on the lower or upper end of each band be reserved for emergencies. This is only an idea, and comments are invited. How about a system such as the Marine service uses? Whatever is adopted as far as amateurs are concerned would be an improvement and I believe would greatly benefit the amateur service as far as the public is concerned.

In reference to the ARRL's recent proposals, I do not think they go along with them, but I do believe we could make a change of some sort, such as eliminating the novice and technician license and making some provision for training only in the one watt class. Some Europeans have this system, and it works real well. In reference to CB, made by Mr. Gaston, I do not believe CB will ever be able to replace amateur radio as an emergency service.

In closing, I would like to say, "Wake up, amateurs! Don't sit back and let the C.B.'ers do your job. We are a special brand of radio men, so let's prove it to the nation and to the world!"

Walter Evans W0ASH/DL4PJ
Wurzburg, Germany

Dear Sir:

I know it is more or less useless to write ARRL about this matter. Would be of no use anyway.

My problem is this. ARRL specifies a certain size envelope to be sent to their QSL bureaus. This envelope is of such a size that 1/3 or more is excess and unnecessary. So what does the P. O. do? They fold over the excess, causing the envelope to split open quite often. The recipient of the split envelope never knows if he received all the cards the bureau put in. I very often receive envelopes from the bureau where the envelope is completely in two parts and tied together with string.

This is not necessary. The high up "Fathers" at ARRL that have charge of setting policy on envelopes to be sent to the bureaus should decide on an envelope size 5" x 7" and have the QSL bureaus turn the envelope up the narrow way with flap open. Further, an envelope this size will take all QSL cards except very unusual ones and you would receive your envelope intact from the bureaus.

I'll never know how many rare QSL's I have lost to the P. O. in transit in those number 10 envelopes.

Leander J. Smith W7UVR
Kennewick, Wash.

Dear OM:

Why doesn't someone publish a breakdown book on military surplus. There's more and more new stuff coming up all the time, but what is it and what is it good for? No one seems to know but maybe the guy that is peddling it and in a lot of cases even he doesn't know anything about it but price.

Sam Main W0HQW
Grand Rapids, Minnesota

Sam, I've been trying to sell you the book you described for three years now. Our Index to Surplus lists every piece of equipment that has been written up in any radio magazine and is quite up to date. \$1.50 from 73, Peterborough, N. H.

LEARN RADIO CODE



\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME!

Also available on magnetic tape. See your dealer now!

EPSILON RECORDS

206 East Front Street, Florence, Colorado

CALL LETTER DOOR MATS

Personalize the QTH with your own call letters permanently molded in a rubber door mat. Made in four (4) colors, red, blue, green and black, large 18" x 28" size.

\$5.98 — prepaid, specify color

United Plastic Mold

9607 S. Atlantic Blvd.

South Gate, California

Columbia Gems!!!

ARC-5 COMMAND RECEIVERS

190-550 KC. This is the famous Q-5'er! Excel. \$14.95
3-6 Mc. Excel .. \$14.95 6-9 Mc. Excel .. \$14.95
100-156 Mc. Excellent cond. Terrific buy! 22.50

COMMAND TRANSMITTERS

2.1-3 Mc. New .. \$7.95 4-5.3 Mc. New .. \$7.95
3-4 Mc. Excel 8.95 5.3-7 Mc. Good .. 4.95

HEADSET & MIKE BARGAINS

HS-23 HEADSET: 4,000 ohms. New \$4.95
HS-33 HEADSET: 600 ohms. Brand new \$5.95
T-17D CARBON MICROPHONE: Brand new \$9.95
RS-38 CARBON MIKE: With coil card and PL-68 Plug.
Brand new and bargain buy! \$9.95

COLLINS ART-13 RADIO TRANSMITTER

2-18 Mc. 100 W. output. This is the famous one!
Excellent condition. A terrific buy at only \$49.50

ARB COMMUNICATIONS RECEIVER

Mfg. by RCA. 4 bands. 195 Kc-9 Mc. Excel. \$24.95

BC-348 COMMUNICATIONS RECEIVER

200-500 Kc. AND 1.5-18 Mc. in 6 bands! Like new.
Checked out—and guaranteed! \$89.50

R-105/ARR-15 RECEIVER

1.5-18 Mc. Has 2 Collins PTO Oscillators! Excel. cond \$59.50

RECEIVER SPECIALS! PRIDE OF THE NAVY!

Checked out. Guar. w/AC Power Supplies!

RBA: 15-600 Kc. Direct reading freq. dial \$95.00
RBB: 600 Kc-4 Mc. Direct reading freq. dial \$75.00
RBC: 4-27 Mc. Direct reading freq. dial \$95.00

WE NEED EQUIP.—HIGHEST \$\$ PAID!

We will pay top dollar if you will write us IMMEDIATELY! We urgently want: BC-160 (models H and I preferred), SP-600, R-388, R-390, TED, TCS, TRC, CV43/APR-9, TN-131/APR-9, ARC-34,-52. Test Equipment, Aircraft Comm. Equip., GRC, PRC, ALL SG Signal Generators. We pay freight!

COLUMBIA ELECTRONICS

4365 WEST PICO BLVD. LOS ANGELES CALIF.

World's Finest VHF Ham Shack for Sale.



High up on Mt. Monadnock, the highest peak in southern New Ham Shire, is one of the most exciting VHF locations you could ask for. The installation consists of a six room house, newly painted and newly roofed, all wood paneled inside, four acres of ground . . . the only private property on the mountain, all conveniences, five radio towers, the highest being 120 feet, beams up for 20-15-10-6-2-220-432 and a dish for 1296. Complete with ham gear if you like . . . receivers and converters for all bands up through 432 . . . transmitters for 75-40-20-15-10-6-2. Good solid kilowatt on two meters, mod by pp 4-400's. 288 elements on two meters. No TV sets for over a mile in any direction and darned few for several miles. 20 kilowatts of town power. 1 1/4 mile private road to house kept up by sight-seeing concessionaire nearby (who also protects house when unoccupied). Price \$21,500. Over 2000 feet up the mountain . . . breathtaking view. Will sell only to a ham.

Wayne Green W2NSD/1, Peterborough, N. H.

WANTED

MILITARY SURPLUS UNMODIFIED:

ARC-27, ARC-34, ARC-38, ARC-52,
ARC-55, ARC-57, ARC-73, ARC-84,
R-540/ARN-14C, ARN-18, R-220C/
ARN-21, APN-22, APR-13, APR-14,
ARR-41. COLLINS 51X-2 RECEIVER,
17L-7 TRANSMITTER, 51V-3, 51Y-3,
618S-1. RECEIVERS R-390, R-390A,
R-391. RT-66 THRU RT-70/GRC.,
R-108, R-109, AM-65, RT-77/GRC-9,
GRC-10, GRC-19. TEST EQUIPMENT
WITH ARM, SG, URM, UPM, USM
PREFIXES. COLLINS KWS-1.

**TOP CASH DOLLAR PAID PLUS SHIPPING
ADVISE CONDITION AND QUANTITY!**

WRITE, WIRE, PHONE (813) 722-1843,
BILL SLEP, W4FHY, EXPORT DIVISION
SLEP ELECTRONICS CO.
DRAWER 178, ELLENTON, FLORIDA 33532

6146B

Dear Wayne:

I've been reading 73 for almost two years now, and don't think I've ever seen an RCA ad yet. The back cover of every QST has one—I don't know about CQ; never touch the stuff—but none in 73. I was somewhat astonished, therefore, when you paid for a full-page RCA ad and a misleading one, at that.

I am referring, of course to the article "Easier Higher Power" in the March issue. This article contains nothing that the RCA full-page 6146B advertisements do not.

Why do I call it misleading? Think of the power gain in decibels and you will see. The db formula is $10 \log(P2 \div P1)$. This works out to a power gain of $10 \log(1.33 \div 1)$ db or, at the most, 1.25 db increase. At six db per S-unit, this comes out to .28 S-units higher than using plain old 6146's. And although the power gain will increase when you use two or more tubes in the final, the ratio of powers, and thus the S-unit increase remain the same. I'll stick with my 6146.

Mike Prager K1VSI
Providence, Rhode Island

They'll never advertise now.

Dear Wayne:

Now here's a thought that just might make you some money.

There is an impression in ham circles that the 6146B is an RCA exclusive. This is mostly because of the power of advertising—let's face it—on the back page of you know where.

I was recently at a meeting with some people from the Sylvania factory, and they were very sensitive about the fact that people in the commercial field didn't seem to be aware that Sylvania made a 6146B which Sylvania claim is even better than the RCA version.

The article by K9FWF tends to perpetuate the myth of RCA exclusivity.

I suggest you approach Sylvania with these facts, and show them that a series of full page ads in 73 devoted exclusively to the 6146B and possibly some of their wonderful new frame-grid tubes with fantastic Gm, might off-set the unfortunate impression which RCA has managed to create.

Bob Eldridge VE7BS
Vancouver, B. C.

Dear Wayne:

Enclosed is a postal money order for my subscription. Hope it's in time for the mailing of the February issue 'cause even as good as 73 is, I'm tired of driving a hundred miles for a copy!

I don't know when I've enjoyed a magazine so much. Your staff is to be complimented for being able to draw together so many interesting and informative articles. With my strong interest in building, but with limited ability to understand, I find a wealth of ideas expressed in language which doesn't take a degree in engineering to follow.

The purpose of this letter is not to knock things (or publications), but I can't help but note how nice it is to see a magazine *not* made up of monthly traffic reports, contest results, and such. Keep it up!

Merton D. Short W4JRJ

Dear Wayne:

Your very fine magazine came to my attention last December. Might I mention a few features of 73 that I find to be outstanding: Heavier paper stock; glossy finish; articles not continued at the end of the magazine; page to price ratio (Feb. CQ 28 pages shy, QST 1 page); opens and lays flat while reading or building; items like "The Callbook Game" . . . more!; the editorial is worth the price of the issue on its own merits; but above all I appreciate the well written features, the lay-outs and the up-to-the-minute information in regards to the amateur ranks. Some other points that enhance 73 are: authors full name and address given; advertising mixed throughout the magazine with the articles; most articles written, tested and explained by hams.

Joseph Gaudet
Haverhill, Massachusetts

Dear Wayne,

Many thanks for the fine articles you publish in 73. This is one of the most progressive magazines for amateurs that I have seen. I am a so-called "Charter Subscriber" and will continue to renew because of the fine contents of 73.

I have some info on telephone toroids that might be of interest to the Teletype gang. The list gives the WECO part or coil numbers, inductance in millihenrys (with the coils connected series aiding) and resistance of each coil per line winding (1/2 total resistance wired series aiding).

Toroid #	Inductance	Resistance per Line Wiring (ohms)
632	.088	4.2
638	.044	2.3
639	.022	1.1
641	.044	2.8
643	.135	4.5
644	.175	6.3
645	.250	9.4
651	.044	3.8

Also Wayne, I have the resistance and impedance ratio of the 120 series Repeat Coils. They are quite nice for matching and matching.

Repeat Coil #	Term				Impedance Ratio
	1 & 2	3 & 4	5 & 6	7 & 8	
120C	7.8	5.5	7.8	5.5	1 to 1
120D	12.7	5.5	12.7	5.5	1.5 to 1
120E	5.0	5.5	5.0	5.5	1 to 1.5
120H	7.8	5.5	7.8	5.5	1 to 1
120J	12.7	5.5	12.7	5.5	1.5 to 1
120K	5.0	5.5	5.0	5.5	1 to 1.5

I hope this info can be of use to you and the group. I have a quantity of the 632 88 mh and 638 44 mh coils in stock if for any of your future Teletype articles you would like to have a known source to mention. 50c each for the 44 mh and 75c each for the 88 mh.

W. O. Depelheuer W6GTE
R R 1 Box 145
Ellisville, Mo.

Dear Wayne,

I would like to take this opportunity to voice my approval of your battle against the "Powers That Be" in Newington. RM-499 is just so much QRM plus QRN and I feel it is now entering the QSB phase—I hope. ARRL appears to be working two ends against the middle. It seems obvious that with RM-499 at one end, they are attempting to eliminate many lone operators for the benefit of a few, while on the other end they are sponsoring all kinds of aids and encouragements to induce newcomers to hamdom. They cry loudly for "upgrading" or "preserve" our frequency privileges which of course means they think us hams should knuckle down and delve into all the theory books we can get our hands on, or get the heck off the air! But on the other end again, they are supplying books saying how easy it is to become a ham. A glaring example of their inconsistency is the cover of their latest edition of the "Radio Amateur's License Manual." A large illustration on the cover indicates "all you need to know—in a nut shell," while in the background is shown a group of what purports to be real solid study books—but ARRL puts a big black cross on these to indicate they are not needed—no—just buy their License Manual for 50c and you're in business!

WB2FKZ
Ballston Spa, N. Y.

Dear Wayne:

At the time I submitted the original manuscript for my article, "Improved Halo Mount," which appeared on page 84 of the March, 1965, issue of "73," I was still flogging up the mount with an old champagne bottle cork whenever going through the automatic car wash. Hesitating to mention this I made no specific recommendations. In the meantime, however, I found a standard size crutch tip caps the mount nicely whenever the antenna is removed. They're cheap and readily available at most hardware stores in both black and white.

Jack Ayres K3JZH

DIRECT TUBE REPLACEMENTS NO REWIRING NECESSARY

JUST PLUG IN—OUR ITEM SA
REPLACES THE FOLLOWING

5Y3, 5U4, 5Y3G, 5Y3GT, 5V4, 5V4GT, 5AU4, 5T4, 5W4, 5Z4, 5AW4, 5V3, 5AS4, 5AX4, 5AZ4

At Least 30-60V more B+ and
Current Capabilities up to 1 Amp.

PRICE: \$1.95 ITEM SA

DIRECT 5R4 REPLACEMENT

ITEM SC

Replaces 5R4, 5R4GB, 5R4GYB, Compensation network built-in.

PRICE: \$3.95 ITEM SC

STUD MOUNT SILICON TYPE 1032

All 5 amps.

200-400 V	price	39c ea.
400-600 V	price	49c ea.
700 V	price	69c ea.
800 V	price	84c ea.
1000 V	price	\$1.99 ea.

POWER TESTED SILICON RECTIFIER UNITS

(1 amp. @ 1 ma. max. leakage)

50-200 PIV	price	6c ea.
200-400 PIV	price	14c ea.
400-600 PIV	price	24c ea.
600-800 PIV	price	36c ea.
800 or better	price	44c ea.
1000 PIV	price	54c ea.

AERIAL WIRE

Reel contains approximately 138 feet of phosphor bronze, no. 16 stranded, 200 lb. test antenna wire. Has galvanized clips on ends. Brand new. Shpg. Wt., 3 lbs.

Cat. No. S-6313 \$1.50; 4 for \$5.00

SUPER PRO POWER SUPPLY

Rack Mounted Excellent condition.
Shpg. wt. 60# Price \$19.95 S-6609

TUBULAR HIGH CAP. ELECTROLYTICS

cap.	w.v.d.c.	price	2 for	Cat. #
20,000	MFD 25v.	\$.95	\$1.50	S-7120
25,000	MFD 25v.	1.25	2.00	7121
20,000	MFD 30v.	1.25	2.00	7122
40,000	MFD 10v.	.95	1.50	7123
40,000	MFD 30v.	1.75	3.00	7124
8,000	MFD 55v.	.95	1.50	7125

SPECIAL KITS

SK-3
1 SA Tube Replacement
10 600V lamp. Silicon Diodes PRICE: \$4.75


MICRO-SWITCH KIT

SK-6 99c
6 Micro Switches
SK-21 99c
20 Sil. Diodes 100 P.I.V. @ 1 amp.

SPECIAL MODULE LITE-UP BOARDS

Contains 30 neon bulbs. Lites up by applying 115V-60 cy. with 30-100K resistors, one for each bulb. Can be used for readouts and making computers, and freq. counters, etc. PRICE: 99c ea. or 3/\$2.50

REGULATED POWER SUPPLY

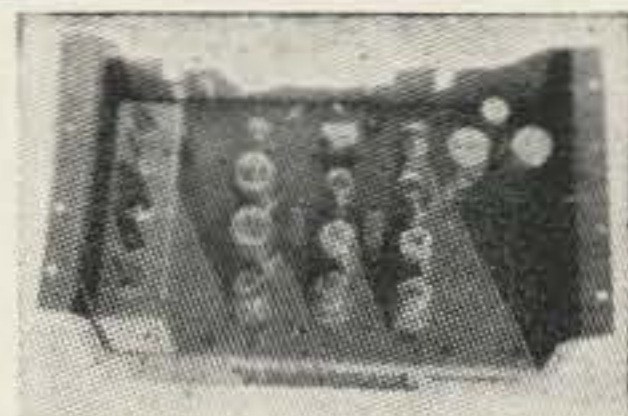

Wickes Model PS-3. Power Input 105-125V, 50-60cps
370 Watts. Regulated D.C. output (adjustable) 270-300V.
Max. output current—400ma regulation: 100 to 400 ma—
less than 0.5 volt. A C ripple, peak to peak—less than
0.015 volt. Output impedance—less than 0.7 ohm. Over-
all Dimensions + 19"W x 10 1/2"H x 12 3/8"D. Recessed
rack mounting. Shpg. Wt., 85 lbs.
Cat. No. S-6425 \$34.95

ALL ITEMS FOB OUR WAREHOUSE,
PHILA. PA. — MINIMUM ORDER \$3.00

SELECTRONICS

1206 S. Napa St. Phila. 46, Pa. HO-8 4645

W2NSD/1 from p. 3.

should all give the League a rousing cheer (Bronx) for coming up with such a winner. If they do as well for us with the FCC we can turn to stamp collecting.

Good Old Oscar

Along early in March I began to suspect that they really might get that overgrown shoebox into orbit. I think they really hit home when the Oscar III crowd answered my request for launch data or perhaps a collect phone call with a particularly evasive letter, telling me to listen to WIAW like everyone else. Judging from the almost complete lack of public press coverage the committee for Oscar III must have given the rest of the press the same brush-off I got.

So here we are with an operating amateur radio satellite. This should be one of the biggest news stories yet . . . and through unbelievable negligence the story has not been told. This is another clear indication of the immediate need for a change of leadership at ARRL HQ. ARRL Director Howard Shepard was in charge of Oscar III. To date . . . some three weeks after the launching, I have not had one single news release from ARRL, or the Oscar III Committee. Great, eh? I'll leave it to you to project this adept handling of key amateur radio publicity into the international amateur situation.

When I realized that O3 might be up at any minute I called Cushcraft and got them to stop making Squalos for a few minutes and whip up a 22 element Multi-Polarized Twist antenna for me. It arrived a couple days later and my first inclination was to put it up on 73 Mountain on my 120 foot tower. Then I got to brooding about hearing Europe and the ridge to the east which would probably block such goings-on. The result of this was that we installed it at the Hq shack in Peterborough.

O3 went up on the 9th of March and my antenna went up on the 13th. This is about par for me. While Dave WA1DUN and Barry K2YDD/1 were getting the antenna up, Paul WA1CCH and I turned our attention to the rest of the gear. The receiver was easy . . . a converter into my NC-300. The transmitter was more of a problem. A new 826 got my Gonset 2M linear working again (those darned tubes cost over \$4 now . . . and they used to sell for 30c!) . . . I also siliconized the power supply so I wouldn't have to worry about 5U4's any more. Four of Meshna's bargain 1000 PIV units worked fine.

I suspected that the 100 watts suggested by O3 Committee was a bit dreamy so I started

modernizing an old 500 watt 2M rig (from the W2BFD auction). Silicons in the power supplies . . . tracing out the control circuits . . . new meter panel . . . etc. After only minor catastrophies Paul and I had it perking just fine. One thing I could never understand is why those 4-125A's have to have about 50 watts of drive to work right when the Eimac data sheets call for about one tenth of that. I've never known anyone to get away with the rated input to the grids. I checked with the local FM servicing people and find that they do the same as I do . . . 50 watts drive.

So there we were . . . antenna up and ready to aim . . . converter dishing out beaucoup hiss . . . transmitter ready to grunt out gobs of rf. A short check of the band and I had all the data on the next few orbits from WIJZD. The first orbit was supposed to be very low to the east . . . great for hearing Europe. I didn't even hear the hi signals. On the next orbit, an hour and a half later, the hi's came in quite well and I heard a couple of relayed ham signals fade in and out . . . nothing I could copy. This was going to be harder than I expected. I tried horizontal polarization . . . vertical . . . right hand circular . . . left hand circular . . . horizontal and vertical together . . . all worked about the same . . . I think. I really couldn't tell much because the darned thing was fading in and out and I had to try to keep the antenna following it too. It suddenly became quite clear to me that I needed a lot more sophistication in equipment before I was going to do any serious O3 communications.

In the two weeks since that great discovery I have listened to many of the passes of the satellite and have managed to copy quite a list of calls . . . I've heard a few fellows managing two way copy . . . but very few. I hear Sam WIBU up here on a direct basis, though I've never heard his signal come through O3, and he seems to hear Oscar a couple of minutes before and after I do. I understand that he has had contacts with Germany and Switzerland. Some of the signals peak up to an S6 here, but most are S2 or worse. The most often heard are W8YIO, K2GUG and W8KAY. I have yet to send a dot.

Advertising

If 73 is just another ham magazine to you please skip over this part of the editorial. If you are interested in what I am trying to accomplish then lend me your eyes for a couple minutes.

A digression is obviously called for here. What *am* I trying to accomplish? Basically I

COME TO THE HAMFEST

SUNDAY JULY 4

PETERBOROUGH, N.H.

73 is having a hamfest. It's going to be a real old fashioned hamfest with fun for all. There'll be no admission charge, no "donation" and no registration fee. Come away from the hot, muggy city to the beautiful Monadnock Region of New Ham Shire to meet us and have a pleasant day with all of your ham friends and all of the activities you enjoy:

Tremendous auction: clean out all of that useless old junk. There'll be no charge and no commission. A special feature will be part of W2NSD's legendary collection for sale.

Antenna measuring contest: Prove that you can make (or buy . . .) a better antenna than everybody else. Find the true gain of your beam. Any horizontally polarized antenna for 2 or 432 that one person can hold is eligible. Have 10 feet of RG58 with a male BNC connector attached for the lead. Prizes and glory for the winner.

Homebrew contest: Bring that gear you've built and show it off. Separate judging for simple and complex equipment, gear built from 73 articles, and on neatness, originality, performance, etc. Prizes.

Two meter hidden transmitter hunt. A contest that

belongs at every hamfest. Prizes for the winners.

Dealers: Surplus and other dealers with goodies for sale.

Technical talks and demonstrations by well-known hams and manufacturers.

Special bookshop sale. Unbelievable 73 subscription price. Back issue grab-bag.

73 Mountain and Pack Monadnock for fascinating VHF operation. Bring your portable and mobile gear. Open house at 73.

For the wife and kids: Nearby state parks and mountains with swimming and climbing. Antique shops. Beautiful scenery and pleasant driving. Have a picnic. Bring your food or buy some at nearby shops.

Let us know if you are coming so we can plan accordingly:

73, Peterborough, N. H.

Write to the Monadnock Region Association in Peterborough for information on inns, motels, parks, covered bridges, antique shops, tourist attractions, etc.

10 A.M. Sunday, July 4th at the National Guard Armory three blocks west of the junction of routes 101 and 202 in Peterborough, N. H.

Y'all come.

want to make amateur radio as much fun for everyone as I can. This seems to me to include my attempts at holding down the dictatorial behavior of certain ARRL officials . . . the formation of the Institute of Amateur Radio, and the inclusion of as much technical and construction material in 73 as possible. Sure, I botch things up now and then . . . and you have to suffer along with exposures of ego, but for the most part I think we are doing what we set out to do.

The medium for all this is 73 . . . without it you are back to the few articles published in QST and CQ every month and *no* one to speak up when something rotten is perpetrated.

73 is paid for by the advertisers. Your subscriptions pay for us to mail you your copies and provide the readership which encourages the advertisers to advertise . . . but the magazine is paid for entirely by advertising. This means quite simply that the more advertisers we have the more magazine we can publish.

No doubt you've noticed that several of the larger manufacturers are not advertising in 73. There are several reasons for this. A few of the companies count their advertising results by the number of catalogs requested . . . and 73 comes out very poor on this because over 90% of our readers already have most of the

URGENT, NEED IMMEDIATELY

Very high prices paid. Freight prepaid. AN/GRC; PRC; APR; APN; ARC; ALT; URM; UPM; TS. We also buy all military and commercial test, radar, and communication equipment.

CALL COLLECT. IT COSTS YOU NOTHING TO HEAR OUR HIGH OFFER.

SPACE ELECTRONICS

4178 Park Ave., Bronx, N. Y. • (212) CY 9-0300

TWO-WAY COMMUNICATION CRYSTALS

**AMERICAN CRYSTAL CO.
PO BOX 2366 KANSAS CITY, MO.**

Ballantine 300 Voltmeter	\$49.50
Hewlett Packard 500B Freq. Meter, 3cps-100kc,	\$125.00
H.P. 616A UHF Sig. Gen. 1800mc-4000mc.	\$475.00
H.P. 475B Tunable Bolometer Mount 1 kmc-4 kmc.	\$39.50
H.P. 335B FM Monitor	\$275.00
H.P. 415A S W Indicator	\$65.00
General Radio 667A Inductance Bridge	\$135.00
G.R. 650A Impedance Bridge	\$95.00
G.R. 805C Sig. Gen. 16kc to 50 mc. 7 Bands	\$450.00
Fairbanks Morse 400cps Generators, 600cps in, 4KVA	\$150.00
Microline (Sperry) Model 444 Klystron Signal Source	\$175.00
PRD 650 Power Meter	\$95.00
PRD 801A Klystron Power Supply	\$195.00

Government Warehouse, Inc.

264 Shrewsbury Ave., Red Bank, N. J.

BARGAIN BUYS IN LIMITED QUANTITY SPECIALS!

TEKTRONIC-517 SCOPE	Checked out. Like new	...\$475.00
TS-175/U FREQ METER	85 to 1000 mc/s Checked out	129.00
BC-221 FREQ METER	125 to 20,000 kc Checked out	75.00
TS-34A/AP Scope	Checked out	49.00
TDQ XMITTER	115 to 156 mc 45 watts Checked out	129.00
RBL RECEIVER	15 to 600kc. Checked out	69.00
RAO Receiver	540 to 30,000 kc Checked out	89.00
BC-342	1.5 to 18 mc 6 bands Checked out	79.00
BC-348	200 to 500 kc & 1.5 to 18 mc Checked out	89.00

HEADSETS:

HS-23	2000 ohms	...\$4.95
HS-33	600 ohms	...5.95
H1-Fi	Headset 600 ohms	...9.95

Money Back Guarantee on Everything We Sell.
Write for free bargain flyer.
All orders F.O.B. North Hollywood.

COMMUNICATION SALES CO.

7231 Hinds Avenue North Hollywood, Calif.
Phone: (213) 765-4418

TRANSTENNA 102A

A PRESELECTOR SECOND TO NONE AND A T-R SWITCH BEYOND COMPARISON

Pat. Pndg. U.S.A. & Canada

MODEL 102A

\$69.45 (Add \$7 for Sidetone
— either model)
15 DAY TRIAL

Return For Full Refund If
You Burn It Out Or Are
Not FULLY PLEASSED

- Std. coax coupler (xmtr to feedline)
- No TVI or Suck out
- 30 DB Min. Gain (10-80 mtrs)
- No Effect on Transmission
- Monitored switching
- Full Legal Input
- Burnout Proof
- CW Sidetone (optional)

Write for Free Literature

33 Myrtle Avenue

Cedar Grove, N. J.

Tel: CEnter 9-6412

Improved 102A Adjustable Mute Circuit
Breaks Any Xmtr-Rcvr Between Dots &
Dashes Without Clicks. Improved Semi-
conductor Through-Position Switch
Switches Rcvr Directly to Antenna
for Unity Gain 6-80 Mtrs.

102B, \$59.00 like 102A exc. rcvr. muting

FICHTER

ELECTRONICS

SURPLUS BARGAINS

We have moved to new quarters to start the new year
with. Lucky finds and scarce items.

TCS DYNAMOTOR MOBILE POWER SUPPLY

NEW 12 v dc input, 400 v dc @ 200 ma output.
\$3.95 postpaid west of Denver. \$4.95 postpaid east

Dow Trading Company

N. Dowdell W6LR
Elliott 7-3981

2057 E. Huntington
Duarte, California

SG93/URM75	4-220mc Signal & Sweep Generator. Crystal	EX	67.75
Polarad LTU-3A	Tune. Unit 4460-16520 megacycles.	EX	\$355
Ferris 32-B	RF Noise and Field Strength Meter	EX	\$195
Tektronix 121	Wide Band Preamp for 511 Scope	EX	47.75
Gen. Radio 667A	Induct. Bridge .1 microhenry-1H	EX	\$155
Rollins Mod. 80	H1 Level Sig. Gen. 2.7-3kmc @ 10W	EX	\$475
Ballantine 300	AC VTVM in 19" rack panel	EX	38.50
Lambda 28	200-325VDC @ 100ma 1% Reg. 6.3VAC	EX	22.50
Lambda 32	200-325VDC @ 300ma 1% Reg. 2X6.3VAC	EX	31.75
T61/AXT2	TV Xmtr W/Video 7 Sync Modulators	NEW	17.50
RT82/APX6	Converts to 1215-1296 mc X'ceiver	NEW	21.75
UPM8	Tests APX6. 27 Tubes, 10 Diodes. For 60 cy. GD		14.50
Manual for TS726/UPM8	above. Postpaid	NEW	2.90
SWR Bridge	Micromatch-Reflectometer. 30-1000mc.	EX	8.25
R23/ARC5	The "Q5-er" tunable IF. 190-550kc.	GOOD	11.25
RT18/ARC1	100-156mc Xceiver. W/Tubes & DY9	GOOD	19.75
Same less tubes	and Dynamotor DY-9	GOOD	9.75
T465/ALT7	Xmitter 168-352mc W/2-6161s, 100W out.	EX	22.50
Schematic for T465/ALT7	with parts values.		1.00
Tuba Type 6161	W/connectors. Good to 2000 mc	EX	7.50
SA325/U	Coaxial Relay SP4T. With 28 VDC Motor	EX	3.25
Set of 120	Xtals Type FT243 5675 thru 8650kc		120/17.50
CU119A	Coupler 13 one-tube amplifiers w/tubes	NEW	4.75
CU48/ARA6	50 ohm coax to twin-line coupler	NEW	3/5.00
RE2/ARC5	Ant. Relay W/Meter & Vac. Capacitor	EX	3/6.00
Meter Weston	Model 843 500-0-500 microamps. 3"	EX	3.85
APN1	Xceiver 420mc. Less modulator and Tubes	GOOD	3.75
IC/VRW7	Wire Recorder 28 VDC W/Tubes	GOOD	4.75
R122A/ARN12	75 mc Superhet. W/9 Tubes & Xtal. GD		2/7.00
Rt. Angle Drive	W/Gears & Universal. 1/4" shaft	EX	3/5.00
UPM11A	AFC Unit W/8 Tubes & Wiring Diagram	NEW	3.75

AN/APR9 Microwave Test Set for APR9 Receiver LN \$650

E. C. HAYDEN

BOX 294 Bay Saint Louis
Mississippi

Shipment: FOB Bay Saint Louis.

Terms: Net, Cash.

catalogs. I've been trying to interest them in selling their products rather than catalogs in the ads, but haven't done too well with this novel approach as yet.

That still leaves quite a number of major firms who are not advertising in 73 and I don't know for sure why they aren't. I do know that those companies who are advertising claim very good results. Some claim astounding results. Perhaps you can do something to help us in this matter.

If you mention 73 when you write for information to companies that are not advertising in 73 . . . ask them about it at conventions . . . ask their distributors . . . their manufacturers representatives. Let them know which magazine you want them to support . . . which one will get to *you*, their prospective customer. Let's see if we can get any one of the advertisers in the first pages of QST to support 73 . . . now *there's* a challenge for you.

There really aren't many logical reasons for not advertising in 73. Our rates are a lot lower than the other two magazines, one of which seems to have considerably less circulation than 73. Our results for most advertisers have been outstanding. How about a job as Assistant Advertising Manager?

Help! He Says . . .

Several readers have forwarded a letter to them by the Midwest ARRL Director. It makes morbid reading. "Frankly speaking, our amateur bands are going to be in more danger at the next international allocations conference than at any time in my memory." Then he goes on, frequently saying, ". . . the League's efforts to save amateur radio as we know it . . . to help save amateur radio . . . to help save the amateur bands . . . to help save amateur radio. . ." Then, "The ARRL has saved amateur radio on several occasions in the past . . . the ARRL can save it again with your help."

The ARRL has not, during the 27 years I've been a member, saved amateur radio from anything. Sure, Percy Maxim saved ham radio back after WWI, almost 50 years ago . . . but that wasn't any ARRL that I am familiar with and it seems to me that if that is the saving job they have been using on us all these years that it is just a little thin by now.

The most interesting thing to me is that an ARRL Director is writing exactly the same things that I have been criticized by the League paid management for writing . . . that we face a very threatening future. I doubt if anyone in the history of the League has ever been so personally maligned in QST editorials as I was for saying just that.



GENERAL RADIO

VARIAC 26 amp max output model V-20, 115 volts AC 60 cycle in. 0-135 volts out. These are brand new surplus w/knob & plate. Priced about 1/2 cost.

\$24.00

88 MH TOROIDS. Two types available. Open and potted. Used for many applications such as power supplies and teletype.

Open style 50c each, 12/\$5.00
Potted style 65c each, 12/\$6.00




MESHNA

19 ALLERTON ST., LYNN, MASS.

All Material F.O.B. Lynn, Mass.

SIGMA Relays 115 volt, 60 cycle, 2 amp contacts SPDT.

75c ea. 8 for \$5.00

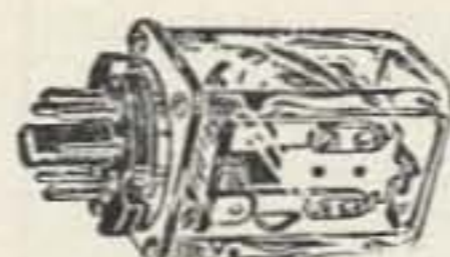


SIGMA: DPDT, 5 amp contacts, operation 1.5 volt dc or 12 v ac. DPDT Enclosed, plug-in \$1.00 ea.

6 for \$5.00

11/16" TELETYPE PUNCH TAPE Buy 2, save on shipping. **SPECIAL:** 6 cartons \$25.00 Carton 40 Rolls \$5.00

AN/ART-13 100-WATT XMTR
11 CHANNELS
200-1500 Kc
2 to 18.1 Mc

\$39

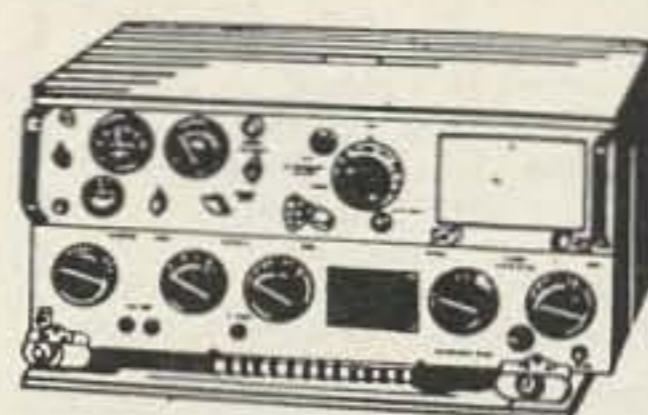

Collins Autotune Transmitter, extremely stable and suited for side band. Written up in QST Oct. issue 1953. Used, with tubes.

CQ's NEW Conversion Book \$3.00. Pages of surplus Conversions plus 3 articles on ART-13.

Meshna's new Winter catalog now ready. Send 20c for yours before they are all gone.

If enough Directors come to understand what we are facing they may possibly be able to communicate a sense of urgency to their paid management and get them to stop the deluge of actions which are so seriously hurting amateur radio. If they could but heal the deep wounds in IARU this would be a major step forward.

Executive Opening

The Institute of Amateur Radio, Inc., is looking for a full time Secretary to work at the 73 headquarters in New Hampshire and coordinate the activities of the Institute. He will be in charge of preparing mailings for Congress to keep our Senators and Representatives aware of the activities and value of amateur radio. He will investigate legal cases being fought by amateurs and help them with information and administer grants by the Institute to help fight important legal battles. He will work to implement the wishes of the Directors of the Institute. He will work to keep the membership informed through newsletters and the pages of 73.

This is one of the most important jobs in amateur radio today and the effectiveness of the man who takes on this job may have more influence on the future of our hobby than any

Rectifiers & Transistors

750 ma Silicon diodes "Epoxy" or "Top Hat"				Silicon Power Diode Studs			
PIV		PIV		PIV	3 amps	PIV	
50	5c	600	21c	25	6c	300	25c
100	7c	*700	25c	50	8c	400	28c
200	10c	*800	32c	100	14c	500	35c
400	14c	*900	40c	150	16c	600	40c
500	18c	*Top Hat only		200	22c	All Tests	

Full Leads, Tested, Guaranteed, American made

10 Watt Sil. Zener studs, 6-150v, any voltage	95c ea.
1 Watt Zener Diode Axial leads 6v-200v	50c ea.
Sil. diode stud 1500 PIV 300ma	50c ea.
18 Amp Stud Sil. Rect. 100 PIV	75c ea.
Hi-Voltage-Silicon epoxy diode, 2 1/2" x 3/8" x 1/2",	
Hoffman-3000 PIV-200ma.	\$1.49 ea.
Hoffman-6000 PIV-200ma.	\$3.49 ea.
Thermistor, glass bead, 1200 ohms, 600°F.	2/\$1.00
Sil. Power 2N174-\$1.95; 85 watts Transistor	

20 Watt Germanium (Internal Heat Sink)

2n1038	6 for \$1.00	2n1042	4 for \$1.00
2n1039	4 for \$1.00	2n1044	2 for \$1.00
261040	3 for \$1.00	2n1043	3 for \$1.00
2n1041	2 for \$1.00	2n1045	70c

Light Sensitive Power Transistor TO-3 Sent With Circuit Instructions \$1.95 ea.

150 Watt Germanium Power

2n250	2 for \$1.00	2n457A	80c
2n456A	70c	2n458A	90c
HF Sil. 2n702-100mc 40c; 2n703-150mc 60c			
Ger. Switching Transistors 2n 1300 series, assorted, tested, PNP or NPN 10 for \$1.00			
Philco Sil., NPN, 2N2479, new 2 for \$1.00			
IN429, 6v Zener 30c			
HF Silicon tetrode, 3N35-75c ea.			
Sil. diodes, IN200 series, assorted, new 15 for \$1.00			
Ger. diodes, glass, new 15 for \$1.00			
Nickel Cadmium Battery 9 1/2" oz. 2 3/4" x 3/4" x 4 1/2", 8 amp-hrs.-\$1.95 ea.			

Varicap-voltage variable capacitor-47 pf at 4v., 4:1 new \$1.25 ea.

12 different pots 2-4 W	\$1.00
80 assorted 1/2 W resistors	\$1.00
25 different power resistors to 50W	\$1.00
Money back guarantee, \$2.00 min. order, include postage, Catalogue 25c	

ELECTRONIC COMPONENTS CO.
Box 2902D Baton Rouge, La. 70821

The Amateur Radio Handbook

This fabulous hardbound 540 page handbook completely and thoroughly covers every aspect of amateur radio: tubes, transistors, receivers, transmitters, VHF gear, antennas, sideband, FM, mobile gear, noise, power supplies and much, much more. This handbook is a necessity of the building ham. Published by the RSGB. \$5.50

Radio Data Reference Book

Have you noticed a basic lack in your ARRL handbook? The RSGB Radio Data Reference Book supplies everything left out and far more. It contains all of the formulae you'll ever need in one hardbound book. Also contains complete design information on RF power amplifiers, pi nets, tanks, filters, antenna design charts, coil data, math, and a tremendous amount more. You need this one. \$2.25

Order 73 Magazine Peterborough, N. H.



CALL-LETTER SIGNS

Order your call in neat 2-inch die cut letters with base. Just right for the shack. You assemble—Letters: 3/32" silver showcard stock. Base: Satin finish black plastic. Price \$1.50 postpaid
GIFT SHOP
Box 73
Northfield, Ohio 44067

WOW

UNBELIEVABLE PRICES

6CW4 NUVISTOR \$1.40
TRANSMITTING, AMATEUR,
SPECIAL PURPOSE,
INDUSTRIAL TUBES !!

ALL BRAND NEW, INDIVIDUALLY BOXED, EIMAC, RCA, AMPEREX, ETC. NO PULLS, NO SECONDS, NO JAN. INDUSTRIAL QUALITY

FULLY GUARANTEED

6146 \$2.55 417A \$3.95 813 \$10.95

SEND FOR FREE CATALOG

Orders under \$5.00 include 50c handling. All shipments FOB Stirling, N.J. Include sufficient postage, excess refunded.

VANBAR

P.O. BOX 444
STIRLING, N.J. 07980

LOOKING? SHOPPING? TRADING? TRYING TO SAVE MONEY?

Write Bob Graham for Special Deals on New and Re-conditioned used gear. Cash or Budget.

Graham Radio

Dept. C., Reading, Mass.

Tel: 944-4000.



FT-243 Crystals

3000 to 8700 kc
\$1 each \pm 2 kc setting
\$2 each .01% tolerance

Air mail—10c per crystal extra

Denver Crystals
776 So. Corona, Denver, Colorado

other single person. This position should pay \$20,000 a year or more . . . no question about it. We are penny wise and pound foolish to try to put a boy in this man's job. But the Institute does not have backing of this magnitude at present so some compromise will have to be made. I suggest that this is an ideal job for a mature ham . . . one with good business background . . . possibly someone who is retired and doesn't need the higher income we don't have as yet. The Interim Directors of the Institute have agreed on a starting salary of \$5000 a year, a sum which does enable one to live quite comfortably up here in economical New Hampshire.

If you are interested in working for the good of amateur radio . . . if you have the background to get this job done and done well . . . if you are free to move up here . . . please send a resume to the Institute of Amateur Radio, Peterborough, New Hampshire.

Institute Wins

The other night I got a call from Mace Warner WØJRQ of Denver. He was just back from court and wanted everyone to know that he won his case . . . a case that, if lost, could have had serious repercussions for all of us. At the instigation of a neighbor, Mace was being sued for \$8000 because his tower and antenna were unsightly and devalued nearby properties. It should be mentioned that Mace lived there and had his antenna up before the suers moved into the neighborhood. There was no TVI involved in the case.

Mace was about at the end of his string, having spent close to \$2000 on attorney fees and costs, when the Institute of Amateur Radio came to his aid and provided \$500 which permitted him to carry the battle into the next court where he won the case. Mace said that he had given up hope and had about spent himself out when the Institute came along and gave him the incentive and backing to fight.

This is a real victory for ham radio . . . and a fine example of what the Institute can accomplish. How many of us are prepared to spend thousands of dollars to prevent a dangerous precedent from being set that could sweep hundreds of hams into trouble all over the country if lost? Battles like this should be fought with group funds . . . we all should pitch in to help in these fights which affect all of us. Only the Institute is carrying on this fight . . . have you joined yet?

Many amateurs are a bit hazy about amateur legal problems and believe that the League is active in supporting amateurs who

are fighting precedent cases. This is not true. The ARRL will on occasion provide legal advise to the lawyer that is on the case, but they will never and have never to my knowledge given one cent to help out the amateur that is in trouble. The Institute and *only* the Institute is sending cash money to help these court battles.

Calling Frequencies

Those of you who are on wide band FM or are thinking of it should give serious consideration to setting up on one national channel. FM nets have sprung up on a good many frequencies around the country . . . which makes it difficult for fellows who are travelling around. Why not make the change this spring to one standard calling frequency on each band? The most popular ones are 52.525 and 146.94 mc. If your nets are not on these channels why not send out for crystals now and get set up with everyone else. In this way visitors will be able to call in while nearby and you will be able to talk to FM'ers in other areas when you're driving around the country.

Need a New One?

If you happen to be prefix hunting you might look for 4U-ITU with numbers 1-6 being used in rotation so that one station can give you six prefixes on May 16-17. Frequencies will be 1810, 1830, 3503, 3797, 7003, 7045, 14113, 14292, 21050, 21400, 28050, 28625, kc and 145.1 mc. It is just possible that you may hear me operating from there if I can make it and if they'll let me in.

Reciprocation

The FCC called the other day to let me know that reciprocal agreements have been completed with Bolivia, Costa Rica and the Dominican Republic so far. They ask that aliens please not apply for permission to operate until an agreement has been signed with their country. Many more are in the works, I know . . . about 35, I believe.

Little Trip

During May I will be visiting Europe. If you know any hams over there that I should visit you might drop me a line with their address. I intend to say hello to as many VHF amateurs as possible as well as officials of the radio societies. My trip will start at Frankfurt and go to Stuttgart, Zurich, Geneva, Milano, Trieste, Zagreb, Budapest, Wein, Praha, Nuremberg, Hanover and Hamburg. I'll try to be on from 4U1ITU during their May 16-17th party.

. . . Wayne

VHF-UHF

Converters & Preamps.
50 thru 432 Mc.

Write for literature

Parks Electronics, Rt. 2, Beaverton, Ore.

EVER THOUGHT ABOUT BUILDING A TV CAMERA?? AFRAID OF THE COST?? TOO COMPLICATED?? YOUR PROBLEMS ARE OVER! Our brand new 1965 focus-deflection coil kit MODEL 65A now makes vidicon camera construction cheaper than ever! Kit includes: 2 vertical deflection coils, 2 horizontal deflection coils, 1 focus coil, 1 shielded target connector, 1 yoke form, aluminum and brass electrostatic shielding, mu-metal electromagnetic shielding and a set of easy-to-follow instruction. Included FREE with each kit is our newly published Vidicon Camera Construction Manual. This manual explains in easy-to-understand language complete details for building the worlds simplest 5 tube vidicon camera! This camera requires nothing but ordinary junkbox components. Order today! Don't delay! Complete kit with free manual only \$16.95 postpaid anywhere in U.S. and Canada.

ATV RESEARCH

Box 396

South Sioux City, Nebr. 68776

ARROW SPECIALS

PANADAPTER Convert this IP69C/ALA2 per June 1964 issue 73. New with tubes. **\$22.50**
Used with tubes. **\$17.50**
R19/ARC12 2 meter receiver—tunable 118 to 148 mc. Complete with 9 tubes. **\$29.95**
COLLINS RECEIVER R105/ARR15. 1500 to 18500 kc. Complete with 14 tubes. **\$47.50**
T271/ART28 420 mc transmitter **\$69.50**
APX6 TRANSPONDER 1296 mc less tubes **\$7.95**
COLLINS Single Side Band Multiplex Generator using mechanical Filter #F84Z-2 or similar **\$24.50**
T179/ART26 TV Transmitter Complete with all tubes **\$49.50**
NICAD BATTERIES BB 403—3½ AH **\$1.49**
AS 400—20 AH **\$2.95**
2C39A Tripler cavity—Less Tube **\$3.95**
ELECTRONIC GALVANOMETER Cohu Model 204 **\$175.00**
LM Navy Frequency Meter with original Book **\$47.50**
Q-5'er Navy Beam Filter **1.95**
TS226 Watt meter ideal for 150 mc and above **9.95**
MICROAMP Panel meter. GE 2½" square. 50-0-50 calib. 15-0-15 New **3.59**
100-0-100 microamp meter. 3½" round. Weston **5.95**
0-1 ma. 3½" round in oak box with lid etc. BE67. **4.95**
SCR Silicon controlled rectifier. GE C40B. 200 v 25A **3.75**
TOP HAT 600 PIV 200 ma **39c**
SELENIUM 36 v, 1 A Full wave **49c**
RTTY 1 193 Polar Relay Test Set. New **19.95**
RTTY 255A Polar Relay **2.95**
RTTY SSB Phone patch Line Transformer. GH-1203-2H **98c**
TRANSFORMERS 115 v 60 cy **6.95**
530-0-530, 420 ma **39.95**
2000-1500-0-1500-2000, 500 ma **49.95**
1900-0-1900, 3 amps. 220 v pri **3.95**
400-0-400, 175 ma plus 12 v, 3 A and 5 v, 3 A

Tubes		Tubes	
2C39 —	\$5.00	807 —	\$1.00
2E26 —	2.00	808 —	1.00
3B24 —	1.00	813 —	9.00
5R4GY —	1.00	815 —	2.50
6L6G —	1.00	832A —	4.00
4X150A —	6.50	416B —	5.00
		902PI —	\$3.00
		5763 —	1.00
		5894 —	12.00
		6146 —	2.00
		304TH-TL —	\$27.50
		866AX —	2.50

Send for Catalog #131 — FREE —


ARROW SALES-CHICAGO, INC.

2534 S. MICHIGAN AVENUE
CHICAGO 16, ILLINOIS

BUDDY NUVISTOR PRE-AMP

2M - \$9.95 6M - \$8.95

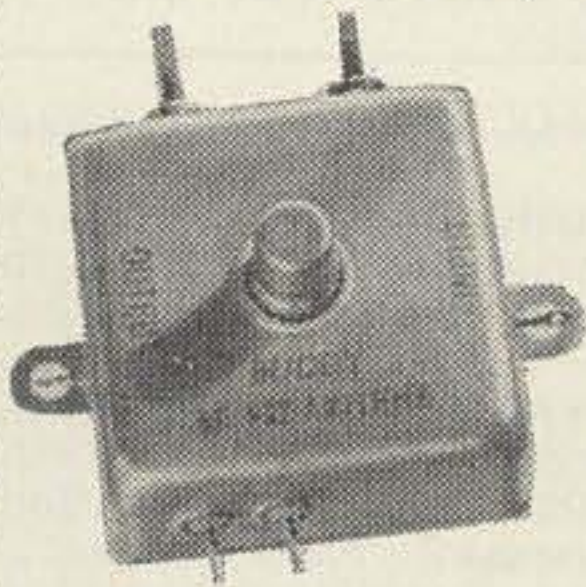- ★ Increases sensitivity up to 20 db.
- ★ Small size 2 x 2 7/8" fits anywhere
- ★ Completely wired and assembled



- ★ Reduces images
- ★ Improves selectivity
- ★ Simply installed
- ★ CB model \$7.95

Autronics Corporation
180 North Vinedo Avenue
Pasadena, California

ALL BAND TRAP ANTENNA!



Reduces Interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 600 Watts AM 1200 SSB PI-Net or Link Direct Feed. Light, Neat, Weatherproof.

Complete as shown total length 102 ft. with 96 ft. of 72 ohm balanced twinline. Hi-impact molded resonant traps. (Wt. 8 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Inconspicuous for Fussy Neighbors! NO HAY-WIRE HOUSE APPEARANCE! EASY INSTALLATION! Complete Instructions.

75-40-20-15-10 meter bands. Complete \$15.95
40-20-15-10 meter. 54-ft. (best for swl's) Complete ... \$14.95

SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Complete installation & technical instructions furnished. Free information on many other 160-6 meter antennas.

Available only from:

WESTERN RADIO • Dept. A7-5 • Kearney, Nebraska

MAY SPECIALS—POWER SUPPLY PARTS

Transformers, all primaries 117v 60 cycle.

2350v NOT C.T. 325 ma. cased, oil filled ceramic terminals. (30 LBS) \$15.00

900v C.T. 160ma (good for 200) potted cased, ceramic terminals (11 LBS) \$4.50

Pri 110. 120v. Sec. taps 0-800, 1000, 1200, 1400 & 1600 (or 1600 CT), 320 ma. open frame wire, color coded, leads. (26 LBS) \$10.00

Pri 110/120v. 750v CT (375-0-375) 170 ma; 6.3v CT 5A; 5v 3A. open frame, color coded wire leads. (8 LBS) \$3.75

Dual 2 1/2v CT 9A (good for 12A), 1750v RMS test. Cased, hypersile core, ceramic termin. (8 LBS) \$5.00

2-8 hry; 600-10 ma; 25 ohm; 3800v pkW. Cased, ceramic terminals. (13 LBS) \$5.50

5 hry; 225 ma; 80 ohm; 400 RMS (1000v) test. Cased, solder terminals. (7 LBS) \$2.25

OIL FILLED CONDENSERS. All rectangular case. 8 mfd 1500v DC \$3.75; 15 mfd 1000v DC* \$1.29; 10 mfd 1000v DC \$1.00; 4 mfd 600v DC 69c.

5 mf 1000v \$1; 6 mf 1000v \$1.25; 4 mf 1500v \$1.95

* take-outs-good. Others BRAND NEW.

SAVE YOUR LOOT. I'll have a wagon load of GOODIES at DeKalb, Ill. May 2; Rochester, N. Y. May 22; Pittsburgh, Pa. BREEZESHOOTER'S May 23.

All orders, except in emergency or I'm at a hamfest, shipped same day received. For free "GOODIE" sheet, send self addressed stamped envelope—PLEASE, PLEASE—include sufficient for postage & insurance. Any excess returned with order.

B C Electronics

Telephone 312 CALumet 5-2235

2333 S. Michigan Ave.

Chicago, Illinois 60616

CAVEAT EMPTOR?

- ★ Price—\$2 per 25 words for non-commercial ads; \$5 per 25 words for business ventures. No display ads or agency discount. Include your check with order.
- ★ Type copy on standard size paper. Phrase and punctuate exactly as you wish it to appear. No all-capital ads. Include your signature with order.
- ★ We can only accept ads related to ham radio. We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.
- ★ For \$1 extra and an SASE, we can maintain a reply box for you.
- ★ We cannot check into each advertiser, so Caveat Emptor . . .

GOLD—You will find a "Gold Mine" in our used equipment. Write for list. W9KP—Green Mill Radio Supply, 145 W. 111th St., Chicago, Illinois 60628.

QRT COLLECTING; Selling antique wireless items and other stuff. What do you want? Free lists. Send large stamped addressed envelope. W6LM. P. O. Box 308, Wrightwood, Cal.

CONVERTERS \$10 and up. World's largest selection of frequencies. Ham TV vidicon cameras and parts at low factory-direct prices. See them all now in our full page ad in this issue. Vanguard Labs, 190-48 99th Ave., Hollis, N. Y. 11423.

SONAR SRT-120P TRANSMITTER. 10-80 M, 120 watts, 100 watts phone, PPT, built-in power supply, 5984 final VFO-xtal. Excellent condition. Cost \$300. Will sell for \$100 complete. Box 151, 73 Magazine, Peterborough, N. H.

TELETYPE MODEL 30A PRINTER. Tiny light weight unit (19 lbs). Has 28 type keyboard, 115 vac motor, end-of-line indicator, aluminum case. Excellent condition. Just the thing for portable operation and demonstrations. \$90. Box 152, 73 Magazine, Peterborough, N. H.

WIDE SCREEN TV CAMERA AND 18" MONITOR. Made by Crimson Color, Inc. Model 700. Sells for over \$1000 new. Complete in excellent working condition. Like new with all cables, power supplies and manuals. \$649. Box 153, 73 Magazine, Peterborough, N. H.

SX-101A. Excellent condition. Cost \$445 new, asking \$275. Will consider any reasonable offer. Jim Coulter K8HKQ, 191 Union St., Hillsdale, Mich.

POLAR RELAYS-WE-255. New, only \$1.75 each postpaid. Teletype manuals—list available. National PWD gear drive—new, \$3.50 postpaid. Quaker Electronics, P.O. Box 215, Hunlock Creek, Pa.

KIT WIRING done by E.E. for fun and \$1 per hour. Top quality work, satisfaction guaranteed. Write Bob Groh WA2CKY, 9233 Main, Clarence, N. Y. 14031.

SELLING OUT MY ANTIQUE COLLECTION. tubes: VT-1 @ \$2.50. Your choice @ \$1.25: 00A, 01A, 12A, VT-5, Philco #2. Also W.E. 270A 500 watt antique triode, \$4.00. Crosley 1923 Trirdyn receiver exc. \$35.00. Samkofsky, 201 Eastern Parkway, Brooklyn, N. Y.

KNIGHT T-60 transmitter with 5 crystals. \$35. Jesse Bryant, Box 829, Haley Rd., Kittery, Maine.

BRAND NEW NCX-5, original carton with NCX-AC power supply. \$700. FOB N. Y. John Mrozinski WB2EXI, 155 Eckford St., Brooklyn, N. Y.

HE-74 VFO (new) \$25.00; Heath Tunnel Dipper (new) \$20.00; RF Panel, TR-SWR-SPKR-ANT-SW, 19" \$10.00 Money order to W4BEX 1828 Highland Avenue, Eau Gallie, Fla. 32935.

Over 3000 Sold in 3 Months! Not One Returned To Date!

JUMBO PAKS!

RADIO-TV PARTS BY THE POUND 500-1000 pcs. per pound


16 TONS of mfr's Over-runs

COMPLETE SATISFACTION—MONEY BACK GUARANTEE
1,000,000 PARTS SALE

- ONE POUND Disc CondensersWorth \$50, NOW
- ONE POUND Ceramic CondensersWorth \$85, NOW
- ONE POUND Discs & CeramicsWorth \$75, NOW
- ONE POUND Discs, Ceramics, Precisions..Worth \$70, NOW

\$4.88 per pound

85 WATT SILICON NPN

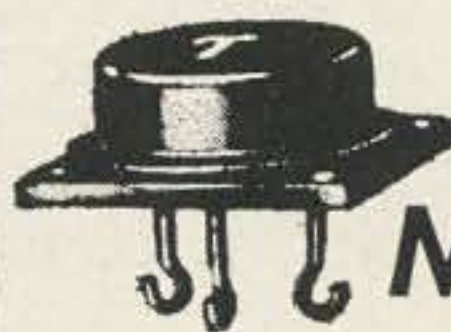

2N424
MESA
Just **1.25**

WORTH \$42.00

DOUBLE BONUS

\$25

WORTH OF TRANSISTORS RECTIFIERS RESISTORS CONDENSERS DIODES ETC

Add 25¢ for handling

BOTH FREE WITH ANY \$10 ORDER

PLUS CHOOSE ANY \$1.00 ITEM FREE

Poly Paks Exclusive TRANSISTOR JUMBOPAK



Power, Audio, RF, untested

100 for \$2.98

GERMANIUM DIODES 100 FOR \$1.03

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 25 AEROVOX CERAFIL COND, to .05mf. "TINY" \$1
- 5 NES1 BULBS, GE, mini bayonet. \$1
- 1 FILAMENT TRANSFORMER, 117 to 6.3vct, 3A. \$1
- 1—\$25 RELAY SURPRISE, sealed, tiny types. \$1
- 3 INFRA-RED DETECTORS, with leads. \$1
- \$25 SURPRISE PAK: transistors, rects, diodes, etc. \$1
- 40 PRECISION RESISTORS, 1/2, 1, 2W; 1% values \$1
- 30 CORNING "LOW NOISE" resistors, asst. \$1
- 60 TUBULAR CONDENSERS, to .5mf, to 1Kv, asst \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1KV. \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W. to 24 Kohms. \$1
- 50 MICA CONDENSERS, to .1mf, silvers too! \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! \$1
- 10 ELECTROLYTICS, to 500mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd. colors & styles. \$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 500mf \$1
- 50 COILS & CHOKES, if, rf, ant, osc, & more. \$1
- 35 TWO WATTERS, asst incl: A.B., 5% too! \$1
- 75 HALF WATTERS, asst incl: A.B., 5% too! \$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W, 1% & 5% values \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps. \$1
- 50 TERMINAL STRIPS, 1 to 8 solder lug types. \$1
- 30 SPRAGUE "YELLOW-FILM" MYLARS, asst. \$1
- 60 CERAMIC CONDENSERS, discs, npo's, to .05. \$1
- 40 "TINY" RESISTORS, 1/10W, 5% too! \$1
- 10 TRANSISTOR SOCKETS for pnp-npn transistors \$1
- 30 MOLDED COND'S, mylar, porc, black beauty. \$1
- 3 GEIGER COUNTER DETECTOR, tubes, assorted. \$1
- 10 LOGIC TRANSISTOR, toroid transformers. \$1
- 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1



FACTORY TESTED

SEMI-KON-DUCTORS

- 10 MICRODIODE STABISTORS, epoxy, silicon. \$1
- 2 2N706 500MW, 300MC NPN PLANAR, TO18 \$1
- 10 30-MC TRANSISTORS, w/shield, TO5, no test. \$1
- 5—2N155 TRANSISTORS, or equals, TO3 cases. \$1
- 3 10-AMP "CARTWHEEL" rects 100 to 600V. \$1
- 10 "PIN HEAD" TRANSTRS, 2N800, pnp, 10 mc. \$1
- 15 "QUICK-FIT" TRANSISTORS, rf, audio, TO5 \$1
- 2 25-AMP SILICON RECTIFIERS, 1-50V, 1-100V \$1
- 4 ZENER REFERENCES, 1N429, 6-volt, silicon. \$1
- 1 "TINY" 2N1613 2W, 100MC, TO46 case, npn \$1
- 2 500MC TRANSISTORS, 2N964, mesas, pnp, TO18. \$1
- 4 PIN HEAD 2N790 NPN SILICON transtrs, TO18 \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4 2N333 NPN SILICON transistors, by GE, TO5 \$1
- 10 2-6Amp RECT's, studs, silicon, 50 to 400V. \$1
- 1 25-AMP SILICON CONTROL RECT, 100 PRV. \$1
- 2 4-WATT PLANAR TRANSISTRS, 2N497, 2N498. \$1
- 4 2N35 TRANSISTORS, npn, by Sylvania, TO22. \$1
- 4 "MICRO" TRANSISTORS, 2N131's, 1/16", rf. \$1
- 4 CK721 TRANSISTORS, pnp, aluminum case. \$1
- 3 TRANSITRON TRANS'TRS, 2N341, 42, 1W, npn. \$1
- 3 "TEXAS" 20 WATTERS, 2N1038—1042, w/sink. \$1
- 4 2N170 TRANSISTORS, by GE., npn for gen'l rf. \$1
- 6 TRANSISTOR RADIO SET, osc-ifs, driver-pp. \$1
- 25 GERMANIUM & SILICON DIODES, no test. \$1
- 25 TOP HAT RECTIFIERS, silicon, 750ma, no test. \$1
- 25 EPOXY RECTIFIERS, silicon, 750ma, no test. \$1
- 5 30MC TRANSISTORS, like 2N247, Sylvania. \$1
- 15 TEXAS PNP & NPN TRANSISTORS, no test. \$1
- 1 3N35 TETRODE, 150mc transistor, silicon. \$1
- 10 PNP SWITCHING TRANSISTORS, 2N1305, TO5 \$1
- 10 NPN SWITCHING TRANSISTORS, 2N338, 440. \$1
- 15 PNP TRANSISTORS, CK722, 2N35, 107 no test \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test. \$1
- 30 TRANSISTORS, rf, if, audio, no test, TO5. \$1
- 4 35-W. TRANS'TRS, 2N1434, CBS, TO10, stud. \$1
- 10 1000-MIL "CERAMIC" RECT. silicon, 50-400V. \$1
- 10 POPULAR CK722 TRANSISTORS, pnp, no test \$1
- 5 2N107 TRANS'TRS, by GE, pnp, pop. audio pak \$1
- 1 40W. 2N1648 TRANS'TR silicon mesa, 80BVolts \$1
- 10 ZENERS, GLASS SILICON DIODES, axial, leads \$1
- 6 2N408 TRANSISTORS, TO1, pnp, driver. \$1
- 2 2N718 NPN SILICON PLANARS, by Fairchild \$1
- 4 2N219 TRANSISTORS, mixer-conv, TO22. \$1

TESTED TRANSITRON

PRV	Silicon SCR's		
	7 AMP	15 AMP	25 AMP
50	1.00	1.25	1.50
100	1.50	1.95	2.25
150	1.75	2.25	2.75
200	1.95	2.75	2.95
250	2.25	2.95	3.25
300	2.69	3.19	3.50
350	2.95	3.50	4.25
400	3.25	3.95	4.50

10 WATT ZENERS

<input type="checkbox"/> 5V	<input type="checkbox"/> 1.00
<input type="checkbox"/> 6V	<input type="checkbox"/> Each
<input type="checkbox"/> 12V	<input type="checkbox"/> 70V
<input type="checkbox"/> 14V	<input type="checkbox"/> 80V
<input type="checkbox"/> 20V	<input type="checkbox"/> 90V
<input type="checkbox"/> 24V	<input type="checkbox"/> 100V
<input type="checkbox"/> 42V	<input type="checkbox"/> 110V
<input type="checkbox"/> 45V	<input type="checkbox"/> 124V
<input type="checkbox"/> 60V	

10¢ GIANT SPRING CATALOG ON: PARTS REC-TIFIERS TRANSISTORS SCR'S ZENERS

POLY PAKS

TERMS: Send check, money order. Add postage—avg. wt. per pak 1 lb. Rat'd net 30 days. COD 25% deposit.
P.O. BOX 942A
SO. LYNNFIELD, MASS.
"PAK-KING" of the world

3-TRANSISTOR SUBMINIATURE

AMPLIFIER NOW \$1.00 ONLY
★ Only 3" x 2" x 3/4" ★ Wired
★ Printed Circuit ★ Complete with Transistors

HW12-22-32 OWNERS

Convert your rig to a triband transceiver for a total cost of \$25! Look at these specs:

- ★ 200 watts PEP SSB plus 170 watts CW
- ★ Three bands: 14.00-14.35, 7.00-7.35, 3.70-4.00 mc
- ★ Selectable sidebands. Selectable AVC
- ★ Self contained for fixed or mobile with neat appearance
- ★ Other specifications same as original transceiver
- ★ Average construction time—4½ hours

For complete step by step instructions with 17 pictorials and a complete parts list with catalog stock numbers and prices, send \$5 to

Tribander
c/o Robert Christie
88-15, 168th Street
Jamaica, N.Y. 11432

Patent applied for.

Add 50c outside continent.

GUARANTEED RECONDITIONED



HAM GEAR

WRITE NOW
FOR MONTHLY
FLYER.

Phone: (415)
DI 2-5757

ELECTRONICS

999 HOWARD AVE-BURLINGAME, CAL.

FREE Catalog

OF THE WORLD'S FINEST
ELECTRONIC GOV'T
SURPLUS BARGAINS



HUNDREDS OF TOP QUALITY ITEMS—Receivers, Transmitters, Microphones, Inverters, Power Supplies, Meters, Phones, Antennas, Indicators, Filters, Transformers, Amplifiers, Headsets, Converters, Control Boxes, Dynamotors, Test Equipment, Motors, Blowers, Cable, Keyers, Chokes, Handsets, Switches, etc., etc. Send for Free Catalog—Dept. 73.

FAIR RADIO SALES
2133 ELIDA RD. • Box 1105 • LIMA, OHIO

RW MAY BARGAINS

- OIL CAPACITOR**—25 MFD, 2500VDC, ceramic insulators. Xlnt S.S.B. xmtr power supply output filter. Westinghouse, 8" x 4" x 14" H. Brand new. **\$12.95**
- HIGH VOLTAGE PROBE**—Rated to 50KV with VOM or VTVM. Has 500 meg Hi voltage resistor. A Large quality probe that sells for over \$12.00. Brand new. **\$2.95**
- L&N KELVIN-VARLEY PRECISION VOLTAGE DIVIDER**—20K ohms. Ratio 1:10,000, accuracy 0.01%, with 100ua galvanometer. Ship. wt. 37 lbs. Used good. **\$49.50**
- POWER TRANSFORMER STEP DOWN**—24V. @ 10A. with F.W. Bridge or 12V @ 20A. with F.W. center tap rectifier. Double shell, wire leads. Brand new. **\$6.95**
- ARR-2 RECEIVER**—234 to 258mc w/11 tubes, schematic & conv. data for CB & 2 meters. Used good. **\$5.95**
- LAZY MAN'S Q-5er**—Navy Beam Filter, 100 cycle band-pass. Single signal selectivity the easy way—just plug it in! New. **\$2.49**
- MAST BASE & 33' VERTICAL ANTENNA**—Rugged MP-49 mast base 3" x 16½" H with 11 antenna mast sections MS-53 & MS-52. Self supporting to 18'. Ship. weight 24 lbs. Brand new. **\$6.95**

WRITE FOR BULLETIN #40—LOADS OF BARGAINS

Send Check or Money Order—Minimum Order \$2.50
PLEASE INCLUDE AMPLE POSTAGE—EXCESS REFUNDED
Minimum C.O.D. Order \$10.00 with 25% Deposit.

R. W. ELECTRONICS, INC.

2244 South Michigan Ave.
Chicago, Illinois 60616

Dept. 735
Phone CALumet 5-1281

FM RECEIVERS AND TRANSMITTERS for 2 m, 6 m and 432 mc bought, sold and exchanged. Motorola, GE, RCA, etc. Ray K8TJP, 2670 Pinetree, Trenton, Michigan. Phone 676-7460.

HEATH MARAUDER and Hallicrafters SX 111—\$550. Homebrew 2 KW linear with all attachments—\$150. Heath HG-10 VFO—\$30. General purpose scope—\$30. J. Michlin WA2WPN.

7TH ANNUAL PENN-YORK HAMFEST. Morrison's Restaurant, Big Flats, N. Y. (Between Elmira and Corning, N. Y.) June 19th, 12 noon. Grand award NCX-3 SSB Transceiver. Preregistration \$4.50-\$6.00 at door. Send SASE to Earl J. Foster W3BKF, Chairman, RD #2, Gillett, Pa. Last day for pre-reg June 12th. Speakers, swapfest, contests, etc. Smorgasbord dinner, all you can eat. Only 600 tickets available.

KISHWAUKEE RADIO CLUB SWAPFEST Sunday, May 2 at DeKalb, Illinois. Contact Alton L. Brand, 415 E. Sycamore St., Sycamore, Ill.

FT-243 CRYSTALS: \$1 each for 2 kc accuracy, \$2 for 0.01%. Air mail 10c extra each. Denver Crystals, 776 South Corona, Denver, Colorado 80209.

TRI-STATE ARA annual picnic. Camden Park, US 60 West, Huntington, West Virginia. 12 noon to 6 on Sunday June 6th. Displays, surplus, swap. Contact W8VA at 2937 Auburn Road, Huntington, W. Va.

FRESNO ARC HAMFEST. Saturday May 15. More information from Carl Massie WA6ZVY, P. O. Box 783, Fresno, California.

MISSISSIPPI VALLEY HAMFEST sponsored by the Quad City ARC at the Indian Bluff Forest Preserve near Milan, Ill. Wide variety of activities for hams and their families. Starts at 9 AM. For more information write W. M. Coopman K9CHZ, 911-23rd Ave., Moline, Ill.

HAM AUCTION, May 3. Check gear in at 6 pm, auction at 8. River Park ARC, 5100 North Francisco Avenue Chicago, Ill.

BIRMINGHAMFEST. Sunday, May 1st and 2nd. More dope from Mike Thomason K4FQF, Box 603, Birmingham, Ala.

EASTERN WISCONSIN HAMFEST. Sponsored by the Ozaukee RC on May 15, Get more information from Harvey Goldberg, Box 13, Port Washington, Wisconsin.

SWAP FIESTA. Sponsored by the El Paso ARC. May 15 and 16 at the Mall of Bassett Center in El Paso. More information from Hurley Saxon K5QVH, 1501 Golden Hill Terrace, El Paso, Texas.

MOULTRIE ARK Hamfest. Sunday, April 25. Lynn Cunningham, 904 West Jackson, Sullivan, Illinois.

FREE! BLUE BOOK LIST. Leo offers hundreds of bargains on reconditioned gear. Viking II \$97.70; NC300 \$189.00; Collins 62S-1 \$625.50; King 500A \$259.00; SP600 \$296.65; Heath MRI \$59.46; DX-40 \$40.50; Cheyenne \$49.18; SX-140 \$72.15; SX-101 \$160.65; HQ140XA \$134.10. Many more. Also, free 1965 catalog. WØGFQ, WRL, Box 919, Council Bluffs, Iowa.

RCA VTVM WV77E \$20. Simpson #215 VOM \$12. RCA audio generator 30-15000 cy. \$15. ART-13 \$25. FOB W6IIA, Jack Tate, 425 Tufts Avenue, Burbank, California. 91504.

HT-44 and matching PS-120/150. Like new. Original cartons, manual. 200 watts SSB, CW AM. Asking \$375. Gray W2EUQ, Painted Post, N. Y.

HEATH HX-10 transmitter, \$250. Hammarlund HQ145C receiver \$175. J. Deithloff, 401 Lake Street, Bryan, Texas.

DRAKE 2B-AQ speaker like new, \$205. BC-453 Q5'er, New \$18.95. New transmitters BC458A, \$8.95. BC459A, \$12.95. New 829B's \$7.95. FOB W9KAJ, Box 55A, Rt. 2, Delavan, Wisc.

CLEANING SHACK. Low and medium power VHF transistors (other types also) at low prices. Send for list. Jack Pritchard, 4336 Livingston, Dallas, Texas, 75205.

GONSET COMMUNICATOR 111 6 METERS. Will sell for \$140.00 or trade for 2 mtr. gear. Will ship. K9YCA 64357 Pine Road, North Liberty, Indiana 46554.

CASH, SONY TRANSISTOR TV's etc., swapped for G-R, H-P, L&N etc. laboratory equipment, special tubes, manuals, military electronics. ENGINEERING ASSOCIATES, 438 Patterson Road, Dayton, Ohio 45419.

COLLINS KWM-2, 516EL & PM-2 Power Supplies, Mosley automatic 5 band mobile antenna TM-5, portable Gote-Tenna & case. New cost \$1,847. Will sell for \$1,200. All in excellent condition. Call Manchester, N. H. evening 472-3641 or address W1ACC P. O. Box 808, 1217 Elm St., Manchester, N. H.

NCX-3 with NCX-A, used only few months, perfect condition, \$300. Heath Sixer and Twoer, 4 xtals with each, both \$65. New B&K Dynamatic 375 VTVM, warranty card, cost \$90, sell \$55. All with original accessories and manuals. W3PQK, 615 Market St., South Williamsport, Pa. 17707.

PRECISION COAXIAL TERMINATIONS—Extremely low VSWR from d-c to 1300 mc. Many uses. Send for brochure PTC-1. Radiation Devices Company, P. O. Box 3450, Baltimore, Md. 21234.

SCHEMATICS—of transistorized receivers, transmitters, converters, etc. Send 10c and self addressed stamped envelope for list to: COMMUNICATION INSTRUMENTS CO., Box 466, Yorba Linda, Calif.

MODEL 28 KSR TELETYPE—Mint Condition. John R. Niehaus, 208½ Church Street, Doylestown, Ohio 44230.

SIXTH ANNUAL GREENVILLE HAMFEST will be held Sunday May 2, 1965, at the Greenville County Fairgrounds, Greenville, S. C. Complete program for the family. Plenty of shelter space in case of bad weather. Lunch included in admission price. Information from Don Robertson, WA4KLT, 101 Grin Drive, Greenville, S. C. Sponsored by the Blue Ridge Radio Society.

TOROIDS, uncased, removed from space age surplus. 1.0 Hy .83 Hy .25 Hy 50c ea. Lock City Electronics R.1, Sault Ste Marie, Michigan.

WANTED, all types, Military, Commercial, Airborne, Ground, Electronics Items-Testsets, GRC, PRC, COLLINS, Bendix, Others—We pay Freight. RITCO Box 156, Annandale, Virginia.

UNITS 6, 8, 9, 10, 11A, 11B, SRT14 Synthesizer, New less tubes. Schematic Unit 6 only—\$8.00 ea. 3 for \$20.00. RITCO Box 156, Annandale, Virginia.

Z-201 First I.F. Amplifier for R423/ARW56 by Collins—\$9.5 to 98.5 MC. 1 MC Steps Input 24.9 MC output—NEW with tubes \$4.00. RITCO Box 156, Annandale, Virginia.

TELETYPE (TYPEWRITER) RIBBONS—Black, New-boxed, all models except 28, also many typewriters, 75 ea—5 for \$3.00—Dozen \$5.00—Postpaid. RITCO Box 156, Annandale, Virginia.

DRAKE 2B, 2BQ, xtal Cal., Mint cond., \$200.00, shipping extra, also HX 11, CW xmtr \$35.00. Omer Robbins, 13205 Byers Rd., Grandview, Mo.

HA-6 HALLICRAFTERS SSB/AM/CW TRANSVERTER, HA-2 Converted to 220 mc, both with added voltage regulation for improved stability, AMECO Nuvistor preamps added under chassis, premium quality, first \$150 each. Power Supply P-26 \$45, manuals. SSB rig HB 80-10 Meters \$50; unusual VHF/UHF 50 thru 4000 mc and other gear including 100 Watt Varactors, stamp for list W4API, Box 4095, Arlington, Virginia 22204.

SIX METER COMMUNICATOR III, Good, \$125. DX-40, built-in antenna relay, \$30. DSB-100 (Sideband) converted to six meters, \$35. KØMVR, 424 Twentieth Street N.E., Cedar Rapids, Iowa.

SONAR 20M SSB/CW transceiver with matching AC pwr supply. 200w PEP & full 20m coverage. In good cond. \$180. S. Weinrich WA2QKC, 1407 Linden Blvd., Brooklyn 12, N. Y.

RANGER ONE \$75. Ranger Two \$175. Bill Witsman, K9TMA 23W511 Bryn Mawr Ave., Roselle, Illinois.

ANTENNAS! Mosley TA-33, \$45.00; Hy-gain 12AVS, roof mount, extra traps, \$18.00; Saturn Six halo with bumper mount, \$10.00; Albert Johnson K11IK, Pinnacle Road, Newport, N. H.

THE BEST WAY TO BUY SURPLUS:

Ask for what you need. We will then send you **COMPREHENSIVE DATA** on what we have to meet your needs. **DON'T** ask for a catalog . . . it would take a fat book . . . and then it would give you less details about the thing you are interested in than we will give you in answer to your letter. Be as specific as possible as to frequency, power needed, etc.


For example, we have **THIRTY DIFFERENT MODELS** of calibrated-output laboratory-grade Signal Generators ranging from 10 kc to 21,000 mc, and some with power outputs over 10 watts for R.F.I. work, etc. Some FM, some PM, some CW and/or AM.

We have Meters, VTVM's, Bridges, Galvos, Voltage Dividers DC and AC, Digital Voltmeters DC and AC, Counters, Pulse Generators and Delay Systems, other Frequency Meters than those mentioned above, wide variety of Regulated Power Supplies, Line Voltage Regulators from ½ to 10 KVA, Tektronix and other Oscilloscopes, scope Cameras, many types of Graphic Recorders, Spectrum Analyzers, Teletype, Tuning-Fork-controlled Oscillators, Direction Finders, FM Ground Station, Tube Testers, Noise & Field Strength Meters, Ultrasonic generators and test gear, Aeronautical Radio Test Gear, etc. etc. and etc. . . . and we **KEEP BUYING NEW MATERIAL ALL THE TIME!** Just got in some laboratory Calorimeters, a few Magnetometers, a high-vacuum pump, and even a shipboard Rangefinder and two complete Submarine Periscopes! Much material is here today and gone tomorrow, but we keep a lists of **WANTS** and will notify you if the item you need gets acquired.

We **DON'T** sell mdse the way we get it in just to be able to advertise at a price lower than someone else's. We work it over . . . test it . . . overhaul and calibrate it . . . and **GUARANTEE SATISFACTION OR MONEY REFUNDED!**

WE ALSO BUY so if you have anything to sell, tell us about it and how much you want for it. When we answer your inquiries and describe material we are offering, we also price it. . . . You wouldn't think very much of us if we asked you to make us an offer!

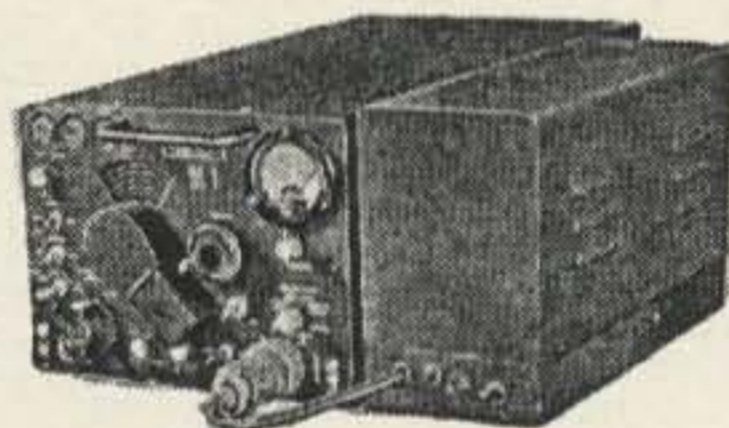BROADCAST-BAND COMMAND RECEIVER: ARC Type 12, No. R-22. Late type! 540-1600 kc, 6 tubes: RF, converter, 2 IF's & AVC, det. & Noise Limiter, & AF. 2 uv sensit. Needs external pwr sply & control ckts & has no tuning dial. With spline tuning knob, chart to tune exact freq. by turns count, lots of tech data, OK **17.95** grtd. 9 lbs. FOB Los Angeles (Add \$3 for extra-clean selected unit.)



ALL-BAND SSB RCVR BARGAIN: Hallicrafters R-45/ARR-7. 550 kc to 43 mc continuous: Voice, CW, MCW: 2 RF's. 2 IF's: S-meter: 455 kc Xtl. 6 select. choices. Ready to use. w/60 cy pwr sply & book. aligned. fob Los Angeles **199.50**

Deduct \$30 if you make your own pwr sply from schematic we furnish. Deduct \$20 if SSB not required, or deduct \$15 if you will wire in your own SSB with kit & diagram we furnish.

TIME PAY PLAN: Any purchase totaling \$160.00 or more, down payment only **10%**

ARC-5 Q-5'er Rcvr 190-550 kc w/85 kc IF's. Use as 2nd converter for above or other rcvrs. Checked electrically. w/lots of tech. data. w/spline knob. 9 lbs. fob Los Angeles **14.95** (Add \$3 for extra-clean selected unit.)

AC PWR for SCR-522: RA-62-B made by Signal Corps for the specific job! 115/230v, 40 60 cy in. Regul. & flt. outputs 300v, .26A; 13v, 4A; -150v. 10 ma. OK **29.95** grtd, w/data, 90 lbs. fob Sacramento

AN/APR-4 RECEIVING UNIT w/tuning units to tune 38-1000 mc plug & handbook. all checked & grtd 100% OK, ready to use on 60 cy fob Los Angeles **179.50**

Add \$30 for am/fm version modified for 60 cy pwr input: add \$60 for TN-19, 975-2200 mc; add \$125 for TN-54, 2175-4000 mc. All uncond. grtd. OK.

LM FREQ METER 125 kc to 20 mc is combin. heter. freq. meter & signal source. CW or AM, accuracy .01%. xtl callb. Clean, checked 100% grtd. w/plug, data. **57.50** 16 lbs fob Los Angeles

Add \$10 for EAO, converts for LM Power Supply w/parts, data. included 47 lbs fob San Diego

TS-323/UR, 20-480 mc. Crystal. 001%. W/handbook supplement giving supplementary xtl check points & instruct. closely approach crystal accuracy. W/schematic, instruct., pwr sply data, clean, checked. 100% grtd. fob Los Angeles **199.50**

R. E. GOODHEART CO., INC.

Box 1220-GC BEVERLY HILLS, CALIF. 90213

Phones: Area 213, office 272-5707, messages 275-5342.


ARC-1 Transceiver. 100-156 mc with tubes. Less dynamotor. Good used. Special. FOB **\$19.00**
 APX-6 1215 mc Transponder. Door section only, with RF and IF sections. With tubes. Good used. FOB **\$10.00**
 3E29 tubes. Checked. **\$ 4.00**
 3BP1 CRT tubes. New **\$ 2.49**

All items FOB Cleveland, Ohio
 Send for catalog of surplus and amateur gear.

JEFF-TRONICS

4791 Memphis Ave. Cleveland, Ohio 44109

HYE-QUE ANTENNA-FEEDLINE CONNECTOR

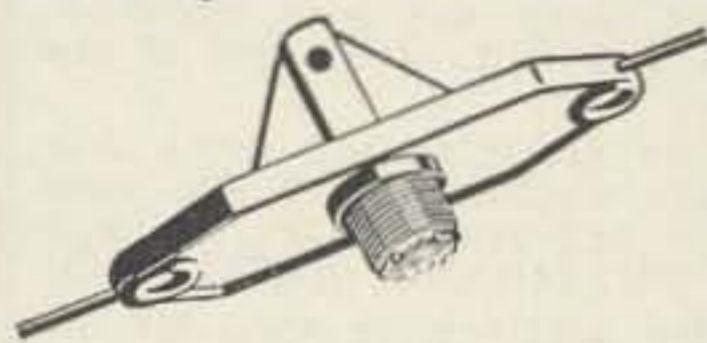

New 3-in-1 molded plastic-and-metal fitting provides: coax feeder connection, heavy copper leads to elements, antenna center support. Hye-Que 1 Connector fits standard PL259. Reinforced, weather protected, ultra-efficient. At your ham store, or \$2.95 ppd. Companion insulators, 2 for 99c ppd. Includes complete instructions.

BUDWIG MFG. CO., P.O. Box 97, Ramona, Calif. 92065

RTTY DUAL FREQUENCY SHIFT TONE CONVERTER

Northern Radio type 152, less frequency determining networks. Use 88 mh toroids. Each tone converter unit is self contained including power supply. 110-220 v, 50-60 c, 1 phase. O/A dimensions. 17" x 3 1/2" x 19". Complete with tubes and cables. Used excellent. **\$50.00**

RTTY DUAL FREQUENCY SHIFT TONE KEYS

Northern Radio type 153, less network. Use 88 mh toroids. Each tone keyer is self contained including power supply. Specs and size same as 152. Complete with tubes, cables and instruction book. New in original case. **\$50.00**

Teletype synchronous motors for 14 and 15 teletypewriter and for T.D.s with fan-base and plate. Used excellent. **\$10.00**

Send for catalog of teletype equipment.

ATLANTIC SURPLUS SALES
 250 COLUMBIA STREET, BROOKLYN, N. Y. 11231

RADIO TELETYPE EQUIPMENT

Teletype Models 14, 15, 19, 20, FRXD, 28, Kleinschmidt printers. Boehme CW keyers. Radio Receivers Collins 51J-3, 51J-4, R-390, R-390A, R-391, Hammarlund SP-600JX. Frequency Shift Converters.

ALLTRONICS HOWARD CO.

Box 19, Boston, Mass. 02101 Tel. 617-742-0048

**AMERICAN
MADE**

TRANSISTORS


WHILE LIMITED
QUANTITY LASTS



4¢

SPECIAL LOW PRICE ONLY

Each

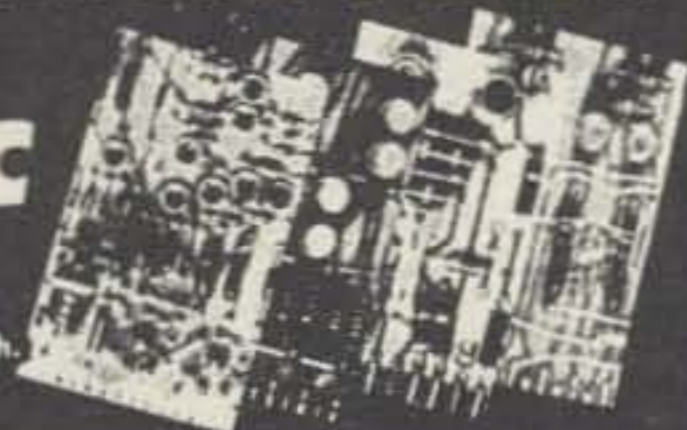

A fortunate purchase allows us to offer these high priced computer grade transistors at such ridiculously low prices. All are mounted on printed circuit boards along with assorted components such as resistors, capacitors and a host of other surprises. You pay only for the transistors, other parts are FREE!

BUY 100 FOR \$4.00 or 1000 FOR \$35.00 PREPAID

... NOW TAKE ADVANTAGE OF THIS SPECIAL PRICE

SEND YOUR ORDERS TO **ALCO** LAWRENCE, MASS.

SWAN 350, two months old, including A.C. supply and new VOX accessory \$490; Heathkit Twoer \$40; Twoer D.C. supply \$15; Webster Top Sider mobile antenna \$11; 75 meter coil \$4; 40 meter coil \$4; 20 meter coil \$3; \$550 takes all or will trade for perfect Heathkit SB-300 and SB-400. All equipment barely used, absolutely perfect in original cartons. FOB Bill Siefkin WB6KEH, 603 Johnson #4, San Luis Obispo, California; 805-543-9890 evenings, weekends.

ART-13's Several unmodified ART-13's without the 811 and 811's for sale. Only \$16 each. Sorry I can't ship. Write first to: Bob Fairfield, WA6EOB, 1782 Industrial Way, Los Angeles, California, 90023.

MINIATURE 10K surplus plate relays, DPDT with sockets. Have 50 only. \$1.50 each postpaid. R. G. Crouse, W7GJS, 2724 West Peninsula, Moses Lake, Washington.

CLEGG INTERCEPTOR VHF receiver in mint condition. \$200 firm FOB New Jersey. Glenn C. Ward, WA2KZF, RFD 1, Stanhope, N. J.

COLLINS S LINE: 75S3, 32S1, 516F-2, 30L1. Extra clean gear, will trade for 63 or 64 automobile or station wagon. Transtenna 102A, \$\$\$38. WA4LXX. 251 Collier Avenue, Nashville, Tenn. 37211.


COME TO THE BIG 73 HAMFEST. Sunday, July 4th, Peterborough, N. H. Fun for everyone. See page 101.

KILOWATT SSB station with complete antenna system. Station includes Heath SB-300, SB-400, SB-200, HM-11, HO-13, Astatic D-104C. Write for details. W9FMW, 1567 Southfield Road, Evansville, Indiana.

GONSET COMMUNICATOR III-6, microphone, cords, book, \$155.00. Heath Sixer with 12v supply, \$35.00. Both excellent. Dan Rogers, 3012 Battersea Lane, Alexandria, Virginia 22309.

CLEGG ZEUS & INTERCEPTOR \$500 for pair. Worth more than that just to admire. Perfect condition. G. McDowell W7UB, 2455 SW Montgomery Dr., Portland, Ore.

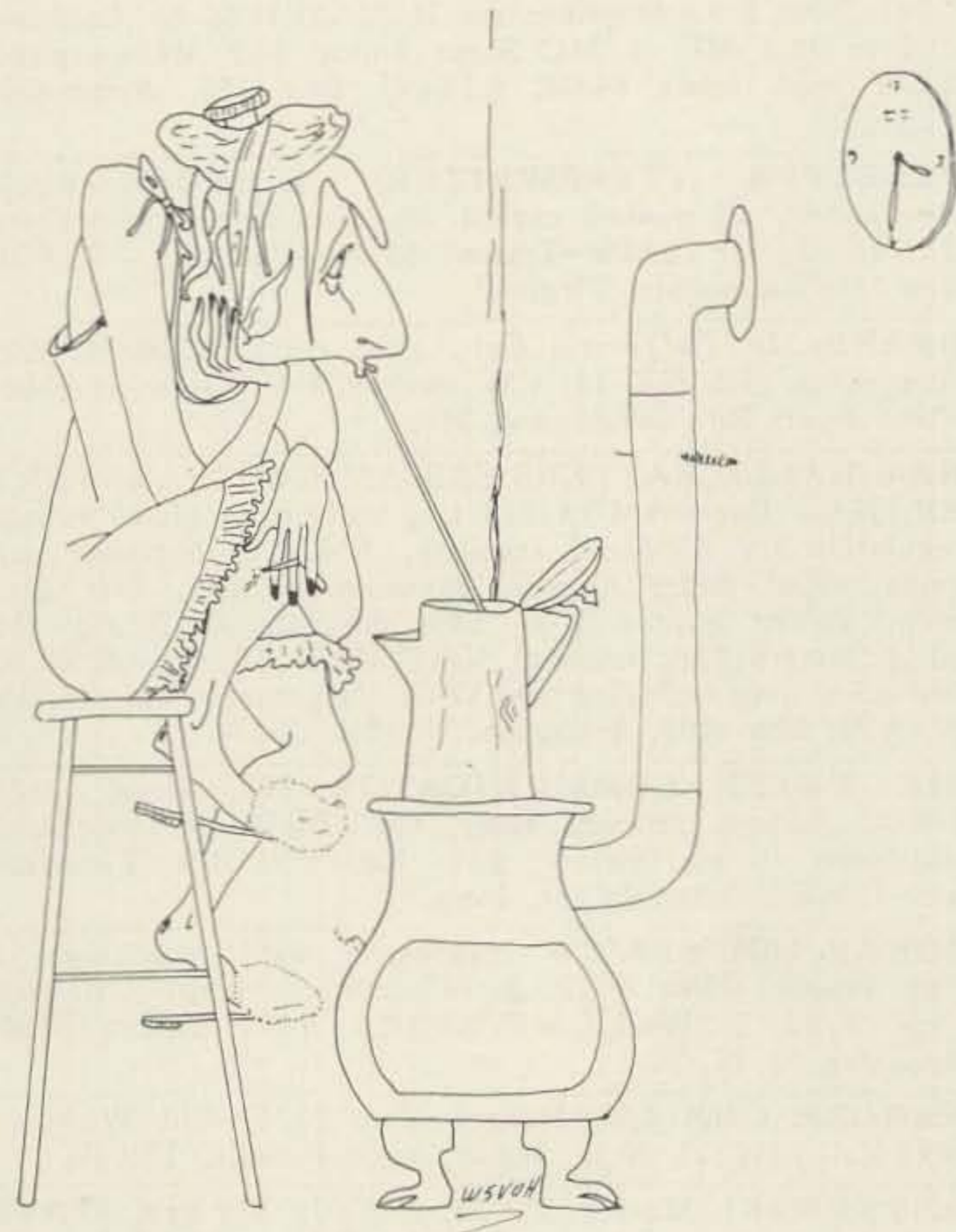SELLING OUT!!—DX-40 xmtr with Eico 730 modulator and VF-1 vfo, \$100. NC-270 rcvr, \$165. All mint condx with manuals. Raymond Secrest, Box 102, Pleasant City, Ohio.



Walt, Baby, these DX contests sure are playing hell with our togetherness.

"TAB" * TRANSISTORS * DIODES!!
GTD! FACTORY TESTED —
FULL LEADS.

PNP 100Watt/15 Amp HPower
 T036 Case! 2N441, 442, 277,
 278, DS501 up to 50 Volts/
 VCBO \$1.25 @, 5 for \$5.
 2N278, 443, 174 up to 80V
 \$3 @, 2 for \$5.



PNP 30 Watt, 2N155, 156, 235, 242,
 254, 255, 256, 257, 301, 392, @ 35c, 4 for \$1
 PNP 2N670/300Mw 35c @, 4 for \$1
 PNP 2N671/1Watt 50c @, 3 for \$1

PNP 25W/TO 2N538, 539, 540, 2 for \$1
 2N1038 6/\$1, 1039 4/\$1, 1040 \$1
 PNP/TO5 SIGNAL 350Mw 25c @, 5/\$1
 NPN/TO5 SIGNAL IF, RF, OSC 25c @,
 6 for \$1

Silicon PNP/TO5 & TO18 25c @, 5 for \$1
 2N1046/\$1.40 @, 3/\$4. 2N1907/\$2 @, 4/\$6
 Power Heat Sink Finned Equal to 100
 Sq" Surface \$1 @, 6 for \$5
 TO36, TO3, TO10 Mica Mtg 30c @, 4/\$1
 Diode Power Stud Mica Mtg 30c @, 4/\$1

ZENERS 1Watt 6 to 200v 70c @, 3/\$2
 ZENERS 10Watt 6 to 150v \$1.45 @, 4/\$5
 ZENER Kit Asstd up to 10w 3 for \$1
 STABISTORS up to 1watt 5 for \$1

TRANSISTORS—TOO MANY! U-TEST

Untested Pwr Diamonds/TO3 10 for \$1
 Untested TO36 up to 100Watts 3 for \$1
 Untested TO5/SIGNAL/sistors, 20 for \$1
 Untested Power Diodes 35 Amp 4 for \$1
 Untested Pwr Studs up to 12Amp 12 for \$1

D.C. Power Supply 115v/60 to 800
 Cys. Output \$30 : Tap 165V up to
 150Ma, Cased \$5 @, 2 for \$9

SILICON POWER DIODES * STUDS

DC AMP	50Piv 35Rms	100Piv 70Rms	150Piv 105Rms	200Piv 140Rms
3	.08	.14	.17	.24
12	.30	.55	.70	.85
18*	.20	.30	.50	.75
35	.70	1.00	1.50	2.00
100	1.65	2.05	2.50	3.15
240	3.75	4.75	5.75	8.75

DC AMP	300Piv 210Rms	400Piv 280Rms	500Piv 350Rms	600Piv 420Rms
3	.29	.30	.40	.48
12	1.00	1.35	1.45	1.70
18*	1.00	1.50	Query	Query
35	2.15	2.45	2.75	3.35
100	3.75	4.60	5.50	8.00
240	11.70	17.10	23.94	29.70

P.P. PRESS-FIT AUTOMOTIVE TYPE!

18 Amp Press Fit up to 200Piv 4/\$1
 2 to 3 Amp Studs up to 600Piv 6/\$1
 35 Amp Studs 150 to 200Piv 5 for \$5

"TAB" * SILICON 750MA DIODES
NEWEST TYPE! LOW LEAKAGE

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35	100/70	200/140	300/210
.05	.09	.12	.14
Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
400/280	500/350	600/420	700/490
.15	.19	.23	.27
Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
800/560	900/630	1000/700	1100/770
.35	.45	.65	.75

GTD ALL TESTS AC/DC & LOAD!

1700 Piv/1200 Rms/750 Ma/\$1.20 @,
 10/\$10
 Same 1100 Piv/770 Rms 75c @, 16/\$11
 3 Kv/2100 Rms/200 Ma/\$1.80 @, 6/\$10
 6 Kv/4200 Rms/200 Ma/\$4 @, 3/\$9
 12 KV/8400 Rms/200 Ma \$8 @, 2/\$14

SCR—SILICON CONTROL RECTIFIERS!

PRV	7A	16A	PRV	7A	16A
25	.60	1.00	260	2.70	3.00
50	1.00	1.35	300	3.00	3.45
100	1.60	2.15	400	3.75	3.90
150	1.95	2.45	500	4.75	4.80
200	2.20	2.80	600	5.45	5.65

UNTESTED "SCR" Up to 25 Amps, 6/\$2
 Glass Diodes IN34, 48, 60, 64, 20 for \$1

Two RCA 2N408 & Two Regulators
 RCA IN2326 on prtd ckt. 30c @, 4/\$1



"TAB" Tubes Factory Tested, Insptd.
 Six Months Guaranteed! No Rejects! Boxed!
 GOVT & MFGRS Surplus! new & Used

Low Prices! New XMTTG Tubes!

4-65A \$7.00	4X150A \$6.75	OB2 .55
4-125A 15.00	826 Query	5R4WGA .55
4-400A 25.00	829B 7.20	3.50
4-1000A 75.00	872A 3.50	24G Query
	OA2 .65	

We Swap Tubes! What Do/ U Have?

OA3 .80	5R4 1.00	6F7 .99
OC3 .70	5T4 .90	6F8 1.39
OD3 .59	5V4 .89	6H6 .59
OZ4 .79	5Z3 .89	6J5 .59
IL4 .82	6A7 1.00	6J6 .59
IR4 5/\$1	6A8 .99	6K6 .59
IS4 .78	6AB4 .59	6L6 1.19
IS5 .68	6AC7 .72	6SN7 .72

Send 25c for Catalog!

IT4 .85	6AG5 .65	6V6GT .90
IT5 .95	6AG7 .75	12AU7 .69
IU4 6/\$1	6AK5 .69	12A6 .45
IU5 .75	6AL5 .55	25L6 .72
2C39A Q	6AQ5 .66	25T 4.00
2C40 5.50	6AR6 1.95	28D7 .89
2C43 6.50	6AS7 3.49	50L6 .59
2C51 2.00	6AT6 2/\$1	83V .95

We Buy! We Sell! We Trade!

2D21 .65	6BA6 .59	250TL 19.45
2K25 9.75	6BE6 .59	VR92 5/\$1
2K28 30.00	6BK7 .99	388A 3/\$1
2V3 2/\$1	6BQ6 1.19	416B 16.00
2X2 .48	6BY5 1.19	450TL 43.00
4X250B 30.00	6BZ6 .91	813 9.95
5BP4 7.95	6C4 .45	815 1.75

Top \$\$\$ Paid for All Tubes!

"VOLT-TAB" 600Watt Speed Control
 115VAC \$4.50 @, 2 for \$8

866A Xfmr 2.5V/10A/10Kv/Ins! \$3 @
 Ballentine #300 AC/Lab Mtr. \$54
 (Sd) Choke 4Hy/0.5A/27Ω \$40 @, 2/\$6
 "VARIACS" L/N 0-135v/7.5A \$15
 "VARIACS" L/N 0-135v/3A \$10
 TWO 866A's & Fil. Xfmr. \$6

SILICON TUBE REPLACEMENTS

OZ4 UNIVERSAL \$1.75 @, 2/\$3
 5U4 1120Rms/1600Inv \$2 @, 3/\$5
 5R4 1900Rms/2800Inv \$9 @, 2/\$15
 866 5Kv/Rms - 10.4Kv Inv
 \$11 @, 2/\$20

Mica Condr .006 @ 2500V 4/\$1
 Snooper Scope Tube 2" \$5 @, 2/\$9
 Mini-Fan 6 or 12Vac/60Cys \$2 @, 3/\$5
 4X150 Ceramic Loktal \$1.25 @, 2/\$2
 Line Filter
 Line Filter 50Amp/250VAC \$10 @, 2/\$16

DC 3 1/2" Meter/RD/800Ma \$4 @, 2/\$7
 DC 2 1/2" Meter/RD/100Ma \$3 @
 DC 2 1/2" Meter/RD/30VDC \$3 @, 2/\$5
 AC 3 1/2" Meter/RD/130VOC \$5 @, 2/\$9
 DC 4" Meter/RD/1Ma/\$5 @, 2/\$9

Battery Charger 6&12V Charges up
 to 5Amp "Approved" Heavy Duty Design
 with Klixon Circuit Breaker.
 Operates 220 or 110VAC @ 50 or
 60 Cys \$8, 2 for \$15, 7/\$49

Transformers—All Input 115v/60Cys VCT
 @ 250Ma, 6V/8A/5A/3A \$6, 2/\$10
 400VDC Supply @ 200MA & Silicon Rect
 & Filters \$10
 20VAC & TAPS/.8,12,16, 20V @ 4A, \$3
 32VCT/1A or 2X16V @ 1A, \$8 @, 2/\$5

Line Filter 4.5A @ 115VAC 4 for \$1
 Line Filter 5A @ 125VAC 2 for \$1
 Converter Filter 400 Ma @ 28VDC 4 for \$1
 Converter Filter Input/3A @ 30VDC 4/\$1
 2.5MH PiWound Choke/National 5 for \$1

We Buy, Sell & Trade

SEND 25c FOR CATALOG

"TAB" Terms Min Order \$3
 FOB New York.
 10 Day Gtd.
 Our 20th Year.

111NM Liberty St., N.Y. 6, N.Y. Re 2-6245

"TAB" FOR THE BEST KITS!

Each "TAB" Kit Contains The Finest Selection!!!

Kit 35 Precision Resistors
 Kit 75 Resistors 1/2/1&2W
 Kit 12 Electrolytic Cond's.
 Kit 65 Tubular Condensers
 Kit 500 Lugs & Eyelets
 Kit 10 Bathub Oil Cond's.
 Kit 5 lbs. Surprise Package
 Kit 10 Transmit Mica Cond's.
 Kit 8 Phone/Patch Xfms
 Kit 10 Insld Tuning Tools
 Kit 6 "SunCells", Batts
 Kit 10 Sub-Min Tubes
 Kit 12 Alligator Clips Asstd
 Kit (6) Tube Clamps Asstd
 Kit (82) Transistors PNP & NPN
 Kit (12) 2Amp Stud Rectifiers

Kit 75 Mica Condensers
 Kit 10 Crystal Diodes
 Kit 200ft Hook Up Wire
 Kit 4 Rolls, 500ft/ea. Assorted Color
 Kit 5 FT243 Xtal Holders
 Kit 10 Xtal Osc. Blanks
 Kit 4 Asstd Rectifiers
 Kit 100 Self/Tap Screws
 Kit Adj Wire Stripper & Cut
 Kit Hi Gain Xtal Mike
 Kit 2 pair S0239 & PL59
 Kit 12 Binding Posts Asstd
 Kit (3) T036/50Watt Untested
 Kit (50) TOPHAT 3/4A/Diodes Untested
 Kit (12) T03/3A Transistors Untested
 Kit (4) PF/PressFit 18Amp Studs

Order Ten (10) Kits—We Ship Eleven
 One Each Above Kit Only. Each Kit 99c

W.E. Polar Relay #255A/\$5 @, 2 for \$9
 W.E. Socket for #255A Relay, \$2.50
 Toroids 88Mhy New Pckg \$1 @, 6/\$5
 6.3VCT @ 15.5A & 6.3VCT @ 2A \$4 @,
 2/\$6
 200KC Freq Std Xtals \$2 @, 2/\$3
 Printed Ckt Bd New Blank 9x12" \$1 @,
 6/\$5
 Klixon 5A Reset Ckt Breaker \$1 @, 8/\$5
 2K to 8K Headsets Good Used \$3 @, 2/\$5
 Xtal Blanks Asst Types 12 for \$1

WANTED TEST SETS
& EQUIPMENT

Bandwitch Ceramic 500W 2P/6Pos \$3 @,
 2 for \$5
 6Hy-305Ma Choke Cased \$3 @, 2/\$5
 7-1/2Hy-400Ma Choke Cased \$7 @, 2/\$12
 250Mfd @ 450 Wv Lectlytic 4/SSB \$3 @,
 4/\$10
 Cndsr Oil 10Mfd x 600-2x2.5 & 5Mfd \$1
 @, 15/\$10
 Cndsr Oil 6Mfd @ 1500V \$4 @, 4/\$10
 880Vct @ 735Ma for SSB \$9 @, 2/\$16
 480Vct @ 40Ma & 6.3 @ 1.5A CSD \$1.50
 @, 4/\$5
 10Vct @ 5A & 7.5Vct @ 3A CSD \$6 @,
 2 for \$10

WANTED LAB METERS! BRIDGES!
K-POTS!

Pwr Sup Kit 900VDC @ 500Ma & 4/
 Silicon Diodes 1700Piv FWB \$12
 Pwr Sup Kit 1200VDC @ 200Ma/Xfmr
 & FWB Silicon Rect \$10 @, 2 for \$18
 Modulation Xfmr 60W/15K to 5.7K \$5
 Headset Rubber Bunyon Pads pair \$1
 Socket Ceramic 1625 Tube 4/\$1
 Socket Ceramic 866 Tube 4/\$1
 Socket Ceramic 4X150/Loktal 4/\$2

WANTED YOUR - ORDER - TODAY!
 6MTR Ground-Plane Ant (R Exp) \$4
 Knob Spin-Crank BC348 Type \$1
 MiniFan 6 or 12 VAC \$1.50 @, 4 for \$5
 Beam Indicator Selsyns 24VAC 2 for \$10
 Precision TL147 Feeler Relay Gage \$1
 8 foot Elec. Cord #16ga & Plug 39c @,
 3/\$1
 Fuse 250Ma/3AG 5 for 30c, 100 for \$3
DON'T C-WRITE & SEND ORDER!
 XMTTG Mica Cndsr .006 @ 2.5Kv 39c
 @, 5/\$1
 XMTTG Mica Cndsr .00025 @ 8Kv 75c
 @, 4/\$2
 Mini-Rectifier FWB 25Ma @ 115VDC
 3 for \$1
 Micro-Switch Rated 40Amp AC & DC
 4 for \$1
 BandPass Filters 60 or 90 or 150Cys
 3 for \$5
 T30 Throat Mikes \$1 @, 4 for \$3
 "Bruning" 6" Parallel Rule #1 @
 3 for \$2
 Linear SawTooth Pot KSI5138/W. E.
 3 for \$1

RUSH YOUR ORDER TODAY.
QTYS LIMITED!

SUBSCRIBE TO 73

In addition to considerable discussion on the new FCC proposals, we'll have a big June surplus issue next month and a giant VHF issue in July. Of course you can follow the "party line" in brand X, if you want . . . but we'll have the real stuff here.

Name _____ Call _____

Address _____

City _____

State _____ Zip Code _____

73 Subscriptions:

1 year \$4 _____ 2 years \$7 _____

3 years \$10 _____ New subscription _____

Renewal _____ Extension of sub _____

loAR for one year \$5 _____

loAR for one year and 73 for one year \$7 _____

INDEX TO ADVERTISERS

Alco, 110	Hammarlund, 11
Algeradio, Jan. 65	Hayden, 102
Alltronics-Howard, 110	HCJ, 85
Atlantic, 110	Heffron, April 65
Ameco, April 65	Henry, 67
American Crystal, 101	Hill, Feb. 65
Amperex, 20	Hi-Par, 95
Amplidyne, 91	Hy Gain, 52
Amrad, 108	Int. Crystal, 4
Arrow Electronics, Dec. 64	Irving, 87
Arrow Sales, 105	Jefftronic, 110
ATV Research, 105	Juge, Mar. 65
Autronics, 106	Linear Systems, Mar. 65
Aztec, Jan. 65	Mann, Mar. 65
Babcock, April 65	Master Mobile, April 65
BC Electronics, 106	McCoy, 47
Budwig, 110	Meshna, 103
Burghardt, 39, 52	Mission, 75
Burstein-Applebee, Jan. 65	Mor-Gain, 42
B & W, Mar. 65	Mosley, Mar. 65
Callbook, 77	National, Cover IV
C & H, Feb. 65	Newtronics, 65
Christie, 108	Parks, 105
Columbia, 97	Path, April 65
Commercial, 102	Poly-Paks, 107
Cornell-Dubilier, Jan. 65	Quaker, April 65
Cubex, Jan. 65	Quement, 89
Cushcraft, 43	Reyco, Mar. 65
Datak, 24, 25	Rohn, 10
Davco, 35	RSGB Books, 104
Denver Crystals, 104	RW Electronics, 108
Denson, Jan. 65	Salch, Mar. 65
Dow Key, 71	Scientific Asc., Mar. 65
Dow Trading, 102	Selectronics, 99
Drake, 29	Sideband Engineers, April 65
East Coast, Jan. 65	Skylane, April 65
Editors & Engineer, 19	Slep, 98
Edwards, 93	Space, 101
Electronicraft, Jan. 65	Sterman, April 65
Electronic Comp., 103	Swan, 17
Ell-Conn, 81	T A B, 111
Epsilon, 97	Telrex, 38, 70, 81
Evans, 85	Texas Crystal, 51
Fair, 108	Transistors Ult., Mar. 65
Fichter, 102	Tri-Ex, April 65
Finney, April 65	United Plastic Mold, 97
Fulton, April 65	U. T. C., Cover II
Gain, 37	Vanbar, 104
Galaxy, Cover III	Vanguard, 83
Gem Electronics, Feb. 65	Viking, Mar. 65
Gift Shop, 104	Waters, 56
G & G, Feb. 65	Western (Calif.), 81
Glass, J. J., Mar. 65	Western (Neb.), 106
Gonset, Feb. 65	Wilson, April 15
Goodheart, 109	World Radio Labs, 49
Government Whse., 101	73 Books, 95
Graham Radio, 104	73 Subscriptions, 112

Propagation Chart

May 1965

J. H. Nelson

EASTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7*	7	7	7	7	7	14	14	14	14	14
ARGENTINA	14	14	14	7*	7	7	14	14	14*	21	21*	21	21
AUSTRALIA	14	14	14	7#	7#	7	7	7	7	7#	14	14	14
CANAL ZONE	21	14	7	7	7	7	14	14	14	14	14	14	21
ENGLAND	14	7	7	7	7	14	14	14	14	14	14	14	14
HAWAII	14	14	14	7	7	7	7	7#	14	14	14	14	14
INDIA	7	7#	7#	7#	7#	7#	14	14	14	14	14	14	7*
JAPAN	14	14	7#	14	7	7#	7#	7*	7	7#	14	14	14
MEXICO	14	14	7*	7	7	7	14	14	14	14	14	14	14
PHILIPPINES	14	14	7#	7#	7#	7#	7*	14	14	14	14	14	14
PUERTO RICO	14	7*	7	7	7	7	14	14	14	14	14	14	14
SOUTH AFRICA	7#	7	7	7#	7#	14	14	14	14	14	14	14	7#
U. S. S. R.	7	7	7	7	7	7*	14	14	14	14	14	14	7*
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14	14

CENTRAL UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	7	7	7	7	7*	14	14	14	14	14
ARGENTINA	14	14	14	7*	7	7	14	14	14	14	14	21*	21*
AUSTRALIA	14	14	14	7#	7	7	7	7	7	7*	14	14	14
CANAL ZONE	21	14	7*	7	7	7	14	14	14	14	14*	21	21
ENGLAND	14	7	7	7	7	7	14	14	14	14	14	14	14
HAWAII	14	14	14	7	7	7	7	7*	14	14	14	14	14
INDIA	14	14	7#	7#	7#	7#	7#	14	14	14	14	14	14
JAPAN	14	14	14	7#	7	7#	7#	7*	7	7#	14	14	14
MEXICO	14	14	7	7	7	7	7	7*	14	14	14	14	14
PHILIPPINES	14	14	14	7#	7#	7#	7#	7*	14	14	14	14	14
PUERTO RICO	14	14	7*	7	7	7	14	14	14	14	14	14	14
SOUTH AFRICA	7#	7	7	7#	7#	14	14	14	14	14	14	14	7#
U. S. S. R.	7	7	7	7	7	7	7*	14	14	14	14	14	7*

WESTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	14	7	7	7	7	7*	14	14	14	14
ARGENTINA	14	14	14	14	7	7	7#	14	14	14	14	21*	21*
AUSTRALIA	21	21*	21	14	14	14	7	7	7	7	7	14	21
CANAL ZONE	21	14	14	7*	7	7	7*	14	14	14	14*	21	21
ENGLAND	14	7	7	7	7	7	7	7*	14	14	14	14	14
HAWAII	21	21*	21	14	14	7	7	7	14	14	14	14	14
INDIA	14	14	14	14	7#	7#	7#	7#	14	14	14	14	14
JAPAN	14	14	14	14	7#	7	7	7	7	7#	14	14	14
MEXICO	14	14	7*	7	7	7	7	7	7*	14	14	14	14
PHILIPPINES	14	14	14	14	14	7#	7	7#	14	14	14	14	14
PUERTO RICO	14	14	14	7	7	7	7*	14	14	14	14	14	14
SOUTH AFRICA	7#	7#	7	7#	7#	7#	7#	14	14	14	14	14	7#
U. S. S. R.	7	7	7	7	7	7	7	7*	14	14	14	14	7*
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14	14

Very difficult circuit this hour.

* Next higher frequency may be useful this hour.

Good: 1-9, 12-14, 20-22, 26-29

Fair: 11, 17-18, 23-25

Poor: 10, 15, 16, 19, 30-31

VHF DX: 7, 8, 18, 19, 26

WRL OFFERS YOU A FREE TWO-WEEK TRIAL IN YOUR HOME ON EITHER THE GALAXY III OR GALAXY V!*



WRL GUARANTEES SATISFACTION! YOU BE THE JUDGE AFTER A TWO-WEEK FREE TRIAL . . . NO OBLIGATION. GALAXY TRANSCEIVERS OFFER YOU MORE FEATURES PER DOLLAR THAN ANY COMPARABLE TRANSCEIVER ON THE MARKET • 300 Watts SSB/CW Input • Best Filter Available • Transistorized AVC/AUDIO/VOX • Most Compact Transceivers With 5 or 3 band Full Coverage • New VFO Side View Dial • Selectable USB or LSB • Portable For Mobile or Fixed Operation.

*WRITE FOR DETAILS ON FREE TRIAL OFFER!

GALAXY III

80-40-20 Meters

only **\$349.95**

No down payment
\$17.00 monthly

WRL Charg-A-Plan

GALAXY V

80-40-20-15-10 Meters

only **\$469.95**

No down payment
\$21.00 monthly

WRL Charg-A-Plan

NEW DELUXE CW MONITOR



only **\$29.95**

Monitor and improve your CW. A must for every CW operator. Use with any transmitter or transceiver.

NEW Rejector NOTCH FILTER

Tunable — Transistorized — Powerful suppression of heterodynes and QRM. Use with any receiver or transceiver. Just connects between receiver and PM speaker.



only **\$34.95**

"Got Our 1965 Catalog?"

FINEST SELECTION OF HAM EQUIPMENT EVER ASSEMBLED

ALWAYS the TOP TRADE allowance

ALWAYS the best in terms from

"the house the hams built"

Leo I. Meyerson-WØGFQ
President



WRL

WORLD RADIO LABORATORIES

3415 West Broadway
Council Bluffs, Iowa 51504

- | | |
|---|--|
| <input type="checkbox"/> Send details on Galaxy FREE Trial offer. | <input type="checkbox"/> Ship Rejector for \$34.95 + postage. |
| <input type="checkbox"/> Ship CW Monitor for \$29.95 + postage. | <input type="checkbox"/> Send Reconditioned "Blue Book" prices |
| <input type="checkbox"/> Send 1965 Catalog | |

Name _____

Address _____

City _____ State _____

Zip _____ Call _____

2 Full Gallons in a pint size container

Nothing under the table . . . National's self-contained NCL-2000 amplifier packs a full 2000 watts PEP in its desktop cabinet. A real rock-crusher, the NCL-2000 delivers up to 1400 watts of peak SSB output into your antenna on the 80 through 10 meter bands, and is fully rated for 1000 watts D.C. input in CW, AM, and RTTY operation.

National's two-gallon package has features you won't find elsewhere at twice the price: two husky RCA 8122 output tubes, designed specifically for high-power SSB service, provide 800 watts of available plate dissipation; adjustable passive grid circuit allows operation with exciters providing from 20 to 200 watts output, and may be used as exciter dummy load for easy

exciter tune-up with amplifier plate voltage removed; ALC output for use with the NCX-5 and other exciters incorporating ALC provisions; separate plate and multi-meters; high-efficiency operation in CW and RTTY modes; all changeover relays incorporated for use with either transceiver or transmitter-receiver combinations; automatic switch-over to exciter-only when plate voltage is removed; and complete safety and overload protection, including lid interlock, automatic B+ shorting bar, time delay, and current overload relays. To top it all off, the NCL-2000 carries National's One-Year Warranty.

Your National dealer will wrap up this potent little package for you at the pint-sized price of \$685.



NATIONAL RADIO COMPANY, INC. 

37 Washington Street, Melrose, Massachusetts, 02176 World Wide Export Sales: Auriema International Group,
85 Broad Street, New York City, N. Y.; Canada Tri-Tel Associates, 81 Sheppard Ave. W., Willowdale, Ontario

See us at the AFCEA show booth 82



The

INSTITUTE

OF

AMATEUR

RADIO

Dear IoAR Member

Enclosed you will find the proposed Constitution and By-Laws for the Institute. I've prepared them separately so you can file them away. If you have any proposed changes to make please send them in the form indicated. We will then send you a copy of the modifications proposed for your consideration and vote.

The matter of officers of the Institute is left up to the Directors under these By-Laws, the idea being not to be tied down as to officers until the Institute has grown a bit and the needs of the Institute dictate the election of officers. The present system puts the Institute directly in the hands of the Directors, who are elected by all of the members. The Directors then can select any officers they need for the functioning of the Institute. Right now this officership consists of one unpaid Secretary.

The Institute is continuing this year the informational mailings to Congress. Under preparation at present is a booklet explaining the difference between Citizens' Band and Amateur Radio. This is particularly important right now when all Congressmen are being flooded with mail from angry CB'ers who want hobby-type operation continued on the CB channels.

The future of Amateur Radio is closely linked with our Congress. Remember that the FCC is an agency set up and controlled by Congress. It is therefore of vital importance for Amateur Radio to be in good communications with Congress...to have the Congressmen understand Amateur Radio and appreciate it.

As you know, only the Institute of Amateur Radio is registered to lobby for Amateur Radio and no other organization is, under severe penalties, permitted to do so. This means that the ARRL is prohibited by law from representing Amateur Radio unless they make

CONSTITUTION AND BY-LAWS
OF
THE INSTITUTE OF AMATEUR RADIO

ARTICLE I
PURPOSE OF THE INSTITUTE

Section 1. THE INSTITUTE OF AMATEUR RADIO is a non-profit corporation organized and existing under the laws of the State of New Hampshire, pursuant to provisions of Chapter 292, R. S. A., having been duly qualified as a corporation on the 28th day of August, 1963.

Section 2. The purpose for which the Institute is founded is to promote national and international friendship and to enhance the technical state of the art of amateur radio.

Section 3. The Institute is entitled to enjoy all the rights and privileges granted to non-profit corporations under the laws of the State of New Hampshire.

Section 4. The Institute, as a non-profit corporation, is entitled to acquire money, funds, and property, and to deal with the same in the best interests of the Institute and in the best interests of amateur radio. In the event of dissolution of the Institute, then in that event, none of the money, assets, or property of the Institute shall be distributed to any individual member, person or persons, but the same shall be conveyed in trust to a corporate trustee duly qualified to conduct a trust business within the State of New Hampshire, the said property to be used by said trustee in the furtherance of the aims and purposes of the Institute, or else donated to a non-profit humanitarian organization.

Dear Institute Member,


Here are the proposed Constitution and By-Laws of the Institute. These have been worked and re-worked by the Directors and are still not all we could hope for. But they do represent a good foundation for the Institute to build on and seem to answer most of the pressing problems immediately facing the Institute.

Please read the by-laws over carefully and make notes on any sections that you think can be improved. Then, rather than writing in saying that you don't agree with article such and such, send in your proposed article which will supplant it. In this way we can make all proposed improvements available as votable alternates to all members without any question of editing or changing by me. All changes and additions submitted during the next two weeks will be considered. Informal suggestions will not be considered.

The next step will be to submit all proposed changes to you for a vote. The result of this vote will be our finished by-laws. These by-laws will be sent to you and will be published in 73.

With or without accepted by-laws the work of the Institute has been going on. Rather than spend our few funds on continuous communications with the membership we have been allocating them to our work in Washington, where we will do the most long range good.

73

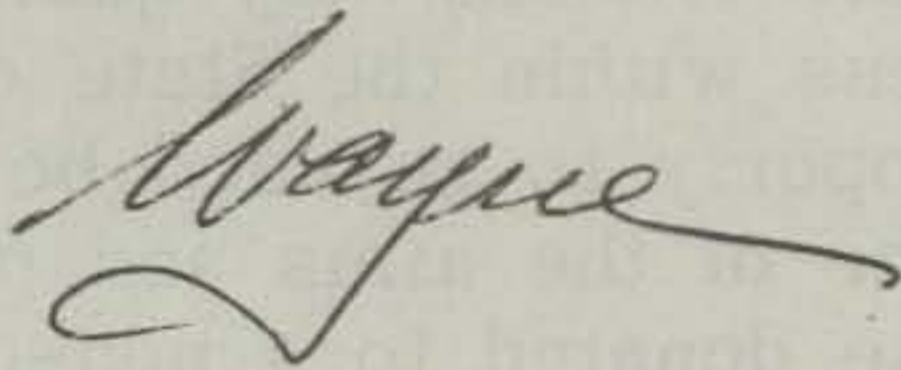A handwritten signature in cursive script, appearing to read "Wayne".

ARTICLE II DIRECTORS

Section 1. The Institute shall have five Directors whose term of office shall be for three years, except that two of the first five Directors shall hold office for a term of two years, and one shall hold office for a term of one year only. Thereafter, all Directors shall hold office for three years.

Section 2. The Directors shall exercise all authority and shall be in active management and control during the term of their office of all the business of the Institute, and all power with reference to the management and control of the said Institute shall vest in said Directors subject only to the laws of the State of New Hampshire. The Directors shall have the power to create an executive committee, all of the voting members of which shall be members of the Board of Directors, and which committee shall consist of not less than three members, but said executive committee shall in no event have the power to make policy decisions and shall be restricted in its powers to the carrying on of the day to day business of the Institute between meetings of the Board of Directors.

Section 3. In the event of the resignation, death, disability, or removal of any Director prior to the expiration of his elected term of office, such vacancy shall be filled by the remaining members of the Board of Directors until the next regular election.

Section 4. No person shall be eligible to hold office as a Director of the Institute unless he shall have been a member in good standing of the Institute for a period of not less than six months prior to the date of his election, and held a valid amateur radio license for a period of not less than 18 consecutive months prior to the date of his

nomination or election.

Section 5. The Directors shall hold regular meetings at least four times per year, said regular meetings shall be held on the second Monday of each January, April, July, and October.

Section 6. The Directors may hold such additional meetings as frequently in their opinion as the business of the Institute requires the same.

Section 7. Special notice of the holding of the regular meetings of the Board of Directors shall not be required, but no special meetings of the Board of Directors shall be held unless and until each Director shall have been given at least 48 hours actual notice of such meeting.

Section 8. A majority of the authorized number of Directors shall be necessary to constitute a quorum for the transaction of business, except to adjourn a meeting. Every act or decision done or made by a majority of the Directors present at a duly held meeting of the Board at which a quorum is present shall be regarded as the act of the Board of Directors.

Section 9. The Directors shall receive no fees or compensation for their services as Directors, but nothing herein contained shall be deemed as preventing said Directors from being reimbursed for necessary traveling expenses in connection with their attendance at Directors' meetings.

Section 10. The Directors shall be elected by a secret ballot of the members of the Institute.

Section 11. A Director may be removed from office by a majority of all votes cast by members of the Institute.

the necessary disclosures for registering. So far they have not seen fit to make these disclosures. It is entirely possible that this fear of disclosure is tied in with the mysterious tax situation that ARRL enjoys. We understand that the Internal Revenue Service is starting a careful investigation of this situation and it is possible that the League may soon have to dig into that half million that is rumored to have been put aside to bail them out of expected tax liens.

Since a good deal of the problems that beset Amateur Radio today are the direct responsibility of the League it would not be fair to you, as a member, if we were to try to ignore them. After all, if the ARRL were adequately representing Amateur Radio there would be no need for the Institute.

So let's look at the current situation.

The League is faced with more problems than it has ever had before in its existence...and all of them are the direct result of bad management. Probably most important of all for the future of Amateur Radio is the widening split between the ARRL and the European Amateur Radio Societies. The IARU is in a turmoil over the parochial thinking and lack of leadership of ARRL management. It now looks as though IARU region I (Europe and Africa) may make a complete break from ARRL.

Another matter of grave import to ARRL members is the libel suit brought against Huntoon and the League by W2BIB. In his letter of last June to all member clubs, Huntoon printed what looked to me like libelous statements about a ham, identifying him to the extent that there was no question in my mind...or in those of many people whom I talked to about this...about who was meant. And since this fellow has done highly paid work for amateur equipment manufacturers this sort of publicity could and perhaps already has hurt him severely. There is no possible way that the harm Huntoon foolishly

has done can be undone and this could easily cost the League well over a million dollars.

Suppose you were a fellow who had spent a lifetime building up the world-wide contacts to make you worth a hundred thousand a year or more to the companies you represent. You are in your fifties with no possibility of starting over again. Then along comes a magazine editor, irritated with you over a clever deal of his that you exposed, and he libels you. Would you sue for a million? You bet you would.

Now what is Huntoon doing about this? I hear that he has hired the most expensive libel lawyer in the world, Louis Nizer, to try to beat the rap. Nizer's fees usually start at around \$25,000. It would have been a lot less expensive to have checked the letter with the ARRL's General Counsel Booth in the first place. Huntoon, like Hoffa, is going to let the members pay for his mistakes, so it means nothing to him. Will the Directors fire him for this million dollar blunder? Will they dock his \$20,000 a year salary? Don't count on it.

You can get more details on the libel suit in the K6BX News Letter. It is worth every bit of the 50¢ price tag. Write K6BX, Box 385, Bonita, California and read a 22 page indictment of the League. He quotes letter after letter after letter from ARRL Directors to other Directors and Assistant Directors. You should read this one.

All is not bad by a long shot. I'm encouraged to find that Herb Hoover is making plans to pay for a spectrum study by an independant laboratory out of the \$100,000 slush fund voted by the Directors last May. I suggested that this be done in my editorials several times...I'm glad to see that this didn't prevent it. Also, I was afraid that the 100G would get sort of used up on family trips to Europe by League

Continued on page 14

then the Board of Directors at the next regular meeting shall be required to place the matter on their agenda and shall be required to hear from a representative of such petitioning members with reference to their objections or grievances. Said petitioning members shall be notified by the Institute of the date, time, and place of the holding of such a meeting when said petition will be considered. In the event that such a petition be heard by the Board, and the said member or members be still dissatisfied with the action of the Board, then the said petitioning member shall have the right to petition the members for a referendum. In the event that the said petition for such referendum be signed by one hundred members of the Institute, and the said petition be filed with the Institute, then the Board of Directors shall meet within fourteen days after such filing and at such special meeting representatives of the petitioning members shall be entitled to a further hearing. The Directors shall render a full and fair report of such meeting to the membership within fourteen days thereafter.

ARTICLE VI AMENDMENTS TO THE BY-LAWS AND CONSTITUTION

Section 1. The constitution and these by-laws may be repealed or amended by the members at any time as follows:

(a) Any member or members desiring to amend or repeal any provisions of these by-laws may circulate a petition among the members wherein the changes or amendments sought to be made are set forth, and whenever 25% of the members have signed such a petition to amend the by-laws, the said petition shall be filed with the Institute, who shall thereafter put the proposed changes to a vote of the membership. The by-laws or the constitution may thereupon be amended by a two thirds majority vote of all votes cast by members eligible to vote.

(b) The Directors shall have the authority to propose amendments or modifications to the by-laws and the constitution whenever in their judgement they may consider such change as beneficial to the operation of the Institute. Amendments or modifications of the by-laws proposed by the Directors shall become effective on an ad-interim basis by unanimous vote of all Directors.

ARTICLE VII

FINANCIAL REPORTS

Section 1. The financial condition of the books and records of account of the Institute of Amateur Radio shall be prepared annually by a Certified Public Accountant and a copy of the financial condition of the Institute as well as its current operating statement shall be submitted to all members.

ARTICLE VIII

EFFECTIVE DATE OF THE BY-LAWS AND CONSTITUTION

Section 1. The foregoing shall be designated as the Constitution and By-Laws of the Institute, and reference thereto may be made either as the Constitution or the By-Laws, said terms being interchangeable as used herein.

Section 2. These By-Laws shall become effective upon adoption by the interim Board of Directors and upon ratification and approval by a two thirds majority vote of all votes cast by members of the Institute.

IoAR STATEMENT 10 MARCH 1965

INCOME

486 members @ \$10 - - - - -	\$4860.00
115 members @ \$ 9 - - - - -	1035.00
17 members @ \$ 8 - - - - -	136.00
	6031.00

EXPENSES

Legal aid for WØJRQ in antenna fight - - - - -	\$ 500.00
Washington Newsletters (congress) -	250.00
Clipping service for newsletter - -	246.75
Membership supplies (buttons, stickers, cards, etc.) - - - - -	527.00
Stationery and paper supplies - - -	306.23
Postage - - - - -	189.79
Labor (processing memberships, keeping records, preparing certificates and membership cards, writing and preparing booklets and mailings, making stencils, filing stencils, pho- tography, printing, etc. - - - - -	752.00
Phone, electricity, office space - -	00.00
Miscellaneous - - - - -	3.19
	\$2774.96

ON HAND - - - - - \$3256.04

employees. Since no public accounting ever seems to be made on funds like this one never knows what is happening.

The Institute Directors had a short meeting in Washington at the year end and decided, in view of the unexpectedly low expenditures for 1964, to lower dues for 1965 to \$5 and extend all Founding Members for another year. Since there has been considerable pressure to arrange for some sort of combination Institute membership and 73 subscription it was decided that a special price for the combination would be set at \$7. In order to align subscriptions and memberships in the Institute it was decided to accept combinations at \$7 and extend the Institute membership to the end of the current 73 subscription plus one year so that both would in the future end simultaneously.

It was decided that the original Charter Members of the Institute would hold their seniority and that any future memberships would be indicated as Charter Memberships, even though there may have been a lapse in membership.

Your Support

The Institute is planning on continuing its series of information booklets to Congress, as mentioned earlier. This will particularly emphasize the benefits of Amateur Radio to the country...and to them. Our approach will be to try to interest them personally in taking up ham radio...explaining why it will be valuable to them in keeping in touch with their constituents and giving them a broader knowledge of our technical world. We'll point out how simple it is to get the first license for Novice operation and what is necessary to progress to the General license. We'll lean heavily on the public service aspects of our hobby and also the international good will and benefits. It is hoped that this approach will get more personal attention that a straight information sheet might.

Institute
of
Amateur
Radio
Membership
Application

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

_____ \$5 enclosed for one year membership dues.

_____ \$7 enclosed for one year membership PLUS
one year of 73 Magazine. (Please fill out
the form below, too.)

_____ I am not now a subscriber to 73.

_____ I am a subscriber, so please extend my
IoAR membership to terminate with my
current 73 subscription plus one year. *

* All combination membership and subscriptions will extend the current subscription of 73 for one year and the Institute membership until the end of the 73 subscription so the two will end together. Thus if your present 73 subscription runs until December 1965 (your stencil will say D5) then both your subscription and your IoAR membership would run until December 1966. Naturally we can not extend any memberships in the Institute on the basis of subscriptions sent in to 73 after this offer has been announced.

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

_____ \$7 enclosed for 73 subscription
and IoAR membership.

_____ This is a new subscription to 73.

_____ This is an extension of a current sub.

_____ This is a renewal of an expired sub.

_____ \$4 enclosed for a one year subscrip-
tion to 73 with NO Institute Membership.

_____ \$7 enclosed for two years of 73, with
NO Institute membership.

73
Subscription
Form



BULK RATE
U.S. POSTAGE
PAID
Peterborough, N.H.
Permit No. 73

PETERBOROUGH, NEW HAMPSHIRE Joseph C. Strolin, K1REC

21 Ellen St.
Norwalk, Conn.

All this work costs money, obviously. We are doing it all at an absolute minimum cost with no paid employees of the Institute so far and taking full advantage of the sizeable investment in printing and production facilities and personnel at 73 magazine. Sure, we could have mailed you a bulletin every month telling you what was going on, but this would have taken funds from our work on Congress and that is our main reason for existence. Bear with us.

Support of the Institute will, more than any other way, bring you results in keeping ham radio alive. 100% of the money of the Institute is devoted to Institute pursuits as compared with about 10% of the money received by the ARRL being spent on League matters, with about 90% being spent on their giant publishing business. You get \$5 worth of representation with the Institute for your \$5 investment and about 50¢ worth of contests, QSL's, and activities from your \$5 to ARRL. It comes down to investing in your fun here and now or investing in the future.

Said Nominating Petition shall be filed with the Institute not less than sixty days prior to the date of the election of Directors. Immediately upon the filing of such a petition the Secretary of the Institute shall verify the eligibility of the person so nominated, and if said person is found to be eligible, then his name shall be placed upon the ballot.

Section 5. All elections shall be by secret written ballot.

ARTICLE IV RECORDS, REPORTS AND INSPECTIONS

Section 1. The Institute shall maintain adequate and correct accounts, books, and records of its business, properties, and affairs. All such books, records and accounts shall be kept at its principal place of business within the State of New Hampshire, said place of business to be fixed by the Board of Directors.

Section 2. All books and records provided for in these by-laws or which may be required by the laws of the State of New Hampshire, shall be open for the inspection of the Directors and any member at any time during regular and usual business hours. The Board of Directors shall render to the members a full and fair report of the affairs of the Institute within thirty days after each regular meeting of the Board.

ARTICLE V MEMBERSHIP REFERENDUM

Section 1. In the event that any member or members should feel aggrieved by any act or decision of the Board of Directors, said member or members shall have the right to petition the Board of Directors for redress or corrective action. Said petition for redress or corrective action shall be signed by a minimum of ten members. In the event that such a petition be filed with the Institute,

ARTICLE III
MEMBERSHIP

Section 1. There shall be one class of membership only in the Institute.

Section 2. Membership dues or fees shall be fixed by the Board of Directors.

Section 3. The members shall have the right to nominate and elect the Board of Directors.

Section 4. Nomination for Directors shall originate with the membership. Any member or members desiring to place in nomination any person as Director shall sign and file with the Institute a nominating petition, which shall read in substance as follows:

The undersigned hereby nominates _____
_____ to serve as a Director of the
Institute of Amateur Radio. The undersigned
requests that the Secretary certify his eligi-
bility and place his name on the ballot.

Dated:

This nomination meets with my approval:

nominee

Said Nominating Petition shall be signed by a minimum of three members, and the nominee.