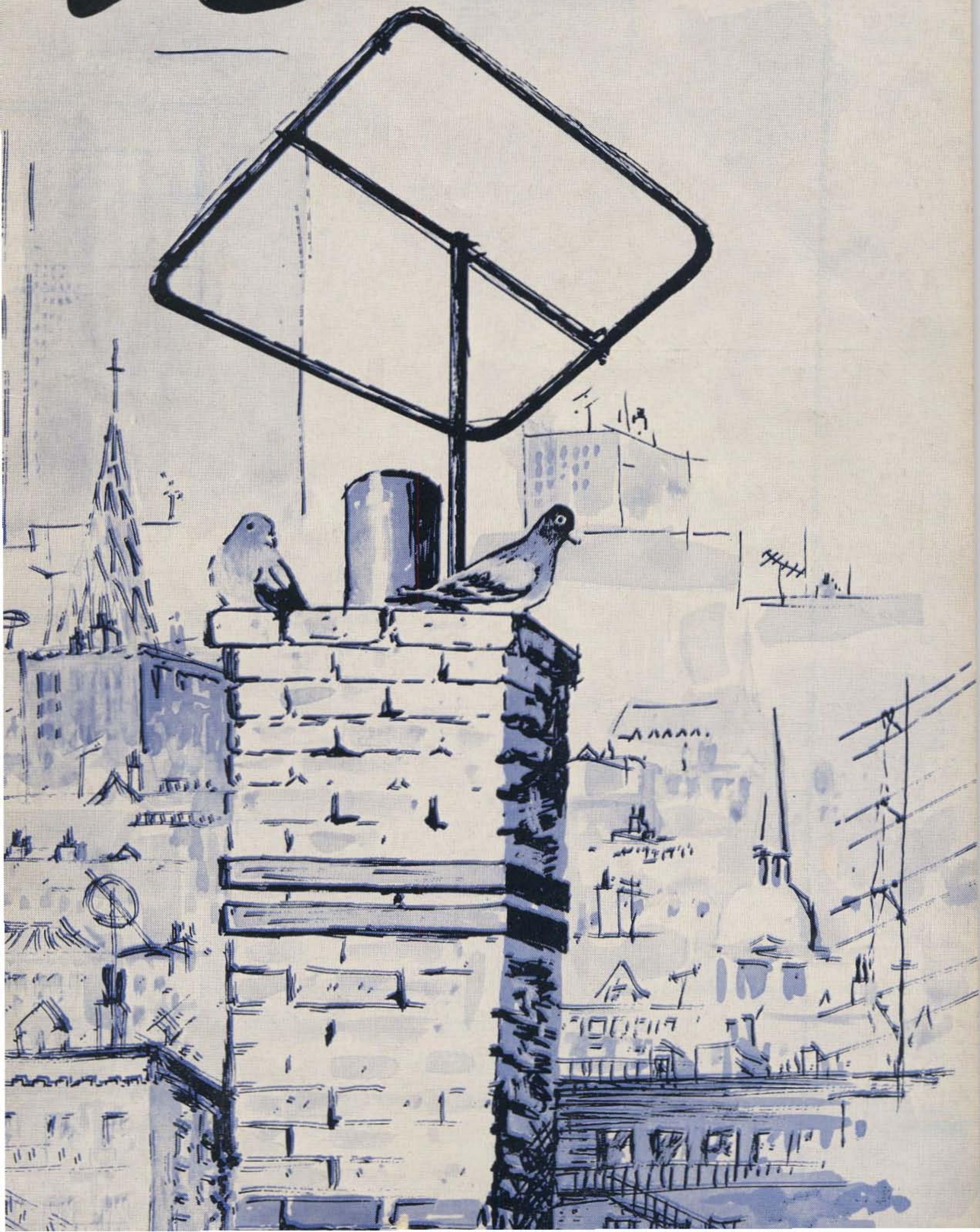


73

Amateur Radio

SEPTEMBER 1966


60¢? Certainly!





"S" SERIES

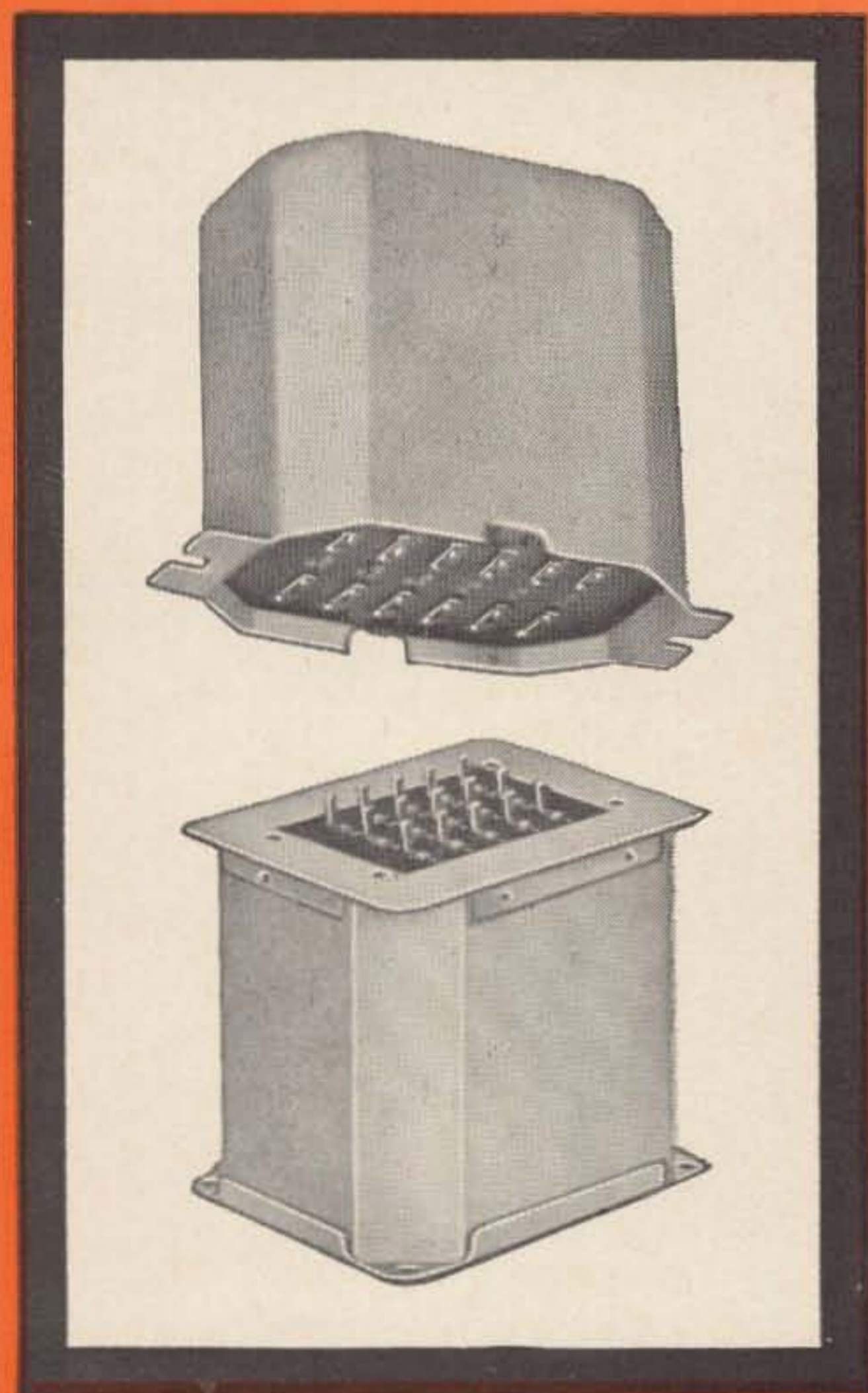AUDIO & POWER TRANSFORMERS & REACTORS For Complete Ham Systems



**Popular Priced
Matched Components
for
Power Supplies
Modulation
Pre-Amp &
Power Amplifiers
... for entire ham rigs**

Thirty years of attention to ham requirements have resulted in a complete line of reliable, high quality components geared especially to your needs. The "S" series of audio and power transformers and reactors, designed specifically for ham and PA service, are completely matched for compatibility in constructing a rig. These are popular priced units which afford the ham the full benefits of UTC's established excellence for quality components coupled with high reliability.

Write for catalog of over
1,300 STOCK ITEMS
with UTC top Quality



UNITED TRANSFORMER CO.

DIVISION OF TRW INC. • 150 VARICK STREET, NEW YORK, N. Y. 10013

73 Magazine

Wayne Green W2NSD/5Z4
Publisher

Paul Franson WA1CCH
Editor

Jim Fisk WA6BSO
Technical Editor

Jack Morgan WØRA
Advertising Manager

September 1966

Vol. XLII, No. 1

Our cover this month is by Sidney Willis of Bennington, N.H. Sid is a well-known artist who specializes in still lifes of objects associated with Old New England; he has won a number of gold medals at N.E. Art Shows.

ADVERTISING RATES

	1X	6X	12X
1 p	\$298	\$281	\$264
1/2 p	155	147	139
1/4 p	80	76	72
2"	42	40	38
1"	23	22	21

No extra charge for second color (red, usually) or bleed on full page ads. If you're interested in advertising to hams, get our full rate card and other information from Jack Morgan WØRA.

Compact Six and Two Transmitter K6RIL	6
Here's a very clever 60 watt rig; easy to build, too.	
Poorboy Mark II Quad K4USK	14
A simple, light, three-band quad.	
5dB Gain on 75 m Mobile W3BTQ	20
Increase your mobile signal at low cost.	
Accurate VHF Frequency Measurements W5WGF	22
Use your BC-221 for high accuracy on two meters.	
Add SSB AGC to Your Receiver W1OOP	26
It's not hard or expensive.	
Ultimate Station Control W2AJW	30
You mean you're using a 89¢ knife switch??	
Match Box Tuner W6BLZ	38
W6BLZ's version of a Johnson antenna tuner.	
Two Transistor Testers W6AJF	42
One simple, the other simpler. Both work well.	
Transistor Voltage Regulator WB6MOC	46
Need 9 to 28 V at 10 A?	
A Visit to the R. L. Drake Company . . . WØPEM	50
A short tour of their factory.	
Try Homebrewing Now WB2JQC	52
It's not hard or expensive.	
Diodes for OT's and Beginners W2DXH	54
There's no reason not to understand them.	
Two Meter Repeater W5KPZ	58
Even if you don't need a repeater, this is interesting.	
Complete Overload Protection W4ZUS	66
This one's pretty original.	
Heathkit HM-15 SWR Meter W7IDF	68
Ken likes it.	
A Pox on Your Junk Box WA6JNI	70
Maybe some people shouldn't build . . .	
Drafting for the Ham Writer KØEFC	72
This article contains charts of our schematic symbols.	
Lafayette HA-650 Transceiver WA1CCH	78
Six meters—portable and carefree.	
Conar 800 TV Camera Kit W3WTO	82
Like to get on ham TV inexpensively? This'll help.	
Gus: Part 15 W4BPD	86
Gus continues his visit to the Seychelles.	

SPECIAL BOOK FEATURE

Coaxial Accessories Handbook WA6BSO	93
---	----

The third part of Jim's series on coaxial systems covers antenna tuners, baluns, switches, relays, dummy loads, SWR bridges and attenuators.

De W2NSD/1	2	Improved Gamma Match	48
Editor's Ramblings	4	New Books	69
Double Sixer Power	40	Propagation	126
Debugging Hi Fi	44	Index to Advertisers	126

73 Magazine is published monthly by 73, Inc., Peterborough, N. H. 03458. The phone is 603-924-3873. Subscription rates \$4.00 per year, \$7.00 two years, \$10 three years world wide. Second class postage is paid at Peterborough, New Hampshire and at additional mailing offices. Printed in Bristol, Conn., U.S.A. Entire contents copyright 1966 by 73, Inc. Postmasters, please send form 3579 to 73 Magazine, Peterborough, New Hampshire. Why not make a DX friend of yours happy with a gift subscription to 73?

de W2NSD/1

never say die

First WTW Winner

The first complete collection of QSL's for the Worked the World Certificate was received here in Peterborough July 8. Cdr. Gay Milius W4NJJ of Norfolk, Virginia sent in 104 good cards to be the first winner. Gay is a Legal Officer at the U.S. Naval Station in Norfolk; he has an AB from Dartmouth and LLB from Fordham. Gay has written a number of articles for ham magazines, and, as the photo shows, is an avid DX'er.

Who's going to be next?

ET3AC system

One of the problems facing all DXpeditions, and for that matter, just about all rare DX stations, is how to go about working the maximum number of stations in a minimum amount of time. Those of you who chase DX know only too well how terrible some of the stations do at this art form.

Our more experienced DXpeditioners have got the business fairly streamlined. Don Miller cranks out one or two contacts a minute for hours on end. Gus does likewise. Don and Gus use split frequencies. They usually operate down around 14100 kHz on sideband and then listen from 14200 up for calls. This works



Gay Milius W4NJJ, winner of the first WTW award.

pretty fast, but they do have to sit and wait for each caller they hear to stop sending before they can work him. Most savvy DXers make their calls short, but now and then you run across an idiot that spells out his call four times and you wonder if he is ever going to shut up.

When you are transceiving on your own frequency the pileup problem can be devilish. Some DX stations find they have to wait several minutes before fellows stop calling them long enough to let anyone hear them come back. This only happens when the DX station lets the situation get out of control. I've had good success on my own frequency from rare spots by standing by for short calls from specific areas and using fast break-in. I can usually keep up with Don and Gus in contacts per hour using this system.

The other day I heard Blake, ET3AC, using a new idea while he was knocking them off from FL8AC. The idea seems like a good one to me and I'd like to pass it along because I think it has possibilities for working even more stations per given time than those we've been using. Blake would announce that he was going to tune a band of frequencies for given time and write down all the calls he heard. He would then look for the fellows on his own frequency with fast break-in. This spread out all of the calling stations over a ten or twenty kilocycle band so he could get their calls easily, and this is the hardest part of the contacts. He knocked off two to three a minute average this way.

Some rare DX operators complain that they get mobbed every time they come on the air by all the fellows who want a QSL card. Sure they do . . . because they haven't taken the few days it takes to work the several thousand DXers. If they would just devote a few days to working stations as fast as they can and get the services of a QSL manager they would be able to operate with little interference in the future.

It is possible to take the heat off by working all the DXers. We have several countries with just one or two stations, but which are not considered rare by any means. I've operated from 4U1ITU many times and it is so common even though it is the only station in the "country" that I frequently have to call CQ a couple of times to get a contact from there. To perk up interest in this station they had to run through some new prefixes (4U2ITU, etc.).

And let's just have a word on QSL's. They are a heck of a lot of trouble, as I know only

(Continued on page 80)

NEW from International

SINGLE SIDEBAND 9mc EXCITER-DRIVER 50-54mc MIXER-AMPLIFIER

The SBX-9 Exciter-Driver and the SBA-50 Mixer-Amplifier provide the perfect combination for 50-54mc SSB operation. Performance, versatility and reliability are incorporated into this new SSB pair. A tremendous value at a low price!



Model SBX-9

SPECIFICATIONS:

Exciter-Driver 9mc

Tubes: 6BH6 Oscillator

12AX7 Audio

7360 Bal Modulator

6BA6 RF Amplifier

Filter: Four crystal half lattice

Carrier Suppression 45db min.

Unwanted SB Atten. 40db min.

Output: Provides voltage drive for mixer such as SBA-50

Controls: Carrier Balance

Microphone Gain

Test Switch

USB-LSB Switch

Metering: RF output for balance

adjust. Two sensitivity

ranges available with

front panel switch.

Misc: Relay included for push-to-talk

operation. Crystals for upper


and lower sideband included.

Requires high impedance microphone.

For operation on 117 vac 60 cycle power.

\$125.00

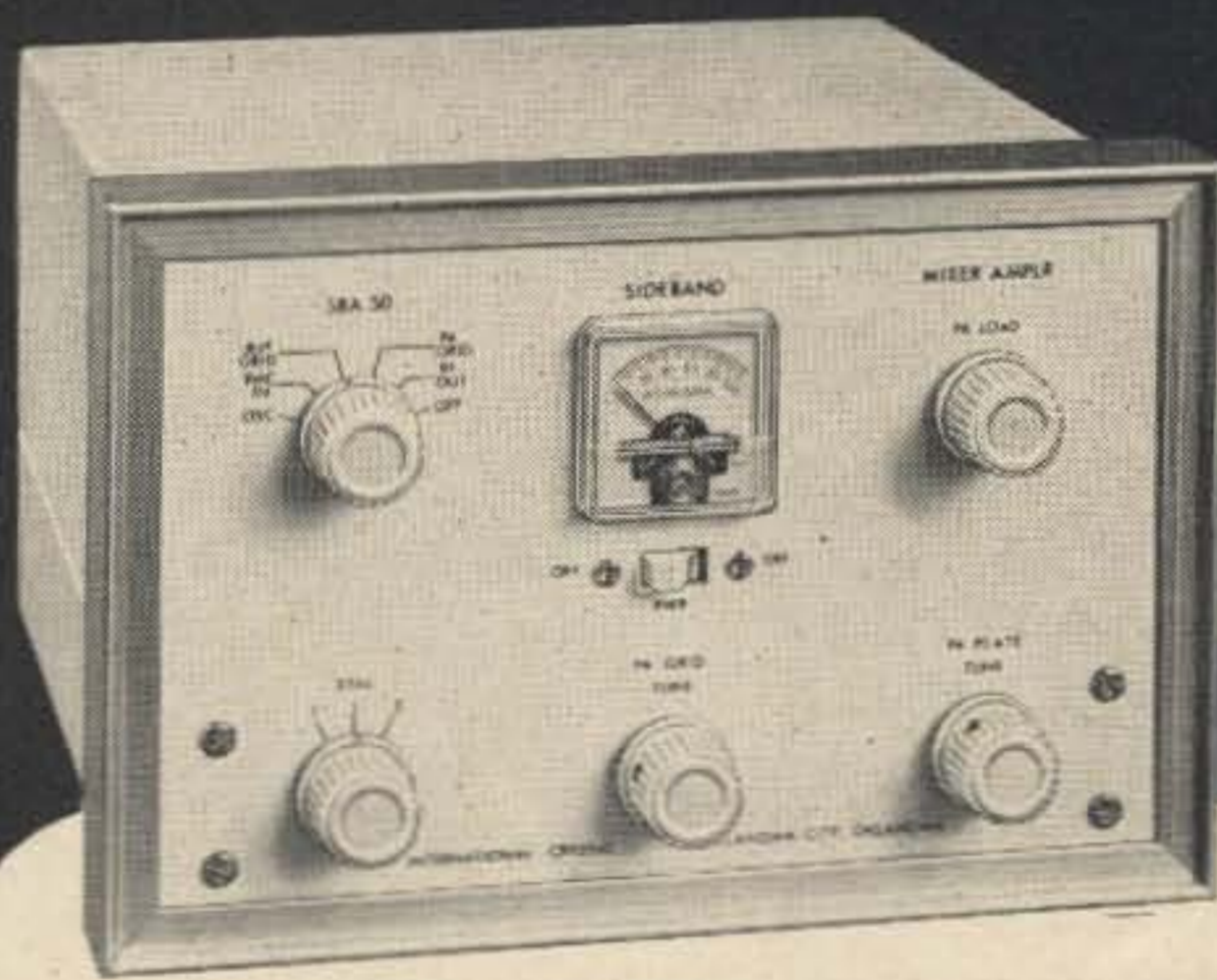Order direct from
International Crystal Mfg. Co.



Model SBA-50

SPECIFICATIONS:

Mixer-Amplifier 50-54mc

Tubes: 6U8A Oscillator-Mixer

12BY7A Amplifier

6360 Linear power amplifier

Drive: Requires 9mc sideband signal from SBX-9

Output: SSB single tone 10 watts

Controls: On-Off Power

PA Grid Tune

PA Plate Tune

PA Load Tune

Metering Switch

Metering: Oscillator

9mc Drive

Buffer Grid

PA Grid

RF Out

Crystals: Three positions, uses 3rd

overtone 41-45mc range.

Crystal frequency = final

frequency —9mc

Misc: Accessory socket provided for

connecting keying circuit to

SBX-9. Comes with three crystals.

Specify frequency when ordering.

For operation on 117 vac 60 cycle power.

\$145.00



CRYSTAL MFG. CO., INC.

18 NO. LEE • OKLA. CITY, OKLA. 73102

Editor's Ramblings

Paul Franson WA1CCH

Abbreviations—again

I've been very surprised at the smallness of the uproar over our adopting the modern *hertz* for the older term, *cycles per second*. We've only received three letters so far, and two of them end with the clever pun, "... it *hertz*."

The tables on this page list the rest of the relevant abbreviations for units from the international system adopted by the NBS, the IEEE, and many U.S. magazines—including 73. Most of the changes are minor, and serve mostly to avoid the inconsistencies of the older system: *m* means *milli*, *micro* and *mega* in *mh*, *mf* and *mc* as used by older magazines. Nevertheless, some of them look a bit peculiar at first, though not as bad as *Hz*. In a few years, we'll be so used to the newer system that the old abbreviations will look as odd as the old schematics in *Radio* or pre-war QSTs. Here are some of the abbreviations we normally use:

capacitance: pF, μ F
 current: μ A, mA, A
 frequency: Hz, kHz, MHz
 inductance: μ H, mH, H
 power: μ W, mW, W, kW
 power gain: dB
 resistance or impedance: Ω , k Ω , M Ω
 time: ms, s
 voltage: μ V, mV, V, kV

Some of the units are rarely used in elec-

Abbreviations for Basic Units

Name	Quantity	Abbreviation
ampere	current	A
bel	gain, loss	B
coulomb	charge	C
farad	capacitance	F
henry	inductance	H
hertz (old cps)	frequency	Hz
joule	work, energy	J
meter	length	m
ohm	resistance	Ω
second	time	s
siemens (old mho)	conductance	S
volt	voltage	V
watt	power	W
weber	magnetic flux	Wb

Note that abbreviations for units derived from proper names are capitalized. Other units such as hour and foot can also be used, of course. Liter and ampere-hour are units of capacity, but the farad is the unit of capacitance.

tronics, of course. Many of the prefixes are also rare: *tera* is almost unknown; *giga* is used only in gigahertz; *hecto* and *deka* aren't used; *deci* is used only in *decibel* and *centi* in *centimeter*; *nanofarad* (.001 μ F or 1000 pF) is used in continental Europe but not often in the U.S.; *femto* and *atto* aren't used in radio—at least by hams.

Many possible combinations of prefixes and units are not used or are rarely used. Here are some surprises:

MC: megacoulomb
 μ S: microsiemens (micromho)
 mF: millifarad (1000 μ F)
 MF: megafarad (1,000,000,000 μ F)
 MA: megaampere (1,000,000 ampere)

Confused? You needn't be. The whole system is straightforward and easy to understand after a few minutes' study.

... WA1CCH

Prefixes Used with Basic Units


Name	Abbreviation	Multiply by
tera	T	10^{12} or 1,000,000,000,000
giga	G	10^9 or 1,000,000,000
mega	M	10^6 or 1,000,000
kilo	k	10^3 or 1,000
hecto	h	10^2 or 100
deka	da	10
deci	d	10^{-1} or 1/10 or .1
centi	c	10^{-2} or 1/100 or .01
milli	m	10^{-3} or .001
micro	μ	10^{-6} or .000 001
nano	n	10^{-9} or .000 000 001
pico	p	10^{-12} or .000 000 000 001
femto	f	10^{-15} or .000 000 000 000 001
atto	a	10^{-18} or .000 000 000 000 000 001

Some prefixes are capitalized and some small. The distinction is important. Not all of the prefixes are used in electronics.

CONVENIENCE ENGINEERED HAM GEAR

by *Waters*

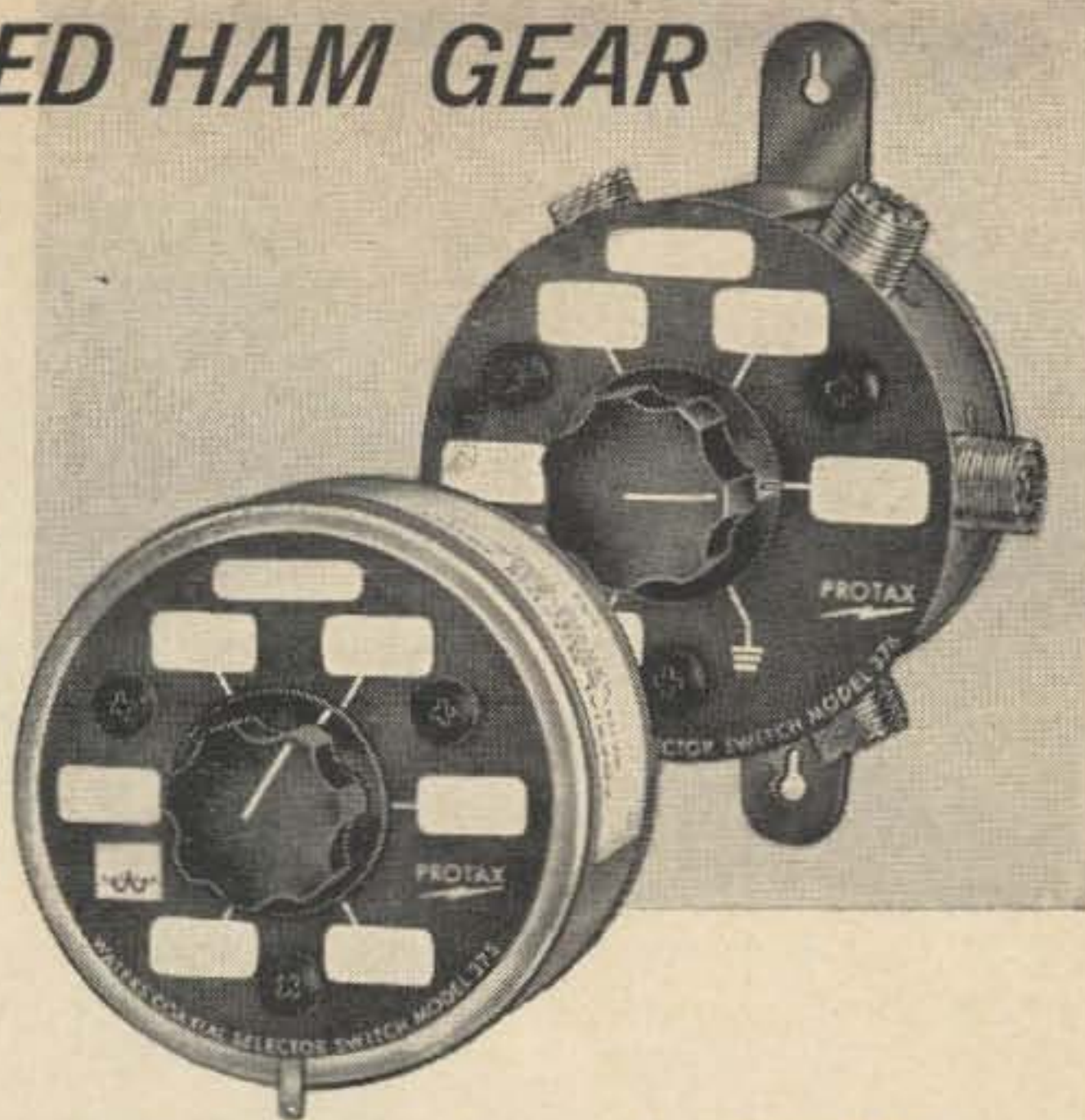PROTAX™ COAXIAL ANTENNA SWITCH with AUTOMATIC GROUNDING



Another first from Waters! Now, as easily as you switch from beam to dipole . . . from 40 meters to 75, you can switch your entire antenna system to ground with the newest addition to our line of coaxial switches, PROTAX, automatic-grounding coaxial antenna switch! Designed with the same advanced engineering skill that outmoded all other coaxial switches two years ago, PROTAX is another giant step forward in "Convenience Engineered" ham gear by Waters. In effect, PROTAX is two switches in one . . . a regular antenna-selector switch with power-carrying capacity of 1,000 watts that becomes a grounding switch for all antennas (leaving the receiver input open) when the rig is not in use. In two distinctive models: #375 — six position and ground with back connectors; #376 — five position and ground with connectors in radial arrangement. (#376 has its own wall-mounting bracket.)

Model 375 \$13.95

Model 376 \$12.50

Waters AUTO- MATCH

You'll boost your signals up to 4 db with AUTO-MATCH, the built-to-last mobile antenna. Operates all bands with only a change of Top-Center loading coils . . . has rugged new fold-over hinge . . . fits any standard base or bumper mount.

PRICES

MAST 370-1	\$12.95
RADIATOR TIP 370-2	9.95
COIL 370-75	15.95
COIL 370-40	14.95
COIL 370-20	13.45
COIL 370-15	12.75
COIL 370-11	11.95
COIL 370-10	11.95



Waters

REFLECTOMETER

Amazing new REFLECTOMETER tells you both forward and reflected power in RF watts on every transmission. Two separate scales insure accurate readings to 1000 watts. VSWR easily determined, too! Complete with directional coupler and cable.

Model 369 \$115.00




Model 3002

Waters UNIVERSAL HYBRID COUPLER II PHONE PATCH

The ultimate in phone patches providing effortless, positive VOX operation . . . and it also connects tape recorder for both IN and OUT. Built-in Waters "Compreamp" increases low telephone line signals while simultaneously preventing over-modulation. "Compreamp" also operates alone (without patch) with station mike.

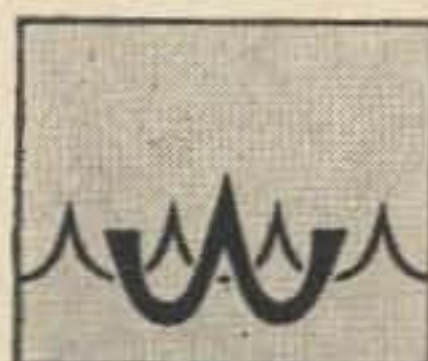
Model 3002 \$69.95
(less battery)
Model 3001 \$49.50
(without "Compreamp")



WATERS

MANUFACTURING INC.
WAYLAND, MASSACHUSETTS

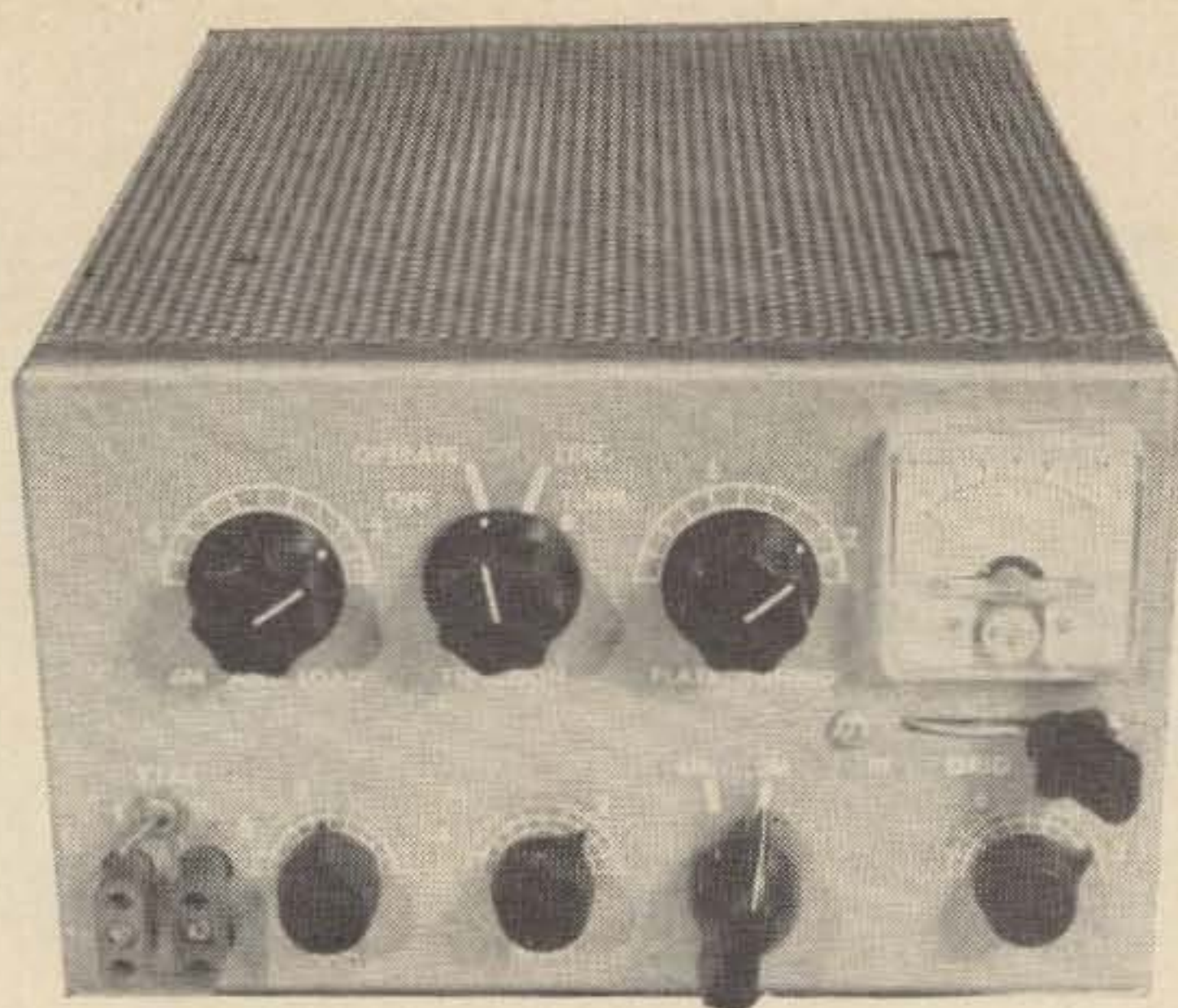WATERS PRODUCTS ARE SOLD ONLY THROUGH WATERS QUALIFIED DISTRIBUTORS



Del Crowell K6RIL
1674 Morgan Street
Mountain View, Cal.

A Compact Transmitter for Six and Two

Here's one of the cleverest, simplest and most effective two-band VHF transmitters we've seen. Wouldn't you like one?

Many VHF operators have, at one time or other, had the urge to have a signal with punch. After looking through many issues of magazines and handbooks, I noticed there is very little information published on band-switching VHF transmitters. This inspired me to design this compact transmitter, in which changing bands and retuning can be done in very few minutes. Using 600 volts on the final the power output is approximately 60 watts on 2 and 70 watts on 6.

This article covers the rf section only. The power supply and modulation is left up to the builder.

Circuit description

The circuit is a simple but very effective design using the following tube lineup: A 6CL6 oscillator (VI) uses crystals in the 8-9 or 24-27 MHz range and the plate tunes from 23.5 to 27 MHz. Next a 6CL6 multiplier (V-2) either doubles to 50 MHz or triples to 72 MHz. The plate is tuned to 72 MHz on 2 meters and on 6 meters a shunt capacitor C9 is switched in to tune the 50 MHz range. The drive uses a 7558 as a straight thru amplifier on 6 meters, or as a doubler on 2 meters, because of loss of driving power on 2 meters the screen voltage on V2 and V3 is increased by shorting out a 27 k resistor R-11 with the bandswitch. This increases the driving power to obtain satisfactory final grid drive. The 7558 uses an unusual tank circuit which has two resonances. On 6 meters, one half of L3 and L4 is resonant at 50 MHz and on 2 meters L3 is resonant at 144 MHz, with L4 acting as an rf choke. C-15 is adjusted so that at 50 MHz the capacitance is near maximum and at 144

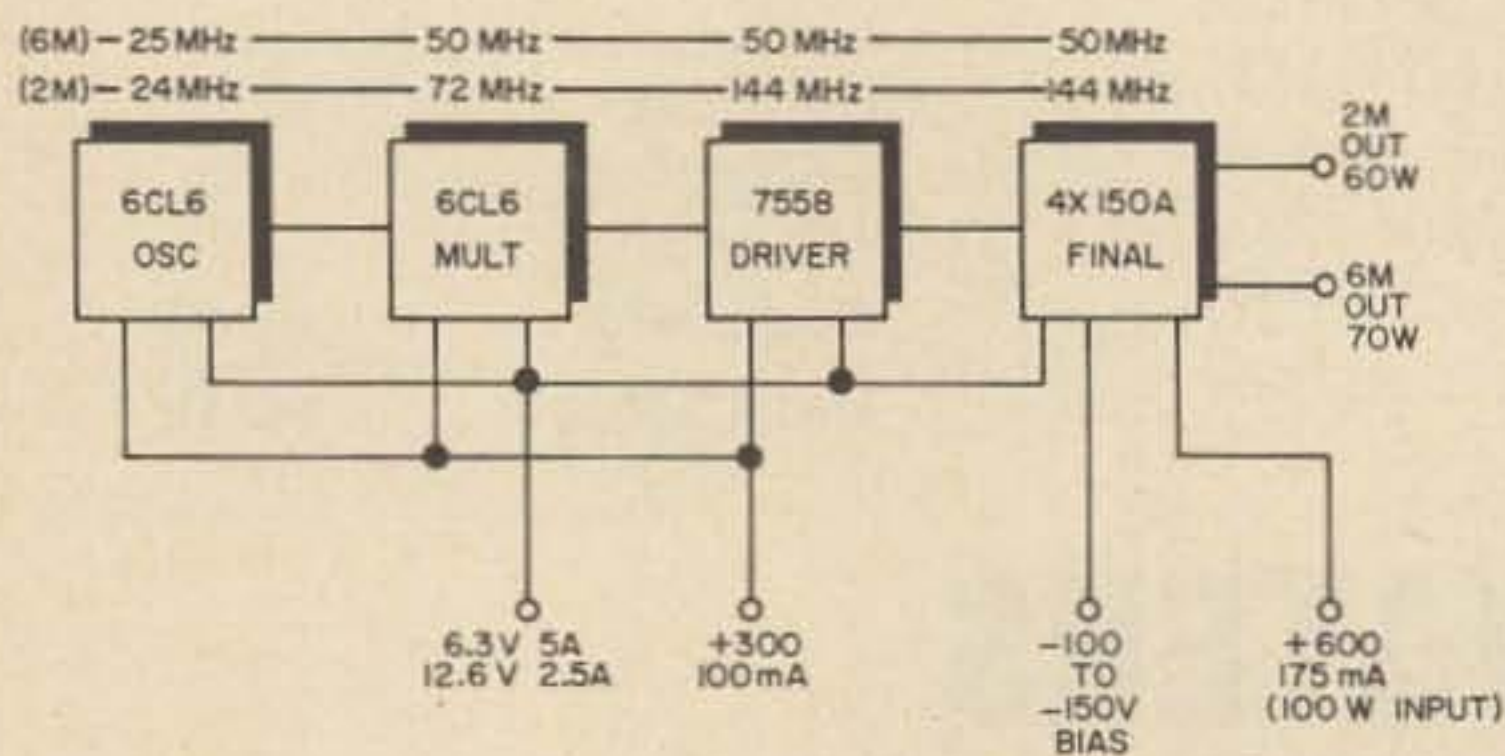


Fig. 1. Block diagram of the simple six and two meter band-switching transmitter with 60 watts output.

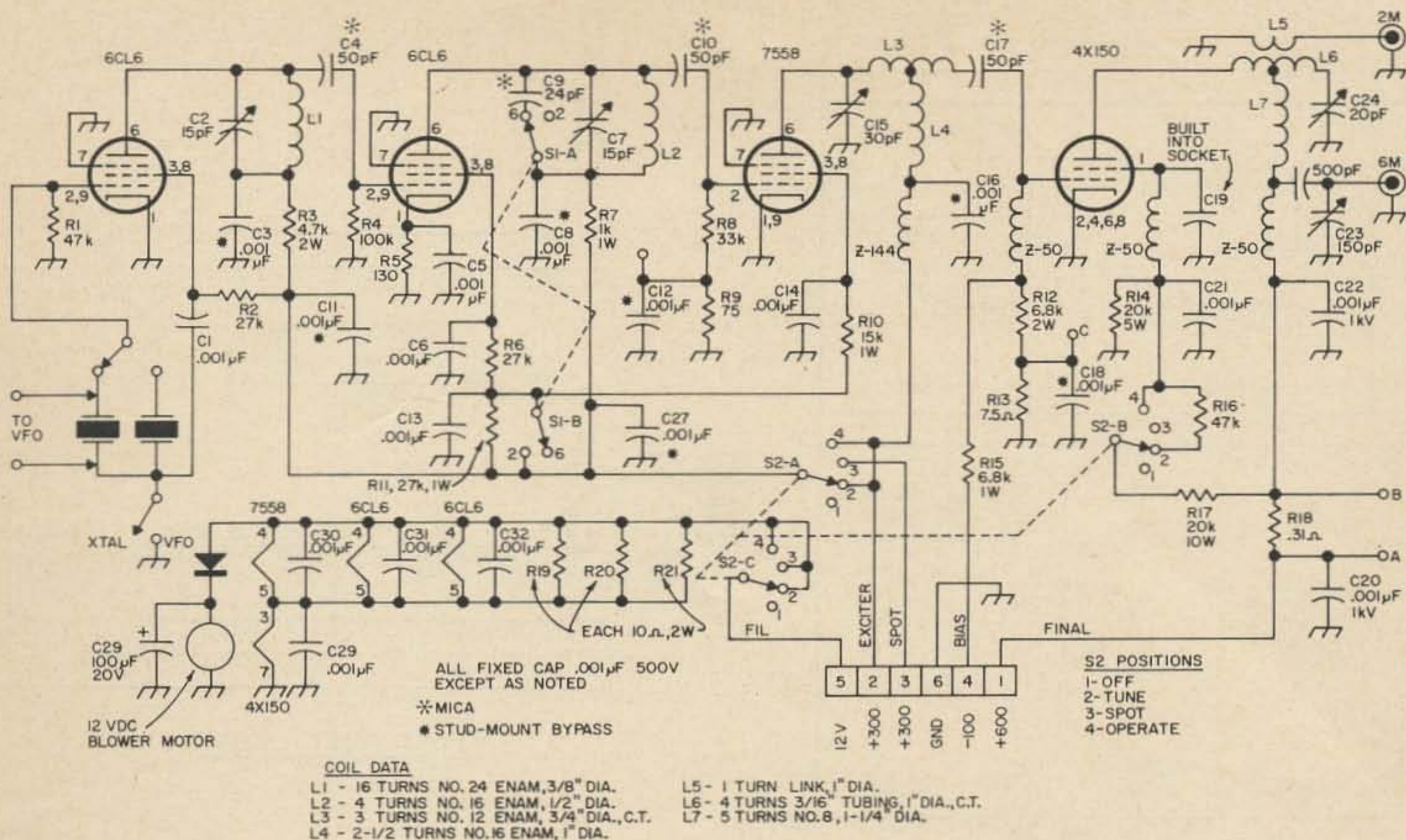


Fig. 2. Schematic of K6RIL's bandswitching six and two meter transmitter. Output from the

4X150A with about 100 watts input at 600 volts is about 60 watts. For metering, see Fig. 3.

MHz C-15 is near minimum. This prevents the resonances from becoming harmonically related, as example, while tuned to 50 MHz the 144 tank will tune near 130 MHz.

The 4X150A performs very nicely as the final amplifier. By using low plate voltage the tube requires a small amount of air flow to cool. Any small fan which will move air thru the socket and fins would do very well, (be sure to use the chimney). The final operates in class C service and requires at least 8 mA of grid current for plate modulation. The tank circuit L6 and L7 is similar to the

one described for V3 (7558), operates as a link coupled output on 2 meters with L7 acting as the rf choke. On 6 meters the tank operates as a pi network output, providing separate outputs for 2 meters and 6 meters, again the tank should be adjusted with C-24 at minimum capacitance for 2 meters and maximum for 6 meters. C-23 adjusts the pi network loading for the 6 meter output. On 2 meters the link is inserted about half way for optimum coupling.

If plate modulation is used the screen must be modulated approximately 30% in phase with the plate. Screen voltage is obtained by a resistive divider from the plate supply. Adjusting the screen voltage to less than 200V will allow about 25% increase on modulation peaks. With



Back view of the transmitter showing the small blower, power receptacle, and the output jacks.



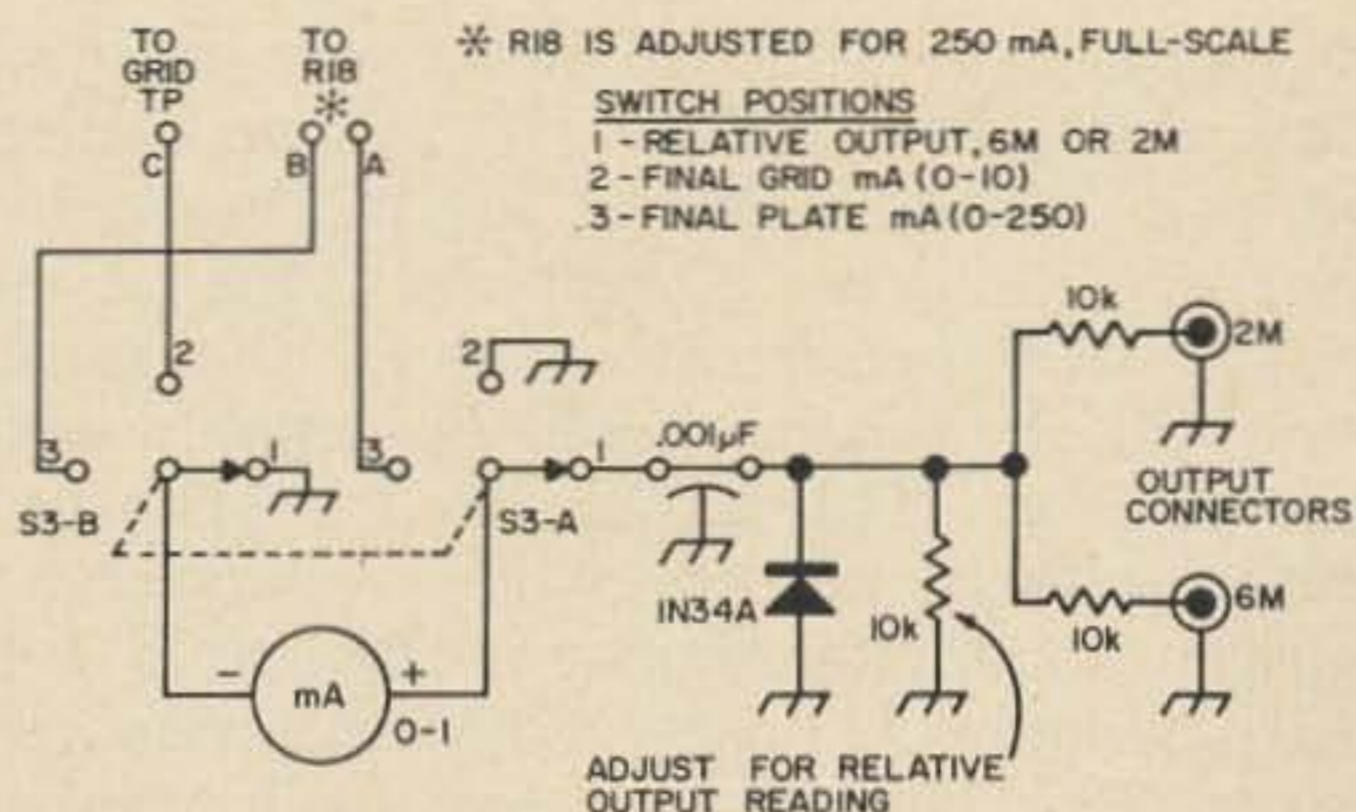
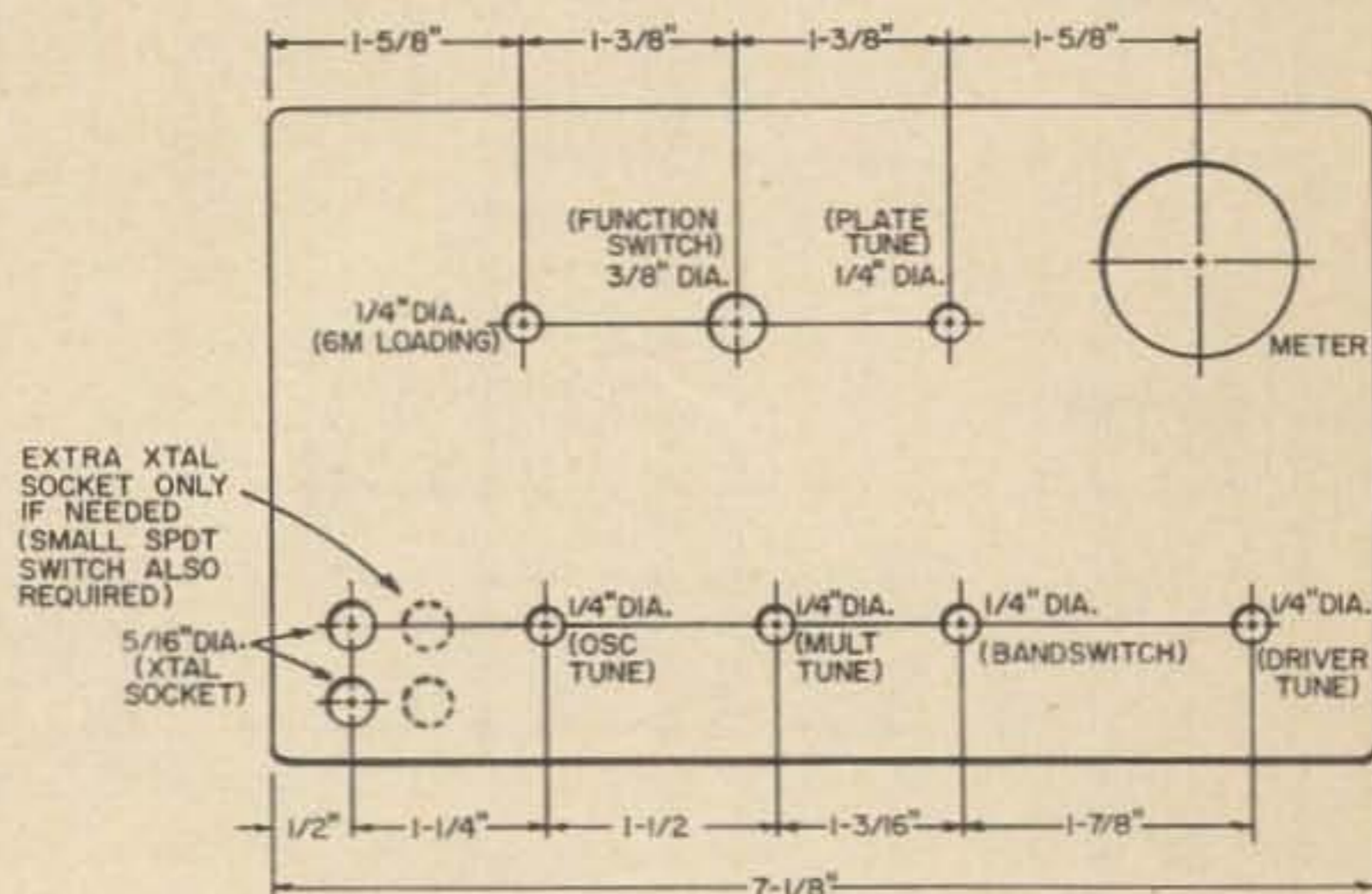



Fig. 3. Metering circuit for the six and two transmitter.

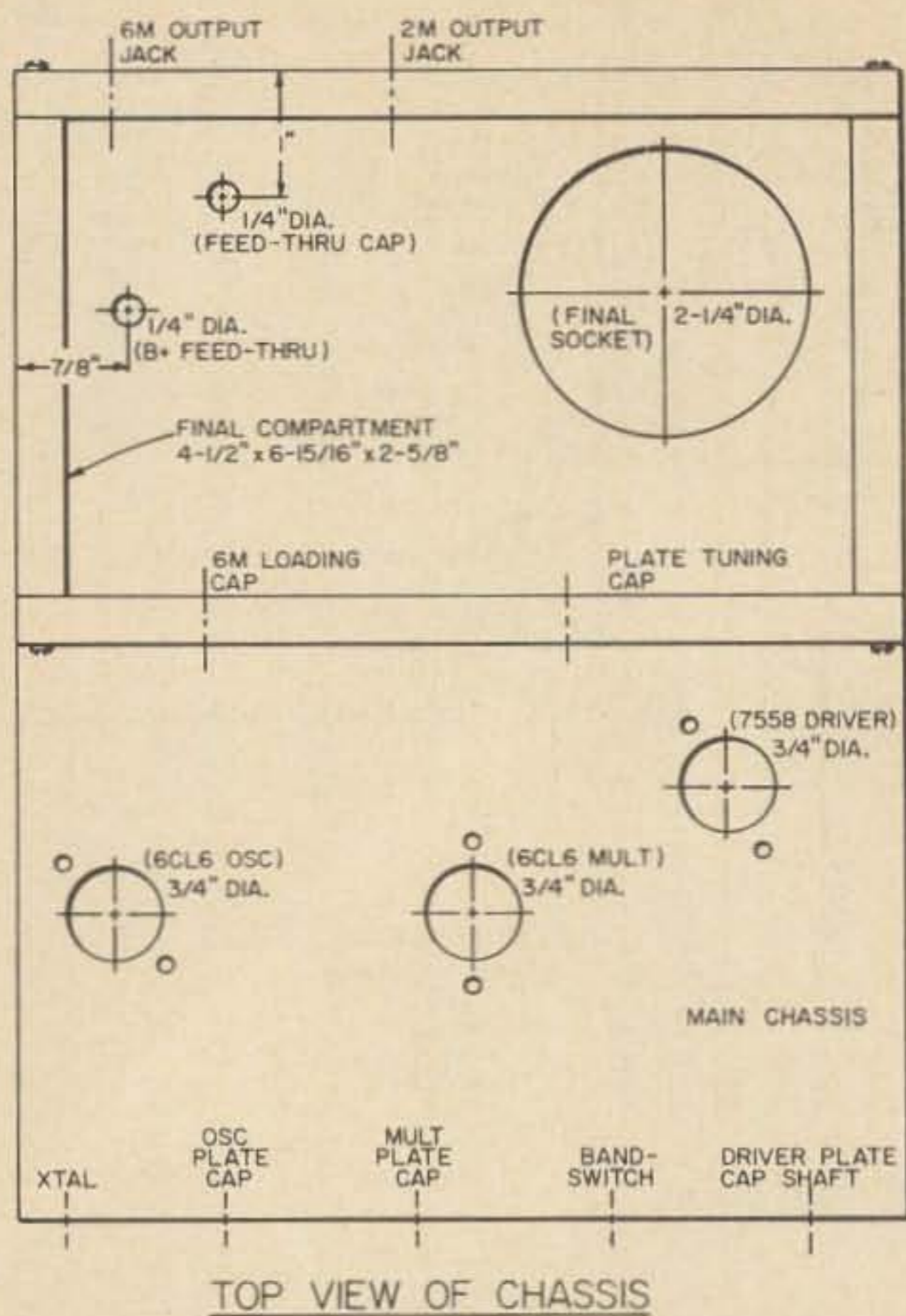

FRONT PANEL LAYOUT

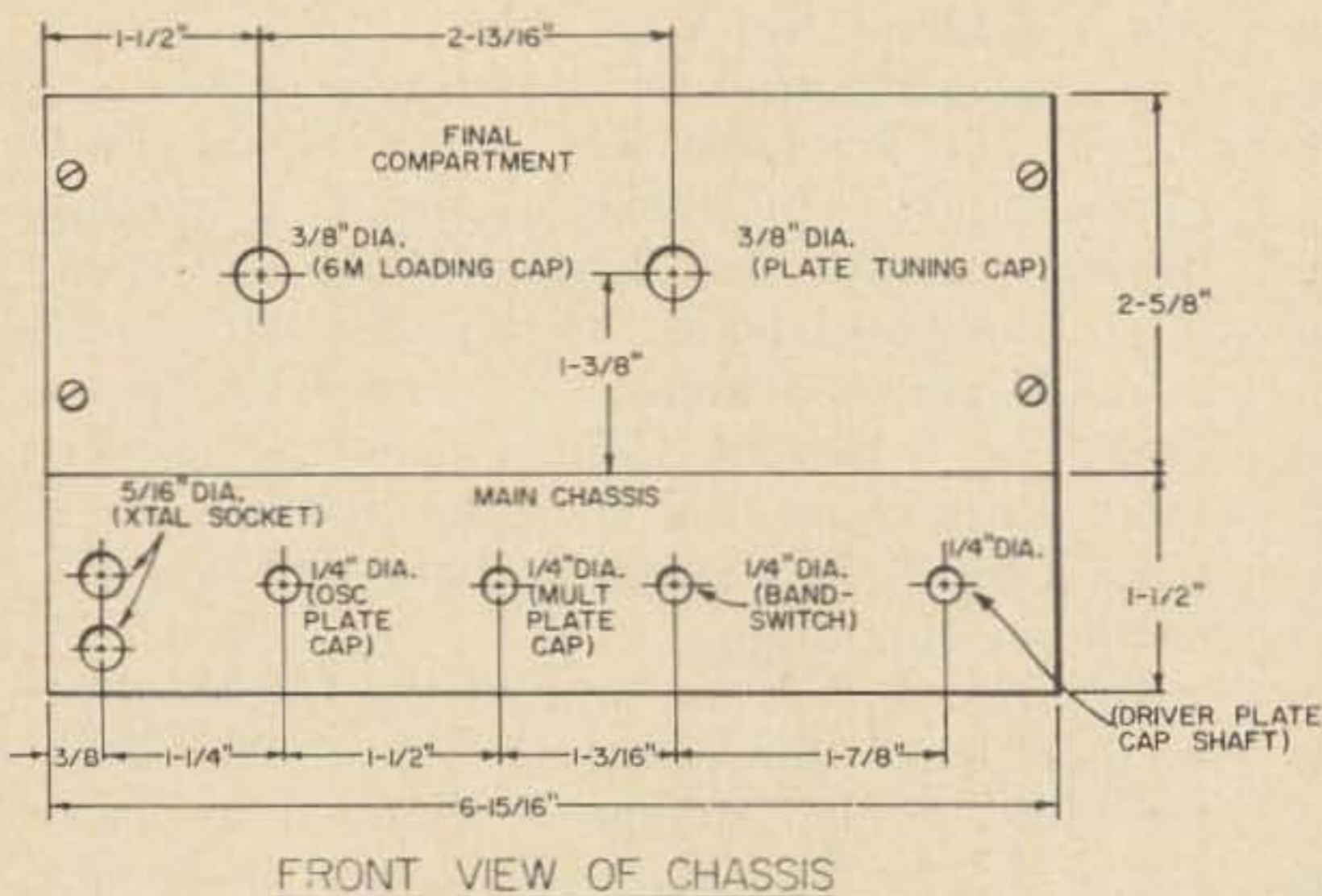

FRONT VIEW OF CHASSIS

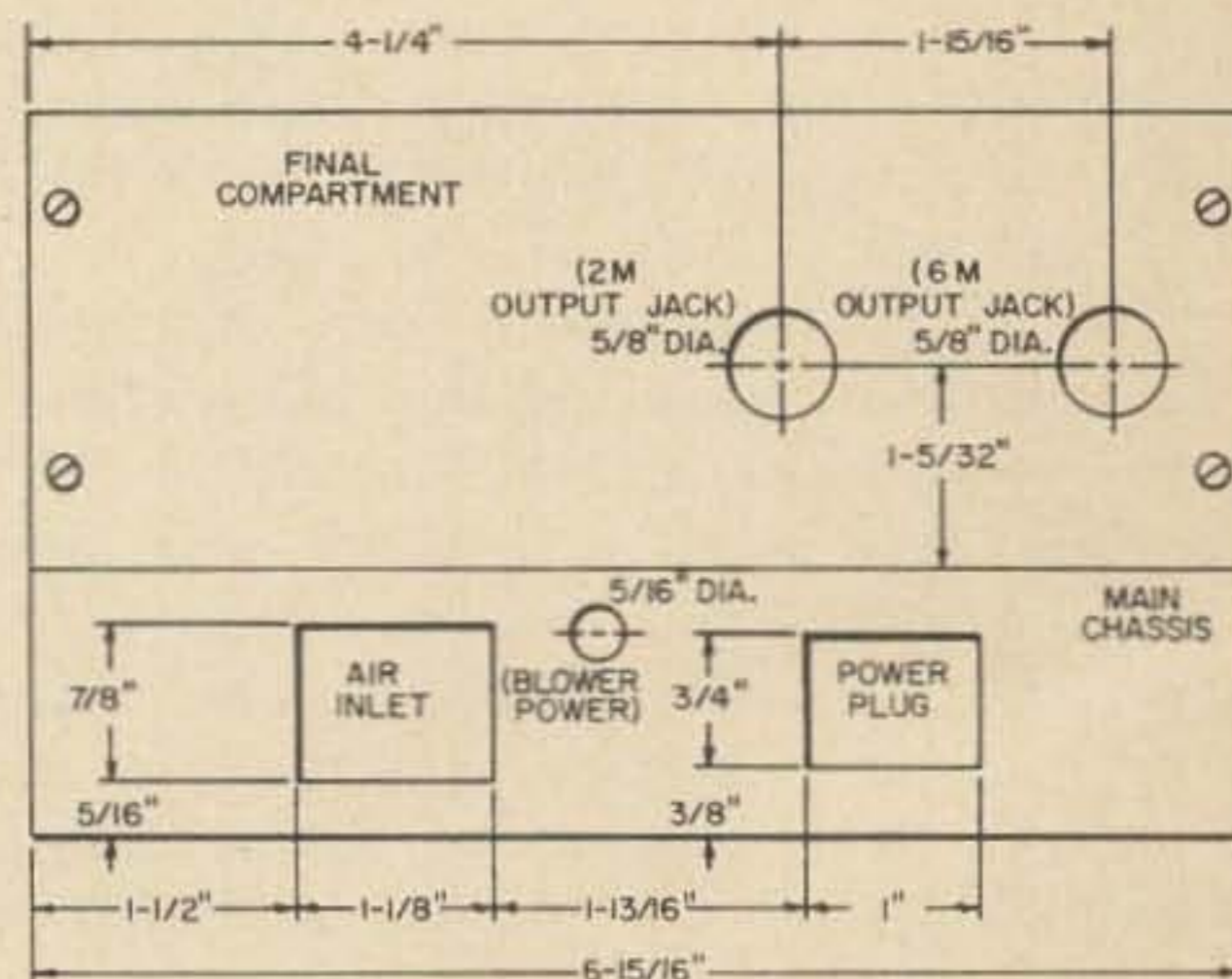

REAR VIEW OF CHASSIS

Fig. 4. Layout of the six and two transmitter. These drawings are one-third full size. Cabinet


used is a California Chassis Company LTC-436. See comments at end of article for some modifications.

this method the 4X150A shows very good stability, using 600 V B at 170 mA and screen voltage of 200 V at 10 mA the transmitter delivers approximately 60 watts at 2 meters and 70 watts at 6 meters with close to 100% modulation, the modulator should be capable of 50 watts or more. This transmitter has been used mobile with a transistor power supply and transistor modulator similar to the one in 1962 ARRL Handbook (page 478) with very nice results. The blower used for cooling was a small dc motor and squirrel cage blower operating from the 12 volt battery.

Construction details

The chassis and cabinet shown in pictures is a ready made unit by California Chassis Co., Lynwood, Calif., model LTC436, measures 4 3/8" H x 7 1/4" W x 9 1/4" D. Final tank compartment was fabricated from 1/16" aluminum and measures 4 5/8" x 6 15/16" x 2 5/8". A perforated cover allows air to escape but shields the rf. The bottom cover is made from 1/16" aluminum and seals the under side of the chassis to provide a pressurized compartment to cool the 4X150A. A homemade gasket seals between the blower and the chassis.

NEW FROM SWAN

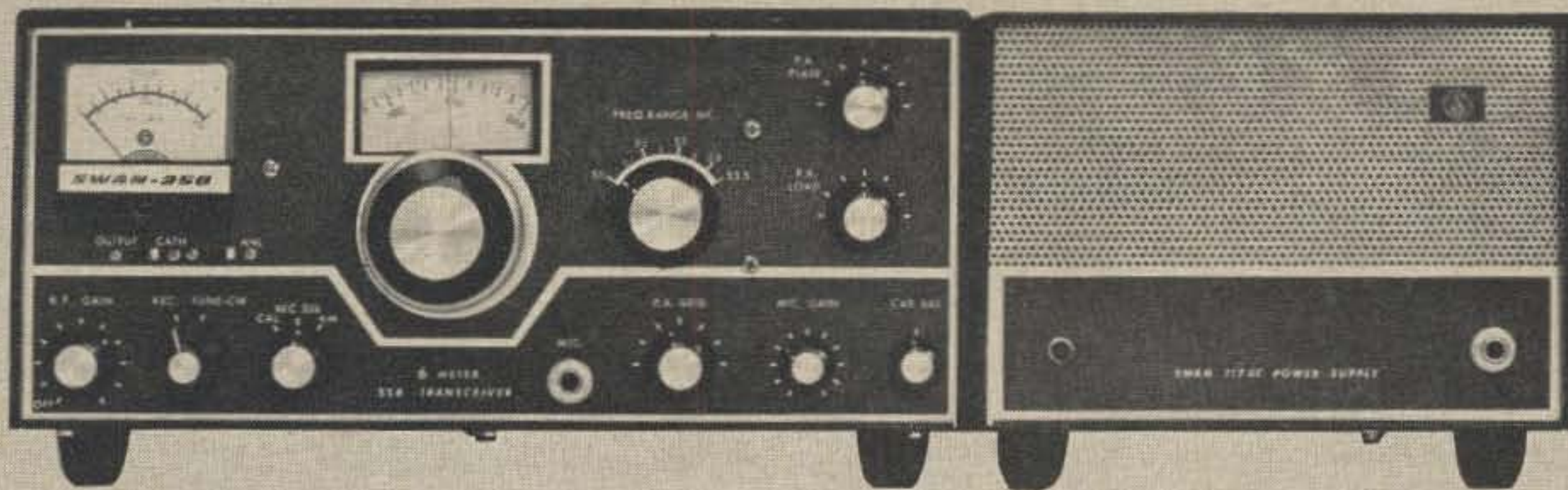


SWAN 250

6 METER SSB TRANSCEIVER

SPECIFICATIONS:

- ★ 240 watts P.E.P. input on single sideband, 180 watts cw input, 75 watts AM input with carrier insertion.
- ★ Two 6146B tubes in Power Amplifier.
- ★ Complete band coverage, 50-54 mc.
- ★ Velvet smooth vernier tuning covers 500 kc, calibrated in 5 kc increments.
- ★ Transmits and receives on Upper Sideband.
- ★ 2.8 kc bandwidth with crystal filter at 10.7 mc.
- ★ Single conversion design for minimum image and spurious.
- ★ 40 db unwanted-sideband suppression, 50 db carrier suppression.
- ★ Receiver noise figure better than 3 db. 6HA5 triode R.F. amp., 6HA5 triode mixer. Includes **Separate AM detector.**
- ★ **Automatic noise limiter.**
- ★ Audio response essentially flat from 300 to 3100 cycles.
- ★ Pi output coupling for matching wide range of load impedances.
- ★ Meter indicates either cathode current or relative output for optimum tuning and loading.
- ★ Provisions for adding 500 kc calibrator, or plug-in Vox unit.
- ★ Dimensions: 5½ in. high, 13 in. wide, 11 in. deep. Weight: 17 lbs.
- ★ Automatic noise limiter.
- ★ **Price, amateur net:**
Swan-250\$325

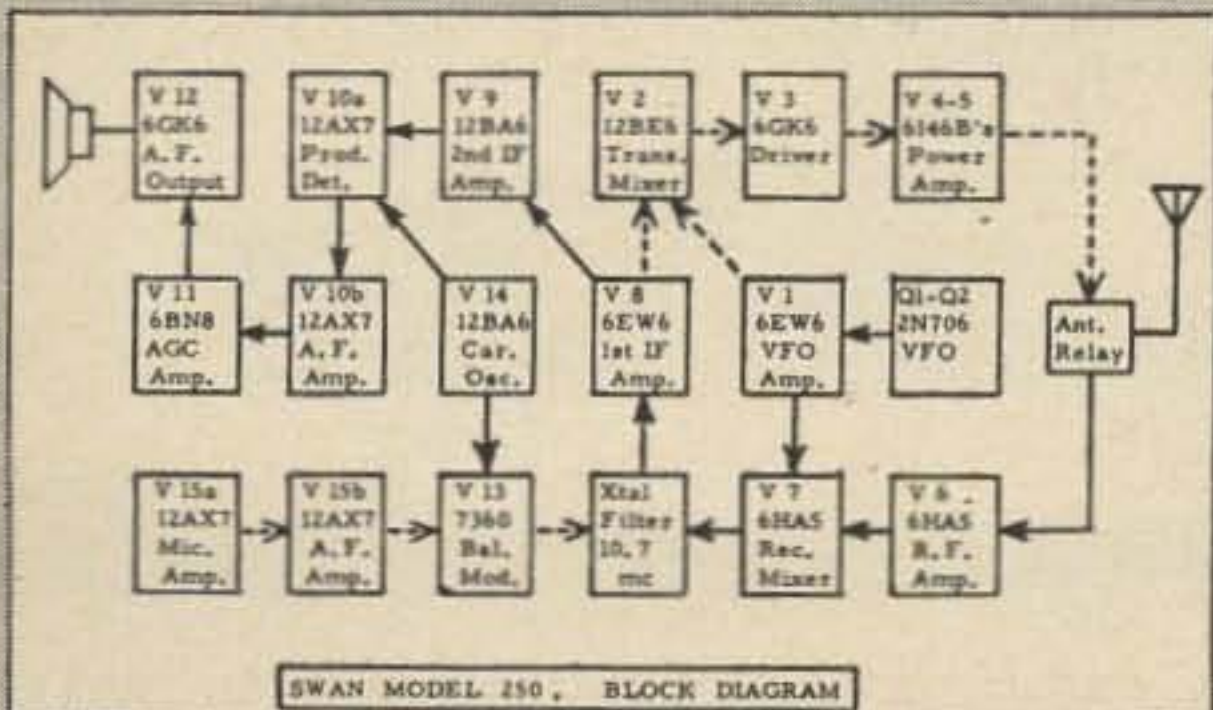External VFO for separate transmit-receive control available soon.



6 Meter Band Openings Increase!

With sun spot activity now on the increase, 6 meters is rapidly becoming one of the most interesting bands to operate, and the next few years will undoubtedly see tremendous activity on this band. Sporadic E openings are occurring several times each week over all parts of the country, making excellent contacts possible from Coast to Coast and over intermediate paths. With long F2 skip and trans-equatorial propagation to look forward to, plus the consistent ground wave and tropospheric scatter contacts made possible with the power of the Swan 250, there is practically no limit to the operating pleasure you can find in the VHF world above 50 mc.

The Swan 250 is at its best in the SSB mode, for which it was primarily designed. With 240 watts PEP input and an average beam antenna, its talk power does an outstanding job. To work your AM friends you simply insert carrier to 75 watts input, and they will read you loud and clear. AM reception is provided for by the receiver function switch. Also, a noise limiting circuit is effective on both AM and SSB.

The Swan 250 is engineered to provide the same excellent voice quality which has become the trademark of all Swan transceivers. And, naturally, the same customer service policy, second to none, applies to our VHF models.

If you are seriously interested in working 6 meters, see the new Swan 250 at your dealer. We are delivering now, but the back order list is getting longer, and we suggest you place your order soon.

73 Herb Johnson
W6QKI



SWAN
ELECTRONICS CORP.
OCEANSIDE, CALIFORNIA

6 and 2 Meter Transmitter Operating Voltages

	Osc 6CL6-V1		Mult 6CL6-V2		Driver 7558-V3		Final 4X150A-V4	
	2M	6M	2M	6M	2M	6M	2M	6M
Plate mA	15	15					170	175
Screen V	160	170	170	150	210	195	210	215
Screen mA	1.2	1.2	3.0	4.5	4.0	3.5	9.2	9.0
Grid V	-37	-37	-50	-70	-40	-42	-90	-95
Grid mA	.7	.7	.5	.7	1.25	1.35	13	14
Supply V	280	280	280	280	280	280	600	600
Plate V	190	200	240	260	270	250	600	600
Power output							60W	70W

Although the circuit shows the heaters wired for 12 V operation the builder may do as he chooses.


Voltages required are as follows 6 V at 5 Amps or 12 V at 2.5 amps and + 300 V at 100 mA for exciter section and + 500 to + 800 volts at 200 mA and - 130 V bias for final. Originally the final was wired for self bias but for mobile operation proved to be troublesome and fixed bias for protection was added later.

As shown in pictures the controls are marked with the proper positions for both bands as this simplifies changing bands. The panel meter monitors final grid current, plate

current and relative rf output. The chart shows the approximate readings for all tubes while tuned and operating on each band.


Power supply and modulator used can be any one of the units constructed from the many handbooks available on the subject. This is left up to the builder depending on the type of operation he desires.

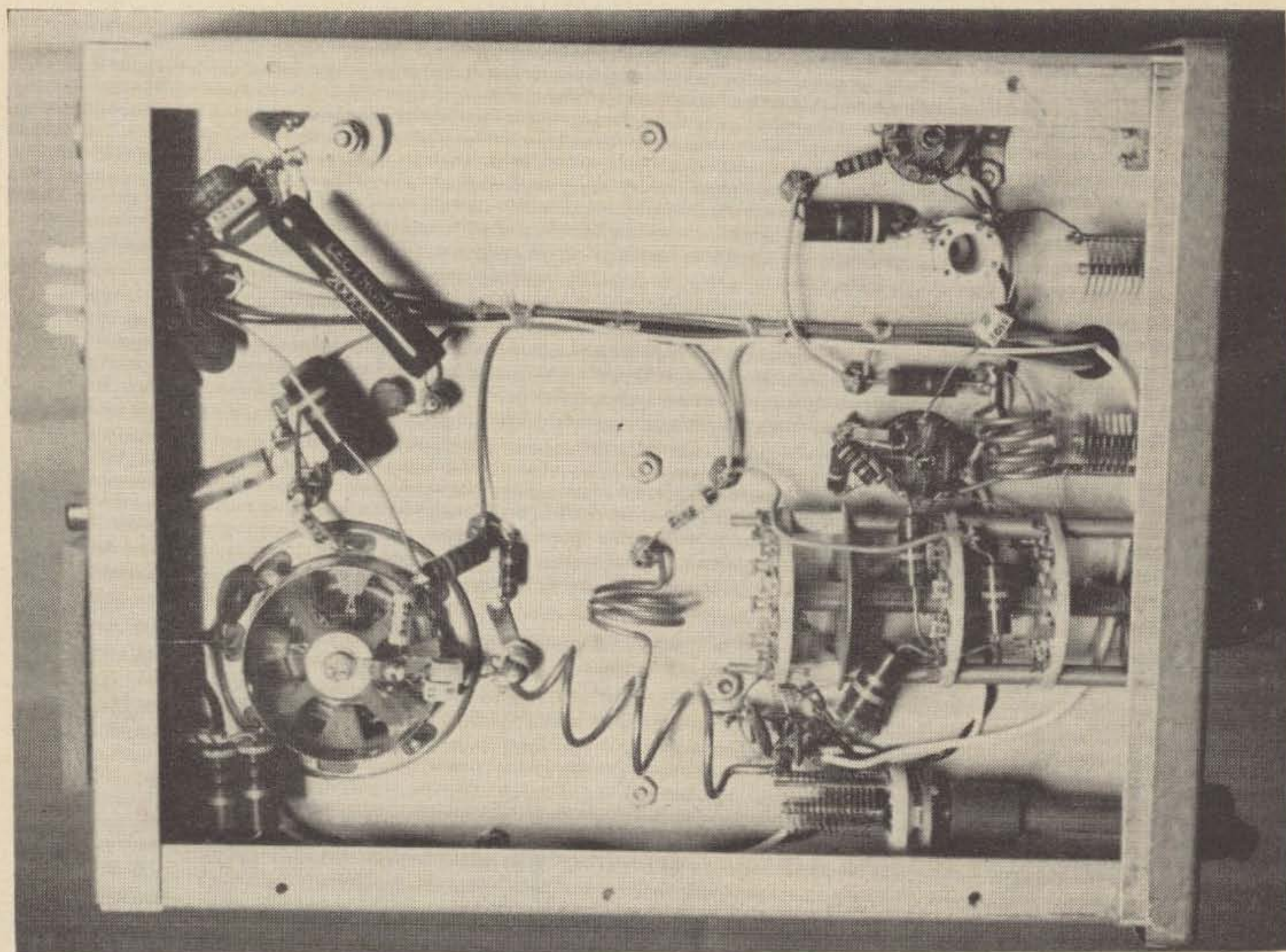This transmitter has proved to be very enjoyable for over two years of mobile operation. Crystal control was originally used and for the last 1½ years a transistor VFO to be described in 73 has given very good results. The transmitter has also been used in a fixed station with equal results. It won second place



Bottom view of the transmitter showing the two-band grid circuit of the 4X150A. It is very similar to the final plate tank. Note how simple and clean

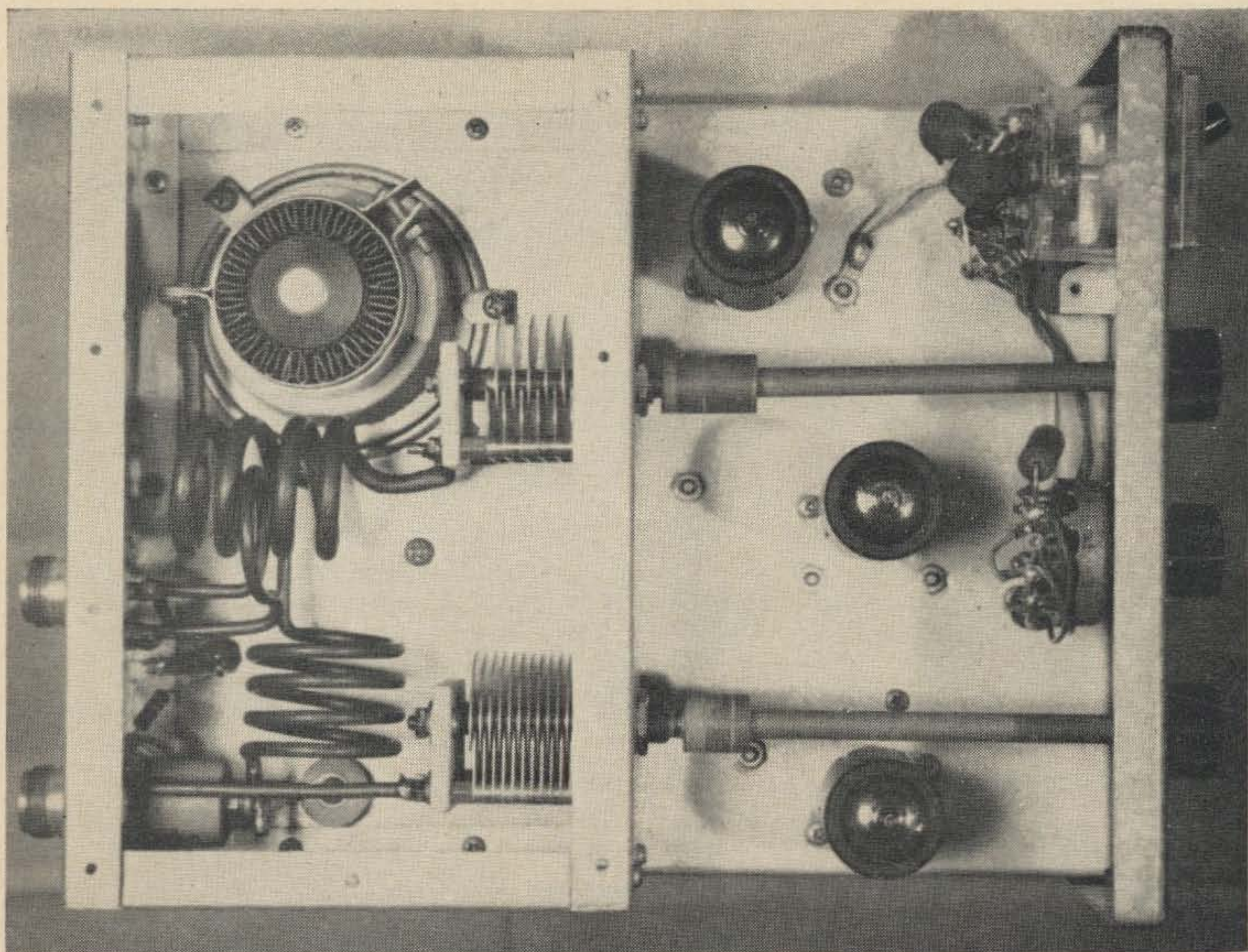the circuit is, especially when you realize that only two poles of that bandswitch are used. Note that the chassis must be sealed for cooling.



Top of K6RIL's transmitter. The right side contains the three exciter stages and the left the 4X150A final. The final tank is a clever two band circuit. On two, the coil next to the tube acts as a "series" tuned coil resonant at about 146 MHz

and the coil below it acts as an rf choke. The six meter loading capacitor has very little affect on two. The two meter output is from a link in the coil. On six, the two meter coil acts as a connection to the pi network tank used for tuning.

in the homebrew contest at ARRL Convention July 1965 at San Jose, Calif.

Using this transmitter has brought great pleasure and many compliments from other stations.

. . . K6RIL

Editor's note: I couldn't resist the simplicity of this transmitter, so built myself one. Of course, I made some changes. John Boyd WAØAYP bent me a nice case and chassis the same size as the one K6RIL used. I made the bottom row of controls on the panel symmetrical by using a smaller band switch and a five-position

switch for crystal-VFO switching instead of the panel sockets. A 5763 worked as a driver, but I imagine the 7558 would be better. I found that the 4X150A grid circuit tuned to both 72 and 144 MHz at once, so I added a 72 MHz series tuned trap there to prevent radiating some strong competition for channels 4 and 5. You could probably avoid this by fiddling with the tank instead of the trap. Instead of the socket recommended, I used a surplus one without a bypass, and the home-made bypass I used wasn't quite good enough, so I'd suggest that you use a good Johnson socket...WAICCH.



telrex "BALUN" FED INVERTED "V" ANTENNA KITS

SIMPLE-TO-INSTALL, HI-PERFORMANCE ANTENNA SYSTEMS:

- 1 KW P.E.P. Mono-Band Kit... 1KMB1V/81K... \$21.95*
- 2 KW P.E.P. Mono-Band Kit... 2KMB1V/81K... \$26.95*

*Kit comprises, encapsulated, "Balun," copperweld, insulators, plus installation and adjustment instructions for any Mono-band 80 thru 10 Meters. Also available 2, 3, 4, 5 Band Models.



Mfd.
under Pat.
2,576,929

Write
for TELREX
PL 67

TELREX LABORATORIES
ASBURY PARK, N.J. 07712

Now A Flip-Of-A-Switch Selects Transceive Or



New HEATHKIT® SB-301 amateur band receiver

With These New Extra-Performance Features

- RTTY position on mode switch — SB-301 is a fully capable RTTY receiver
- 15 to 15.5 MHz coverage for WWV reception
- Built-in switch-selected ANL
- Front-panel switching for control of 6 and 2 meter plug-in converters — enables complete 80 through 2 meter amateur band coverage
- Improved product detector and audio circuitry
- Simplified assembly procedure through "sub-pack" packaging and assembly techniques

Plus These Pace-Setting Features That Have Already Made The SB-300 Famous In Amateur Radio

- 80 through 10 meter AM, CW, & SSB reception with all crystals furnished
- Crystal controlled front-end for same rate tuning on all bands
- Famous Heath factory-assembled & tuned LMO for the ultimate in high stability and linear tuning
- 1 kHz dial calibration — 100 kHz per dial revolution
- Bandspread equal to 10 feet per megahertz
- Tuning dial to knob ratio approximately 4-to-1
- The unequaled-satisfaction of using a truly high-performance receiver you have assembled yourself

THE NEW SB-301 SETS "THE STATE OF THE ART" FOR AMATEUR BAND RECEIVERS. The new 15 to 15.5 MHz tuning range enables the most accurate attainable frequency check with the built-in 100 kHz crystal calibrator and WWV . . . and as you read the specifications, notice the Heath pre-built LMO surpasses the tuning characteristics of every other receiver on the market. What's more, if your QTH is a high noise location, you'll appreciate the new ANL, providing excellent impulse noise rejection.

NEW "SUB-PACK" PACKAGING & ASSEMBLY SPEEDS CONSTRUCTION TIME. Components are packaged separately for each phase of construction . . . saves you time in selecting components . . . lets you see your progress more clearly as each phase is completed. Order the new SB-301 for unmatched value in a deluxe AM, CW, SSB, and now RTTY amateur band communications receiver.

Kit SB-301, Amateur Band Receiver, less speaker, 23 lbs.	\$260.00
SBA-301-1, Optional AM crystal filter (3.75 kHz), 1 lb. . .	\$20.95
SBA-301-2, Optional CW crystal filter (400 Hz), 1 lb. . . .	\$20.95
Kit SBA-300-3, 6-Meter Plug-in Converter, 2 lbs.	\$19.95
Kit SBA-300-4, 2-Meter Plug-in Converter, 2 lbs.	\$19.95
Kit SB-600, Communications Speaker, 5 lbs.	\$17.95

SB-301 SPECIFICATIONS — Frequency range (megahertz): 3.5 to 4.0, 7.0 to 7.5, 14.0 to 14.5, 15.0 to 15.5, 21.0 to 21.5, 28.0 to 28.5, 28.5 to 29.0, 29.0 to 29.5, 29.5 to 30. Intermediate frequency: 3.395 megahertz. Frequency stability: Less than 100 Hz per hour after 20 min. warmup under normal ambient conditions. Less than 100 Hz for $\pm 10\%$ line voltage variation. Visual dial accuracy: Within 200 Hz on all bands. Electric dial accuracy: Within 400 Hz on all bands after calibration at nearest 100 kHz point. Backlash: No more than 50 Hz. Sensitivity: Less than 0.3 microvolt for 10 db signal-plus-noise to noise ratio for SSB operation. Modes of operation: Switch selected; LSB, USB, CW, AM, RTTY. Selectivity: RTTY; 2.1 kHz at 6 db down, 5.0 kHz at 60 db down (crystal filter supplied). SSB; 2.1 kHz at 6 db down, 5.0 kHz at 60 db down (crystal filter supplied). AM; 3.75 kHz at 6 db down, 10 kHz at 60 db down (crystal filter available as accessory). CW; 400 Hz at 6 db down, 2.0 kHz at 60 db down (crystal filter available as accessory). Spurious response: Image and IF rejection better than 50 db. Internal spurious signals below equivalent antenna input of 1 microvolt. Audio response: SSB; 350 to 2450 Hz nominal at 6 db. AM; 200 to 3500 Hz nominal at 6 db. CW; 800 to 1200 Hz nominal at 6 db. Audio output impedance: Unbalanced nominal 8 ohm speaker and high impedance headphone. Audio output power: 1 watt with less than 8% distortion. Antenna input impedance: 50 ohms nominal. Muting: Open external ground at Mute socket. Crystal calibrator: 100 kHz crystal. Front panel controls: Main tuning dial; function switch; mode switch; AGC switch; band switch; AF gain control; RF gain control; preselector; connector & ANL switch; phone jack. Rear apron connections: Accessory power plug; HF antenna; VHF #1 antenna; VHF #2 antenna; mute; spare; anti-trip; 500 ohm; 8 ohm speaker; line cord socket; heterodyne oscillator output; LMO output; BFO output; VHF converter switch. Tube complement: (1) 6BZ6 RF amplifier; (1) 6AU6 Heterodyne mixer; (1) 6AB4 Heterodyne oscillator; (1) 6AU6 LMO osc.; (1) 6AU6 LMO mixer; (2) 6BA6 IF amplifier; (1) 6AU6 Crystal calibrator; (1) 6HF8 1st audio, audio output; (1) 6AS11 Product Detector, BFO, BFO Amplifier. Power supply: Transformer operated with silicon diode rectifiers. Power requirements: 120 volts AC, 50/60 Hz, 50 watts. Dimensions: 14 $\frac{7}{8}$ " W x 6 $\frac{3}{8}$ " H x 13 $\frac{3}{8}$ " D. Net weight: 17 lbs.

Independent Operation On This New SB-Combo



New HEATHKIT® SB-401 5-band SSB transmitter

With Expanded Versatility — Whether You're DXing, In A Round Table, Net, Or Rag-Chew

- A single panel switch selects transceive or independent operation of SB-401 and SB-301 (or SB-300) combination — no cable changing required • Can be operated as an independent transmitter with any receiver when SBA-401-1 crystal group is installed • New simplified assembly procedure through "sub-pack" packaging and assembly techniques

Plus The Innovations And Rugged Performance Capabilities That Have Put The SB-400 Among The "Standard-Bearers" of Amateur Radio

- A completely self-contained desk-top transmitter with built-in power supply • Built-in antenna change-over relay • Famous Heath pre-built & tuned LMO frequency control • ALC for higher talk power • Optimum power level for operation "bare foot" or as a driver — 180 watts PEP SSB, 170 watts CW • Crystal filter SSB generation • Operates upper or lower sideband • VOX and PTT control • The same uncompromized tuning calibration, linearity, and stability that have made the Heath SB-Series unequalled not only in specifications but on-the-air performance.

VALUE COMPANION TO THE SB-301 OR SB-300. The Heathkit SB-401 provides full transceive operation with the SB-301 or SB-300 . . . gives you outstanding performance 80-10 meters with single-knob LMO control. In addition the SB-Series "combo" goes from transceive to independent transmitter-receiver operation with a flip

of a single switch on the SB-401 front panel . . . perfect for DXing! The SB-401 derives all the necessary crystal oscillator voltages from the SB-301 or SB-300 . . . eliminates redundant circuitry! Include the SBA-401-1 crystal pack for complete, independent transmitter operation with receivers other than the SB-301 or SB-300.


Kit SB-401, 34 lbs. \$285.00
SBA-401-1, Crystal Pack, 1 lb. \$29.95

SB-401 SPECIFICATIONS — **Emission:** SSB (upper or lower sideband) and CW. **Power input:** 170 watts CW, 180 watts P.E.P. SSB. **Power output:** 100 watts (80-15 meters), 80 watts (10 meters). **Output impedance:** 50 to 75 ohm — less than 2:1 SWR. **Frequency range:** (MHz) 3.5 — 4.0; 7.0 — 7.5; 14.0 — 14.5; 21.0 — 21.5; 28.0 — 28.5; 28.5 — 29.0; 29.0 — 29.5; 29.5 — 30.0. **Frequency stability:** Less than 100 Hz per hr. after 20 min. warmup. **Carrier suppression:** 55 db below peak output. **Unwanted sideband suppression:** 55 db @ 1 kHz. **Intermodulation distortion:** 30 db below peak output (two-tone test). **Keying characteristics:** Break-in CW provided by operating VOX from a keyed tone (Grid block keying). **CW sidetone:** 1000 Hz. **ALC characteristics:** 10 db or greater @ 0.2 ma final grid current. **Noise level:** 40 db below rated carrier. **Visual dial accuracy:** Within 200 Hz (all bands). **Electrical dial accuracy:** Within 400 Hz after calibration at nearest 100 kHz point (all bands). **Backlash:** Less than 50 Hz. **Oscillator feedthrough or mixer products:** 55 db below rated output (except 3910 kHz crossover which is 45 db). **Harmonic radiation:** 35 db below rated output. **Audio input:** High impedance microphone or phone patch. **Audio frequency response:** 350-2450 ±3 db. **Power requirements:** 80 watts STBY, 260 watts key down @ 120 V AC line. **Dimensions:** 14⁷/₈" W x 6⁵/₈" H x 13³/₈" D.



FREE CATALOG

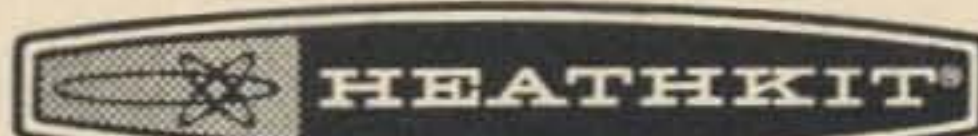Describes these and over 250 other Heathkits. Save up to 50% by building them yourself. Use coupon and send for your FREE copy!



HEATH COMPANY, Dept. 11-10
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Name _____
(Please Print)

Address _____

City _____ State _____ Zip _____

Prices & specifications subject to change without notice.

AM-169

Poorboy Mark II Quad

Here's an easy-to-handle three band quad made from inexpensive aluminum tubing.

As a result of the article in January, 1964 QST indicating that the cubical quad is the top choice among DX'ers, a renewed interest in this proven performer has been generated on the ham bands.

Many of you yearn to try the quad and have searched hopefully for a design worth investigation.

About the second paragraph of the usual quad article, the words "Take it to your friendly neighborhood welder . . ." leap up from the page to strike you where it hurts. Your neighborhood welder isn't so friendly--he charges, and how!! Besides, did you ever try to explain a "gizmo" that you understood perfectly to someone who didn't? So you get discouraged but still you read on . . .

A couple of paragraphs further down appears the word "bamboo," followed by more words telling you to take tape and wrap every cotton-picking inch of all that bamboo so the weather can't get at it quite so quickly. Let's see: 100' of bamboo. That means X hundred feet of tape, times Y number of hours wrapping time. Then after that comes . . . ah, heck!

Or, possibly the author urges: "Use wood dowel to join two pieces of EMT to form the crossarms." Dowel is cheap. So is EMT. But, wait! Wood isn't very strong, is it? And, didn't someone tell you that EMT was the stuff that skilled metallurgists developed especially so that it could be easily bent? Remember the time you tried to "unbend" a piece of tubing?

Shucks, you say, it just isn't worth it. Besides, this guy says that the element lengths

and the length of the boom are entirely different from the last article you read.

Take heart, OM, and read on about the Poorboy MK II, a quad that will solve all your problems--a tri-band quad made of aluminum tubing, light enough to be handled by a TV rotor, of simplest construction, weather-proof and at a cost of about two-thirds that of a commercial quad made of conventional bamboo.

With this quad, there is no "machine-shop" type work to be done, no welding, no special tools and, except for the tubing, no parts that cannot be obtained at your nearest TV wholesaler, or your neighborhood hardware dealer, etc.

The unique construction design of this quad eliminates the usual bugaboos normally found in the building and raising of the conventional quad. Its two-piece boom eliminates the necessity of having to turn it over on the ground. It can be hoisted into final operating position, one section at a time, by one man.

The Poorboy MK II has been in use at this QTH for five years, using an inexpensive TV rotor on a 30' slip-up mast and has survived the 90 mph winds of Hurricane Donna and, on two occasions, winds in excess of 70 mph. In addition, it has withstood winds in the 40-50 mph range which are fairly common locally. It is still in perfect alignment and recent examination disclosed that revarnishing of the wood parts was the only item needing attention.

Investigation of Bill Orr's handbook, *Quad Antennas* shows that the gain of a quad is almost constant with spacings from .1 to .2 wavelength between the driven element and the reflector. Further investigation shows that the impedance values in this range of spacings

Jim is a printer for the Tampa Tribune-Times.

vary from 60 to 110 ohms at an antenna height of $\frac{1}{2}$ wavelength. Arithmetic shows that .1 at 14 MHz is .15 at 21 MHz and .2 at 28 MHz.

The .1 and .15 spacings give impedances of about 60 and 75 ohms which are right smack in the middle of the ball park. But the .2 spacing gives an impedance of about 110 which is somewhat out in left field. The 28 MHz antenna could be fed with 93 or 125 ohm coax. However, in order to use the more readily available 72 ohm coax, an impedance value of about 90 ohms is obtained by the use of $7\frac{1}{2}$ " TV stand-off insulators on both the driven element and the reflector which reduces the element spacing at 28 MHz.

Further arithmetic at these spacings gives a boom length of 7'1" but the boom is cut to 7'9" to allow for mounting of the crossarms and a slight bowing effect.

The heart of the Poorboy MK II is the boom which is made from two 5-foot sections of standard $1\frac{1}{4}$ " galvanized TV mast (flared for stacking) joined into a single 10-foot length. Cut the boom 7'9" long, locating the center of the joint 1' from the center of the boom. This is to facilitate mounting to the boom clamp. Locate the large part of the joint on the short side of the boom. The driven elements are built on this short section so that any desired changes may be made by lowering only the driven elements. Minor changes to the reflectors can be made by repositioning the tuning stubs.

Drill a small hole through the joint and insert a steel bolt to insure exact realignment of the boom during assembly. The hole should be barely large enough to accommodate the bolt as insurance against the two sections slipping out of alignment at any time.

The boom clamp is simplicity itself and quite possibly you can scrounge up the materials at no cost to the XYL. Cut a piece of plywood at least $\frac{5}{8}$ " thick into an 8" square. Fasten an 8" square of galvanized sheet metal (about 18 gauge) on one side of the plywood with several small wood screws.

Use two U-bolt type TV mast clamps with serrated yokes to mount the boom diagonally across the wood side of the boom clamp with the TV clamps as near the corners as possible. Mount the metal side of the boom clamp to the mast with another identical pair of TV mast clamps. Use metal straps similar to those furnished with ordinary U-bolts to lock down on the wood side. Run the mast through the two remaining corners of the boom clamp with one TV clamp at the bottom corner and the second just far enough above the boom to insure clearance. Cut off the tip of the boom clamp above the top mast clamp.

Tubing designated 6061-T6 is generally considered to be an excellent choice for purposes as described here. This is based on economy, strength, corrosion resistance and general availability. Tubing generally comes in 12' lengths but try to get the $\frac{3}{4}$ " in an 18' length which is sometimes available. Use .049 wall


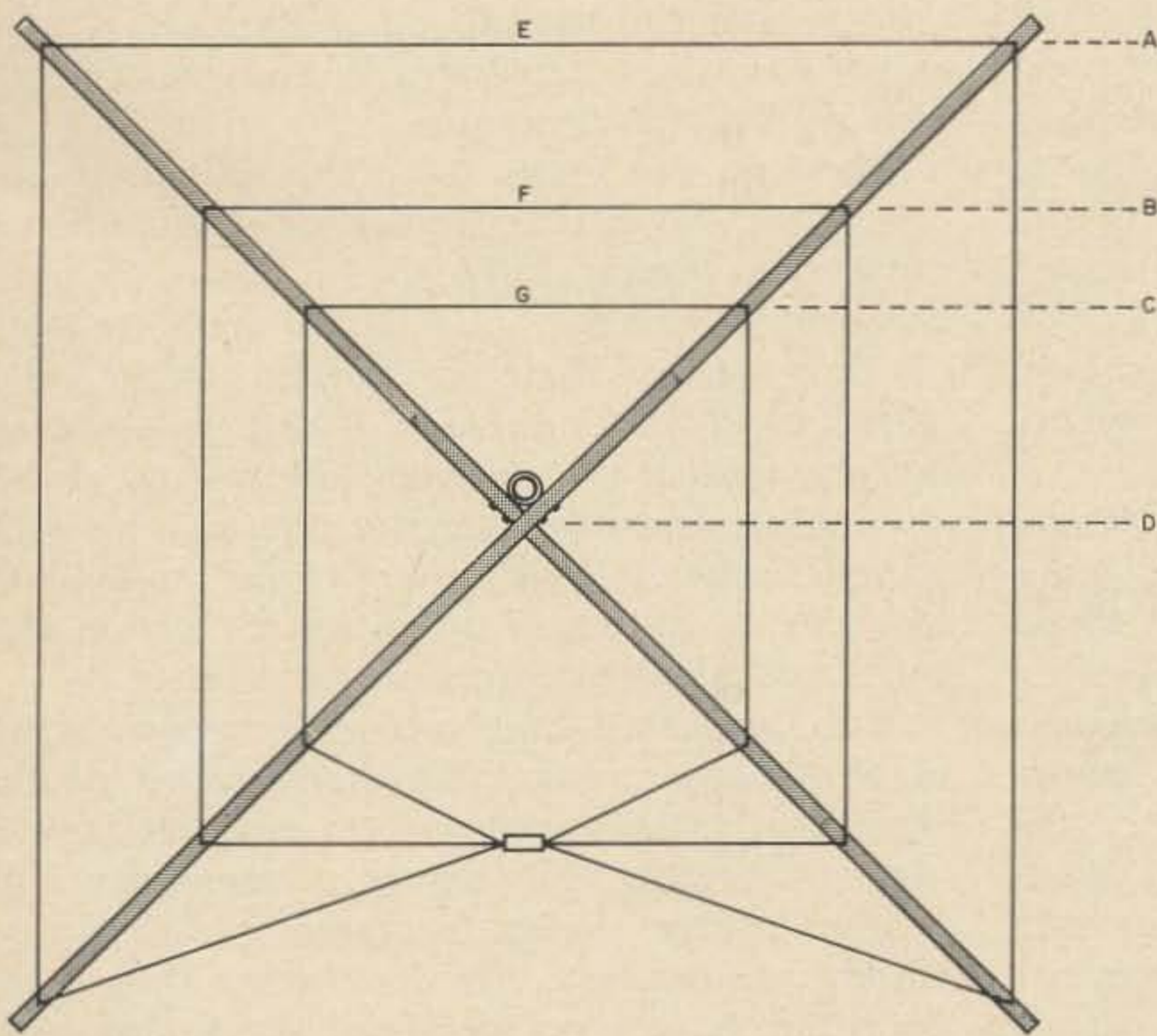


Fig. 1. Left: Arrangement of driven elements when using single feedline. Note boom above point where arms cross. Dimensions are: AD 12'6", BD

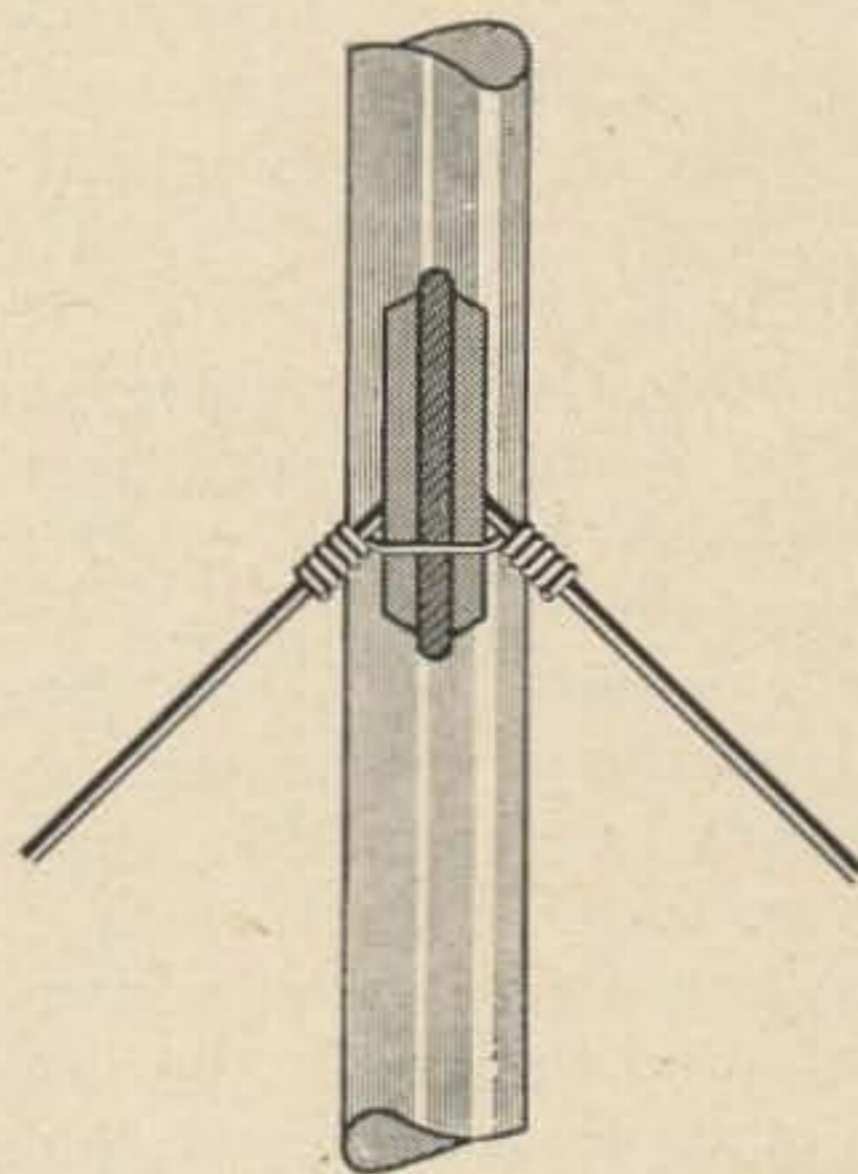

8'4", CD 6'2", E 17'8", F 11'9", G 8'7". Right: Exploded view of TV mast clamps used to secure center section of boom and stand-off insulator to tubing.

if possible. It may be difficult to obtain $\frac{5}{8}$ " and $\frac{1}{2}$ " in anything heavier than .035 which can be used as tip sections with no problems. If it must be used as inner sections, it will be necessary to shim up the inside tube. This is not recommended. Going to larger diameter tubing would be preferable.

Each crossarm is constructed from five sections:

- A. One center section of $\frac{3}{4}$ " .049 wall tubing, 4 $\frac{1}{2}$ ' long.
- B. Two inner sections of $\frac{5}{8}$ " .049 wall tubing, 6' long.
- C. Two tip sections of $\frac{1}{2}$ " .049 or .035 wall tubing, 6' long.

The inner and tip sections are telescoped about 1' to provide a total length of 24 $\frac{1}{2}$ '. A 1' length of $\frac{3}{8}$ " wood dowel is inserted 6" into each tip section. These serve as insulators for the 20M elements.

Cut a slot 8" long into both ends of the $\frac{3}{4}$ " tubing and one end of the inner sections. Cut a slot 4" long in one end of each tip section. Remove all burrs inside and out with a file. Sand 6" of the dowel until it slides easily into the tip sections. Drill a hole in the dowel 3" from the metal, just large enough to accept the wire easily. Drill two or three small holes in the tip sections as near as possible to the inner end of the dowel to prevent moisture buildup inside the arms.

Drilling the holes to accommodate the TV mast clamps which hold the center sections of the arms to the boom is the only part of construction requiring special care. It would be prudent to practice on pieces of scrap to drill holes straight through the tubing. A drill press is best, but with care it can be done with a hand drill. Be sure holes are perpendicular to the tubing. The diameter of the holes should only be large enough to insure 90 degree alignment of the arms to the boom. Locate the holes in the middle of the center sections.

Join the two sections of boom and secure with bolt.

Clamp a center section loosely to each end of the boom. To align these sections, place four small blocks of wood of identical thickness under the ends on a flat surface. With a large square borrowed from your friendly neighborhood carpenter, make sure center sections are exactly perpendicular to the boom. Carefully secure the clamps but avoid crushing the boom or tubing. Use clamps with contoured bar under the nuts. These bars can be made from scraps of tubing if they do not come with the clamps.

Once these two sections are aligned, place the ends on something high enough so that the remaining center sections will clear the

flat surface an inch or so when in the vertical position. Here is where the XYL can help. Borrow her kitchen chairs. Use blocks of wood and, if necessary, QSL cards to make sure the previously aligned sections and the boom are exactly horizontal by means of a spirit level. The longer the better.

Place the inner center sections about $\frac{1}{4}$ " inside the outer sections. Adjust the inner sections exactly vertical in all planes with the level. Cross check by placing the inner sections on the chairs and use the level to see if the outer sections are vertical.

Clamps for the slotted ends of the tubing are of the garden hose variety. Note: The sizes marked on the clamps are for the INSIDE diameter of the hose. Use two clamps at each joint except the tips where only one is necessary to secure the dowel.

Insulators for the 10 M and 15 M elements are the common 7 $\frac{1}{2}$ " and 3 $\frac{1}{2}$ " stand-off strap variety used for holding a single TV lead clear of the mast. Get those with the V-ends made of solid, flat metal.

With a light hammer, carefully tap both sides of the V narrow enough to rest on the tubing. Place the V on the tubing and run the strap through the slots. Tighten the shaft enough to get a light fit on the tubing. Release the shaft and run the strap around the tubing a second time and repeat the process. You should have a snug, but not tight fit.

With regard to the lengths of the elements, there are almost as many figures available as there are articles written about it. In addition, the usual modifying factors of location, height, construction, etc., enter into the overall picture as with any antenna.

Through the years since the advent of the first quad, the unrealistic claims and confusing dimension figures have jelled down to more conservative claims and a fairly accurate table of dimensions. Bear in mind, always, that stated element dimensions of any antenna are merely typical or average. However, unless something drastic enters the picture, the completed antenna will usually be sufficiently close to its optimum operating condition that tuning adjustments are a simple matter.

It is suggested that you make generous use of a grid-dip meter. The construction of this quad lends itself very well to easy changes of element lengths. The driven elements must be resonant at the design frequency before proper tuning adjustments can be made. Unless this condition is met, no setting of the tuning stubs will produce maximum gain, F/B or minimum SWR. The reflector elements are duplicates of the driven elements with tuning stubs added.

The performance curves of a two-element

DRAKE **2-C** RCVR & **2-NT** CW XMTR



*Basic pair for all Hams...
Novice or General*

**Receiver
Model 2-C
\$229.00**

*Excellent
performance
at low cost*

● Triple Conversion ● Crystal-controlled First Converter ● 500 kc ranges for 80, 40, 20, 15 and 10 Meters ● Also any 500 kc range between 3.0 mc and 30 mc by inserting an accessory Crystal ● Temperature-compensated VFO Tuning ● Selectable Sidebands without retuning ● Three Bandwidths—.4, 2.4, 4.8 kc at 6 db ● Solid-state Audio, Product and AM Detectors, AVC Amp and Xtal Osc ● AVC Switch (Fast, Slow and Off) ● SSB, AM and CW with AVC and S-meter ● Works Break-in CW with 2-NT Xmtr ● 19 Tubes and Semi-Conductors ● Dimensions: 11⁵/₁₆"W x 6³/₃₂"H x 9³/₃₂"D. Wt.: 13¹/₂ lbs.

Accessories available: 100 kc Calibrator, Q Multiplier, Matching Speaker, Noise Blanker, Crystals for other ranges.

**CW
Transmitter
Model 2-NT
\$129.00**

*Built-in
essentials and
accessories*

● 100 Watts Input (can be reduced to 75 watts for novice) ● Operates Break-in CW, Semi Break-in CW or Manual CW with Drake 2-C or other receivers ● Automatic Transmit Switching ● Side Tone Oscillator built in ● Antenna Change-over Relay built in ● Pi-Network output with fixed loading ● Lo Pass Filter against TVI built in ● Drop-out delay of change-over relay adjustable ● CW Coverage on 80, 40, 20, 15, 10 Meters ● Simplified Tuning ● Frequency Spotting without xmtr output ● Grid Block Keying ● Code Practice in stand-by position ● 13 Tubes and Semi-Conductors ● Dimensions: 9⁷/₈"W x 6³/₃₂"H x 9³/₃₂"D. Wt.: 12¹/₂ lbs. Accessories available: Antenna Matching Network, VFO, and Crystals.

All prices are Amateur Net. See your distributor or write for free brochure.

R. L. DRAKE COMPANY • MIAMISBURG, OHIO 45342

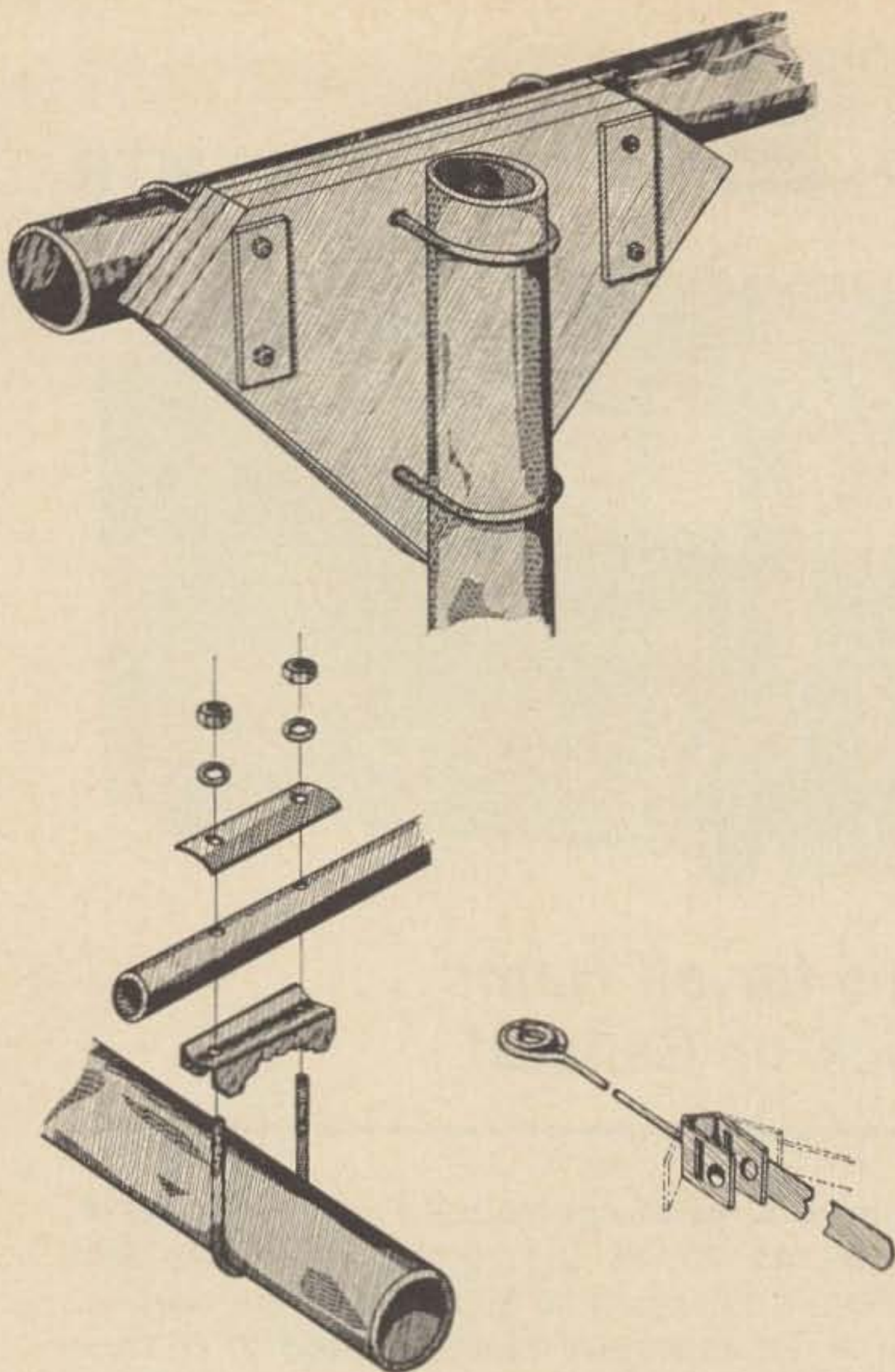


Fig. 2. Top: Boom clamp. Not shown are serrated yokes used with TV mast clamps to attach boom clamp to mast. Bottom: End view of stand-off insulator showing insulated wire twisted around element wire on one side of insulator, passed around outside of loop and twisted on opposite side to secure element wire to stand-off insulator.

beam show that the greatest usable portions fall above the design frequency in the case of the reflector-type beam. On the high side, the curves drop off slowly, while on the low side, they drop off rapidly as they near the self-resonant frequency of the reflector. For this reason, a design frequency in the low end of each band was chosen. The performance curves for the quad indicate that it will perform with near-maximum effectiveness across the entire 20 M and 15 M bands and across the greater portion of the 10 M band.

The design frequencies for the Poorboy MK II are 14.1, 21.2 and 28.8. The side dimensions as determined by the formula $250 \div f$ (MHz) are 17'8", 11'9", and 8'7".

Use #14 stranded wire as it is inexpensive, easy to handle and lightweight. Place a small dot of the XYL's brightest nail polish about 6" from one end. Measure half the distance of one side and mark it with polish. Measure three full sides and mark each with polish. Last is another half side. Cut the wire about

6" beyond the last mark.

Complete the 10 M and 15 M elements by fastening the ends of the wires to 3" center insulators at the dots and solder. The 20 M elements must be left unfastened on one end until later.

Tuning stubs provide the mechanical means for varying the length of the reflector elements to tune the antenna to its maximum effectiveness. The reflector is approximately 5% longer than the driven element. The stubs consist of suitable lengths of #12 bare solid wire spaced 3" apart and soldered across the center insulators of the reflectors. Sliding shorting bars used for tuning are made from small bits of solid wire with clips attached to each end to facilitate moving them easily.

Tuning stubs are 38" long for 20 M, 22" long for 15 M and 18" long for 10 M. These are maximum lengths and after the proper positions for the shorting bars are found, cut off the excess stubs and solder permanent shorting bars at these points.

Select the long section of the frame. This will be the reflector. Lay it with the boom upward on the most level area of the lawn. Slide two hose clamps on each end of the center sections and insert inner sections. Slide a 7½" SO insulator followed by two more clamps on each inner section. Next, insert tip sections with dowel locked in place and with a 3½" SO insulator attached.

Note that the length of the arms is to be measured from the point where the arms cross. Measure from cross to ends of inner sections and equalize with about 1' insertion. Set tip sections so that holes in dowel are 12'6" from cross and in line with wire direction. Place SO insulators exactly vertical at 8'4" and 6'2". These settings are approximately correct as a starting point.

Tighten all clamps and insulators enough that they will not slip but do not lock.

Raise assembled section in the air by the boom enough to clear the ground. Gently lower straight down to allow arms to fall naturally into position. Measure to be sure tips are equidistant from each other. Drive small pegs in the ground in pairs at several points along the arms to insure their staying in place.

Slide 20 M element into place with its center insulator on the cross side of the boom. Place dots at holes in dowel. Use small scraps of wire to tie elements to dowel to prevent slipping. Attach the other two elements in a similar manner and adjust by manipulating the SO insulators. Use INSULATED wire to tie these elements to insulators.

Do not attempt to pull element wires tight as this will cause a severe bowing effect. Allow

all wires to hang loosely. Attach tuning stubs.

Securely fasten boom clamp to mast and loosen clamps used to hold boom. Raise reflector section, slide through clamps and lightly lock into place to await completion of the other section.

Assembly of the second section is identical to the first. 72 ohm coax is connected directly across the insulators. Upon completion, hoist it up and mate it to the first section, and lock in place with the aligning bolt.

Although a lower boom is not an absolute necessity, it serves several purposes. It will eliminate much of the quad's tendency to whip in severe winds. It supports the weight of the feedlines and tuning stubs and reduces the bowing of the arms from the weight of the elements, etc.

A light, well-varnished piece of wood of sufficient length will serve well. Mount it to the mast by a TV clamp or U-bolt at the height of the 15 M insulators. Tie the 15 M elements to the lower boom. Run feedlines out one end of the boom and tie tuning stubs to the other end and this completes construction.

With proper care and consideration in construction, the Poorboy MK II should last for years. Treat all wood with several coats of good, high grade, spar varnish before assembly. Hang the dowel with a thumbtack driven in one end from a clothesline and this job is no problem. Remember to cover the ends of the dowel and the insides of the holes. After assembly, give it another couple of coats to protest against unseen nicks and scratches. Give all metal, except the tubing, generous coats of aluminum paint both before and after assembly.

Tuning is accomplished by pointing the back of the quad at a nearby cooperative ham buddy who provides a steady, horizontally polarized carrier at the design frequency which is tuned for the lowest reading on the station S-meter by sliding the shorting bar along the stub. After each band is tuned, check the other bands for deterioration of F/B. Readjust as necessary. The point of highest F/B lies in a narrow range. Remember that the F/B obtained during tuning will not be the same for all received signals due to different angles of received signals. It would be wise to test F/B with as many local hams as possible and choose a best average setting.

Tests were run using separate feedlines and using a single feedline for the three bands. Interaction during tuning was more noticeable in the case of the single feedline but tuning was no more difficult. In actual operation, there is little to indicate that one system is

superior to the other. However, as with all multi-band antennas fed with a single feedline, the chance of harmonic radiation is great enough to give the nod to the separate feedline system.

To connect the three driven elements to a common insulator for a single feedline, adjust the two lower corners of the 20 M element in toward the boom enough to allow the wire to reach the 15 M insulator. Adjust the lower SO insulators of the 10 M element toward the boom and run the wire to the now-common insulator centered in the 15 M element.

The frame of the Poorboy MK II can be used for a mono-band 20 M quad, a 20/15 M and 20/10 M dual-bander. In the event a 15/10 M dual-bander is desired, the metal part of the arms can be reduced to a length of 12' with suitable 3' lengths of wood dowel inserted 6" into the tip sections to bring the total length to 17'. Both the 15 M and 10 M elements can be threaded through the dowel, eliminating the SO insulators. The boom can be simplified by using a single section of TV mast cut to 5½'. In case you've been wondering, this version was the MK I which was cannibalized in the development of the MK II.

Antenna purists frown on the use of coax to feed a balanced antenna such as the quad with no matching device. However, it is a common practice and the performance of such an arrangement seems to suggest that it works better than a casual reading of the textbooks indicates.

The use of metal arms for the quad seems to be a neglected subject. The greatest danger is resonance at an operating frequency. In this case, the arms are close to resonance at 21 MHz. Avoid an arm length of less than 24'.

During the experiments with multi-band quads, the author received the distinct impression that the use of 20 M and 10 M quads on the same frame left a lot to be desired. Interaction between these two was definitely more noticeable than other combinations on the same frame. The answer is probably due to the harmonic relationship. For this reason, a design frequency of 28.8 MHz was chosen on 10 M. Also, this combination never seemed to produce as sharp a pattern as other combinations. Lacking the wherewithal to continue it further, the matter was never fully pursued.


The author realizes that the Poorboy MK II is not the ultimate in quad design but offers it as a good compromise for the average ham with limited resources. . . . K4USK

Want 5dB Gain on 75 Meter Mobile?

This article will tell you how to substantially increase your 75 meter mobile signal. The solution is not for the timid or the finicky. It's for the ham who is master of his own car, and really wants a big signal.

In case you haven't given it a try, 75 meters is a very good mobile band. It doesn't close down at night like 20 meters, or become infested with commercials like 40 meters. Also, the home stations don't have big beams on 75 meters, so you can give them a tussle.

Most commercial mobile antennas have calculated overall efficiencies of between 2% and 4%. There may be some arguments at this point, but check with the mobile antenna books and Terman's, and figure it out for yourself. The radiation resistance is very low for short antennas, and the loading coil resistance, and car body and ground resistances are very high. With 75 meter mobile antennas nearly everything goes up in heat. Let's see how we can radiate more and heat less.

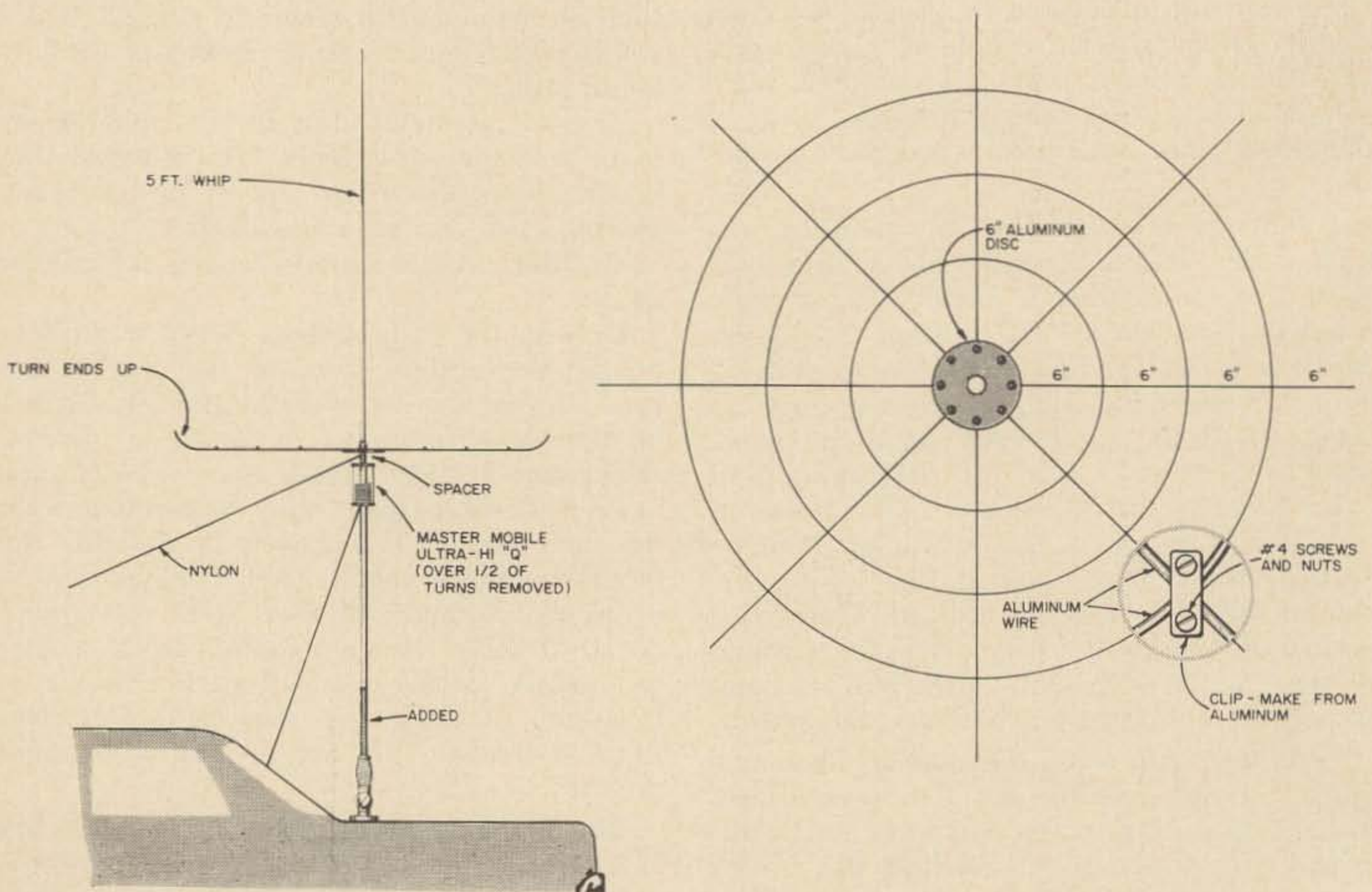

The Big Signal 75 meter capacitance loaded mobile antenna.

First, make the antenna as high as the law and your normal travel route permit. Also, mount it up on the back deck of the car where it is out in the clear. You can probably add two feet or so to the regular base section and still not exceed the height limit.

Up goes the radiation resistance and up goes the efficiency. Now perhaps the efficiency becomes 3% to 5%. The center loading coil has moved up, but that hasn't done any harm—perhaps helped a little.


To match the antenna to your 52 ohm feed line, shunt about 1500 picofarads from the base of the antenna directly to the car body. Don't use a coil at the base. It is more trouble to install, and has more loss. The capacitor will do the trick. You may have to adjust the value somewhat. Use your VSWR meter.

What next? We can't go higher. Let's look at the loading coil. Larger wire has less loss, but as the wire becomes larger the coil begins to grow in size and weight to hold the same inductance. A good high Q coil is fine, such as the Master Ultra Hi Q. Trying to improve over this coil is a rough game to play. Silver plate the wire? The improvement is hardly worth the trouble. The way to lower the coil resistance is to cut down on the number of turns. The way to cut this down is to increase the antenna capacitance above it.

One way to increase the capacitance would be to use a large diameter pipe above the coil, but this is not practical. Think of the trees, and the five foot flexible whip remains. What can be done with a capacity hat? The answer is—plenty!

If you want to develop your own top loading arrangement, start by obtaining a coil of aluminum clothes line wire. It appears to be a little larger than #8. Cut an 18 inch piece, and install it on about a 3 inch spacing rod above the coil. Head the wire aft. You will be able to take a few turns off the coil and still be resonant on the same frequency. Fine, how about four of these lengths, arranged like a two meter ground plane. Off come more turns. You can do the trimming with nothing but your rig and a VSWR meter if you go slowly. Keep the power way down. Don't add too much capacitance at once or you may find resonance outside the band, and you will need more than the rig and a VSWR meter to straighten things out.

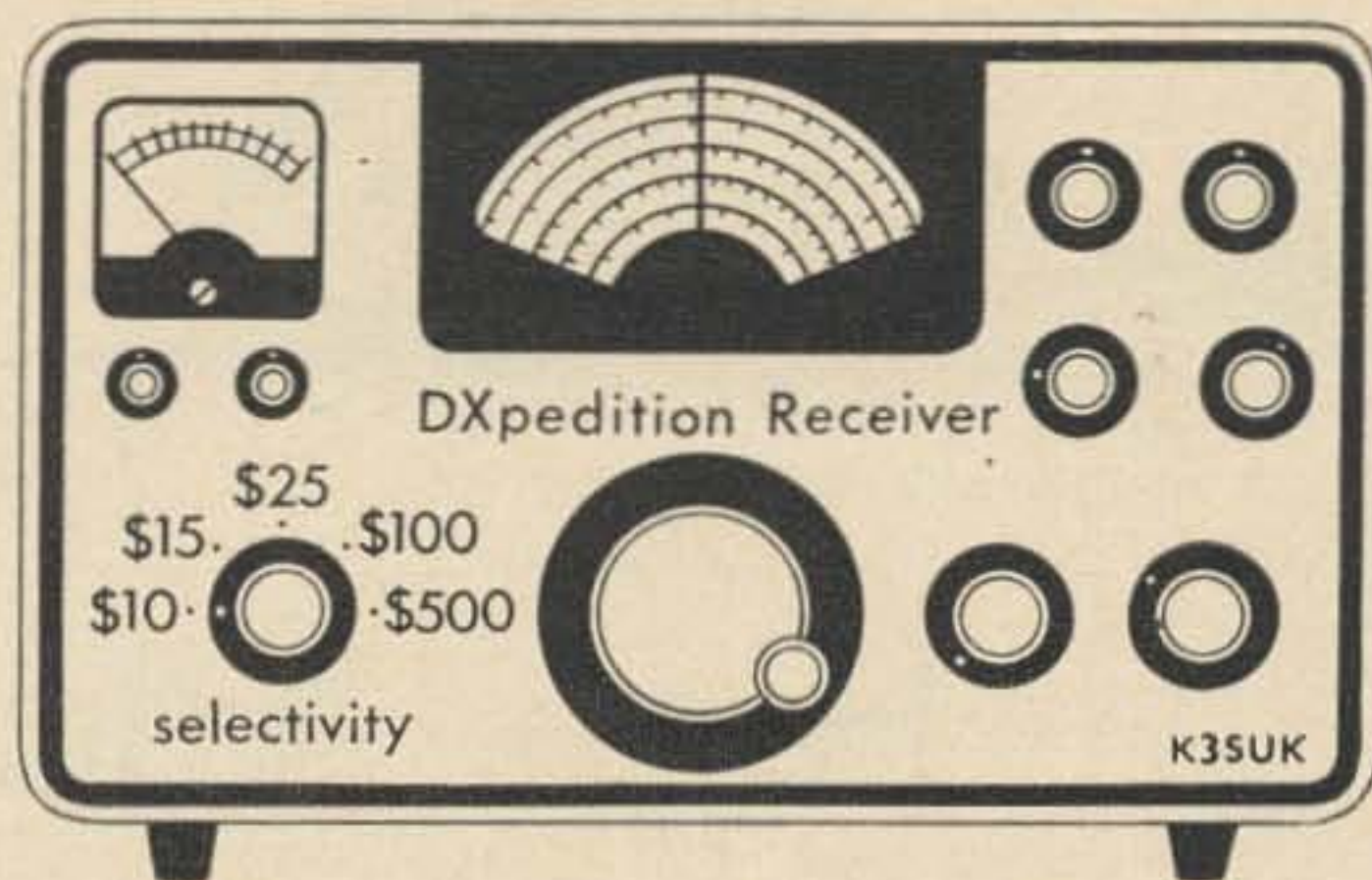The aluminum wire is surprisingly strong, and is self supporting at lengths up to more than two feet at fast car speeds. With the four radials and the increased height, the antenna efficiency has now become somewhere near 8%. File sharp edges to prevent corona and receiver noise.



If you still have courage, lengthen the radials a little, double the number, and strengthen them with three concentric circles of the same material. You now have a big capacitance hat of good strength. A 6 inch aluminum disc in the center can serve as a good building platform. The aluminum wire can be joined by small clips and screws, or binding with wire and covering with aluminum solder, or better yet by means of Heli-arc.


A capacitance hat of this type will allow you to cut your coil down to less than half of its original size. Efficiency will now calculate to be 10% or higher. Your actual output should have increased by at least 5dB. The 200 watt PEP rig has now become the equivalent of about 700 watts. You don't need a linear, and all of the problems of supplying power. Now, at 10% efficiency, you have a good vertically polarized signal. The efficiency has started to approach the efficiency of some home station ground plane antennas.

It is recommended that a light nylon cord be run from just above the antenna coil to the forward rain gutter, and another to the deck opposite the antenna base. These guys will stabilize the antenna at high speeds, and prevent it from swinging over the highway in a cross wind.

A second coil, which will resonate without the capacitance hat, is recommended for use when the hat or guy lines are not desired.

The writer has used an antenna of this type for over a year. Results have been very gratifying. The mobile signal is consistently stronger than other mobile signals of equal power using conventional antennas.

. . . W3BTQ/5

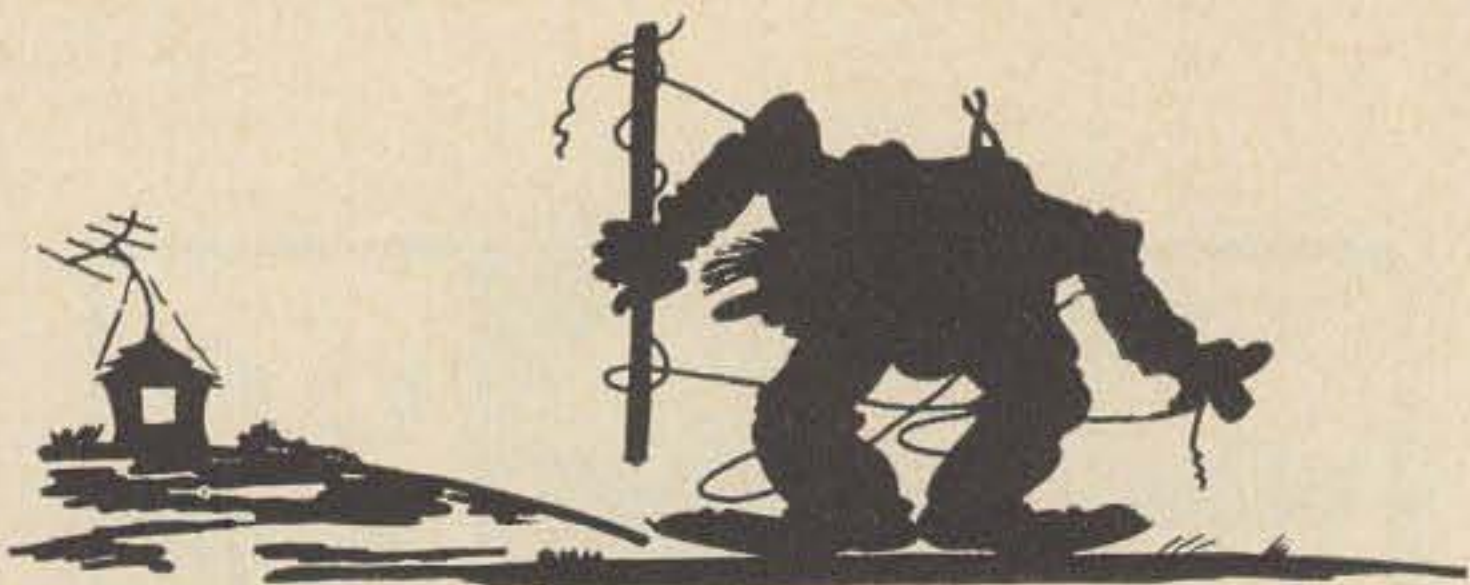

. . . a couple of wires, a long ruler, and a short conscience.

Howard F. Burgess W5WGF
1801 Dorothy Street N.E.
Albuquerque, New Mexico

High Accuracy VHF Frequency Measurements

Measure your VHF frequency to better than .00015%.

In years past the only need for a VHF frequency measurement was to make sure that the transmitter was in the right band. This could usually be taken care of with a couple of wires, a long ruler, and a short conscience. But life in the ham bands has changed. New narrow-band techniques and equipment make it necessary to know much more about frequency than just how to find the band. This is especially true in certain types of DX work. Frequency measurement capability also has its fringe benefits if you happen to belong to the "net set." You can alienate your friends, lose your peace of mind, and do wonders for the net by just reminding everyone at frequent intervals that he is off frequency, or drifting too badly to be measured.


Accurate frequency measurements can be a problem for the amateur with a limited budget. However with some home construction and careful operation the average ham can make VHF frequency measurements to an accuracy better than .00015% at two meters. This is the equivalent of measuring the distance from New York to Los Angeles with an error of only 25 feet. Many commercial units cannot equal this figure. The same method can also be used for HF and UHF measurements.

There are many ways to measure frequency but few of them are satisfactory for use at the

very high frequencies. The well known heterodyne frequency meter becomes unstable when its oscillator is operated at VHF. It can no longer be held or read to any degree of accuracy. The oscillator can be operated at a low frequency and one of the harmonics used at VHF, but any error in the oscillator will be multiplied by the number of the harmonic used. A frequency meter that can be held to within 200 hertz at 4 MHz will be off by 7.4 kHz at the 148 MHz harmonic.

A second method of much greater accuracy uses low frequency crystals which are referenced to a known standard such as WWV. The harmonics of these oscillators will be quite accurate and useful far into the UHF region. However this system has its limitations. Even when used with multivibrators and harmonic amplifiers it produces only spot frequencies.

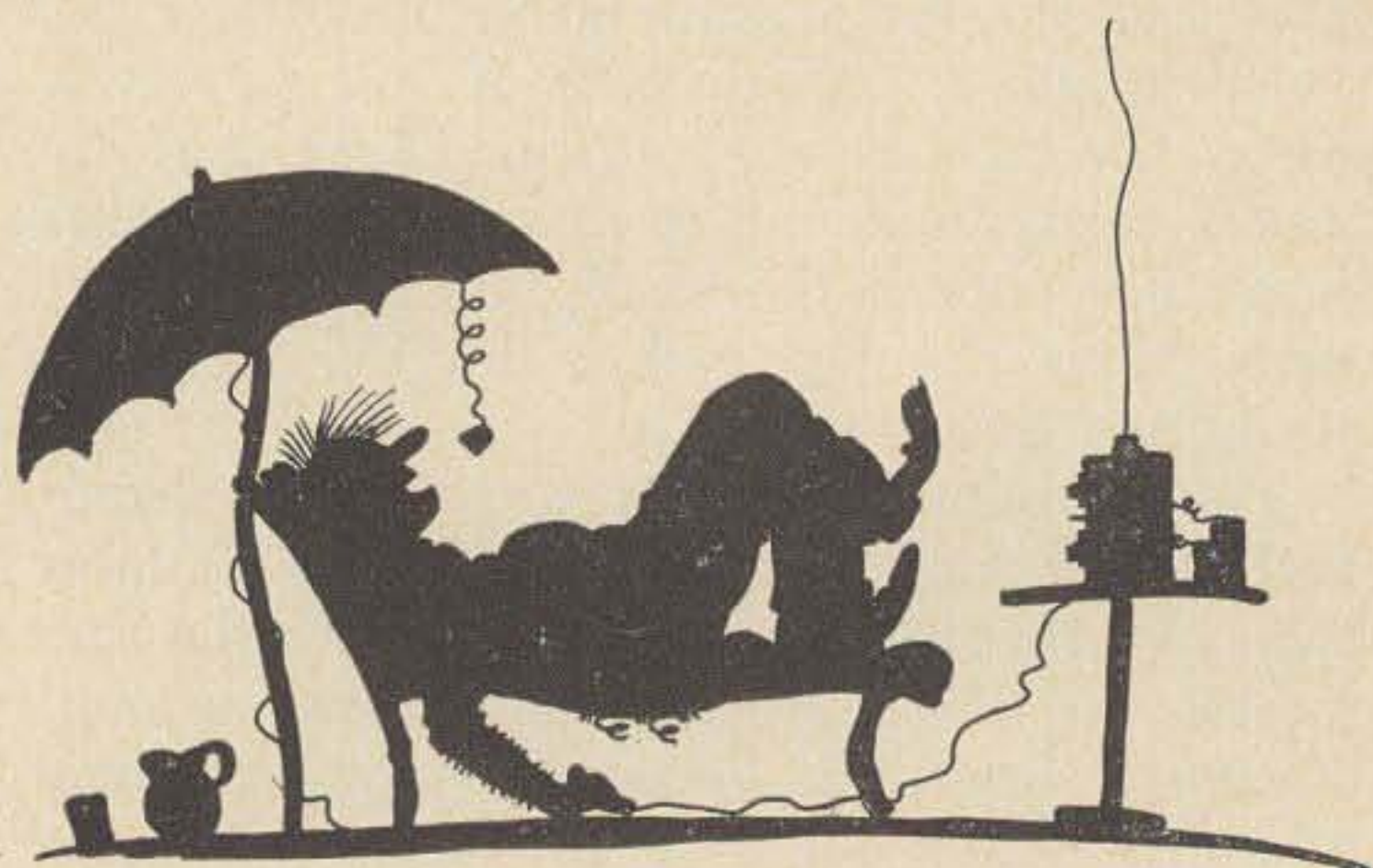Although neither of these two methods is satisfactory when used alone, they can be combined to make an accurate and versatile



But life in the ham bands has changed.

Howard, former W9TGU, W7KGD and WØBDH, has written many articles in his 32 years of licensed hamming. He now works for Sandia in AEC primary standards.



... from New York to Los Angeles with an error of only 25 feet.

system. If you haven't guessed it by now, the system works like this. A crystal oscillator operates on 5 MHz. This oscillator can be kept to zero beat with WWV with very little effort. With a simple harmonic amplifier following it, strong markers are available every 5 MHz far into the UHF region. To fill in between the 5 MHz points, and get full tuneable coverage, all that is required is to add the output of a stable low frequency VFO to the proper marker. Example: To measure 146.25 MHz just add 1.25 MHz from a calibrated tuneable oscillator to the 145 MHz harmonic of the crystal. The same results can be had by using the 150 MHz marker and subtracting 3.75 MHz.

The tuneable low frequency oscillator of this heterodyne system can be any stable, calibrated, oscillator that will give the desired frequencies. A good signal generator can be used but better yet is the old faithful BC-221 frequency meter. The crystal oscillator that supplies the 5 MHz markers should be designed for high stability. However, even simple crystal-controlled units can be kept zero beat with WWV for periods long enough to make most measurements.

Earlier we quoted a figure of .00015% or better for the accuracy of this system. Perhaps we should show how this is possible. The crystal oscillator can be held to near zero beat with WWV but due to propagation errors in the signal of WWV, we can never be sure that our crystal is closer than 2 parts in 10 million. This would be 2 hertz of error at 10 MHz or an uncertainty of 29 Hz in the 145 MHz marker. The BC-221 is normally considered to be a .05% instrument. This would be an error of about 1.75 kHz at 3.5 MHz. However with care in calibration, and reading it is not difficult to reduce this value to 200 hertz or less. In a heterodyne system the error of the VFO is not multiplied at VHF but is just added to the error of the crystal marker used.

The total error at 2 meters is 29 Hz contributed by the crystal and 200 Hz by the VFO for a total of 229 Hz. This is a little more than 1.5 hertz per million hertz for a tuneable system. Of course these values are approximate and with careful operation they can be reduced by 50% or more.

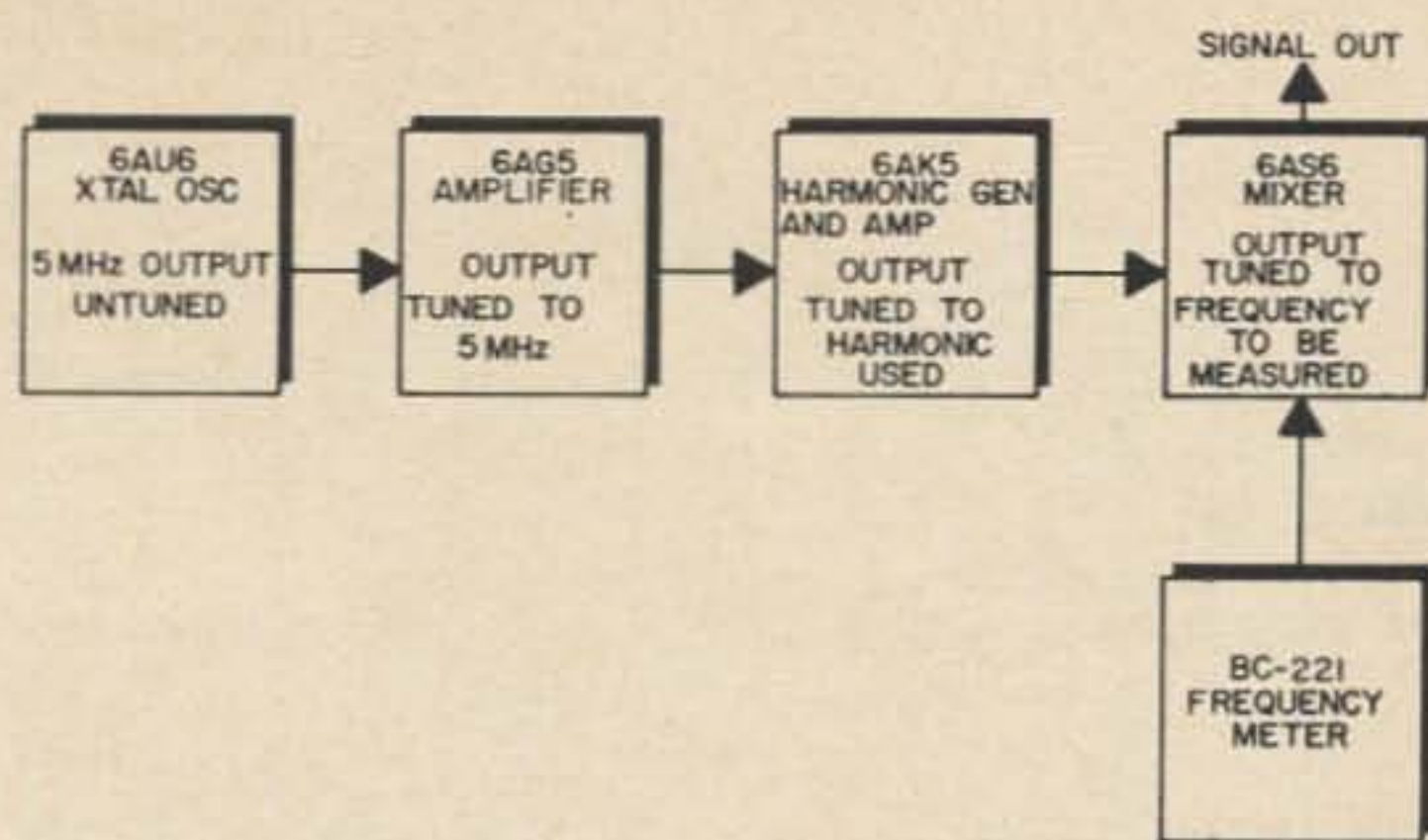


Fig. 1. Block diagram of the VHF frequency meter.


In the 146.25 MHz example used earlier, the VFO was required to furnish less than 1% of the total output. To put it another way, the only wobble is in the smallest cog and its contribution is so small it can't shake up the machinery too much.

The circuit shown in Figs. 1 and 2 has been used for monitoring MARS, CAP, and several other services. The crystal oscillator is quite stable but can be tuned enough to zero with WWV. Tuning is done with C1. One stage of harmonic amplification is sufficient to give strong signals well above 150 MHz. The plate circuit of this amplifier stage is tuned to the harmonic to be used. This feeds one input grid of the mixer. The other grid of the mixer is driven by the output of the BC-221 frequency meter. The tuned circuit shown in this grid resonates broadly in the 2-4 MHz range of the BC-221. This helps to keep the higher harmonics of the BC-221 out of the mixer.

The output of the mixer is resonated to the desired operating frequency. This will be either the sum or difference of the two input signals. The level of the output signal can be controlled by R6.

Operation of this system is simple. The "cook book" would read as follows:

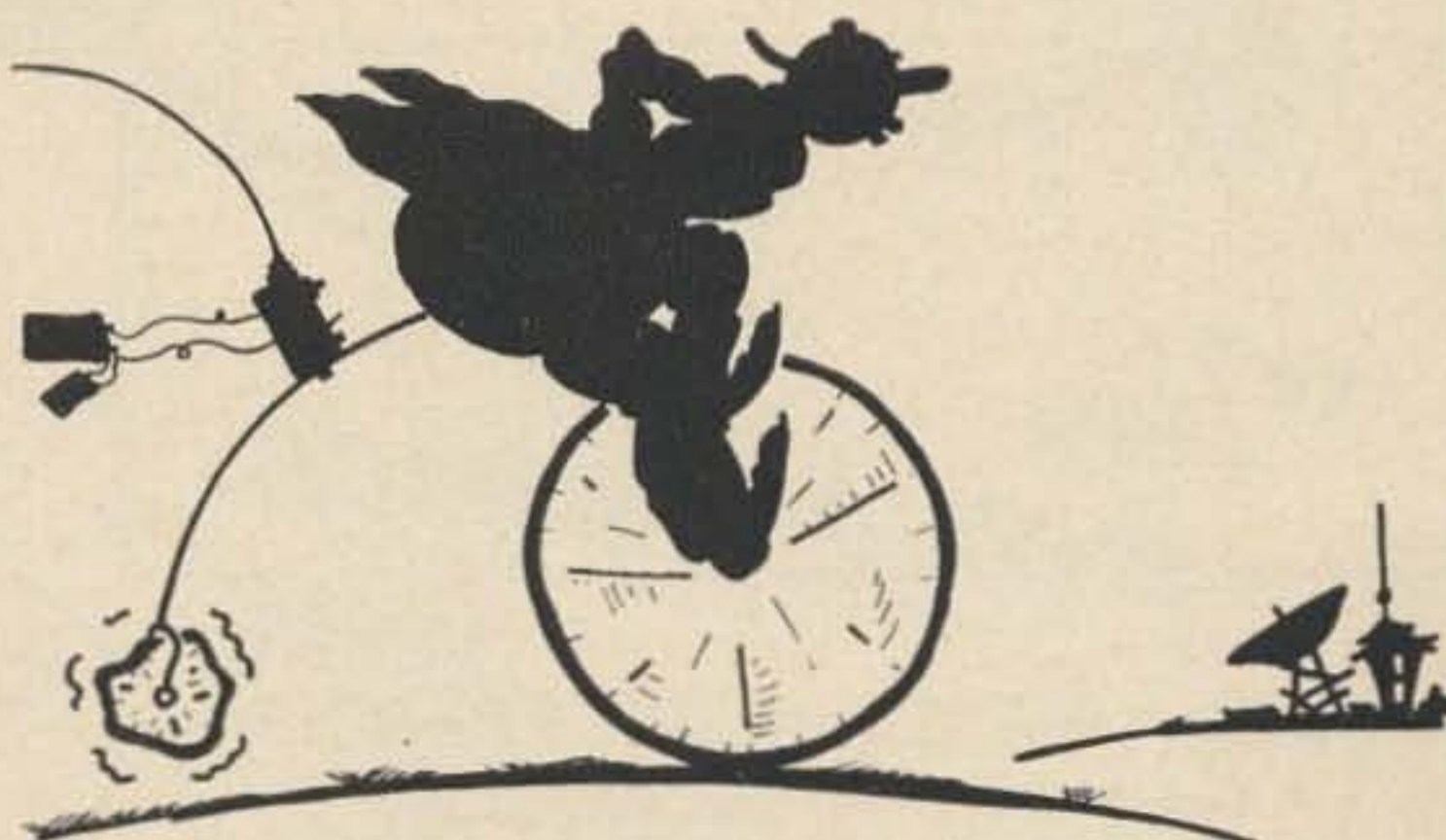1. Couple the output to the antenna of the VHF receiver.
2. Determine the crystal harmonic and VFO frequency that will give the frequency of the signal to be checked.



... the only wobble is in the small cog ...

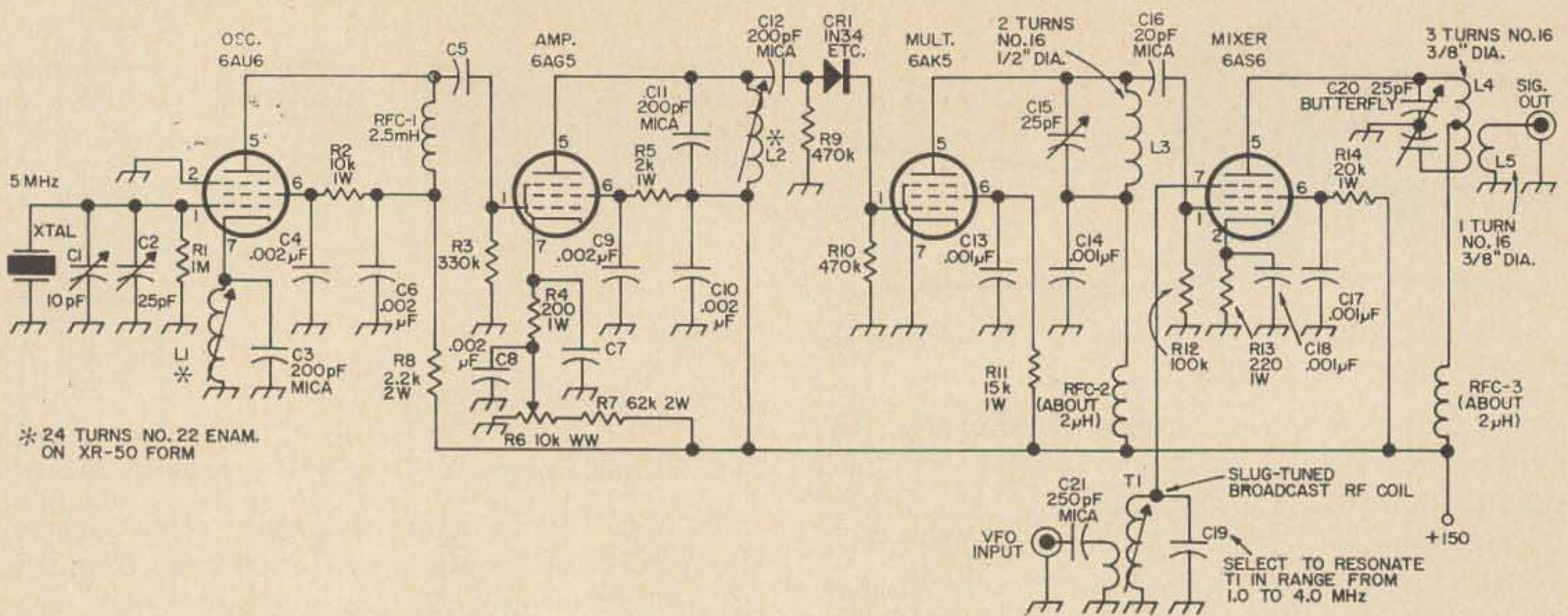


Fig. 2. Schematic of the oscillator, multipliers and mixer for using a BC-221 on the VHF ham bands.

3. Tune the VHF receiver to the signal to be checked.
4. Tune the BC-221 until the output of the frequency monitor zero beats the received signal.
5. If required, peak the tuned circuits in the monitor for maximum output and adjust R6 as needed.
6. The frequency of the received signal will be the crystal harmonic plus (or minus) the reading of the BC-221.


Many details cannot be covered in one story due to lack of space. The operator will have to determine the most effective method of coupling to this particular receiver. He will also have to explore the many combinations of frequencies which can be used. These and

many other questions cannot be included at this time. However those who require such a system as this will probably be capable of filling these details.

One word of caution is in order. With two oscillators that are rich in harmonics, there can be many unwanted "birdies." These present no problem after the operator has gained experience but the new user should be very cautious. Many times an unwanted beat can be eliminated at a critical spot by changing the two frequencies that are being mixed (shift from sum to difference).

Perhaps we should emphasize that this system is a "trade off" where the amateur can trade his skill and patience for highly accurate measurements with simple equipment.

... W5WGF

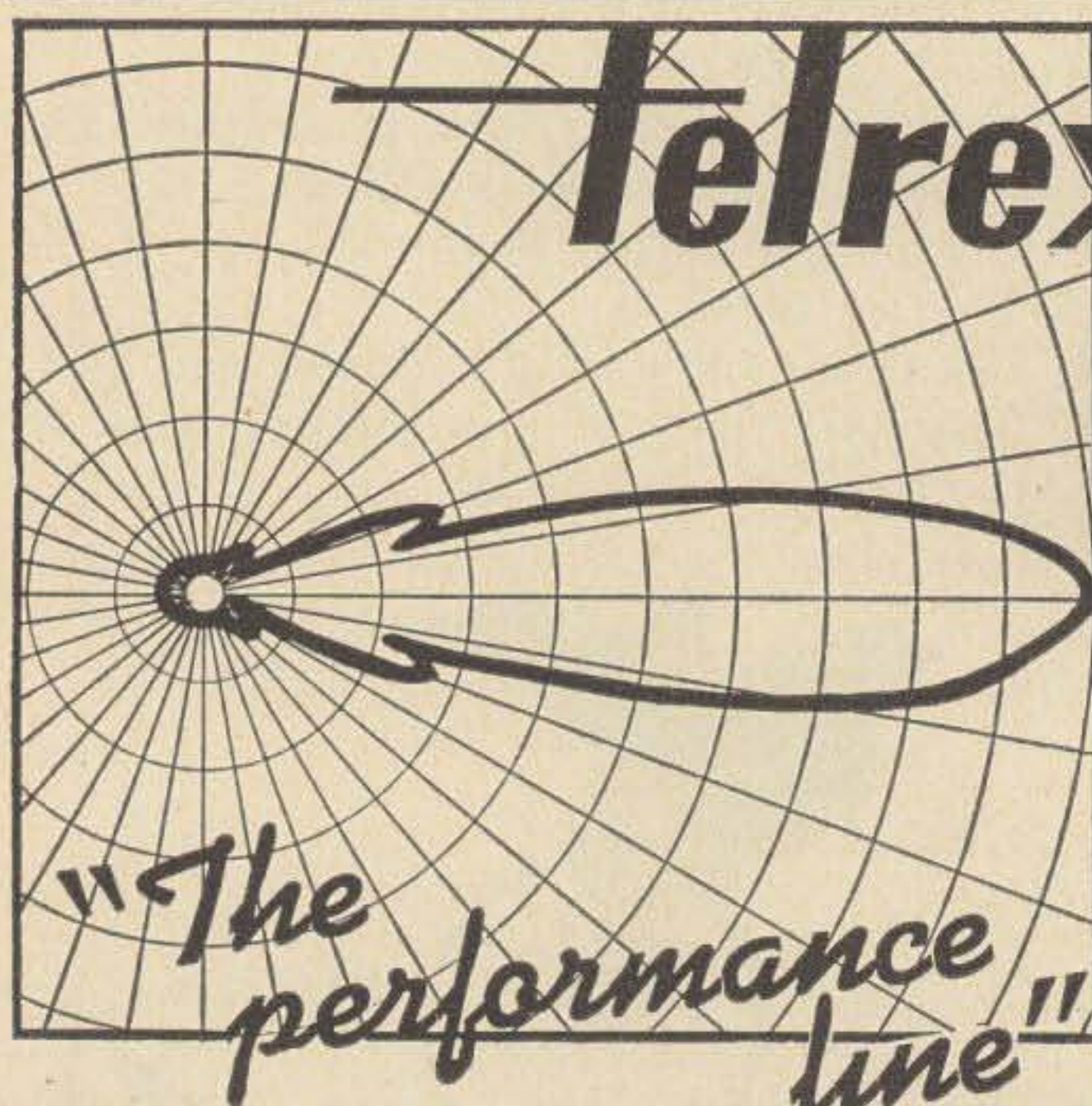

"Beamed-Power" ANTENNAS, "BALUNS" I. V. KITS and ROTATOR SYSTEMS!

Most Technically-Perfect, Finest Communication Arrays in the World! Precision-Tuned-Matched and "Balun" Fed for "Balanced-Pattern" to assure "TOP-MAN-ON-THE-FREQUENCY" Results

You, too—can enjoy World renown TELREX performance and value! Send for P1.67 tech data and pricing Catalog, describing the World's most popular communication antennas, rotator-selsyn-indicator systems and accessories! Expanded data sheets, including your favorite band, also available.

— with a MATERIAL DIFFERENCE!

Use, is one of the most dependable testimonials of endorsement, and Telrex products are in use in 135 Lands

ANTENNAS

SINCE 1921

COMMUNICATION SYSTEMS
telrex LABORATORIES

ASBURY PARK, NEW JERSEY 07712, U. S. A.

NEW
FROM
ALLIED

knight-kit[®]

6 and 2-Meter Transceiver Kits



Knight-Kit 6-Meter Transceiver Kit

New top-performing Ham rig with many extras. Covers 50-52 mc and 49.980 MARS. Solid-state universal power supply for 12 VDC mobile and 110-130 VAC. Noise-canceling push-to-talk mike. 3-stage transmitter has doubler, tripler and straight-through final. Selective dual-conversion receiver. Illuminated "S" Meter/Output Meter. Complete with all parts, wire, solder, and easy step-by-step instructions. **\$139⁹⁵**

Read the unique money-back guarantee . . . exclusive in the industry . . . then rush coupon below for full details and Special Introductory Offer on 6 and 2 Meter Transceivers.

Knight-Kit 2-Meter Transceiver Kit

Compact and versatile Ham transceiver for General, Technician, or Novice class. Covers 144-148 mc. Built-in solid-state universal power supply. Dual-conversion receiver has spectacular 1.0 micro volt sensitivity. Factory-aligned crystal-controlled RF and mixer sub-assembly simplifies construction. AVC action prevents blasting. Noise-canceling push-to-talk mike. Complete with all parts, wire, solder and step-by-step instructions. **\$144⁹⁵**

VFO KIT. Calibrated for 6 and 2 meters. Features Clapp Oscillator. Takes power from transceiver. B+ switch and indicator light. Complete with all parts, wire, solder, instructions for **\$19.95**

KNIGHT-KIT GUARANTEE

Build a Knight-Kit in accordance with our easy-to-follow instructions. When you have completely assembled the kit, you must be satisfied or we will return your money, less transportation charges, under the Allied guarantee of satisfaction.

ALLIED RADIO

ALLIED RADIO, Knight-Kit., Dept. 14-JJ
P. O. Box 4398, Chicago, Ill. 60680

Send me full details and Special Introductory Offer on Knight-Kit 6 and 2-Meter Transceiver Kits.

Name _____ PLEASE PRINT

Address _____

City _____ State _____ Zip _____

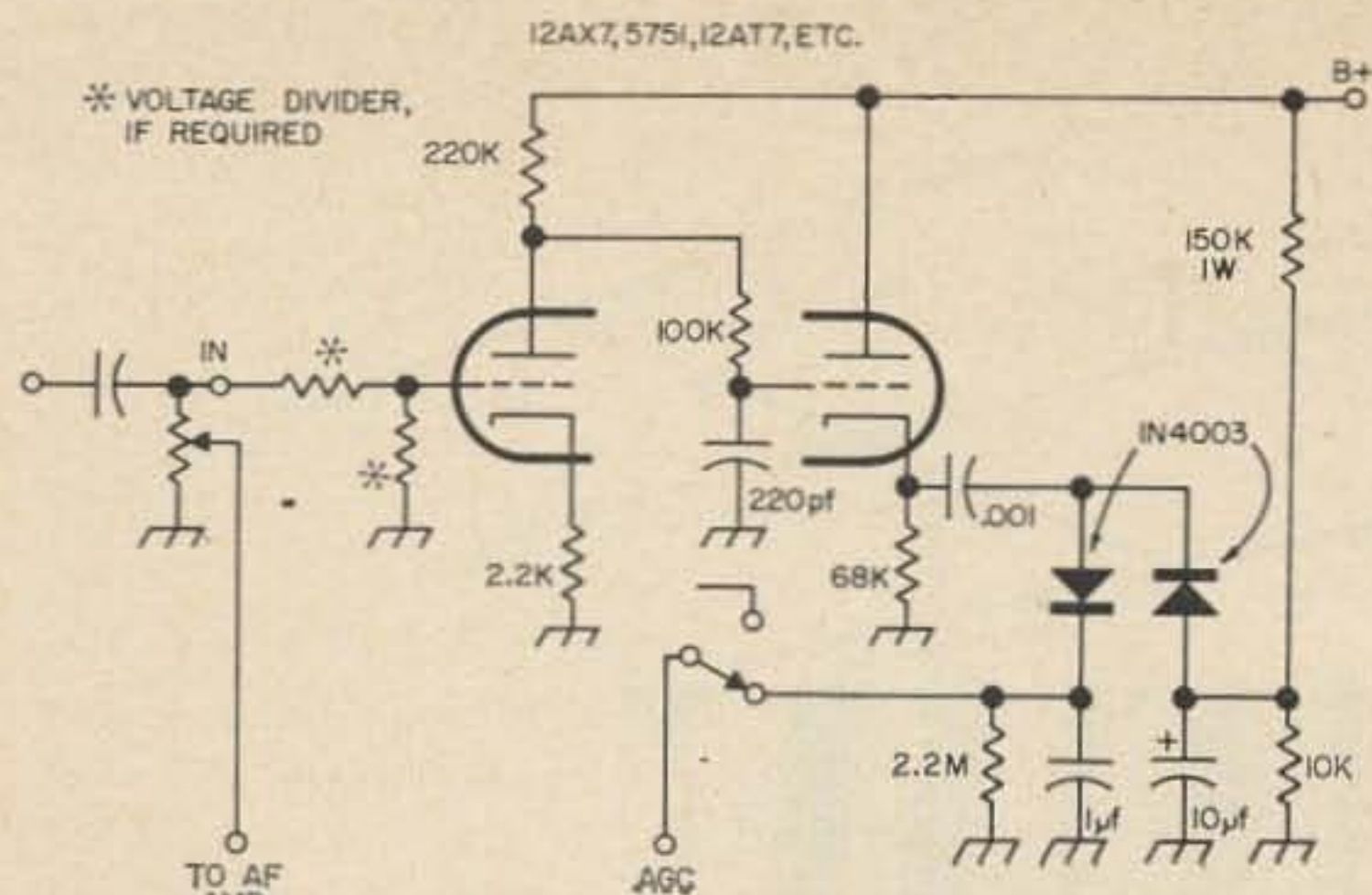


Fig. 2. Tube type audio derived AGC. Take audio from after noise limiter and before audio gain control.

CWV sends you, I could send a circuit (in a SASE).

The audio-derived AGC was originally suggested by a note in a *Swan* manual. Incidentally, doing it their way worked in one receiver but in another the silicon power diodes used to rectify the audio voltage produced harmonics which got into the *if* and fed back. The resistor (1000 ohms in the diagram; the value is not critical at all) ruins this "varactor action" without any other ill effects. The charge time constant, in practice, is a few milliseconds; if it's made too short, the receiver quits whenever a Ford drives by. The AGC "delay" bias (the value of peak voltage below which no AGC voltage is developed) is adjusted by the potentiometer labeled SB LEVEL. I found that this worked best if it was ganged to the volume control, so that the volume adjusted by the same knob in either mode. If this is done, the volume control circuit must be doctored up so that the gain of the audio section is never reduced all the way, (although *some* variation in the audio gain did turn out to be desirable) and the net result is the circuit shown.

Whether you like the manual gain control ganged with the audio gain (BC-348 style) is a matter of taste; it only operates in the MGC mode, which is when the audio pot doesn't in those receivers. Ganging THAT with the other two is a possible way of freeing a panel hole for use as a switch for AM-SSB. The only way I know to buy a three-gang pot is to make it up from IRC parts.²

Some of the switching is to make sure that the 1 µF capacitor cannot start out with a charge when you switch to SSB. For some other ideas, see a previous article³ on the same

2. 73 Magazine, Feb. 1964. "Unusual Receiver Circuits."
3. For two-gang, 500k audio is Mallory FA55A, 100k is 15A (second section). There is also a shaft required, you pick it. For two gang, IRC Q- or PQ-13-133 plus M13-128. The RF section can be piggybacked on later, buy IRC M17-116, making three.

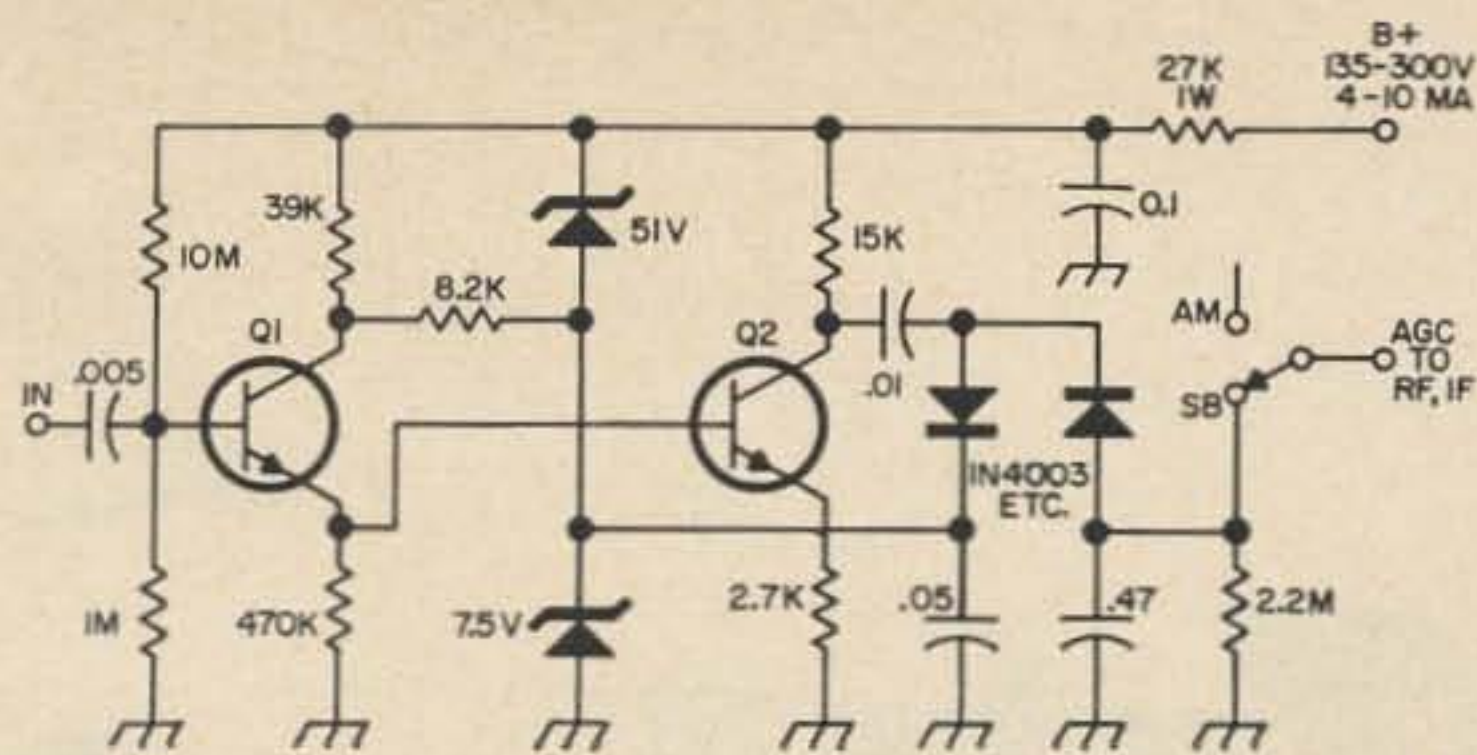


Fig. 3. Transistor audio derived AGC. Q1 is a 2N2925 (25¢), Q2 a 2N3404 (85¢). The 7.5 volt zener is ¼ or ½ watt, such as the 1N958 or 1N755. The 51 volt zener is a ½ or 1 watt one, such as the 1N3036. Pick up the signal as in Fig. 2.


sort of thing.

The S-meter circuit requires a silicon PNP and an NPN transistor. These both are now fairly cheap and common. The AGC delay on AM is about three volts, caused by the bleed current through the 44 megs or so in the divider which is part of the S-meter circuit, the 1 meg AGC filter resistor, and the 1N629 diode clamping the AGC bus. The bleed current also affects the release time of the AGC in the sideband mode. The 2 M pot is to set the S-meter to zero for no signal, and the "CAL" pot is to set the *maximum* meter reading. With the values given, the motion was reasonable over the range of AGC volts from 0 to minus 10. Q1 and Q2 should have reasonably high gain at low currents and BV_{ce0} at least as high as the rated cathode bias of the output tube. I put both transistors on a card screwed to the back of the S-meter by its terminal posts. The holes for the pots were already in the chassis from the previous S-meter circuit.


If you'd like a little simpler modification, almost any receiver (without restriction, if it uses tubes) can have audio-derived AGC added by attaching one of the amplifier-rectifier units shown in Figs. 2 and 3. The input impedance is high, and the extra power needed is small; the gain is adequate and, in fact, may be excessive. If it is too high, the receiver will be short of audio output on sideband. A suitable cure is to put a one megohm potentiometer at the input and adjust so that the sideband audio matches the AM audio. The cost for all parts for the transistor model is just under \$15, and the silicon transistors permit it to be put in a fairly hot spot inside the receiver without loss of performance. I built it up on a piece of perforated circuit board and taped it to an *if* can to try it out. Eventually it's going in another receiver, which will have transistor audio and audio-AGC sections but tubes for the RF and *if*.

... W10OP

Mosley TRAP
MASTER

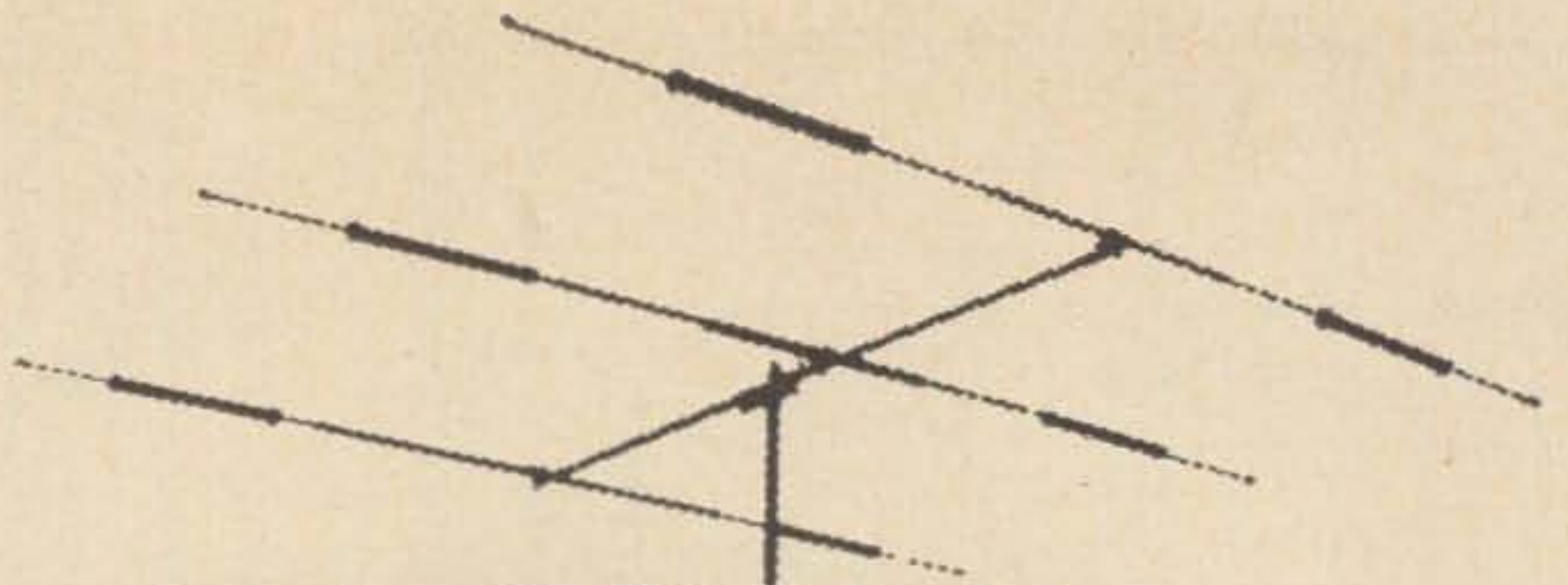

NEW

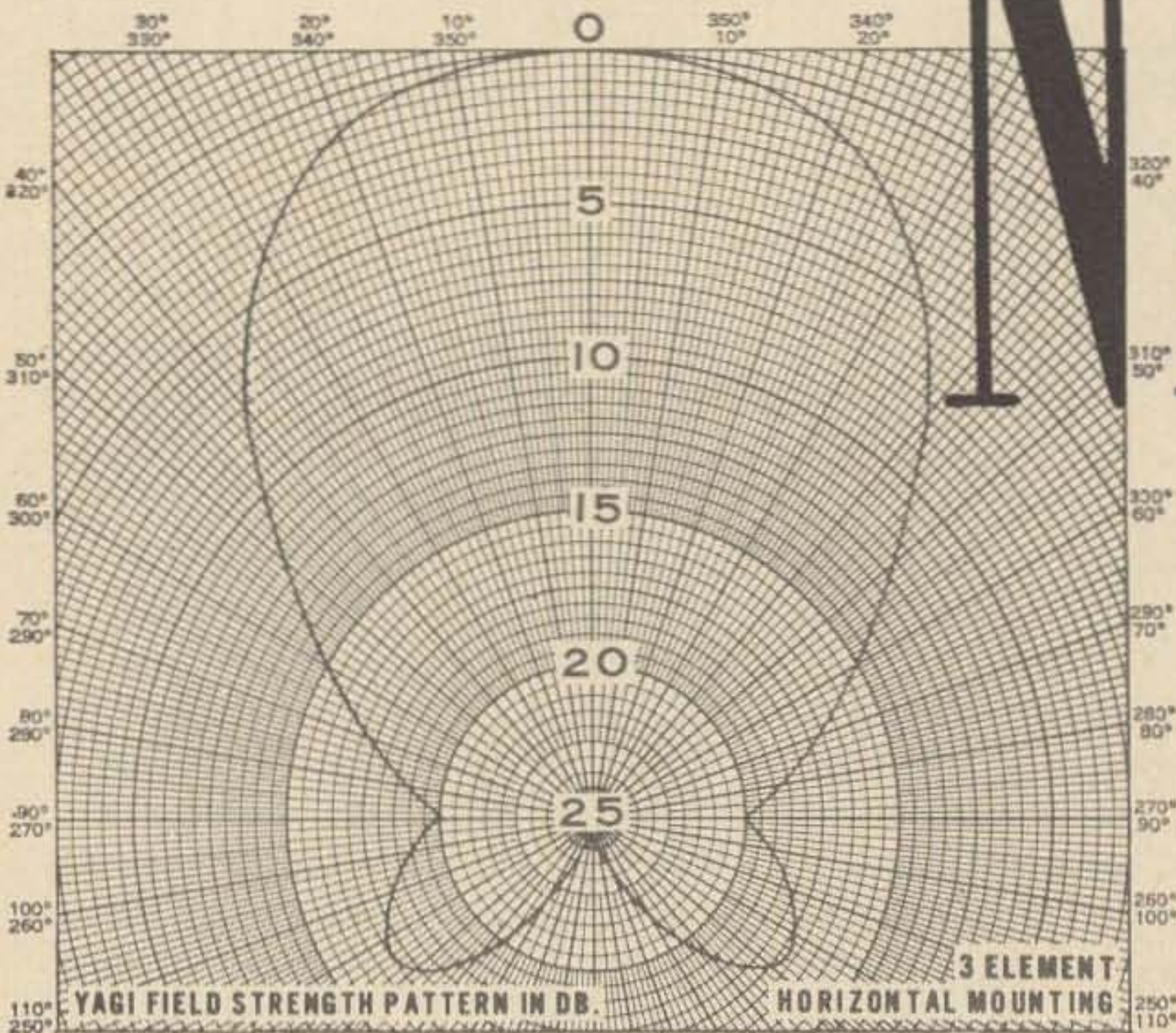

Beam WITH
Advanced
Matching System FOR
Added Gain

The Classic 33 You've been hearing about it — maybe you've worked Carl Mosley WØFQY— 'The Old Man Himself' using it. Now here it is . . . A Revolutionary New 3-element beam featuring an advanced Mosley-engineered matching system called 'Broad Band Capacitive Matching' with coax fed balanced element for more efficient beam performance and extra gain over comparative 3-element beams. A New Tri-Band beam rated for 1 KW AM/CW & 2 KW P.E.P. input to the final amplifier SSB on 10, 15, & 20 meters; with a full 8 db. gain on all three bands over reference dipole (10.1 db. compared to isotropic source); a maximum front-to-back
. . . The CLASSIC 33 . . . This new rugged beam in the Mosley Trap-Master tradition of quality beams brings you all the exclusive features of high priced beams — added gain, improved boom to element and mast clamping; wider element spacing. Priced well within your budget. What more could you possibly want in a 3-element Tri-Band beam?

. . . For Further Information Write Code 97 . . .

Mosley Electronics, Inc. 4610 N. LINDBERGH BLVD.,
BRIDGETON MO. 63042



The Classic Feed System

By W. E. "BARNEY" ST. VRAIN, WØPXE

DESIGNING ENGINEER - CLASSIC 33 PROJECT
 MOSLEY ELECTRONICS, INCORPORATED
 4610 N. Lindbergh Blvd., Bridgeton, Mo. 63042.

Code 107.

SINCE the introduction of multi-frequency beams several years ago, the method of feeding such antennas has been a subject of much disagreement. When these antennas were introduced a few years ago, Mosley Electronics ran a series of advertisements in the technical magazines explaining the method used on our Trap-Master and Power-Master series. Since that time we have tried a wide variety of feed systems endeavoring to improve on the original system.

Testing Other Feed Systems

In testing, we found a three band gamma system ineffective without isolation networks which resulted in the feed system costing about equal to the antenna cost; with a system using hairpins, the cost proved low but did not provide a better match than the original Mosley matching system. It became quite clear to us, the Mosley system was hard to beat, for we had found only one slight disadvantage, the elements needed to be stagger tuned to raise the feed point resistance from about 30 to 50 ohms. This slight detuning, which proved advantageous in increasing the bandwidth, brought about, in turn, a slight gain loss of about 0.5 to 1.0 db. at resonance.

The Classic-33 System

In order to give hams a new choice in beam matching systems and an antenna featuring maximum gain with increased bandwidth, we devised the matching method used on our New Classic 33 antenna, a method which takes advantage of the principle that antenna resistance at the center driving point increases as the antenna length increases. Figure No. 1 shows the radiator element of a three element beam at resonance having an impedance at the driving point (Z_A) of about $30 + j0$ ohms. If the element is made longer, Z_A can be raised to about $50 + j50$ ohms. (Figure No. 2) Since the reactance is inductive, it can be canceled with a series capacitor of 50 ohms reactance, leaving 50 ohms

feed point resistance. (Figure No. 3) Series capacitors used on the Classic 33 are made by inserting a suitable length of heavily insulated wire into each half of the element tube at the center. The wires are terminated in a plastic tube enclosure with a type "N" connector for connection of the coaxial cable. To isolate the outer coax conductor from ground, the coax line is coiled for a few turns near the antenna end. This is designed to prevent the very unlikely affect of "Feed Line Radiation".

Fig. 1.

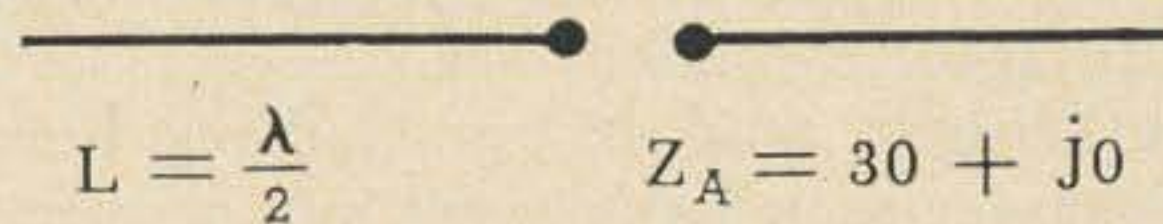


Fig. 2.


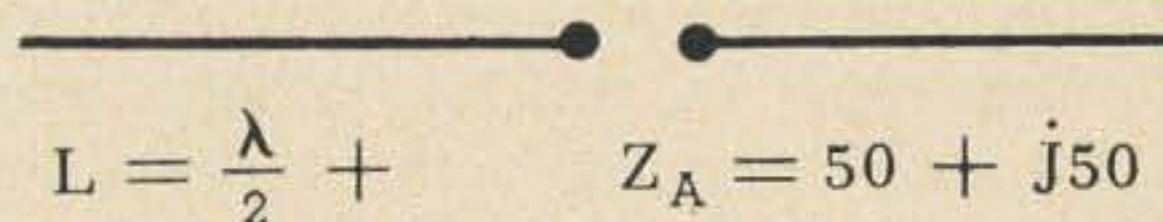


Fig. 3.

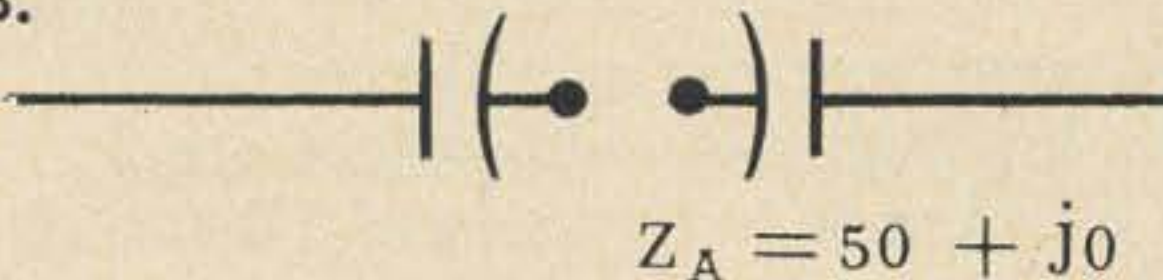

Converting Other Beams

This feed system could feasibly be used on our other Trap-Master beams, but little would be gained and the antenna would need to be completely rebuilt. The big difference between the new Trap-Master beam and the TA-33 is that the latter has conversion features, while the Classic 33 does not. The engineers at Mosley designed the Classic 33 to give the ham a little extra gain on all bands. It is our conviction that discriminating DX'ers will find this new tri bander specifically suited to their needs, but hams buying the well-known TA-33 will still enjoy a superior quality DX antenna with a gain very close to that of the Classic 33.

The Ultimate Station Control

Arrange your station for perfect break-in and complete control of antennas, power and changes of equipment.

How many times have you visited a fellow ham's shack and left wishing that you had a set-up like his—a set-up that was a pure pleasure to operate? How many times have you tuned the low ends of 80 and 40 and listened to the brass pounders operate full CW break in and felt like joining the fun? You knew you couldn't join in because of the manual receive-transmit switching you have and so you dejectedly tune off frequency looking for a "you send awhile—then I send awhile" QSO. How many times have you rejected the idea of building or buying a TR switch because they "suck-out" signals in the transmitter tank circuits in receive mode?

Well friend, read on and find out how you can organize your equipment into a sweet running system that'll make you beam with pride. But—WARNING!—you may have to buy your XYL a fur coat to compensate for all the operating time you'll be putting in with your rig once you get it working in this type of system.

Although few hams will have the exact equipment configuration as this system the features of this control unit can be applied to almost anything you may have.

The highlights of this system are:

1. Full break in by using a TR switch with no signal "suck-out" at all after being in receive mode for a couple of seconds.
2. Automatically switches to transmit mode when the key contacts close or the VOX relay is activated.
3. Allows rapid change (flip of a switch) between exciter only or amplifier operation.
4. Controls DC input to final amplifier.
5. Gives rapid selection of antennas.
6. Automatically mutes receiver when the key is closed.
7. Provides CW side tone. Can be used as a code practice oscillator.
8. Allows rapid changes in equipment configurations.
9. Puts only 17 volts, low current, across

key contacts—eliminates exposed shock hazard and arcing.

At the end of this article is a list of component functions that will assist your "trek" thru the diagrams without wasting time. A more thorough explanation of the more involved functions is in the text between here and there.

Fig. 1 is a diagram of the RF and antenna selection circuits of the system. By bringing all low level RF circuits up to a patch board on the side of the station control units it is possible to change the system configuration without getting out of your chair. Sure beats crawling behind the desk or table to change connections.

Note that when RL2 is down (de-energized) RF is fed straight thru the amplifier to the antenna circuit. When RL2 is up (energized) the exciter is coupled to the amplifier input and the amplifier output is connected to the antenna circuit.

RL5 is the little gem that prevents receiver signal "suck-out" after the system is in receive mode for a couple of seconds. RL5 is normally down, isolating the antenna circuit from the amplifier or exciter tank circuit, and comes up when the key contacts close or the VOX relay is activated. The use of RL5 along with a TR switch allows you to operate full break in and still be able to hear the real weak DX stations when you are in receive mode.

When S5 is in the 160 meter position RL6 will be picked up. RL9 will stay down because current will not flow thru D9. When S5 is in the 80 meter position RL9 will be picked up and at the same time current will flow thru D9 picking RL6. Although RL6 thru RL9 have 12 volt coils 17 volts is applied because of the long line run to the relays and resulting voltage drop.

The Marconi antenna in this system is $\frac{3}{4}$ wavelength long on 160 meters and has a feed point impedance of 120 ohms. Even though this requires a reverse-pi matching network

the higher impedance reduces ground losses commonly associated with Marconi antennas. With the low power restrictions on 160 meters you cannot afford unnecessary losses.

Fig. 1 also shows the RF patch board and jumper diagrams for: 160 meter CW/AM, 80-20 meter CW/AM, and 80 meter SSB. Any of these configurations can be patched in less than a minute. The patch board is made up of phono type sockets mounted on an aluminum bracket. Coax cables going to the various units are soldered to the jacks and have plugs to match the units on the other ends. When you get that new piece of equipment all you have to do is unplug the old unit and plug the new unit in. All the RF circuits of the new unit will be available at the patch board ready to go.

Fig. 2 shows the 110 VAC primary circuits of the control unit. The operation of the primary circuits is quite straightforward. It is important that S1 and S2 have the indicated current rating. RL2, RL4, and RL5 are Guardian Series 200 DPST relays with like contacts wired in parallel to increase their current carrying capacities. Here also, flexibility was the prime goal. Jacks J7 thru J11 will provide controlled primary power for any piece of equipment you have—unless you're bootlegging with a 10 kW job.

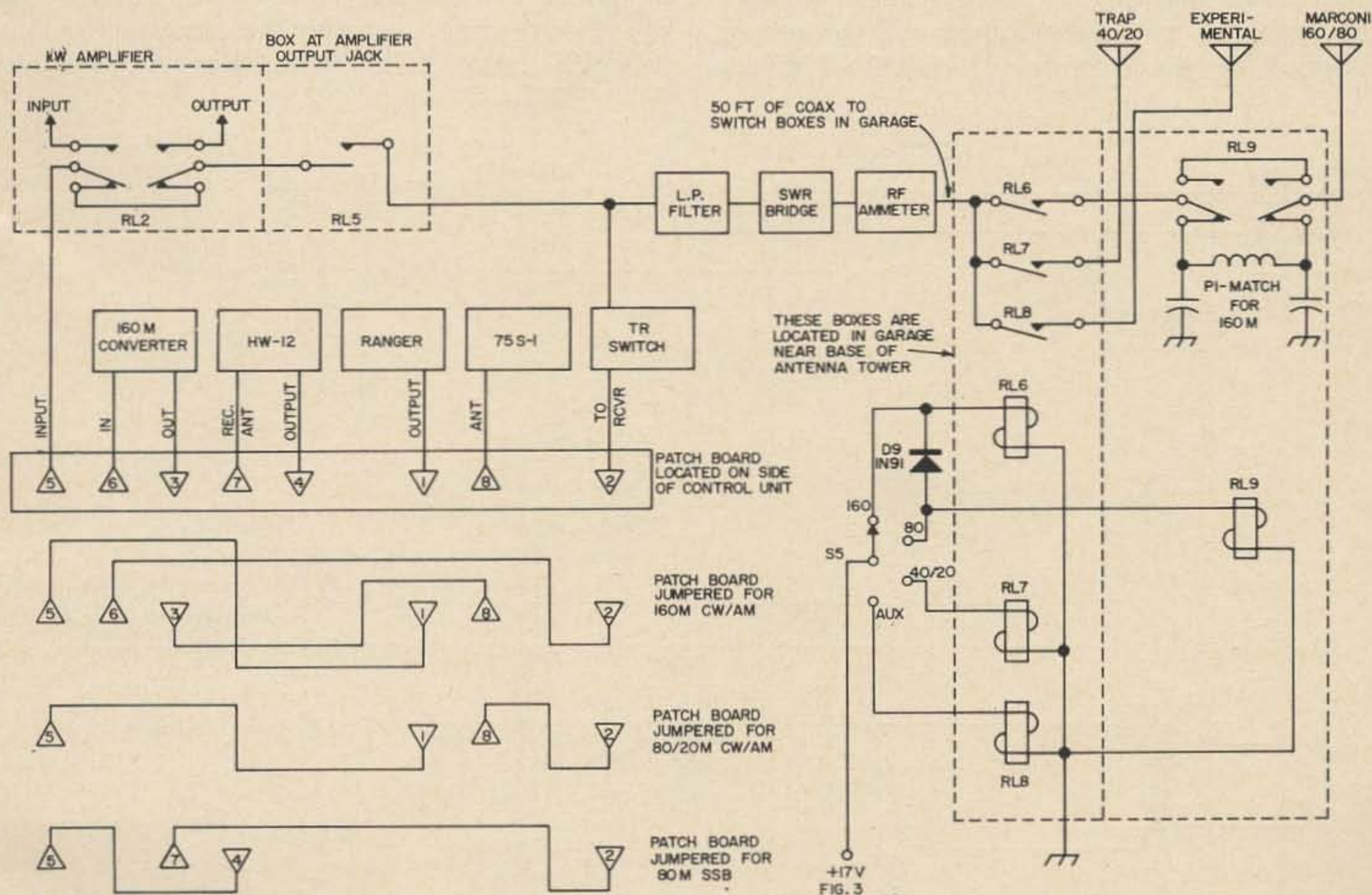


Fig. 1. RF routing and station configuration of W2AJW's station control system. The function of each major part is explained at the end of the article.

Fig. 4 is a graphic representation of what actually happens inside the control unit when the key contacts close or the VOX relay is activated. The lines shown in Figs. 4A, C, and D and referenced to 4B which represents in this case the letter "L" being sent with the key. The up levels show the key contacts closed and the down levels show the key contacts open. By working your way from left to right on line 4B and taking a reading on lines 4A, C, and D each time the level of line 4B changes you can see exactly how the break in function of the control unit works.

At first glance the transistor circuits shown in Fig. 3 looks a bit complicated to digest. Actually, all the transistors except Q8 and Q9 are used as switches. They are either in a state of conduction or completely cut-off. This makes the selection of transistors to use quite simple. About anything you have in your junk box will work. The ones used here, other than Q8 and Q9, were obtained from Radio Shack and didn't have any commercial type indicated on them. They were removed from scrapped computer circuit boards that Radio Shack has for sale. Q8 is a 2N718 and Q9 is a 2N269 as recommended by Robert D. Corbett in his July 1965 73 Magazine article "CPO-CWM" that described the CW sidetone oscillator used in this control unit.

To determine if a transistor is conducting note the relationship of base voltage to emitter voltage. If the transistor is an NPN type like Q1 and the base is more positive than the emitter it will be conducting. If, in the case of Q1, the base is negative in respect to the emitter the transistor will be cut-off and no current will be flowing thru it. Just the opposite is true of PNP transistors, like Q4. When the base of Q4 is positive in respect to its emitter it will be cut-off.

Let's take a look at Q1, Q2 and RL3A and RL3B. In receive mode with the key contacts open the bases of Q1 and Q2 are at minus 17 volts. Because the emitters of Q1 and Q2 are biased to a minus six volts they will be cut-off and RL3 will be down. When the key contacts are closed, as in the first dit of the character "L" shown in Fig. 4, the bases of Q1 and Q2 will be shorted to ground thru the 330 ohm resistor. Now that the bases are more positive than the emitters Q1 and Q2 will go into heavy conduction with current flowing thru RL3A and RL3B picking up RL3.

Simple huh?

By keying the bases of Q1 and Q2 rather than keying the relay directly you have removed that source of high current from the key contacts and eliminated that source of arcing and key-clicks.

RL3 has two coils mounted side by side. The coils are each 5000 ohms and are wired in series by the manufacturer. This applica-

tion requires that the connecting wires be removed so that the coils can be wired as shown. You must experimentally determine how to wire the coils so that when both coils are wired in this circuit the fields do not oppose each other. If they do oppose each other the relay will not pick up. Why do we split the coils of RL3 into two coils, RL3A and RL3B? This is done to satisfy two conditions. First-to allow RL3 to pick up and close its contacts as quickly as possible to reduce the amount of the first dit or dah that is missed while the station is going into transmit mode. Second-to provide a hold-up circuit for RL3 and therefore stay in transmit mode between characters and words Q1 and RL3A take care of the first condition and Q2 and RL3B and C1 the second.

Diode D5 isolates Q2, RL3B, and C1 from Q1 and RL3A at the instant the key is closed and Q1 and Q2 conduct. Because at this instant C1 is discharged it will act as a dead short across RL3B. If RL3B was the only coil on RL3, RL3 would not pick up until C1 had charged up to the point that enough current started to re-route thru RL3B to attract the relay armature. This would cause a considerable portion of the first dit or dah, in fact quite a bit of the first character, to be lost. Coil RL3A, because it is not shunted by a capacitor and is isolated from C1 by D5 at key closure time, provides the necessary quick pick up time of RL3. When the key contacts

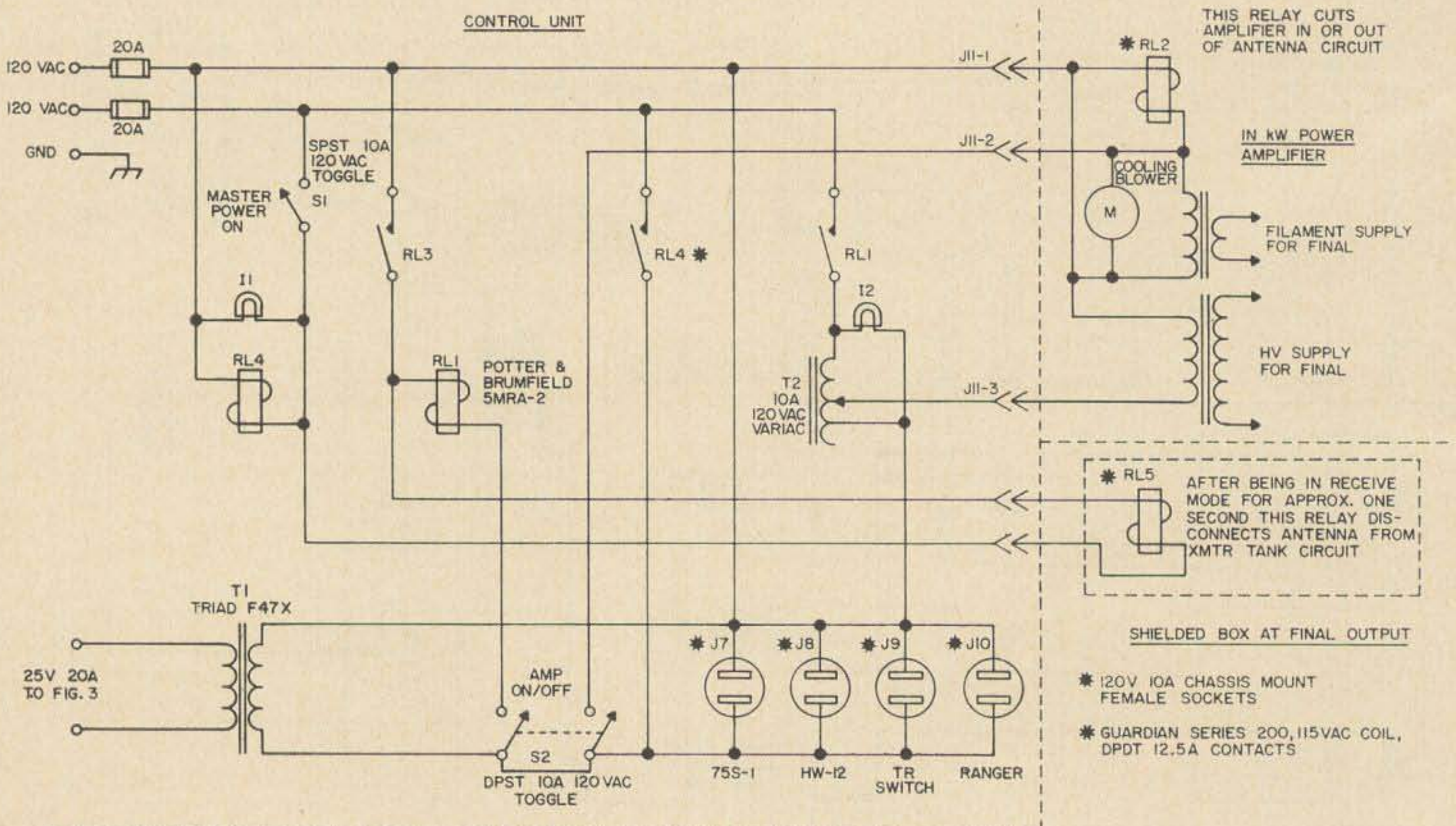


Fig. 2. Primary power circuits and control of W2AJW's control system.

SUPPRESS RFI IN YOUR MOBILE RADIO GEAR!



SPRAGUE SUPPRESSIKITS FOR VEHICLES WITH ALTERNATOR SYSTEMS

Easily installed on cars or light trucks with citizens' band, amateur, industrial, or public service mobile radio equipment

★ Four different Suppressikits to choose from—Type SK-10 for Chrysler Corp. cars and trucks, Type SK-20 for Ford Motor Co. vehicles with FoMoCo alternators, Type SK-21 for Ford equipment with Autolite alternators, and Type SK-30 for General Motors Corp. vehicles.

★ Designed to fit most newer vehicles through the 1966 model year. (for older vehicles, see the SK-1 Suppressikit, below.)

★ Well-engineered L-C Networks and/or heavy-duty Thru-pass Capacitors handle the hash and eliminate the siren-like whine caused by the alternator output.

★ Extremely easy to install—no cutting, no soldering, no wiring harnesses. All components are neatly marked and packaged, and come complete with comprehensive step-by-step installation instructions.

★ Provide really *effective* interference suppression through 400 mc, at moderate cost.

★ Will stand up under continuous operation in hot engine compartments.

★ Permit faster, more readable, less tiring communication at greater ranges.

TYPE SK-1 SUPPRESSIKIT FOR VEHICLES WITH D-C GENERATORS



Designed for simple but effective installation. The generator capacitor is built for continuous heavy duty 257°F (125°C) operation. A full 60 ampere current rating plus the high rated operating temperature provide an extra factor of safety against expensive generator burnouts, unlike many suppression assemblies containing general-purpose capacitors. Effectively suppresses RFI through 400 mc. Includes easy-to-follow installation instructions.

SPRAGUE®
THE MARK OF RELIABILITY

GET YOUR SUPPRESSIKIT FROM A SPRAGUE DISTRIBUTOR TODAY!

88-8110R2

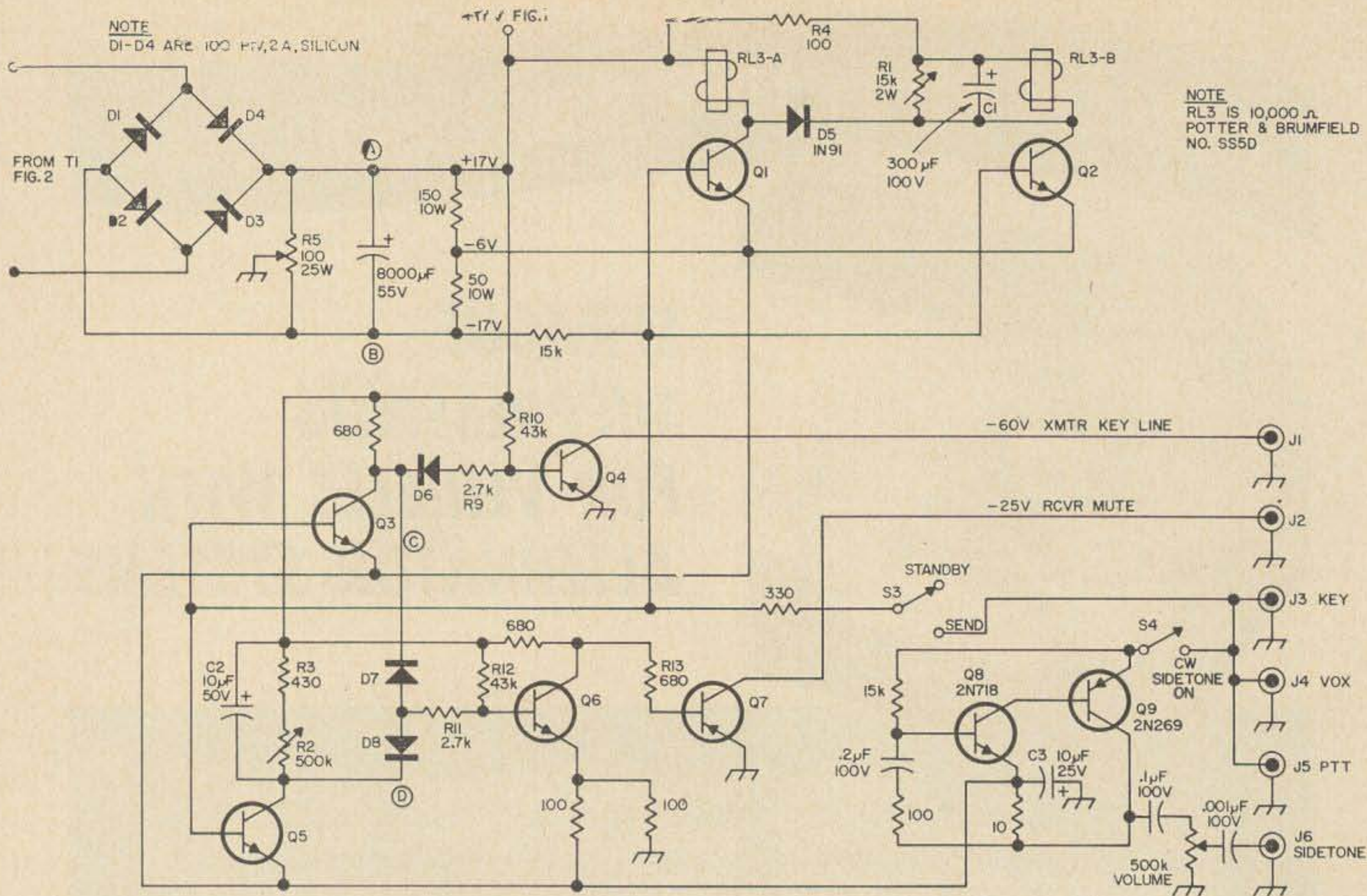


Fig. 3. Transistor switching circuits and code monitor.

open Q1 and Q2 will be cut-off and C1 will have three discharge paths: 1-thru RL3B, 2-thru R1, 3-thru R4, RL3A, and D5. The discharge path thru RL3A as well as RL3B gives a more uniform pull on RL3 armature and better control on its drop out time. Note that the discharge path thru R1 is variable. Decreasing the resistance of R1 will make C1 discharge more rapidly and cause RL3 to drop out quicker.

Q3 and Q5, along with Q1 and Q2, are controlled directly by the key contacts or VOX relay. Like Q1 and Q2, Q3 and Q4 are normally cut-off and conduct when the key contacts close. Q3 controls Q4 and Q6. Q5 controls only Q6. When Q3 conducts its collector goes to a minus 6 volts, current will flow thru D6, R9, and R10. It can be seen from the values of R9 and R10 that the base of Q4 will go to about a minus 4 volts (from plus 17) and Q4 will conduct keying the transmitter.

Now we run into a circuit known as a "minus or". This is made up of diodes D7, D8; resistors R11, R12; and transistor Q6. When the key contacts are open Q3 and Q5 are cut-off and points C and D of diodes D7 and D8 are at a plus 17 volts. Since R12 ties back to plus 17 volts the base of Q6 will be biased so that it will be conducting. With Q6 conducting its collector will be at a minus two volts. This same voltage is applied to the base of

Q7 making it conduct putting the receiver in receive mode. (Like many receivers this one is in receive mode when the "receiver mute" line is grounded.)

In order to satisfy a "minus or" all you have to do is "make" one leg of the switch. For instance, if point C was minus and point D was plus, current would flow thru D7, R11, and R12 to plus 17 volts. Since R11 has a much smaller resistance than R12 most of the voltage drop would be across R12. The voltage at the junction of R11 and R12, point E, would be negative. Conversely, if point D was minus and point C was plus current would flow thru D8, R11, and R12 to plus 17 volts. In either case the base of Q6 would be biased to cut-off and the collector would go to plus 17 volts and in turn cut-off Q7 muting the receiver. At the same time we could call this a plus "and" circuit. That is, if both points C and D are plus Q6 will conduct.

When the key contacts close Q3 and Q5 will conduct and points C and D will go to a minus six volts and the receiver will be muted. Capacitor C2 will charge thru the path; minus six volts, Q5, C2, to plus 17 volts. At the instant the key contacts open the transmitter oscillator STARTS to turn off. The turn off time of the transmitter oscillator takes but a fraction of a second but if your receiver has a rapid recovery time, as in my case, you will hear a "thump" in the speaker. Q5, C2, and

D8 eliminate this "thump". Remember it was said that C2 charges when the key contacts close? Well, when the key contacts open C2 has two discharge paths: 1- thru R3 and R2; 2- thru D8, R11, and R12. The first path is variable and is used to control the length of time the receiver will be muted between dits and dahs or characters. The second path is the one that actually holds the receiver muted after the key contacts open. The smaller the resistance of R2 the quicker the receiver will recover. It is possible to set R2 so that all transmitter sound is removed but still be able to hear a break in signal between bits of a character when sending at 20 wpm.

Fig. 5 shows an alternate method of keying a transmitter or muting a receiver. This method would have to be used if your transmitter has cathode keying or if your receiver has a positive mute line. Of course a combination of Fig. 5 for the transmitter and Fig. 3 for the receiver could be used, or vice versa.

The relays shown in Fig. 5 are ultra sensitive radio control units that pull in with only 1.4 mA coil current. If a less sensitive relay is used it will be necessary to increase the voltage fed to the relay. Diodes D10 and D11 prevent ringing in the circuits when Q4 and Q7 are cut-off. At the instant the circuit thru the relay coils is cut-off the voltage in the coils will spike to a very high value and possibly ruin Q4 or Q7. In any case this spike will generate electrical noise.

So there you are. If you want the ultimate in station control then drag out the tools and get busy. The effort will be well worth it and besides—here's that "built it yourself" project you've been waiting for. A project that will not only give you that sense of accomplishment in building something yourself but will also add immeasurably to your operating pleasure.

Here is the list of component functions that I promised you earlier.

- C1— Provides a hold for RL3. When Q2 conducts C1 will build up a charge. When Q2 is cut-off C1 will discharge thru R1 and RL3 and keep RL3 picked up. The length of time that RL3 will stay up depends on the setting of R1. The smaller the resistance of R1 the quicker RL3 will drop out.
- C2— Keeps the receiver muted for a short period after the key contacts break. This prevents break clicks or thumps. The discharge rate of C2 and consequent mute time is controlled by the setting of R2.
- C3— Bypasses CW side tone on minus

six line to ground.

- D5— Isolates RL3A from RL3B at the instant Q1 and Q2 are put into conduction. Provides a C1 discharge path thru RL3A as well as RL3B after Q1 and Q2 are cut-off.
- D6— Allows a rapid cut-off time of Q4 when the key contacts open.
- D7-D8— Make up a two legged "minus or" switch. A minus shift into either D7 or D8 will cut-off Q6.
- D9— Allows the pick up of RL6 when S5 is in the 80 meter position as well when S5 is in the 160 meter position.
- D10-D11— Prevent ringing in relay coils at the instant Q4 or Q7 in Fig. 5 are cut-off.
- I1— Lights when primary power is on.
- I2— Lights when high voltage is on in amplifier.
- J3-J5— Any device that switches to ground can be connected here. When one of these jacks is shorted to ground, with S3 in the send position, the control unit is put in the transmit mode.
- J6— Provides CW side tone if S4 is on and one of jacks J3 thru J5 is shorted to ground.
- J7-J10— Provide 110 VAC to station units (receiver, TR switch, etc.).
- Q1— Allows a rapid pick of RL3. Normally cut-off.
- Q2— Charges C1 to provide a hold up voltage to RL3 after Q1 and Q2 are cut-off when the key contacts open or VOX relay drops out.
- Q3— Provides a minus switch voltage to Q4 and Q6. Q3 is normally cut-off and conducts when the key contacts close.
- Q4— Keys the transmitter. Q4 is normally cut-off. Q4 conducts when a

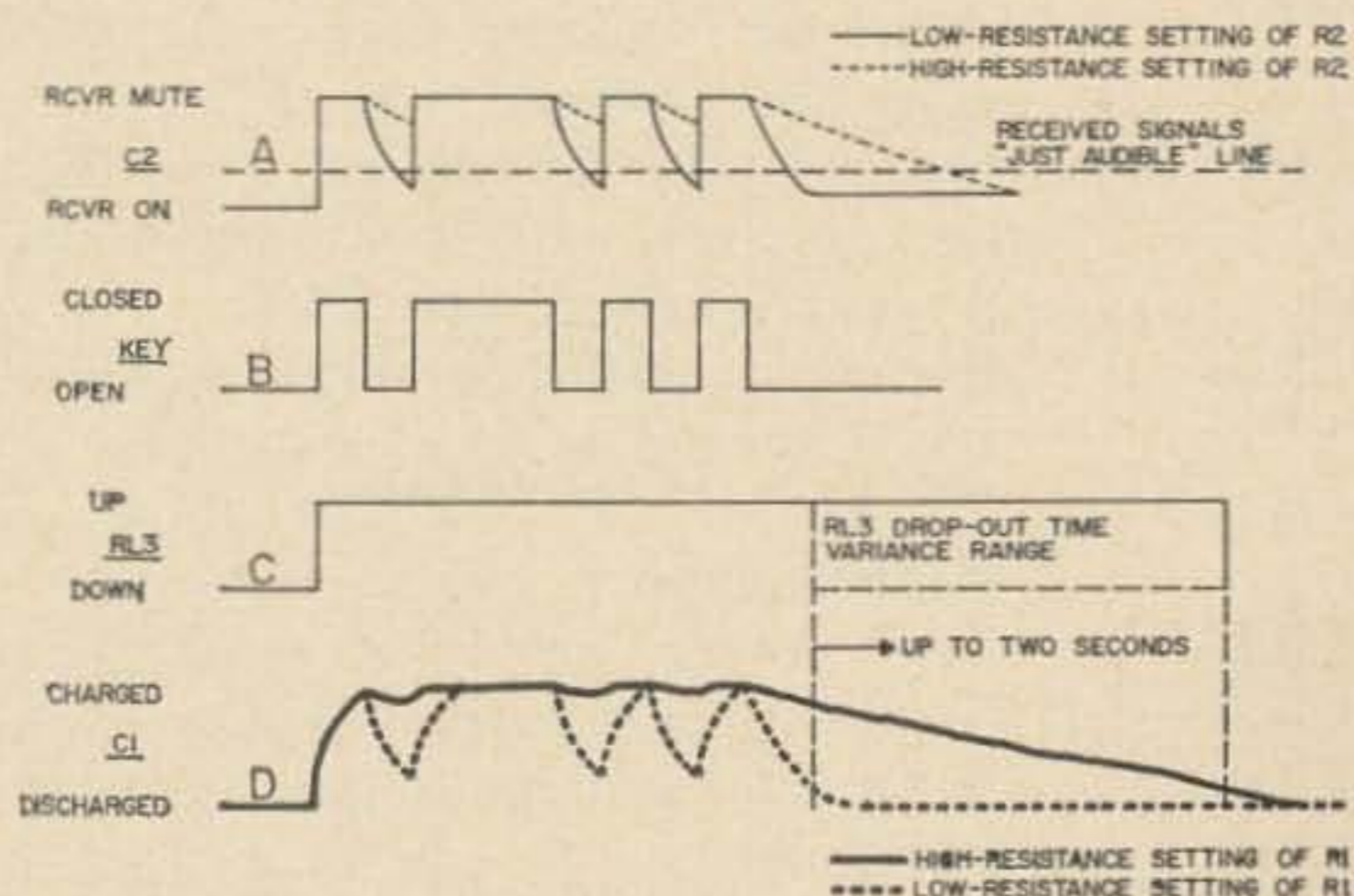


Fig. 4. Control unit timing.

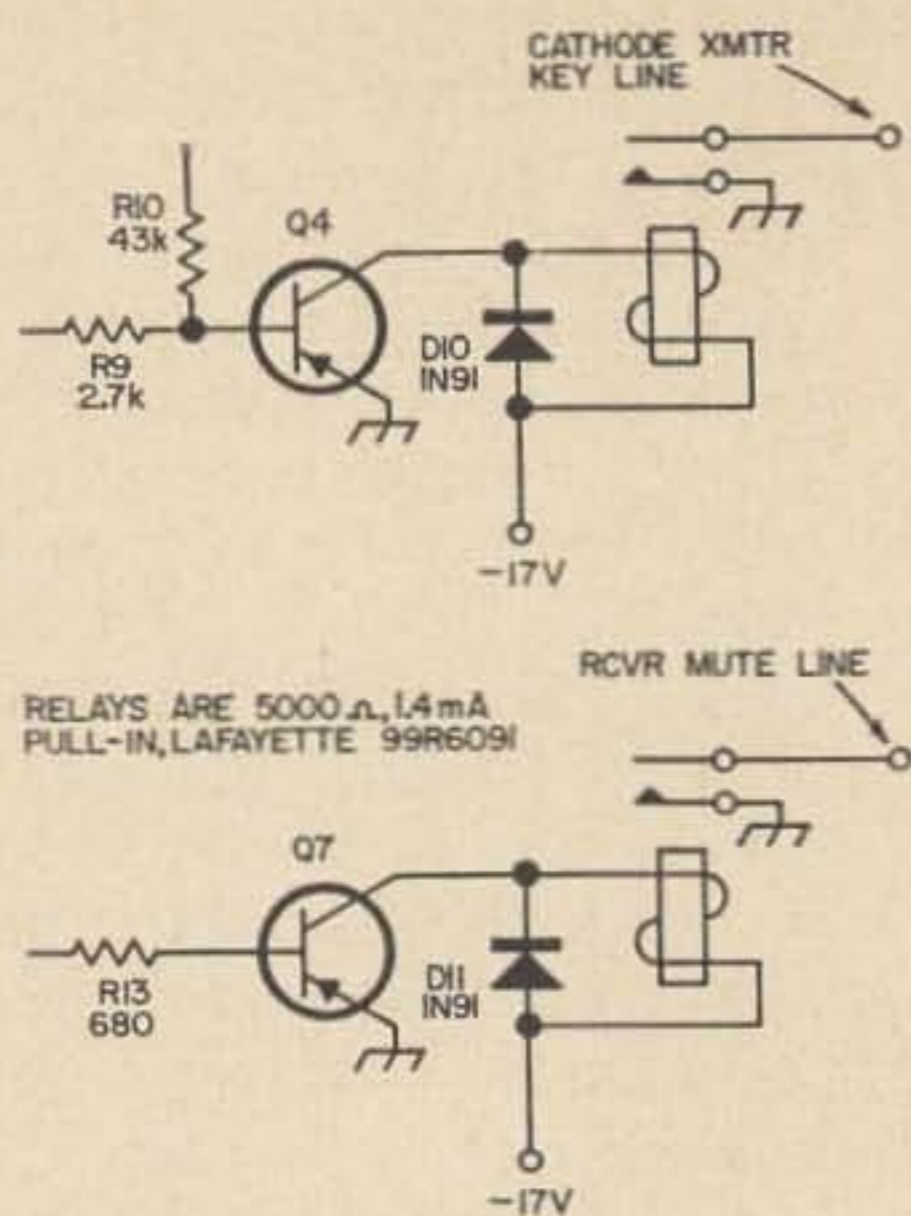


Fig. 5. Alternate key and mute circuits.

- minus voltage is applied to its base thru D6.
- Q5— Provides a minus hold voltage to Q6. Q5 is normally cut-off and conducts when the key contacts close. When Q5 conducts C2 develops a charge. When Q5 is cut-off when the key contacts open C2 will discharge thru R2 and R3. The time that C2 takes to discharge depends on the setting of R2. The charge on C2 will keep Q6 cut-off.
- Q6— Provides a minus switch voltage to Q7. Q6 is normally conducting. Q6 is cut-off when either Q3 or Q5 conducts providing a minus input to D7 or D8.
- Q7— Mutes the receiver. Q7 is normally conducting and is cut-off, muting the receiver, when the key contacts close.
- Q8-Q9— CW side tone oscillator. July 1965 73 Magazine.
- R1— Controls the length of time that RL3 stays up and therefore, how long the control unit will stay in transmitt mode after the last CW character has been sent or the VOX relay has dropped out.
- R2— Controls the length of time that; the receiver will stay muted after the key contacts open.
- R3— Prevents ruining of Q5 in the event R1 is turned to zero resistance.
- R4— Prevents ruining of Q2 in the event R1 is turned to zero resistance.
- R5— Sets power supply ground point. Should be set so that points A and B are of equal potential but opposite polarity.
- RL1— Completes the circuit to the Variac, T2, which in turn applies primary

- power to the amplifier high voltage power transformer. RL1 picks up if S2 is on and RL3 picks up.
- RL2— Connects the amplifier between the exciter and the antenna. RL2 picks up when S2 is on and RL4 picks up.
- RL3— RL3 contacts pick up RL1 (if S2 is on) to turn on the amplifier high voltage supply and to pick up RL5 to connect the antenna circuit to the exciter or amplifier output circuits. RL3 picks up when Q1 and Q2 conduct.
- RL4— RL4 contacts provide primary power to T1 and units connected to sockets J7 thru J10. RL4 picks up when S1 is turned on.
- RL5— RL5 contacts connect the antenna circuit to the exciter or amplifier output circuits. RL5 prevents transmitter tank circuit signal "suck out" when in receive mode. RL5 picks up when RL3 contacts close.
- RL6— Routes RF voltage to RL9. RL6 picks up when S5 is in either the 160 or 80 meter positions.
- RL7— Selects the 40-20 meter trap inverted vee antenna. RL7 picks up when S5 is in the 40-20 meter position.
- RL8— Selects the experimental antenna. RL8 picks up when S5 is in the AUX position.
- RL9— Picks up when S5 is in the 80 meter position. When RL9 is down the pi network is connected between the 52 ohm line and 120 ohm Marconi antenna. When RL9 is up RF is fed straight thru to the Marconi antenna. (This Marconi matches 52 ohms on 80 meters).
- S1— Turns on the control unit and supplies 110 VAC to the receiver, exciter, TR switch, etc.
- S2— Turns on RF amplifier. S2 also switches the amplifier into the antenna circuit.
- S3— In the "SEND" position allows the station to be put in transmit mode when the key is closed or VOX is operated. In the "STBY" position allows the CW side tone oscillator to be used as a code practice oscillator.
- S4— In the "CW SIDE TONE" position gives side tone when the key is depressed.
- S5— Selects the antenna to be used.

... W2AJW

MASTER ORDER BLANK

Name Call

Address

City State Zip or Country

Subscription to 73: 1 year \$4 2 years \$7 3 years \$10 Life \$50

New Renewal Extension

VHF Antenna Handbook \$2

Parametric Amplifiers \$2

ATV Anthology \$3

CW 50¢

Care and Feeding of Ham Clubs \$1

Ham RTTY \$2

Receivers \$2

Surplus TV Schematics \$1

Revised Index to Surplus \$1.50

Simplified Math 50¢

Test Equipment 50¢

Binders \$3 per year: 60-61, 62, 63, 64, 65, 66

1963 Bound Volumes \$15

Back Issues: O, N, D 1960 are \$1

F 1961 through present are 50¢

Frequency Measuring, Coils and Ham TV are out of print.

Subscriptions take six to eight weeks to process.


73 Magazine

Peterborough, N.H. 03458

ARTICLES COMING UP IN 73

K1CLL: 80 watts on 144 for \$80
 K1CLL: 150 watt Compactron two meter linear
 W2DXH: Zener diodes—the complete story
 W2DXH: \$5 WWV receiver
 WB2GYS: Video camera tubes
 K3LNZ: Negative cycle loading for you
 K3QKO: Portable electronic keyer
 K5JKX: Equipment protection
 K5JKX: Antenna stacking
 K5JKX: T-pads
 W6BLZ: The ancient mariner
 W6BLZ: 75 meter SSB transceiver
 W6DDB: Making radio clubs work
 WA6PZR: Amateur microwave propagation
 K6RIL: 432 MHz SSB mixer
 K6ZGQ: SSB power supply
 K8ERV: Equalizing AFSK tones
 K9EID: Six meter linear
 K9EID: Two tube two meter SSB mixer
 K9VXL: The multicalibrator
 WB2EGZ: 220 MHz superregen
 K3ADS: Ham TV, parts one and two
 K6MIO: Illumination and parabolic design
 K6RIL: Transistor VFO for VHF or HF SSB
 W6TAQ: SSB speech clipper
 K6ZGQ: A little about noise
 W7CSD: 6JB6 linear
 Nelson: Propagation
 W6OSA: Improved multiplier for 144, 432 and 1296
 W6AJF: VHF antennas
 W7CSD: KW linear with 6KG6's
 W1JL: Novice transistor receiver
 W1JL: Novice transistor transmitter
 And much, much more

PARAMETRIC AMPLIFIERS

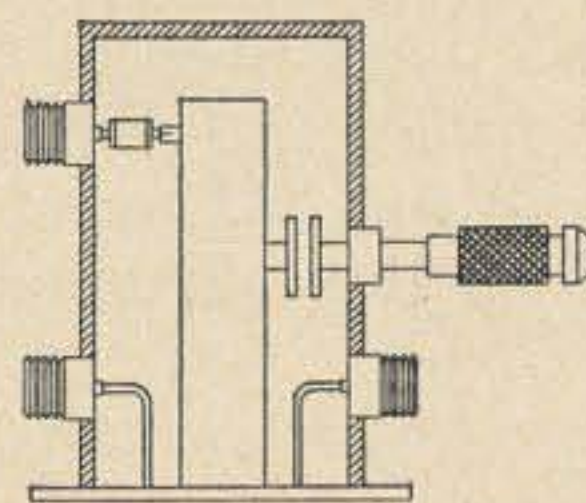

Jim Fisk WA6BSO

COPYRIGHT 1964 BY 73 INC., PETERBOROUGH, N.H. \$2

Is your VHF converter noisy? Are you interested in working moonbounce on 432? How about DX on 1296 or 2300? If you're in the forefront of VHF and UHF developments, you are probably working well into the noise of your receiver. Even with many of the recent low noise transistor developments, short of a maser the PARAMETRIC AMPLIFIER is still the *only* way to get really low noise figures above 300 MHz. PARAMETRIC AMPLIFIERS is the only book written explicitly with the amateur in mind; it explains how they work, how to build them and what diodes to use. If you're interested in weak signal work, you should have this book. \$2.00 postpaid, or from your local parts distributor.

73 Magazine
Peterborough, N. H. 03458



Ed Marriner W6BLZ
528 Colima Street
La Jolla, California

Match Box Tuner

That Old Tuned Line

*When I was young and in my prime
I used antenna tuners all the time,
But now that I am old and grey
I use coax the modern way.
I think I've strayed and find it's time,
I went back to that old tuned line
I went back to that old tuned line.*

About thirty years ago most radio amateurs used tuned feeder lines in conjunction with an antenna tuner. Today just about all amateur stations use coax fed antennas, but some station operators are going back to the old method. Why? Until recently transmitters and SSB transceivers used large plate dissipation tubes in the output stage. If these tubes are overloaded they might get a little cherry red, but it did not seem to hurt them. Every one was happy, no problems, even if the rig was operated far from the resonant frequency of the antenna.

Today every radio gadget is smaller, and so are the tubes. Many manufacturers are using small TV sweep tubes in transceivers to keep the size compact. They hope the amateur op-

erators using them have a flat antenna feeder line with no SWR (standing waves), and they also hope that he stays on SSB and does not hold the key down too long when tuning. The use of small tubes is based on the SSB operation with its low duty cycle, and that type of operation is not hard on the output tubes.

Just how many amateurs are using beams or dipole type antennas fed with coax today? Just about all of them, and how many of these have tuned the transmitter off from the resonant frequency of the antenna and taken a good hard look at the SWR and the color of the output tubes? The SWR does not have to go up in value very much before the rf begins to stay in the rig and be dissipated in the plates of the output tube rather than in the antenna.

Well, just what can be done about all of this faulty operation? Really there isn't a thing the coax fed operators can do about SWR except keep the rig looking into 50 ohms by a matching network, or change to an antenna that can be resonated to the operating frequency. The only reasonable way to use a resonant antenna is to go back to the antenna tuner and some type of antenna that can be tuned. Those operators who have fussed with antenna tuners in the old days will back away from the idea and shudder because it brings back

memories of trying to locate the feeders on the proper matching point on the tuner coil. This can be an exasperating job. However, the old timers can relax. The Johnson Company makes a gadget to replace tapping the coil. It is called a duo-differential capacitor. This capacitor when put across the coil acts as a capacitance tap, and in conjunction with the tuning capacitor keeps the coil in resonance. The old pain is gone. It's now easy to tune up the tuner.

The duo-differential capacitor is only made by the E. F. Johnson Co., and is generally not found in the catalogs or radio stores. It has to be ordered directly from the factory under the part number 169-25. When constructed the antenna tuner will handle 300 watts of CW or SSB on all bands, and maybe more depending on the insulation. Actually this match box is the same as the regular standard Johnson Matchbox but with modifications. The coil has been adapted to the Air-Dux coil in place of the specially wound Johnson coil which has a variable pitch in the center for the high frequency bands. The insulated switch shaft used by the manufacturer was also impossible to duplicate, and other arrangements were used to change bands. A battery clip fastened to flexible leads was used in place of a switch and worked very satisfactorily.

In this constructed tuner two separate coils were used. One coil tunes the 80-40-20 meter ham bands, another the 10-15 meter bands. Two separate inputs are used, as the link for the big coil is matched better with three turns, and the small coil with two.

To change bands the lid is lifted on the tuner box, the fahnstock battery clips are quickly pressed with the finger and moved to the taps desired for the proper band. The dial is moved to pre-marked settings for the various bands and slightly adjusted for minimum SWR.

As it turns out the maximum received signal on a receiver is just about the proper adjustment for the minimum SWR point when the transmitter is used.

For an all band antenna it is recommended that a 136 foot center fed zepp antenna be used if possible, with 600 ohm feeders about 45 feet long. Another suggestion would be to use 450 ohm manufactured feeders made from number 12 wire. Another suggestion is to use screw-in type electrical insulators for long runs of wire under the eaves of the house and pulling #12 wire through them and soldering tight. This method cuts down on the use of spacers except for the part actually going up to the antenna.

Construction

There is no special way to build the tuner. It is nice if it can be put in a box, but construction on just a chassis will be fine. The split-stator capacitor is mounted on metal studs to the chassis and the duo-differential capacitor is mounted on stand-off insulators. Two, 4½ inch lucite insulators are mounted at each end of the duo-differential capacitor to hold a ¼ inch thick by one inch wide lucite bar. Some long 4-40 machine screws with lugs were put in the strip to slip the band switching clip lead over when changing bands. The coil could have been shorted out when changing bands if separate coils had not been used, but in this construction the surplus turns are left floating rather than shorting them out.

Tuning

The transceiver output probably should be first tuned using a 50 ohm dummy load resistor to get the pi-network setting correct for 50 ohm output. The rig can then be connected to the tuner input. The tuner condensers can be varied for maximum signal strength, and then tuned for the low SWR indication which is between the tuner box and the transmitter in the coax link. When correctly tuned it should read very close to zero! Now you can increase the output power and are on the air. If a center fed zepp 136 feet long is used, operators will be surprised how much better signal reports will be over the old antenna especially when it is used on the higher frequency bands where the lobes begin to reach out. The main comparison from the long wire against the beam is that more noise is apparent on the zepp because it is not very directional. It is fun to switch from the zepp to the beam, there is not as much difference as one might suspect. It is also easier to use the center fed zepp for round table QSO's. I predict


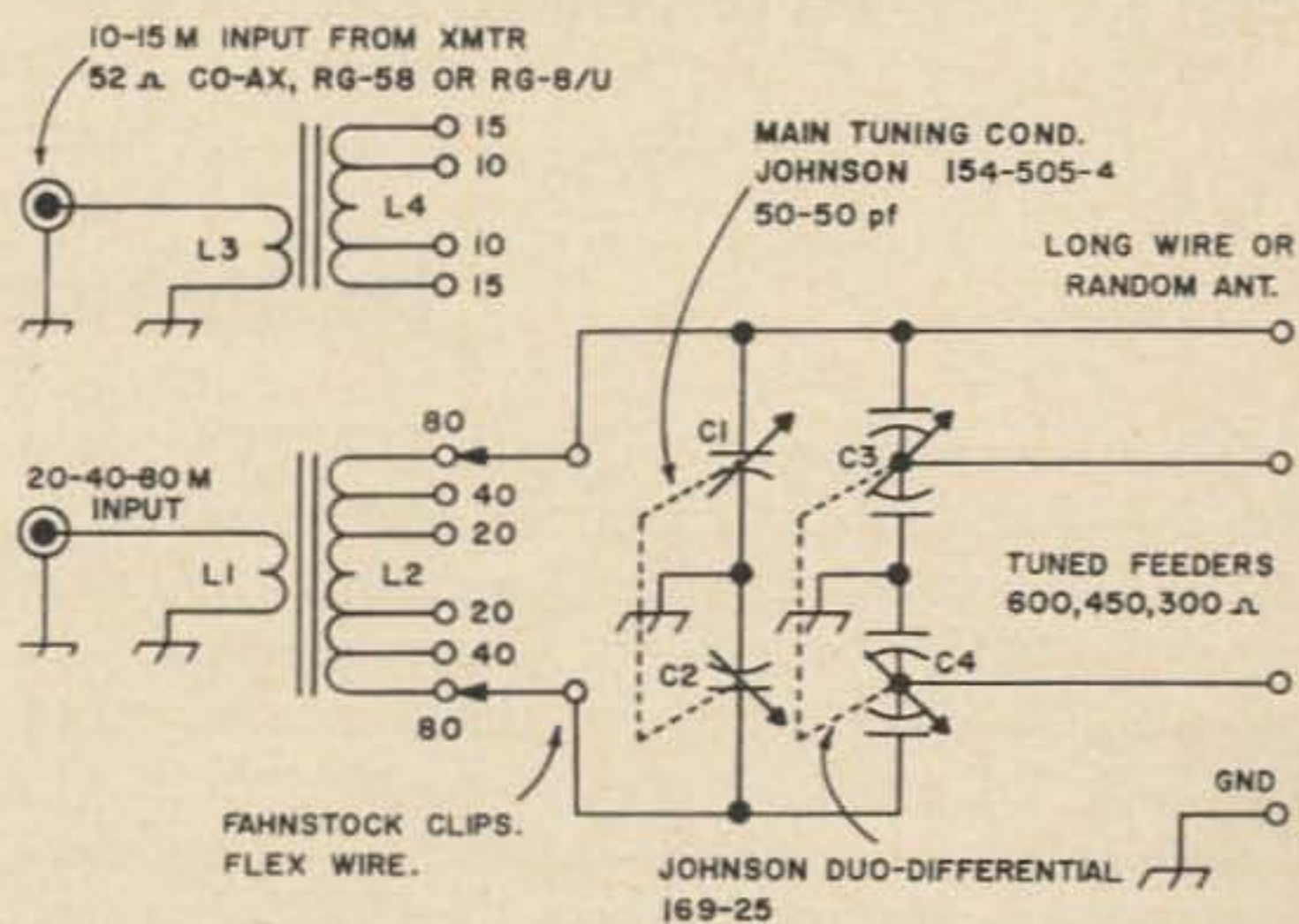


Fig. 1. W6BLZ's match box tuner. The coils should be shown as air wound.

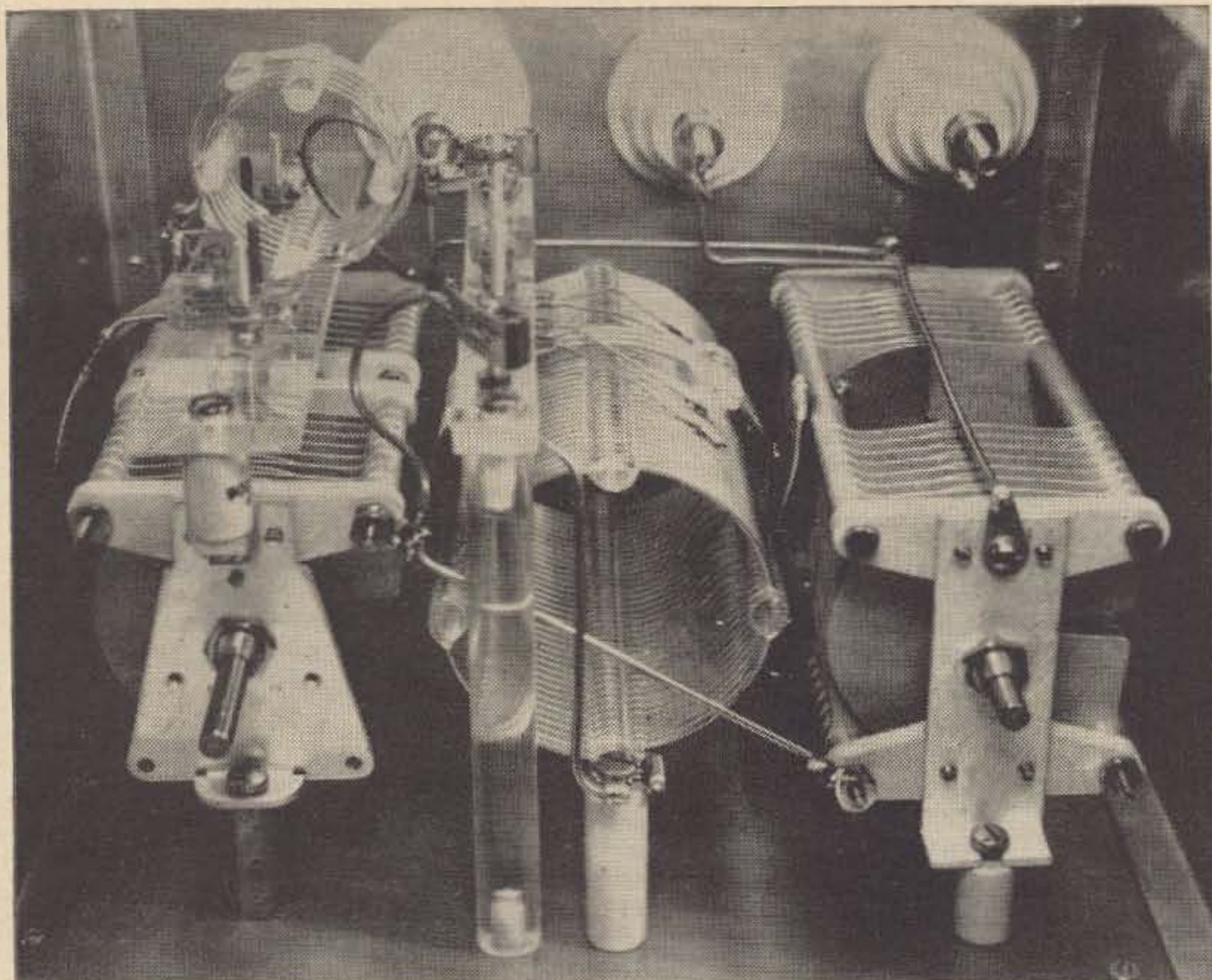

Rear of the match box tuner.

in the future more amateurs will return to this ancient type antenna with the old tuned line.

General information

This tuner will match a 52 ohm coaxial line from the transmitter output into any line from 25 to 1200 ohms. For unbalanced lines it will match up to 3000 ohms making it suitable for using a long wire, or random wire antenna. The coupler is designed for antenna and transmission line matching and switching within the amateur bands from 3.5 to 30 MHz. A SWR indicator should be used between the coupler and the transmitter, inserted in the 52 ohm transmission line. The coupler cannot be expected to correct standing waves on the transmission line, which is a matter of match between the antenna and the line. The coupler will, however, properly terminate the co-

axial line from the transmitter and match it to the transmission line terminal impedance. The link itself will have no standing waves on it. By doing this there will be a maximum transfer of energy from the transmitter to the antenna system and the tubes in the final will keep cool.

When the coupler is used with broad band antennas the tuning will cover the whole band with one setting. The system will become more frequently critical as the SWR on the transmission line is increased. If the resistance at the coupler terminals is too high for the range of the coupler, the line should be either lengthened or shortened until the capacitors inserted into the line correct for it. This might occur when a random piece of wire is used for an antenna.

... W6BLZ

Double Your Sixer Power

The power input of a Heath HW-29A Sixer can be doubled by a simple reconnection to the 6CL6 output tube and a change in tubes from the 6CL6 to a 7558. Components C8-10 pF and R4-47 k must be disconnected from pin 9 of V4 (6CL6) and re-connected to pin 2 of V4. The oscillator, doubler, and final tuning must be retuned when the 7558 is used. The cathode current should run about 60 mA compared to 30 mA for the 6CL6. The 12 V

power cable filament jumper must also have the 150 Ω resistor replaced with a 50 Ω -1 watt resistor for mobile operation to correct for the higher filament current of the 7558. Improved audio can also be obtained by changing R-14 10 megohms to a 500 k Ω resistor located between pins 2 and 4 on V-B (12AX7). The pin changes to V4 permit the use of either the 6CL6 or 7558 interchangeably when used on 110 VAC. ... K3QAY

58. 90.9 21.

WOULD YOU BELIEVE TWENTY-ONE?

At least twenty-one
important and advanced
features built-in the brand new

BTI LINEAR AMPLIFIER MODEL LK-2000

YOU'RE THE EXPERT — CHECK FOR YOURSELF

■ 1. Designed for maximum legal input all modes. 2000 watts PEP SSB—1000 watts CW-AM-RTTY. ■ 2. Full 1000 watts plate dissipation using Eimac 3-1000Z. ■ 3. New tank circuit design provides greater output on higher frequencies including 10 meters. ■ 4. High Reliability Solid State Power Supply using Computer Grade capacitors for continuous duty. ■ 5. Instant transmit—no warm up—accomplished by BTI Solid State Supply and use of thoriated tungsten filament in 3-1000Z. ■ 6. Longer tube life because of exclusive after off cooling. ■ 7. A.L.C. output provides higher audio level without flat topping. ■ 8. Tuned cathode input for minimum distortion and higher efficiency (50 ohm inp.). ■ 9. Choice of Line Voltages—220V AC @ 10 amps or 115V AC @ 20 amps (Solid State Supply permits efficient

115 VAC operation). ■ 10. Metered relative R. F. watts output to antenna. ■ 11. Built in metering and switching for Dummy Load accessory which when attached provides dummy load for linear or exciter. ■ 12. Meter overload protection. ■ 13. Changeover relay feeds exciter direct to antenna when linear is off. ■ 14. All relays have D.C. coils for hum free operation. ■ 15. Safety switch and shorting bars for personal safety and component protection. ■ 16. High voltage overload circuit breakers. ■ 17. Fused filament and control supplies using lighted fuse indicators. ■ 18. Distinguished console (TVI preventive) design (29" H x 16" W x 14³/₄" D.) ■ 19. No exposed high voltage in lower console. ■ 20. Precision console casters for easy mobility. ■ 21. Grounded grid, zero-bias linear operation.

BRAD THOMPSON INDUSTRIES, long recognized for innovation in the electronics field, realized the need for a quality linear amplifier which would offer more features with reliable and rugged construction, at a price within practical limits.


Well-engineered, foolproof, simple operation, reasonably priced, fully guaranteed, the B. T. I Linear Amplifier provides the signal impact you've been wanting.

WRITE, WIRE, PHONE:
MISSION HAM SUPPLIES
3316 Main Street
Riverside, California

B. T. I. (Amateur Division)
83-810 Tamarisk Street—P.O. Box CCCC
Indio, California 92201

\$795

COMPLETE READY TO GO!

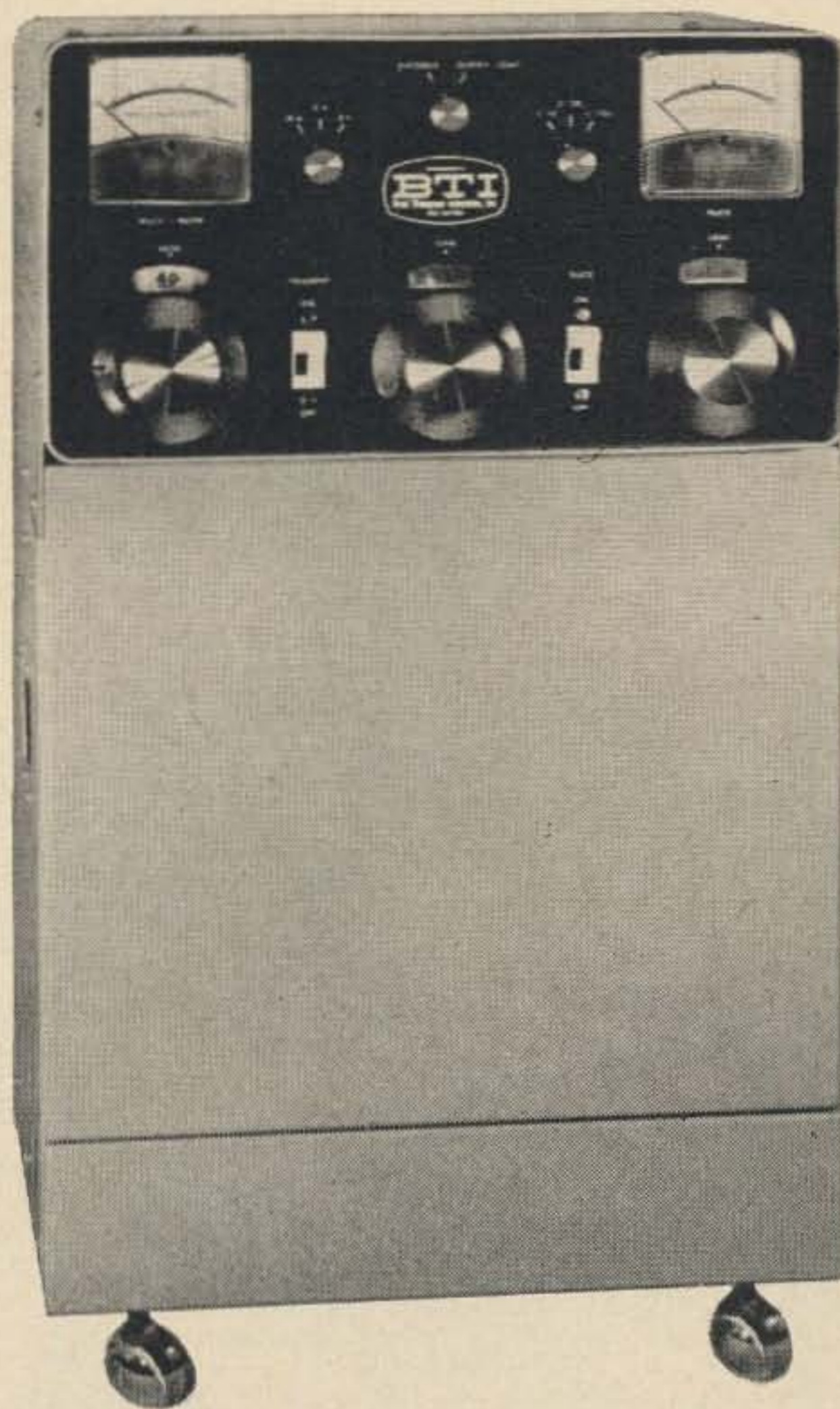


Two Transistor Testers

One of these two very simple transistor testers belongs in the shack of every up-to-date ham.


Two simple transistor testers are shown here both having the same basic circuit. The one shown in Fig. 1 is about as simple as can be made for measuring the relative dc beta of either an NPN or PNP transistor. It was built into an aluminum box 3 x 5 x 2 inches with an old 0-200 Am meter. The latter had the internal shunt removed, giving a 0-2 Am meter with a 0 to 200 scale reading. A small half ohm resistor was shunted across it to make it read somewhere between 5 and 10 milliamperes full scale since most small transistors operate within this value of collector current.

The exact reading is not important since the beta reading can be set to use the 0-200 division scale on the meter by adjusting the potentiometer in the bias circuit.

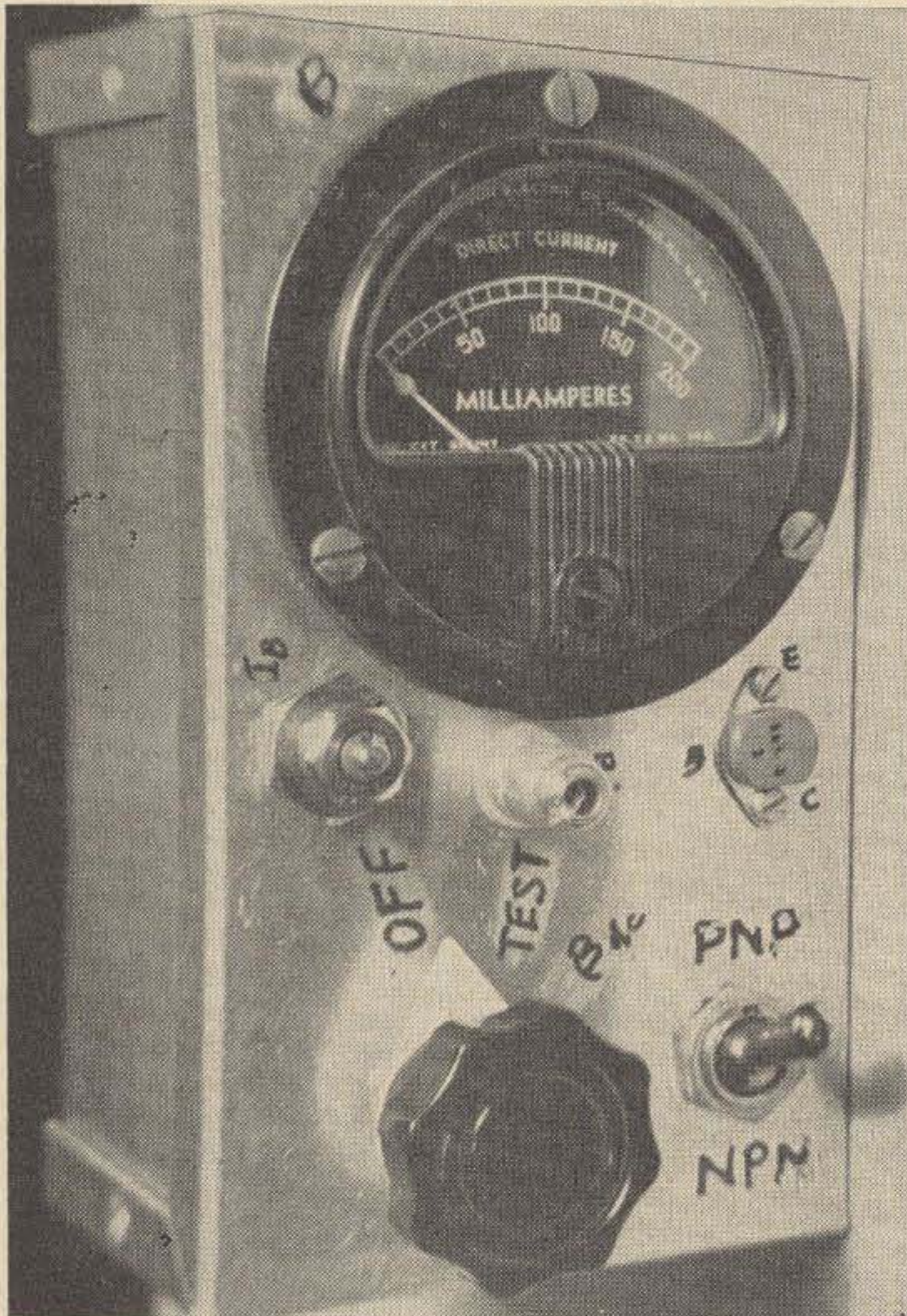
A battery and meter polarity reversing switch in Fig. 1 is a DPDT toggle switch labeled NPN and PNP. By having a "test" position on the other switch, an unknown type of transistor can be plugged in for test without damaging it or the meter. The protective resistor should be 150 ohms for a 0 to 10 Am meter, or 300 ohms for a 0 to 5 Am meter in order to keep the meter reading to within



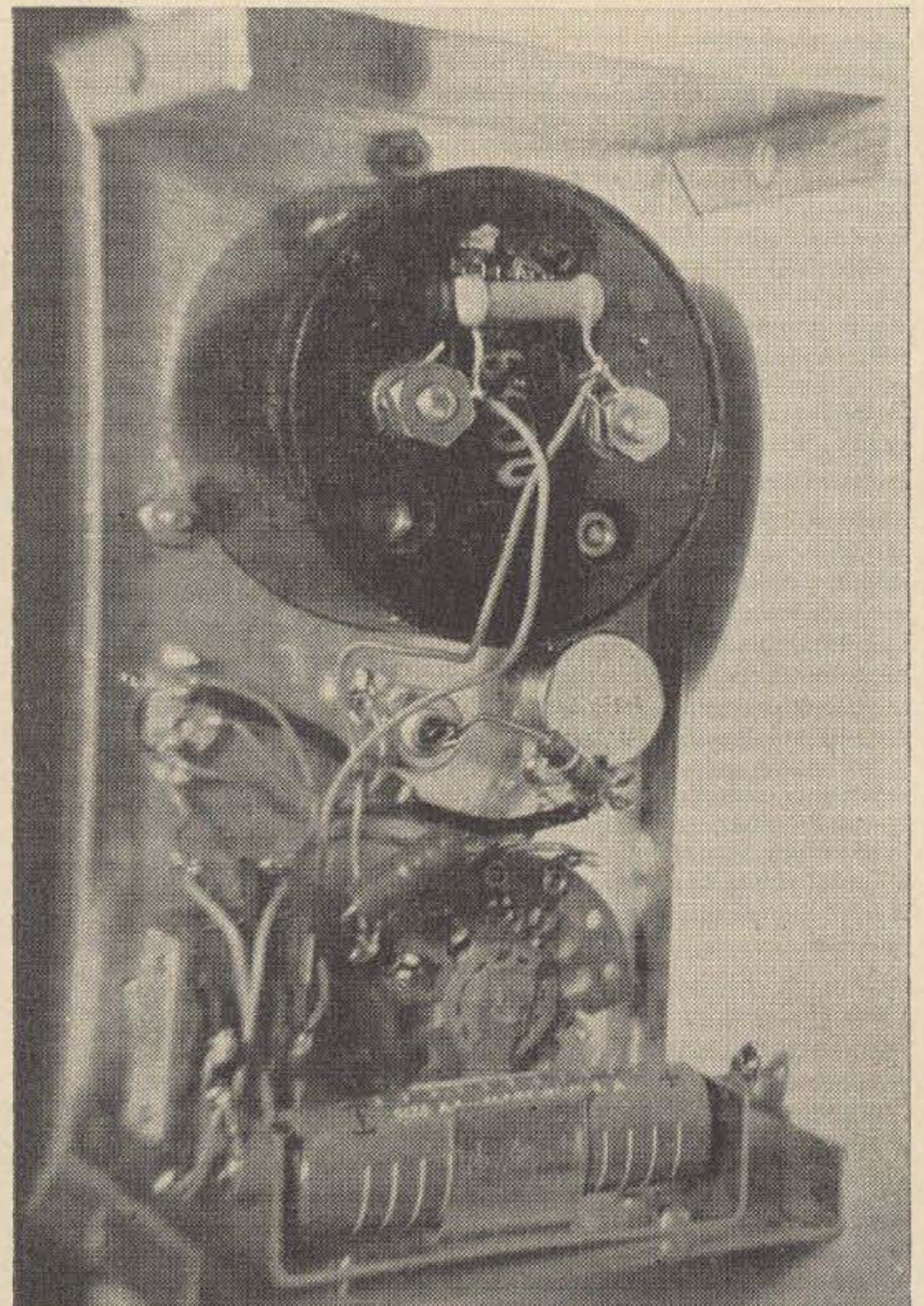Front of the simple transistor tester in Fig. 1.



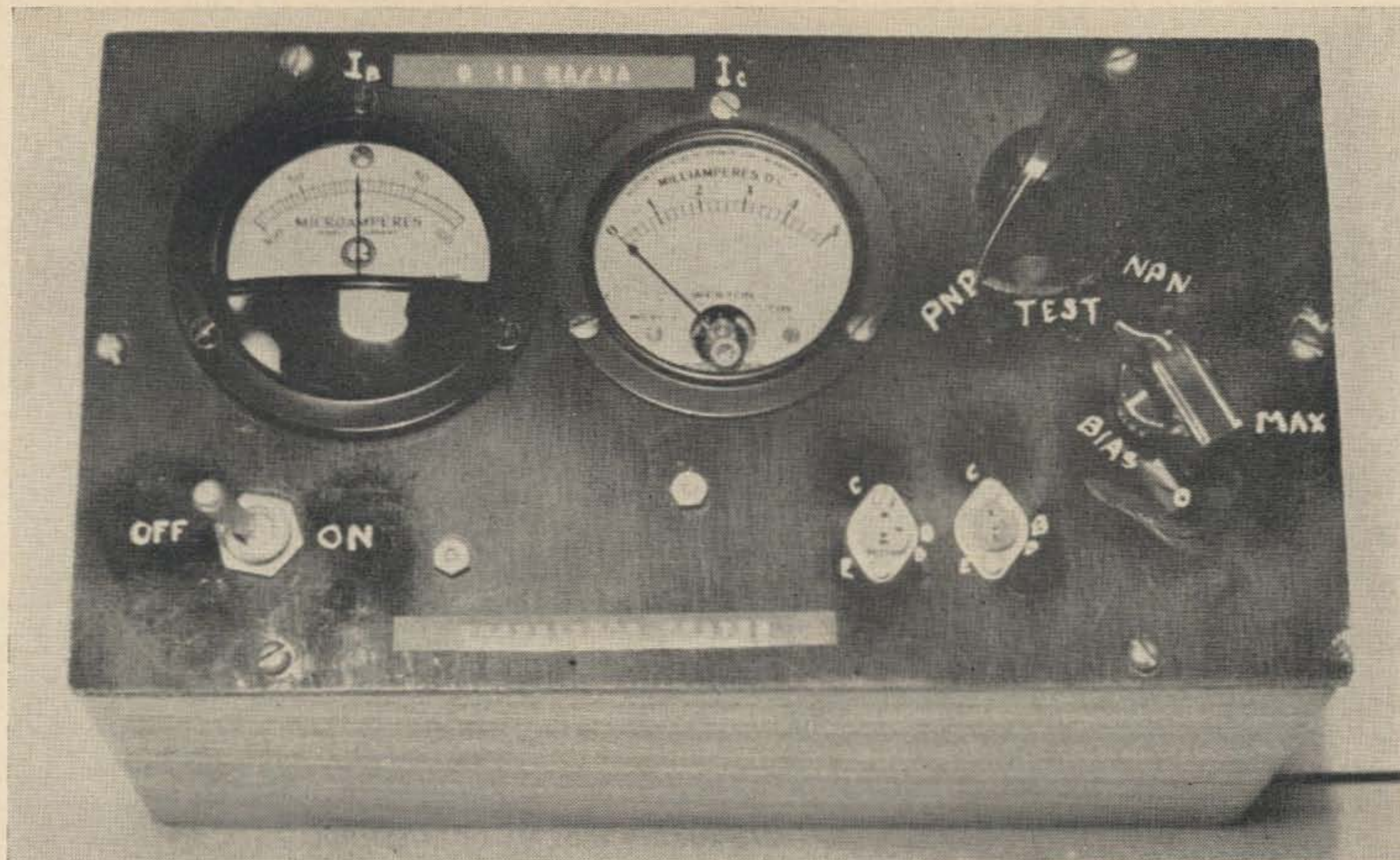Inside of the transistor tester shown in Fig. 1.



Here's the front panel of the transistor tester shown in Fig. 2. Note the use of a zero-center

range even with a short-circuited transistor. If no reading is obtained with the NPN-PNP switch in either position, it indicates a very weak transistor or one with an open lead. Once these tests have been made, the dc beta can be read on the meter in the third position of the "test" and "off" switch.

The calibrating potentiometer can be set to read correct beta for a known type of transistor which has been measured on a more accurate transistor tester. The battery voltage affects the beta reading which means it should be checked occasionally to be sure it is near the 1.5 or 1.4 volt reading. The ordinary penlite sized cell should measure 1.5 volts and a single mercury battery cell should read 1.4 volts. Either type is suitable in this tester.

A more accurate type of dc beta tester is

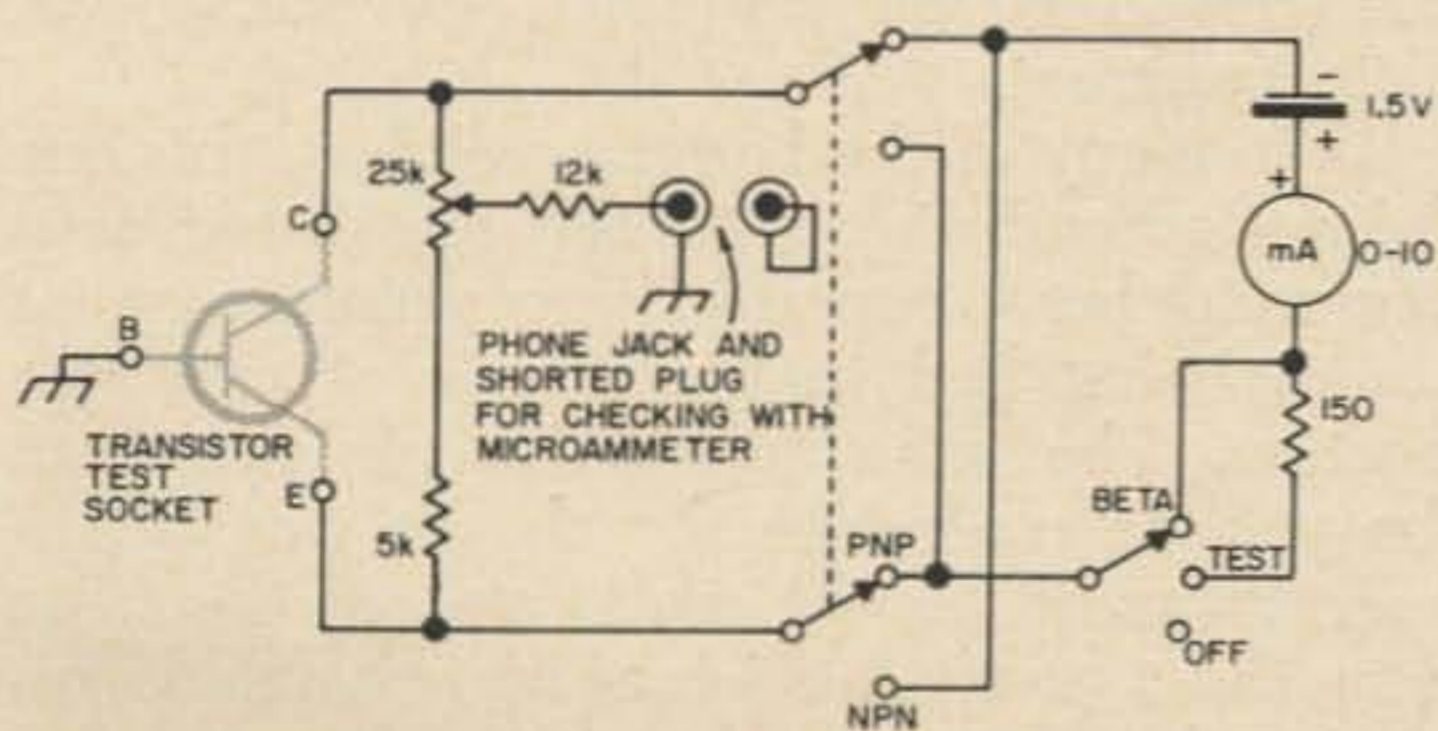


Fig. 1. The simpler of the two transistor checkers described by W6AJF in this article. The proper scale can be set by adjusting the potentiometer.

meter for measuring base current. This avoids the necessity of using a meter-reversing switch there.

shown in Fig. 2. This tester was built into a larger box with two meters, one a zero center microammeter for reading the transistor base current for either NPN or PNP transistors without need of a reversing switch. The other meter, a 0 to 5 Am unit, reads the collector current for any particular value of base bias voltage and current. The milliampere reading can be set to any desired value such as 2 Am by means of the bias potentiometer knob. The reading multiplied by 1000 gives the collector current in microamperes. This value is then divided by the base current reading to give the dc beta of the transistor being tested. If the latter reading was 20 microamperes then


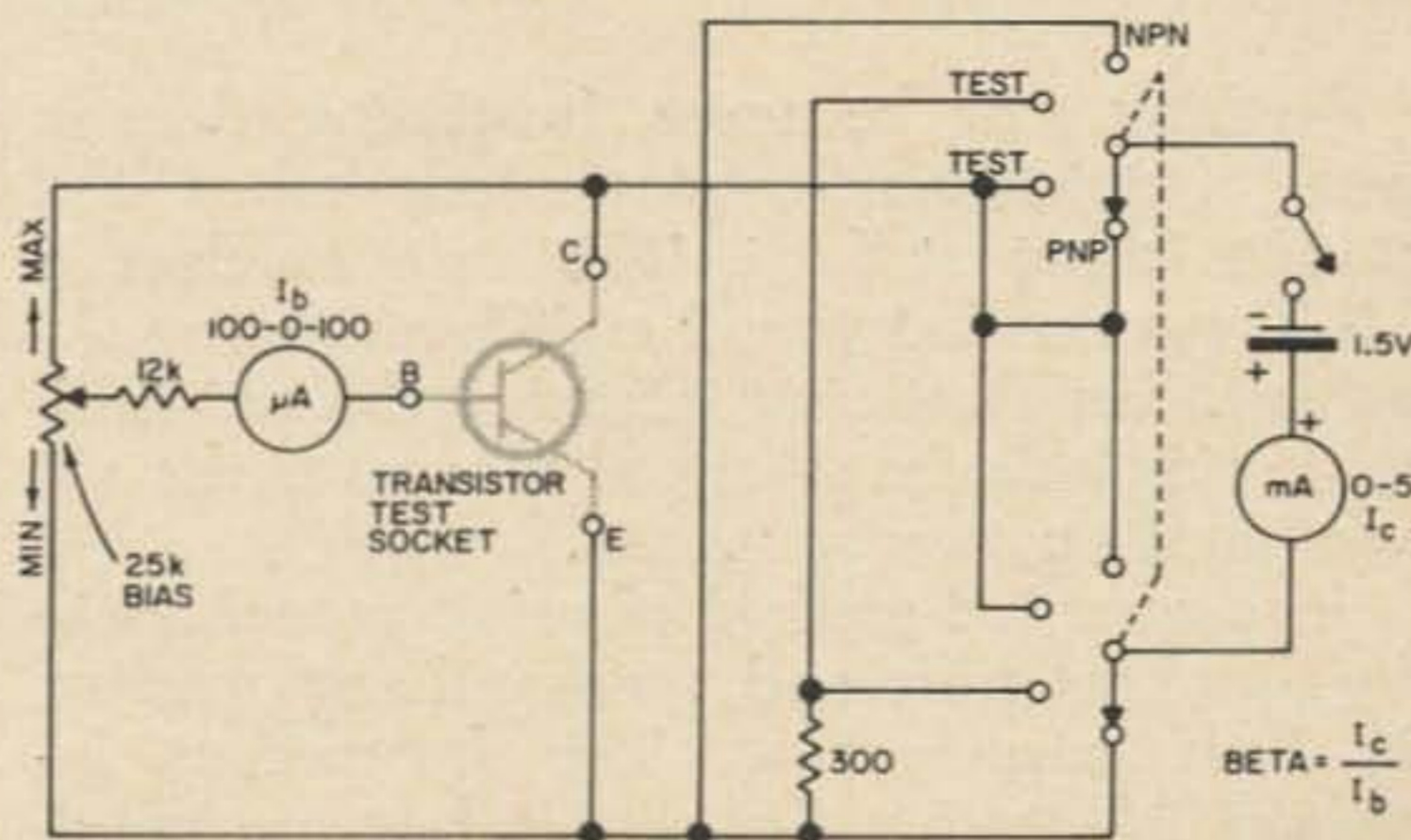


Fig. 2. The more complex of the two simple testers. You can figure the beta of the transistor under test more accurately with this tester than the one in Fig. 1 since you get a specific collector current for each value of base current you use.

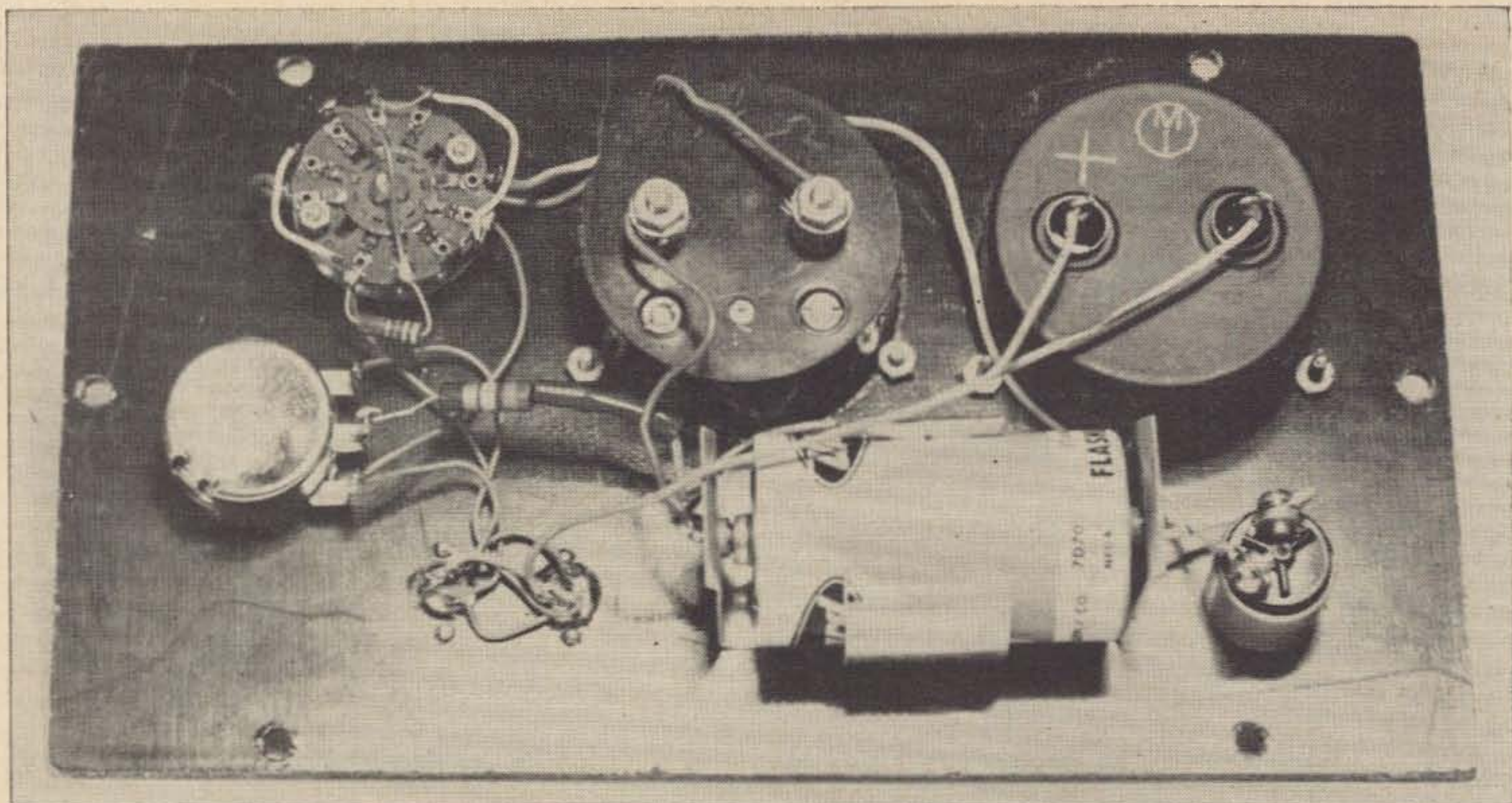

Back view of W6AJF's transistor tester as shown in Fig. 2. The circuit is very simple and construc-

tion is completely non-critical. Either a mercury cell or a regular flashlight battery (shown) can be used.

for our example the beta is $2000/20 = 100$.

The PNP-test-test-NPN switch is a DP4T wafer switch. Two test positions were used with the 300 ohm protective resistor inserted series with the meter to prevent burnout for the case of a short-circuited transistor. Another protective resistor of 12,000 ohms was connected in series with the base circuit microammeter in case of a faulty transistor. A single flashlight battery was used to power the tester.

In testing either NPN or PNP transistors the current of both meters should increase simultaneously as the bias is increased from 0 towards maximum. If such is not the case, try the other switch position PNP instead of NPN

or vice versa. If the beta reading is too much lower than transistor handbook values listed for "hfe" for a given type of transistor, it should be discarded. Higher values generally mean that you are in luck, as the transistor has a higher dc beta and hfe than the average units.

These testers do not measure anything except the relative efficiency as a dc device. It does not show up noisy transistors or give any indication of the operating frequency range. However, if it tests good on dc values, the transistor will probably work well in the frequency ranges listed in transistor handbooks.

. . . W6AJF

De-Bugging the Hi-Fi

Nothing can be more frustrating than a case of interference, particularly when the station is not at fault. This case involves a Hi-Fi system that would emit from the speaker, with ear-shattering intensity, the unintelligible single-sideband signal whenever the rig was used on twenty meters.

The accepted method of using capacitors to by-pass the grids and speaker leads resulted in little improvement. The frustrations involved in locating the elusive bug are unimportant but the specific cause is worth mentioning. After all, it could happen to you.

The final cure was the use of a capacitor from one side of the volume control to the


chassis. According to the schematic this point was already grounded. After another careful examination of the amplifier, the cause was quite apparent.

As in many of the better amplifiers, this one did not ground directly to the chassis but used a ground buss, running from point to point before being tied to the chassis at only one location. The extra foot or so of wire from the volume control to the chassis was an excellent ground for the audio and, at the same time, did a pretty fair job as an antenna. Eliminating the rf at the volume control cured this particular source of interference.

. . . Ronald Farren WAØBGQ

How To Build A FET Voltmeter

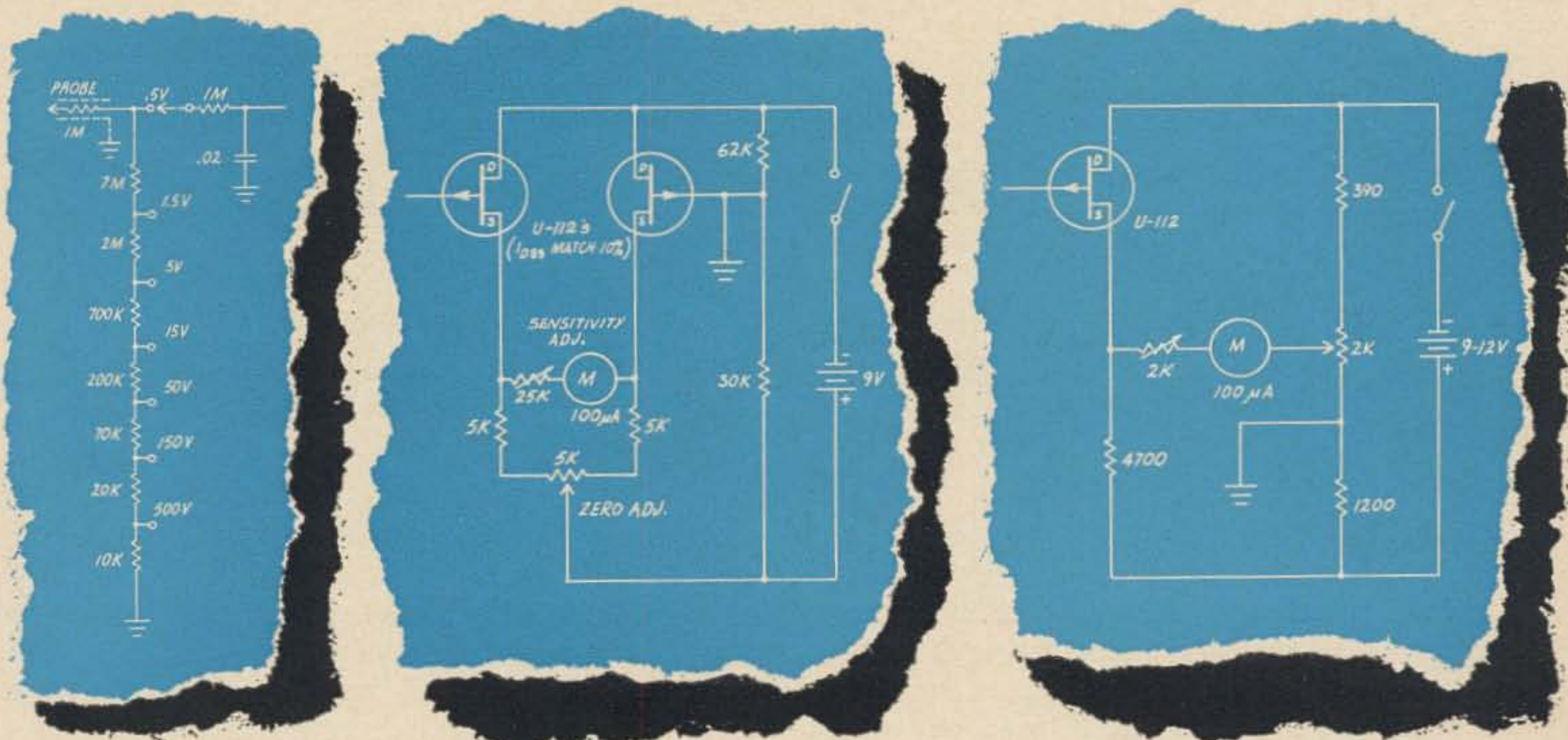Take the VT out of VTVM with the transistor that behaves like a tube.



Siliconix assumes no responsibility for circuits shown, nor does it represent or warrant that they do not infringe any patents.

The voltage divider on the left works with both; in the middle circuit, the matched FET pair means no re-zeroing with temperature changes. If you're willing to re-zero try the one on the right. Either circuit with a $100 \mu\text{a}$ meter gives a full scale sensitivity of 0.5v and better than 1% linearity. For AC add a diode peak detector and change the multiplier resistors. To modify your present VTVM for instant warmup and portability just remove the tube and all the power supply business. Change a couple of resistors, then install a FET and a battery. The battery should last a year, even with daily use.

GET STARTED FOR AS LITTLE AS \$1.00

Take any tube circuit handbook, pick the circuit you want, then design it with FETs. To make it easier, we offer four experimental FET packages, each with applications data. You can buy one FET, or one of each, or a matched pair... all at special experimenter prices. Clip the coupon and mail it today with check or money order!

Siliconix incorporated
 1140 W. Evelyn Avenue • Sunnyvale, California 94086
 Phone 245-1000 • Area Code 408 • TWX 408-737-9948

To: Bill Shipe K6RLM
 SILICONIX INCORPORATED, 1140 West Evelyn Avenue
 Sunnyvale, California 94086

Enclosed is \$1 for one U110 FET and data
 \$2 for one U112 FET and data
 \$2.75 for both FETs and data
 \$6 for one pair matched U112's
 (Calif. residents add 4c, 8c, 11c, or 24c sales tax)

Name _____ Call _____
 Address _____
 City _____ State _____ Zip _____

This is a limited offer, for experimenters only, one order to a customer (no purchase orders, please). Offer closes September 30, 1966.

The Transistor for Voltage Regulation

Here's a voltage regulator that puts out 9 to 28 volts at up to 10 amperes with excellent regulation.

In many instances the amateur is interested in using or adapting a circuit using transistors, only to find that he has no means for supplying properly regulated and filtered power. Unlike the vacuum tube, which is relatively insensitive to minor voltage excursions and ripple in dc, the semiconductor demands a stable supply source and negligible ac in the dc to give optimum performance.

A change in bias voltage of 1 volt on a vac-

Gary has been W3AEX, W8LWL, WAØEFT and K1FPM. He's an electronics research engineer with a BSEE from Ohio and an AMIEE pending.

uum tube usually has very little effect upon the tubes operation. A one volt bias change on a transistor however is usually disastrous. One volt can mean the difference between class A and class C operation, or possibly no operation at all.

Circuit theory

The circuit of Fig. 1, is a rather standard series voltage regulator in the commercial field but needs a bit of explaining here because it is rather rare in amateur usage.

The easiest way to understand how the circuit works is to imagine the series transistor Q_1


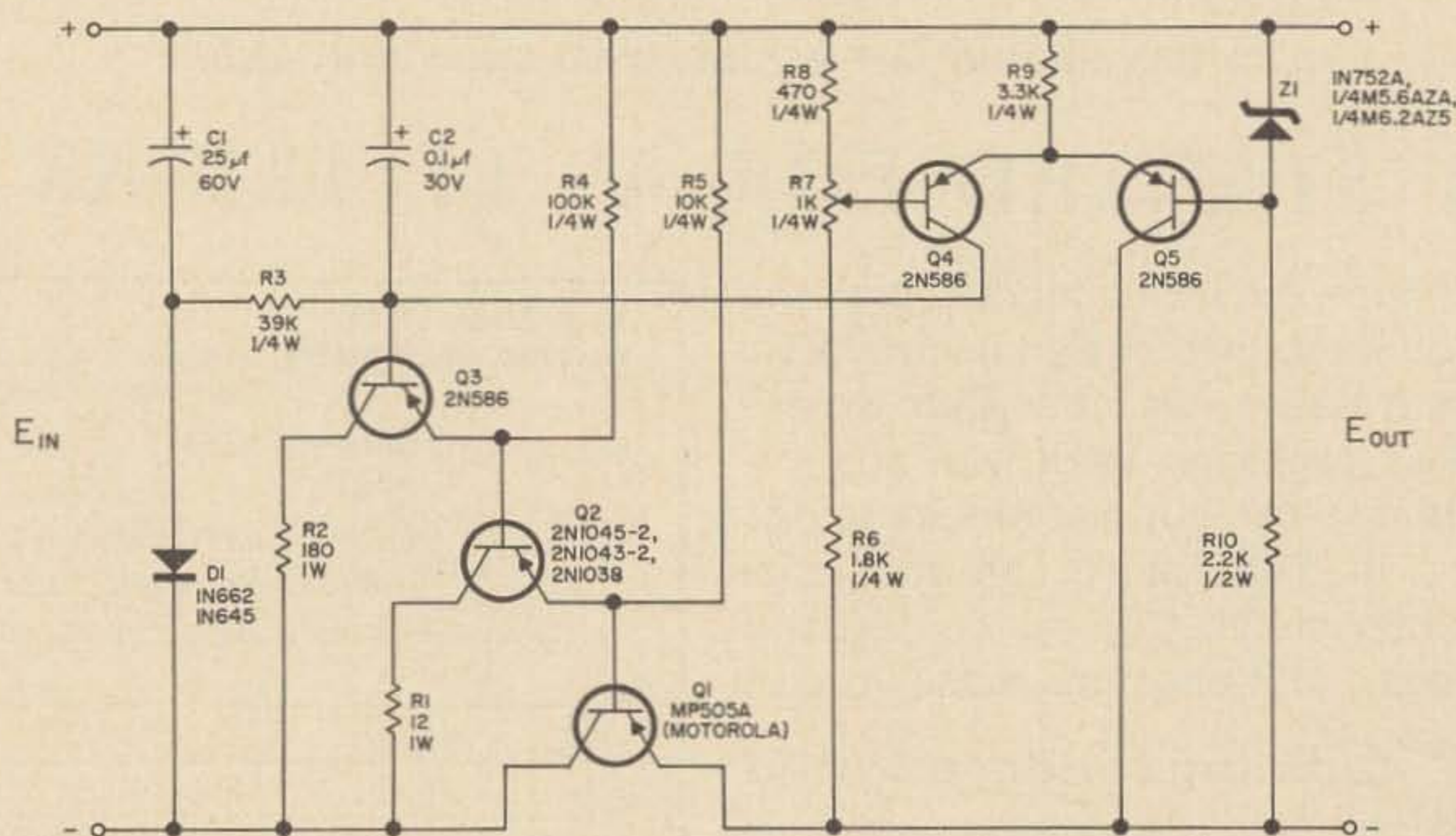


Fig. 1. Transistor regulator for 9 to 28 V output at up to 10 A. You can omit Q_1 for a maximum current of 3 A.

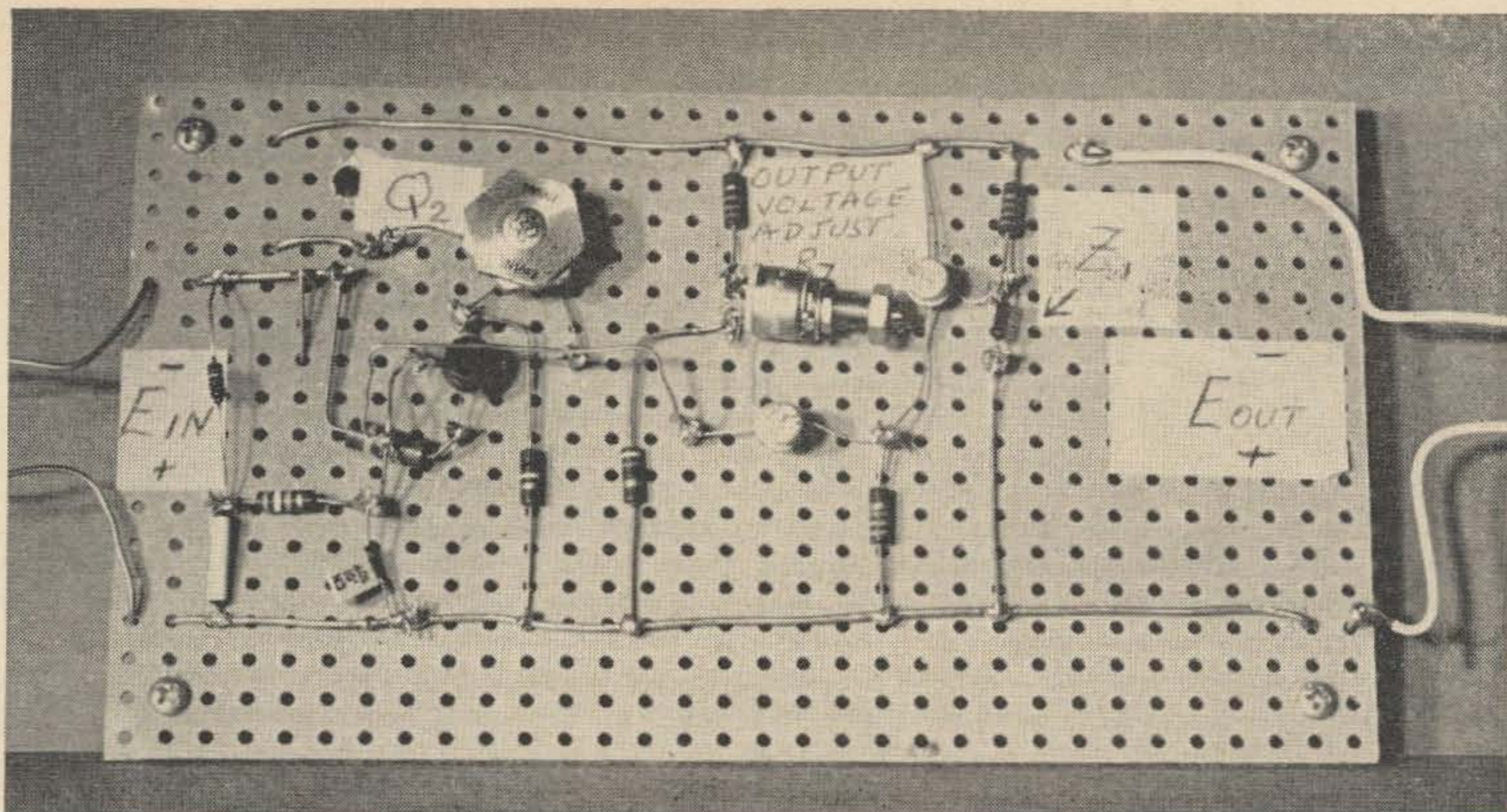

Breadboard of the regulator shown in Fig. 1.

as a variable resistor that is automatically controlled. If the input voltage E_{in} were to increase, or the current being drawn by a load at E_{out} to decrease, the resistance across Q_1 must increase to keep the voltage at the E_{out} terminals constant. Similarly, if the load current goes up then the resistance of Q_1 should decrease to keep E_{out} fixed.

Now we might want to draw quite a bit of current through Q_1 , maybe as much as 10 A. Since the current required by the base of Q_1 is approximately the current through the transistor divided by its amplification factor B (which may be any where from a value of 10 to about 30) a bit of dc amplification is in order. Q_2 and Q_3 provide this amplification in a so-called Darlington configuration. Darlington circuits are simply those that hook the base of one transistor directly to the emitter of another, providing a very simple means of increasing gain. In effect, the gain, or B , of Q_3 is multiplied by the gain of Q_2 which is multiplied again by the gain of Q_1 . Thus a very small current at the input of Q_3 can control very large currents through the series transistor.

Now all that remains is to provide some sort of feedback network which will sense the output voltage and control the series transistor. The sensing of the output voltage is done with a simple resistor string across the output, in this case the R_{6-7-8} string. Also, we need a stable voltage source as a reference, and you will note a simple zener diode does the whole trick admirably here.

With the zener providing a good stable reference we can now compare the output voltage to the reference and make the series regulating transistor "take up the slack." This is accomplished by a simple differential amplifier, of which the operating theory is adequately covered in most transistor manuals.

If you've made it this far you should have a fair idea of how the gadget works, so now to the easy part, the "makings."

Construction and operation

The circuit shown can provide any regulated output voltage from 9 through 28 volts. The value of E_{in} is best selected as 25 to 50% greater than the desired output voltage, E_{out} . The input voltage can be easily obtained by a simple bridge rectifier and single capacitive filter, as shown in Fig. 2. With Q_1 in the circuit, a 10-A load current may be drawn continuously. Omitting Q_1 and connecting Q_2 in its place allows 3 A maximum.

Both Q_1 and Q_2 should be mounted on a suitable heat sink, such as a chassis, with an area of 20 square inches or more. Use the insulating material supplied with the transistors to keep the cases electrically isolated from the chassis, as the collectors are connected internally to the case.

Use the value of capacitors specified; they provide proper time constants for regulation and for damping feedback oscillations that can occur.

The output of the regulator should not be

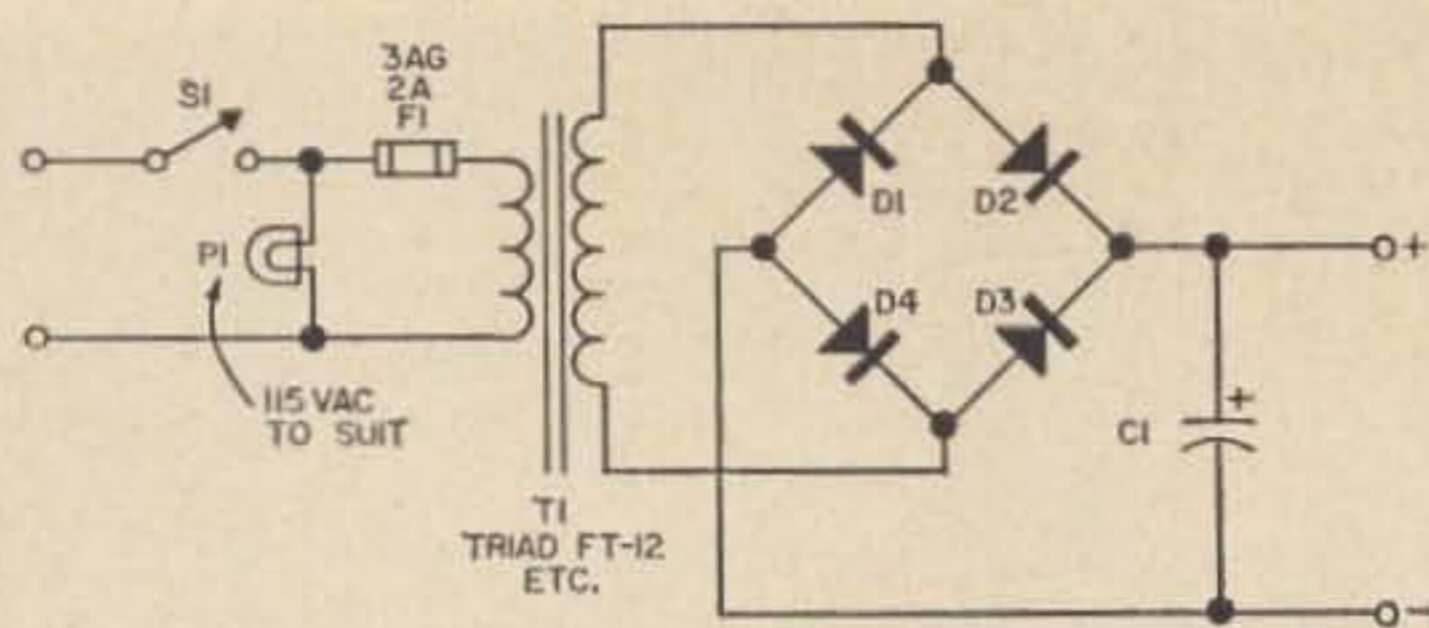


Fig. 2. Power supply for the regulator in Fig. 1. D1 through D4 can be 1N538 for values of C1 below 2000 μ F or 1N2610 for larger C1. C1 should be as large as possible and rated at 60 to 75 V.

short circuited even if a fuze is used in the transformer primary supply, because either Q_1 or Q_2 may exceed current ratings and fail before the fuze opens. A more advanced version of this circuit would include some provision for current limiting. Other than these restrictions,

the circuit can be built in any reasonable configuration and will work quite well. Output voltage can be easily set and adjusted by adjusting R_7 ; once set, it may be forgotten or varied at will.

Use of the circuit

Similar regulators have been built and used with excellent results. Specifications and requirements for professional uses far exceed those needed by amateurs, yet the cost of this circuit is now reduced to its most economical form without sacrifice of good characteristics.

Amateurs should find this circuit quite useful, because either side of the output may be grounded, and regulation and ripple reduction are such that a home laboratory or equipment supply is as feasible as the more common vacuum tube B+ supply. . . . WB6MOC

Improved Gamma Match

Prior to constructing my homebrew tri-band quad I had concluded from on-the-air discussions that a gamma match was a mighty good investment but was somewhat complicated due to problems in waterproofing the large air-gap gamma capacitors.

After giving the matter considerable thought, the following relatively simple approach was developed and has been used very successfully at this QTH.

Bill Orr's Quad Handbook gives dimensions for gamma rod spacing and length; however, in lieu of air-gap variable gamma capacitors simple fixed capacitors were constructed from 1/16" thick double surfaced copper printed circuit board material.

First, a separate gamma match assembly was constructed for each band per Bill Orr's dimensions as shown in Fig. 1 except that a small variable capacitor was temporarily sub-

stituted for the printed circuit boards and the support block was added. Capacitors can be 150, 100, and 75 pF for 20, 15, and ten meters.

The transmitter (use low power 200 watt type) was then tuned for 14,300, 21,300 and 28,600 kHz and each capacitor was adjusted for minimum SWR.


The capacitors were then carefully removed without changing their settings and the capacitance of each was measured. Printed circuit board material was then cut with a hacksaw to slightly larger values (+5 pF) and edges bevelled as shown using a small wood rasp. These were then soldered into place and the SWR was again checked on each band. The boards had to be cut down slightly using a pair of dikes or tin snips to achieve minimum SWR. Plastic tape was wrapped around each board and VOILA!—we had a light weight weather-proof gamma match.


If you want to gamble and avoid the variable capacitor substitution method the following sizes will be more than enough and can be easily trimmed on the spot to give minimum SWR.

Band	PC Board	Gamma Capacitor
20 Meters	1½ x 3"	Approx. size
15 Meters	1½" x 2"	" "
10 Meters	1" x 1½"	" "

Two separate feedlines should be used, one for 10 meters and a common 15-20 meter line or three separate lines may be used.

. . . W. H. Paxton K6ZHO

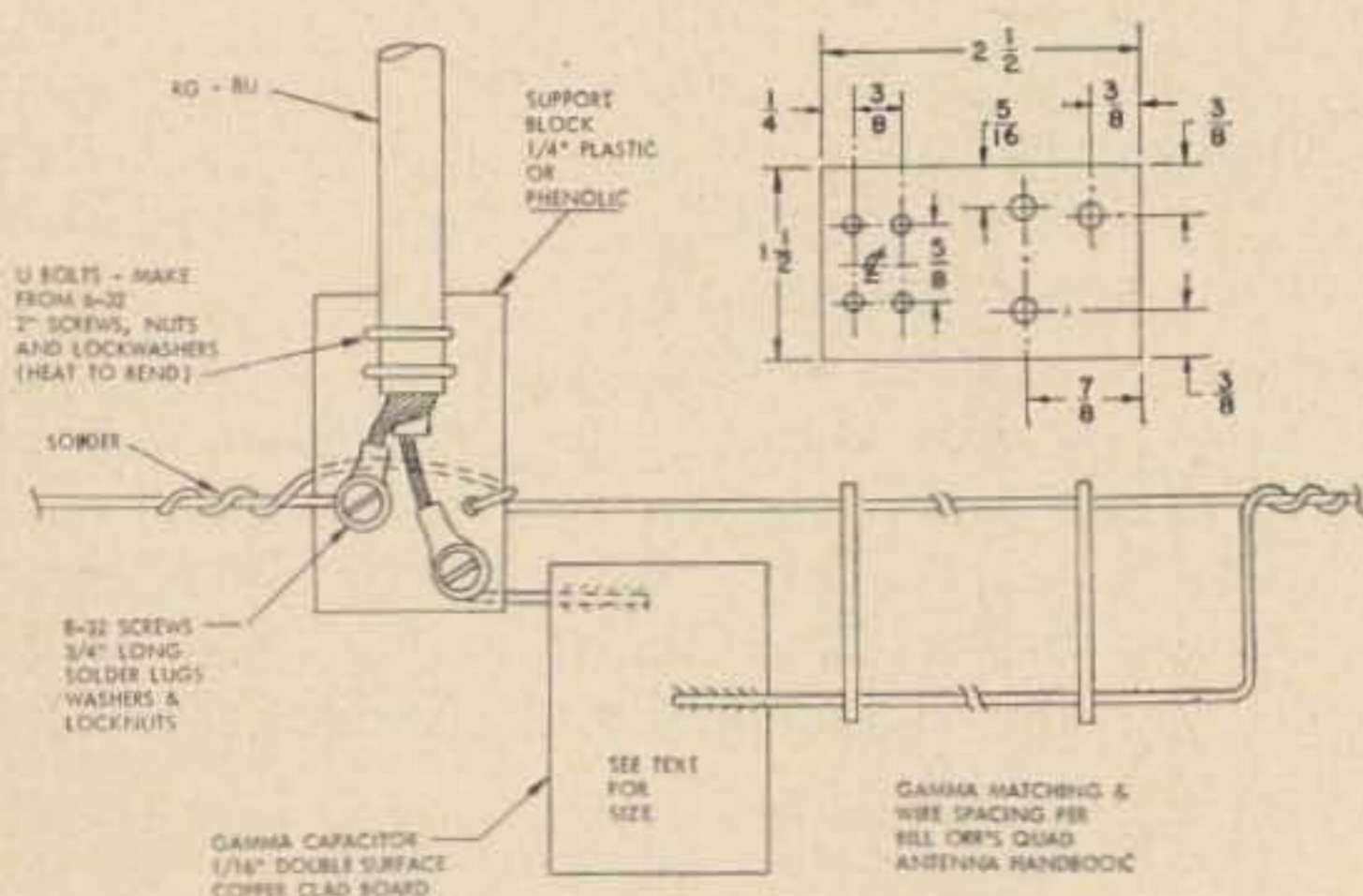

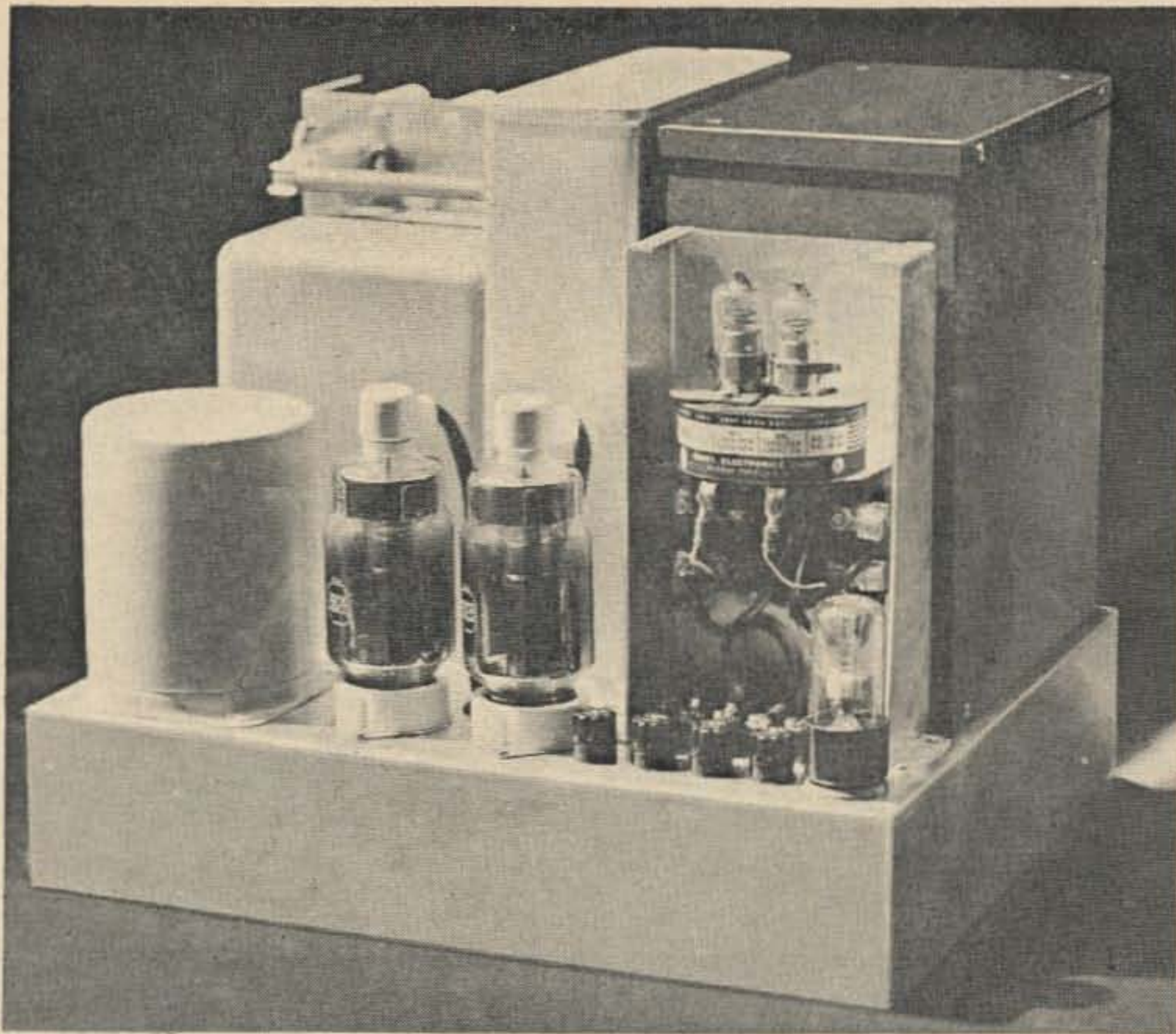

The 2-K linear means **HEAVY DUTY**

In two short years the 2-K has become synonymous with high quality, heavy duty performance in the amateur radio service.

The 2-K breezes effortlessly at the legal limit in any mode . . . SSB, CW, AM, or FSK. It is 175 compact pounds of pure communication.

The power supply symbolizes the 2-K's all around ruggedness. Notice the high reliability mercury power relay, the brute of a power transformer, the magnificent 20 mfd oil-filter condenser, the 800 milliamperere cased filter choke. No other amateur service linear comes within a country mile of using such high cost, high quality components. Is this power supply the reason the big, clean signals you hear on the air are 2-K signals? It's one! We invite you to discover the others yourself. Write today for complete information. **The 2-K console or desk model \$675.00 RF unit only \$425.00**

6% FINANCE CHARGE • 10% DOWN OR TRADE-IN DOWN • NO FINANCE CHARGE IF PAID IN 90 DAYS • GOOD RECONDITIONED APPARATUS • Nearly all makes & models. 15 day trial. 90 day Warranty. 90 day trade back on NEW apparatus. Write for bulletin.

TED HENRY (W6UOU)

BOB HENRY (WØARA)

WALT HENRY (W6NRV)

Henry Radio Stores

CALL DIRECT . . . USE AREA CODE

Butler 1, Missouri, 64730

816 679-3127

11240 W. Olympic, Los Angeles, Calif., 90064

213 477-6701

931 N. Euclid, Anaheim, Calif., 92801

714 772-9200

6116 N. 27th Ave., Phoenix, Ariz., 85017

602 AM 4-3895

"Worlds Largest Distributors of Short Wave Receivers"



Bill Hayward WØPEM
3408 Monterey
St. Joseph, Mo. 64507

I recently found myself in Miamisburg, Ohio, home of all that good Drake gear, so thought I'd drop in for a visit. I found their building, was warmly received and shown around by Peter Drake.

A Visit to the R. L. Drake Company

Here is part of the Drake production line. Drake only makes ham gear and TVI filters.



Here's more of the production line. The engineering department and metal work are in another building.

Here are some of the new products shown at the Dayton Hamfest: The 2-NT CW transmitter and the 2-C Ham band receiver. Another product they make is the SW-4 short wave broadcast receiver. Watch for details in 73.



The new Drake L-4 linear offers 2000 watts PEP—1000 watts DC. Tubes are two Amperex 8163's. Price with separate power supply and tubes is under \$700.



Here next to the Drake factory is the new addition they've been working on. Business is good. Also notice Bob Drake's Triumph. I enjoyed my visit with Drake. I'm sure you would, too.

Try Homebrewing Now

When I sit around a swimming pool, I'll notice three groups of people: there is one group that stays around the pool, soaking up sun but never getting their feet wet; another group that dives in, discovers that the water is cold and runs out again; and a final group that edges into the water slowly. These people usually have the most fun and stay in the longest time.

Ham radio homebrewing has the same groups. Some never bother to homebrew; they sit home, their pudgy fingers glued to a knob, praying that a tube doesn't go. On the other hand, some guys buy up their local electronics store and try to build an imitation NCX-5 before they have learned how to solder. Finally there is a group that thinks about building, works on it carefully, stays in the longest and has the most fun. This is the group to join.

How, you say. How can I "edge in" to homebrew? Tools cost, and besides the thing will probably do nothing more than exude black noxious fumes when I plug it in. But this doesn't have to be so. It is easy to get started in homebrew without money, parts, or even tools.

No tools? Most—if not all—towns have a ham with a set of chassis punches and drills. Being a homebrew fan, he'll be glad to help out and get another convert. Seek this man out and swipe a weekend of his time. Hams are notorious for their brotherhood; use it.

No parts? Old TV's, radios, tuners, anything electronic will furnish parts. The best thing to salvage is a good power supply. Again, most hams in any reasonable sized town have an overstuffed junk box. Grub a few parts from them and you won't have to spend more than five dollars a project. If you load yourself with catalogs and flyers (Say you saw it in 73) you'll be able to save money to the point where you'll feel sorry for the manufacturer. Parts? No problem.

No money? A five dollar bill will take care of preselectors, Q-multipliers, a VOX, full CW break-in, a code monitor or two, a noise limiter, a product detector, a crystal BFO . . .

I could go on forever. And how do I know? Either I or a friend has built one of the above items for a five dollar bill. Don't say it can't be done.

By now, hopefully, you see that all the myths about the great expense, great labor, high rate of failure, etc., are a lot of pap. Armed with this knowledge, you desperately go searching through your old back issues of 73 in order to find that six-meter converter you never had guts enough to build. But let us suppose that you are a hard-core cynic who still believes that homebrewing is for the birds. Here are a few reasons why homebrew pays.

First of all, satisfaction. Big deal, you say. Well, if you don't care about the personal satisfaction involved, read on. But it means a lot to a lot of guys.

Second of all, you can own equipment that no manufacturer could supply. Who is going to produce a product detector that you can put in your old decrepit receiver? That, believe me, is a limited market. Where are you going to get hundreds of accessories? The only way you can get them is by homebrew. That, I think, is one of the best reasons.

You learn a lot. Big deal again, you say. You say you don't need to learn; you simply push a button and you're on the air. Yeah? What happens when your receiver kicks out? Try sending your 105 lb transceiver back for servicing. And have fun packing it.

You save money. How much money? To get off ham matters, I know a guitar-playing friend who paid forty dollars for a fuzz-tone. A ham friend copied the schematic and built one for ten dollars. In most cases of homebrew there's nothing to compare it to since there are no equivalent units available. But look up the price of a VOX and see how much it would take you to build it, using the techniques of sophisticated grubbing mentioned before.

If you haven't tried homebrew, start edging into the swim of things. In a while, it'll get mighty hot for the boys sitting around the pool doing nothing. Get a head start on them.

. . . WB2JQC

DO YOU WANT TO BE ONE OF THE TOP STATIONS ON THE FREQUENCY,

getting a quick response to all your calls?


IF YOU DO, WHY NOT TREAT YOURSELF TO SOMETHING NEW AND NEAT

THE ELECTRONIC BOOSTER — BAND FILTER MODEL B-1000A

Use with your present transceiver or transmitter-receiver combination, SSB and AM, fixed or mobile, all makes and models!



Front Panel View
B-1000A

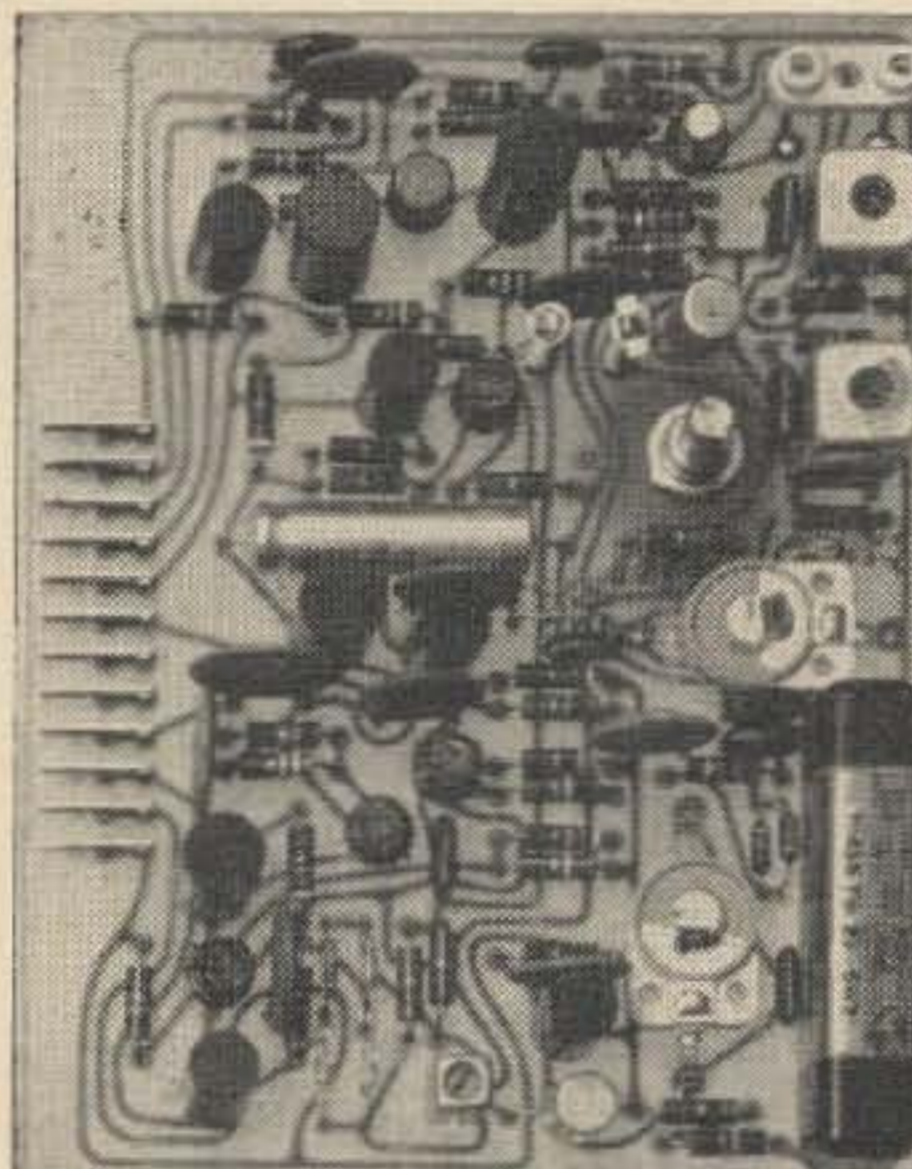

One Of The Computer
Type Circuit Boards
Used In The B-1000A

WHAT DOES THE B-1000A DO FOR YOU?

ON TRANSMIT—Adds a fabulous increase in average talk-power to your transmitted SSB signal—equally outstanding on AM! Makes a 200 watt signal sound like 1-kw! Makes a 2-kw p.e.p. signal sound like 10-kw!

THOSE ELUSIVE DX STATIONS REALLY HEAR YOU!

ON RECEIVE—adds 1-kc, 2-kc, & 3-kc continuously adjustable Collins Mechanical Filter type selectivity (2:1 Shape Factor) to your present fixed selectivity receiver or transceiver!

THOSE ELUSIVE DX STATIONS CAN REALLY BE HEARD!

WHAT ELSE DOES THE B-1000A DO IN YOUR STATION?

ATTENUATES or rejects received high-pitched "monkey-chatter" or low-pitched "gurgles" and other spurious signal components from adjacent channel stations.

SPEECH PENETRATION CONTROL allows your transmitter to "punch a hole" in the band so you can be heard thru the QRM and noise!

CONCENTRATES your transmitter's talk-power into a narrower channel to provide increased spectrum utilization, leaving more space for neighboring stations—**MINIMIZES QRM!**

RECOMMENDATION for good operating procedure: Always use minimum bandwidth consistent with good engineering practice and compatible with the mode of transmission being employed. **THEREFORE**, the

B-1000A contains a steep-skirted (2:1 Shape Factor) adjustable **TRANSMISSION BANDWIDTH CONTROL** to give the sharpest signal possible!

YOU MAY SELECT ANY DISTINCTIVE TYPE OF SSB OR AM SPEECH QUALITY YOU DESIRE!

AUTOMATIC transfer of circuits from transmitter to receiver allows you to fully utilize the merits of this outstanding communications development at all times when you are operating—not just on transmit or receive—**BUT BOTH WAYS!**

ATTACHED to your present set with only three simple **EXTERNAL** connections—all cables and plugs are furnished with the B-1000A!

MAY BE USED optionally as a basic SSB generator! **TAPE JACK**—permits using any popular tape recorder, if desired, to simply and directly record both sides of a QSO or phone patch!

INCLUDES a self-contained power supply for both 117 v., 60 cycle fixed station and 12 v. d-c mobile installations!

ALL SOLID STATE circuitry for top reliability!

PRICE

MODEL B-1000A \$435 Complete
THE PRICE is considerably less than a linear amplifier—and look at what the B-1000A does for your station performance. If you already use a linear on your set, and add the B-1000A—**WOW!!!**

GET ON OUR LIST for early delivery—Place your order now—Please send check or money order.

DO YOU WANT more information? **A NEW TECHNICAL DATA PACKAGE IS AVAILABLE AT \$2.00 A SET.** Contains complete B-1000A circuit diagrams, a circuit discussion, installation and operation, parts lists, glossy print photos, etc.

L. E. BABCOCK & COMPANY

28 Durant Avenue
Maynard, Mass. 01754

Diodes for Oldtimers and Beginners

A few simple games help explain electron current in a vacuum, wire or semiconductor.

One evening a venerable oldtimer presented me with a problem. He said, "If a diode conducts with the anode end plus, why does the cathode end carry the plus sign?" I said, "That's the end that goes plus." He replied, "It has to be minus." Round and round we went, and it turned out to be quite a problem. I finally had to write this article to clear it up!

What's confusing about such a thing? From a practical viewpoint, diodes are too simple to raise serious questions. But the problem is not diodes, it is words. We say a current flows this way, or that. But which way does it *really* flow?

About 1747 Ben Franklin believed electricity flowed from plus to minus. It was the best opinion available in his day. In 1891 the researchers just starting atomic physics had found some puzzling things, for which the Irish physicist Johnstone Stoney (three cheers, etc!) suggested the term 'electrons'. Finally, in 1895, J. J. Thompson showed that electrons really exist. This should have settled the matter permanently.

But the plus-to-minus convention is still with us. And in some semiconductors it is correct! We call it hole current. I'll tell you something if it won't see print: I'm still confused sometimes.

The best way to avoid this confusion is to get past the terms, right down to a clear picture of what actually happens inside conductors and diodes. Three games, described later, will help to make this picture clearer. You'll get the most from them if you read from the bibliography about some of the things I left out to make the games simple.

Diode current

What the old-timers called just plain current, back around World War II and earlier, I'll call electron current. This absolutely eliminates the question of which way it goes, because we can tell any time by thinking about vacuum tubes. But how many electrons are

actually moving when an electron current is flowing? If you use an ammeter, the magic number is 6.3 billion billion electrons per second per ampere!

The vacuum tube not only tells us which way electron current flows, it supplies the simplest picture. The cathode serves as a source of electrons. The anode takes them out of the picture again and not very much happens in between. This is the first illustrative game, the Diode Game.

Fig. 1 shows what labels are required. This is marked out on a piece of paper which is then attached to a board or book and tilted as indicated. Marbles or pennies will do for electrons. Drop them at the cathode end and watch them exit at the anode end. You may feel stupid, but do it anyway. The important thing is to get into your bones the idea that something like this *really happens* when a current is flowing in a vacuum diode.

Wire current

All electron currents flow in a vacuum! From the electron's viewpoint, the interior of a wire is mostly open space. The atoms are well separated, and serve partly as a source of electrons for conduction. Is that a little hard to believe? It took thousands of years to discover this fact, and even now practically nobody appreciates its truth or value.

Because the wire's interior isn't quite all open space, wire conduction differs from vacuum conduction in two ways. In the first place, the electrons travel within the wire in relatively straight lines. Sooner or later each will collide with an atom. That's the end of its trip, which is taken up by another electron. And each time an electron comes to a sudden stop, the atom is slightly warmed.

That's why wires get hot if they carry enough current. This knocking about, recurring billions upon billions of times per second, heats the wire. The result is very useful in vacuum tubes, not so desirable in transistors.

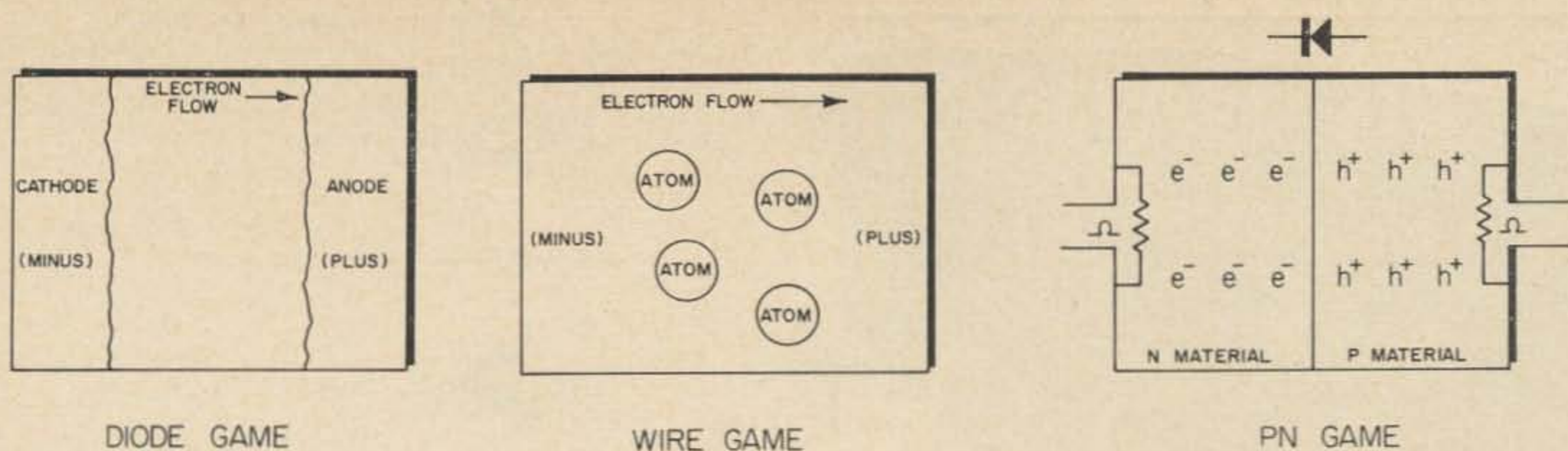


Fig. 1. W2DXH's three games illustrates what really happens in vacuum tubes, wires and PN

junctions as electrons flow from one end to another. The games are explained a bit more fully in the text.

There may be some question of how many electrons belong in the piece of wire. Of the various answers, the simplest is: as many must leave as enter. This preserves the electrical balance of the wire, which in a more elaborate explanation is not necessary. Leave this problem 'til later!

You might try working out a game to illustrate wire current. But if you want to copy mine, refer to the Wire Game chart in Fig. 1. It resembles the Diode Game chart, but cathode and anode are omitted and some atoms have been added.

The atoms are physical obstacles pasted to the paper. Bottle caps will do admirably. One end is labeled minus, the other plus, the sheet it tilted with the plus end down, and you can start sliding electrons down between the atoms.

Remind yourself that if an electron strikes an atom, it sticks and another continues the journey. The atom gets warmer. And as you watch things go, think about those big numbers, amounting to millions of millions of electrons moving for each microamp of current!

PN junction current

Solid state conduction resembles wire conduction. But there are two kinds of solid state conduction. Both require that the material be crystalline, and that it be doped with carefully regulated amounts of impurities. The type of conduction depends on the impurities chosen.

The first type of solid state conductor, N type material, depends on the presence of impurities with extra electrons. If there is no such impurity, the electrons in the crystal will be all tied up holding it together, none available to move as a current. Conduction in N type material closely resembles wire conduction.

P type material is doped with an impurity having too few electrons. As a result, many

sites within the crystal should, but do not, contain electrons. But they can get electrons from other regions in the crystal. If a hole captures an electron, the hole and electron seem to trade places.

The sequence of events is best explained by going on to the PN game in Fig. 1. From left to right across the drawing, we have a piece of wire entering the diode, an ohmic, or bidirectional contact between the wire and N material, a PN junction between the two types of semiconductor, another ohmic contact between P material and wire, and finally a wire leaving the diode.

If we push an electron into the LH wire, electrons will be displaced along the wire and shortly one will cross the ohmic junction into the N type material. But since the N conductor is already balanced, another electron is pushed over the PN junction into the P type material, where it promptly falls into a hole. The P material, unbalanced, kicks an electron across the ohmic junction into the RH piece of wire. And our electron, many times removed, continues its journey. This is a forward conduction process.

Suppose, now, that we push the electron into the RH wire. With a little urging (reverse bias) it crosses the ohmic junction and falls into a hole, leaving the entire region charged slightly negative. No electrons from the N region are interested in stepping into this; in fact they will retreat a little way from the PN junction. A similar event occurs if an electron is removed from the N region. This is the fundamental process of reverse biasing.

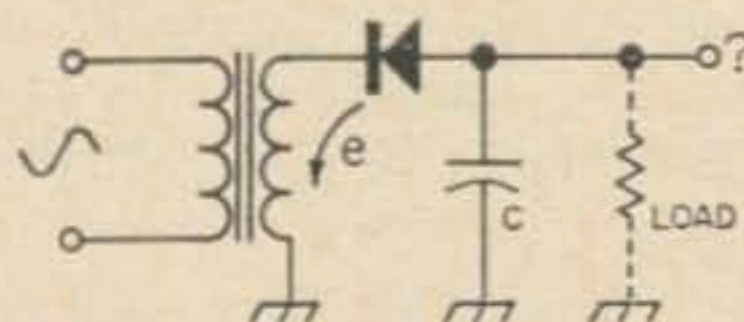


Fig. 2. W2DXH's transformer and diode problem.



VANGUARD
MODEL 501

\$259⁹⁵ SHIPPING
COLLECT
COMPLETE WITH LENS

SUB-MINIATURE SOLID STATE TV CAMERA

FOR CLOSED CIRCUIT OR AMATEUR TV

- Measures only 2 $\frac{3}{4}$ " x 4" x 7" (excluding lens and connectors).
- Weighs only 3 $\frac{1}{2}$ lbs.
- Advanced circuitry utilizing 35 semi-conductors most of which are *silicon*.
- Resolution guaranteed to exceed best capabilities of standard 525 line TV receivers.
- Field-effect input circuit provides noise-free video. This is a VANGUARD exclusive.
- RF output 30,000 microvolts adjustable for channels 2-6.
- Video output 1.5 V p-p composite with standard negative sync.
- Viewable pictures obtainable from as low as 1 ft. candle of illumination to bright sunlight.
- Vidicon controlled automatic light compensation eliminates electric eye and provides error-free compensation for light level changes of up to 120 to 1.
- New VANGUARD "HI-FI" vidicon enables use of any 8 mm movie lens instead of 16 mm lens required by other TV cameras.
- Electronically regulated power supply and thermally compensated circuits eliminate change in picture quality when line voltage and temperature fluctuate.
- All parts guaranteed for 1 year (except for open filament on vidicon or breakage). Made in USA.

Building your own TV camera? Send 10¢ for our new catalog describing our complete line of sub-assemblies and parts incorporating the latest advances in technology.

VANGUARD LABS
196-23 Jamaica Ave. Hollis, N.Y. 11423

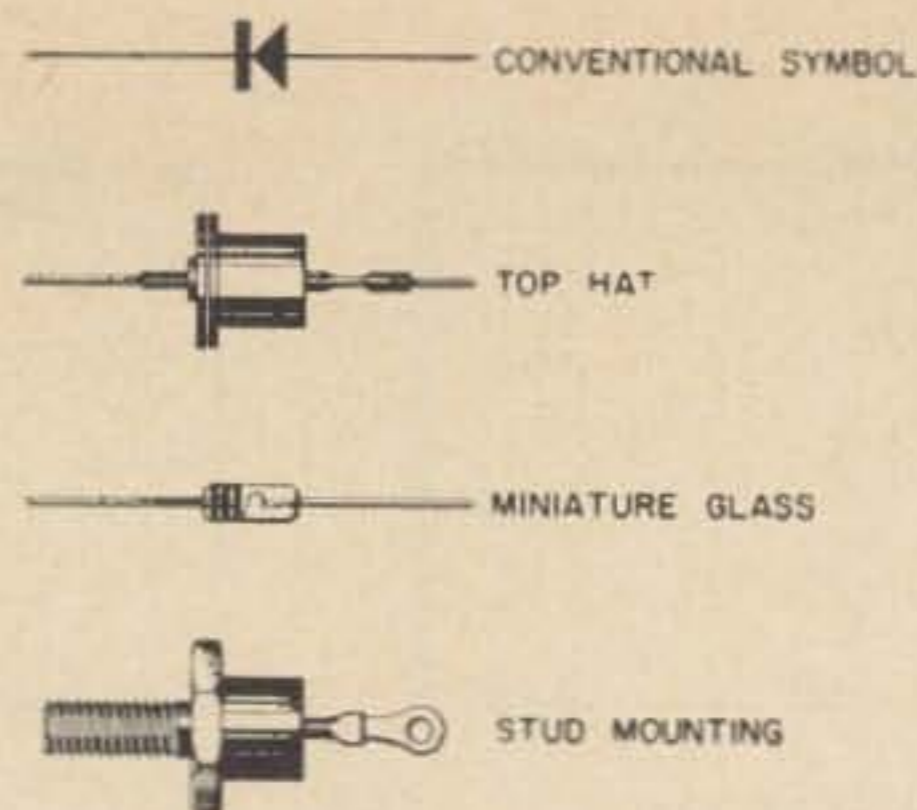


Fig. 3. Some kinds of diodes that we often use.

Diode circuits

When these games have been played out, the diode problem should be clearing up. Just to make sure let's look at a simple diode and transformer circuit (Fig. 2) and watch its operation through a single cycle.

The diode is drawn in the same orientation as shown in the PN game diagram. We immediately know that electrons will flow from left to right but not from right to left. If we look at the transformer as a device which tries to sweep electrons through its secondary first one way and then the other, everything works out promptly. The slightly curved arrow indicates which way the transformer tries to sweep electrons in the first half-cycle, and a letter "e" is placed by it as a reminder. We see right away that no electrons flow during the first half-cycle. They flow against the arrow of the diode, so during the second half-cycle, electrons swept the other way pass through the PN junction and collect in the capacitor. After one or a few half-cycles of conduction the capacitor has developed enough charge so that no further current flows, except that through the optional load resistor. Try to work this out for yourself.

We get exactly the same final result if the current is assumed to flow from plus to minus. But then the diode seems to conduct in the direction its arrow points, and it appears that positive charges have been removed from the capacitor, rather than negative charges collected there. Have you ever read Orwell's "1984"? Well, here's a good example of something like this "double-think." When you've caught the trick, try it out on the best man you know. You just might surprise him!

... W2DXH

Bibliography

- G E Transistor Manual, 7th ed. pages 4-25.
- Radio Handbook, 16th ed. p. 90.
- Radio Amateur's Handbook, 1965. p. 79.
- Cutler: Semiconductor Circuit Analysis, McGraw-Hill, 1964. Ch. 1 & 2.

SOLID STATE FREQUENCY CONVERTERS

WORLD'S LARGEST SELECTION OF STOCK FREQUENCIES

Available in the following frequencies from stock:

	Model	Input mc	Output mc
2M	301-D	144-148	50-54
	301-E1	144-145	.6-1.6
	301-E2	145-146	.6-1.6
	301-F	144-146	28-30
	301-Q	144-148	14-18
	301-R	144-148	7-11
	301-S	143.5-148.5	30-35
6M	301-B1	50-51	.6-1.6
	301-B2	51-52	.6-1.6
	301-C1	50-54	7-11
	301-C2	50-54	14-18
	301-J	50-52	28-30
20M	301-G	13.6-14.6	.6-1.6
CB	301-A1	26.5-27.5	.6-1.6
	301-A2	26.8-27.3	3.5-4.0
40M	301-K	7-8	.6-1.6
CHU	301-L	3.35	1.0
WWV	301-H	5.0	1.0
Int'l. Marine	301-I1	9-10	.6-1.6
	301-I2	15-16	.6-1.6
	301-M	2-3	.6-1.6
Aircraft	301-N1	118-119	.6-1.6
	301-N2	119-120	.6-1.6
	301-N3	120-121	.6-1.6
	301-N4	121-122	.6-1.6
	301-N5	122-123	.6-1.6
	301-N6	123-124	.6-1.6
Fire, Police etc.	301-P1	154-155	.6-1.6
	301-P2	155-156	.6-1.6
	301-P3	154-158	7-11
	301-P4	154-158	104-108
VHF Marine	301-P5	156.3-157.3	.6-1.6
Weather	301-W1	162.55	1.0
	301-W2	162.55	10.7
	301-W3	162.55	107.0
CUSTOM MADE	301-X	Your choice of any one input and output frequency between .6 and 163 mc.	

(6-8 weeks delivery on custom converters)

For prompt shipment please include postal money order or cashier's check. With personal checks, allow 2 weeks to clear the bank before shipment can be made. COD's must include 20% deposit. New York City residents add 5% sales tax. New York State residents add 2% sales tax.



ANY CONVERTER
NOW ONLY

\$16.95
ppd

except 301-X, \$18.95 ppd.

The model 301 uses 3 of the very latest type epitaxial planar UHF transistors for unsurpassed gain and low noise at all frequencies. It can operate from 6 to 18 volts (positive or negative ground) without any significant change in gain or frequency. The circuit consists of a tuned R.F. amplifier, crystal controlled oscillator and a low noise mixer. More than 30 high quality parts carefully assembled and tested. Sensitivity is better than 1/2 micro-volt for a 6 db signal to noise ratio even at 160 mc.

- Enclosed in a sturdy 16 gauge, 3 1/8" x 2 5/8" x 1 3/4" aluminum case with mounting ears, transfer switch and two SO-239 (UHF) receptacles.
- 100% made in the U.S.A.
- 2 year guarantee on all parts including transistors!
- Free 24 hr. SPECIAL DELIVERY anywhere in the U.S.A. if you send a money order or cashier's check. No shipments made on Saturdays, Sundays, holidays, and 2 weeks in August.

OPTIONAL ACCESSORIES:

9 volt battery eliminator with 110 volt cord. Only \$2.95 ppd.

R.F. cable adapters in 6", 12" or 18" lengths with PL-259 plug on one end (mates with converter). Other end your choice of Motorola male or female, RCA, BNC or PL-259. Price \$1.25 each postpaid cable with 2 plugs.

VANGUARD LABS

Dept. H
196-23 Jamaica Ave.
Hollis, N.Y. 11423

Dave Baxter W5KPZ/AF5KPZ
John Douglas W5OBV/AF5OBV
Route 9, Box 391
Tyler, Texas 75701

Two Meter Repeater

This repeater offers very wide coverage for fixed or mobile.

As more stations are moving up into the two meter band, a desire to increase their reliable range has caused many to look toward the repeater as an answer. This is a story of just such a repeater that was built by Air Force MARS people from surplus military and commercial FM equipment. Outmoded FM equipment was used because of the large


amount available from commercial users. No effort will be made to endorse any piece of equipment as this is what we used and other gear could probably be used just as well.

As can be seen in the block diagram, **Fig. 1**, the receive and transmit frequencies are separated by only 490 kHz. The methods used to prevent the receiver from being desensitized by the transmitter are little known to hams and should prove interesting to other amateurs who are plagued by strong carriers near their operating frequency. A cavity transistor pre-amp has been added to the receiver and can be placed on the tower to make up for the loss in a long transmission line.

This repeater was developed to receive on 143.46 MHz and transmit on 143.95 MHz, Air Force MARS frequencies just below the two meter band. Although these are not amateur frequencies the information supplied here has been used by amateurs using repeaters on 146.94 MHz. Different crystal frequencies are the only changes necessary to operate in the two meter band.

We used a surplus FRC-27; however, the TRC-34 and VRC-19 are very similar. The FRC-27 and TRC-34 are ac powered units and are almost identical. The VRC-19 is a mobile unit designed for a 28 V electrical system so would need an ac supply.

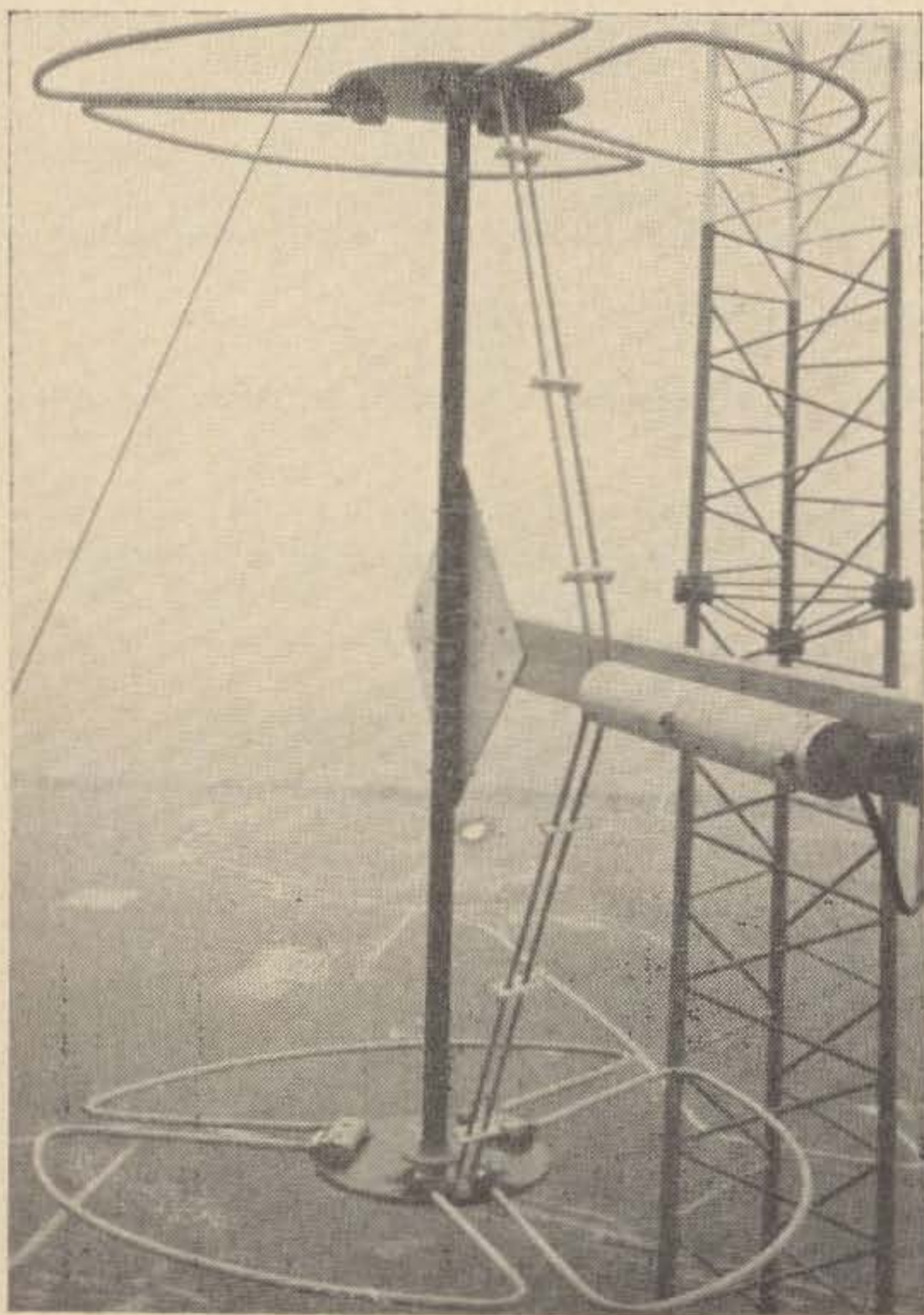The block diagram (**Fig. 1**) shows the complete repeater. It will be noted that the companion receiver R-394-U is not used. It was very unreliable. A GE Progress line 4ER25D was modified and substituted to give very reliable performance. This wide band receiver is expensive to narrow band so is available at very low cost.



The transmitting antenna with coax balun as it looks on the 1400 ft. tower also used for KPRC-TV.

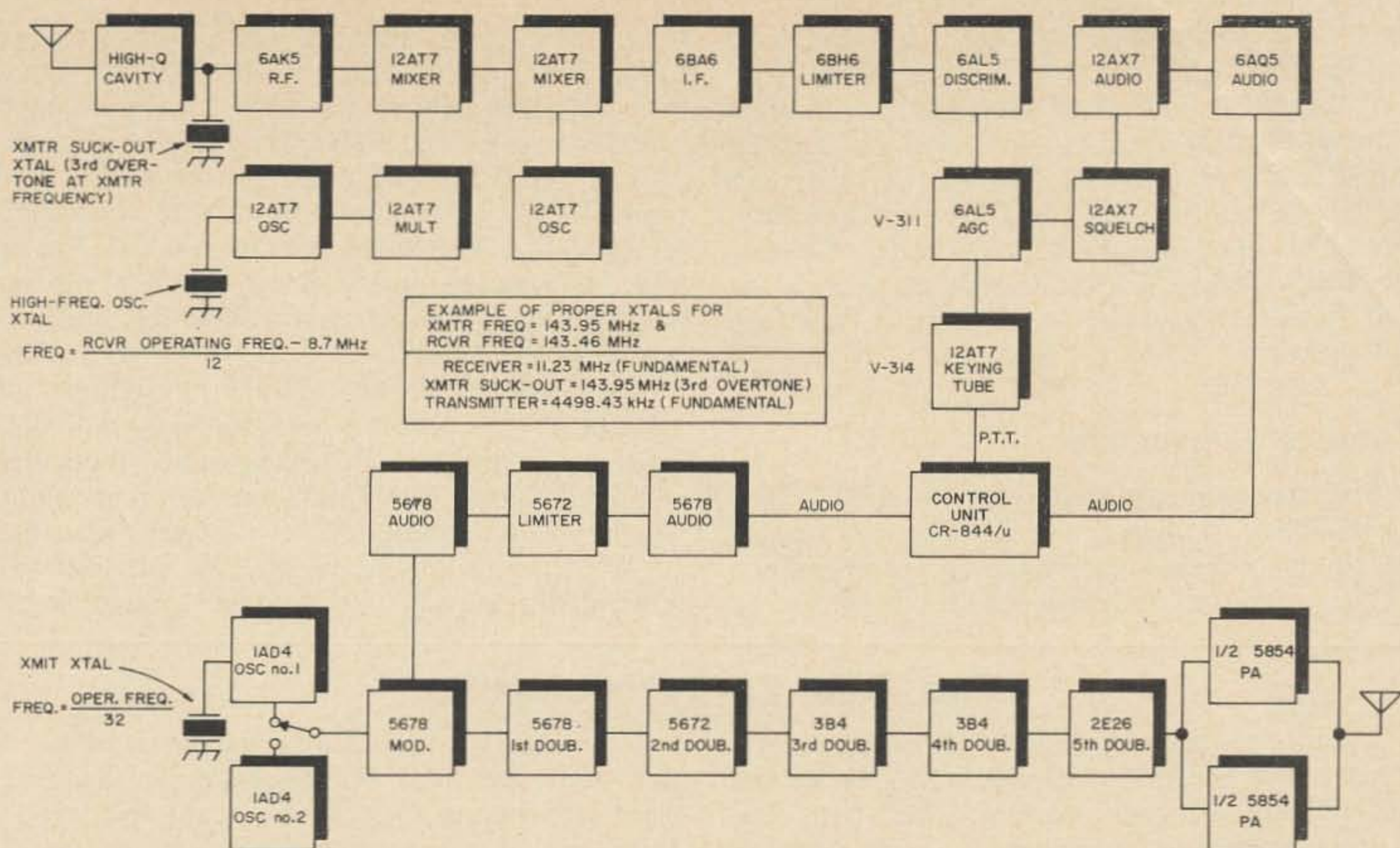


Fig. 1. Block diagram of the 2 meter FM repeater described in this article. The transmitter is a sur-

plus unit from the FRC-27 and the receiver is an out-dated GE wideband commercial receiver.

Transmitter Adjustment

The transmitter is coded T-416-GR and is installed in the lower right compartment. This unit uses instant heating tubes up to the driver, so only two tubes draw filament power during stand-by. The 5894 final operates in a very efficient push pull circuit and is capable of about 70 watts output. This unit uses a crystal multiplication of 32 times. The crystals shown are for either the 146.94 MHz or 143.95 MHz frequencies. These crystals should be in the HC-6U holder to take advantage of the ovens in the units; however, a FT-243 may be used if the oven is not desired.

A test card CX-2371U to allow removing the transmitter from the cabinet was found with some units; however, several have been made by using surplus connectors. A VTVM is used for the tune-up. Insert a crystal into the socket and switch transmitter to tune. Do not operate the transmitter for longer than 10 seconds until the final has been tuned. Remove both side covers and note the test point marked J401, etc.

Turn on the unit and allow time for the final and driver to heat. Switch the frequency select switch to the socket which has the crystal in it as this is a two frequency unit. The transmitter is keyed by turning the test switch to on. The switch should be returned to the off position as stages are tuned and the meter

is advanced to each test point. Place a 50 ohm dummy load on output jack P1902.

Tune up as follows:

VTVM connected to	Adjust	Indication	Reading
J-401	Z-401	Max	-5 V
J-402	Z-402	Max	-23 V
J-403	Z-403	Max	-30 V
J-404	Z-404	Max	-70 V
J-501	Z-405 C-502	Max	-40 V
J-502	C-507 C-508 C-509	Max	-45 V

Insert the VTVM in J-505-506 PLT CWR JKS. (Caution: HV to ground is present on these lugs). Adjust C-514 PA tune condenser for a dip on VTVM. Now load the PA to


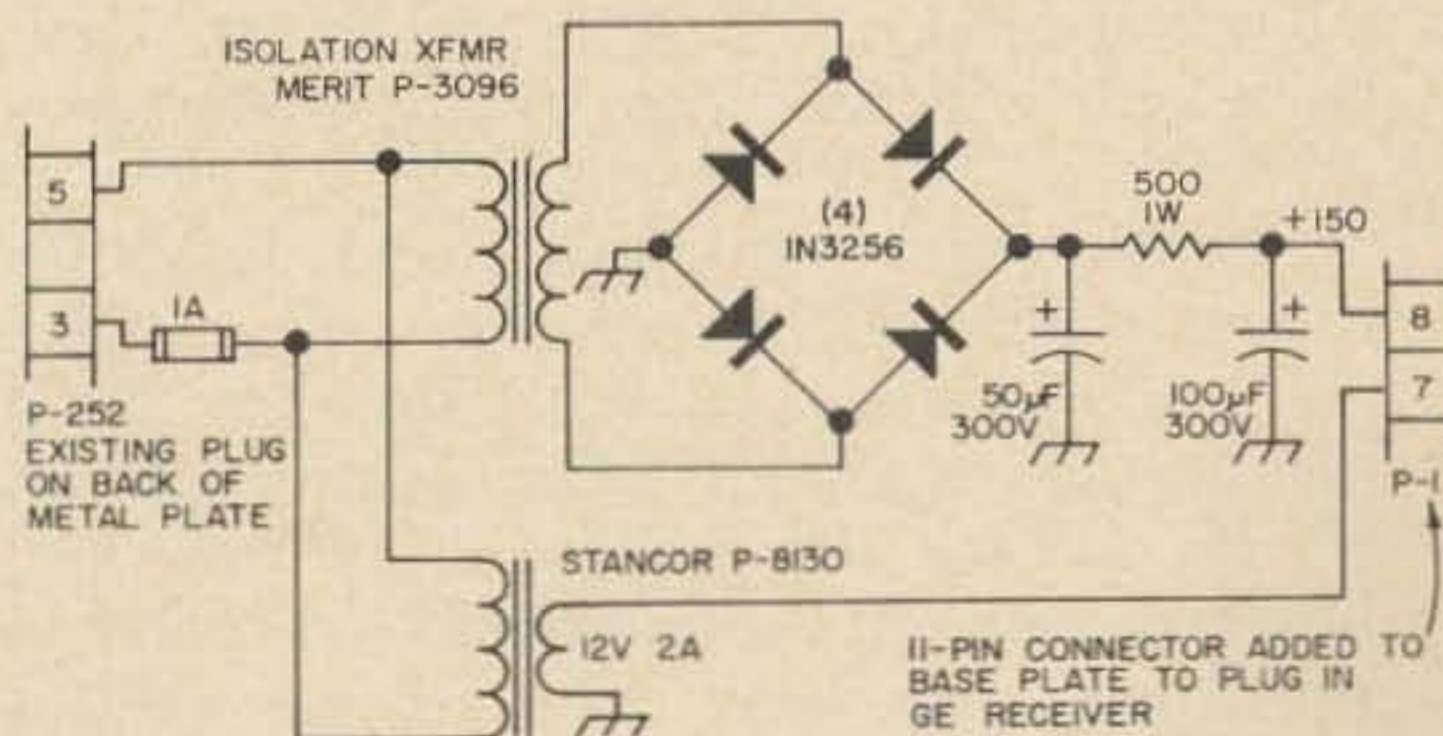


Fig. 2. Receiver power supply for the repeater.

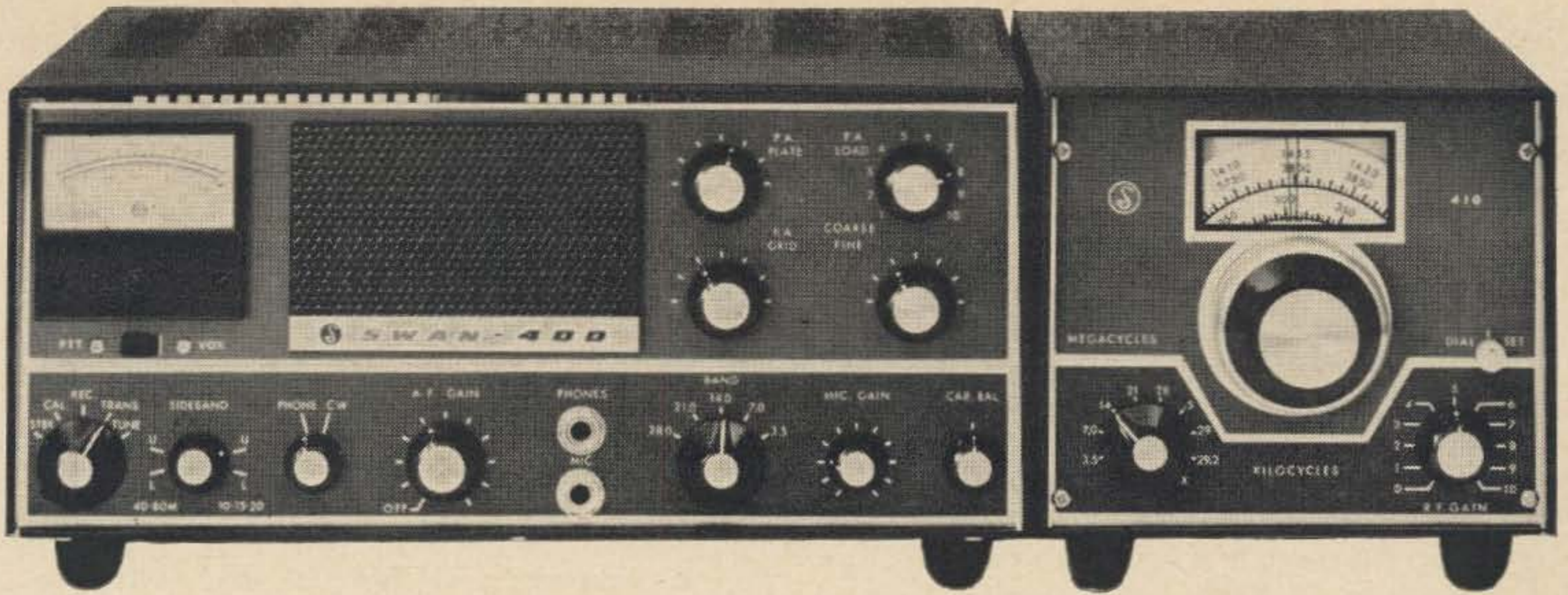

SWAN 400 SSB TRANSCEIVER

FIVE BANDS-400 WATTS

So often when thinking of investing in a mobile rig, the thought occurs that it will have to be a cheap outfit, without many of the excellent features of the home station. Can't afford two rigs like the home station, you say? This may be true, but when you have the combination that is designed for the job, the home station can be the mobile station, too, and the changeover simply a matter of moving the transceiver and VFO from the house to the car.

The SWAN 400 and its components fit together conveniently for this type of service. With the basic 400 you can operate as a fixed station using Model 410 VFO (for ham bands) and/or Model 405 MARS Frequency Oscillator (5 pre-set and locked channels on any 5 frequencies in the MARS allocations), both attached to the 400 at the same time through an adaptor on the back of the 400 that has a switch for changing from one VFO to the other, and both VFOs are kept warm so long as the 400 is "on". If you have the means of supplying the home station from a DC source such as batteries, gas generator or AC inverter (and a DC source for the home

station is a mighty useful item in an emergency), you would need only a DC power supply for the SWAN 400, and could put both the Swan and the power supply in the trunk of the car, connect them with the cables from the VFOs under the dashboard, Model 406B Mobile VFO and/or Model 405 MARS, using the RC-2 remote control assembly, and be ready for business as completely as if you were in the house, taking very little space in the front seat area of the car.

How, you ask can I latch on these gems? Nothing could be easier: Pick up the phone and call us and let's talk it over . . . or drop us a line and tell us what kind of a proposition you have in mind.

Swan 400	\$420.00
117-XB AC Power Supply	75.00
14-117 500 Watt Mobile Power Supply	130.00
Model 410 VFO	95.00
Model 406B Mobile VFO	75.00
MARS Oscillator Model 405	45.00
Dual VFO Adapter Model 22	25.00


Adirondack Radio Supply

Ward J. Hinkle, W2FEU, Owner

185-191 W. Main St., Amsterdam, N.Y. 12011, 518-842-8350

are visible mounted on the base plate. Punch a hole in the base chassis and mount a 11 pin socket (P1) so that the receiver power plug can be connected. A small power supply, delivering 12.6 V ac and 150 V dc can be constructed to furnish power to the receiver as shown in Fig. 2. It is suggested that this be constructed on the receiver chassis base plate. By carefully orienting the transformers, the parts can be fitted. The voltages are now fed to P1 on the base. There are many variations of transformers but they must be small. Most any 110 V 40 watt isolation transformer will work. On the front of the base assembly between the four small holes that were used as the old receiver test points, mount two miniature pots, 10 kΩ for the squelch and 100 kΩ for the volume. Connect these to P1 as shown (Fig. 3). The receiver has a provision for a second crystal using one half of the 12AT7 as oscillator. This half of the tube is not needed, and for repeater service is wired to key the PTT line in the transmitter. Build the circuit as shown in Fig. 3 using the unused half of the 12AT7. The frequency 2 lead to the power plug can now be used to connect the PTT line to the transmitter as shown. The frequency 2 lead is the middle lug on the three lug terminal strip next to the oscillator tube (lug 2 of TB 15). It can be seen that a small positive voltage on pin 5 of V-311 will cause tube V-314 to conduct. This current will hold the keying relay operated. A received signal causes pin 5 of V-311 to go negative and this cuts off V-314. This in turn will release the relay and ground will be applied through the now closed contacts of the relay. This ground will now key the transmitter. Audio from the receiver is fed through plug P1 to the FM modulator.

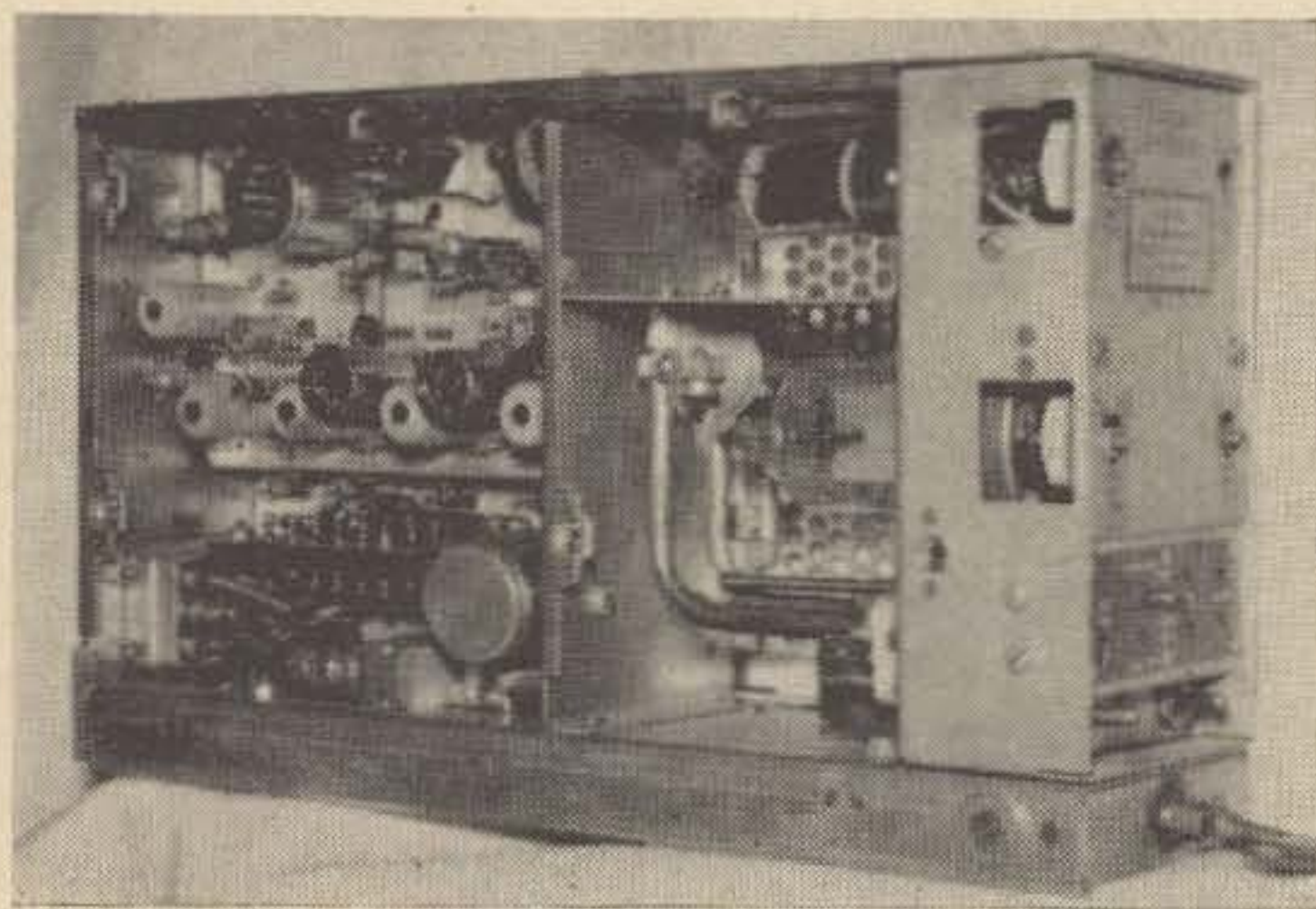The receiver will require two crystals; one



The transmitter is shown with one side removed. The 5894 final amplifier can be seen with its quarter wave tuned lines. The oscillator and multiplier stages are in the rear compartment at the left.

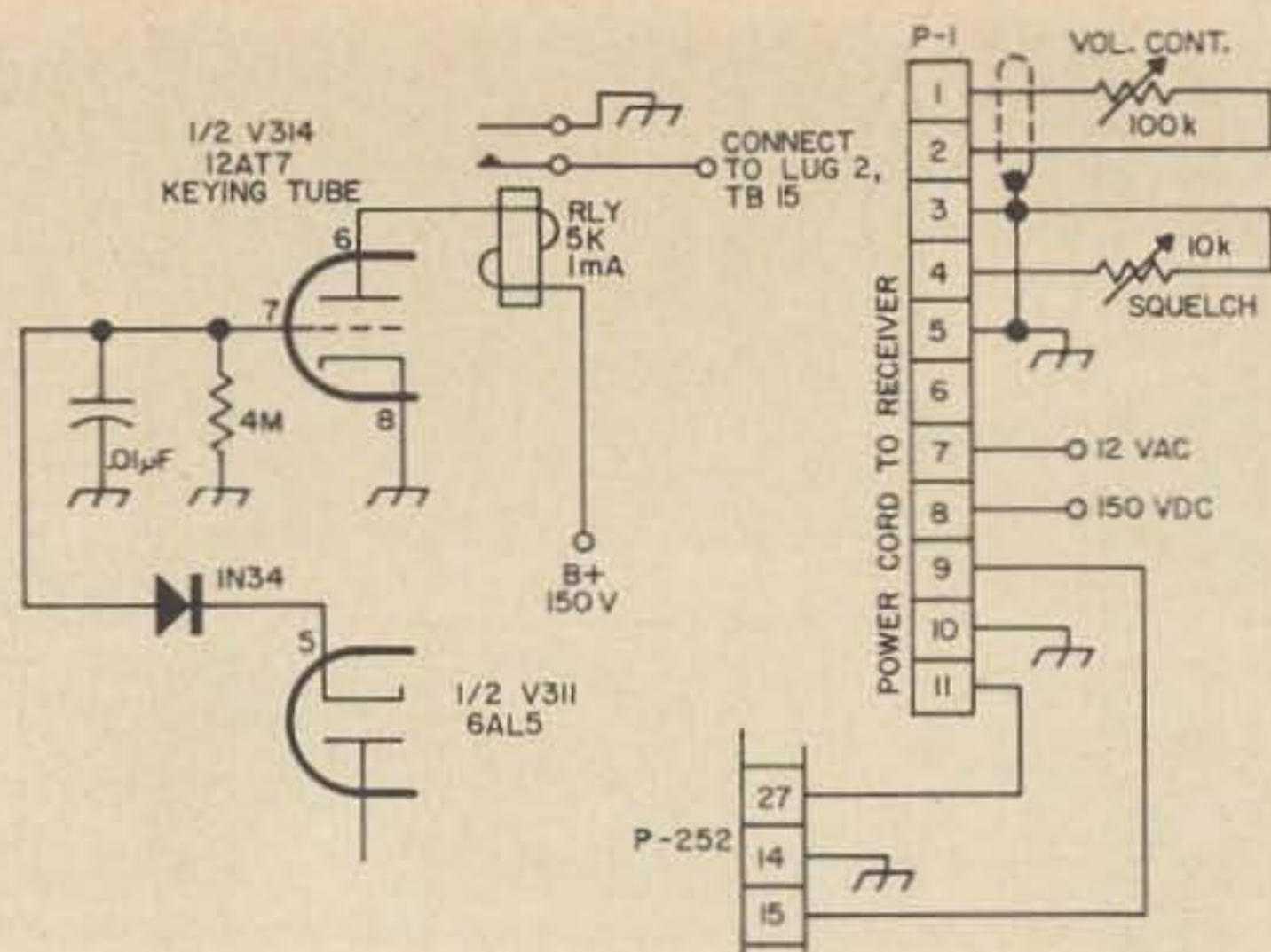


Fig. 3. Transmitter keying tube and control circuits.

for the high frequency oscillator and the other is used as a transmitter frequency suck-out crystal to place a low impedance path to ground at the transmit frequency. This crystal connected in this manner prevents the receiver from being overloaded and thus desensitized by the strong transmitter carrier. To figure the high frequency crystal use the formula below.

$$\text{crystal frequency} = \frac{\text{operating frequency} - 8.7}{12}$$

for a receive frequency of 143.46 this would be 11.23 MHz.

The transmit frequency eliminator crystal is shown in Fig. 4. This crystal was ordered from International Crystal Company, Oklahoma City, Oklahoma. They are familiar with this. When ordering this crystal give the following information: *Example:* 143.95 MHz third overtone crystal—This crystal will be connected from grid to ground of the 6AK5 rf amplifier in a GE 4ER25D receiver to eliminate a strong transmitter carried on 143.95 MHz. This receiver will be tuned to 143.46 MHz and a high Q coax cavity will be inserted between the antenna and receiver. This crystal is to prevent the receiver from being desensitized by the 143.95 MHz transmitter. This crystal should be ordered with wire leads. The cost \$6.90.

Connect this crystal in the antenna coil can across the rf amp grid coil as shown in Fig. 4. On using this crystal in this manner, it can be seen that any power present here will destroy the crystal so be careful. This crystal is not guaranteed in this application but if installed and operated as shown, no problems should be encountered.

Install a phono type plug on the antenna coax that goes to A2 of P-252. This will plug into the antenna jack on the receiver. The fuse in the receiver can be mounted in the base at any convenient spot. The 0.1 μF capacitor and 4 MΩ resistor in Fig. 3 act to

hold the transmitter operated for about 1 second after the 143.46 MHz signal is gone. This was done to prevent the rapid flutter so common in two meter mobile communications from causing the repeater to chop.

Turn power on to unit and check for proper voltages. A signal generator and a vom of at least 20,000 ohms per volt is needed for alignment. Connect signal generator to P-1901 on back of cabinet and tune generator of operating frequency of receiver.

Use a 20,000 ohm/volt meter with one lead to ground and connect the other as directed:

<u>Connect to</u>	<u>Adjust</u>	<u>Required Reading</u>
	Top OSC	
OSC	Coil Maximum	1.3 V
	Mult Can Top	
MULT	and Bottom	Maximum
Feed 143.46 MHz signal at the antenna jack		
—increase level till LIM 1 shows indication—		
	LIM 1—Mult 2 both capacitors	
	RF amp both capacitors	
	Ant top and bottom	

Repeat all adjustments (except oscillator coil) until required sensitivity is obtained. (Requirements .5 μ V for 20 dB of quieting). With a known accurate signal at 143.46 MHz adjust the oscillator crystal frequency adjust capacitor for zero reading when meter is connected to the discriminator. This completes the receiver alignment.

Final adjustments

Remove the back cover of the FRC-27 and make the following connection to the terminal strips:

TB-1901	Connect terms	6-7
	Connect terms	8-10
	Remove wire between	2-3
TB-1902	Connect terms	2-3
	Control Unit C 844U	
TB-701	Connect terms	2-3
	Remove wire between	1-2

This completes the conversion and it is only necessary to set the levels of transmis-


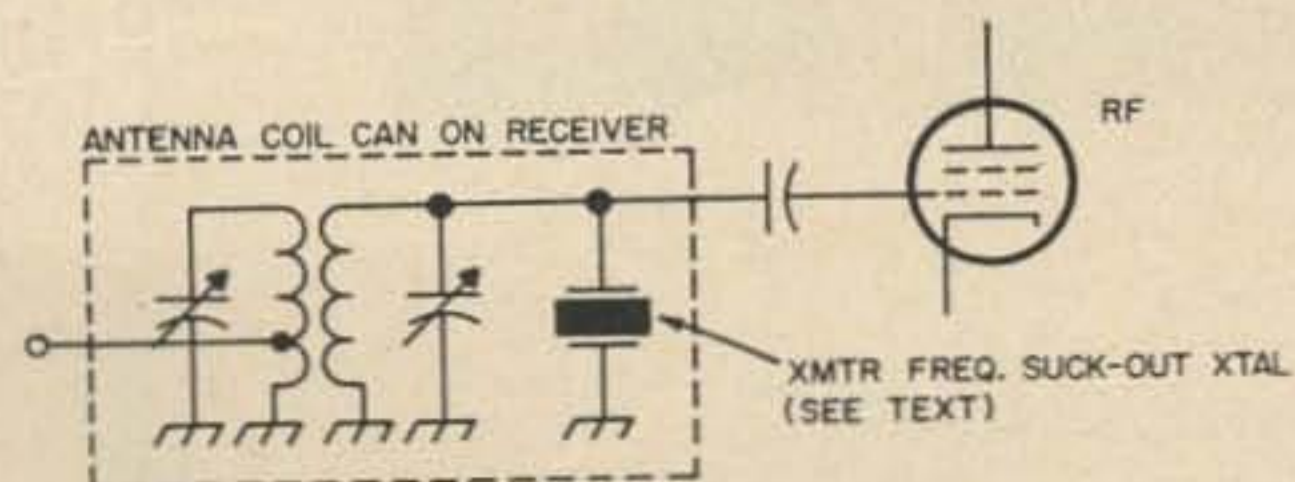


Fig. 4. Connection of the transmit suck-out crystal.

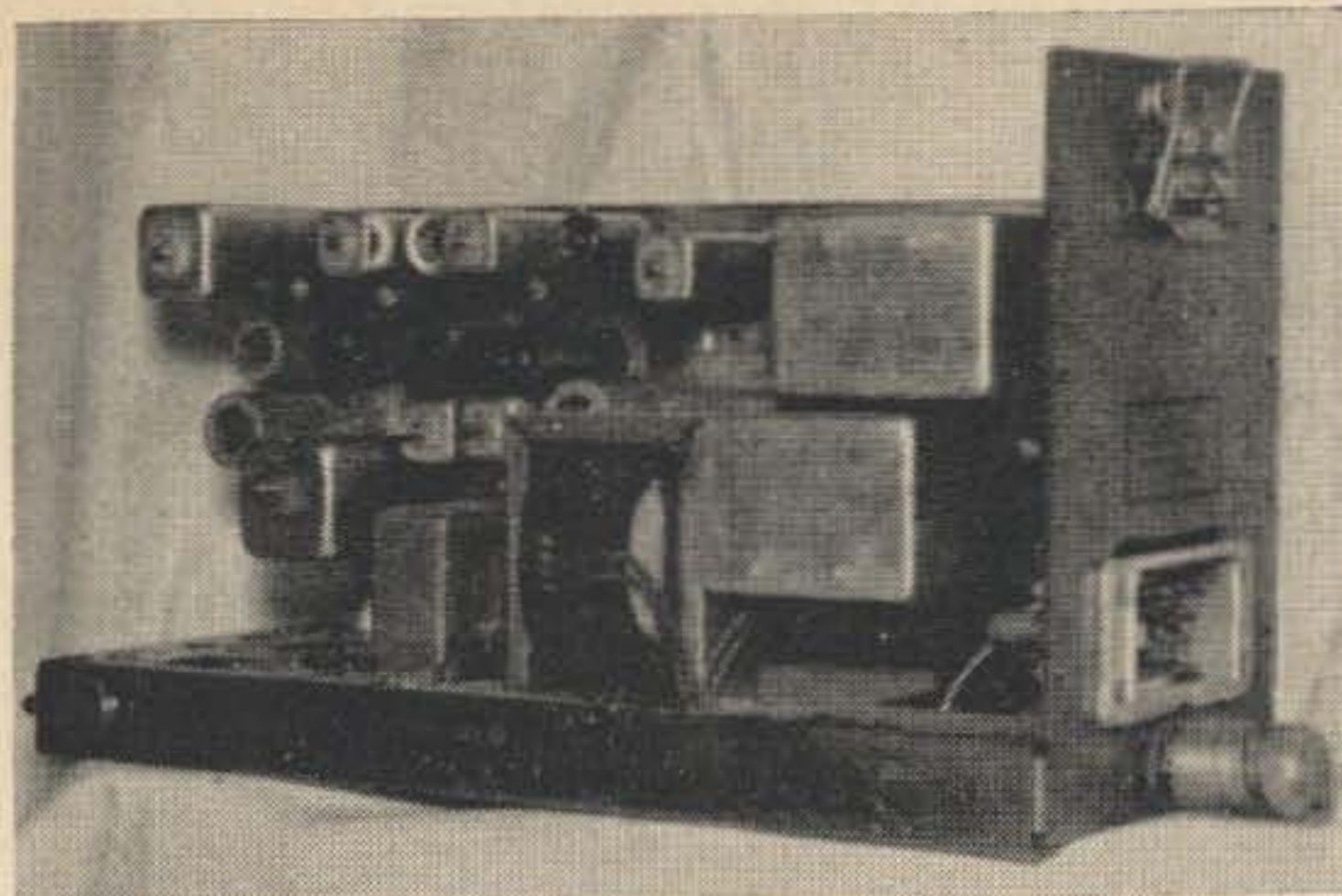

The modified GE receiver is mounted on its side so it will fit on the existing chassis. Plug P252 is shown on the back and the filament and plate transformers are visible mounted on the base plate.

sion. There will be three controls in the audio line: receiver volume, L pad in control unit and deviation control in the transmitter. As a guide to start with, keep the receiver level low as this will lessen the noise level on the transmitter audio. The L pad is a very effective impedance matching device and when used with the deviation control, it should be possible to get full deviation on most all levels of input signal. The squelch control is adjusted to the point where noise does not trip the repeater.

The antennas used here are stacked horizontally polarized big wheels separated by about twenty feet between transmit and receive.

The work in building this repeater was not done overnight and many hours of cut and try and looking into problems in other repeaters were necessary. We feel this has paid off, however, in the quality of retransmission and dependability we have obtained. The repeater at Houston is located on the KPRC-TV tower (1400 ft.) and excellent mobile coverage is obtained up to 60 miles radius. Base stations work out about 150 miles and farther in some directions. I am located 220 miles from Houston and can use the repeater most of the time.

I have worked San Antonio through the repeater on many occasions which is in excess of 400 miles from Tyler.

The holdover of the receiver gives me a constant check on the band conditions as I can listen for the repeater to drop out.

This repeater project was built by AFCS Air Force MARS people to operate on two meter MARS frequencies, and plans call for 23 of these repeaters to cover ten states in the Central United States. At this time four units are operational with five more near completion. These units were built according to these instructions, and all have worked properly.

. . . W5KPZ


HUSTLER® *for the first time...*

FIXED STATION TRAP VERTICAL

Hustler quality and reliability with

**ONE TUNING ADJUSTMENT
TO COVER BOTH PHONE and CW**

4-BTV... Only \$3295

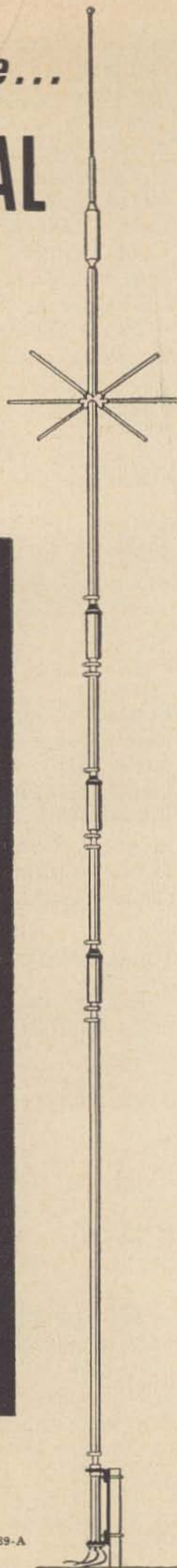

**Here's why the Hustler 4-BTV
is the best trap vertical for the money.**

- You'll get superb operation... 40 through 10 meters. (Also 75 meters with a Super Hustler RM-75-S on top.)
- 4-BTV performs as a true vertical... not as a bent dipole.
- Optimum-Q traps are individually and precisely tuned.
- 4-BTV handles full legal power on SSB.
- The lowest SWR (1.5 to 1 or better) and best bandwidths are possible with the 4-BTV... and it outperforms all other verticals.
- Vertical radiating sections between traps are tunable for peak performance.
- Sturdy heavy-walled aluminum construction with stainless steel clamps and cyclac base resists all weather.
- Guying is not needed... only the smallest space is required to install on the ground, roof top or chimney clamp.

BE A HUSTLER... USE A HUSTLER

See the new Hustler 4-BTV at your dealer today.

Ask about the complete Hustler line.

"The
home of
ORIGINALS"

NEW-TRONICS CORP.

3455 Vega Avenue • Cleveland, Ohio 44113

6439-A

ALL NEW from NEW-TRONICS

SUPER

HUSTLER T.M.

unbelievable mobile performance

The Super Hustler has...

High Power Capability—Capable of maximum legal limit on SSB.

Widest Bandwidth—Better than ever... maintains minimum SWR over phone portion of 40, 20, 15, and 10, — 60 KC wide at 2 to 1 SWR on 75 meters.

Low SWR—1.1 to 1 or better at resonance... no special matching required.

Proper Base Impedance—Nominal 52 ohms at resonance—no magic lengths of feed line or matching devices required.

Low Frequency Drift—Frequency drift from heat held to absolute minimum.




SWR chart and comparative information supplied on request.

Here's 413 reasons for exceptional performance.

Coil wire contains 413 individual conductors insulated from each other for top performance value.

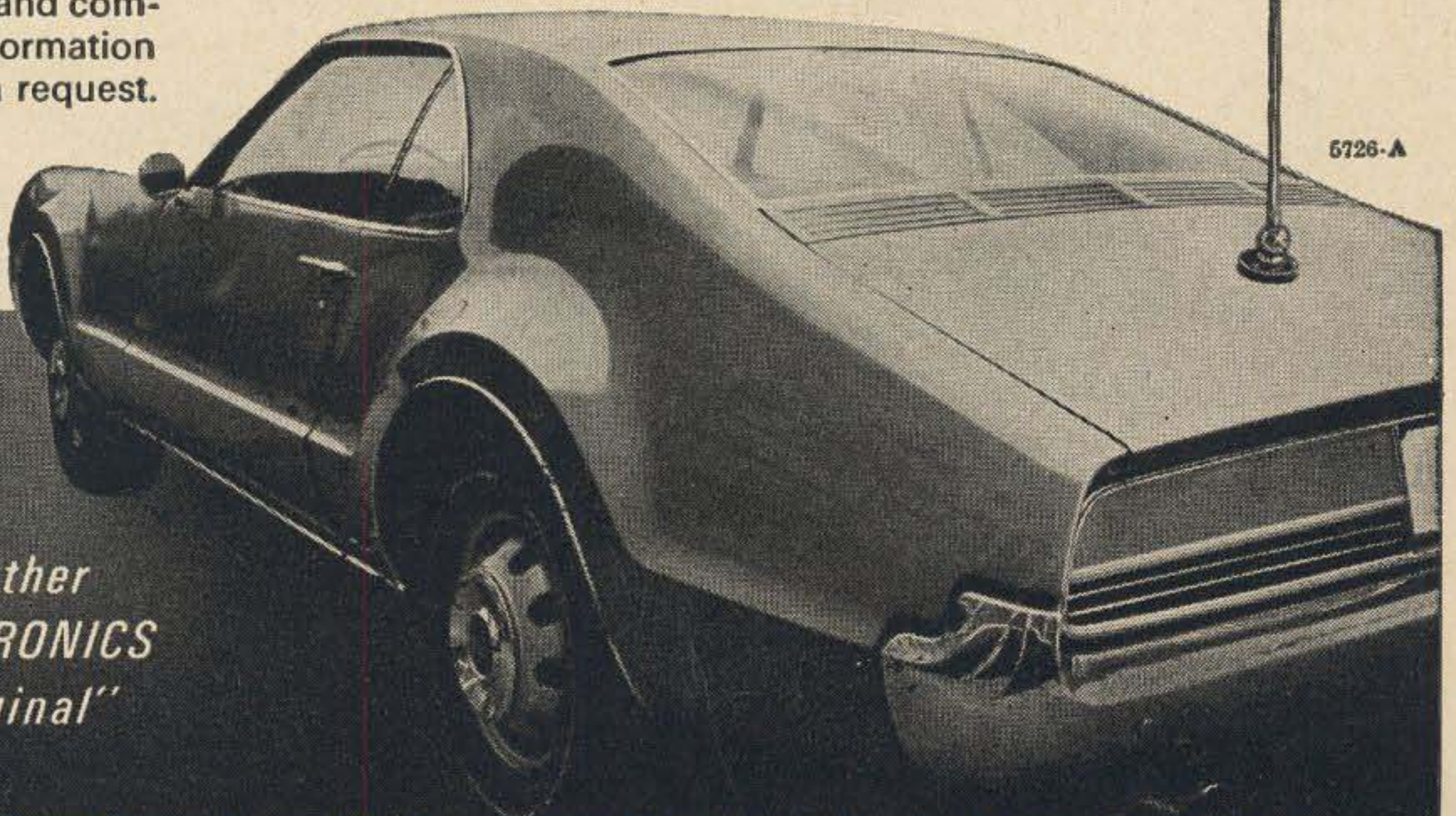See the new Super Hustler at your distributor NOW... get the facts.



*"Another
NEW-TRONICS
Original"*

NEW-TRONICS CORP.

3455 Vega Avenue • Cleveland, Ohio 44113

Complete Overload Protection

Here's one of the more original schemes we've seen recently.

Here is a circuit that offers much for all builders and nuts that dream up rigs that are as well engineered as the state of the art. This circuit offers complete overload protection for the whole rig (including output, temperature, and VSWR as well as the more common current protection) with one, or at the most two, relays. As many sensors as wanted may be included.

The basic circuit (see Fig. 1) uses a silicon-controlled rectifier, or SCR, that semiconductor equivalent of the thyratron. Whenever the gate current exceeds the threshold the SCR saturates and remains conducting until the anode circuit is opened. When the SCR fires, K1 is actuated and can open the PA cathode circuit, operate a heavier relay, light an indicator lamp, or any other desired function.

With this basic actuator circuit you can use

any or all of several sensors. The only requirement is that the sensor develop a few volts positive. With the unmarked junkbox SCR I use 0.2 MA of gate current, 2 volts across the 1 k gate resistor causes the SCR to fire with 10 volts on the anode (stolen from the filament transformer).

For plate current protection a 5 ohm resistor (of suitable wattage) is put between ground and the PA tube cathode (or in the B-return of the PS). For 1 ampere of plate current 5 volts are developed. (See Fig. 2A.) Using about 5 k for the adjusting resistor "R" you can set the voltage to the gate for any value at the predetermined plate current (for me it trips at 800 MA).

Screen protection is provided by monitoring the current drawn by the shunt screen regulator, a string of 10 watt zener diodes in my rig. (See Fig. 2B.) As screen current increases the regulator current decreases equally. By placing a small resistor in the ground return of the regulator you can pick off a couple of volts. Here a transistor (PNP) is used to get a phase reversal, rising positive voltage for decreasing regulator current. A blocking diode is

Mick is an Electronics Technician Senior Chief in the U. S. Navy. He has taught electronics courses in the Navy, enjoys building and rag-chewing. He's now stationed on the USS F. D. Roosevelt.

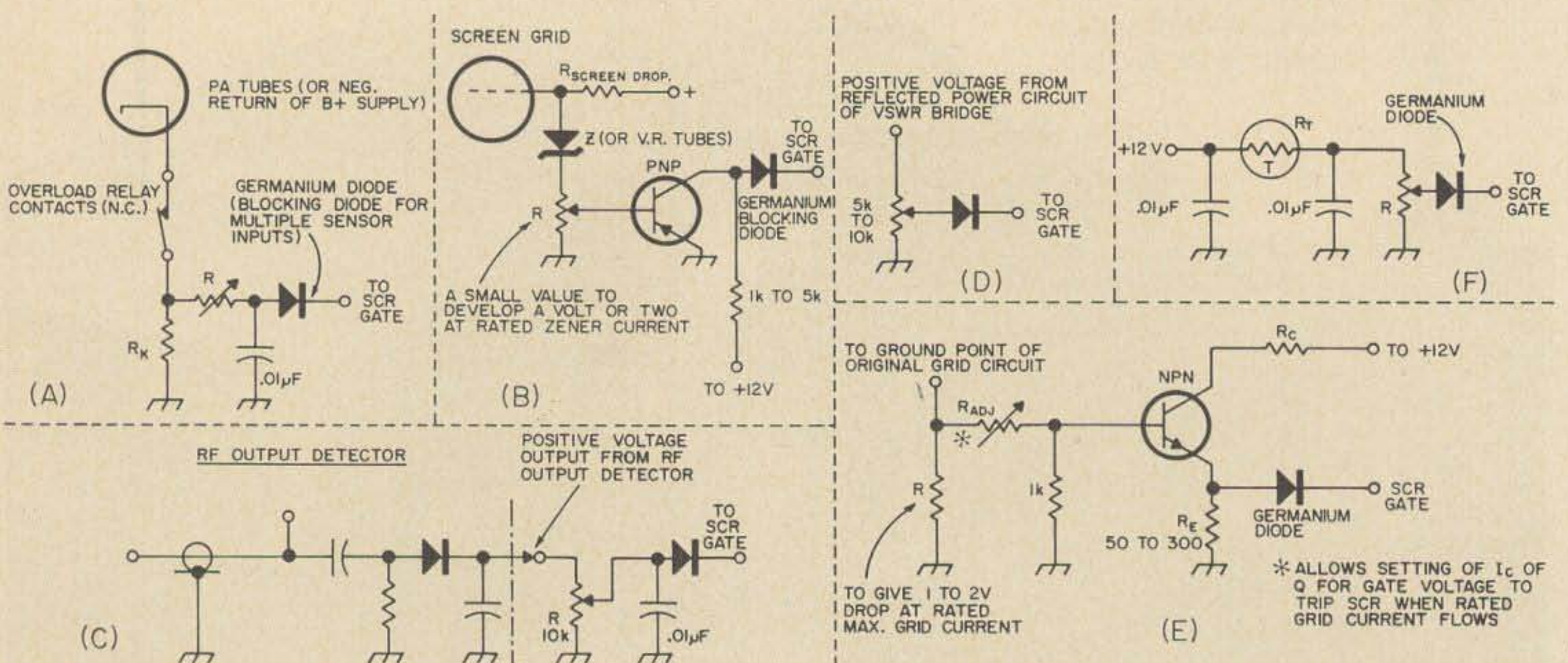


Fig. 2. Sensors for the overload circuit in Fig. 1. A. Protection against too much plate current. B. Screen current protection. C. Excessive output protection (You don't want to exceed the legal limit,

do you?) D. High VSWR protection. E. Protection against loss of grid drive. F. Excessive temperature protection. See text for more complete explanation of these circuits.

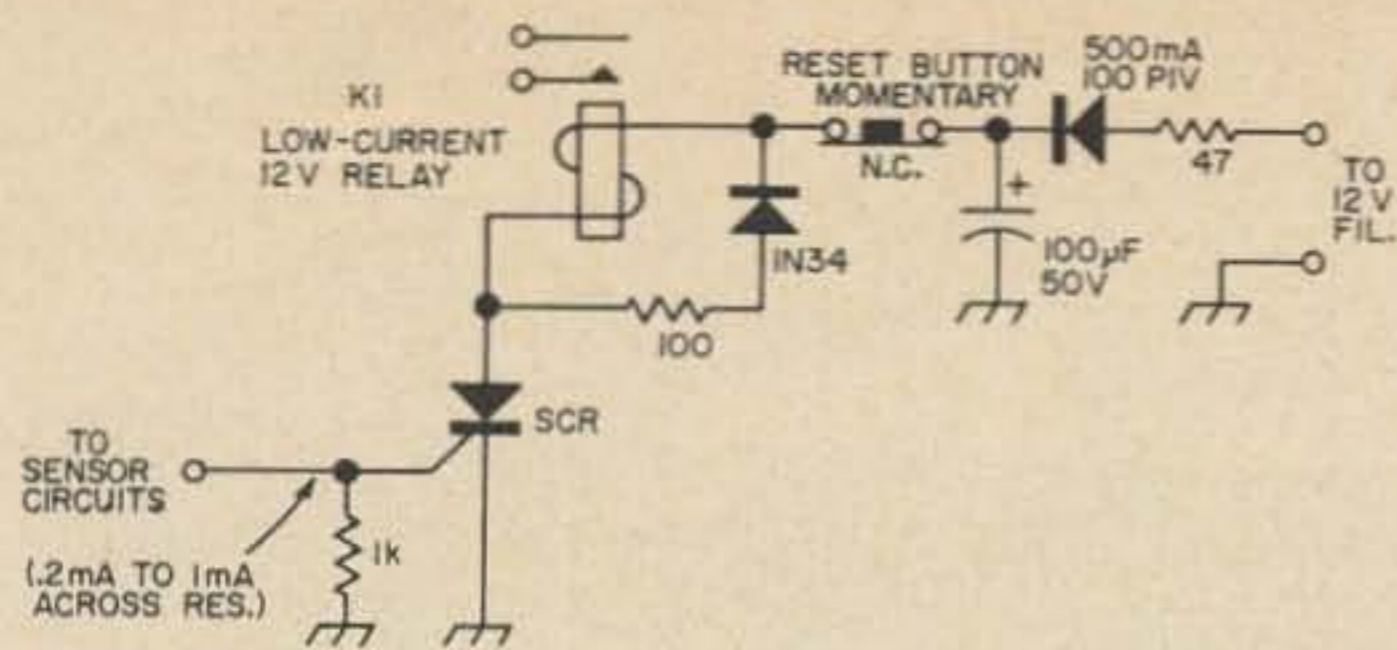


Fig. 1. Basic circuit for overload protection. This SCR and relay will turn off your transmitter (or ring a bell) when almost anything goes wrong with your station. See Fig. 2 for examples of sensors.

used on this (as well as on all the other sensors to prevent interaction between the inputs). Adding the few ohms of resistance in the screen regulator won't affect the regulation by more than a percent or so.

By using an output rf voltmeter diode circuit you can set a safe maximum power output level and protect the tubes from excessive power (or keep from running illegal power!) See Fig. 2C.

Another outstanding protective circuit can use the reflected power output from your VSWR bridge (positive diode polarity) to remove power in case of a damaging high VSWR. This could save a PA stage if an antenna or coax fails (or in my case if I patch the wrong antenna into the rig). See Fig. 2D.

Grid current can be likewise monitored, again using a transistor (NPN) to get the proper sensor output signal. See Fig. 2E.

Another important function can be monitored by using a thermistor of the proper temperature/resistance characteristic in a voltage divider circuit. Placing the thermistor close to the tubes or in the exhaust air stream will let the monitor keep watch on those precious bottles and shut things down before the plates melt or the seals rupture. See Fig. 2F.

You can probably dream up several other circuits for different applications. Using a microphone and audio amplifier with a rectified output the telephone bell or the XYL's last chow call will terminate transmission effectively.

One important point: These circuits must be carefully bypassed and shielded in most cases to prevent rf pickup and rectification by the sensors and/or the SCR.

Try this one relay, multi-function overload protector and I think you'll have as much fun and get as much peace of mind as I have. It works, smoothly and positively, is cheap and small. Its applications are limited only by your imagination.

. . . W4ZUS

ABSOLUTELY NEW

TRI-EX

W-51

**FREE STANDING
TOWER.**

**SUPPORTS 9 SQ. FT.
OF ANTENNA.**

Shown with internal Ham M
rotator and 2" mast.

INCLUDES

- **FREE: RIGID BASE MOUNT**
- **PRE-DRILLED TOP PLATE — For TB-2 thrust bearing.**
- **HIGH STRENGTH STEEL TUBING LEGS. Solid rod, "W" bracing.**
- **EASY MAINTENANCE — No guys or house brackets needed.**
- **RISES TO 51 FT. — Nests down to 21 ft.**
- **HOT DIPPED GALVANIZED AFTER FABRICATION! All welding by certified welders.**

IMMEDIATE DELIVERY

\$362⁶⁰

FREIGHT PREPAID INSIDE
CONTINENTAL U.S.A.



Iri-Ex TOWER CORPORATION

7182 RASMUSSEN AVE., VISALIA, CALIF.



Ken Cole W7IDF
 P.O. Box 3
 Vashon, Wash. 98070

Heathkit HM-15 SWR Meter

If you have a ten dollar imported SWR meter and like it, as I do, you may wonder if a few bucks extra for the Heath HM-15 can be justified, as I did, but you may not have an opportunity to try them side by side, as I have. (They won't measure prepositional phases, so they won't really work in parallel.) Some of the Heath meter advantages that impressed me are reflected below.

Terminating resistors are supplied for both 72 and 52 ohm operation—a worthwhile provision. To change from one to the other requires removal of the chassis from the cabinet and application of a soldering iron, but this takes only a couple of minutes, and it isn't something you would do very often. The change could be made by switching, but the instant convenience gained would be too expensive in terms of added capacitance, asymmetry and associated problems which would have to be solved. It's nice to have the two impedance ranges simply and cheaply.

Some HM-15 Specifications

Operation: Indicate percent of forward and reflected power, and voltage standing wave ratio.
 Power Handling Capability: One kilowatt of rf.
 Impedance: 50 or 75 ohms.
 Frequency Coverage: 160 through 6 meters.
 Meter: 100 microamperes.
 Dimensions: 9¼ x 3⅝ x 2⅝ inches.

The cabinet is attractive, stiff, and designed to sit prettily atop your transceiver—rubber feet on the bottom and coax connectors in the back. For mobile operation the HM-15 takes little room under the dash, and if it is mounted with screws through the cabinet top you can remove the chassis in about thirty seconds by unscrewing the two self-tappers on each end.

Besides being fun, kit-building is a relatively painless educational experience, and this is one kit you really can assemble in an evening. In fact, you can put it together, squirt your transmitter through it, check the SWR, test the surplus lengths of coax on hand, confirm the non-reactive behavior of your dummy load, roundtable for an hour (while you watch the HM-15 for evidence of carrier non-suppression) and still beat the kids to bed.

The manual is a useful bonus. A thoughtful effort has been made to explain clearly the theory and operation of SWR meters. With two charts and a couple of pages of text the manual makes the most of the benefits offered by the put-it-together-yourself approach. The limitations as well as the capabilities of SWR meters are noted, and the comments may leave you with an irresistible urge to dig out 73 articles on the taming and feeding of antennas. All to the good.

At \$14.95 the HM-15 is one of life's inexpensive necessities.

... W7IDF

1966 Eico Catalog

Eico's new 48 page catalog illustrates and describes their complete line of more than 250 products, including amateur radio equipment, test instruments and stereo hi-fi components. Copies of this new catalog are available free from Eico Electronic Instrument Company, 131-01 39th Avenue, Flushing, New York.

Creative Electronics Fabrication

If you like to make professional-looking electronic equipment, this new book by Owen Patrick should be of interest to you. The title is *Creative Electronics Fabrication* and it's published by Holt, Rinehart and Winston. Virtually all electronic construction techniques that the amateur could need are covered. You can order a copy through your local bookshop.

Radio Products Sales' Catalog

Radio Products Sales Inc., has just announced a new 300-page catalog of electronics parts and equipment. This new catalog covers a wide variety of electronic components from 86 leading manufacturers and is of considerable use to amateurs and electronics engineers. It is thoroughly and accurately indexed for easy reference, profusely illustrated and where applicable, contains industrial net prices. These new catalogs may be obtained by writing to Radio Products Sales Inc., 1501 South Hill Street, Los Angeles, California 90015.

Electronic Design Charts

Most hams seem to like to avoid using mathematical formulas and equations as much as possible, but if they do much experimenting and designing, they have to figure out many things. Graphs and nomographs are one way to find specific values for components and other electronics quantities without much math. Norman Crowhurst's *Electronic Design Charts* contains 59 useful charts that will help you design many circuits and networks. It's bound in a very convenient loose leaf fashion with complete and clear explanations and examples for each chart. Cost is \$5.95 and you can buy a copy from your distributor or Gernsback Library, 154 West 14th Street, New York, N.Y. 10011.

1967 Lafayette Catalog

Lafayette's new catalog is now available at no charge. You're already familiar with them and know that it's something you'll have to have, so why not send for your copy now? Lafayette, P.O. Box 10, Dept. PR73, Syosset, N.Y. 11791.

Build the modern, easy way with circuit boards and solid state!



W1JJL's code practice oscillator-monitor described in the July '65 73 belongs in every shack and shack-to-be. It's inexpensive and works well. The drilled board with all components locations marked is only \$1. The board with the parts mounted on it is \$3. Or you can buy it mounted in an attractive case as shown above, complete with battery, for \$7.95.



Here's an excellent field strength meter. It's easy to use with a built-in amplifier for use with any 1 mA meter. See the article in the December '65 73. The drilled screened board is \$1. With the components mounted it's \$3. Complete in an attractive case, the price is only \$5.95.

A good HF-VHF SWR bridge doesn't have to cost a lot. You can make one from an inexpensive meter and our special pick-up line described by W1JJL in the September '65 73. The line with holes drilled is only \$1, or you can get it with parts already mounted for \$3.50.

Want a good keyer? We've got boards for two: WA6TSA's Uni-Junction Keyer in the January '66 73 can be built on our fiber glass board with the holes drilled and parts locations shown for \$4.95. With the transistors mounted on it, it's \$8.95.

Another good keyer is WB6AIG's Kindly Keyer in the July '66 73. The fiber glass board for this keyer, with all those 120 tiny holes drilled is only \$4.95.

K3LCV's FET Voltmeter is very useful. It's described in the July '66 73 and a fiber glass board for it is \$3.50. See the Siliconix ad in this issue for the FET's at a fantastic price.

COMING SOON: WATCH 73 FOR THESE PROJECTS!

Novice receiver and transmitter. VHF and UHF dip-meters. One watt six meter transceiver. Capacitor-resistor checker. Portable FM monitor. Wavemeters. Calibrators.


Prices include postage in U.S.A. Connecticut residents include sales tax. All boards in stock for immediate delivery.

Harris Company

56 E. Main Street

Torrington, Conn. 06790

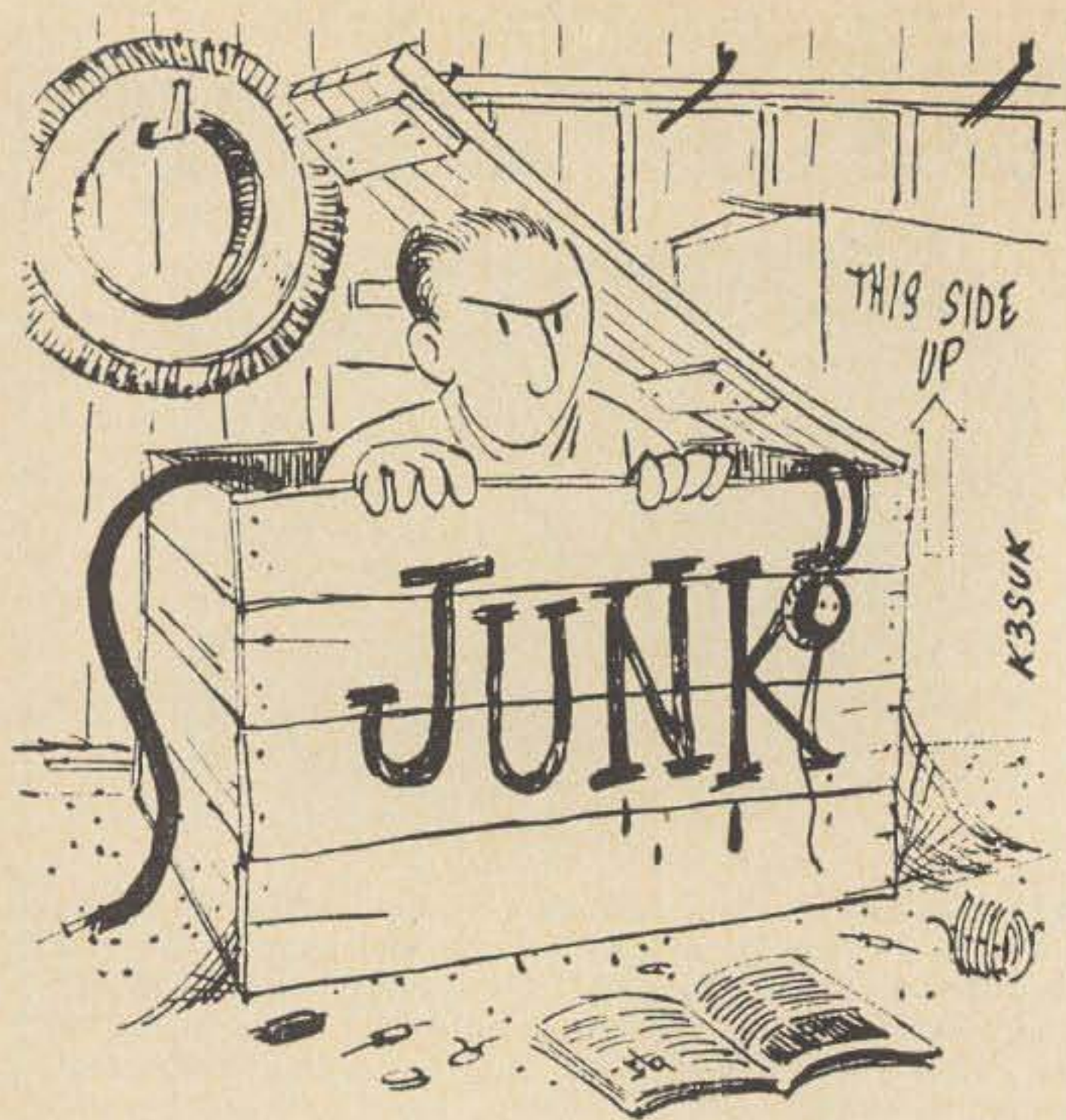Merritt Franken WA6JNI
3714 Mound View Ave.
Studio City, California



A Pox on Your Junk Box

Been a ham now ten or twelve years or so, give or take a bit. It all happened when I had the dubious fortune to meet Wayne Green in the living, quivering flesh. Exposed to his torrent of talk it wasn't long before I went the way of so many others and there was the code oscillator and the hand key and the books and the butterflies in the stomach at the thought of taking the test. So here I am, a decade or so later, duly licensed, poorer by several thousands of dollars, richer by a number of hammet friends and sizzling with a long-smoldering peeve.

The peeve? Easy. It's this junk box jazz I keep reading about.

Almost the first thing I noticed when I started reading ham magazines is that they all seem to be liberal in referring me—or any other reader—to the junk box. Building an antenna, That little plastic dimity you need is bound to be in your junk box. Whacking away at a speech compressor? That capacitor you need to make your next contact think your audio sounds like the squeaks of a lovesick porpoise is in your junk box. Right on top if you'll look carefully. Etc. etc. etc.

Oh, I have a junk box, all right. Matter of fact my wife (she's a ham too and truth be known beat me to it in getting the general ticket) says I have junk boxes all over the place. In several drawers in the shack desk. A clutter in the workshop. Boxes of moldy goodies in the garage. I often wonder how come and why the XYL became a ham but it seems damn sure to me that if she hadn't

there'd have been a divorce in these parts for sure.

So the other day I got to thinking about the junk box. What started me was that several articles I'd just read, each of which said the whole project would cost about 38¢ and even less if I took recourse to you-know-what, had led me down the primrose path again. As a result, I now have, in various stages of non-completion, a variety of junk box projects, including a 40 meter QRP cw rig, a transistorized keyer and a couple of others I'm too irritated to mention. What happened in each instance is that my capacious junk box wasn't capacious or junky enough and by the time I finished pricing out parts I needed I could have bought my wife a dress (as she often reminds me) or paid for a week's vacation or maybe gone to a local ham emporium and bought the thing to begin with.

That's when I came to my Big Decision. I was going to breadboard The Project, right out of my own junk box. Just start out easy and see where it led. First thing I needed was a breadboard. No problem. We got a beaut from some travelling friends a year or so ago. They sent it to us from Africa and the fact that it was ebony didn't make any particular difference to me. Next, start mounting components. That beautiful butterfly variable would look real nice in the lower right hand corner. I got that little goody when I made an ill-advised trip to a surplus joint and if you remember, the poet said, "A butterfly capacitor is a thing of beauty forever"—or words to that

effect.

Next came a series of resistors, or vice versa. Got those as a going away gift from a friend when we moved to California from New York. In the hundreds of times I've needed resistors since then I've never been able to find anything even close to the sought after value in the whole batch, so might just as well get rid of them.

All sorts of goodies followed in quick succession. Some diodes I got because I thought I could use the little plastic boxes they came in; couple of transformers, one of which was painted forest green to serve a better purpose as a door stop; tube sockets; my original hand key; the first 807 to go flat in my fondly-remembered Harvey-Well TBS50D. There was still some room on the ebony breadboard so I covered some of the space with some of my old K2KEH (my New York call) QSL's I'd saved for sentimental reasons and in the remaining space I mounted some SO 239's because they looked so pretty.

That's when the XYL marched in. Neither of us said a word but I started hearing a sizzling sound and that puzzled me because I hadn't turned on the B plus. The sizzle got louder, like tube noise only more so. It stopped only when she spoke:

"What's that?" said she.

"I'm not sure," said I, "but I think it may work out to be a miniaturized digital computer. Maybe in color."

"Is that my good bread board?" said she.

"It is," said I.

"You mean it was," said she.

"Yes," said I, and now I was getting that little scary feeling that says to all married men, "Look out, chum, there's domestic QRM upcoming."

"Isn't silver an excellent conductor?" said she—a little out of sequence I thought.

"Yes."

"Then why don't you take the good sterling," she said sweetly, "and hook up all the components with it. And you can use the good china for insulators, while you're at it."

And she walked out of the room. The sizzle was S9 plus.

She came back home from mother's a few days later. She had only one suggestion for me. "If you're going to breadboard something from scratch," she said, "why don't you really start from scratch? Like go out to begin with and get me a brand new bread board."

So I went out and bought an axe and now I'm looking for an ebony tree. Africa, anyone?

A pox on your junk box.

. . . WA6JNI

NEW 17TH EDITION
of the world-famous
RADIO HANDBOOK



- Most comprehensive how-to-build-it source
- Problem-solver for designers & builders

Completely revised and enlarged by William I. Orr, W6SAI. This is the comprehensive communications manual which is the industry standard for electronic engineers, technicians, and advanced radio amateurs. Explains in authoritative detail how to design and build all types of radio communications equipment.

LATEST HOW-TO-BUILD DATA

The new 17th Edition of the RADIO HANDBOOK presents design data on the latest amplifiers, transmitters, receivers, and transceivers. Includes greatly enlarged sections on single-sideband equipment and design, and semiconductors. Gives extended coverage to r-f amplifiers, special vacuum-tube circuits, and computers. All equipment described is of modern design, free of TVI-producing problems.

THOROUGHLY REVISED & UPDATED

Provides a complete understanding of the theory and construction of all modern circuitry, semiconductors, antennas, power supplies; full data on workshop practice, test equipment, radio math and calculations. Includes aspects of the industrial and military electronics fields of special interest to the engineer and advanced amateur. The 17th Edition of the RADIO HANDBOOK provides the broadest coverage in the field—complete information on building and operating a comprehensive variety of high-performance equipment. All data is clearly indexed. 832 pages; 6½ x 9¼"; hardbound. Invaluable for amateurs, electronic engineers, and designers.

SAVE SPECIAL PRE-PUBLICATION PRICE!

EE166, New 17th Ed. RADIO HANDBOOK. Special Pre-Publication price until Sept. 30, 1966, Only..... **\$10.95**
(After Sept. 30, 1966, regular price will be \$12.95)

Available also in Spanish and Italian editions.

Order from your electronic parts distributor or send coupon below.



EDITORS and ENGINEERS, Ltd.

P.O. Box 68003, New Augusta, Ind., Dept. 73E-9

Ship me EE166, the new 17th Edition RADIO HANDBOOK at the special pre-publication price of \$10.95.

\$_____ enclosed. Check Money Order

Name _____

Address _____

City _____ State _____ Zip _____

Electronic Drafting for the Ham Writer

*Even if you aren't a ham writer
you'll find this article interesting.*

It is an indisputable fact that successful communication, in even the broadest sense, is dependent upon three vital factors which are coincidentally related to amateur radio.

The first of these factors is the transmitter, or a person who speaks, writes, or in some way seeks to communicate. Here we may make an analogy to 73's authors, who are among the finest in amateur radio writing circles.

The second requirement is the receiver, or listener, or in the context of this article, the reader. Most of us read an amateur radio pub-

lication for the express purpose of educating ourselves in one way or another. No problem here, unless. . . .


You guessed it! Unless we use the wrong *third* factor, the *code*. It is essential that this code be a language which is mutually understood.

Lest I be set upon by a battalion of irate 73 authors and hanged from the corner of my drawing board, let me hasten to explain that the primary purpose of this article is to explain the standard drafting symbols and methods used in 73 and many other electronics magazines such as 73. A welcome by-product would be the successful stimulation of any potentially good but currently latent writers who hesitate to submit articles because they fear their drafting ability is not up to par.

Many of us, I am sure, read 73 and build according to the schematics without giving much thought to what goes on behind the scenes. We probably concern ourselves but little about the fact that the author's original sketches might have looked somewhat different from the drawings which appeared in the magazine. This is common, the reason being that the staff artist is governed by strict policies of the magazine concerning space and shape requirements, and standardization of drafting procedures.

So, now that we agree that our drawings are going to appear in 73 in accordance with a standard format, come TVI or high water, why make the artist work so hard for his money?

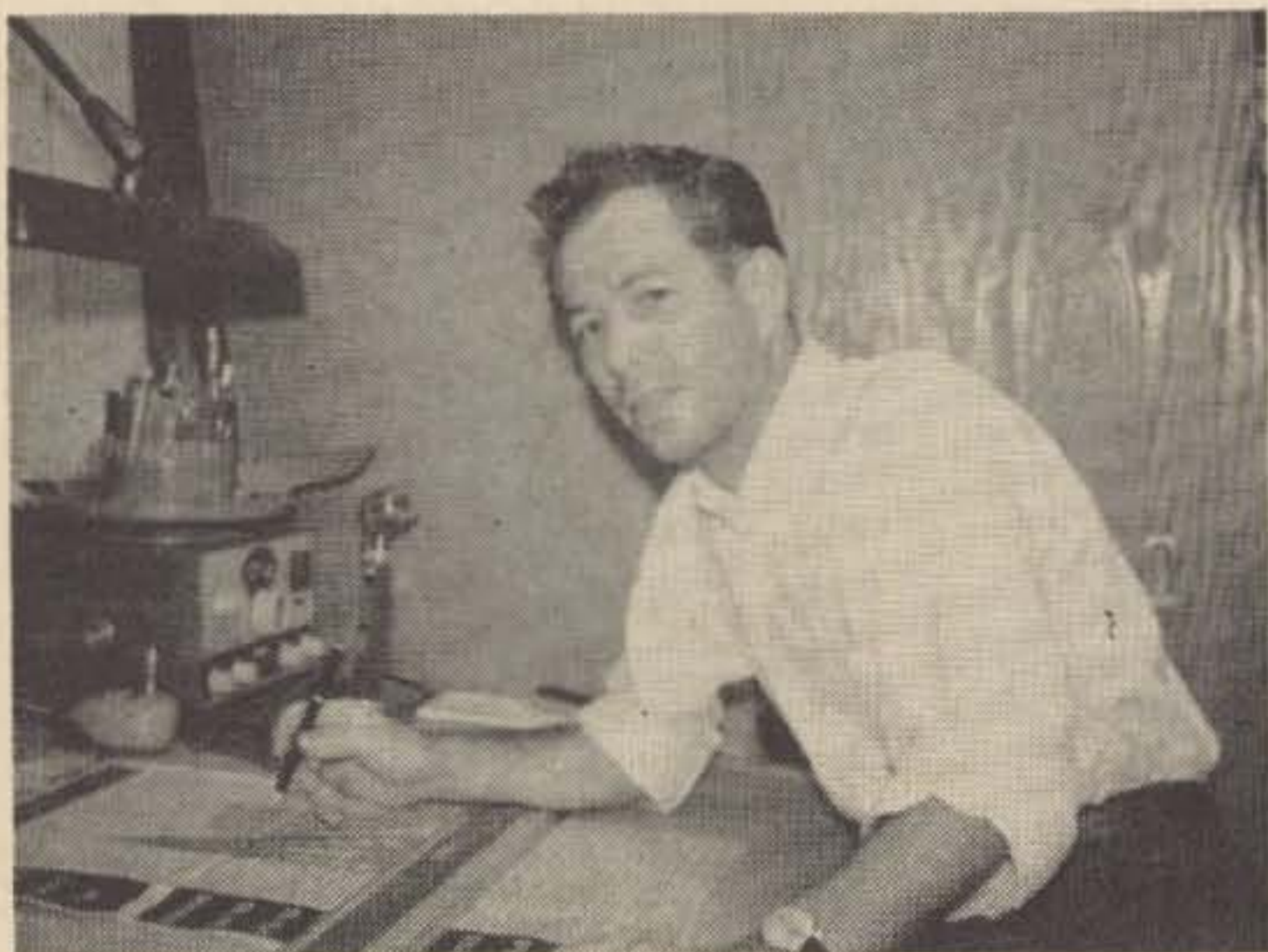Included with this article is a chart which describes most of the symbols and abbrevia-
(Text continued on page 76.)



Scottie is 73's main draftsman. He's the one who gets the credit for most of the excellent drawings we publish. Long time readers of 73 will notice the great improvement in layout, consistency, attractiveness, completeness and accuracy in Scottie's work over earlier drawings. Aside from his work for 73, Scottie is a design draftsman for the Security Fire Door Company of St. Louis.

NEW **SWAN-350** TRANSCEIVER



5 BANDS
400 WATTS
\$420

**ONLY 10% DOWN
OR TRADE-IN EQUIPMENT**

**AT EDWARDS YOU
GET:**


BIG TRADE-INS
NO FINANCE CHARGE if
balance paid within
90 days

OTHER FEATURES

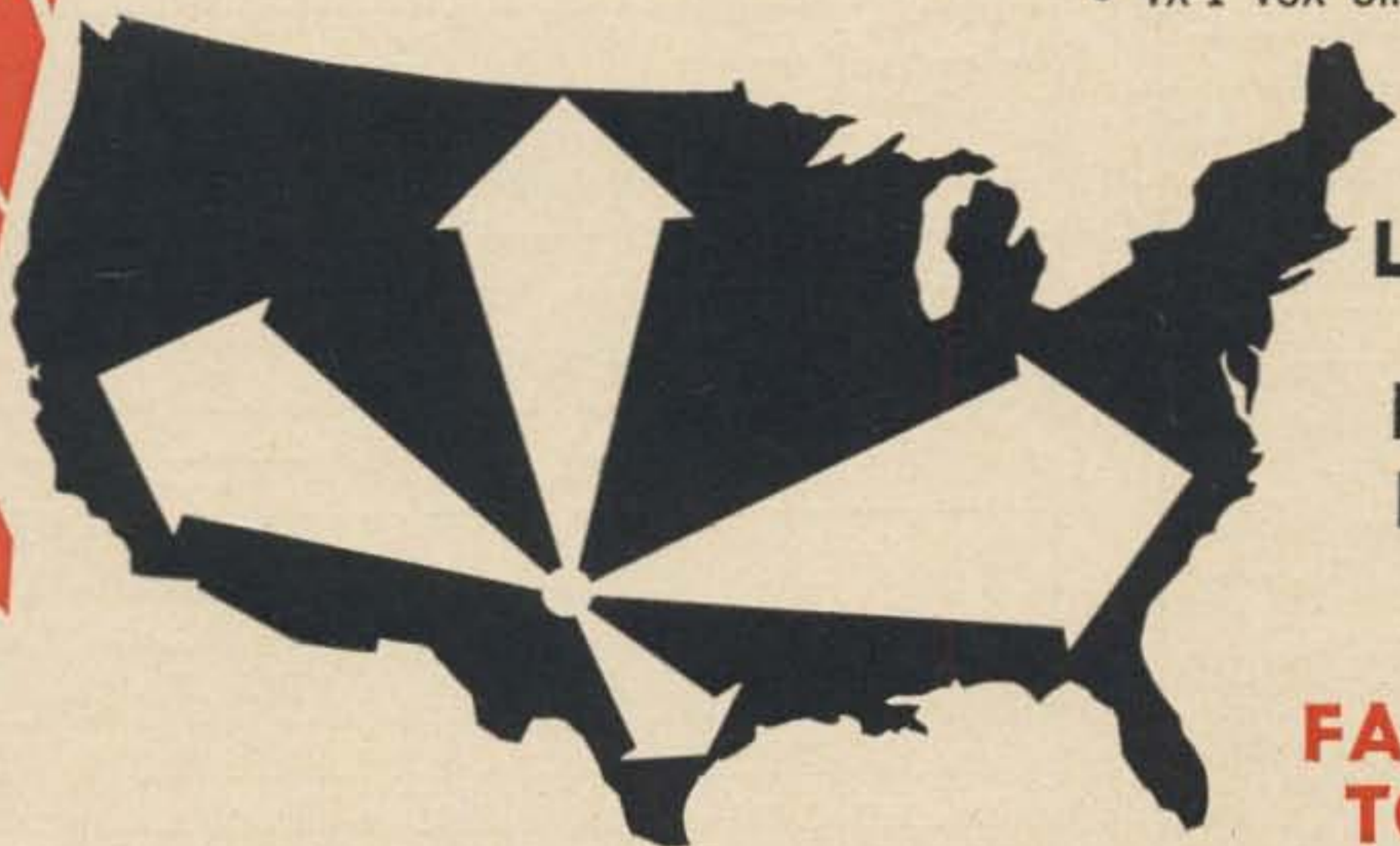- 3.5 - 4.0 mc, 7.0 - 7.5 mc, 13.85 - 14.35 mc, 21.0 - 21.5 mc, 28.5 - 29.0 mc (10 meter full coverage kit available).
- Transistorized VFO.
- Crystal lattice filter.
- ALC . . . AGC . . . S-Meter.
- 5½ in. high, 13 in. wide, 11 in. deep.
- 400 watts SSB input.
- Lower sideband on 80M and 40M. Upper sideband on 20M, 15M, and 10M. (Opposite sideband kit available.)

ACCESSORIES:

- SW-117XC AC P/S \$ 95
- SW-14-117 DC P/S 130
- SW-14X DC Module 65
- VX-1 VOX Unit 35



**A
LARGE SELECTION
OF
RECONDITIONED
EQUIPMENT . . .
INQUIRE.**

**FASTEST DELIVERY
TO ALL POINTS!**

EDWARDS
ELECTRONICS

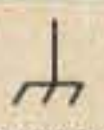

TELEPHONE POrter 2-8759 / 1320 19th ST. / LUBBOCK, TEXAS 79401

ANTENNA





NORMALLY USED IN BLOCK DIAGRAMS, BUT MAY BE USED IN ANY SCHEMATIC WHERE ANTENNA IS CONNECTED DIRECTLY TO CIRCUIT WITHOUT BENEFIT OF RF CONNECTOR

GROUND CONNECTIONS

CHASSIS GROUND SYMBOL IS NORMALLY THE ONLY TYPE USED IN SCHEMATICS
EACH GROUNDED CIRCUIT COMPONENT WILL BE SHOWN CONNECTED TO AN INDIVIDUAL CHASSIS GROUND, UNLESS A COMMON GROUND BUS IS ESSENTIAL TO PROPER CIRCUIT OPERATION


BATTERY

DO NOT FORGET TO INDICATE VOLTAGE AND POLARITY




SINGLE CELL MORE THAN ONE CELL

HEADSET






NORMALLY USED IN BLOCK DIAGRAMS, BUT MAY BE USED IN ANY SCHEMATIC WHERE CONNECTED DIRECTLY INTO CIRCUIT WITHOUT PHONE PLUG
INDICATE IMPEDANCE IF VALUE IS CRITICAL

CAPACITORS




BASIC ELECTROLYTIC VARIABLE

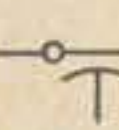NOTE THAT CURVED PORTION OF SYMBOL ALWAYS DESIGNATES OUTSIDE FOIL OF FIXED CAPACITORS (EXCEPT ELECTROLYTICS, WHERE IT INDICATES THE NEGATIVE TERMINAL)

FEEDTHRU SPLIT-STATOR GANGED

THE CURVED PORTION IN THE CASE OF A VARIABLE WILL INDICATE THE MOVABLE PART

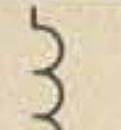

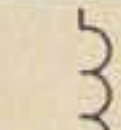




DIFFERENTIAL VACUUM VAC. VAR.

* INDICATE POLARITY, AND VALUE IN μF

WHEN OTHER THAN ELECTROLYTIC, VALUES ARE ASSUMED TO BE pF WHEN 1 OR GREATER, AND μF WHEN LESS THAN 1




INDUCTORS

BASIC TAPPED ADJ. TAP

INCLUDE ALL NECESSARY DATA INCLUDING ANY OF FOLLOWING INFORMATION WHICH IS APPLICABLE:




WIRE SIZE & TYPE
COIL OR FORM O.D. OR I.D.
NUMBER OF TURNS AND/OR LENGTH
MANUFACTURER'S PART NUMBER
TAP POSITION ABOVE COLD END

ADJ. SLUG * FILTER CHOKE RF CHOKE

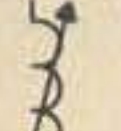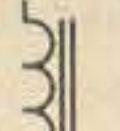
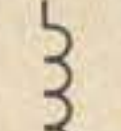
* FERRITE CORE WILL BE ASSUMED UNLESS BRASS IS SPECIFIED. INDICATE TYPE OF FERRITE, IF CRITICAL

CONDUCTORS

BASIC CONNECTED CROSSED

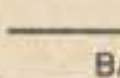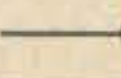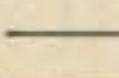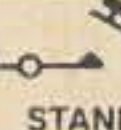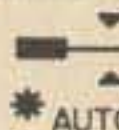
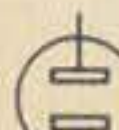
KEYS




STANDARD * AUTOMATIC

* BE SURE TO DESIGNATE "DIT" & "DAH" CONTACTS



CONNECTORS

MALE FEMALE AC LINE

MALE FEMALE BASIC TERMINALS

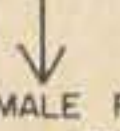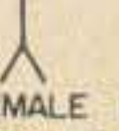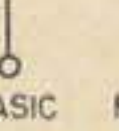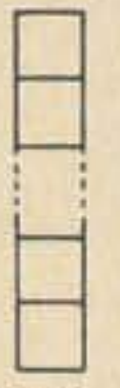





FIXED MULTIPLE * MOVABLE MULTIPLE *

SHOULD NONE OF THE SYMBOLS DESCRIBED HERE SEEM TO MATCH YOUR SITUATION, DESCRIBE THE CONNECTOR AND/OR LIST THE MANUFACTURER'S PART NUMBER


* FOR ANY COAXIAL-TYPE CONNECTOR, SUCH AS RF, MICROPHONE, PHONO, ETC.

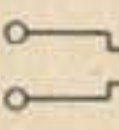* NUMBER THE BLOCKS TO CORRESPOND TO TERMINAL MARKINGS, WHEN APPROPRIATE

PHONE PLUG PHONE JACK COAXIAL *


LAMPS

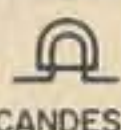


INCANDESCENT NEON


INDICATE MANUFACTURER'S PART NUMBER AND/OR VOLTAGE & CURRENT RATING

LOUDSPEAKER




INDICATE VOICE COIL IMPEDANCE & POWER RATING, ETC., WHEN CRITICAL

METERS




* INDICATE TYPE OF METER HERE (μA , mA , V , ETC.)
* INDICATE SCALE RANGE HERE (0-1, 0-50, ETC.)
DON'T FORGET TO INDICATE PROPER POLARITY

MICROPHONE

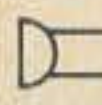

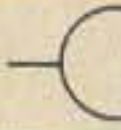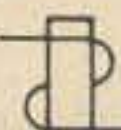
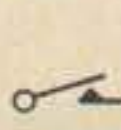

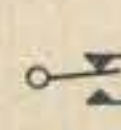
NORMALLY USED IN BLOCK DIAGRAMS BUT MAY BE USED IN SCHEMATIC WHEN WIRED DIRECTLY INTO CIRCUIT WITHOUT CONNECTOR
INDICATE TYPE (CARBON, XTAL, ETC.)

MOTOR



LABEL AS MOTOR, FAN MOTOR, ETC.
INDICATE OPERATING VOLTAGE & CURRENT AND/OR MANUFACTURER'S PART NUMBER

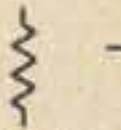

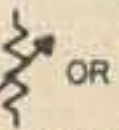

RELAYS

RELAY COIL SPST DPST SPDT CONTACT CONFIGURATIONS

SPECIFY COIL VOLTAGE, RESISTANCE, ETC., AND/OR MANUFACTURER'S PART NUMBER
CONTACT CONFIGURATIONS SHOWN ARE BASIC AND MAY BE EXPANDED


RESISTORS

FIXED TAPPED ADJUSTABLE TEMP. COMP.





INDICATE VALUE, IN OHMS (Ω), KILOHMS (k), OR MEGOHMS (M), AND/OR MANUFACTURER'S PART NUMBER.
1/2 W 10% IS ASSUMED UNLESS OTHERWISE NOTED

CRYSTAL



ALWAYS INDICATE CRYSTAL FREQUENCY (IN kHz, MHz, ETC.)




ELECTRON TUBES

DIODE TRIODE TETRODE PENTODE


ALWAYS LABEL ELEMENTS WITH TUBE PIN NUMBERS

REFER TO TUBE MANUAL FOR DATA ON INDIVIDUAL TUBE TYPES

PENTAGRID VOLTAGE REGULATOR EXAMPLE OF MULTIPLE-SECTION TUBE

* FILAMENTS OR HEATERS (WITH THE EXCEPTION OF DIRECTLY-HEATED CATHODES) SHOULD BE SHOWN EXTERNAL TO TUBE CIRCLE, AND PREFERABLY IN THE POWER SUPPLY








CATHODE RAY

PLATE ---
GRID ---
CATHODE ---
* HEATER (FILAMENT) ---

DEFLECTION PLATE
GAS FILLED
COLD CATHODE


SEMICONDUCTOR DIODES

BASIC ZENER VARACTOR SYMMETRICAL ZENER P-I-N





INDICATE MANUFACTURER'S PART NUMBER AND/OR APPROPRIATE RATINGS
REFER TO MANUALS FOR SYMBOLS NOT SHOWN

FUSE

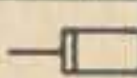

INDICATE CURRENT, VOLTAGE RATINGS, AND SLO-BLO, ETC., AS APPROPRIATE

ELECTRONIC SYMBOLS

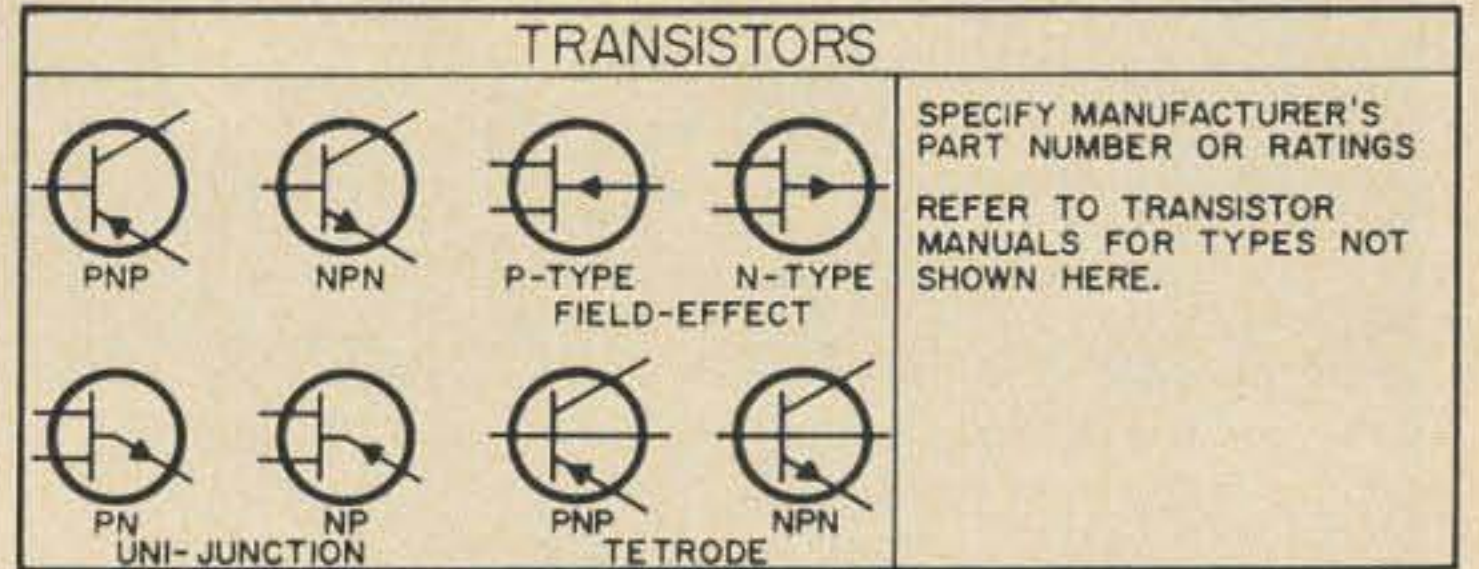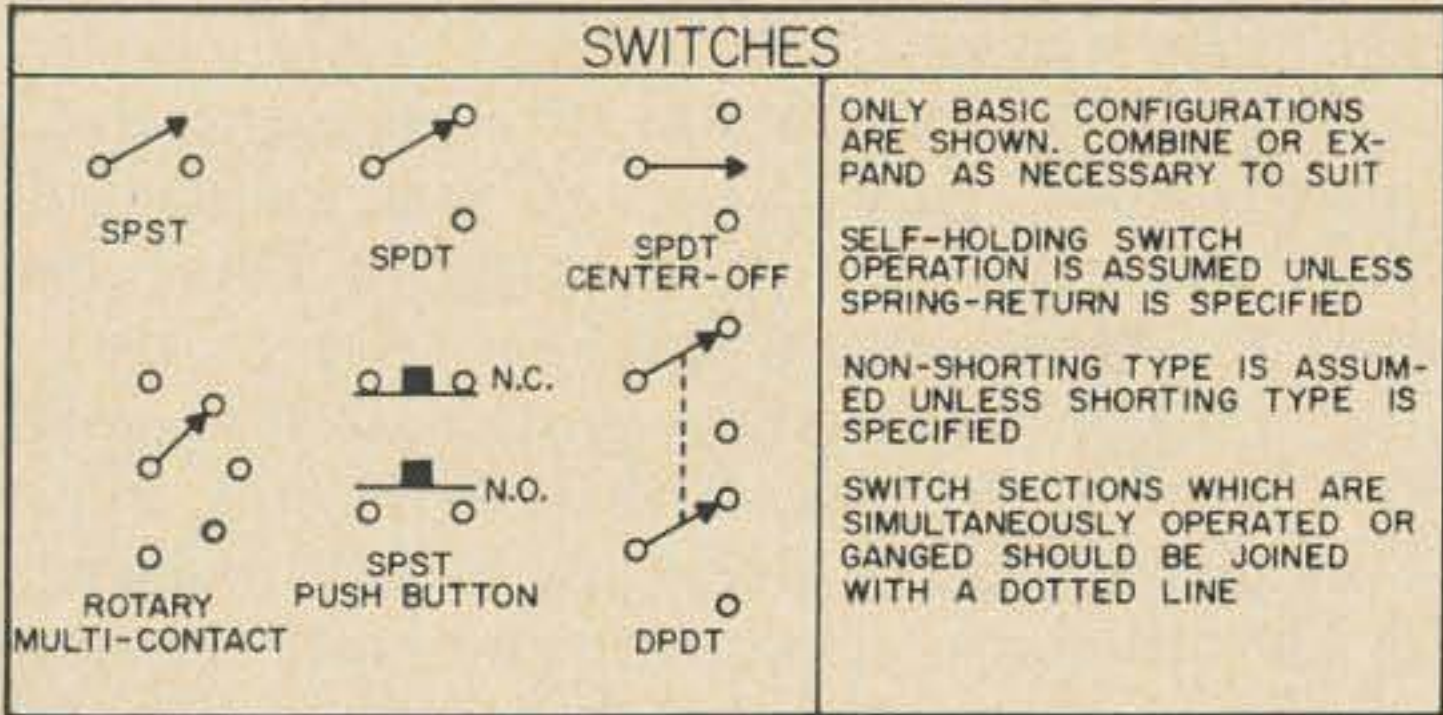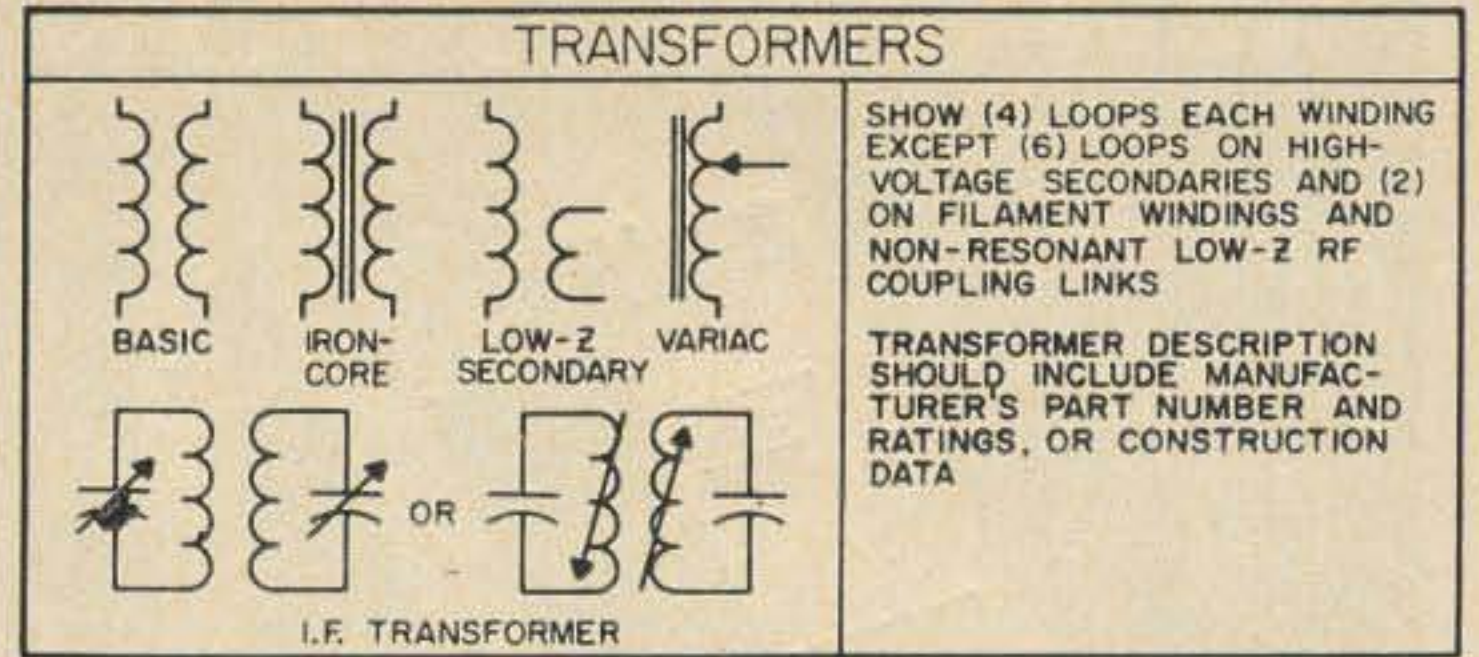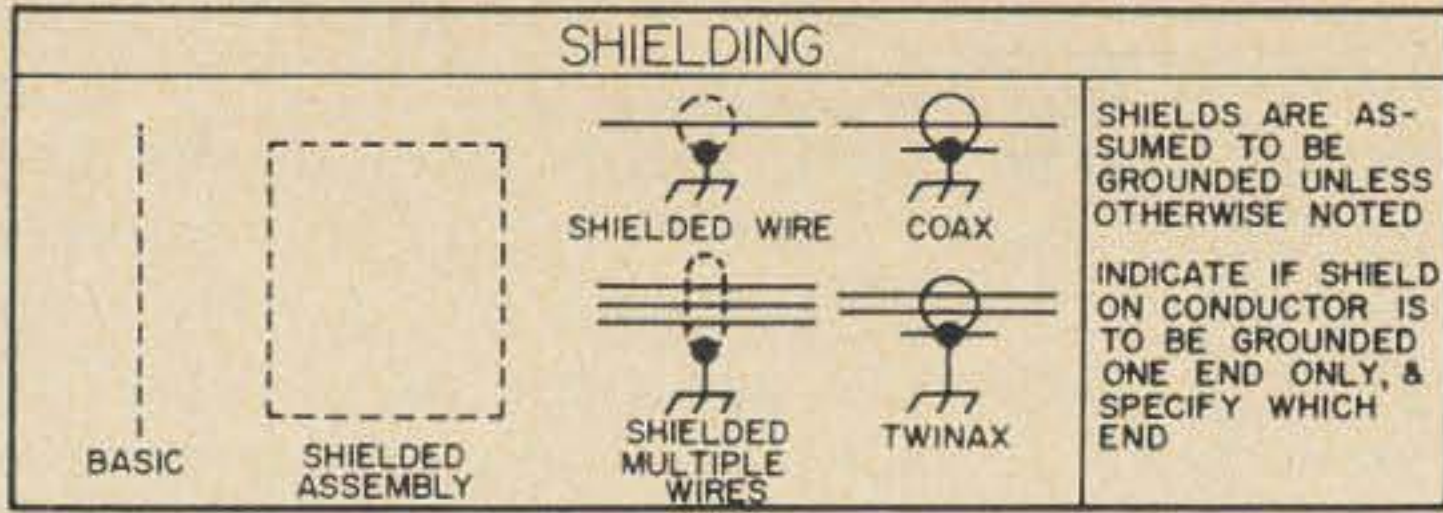

ELECTRONIC ABBREVIATIONS (AS USED ON DRAWINGS AND SCHEMATICS)

NOMENCLATURE	ABBREVIATION(S)
ALTERNATING CURRENT	AC
AMPERE	A
AMPLIFIER	AMP
AMPLITUDE MODULATION	AM
ANTENNA	ANT
AUDIO FREQUENCY	AF
AUTOMATIC FREQUENCY CONTROL	AFC
AUTOMATIC GAIN CONTROL	AGC
AUTOMATIC VOLUME CONTROL	AVC
BATTERY	B
BEAT FREQUENCY OSCILLATOR	BFO
BROADCAST	BC
CAPACITANCE, CAPACITOR	C
CONTINUOUS WAVE	CW
CRYSTAL	X, XTAL
CURRENT	I
DECIBEL	dB
DIODE, SEMICONDUCTOR (ALL TYPES)	D
DIRECT CURRENT	DC
DOUBLE COTTON COVERED	D.C.C.
DOUBLE POLE DOUBLE THROW	DPDT
DOUBLE POLE SINGLE THROW	DPST
DOUBLE SILK COVERED	D.S.C.
ELECTRON TUBE (ALL TYPES)	V
ENAMEL COVERED	ENAM
FILAMENT	FIL
FREQUENCY	FREQ, f
FREQUENCY MODULATION	FM
FUSE	F
GROUND	GND
HENRY	H
HERTZ (CYCLES PER SECOND)	Hz
IMPEDANCE	Z
INDUCTANCE, INDUCTOR	L
INSIDE DIAMETER	I.D.
INTERMEDIATE FREQUENCY	I.F.
JACK	J
KILOHERTZ (KILOCYCLES PER SECOND)	kHz
KILOHM	k, k Ω
KILOVOLT	kV
KILOWATT	kW
LAMP	I
LOUDSPEAKER	SPKR
MEGAHERTZ (MEGACYCLES PER SECOND)	MHz
MEGOHM	M, M Ω
METER	M
MICROAMPERE	μ A
MICROFARAD	μ F
MICROHENRY	μ H

NOMENCLATURE	ABBREVIATION(S)
MICROPHONE	MIC
MICROVOLT	μ V
MICROWATT	μ W
MILLIAMPERE	mA
MILLIHENRY	mH
MILLIVOLT	mV
MILLIWATT	mW
NEGATIVE (POLARITY)	-, NEG
NORMALLY CLOSED	NC
NORMALLY OPEN	NO
OHM	Ω
OSCILLATOR	OSC
OUTSIDE DIAMETER	O.D.
PICOFARAD	pF
PLUG	P
POSITIVE (POLARITY)	+, POS
POWER AMPLIFIER	PA
PRIMARY	PRI
PUSHBUTTON	PB
RADIO FREQUENCY	RF
RADIO FREQUENCY CHOKE	RFC
RECEIVE	REC
RECEIVER	RCVR
RELAY	K
RESISTANCE, RESISTOR (ALL TYPES)	R
ROOT MEAN SQUARE	RMS
SECONDARY	SEC
SHORTWAVE	SW
SINGLE COTTON COVERED	S.C.C.
SINGLE POLE DOUBLE THROW	SPDT
SINGLE POLE SINGLE THROW	SPST
SINGLE SILK COVERED	S.S.C.
SWITCH	S
TIME	t
TRANSFORMER	XFMR, T
TRANSISTOR (ALL TYPES)	Q
TRANSMIT	XMIT
TRANSMITTER	XMTR
ULTRA HIGH FREQUENCY	UHF
VACUUM TUBE VOLTMETER	VTVM
VERY HIGH FREQUENCY	VHF
VOLT OHM METER	VOM
VOLT, VOLTS	V
VOLTAGE	E
WATT	W
WAVELENGTH	λ

NEW callbook

**HOT OFF
THE
PRESS!**



**Over 60% of listings
changed in only a year!**

- Great Circle Bearings
 - Great Circle Charts
 - Prefixes by Countries
 - "Q" and "Z" Signals
 - World Time Chart
 - Int'l. Postal Rates
- United States Listings... \$5.00**
DX Listings..... 3.25

See your favorite dealer or order direct (add 25¢ for mailing)

RADIO AMATEURS REFERENCE LIBRARY OF MAPS — ORDER YOUR SET TODAY!



WORLD PREFIX MAP—Full color, 42" x 29", shows prefixes on each country... DX zones, time zones, cities, cross referenced tables.....postpaid **\$1.00**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD—from the center of the United States! Full color, 29" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. postpaid **\$1.00**

UNITED STATES MAP—All 50 States with call areas, prefixes, DX and time zones, FCC frequency allocation chart. Plus interesting information on all 50 States. full color, 29" x 17".....postpaid **50¢**

WORLD ATLAS—Only Atlas compiled for amateurs. Polar projection, six continents, prefixes on each country... full color, 16 pages.....postpaid **\$1.50**

Complete reference library of maps—set of 4 as listed above.....postpaid **\$2.50**
See your favorite dealer or order direct.

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR



callbook INC.

Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639

(Continued from page 72)

tions which have been found acceptable to the editor of 73. Relative information has been included in the chart, rather than in the text, for convenience. Should none of this information seem to suit your situation, merely make your description as complete as possible. Always bear in mind that you are seeking to communicate with the artist, and ultimately, with the reader.

Hopefully, we are still in agreement at this point. Now, let's draw all schematics with input at left and output at right. Don't hesitate to direct an explanatory note or two to the artist if you think a particular item might not be clear to him. This is especially important in the case of pictorials, where a drawing might otherwise appear in print embarrassingly unlike a photograph of the same object. Use templates if you like, but free-hand is just as good as long as it is legible. Try to include most of the information on the schematics, thereby keeping the parts list to a minimum. When finished with your drawings, inspect for errors or omissions.

If you are an old hand at writing in the electronics field, perhaps you are one of the many who already adhere fastidiously to the use of standard symbols and layouts. If not, won't you please bend a little? It *could* prevent the artist from accidentally blowing an otherwise excellent article.

Those of you who have originated interesting and useful circuits, and have never submitted them for publication, are cheating amateur radio out of the benefit of your knowledge, and yourself out of a couple of bucks. I can't tell you how to write the article because that is way out of my line. I can tell you, however, that a pencil, paper, and an unyielding determination to use standard symbols, abbreviations, and format, will satisfy the drafting requirement. Don't forget to retain a copy of everything, for reference, in case the editor wants to contact you about a point or two.

In conclusion, may I say that the objectives of this article are intended to be neither in defiance of nor in compliance with the policies of publications other than 73 magazine. The symbols and abbreviations which appear in the chart have been proven to be simple to execute, and adequately descriptive.

... KØEFC

References

- A.R.R.L. "The Radio Amateur's Handbook," 1966 Edition, page 516
- Howard W. Sams "Handbook of Electronic Tables & Formulas," 1962, pp. 82-94

Live Better Electronically With

LAFAYETTE RADIO ELECTRONICS

Value Leader in Amateur Gear Since 1923

LAFAYETTE 400 SERIES 6 AND 10 METER AMATEUR TRANSCEIVERS

BUILT-IN VFO

COMPLETELY WIRED




149⁹⁵

- 2E26 Final—20 Watts DC Input
- Tuned Nuvistor RF Amplifier
- Dual Conversion
 - Built-In 117 VAC & 12 VDC Power Supplies
 - Built-In Low Pass TVI Filter

99-2575WX—Model HA-410 for 28-29.7 MC

99-2579WX—Model HA-460 for 50-52 MC

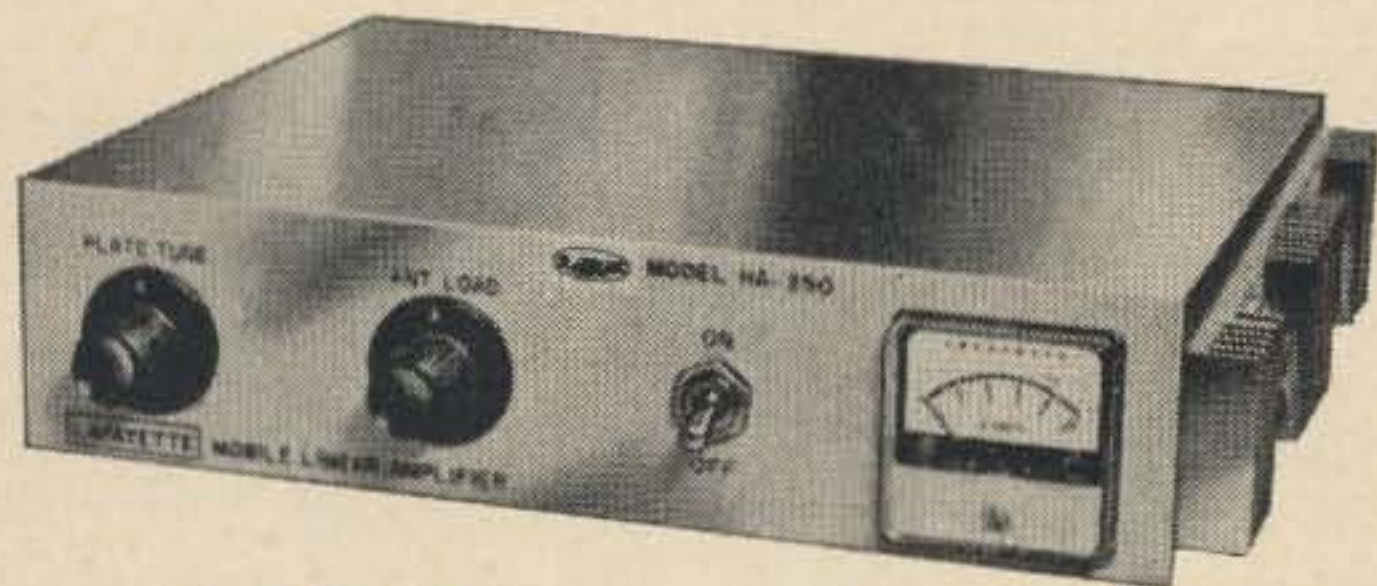LAFAYETTE 100 WATT PEP MOBILE LINEAR AMPLIFIER MODEL HA-250



79⁹⁵

40-0106WX

- Covers 20 to 54 MC—Perfect for 6 Meters
- Operates All Modes—AM, FM, CW, SSB, DSB
- No External Switching Circuit Required
- Efficient Built-in 12-volt Power Supply
- Small . . . Compact . . . Only 2-inches High

See June 1966 QST For Details

MODEL HA-350 80-10 METER SSB/AM/CW AMATEUR RECEIVER



HA-94 Speaker Mate

Model HA-350

99-2571 129⁹⁵

5 HAM BANDS PLUS WWV

3.5 — 4.0Mc	21.0 — 21.5Mc
7.0 — 7.5Mc	28.0 — 29.7Mc
14.0 — 14.5Mc	WWV at 15Mc

- Mechanical Filter for Exceptional Selectivity
- Complete with Crystals for 80, 40, 20, 15 and 10 Meters
- Product Detector—Selectable Upper Lower Sideband Reception
- 100 KC Crystal Calibrator and Crystal BFO
- Dual Conversion with Automatic Noise Limiter

SALE! 129⁹⁵

99-2524 WX

FREE!

Over 500 Pages

Featuring Everything in Electronics for

- HOME • INDUSTRY
- LABORATORY

from "World's Hi-Fi & Electronics Center"

111 Jericho Turnpike
Syosset, L. I., New York 11791



LAFAYETTE 1967 CATALOG 670

LAFAYETTE Radio ELECTRONICS
Dept. 73-6 P.O. Box 10
Syosset, L.I., N.Y. 11791

Send me the FREE 1967 Lafayette Catalog 670 73-6

Name

Address

City

State Zip



The Lafayette HA-650 Six Meter Transceiver

A battery-operated portable or fixed transceiver

Most hams would like to have a completely portable transceiver. Some want to be prepared for emergencies. Some like to mountaintop. Some just like the idea of having a completely independent rig to carry around for special events or picnics. The Lafayette HA-650 is perfect for these uses. It is small, light, has a sensitive receiver, and adequate power for most of these uses. Let's take a quick look at what's in it:

The receiver uses five modern silicon transistors in a single conversion superheterodyne. The rf amplifier is protected by a diode against nearby transmitters, and the oscillator is zener diode stabilized. Two *if* stages at 1650 kHz furnish plenty of amplification. A noise limiter is wired in the circuit and the AGC has a squelch-like action: when no signals are being received, there's very little output from the speaker until a signal is received. There's plenty of audio for use except in very noisy locations when earphones would probably be worthwhile. A spot switch lets you find your operating frequency.

The transmitter uses 8 MHz crystals and sockets and a switch are provided for six crystals. Five silicon transistors are used in the transmitter and the circuit has plenty of filtering and selective circuits to prevent TVI. Both the driver and final are modulated for full modulation. There were many excellent comments on the audio. It has a very clean, communications-shaped quality and gets through interference very well.

The HA-650 operates from 12 volts or so. The package includes space for eight flashlight batteries, which seem to last quite a while, or you can install the rig in your car (positive or negative ground) using the mobile mount, power cord and instructions provided. You can also buy an AC adapter from Lafayette.

A whip antenna is built into the transceiver, and it is convenient to use for walking-portable use with the nice leather carrying case that comes with the rig. As this area is horizontally polarized, results with the whip weren't particularly dramatic, but stations 40 or 50 miles away were worked from a good location. Using the HA-650 with a beam or dipole made from a couple of Lafayette 58 inch telescoping whips is another story. We worked a number of stations 150 miles away from Pack Monadnock. Reports were S9 and better and everyone commented on the excellent modulation. The receiver stands up well to strong stations unless they are very close, when some cross-modulation becomes evident. It's not too serious though.

The instruction book is satisfactory in comparison with many other equipment manuals. It answers most of the questions you're liable to have about installing or using the rig, and also gives alignment instructions and a large schematic. Someone who isn't very familiar with semiconductors isn't going to enjoy servicing the transceiver, but otherwise it shouldn't be too bad—if service is ever needed, since everything seems to be well made and the parts

Lafayette HA-650 Specifications

Receiver

Sensitivity: better than 1 uV for 10 dB S/N ratio
 Selectivity: 6 dB down at =3 kHz, 40 dB at =8 kHz
 Image rejection: 55 dB
 Frequency range: 50-52 MHz
 Current drain: 80 mA

Transmitter

Input to final: 2½ watts
 Modulation: Class B, 100% capability
 Current drain: 400 mA maximum
 T-R switching: relay type
 Antenna output impedance: 50 ohms nominal

Miscellaneous

Power supply: 12 to 16 V dc
 Dimensions: 9½ W x 5½ H x 2¼ D.
 Weight: 9 pounds with battery
 Price: \$119.95

are conservatively rated. The driver and final transistors are made by Motorola, and the others would be easy to replace with standard American replacements if you had trouble finding the Japanese ones.

I was quite pleased with the HA-650. It's compact and well-made and offers excellent performance for its price. I think that anyone who buys or uses one will be very happy with it.

... WAICCH

Removing Excess Soldering Flux

Appearance of much otherwise good electronic work is quite frequently spoiled by excess soldering flux on connections, and by the dust that eventually accumulates on the residual flux.

Larger accumulations of natural and synthetic rosin can be removed by careful scraping, followed by use of a solvent on a cotton swab or a small brush. Good solvents, in order of increasing strength, are carbon tetrachloride, denatured alcohol, rubber cement thinner, type cleaner, and acetone. All should be used with caution, with adequate ventilation, and away from flames and hot objects. Carbon tetrachloride will not burn, but oxidizes to phosgene if it falls on a hot object, such as a soldering iron.


Do not use these solvents on plastics without a preliminary test. Some plastics soften on contact with acetone and similar substances.

... Donald Ives

DOW KEY COAXIAL RELAYS



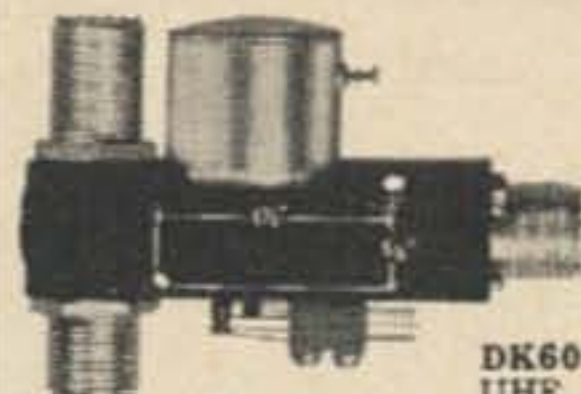
OUR SPECIALTY . . . Your No. 1 source for standard and special application units.



DK60 SERIES

HEAVY DUTY SPDT COAXIAL RELAYS

DK60 SERIES, AC or DC UHF connectors ----- from \$12.45

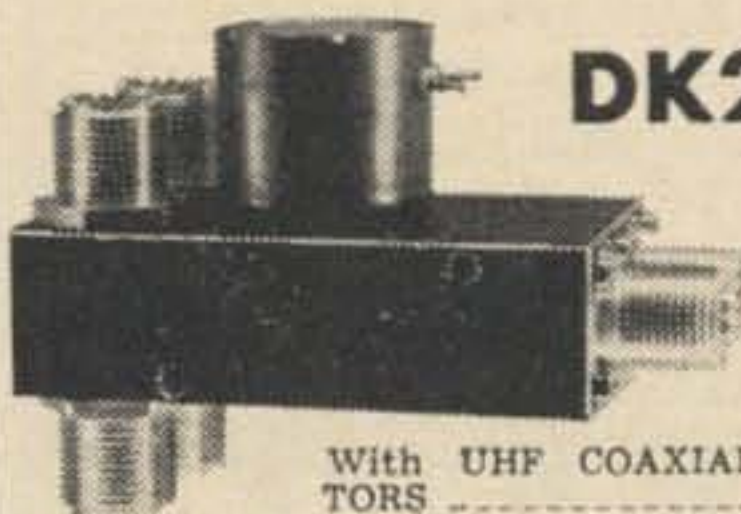

DK2-60 SERIES

A DPDT SWITCH for SWITCHING 2 COAXIAL LINES SIMULTANEOUSLY


With UHF COAXIAL CONNECTORS ----- from \$19.00 ea.



DK2-60B SERIES

A DPDT SWITCH INTERNALLY CONNECTED IN DE-ENERGIZED POSITION

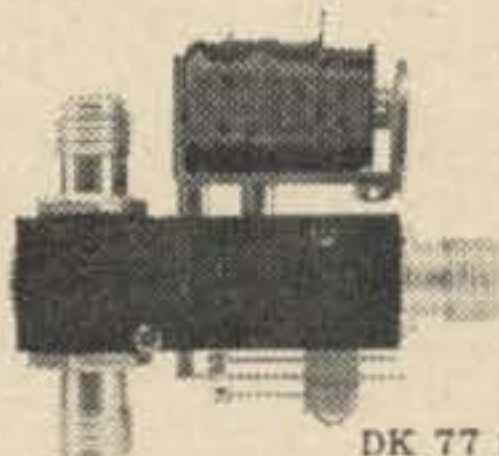
Available in all standard AC, DC voltages ----- from \$19.00 ea.



DK77 SERIES

MINIATURE, LOW COST 50 ohm SPDT COAXIAL RELAYS

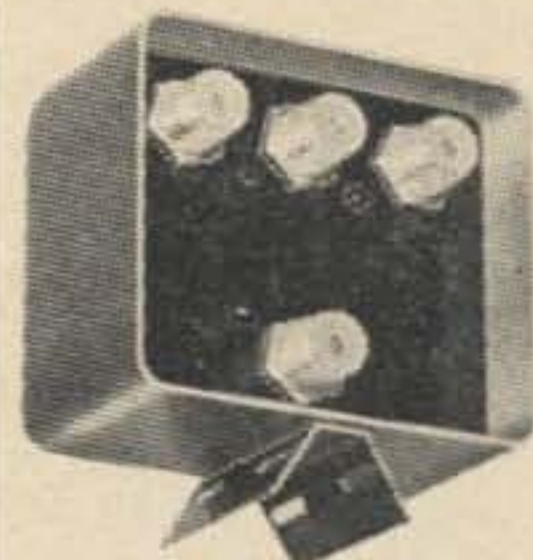
DK 77 relays available with phono, TNC and BNC coaxial connectors— from \$7.90 ea.



DK72 SERIES

1P3T COAXIAL RELAY FOR REMOTE SWITCHING of r.f. SOURCES

WITH UHF CONNECTORS \$22.95 ea.

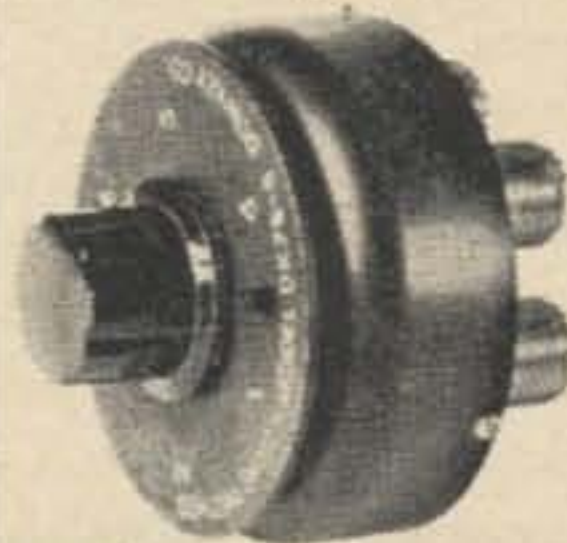

DK78 SERIES

NEW MANUAL COAXIAL SWITCHES (Not Wafer Switches)

Available: 1P2T, SP3T, 1P6T and crossover switch ----- from \$12.75 ea.

available at your distributor or write:

DOW-KEY CO.

Thief River Falls, Minnesota

"Your Friendly Supplier"

OFFERS

A SPECIAL



PL-259
STOCK NO. 259-34



SO-239
STOCK NO. 239-34

ONLY **34¢** EACH
IN LOTS OF 10 OR MORE



NEW! RG-8U Coaxial Cable
13¢ per foot

Minimum order 100 feet Stock No. 7328

For Prepaid Shipment Continental U. S.
Order by above Stock Numbers

ALSO—we can handle your antenna requirements! We stock ANTENNA SPECIALISTS, CUSH-CRAFT, HY-GAIN, MOSLEY, NEW-TRONICS, & WEBSTER—both fixed station & mobile, plus accessories.

"Write for Latest Used Equipment List"

Evans RADIO


P. O. BOX 312

CONCORD, N. H. 03301

FONE 603-225-3358

10 - 15 - 20 METER MONOBEAMS

FOR
MORE
DX PUNCH

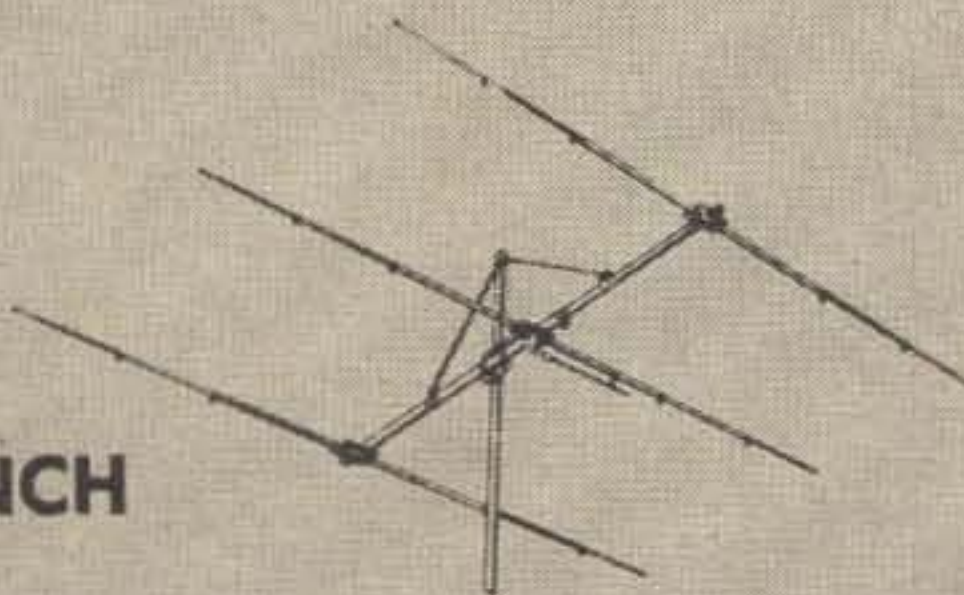

Cush Craft Monobeams combine superior electrical and mechanical features with the best quality materials and workmanship. They will provide reliable day to day amateur communications and that extra DX punch, when needed, for contest work or emergency communications.

A28-3	10 Meter, 3 Element, Boom 10'	\$31.95
A28-4	10 Meter, 4 Element, Boom 18'	42.95
A21-3	15 Meter, 3 Element, Boom 12'	39.95
A21-4	15 Meter, 4 Element, Boom 22'	59.95
A14-2	20 Meter, 2 Element, Boom 10'	49.95
A14-3	20 Meter, 3 Element, Boom 20'	77.50

SEE YOUR DEALER OR WRITE FOR CATALOG.

Cush Craft

621 HAYWARD STREET
MANCHESTER, N. H. 03103

(Continued from page 2)

too well, but they are important to DXers. I would say that a lot can be done to make our QSL's more interesting. I know I keep the better ones on the wall of my shack and I like to look up at them when I am working the fellow again. In the past I was gung ho for the card with an interesting design . . . the one that really stands out on the wall. Now I'm swinging to the idea that it is nice to have a picture of yourself, your shack, perhaps your house or even your town on the card.

On my card I have a picture of my mountain shack with all the towers and VHF beams. It makes quite an impression, apparently, because a number of DX stations have particularly mentioned looking at it. Just last night I worked 9L1TL and he said he had seen my card at 9L1HX's! The antennas and towers draw the gasps . . . no one has mentioned the little picture of me and my two Italian Greyhounds on the other side. Aha, that gives me an idea. I'll get out the Polaroid and take a picture of myself holding a gun to my head and print a caption, "Send me a QSL or else."

No DX station has any excuse for not QSL'ing any more. The institution of the QSL manager is well accepted and there are hundreds of fellows waiting to manage someone. Some managers even print up the cards, but this is asking a lot. All a DXer has to do is send in his logs to the manager and everything is done. I know that I much prefer to deal with a manager . . . then I know that I am going to get a QSL. I have too many blank places on my wall where fellows who have promised to QSL haven't. Probably the worst of all in this category has been FY7YL. Ernest earnestly promises QSL cards to one and all, but you virtually have to go to his shack to get one. Some fellows that have sent him ready-made cards waiting only his signature, complete with a self addressed envelope with the right postage in his own stamps haven't gotten a card. Fortunately Monique FG7XL has rescued us from this monster and is busy answering the cards for Ernest. The next time you talk to Ernest try to explain to him about the importance of QSLing . . . it will cost him nothing.

Weaker DX stations get completely covered up by the calling stations and we experience the complete stupidity of many minutes of calling with no one being able to hear whether the DX station is answering or not. It would seem to me that once a DX operator finds himself in this spot he should run not walk for some help and select one of the biggest

WHOLESALE

QSL'S

FREE! - 1966 CATALOG & SAMPLES

Thousands upon Thousands of Completely Satisfied Customers

Write Today To:

HAM WHOLESALE CARD CLUB

Dept. H

Box 461 - Lexington, N.C. 27292

signals to MC for him and collect the calls of those trying for a contact. I would further suggest that the MC spend as little time on the air as possible . . . first get everyone on the frequency familiar with what is happening, then ask for the spread out system of ET3AC and log calls. Then read off the calls to the DX station and insist that everyone shut up until called by the DX for a report.

By the way, while on the subject, let's come to an understanding . . . either you are working DX or you are rag chewing. Why try to mix the two? That doesn't mean you can't rag chew with DX, just don't start a rag chew when a DX op is obviously trying to give out reports to a number of stations. And this, to my mind, includes such time wasters as spelling out your city, name, or remarks to the effect that you are going to keep it short because a lot of others are waiting. Give the report, say your 73 and sign off and clear and get away. Make sense? And for heaven's sake don't start asking about QSL's . . . he knows that's what you want. If you don't know where to send the card wait until you are through and ask someone else that has been doing more listening and less talking.

. . . Wayne



Look! Here's an actual televised picture taken with the ATV RESEARCH Model XT-1A transistor camera.

FINALLY! A TRANSISTOR CAMERA KIT SELLING FOR UNDER \$150.00. THIS IS LESS THAN THE COST OF ANY OTHER NATIONALLY ADVERTISED CAMERA --EITHER TRANSISTOR OR TUBE!

BUT DON'T BE FOOLED INTO THINKING WE'VE SACRIFICED QUALITY FOR ECONOMY, WE HAVEN'T! IT'S PERFORMANCE WILL DELIGHT YOU.

Some of the outstanding features include:

- * Single piece printed circuit board for trouble-free assembly.
- * 6 stage, high gain, low noise video amp.
- * Regulated power supply.
- * Self-contained sync and blanking gen.
- * 26 semiconductor circuit (17 transistors, 8 silicon diodes and 1 zener).
- * RF or VIDEO outputs. No need to modify TV set, just connect to ant. terminals and tune to a blank channel between 2 and 6!
- * Extremely easy-to-understand 31 page step-by-step construction manual.

Space simply doesn't permit us to go into great detail, so if you're interested why not send for a copy of our new 1966 TV catalog? It's loaded with detailed info, block diagrams, actual televised pictures, plus a comprehensive listing of hard-to-find components, tube and transistor "starter" type kits, lenses, vidicons, etc. Please include 10¢ to cover postage.



MODEL XT-1A CAMERA KIT less vidicon.....\$149.50. Postpaid delivery anywhere in U.S.A. and Canada.

Introducing a NEW TRANSISTOR TV CAMERA KIT

PERFECT FOR HAMS, EXPERIMENTERS, & LOW BUDGET INDUSTRIAL APPLICATIONS.


GUARANTEED TO PUT "ZIP" IN YOUR HOBBY!



ATV RESEARCH

Post Office Box 396-S

South Sioux City, Nebraska 68776

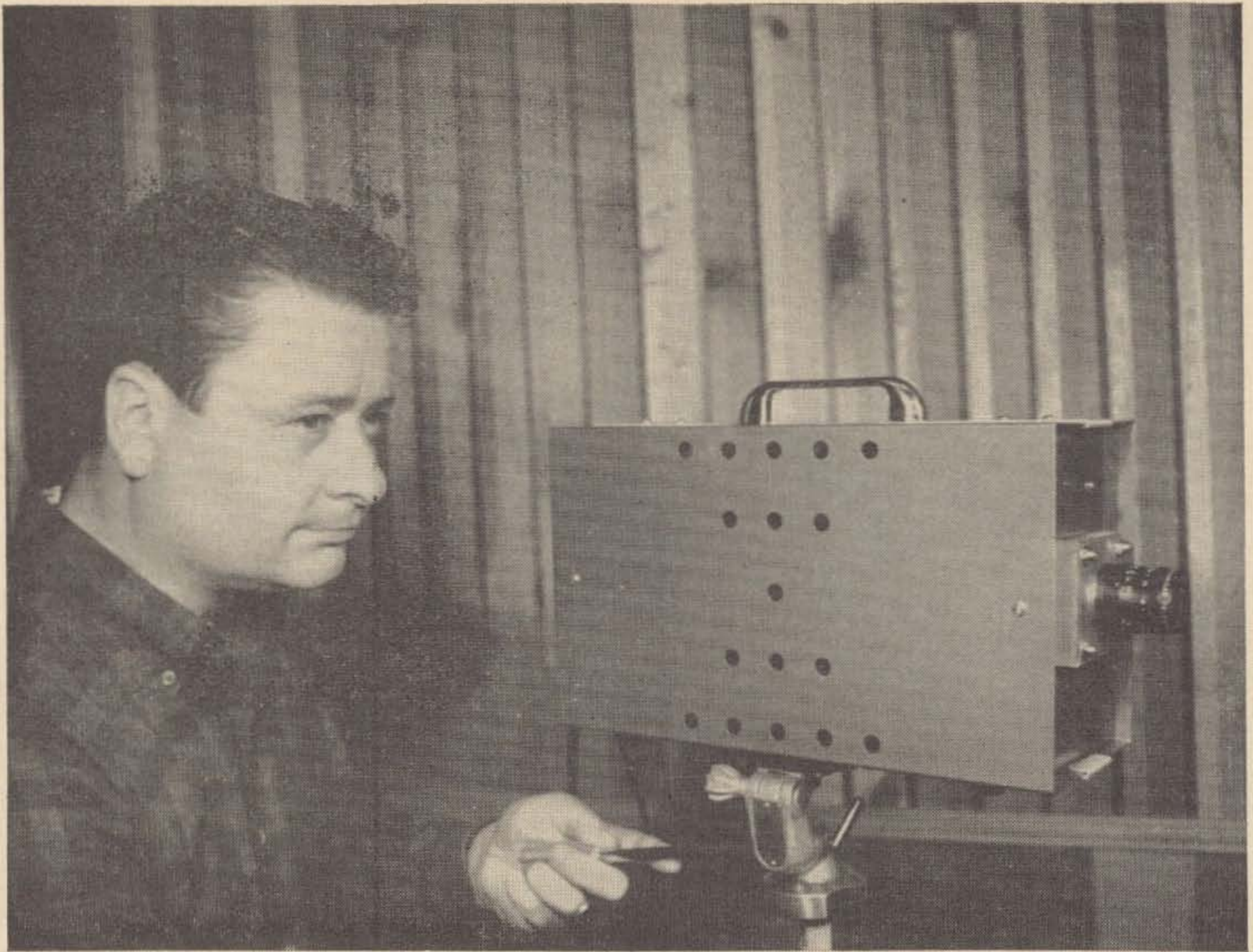

Kent A. Mitchell W3WTO
1760 Preston Road
Hagerstown, Maryland 21740

The Conar 800 TV Camera Kit

Once the word gets around, CONAR INSTRUMENTS will undoubtedly find that their introduction of the Model 800 TV camera kit has won them a permanent place in the hearts of Amateur TV experimenters. They have a real winner! Priced at \$209.50 in kit form, this is certainly the lowest priced *complete* TV camera on the market today. Included as standard equipment is a 25 mm, f1.9 lens, with wide angle and telephoto lenses available as optional accessories at a reasonable \$36.00 and \$28.00 additional, respectively.

The all important divicon tube is the popular 7038.


While contained in a small package, the circuitry is not crowded and no problems were encountered during construction. With the exception of the power supply circuits and the rear panel controls, the majority of the components are mounted on a large, heavy foil, etched circuit board. This circuit board certainly contributes to the low assembly time of approximately eight hours. I could find no errors in the construction manual . . . but read

the text carefully and don't just try to see how fast you can place your check marks next to the assembly steps. There are several areas where an inexperienced builder might have to backtrack and reposition some components because the hints hidden in the text were not followed. However, I don't suppose anyone would be building a TV camera as his first construction effort!

The kit arrived at the QTH of W3WTO in a surprisingly small and light package. Being used to watching my delivery-man trudge up the steep slope of my lawn with a kit and appearing to be carrying a carton of surplus cannon balls, I began to wonder if I was getting my money's worth! However, as you know, TV circuits don't require ultra-stable vfo's . . . and their associated boiler-plate stiff chassis, nor heavy high current transformers in the power supply section.

The majority of the kit's components come mounted on three folded 17½ by 30 inch corrugated cardboard sheets and are held in position by a plastic film. The plastic may be stripped away to expose only the components required during a particular phase of construction. Then too, when the evenings work is done, the remainder of the parts may be quickly removed from the kitchen table . . . or wherever else you have been incurring the wrath of your XYL.

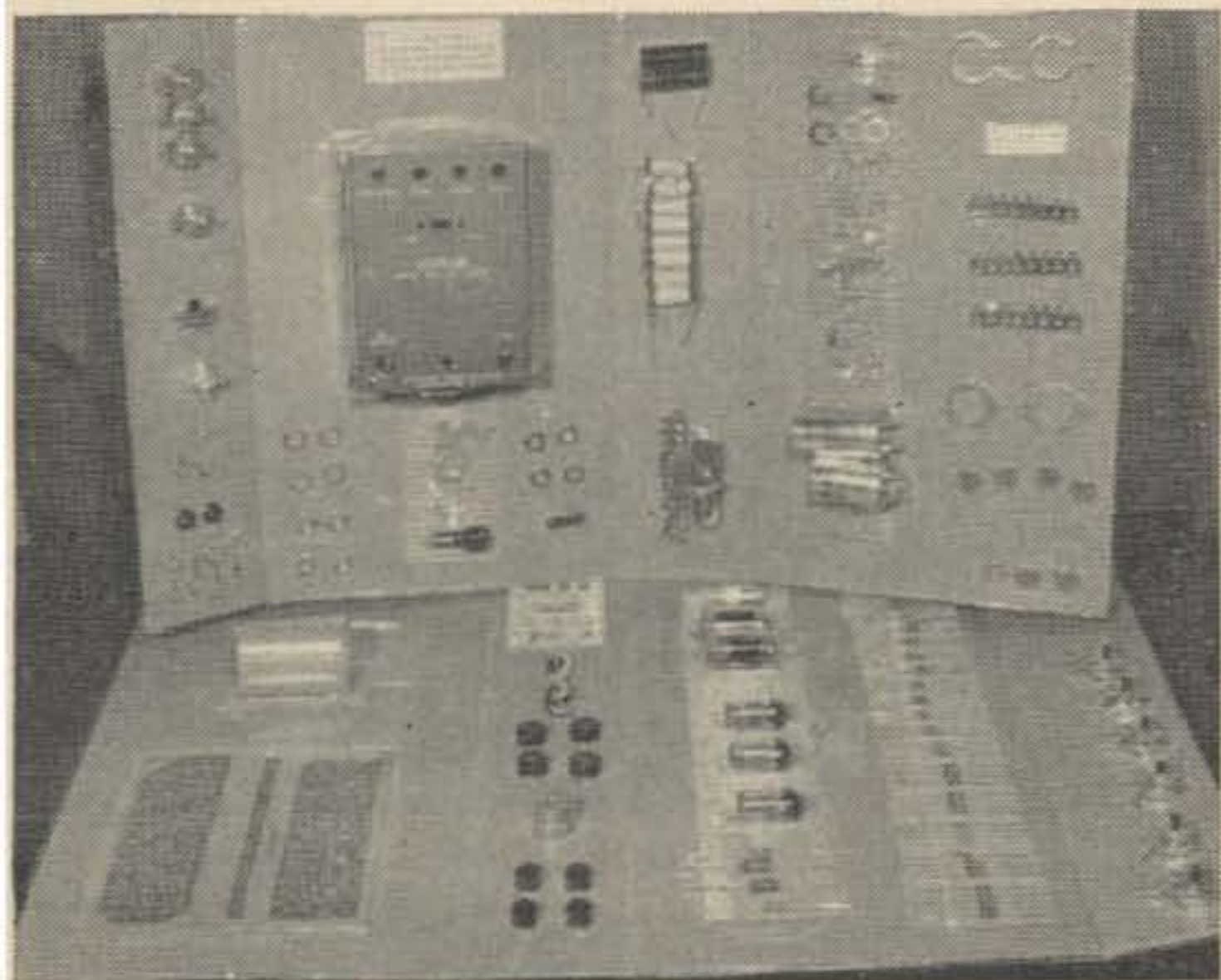Upon completing the assembly of the kit, all the controls are pre-set to approximate positions as per the instruction manual, a TV receiver is connected to the camera output cable, the camera power switch is placed to the ON position, and a hex alignment tool is utilized to adjust the camera rf oscillator slug-tuned adjustment to any desired channel from



Here's what comes in the Conar TV kit. All parts including the expensive lens and vidicon are included.

ROHN

sets the standard

for CRANK-UP TOWERS

Why settle for less than the best?

TWO CATEGORIES TO CHOOSE FROM

Standard Duty Guyed in Heights of 37 - 54 - 88 - 105 and 122 feet

Heavy Duty Self Supporting and Guyed in Heights of 37 - 54 feet (SS) 71 - 88 feet (guyed)

ROHN has these 6 IMPORTANT POINTS:

Ease of Operation—roller guides between sections assure easy, safe, friction-free raising and lowering. **Strength**—welded tubular steel sections overlap 3 feet at maximum height for extra sturdiness and strength. Unique ROHN raising procedure **raises all sections together**—uniformly with an equal section overlap at all heights! **Versatility**—designed to support the largest antennae with complete safety and assurance **at any height desired!** **Simple Installation**—install it yourself—use either flat base or special tilting base (illustrated above) depending on your needs. **Rated and Tested**—entire line engineered so you can get exactly the right size and properly rated tower for **your** antenna. The ROHN line of towers is **complete**. **Zinc Galvanized**—hot dipped galvanizing a standard—not an extra—with all ROHN towers! Prices start at less than \$100.

SEND FOR ROHN TOWER HANDBOOK

—\$1.25 Value

—**ONLY \$100** postpaid (special to readers of this magazine). Nearest source of supply sent on request. Representatives world-wide to serve you. Write today to:




ROHN Manufacturing Co.

P. O. Box 2000

Peoria, Illinois

"World's Largest EXCLUSIVE Manufacturer of Towers; designers, engineers, and installers of complete communication tower systems."

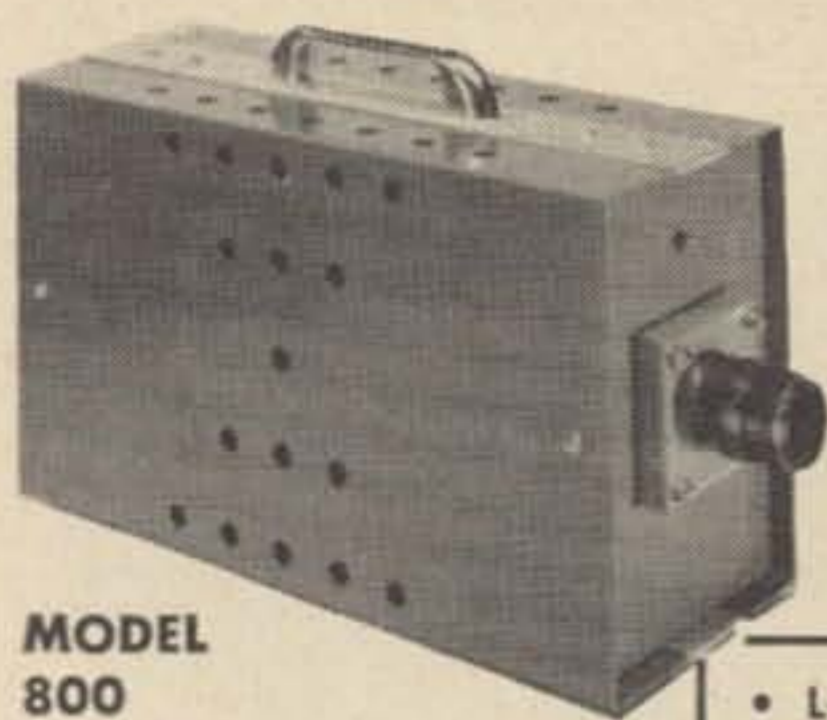**FROM CONAR—THE CCTV CAMERA KIT
THAT BREAKS THE PRICE BARRIER!**



**MODEL
800**

1001 uses in home, school, industry. Needs no expensive monitor sets, connects instantly to antenna terminals of your set. Uses any unused channel from 2 to 6. Sharp 1.9 lens gives clear pictures even under shaded conditions. Guaranteed for one year on all parts with exception of vidicon tube, which carries 90-day warranty. Order yours today!

**Complete
Nothing else to buy
ONLY**

\$209.50

WIRED \$259.50

- Lowest priced complete TV camera on the market
- Connects instantly to any standard TV set
- On the air in less than 8 hours assembly time

**CONAR
INSTRUMENTS
DEPT. KJ6C**

Division of National Radio Institute
3939 Wisconsin Ave., N.W.
Washington, D.C. 20016

**Send for New Free
CONAR CATALOG**

WE WANT TO BUY

Surplus Aircraft Radio & Test Equipment

We will pay cash or trade you (whatever you need) for the following items:

Test Equip. Signal Generators.

Measurements Corp. Models 65-B
Boonton Radio Co. Models 232A, 235A.
Hewlett-Packard Co. Models 608D, 612A, 624C.
Military Models. SG-1A, SG-2, SG-13, SG--66A, MD-83A, TS-510A.

Aircraft Navigation & Communication Equip.


ARC-34, ARC-38, ARC-52, ARC-73, ARN-14, ARN-59, ARN-73.

Aircraft Instruments.

ID-249A, ID-250A, ID-251A, ID-351A, ID-387.
We also want late type Aircraft Radio and Radar equipment manufactured by Collins Radio Bendix Radio and Aircraft Radio Corp.
Write, Wire or Phone if you can supply any of these. Ask for Norm Eichner.

Norman Electronic Sales

1413 Howard St. Chicago, Ill. 60626

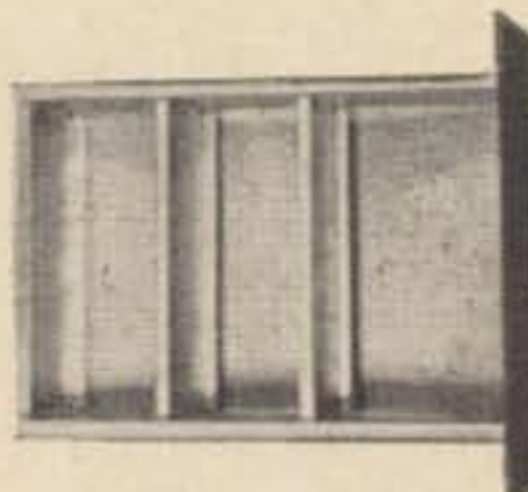

3 1/2" HALF RACK PANEL
10" Depth \$5.00 PPD
Check or M.O. No COD
NYC Res. Add 5%
NYS Res. Add 2%

DEVICES

BOX 136 BRONX N.Y. 10463

**CONSTRUCT YOUR
EQUIPMENT THE
EASY WAY—USE
THE UNIT CHASSIS**

Wire and rest the subchassis outside where everything is accessible. Assemble the subchassis into the unit chassis and you have a professional package.




3" x 6 1/2"
subchassis

Specifications


Horizontal Sweep Rate	15,750 Hz nominal
Vertical Sweep Rate	60 Hz (line locked)
Scanning	Random interlace, 2:1 ratio, 525 lines per frame, 30 frames per second.
Sync and Blanking	Combined sync and blanking signals.
Scan Failure Protection	Beam defocussing in the event of horizontal scan failure.
Output	100,000 μ V of modulated rf on an adjustable carrier frequency of channel 2 to channel 6 (\pm 2 MHz band-pass) into an output impedance of 75 ohms, unbalanced.
Resolution	240 lines (3 MHz)
Standard Lens	25 mm, f 1.9, focussing 2' to infinity.
Dimensions	5" X 7" X 12-1/4"
Weight	11 pounds
Kit Price	\$209.50

2 through 6. Next the HORIZONTAL control is adjusted until the camera sweep is synchronized with the TV receiver. Then, the vidicon tube is inserted into its socket, and the TARGET, BEAM, and FOCUS controls are adjusted carefully until . . . there it is!! A beautiful, clear, video picture! The thrill of looking at your first home grown video is almost akin to that of the reply to your first long shaky CQ.

Including the vidicon, there are only six tubes in the camera. The video output of the 7038 vidicon (VI) is amplified by the dual sections of the two 6U8 video amplifiers (V2 and V3) and applied to the grid of the triode section of still another 6U8 (V4A). The second half of the 6U8 (V4B) is functioning as an electron-coupled ultra audion rf oscillator. The oscillator output is coupled to the cathode of the triode section where the rf is modulated by the video. The vertical sync pulse for the camera is developed in a clever little circuit consisting of the neon pilot lamp which is

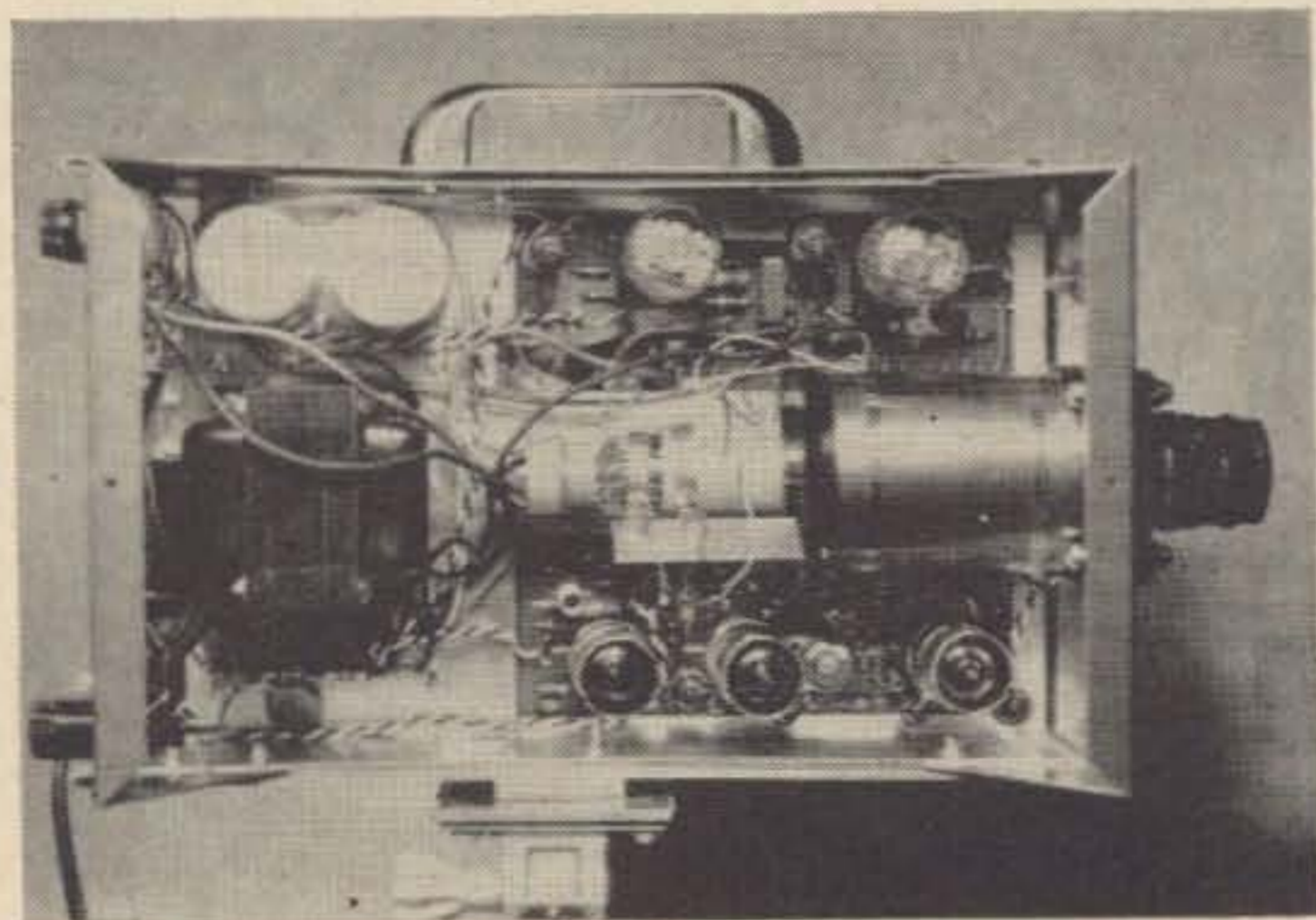

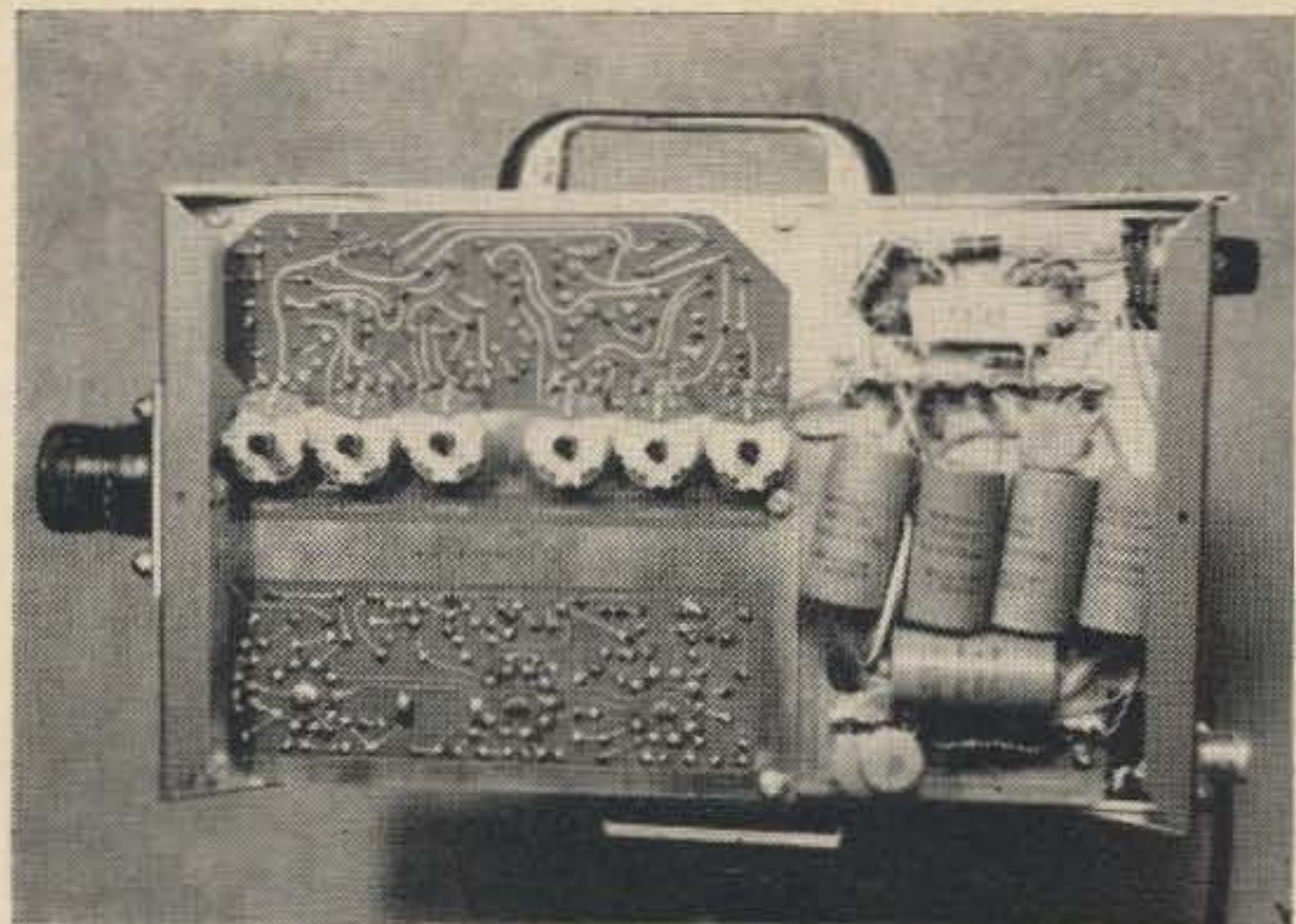Here's the vidicon side of the camera assembled. Watch 73 for complete instructions for setting up your own amateur TV station.



You can see from this side view that most of the parts are mounted on an etched circuit board.

fired by 60-hertz ac from the secondary of the power supply transformer and the resultant spike is utilized to drive vertical discharge tube (V5A), one half of a 6FD7, to cut-off . . . producing a more husky and better shaped pulse with which to work. The pulse, as developed across the cathode resistor of V5A, is utilized as the vertical sync pulse and the blanking pulse for the vidicon. The same pulse, as developed in the plate circuit of V5A, is coupled through a long time-constant resistor-capacitor circuit to produce a saw-tooth waveform which, when amplified by V5B and applied to the vertical deflection yoke, becomes the vertical sweep. The horizontal sweep is generated by a free running multivibrator (V6A and V6B) set to approximately 15,750 cps and is applied to the horizontal deflection yoke. Should the multivibrator cease to function, the cathode current of V6B increases and since the vidicon focus coil is in series with the cathode circuit, the vidicon electron beam is defocused so that a spot will not be burnt on the target area of the tube.

After you have your camera in operation and adjusted to your satisfaction, and everyone in the family and neighborhood have made faces at themselves on the living room TV, you are ready to carry it into the ham shack for its first exposure to ATV . . . which of course means modification! However, in this case we are only speaking about the addition of a second coax jack to the rear panel of the camera so that the video may bypass the camera's rf stage and connect to your 440 mc transmitter. The video should be tapped from the grid of modulator V4A. Adequate room to mount a BNC type coax jack may be found just above the rf output jack.

See you on TV!

. . . W3WTO

CLEGG "66'er"



Everything
you've
wanted
in a 6-meter
transceiver

Complete flexibility—built-in dual power supply for 115 VAC or 12 VDC, compact size make it ideal for mobile, fixed or field use. Loud and clear reception—highly sensitive and selective dual conversion receiver offers great freedom from birdies, tweets and spurious signals. Front end design provides superb signal capture, freedom from cross modulation and overload. High Talk Power Modulation is achieved by an effective 22 watt input transmitter, with speech clipping. For a clean 70-75 watts output, combine the "66'er" with the powerful Clegg Apollo Linear Amplifier. Built-in S-meter serves as tune-up meter for transmitter. The spectacular new 66'er is great for hams, CD, MARS and CAP operators. See Clegg and Squires-Sanders communications products at your dealer. Write for literature today to:
Squires-Sanders, Martinsville Rd., Millington, N.J. 07946

Squires  Sanders

TICKLE YOUR TIGER!

Now that you have overcome your ignition noise, install a

DELTA MARK TEN CAPACITIVE DISCHARGE IGNITION SYSTEM

Enjoy dramatically improved acceleration — eliminate plug fouling and the effects of point bounce. Get better gas mileage and instant starts.

Installs in ten minutes utilizing original coil. Utterly reliable and fully warranted. Not to be confused with earlier "transistor ignition systems."

Factory Wired	\$44.95
Kit Form	\$29.95

Postage Paid.


Send check with order to . . .

**BROWN
ELECTRONICS, Inc.**

Broadway at Jefferson
Fort Wayne, Indiana 46802

NEW

UNIQUE

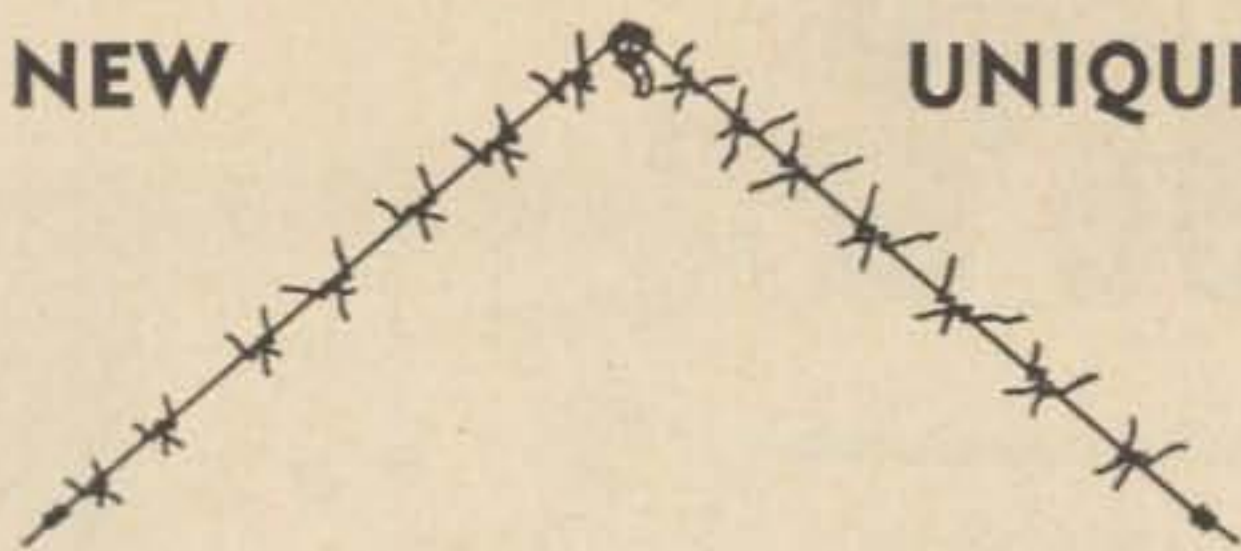

CTK'S BARB'D WIRE ANTENNA

Full radiating surface but shorter than a dipole. No coils or traps to distort the radiation pattern. The design results in increased capacitance, and therefore, shorter length, for resonance. Ideal for places where a full-length dipole is too long.

The 80/75 meter BARB'D WIRE DIPOLE is only 96 feet long. The 40 meter BARB'D WIRE DIPOLE is only 50 feet long, and will work on 15 meters, too.

May be fed with 50/75 ohm coax, or 72 ohm balanced pair. Needs no tuners, loading coils or baluns.

Send \$2 for instruction sheet and build your own, or send \$15 for the complete antenna (either size), shipped parcel post prepaid in the USA.

**C. LeRoy Kerr, WA6CTK
P.O. Box 444
Montebello, California 90641**

HW12, 22, 32 OWNER

**New three band modification
delivers the performance of your
transceiver on five 200 kc band segments.**



Featuring selectable upper or lower SSB* Selectable AVC* Coverage: 3.8-4.0; 7.0-7.2, 7.2-7.4, 14.0-14.2, 14.2-14.4 Mc*

Front panel key jack* New front panel and plastic dial included*

COMPLETE KIT PRICE ONLY \$59⁹⁵

Send for free brochure!


DRC KIT

215-28 Spencer Ave. Queens Village, N.Y. 11427

Name Call

Address

..... Zip

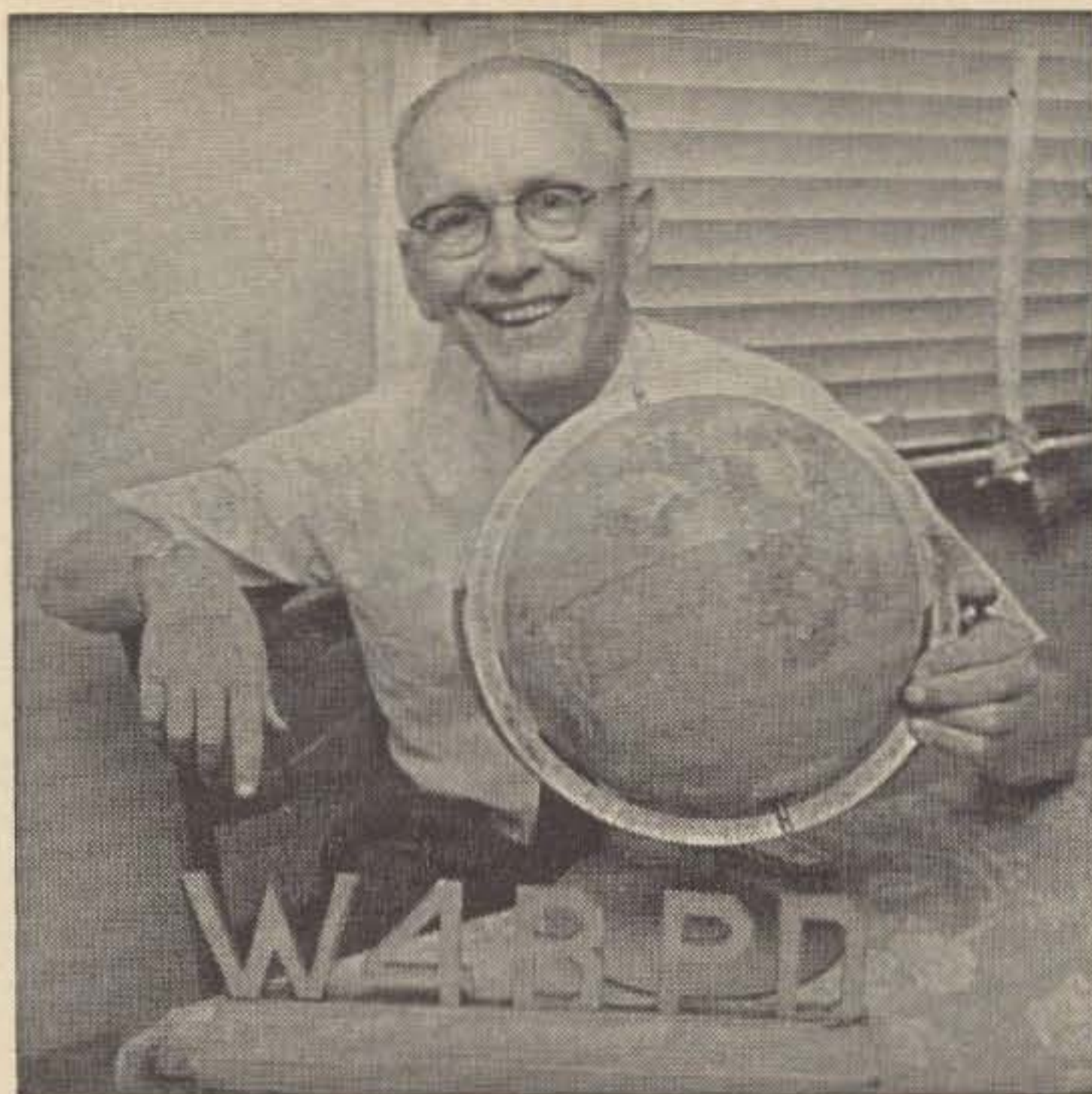

The total population we found on the Aldabras were about 20 people practically 100% men. One old man I met there had been born on Aldabras some 80 years before and left the island only once, going to Mahe for only a few days. He told me he had no desire whatsoever to leave the Aldabras and see the outside world. This old man had been employed all his life on Aldabra, was sending his salary to Mahe where it was being invested for him. They said he had become quite wealthy. Can you imagine his outlook of the world? His entire world was the Aldabras and nothing else, and HE WAS VERY HAPPY. All the employees on the island are usually on an 18 month work contract to the island leasee, and are fairly well taken care of. If they don't smoke they have no use whatsoever for any money. The leasee of the island furnishes them with food and all the fish they want is also furnished them. Many other items from the sea are also furnished them, they just don't need any money at all. Most of them work hard at their 18 month contract and go back to Mahe (so I have been told) and have one or two weeks of drinking, and running around, until they are flat broke and are then ready to come back for another 18 month contract. Either to Aldabras, Farquahar, Chagoes etc. These fellows are a happy-go-lucky lot and none of the worries of the outside world bother them at all. Maybe this old fellow who was born on Aldabra has a good thing at that. There is nothing like a store on the island so you need no money.

Every night about 7:30 PM everyone gathers around the front door of the manager's and listen to the radio belonging to the manager, usually listening to Mombassa, Nairobi, Tananarive, Ceylon or at times even London.

Gus: Part 15

He has a small Japanese transistor set with short wave. These people have a good life with no worries about anything. All you need to wear on the island is a pair of short shorts. The temperature is absolutely perfect during the days and nights, I estimate it varies from 75 at night to about 90 during the daytime. If you like sea shells they are there just waiting to be picked up.

After Harvey and Jake finished eating they departed for the boat. They were going to hunt a sand bar on the other end of the island and beach the boat and repaint it from stem to stern. Since it was very high tide, and the full moon was due that night, they would not have to go too far up on the beach to be sure the boat was high and dry for they wanted plenty of time to do the boat all over. Harvey was going ashore with his tent and set up his operation from there with his wind charger, etc. They told me I would have about 14 days to operate while they were awaiting the next very high tide so they could float the boat again during the height of the tide that was about two weeks off. This suited me fine—boy 14 days of hamming from Aldabra, that suited me 100%.

After they had departed with plenty of help from the islanders I soon had up my antenna. During this DXpedition I only had horizontal dipoles. I knew nothing about the Hy-Gain Antenna Company and their fine all band vertical ground plane antennas. I wish I had known about them because I am sure I would have put out much better signals than I did. I asked the manager in what direction did the sun rise and set. Not having a compass with me I took his word and got the dipole up broadside to Europe and the USA. The old putt-putt was fired up and VQ9AA was on the



RCA SSB-5 Transceiver

Because we sold out last spring on this popular item—I have been anxious to obtain more of these fine SSB transceivers. Only 11 pieces were found—so first come first served. Here's the dope.

The SSB-5 has four channels, each of which may be set up between 3 and 15 MC with one oven mounted crystal for each channel (rec and transmit). Four sets of adjustments plus an ant terminal for each channel are furnished. A self contained audio oscillator for tune up is available. 250 Watts PEP input, furnished with 1400 kHz, 6-pole crystal lattice filters (upper and lower) and 4 crystals of your choice, with AC or DC power supply, mike, instructions and speaker, at only \$330.50. The DC supply and the AC supply are separately available at \$75.00.

Unit weighs only 16 lbs and measures 12½ x 7½ x 13".

Push to talk operation, AM or SB on either sideband at a flick of switch.


AM gain and RF gain controls and a delta control for netting are also supplied.

The receiver is hot—better than 1 μ v for 50 mw output with a 10 db signal-plus-noise to noise ratio. Automatic speech clipping up to 12 db included.

Will pi match any antenna from 10 to 80 ohms including mobile whips.

RCA's price was \$742.50. These new sets are guaranteed to please—But there are only 11 left—No foolin!

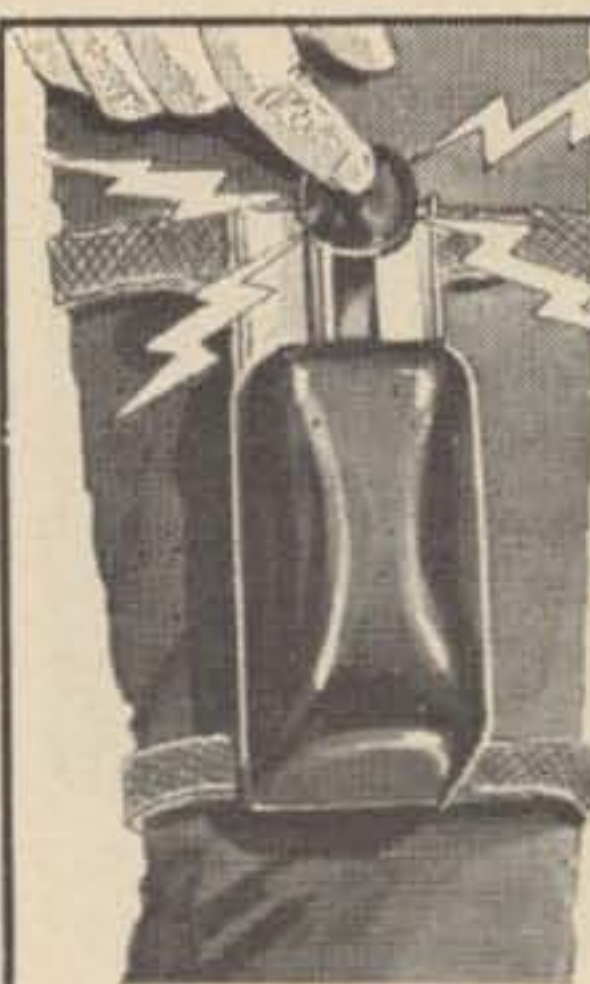HERBERT W. GORDON CO.
Woodchuck Hill, Harvard, Mass. 01451
Telephone 617-456-3548




THE BUY OF A LIFETIME!

Canadian Air Force C.W. TELEGRAPH KEYS

Complete unit with case, cord & plug. Can be leg operated or desk mounted.

\$1.95
complete
MONEY BACK
GUARANTEE

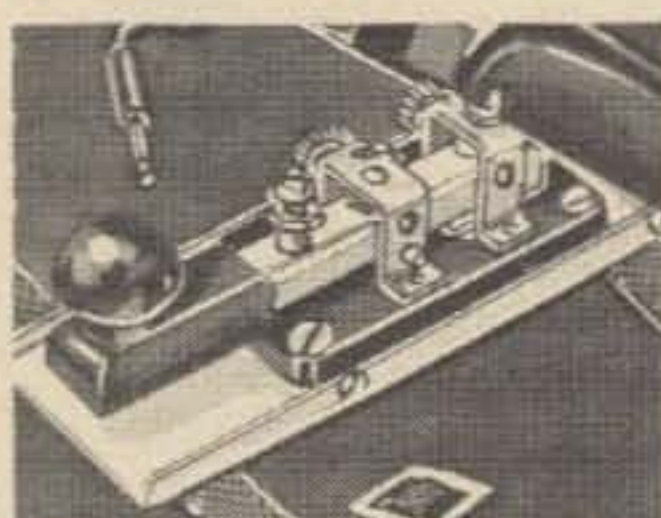TERMS: Postage is Prepaid. Send check or money order for \$1.95 to:



FEDERATED PURCHASER, INC.

SPRINGFIELD, NEW JERSEY, 155 U.S. Route 22, (201) DR. 6-8900
LOS ANGELES, CAL., 11820 West Olympic Blvd., (213) GR 7-8274
SHREWSBURY, N. J. • ALLENTOWN, PA. • SILVER SPRING, MD.



to the following manufacturers who helped to make the first annual SAROC a real "Fun" hamfest . . .

Linear Systems • Galaxy Electronics • IOAR • Herb Becker Co. • Tri-Ex Towers • Transcom Electronics • Collins Radio Co. • Wispride Cheese • Sideband Engineers • Henry Radio • Amphenol Corp. • Manley Electronics • Swan Electronics • Electro-Voice • Weatherbie Electronics • E-Z Way Products • New-Tronics Corp. • Mission Ham Supply

MAKE PLANS NOW!

. . . to attend the second annual

SAROC* JAN. 5-8, 1967

Write to John Romero, Hotel Sahara, Las Vegas, for complete details.

*Sahara Amateur Radio Operator's Convention



air.

The fun began immediately, I mean to tell you I did business with a bang, it was one solid pile-up for over 12 hours without a let up. When I first got going, the island manager came to visit me, wanting to show the visiting American the island, its turtles, birds, etc. I could see that this fellow had the wrong impression of why I was there. He took me to be a tourist, I turned off the putt-putt and told him I wanted to have a good talk with him. We sat down on the back porch where my equipment was installed on the eating table of the guest house. I explained to him what ham radio was all about, telling him about DXers, telling him that Aldabra Island was one of the rarest spots on the world and that thousands of people all over the world were standing by to QSO me while I was there. I explained to him that lots of the expense of my getting there was paid by these fellows, and since I was an honest fellow I was obligated to do NOTHING BUT OPERATE while I was on the island. I told him if things sort of quieted down that I MIGHT HAVE TIME later on to do some visiting of the various parts of the island. I told him all I wanted to do was to sit at my operating table, hour after hour, day after day, and work the boys one after another until I had worked them all. I even asked him to have my meals at certain odd hours, during times I thought the bands' activity would be at their lowest. After that I had no more trouble with him wanting to show me around the island. After about 3 days operation I happened to notice EXACTLY where the sun settled into the sea and to my surprise it was not at the spot indicated to me before. My antennas were not broadside to Europe or the USA, they were off the ends.

The next day I changed this and all signals picked up about 2 S points from Europe and the USA. Another must for DXpeditioners—bring along your own compass and let it tell you where to squirt your signals. Don't take the words of anyone as to where is East and West, most of them don't know, they just think they do. Things were going fine with me. The food was very fine. Have any of you ever eaten real turtle steak or turtle liver? Or scrambled turtle eggs? The turtle steak is about twice as tender and twice as white as veal cutlets. The livers from these turtles are out of this world and could be cut with your fork. The eggs were about 75% yolk and were very fine when scrambled. I never did get tired of eating turtle meat, etc. Fish were prepared in many different ways. Fried, fish soup,

Quement ELECTRONICS

"YOUR COLLINS HEADQUARTERS"

HAMMARLUND

SWAN

DRAKE

SBE

HALLICRAFTER

MOSLEY

HY-GAIN




ANOTHER QUEMENT FIRST!

QUEMENT MODEL
QEC-2

VERY EXCLUSIVE

\$24.95

SHIPPED EXPRESS ONLY

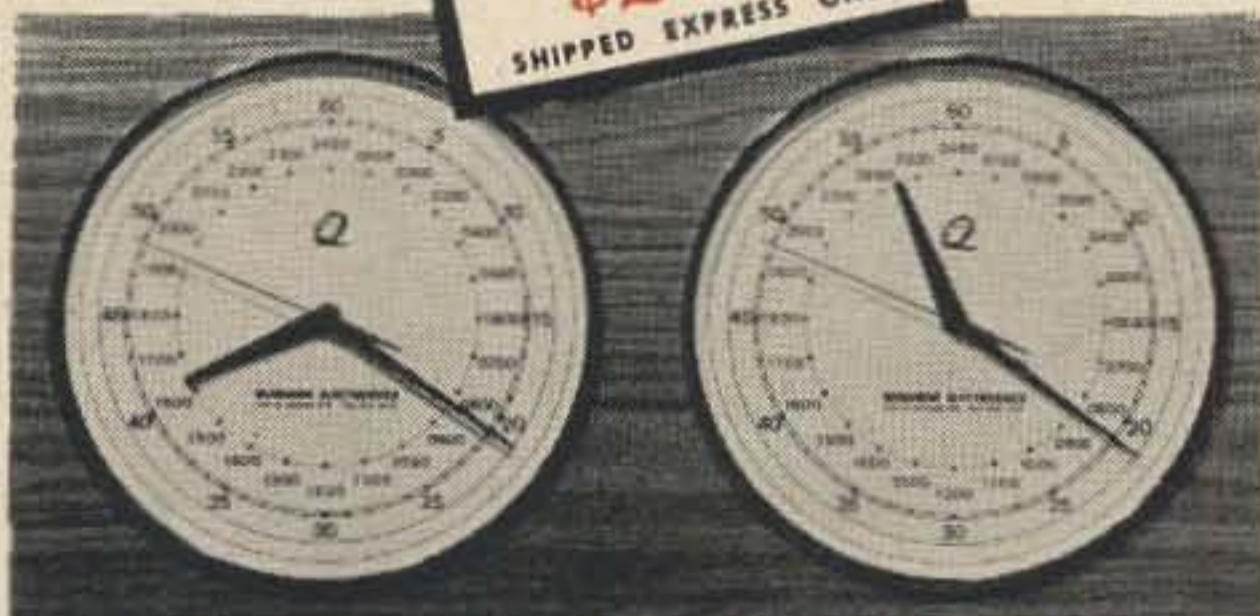

TWO BEAUTIFUL SYNCHRONOUS 24 HOUR ELECTRIC CLOCKS
ONE FOR LOCAL AND ONE FOR ZULU OR ??? TIME

VERY RICH LOOKING 12"X24"X2" WOOD CABINET CONTAINS TWO TEN INCH MATCHED CLOCKS WITH CHROME TRIM RINGS AND STYLING TO ENHANCE ANY ROOM. RED SWEEP SECOND HANDS. SHIPPING WT. 20 LBS.

- Compact
- Accurate
- Self-contained
- Highest Stability
- Heavy Dip

**ALL-TRANSISTORIZED
GRID DIP METER**

\$29.95

Allow \$1.00 for packing and shipping. California residents include 4% sales tax.

Assembled & tested, complete with six coils, ear phone and battery.

TUNES 500 Kc
THRU 150 Mc
DOZENS OF USES



GDM-3

NEVER BEFORE HAS A PRECISION INSTRUMENT LIKE THIS BEEN OFFERED AT SUCH A LOW PRICE.

OUR FAMOUS MT-2 VOM



20,000 OHMS per VOLT DC **\$12.95** 1% Precision Resistors

POST-PAID USA

NINE TRANSISTOR SUPERHETERODYNE

WOW!
METAL CASES
100 MW
HOT!



Allow \$1.00 for packing and shipping

Supplied with batteries

\$31.95 PAIR

LOOK! PROFESSIONAL
stereo or monaural listening
20-20,000 CPS 8-16 OHMS

HI-FI
HAM
ORGAN



Allow \$1.00 for packing and shipping. California residents include 4% sales tax.

QUEMENT QPH-1

\$12.95

S.W.R. BRIDGE and
FIELD STRENGTH METER

9.95

Allow 50c for packing and shipping. California residents include 4% sales tax.

MAY BE LEFT IN LINE, UP TO 2000 WATTS.

GOOD THROUGH 2 METERS



THE BEST VALUE WE HAVE EVER OFFERED!

POPULAR MT-1 VOM



Allow 50c for packing & shipping. Calif. residents add 4% sales tax.

Test Leads

\$5.95

QUEMENT
FLEXIBLE NECK
FLASHLIGHTS
HANDIEST TOOL
IN YOUR SHOP

\$1.95 EA.

"Q LITE"

PPD IN USA



SINCE 1933

FAST SERVICE


Phone CY 4-0464

QUEMENT ELECTRONICS

1000 SOUTH BASCOM AVENUE

SAN JOSE, CALIFORNIA

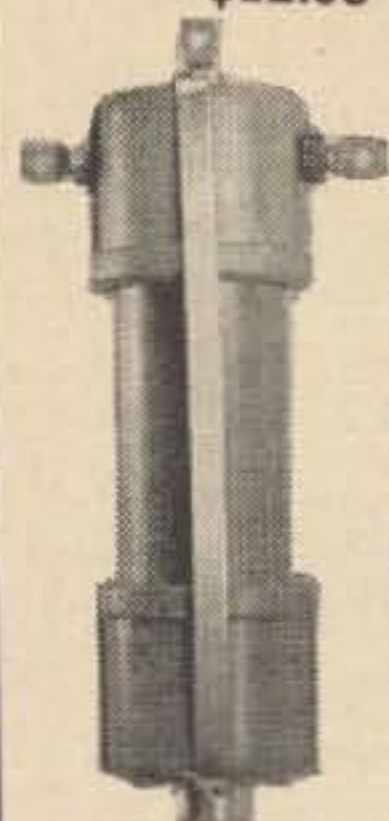"Northern California's Most Complete Ham Store"



See Coax
Accessory
Book for
More Data

\$12.95 W2AU \$12.95 • FOUR PURPOSE BALUN

The Balun Everyone has been waiting for. Will Help a TVI Problem. • Broad-banded 3-32 mc. • Center hang-up hook for inverted Vees. • Handles full legal power, 2KW PEP • Built-in lightning arrester • SO239 RF connector for coax transmission feed line eliminates center insulator • Withstands up to 600 lb. antenna pull • For use with all type antennas fed with unbalanced coax line. • Weighs only 6½ oz. 1½" diam. 6" long 2 Models: 1:1 matches 50 or 75 ohm unbalanced coax to 50 or 75 antenna load. 4:1 matches 50 or 75 ohm unbalanced coax to 200 or 300 ohm antenna load. • Helps eliminate TVI.

- All New W2AU Super Vinyl 2 el 10-15-20 quad. Complete \$54.95
- W2AU Super Fiberglass 2 el 10-15-20 me'er quad. Complete quad \$99.95

UNADILLA RADIATION PRODUCTS
UNADILLA NEW YORK

ELIMINATE GUY WIRES

USE MYLAR ROPE

We stock all sizes: 1/8"-10¢; 1/4"-30¢; 3/8"-60¢; 1/2"-\$1.10 per foot. Other sizes available.

We also carry a complete stock of Hy Gain Antennas new and used. All materials for any antenna installation. Write for information and prices.

ANTENNA MART
BOX 7, RIPPEY, IOWA

**ALL NEW TRANSISTORIZED
CW MONITOR AND
CODE PRACTICE
OSCILLATOR**



JUST \$9.95 COMPLETE
(except battery)

Use as CW monitor... use as code practice oscillator. This new complete unit from hth Electronics is powered by a standard 9-volt battery, contains a built-in speaker, on-off switch with individual volume and tone controls for a loud, clear tone without clicks or chirps.

NO EQUIPMENT MODIFICATION—Simply connect spade lugs to terminals of CW key, plug in jack, turn on and adjust volume and tone controls... operates automatically... no accessory relay... no pickup antenna... no battery drain until key is depressed.

Precision Engineered. 100% Warranted.
Designed and Developed in U.S.A. (foreign mfg.)

ORDER TODAY! Allow 2 weeks for delivery.

ELECTRONIC HOUSE, P.O. BOX 873, TARZANA, CALIF.

Gentlemen:	Ship to:	Dept. 2
Please ship me _____	NAME _____	
CW monitor and code practice oscillator(s) @ \$9.95. Enclosed is	ADDRESS _____	
<input type="checkbox"/> cash <input type="checkbox"/> check	CITY _____	
<input type="checkbox"/> money order for	STATE _____	
\$ _____		

boiled fish, baked fish, fish curried and rice being very nice. They eat plenty of rice there and since I was from one of the rice eating parts of the world, I was right at home with it piled up high on my plate. Certain parts of coconut trees were nice, when boiled in soups, as well as bamboo shoots. I even had some sea shell soup, the sea shells are placed in boiling water, the meaty part cooked and then it sheds away from the sea shell. Maybe some people call this snail soup. They like plenty of pepper in their food. After explaining to my cook I did not like pepper he cut down from 195 degrees of pepper to about 125 degrees, explaining that he could not cook anything with less pepper. After a while my mouth got tough enough to take it OK.

I tried listening for Harvey, and finally heard him on about 14085 kHz about S 3. We were separated far enough apart so that we caused each other no QRM whatsoever since I had always used 14065 or 14035 kHz when on CW and about 14125 plus or minus when on SSB.

After about 3 days of operation my power plant konked out. Have you ever tried taking off the cylinder head of an engine with only a pair of regular pliers? Well I did. After cleaning off the surplus carbon, adjusting and cleaning the spark plug and even trying to clean up the valves the engine was put back together and still it was dead as a door knob. Plenty of spark was on the plug so it had to be the fuel system. Off came the carburetor and apart it came. One valve seat was completely plugged shut, this was cleaned and while trying to force the carburetor back together something went "crack." Apart came the carburetor again and I found that I had broken one of the needle valves that was made out of Teflon. No spare parts were along with me. It was either repair this broken needle valve or no more VQ9AA operation. I had my electric soldering iron with me but no electric current to heat it with. Try heating up your electric iron with 4 candles as I did. By being very careful I welded the Teflon needle valve back together, smoothing the welded spot with the hot iron, found that the carburetor gasket had got broken and found that a call book cover made a FB gasket for the carburetor. Back together went everything, and the putt-putt cranked up immediately, and I was back in business. The moral to this story for you future DXpeditioners—bring along at least some small spare parts and a few tools to take your power supply engine apart with. This is a MUST in my book.

At about sundown time on my first night on

Aldabra I was on the air with a big pile-up and all of a sudden I heard the doggondest noise outside. Flapping wings, squawking, screeching, thuds, etc. I rushed outside to see what was causing all this commotion and there were birds by the hundreds in what seemed to be a free-for-all. After watching this battle royal for a while I soon saw the pattern of what was taking place. The booby birds that were out fishing all day, filling their craws full of little fish for their young on Aldabra were coming home at sun-down and the other birds (let's call them falcons—they have another name; I forgot what it is) would hover way up high, spot a certain booby coming in about 50 feet above the water. The falcon would close his wings and down he would come like a stone, hitting the booby bird in the middle of his back, almost knocking the booby bird breathless I guess, this sudden jolt would cause the booby to heave up its crawful of little fish, the falcon would then curve up under the booby and grab a big mouthful of fish that had been spewed from the booby. This little episode took place every evening just before darkness came and it was better than Red Skelton on TV. I never did see any booby get thru with his crawful for the young. I was told that this has been studied and about 3 to 4% of the boobies do get thru. Whoever named these birds booby birds certainly selected a very descriptive name for them. They certainly are a booby to fish every day for the falcons to get their catch without working for it.

I soon settled down to a sort of regular operating schedule. About 5:30 AM (all these times local) I would get up, crank the power plant up, work the fellows until the band sort of leveled off at 10:00 AM; then eat breakfast; in the sack until about 2 or 3 PM, then it was dinner and on the air until about 2:30 AM a late snack to eat and to bed with the alarm clock set at 5:30 AM. This gave me enough sleep and still satisfied the gang with enough activity and openings for everyone.

After the first week the big pile had been worked down to a small one and I began to have more time to look around the island like a good tourist should. I was shown the turtle pond where they kept usually around 200 of those big turtles awaiting the boat from Mahe which came when it was available. No certain schedule at all but usually every 3 or 4 months to pick up the live turtles and take them on deck back to Mahe where they were put into the turtle pond there and sold as they were needed. Fishing on Aldabra is done on what looked to me to be a large scale. Each

Two Extra Good Values



Phone Patch Kit

In our June ad we listed a darned good phone patch kit selling at only \$5.95. With 50 kits made up—we thought we might sell 25 to 30. Were we surprised when more than 65 were ordered—You bet we were—and so we hunted up more of the special high quality repeating coil transformers which enabled this patch to be so successful. Having four 600 ohm windings and made so as to induce the least amount of hum, this transformer, worth \$60, really makes this patch a snap to build. We supply this kit complete with all parts and instructions—but less the chassis or box to build it in for only \$5.95 FOB Harvard—or if you want to gamble \$6.95 postpaid to U.S. or Canadian points. Three Hundred Kits available. That's all the transformers we could find.



RCA Model 508 Mike

Another very popular value is our RCA Model 508 Dynamic mike. Many hams who bought one from our ad in the June issue have reordered. One fellow down Jersey way bought four. There must be a good reason—and that is that this mike has such a smooth response for single side band. Crisp without being harsh. This is a new high impedance mike furnished with 20 foot shielded cable, heavily chrome plated with response from 200 to 8000 cycles but very flat from 300-2700 cycles. RCA's price is better than \$39.95. My price while they last \$15.00 FOB or \$16.00 postpaid in the USA.

HERBERT W. GORDON CO.
Woodchuck Hill, Harvard, Mass. 01451
Telephone 617-456-3548

GIANT MIKE SALE

MODEL 454X

Outstanding base station microphone. Single sideband (Limited to voice) frequency response of 300-3000 C.P.S. Attractive telephone black satin finish on all metal alloy case. May be wired for VOX. Comes wired for push to talk. Has extra lock-on switch for continuous transmission. Complete with coiled cord (Three conductor—one shielded). Output level is -48 db.

List Price \$26.50

MODEL 454C

Same as Model 454X except with heat and humidity proof ceramic element. Output level -52 db.

List Price \$26.50



SALE \$13.99



Dynamic mobile mike, 600 ohm imp.

3 cond.(one shielded)coiled cord.

-66 db. 300 to 6,000 c.p.s.

SALE \$12.99



THE TURNER TRANSISTORIZED

~~\$30.00~~ **+2**

WITH VARIABLE OUTPUT LEVEL

Now, from Turner comes the very finest base station microphone ever designed. The **+2** features a two transistor pre-amp with volume control to give you up to 50 times the output level you now have. Yes, just dial your desired signal for maximum modulation all the time — every time. You can work close or far away from this microphone, or change the output for a big or little voice.

Eventually, all sets lose some of their initial power. Turner's **+2** puts the zip back into your set and keeps it up to full strength at all times!

The **+2** has tailored frequency response of 300-3500 c.p.s. for best and clearest voice transmissions with knocked down local noise interference.

Exclusive touch-to-talk or lock on-off switching — the **+2** works with all tube or transistor sets regardless of switching requirements or type.

LIST PRICE \$49.50

SALE \$26.99

FIELD STRENGTH and SWR METER

ZAP!



SALE \$8.99

~~\$15.95~~

Model FS-45

POW!

A combination unit that will give relative field strength readings in forward and reflected power. Coaxial fittings allow permanent installation for constant monitoring of transmitter output. Meter has sensitive 100 micro-amp movement with two-color bold easy-to-read scale. Individually boxed with instructions.

GROVE ELECTRONICS

3256 N. PULASKI RD. CHICAGO, ILL. 60641

Send check with order. Include postage, extra returned

SEND FOR GIANT SALE CATALOG!!!

LATE SPECIALS: ASSORTED KELLOGG RELAYS!!


6/35 volts 4PDT,6PDT,8PDT,etc. (reg. \$10 ea.)

SALE 3 FOR \$1.99

boat went out every day and caught a boat full of fish. It did it the hard way, by spearing the fish. When the fish are brought ashore they are cleaned up, covered with what looked like ice cream salt and put out in the sun to dry. Later on this dried fish is sent back to Mahe to be used there and some shipped probably to Africa. Copra (dried coconut meat) is done on a fairly large scale, too. No one seemed to be working very hard. They have a certain amount of work to do each day and most of them could do their daily task in about 6 hours. Of course a few eager beavers worked longer for extra consideration. But this was the exception rather than the rule.

I finally had a QSO with Harvey who was operating from the other end of the island and was told that we were going to stay there for a total of 17 days—this was indeed FB news for me. If there is ever a repeat of Aldabra I will be prepared for some 40 and 80 meter operation and thereby hand out a new country to everyone on these bands. Maybe even 160 meters. Conditions seemed very good to me while I was there, I wonder how they would sound if I were there during the good part of the sunspot cycle? Can you picture the stations you could work from there when 10 meters thru 80 opened up. Around the clock openings would really work a fellow to death. But what a FB way to die? Hi, Hi!

While on Aldabra I got a message from Peggy thru Ack that we had to build a new house. It's a long story about a land deal I will not take the time to repeat on these pages. But on account of a deal on land Peggy said a new house had to be built. I told her to go ahead and build it and to not forget THE HAM SHACK. Let me tell you I did get a ham shack built too. A lot larger and nicer than I would have had the nerve to build myself. Peggy even got my 150 tower taken down and the 5 element beam taken apart too. Boy I really found out what a nice XYL I had and to this day she has not changed in the least—in fact she gets better all the time, still bringing my breakfast into the ham shack each morning, and even supper if I ask her to. There just aren't many like good old Peggy, this I am sure of. How many of you fellows' wives would let you leave them for first 7 months, then for TWO YEARS? I think the percentage would be below 1%. Peggy says to me her first obligation in our marriage is to make me happy and she likes to also make others happy and this is her method of doing just this.

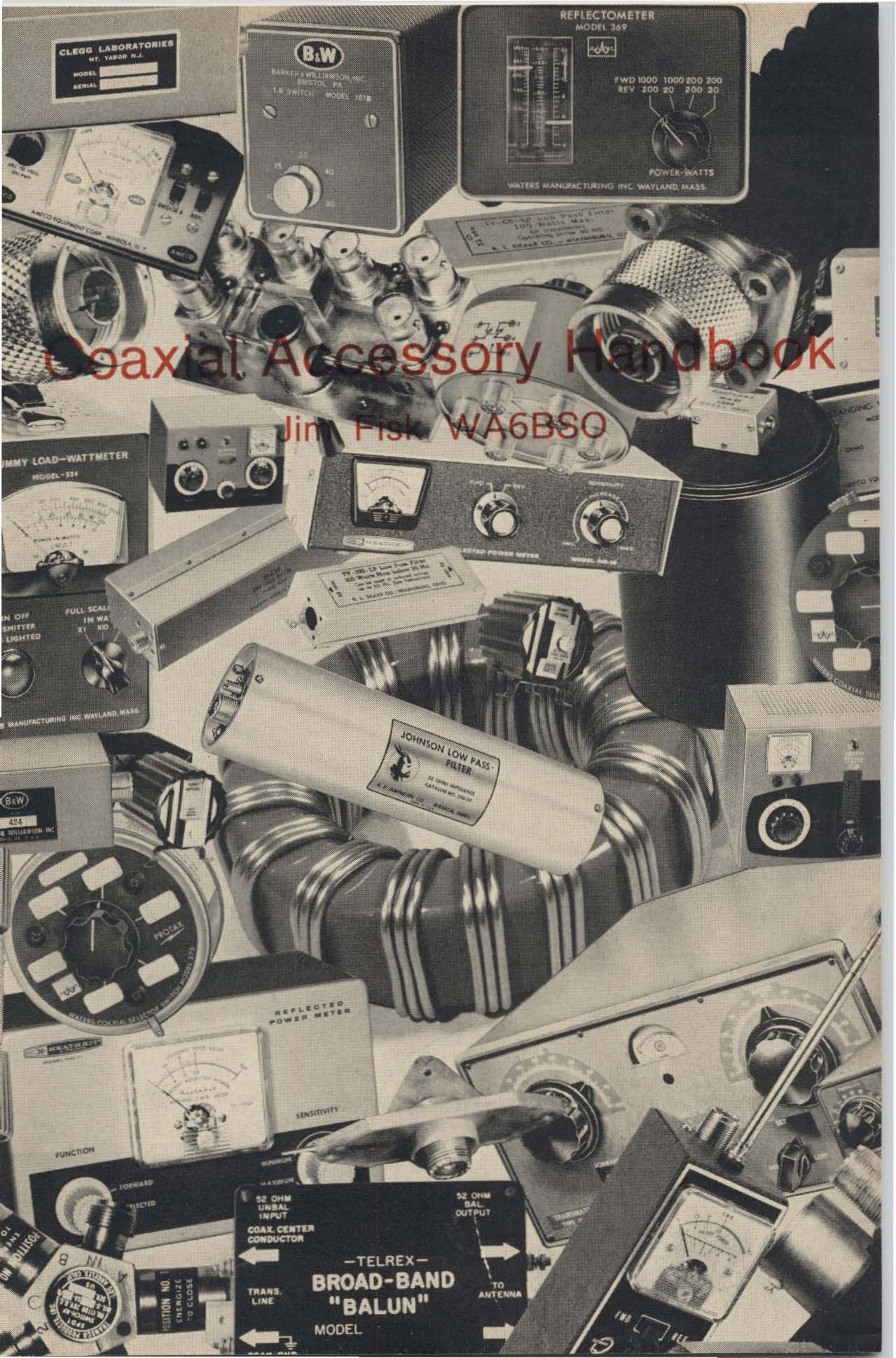

CLEGG LABORATORIES
MT. YABOR N.J.
MODEL _____
SERIAL _____

B&W
BARKER & WILLIAMSON, INC.
BRISTOL, PA.
T-R SWITCH MODEL 381B

REFLECTOMETER
MODEL 369
WATERS MANUFACTURING INC. WAYLAND, MASS.
FWD 1000 1000 200 200
REV 200 20 200 20
POWER-WATTS

Coaxial Accessory Handbook

Jim Fisk WA6BSO

IMMUNITY LOAD-WATTMETER
MODEL-334

REAR VIEW
ATTEN. DIV. 100
REAR VIEW
ATTEN. DIV. 100
MODEL 445-10

ON/OFF SWITCH
SMITTER LIGHTED
FULL SCALE IN WA
X1 X10

TV-100-12 Low Pass Filter
50 Watts Max. Below 30 Mc.
Can be used as output filter
up to 30 Mc. See Technical
E. L. DRAKE CO. HAWTHORNE, CALIF.

JOHNSON LOW PASS FILTER
52 OHM IMPEDANCE
CATALOG NO. 200-107
E. L. JOHNSON CO. WABEKA, OREG.

B&W
424
BARKER & WILLIAMSON, INC.

PROTAX
WATERS COAXIAL SELECTOR SWITCH MODEL 375

REFLECTED POWER METER
SENSITIVITY
FUNCTION



POSITION NO. _____
ENERGIZE TO CLOSE

TRANSMITTER
TYPE _____

In addition to the coaxial cable and connectors required in a coaxial transmission system, coaxial relays, switches, standing wave meters, attenuators and dummy loads are often included as operating conveniences. When choosing these coaxial accessories, the operating parameters should be evaluated in exactly the same way as for the cable and connectors. If the selected accessory exhibits excessive power loss or results in a large standing wave ratio, deterioration in transmission line efficiency may be expected.

Coaxial relays

Of all the coaxial accessories available, the coaxial changeover relay is probably the most important. In almost every amateur station where a coaxial transmission line is employed, some type of coaxial relay is used to switch the antenna between the receiver and transmitter. However, the indiscriminate selection and use of a coaxial relay may lead to problems, particularly in the VHF or UHF bands or when using a transistorized rf stage in the receiver.

Generally speaking, coaxial switches may be grouped into two general categories, depending upon the switching mechanism. The more familiar of these is the bladed variety, in which the center conductor of a coaxial section is actuated by a solenoid. Most relays in current use are of this type. In the second category, a moving coaxial section (both inner and outer conductors) transfers rf power by solenoid actuated rotation. This switch is the more complex of the two and is normally used only at frequencies above 500 mc.

The contact arrangement most commonly found is the single pole, double throw (SPDT) type, but other arrangements are available for special applications. Most coaxial relay manufacturers will provide additional auxiliary contacts at a slightly higher cost.

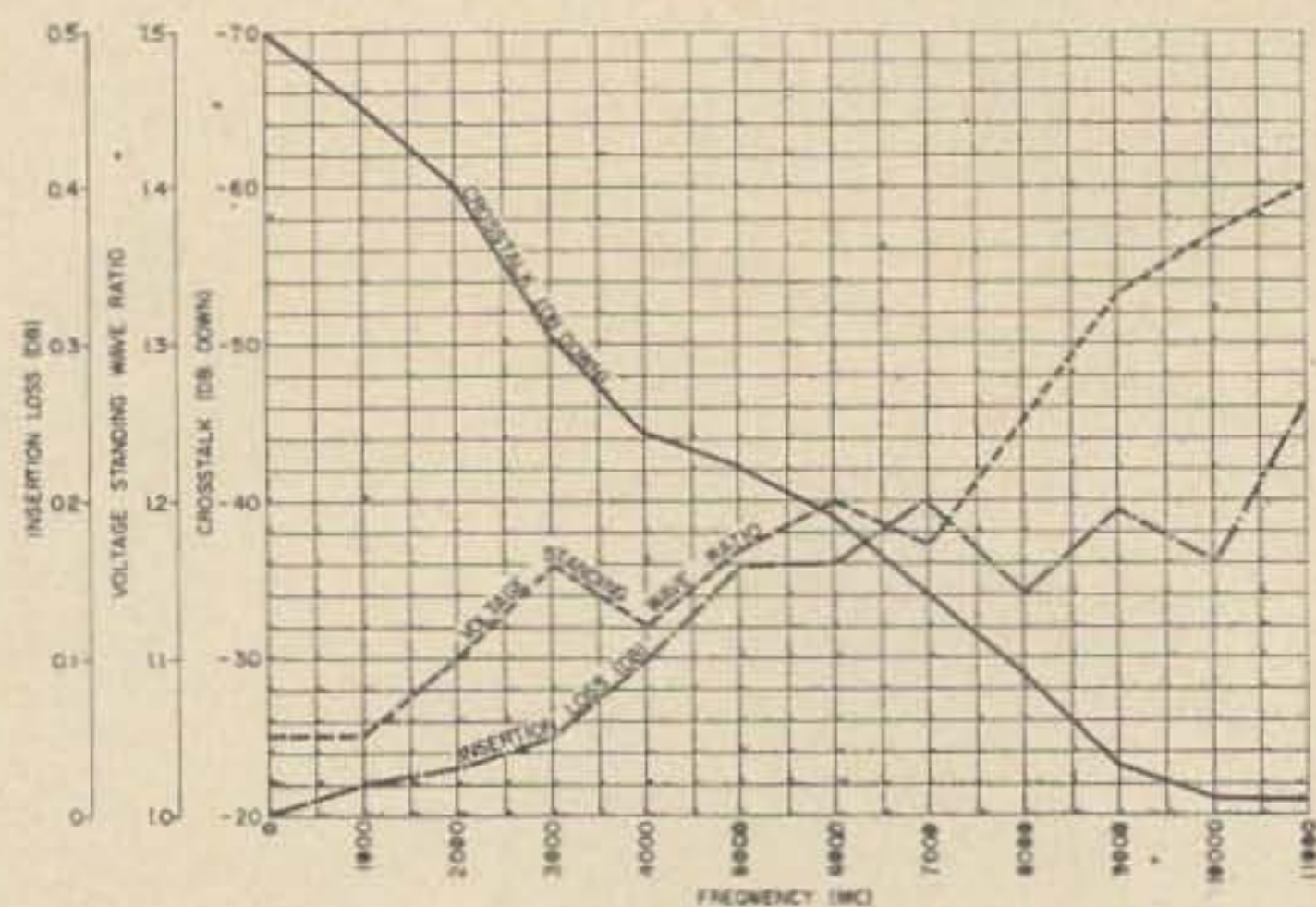


Fig. 1. Typical operating characteristics of the Transco Series-Y coaxial switches.

These contacts are useful for switching other circuits simultaneously with the antenna.

Once the basic type of switch and the required contact arrangement have been determined, the standing wave ratio, insertion loss and isolation of the switch should be reviewed.

The standing wave ratio is the major element of transmission efficiency through the switch. Basically, it is a comparison of the characteristic impedance of the switch to that of the transmission line into which it is installed. For most amateur applications, an SWR up to 1.5 or occasionally 2.0 is satisfactory, but seldom greater than 2.0:1.

Crosstalk is another important consideration. This is a measure of the rf leakage between the used and unused contacts of the relay. This relative isolation between contacts is expressed in "decibels down," meaning the leakage signal is down to some percentage of the operating signal. Since crosstalk is a result of the capacitive coupling between the operating and unused circuits, it increases at high operating frequencies (i.e., as the capacitive reactance decreases). At 400 mc, the single bladed coaxial switch exhibits typical crosstalk of 40 db down. To reduce crosstalk further, it is necessary to employ shorting contact construction in which the unused connector is terminated in a short-circuit. This is an absolute necessity when transistorized rf amplifiers are used in the receiver. The Dowkey DK-60G coaxial relay is of this type construction and exhibits greater than 100 db isolation at 500 mc.

Insertion loss is a measure of the power loss within the switch itself and is expressed as:

$$\text{Loss in db} = 10 \log \frac{(\text{power output})}{(\text{power input})}$$

This loss includes the resistive loss of the con-

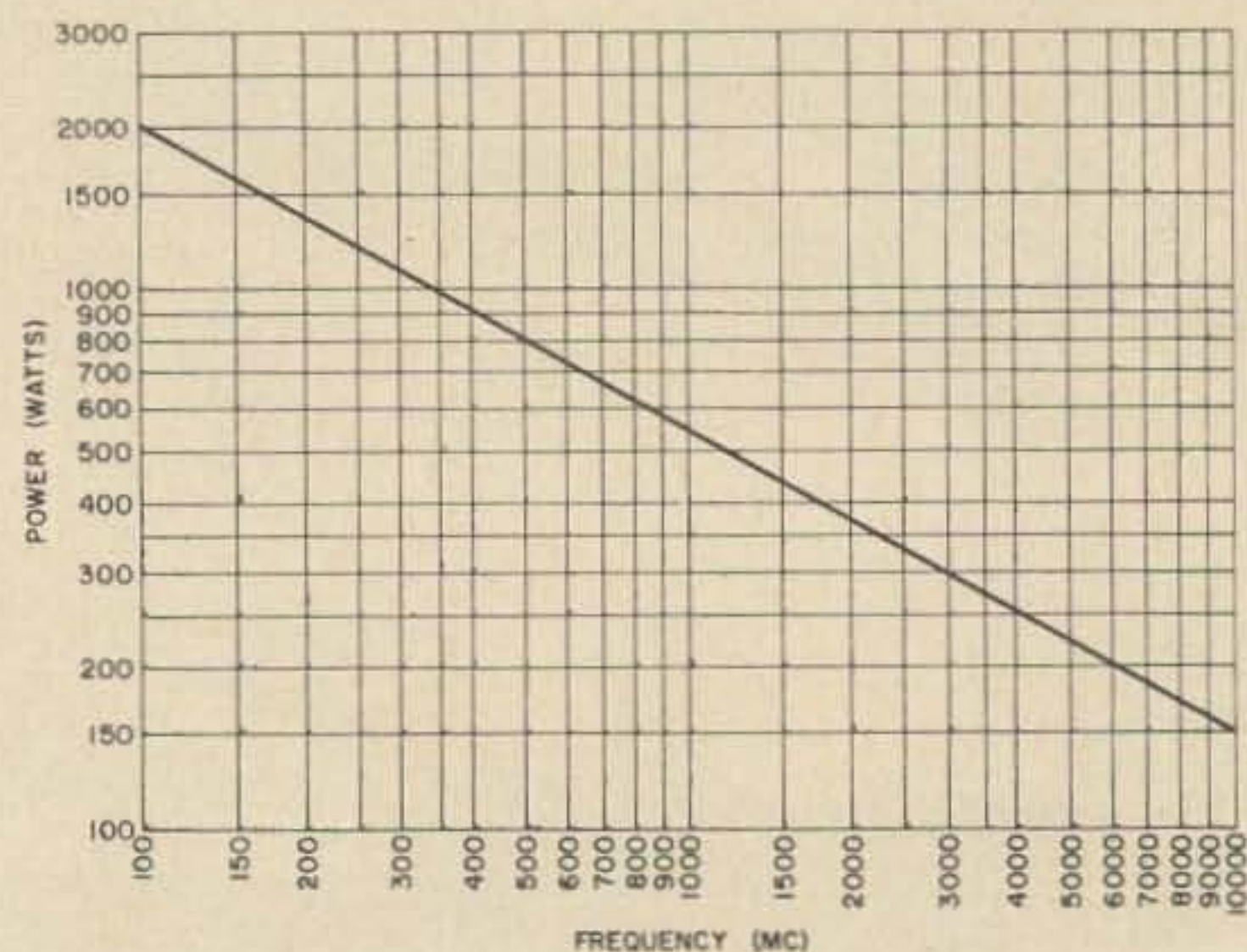


Fig. 2. Power handling ability of the Transco Series-Y coaxial switches.

Table 1. 50 ohm Coaxial Changeover Relays

Manufacturer	Switch Type	Model Number	SWR	Maximum Frequency	Power (watts)	Auxiliary Contact	Solenoid Voltages	Connector Types
Advance	SPDT	CB/1C	—	300	—	Yes	12, 24 VDC, 115 VAC	UHF
Amphenol	SPDT	315	1.15 at 500 mc	1000	100 at 1000 mc	No	6-120 VDC or AC	BNC
Amphenol	SPDT	316	1.20 at 2200 mc	2750	100 at 2750 mc	No	6-120 VDC or AC	BNC
Amphenol	SPDT	316	1.20 at 2400 mc	4000	100 at 4000 mc	No	6-120 VDC or AC	N
Amphenol	SPDT	317	1.20 at 2200 mc	2750	100 at 2750 mc	No	26 VDC, 115 VAC	BNC
Amphenol	SPDT	317	1.20 at 2400 mc	4000	100 at 4000 mc	No	26 VDC, 115 VAC	N
Amphenol	SPDT	318	1.20 at 2200 mc	2750	100 at 2750 mc	No	26 VDC	BNC
Amphenol	DPDT	321	1.15 at 500 mc	1000	100 at 1000 mc	No	115 VAC	BNC
Dow-Key	DPDT	DK2-60	1.15 at 500 mc	500	1000 at 500 mc	Yes	6-220 VDC or AC	BNC, N, C, UHF
Dow-Key	SPDT	DK-60	1.50 at 500 mc	500	1000 at 500 mc	Yes	6-220 VDC or AC	BNC, N, C, UHF
Dow-Key	SPDT	DK-61	1.10 at 400 mc	1000	100 at 1000 mc	Yes	6-220 VDC	BNC
Dow-Key	SPDT	DK-67	1.30 at 2000 mc	2000	100 at 2000 mc	Yes	6-220 VDC or AC	BNC
Dow-Key	SPDT	DK-77	1.10 at 400 mc	1000	250 at 1000 mc	Yes	6-110 VDC	BNC
Magnecraft	SPDT	128	1.25 at 500 mc	500	100 at 400 mc	Yes	12, 24 VDC, 115 VAC	UHF

tacts, the dielectric loss of the insulators and any reflective loss due to impedance discontinuities. The dielectric loss is normally quite low in modern coaxial relay design and the resistive and reflective losses contribute most to the overall insertion loss of the unit. The resistive losses are minimized by using short, silver-plated conductors but the reflective loss is more difficult to control, especially at high frequencies. However, up to about 1000 mc, the insertion loss of well designed coaxial switches is negligible when compared to the transmission lines with which they are used.

Most coaxial relay manufacturers have a wide assortment of units available which will satisfy nearly any application. These relays may be furnished with 6 volt to 220 volts ac or dc solenoids, UHF, BNC, N, or C connectors, power ratings up to 1000 watts at 1000 mc and low standing wave ratios up to 10,000 mc. Although the Dow-Key line of coaxial relays probably finds the greatest use in amateur stations because of their wide availability and relatively low cost, other manufacturers include Advance, Amphenol, Magnecraft and Transco. Table 1 lists the operating characteristics of the major types of coaxial relays available from these manufacturers.

Whereas most of the switches in Table 1 are of the leaf variety, the Transco relay uses a moving coaxial section for greater power handling, isolation and low SWR characteristics up to 11,000 mc. This unit was designed

to meet the requirements for a small, light-weight, coaxial switch having good rf characteristics over a broad bandwidth and is widely used by the military. In the Transco switch, two independently operating solenoids allow either make before break or break before make operation. Also, rf positions may be both on or off simultaneously. For the UHF enthusiast the surplus Transco switch offers superior operating characteristics at a modest cost. Typical operating and power handling properties of this unit are shown in Fig. 1 and 2.

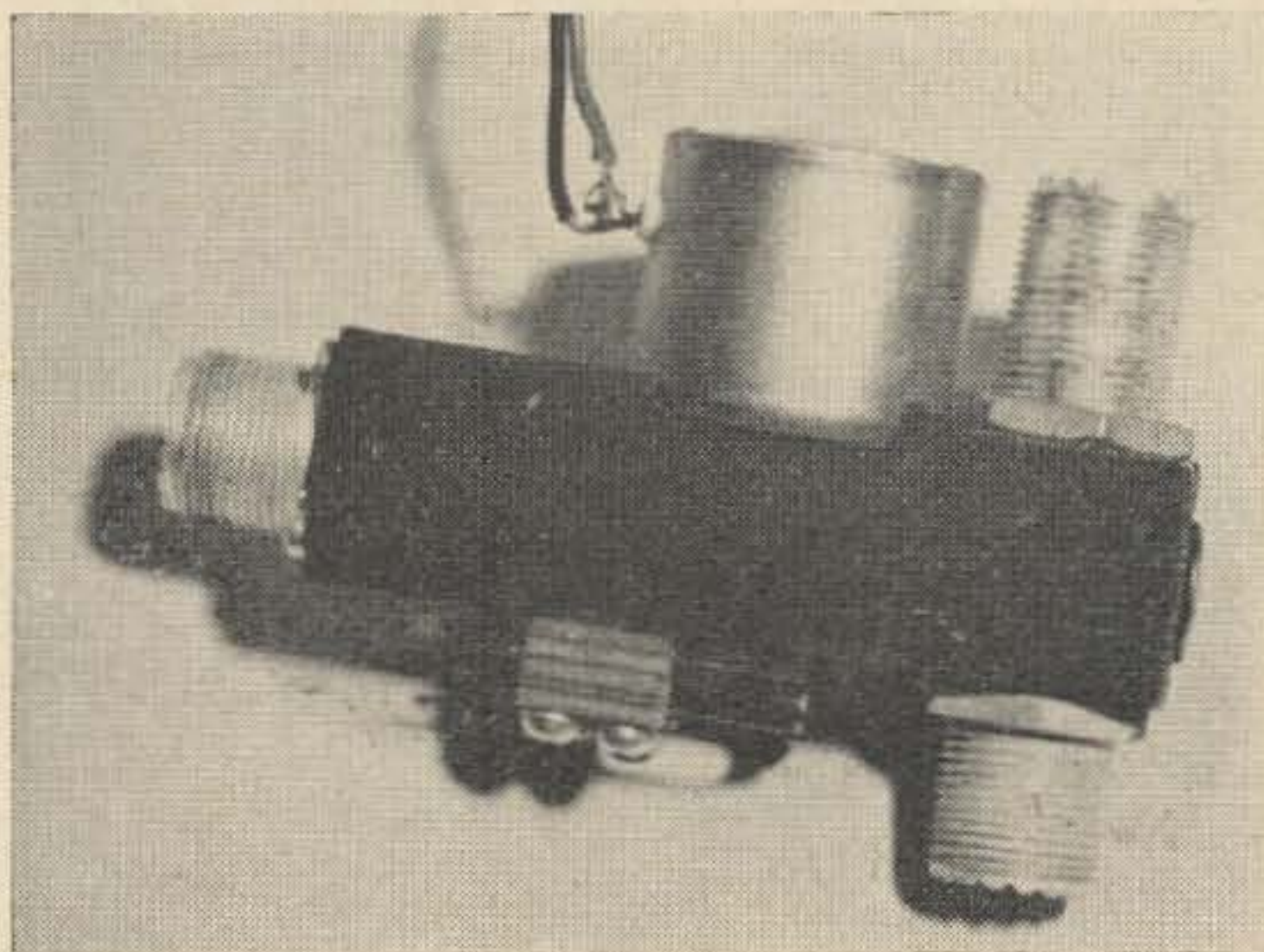


Photo by WA6IAK.

The Dow-Key Model DK60-G2C coaxial relay. The design of this unit is such that it provides excellent isolation up to 500 mc with minimum insertion loss.

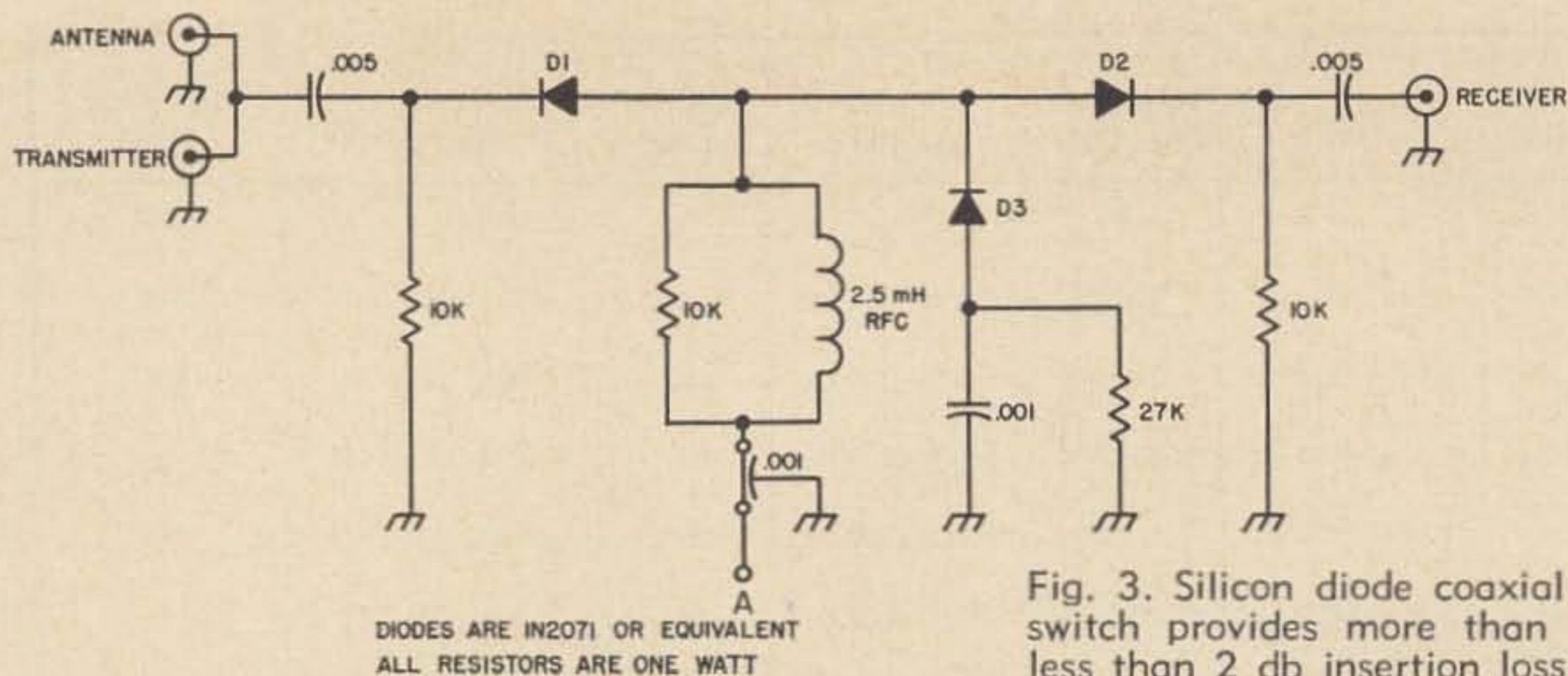


Fig. 3. Silicon diode coaxial antenna switch. This switch provides more than 80 db isolation with less than 2 db insertion loss.

Although the coaxial type of changeover relay seems like the simplest and most direct way of switching the transmission line from transmitter to receiver, it is somewhat noisy and in some cases, slow. There have been several electronic T-R switches introduced over the past few years, first with vacuum tubes and more recently with silicon diodes, which solve these problems. The solid state diode switch for example, is extremely fast, completely noiseless, exhibits up to 80 db of isolation with only 2 db insertion loss and is very simple and economical to build. The simplest of these switches is illustrated in Fig. 3. This switch uses three inexpensive silicon diodes, a few bias resistors, several capacitors and a choke to perform efficient switching of

coaxial transmission lines up to 30 mc. To understand the mechanics of this switch, it must be remembered that a reverse biased diode presents an extremely high impedance while the forward biased device looks essentially like a short-circuit. With these facts in mind, consider the operation of this three diode switch when a positive voltage is applied to point A; diode D1 and D2 will conduct and present a low impedance while diode D3 presents a high impedance because it is reverse biased. Under this condition an rf signal on the antenna passes to the receiver with very little attenuation.

If a negative voltage is introduced at point A however, diode D1 and D2 will no longer conduct and diode D3 will present a low impedance to ground because it is forward biased. Any rf signal on the antenna is confronted by the high impedance presented by the reverse biased diode D1. A certain amount of rf energy will leak by this high impedance, but the high impedance presented by diode D2 must still be surmounted. A much easier path for the rf exists through the low impedance path to ground provided by diode D3 and the series bypass capacitor. With this type of switching up to 80 db isolation can be obtained with a minimum of effort.

One of the most important considerations in diode switches is the amount of rf power they can safely handle. Actually, there are two separate and distinct ratings that are of interest; peak power and average power. The peak inverse voltage (PIV) rating of the diode determines the maximum peak power that the diode can control. The average power which the diode can safely switch is dictated by its power dissipation and series resistance. Since the series and shunt diode circuits operate in somewhat opposite ways, it would not be unusual to expect that their power ratings might be different. This is in-



Photo courtesy Barker & Williamson, Inc.
The B&W electronic T-R switch is an automatic unit that automatically switches the transmission line from receiver to transmitter when transmitting. This type of a switch is ideal for break-in operation and results in substantial receiver gain in most installations.

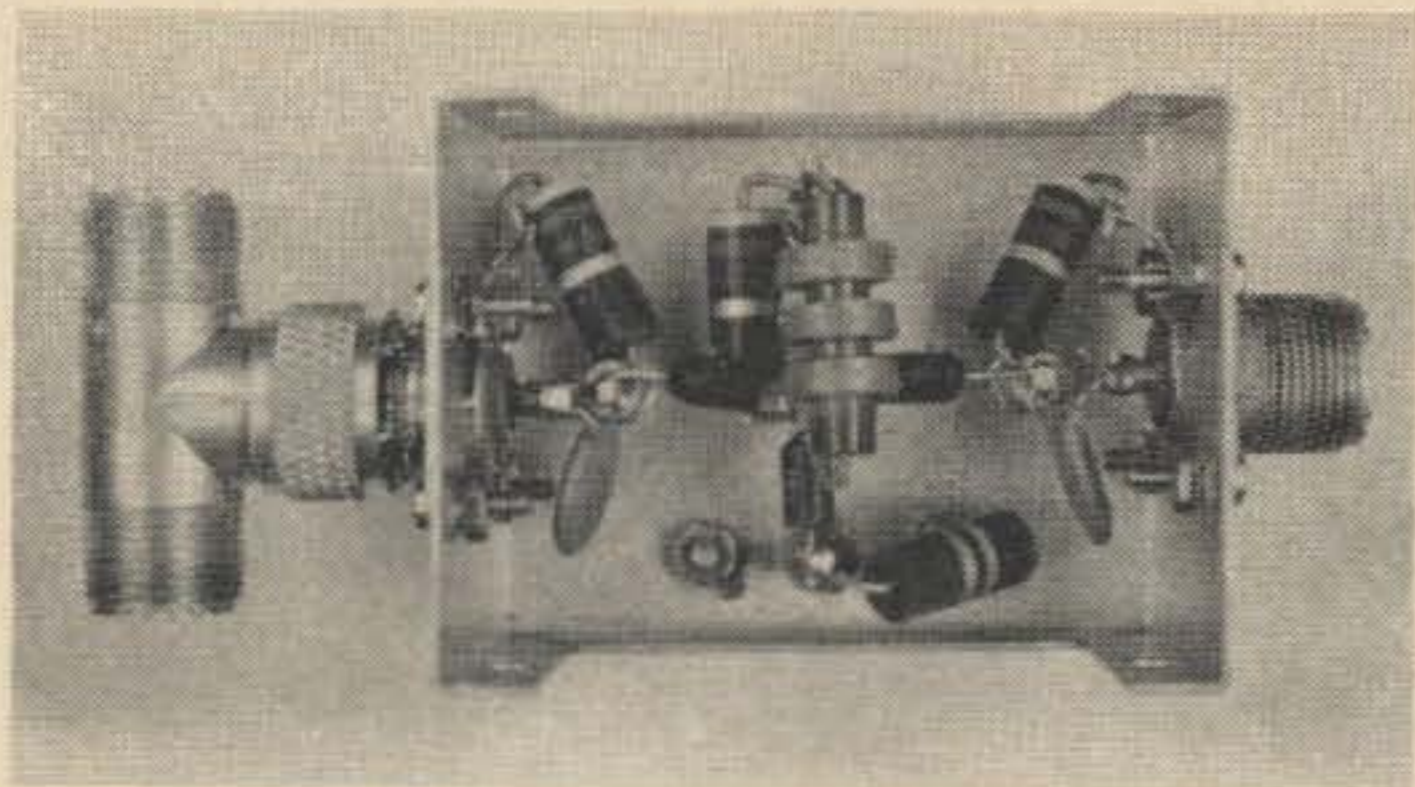


Photo by VE2AUB.

This simple silicon diode controlled T-R switch provides more than 80 db isolation and less than 2 db insertion loss from 3.5 to 30 mc. This unit uses three inexpensive silicon diodes and may be easily duplicated in the home workshop.

deed the case and it is interesting to note that although the shunt circuit has twice the peak power rating of the series circuit, its average power rating is only one-quarter as much as that of the series arrangement. For 50 ohm coaxial transmission lines operating with an SWR of 1:1, the respective power ratings may be calculated from the following equations:

Series

$$\text{Peak power} = (\text{PIV})^2/1600$$

$$\text{Average power} = 25 P_d$$

Shunt


$$\text{Peak power} = (\text{PIV})^2/400$$

$$\text{Average power} = 6.25 P_d$$

Where: PIV = Peak inverse rating of the diode (volts)

P_d = Power dissipation rating of the diode (watts)

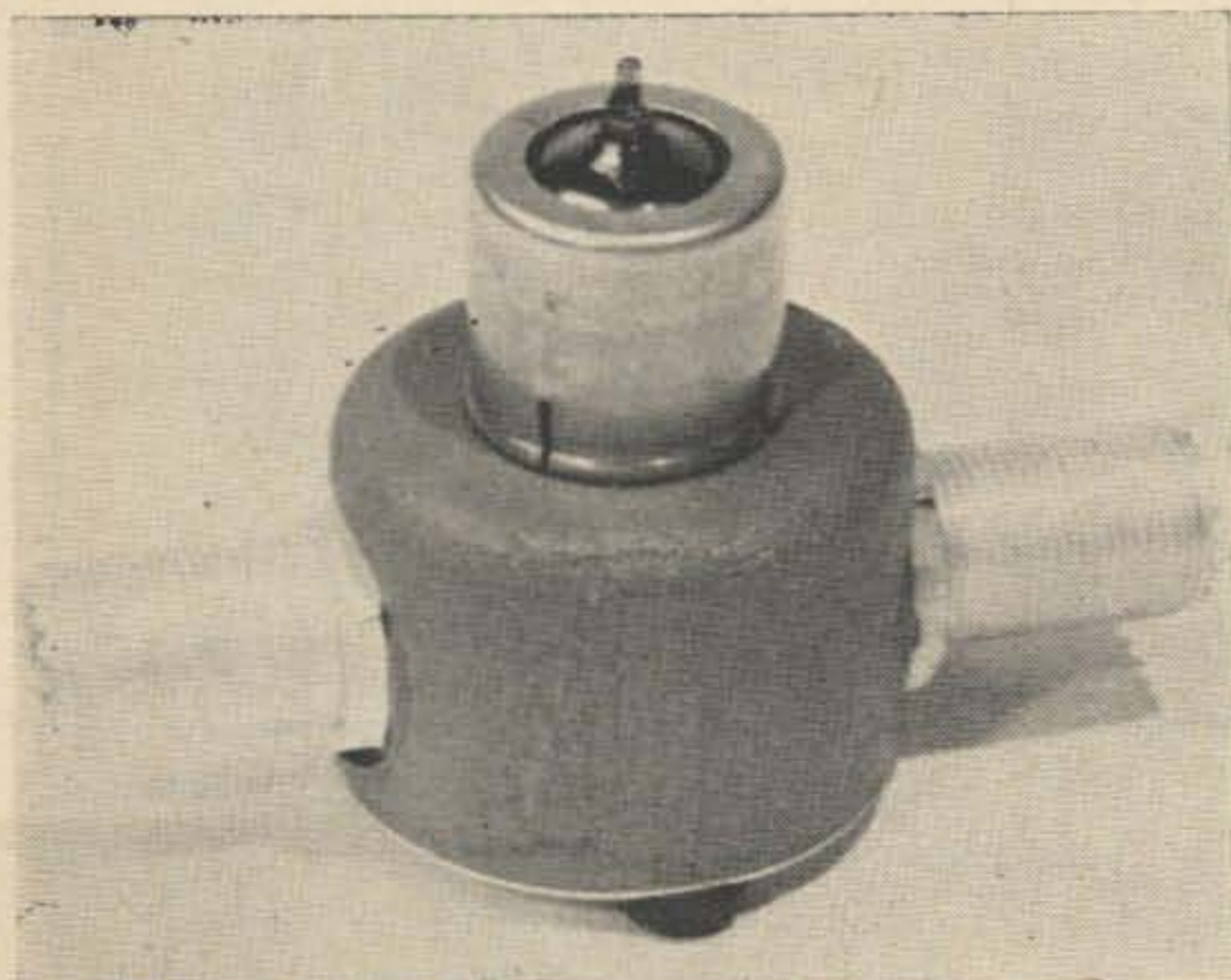From these formulas it can be readily found that to control the peak power of a 1000 watt



The Dow-Key DK1 is an untuned electronic transmit-receive switch for coaxial lines which may be used from 80 through 10 meters.

CW transmitter operating at 70% efficiency (700 watts into the transmission line), a series diode would require a PIV of 1058 volts; under the same conditions a shunt switching diode would require a PIV of 529 volts. For insurance against blowing the diodes under peak power loads or SWR changes, a safety factor of 50% should be added to these figures. In the diode switch in Fig. 3, both the shunt and series diodes are used, so both of the above power formulas must be considered in using a switch of this type.

Coaxial switches

When it is necessary to switch several circuits simultaneously or to increase the number of throws over the simple SPDT coaxial changeover relay, the most straightforward approach is to use a rotary coaxial switch. With these units, switching may be accomplished in a fraction of a second, thereby eliminating the need for screwing and unscrewing coaxial fittings and the possibility of an incorrect connection.

These switches are available in both manual and solenoid operated versions suitable for frequencies up to 1000 mc. Usually the leaf-type wafer switch is used as the switching mechanism, but more expensive types employ a moving coaxial section similar to that illustrated in Fig. 4.

Selection of rotary coaxial switches is much the same as that for coaxial relays, with SWR, isolation, and power capacity being the main points of interest. For comparison purposes, the operating characteristics of various rotary

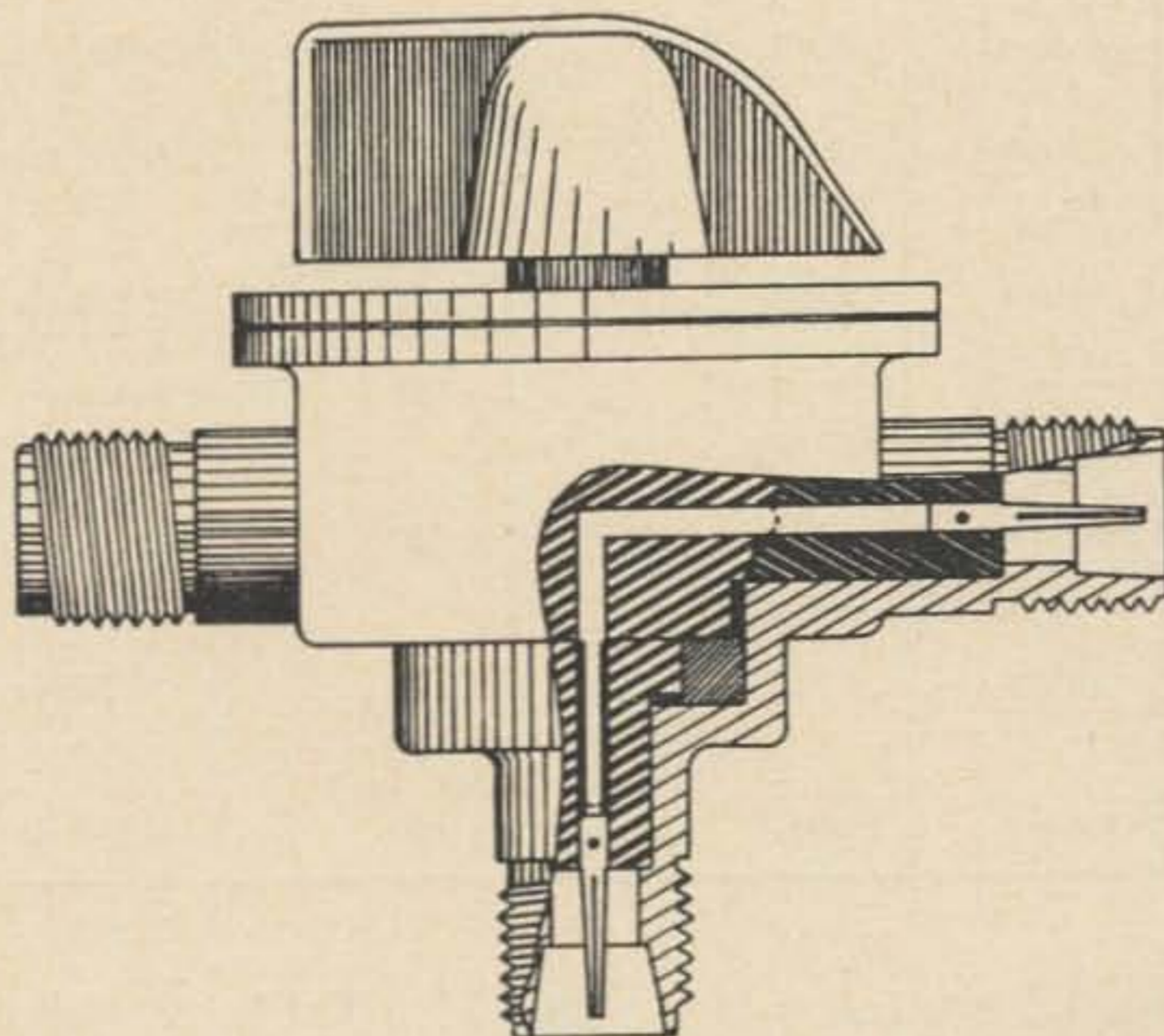


Fig. 4. Cross section of a coaxial switch which has a low standing wave ratio up to several thousand megacycles. Note that both the inner and outer conductors are switched together.

Table 2. Coaxial Switches

Manu- facturer	Switch	Model Number	Impedance (ohms)	SWR	Maximum Frequency	Power (watts)	Isolation	Connectors
B & W	SP5T	550A	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
B & W	SP2T	550A2	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
B & W	Single Transfer	551A	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
B & W	SP5T	560	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	BNC
B & W	Single Transfer	561	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	BNC
B & W	SP5T	570	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	N
B & W	SP5T	580	52 or 75	—	50 mc	250 at 50 mc	45 db at 30 mc	Phono
B & W	SP5T	590	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
B & W	2P2T	591	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
B & W	SP2T	592	52 or 75	—	50 mc	1000 at 50 mc	45 db at 30 mc	UHF
Dow-Key	SPDT	DK78-2	50	1.10 at 500 mc	500 mc	1000 at 500 mc	60 db at 400 mc	UHF, BNC, C, N
Dow-Key	SP3T	DK78-3	50	1.10 at 500 mc	500 mc	1000 at 500 mc	60 db at 400 mc	UHF, BNC, C, N
Dow-Key	SP6T	DK78-6	50	1.10 at 500 mc	500 mc	1000 at 500 mc	60 db at 400 mc	UHF, BNC, C, N
Dow-Key	Single Transfer	DK78-T	50	1.10 at 500 mc	500 mc	1000 at 500 mc	50 db at 400 mc	UHF, BNC, C, N
Dow-Key	SP6T	DK71	50	1.10 at 100 mc	500 mc	1000 at 500 mc	40 db at 100 mc	UHF, BNC, C, N
Dow-Key	SP3T	DK-72	50	1.10 at 100 mc	500 mc	1000 at 500 mc	40 db at 100 mc	UHF, BNC, C, N
PIC	SP5T	PS750	50 or 72	1.2 at 100 mc	100 mc	1000	45 db at 30 mc	UHF
PIC	SPDT	PS751	50 or 72	1.2 at 100 mc	100 mc	1000	45 db at 30 mc	UHF
PIC	Single Transfer	PS752	50 or 72	1.2 at 100 mc	100 mc	1000	45 db at 30 mc	UHF
Sentry	SP3T	—	52 or 75	—	50 mc	250 at 50 mc	—	UHF
Waters	SP6T	335	50	1.20 at 150 mc	150 mc	1000	—	UHF
Waters	Single Transfer	336	50	1.20 at 150 mc	150 mc	1000	—	UHF
Waters	SPDT	341	50	1.20 at 150 mc	150 mc	1000	—	UHF
Waters	Dual Transfer	351	50	1.20 at 150 mc	150 mc	1000	—	UHF
Waters	SP6T	375 Protax	50	1.2 at 150 mc	150 mc	1000	—	UHF
Waters	SP5T	376 Protax	50	1.2 at 150 mc	150 mc	1000	—	UHF
Waters	SP5T	378	50	1.2 at 150 mc	150 mc	1000	—	UHF

coaxial switches are listed in Table 2. The majority of coaxial switches currently available fall into one of the six basic switching configurations illustrated in Fig. 5.

Selector switches were designed primarily

for switching the output (or input) of a coaxial transmission line between various antennas, or dummy loads. However, they may be used in any installation where similar type switching is desired. The single transfer

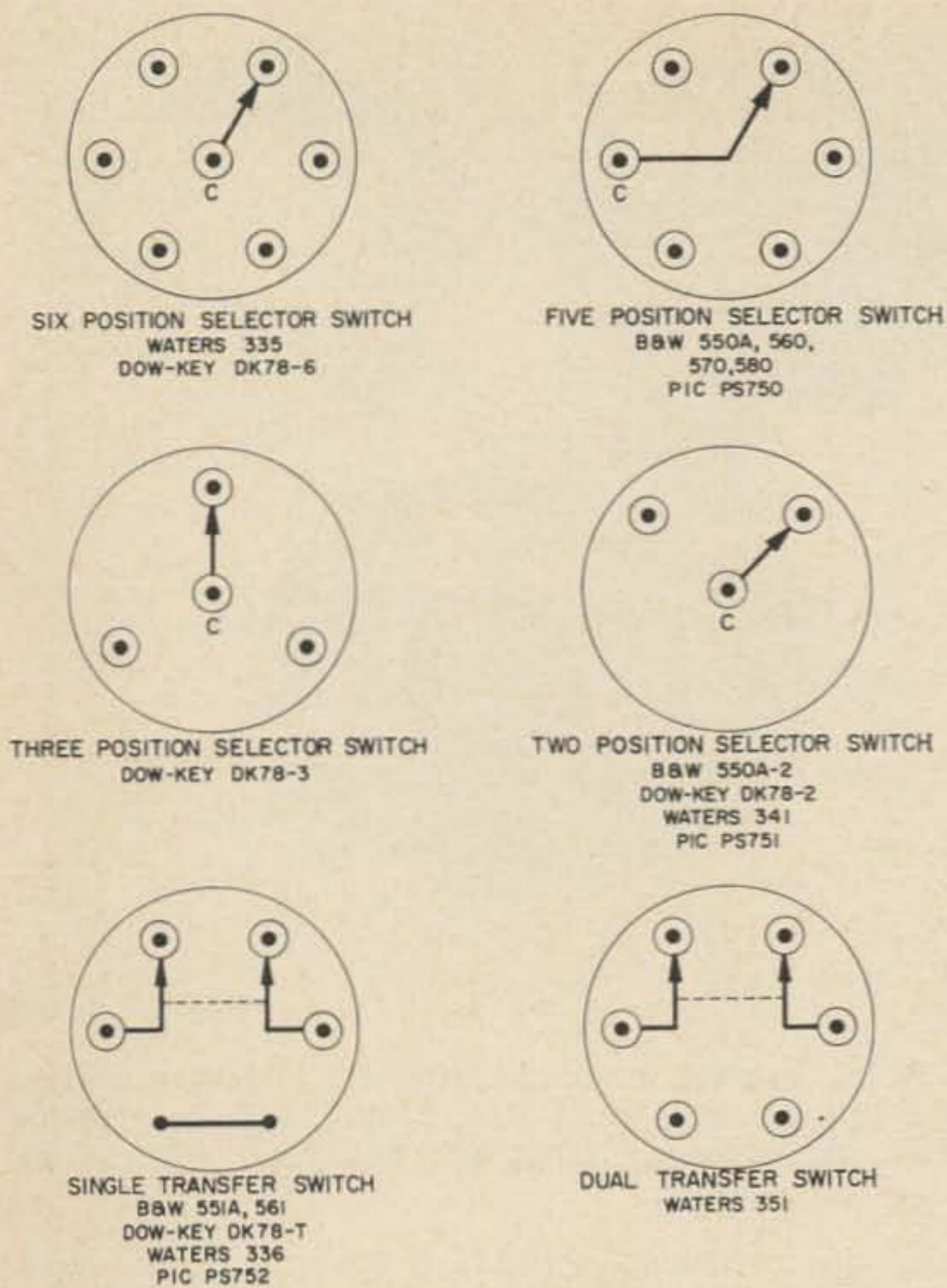


Fig. 5. Switch contact arrangements of commercial coaxial switches.

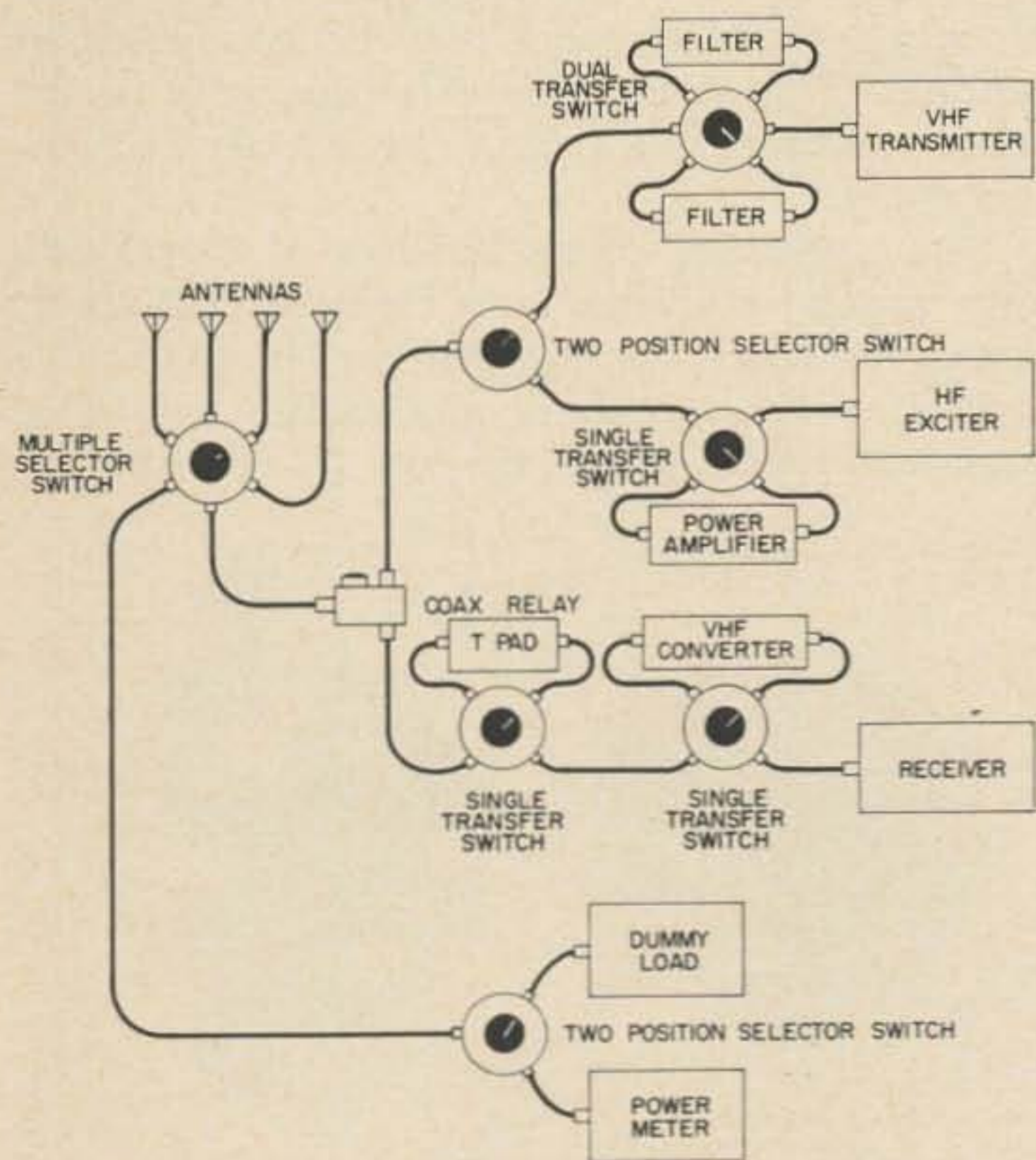


Fig. 6. A typical coaxial switching arrangement, with all the coaxial switching requirements of a ham station being accomplished with coaxial switches. This arrangement is much handier than screwing and unscrewing fittings every time you want to change a cable.

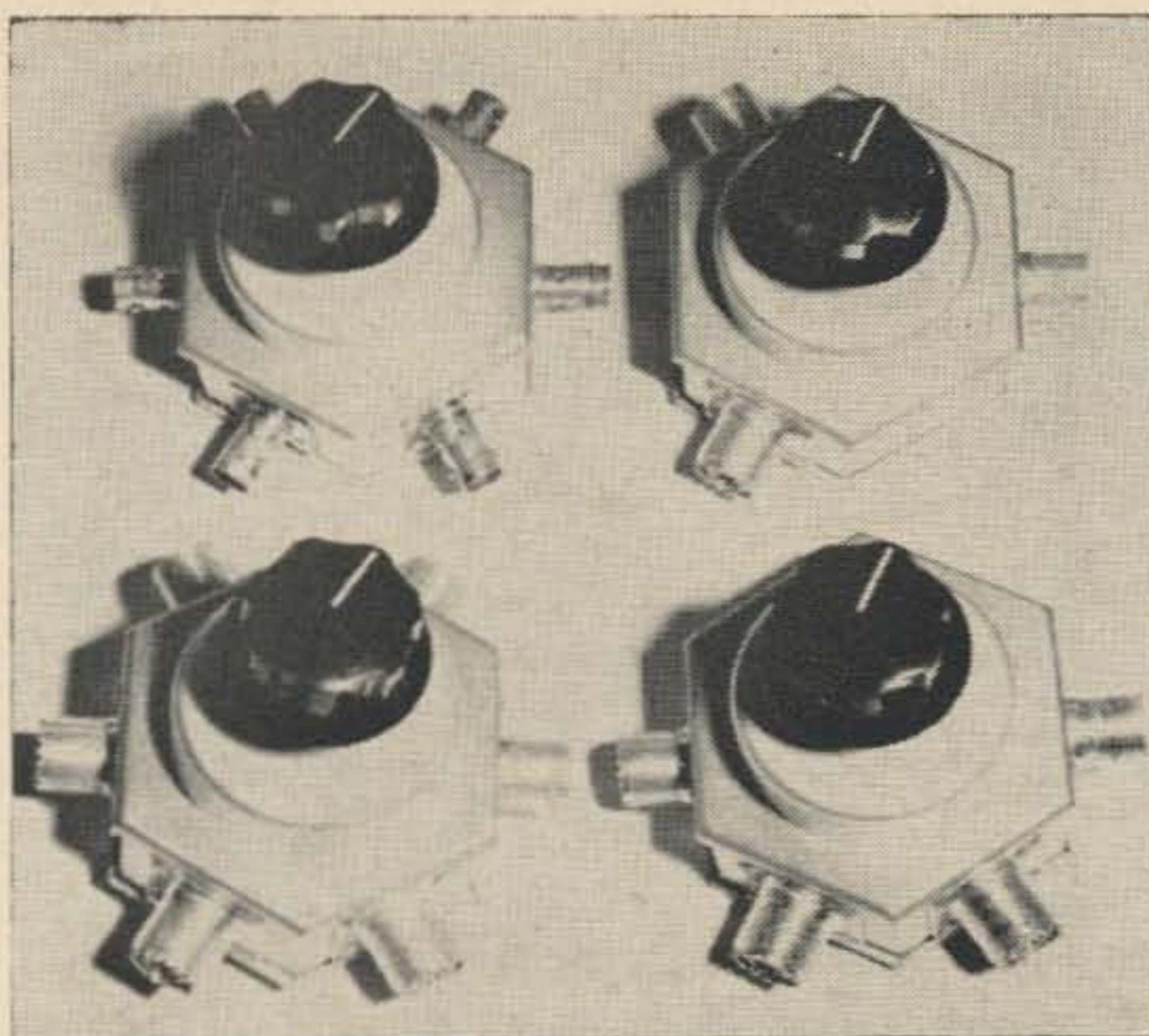


Photo by WA6IAK.

Several Barker and Williamson coaxial switches. Clockwise from the upper left: Model 560 with BNC connectors, Model 550A2 with UHF connectors, Model 551A coaxial transfer switch and Model 550A with UHF connectors.

switch is intended for switching various devices in or out of series connection with low impedance coaxial lines. Some of the uses are switching antenna current meters, antenna tuning devices, baluns, etc., in or out of the antenna feedline system. They may also be used to switch coaxial coupled power amplifiers in or out of the antenna circuit at will, thereby permitting the exciter to be connected directly to the antenna during local communications. The dual transfer switch is useful in switching converters, filters, etc., in



Photo courtesy Polyphase Instrument Co.

The PIC Polyswitch is a compact rf switch of modern design which may be used with a full 2 kilowatts PEP up to 100 mc. These switches are available in three basic models which will satisfy nearly any requirement.

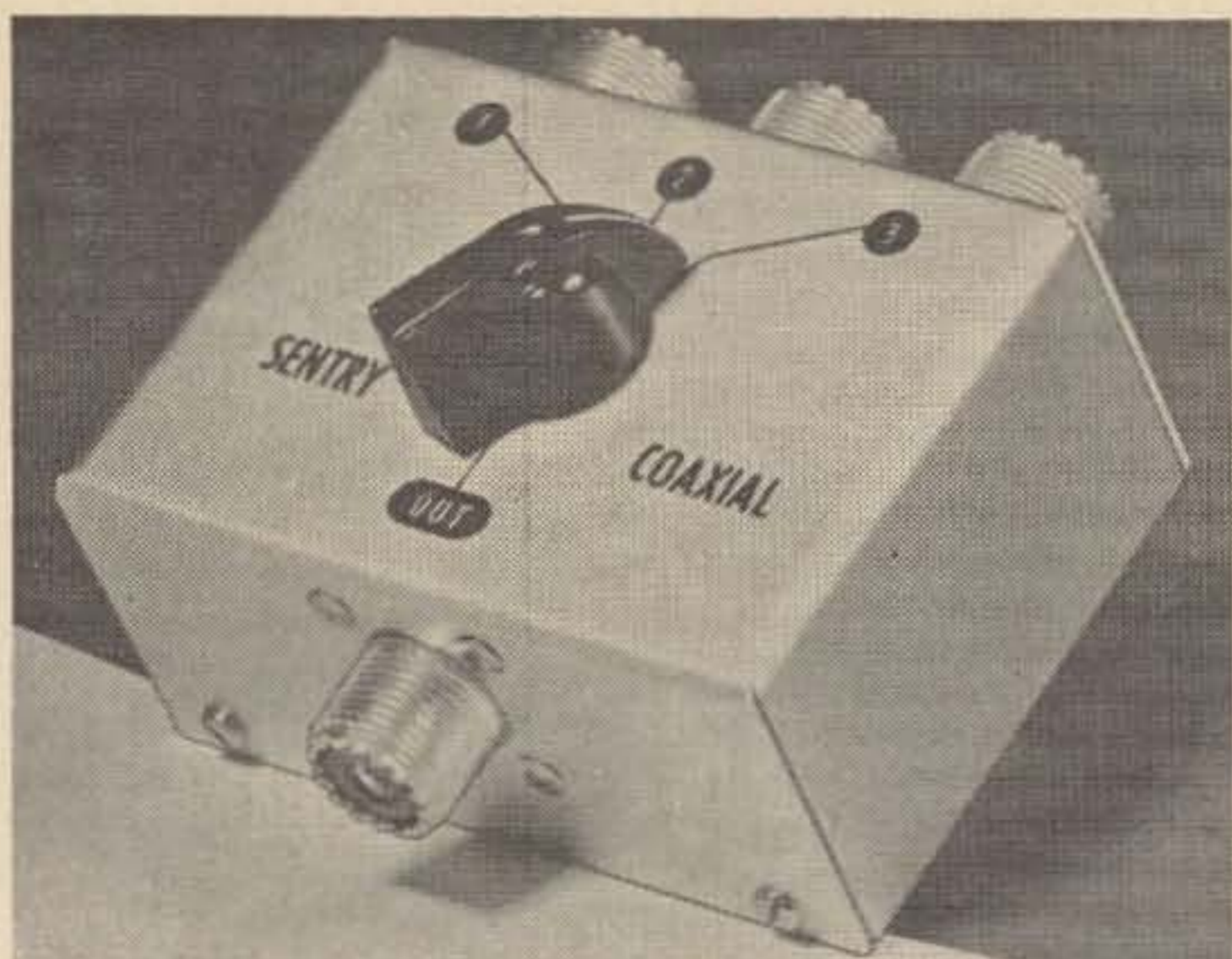


Photo courtesy Sentry Manufacturing Co.

The Sentry SP3T coaxial switch may be used to switch up to three coaxial transmission lines. It is furnished with standard series UHF connectors and will handle up to 250 watts of rf power.

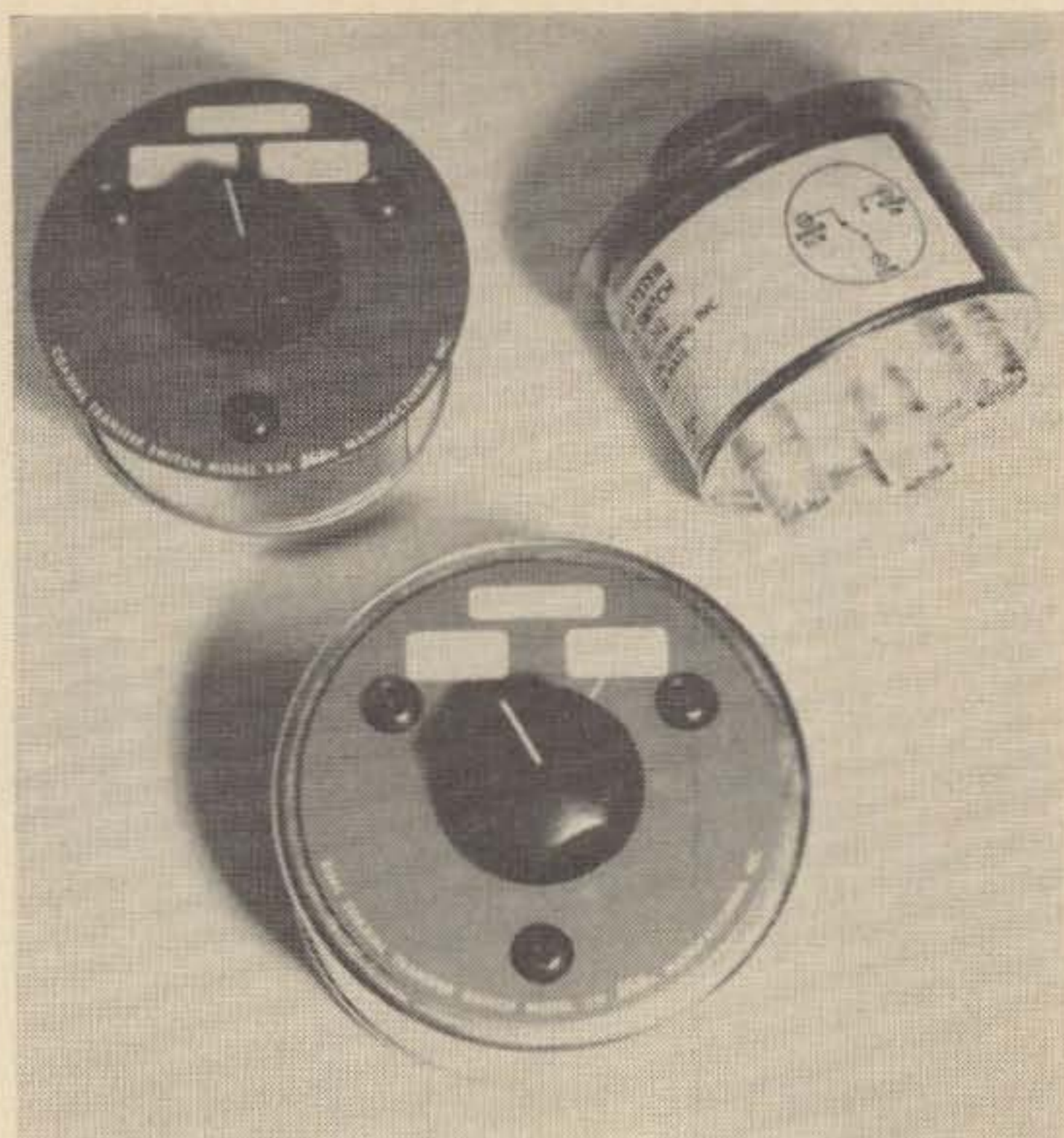


Photo by WA6IAK.

Several Waters coaxial switches. Clockwise from the upper left: Model 336, Model 341 and Model 351. All these switches are equipped with series UHF connectors.

and out of the transmission system. Some typical applications for these switches are depicted in Fig. 6.

In addition to their normal line of single section coaxial switches, Barker and Williamson offers multiple gang types where up to six single gang switches may be connected in tandem. This arrangement is especially useful where several circuits must be switched simultaneously.

The operating characteristics of the Dow-Key coaxial switches are charted in Fig. 7. These switches do not use the simple wafer switch as the switching mechanism and offer excellent rf characteristics up to 500 mc. In

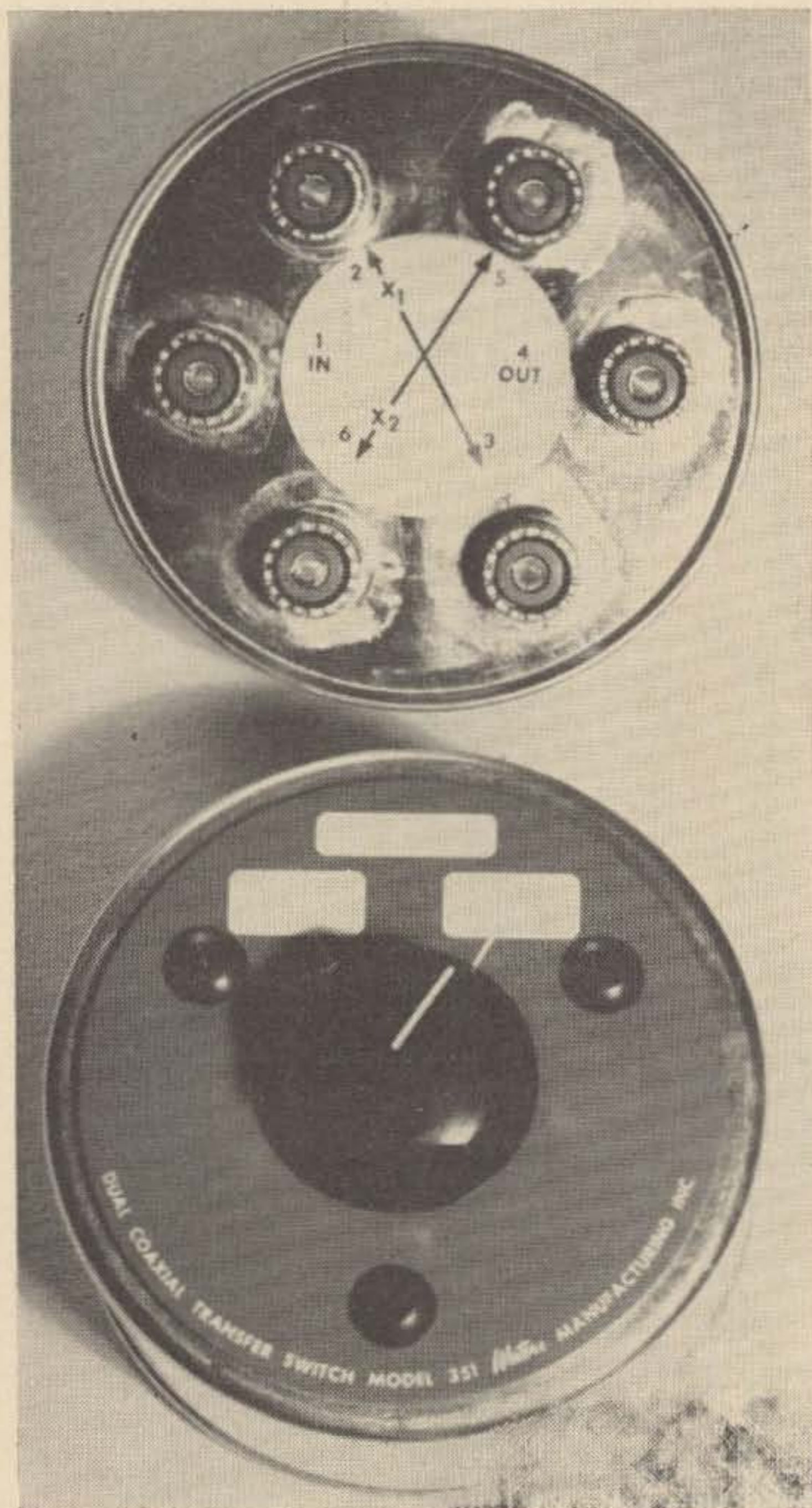


Photo by WA6IAK.
The Waters Model 351 coaxial transfer switch.

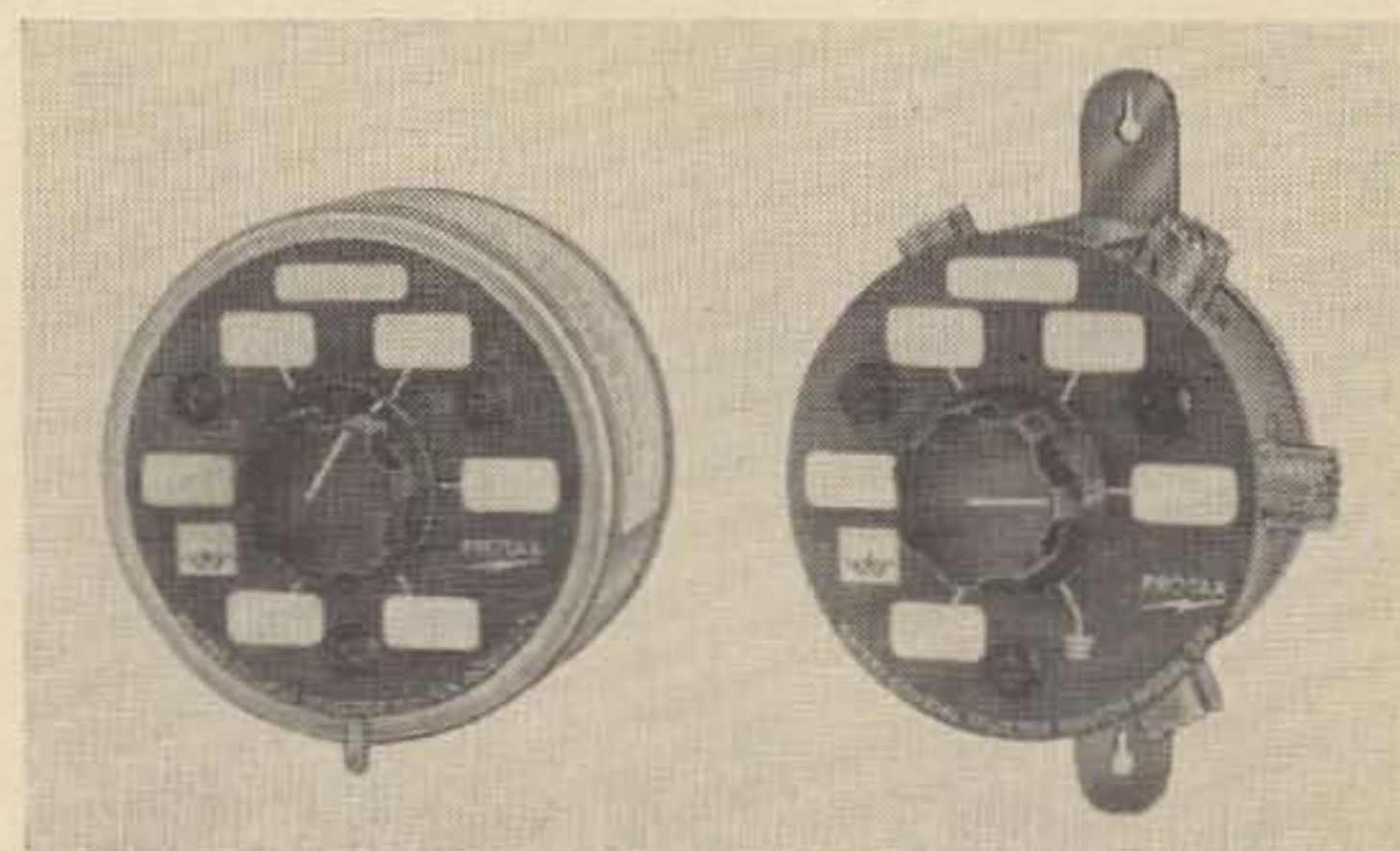


Photo courtesy Waters Manufacturing Inc.

Waters' Protax™ coaxial antenna switches are designed to ground all the station antennas when the rig is not in use. The Model 375 on the left is made for panel mounting and has six connectors mounted in the rear. The Model 376 on the right has five side mounted connectors and is made for wall mounting.

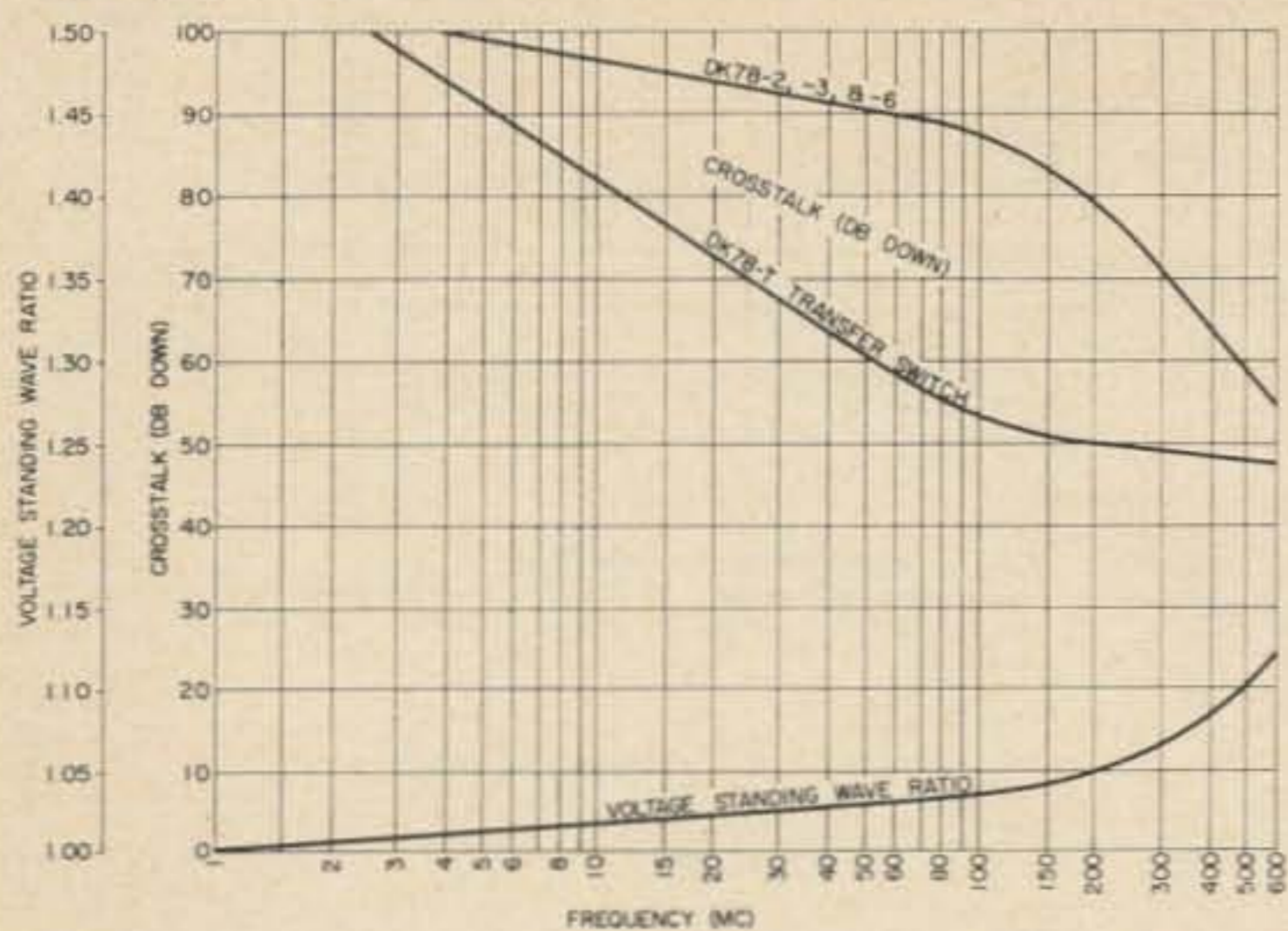


Fig. 7. Typical operating characteristics of the Dow-Key coaxial switches. Note that these switches provide low standing wave ratios and high isolation even at 500 mc.

In addition to their manually operated switches, Dow-Key offers electrically operated units that may be used for remote switching of antennas, transmission lines or other equipment. These switches (series DK71 and DK72) exhibit essentially the same operating characteristics as the DK78 series (Fig. 7). These units are in waterproof housings with mounting straps suitable for direct installation to outdoor antenna masts. With this type of installation, up to six antennas may be fed with one coaxial line.

The Polyphase Instrument Company (PIC) offers several compact coaxial switches that will handle up to 1000 watts at moderate rf frequencies. The main advantage of these switches is their small size.

Waters coaxial switches are mounted in sealed metal cases and are furnished with an appropriate self-marking escutcheon plate and molded phenolic knob. These switches are furnished with UHF connectors mounted on the rear side of the switch; this connector arrangement minimizes behind-the-panel installation space and eliminates the necessity for auxiliary coaxial elbow fittings. Waters switches are rated at 1000 watts and exhibit an SWR of less than 1.2:1 up to 150 mc.

A recent addition to the Waters line of coaxial switches is the "Protax." Basically, this model is two switches in one; a regular antenna selector switch with a rating of 1000 watts and an auxiliary contact for grounding all antennas (leaving the receiver input open) when the transmitter is not in use. This arrangement is designed to minimize the danger of injury or fire during electrical storms. Protax switches are available in either five or six position configurations with UHF type connectors.

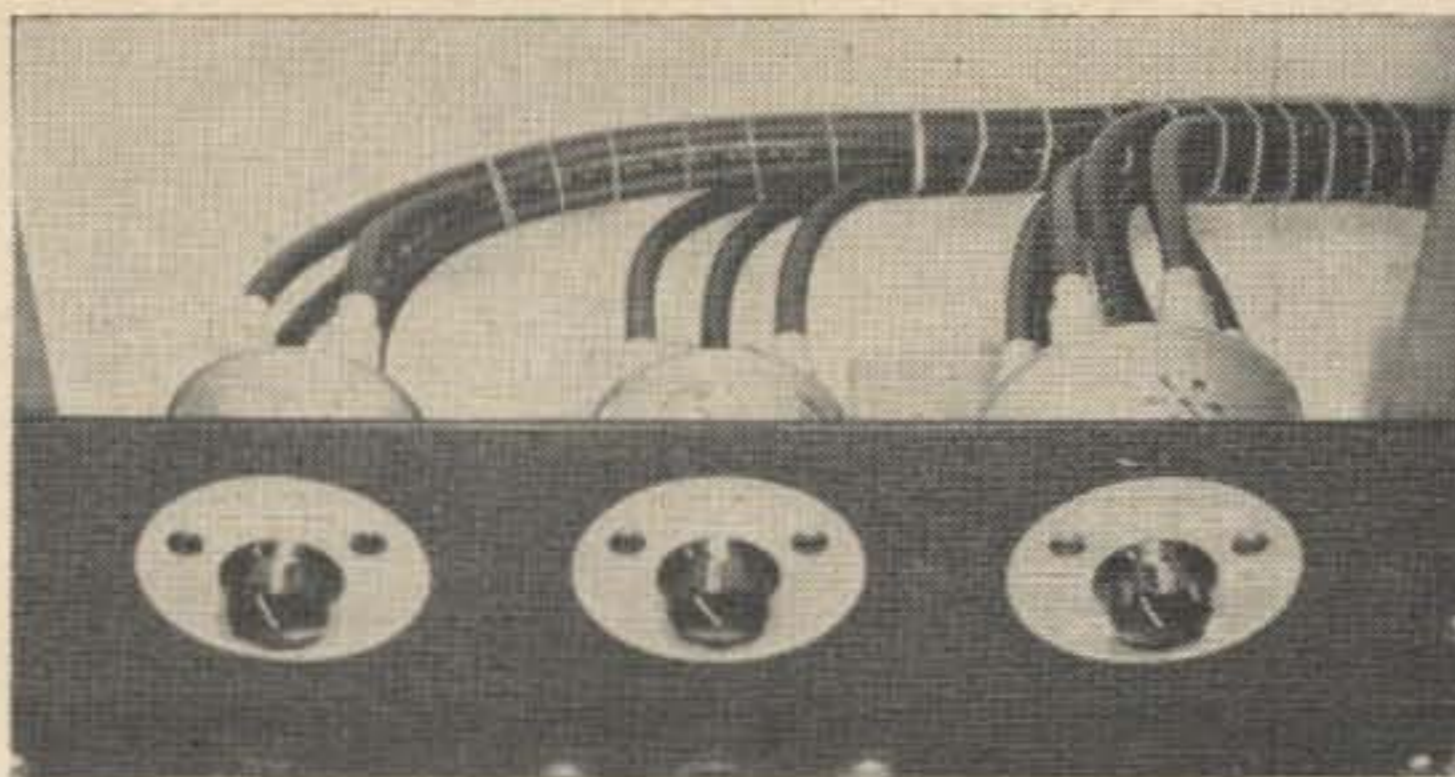


Photo courtesy Waters Manufacturing Co.

A neat coaxial switch installation. These switches are arranged for switching the receivers, transmitters and antennas in a typical amateur station.

Standing wave meters

One of the most convenient methods of monitoring coaxial transmission line operation is the standing wave meter. There are many devices available for this purpose as indicated in Table 3, but most of the currently available units use the familiar "monimatch" design introduced in the 1950's. Standing wave meters built using this principle may be left in the transmission line at all times without affecting line performance.

It is essential to the understanding of the directional coupler or reflectometer type of standing wave meter to realize that the current and voltage of the rf power propagating along a transmission line toward the load are in phase. On the other hand, it must be further understood that the reflected components of voltage and current are exactly 180 degrees out of phase. This may be a little difficult to envision, but none the less it is true, and al-



Photo by WA6IAK.

A surplus coaxial switch that is actuated by a toggle lever. This switch has excellent operating characteristics and may be used up to several thousand megacycles.

though it is beyond the scope of this handbook to explain wave mechanics, complete details have been included in many articles and in most antenna and transmission line handbooks.

When the load is perfectly matched to a transmission line, all the power which is transmitted toward the load (incident) is dissipated by the load. If the load does not match the transmission line however, a portion of the incident or forward power is reflected; the reflected components of voltage and current combine with the forward components to produce standing waves. The standing waves are so called because they have a fixed position for any given load impedance. When the reflected and incident components combine, a voltage (or current) maximum occurs where the two components are in phase, and where they are out of phase, a minimum occurs.

The directional coupler takes advantage of the fact that the forward components are in phase while the reflected components are 180 degrees out of phase. The pickup unit which most manufacturers are currently using was

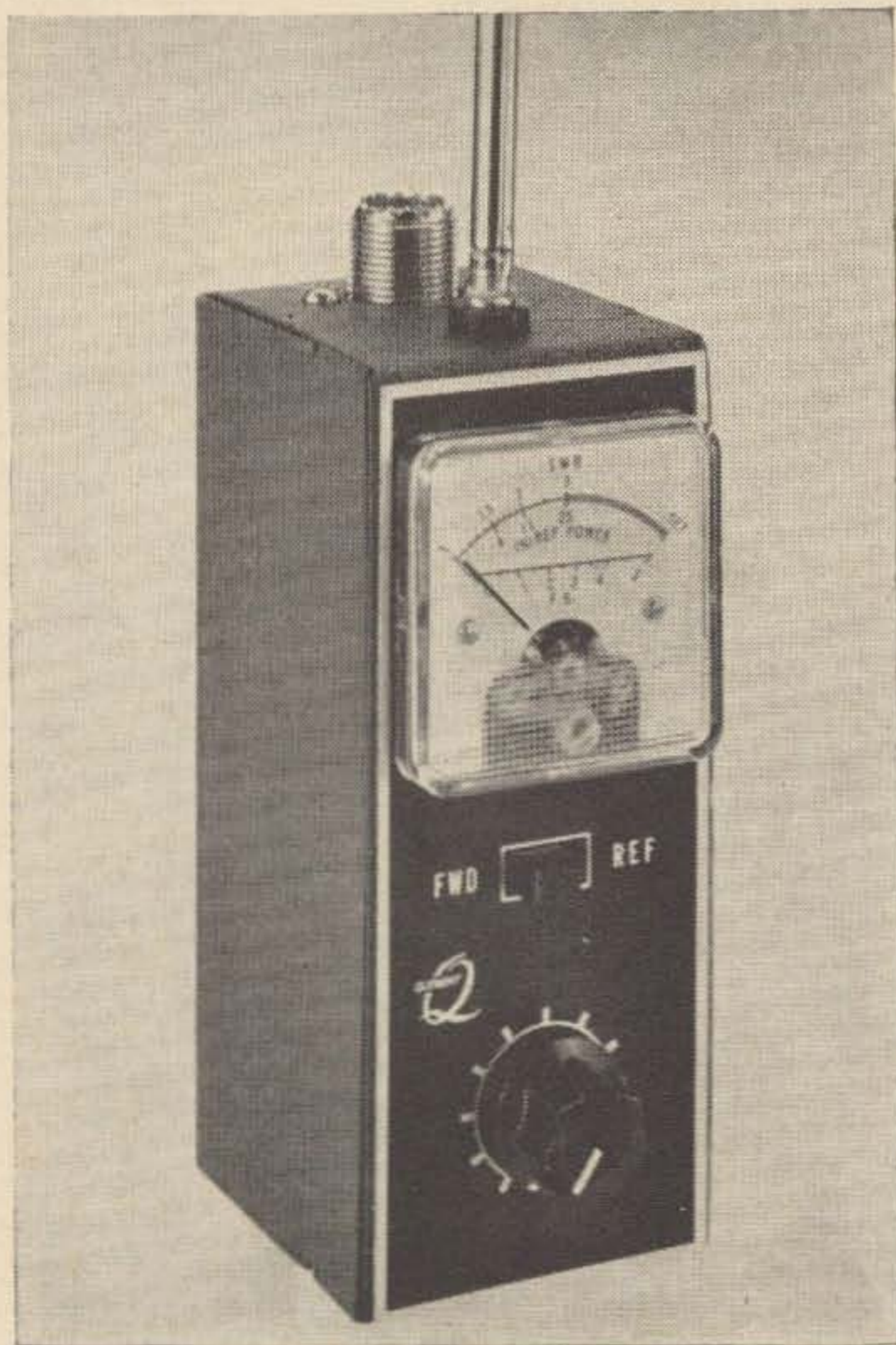


Photo courtesy Quement Electronics.

Quement Electronics' combination swr bridge and field strength meter is a compact and versatile instrument. In addition to swr measurements in 52 ohm lines, it serves as a field strength meter with the antenna provided.

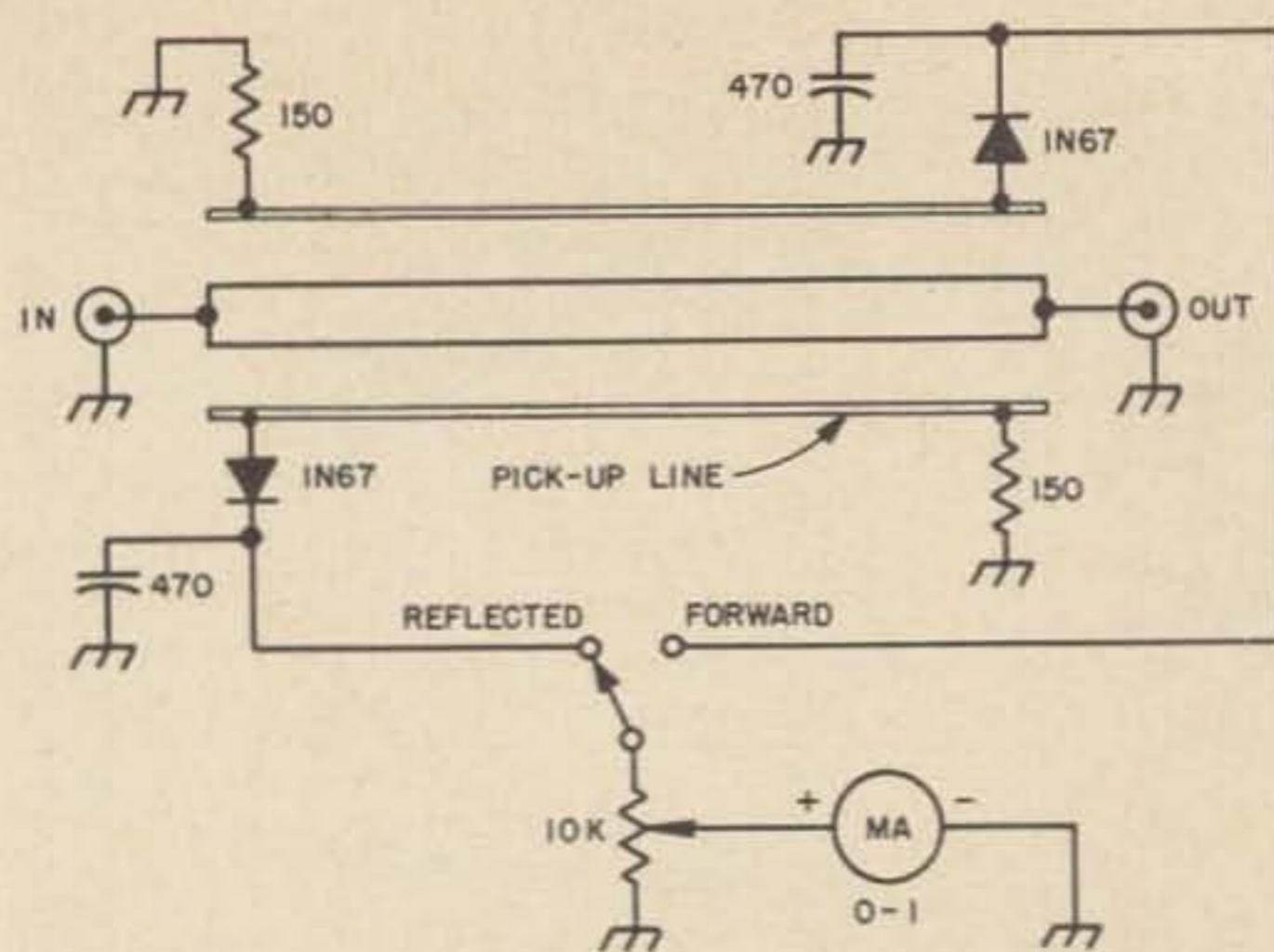


Fig. 8. Schematic of a pickup unit for the directional coupler type of swr meter.

originally developed by the Naval Research Laboratories¹ and popularized by WIICP.² This device uses a pickup wire which is parallel to the inner conductor of the coaxial line as shown in Fig. 8. Different manufacturers use various constructional techniques, but the principle of operation remains the same. Since the pickup wire is parallel to the inner conductor of the transmission line, a small voltage is induced in it by inductive coupling. At the same time, the voltage on the transmission line is sampled by capacitive coupling of the pickup wire; due to this voltage, a current flows through the terminating resistor and there is a voltage developed across it. When the layout of the pickup unit is such that the forward components of voltage and current cause these two voltages to be in phase, the resultant output is indicated on the meter. The reflected components would have no effect on this pickup line because the two voltages would be out of phase and cancel each other out. To detect the reflected components, another pickup line has to be constructed with the terminating resistor at the opposite end; the forward components would have no effect on this line of course because the two voltages would again be out of phase and cancel out. Although the effect of both the inductive and capacitive portions of the pickup line vary with frequency, their ratio remains the same. This just means that this type of a unit is more sensitive on the higher frequencies.

Usually when designing or building a standing wave meter, the pickup unit should be made much shorter than a quarter wavelength long. The only other precaution lies in the selection of the terminating resistors. First of all, if they are too large, they will introduce a phase error in the voltage pickup and cause poor nulls. On the other hand, if it is too small,

Table 3. Standing Wave Ratio Meters

Manufacturer	Model Number	Impedance (ohms)	Connector Type	SWR Range	Maximum Power (watts)	Frequency Range (mc)
Ameco	BIU	52	UHF	20:1	1000	1.8 - 225
Bird	ThruLine	50	N, C, UHF	∞ :1	5000*	2.0 - 2300
Cesco	CM52	52	UHF	100:1	1000	3.0 - 200
Cesco	CM52-2	52	UHF	100:1	1000	3.0 - 200
Heathkit	HM-15	50 or 75	UHF	3:1	1000	1.8 - 56
M. C. Jones	250	50 or 72	N, C, UHF	20:1	500	3.0 - 225
M. C. Jones	260	50	N, UHF	20:1	1000	0.5 - 225
M. C. Jones	300	50	N, C, HN	20:1	120	25 - 2000
M. C. Jones	500	50	N, C, HN	8:1	1200	20 - 2000
M. C. Jones	590	50	N, C	8:1	120	1000 - 3000
M. C. Jones	700	50	N, C, UHF	100:1	1200	20 - 1000
M. C. Jones	720	50	N, C	15:1	120	1000 - 3000
E. F. Johnson	250-37 250-38	52	UHF	10:1	1000	3.5 - 150
Knight-Kit	P-2	52 or 72	UHF	20:1	1000	1.8 - 432
Lafayette	TM-28	52 or 72	UHF	20:1	1000	2.0 - 50
Lincoln	L2501	52	UHF	20:1	1000	2.0 - 200
Quement	—	52	UHF	3:1	1000	2.0 - 50
Sierra	164B	50	N, C, UHF	∞ :1	5000*	2.0 - 1000

*Depends on plug-in element.

there won't be enough voltage developed across it. However, proper choice of circuit dimensions and component values will permit operation over all of the ham bands up to 50 mc; some specialized units are useable up to 1000 mc.

Of course, the accuracy of this instrument depends quite strongly on the fact that the voltage induced by the transmission line current just precisely cancels out the voltage sample. What this means is that the pickup line has to be adjusted to obtain a good null when the line is properly terminated and there are no reflected components. Another, and perhaps easier way of nulling out the pickup unit is to adjust the value of the terminating resistor⁶; by adjusting this resistor, you can set the voltage drop across it so that it exactly equals the voltage sampled.

Usually two identical pickup units are used, one for forward power, the other for reverse power. However, in some designs, only one

pickup is used; it is connected in such a way that it does the work of two. This may sound like you are getting something for nothing, but although the pickup is physically only one piece, electrically it looks like two separate units.

Possibly the biggest source of error in the



Photo courtesy Heathkit.

The Heathkit reflected power meter provides a reliable method of determining the swr on any 50 or 70 ohm transmission line up to 6 meters. It may be installed permanently in the line and permits continuous monitoring of line operation.

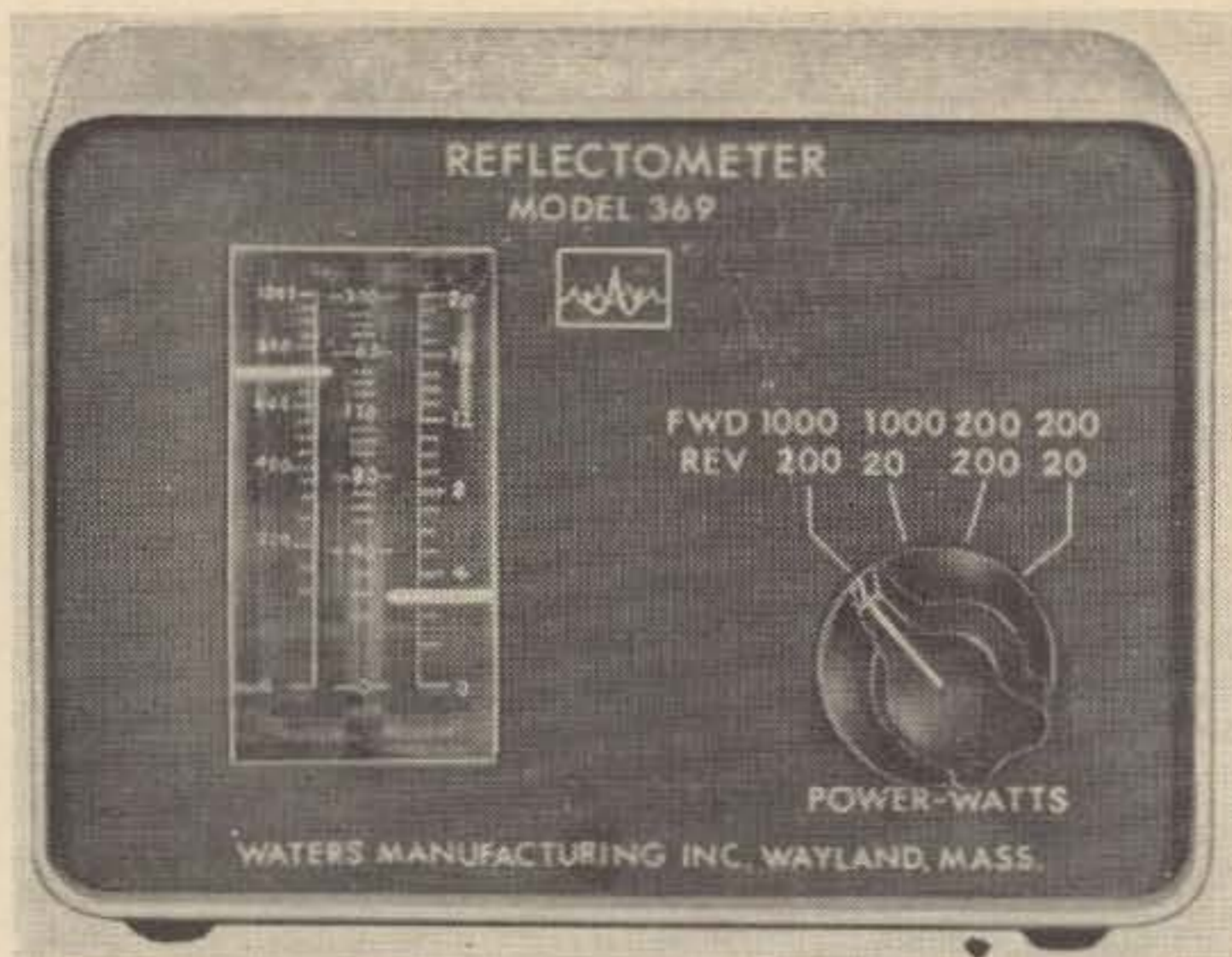


Photo courtesy Waters Manufacturing Inc.

The Waters reflectometer shows both forward and reflected power in 52 ohm transmission lines. In addition, this instrument has multiple scales that provide increased sensitivity for accurate readings of low reverse power values.

standing wave meter lies in nonlinearity of the semiconductor diodes. For this reason you might find that you don't get the same SWR readings at high power levels as you do at low levels. However, the differences are usually quite insignificant, if even noticeable at all.

Although all of the reflectometer standing wave meters of this type are identical electrically, there are any number of constructional variations. The early units consisted simply of a small loop of wire placed inside a waveguide or between the inner and outer conductors of the coaxial line. This type of construction is a little difficult to duplicate however, and later designs were laid out with the ham in mind. Perhaps the most popular of these is the trough type line with two pickup wires laid out on each side. Later variations of this theme use a piece of enameled copper



The Harris Company's standing wave ratio meter. This unit is unique because it uses a printed circuit pickup assembly.

wire threaded under the outer braid of a piece of RG-8A/U coaxial cable. This latter technique is quite easy to duplicate and has proven to be quite successful on the VHF bands because it preserves the characteristic impedance of the system.

Another method of construction which has been used by some manufacturers and written up in several amateur journals uses an entirely different technique. In this approach, a toroidal current transformer is very closely coupled to the transmission line. In addition, a small amount of voltage is picked off the line with small variable capacitors. This type of construction has the advantage that the current transformer may be electrostatically shielded so that it is only *inductively* coupled to the line. Furthermore, the capacitors can be laid out so that the voltage pickup may be controlled and not effected by stray capacity. In this way an instrument can be constructed which is quite accurate over a broad frequency range, and more important, provides consistent and reliable measurements.

The primary consideration in selecting standing wave meters is the characteristic impedance of the unit and its variations with frequency. The more expensive units exhibit a constant impedance at frequencies in excess of 1000 mc, but many of the inexpensive units exhibit non-constant impedance and may be used in either 50 or 75 ohm lines up to 30 megacycles with almost no detectable difference. In the Heathkit HM-15, different values of load resistors are provided to compensate for differences in 50 and 75 ohm transmission systems.

In addition to standing wave measurements, many of the instruments of this type may be used to accurately measure rf power. In the inexpensive devices, only relative power may be determined.



Photo courtesy Allied Radio Corp.

The Knight-Kit swr/power meter is a flexible two-unit instrument that may be used on all the ham bands up to 432 mc. It is suitable for use with either 50 or 70 ohm lines and its negligible insertion loss allows it to be left in the line as a constant monitor.

Coaxial attenuators

The coaxial attenuator or pad is a device that is unfamiliar to many amateurs, but which is very useful in many applications. Basically, the attenuator consists of a resistance network which reduces the rf power between the input and output while maintaining the characteristic impedance of the transmission line. They are categorized by the amount of power loss through them in decibels; a 3 db attenuator for example will reduce the power by approximately one-half.

Accurate rf attenuators may be used in s-meter calibration, checking sideband suppression, and measuring crosstalk, receiver image and *if* signal rejection, relative antenna gain and receiver noise figure. A 20 db attenuator installed at the antenna terminals of a receiver is particularly helpful in reducing cross-modulation and overload when working local stations. Attenuators are also used between SSB exciters and linear amplifiers when the exciter output exceeds the recommended driving power of the amplifier.

The two basic constant impedance attenuating circuits are the "tee" and "pi" illustrated in Fig. 9. The names for these circuits were derived from the similarity of the circuits to the letter "T" and the Greek letter "π" respectively.


Most commercial attenuators are constructed using disc resistors as shown in Fig. 9. This type of resistance element presents a *sheet* of resistance to the circuit and has been used successfully at frequencies in excess of 1000 mc. However, these disc resistors are quite expensive and for amateur applications, composition resistors may be used with no noticeable effect up to about 250 mc. Above 250 mc it is difficult to predict the rf resistance of composition resistors however, and the more sophisticated disc resistors should be used.

Simple 50 ohm tee attenuators may be constructed using composition resistors as shown in Fig. 9. The required resistance values for various amounts of attenuation are listed in Table 4. These values are based on the use of standard 5% tolerance resistors and are not 100% accurate in terms of attenuation, but are within $\pm 2\%$ of the proper value. For other than 50 ohm systems, the required tee attenuator resistance values may be calculated from the following equations:

$$R_2 = \frac{2Z_0\sqrt{N}}{N-1}$$

$$R_1 = Z_0 \left(\frac{N+1}{N-1} \right) - R_2$$

Table 6. 50 ohm T-Pad Attenuator Resistance

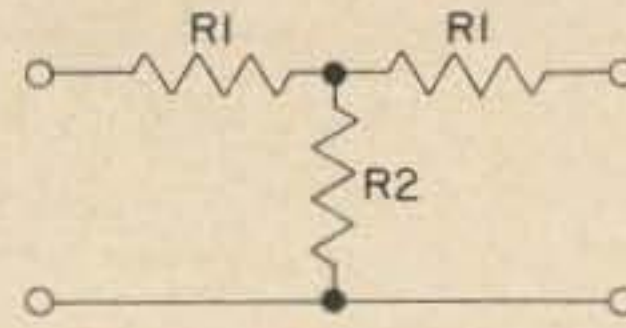

db	R1	R2	db	R1	R2
0.1	0.30	4300	4	11	100
0.2	0.56	2200	5	15	91
0.3	0.82	1500	6	16	68
0.4	1.1	1100	7	20	56
0.5	1.5	910	8	22	47
0.6	1.8	750	9	24	39
0.7	2.0	620	10	27	36
0.8	2.4	560	11	27	30
0.9	2.7	470	12	30	27
1.0	3.0	430	13	33	24
1.1	3.3	390	14	33	20
1.2	3.3	360	15	36	18
1.3	3.6	330	16	36	16
1.4	3.9	300	17	39	15
1.5	4.3	300	18	39	13
1.6	4.7	270	19	39	11
1.7	4.7	240	20	39	10
1.8	5.1	240	25	43	5.6
2.0	5.6	220	30	47	3.3
2.2	6.2	200	35	47	1.8
2.5	6.8	180	40	51	1.0
3.0	8.2	150	45	51	0.56
3.5	10.0	120	50	51	0.33



Photo courtesy Waters Manufacturing Co.

This Waters wide range coaxial attenuator provides up to 61 dB attenuation in 1 dB steps. It is accurate within one dB from dc to 225 mc.

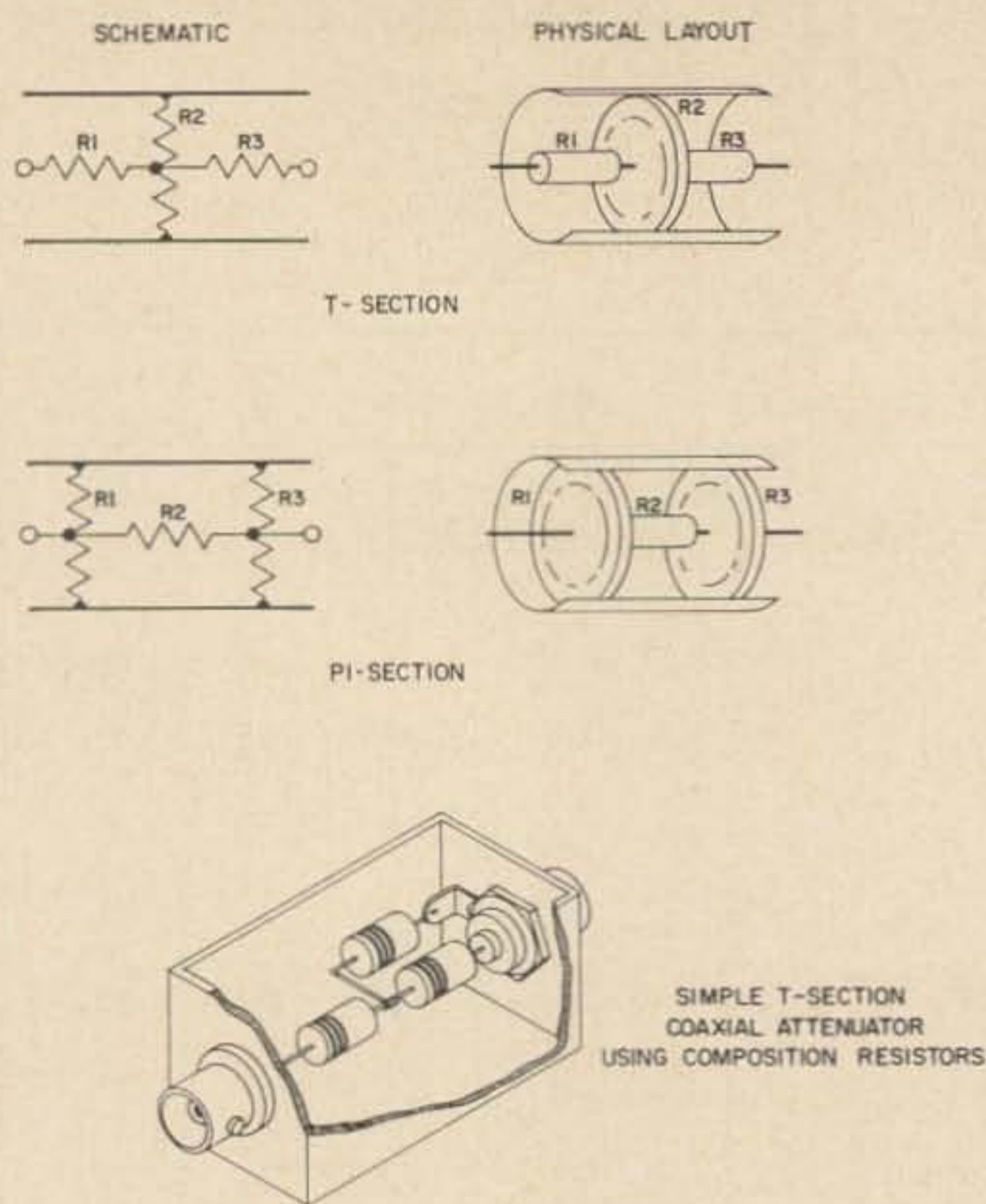


Fig. 9. Circuits and typical layout of attenuators for use in amateur equipment.

Example What resistance values are required for a tee attenuator with a characteristic impedance of 75 ohms and attenuation of 20 db? From a db-power ratio table or from the expression $N = \text{antilog}(\text{db}/10)$, it is determined that 20 db corresponds to a power ratio of 100. Therefore:

$$R_2 = \frac{2Z_0\sqrt{N}}{N-1} = \frac{2(75)\sqrt{100}}{100-1} = 15.2 \text{ ohms}$$

$$R_1 = Z_0 \left(\frac{N+1}{N-1} \right) - R_2 = 75 \left(\frac{100+1}{100-1} \right) - 15.2 = 61.3 \text{ ohms}$$

One commercial attenuator that is designed specifically for amateur use is the Waters Model 371 Wide Range Attenuator. This unit is usable from dc to 225 mc and provides up to 61 db attenuation in one db steps.

Baluns

One of the advantages of the coaxial transmission line system is that the rf power is confined within the outer conductor of the cable. This insures that the transmission line doesn't act like an antenna, but transmits the power to the antenna where it is properly radiated; this increases the efficiency of the antenna/transmission line system and greatly reduces TVI and other sources of interference. Unfortunately however, most antennas are balanced devices and for proper operation,

they should be fed with a balanced transmission line. In most amateur stations, coaxial feedline is indiscriminately connected to a dipole or multi-element array, both of which are balanced, with little thought to the balance-unbalance mismatch that occurs. The results can often be quite confusing. For instance, it is almost impossible to obtain meaningful standing wave measurements when there is a balance-unbalance mismatch in the system. Furthermore, almost all antennas, and tri-band beams in particular, display very confusing and esoteric resonance curves when fed with this type of a system. In addition, to obtain the desired pattern in high-gain antenna systems, it is imperative that a good balance to ground be preserved. When an inherently balanced antenna is fed with a coaxial feedline, the electrical feed point may be shifted away from the designed point, changing the ohmic value of the load and introducing reactance into the system.

On the other hand, when a balanced load is connected to an unbalanced transmission line, the resultant balance/unbalance mismatch may cause standing waves, cause rf currents to flow on the outside braid of the coaxial line resulting in unwanted radiation, or couple the load reactance back to the transmitter or receiver. The important point here is that this can happen even if the antenna is resistive and matches the impedance of the coaxial line.

The solution to this problem of course lies in the balance-to-unbalance converter or *balun*. There are several different types of baluns, three of which are illustrated in Fig.

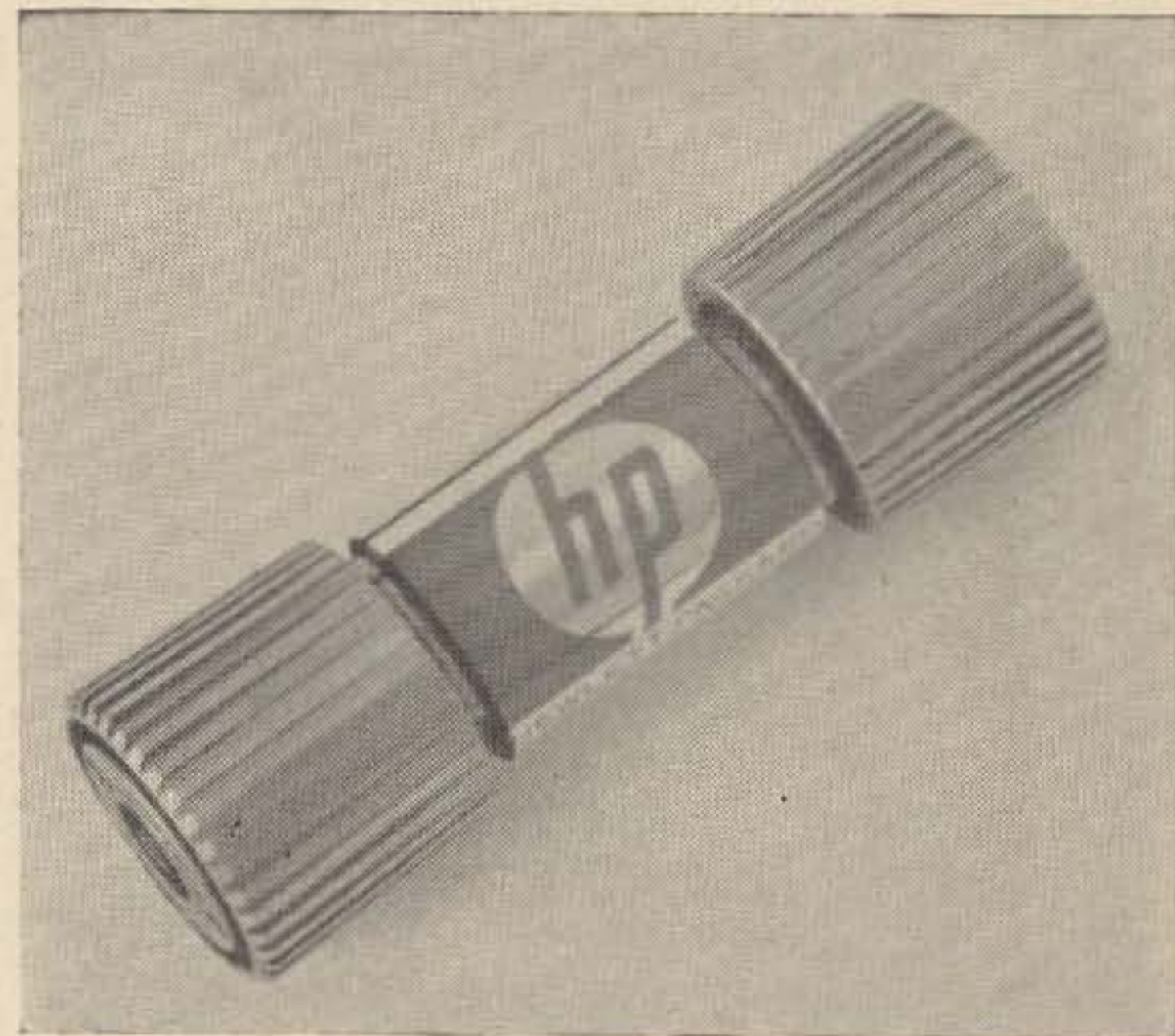


Photo courtesy Hewlett-Packard. Hewlett-Packard fixed coaxial attenuators are representative of the types of commercial attenuators presently available. These units are available in 3, 6, 10 or 20 db attenuation and are usable from dc to 18,000 mc.

10. The coaxial sleeve balun or *bazooka* is quite popular on the UHF bands and operates on the principle that a shorted quarter-wave line presents a high impedance at the open end. A relatively high impedance exists between the inner and outer conductors of the transmission line and with the addition of the shorted quarter-wave sleeve, a high impedance appears between the outer conductor of the transmission line and the outer shell of the sleeve. In other words, the quarter-wave detuning sleeve has the effect of freeing the outer conductor of the coaxial cable from ground and if the balun is connected to a balanced load, the two output leads will assume equal impedance to ground.

Although the coaxial sleeve balun is primarily a 1:1 impedance converter, the quarter-wave sleeve and coaxial line with which it is used can be designed so that it will serve as an impedance matching transformer or Q section. By using the procedure laid out by K6HCP and WA6GYD,¹³ this type of balun may be used for matching 52 ohm coaxial lines to 200, 300 or 450 ohm balanced lines. Although this type of a balance to unbalance converter is not too practical on the high-frequency bands, it has proven very useful on 144, 220 and 432 mc.

The quarter-wave open balun is nothing more than a simple method of making a quarter-wave coaxial detuning sleeve. Although this type of construction is simple and expedient, the results are not as good as those provided by the coaxial sleeve. This is because the open type construction is not as efficient in detuning as the sleeve which completely encircles the coaxial transmission line.

The balun which has been most popular with amateurs is the simple half-wave phase inverter balun shown in Fig. 10 and 11. This type of balun is very easy to build, but it suffers from two very serious disadvantages. First of all, it is useable over a narrow band of frequencies; whenever the length of the phasing line deviates very much from the required half-wavelength, it no longer provides the necessary balance to unbalance conversion. This means that a different balun has to be built for each ham band; on the VHF bands the line length is so critical it is nearly impossible to obtain proper operation.

This type of a balun takes advantage of the 180 degree phase inversion which takes place along a half wavelength line. When a negative peak of the sinusoidal rf current appears at A, a positive peak appears at B. Since both of these peaks appear on the center conductor, they exhibit a high impedance to ground and


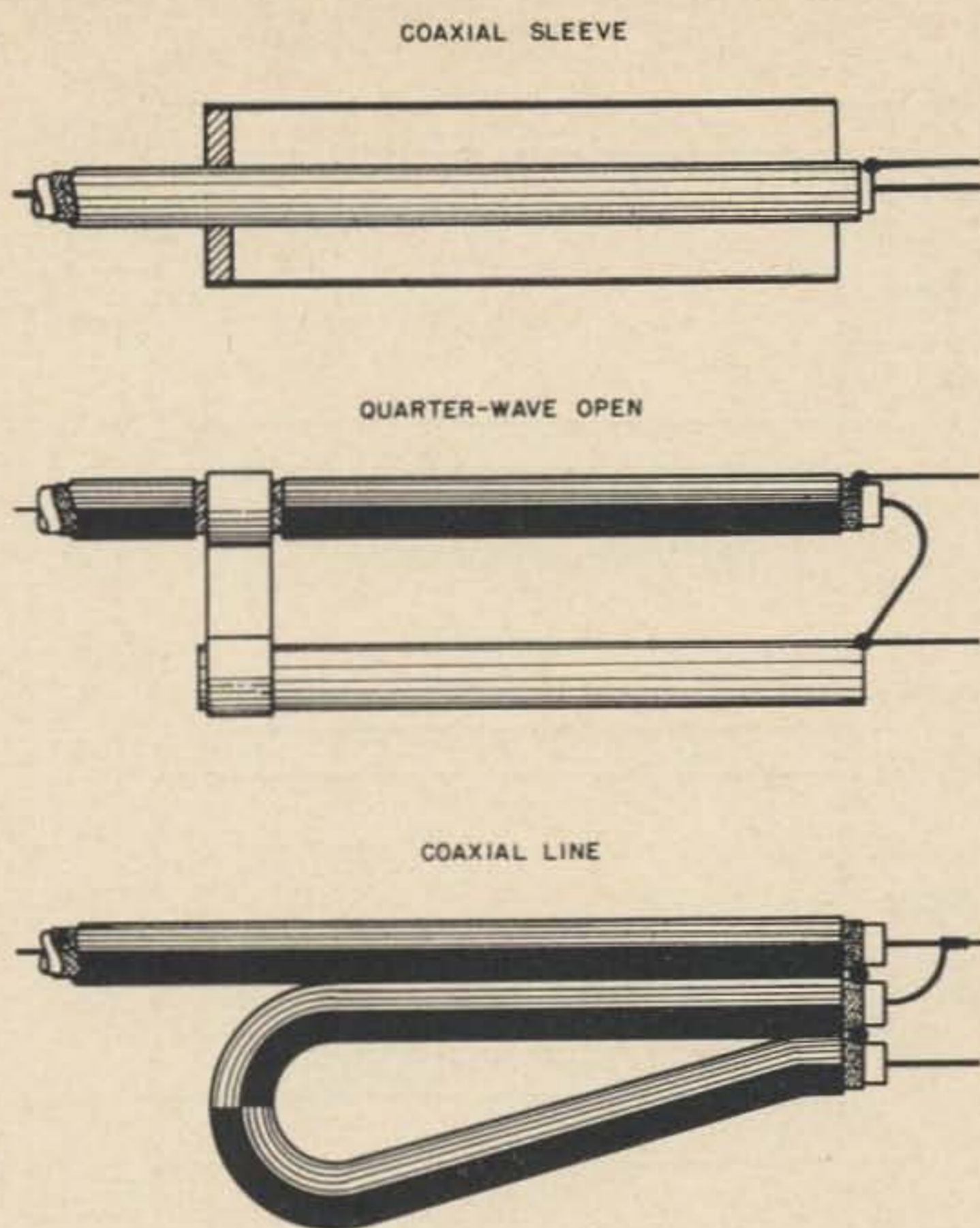


Fig. 10. Various types of balance to unbalance converters or baluns. The coaxial sleeve balun is most satisfactory for the VHF and UHF bands while the other two types find use on the high-frequency bands up to 30 mc.


present a balanced output. The half-wave phase inverter balun gives an impedance ratio of 4:1 because the phase inverter provides a voltage step-up of 2:1.

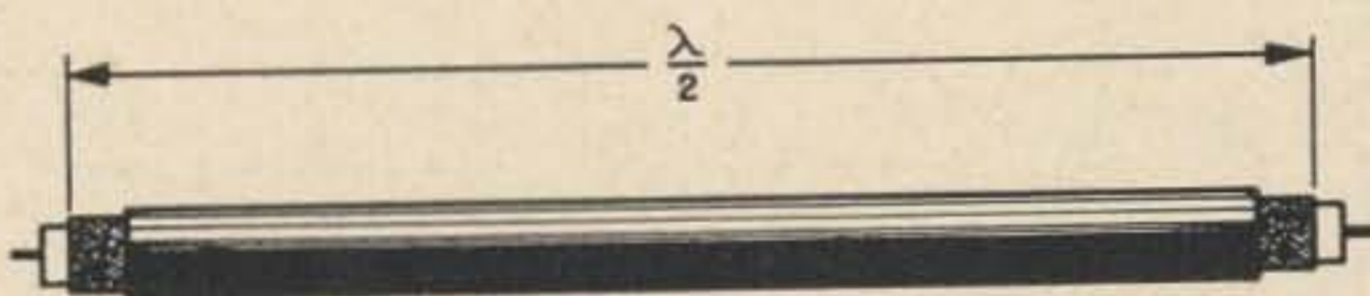Each of these three baluns depends upon a



1. CUT A SECTION OF COAXIAL CABLE 1/2 WAVELENGTH LONG AT THE OPERATING FREQUENCY. USE THE APPROPRIATE LENGTH TO COMPENSATE FOR THE EFFECT OF THE VELOCITY FACTOR OF THE CABLE BEING USED.
2. STRIP BACK THE OUTER JACKET AND DIELECTRIC TO EXPOSE THE CENTER CONDUCTOR. FORM THE CABLE SECTION INTO A "U" AND CONNECT IT TO THE MAIN FEEDLINE AS SHOWN IN THE DRAWING. SOLDER ALL THE OUTER CONDUCTORS TOGETHER. CONNECT THE CENTER CONDUCTORS AS SHOWN.
3. ATTACH THE COMPLETED BALUN TO THE ANTENNA OR OTHER BALANCED LOAD AND COMPLETELY SEAL WITH WEATHERPROOF PLASTIC TAPE.

Fig. 11. Construction of the half-wave phase inverter balun. This balun is relatively narrow-banded, but it is easy to build and satisfactory for many applications.

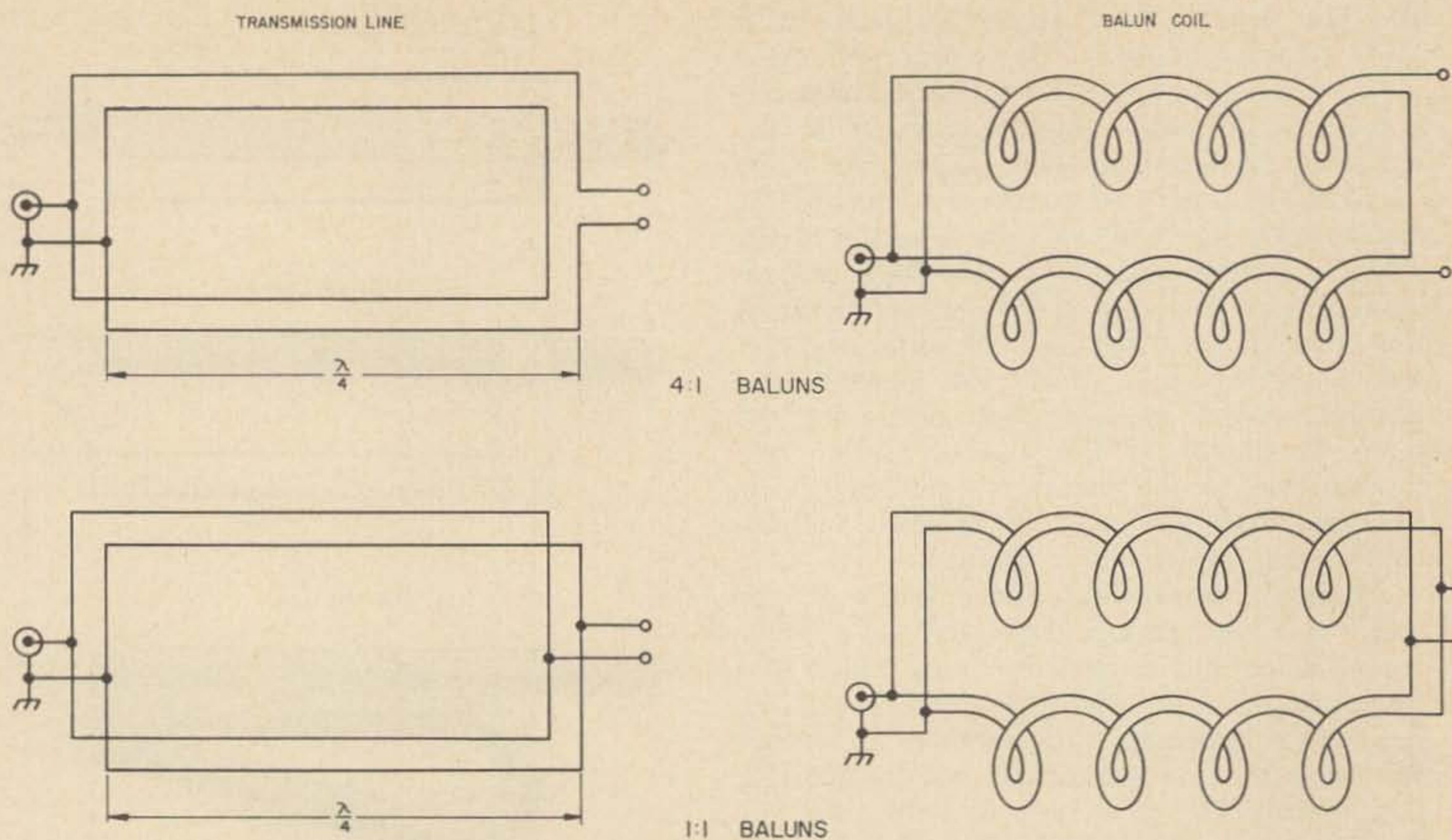


Development of the broadband balun coil from linear transmission line theory.

frequency dependent length of transmission line. This is suitable for single band operation, but for wide bandwidths, another approach must be used. By applying a closely coupled bifilar air-wound transformer, a balun can be made that will work effectively from 3.5 to 30


mc. The air-wound balun is somewhat bulky and limited in power handling ability, but recent advances with ferrites have resulted in small, compact and efficient baluns that will work over extremely wide bandwidths.⁸

To explain how these balun transformers work, we have to resort back to the transmission line for a moment. If two transmission lines of equal length which have a characteristic impedance (Z_0) of 100 ohms are connected in series at one end and in parallel at the other, at the series connected end the lines are balanced to ground and will match 200 ohms. On the other hand, at the parallel connected end the lines will be matched by an impedance equal to 50 ohms. This shouldn't be hard to understand if we remember for a moment that two resistors in series add while the equivalent resistance of two equal resistors in parallel is one half of the resistance value of the resistors. If the length of the series/parallel connected transmission lines is an odd multiple of one-quarter wavelength, one side of the parallel connected end may be grounded and the balanced end (series connected) will be effectively decoupled from it. Since the input impedance of this balun is 50 ohms and the output is 200 ohms, it exhibits an impedance transformation ratio of 4:1.

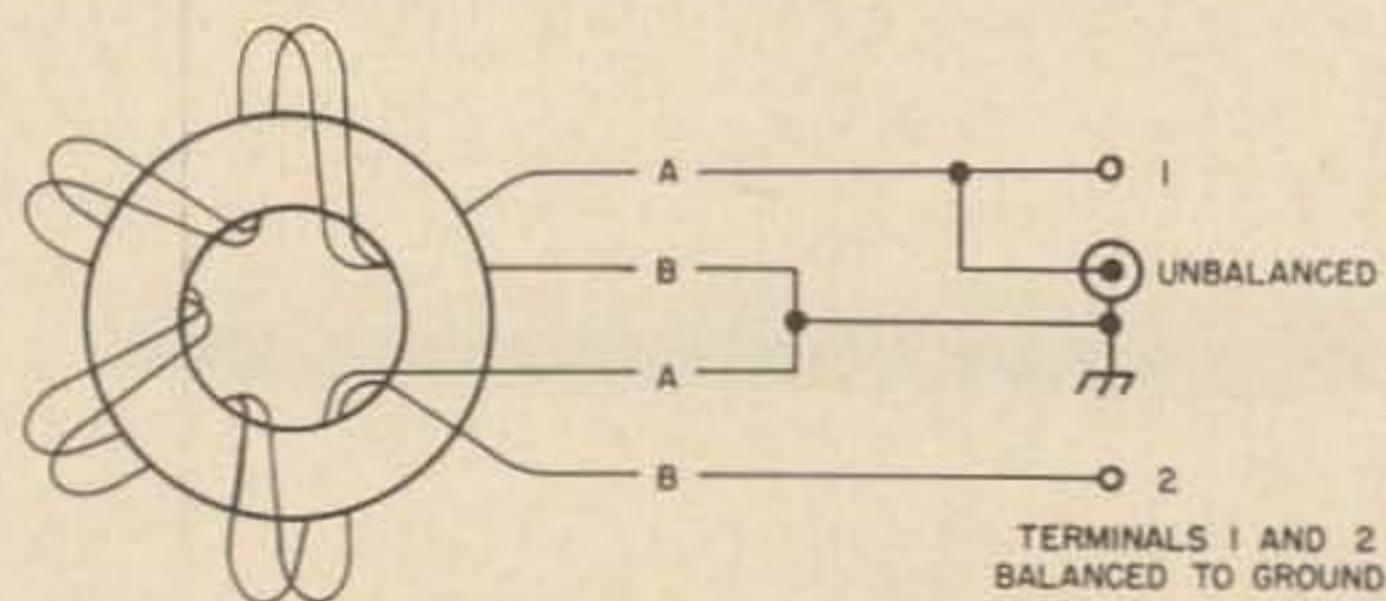To obtain an impedance transformation ratio of 1:1 with this type of balun, the lines are connected in parallel at both ends. As previously, one side of either parallel con-



4:1 BALUN

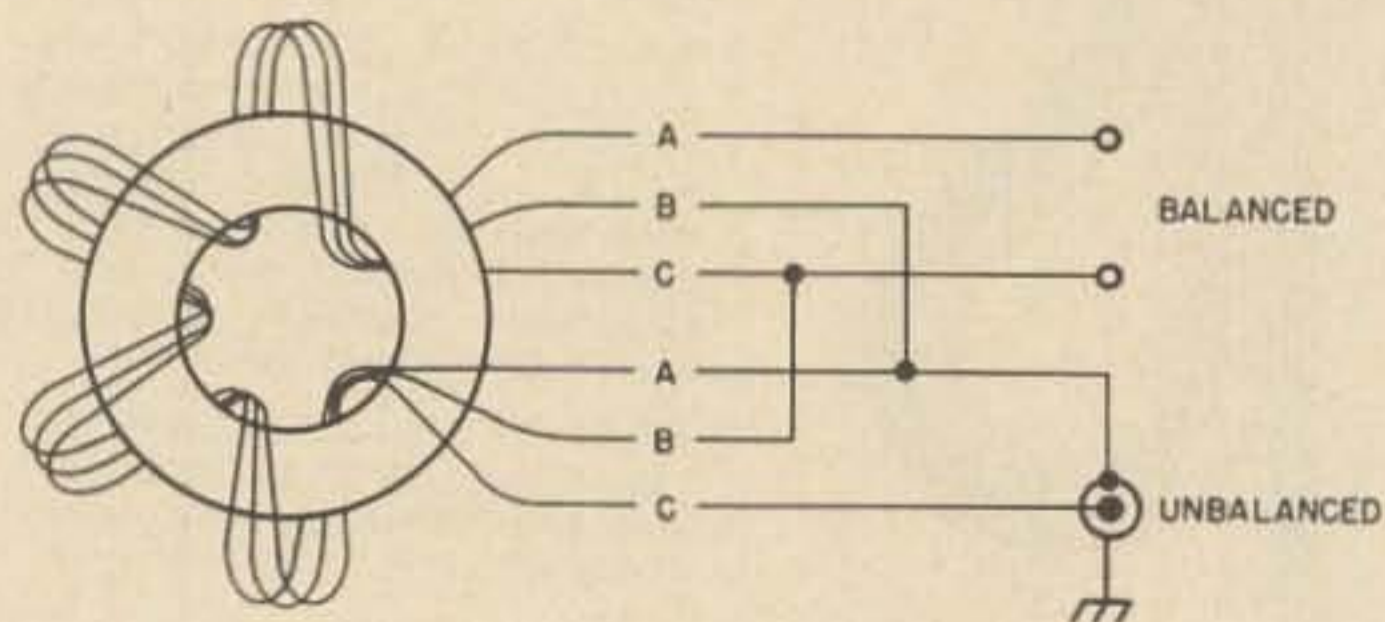

1:1 BALUN

Fig. 12. Method of winding and connecting ferrite cored baluns to obtain either 1:1 or 4:1 impedance ratio. This type of balun may be used over a bandwidth from 3 to 30 mc.

Table 5. Baluns

Manufacturer	Model Number	Unbalanced Impedance (ohms)	Frequency Range (mc)	Power (watts)	Impedance Ratio	Connector
Ami-Tron	Kit	50 or 75	1.0 - 60	1000	1:1, 4:1, 9:1	None
B&W	725	75	1.5 - 30	2000	4:1	UHF
B&W	3975	75	3.5 - 30	250	1:1 or 4:1	UHF
Fugle	—	50 or 75	3.0 - 30	1000	1:1 or 4:1	None
Millen	46672	50 or 75	3.5 - 30*	—	4:1	UHF
Telrex	1K81B	52	3.5 - 30	500	1:1**	None
Telrex	2K81B	52	3.5 - 30	1000	1:1**	None
Telrex	4K81B	52	3.5 - 30	2000	1:1**	None
Telrex	2K816B	52	1.7 - 14	1000	1:1**	None
Translab	601	50 or 75	2.0 - 30	1000	1:1	N
Translab	601A	50 or 75	2.0 - 30	1000	4:1	N
W2AU	—	50 or 75	3.0 - 30	1000	1:1 or 4:1	UHF

*Five models required to cover this range.

**Available in 4:1 impedance ratio at slightly higher cost.

nected end may be grounded, and the other end may be connected to a balanced load and be effectively decoupled from the grounded end.

Although this discussion has assumed the use of regular transmission lines, the two lines can be wound into a coil, either air-wound or ferrite cored. The inductances formed by these windings act as chokes and tend to further isolate the balanced end from the grounded end. In fact, the frequency range of this type of balun is greatly extended because

of the greater isolation obtained through choke action. At the high frequency end of their range, these transformers act like transmission lines, and at the low frequency end, like very closely coupled coils.

The majority of the commercial baluns come completely assembled and ready to install, but one company, Ami-Tron Associates, provides a ferrite core and a length of number 14 wire so you can wind your own. To make a 1:1 impedance ratio balun, you wind ten trifilar turns on the core and connect it as shown in Fig. 12A; for a 4:1 impedance balun, wind ten



Photo courtesy Ami-Tron Associates.

The Ami-Tron Associates toroidal balun is furnished as a kit which may be easily made into a wide band balun. By simply changing the number of turns of wire and their connections, this kit will make either a 1:1, a 4:1 or a 9:1 balun that is usable from 160 meters to 60 mc.

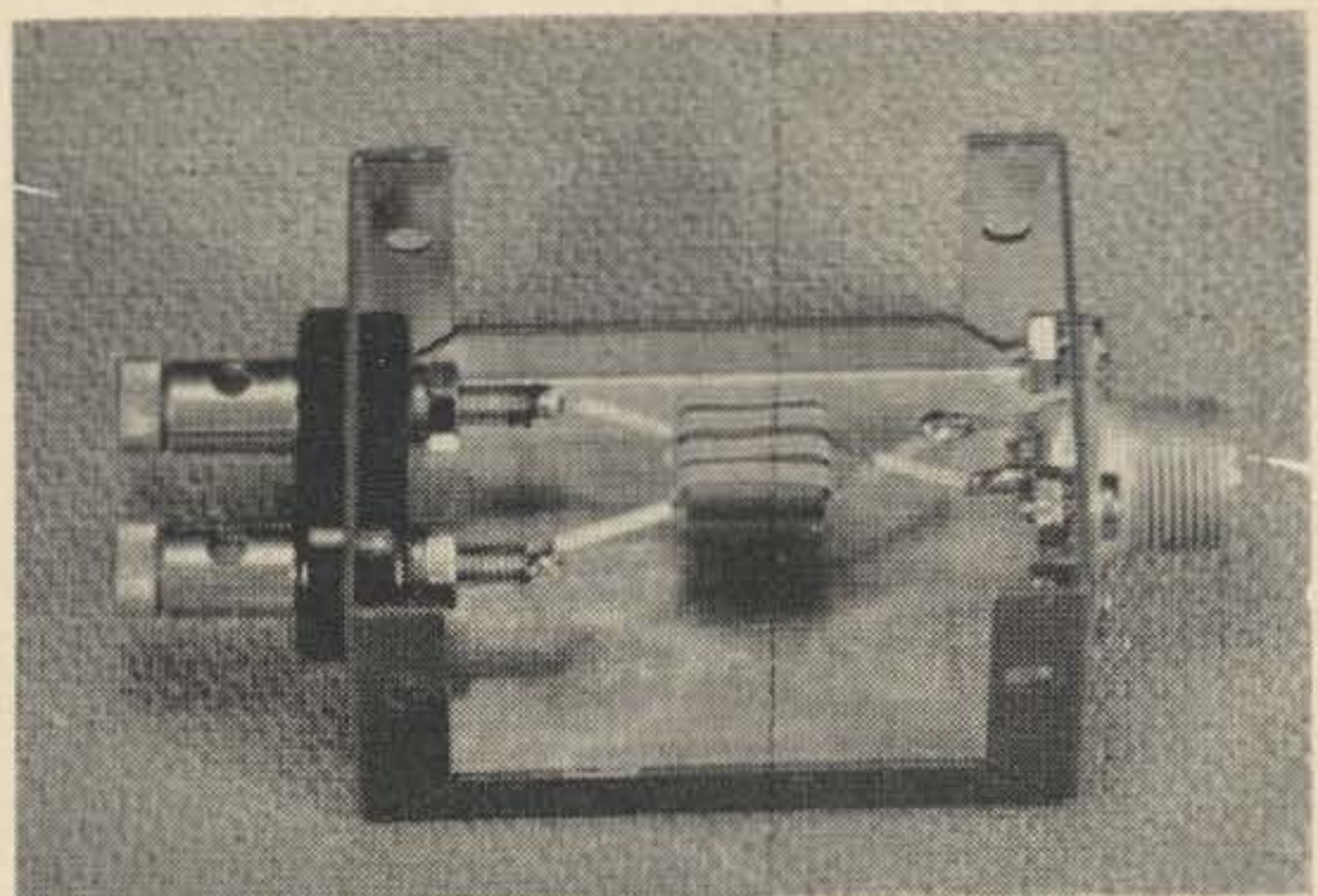


Photo by M. S. Gassman, Jr.

A VHF balun using a commercially available TV receiver antenna transformer. This balun may be used in the frequency range from 20 to 150 mc with up to 20 watts; over 20 watts of power results in excessive heating.

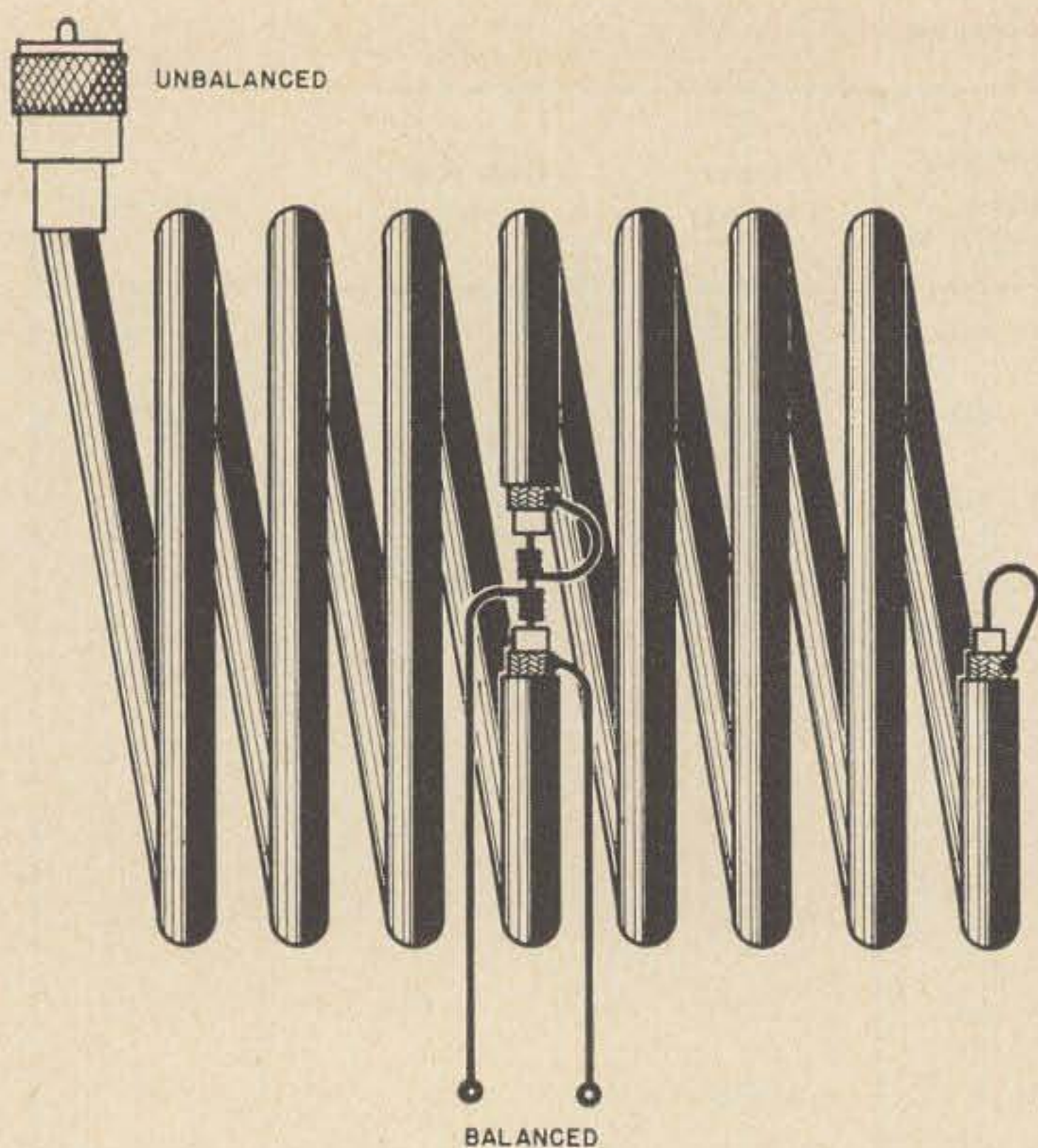


Fig. 13. A broad band coaxial balun using a length of coaxial cable. This balun may be used over all the ham bands below 30 mc with excellent results.

bifilar turns on the core and connect it as shown in Fig. 12B. Both of these baluns may be used over the frequency range from 3.5 to 54 mc and will handle a full kilowatt of rf.

Although the ferrite core balun is extremely compact, it is somewhat expensive, and a very reasonable way of obtaining the same electrical characteristics was described by K2HLT some time ago.⁷ In his approach approximately 30 feet of RG-59/U is wound into a coil as shown in Fig. 13. The coil is center-tapped and the balanced output taken from the inner and outer conductors as shown in the drawing. The inner and outer conductors are shorted

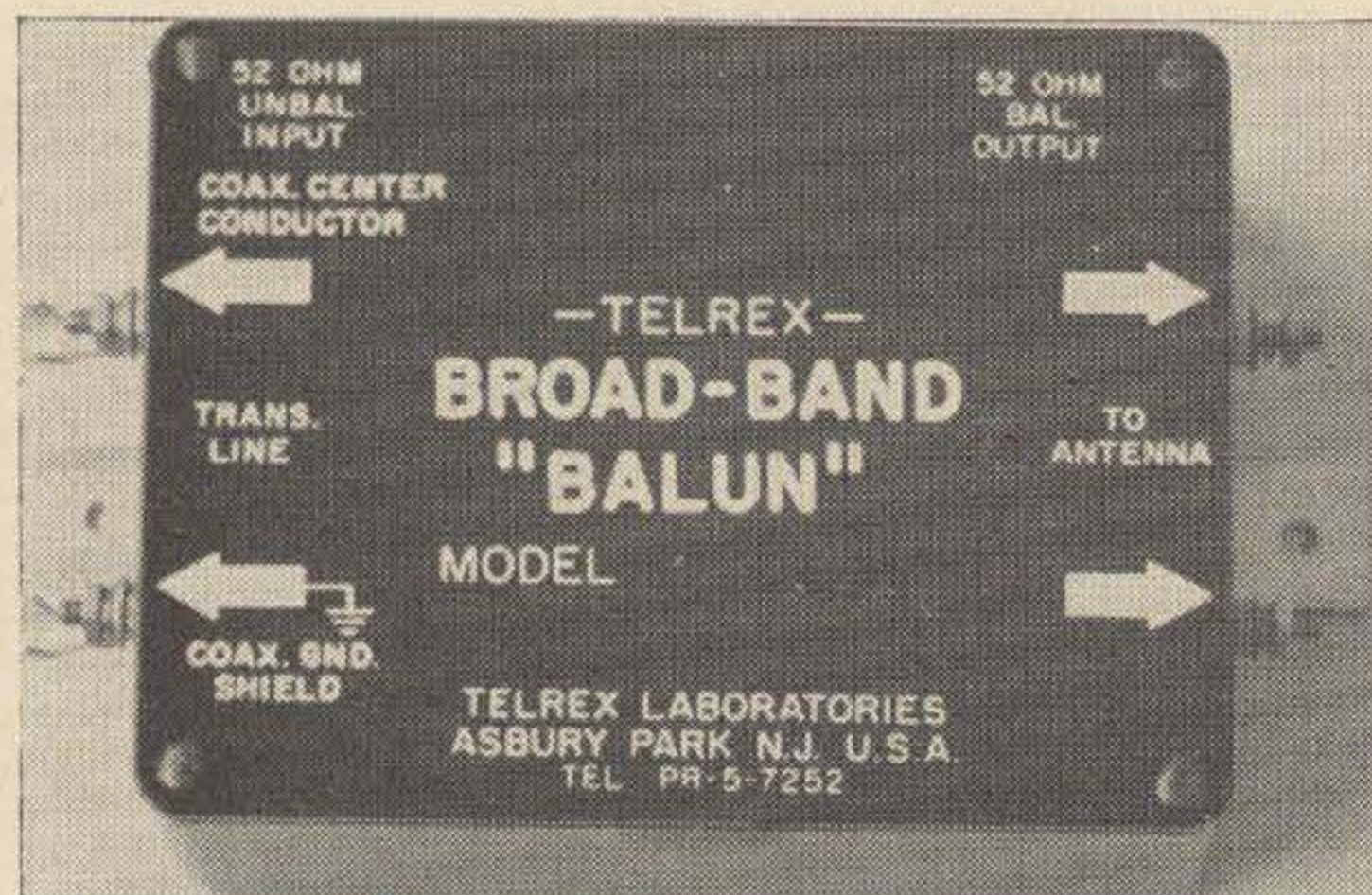


Photo courtesy Telrex Laboratories.

The Telrex broad-band baluns are available in several models that will handle up to 4 kilowatts PEP. These baluns may be mounted at the antenna feedpoint and provide a convenient and efficient method of feeding balanced antennas with coaxial transmission line.

together on the lower part of the coaxial cable coil while the unbalanced input is at the top. Actually this balun represents a simple autotransformer, tuned to resonance at approximately 14 mc by the distributed capacity of the coaxial cable on the top half of the coil. Because the Q of the cable is in the vicinity of 200, there are very low losses associated with this type of construction. However, when the balun is loaded with a 75 ohm load, the selectivity of the circuit is broadened out to encompass a 30 mc bandpass.

The transmitter signal is coupled by the coaxial cable in the upper half of the coil to the bottom half, which is simply a coil to ground. However, the bottom coil is inductively coupled to the top coil with essentially unity coupling. Since each coil feeds one side of the balanced output and each side has equal inductance, the output is balanced.

Measurements made by K2HLT on this 72 ohm 1:1 balun indicate that over the bandpass of 1.6 to 30 mc, it has less than 0.5 db attenuation, less than 0.5 db of unbalance and a standing wave ratio less than 1.2:1. Although this balun uses the small diameter RG-59/U, larger coaxial cables may be used in a balun of this type. W6SAI has described a broadband 52 ohm balun using essentially the same technique but employing 52 ohm RG-8A/U cable.⁹ This balun had an over-all passband from 6 to 32 mc and would handle a full kilowatt. Since the operation of this device is limited at the low frequency end by the inductance of the windings, the use of a longer length of cable should result in lower useable operating frequencies. The coil must be redesigned for the differences of each cable, but the required procedure is quite simple. All you have to do is adjust the length and size of the coil to resonate at approxi-

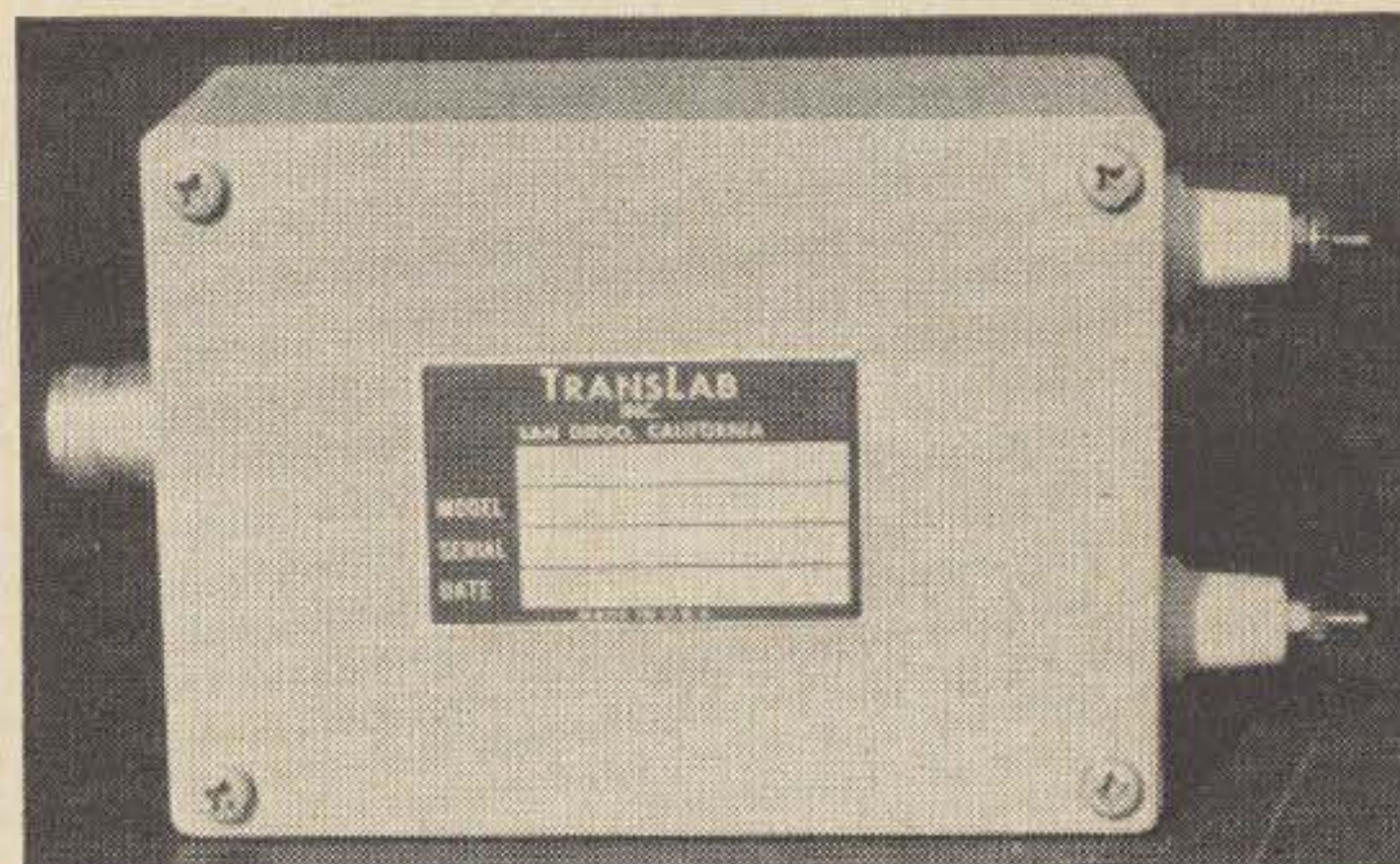


Photo courtesy Translab Inc.

Translab's broadband ferrite balun is a completely weatherproof unit which provides a balanced output from 50 or 70 ohm coaxial lines over a frequency range from 2 to 30 mc. It will handle 2 kilowatts PEP and is available with either a 1:1 or 4:1 impedance ratio.

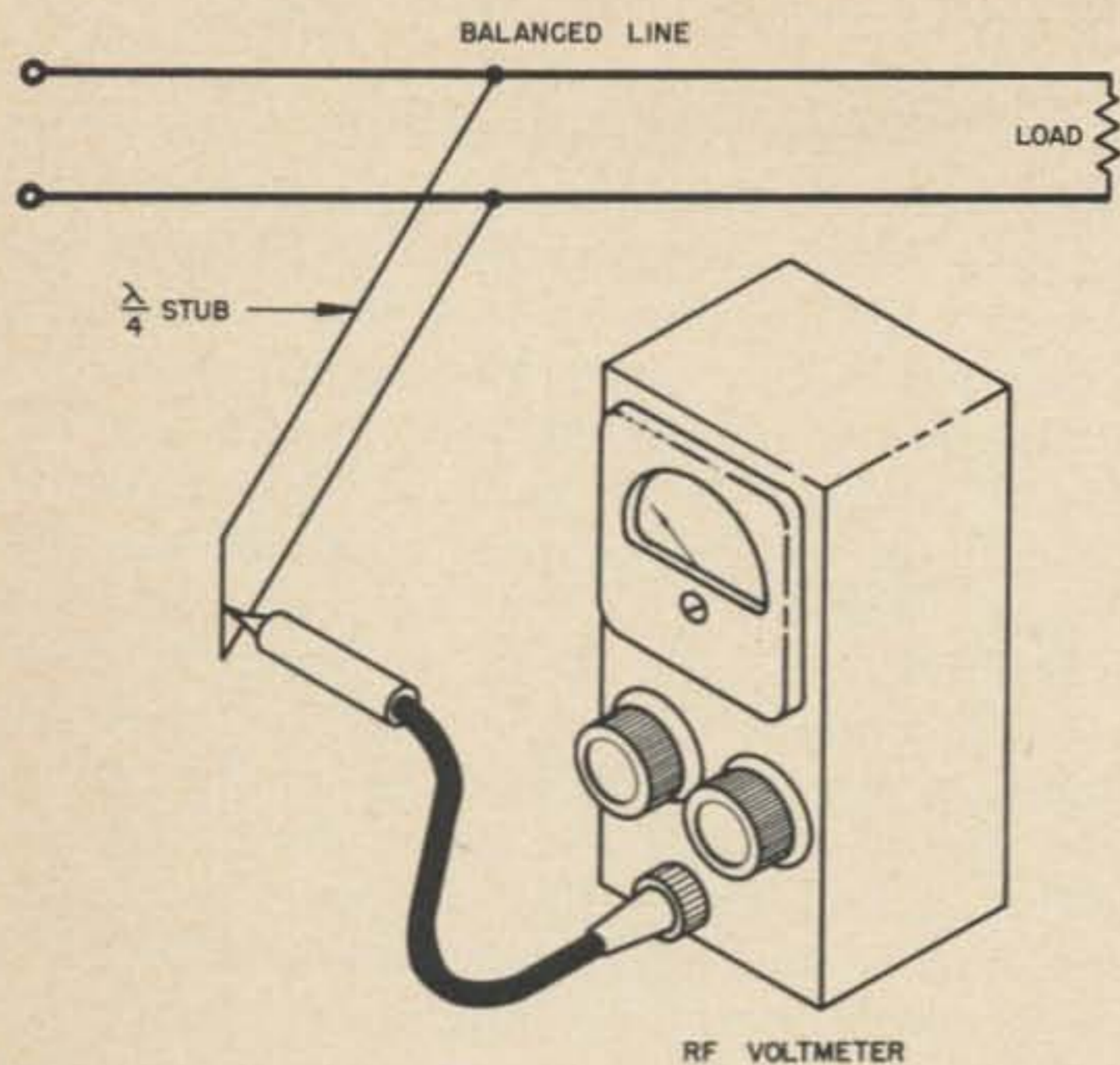


Fig. 14. Measuring the balance of the balance to unbalance converter. If the balun is providing an exactly balanced output, there will be no indication on the voltmeter.

mately 14 mc while retaining the required bandwidth under load conditions.

The chief item of concern in the performance of a balun is the amount of balance that exists on the balanced output line. This may be determined by measuring the voltages from each of the balanced conductors to ground. Many high-frequency VTVM's are suitable for this purpose, but the input impedance of the VTVM must be very high so that it will not introduce any unbalance of its own.

Since the voltmeter only gives a reading proportional to amplitude, this method will not detect unbalance in which the peak amplitudes of the voltages on the two lines are equal but do not occur 180 degrees apart in time. A better method of detecting this *phase* unbalance is illustrated in Fig. 14. Since

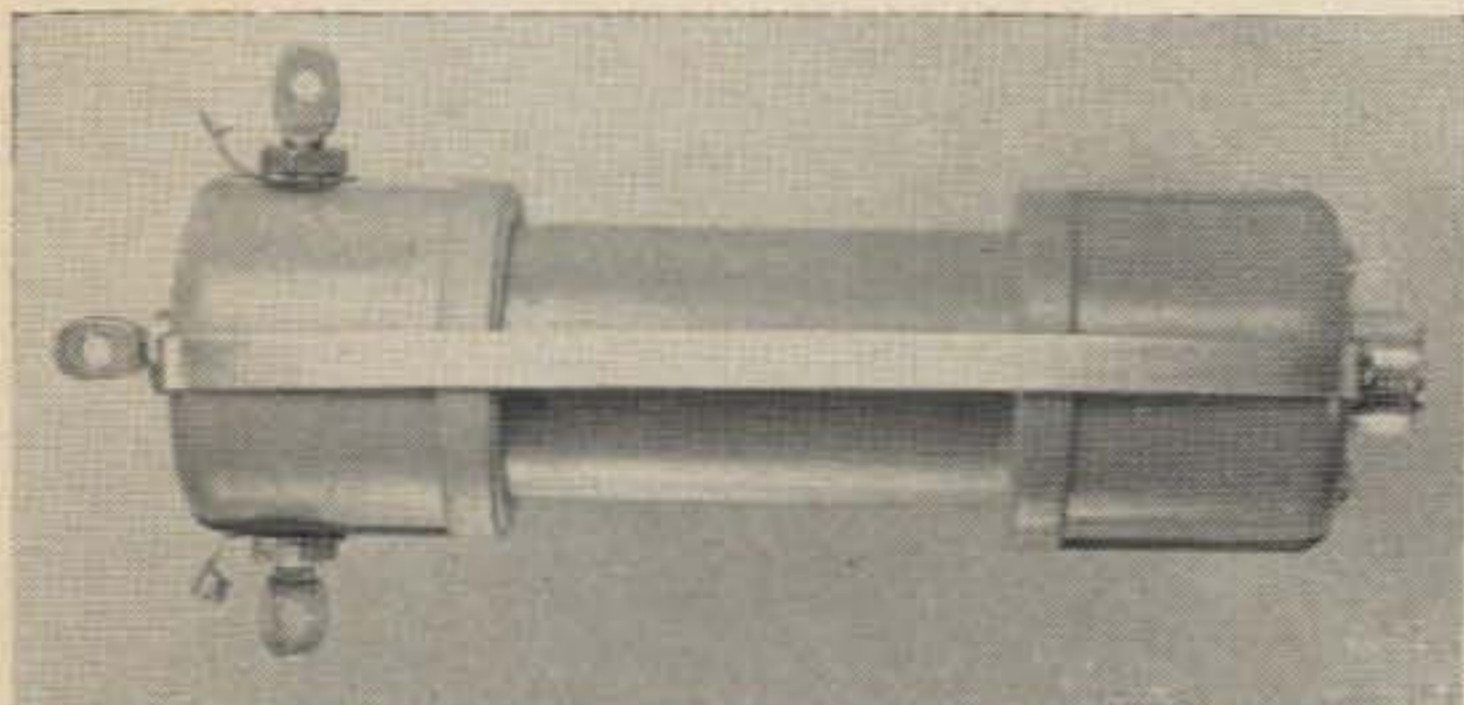


Photo courtesy Unadilla Radiation Products.

The W2AU balun is a wideband unit available in either 1:1 or 4:1 impedance ratios. It can serve as the center insulator in a dipole or inverted vee antenna and has a built in hang-up hook and lightning arrester. This balun may be used from 3 to 30 mc with 50 or 70 ohm coaxial transmission lines and will handle over 2 kilowatts PEP.

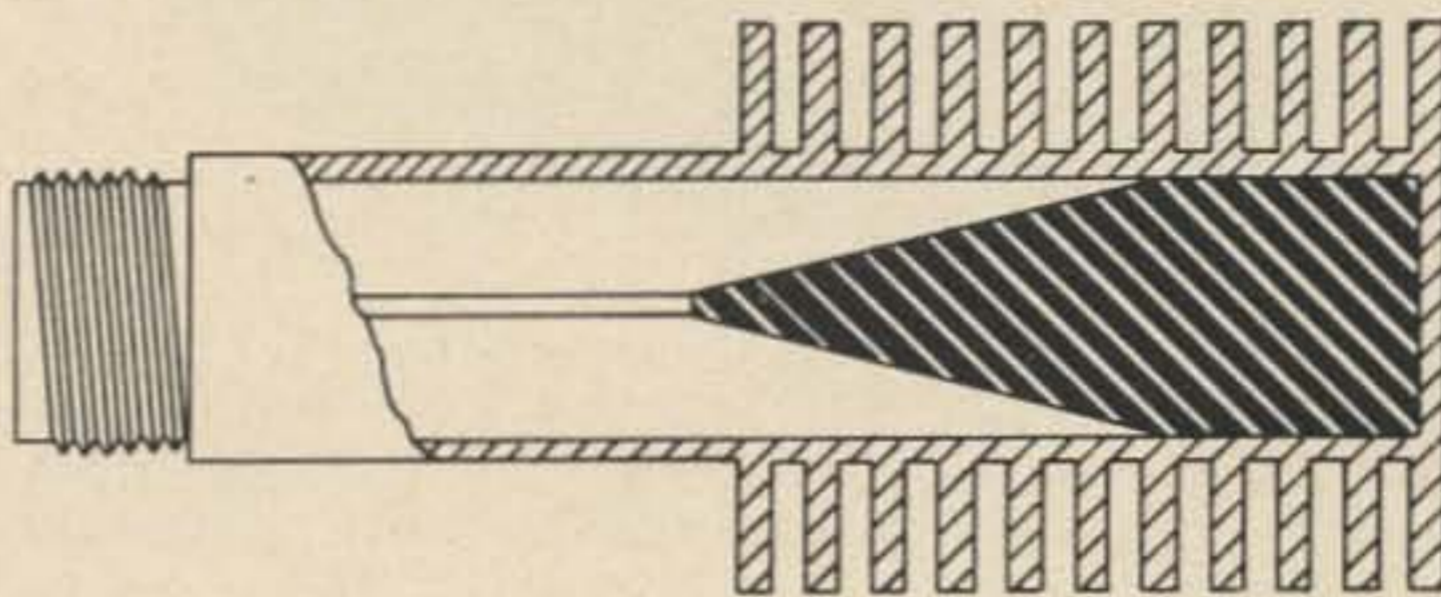
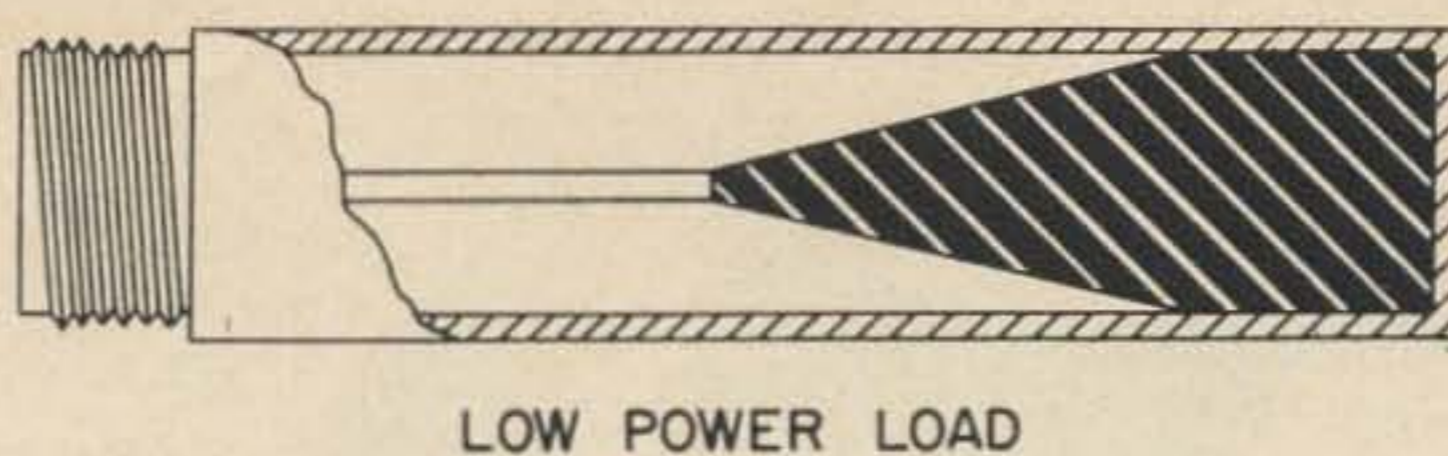


Fig. 15. Construction of broad band coaxial dummy loads. The tapered resistance element of these loads insures that they will provide a matched load up to several thousand megacycles.

the stub is short-circuited, it will present an infinite impedance to the balanced voltage. For unbalance voltages, however, the quarter-wave stub is open-circuited at its end so that the points on the dual line at which the stub is attached are short-circuited for unbalanced currents. Therefore, there will be some voltage from the end of the stub to ground if any unbalance exists on the line.

Dummy loads

The dummy load is an indispensable coaxial accessory which is used primarily for tuning transmitters. However, an accurate dummy load is also useful for calibrating SWR meters and measuring rf power. Although the common household light bulb is sometimes used as a load, it is not too suitable because it does not present a constant load to the transmitter. This is because as the light bulb heats up (becomes brighter), the rf impedance of the filament increases.

Commercial dummy loads suitable for use from dc to microwave are constructed as shown in Fig. 15. Here the resistance element consists of a conical block of resistive material mounted in the end of a metal tube. The tapered section from the center to outer conductor is used to provide a good impedance match over a broad range of frequencies. For

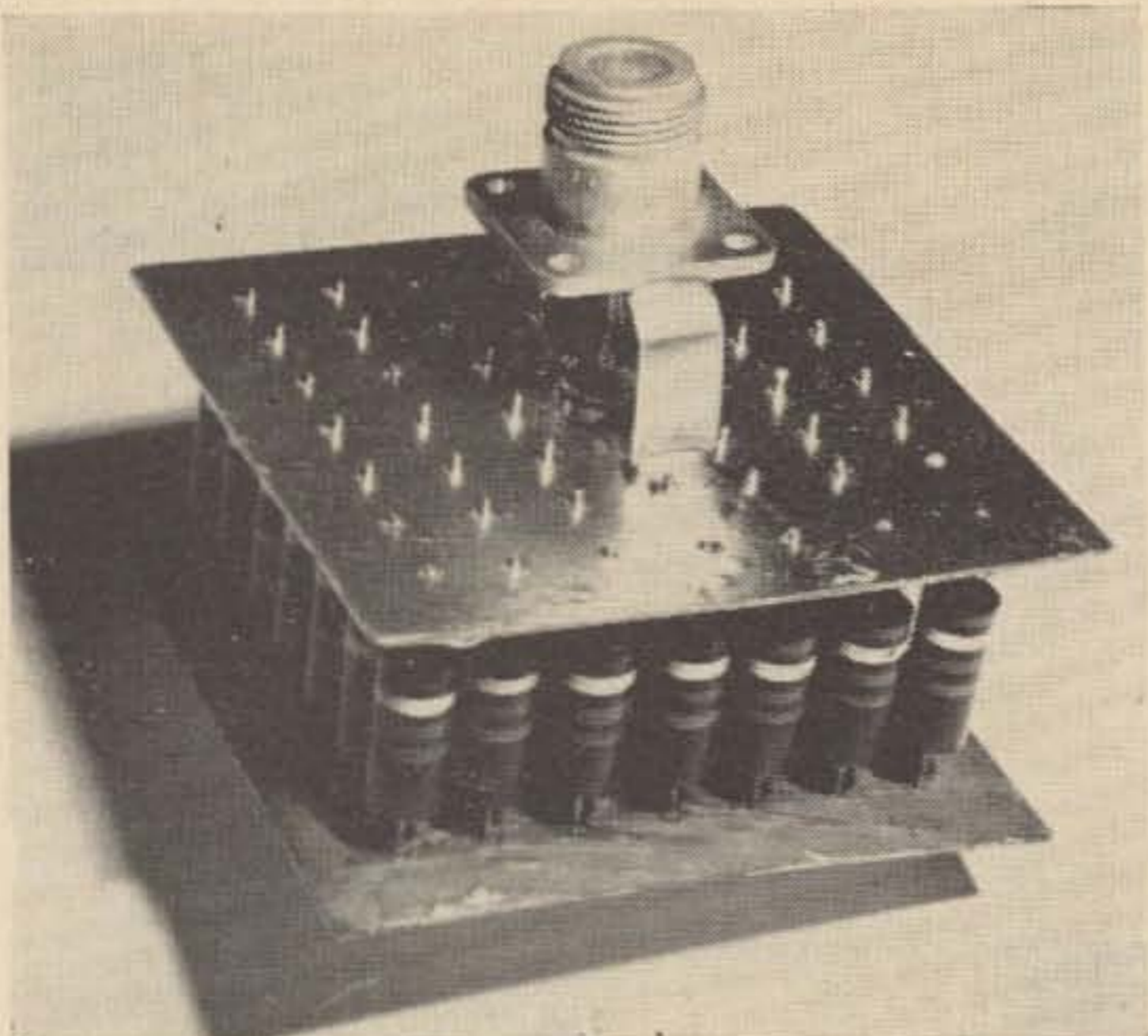


Photo by WA6IAK.

A homemade 100 watt dummy load that is suitable for use to 200 mc. This load is made by installing ordinary two watt carbon resistors between two copper plates.

higher power applications, the metal case may be provided with cooling fins or immersed in a bath of transformer oil.

For frequencies up to about 200 mc, a suitable load may be made by mounting a number of common composition resistors in parallel. In the homemade unit pictured, forty-eight 2400 ohm, 2 watt resistors are mounted between two copper sheets 2 inches square. This load will dissipate 50 watts continuously and up to 200 watts for short periods; the power capacity may be increased by simply immersing the load in a can of ordinary motor oil.

For higher power capacity, a non-inductive carborundum resistor may be used as a



Photo courtesy Heathkit.

The Heathkit "Cantenna" is a dummy load which will dissipate up to a kilowatt for short periods of time. An rf sampling probe is mounted on the top of the container for measuring power output.

dummy load. The Heathkit HN-31 "Cantenna" uses this type of construction to provide a dummy load that will dissipate up to 1000 watts ICAS (intermittent commercial or amateur service) and provide an SWR of less than 2:1 all the way up to 400 mc. The Cantenna has a continuous power rating of 200 watts, but when cooled with transformer oil, it will dissipate 1000 watts for periods up to 10 minutes. Actually, up to about 50 mc this dummy load exhibits an essentially resistive characteristic; above 50 mc it begins to show a small amount of reactance that causes the standing wave ratio to be greater than unity. The overall effect is not too severe on 50 mc, but at 432 mc an SWR of 2:1 can raise havoc with power and SWR measurements. K6MIO has shown¹² that the Cantenna is slightly inductive at 432; by placing a small variable shunt capacitor across the load, this inductive reactance can be nulled out. Installation of a variable 20 pf capacitor will allow the Cantenna to be tuned for minimum SWR over the entire VHF range. Furthermore, tests have shown that this capacitor has almost no effect on the operation of the load below 30 mc.

The Gentec dummy loads are hermetically sealed, nonreactive loads with a nominal impedance of 50 or 70 ohms, depending on the model. The excellent rf characteristics of these loads are a result of the film-type resistors which are mounted in a coaxial cavity inside the can. Radiation fins and ribbed surfaces permit good heat radiation. The model 525 (50 ohm) and 725 (70 ohm) loads will dissipate 125 watts continuous and 250 watts ICAS. For higher power applications, the model 510 will handle 500 watts continuous or 1000 watts ICAS. The model 525 and 725

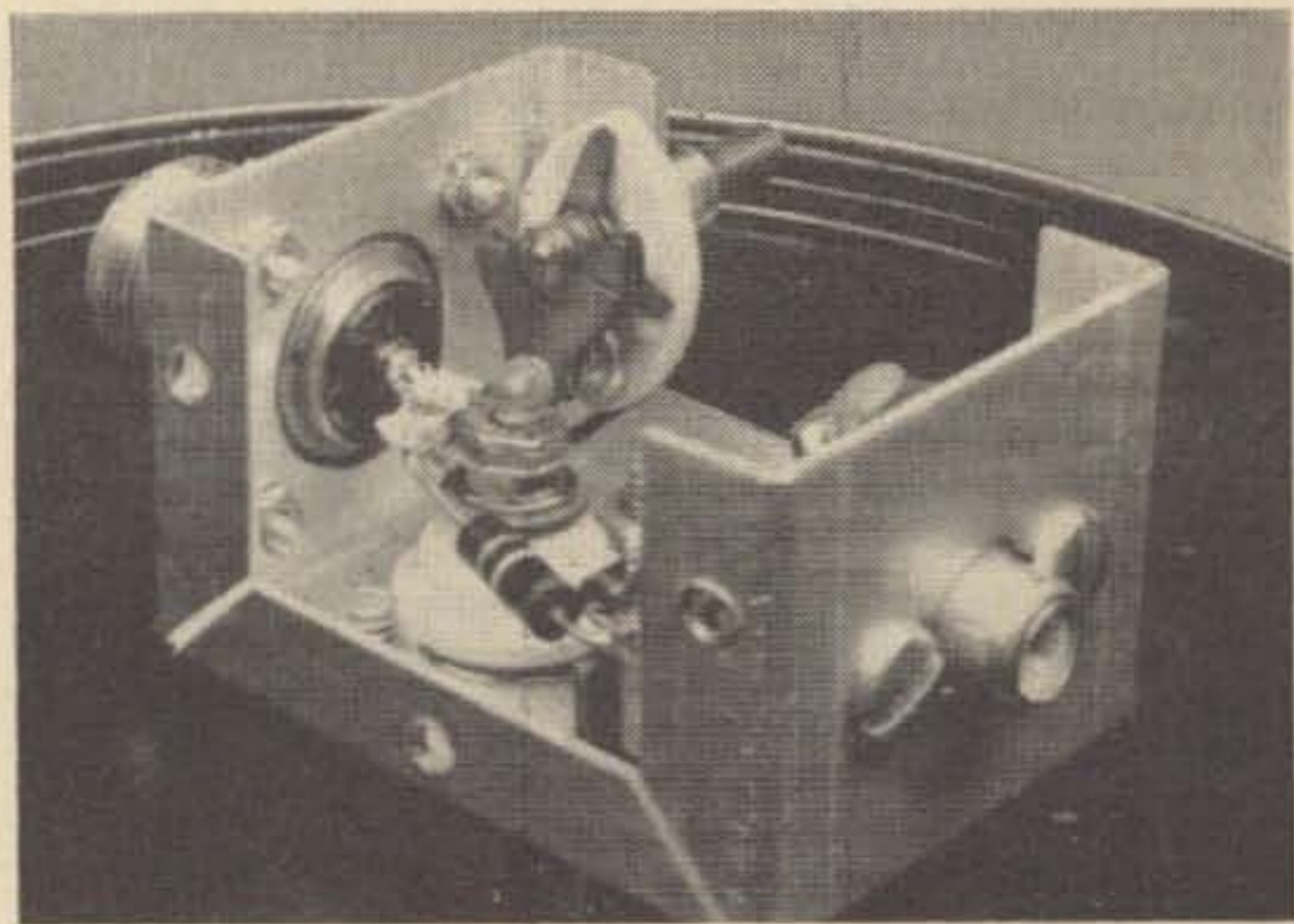


Photo by WA6CQL.

Installation of a 15 pf variable trimmer in the Heathkit HN-31 "Cantenna." This capacitor cancels the slight amount of inductive reactance that is present in the range from 220 to 450 mc so that the "Cantenna" presents an essentially resistive 50 ohm load at 432 mc.

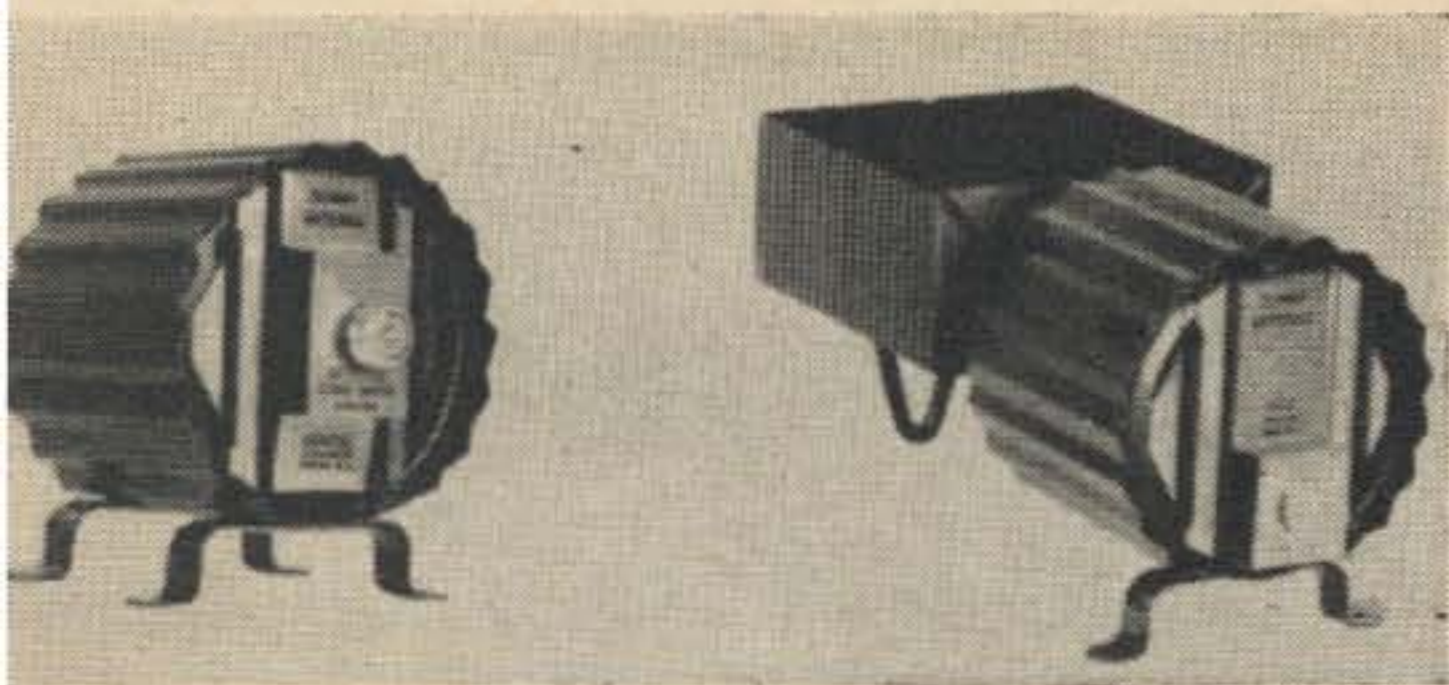


Photo courtesy Gentec, Inc.

The Gentec dummy antennas are hermetically sealed nonreactive loads designed for use from dc to 250 mc. The Model 525 on the left will dissipate 250 watts ICAS; the higher power Model 510U on the right will handle 1000 watts ICAS.

Loads are furnished with type UHF connectors, but the model 510 is available with either UHF, N, or BNC fittings. For low power applications, the Gentec model 507 (50 ohms) and 707 (70 ohms) exhibit an SWR of less than 1.05:1 from dc to over 250 mc and have a continuous power rating of seven watts.

The Radiation Devices Company's coaxial terminations are typical of commercial dummy loads designed to work well into the microwave region. These loads have an SWR of less than 1.05:1 from dc up to 1300 mc and less than 1.15:1 up to 4000 mc. These precision loads are constructed around special microwave film resistors which are carefully mounted in machined assemblies. These loads are available in a low power model (LP-1 series) which has the characteristics noted above, and a higher power version, the MP-1 series, which will dissipate up to 12 watts; 25 watts dissipation may be obtained by mounting the MP-1 series load on a suitable heat sink. The MP-1 series exhibits a maximum SWR of 1.1:1 from dc to 1300 mc and 1.2:1 maximum up to 2000 mc.

Another type of dummy load that has proven to be particularly useful, especially for high power above 300 mc, is the lossy coaxial cable load. In this type of a load, a long length of coaxial line is terminated with a low-wattage, non-inductive 50 or 70 ohm resistor. The length of the line is chosen so that the loss at the frequency of operation is such that only a small portion of the incident power reaches the resistor termination. The loss of RG-8A/U at 432 mc for example is pretty close to 5 db per 100 feet; 600 feet of RG-8A/U then has a total loss of 30 db. This means that if 1000 watts of power is pumped into the input end of the cable, only one watt will be dissipated by the small terminating resistor at the opposite end. The beauty of this type of load is that it is almost purely

resistive and exhibits a low SWR up to several thousand megacycles. However, before constructing a load of this type, consult the coaxial cable power charts to determine the maximum amount of power the cable can handle at the desired operating frequency.

If the impedance of the load is properly matched to the transmission line, the rf power being dissipated in the load may be determined by measuring the rf voltage across the load and using the relationship:

$$P = E^2/Z$$

Where: P = Rf power in watts
 E = Rf voltage across the matched load (RMS)
 Z = Rf impedance of the load in ohms

Example If the rf voltage across a 50 ohm load is 75 volts, what is the rf power?
 $P = E^2/Z = (75)^2/50 = 5625/50 = 112.5$ watts

The Waters model 334 Dummy Load/Wattmeter was designed specifically for amateurs and combines a non-inductive, oil cooled load with an integral direct reading rf wattmeter. This instrument may be used to accurately measure rf power up to 1000 watts from 2 to 230 mc.

A more accurate method of measuring power that requires a little more equipment is the standard *calorimetric* technique.¹⁴ In this method of measurement, the dummy load is cooled by the flow of coolant over it. The average power dissipated by the load can then

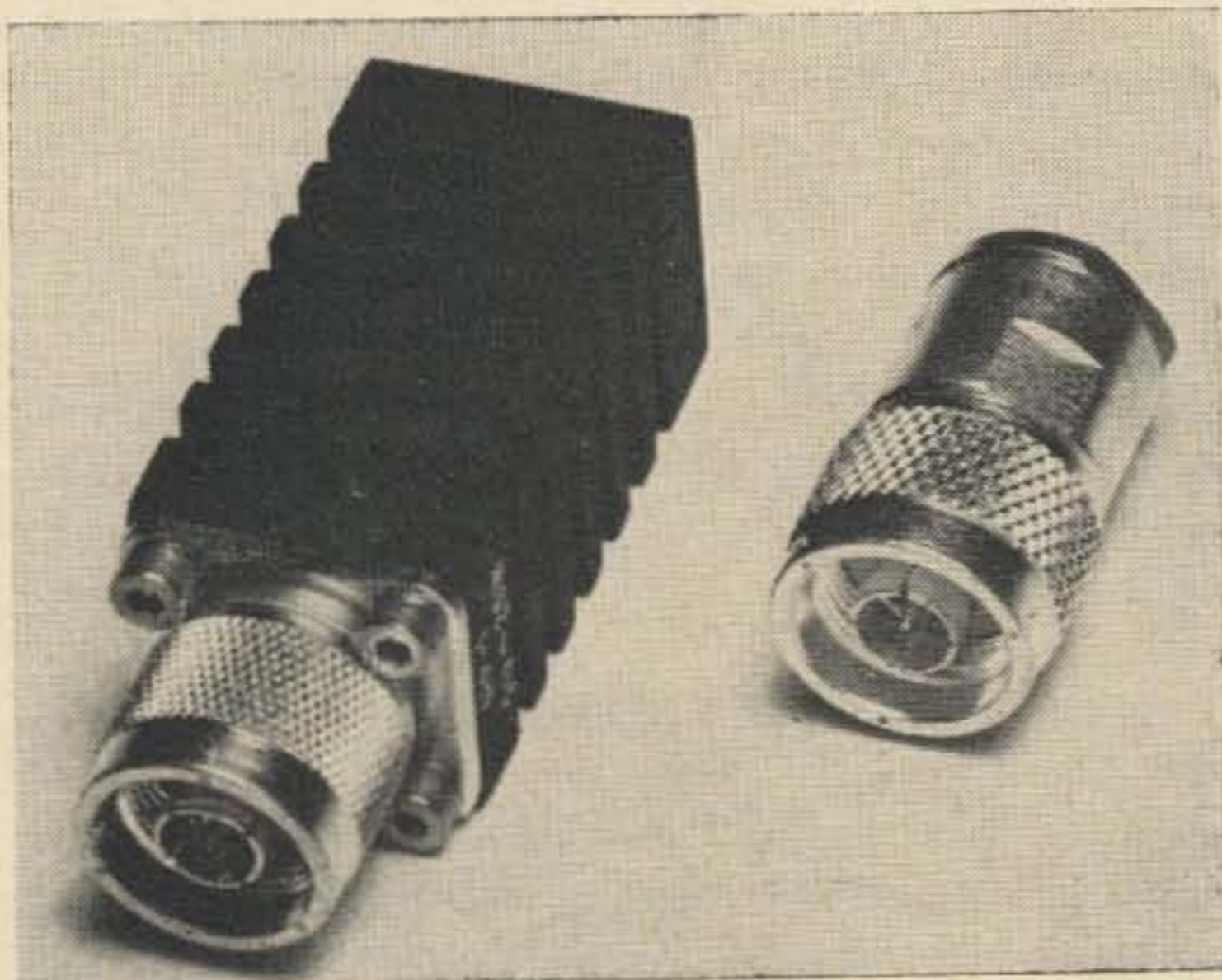


Photo courtesy Radiation Devices Co.

Radiation Devices' precision coaxial terminations. The model on the left will dissipate 12 watts while providing a matched load up to 2000 mc; the dissipation may be increased to 25 watts by mounting the load on a larger heat sink. The load on the right provides a matched load up to 4000 mc and will dissipate one watt.



Photo by WA6IAK.

This commercial dummy load for 50 ohm lines provides a matched load up to 12,000 mc.

be determined by measuring the rate of flow and temperature rise of the coolant and using the following formula:

$$P = 264 Q g S (T_o - T_i)$$

Where: P = Average power dissipated in watts

Q = Rate of coolant flow in US gallons per minute

g = Specific gravity of the coolant

S = Specific heat of the coolant

T_o = Outlet temperature of the coolant °C

T_i = Inlet temperature of the coolant °C

If distilled water is used as the coolant, this formula reduces to the following:

$$P = 264 Q (T_o - T_i)$$

The accuracy of this technique is highly dependent upon the accuracy of the rate-of-flow and temperature measurements, but with the proper instruments, this is not too difficult to obtain. One other important point when using this method is to insure that the heat loss between the input and output measurement points is absolutely negligible; otherwise, erroneous power measurements will result. Also, sufficient stabilizing time must be allowed before the temperature measurements are made because the thermal time constant of this type of equipment is quite long.

Example A dummy load is immersed in a container of distilled water which is being pumped by the load at the rate of 0.5 gallons per minute. If the inlet temperature of the water is 22°C and the outlet temperature is 28°C, what is the average power being dissipated by the load?

$$\begin{aligned} P &= 264 Q (T_o - T_i) \\ &= 264 (0.5) (28 - 22) \\ &= (132) (6) \\ &= 792 \text{ watts} \end{aligned}$$

Transmission line filters

A *low pass* filter is placed between the transmitter and antenna to prevent harmonics of the transmitter from interfering with television reception. After the transmitter has been completely shielded and all the power leads bypassed, the only way that interfering harmonic energy can be radiated is through the antenna. By placing a low pass filter in the transmission line, this type of interfering signal may be effectively controlled. For transmitters operating on the ham bands up to 30 mc, a low pass filter is usually designed so that it has a cutoff frequency of approximately 45 mc. With this type of cutoff, maximum attenuation occurs in the middle of channel 2 and TVI is minimized.

For the operator who is interested in operating on six meters, the problem is somewhat more complex. Since the six meter amateur band is immediately adjacent to television's channel 2, it is difficult to design a filter that is effective in eliminating radiation only two megacycles away. Unfortunately, filters are just not that good. However, by limiting six meter operation to the first one megacycle of the

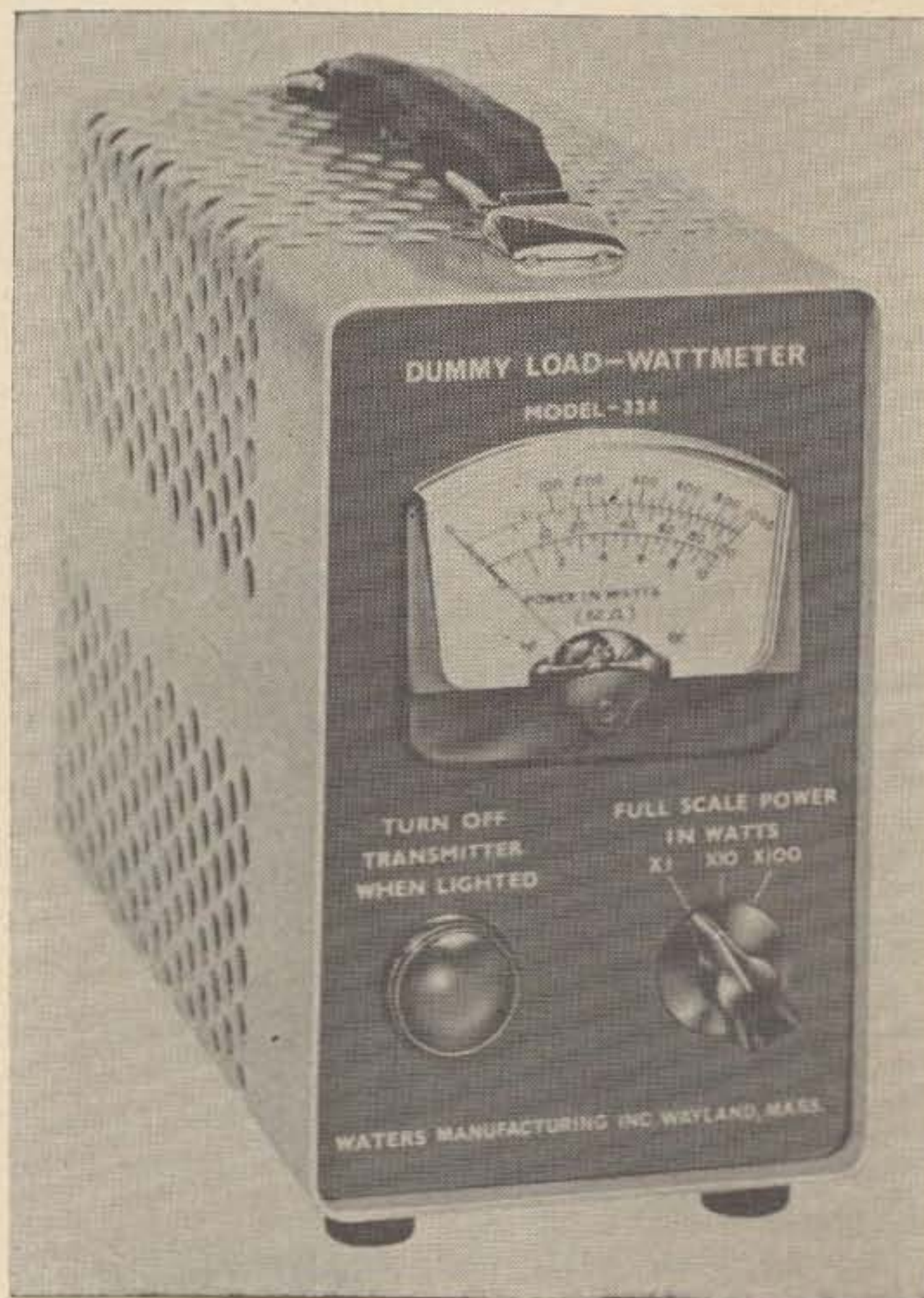


Photo courtesy Waters Manufacturing Co.

The Waters dummy load—wattmeter is an rf power absorption device with an integral direct reading rf wattmeter. It is rated at 50 watts continuous duty or 1000 watts intermittent over a frequency range of 2 to 230 mc.

Table 4. Low pass filters

Manufacturer	Model Number	Impedance (ohms)	Attenuation	Maximum Power (watts)	Cutoff Freq. (mc)	Connectors
Ameco	LN-2	52	35 db above 50 mc	200	40	UHF
Bud	LF-601	52 or 72	85 db above 54 mc	1000	42	UHF
B&W	423	52 or 75	50 db above 62 mc	100	54	UHF
B&W	424	52 or 75	50 db above 54 mc	100	40	UHF
B&W	425	52	85 db above 54 mc	1000	40	UHF
B&W	426	75	85 db above 54 mc	1000	40	UHF
B&W	427	52 or 72	60 db above 62 mc	1000	54	UHF
Clegg	372	52	40 db above 68 mc	240	54	UHF
R. L. Drake	TV-1000-LP	52	60 db above 57 mc	1000	52	UHF
R. L. Drake	TV-100-LP	52	60 db above 57 mc	100	52	—
R. L. Drake	TV-CB-LP	52	60 db above 50 mc	100	43	UHF
E. F. Johnson	250-20	52	75 db above 54 mc	1000	45	UHF
E. F. Johnson	250-35	72	75 db above 54 mc	1000	45	UHF

band, it is possible to employ filters that have a cutoff frequency at 53 mc. These filters don't have as much attenuation on channel 2 as do those with a cutoff frequency of 45 mc, but they will eliminate many cases of television interference. However, since the cutoff frequency is so close to the operating frequency, effective low pass filters for six meters will not handle a full kilowatt with realistically sized components; most are limited to approximately 200 watts.

Although low pass filters are by far the most common transmission line filters used in

amateur stations, *band pass* filters are very useful in many applications. When operating on VHF and UHF bands, in many cases there are interfering signals from FM stations, television stations and radar installations which are using assigned channels very close to the amateur frequencies. In some cases these interfering signals completely obliterate signals on the amateur bands. By installing a band pass filter in the feed line, this type of interference may be minimized. Other places where band pass filters are helpful are in local oscillator chains for 432 and 1296 mc converters and



Photo courtesy Squires-Sanders Inc.

Clegg Laboratories low pass filter for 52 ohm lines provides more than 28 db rejection from 55 to 68 mc; more than 40 db rejection on any TV channel above 68 mc. A built in notch filter may be adjusted to provide up to 35 db rejection from 55 to 68 mc.



Photo courtesy E. F. Johnson Co.

E. F. Johnson's low pass filter exhibits a cutoff frequency of 45 mc and provides maximum attenuation at 57 mc, the center of TV channel 2. This filter will handle a full 1000 watts of AM or 5000 watts peak SSB.

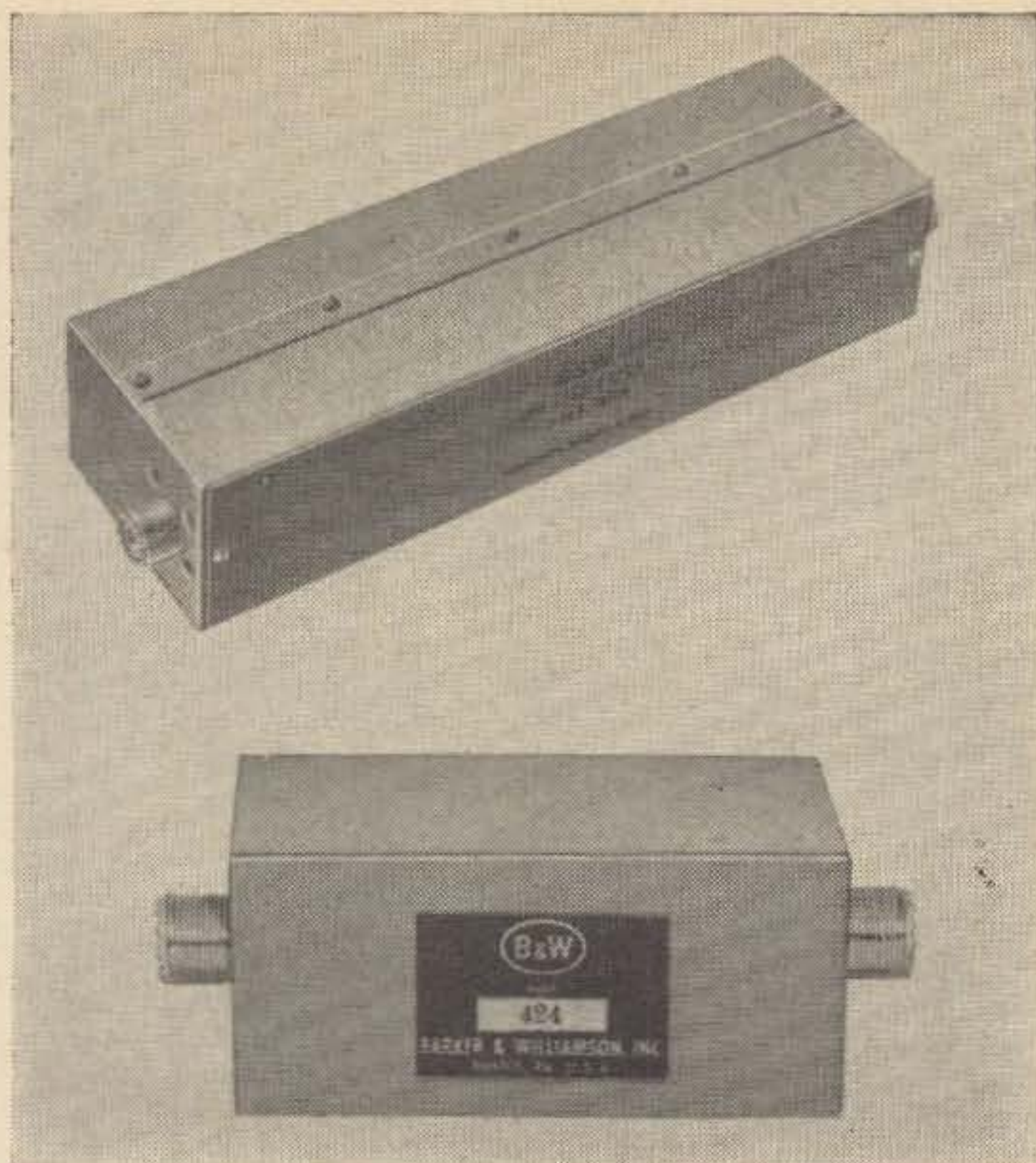


Photo courtesy Barker & Williamson, Inc.

These B&W low pass filters prevent the radiation of spurious and harmonic rf energy which causes TVI. The Model 425 on the left will handle the legal limit while the Model 424 in the foreground is limited to 100 watts.

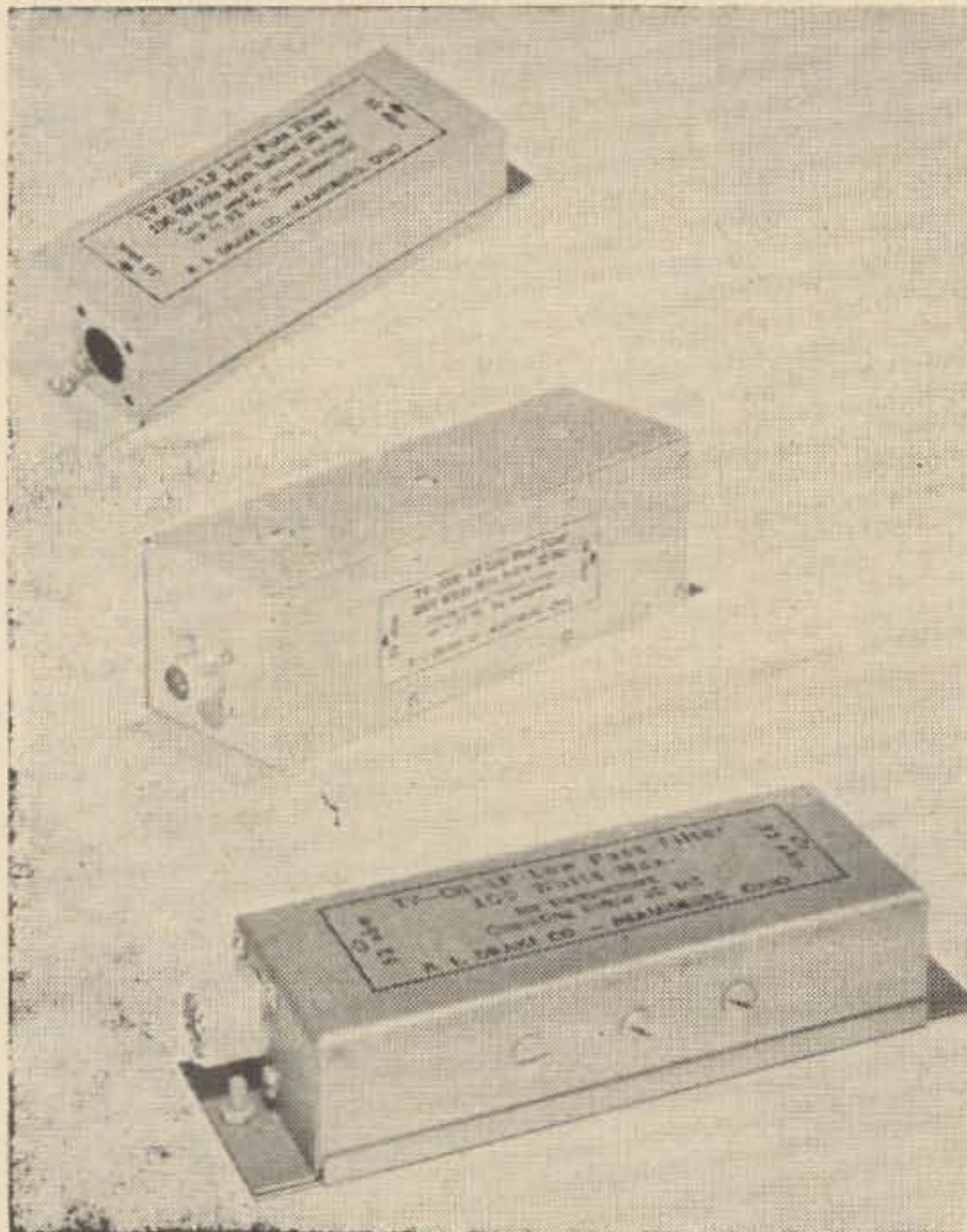


Photo courtesy R. L. Drake Co.

These R. L. Drake low pass filters are designed to prevent TVI from amateur transmitters operating up through 6 meters. The TV-1000-LP filter in the center will safely handle a full kW on the bands up to 10 meters and 200 watts on 6 meters. The smaller TV-100-LP is capable of 100 watts below 30 mc and 20 watts on 6 meters.

when tripling from 144 to 432 mc or from 432 to 1296 mc. In these cases the band pass filter will eliminate birdies in the receiver and/or undesirable out-of-band radiation.

A properly designed filter will introduce very little loss into the transmission system, typically 0.5 db or less. However, to obtain proper filtering, it is imperative that the filter operate into a matched transmission line. If the SWR on the transmission line is greater than about 2:1, the filter will not operate properly and the insertion loss will rise astronomically. Also, if there is a high SWR on the line, irreparable damage may occur to the filter because of the higher effective voltages and currents associated with the high SWR.

Antenna tuners

Antenna tuners are often included in an antenna/transmission line system so that the transmitter and receiver will look into the proper load. However, it should be emphasized that the installation of an antenna tuner is not a cure-all for high standing wave ratios and mismatched antennas; all the antenna tuner can do is provide the transmitter with the load that it was originally designed for. In this respect it will lower the SWR that the transmitter must work into. However, only changing the antenna matching system or the transmission line or both will lower any standing waves that may be residing between the antenna tuner and the antenna.

The addition of an antenna tuner in the line is particularly advantageous when it is desirable to use a low pass filter with a high SWR on the antenna feed line. As has been



Photo courtesy James Millen Mfg. Co.

The Millen Company's Transmatches are designed to provide a match from the 50 to 70 ohm output of a transmitter to unbalanced loads from 10 to 500 ohms. The Transmatch on the left will handle 2kW peak, while the Transmatch Junior on the right will handle 300 watts peak. Both of these units have a built in reflectometer for measuring swr.

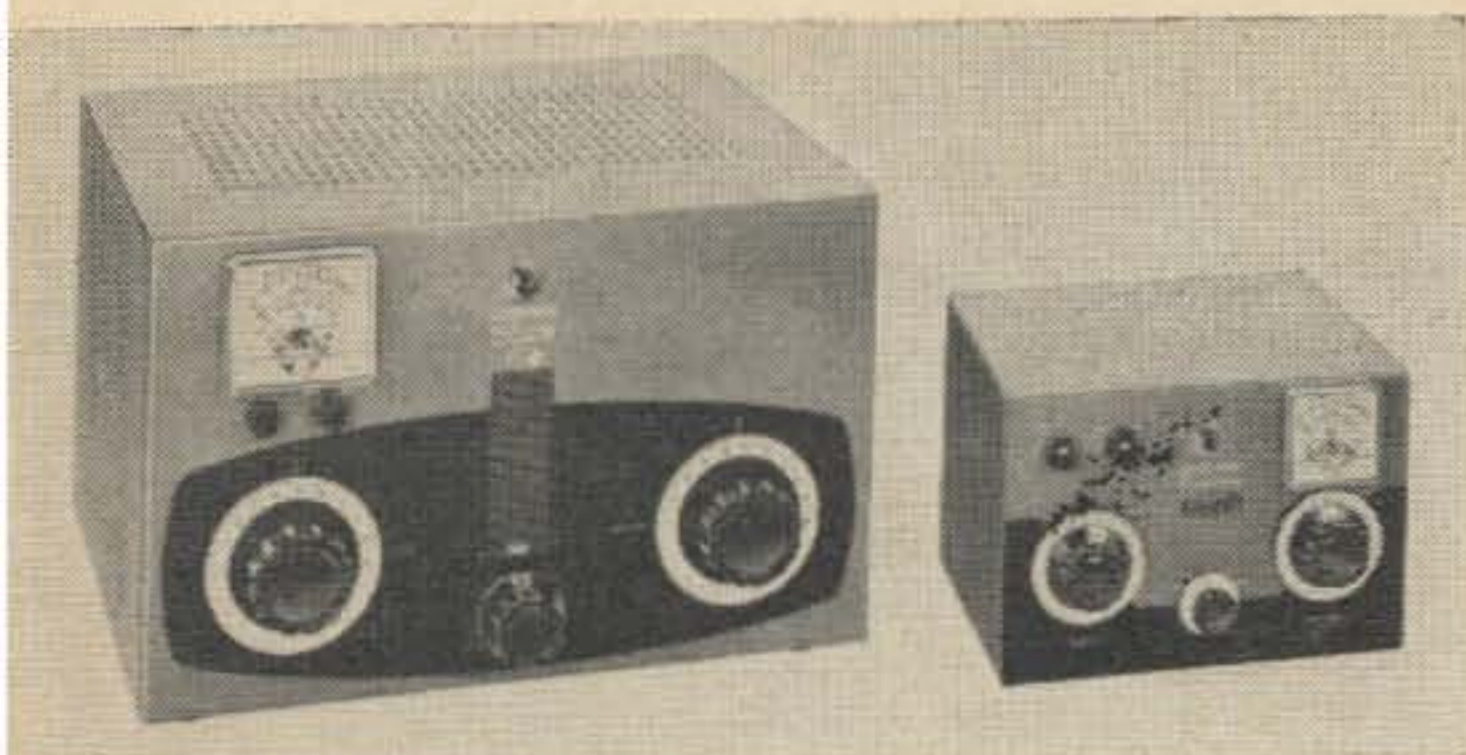


Photo courtesy E. F. Johnson Co.

The Johnson "Matchboxes" are designed to match 52 ohm coaxial line to both balanced and unbalanced reactive and non-reactive loads. These units will operate throughout the 3.5 to 30 mc amateur bands and are available with built-in swr indicators. The kilowatt "Matchbox" on the left will take the legal limit while the smaller unit on the right is limited to 275 watts.

previously noted, the filter must be properly terminated if it is to work properly. If the filter is installed between the transmitter and the antenna tuner, and the tuner is properly adjusted, the filter will be properly terminated and will exhibit the proper cutoff and insertion loss characteristics. Often the inclusion of an antenna tuner in the system is helpful in the reduction of harmonics. This is because the natural Q of the tuned circuits used in the tuner inherently discriminate against frequencies other than those to which they are tuned.

The James Millen "Transmatch" is designed to convert the impedance of any 15 to 500 ohm unbalanced coaxial fed antenna system to 50 ohms so that the transmitter will load properly. Actually, on the lower bands the impedance range of the Transmatch is higher, going up to 4000 ohms, but on ten meters it is somewhat lower. This is because the reactance of the components used in the tuner change with frequency.

There are two models of the Transmatch available, the regular model which is capable of handling the full legal limit and the Transmatch Junior, which is limited to 300 watts peak. A reflectometer is built into each of these units as a constant monitor of line SWR and as an aid in tuning them on each of the bands.

The E. F. Johnson "Matchbox" is an antenna matching and switching system which is designed to match 50 ohm coaxial lines to reactive or nonreactive loads, either balanced or unbalanced. The Matchbox is also designed to provide a separate matching network for the station receiver. A built-in antenna changeover relay is included and it has a provision for muting the receiver when transmitting. The Kilowatt Matchbox antenna changeover system includes a time delay circuit for the relay, providing fast make-slow break action that

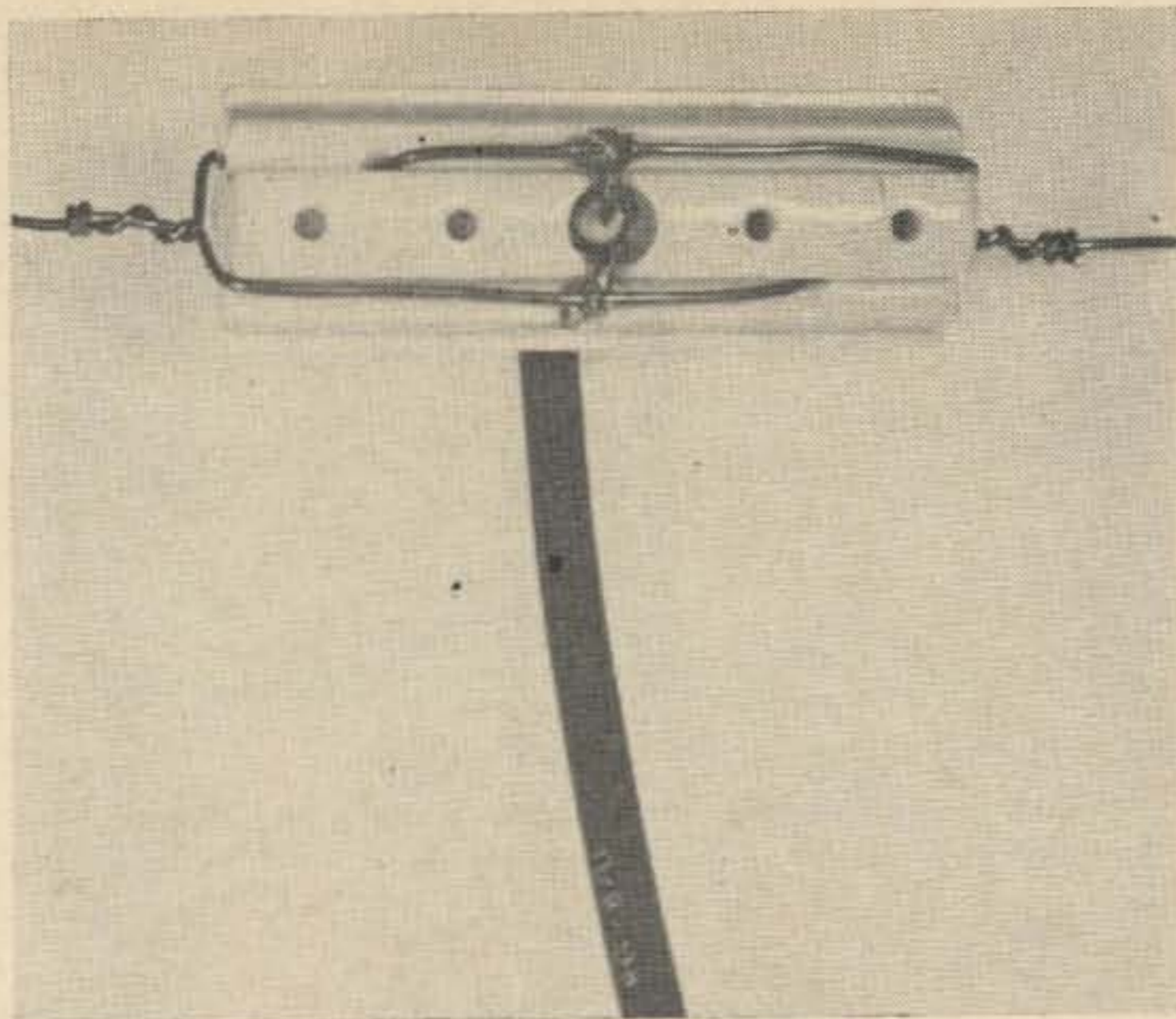


Photo courtesy Yatter Laboratories.

A Yatter Laboratories solid porcelain strain insulator provides a neat and economical method of feeding a dipole antenna with coaxial line. This strain insulator has provisions for mounting a 1:1 coaxial balun, loading coils or even open wire line. When assembled according to the manufacturer's instructions, the completed unit is permanently weather proof and cannot be pulled apart.

prevents arcing or sticking of the relay contacts. This also protects the receiver from high voltage transients which might occur during the antenna changeover from the transmitter. A self-contained directional coupler provides a constant monitor of line operation.

The 275 watt Matchbox is a smaller version

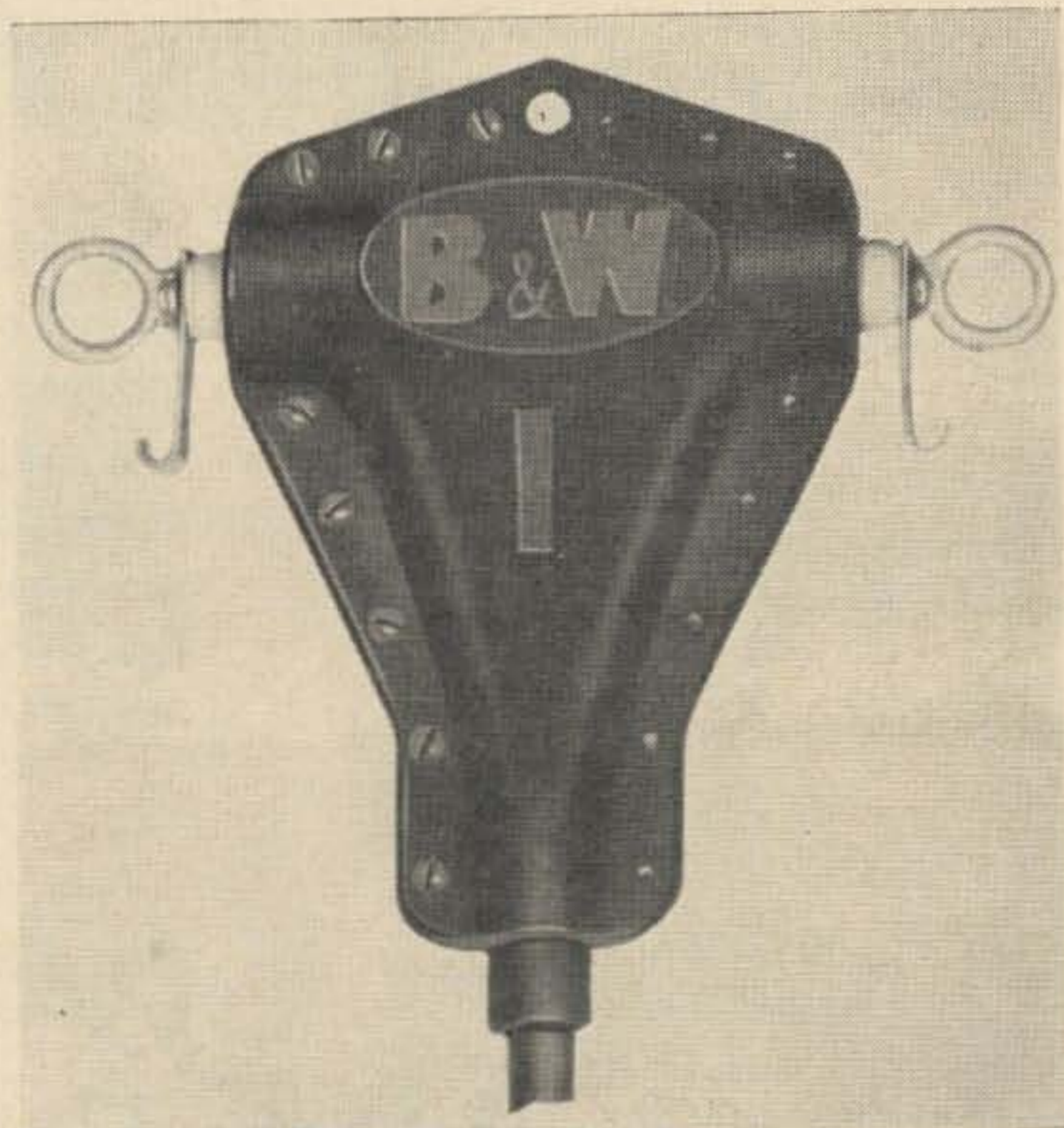


Photo courtesy Barker & Williamson, Inc.

This B&W coaxial cable connector provides a strong, weatherproof connection between the coaxial feed line and the center of a dipole antenna.

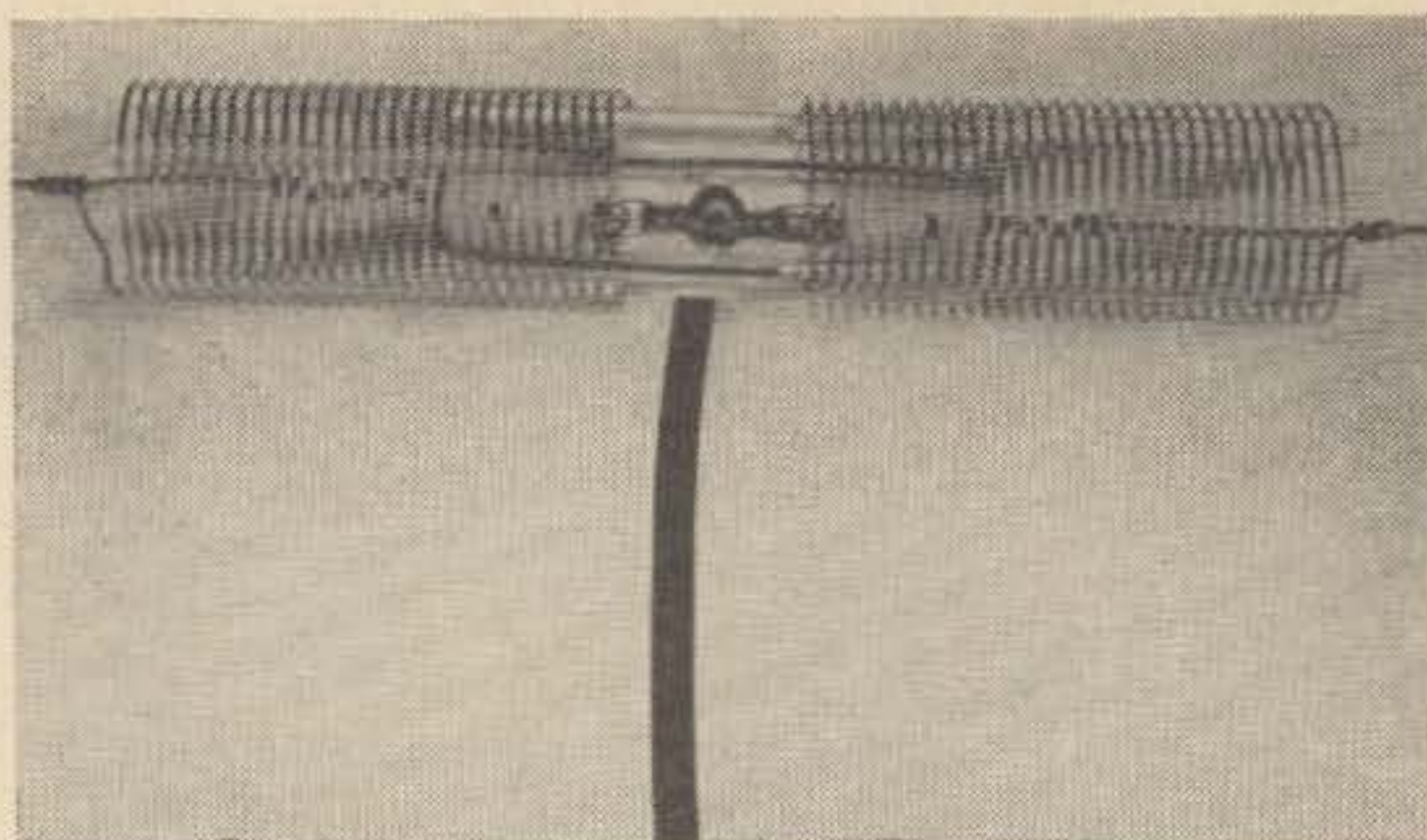


Photo courtesy Yatter Laboratories.
A Yatters Laboratories strain insulator, showing the installation of loading coils and coaxial feedline.

of the kilowatt unit for lower power applications where the high power capabilities of the larger unit are not required. The small unit is almost identical to the larger unit except that it is available with or without the directional coupler.

The World Radio Laboratories MM-100 "Mini-Matcher" is designed to match the low impedance output of an amateur transmitter to a high impedance antenna. This is particularly useful when using an end fed antenna; in many cases the installation of an end fed antenna is more practical than the common center fed doublet. The Mini-Matcher may be used with transmitters that have input powers up to 100 watts SSB/CW or 75 watts AM.



Photo courtesy Budwig Manufacturing Co.
The Budwig antenna-coax connector. This molded unit features holes at both ends for element tie points and has molded-in copper leads for connection to the UHF coaxial connector.

REFERENCES

1. Norgorden, "A Reflectometer for the H-F Band," NRL Report 3538
2. L. G. McCoy W1ICP, "The Monimatch," QST, October 1956
3. L. G. McCoy, W1ICP, "The Monimatch—Mark II," QST, February 1957
4. A. F. Prescott W8DLD and W. C. Loudon W8WFH, "Low-cost RF Wattmeter," GE Ham News, May-June 1961
5. W. B. Bruene W0TTK, "An Inside Picture of Directional Wattmeters," QST, April 1959
6. D. DeMaw W1CER, "The Varimatcher," QST, May 1966
7. C. Byler K2HLT, "All Band Balun Coil," GE Ham News, January-February 1960
8. R. Turrin W2IMU, "Broad-Band Balun Transformers," QST, August 1964
9. W. L. Orr W6SAI, "A Broad-Band Balun for a Buck," CQ, February 1966
10. R. Pafenberg W4WKM, "A Cast-Iron Balun," 73, September 1963
11. M. Hughes VE2AUB, "Diode Controlled Break-In," 73, January 1965
12. J. Kennedy K6MIO, "Modifying the Heath Cantenna for UHF," 73, January 1965
13. K. Holladay K6HCP and D. Farwell WA6GYD, "Beer-Can Baluns for 144, 220 and 432 mc," QST, February 1965
14. National Bureau of Standards Circular 536, March 16, 1953

LIBERTY ELECTRONICS WANTS TO BUY FOR CASH

Electron tubes and semiconductors

Most any type or quantity
Receiving, transmitting, special
purpose, magnetrons, klystrons
We will make you an immediate
offer in cash.

Special sale

HP-200BR audio
oscillator \$65

Surplus communication and test equipment

AN/GRC-3, 4, 5, 6, 7, 8, 10, 19, 26, 27, 46, VRC-12

AN/PRC-8, 9, 10, 25

Test equipment with ARM, SG, URM, UPM, USM, and TS prefixes

Communications: AN/TRC-1, 24, 35, 36

Receivers: AN/APR-9, 13, 14, R-388A, R-274, R-390A, R-391, etc.

Indicators: ID-250, 251, 387, 257A, etc.

Aircraft: AN/ARC-27, 34, 38, 44, 52, 55, 57, 73, 84

AN/ARN-14, 59, 67, 70

AN/APS-42, 81


AN/APN-1, AN/GPN-2A

Also: Tektronix, Hewlett Packard, Booten, and General Radio
equipment, etc.

Liberty Electronics, Inc.

548 Broadway, New York, New York 10012, Phone 212-925-6000

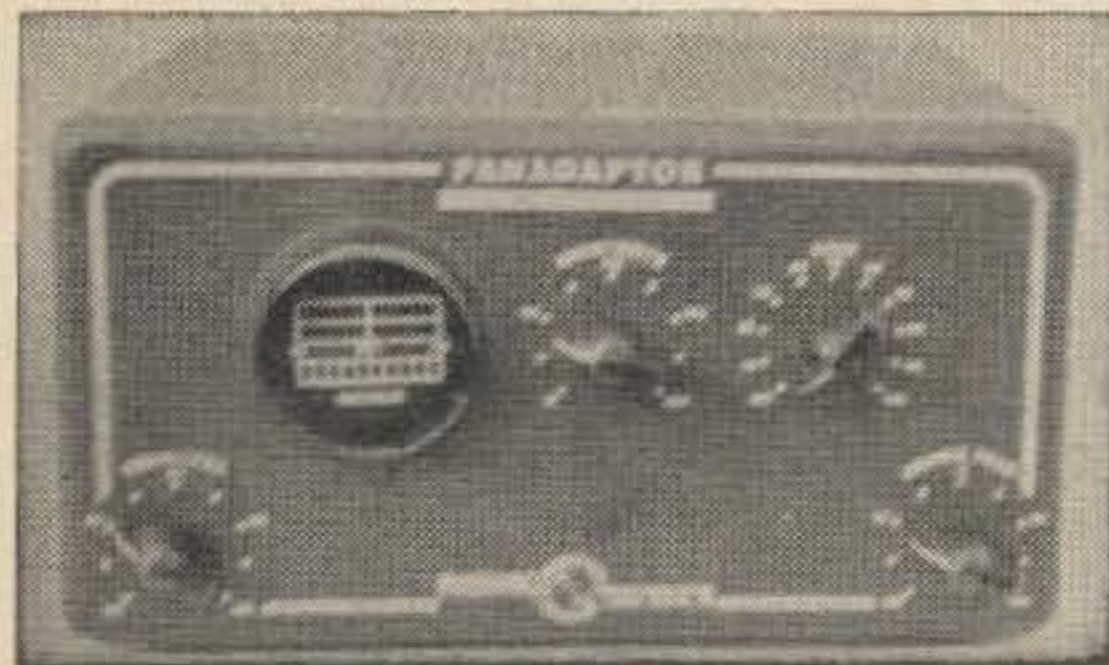BRAND NEW PANADAPTOR PANORAMIC MODEL PCA-2 TYPE T-200




Here is another scoop by SELECTRONIC: A BRAND NEW GENUINE PANORAMIC RADIO PRODUCTS INC. PANANADAPTOR. These units are small and of a modern decor, so that they will blend with any station. They come complete with instruction manual.

SPECS:

Power Rec'd.: 115V 50-60 cycles
I.F. Range: 450-470KC
Screen Size: 2" dia.
Sweep Width: \pm 100 KC to 0 KC
Tubes: 11
Size: 11"W x 6 $\frac{1}{2}$ "H x 10"D.
Shipping Weight: 20 lbs.
Price: \$79.95

BRAND NEW FR-4/U/URM-79 FREQUENCY METERS

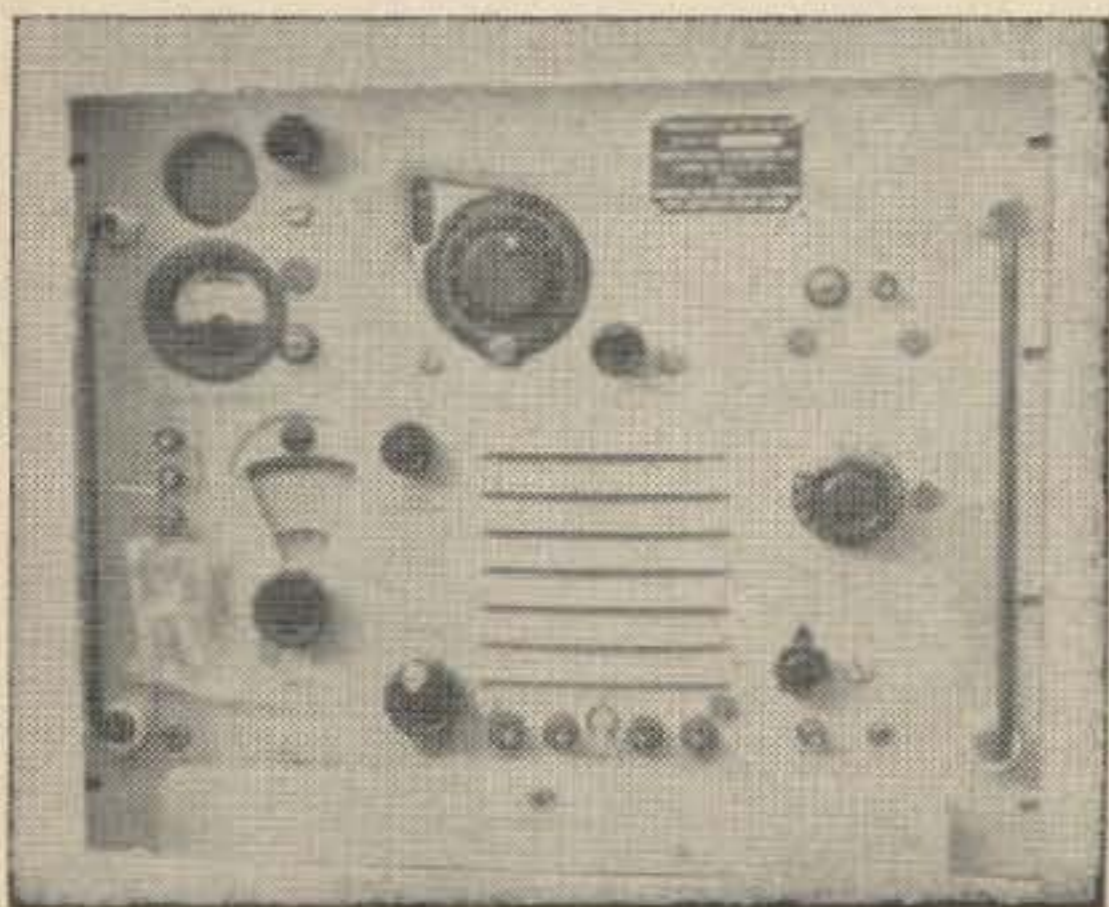Here is a real hot item for you discriminating hams or labs who are interested in the ultimate accuracy in frequency measurements. All units are brand new in original crates with spare parts, instruction manual and two calibration books. The spare parts even include a spare crystal oven and crystals, and all tubes.



SPECS:

Frequency range: 100 KC to 20 MC (7 bands) usable to 1000 MC.
Oscillator freq.: 100 KC to 250 KC (proxy) 1250 KC crystal, 15 to 20 KC (interpolation), 10 KC (blocking)
Frequency stability: .0001%
Accuracy: .001%

R.F. Output: 100 microvolts min. in 51 ohms.
Audio Output: 2 MW min. in 600 ohms
Method of Interpolation: Visual, with built in oscilloscope
Tubes: 30
Harmonic selector: 9th thru 26th
Power Required: 115 or 230 V, 50 to 1000 CPS, 136 watts.
Weight: 146 lbs. in case
Size: 22"H x 26 $\frac{1}{4}$ "W x 20 $\frac{3}{4}$ "D
Description: a portable heterodyne type frequency meter for portable or fixed use. May be removed from the case and rack mounted, or used in the case with the tilt base as a table model.
Shipping Weight: 160 lbs.
Price: \$350.00

DIRECT PLUG-IN REPLACEMENTS

PREMIUM 5R4 SILICON PLUG-IN REPLACEMENT RECTIFIER RATINGS: 400 PIV @ 1 amp. D.C.

These are a direct plug-in replacement unit that will eliminate tube replacements, greatly reduce heating, and provide instant warm-up. All units are properly compensated, potted and power tested at 1 amp. average D.C. current.

PRICE: \$6.00

5U4/5Y3/5Y3GT/5V4/5V4GT/5AU4/5T4/5W4/5Z4/
5AW4/5V3/5AX4/5AZ4/5Y3G (1800 PIV)

Our #SA will replace any of the above tubes.

PRICE: \$1.95

80/5Z3 Our replacement #SH

PRICE: \$1.95

OZ4/64 Our replacement #SE

PRICE: \$1.95

EPOXY SILICON DIODES with silver leads @ 1.5
amps

50—200 V	@ .06
200—400 V	@ .14
400—600 V	@ .24
600—800 V	@ .36
800	@ .44
1000 or better	@ .54

RDR RECEIVER & SPARE PARTS WITH 10 CRYSTALS

Mfg. by RCA BRAND NEW

Freq. range: 225—390 mcs.

You get two wooden crates which include:

Box #1

RDR RECEIVER with 13 V dynamotor output is 385 VDC @ 500 ma

Box #2

1—set of spare parts which includes:

- 1 Headset
- 1 Set of operating tubes (spares)
- 1 Headset extension cord
- 10 sets of fuses
- 2 pilots lights
- 1 set of connecting cables and other parts too numerous to mention.

All this in original military boxes, receiver packed in Aluminum water proof case, manual included. Easily converted to 200 mc Ham Band or use as they are for UHF aircraft band. You get all that is required to operate except the 12 VDC Source and the Antenna. BRAND NEW

PRICE \$34.95 each while they last f.o.b. our Warehouse.

SELECTRONICS

1206 S. Napa Street
Philadelphia, Pa.

HO 8-7891

HO 8-4645

All prices are FOB our Philadelphia warehouse. All merchandise described accurately to the best of our knowledge. Your purchase money refunded if not satisfied. Terms are cash. Minimum order is \$5. The public is welcome to browse. We're open weekdays 8 to 5 and Saturdays 8 to 1.

GET IT from GOODHEART!

EVERYTHING UNCONDITIONALLY GUARANTEED!!

PROFESSIONAL HI-FI CONDENSER MICROPHONE

Brand new \$114.85 capsule only, but we include dwg of Paramount Picture's cathode-follower preamp using only 3 batteries, 3 resistors, 3 capacitors, 1 #5718 tube. Mnfr's specs: "+1 db from DC to 12 1/2 kc, usable beyond 25 kc; 25 pf; -75 db across 10 meg load for 10 bar signal at 180 v polarizing; will work past 170 dbm; will stand 200 G shock." Unidirectional. Size: Will fit in 2-1/16" circle; 7/8" thick OA. **WHILE THEY LAST.** postpaid, only 27.50

KEEP LINE VOLTS CONSTANT AUTOMATICALLY

These Regulators. **ALL AT LOW SURPLUS BARGAIN PRICES,** hold output at 115/120 v despite line changes 95-130 v and load changes 0 to full load. **CV:** Tuned saturating isolating transformers hold to 1%, have 14% harmonics. **EM:** Servo, hold to 1%, **ZERO** harmon. **S/EI** Electronic, hold to 0.1%, 3% max. harm. Sola, Sorensen, Superior Electric.

CV: 250 VA \$ 22.50	500 VA \$ 37.50
1 KVA 69.50	2 KVA (230v) ... 99.50
S/EI: 500 VA 99.50	5 KVA (230v) ... 350.00
2 KVA * 129.50	1 KVA 129.50
2 1/2 KVA * 199.50	2 KVA 199.50
*Items are special values	3 KVA 279.50
10KVA	595.00

EM: 6 KVA, \$279.50 (Incl. Gen. Radio 1570AL)
EMI (transistorized) 28 KVA 230V 350.00

ALL-BAND SSB RCVR BARGAIN: Hallicrafters R-45/ARR-7, 550 kc to 43 mc continuous. Voice, CW, MCW, aligned, grtd, w/ book; 2 RF, 2-IF's. S-meter: noise lmtr; 3 xtl, 3 non-xtl selectivity choices. Less pwr supply 149.50
 60 cy pwr sply: \$30. SSB product detector: \$20

TIME LAY PLAN: Any purchase totaling \$160.00 or more down payment only 10%

R-23/ARC-5 Command rcvr 190-550 kc.	14.95
A.R.C. 12 #22 Command rcvr 540-1600 kc.	17.95
ARR-5 rcvr, 60 cy, am/fm, 27-140 mc.	149.50
APR-4Y AM/FM Rcvr mod. to 115 v 50/60 cy, with pwr plug, book, tuners 38-1000 mc.	250.00
P.U.R. for tuners 975-2200 and 2175-4000 mc.	
RA-62-B is AC pwr sply for SCR-522, only	17.95
LM-14 freq. meter, .01% 125 kc-20 mc.	57.50
TS-323/UR freq. meter 20-480 mc., .001%	169.50

OTHER MATERIAL: Hewl-Pack & Tekt. Scopes. 30 types of Signal Generators, Gertsch material, Bridges, VLF Receivers, Noise/Field-Strength Meters, DVM's, etc. etc. **WRITE! WE ALSO BUY!**

R. E. GOODHEART CO. INC.

Box 1220GC Beverly Hills, Calif. 90213
 Phone: Area 213, office 272-5707, messages 275-5347

Transformer pri. 117v 60 cy. Tapped sec. 1200v C.T. @ 200 ma. and 740 C.T. @ 235 Ma. 3200v test. Wt. 12 lb. \$3.25. Sealed. Mtg. screws. Stand-off terms.

Transformer pri. 105, 115 & 125v 60 cy. Sec. 700v C.T. @ 250 ma. Sealed case. Mtg. screws. Stand-off terms. Wt. 8 lb. \$2.50.

Isolation transformer. 115v 60 cy. pri. Sec. 115v. 50 watt. Open frame. Mtg. holes. Wt. 3lb. \$1.75.

1 KW. Variable Inductor. Johnson 226-5. Shpg. Wt. 10 lb. A rare bargain at \$25.00.

5 mfd. at 2000 volts electrolytic. Mtg. bracket. Wt. 3 lb. \$1.25 ea.

3.7 to 52 mmfd. variable cap. HF-50. Single hole panel mount. 60¢ ea. or 2/\$1.00.

All items are new and F.O.B. Worthington, Ohio

A.R.C. Sales, P.O. Box 12, Worthington, Ohio 43085

SURPLUS WANTED

We'll pay you the absolutely Highest Prices for almost any piece of equipment in any condition. We'll trade also. We'll pay in 24 hours too. Just send list, or telephone collect for quick quote. Particularly interested in all AN/GRC, PRC, ARC, ARM, UPM, USM, APR, APN, URM, RT-66-70, T-195, R-392, etc.

MILITARY ELECTRONICS CORP./DIV. SPACE ELECTRONICS

4178 Park Ave., Bronx, N.Y. 10457 (212) CY 9-0300

SURPLUS WANTED

Lower prices on KK IC's

Fairchild has reduced the already-low prices on the integrated circuits used in WB6AIG's Kindly Keyer in the July issue. The old price on the JK Flip Flops was \$3.95; the new is \$1.50, not a bad price for a tiny package containing 12 transistors and 16 resistors. The Dual Two Input Gates were \$1.65. Now they're only 80¢.

Somehow the price and source of the etched circuit board used in this keyer was left out of the article. The board is small and a real horror to make and drill with its 120 tiny holes (part of them number 60), so it would probably be a lot better to buy than make. At any rate, the fiber glass board with all holes drilled is \$4.95. You can buy it from Harris Company, 56 E. Main Street, Torrington, Conn.

T. T. FRECK, W4WL—FRECK RADIO AND SUPPLY

—BILL BECK, K4QOK

38-40 Biltmore Ave., Asheville, N.C. 28801, phone 254-9551
 Collins 32V1 \$129 " 2BQ \$29.50 Hallicrafters
 " KWM1 \$275 Globe 400D \$100 SX99 ... \$65
 C.E. 10B/458 " LA-1 lin. \$45 Hallicrafters
 vfo \$85 Globe DBS100 HT40 trans-
 Drake TR3/ kit \$45 mitter ... \$45
 ACPS \$495 Gonset G77 Hallicrafters
 Drake 2B Revr \$189 mob. xmtr. \$59 SX140/spkr \$45
 Write for used-equipment list covering many other pieces of good used gear. All guaranteed and check out before shipment.

ALL BAND TRAP ANTENNA!



Reduces Interference and Noise on All Makes Short Wave Receivers. Makes World Wide Reception Stronger. Clearer on All Bands!

For ALL Amateur Transmitters. Guaranteed for 1000 Watts AM 2000 SSB Pi-Net or Link Direct Feed. Light, Neat, Weatherproof.

Complete as shown total length 102 ft. with 96 ft. of 72 ohm balanced twinline. Hi-impact molded resonant traps. (Wt. 3 oz. 1" x 5" long). You just tune to desired band for beamlike results. Excellent for ALL world-wide short-wave receivers and amateur transmitters. For NOVICE AND ALL CLASS AMATEURS! NO EXTRA TUNERS OR GADGETS NEEDED! Eliminates 5 separate antennas with excellent performance guaranteed. Inconspicuous for Fussy Neighbors! NO HAY-WIRE HOUSE APPEARANCE! EASY INSTALLATION! Complete Instructions.
 75-40-20-15-10 meter bands. Complete \$17.95
 40-20-15-10 meter. 54-ft. (best for swl's) Complete .. \$16.95
SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival or send full price for postpaid delivery. Complete installation & technical instructions furnished. Free information on many other 160-6 meter antennas. Available only from:

MIDWAY ANTENNA • Dept. A7-8 • Kearney, Nebraska

Interested in VHF?

Then why not send for a free sample of the VHF'er Magazine. It's devoted entirely to serious VHF and UHF hamming. It contains articles by well-known and capable VHF'ers. All who want to improve their knowledge of VHF are invited to subscribe.

Subscriptions are \$2 a year (foreign \$3)

The VHF'er

Parks Laboratories, 419 SW First, Beaverton, Oregon

DOUBLE BONUS

\$25

WORTH OF
 TRANSISTORS
 RECTIFIERS
 RESISTORS
 CONDENSERS
 DIODES & ETC

PLUS
 CHOOSE
 ANY
\$100
 ITEM
 FREE


Add 25¢ for handling
BOTH FREE WITH ANY \$10 ORDER

Sale

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 3 INFRA-RED DETECTORS, with leads\$1
- \$25 SURPRISE PAK: transistors, rect, diodes, etc.\$1
- 40 PRECISION RESISTORS, 1/2, 1, 2W; 1% values \$1
- 30 CORNING "LOW NOISE" resistors, 5% too! \$1
- 60 TUBULAR CONDENSERS, to .5mf, to 1Kv, asst \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1KV \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W, to 24 Kohms. \$1
- 50 MICA CONDENSERS, to .1mf, silvers tool ..\$1
- 10 VOLUME CONTROLS, to 1 meg, switch tool ..\$1
- 10° ELECTROLYTICS, to 500mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd. colors & styles ..\$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 500mf \$1
- 50 COILS & CHOKES, if, rf, ant, osc, & more ..\$1
- 35 TWO WATTERS, asst incl: A.B., 5% tool ...\$1
- 75 HALF WATTERS, asst incl: A.B., 5% tool ...\$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W, 1% & 5% values \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps ..\$1

ZENER VOLTAGE REGULATORS 1 WATT

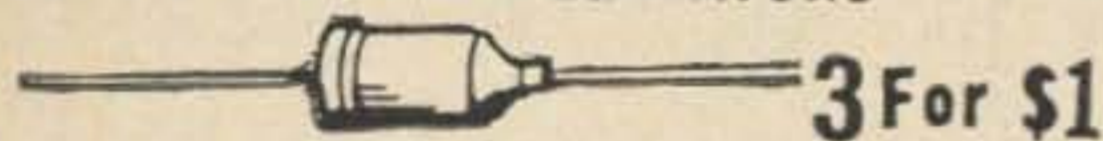

3 For \$1

Volts Volts Volts Volts Volts Volts Volts

<input type="checkbox"/> 10	<input type="checkbox"/> 15	<input type="checkbox"/> 22	<input type="checkbox"/> 33	<input type="checkbox"/> 47	<input type="checkbox"/> 68	<input type="checkbox"/> 100	<input type="checkbox"/> 150
<input type="checkbox"/> 11	<input type="checkbox"/> 16	<input type="checkbox"/> 24	<input type="checkbox"/> 36	<input type="checkbox"/> 51	<input type="checkbox"/> 75	<input type="checkbox"/> 110	<input type="checkbox"/> 160
<input type="checkbox"/> 12	<input type="checkbox"/> 18	<input type="checkbox"/> 27	<input type="checkbox"/> 39	<input type="checkbox"/> 56	<input type="checkbox"/> 82	<input type="checkbox"/> 120	<input type="checkbox"/> 180
<input type="checkbox"/> 13	<input type="checkbox"/> 20	<input type="checkbox"/> 30	<input type="checkbox"/> 43	<input type="checkbox"/> 62	<input type="checkbox"/> 91	<input type="checkbox"/> 130	<input type="checkbox"/> 200

- 10 TUBULAR ELECTROLYTICS, to 500 mf ..\$1
- INFRA-RED PHOTO DETECTOR TRANSDUCER ..\$1
- INFRA-RED PARABOLIC REFLECTOR & FILTER ..\$1
- 40 WORLD'S SMALLEST COND., to .05mf ...\$1
- 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1
- 2 CLAIREX PHOTO ELECTRIC CELL, CL607\$1
- 60 CERAMIC CONDENSERS, discs, npo's, to .05 \$1
- 40 "TINY" RESISTORS, 1/10W, 5% tool!\$1
- 10 TRANSISTOR SOCKETS for pnp-npn transistors \$1
- 30 MOLDED COND'S, mylar, porc, black beauty \$1

750 MIL TOP HAT AND EPOXIES

PIV	Sale	PIV	Sale	PIV	Sale
50	<input type="checkbox"/> 5¢	600	<input type="checkbox"/> 19¢	1400	<input type="checkbox"/> 95¢
100	<input type="checkbox"/> 7¢	800	<input type="checkbox"/> 29¢	1600	<input type="checkbox"/> 1.10
200	<input type="checkbox"/> 9¢	1000	<input type="checkbox"/> 51¢	1800	<input type="checkbox"/> 1.35
400	<input type="checkbox"/> 13¢	1200	<input type="checkbox"/> 69¢	2000	<input type="checkbox"/> 1.50

PLANAR SCRS Silicon Controlled Rect.

	<input type="checkbox"/> 7-Amps		<input type="checkbox"/> 7-Amps	
	PRV	Sale	PRV	Sale
<input type="checkbox"/> 50	1.00	<input type="checkbox"/> 600	3.25	
<input type="checkbox"/> 100	1.50	<input type="checkbox"/> 800	3.89	
<input type="checkbox"/> 200	1.95	<input type="checkbox"/> 1000	4.50	
<input type="checkbox"/> 400	2.50	<input type="checkbox"/> 1200	4.95	

10¢ FOR OUR "FALL" BARGAIN CATALOG ON:
 Semiconductors Poly Paks Parts

POLY PAKS

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25%

P.O. BOX 942A
 SO. LYNNFIELD, MASS.
 "PAK-KING" OF THE WORLD

FACTORY TESTED SEMI-KON-DUCTORS

- 2 Bidirectional Transistors 2N1641\$1
- 4 2N170 TRANSISTORS, by GE., npn for gen'l rf \$1
- 1 IGNITION SWITCHING TRANSISTORS, 10-AMP \$1
- 4 2N336 NPN SILICON transistors, Transistron \$1
- 10 ZENERS REFERENCES stud, asst types\$1

1. AMP 800 PRV

SUBMINIATURE **4 for \$1**

RECTIFIERS

- 25 GERMANIUM & SILICON DIODES, no test ..\$1.
- 25 TOP HAT RECTIFIERS, silicon, 750ma, no test \$1
- 10 1000 MC-1N251 GERMANIUM DIODES ...\$1
- 10 30-MC TRANSISTORS, silicon, TO18, no test \$1
- 3 -2N705 MESA, 300 mc, 300 mw, pnp, TO18 ..\$1
- 2-800 MC, 2N709 NPN Silicon planar TO46 ..\$1
- 10 PNP SWITCHING TRANSISTORS, 2N 404, TO5 \$1
- 10 NPN SWITCHING TRANSISTORS, 2N338, 440 \$1
- 15 PNP TRANSISTORS, CK722, 2N35, 107 no test \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test \$1
- 30 TRANSISTORS, rf, lf, audio osc-ifs, TO5 no test \$1

SILICON POWER STUD RECTIFIERS

AMPS	25 PIV	50 PIV	100 PIV	200 PIV
3	<input type="checkbox"/> 5¢	<input type="checkbox"/> 7¢	<input type="checkbox"/> 12¢	<input type="checkbox"/> 19¢
15	<input type="checkbox"/> 15¢	<input type="checkbox"/> 22¢	<input type="checkbox"/> 40¢	<input type="checkbox"/> 65¢
35	<input type="checkbox"/> 39¢	<input type="checkbox"/> 50¢	<input type="checkbox"/> 75¢	<input type="checkbox"/> 1.19
AMPS	400 PIV	600 PIV	800 PIV	1000 PIV
3	<input type="checkbox"/> 25¢	<input type="checkbox"/> 35¢	<input type="checkbox"/> 45¢	<input type="checkbox"/> 69¢
15	<input type="checkbox"/> 90¢	<input type="checkbox"/> 1.35	<input type="checkbox"/> 1.59	<input type="checkbox"/> 1.79
35	<input type="checkbox"/> 1.90	<input type="checkbox"/> 2.50	<input type="checkbox"/> 2.75	<input type="checkbox"/> 2.95

- 10 FAMOUS CK722 TRANSISTORS, pnp no test \$1
- 5 2N107 TRANS'TRS, by GE, pnp, pop, audio pak \$1
- 2 40W NPN SILICON MESA 2N1648 2N1048 \$1
- 25 ZENERS GLASS SILICON DIODES, no test ..\$1
- 5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive \$1
- 2 2N718 NPN SILICON PLANARS, by Fairchild ..\$1
- 4 2N213 TRANSISTORS, mixer-conv, TO22 ...\$1
- 10 MICRODIODE STABISTORS, epoxy, silicon ..\$1
- 3 2N706 500MW, 300MC NPN PLANAR, TO-18 ..\$1
- 10 PHILCO MAT HI-FREQ. TR'SISTORS, untested. \$1
- 4 2N255 POWER TRANSISTOR EQUALS, TO3 case \$1
- 2-500MC, 2N708 NPN Silicon planar TO46 ..\$1
- 3 2N711 300MW. 300 MC, PNP MESA, TO18 ..\$1
- 15 1AMP 200V epoxy rectifiers, made by Sylvania \$1
- 25 "EPOXY" SILICON DIODES, untested ...\$1
- 4 ZENER REFERENCES, 1N429, 6-volt, silicon ..\$1
- 2 "TINY" 2N1613 2W. 100MC, TO46 case, npn \$1
- 2 500MC TRANS'TRS, 2N964, mesas, pnp, TO18 \$1
- 1 85W SILICON PWR TRANSTR, npn, like 2N1212 \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4 2N333 NPN SILICON transistors, by GE, TO5 \$1

FIELD-EFFECT TRANSISTORS

For experimental & shop use. N-channel P-channel

2\$1 For 1 TO-5

- 10 2-6Amp RECT's, studs, silicon, 50 to 400V ..\$1
- 3 -25-AMP SILICON STUD RECTIFIERS\$1
- 3 2-WATT PLANAR TRANS'TRS, 2N697, 100mc \$1
- 4 2N35 TRANSISTORS, npn, by Sylvania, TO22 ..\$1

LEARN RADIO CODE



\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in LESS THAN HALF THE TIME!

Also available on magnetic tape. See your dealer now!

EPSILON RECORDS

206 East Front Street, Florence, Colorado

MARIN AMATEUR RADIO SUPPLY

COMPLETE STOCK ALL BRANDS
BUY & SELL USED

70 Woodland Avenue
San Rafael, California 94901

PRICE BREAKTHROUGH ON BEAMS

FULL SIZE; new; complete with boom and hardware; SWR 1:1; handles 5 KW; adjustable entire band; 3/8" and 1" alum. alloy tubing; coaxial feed:

3 EI 20	\$22.00	3 EI 15	\$16.00
2 EI 20	16.00	2 EI 15	12.00
4 EI 10	18.00	4 EI 6	15.00

ALL BAND VERTICAL: V160 (6 thru 160)

QUADS: NEW! NEW! ALL METAL (except insulators) Cubical Quads: 2 EI; full size; complete with boom, all hardware; terrific gain and directivity; best quad ever made; no bamboo; 20 meter \$25; 15 meter \$24; remit with order; shipped exp. coll. GOTHAM, 1805 Purdy Ave., Dept. 73, Miami Beach, Fla. 33139

LARGEST SELECTION in United States
AT LOWEST PRICES—48 hr. delivery



Thousands of frequencies in stock. Types include HC6/U, HC18/U, FT-241, FT-243, FT-171, etc.

SEND 10¢ for catalog with oscillator 2400B Crystal Dr., Ft. Myers, Fla. 33901 circuits. Refunded on first order.

LOOK...NO HOLES!

FITS ANY C.B. OR HAM ANTENNA

THIS RIGID RUSTPROOF ANODIZED ALUMINUM ANTENNA MOUNT FASTENS TO YOUR CAR TRUNK LID IN MINUTES... AND NO BODY HOLES ARE NECESSARY!

SEE THESE SUPERIOR MOUNTS AT YOUR DISTRIBUTOR/DEALER OR REMIT \$8.95 (check or M.O.) TO E-Z MOBILE ANTENNA MOUNT INC., P.O. BOX 277, ALGONAC, MICHIGAN (Michigan residents add 4% sales tax) PHONE 313 794-7343

SPECIFY ANTENNA MOUNT HOLE DESIRED (3/8" - 3/4" - SMALL OR MEDIUM BALL)



DEALER INQUIRIES INVITED

E-Z MOBILE ANTENNA MOUNT

PATENT PENDING

Caveat Emptor?

- ★ Price—\$2 per 25 words for non-commercial ads; \$5 per 25 words for business ventures. No display ads or agency discount. Include your check with order.
- ★ Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.
- ★ We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.
- ★ For \$1 extra we can maintain a reply box for you.
- ★ We cannot check into each advertiser, so Caveat Emptor . . .

ALL MAKES of new and used amateur equipment. Write or call Bob Grimes, 89 Aspen Road, Swampscott, Mass. Tel: 617-598-9700 or 617-598-2530.

CONVERTERS. World's largest selection of frequencies. Ham TV vidicon cameras and parts at low factory-direct prices. See them all now in our full page ad in this issue. Vanguard Labs, 196-23 Jamaica Ave., Hollis, N.Y. 11423.

WE WILL PAY CASH: Wanted, popular, late model unmodified amateur equipment. Highest prices paid for clean, good operating gear. Write Graham Radio, Dept. 10, Reading, Massachusetts.

ARE YOU SINCERE? Are you really looking for the best deal on a new or fully guaranteed used unit? Let us convince you with a specific quote that will really save you money. Graham Radio, Dept. 10, Reading, Massachusetts.

BUILD W1JL's popular CPO-CWM (code practice oscillator-CW monitor) from the July 1965 73, page 32. The predrilled board with component locations silk-screened on it is only 50¢. The board with all parts mounted on the board is \$3 and the unit assembled in an attractive case is a remarkable \$7.95. Order today from the Harris Co., 56 E. Main St., Torrington, Conn.

25 WORDS FOR \$2. Sell or buy through these want ads, a terrific bargain. Caveat Emptor, 73 Magazine, Peterborough, N. H. 03458.

COMMUNICATIONS RECEIVERS—an excellent booklet from the RSGB. Limited number available for only 50¢ 73 Magazine, Peterborough, N. H. 03458. each.

NOVICE AND TECHNICIAN HANDBOOK by W6SAI and W6TNS. Limited quantity for only \$2.50 each. 73 Magazine, Peterborough, N. H. 03458.

LOUISVILLE, KENVENTION—October 15. Kentucky Fair and Exposition Center. All under roof. Grand banquet, technical forums, Grand indoor trade-o-rama (bring your goodies), booth exhibits. CW contest, homebrew contest. New, different. Registration \$2 at door. First class women's program and luncheon requires advance registration \$3. Deadline October 8. Post office box 20094. Louisville, Kentucky 40220.

HALLICRAFTER HT-30 SSB transmitter 80-10 meters. Excellent condition. \$150 or trade for VHF equipment.

QSL CARDS: Free samples, reasonable prices, fast service. Write S and S Press, Box 282, Valparaiso, Florida 32580.

SIGNAL LACK PUNCH? Slice through the pile-ups! 4-1000A's guaranteed to full specifications. Postpaid, insured \$39.95/each 2/\$75. Money back if not satisfied. K6CAA, 3409 Via Dona, Lompoc, California 93436.

THREE INCH speakers with transformers, 75¢. Bicycle antennas, 50¢. Plug-in electrolytics, 40-40-40 @ 350 volts, \$1. Get on mailing list. Mikes repaired. J & J Electronics, Box 146, Canterbury, Conn.

KW PARTS: Jennings UCS-300 vacuum variable \$40.00; B&W Model 852 Inductor (slight mechanical modification) \$40.00 postpaid. Make me an offer: National RDZ Receiver; I-193 RTTY Test Set; Lambda Model 440 Power Supply. Edgerton, K1ZCC, 32 Hereford St., Boston, Mass. 02115.

VHF-UHF Kilowatt Station: 50, 144, and 432 megacycle kilowatt, some 220 and 1296 megacycle gear, converters, receivers, antennas, test equipment. Huge junkbox. Sell all or part, see it or hear it anytime. Send S.A.S.E. for list to W1KSZ, Richard Solomon, 25 Regina Road, Dorchester, Massachusetts, 02124.

GET OUT with perfect HT-37, SX-101A: \$240 apiece. In so much better condition than average gear, I'll guarantee them for 30 days. Sam Butler, WA5AXS; 618-18th Ave. N.; Texas City, Texas.

HEATH HO-13 Spectrum Monitor wired by engineer for 455 kc, parts included for other IF frequencies, \$65.00. WØICR, Rte 1, Box 357, Parker, Colo. 80134.

WANTED: Military, Commercial, SURPLUS . . . Airborne, Ground, Transmitters, Receivers, Testsets, Accessories. Especially Collins. We pay freight and Cash. RITCO Box 156, Annandale, Virginia (703) 560-5480 COLLECT.

BOEHME MORSE tape reader and motor drive. McElroy perforator. 25 rolls of tape. \$45. LOCAL SALE ONLY. John Riley. Telephone 845-3880. Burbank, Calif.

TELETYPE WANTED—M28 typing units, parts, ASR cabinet, keyboard. Sell 28, 15, 14 machines, gears, motors, parts. W4NYF, 405 NW 30 Ter., Ft. Lauderdale, Fla. 33311.

SELL—SRT-14 subchasses, precision potentiometer set, audio frequency meter; magazines: Electronics, Control Engineering, IRE Proceedings, etc. W4NYF, 405 NW 30 Ter., Ft. Lauderdale, Fla. 33311.

EICO 753; Like new \$150.00, AC power supply \$70.00, with manual and original cartons, W5BGW Box 62, Yellville, Ark. 72687.

SB-300: CW, SSB, AM filters; 75 S-1; noise blanker; \$250.00 each f.o.b., Ed Jurow, 20314 Harding, Olympia Fields, Ill.

GALAXY V, Remote VFO, VOX, AC Supply, and Speaker-Cabinet \$495. Gonset GSB-201 \$190. All offers considered. John T. Null, 407 38th Street, Vienna, West Virginia 26101, 304-295-5616.

SP-600-JX-1 receiver with manual \$275.00, Valiant F/W \$200.00, HQ-145C with speaker \$160.00. Want KW power supply. K1NLW, Glenn Edson, 16 Monticello Dr. Paxton, Mass. 01612.

BUILD A CODETYPER. Transistorized electronic computer-typewriter for Morse teaching or keying your rig with fb fist. For schematic, parts list and technical dope send \$2 to Computronics Engineering Box 6606 Metropolitan Station Los Angeles 90056.

MOHAWK RECEIVER and matching speaker for sale. Moved into housing project and cannot use. Excellent condition. \$150. Brooklyn, N.Y. Call 996-7837 after 7 or weekends.

SEPTEMBER 1966

BROADBAND FERRITE BALUN

- 2-30 MC
- 2 KW P.E.P.
- Completely Weatherproof
- 1:1 or 4:1 Ratio (specify)
- Mounting for Beam or Dipole



Nearly perfect characteristics are obtained by the use of low loss ferrite materials and special winding techniques. The transformer is completely encapsulated in plastic to assure freedom from moisture or shock damage. Model 601 is designed for a 1:1 ratio (50 ohms unbalanced to 50 ohms balanced) and the Model 601A is available for applications requiring a 4:1 ratio (50-200 ohms or 75-300 ohms). Each unit is supplied with a UG58A/U (type N) fitting to provide superior weather resistance.

\$19.95 Plus Postage with mating UG21B/U add \$1.00.
Write for data sheet or see your local dealer

TRANSLAB INC.

4754 Federal Blvd. San Diego, Calif. 92102


"HOW TO MAKE MONEY IN Mobile Radio Maintenance"

AUTHORITATIVE GUIDEBOOK
ABOUT THE BOOM IN TWO-WAY MOBILE RADIO.
GIVES FACTS, FIGURES, PAY RATES.
WRITE TODAY!

FREE



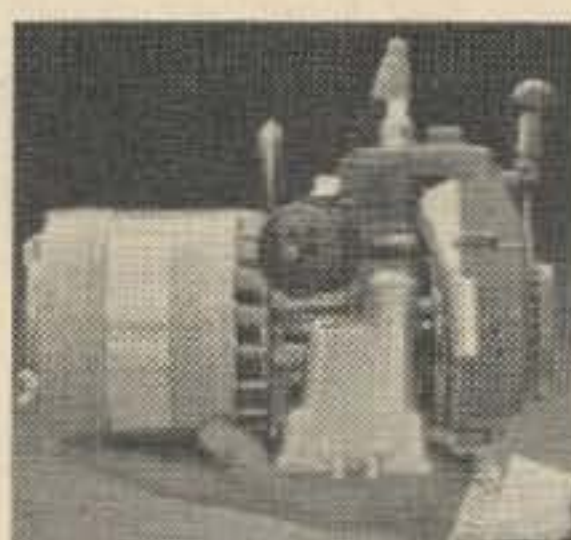LAMPKIN LABORATORIES, INC. Dept. 26 BRADENTON, FLA.



115V-350 WATTS AC 12½ lb. GAS ALTERNATOR

Enough power to operate any popular SSB xmitter plus separate DC output to charge 6 and 12 volt batteries. Great for vacations, field days, campers, boats, etc. May be used

for soldering irons, power tools, tv sets and many other uses. Thousands have been sold to US and foreign govts., armed services, police depts. etc. Fully guaranteed.

Only \$79.50 from: Algert Sales Co.
1805 Wilshire Blvd., L.A.

PLATE TRANSFORMERS—\$39.95

3600-0-3600 VAC @ 1000 Ma., CCS, with 120/240 VAC 60 cps primary. Commercial quality units manufactured by Wagner Electric Co. measure 13" high, 12" wide, and 9" deep. Net weight is 85#. Price \$39.95 F.O.B. Minneapolis. One year unconditional money back guarantee. Terms: Check or M.O. with order. Immediate delivery. Write or Phone:

PETER W. DAHL CO.

3314 Diamond Drive

El Paso, Texas

BIG CATALOG

World's "BEST BUYS"
in GOV'T. SURPLUS
Electronic Equipment

FULL OF TOP QUALITY ITEMS — Transmitters, Receivers, Power Supplies, Inverters, Microphones, Filters, Meters, Cable, Keyers, Phones, Antennas, Chokes, Dynamotors, Blowers, Switches, Test Equipment, Headsets, Amplifiers, Indicators, Handsets, Converters, Control Boxes, etc., etc. SEND 25¢ (stamps or coin) for CATALOG and receive 50¢ CREDIT on your order. Address Dept. 73

FAIR RADIO SALES
P.O. Box 1105 • LIMA, OHIO • 45802

GIANT MULTI METER

Features new diode overload protection, shorting switch position, 1% precision resistors used
 DC Volts: 0-0.5/2.5/10/50/250/500/1,000/5,000
 AC Volts: 0-2.5/10/50/250/500/1,000 (10K opv)
 DC Current: 0-5 μ a/1ma/50ma/250ma/1A/10A
 AC Current: 0-1A/10A
 Ohms: 0-10K/100K/1M/100M



SHIPPED PREPAID WHEN CHECK ACCOMPANIES ORDER
ALCO ELECTRONIC PRODUCTS, INC.
 LAWRENCE, MASSACHUSETTS **44.95** 30K opv

RADIO TELETYPE EQUIPMENT
 TELETYPE MODELS 28 ASR, 28 KSR, 28 LPR, 28 LARP, 28 LXD, 28 LBXD1, 14, 15, 19, Page printers, Perforators, Reperforators, Transmitter-distributors, Polar Relays, Collins Receivers 51J-3, R-388, 51J-4, R-390A. Hammarlund SP-600JX. Frequency Shift Converters.

ALLTRONICS-HOWARD CO.
 Box 19, Boston, Mass 02101 Tel: 617-742-0048



WE DON'T HAVE \$1,000,000!
 But we have enough cash to pay you the mostest for all your late model equipment! We want to buy ground and air communication equip., teletype, GRC, PRC, ARC, ARN, & test equipment. WE PAY FREIGHT! Tell us what you have . . . what you want . . . and we'll give you the best deal in the country—TODAY!

COLUMBIA ELECTRONICS—Dept. S.
 4365 W. Pico Blvd. Los Angeles, Calif. 90019

TUNAVERTER

NEW MODELS! NEW PRICES!

— TUNABILITY — USABILITY — QUALITY —



Amateur
160 M
to
2 Meters

Marine
Police
Short-
wave

TUNABLE, CALIBRATED solid state converters to change your auto and home radios into excellent, sensitive, selective, calibrated Amateur and VHF receivers!

- 6-1 reduction tuning!
- HF—2 gang tuning!
- VHF—3 gang tuning!
- FREE 24" conn. coax!
- 2 WEEK MONEY BACK OFFER!
- Plug into auto radio!
- BC & ham. ant. inputs!
- 100% American Made!
- 9 volt btry powered!
- Mute terminals!
- Size 2 1/4" x 3 1/2" x 4 1/2"

● SHIPPED FROM STOCK!!!

BAND	MODEL	COVERS	OUTPUT	PRICE
Marine	Marine	2.0-3.0 mc	550 kc	\$19.95 ppd
Shortwave & WWV time.	} SWL	9.3-10 mc	800 kc	\$19.95 ppd
		14-18 mc	1500 kc	\$19.95 ppd
160 meters	160	1.8-2.0 mc	550 kc	\$19.95 ppd
75 meters	75	3.8-4.0 mc	800 kc	\$19.95 ppd
CB & 10 M	273	26.9-30 mc	1500 kc	\$29.95 ppd
6 meters	504	49.5-54.5 mc	1500 kc	\$29.95 ppd
2 meters	1450	144-150 mc	1500 kc	\$29.95 ppd
Police, fire, & Marine.	} 308	30-38 mc	1500 kc	\$29.95 ppd
		37-50 mc	1500 kc	\$29.95 ppd
		150-164 mc	1500 kc	\$29.95 ppd
Aircraft	1828	118-128 mc	1500 kc	\$29.95 ppd

Models with Tunable BFO for SSB-CW-AM-FM!

160 M	1600	1.8-2.0 mc	550 kc	\$24.95 ppd
80 M	800	3.4-4.1 mc	550 kc	\$24.95 ppd
75 M	750	3.8-4.0 mc	550 kc	\$24.95 ppd
40 M	400	6.97-7.325 mc	830 kc	\$24.95 ppd
20 M	200	14.0-14.35 mc	830 kc	\$24.95 ppd
15 M	150	20.975-22 mc	1500 kc	\$24.95 ppd

Output kits for use with home radios, (state output) \$1.25. Watch For New Models!! Special VHF Model outputs available!

HERBERT SALCH & CO. Dept. 7, Woodsboro, Texas 7839

TECH MANUALS: Special \$3.00 each—ARC-27, CV-116/URR, ARN-30, TS-186D, BC-1031. Many others, list 10¢. S. Consalvo, W3IHD, 4905 Roanne Drive, Washington, D.C. 20021.

EICO 723 \$35, Mosely TA-33 Jr. tribander \$45. Both nearly new. Or swap for 2 meter transmitter, converter. Pete Hunt, 41 Woodcock, Levittown, N. Y. 11756.

YOUR CALL LETTERS on a 7x2 1/2 steel plate, white on red, weatherproof. For car and shack. Limit 5 characters. \$2.00ppd. 2 for \$3.75ppd. METHODS 1011A Busl St. San Francisco, CA 94109.

WRL'S BLUEBOOK SAVES YOU MONEY! These prices without trades: KWM2—\$675.00; NCX3—\$197.10; GALAXY 300—\$161.10; NCL2000—\$399.60; HT37—\$233.10; HX20—\$152.10; GLOBE KING—\$179.10 up; 75S1—\$278.10; SX117—\$206.10; PMR8—\$67.50; HQ170C—\$197.10; 2A—\$161.10. Hundreds more, free list. WRL, Box 919, Council Bluffs, Iowa 51501.

LPL LULU 6 METER TRANSMITTER. Purchased Spring of '65, like new, never mobile. Complete details on request. WAØILV, Frank Miller, Clarkson, Nebraska 68629.

COMPLETE STATION: Knight T-60, R-55A receiver, Eico 722 VFO. All excellent, \$100 or \$35 each. Charles Jimenez WA4ZQO, 17001 Northwest 53rd Court, Opa-locka, Florida 33054.

HW-22 with HP-23 power supply. Sell or trade for comparable value receiver. W. Ellinwood WIMPY 758 Pleasant St. Athol, Mass. 01331.

FM FOR 2, 6 AND 432. Motorola 150MC base stations (140BY) \$140. Motorola 432MC transceivers T44A6A 6/12V. These are clean and complete, with every tube, crystal, cable, control head, mike, speaker and case. Guaranteed operating. Complete manual with every unit. Rated 18-20 watts output. Require no modification to get on 432MC. \$75 each. Go where the action is: get on 432.9 wideband FM. Over 25 stations in Detroit area on this frequency. 432.9MC xtals available for most FM equipment (inquire). Just arrived: lots of clean 150MC 12V transceivers, with manuals. Send for latest list (S.A.S.E. appreciated). Newsome Electronics (Ray, K8TJP), 2670 Pinetree, Trenton, Mich. 48183.

HAVE COLLINS 75S3, 32S3, 62S1 and 516F2, Johnson 6N2 Thunderbolt. WANT 16 mm movie outfit. K71MH James F. Bingham, P.O. Box 516, Beaverton, Oregon. 97005.

EICO 753 TRANSCEIVER with transistor V.F.O. \$180.00. EICO mobile transistor power supply \$70.00. Both excellent. Don Norman K8LLZ, 204 Emerson Court, Elyria, Ohio.

TWO BEDROOM FRAME HOUSE on large 52' by 170' lot. Land values are still climbing. Has good potential. Will sell completely furnished (ham gear not included but will consider leaving 60' tower, rotor and beam behind) panoramic view of downtown. Good residential neighborhood. Stores, schools, etc. close. Asking \$26,900. Call or write Iverson, WA6ZCQ 1312 Micheltorena Street, Los Angeles 90026. Phone No. 3 1581.

SB-33 SB1LA L.P. filter, New condition with manuals—original boxes. Transceiver tunes I 50KC of transmitter freq. \$350. W1DFN 59 Tahattawan Rd. Littleton, Mass.

WANTED: TELETYPE EQUIPMENT R-388, 51J-3 R-390A. Cash, or trade for new amateur equipment. Alltronic-Howard Co., Box 19, Boston, Mass. Tel-617-742-0048.

NCX5 TRANSCEIVER—NCX-A Power Supply, Perfect—used 20 hours \$425.00 WA4GYA, 2207 Harvard, Ft. Myers, Fla. 33901, Phone WE. 6-1726.

WANTED: BC 221—Original-Calibration Book—Accurate—Good condition. No modifications. Full details and price. Tel 899-7570. Howard Ell, 206 Pearce Ave. Point Pleasant, N.J.

LIKE SIDEBAND? SWAP like new HT37 for Heath Apache or Viking Valiant. C. J. Dixon, K9BQW, 18136 Chicago Ave., Lansing, Illinois 60438.

300 WATTS SSB TRIBAND transceiver galaxy 300 with power supply—excellent condition, \$250—Tony Assenza, 10724 Campana Way—Rancho Cordova, Calif. 95670.

LOW MILEAGE DELUXE DRAKE 2B and HT-37 with coax-relay, microphone. \$450 firm. HO-10 excellent, \$45. B. Binder, 26 Sarah Drive, Spring Valley, N. Y. 10977. 914-352-1482.

DRAKE 2A RECEIVER, speaker \$125. C. E. 20A and VFO \$75. Sorry no shipping. R. Mensing 3160 Waverly, Palo Alto, Calif. 326 5884.

QSL CARDS???? WHOLESALE prices. "America's Finest" Samples 25¢ DeLuxe 35¢. Sakkers Printery, W8DED, Box 218, Holland, Michigan 49423.

TO 18 FIELD EFFECT TRANSISTORS \$1.95, resistors, capacitors, transistors, diodes, and many other bargain packs send for list to: Solid State Pax. P.O. Box 206, Dorchester, Mass. 02014.

ESTATE SALE and bargain list. Send for it and include SSAE. Write Paradd Sales and Engineering Service, 280 Route 10, Dover, N. J. 07801.

TRADE: Preamp CQ May '63 3 nuvistors 10-80M; Wen 2 speed 3/8" drill Wlacc; Hy-Gain 4BD W1100' RG 59 u 6-20 M. OFFER: Stephen Clifton, 800 W. End Ave., N. Y., N. Y. 10025.

RTTY GEAR for sale. List issued monthly. 88 or 44 Mhy toroids five for \$1.75 postpaid. Elliott Buchanan, W 6 VPC, 1067 Mandana Blvd. Oakland, Calif. 94610.

FOR SALE: BC610E; BC 614 Speech Amp; KWS1; 32V1; ART 13; R388 Recv'r. W2ZOL.

EXCESS GEAR AND PARTS, vac, variables, variable coils, tubes, meters, transformers, 2kw linear, diodes (HV), etc. Stamp for complete list. W6MCS, Rt. 1, Box 666, Arroyo Grande, Calif.

FOR SALE: COLLINS STATION \$1100.00. 75S-1 with Waters Q-multiplier, matching speaker \$325.00. 32S-1 with 516F-2 power supply \$450.00. 30L-1 Linear \$425.00. Purchased new. Kept in air conditioned quarters. Absolutely perfect, mint condition. Will bear most scrupulous inspection. New Avionics gear considered. K9DMG, Perry Mowery 21 Waibel Road, Bartonville, Illinois, Phone 697-6597.

FANTASTIC HAM LOCATION atop 1000' hill 180° view of Pacific Ocean Antenna OK Two story 3 bdrm 2 1/2 bth. 2 dens 2 yrs old. shop area B. Ward WB6DLQ 3149 Altalaguna Blvd. Laguna Beach, Calif. Tel (714) 494 6110

SBE-33 with mike and DC supply \$250.00; SB1LA matching Linear \$150.000; DX60A \$65.00; HG-10 VFO \$30.00; W0NAE, James R. Boyer, R.R. #3, Watertown, South Dakota, 57201.

WANTED: MODEL 28 TELETYPE, R-388, R-390A, cash or trade for new amateur equipment. New NCL-2000, \$500. Alltronics-Howard Co., Box 19, Boston, Mass. 02101. 617-742-0048.

STARTING HAMMARLUND HX-50; HX-50A; Problem Information Group. What problems-troubles have you had??? Data will be tabulated and available no charge. WA3CJC- 218 Cook Avenue, Ridgway, Pennsylvania, 15853

1296 MC MOONBOUNCE EQUIPMENT, crystal control, receiver, transmitter, paramp, 16 foot fiberglass dish, SCR-584 autotrack, pedestal; offer over \$1,400 takes, F.O.B. Chiloquin, Oregon, Steve Mieth, K7VXC, Box 324.

EXCEPTIONALLY GOOD EQUIPMENT. Hallicrafters SX-101A-\$250, Johnson Valiant—\$250, Hy-Gain TH4 & Ham-M with cables—\$110, RCA 155 C oscilloscope \$25. Will negotiate on the lot. Substantial associated equipment. Bob Yarmus, K2RGZ, 532 Lefferts Ave., Bklyn, N. Y. 884-6336 or SL6-7044 after 6 P.M.

ARROW SPECIALS FOR SEPTEMBER

H46 Headset/Boom-mike	New	14.95
T17-D Carbon Mike	New	7.95
RS38A Carbon Mike	New	9.95
HS33 Headset 600 Ohm	New	6.95
HS23 Headset 4000 Ohm	New	6.95
H58/U Headset 8000 Ohm	New	3.95
HS30 Headset 600 Ohm	New	2.50
RM52 Phone Patch	New	2.95
TR29 Multimatch Trans.	New	.98

ARROW SALES-CHICAGO, INC.

2534 S. MICHIGAN AVENUE
CHICAGO, ILLINOIS 60616

EVANSVILLE AMATEUR RADIO SUPPLY

September Demo		Specials	
Drake TR-4	\$510	Mark I Lin	\$405
Drake R4-A	340	Mosley TA33	93
Drake T4-X	340	Hy-Gain TH3MK2	85
Swan 350	360	Ham M Rotor	85
SBE 34	325	TR 44	54
Galaxy V	360	Eico 753 F/W	255

Contact Bill Ogg or Dave Clark at
Evansville Amateur Radio Supply
1306 E. Division St. Evansville, Indiana 422-4551

CQ de W2KUW 5% BONUS!!

Paid over any top offer for any piece of aircraft or ground radio units, also test equipments. All types of tubes. Particularly looking for 4-250 • 4-400 • 833A • 304TL • 4-1000A • 4CX5000A et al. 17L • 51X • 390A • ARM • GRM • GRC • UPM • URM • USM units.
TED DAMES CO. • 310 Hickory St., Arlington, N.J.

COLLINS MECHANICAL FILTERS—F-455D-31, 455KC center freq. 6 db bandwidth 3.1KC, 60db bandwidth 6.5 KC. **19.50**

VARIABLE CAPACITORS—R/C's all @ 365 mmf
2 section—180° rotation, 3/8" shaft W/2 1/2" pulley wheel. Dim. 2 1/8" x 1 1/2" x 1 1/2".
2 section—180° rotation, Vernier drive shaft. Dim. 2 1/8 x 1 3/4 x 1 1/2.
3 section—180° rotation, 3/8 shaft. Dim. 3 1/4 x 1 1/2 x 1 1/2".
3 section—180° rotation, 3/8" shaft x 2 1/4" long with 2" diam. pulley wheel. Dim. 4 x 2 3/8" x 1 1/2".
.95 each 2/1.75

P-5883-3 Tank Coil, can be used in Audio Circuits or Side Band.

- Specs: 1. 7500 turns of #39 Double Polyurethane Wire tapped at 2900 turns.
2. Coil when tuned to 750 cycles with .047 plus/minus 1% mfd cap. to have a "Q" of 6 plus/minus 1.
3. Inductance to be 1.6 hy plus/minus 10% in max. pos.
4. Min. inductance to be 600 m hy max.
5. D.C. resistance start to finish 770 ohms plus/minus 10%.
6. D.C. resistance start to tap 232 ohms plus/minus 10%.

P-5883-4 Tank Coil, same applications.

- Specs: 1. 6500 turns of #38 Double Polyurethane wire tapped at 2500 turns.
2. Coil when tuned to 1000 cycles with .033 plus/minus 1% mfd cap. to have a "Q" of 8 plus/minus 1.
3. Inductance to be 1.1 hy plus/minus 10% in max. pos.
4. Min. inductance to be 450 m hy max.
5. D.C. resistance start to finish 520 ohms plus/minus 10%.
6. D.C. resistance start to tap 150 ohms plus/minus 10%.

Wiring diagram included with each order.
.40 each 3/1.00

Orders under 4.00 add .40 for post & pack.

Government Warehouse, Inc.
264 Shrewsbury Ave., Red Bank, New Jersey 07701

GUARANTEED RECONDITIONED



HAM GEAR

Phone: (415)
DI 2-5757

ELECTRONICS

WRITE NOW
FOR MONTHLY
FLYER.

999 HOWARD AVE-BURLINGAME, CAL.

TILT THAT PANEL!

Do it with a CAB-PAC

Complete package includes everything you need to make a tilted front panel on any cabinet or chassis. Four soft plastic feet with brass hole-lining inserts, two rigid front extenders, four 6-32 mounting screws and instructions. At your ham dealers, or air mail post paid. only



89¢

BUDWIG MFG. CO., P.O. Box 978, Ramona, Calif. 92065

VHF-UHF

Converters and Preamps for 50 thru 432 Mc.
Write for literature.

Send for a sample copy of the VHF'er, the only magazine for VHF and UHF hams.
Parks Electronics, 419 S.W. First, Beaverton, Oregon

***TWO-WAY*
COMMUNICATION CRYSTALS**

AMERICAN CRYSTAL CO.
PO BOX 2366 KANSAS CITY, MO.

INDEX TO ADVERTISERS

Alco Electronics, 120
Algert Sales Co., 123
Allied Radio, Inc., 25
Alltronics-Howard, 124
American Crystal Co., 120
Amrad Electric Co., 126
Antenna Mart, 90
ARC Sales, 120
Arrow Sales—Chicago, 125
ATV Research, 81
L. E. Babcock Co., 53
Brown Electronics, 85
Budwig Mfg. Co., 126
Callbook, 76
Columbia Electronics, 124
Conar, 84
CTK's Barb'd Wire Ant., 86
Cush Craft, 80
Peter W. Dahl Co., 123
Ted Dames Co., 120
Devices, 85
Dow-Key Co., Inc., 79
R. L. Drake Co., 17
DRC-KITS, 86
Editors & Engineers, 71
Edwards Electronics, 73
Epsilon Records, 120
Evans Radio, 80
Evansville Amateur Radio Supply, 125
E-Z Mobile Ant. Mt., 122
Fair Radio Sales, 123
Federated Purchaser, 88
Freck Radio, 120
General R. F. Fittings, 90
R. E. Goodheart Co., 120
Herbert W. Gordon, 87, 91
Gotham, 122
Government Warehouse, 125
Grove Electronic Supply, 92

Ham Wholesale QSL, 81
Harris Co., 69
Heath Co., 12-13
Henry Radio, 49
Hotel Sahara, 88
International Crystal Co., 3
JAN Crystals, 120
Lafayette Radio, 77
Lampkin Labs., 123
Liberty Electronics, 118
Marin Amateur Radio Supply, 122
Midway Antenna, 120
Military Electronics Corp., 124
Mission Ham Supplies, 41
Mosley Electronics, Inc., 28, 29
New-Tronics Corp., 64-65
Norman Electronic Sales, 85
Parks Electronics, 126
Poly-Paks, 121
Quement Electronics, 89
Rohn Mfg. Co., 83
Herbert Salch & Co., 124
Selectronics, 119
Siliconix, Inc., 45
Sprague Products, 33
Squires-Sanders, Inc., 84
Swan Engineering, 9
TAB, 127
Telrex Labs., 11, 24
Translab, Inc., 123
Tri-Ex Tower Corp., 67
Unadilla, 90
United Transformer Co., Cover II
Vanguard Labs., 56, 57
VHF'er, 120
Waters Mfg. Inc., 5
Webster Mfg. Co., 37
World Radio Labs., 128, Cover III

Propagation Chart

AUGUST 1966

J. H. Nelson

EASTERN UNITED STATES TO:

	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7*	7	7	7	7	7	14	14	14	14
ARGENTINA	21	14	14	14	7	7	14	14	21	21	21*	21
AUSTRALIA	14*	14*	14	7#	7#	7	7	14	7#	7#	14	14*
CANAL ZONE	21	14	14	7*	7	7	14	14	14	21	21	21
ENGLAND	14	7	7	7	7	14	14	14	14	14	14	14
HAWAII	14	14	14	7#	7	7	7	7#	14	14	14	14
INDIA	14	14	7#	7#	7#	14#	14	14	14	14	14	14
JAPAN	14	14	7#	7#	7	7	7	14	14	7#	14	14
MEXICO	14	14	14	7	7	7	14	14	14	14	14	14
PHILIPPINES	14	14	7#	7#	7#	7#	14	14	14	14#	14#	14
PUERTO RICO	14	14	7	7	7	7	14	14	14	14	14	14
SOUTH AFRICA	14	7	7	7#	7#	14	14	14	14	14	21	14
U. S. S. R.	7	7	7	7	7	14	14	14	14	14	14	14
WEST COAST	14	14	14	7	7	7	7	14	14	14	14	14

CENTRAL UNITED STATES TO:

	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	7	7	7	7	7	14	14	14	14
ARGENTINA	21	14	14	14	7	7	14	14	21	21	21	21*
AUSTRALIA	14*	14*	14	14	14	7	7	14	7#	7#	14	14*
CANAL ZONE	21	14	14	14	7	7	14	14	14	21	21	21
ENGLAND	14	7	7	7	7	7	14	14	14	14	14	14
HAWAII	14	14	14	14	7	7	7	7	14	14	14	14
INDIA	14	14	7#	7#	7#	7#	14#	14	14	14	14	14
JAPAN	14	14	14	7#	7	7	7	14	14	7#	14	14
MEXICO	14	14	7	7	7	7	7	14	14	14	14	14
PHILIPPINES	14	14	14	7#	7#	7#	7#	14	14	14#	14#	14
PUERTO RICO	14	14	14	7*	7	7	14	14	14	14	14	14
SOUTH AFRICA	14	7	7	7#	7#	7#	14	14	14	14	14	14
U. S. S. R.	7	7	7	7	7	7	14	14	14	14	14	14

WESTERN UNITED STATES TO:

	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	14	14	7	7	7	7	14	14	14	14
ARGENTINA	21*	21	14	14	14	7	7	14	14	21	21	21*
AUSTRALIA	21*	21*	21*	14	14	14	14	7	7#	7#	14	21
CANAL ZONE	21	14#	14	14	14	7	7	14	14	14	21	21
ENGLAND	14	7	7	7	7	7	7	14	14	14	14	14
HAWAII	21*	21*	21	14	14	14	7*	7	14	14	14	21
INDIA	14	14	14	14	7#	7#	7#	7#	14	14	14	14
JAPAN	14	14	14	14	14	7	7	7	14	14	14	14
MEXICO	14	14	7	7	7	7	7	14	14	14	14	14
PHILIPPINES	14	14	14	14	14	7#	7#	7#	14	14	14#	14
PUERTO RICO	21	14	14	14	7*	7	7	14	14	14	14	14
SOUTH AFRICA	14	7#	7	7#	7#	7#	7#	14	14	14	14	14
U. S. S. R.	7	7	7	7	7	7	7	7*	14	14	14	14
EAST COAST	14	14	14	7	7	7	7	14	14	14	14	14

Very difficult circuit this hour.

* Next higher frequency may be useful this hour.

Good: 1-3, 6-8, 14-18, 21-27
Fair: 4, 5, 9, 13, 19, 20, 28, 30
Poor: 10-12, 29
VHF DX: 8-10, 14-17, 21, 29, 30

"TAB" * TRANSISTORS * DIODES!!
GTD! FACTORY TESTED —
FULL LEADS.

PNP 100 Watt/15 Amp HI Power
 TO36 Case! 2N441, 442, 277,
 278, DS501 up to 50 Volts/
 VCBO \$1.25 @, 5 for \$5.
 2N278, 443, 174 up to 80V \$3 @,
 2 for \$5, 5 for \$10.

PNP 30 Watt, 2N155, 156, 235, 242, 254,
 255, 256, 257, 301, 392, 40c @, 3 for \$1
 PNP 2N670/300Mw 35c @, 5 for \$1
 PNP 2N671/1 Watt 50c @, 3 for \$1

PNP 25W/TO 2N538, 539, 540, 2 for \$1
 2N1038 6/\$1, 1039 4/\$1, 1040/\$1
 PNP/TO5 SIGNAL 350Mw 25c @, 5/\$1
 NPN/TO5 SIGNAL IF, RF, OSC 25c @,

Silicon PNP/TO5 & TO18 25c @, 5 for \$1
 Power Heat Sink Finned Equal to 180
 Sq" Surface \$1.50 @, 4/\$5, 10/\$10
 TO36, TO3, TO10 Mica Mtg 30c @, 4/\$1
 Diode Power Stud Mica Mtg 30c @, 4/\$1

ZENERS 1 Watt 6 to 200v \$1 @,
 ZENERS 10 Watt 6 to 150v \$1.25 @
 ZENER Kit Asstd up to 10w 3 for \$1
 STABISTORS up to 1 watt 10 for \$1
TRANSISTORS—TOO MANY! U-TEST
 Untested Pwr Diamonds/TO3 10 for \$1
 Untested TO36 up to 100 Watts 3 for \$1
 Untested TO5/SIGNAL/sistors 20 for \$1
 Untested Power Diodes, 35 Amp 4 for \$1
 Untested Pwr Studs, 12 Amp 10 for \$1
 Untested Pwr Studs up to 6 Amp 18/\$1
 Untested 1/4 A Tophats 25/\$1

D.C. Power Supply 115v/60 to 800
 Cys. Output 330 : Tap 165V up to
 150Ma, Cased \$5 @, 2 for \$9

SILICON POWER DIODES STUDS & P.F.**

D. C. Amps	50Piv 35Rms	100Piv 70Rms	200Piv 140Rms	300Piv 210Rms
12	.30	.50	.70	.85
18**	.20	.30	.75	1.10
45	.80	1.25	1.80	2.25
150	2.50	2.90	3.50	4.50
240	3.75	4.75	7.75	10.45

D. C. Amps	400Piv 280Rms	500Piv 350Rms	600Piv 420Rms	750Piv 525Rms
12	1.10	1.30	1.55	1.75
18	1.50	2.00	2.70	3.40
45	3.25	3.50	3.90	4.50
150	5.40	6.50	7.50	12.00

5U4 Silicon Tube \$2 @, 6 for \$10
 5R4 Silicon Tube \$5 @, 2 for \$9

***NEWEST TYPE! LOW LEAKAGE**
***ALL TESTS AC & DC**
& FWD & LOAD!

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35 .07	100/70 .10	200/140 .12	300/210 .15
400/280 .20	500/350 .25	600/420 .30	700/490 .35
800/560 .40	900/630 .50	1000/700 .55	Send 25c for Catalog

1700 Piv/1200 Rms/750 Ma/\$1.20 @,
 10/\$10
 Same 1100 Piv/770 Rms 75c @, 16/\$11
 3 Kv/2100 Rms/200 Ma/\$1.80 @, 6/\$10
 6 Kv/4200 Rms/200 Ma/\$4 @, 3/\$9

Discap .002 @ 6Kv 3/\$1
 Discap .01 @ 1 Kv 6/\$1

SCR-SILICON-CONTROL RECTIFIERS!

PRV	7A	25A	PRV	7A	25A
100	Q	Q	500	2.50	3.75
200	Q	Q	600	3.25	4.25
300	1.80	2.25	700	4.00	5.00
400	2.00	2.90	800	4.75	5.65

UNTESTED "SCR" Up to 25 Amps, 6/\$2
 Glass Diodes IN34, 48, 60, 64, 20 for \$1

Two RCA 2N408 & Two Zeners
 RCA IN2326 on prtd 3/\$1, 8/\$2

TAB

"VOLT-TAB" 1000 Watt Speed Control
 115VAC \$10 @, 2 for \$19

W.E. Polar Relay #255A/\$5 @, 2 for \$9
 W.E. Socket for #255A Relay, \$2.50
 Toroids 88Mhy New Pckg \$1 @, 6/\$5
 6.3VCT @ 15.5A & 6.3VCT @ 2A \$5 @,
 2 for \$8, 20 for \$60
 200 KC Freq Std Xtals \$2 @, 2/\$3, 5/\$5
 Printed Ckt Bd New Blank 9x12" \$1 @
 Klixon 5A Reset Ckt Breaker \$1 @, 10/\$5
 2K to 8K Headsets Good Used \$3 @, 2/\$5
 Finished Xtals Asst Types 20 for \$1

Battery Charger 6&12V Charges up
to 5 Amp "Approved" Heavy Duty
Design with Klixon Circuit Breaker.
Operates 220 or 110 VAC @ 50 or 60
Cys \$10 @, 2 for \$18

WANTED TEST SETS
& EQUIPMENT

Bandswitch Ceramic 500W 2P/6Pos \$3 @
 5Hy-400Ma Choke \$4 @, 2/\$5
 6Hy-500Ma \$5 @, 2/\$6
 250Mfd @ 450 Vv Lectlytic 4/SSB \$3 @
 Cndsr Oil 10Mfd x 600 \$1 @, 4/\$3, 12/\$5
 Cndsr Oil 6Mfd @ 1500V \$4 @, 5 for \$10
 880 Vct @ 735Ma for SSB \$12 @, 2/\$22
 480 Vct @ 40Ma & 6.3 @ 1.5A CSD \$1.50
 10 Vct @ 5A & 7.5Vct @ \$5 @, 2/\$9

SILICON TUBE REPLACEMENTS
 OZ4 UNIVERSAL \$1.75 @, 4/\$5
 5U4 1120 Rms/1600Inv \$2 @, 6/\$8
 5R4 1900 Rms/2800Inv \$6 @, 2/\$10
 866 5Kv/Rms - 10.4Kv \$10 @, 3/\$27

20VAC & TAPS/8, 12, 16, 20V @ 4A, \$2 @,
 32VCT/1A or 2X16V @ 1A, \$5 @, 6/\$24

Line Filter 4.5A @ 115VAC 5 for \$1
 Line Filter 5A @ 125VAC 3 for \$1
 Converter Filter 400 Ma @ 28VDC 8 for \$1
 Converter Filter Input/3A @ 30VDC 6 for \$1
 866A Xfmr 2.5V/10A/10Kv/Insl
 Ballentine #300 AC/Lab Mtr \$45
 Choke 4Hy/0.5A/27Ω \$3 @, 4/\$10
 "VARIACS" L/N 0-135v/7.5A \$15
 "VARIACS" L/N 0-135v/3A \$10
 TWO 866A's & Fil. Xfmr. \$6

RUSH YOUR ORDER TODAY.
QTY'S LIMITED

Mica Condsr .006 @ 2500V 4/\$1
 Snoposcope Tube 2" \$5 @, 2/\$9
 Mini-Fan 6 or 12Vac/60 Cys \$2 @, 3/\$5
 4X150 Ceramic Loktal \$1.25 @, 4/\$2
 Line Filter 200Amp/130VAC \$10 @, 6/\$50
 DC 3 1/2" Meter/RD/800Ma \$4 @, 2/\$7
 DC 2 1/2" Meter/RD/100Ma \$3 @
 DC 2 1/2" Meter/RD/30VDC \$3 @, 2/\$5
 DC 4" Meter/RD/1Ma/\$5 @, 2/\$9

WANTED
LAB METERS! BRIDGES!

Modulation Xfmr 60W/15K to 5.7K \$5
 Socket Ceramic 1625 Tube 4/\$1, 10/\$2
 Socket Ceramic 866 Tube 4/\$1, 10/\$2
 Socket Ceramic 4X150/Loktal 4/\$2
 Wanted 304TL - Top \$\$ Paid !!

WANTED
YOUR - ORDER - TODAY!

2.5M H PiWound 500Ma Choke 3 for \$1
 Knob Spin-Crank BC348 \$1 @, 3 for \$2
 MiniFan 6 or 12 VAC \$1.50 @, 4 for \$5
 Beam Indicator Selsyns 24VAC 2 for \$10
 Precision TL147 Feeler Relay Gage \$1
 Fuse 250Ma/3AG 50 for \$1, 300/\$2

DON'T C-WRITE & SEND ORDER!
 XMTTG Mica Condsr .006 @ 2.5Kv 2/\$1
 Mini-Rectifier FWB 25Ma @ 115VDC
 3 for \$1, 20 for \$5

We Buy, Sell & Trade
!!! SEND 25c FOR CATALOG !!!
 Terms Min. Order \$5
"TAB" FOB New York
 Our 23rd Year.
 111TA Liberty St., N.Y. 6, N.Y. Re 2-6245

Micro-Switch Rated 40Amp AC & DC
 50c @, 5/\$2, 20/\$5
 BandPass Filters 60 or 90 or 150Cys
 3 for \$5

"Bruning" 6" Parallel Rule @ \$1
 Linear SawTooth Pot KS15138/W. E.
 5 or \$1
 2V3G Tube HiV Repl 2X2A 5/\$1
 "SPERRY" Wattmtr Meas. LoPwr RF Self-
 Calib/50MuW to 10MW \$10
 Synchro Differentials C78249/115VAC 60
 Cycles Less Back Plate @, \$5
 Bendix Auto Syn's "AY" Series 2/\$2

PL259A & SO239 CO-AX M&F 3/\$2
 Phone Patch Xfms Asstd 3/\$1
 FT243 Xtals & Holders 2/\$1
 Insld Binding Posts 20/\$1
 Sun-Cells Selenium Asstd 6/\$1
 TO36/100W Untested Transistors 3/\$1

Tube Clamps Asstd 8/\$1
 .01 Mica 600WV Condsr 6/\$1
 .001 to .006 Mica/1200WV Cdsr 4/\$1
 DISCAPS .002 @ 6KV 3/\$1
 DISCAPS .005 @ 1KV 10/\$1
 DISCAPS .0012 @ 6KV 4/\$1
 DISCAPS .01 @ 1KV 6/\$1

Stevens Precision Choppers \$2 @, 3/\$5
 Helipots Multi Ten-Turn @, \$5
 Precision 3-Turn Pot @, \$2
 Precision One-Turn Servo Pot @, \$1
 Helipot Dials \$4 @, 3/\$10
 5 Gang Servo-Pots \$2 @, 5/\$5

Snoposcope Infrared Tube Image Con-
 verter HiSens 2" dia. HiResolution up to
 350 Line/in \$5 @, 3 for \$10

Vibrator Special Asstd 3/\$1
 Crystal Oven & Holder \$2

THERMISTOR-VARISTORS - W. E.
 D167019 Vol. Limit \$3 @, 5/\$10
 D168391 Therm Coup. \$1 @, 10/\$5
 D168392 Therm Coup. \$2 @, 6/\$5
 D170396 HF Pwr Meas. \$2 @, 6/\$5
 1C Bulb Time Del. 2/\$1, 15/\$5
 38C/20259 Bridge \$4 @, 4/\$10

Mold Scope DuoDecal Socket 3/\$1
 Molded Diheptal Socket 3/\$2
 Ceramic Maginal Socket 4/\$1
 Octal Molded 20/\$1
 Octal Ceramic 10/\$1
 304TL or 829 Johnson Socket \$1

X-Formers All 115V-60Cy Primary—
 2500V @ 10Ma & Fil \$2 @, 3/\$5
 1100VCT @ 300Ma, 6V @ 8A, 5V @ 3A &
 125V Bias. abt 1200VDC \$5 @, 4/\$15
 2.5V @ 2A \$1 @, 3 for \$2
 6.3 V @ 1A \$1.50 @, 4 for \$5

I-177 Tube Hickok Type Checker \$39
 G. E. YZ-1 Decade Scaling Counter &
 Dual Channel & Meters \$45
 Pirani Vacuum Gages \$39
 "ESC" Var. Pulse Ten Step Delay Network
 TD. 5USEC/Z100Ω & .05 to .5 \$36

AM TIME PROD 500cys Fork Amp \$33
 "VFC" Vibrator Feeder Controller
 Type 5—(Shake Table) \$100
 Black Light Lamps/UV \$2
 Osram Mercury HBO100W/2
 HiIntensity DC Lamps \$20
 Osram XBO450W/P Lamp \$50
 G. E. #190T3/CL-60V/Q-InfraR Lamp \$10

Tuning Unit BC746 Make
 Bantam 1 Watt less Coils 3/\$2
 Welch Duo-Seal #1402B Lge Cap HiVacuum
 140 Ltrs/M & Mtr \$200
 Consolidated Vac. Corp PMC115A Dif-
 fusion 'ION Pump \$125
 HiVac Valve CVC#VCS21 @, \$75
 Temescal VAC Valve @, \$12

Electronic VAC Deposition JAR less
 Glass Bell 6" ID \$100
 W.E. #293 Spring Relay Tool 2/\$1
 CD307A/6Ft Ext Cord PL55 & JK26 \$1
 Carborundum Fine 6" Stone 2/\$1
 Binding Posts 5Way/30Amp R&B 5/\$1
 Tubes 6AG7 or 6AC7 3/\$1

WANTED TUBES ALL TYPES
We Buy, Sell & Trade As Well!

BREAK

THROUGH

\$450.00
Includes Separate
POWER SUPPLY



**MORE
"TALK POWER"
PER DOLLAR
Than Ever Before!!**

**WRITE US NOW
FOR KING SIZE TRADE-INS ON
YOUR PRESENT GEAR!**

**NOW FOR THE FIRST TIME
2KW+ TABLE TOP LINEAR FOR UNDER \$500.00
GUARANTEED! 2KW+ PEP SSB INPUT and 1200
WATTS PEP OUTPUT, ALL BANDS 80
THROUGH 10 METERS.**

EXCLUSIVE GALAXY LINEAR FEATURES

- * *Revolutionary new circuit.* Sustains Hi-Efficiency 10-80 Meters.
- * *Most compact 2KW Linear ever made.* R.F. unit just 6" x 10¹/₄" x 11¹/₄". Same as Galaxy III and V.
- * *NEW ALS! (Automatic Linearity System)* An improvement over conventional ALC.
- * *MOST TALK-POWER EVER* in this small size.
- * *Operates AB₁* at all times.
- * *Built-in antenna switching relays.*

MORE OUTSTANDING FEATURES

- * *INPUT: 2,000 Watts PEP-SSB, 1,000 Watts-CW, 1,000 Watts-RTTY.*
- * Complete tube replacement cost under \$30.00.
- * Uses ten 6HF5's in new, efficient design.
- * Full Power from any 100-200 watt output exciter.
- * Tubes fan cooled for longer life.
- * SIMPLIFIED, reduced power tune-up.
- * One knob bandswitching, 80 through 10 meters.
- * High efficiency PI-NET, matches 40/90 Ohms impedance.
- * Built-in, adjustable low-pass filter.
- * 3rd order distortion - 30DB.
- * 115/230 VAC power supply.
- * Shipping weight (Linear and Supply) Approx. 55 lbs.

POWER SUPPLY

Heavy duty power supply has 115/230 VAC primary, conservative 2KW CCS rating with grain-oriented silicon steel core, solid state rectifiers. All cables supplied. Power supply can be placed under desk for operating convenience. Protected by attractive cover.



Leo I. Meyerson
WØGFO

**GET
YOUR
FREE
'65 CATALOG**

WRL

**WORLD RADIO
LABORATORIES**

3415 West Broadway
Council Bluffs, Iowa 51504

- Send information on Linear Amplifier.
- Send quote on separate sheet. Dept. 73-9K
- Send new catalog.

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

"The ONLY Transceiver today designed without compromise for the Ultimate in SSB performance!"

You must COMPARE before you Buy - - - why settle for LESS?

- 300 watts — conservatively rated with highest efficiency. Better than 200 watts output on all bands.
- Selectable—Upper or lower side-band.
- Smallest of all the high powered transceivers. (6" x 10¼" x 11¼")
- "Sharpest" of all transceivers—special McCoy 6 crystal filter.
- "Hottest"—receiver of them all— independently tuned RF stage.
- Complete 80 thru 10 meter coverage. 1 megacycle on 10 meters.
- Designed for both mobile and fixed station use.
- "Superior," audio-derived, dual constant AVC — virtually block-proof!
- Features "Shifted Carrier CW."

OPTIONS

D.C. SUPPLY—Efficient transistorized supply, with thermal overload protection. Provides full power for Galaxy V from 12 VDC—\$89.95.

A.C. SUPPLY—Completely solid state. Provides full power for Galaxy V from 115 VAC, 50-60 cycle.—\$78.95.

REMOTE VFO — Provides split frequency operation on receiving/transmitting when used with the Galaxy V—\$69.95.



GALAXY V

5 BAND TRANSCEIVER

The most Powerful—Reliable—Rugged Transceiver ANYWHERE!

Ask the HAM who owns one!

\$399.95

Buy it while you enjoy it for only \$18.00 monthly!

"The House the HAMS Built!"



Leo I. Meyerson
WØGFQ
President



WORLD RADIO LABORATORIES

73-9A

3415 West Broadway Council Bluffs, Iowa Zip 51501

Please ship the following:

- GALAXY V—\$399.95
- Remote VFO—\$69.95
- Enclosed is my Money Order
- Specifications & Package Information
- Quote me on Attached Letter.
- FREE WRL 1966 Catalog
- A.C. SUPPLY—\$79.95
- D.C. SUPPLY—\$89.95
- Check
- Charge it

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

