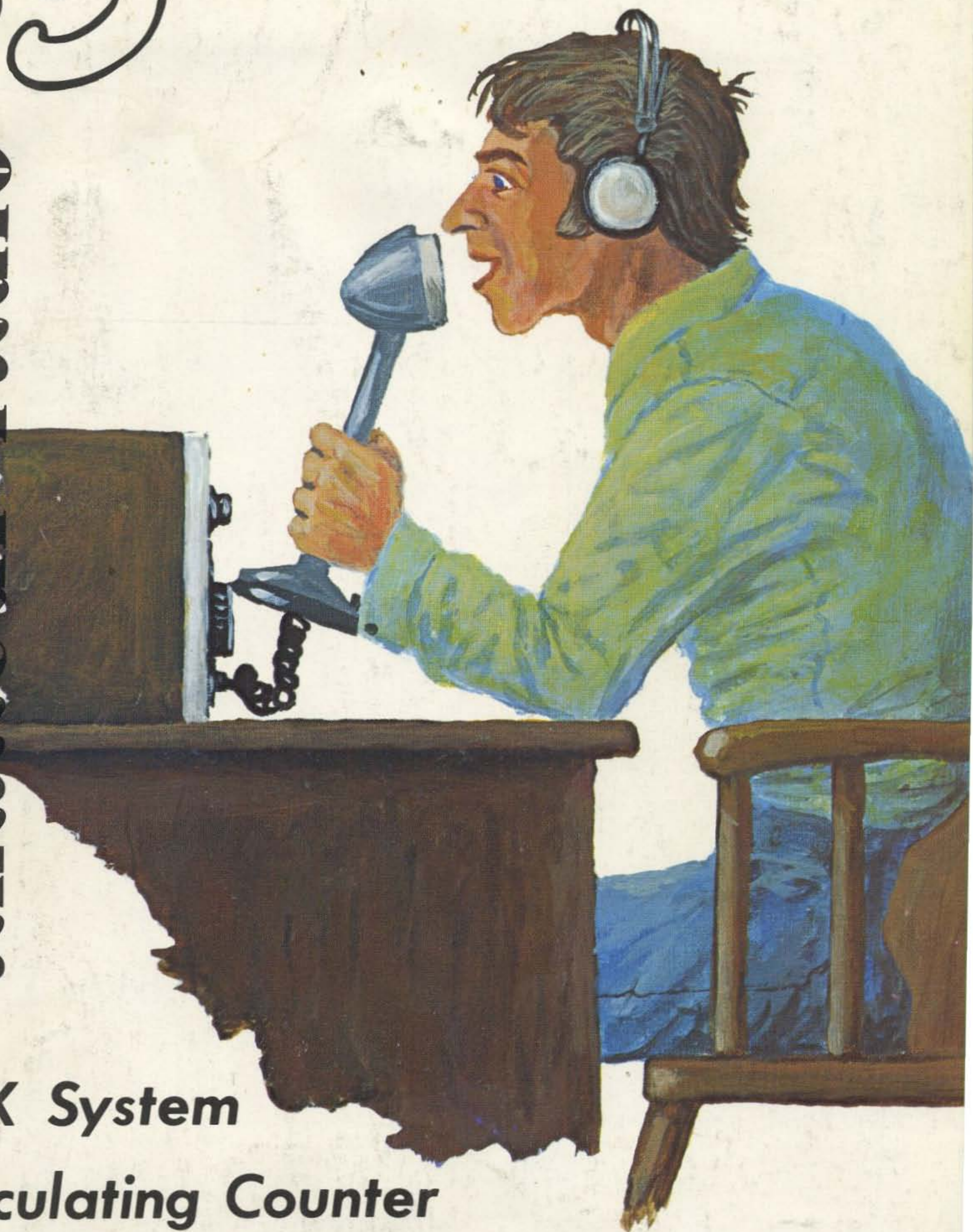


SEPTEMBER 1975
ONE DOLLAR

73

amateur radio



FAX System

Calculating Counter

0-60 MHz Synthesizer

R. W. Geiger

new

HUSTLER

the real performer! specifically for repeater

...or any TWO-METER FIXED STATION OPERATION

With **6** db—
db—

- Gain compared to ½ wave dipole
- FCC accepted for repeater application

mechanical

Vertical element—117"
long, 1-1/8" telescopic
to 3/8" OD high
strength aluminum

Radials—four, 21" x 3/16"
OD aluminum rod

Connector—SO-239

Wind load—26 pounds
at 100 mph.

Wind survival—100 mph.

Completely self-supporting

Mounting—fits vertical
pipe up to 1-3/4" OD

The gain you gain—you gain
transmitting and receiving—
get both with Hustler!

Available from
all distributors
who recognize the best!

electrical

6 db. gain over ½ wave dipole

Omnidirectional radiation pattern

Maximum radiation—at horizon

50 ohm feed impedance

Field adjustable—140-150 MHz

SWR at resonance—1.2:1 measured at antenna

Bandwidth—6 MHz for 2:1 or better SWR

Power—one kilowatt FM

Feed—Shunt with D.C. grounding


Radiator—5/8 wave lower section, ¼ wave
phasing, 5/8 wave upper section

THE HUSTLER MASTER GAINER
MODEL G6-144-A

**new
tronics
corporation**

15800 commerce park drive,
brook park, ohio 44142

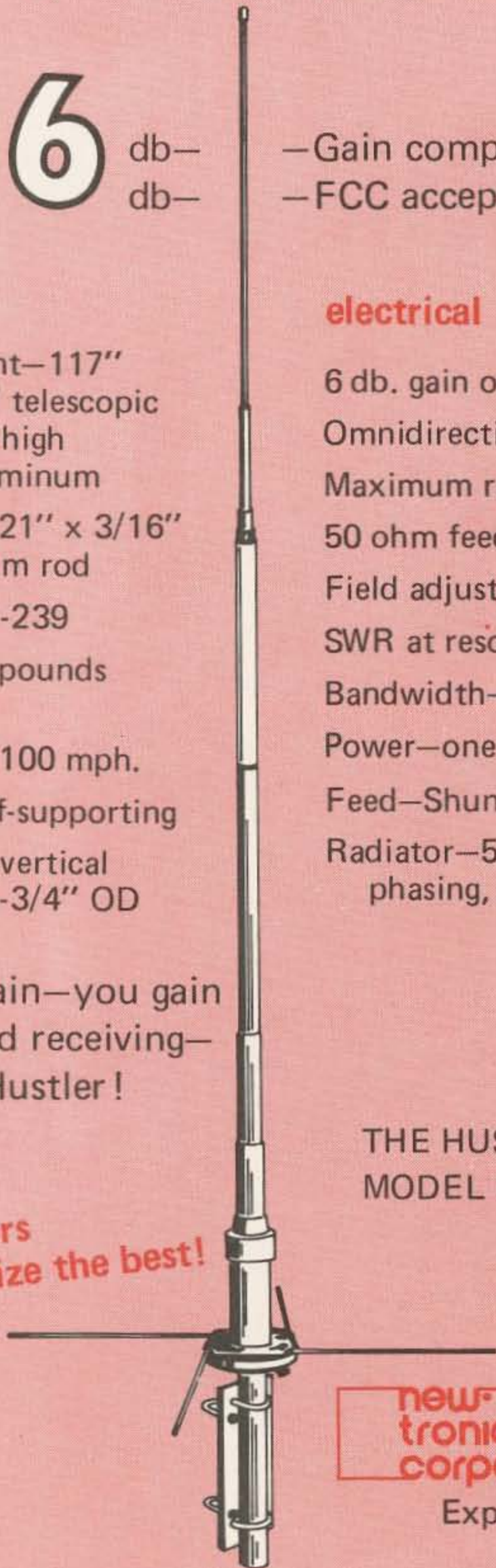Exporter: Roburn Agencies, Inc.,
New York, N.Y.



JOHNSON	22	The Calculating Counter
WB8DQT	39	A Satellite Fax System You Can Build
G3JQQ	49	Where is <i>your</i> simplified, sensitive millivoltmeter?
WAØEDA	52	Three Button TT Decoder
WA3AQS	57	Underground Radio is Dirty Business
K4TWJ	62	What's Wrong with my SSTV?
W7IDF	69	Queen Roger Papa from Hotel Whiskey Seven
W8HXR	78	40m DX Antennas — the Easy Way
WB4VXP	83	The Oscar Zapper
K2OAW	91	Digital SWR Computer
WB6OMT	97	Full Break-in at 60 wpm?
W2JTP	100	Odd Problems with an Old Antenna
WB8EQQ	103	The Alligator Squelcher
W9DJZ	105	You Don't Have a Power Failure Alarm?
W8CHK	110	Portable QRP Power Unit
WØHMK	118	You CAN Fix It!
WA6VVL	124	Precision +10.000 V dc Voltage Reference Standard
K1CLL	127	Building a 135 kHz i-f Strip
W4ZBE	133	A True Tale of the Faked Fist
WA8LEM	137	Adapting Telephone Handsets to FM Transceivers
W6LJU	140	Atlanta 1975
KØMOC	143	ATV on 450 with a T44
CALVIN	145	0-60 MHz Synthesizer
K3DSQ/4	155	Bridging the Information Gap

73 amateur radio

#180 SEPT 1975

2	Never Say Die	16	Caveat Emptor
3	For Your Eyes Only	17	AMSAT
4	Be My Guest	18	New Products
6	Letters	20	Social Events
8	Ancient Aviator	20	Corrections
10	Looking West	172	Ham Help
12	Networks	172	Hamburglar
14	Contests	192	Advertiser Index
		192	Propagation

COVER: Oils on Masonite, by
Jerry W. Geiger, Delafield WI.

73 Magazine is published monthly by 73, Inc., Peterborough, New Hampshire 03458. Subscription rates are \$8 for one year in North American and U.S. Zip Code areas overseas, \$9 per year elsewhere. Three years, \$16 and \$17 overseas. Second class postage paid at Peterborough, New Hampshire 03458 and at additional mailing offices. Phone: 603-924-3873. Microfilm edition of 73 available from University Microfilms, Ann Arbor MI 48106. Magnetic tapes available from Science for the Blind, 332 Rock Hill Rd., Bala Cynwyd PA 19904. Entire contents copyright 1975 by 73 Inc. Peterborough, NH 03458.



staff

73

EDITOR/PUBLISHER
Wayne Green W2NSD/1

MANAGER
Virginia Londner Green

BUSINESS MANAGER
Kim Huegel

MANAGING EDITOR
John C. Burnett

ASSISTANT EDITORS
Alex Barvicks WB4RVH
Fred R. Goldstein WB2ZJQ/1
Susan G. Philbrick

PRODUCTION MANAGER
Lynn Panciera-Fraser

ART DEPARTMENT
Nancy Estle
Neal Kandel
Peri Mahoney
Bob Sawyer

PRINTER
Biff Mahoney

PHOTOGRAPHY
Bill Heydolph

TYPESSETTING
Barbara J. Latti

ADVERTISING
Bill Edwards WB6BED/1
Nancy Cluff

COMPTROLLER
Knud E. M. Keller KV4GG/1

MARKETING
David H. Lodge
Theresa Toussaint

CIRCULATION
Barbara Block
Susan Chandler
Dorothy Gibson
Cheryl Hurd
Pearl Lahey
Marge McCarthy

INVENTORY CONTROL
Marshall Raymond

PLANT MAINTENANCE
Bill Barry
Elaine Mercier

ASSOCIATES
Robert Baker WA1SCX
E. H. Barnett WB0IIX
Schley Cox WB9LHO
Tom DiBiase WB8KZD
Terry Fox WB4JFI
W. Sanger Green
Dave Ingram K4TWJ
Joe Kasser G3ZCZ
Bill Pasternak WA6ITF
John Schulttz W2EEY
Waller Scott K8DIZ
Peter A. Stark K2OAW
Bill Turner WA0ABI

DRAFTING
Bill Morello
Lynn Malo
T. M. Graham Jr. W8FKW



NEVER SAY DIE

...de W2NSD/1

EDITORIAL BY WAYNE GREEN

SECRECY

Amateur and broadcast radio are the two major exceptions to the communications secrecy laws. This means that it is legal to tape record amateur transmissions and retransmit them or play them for others, while it is illegal to do this to CB transmissions, even illegal CB transmissions. Keep in mind that if you ever get involved with recording CBers, that it is illegal. Tapes sent to the FCC, if they have your address on them, can get you in a lot of trouble.

If you happen to hear emergency traffic on other radio services, remember that this is secret and you can't repeat what you've heard.

Section 605 of the Communications Act of 1934, as amended, reads, in part, "...no person not being authorized by the sender shall intercept any radio communication and divulge or publish the existence, contents, substance, purport, effect, or meaning of such intercepted communication to any person. ..."

HOTLINE BYTEN

The first tip of the iceberg for me was the response when we published anything having to do with computers in 73... instant massive reader enthusiasm. Hmm. I started trying to get more articles and also began asking around for information so I would know something about this new field.

RULE CHANGE FOR DEAF PETITIONED

The Mount Diablo Amateur Radio Club has petitioned the FCC to modify part 97.29 of the rules to permit deaf persons to copy code by some method other than ear, as specified in the rules. They suggest receiving via the fingers on a speaker cone or light flashes as viable alternatives. They point out that the present rules discriminate against deaf persons.

Since many of the pioneering developments in RTTY were done by Bob Weitbrecht W6NRM, a deaf amateur, it seems reasonable that this discrimination should be eliminated.

I found that there are a number of small newsletters for computer hobbyists, but not much else. Information was definitely hard to get.

In January this year MITS announced their Altair 8800 micro-computer with a big cover story in Poptronics. I knew right away I wanted one of those...it took a while, since several thousand other people had the same idea. A microprocessor for \$439 in kit form was a real breakthrough.

The more I was able to learn, the more I could see ahead...without turning 73 into a computer magazine there just was no way to cover all of the aspects of this new field. It would take a whole magazine devoted to the subject to do it justice. Hmm, again.

One of the most interesting computer hobby newsletters was being produced by Carl Helmers who, in addition to working full time for a computer firm, was also busy designing and building his own computer system and publishing the data on it. After a couple of talks with Carl the decision was made to go ahead and start a small magazine called BYTE. We thought we might give it a try with perhaps 24 pages and 1000 copies, something we could handle in our spare time.

We started talking it up with possible advertisers and sending out subscription letters on labels they provided. As the response grew, so did the plans for BYTE...to 5000 copies, then to 10,000...15,000...25,000...and still growing! We had enough advertisers to put out a 100 page first issue, and that meant an enormous amount of work for the whole staff. It also meant that something had to give, for we are working out of a big old colonial mansion and there are just so many offices available...and they were all full.

Since Hotline was published more for fun than profit, and since it took an inordinate amount of time for much of the staff to put it out, we reluctantly decided to end it. It was a lot of fun and we'll miss it.

Continued on page 12

FOR YOUR EYES ONLY

Required reading —
by Calvin McCarthy and Eric K. Albrecht K8BFH/1.

THE MOTHER EARTH NEWS HANDBOOK OF HOMEMADE POWER Bantam Book Y8535, \$1.95.

Amateurs today are as concerned about our depleting energy resources as many other people. The sensitivity of a crystal set is limited and it is very difficult to transmit radio energy without a source of electrical power. For the portable and mobile operator this problem is not somewhere over the rainbow, but right beside him. Where will the power come from to talk to the world?

Do you live by a stream? You could power your station by the running water. Do you operate from a windy location? With a six foot propeller in a 15 mph wind you could be extracting 140 free Watts to charge batteries. Do you live on a farm? A South African farmer found in the pig manure all the energy he needed to power his whole farm.

Interested? The HANDBOOK OF HOMEMADE POWER, a pocket book published by the MOTHER EARTH NEWS, gives very detailed and yet readable information on all these subjects. The editors received permission to reprint a five part article from *Popular Science Monthly* on building a stream powered generator. This includes information on calculating the power available in the stream, damming the stream, choosing the water energy to electrical energy transducer, building an impulse wheel, and building an overshot wheel. I can imagine an enterprising amateur build-

ing a small portable system for camping trips.

A section devoted to wind powered generators is just as comprehensive, discussing the amount of energy available in the wind, the various styles of windmills with their advantages and disadvantages, circuits, and pitfalls to avoid in setting up a wind generator.

I must confess that the section about methane was the one which compelled me to buy the book in the first place. Every couple of years I would notice a little article of interest in a newspaper or magazine telling of someone running an automobile or motorcycle on gas from animal waste. But how? There never seemed to be mention of how until this book appeared on the book racks with seventy-five pages devoted to the subject. Facts and figures on materials and conditions needed, as well as informative interviews with two men deeply involved with methane production, move the subject out of the realm of magic into the area of practicality. If a pig farmer can get more energy than he needs for his farm, then an amateur should find a way to get enough for a small station.

The most valuable twelve pages of the book contain its bibliography. Here are listed hundreds of sources of information, such as university papers and government publications, plus almost as many sources of hardware with company names and addresses. You will not be at a loss for information. The book was written as a guide, not as the end of Knowledge, and what an exciting sourcebook it is. Read it!


... McCarthy

ACTIVE FILTER COOKBOOK, by Don Lancaster, Howard Sams, \$14.95.

For this kind of price, you expect a book to be complete, well written, and practical. This one definitely is. Not only does it tell all about active filters — what they are, how they work, and how to design and use them — it also explains operational amplifiers completely. Aside from being the heart of active filters, op amps are very useful devices themselves, and this book will give you a solid background in using op amps, even if you never build an active filter. But if you do plan to use active filters, this book is a must. As for the math, complete mathematical derivations of each and every type of filter are provided, for those who want it. For those who don't, with the aid of this book you can design your own filters with simple algebra. (Even the "heavy" math derivations are done in high school algebra.)

Not only does the author tell what you can do with active filters, which is a lot, but also he plainly states what you cannot do. For instance, you cannot build a stable, high-Q, easy-to-tune bandpass filter with one op amp. Little pointers like this will keep you out of trouble, while the last section in the book stimulates your imagination, listing a wide variety of applications such as brain wave research, music synthesizers, speech therapy equipment, and touchtone decoders. The ACTIVE FILTER COOKBOOK is a welcome addition to 73's technical library, and it belongs in yours, too.

... K8BFH/1

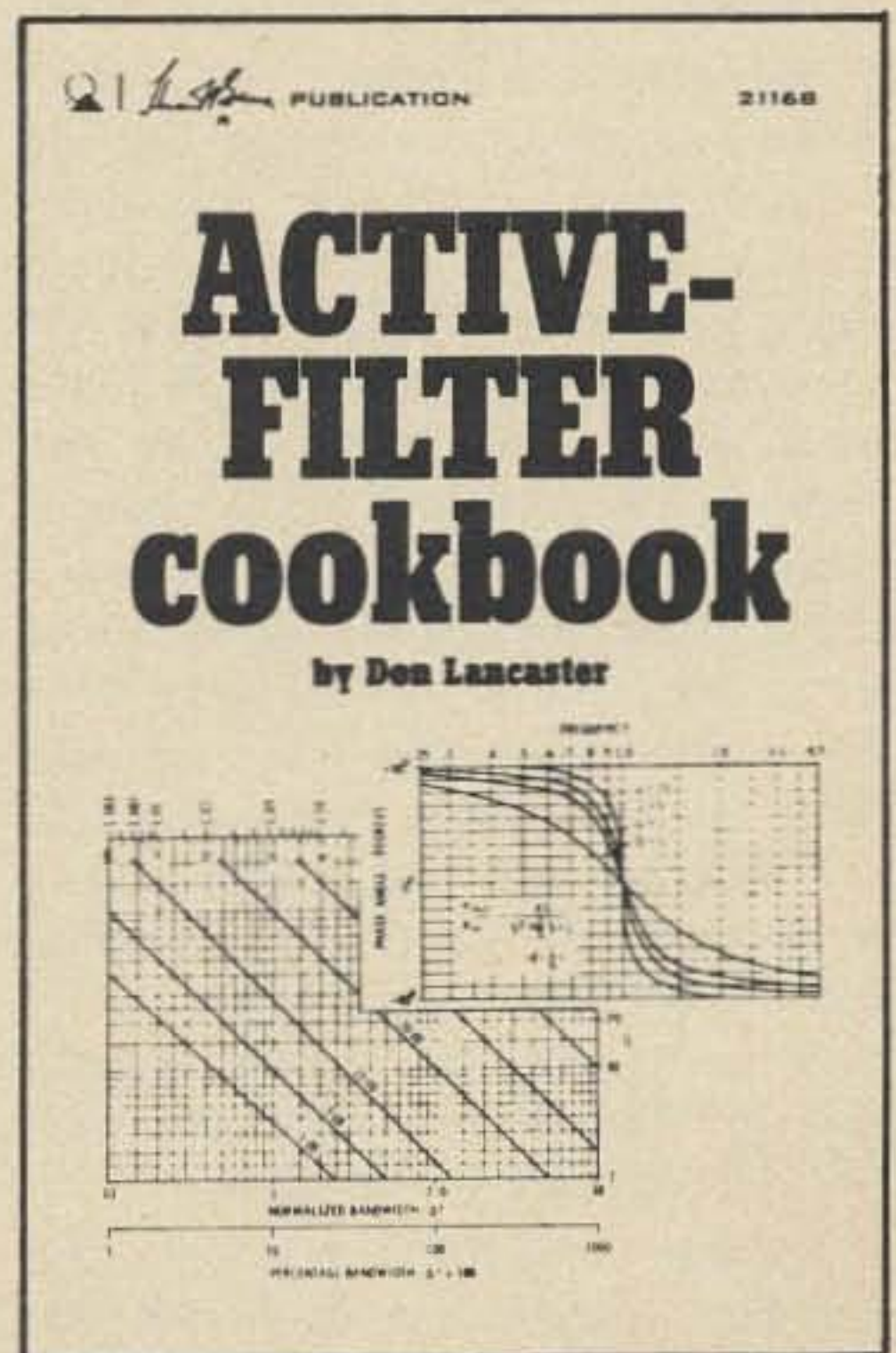

73 solicits reviews of current titles having to do with amateur radio and its periphery. While payment varies according to the size and quality of manuscripts, it is nonetheless uniformly generous. Contact Book Reviews, 73, Peterborough NH 03458.



BE MY GUEST

Visiting views from around the globe.

Frankly, my dear...

I know that anonymous communication is not generally well regarded, but in this instance I hope you will permit me to make a few good faith comments without identifying myself. At this point I will feel more comfortable about what I want to say.

I am a non-ham reader of your magazine. I regularly buy QST and 73 every month and enjoy them both, although I find more enjoyment in 73 than any other ham publication I have read. You may not realize that there are a good many of us aspiring hams who read your magazine and, although I try to learn and understand the terminology, I am lost by a good deal of it. Some of the technical articles are far beyond me. I know these articles are important and essential, but I would like to see more articles emphasizing the fun of radio as a hobby. I am always interested in the "personal experience" articles. For some of us who will never be electronic technicians it is a great incentive just to read about the enjoyment that hams have and, believe me, incentive is needed if you have no close ham friends to help you along.

My interest in amateur radio began when I was about twelve years old and I cut yards in the summer. One of my yard jobs was for a ham (now silent key) who was one great guy. He always asked me into the shack (in his attic) where I would sit silently and listen in amazement to the wonders of radio. I am sure that with his help I could have entered the ranks many years ago; however, my parents moved to another town and I lost contact with the ham world. Some time ago my interest was rekindled, and I decided to make a try for a license, but I have met with a good deal of disappointment and discouragement and, at the moment, I suppose I feel my prospects are not too good.

I know there are some people who can buy a license manual and a code record and have their General in three

months. Unfortunately, I work long hours, have no background in electronics, and find the going a little rough to handle by myself. I wish I had someone to talk to once in a while, and I would also enjoy sitting in the shack now and then and listening. In spite of all the complaints about the ham population diminishing, however, I find most are not willing to get personally involved. I know one very active ham with whom I have had a casual but friendly acquaintance for a number of years. I wrote a letter to him a few months ago and told him how interested I had become and that I would appreciate talking to him and would love to visit sometime, see his rig and to see him in operation. I made him a little gift which I knew he would enjoy and had it ready to take with me when I got his call. The call never came.

I have tried to meet a few other hams and have probably been a little too forward at times, such as, "Say, I notice by your license plate that you're a ham..." or "Isn't that a ham antenna in your back yard..." So far everyone has smiled, shaken hands, and been friendly, but the most encouragement I have gotten for the effort has been, "Lots of luck to you, fellow." Gee, thanks.

My ego suffers every time I read about one of those eight or ten year olds who has just gotten his license. But if the truth were known, I'll bet everyone of them had a dad, or a brother, or at least a good friend who gave them a little guidance and encouragement. It helps to be around someone who can talk the lingo. Right now I'm among the uninitiated which is somewhat akin to an Englishman trying to carry on a conversation with a Ubangi.

I am surprised with all of the tremendous mass of material available on technical advancements that so little has been done toward leading the prospective amateur in a systematic way into the ranks. There

are thousands of people who would like to join the great amateur fraternity (and I am talking about responsible people who play by the rules, not the ones who enjoy hollering "Super Chicken" and "10-4"), but there is no organized step-by-step procedure awaiting them. I am sure that the manufacturers would like a larger market for their products, but what have Drake, Swan and Yaesu done to provide theory instruction or training for aspiring hams? Look at the advertising in your own magazine. How many ads do you carry of training courses which would lead one to his General license? What I am saying is this, the ham industry has done a much better job in servicing the existing ham market than it has in developing the untapped potential market. Take a realistic look at the figures — CB sales are booming while the amateur ranks are thinning. Many hams seem to take an elite view of their status and to look condescendingly on outsiders. I guess they have nothing to lose... but their frequencies.

Don't misunderstand me... I am not asking for a lowering of standards. I like the high standards of amateur radio. I agree with many hams that the floodgates should not be opened to a rush of frustrated CBers who will desecrate the airwaves as they have their own (remember that not all CBers fit into this category). I don't mind working to get a ticket. All I'm saying is, I sure could use a little help and a lot of encouragement. If someone would just give me a push once in a while, I could get the theory — and I am not even griping about the 13 wpm. I don't really know any hams, I can't seem to get acquainted, and it's awfully hard for a guy like me, with no helpful background to draw on, to get it all on his own. I plan to keep on trying. But it sure takes guts to work so hard to get into an organization which epitomizes the immortal words of Rhett Butler.

service after the sale

I enjoy your magazine as an "outsider", whose interest is in good writing, state of the art and some day possibly even joining the amateur ranks. I am a Civil Air Patrol "button pushing" communicator who enjoys being of service.

My reason for writing is to tell Mark Poss (*Be My Guest*, July), et al, why we outsiders don't swarm into the amateur ranks. I must say that Mr. Poss sets out an outstanding public awareness program which, if done as he states it, will probably work well. But I am afraid his blueprint stops short of the real problem — which I refer to as the Ham Mystique.

Many of us non-hams have the bug but find it impossible to get reliable advice. I encourage you to try to put your ham jargon out of your mind and wander in to an amateur radio

store. Unless you speak the language you probably will not get waited on — and if business is slow and someone does stumble across you he might do you a favor and talk *at* you. Unless you are ready to plunk hundred dollar bills on the counter your average ham hardware store is the best place ever devised in which to be ignored.

Hams continually put down Children's Band operators and clubs — but this group has one big advantage over your average amateur group — they will talk with anyone. When on the airwaves this is one of their big problems, but that's not what I want to talk about.

My point to Poss and company is that you do not need to interest more people in amateur radio. If hams would genuinely open their hearts, minds, clubs and associations to that

great mass of people who are anxious to join them, the FCC would be issuing WZ calls within a year.

Be open about your hobby, remember that there once was a day when you didn't know a resistor from a carbon mike and offer your aid to people who seek you out.

It's tough being out here looking in when everyone on the inside has an elitist attitude. As a group, hams and ham hardware houses turn off more potential associates than they could ever hope to attract by the most fantastic public relations programs. It is not enough to simply sell your hobby to the public — you must also provide "service after the sale."

We're out here waiting for your help — what are you going to do about it?

Glenn B. Knight
Milwaukee WI

there's always Hope

Outsiders looking in at amateur radio raise valid points about the seeming indifference of some hams to the plight of the thousands of help-seekers who need aid and can't seem to get it. One YL — Hope Cliver, 10, of Joshua Tree, California — didn't need to go looking around for help: All six members of her family are hams. — Ed.

Hope Cliver, 10, of Joshua Tree, is the youngest General license amateur radio operator in the world, according to the American Radio Relay League.

Hope took the Federal Communications Commission examination in Los Angeles. She passed the radio electronic theory with excellent grades, and the code test at 13 words a minute.

It started for Hope at the Radio Amateurs' Transmitting Society, Palm Desert, headed by Hal Kapp W6WLU. The society initiated an amateur radio class which she attended. Bill Ellis, who drove from Culver City each week, was the instructor for the class.

Hope is the daughter of Betty and Ed Cliver, whose family of six are all radio operators, having held Novice licenses for a year.

She plans to work for her Advanced license while she is still 10, and take her Extra Class examination at the FCC when she is 11.

Hope will work 2, 10, 15, 20, 40 and 80 meters phone and code on her Kenwood TS520 transmitter. She will communicate with thousands of other amateur radio operators located in every nation of the world, including air and sea mobile stations.

With this early beginning she has considerable promise, according to Dr. Fern Stout, president of the College of the Desert, who praised Hope's progress at a recent luncheon of the Desert RATS, a local amateur radio group.

Kelly Shugart

Reprinted from Hi Desert Star, Yucca Valley CA, June 26, 1975.



ou goons don't ever proofr
lasy manuscripts from bab
bunch of trocks preting on
you ignored my comments in
I insist that you print ev

HOW "HOW GATES
WORK" WORKED

My thanks to Larry Kahaner WB2NEL for the July article, "How Gates Work" — it makes sense to an old tube man. When I can see the why and how something takes place, the rest is easy. Let's have more.

Earl L. Wiederhold K6SMT/WB6JOC
Bonita CA

Re "How Gates Work": Yes! We need more articles like this one — even giving very simple applications circuits that don't actually *do* much, except work — for those of us who want to learn more.

Phil Morrison, M.D. WA4AXO
Bristol VA

I am writing to compliment you on the article concerning TTL ICs. I found the article interesting and most stimulating to the ole gray matter. Yes, indeed, I feel that there should be more articles printed on the subject of ICs. It seems that in practically every electronic circuit one looks at these days, there is one type or another IC involved. There are quite a few devices printed about in 73 that I and others may like to build, but are held up due to lack of knowledge about ICs. Once again tnx.

Bruce M. Burkhardt WA3MAS
St. Michaels MD

Thanks for the "basics" on TTL ICs in your July issue. Textbooks assume that you know these things — so you duplicate their work without really knowing what's going on. Hope others liked the article, too, so that we can have some more basics from WB2NEL.

V. M. Shaw WA6BTA
Chatsworth CA

Was glad to see the article by WB2NEL, "How Gates Work." Hope he writes another.

Randy C. Withers ex-WN8OQA
Kettering OH

The article in the July issue by Larry Kahaner WB2NEL was excellent and informative. Kindly "cajole" him into doing another similar exposition.

Jerry Hargest WA5ERG

WB2NEL will attack op amps in the October issue. — Ed.

FISHING

I would appreciate your help. The Fisher Scientific Company and its subsidiaries are attempting to compile a roster of ham employees. We are interested in handle, call, branch, position held, and address of home QTH, and ask that Fisher ham employees please contact me at the address below.

Fred Shetler K3VMS
Fisher Scientific Company
Instrument Manufacturing Division
Indiana PA 15701

LOOKING

I am writing on behalf of our newly-formed Lawndale A.R.C., which is in need of transceivers (both VHF and CW/SSB). New or used contributions would be appreciated in order to help our young amateurs get on the air, and any help your readers could offer would certainly be welcome. Please contact: LARC, c/o WA3SZD, 321 Stevens St., Philadelphia PA 19111. Thank you.

Dennis J. Gazak WA3SZD
President, LARC
Philadelphia PA

DOOMSDAY?

Back in my college days, my fraternity decided to do away with a part of the initiation ceremony concerning paddling of pledges. This decision was greeted by a lot of us as a lowering of our standards and with thoughts of the imminent demise of our fine old fraternity.

Naturally none of these dire prophecies came to pass. I find something of the same "Doomsday" concept in comments now being made by hams writing to you concerning the proposed Communicator class license. All because the code requirement is absent they are all up in arms because they took it, and therefore, everybody should in order to get in the "club".

With the Communicator licensed for 144 MHz and above there seems little need for a code requirement as one rarely, if ever, hears it at these frequencies. I've read and heard all the comments about the need to get new blood in the hobby and now that a way exists a great many seem to be saying, "Hey, let's keep it small and cozy." This kind of an attitude is going to lead to even more stagnation than exists right now.

I am not a ham nor am I in CB, but I've listened to both for enough years to know the difference. With a properly formulated and enforced licensing structure most of the idiots on CB will stay there. A little self-policing on the hams' part will take care of those who do manage to get a ticket.

I agree with many of the remarks you made in the June issue and I can understand the attitude that no one wishes to be inundated by a flock of ex-CBers, but not all of us who may get the Communicator license are of this category. There's a lot of good responsible new blood out here who, given the chance, will prove willing and able to uphold the high standards that hams have enjoyed through the years.

Zachary Thomas Taylor
5410 Canal #4
Memphis TN 38118

P.S. If the Communicator fails, at least now we would-be hams know we can get our code practice by listening on 144 or 220! RIGHT?

MANAGING

I would like to inform you that I am the QSL manager of stations A4XFV, DK7PF/HB0, DK7PV/HB0, and DL0KJ, for their DXpedition to Liechtenstein (Sept 1-16, 1975, all bands CW/SSB, 10-80m). QSL via DJ7OM. Calls: DK7PF/HB0, DK7PV/HB0.

Paul Schmitt DJ7OM
D-657 Kirn
Ubergasse 20
Germany

REALLY GREAT

I started practicing with your 13 wpm cassette and found the transition between it and the 6 wpm cassette quite easy. I plan to go up for my Advanced in 6 weeks or so. I'm still in favor of a reduced speed requirement, but these cassettes are really great!

Fred Findling
Bethlehem NH

WARNING

Your article, "The Ultimate in Variable Selectivity?" (July), prompted me to warn about an often ignored problem when using VC diodes.

What is usually overlooked is that if the signal voltage is a significant percentage of the VC diode bias voltage, the VC diode capacitance is modulated by the signal in an unsymmetrical (and distorting) manner.

Examine the accompanying diagram of a typical FET Hartley oscillator. It is not at all unusual to find several volts of signal at the FET gate. On positive peaks the signal is series opposing to the VC diode bias; on negative peaks it is series aiding. This means that the VC diode capacitance is modulated by the signal in an unsymmetrical manner, producing a frequency (or phase) shift.

A similar effect could occur in your variable selectivity filter if the signal is a significant percentage of the VC diode bias voltage. Hence, the safest place to put the filter would be immediately after the converter stage.

In an FM receiver this could cause audible distortion, and you may never guess what is causing it. I'm not sure what the effect would be in an AM or CW receiver, but it could hardly be desirable.

Searching the literature carefully will lead to the discovery that some (Motorola for one) have published articles on how to compensate for this effect. These circuits usually involve two VC diodes arranged so that the capacitance modulation is cancelled out.

Clyde E. Wade, Jr.
312 S. Cedar
Little Rock AR 72205

Mr. Wade's "The Beauties of Shunt Regulation" will be appearing in an upcoming issue. Editor

MY KIND OF S.O.B.

There are many things that you write in your editorials that I don't agree with, but many times you point out things that I haven't considered — it makes me think again. If you ever change your editorial policy, you can cancel my subscription and keep what's left over.

Keep saying it — it needs to be said. I'm saying nothing you don't already know — but keep that needle sharp.

You're right about training the young people. I'm in two radio clubs now, and training is a major topic and effort — there's much talk on the bands about the young people, too. We have to (attract them), Wayne — they're our only salvation for hanging on to the bands we have now. Expansion, at present, is out of the question; we have to first hang on to what we have. Given population, then *maybe*.

One last comment: You're two (2) years too early on *BYTE* — *it won't make it*. My business is computer engineering, and you're going to sail over the heads of those people you're trying to address. I personally have great difficulty in communicating with a *savvy* electronics guy about logic, microprocessors and stored programs. You're idea is good, but you're too early — too early. If you can eat the losses for two years, OK, but it's going to be tough sledding. Anyway, you're a hard head — you enjoy the invitation to fail — that's the way we all got where we are. *73*, when it started, was pretty shaky, too.

Last thought: Why in the world

would QST want to go to an 8½x11 format? It boggles the mind.

Thanks for hearing me out, Wayne. You may be an S.O.B., but you're my kind of S.O.B. Keep plunging.

David R. Halliburton WA3ZOR
726 Tiffany Court
Gaithersburg MD 20760

ROTATING

Your most attractive July cover is even more interesting if one rotates it clockwise 90° and then views it in a mirror. One can make out Saudi Arabia, the Red Sea, Gulf of Aden and the east coast of Africa, including the Nile River. Even the island of Madagascar is visible in the lower central portion of the picture.


Lloyd Ferns VE3BZF
Orangeville, Ontario

GOOD-BYE Q-STREET

After receiving a bargain rate offer to subscribe to *73*, and get a nifty code practice tape to boot, I decided to once again get a ham magazine. After only two issues, I am hooked. Your special July Oscar issue was long overdue. After reading it, I finally had all the info I needed in order to get started, and I hope to be on soon.


I quit subscribing to *Q-Street* because most of the articles were geared toward only those with degrees in engineering. (Besides, your covers are better!) So congrats on an FB publication — I'm eagerly awaiting the next issue!

Jeff Kline WA1RFF
Sharon MA

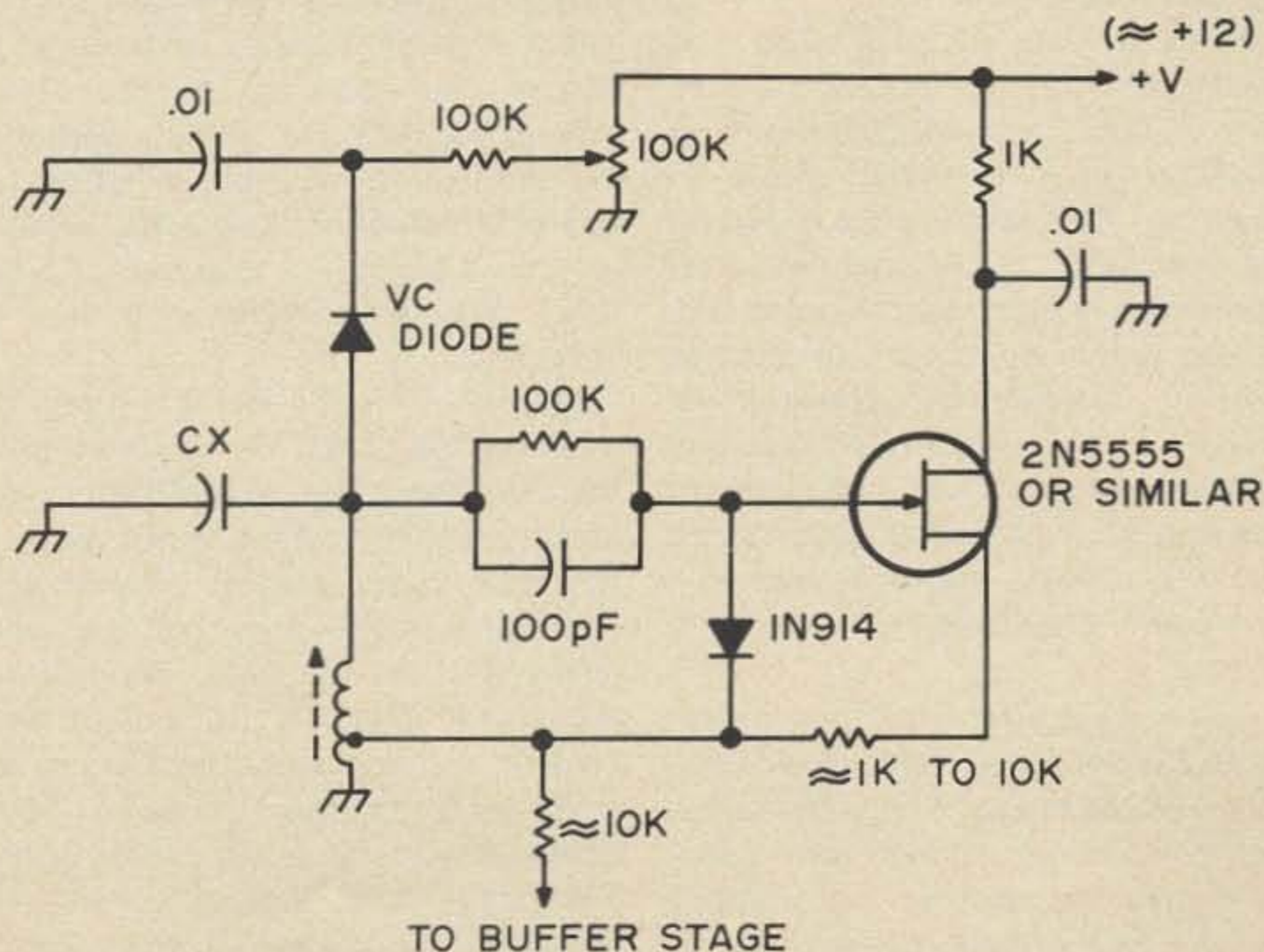

Autobiography of an Ancient Aviator

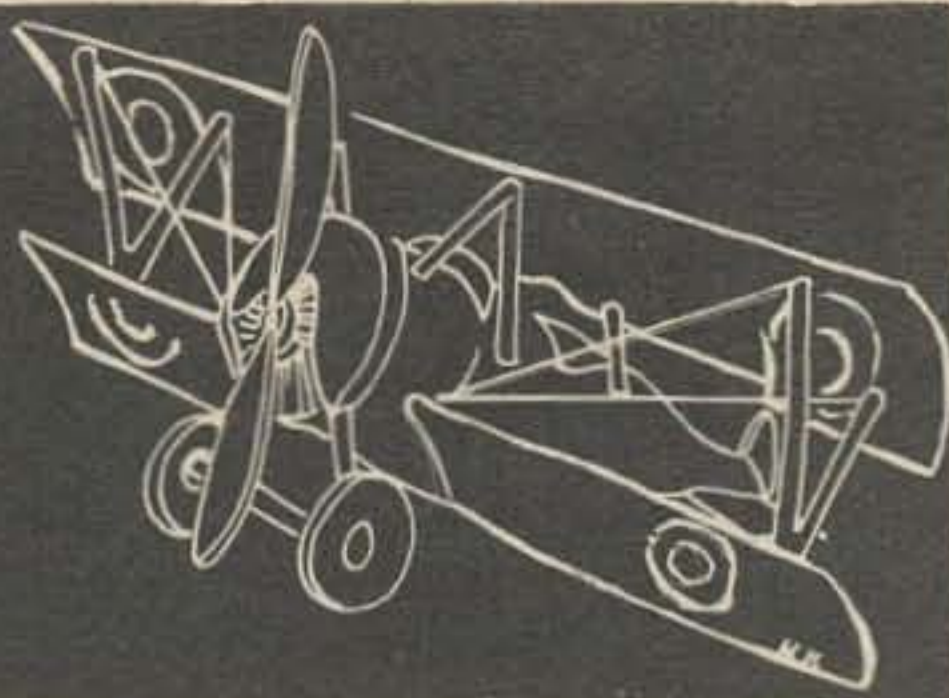W. Sanger Green
1379 E. 15 Street
Brooklyn NY 11230



GOOD BYE KELLY HELLO BROOKLYN

Graduation from the Air Service Advanced Flying School was on December 17, 1922. Forty-one cadets from the combined classes received their "Airplane Pilot" rating and their A.P. wings. All were commissioned 2nd Lieutenants in the Air Service Reserve Corps. All except myself had to buy officer's uniforms. Fortunately, I was able to have my father send me my WW1 uniform so all I had to do was to replace the Infantry Collar insignia with the Air Service prop and wings and pin my A.P. wings above my WW1 medal.

Lt. Chauncy asked Munson and I if we would mind staying over a couple of days to do an artillery adjustment mission that had been requested for December 19th. We agreed, if he would arrange a lift to Dallas for me on the 20th. (Better train service to New York out of Dallas.) We spent half a day near Fredericksburg telling an artillery battery what poor shots

We spent half a day . . . telling an artillery battery what poor shots they were. They had no anti-aircraft guns so we were safe.

they were. They had no anti-aircraft guns so we were safe.

Along in late October Cleo and Wayne had moved from her parents' farm in N.H. back to their home in Brooklyn, N.Y. I arrived there on December 23rd, just in time to put up and decorate the Christmas tree. Wayne was almost four months old. He had grown quite a bit since I had seen him in September. However, he was still small enough to fit nicely in the temporary crib Cleo had made for him out of a bureau drawer with a pillow in it for a mattress. We had a marvelous Christmas — our first together.

A few days after Christmas I went out to Curtiss Field, near Garden City, Long Island, to see if any flying job was available. I talked with Casey Jones and he said he had nothing available but suggested that I go over

to Heller Field in Newark, where an outfit called Federal Aviation had a hangar full of boxed LWF planes. He said he understood that they were assembling them for sale and that possibly one of their customers might want a pilot. Mitchel Field was nearby so I went over there to check in with operations for some army reserve flying.

Next day I went over to Newark and found my way out to Heller Field. Sure enough there was the hangar and I found Mr. Gillespie and his son in a lean-to with a potbelly stove going to keep the place livable. Yes, they owned the crated LWFs in the hangar but had no definite orders with deposits at that time. However, they had several warm prospects and were going to assemble a ship for display and would need some help for that. They explained that LWF stood for laminated wood fuselage (not loose, wobbly and frail as some people thought). The LWFs were originally equipped with a Sturtevant engine that was supposed to put out 200 horsepower. However, these engines had so thoroughly demonstrated their unreliability that Federal was junking them and installing 220 HP Hissos instead. (There is some question as to which of the two was more unreliable.) Gillespie said there was no problem in getting 220 Hissos if you had a case of whiskey to trade at a nearby Air Service depot. They offered me \$8 a day to help assemble the ship. Since my transportation to and from Brooklyn and lunch would be only \$1 a day, I told them I'd be there the next morning with my coveralls.

It took us until late February to assemble the plane. We had to remove the Sturtevant engine and install new hickory engine bearers. Then we got the new Hisso engine, cleaned the cosmoline preservative off it and installed it in the ship. We had to remove all controls from the front cockpit and cut away the fuselage to make seats for four (midgets). This, together with some soft places in the laminated wood fuselage (a result of rain water from a leaky roof), made it

advisable to reinforce said fuselage. This was taken care of by bolting a two by four on each side of the fuselage all the way from nose to tail. Well, it looked like an airplane, anyway.

There was no such thing as flight testing the plane from Heller Field. It may have been a flying field at one time but by 1923 there was barely enough cleared field to take off with no passengers and only enough gas to get to Newark Airport. There was no coming back into Heller, so the ship had to be rigged accurately enough to enable the pilot to get it to a larger field and land it.

By the end of February the LWF was finished but still not sold, so I got a part time job selling Hupmobiles in Brooklyn on salary and commission.

As a reserve officer I was able to get enough flying time in Jennies and DHs

Gillespie said there was no problem in getting 220 Hissos if you had a case of whiskey to trade at a nearby Air Service depot.

to keep my "hand in" at Mitchel Field, Long Island. I'd get out there almost every week and put in an hour or so.

Around the middle of July, Gillespie phoned and told me that the ship we had put together was sold to Hal Bazley of Everett, Mass. Delivery was to be at the East Boston airport and would I be interested in flying it up there? I had just finished a two week tour of active duty at Mitchel so I had some catching up to do on my Hupmobile prospect list. Gillespie offered \$150 plus expenses for the job so I told him I'd be over on July 27th to take the ship out of Heller.

On July 27th we gave the ship a final check and put ten gallons of gas in the tank. I got over the wires at the end of the field by about ten feet on my way to what is now Newark Airport. The ship handled very well with only a few minor adjustments to be made at Newark the next day. On the 30th I took the ship over to Mitchel and let some of the fellows over there look at it and shiver. Then on the 31st I flew her to Boston in two hours and forty-five minutes. Hal Bazley was there to meet me and take over ownership. I came back to New York that night on the "Old Fall River Line".

Next month I'll give you an account of my first experiences with an underpowered seaplane and with a Curtiss R4.

Stability.



That's what you get from Sentry crystals. The best frequency stability you'll find anywhere. Because Sentry crystals are made of the finest quartz to the latest state-of-the-art specifications.

And since Sentry has the largest semi-processed crystal bank in the world, we can custom-make crystals for any rig. And frequency. Faster than anyone else in the business.

Sentry gold-plated crystals are for long term reliability. Our order processing is quick and efficient. And we stand behind our work. With solid guarantees.

So send for our free catalog. And place your next order with Sentry. You can depend on us.

Sentry Manufacturing Company.
Crystal Park, Chickasha, Oklahoma 73018.
Phone: (405) 224-6780,
TWX-910-830-6425.

Sentry

Manufacturing Company

Tuned-In to Quality.



Sentry Manufacturing Co.
Crystal Park
Chickasha, Okla. 73018

73:9

**Please send me your Free 1975 Sentry Catalog.
RIGHT AWAY!**

Name _____

Street _____

City _____ State _____ Zip _____

**Send for
Sentry's
FREE 1975
Catalog!**



Repeater Temps Rising in 'Hot' SoCal

Bill Pasternak WA6ITF
14725 Titus St. #4
Panorama City CA 91402

Let's begin this month's report by clearing the air as to what you are about to read; it will be, I hope, as objective a report as is possible on a rather controversial subject: that of the confrontation between proponents of repeaters and their counterparts favoring simplex operation on 146.76 MHz. To begin, a look back is definitely in order. If one is a traditionalist, and believes that the past must govern the future, then there is no question that "squatters' rights" prevail and that 146.76 must be reserved for simplex operation in the Los Angeles area. The many inhabitants of .76 simplex trace their heritage on that channel back to the late 1950s when they were just about the only occupants of what is today the repeater sub-band. As I understand the story, during the late fifties and early sixties the "in" channel was 146.755, due to the fact that everyone had the same surplus crystal. It was in the early sixties, and no one is quite sure as to why a move was made, that everyone QSYed up to .76 — and they have remained there ever since. Most, though not all, of the .76 simplexers live in the San Fernando Valley area, slightly northwest of L.A. proper.

While most stories have two sides, this one is rather unique in that it has four: that of the simplex inhabitants of .76, that of the Southern California Repeater Association, and that of the two repeaters accused by the simplex users of causing interference to .76 (WR6AJL, Mt. Laguna, in San Diego and WR6AFX on Table Mountain in the Antelope Valley area). As to the latter, WR6AFX, by far they have shown the most cooperation in this matter to date. As I stated in an earlier column filed in very early April, at that time I had yet to hear any signal from WR6AJL while at this QTH WR6AFX was definitely audible. Though I am not a .76 user, I do happen to live right smack in the middle of the San Fernando Valley


and therefore decided to monitor the entire situation for myself.

There were two reasons for this. First, when tempers are running high, I tend to take much of what is told me with the proverbial grain of salt. The thought always goes through my mind at these times, "Wouldn't Joe Blow just love to convince me that he was right and the rest of the world was wrong and then make use of this column to plead his case to the nation?" The day I let that happen is the day when Wayne has my permission and support to pull this column from publication, and that gives you the second reason, to report one must deal in facts and supportable evidence — not heresy and innuendo.

While things grew worse to the south, the people responsible for WR6AFX, working with members of the SCRA Technical Committee, found that by re-orienting their antenna system most if not all of their signal leaking into the San Fernando Valley could be eliminated. At least in the eyes of the non-repeater simplex operators, WR6AFX was no longer a source of interference to them. If you don't mind my digressing for a

moment, I wish to publicly express my appreciation in the name of the Southern California amateur radio community to WR6AFX, its owners and its users, for proving that the concept of mutual cooperation can and does work. As your editor noted in an earlier column, WR6AFX provides a rather invaluable service to those traveling the desert route between L.A. and points east.

During the time that a solution to the AFX vs. .76 simplex problem was being found, the SCRA was also trying hard to solve the Mt. Laguna issue. WR6AJL, Mt. Laguna, was operating under a 90 day temporary SCRA sanction and had specifically stated that its purpose was to provide desert coverage east from San Diego toward Yuma, Arizona. On countless occasions the San Diego Repeater Association (SANDRA) stated publicly that its purpose in erecting AJL was to provide open radio relay coverage to the aforementioned desert area and to Imperial County and that they, SANDRA, would take whatever steps were necessary to insure that there would be no interference to any Los Angeles operations. As early as

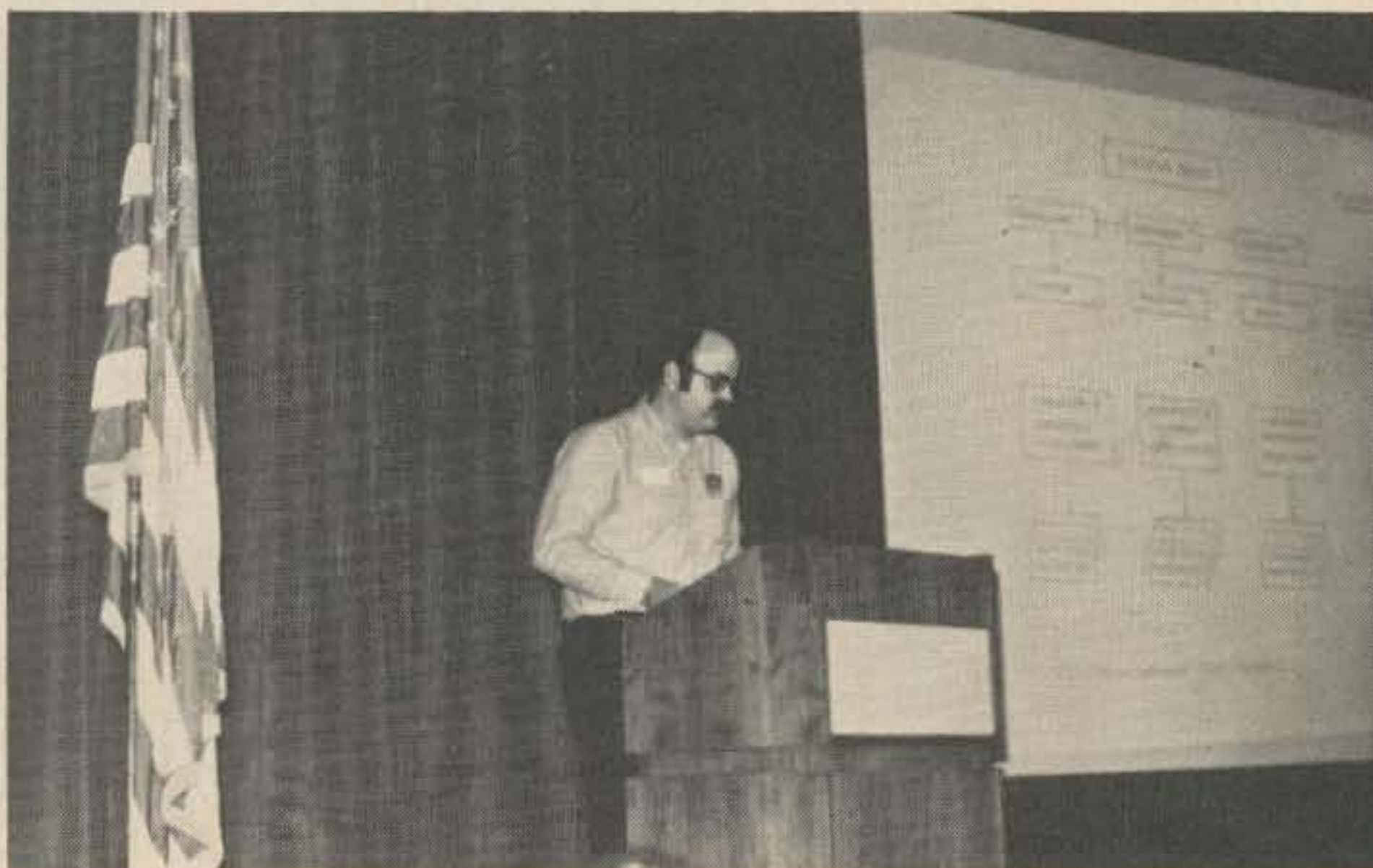

"Mr. Chairperson" Dick Flanagan W6OLD presides over June SCRA meeting at JPL in Pasadena.

October 1974, in meeting notes published in SANDRA's *Squelch Tales* newsletter, in discussing the merits of a .16/.76 repeater, it was stated as point #8 on page 17 of that publication that, "Our repeater should not interfere with Los Angeles, since our antenna will be east-west." In the monthly listing of SANDRA-sponsored repeaters appearing in *Squelch Tales*, WR6AJL is listed as "desert coverage". Yet WR6AJL, sitting atop an 8000' mountain, utilizes a Stationmaster antenna with a 3 degree down-tilt that effectively aims it at the "radio horizon" in a 360 degree pattern. The radio horizon to the north for Mt. Laguna is Los Angeles!

SANDRA claimed and continues to claim that it has done and will continue to do all that is possible to eliminate the problem; however, it is evident that their words don't at this time fully align with their deeds. At the June 21 SCRA General Membership Meeting, it was announced that due to what was felt to be a total lack of cooperation on the part of SANDRA officials to work with the Technical Committee in solving this ever-worsening problem, their failure to file the required 75 day operational test report to the SCRA Technical Committee, and on other documentable matters in regard to this situation, that the temporary authorization (sanction) for WR6AJL had been terminated as of June 17th and that they were being requested to cease operation at once. Rather than adhere to this decision of the SCRA, the representatives of SANDRA withdrew en masse from SCRA membership, stating that they felt SCRA did not properly represent the interests of San



Table Mountain responds to Technical Committee report.

Diego area FMers, and that they would go it alone. It was also stated by SANDRA representatives that their reason for not filing the aforementioned 75 day test report was that, due to the installation of the new Stationmaster antenna, any data contained in the report (data gathered before the new antenna was erected) would be outdated. (Of note, the test report is a necessity according to SCRA rules regardless of what type of modifications are taking place during an initial test period. Data contained therein can always be updated by amending such a report at a later date.) Also of note, though I have made it known publicly that I am following developments in this matter for publication in this column, and while both the SCRA and the simplex users have been most cooperative in furnishing data on this story, I have

yet to hear anything from the San Diego Repeater Association. That is all that is necessary to have their side of the story expressed from their viewpoint.


In the interim, WR6AKC, the Valley .76/.16 "in band talk back", a non-SCRA sanctioned or coordinated repeater, is busy at work locking up WR6AJL (or is it WR6AJL that is locking up WR6AKC?). Frankly, I don't give a damn which machine is doing what to which. I do care, however, about the loathsome creature who has apparently decided to expand this confrontation to include one of our local repeaters here in L.A.: WR6ABN. Of late, the "grunge" from .76 is appearing on the ABN .84 - .24 system and I guess the assumption must be made that due to the fact that ABN's owner supports the L.A. simplex activity, his repeater must be included in the confrontation. How utterly childish and asinine can people who are supposedly competent individuals and licensed amateur radio operators get? When will they ever learn that violence only breeds violence and that acting in such a crass manner can only bring the total wrath of both fellow amateurs and the FCC upon their heads? I for one want to know the individual responsible for this hideous act against the Southern California amateur radio community, so that he or they can be exposed to their peers for the sick malcontents that they are! If you want to fight over .76 then keep your fight on .76 or risk the wrath of your fellow hams nationwide - I will see to it that such is sent your way!



Skip Clark WB6TXX, SCRA Vice Chairman, responds to responses, as Sybil Albright W6GIC, SCRA Secretary and SANDRA Board Member, looks on.

Continued on page 162

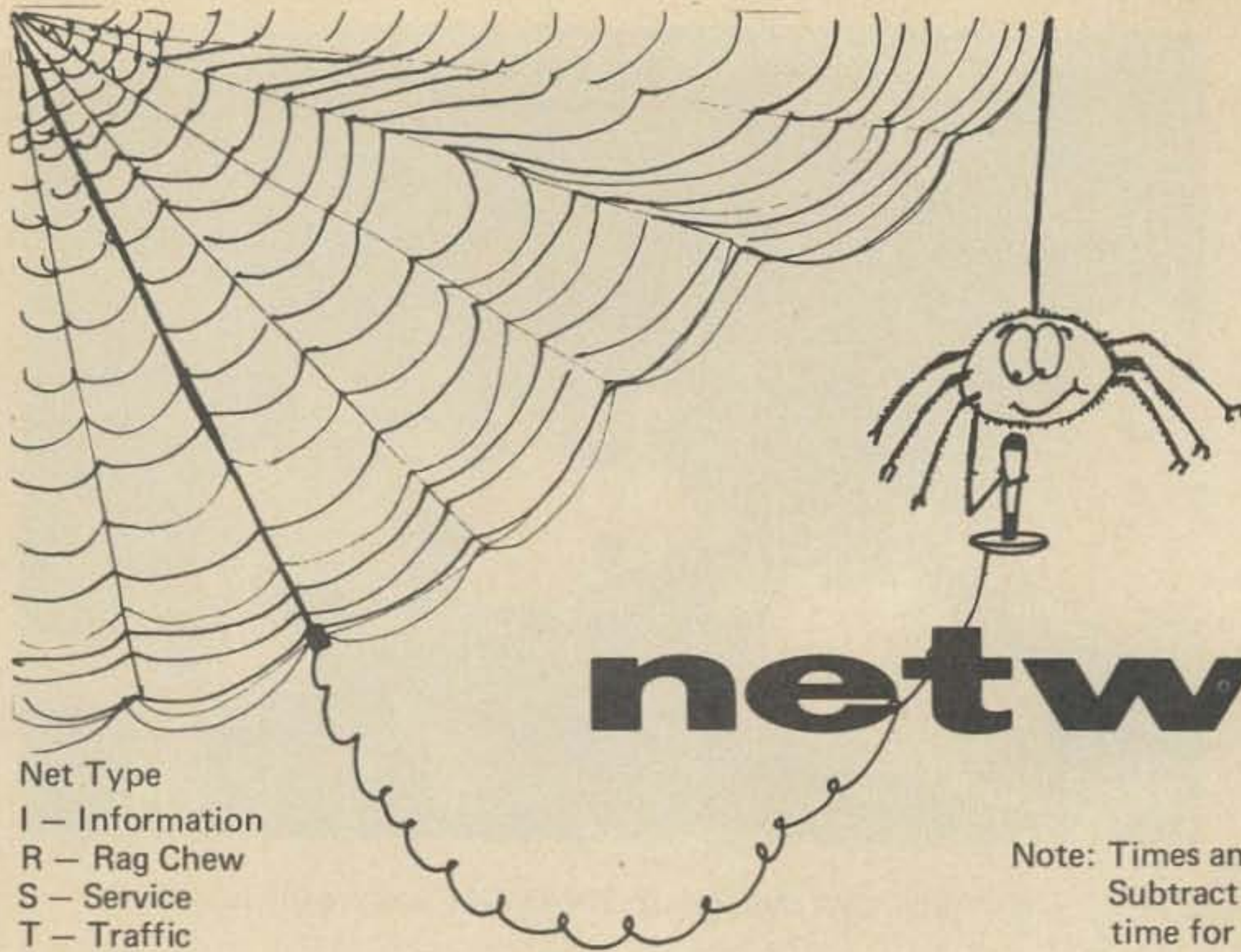E. H. Barnett WB0IIX
Route 1
Ashland, Missouri 65010



networks

Net Type
I - Information
R - Rag Chew
S - Service
T - Traffic

Note: Times and Days are given in GMT.
Subtract one hour for nets changing
time for Daylight Savings Time.

Service Area	Net Type	Name	Time	Days	Freq	Mode
INTERCONTINENTAL						
North & South America	T	Intercontinental Net	1200	Daily	14313	USB
North & South America	T	Americas Net	1800	Mon & Fri	14205	USB
North & South America	T	Intercontinental Net	2300	Daily	14313	USB
NATIONWIDE						
U.S.	S	Eyebank Net	0100	Daily	3970	LSB
U.S.	S	Eyeband Net	1200	Daily	3970	LSB
REGIONAL						
Gulf Coast U.S.	T	Gulf Coast SBN	2330	Daily	3925	LSB
East U.S.	S	ECARS	Cont.	Daily	7255	LSB
Midwest U.S.	S	MWARS	Cont.	Daily	7258	LSB
Southeast U.S.	R	Corncobbers	1130	Mon - Fri	7274	LSB
Mid U.S.	S	Recreational Vehicle Net	1130	Mon - Fri	7280	LSB
STATEWIDE						
NJ	T	NJ Net	0000	Daily	3695	CW
MO	T	Missouri SBN	0000	Tues - Sat	3963	LSB
IA	T	Iowa SBN	0000	Daily	3970	LSB
KS	T	Kansas SBN	1245	Mon - Sat	3920	LSB
IN	T	Indiana Traffic Net	1330	Daily	3910	LSB
FL	R	Florida QCWA Net	1700	Sun	7247	LSB
SC	T	SC Emergency Net	2300	Daily	3907	LSB
IN	T	Indiana Traffic Net	2300	Daily	3910	LSB
KY	T	Kentucky Traffic Net	2345	Daily	3955	LSB
OH	T	Ohio SBN	2345	Daily	3972	LSB

I need your help. There are only so many nets that I can discover for myself. Help me by telling me about nets that you know of. Just drop me a QSL stating: Name, Area served, Time (GMT), Days (GMT), Freq. & Mode.



EDITORIAL BY WAYNE GREEN

from page 2

TIME TO SUBSCRIBE?

There is a lot to dislike about the larger size format for the ham magazines . . . and one of the worst aspects is that, despite what anyone says, it is a lot more expensive than the smaller magazines . . . and this means a higher cost to you.

The new cover price for 73 will be

\$1.50, starting with January, which comes out to \$18 per year on the newsstands. The subscription price will go up, first to \$10 a year . . . more later on. Add to this an extra \$2 for a special secret giant bonus issue which is in the works and you will spend \$20 on the newsstand for the year! That makes the present \$8 per year, \$16 for three year rate look pretty good. These rates will hold until October 15th, then it's up they go. October 15th is the last minute for getting a subscription into the blasted computer system for the December issue . . . which is mailed in early November.

Over a three year period you save about \$44 by spending \$16 now.

BOX SCORE

Readers might not notice, but advertisers and other publishers (particularly) notice little things like the number of pages in a magazine or the number of pages of ads in an issue. You've probably been vaguely aware that it takes longer to read 73 these days and it's a little heavier to prop up in bed.

During the last quarter the ad pages worked out like this . . .

Continued on page 168

The TEMPO line . . . commercial quality at amateur prices

Compare this equipment with any other available. Compare their performance, their quality of construction, their ease of maintenance, and then compare prices. Your choice will have to be TEMPO.

new!



TEMPO/CL 146A

. . . a VHF/FM mobile transceiver for the 2 meter amateur band. It is compact, ruggedly built and completely solid state. One channel supplied plus two channels of your choice

FREE

144 to 148 MHz coverage Multifrequency spread of 2 MHz 12 channel possible Metering of output and receive Internal speaker, dynamic microphone, mounting bracket and power cord supplied. A Tempo "best buy" at \$239.00.



TEMPO CL 220



As new as tomorrow! The superb CL-220 embodies the same general specifications as the CL-146A, but operates in the frequency range of 220-225 MHz (any two MHz without retuning). At \$299.00 it is undoubtedly the best value available today.

TEMPO/fmh

So much for so little! 2 watt VHF/FM hand held 6 Channel capability, solid state, 12 VDC. 144-148 MHz (any two MHz), includes 1 pair of crystals, built-in charging terminals for ni-cad cells, S-meter, battery level meter, telescoping whip antenna, internal speaker & microphone.

\$199.00

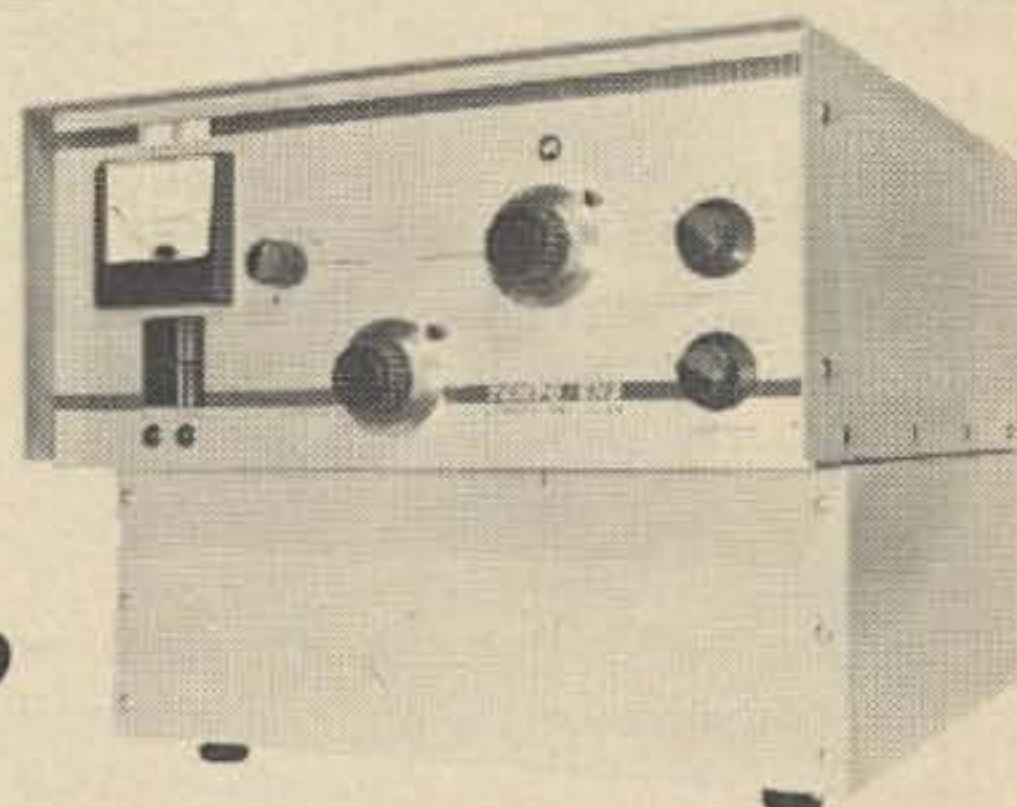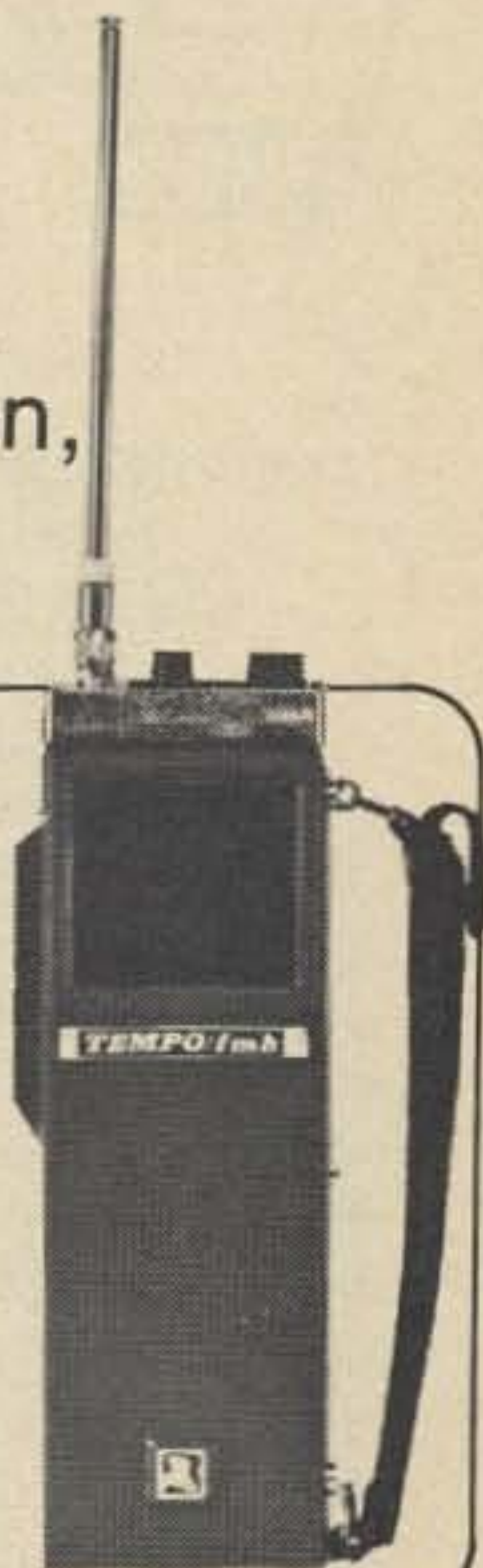FMH-MC for Marine & Commercial service also available.




TEMPO 6N2

The Tempo 6N2 meets the demand for a high power six meter and two meter power amplifier. Using a pair of Eimac 8874 tubes it provides 2000 watts PEP input on SSB and 1000 watts input on CW and FM. Completely self-contained in one small desk mount cabinet with internal solid state power supply, built-in blower and RF relative power indicator.

\$795.00

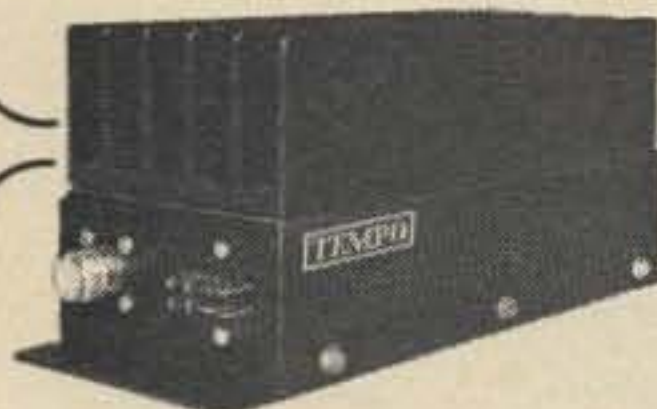The Tempo 2002.. 2 meters only \$695.00
The Tempo 2006.. 6 meters only \$695.00



TEMPO VHF/UHF AMPLIFIERS

Solid state power amplifiers for use in most land mobile applications. Increase the range, clarity, reliability and speed of two-way communications.

VHF (135 to 175 MHz)

Drive Power	Output	Model No.	Price
2W	130W	130A02	\$199
10W	130W	130A10	\$179
30W	130W	130A30	\$189
2W	80W	80A02	\$169
10W	80W	80A10	\$149
30W	80W	80A30	\$159

UHF (400 to 512 MHz)

Drive Power	Output	Model No.	Price
2W	70W	70D02	\$270
10W	70W	70D10	\$250
30W	70W	70D30	\$210
2W	40W	40D02	\$180
10W	40W	40D10	\$145
2W	10W	10D02	\$125

FCC Type accepted models also available.


Available at select dealers throughout the U.S.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Prices subject to change without notice.

CONTESTS

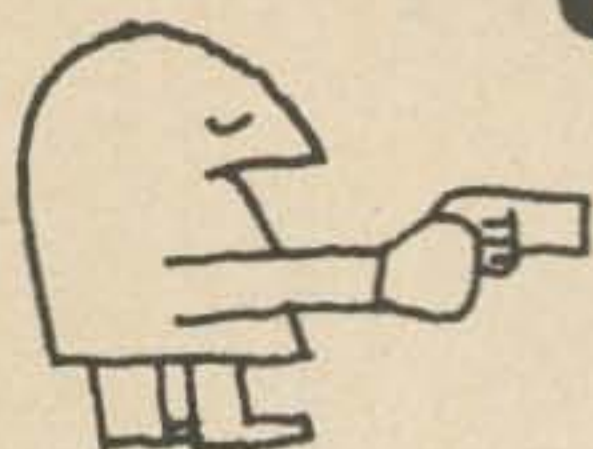

Editor:
Robert Baker WA1SCX
34 White Pine Drive
Littleton MA 01460



OHIO INTERSTATE QSO PARTY

1900 GMT Saturday
August 30 to 0300 GMT
Sunday, August 31
1500 GMT to 2300 GMT
Sunday, August 31

All amateurs are invited to participate in the Ohio Interstate QSO Party sponsored by the Ohio Council of Amateur Radio Clubs. There are no restrictions on operating time, power or number of operators or transmitters. Each station can be worked twice on each band: once on phone, and once on CW. Ohio stations may contact any other station for credit. Non-Ohio stations may contact only Ohio stations for credit. To encourage emergency preparedness and provide contacts from rare Ohio counties, portable stations operating from any Ohio county EXCEPT Butler, Cuyahoga, Franklin, Hamilton, Lorain, Lucas, Mahoning, Montgomery, Stark, Summit, and Trumbull may multiply their final score by 1.5. Portable operation is defined as operation outside the county in which you are licensed and signing your call as /8.

EXCHANGE:

Send QSO number, RS(T), and ARRL section or Ohio county. Stations operating on a county line may issue more than one multiplier, but not more than one QSO number, to an individual station per band per mode.

FREQUENCIES:

1805, 3575, 3975, 7075, 7275, 14075, 14285, 21075, 21375, 28075, 28575, 50.15, and 145.10. Try phone each even hour GMT and CW each odd hour GMT. Try 160 at 0200 GMT August 31.

SCORING:

QSO points are 1 per completed exchange on 80 through 10 meters, and 2 on 160 and all frequencies above 50 MHz. As a bonus, a complete exchange with the Ohio State Fair special event station is 5 QSO points on 80 through 10 meters. For Ohio stations, the final score is the total number of QSO points

multiplied by the number of ARRL sections worked, including Ohio. DX stations may be worked for QSO points but do not count as additional sections. For all others, the number of QSO points is multiplied by the number of Ohio counties worked. Portable stations changing counties during the contest may repeat contacts for QSO points, but multiple contacts may not be claimed by operating on a county line. Stations outside Ohio may claim both QSO points and counties.

AWARDS:

First, second and third place awards will be given to the highest scoring stations inside and outside Ohio, and to the winners in each ARRL section and Ohio county, providing at least 10 different stations are contacted. Separate awards to stations using frequencies above 50 MHz exclusively.

LOGS

Logs showing time, date, stations contacted, QSO exchange, band, mode, location and score must be received by November 1, 1975, by: OHIO QSO Party, 6470 Penick Drive, Reynoldsburg OH 43068. Contest package of log, Ohio County and ARRL section list, and summary sheet will be sent by the OHIO QSO Party upon receipt of SASE.

EUROPEAN DX CONTEST — PHONE

Starts: 0000 GMT Saturday,
September 13
Ends: 2400 GMT Sunday,
September 14

DARC is sponsoring the 21st annual European DX Contest this year. Use all bands, 80 to 10 meters. Only 36 hours of the 48 hour contest period may be used by single operator stations. The 12 hour rest period may be taken in one but not more than 3 periods, anytime during the contest. Single operator-All Band and Multi-operator Single transmitter are the only 2 classes.

EXCHANGE:

Five or six digit number, RS(T), QSO Number (start at 001).

SCORING:

One point per QSO and one point for each QTC reported.

MULTIPLIERS:

Multiplier for Non-Europeans is number of EU stations worked on each band. Europeans will use ARRL list and call areas: JA, PY, VE/V0, VK, W/K, ZL, ZS and UA9/UA0. In addition, the multiplier on 80 meters may be multiplied by 4, on 40 meters by 3, and on 20 to 10 meters by 2.

FINAL SCORE:

Final score equals total QSO points plus QTC points, times the sum total multiplier from all bands.

QTC — TRAFFIC:

Additional QSO point credit may be realized by reporting a QTC. This is a report of a QSO you have made earlier in the contest and later sent back to an EU station. One point is earned for each QSO reported. A QTC can only be sent from a non-EU to an EU station. A QTC contains the time, call and QSO number of the station being reported. Example: 1432 — G4JZ — 157. It may be reported only once and not back to the originating station. A maximum of 10 QTCs are permitted to the same station, and the same station may be worked several times to complete this quota. However, the original QSO is all that may be counted toward QSO points. Try to keep a uniform list of QTCs sent. QTC 4/6 indicates that this is the 4th series with 6 QSOs now being sent.

AWARDS:

Certificates will be awarded to the highest scorers in each country and call area listed above. Continental leaders, and stations having at least half the score of the continental leader, will also be awarded certificates.

DISQUALIFICATIONS:

Violation of the rules, unsportsmanlike conduct, or taking credit for excessive duplicate contacts or multipliers will be deemed cause for disqualification. Decision of the Contest Committee is final.

LOGS:

It is suggested that you use the official DARC log and summary forms. An SASE with sufficient postage or IRCs should be sent to the Contest Committee (or to W1WY or WA3KWD for W/K and VE stations). If making your own logs, use 40 contacts to the page and use a separate sheet for each band. Mailing deadline for logs is October 15, 1975, to the WAEDC Contest Committee, D-895 Kaufbeuren, P.O. Box 262, West Germany.

EUROPEAN COUNTRY LIST:

C31, CT1, CT2, DL, DM, EA, EA6, EI, F, FC, G, GC Guer, GC Jer, GD, GI, GM, GM Shetland, GW, HA, HB9, HB0, HV, I, IS, IT, JW Bear, JW, JX, LA, LX, LZ, M1, OE, OH, OH0, OJ0, OK, ON, OY, OZ, PA, SM, SP, SV, SV Crete, SV Rhodes, SV Athos, TA1, TF, UA1-3-6, UA2, UB5, UC2, UN1, UO5, UP2, UQ2, UR2, UA Franz Josef Land, YO, YU, ZA, ZB2, 3A, 4U1, 9H1.

PENNSYLVANIA QSO PARTY

Operating Periods:

1600 to 2100 GMT Saturday,
September 13
2300 GMT Sat., Sept. 13 to
0500 GMT Sun., Sept. 14
1300 to 2400 GMT Sunday,
September 14

All amateurs are invited to participate in the 18th annual Pennsylvania QSO Party sponsored by the Nittany Amateur Radio Club. Pennsylvania stations may work both in-state and out-of-state stations.

EXCHANGE:

Send QSO number, RS(T), and PA county or ARRL section.

FREQUENCIES:

1810, 3560, 7060, 14060, 21060, 28060, 1815, 3980, 7280, 14315, 21380, 28560. Novice: 3715, 7160, 21115, 28115. Try phone on EVEN hours, 160 meters at 0300, and 10 meters at 1900 GMT.

SCORING:

Pennsylvania stations score 3 points per out-of-state QSO, 1 point for PA QSOs multiplied by the number of ARRL sections worked (EPA & WPA may be counted as sections). All others score 1 point per QSO times the total number of PA counties worked. Stations may be worked once on each CW band and once on each phone band. A bonus of 100 points is offered to each mobile for each county activated during the contest.

LOGS:

Send log and summary sheet including number of QSOs, total number of counties or sections, QSO points, final claimed score, rig description, number of hours operated, comments, gripes, and suggestions by October 15, 1975 to: W3HDH, Douglas Maddox, 1187 S. Garner Street, State College PA 16801. Results will appear in the January issue of the Nittany Amateur Radio Club Newsletter, which will be mailed to all entrants.

YL HOWDY DAYS CONTEST

Starts: 1800 GMT Wednesday,
September 17
Ends: 1800 GMT Friday,
September 18

Only contacts with licensed women operators count. All bands and modes of emission may be used. No cross-band operation and net contacts do not count. Only one contact with each station will be counted.

SCORING:

Score two points for each YLRL member worked and one point for each non-YLRL member worked. There are no multipliers.

AWARDS:

Top scoring YLRL member will receive her choice of a YLRL pin, charm, or stationery. Non-YLRL member will receive a one year membership in YLRL.

LOGS:

Logs must be received no later than October 19, 1975 by Mrs. Myrtle Cunningham WA6ISY, 1105 East Acacia Avenue, El Segundo CA 90245.

DELTA QSO PARTY

Starts: 2000 GMT Saturday,
September 27
Ends: 0200 GMT Monday,
September 29

The sixth annual Delta QSO Party is sponsored by the Delta Division of the ARRL and all amateurs are invited to participate. There are no operating or power restrictions. Amateurs outside of the Delta Division will attempt to contact as many amateurs inside of the Delta Division (Ark - La - Miss - Tenn) as possible. Delta Division stations will attempt to contact as many amateurs as possible both inside of and outside of the Delta Division. The general call will be "CQ Delta QSO Party" on SSB and "CQ Delta" or "CQ Test" on CW.

EXCHANGE:

Send QSO number, RS(T), and QTH (ARRL section for non-Delta Division stations - county and state for Delta Division stations). Portables and mobiles may be reworked on the same band/mode if they change counties.

FREQUENCIES:

CW: 3550, 7050, 14050, 21050, 28050. SSB: 3990, 7290, 14290, 21390, 28590. Novice: 3725, 7125, 21125, 28125.

SCORING:

Delta Division - number of QSOs times the number of ARRL sections (max. 75) equals final score. Outside Division, number of QSOs times the number of counties worked (max.

Continued on page 166



CONTEST CALENDAR

Aug 30-31	Ohio Interstate QSO Party	Oct 11-12	CD Party - Phone
Sept 6-7	ARRL VHF QSO Party	Oct 11-12	VK/ZL/Oceania CW
Sept 6-7	Savaria CCS Contest	Oct 15-16	YL Anniversary Party - CW
Sept 6-8	Four Land QSO Party*	Oct 18-19	CD Party - CW
Sept 6-8	Maryland/D.C. QSO Party	Oct 19-20	Manitoba QSO Party
Sept 7	Tu-Boro RC 2m RTTY Contest	Oct 25-26	CW WW DX Phone Contest
Sept 13-14	CLARA Day Contest	Nov 1-3	North Carolina QSO Party
Sept 13-14	European DX Contest - Phone	Nov 6-7	YL Anniversary Party - Phone
Sept 13-14	Pennsylvania QSO Party	Nov 7-10	IARS/CHC/FHC/SWL- CHC/HTH QSO Party
Sept 13-15	Washington State QSO Party*	Nov 8-9	European RTTY Contest
Sept 17-19	YL Howdy Days	Nov 8-9	ARRL Sweepstakes - CW
Sept 20-21	Scandinavian CW Contest	Nov 22-23	ARRL Sweepstakes - Phone
Sept 20-21	VE/W Contest	Nov 29-30	CQ WW DX CW Contest
Sept 27-28	Scandinavian Phone Contest	Dec 6-7	160 Meter Contest
Sept 27-29	Delta QSO Party	Dec 6-7	TOPS CW Contest
Oct 1-Nov 30	RTTY Art Contest	Dec 13-14	10 Meter Contest
Oct 4-5	California QSO Party	Dec 31	Straight Key Night
Oct 4-5	Rocky Mountain QSO Party		* = described in previous issue.
Oct 4-5	VK/ZL/Oceania Phone		

SPECIAL REQUEST

Now that this contest calendar is underway, I will attempt to list information each month on as many different contests and special events as I can. I will also be listing results for various contests, as space permits. Please send all information on contest announcements, special events, and results directly to me:

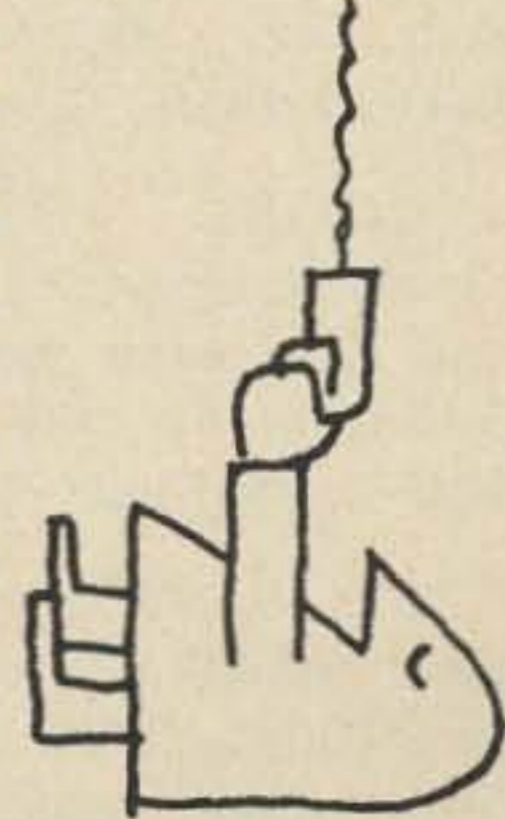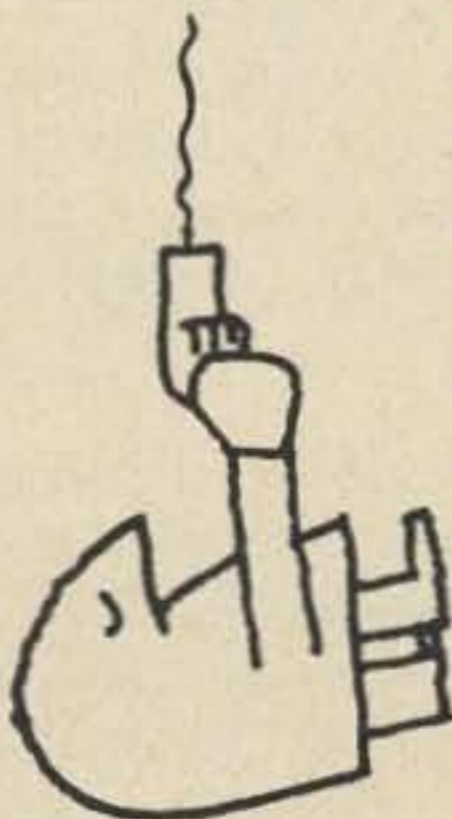Robert Baker WA1SCX
34 White Pine Drive
Littleton MA 01460 USA



Caveat Emptor?

PRICE — \$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order. Deadline for ads is the 1st of the month two months prior to publication. For example: January 1st is the deadline for the March issue which will be mailed on the 10th of February.

We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue. For \$1 extra we can maintain a reply box for you.

WANTED — Make, Model and Serial number of stolen ham gear for big list. W7UD, 3637 West Grandview, Tacoma WA 98466.

NEW VHF Engineering RPT 144-Kit for sale first \$300 takes it. (I won it at Dayton) 419 447-2212 or R. Wright, 185 South Washington, Tiffin OH 44883.

HEATHKIT SB-303 receiver, very good condition, no modifications. Factory-aligned and includes CW filter. \$275 or best offer. Kurt Nilles, 115 Nevada, Dubuque IA 52001.

VERY INTERESTING! Next 5 issues \$1. "The Ham Trader," Sycamore IL 60178. (Ask about our "HAM EQUIPMENT BUYERS GUIDE" covering receivers, transmitters, transceivers, amplifiers 1945-75. Indispensable!)

CINCINNATI HAMFEST: 38th annual — Sunday, September 21, 1975 at the New Stricker's Grove on State Route 128, one mile west of Ross (Venice), Ohio. Flea market, contests, model aircraft flying, food and beverages all day. Advanced tickets \$7.00, covers everything; \$8 at gate. For tickets or further information: Carl J. Dettmar W8NCV, 8630 Cavalier Drive, Cincinnati OH 45231.

CLEANING SHACK — HW-101, Gonset Communicators, Old QST, 73 and CQ, many more goodies. Send SASE for list. K8ILR, 257 National NW, Grand Rapids MI 49504.

FREE: 8 EXTRA CRYSTALS of your choice with the purchase of a new ICOM IC-22A at \$249. With the 10 crystals which come factory

installed in the IC-22A, this gives you a total of 18 crystals! For equally good deals on Kenwood, Drake, Collins, Ten-Tec, Swan, Atlas, Midland, Standard, Regency, Tempo, Alpha, Genave, Hy-Gain, CushCraft, Antenna Specialists, Hustler, Mosley, and others, write or call HOOSIER ELECTRONICS, your ham headquarters in the heart of the Midwest, and become one of our many happy and satisfied customers. HOOSIER ELECTRONICS, P.O. Box 2001, Terre Haute, Indiana 47802. (812) 894-2397.

HP-65 USERS exchange ideas, programs, methods. Monthly newsletter. Request information and sample newsletter. Richard Nelson, 2541 W. Camden Pl, Santa Ana CA 92704.

HEATH SB-301, SB-401, factory aligned. Motorola 6/12 V 2-meter mobile (T43GGV-5) all w/manuals, extras. Make offers. Charlie Wood, 1963 Douglas Dr., Tawas City, Mich., 48763.

SWAN 250C, 6-meter transceiver with P/S speaker, remote VFO, noise blanker & TV2D 2-meter transverter. Mint condition. K3IPM 215 355-2867.

CRUNCHER!! 300 Watts output on 2 meter FM. Motorola AM-494/GR amplifier with T43 transceiver and supplies. Offers? Trades? W9HAJ, 1200 Arundel, Kokomo, Ind. 46901. (317) 452-8971.

FREE BARGAIN CATALOG. LEDs, Xtals, Microphones, Headsets, ICs, Relays, Ultrasonic Devices, Precision Trimmer Capacitors, Unique Components. Low, Low Prices! Chaney's, Box 15431, Lakewood, Colo. 80215.

COLLINS: 30S-1 2KW amplifier excellent operating and physical condition, trade for Bendix R-1051B/E receiver same condition. Sid Sidman, 3571 Gresham Court, Pleasanton, California 94566.

HW-12 \$90; HW-22 \$95; HP-13 P. supply \$45; SR42 \$60; BC-221 \$35; TS-175 \$60; "LDS" mobile ant \$18; F.O.B. Yoakum, Texas 77995, K5QJS.

AMAZING, NEW, UNIQUE, EASY, method of mastering the Morse Code. Fully guaranteed. Send \$5.95 to GENERAL, Dept-978, Box 137, Northridge CA 91324.

SELL: G.E. Voice Commander on 31-91. New case, spare nicad pack, charger. Best offer over \$50.00. P. Smith WB9JSE, 7723 W. Bender Ave., Milwaukee WI 53218.

MEMPHIS is beautiful in October! The Memphis Hamfest, bigger and better than ever, will be held at State Technical Institute, Interstate 40 at Macon Road, on Saturday and Sunday October 4 and 5. Demonstrations, displays, MARS meetings, flea market, XYL entertainment, prizes. Informal dinners Saturday night. Dealers and distributors welcome. Talk-in on 3980, .34-94 and MARS. Contact Harry Simpson W4SCF, Box 27015, Memphis TN 38127 or telephone (901) 358-5707.

COLLINS 30S-1, excellent, new 4CX-1000A, \$1050, alpha 374, brand new, in warranty \$975, Techtronics 310A with cart \$250. Sid Sidman, 3571 Gresham Ct., Pleasanton, Calif. 94566.

VIDICON 7038 — \$15.00; 7262A — \$15.00; 8844 — \$20.00; Peterson 50 MHz Scanner — \$25.00. WB2GKF, Stan Nazimek, 506 Mount Prospect Avenue; Clifton, New Jersey 07012.

WALL TO WALL Drake R4-A, T4-X, AC-3, and MS-4 \$675 postpaid USA, KG4CB, Satellite Communications Detachment, FPO New York NY 09593.

MOTORHOME for sale. 25 ft. Sportscoach (RB) — 1973 — excellent condition — many extras. Antennas — 2 mtr. TV, (2) HF — 4 KW generator, sleeps six. \$1,500 down, assume loan. Send SASE for more info. W6KHS, 212 Magellan St., Capitola CA 95010.

MOTOROLA TWIN V: Like new, gray wrinkle finish case, output meter built-in, power supply permits use on 110VAC, 12VDC or 6VDC. 2 meter transceiver has 16/76, 22/82, 94/94. Was asking \$165.00, will take \$135.00. First cashier's check gets shipment same day. M. T. Henry, 5173 North Hampton Ridge, Norcross, Georgia 30071.

Continued on page 170

AMSAT CONSIDERING SHORT-LIFE HF SATELLITE

While work is progressing on a near synchronous VHF long-life satellite, AMSAT is considering a low orbiting (225 nautical miles) high frequency satellite. Basically, AMSAT would supply the command and control equipment for a bicentennial satellite which would feature a zero order magnitude flashing light prepared by the Brevard County, Florida, Bicentennial Commission. The light would be in operation July 4, 1976. Because a low orbit is necessary for the light, a VHF translator would be impractical. Tentative plans call for a translator with an input on 21.2 to 21.3 MHz and a ten meter output.

Availability in July, 1976 necessitates a March, 1976 launch, leaving precious little time for circuit development; however, it is hoped that this satellite will act as a proving ground

for several sections of the next complex VHF satellite. To meet this goal, several new projects have begun, including an analog telemetry unit under design by WIGBO.

AMSAT-OSCAR 7 HAS A MIND OF ITS OWN

Occasionally Oscar 7 switches modes by itself. This causes considerable work for the command stations, as it is then necessary to reset the satellite into the correct mode and insure the internal 24 hour clock will switch modes at 0000Z.

If you are waiting to acquire the satellite's downlink and it is late, check the other downlink. You could find yourself in the enviable situation of being one of only two or three stations on the satellite. This situation provides armchair copy QSOs. If you should observe a mode switch, it would be appreciated at AMSAT if

you note the time, orbit number and other pertinent conditions that might help AMSAT determine the cause of this phenomenon.

OSCAR 6 BATTERIES DROP TO LOW VOLTAGE

As the satellite sees the sun for the smallest period of its orbit during June, the battery voltage on Oscar 6 dropped dangerously low just before Field Day activities. To insure that Oscar 6 would be operational for all of Field Day, it was turned off several days prior to the event. As the summer wears on, each day the satellite will see more and more energy-giving sunlight, until the maximum sunlight per orbit is reached in February.

UNEXPLAINED NOISE REMAINS ON OSCAR 7 MODE B OUTPUT

Although the Oscar 7 Mode B translator (432.150 to 145.950) is functioning well, occasionally unexplained noise is transmitted to the ground in sections of the passband on two meters. Because the noise comes and goes during different parts of the orbit, this phenomenon has been difficult to identify with any specific cause. AMSAT welcomes your comments and observations as to the cause of the noise, as well as any data you might have which substantiates your conclusions (such as correlation to radars, solar activity, aurora, magnetic storms, etc). Write AMSAT, Box 27, Washington DC 20044.

OSCAR SLIDE SETS AVAILABLE

K6PGX is offering a set of 21 slides, which includes a photo of the launch of Oscar 7, for \$5.40 postpaid. His address is Norman Chalfin K6PGX, PO Box 463, Pasadena CA 91102. All proceeds go to AMSAT and help build future satellites.

Oscar 6 Orbital Information				Oscar 7 Orbital Information				
Orbit	Date (Sept)	Time (GMT)	Longitude of Eq. Crossing °W	Mode	Orbit	Date (Sept)	Time (GMT)	Longitude of Eq. Crossing °W
13153	1	0113.5	69.1	B	3625	1	0056.6	64.0
13165	2	0013.4	54.1	A	3638	2	0150.9	77.6
13178	3	0108.4	67.8	BX	3650	3	0050.3	62.4
13190	4	0008.3	52.8	A	3663	4	0144.5	76.0
13203	5	0103.2	66.5	B	3675	5	0043.9	60.8
13215	6	0003.2	51.5	A	3688	6	0138.2	74.4
13228	7	0058.1	65.2	B	3700	7	0037.5	59.2
13241	8	0153.0	79.0	A	3713	8	0131.8	72.8
13253	9	0052.9	64.0	B	3725	9	0031.1	57.6
13266	10	0147.9	77.7	AX	3738	10	0125.4	71.2
13278	11	0047.8	62.7	B	3750	11	0024.8	56.0
13291	12	0142.7	76.4	A	3763	12	0119.0	69.6
13303	13	0042.7	61.4	B	3775	13	0018.4	54.4
13316	14	0137.6	75.2	A	3788	14	0112.7	68.0
13328	15	0037.5	60.1	B	3800	15	0012.0	52.8
13341	16	0132.5	73.9	A	3813	16	0106.3	66.4
13353	17	0032.4	58.9	BX	3825	17	0005.6	51.2
13366	18	0127.3	72.6	A	3838	18	0059.9	64.8
13378	19	0027.3	57.6	B	3851	19	0154.2	78.4
13391	20	0122.2	71.3	A	3863	20	0053.5	63.2
13403	21	0022.1	56.3	B	3876	21	0147.8	76.8
13416	22	0117.1	70.1	A	3888	22	0047.2	61.6
13428	23	0017.0	55.0	B	3901	23	0141.4	75.2
13441	24	0111.9	68.8	AX	3913	24	0040.8	60.0
13453	25	0011.9	53.8	B	3926	25	0135.1	73.6
13466	26	0106.8	67.5	A	3938	26	0034.4	58.4
13478	27	0006.7	52.5	B	3951	27	0128.7	72.0
13491	28	0101.7	66.2	A	3963	28	0028.0	56.8
13503	29	0001.6	51.2	B	3976	29	0122.3	70.4
13516	30	0056.5	65.0	A	3988	30	0021.7	55.2

amsat


Gary Tater W3HUC, 7925 Nottingham Way, Ellicott City MD 21043



TM

NEW PRODUCTS

The New Clegg

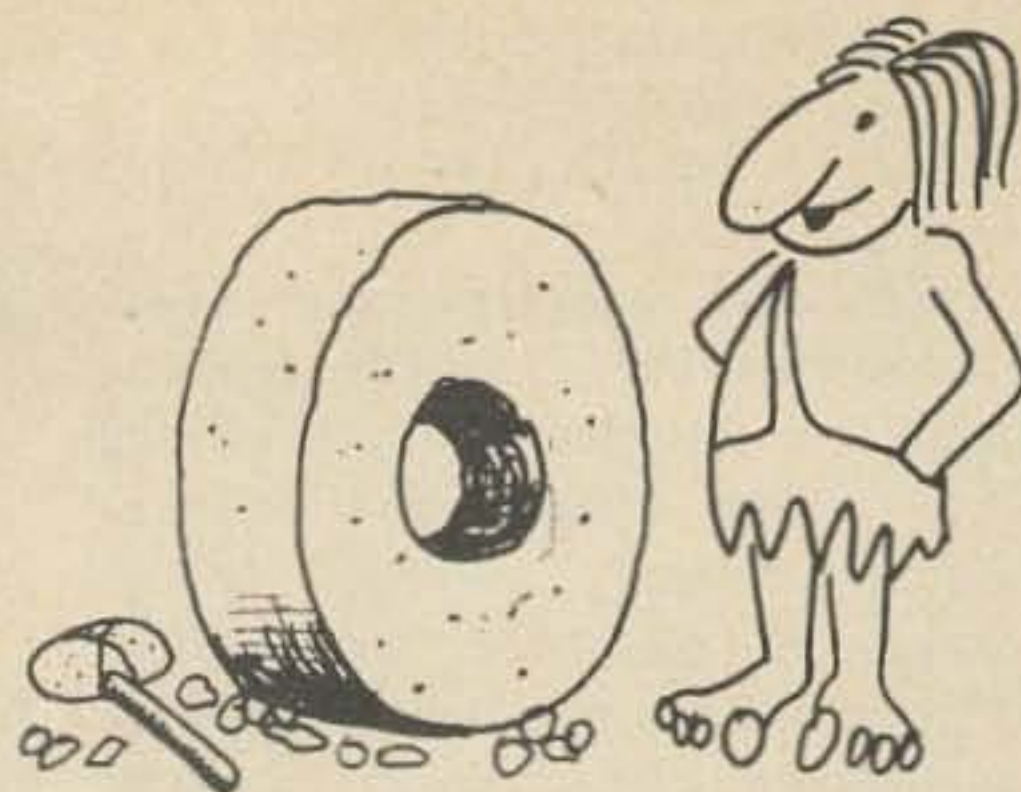

Clegg's response to the encroaching competition is to give more — a lot more. This may be a winning philosophy.

With the filling up of the 146-148 MHz bands, there is more and more interest in being able to flip down below 146 for simplex operation — with the Clegg FMDX you can do this, for it not only covers the two meg repeater band, but also the MARS bands on either end of the two meter ham band — and the MARS chaps have been setting up repeaters too, you know. The FMDX will take you from 143.5 to 148.5 MHz, giving you just about everything you could ask for, including both high and low MARS bands, CAP, the DX part of 2m, and even the Oscar band.

If you are into repeaters at all, and the odds are that you are since over 50% of the active amateurs are using 2m at least part of the time today, you've probably wanted to be able to call in on all of the repeaters in your area . . . and perhaps all those in areas you may visit. This means today that you must be able to have a good deal of flexibility, and it certainly means synthesis. The growing number of "splinter" channel repeaters . . . using the 15 kHz splits . . . has created some problems for early synthesized rig owners where it takes special crystals to hit these channels, and the front panel readout is, to be kind, cryptic. The FMDX covers every 5 kHz of the band, thus giving you all of the splinter repeaters . . . and it will permit you to work those which are avoiding the interference from adjacent channels by being on reversed pairs.

The Clegg system for setting frequency is simple and effective. There is one rotary switch for the megahertz, one for the 100 kHz, one for 10 kHz and a +5 kHz bat handle switch. The readout is like a frequency counter — bright red LEDs indicating the receive or transmit channel. The readout is large enough so you can

read it at a glance while driving — this is one of the easiest rigs yet for mobile use.

The FMDX is set up for 600 kHz splits, but if you have a weirdo in your area with 990 kHz or 1 meg split you can adapt to it by buying a crystal for the new split. The FMDX has a switch on the front panel to permit up to three different extra splits. There's a lot of that wide split stuff going around in New York.

While the chances are that you can do just fine with a ten Watt rig, the fact is that most repeaters run a good deal more than that and you need a little extra zap if you are going to get into downtown areas or out in the country in the valleys. The Clegg runs about 35 Watts output (with a switch for one Watt) and this does a good job of equalizing repeater coverage for you. With ten Watts you often find yourself dropping out and wish for a little more signal, but you may be reluctant to go the price of an amplifier . . . and they aren't cheap.

In operation, the Clegg is a dandy. There is none of the lock-up delay that one popular rig has, so you go from receive to transmit instantly. The receiver has enough power to drive your regular car loudspeaker if you like (plugs into the back and thus disables the built-in smaller speaker). The four pole i-f filter keeps the repeaters from coming in from adjacent channels. The mike gives you excellent quality reports (and some rigs are incredibly bad). The S-meter/power output indicator lights up for mobile use . . . and an S-meter is handy in that it gives you a good indication of how great your chances are of being heard by the repeater.

In order to keep the price on this fantastic package at a level where amateurs can afford it, Clegg has gone to factory-direct sales . . . and the FMDX is certainly an excellent buy at under \$600. You can bet that there will be a lot of the Clegg FMDX units around very quickly.

LINEAR AMPLIFIERS




CR Electronics, in Foster City, California, has introduced their new series of linear amplifiers, which are fully solid state. Two models are available, the CR-150LA, 200 Watt PEP output and the CR-300LA, 400 Watt PEP output. These amplifiers have a frequency range of 1.6 to 30 MHz and they only require a 3-5 Watts drive. Both models are available for amateur use on 80, 40, 20, 15 and 10 meter bands.

COAXIAL COUPLER POWERS ACCESSORIES VIA CABLE

When installed inline on a coaxial cable, Inline Instrument's Type 100 Coupler allows relays, amplifiers, etc., to be powered via the signal cable. Ac, dc, or both simultaneously, may be injected locally and utilized remotely without affecting the original signal characteristics of the coaxial cable. Features include: multi-octave bandwidth; negligible swr and insertion loss; weatherproof construction; and no insertion noise. Two types cover the spectrum from medium frequency through UHF. Power capability is 250 W. Price \$12.50. Write: Inline Instruments, Inc., Box 473, Hooksett NH 03106.

COAXIAL RELAY IS POWERED VIA SIGNAL CABLE

When used with a companion coupler, the coaxial relay derives its control power via the signal cable. Typically, it can be installed on a tower or pole to switch two antennas. Features include swr under 1.1, insertion loss under 1 dB, and weatherproof construction. Selectable control polarity permits multiple relays on a single coaxial line to change antenna patterns or rf loads. Frequency coverage is available from medium frequency through UHF. It will handle minus dBm levels to 150 W. Price \$24.50. Write: Inline Instruments, Inc., Box 473, Hooksett NH 03106.

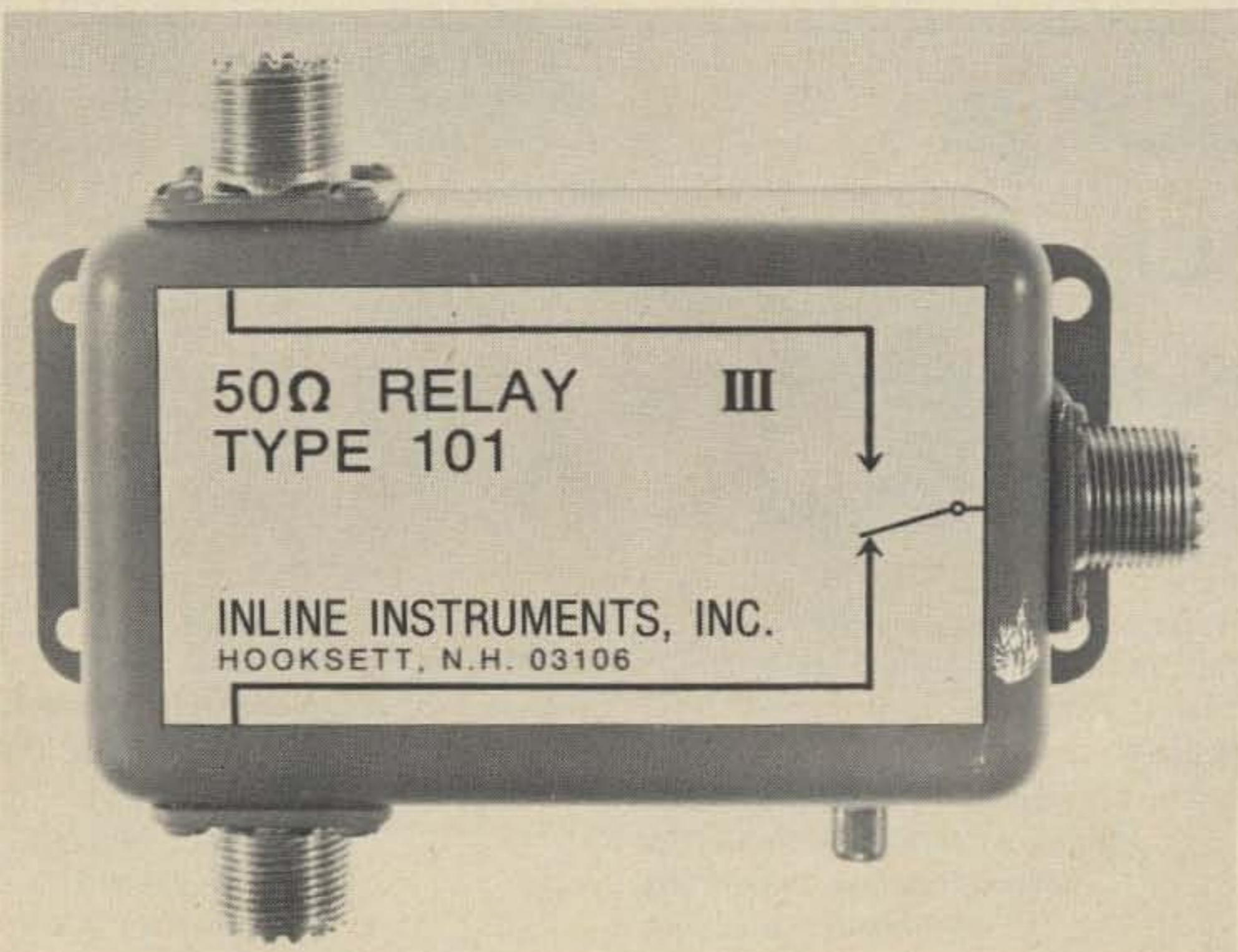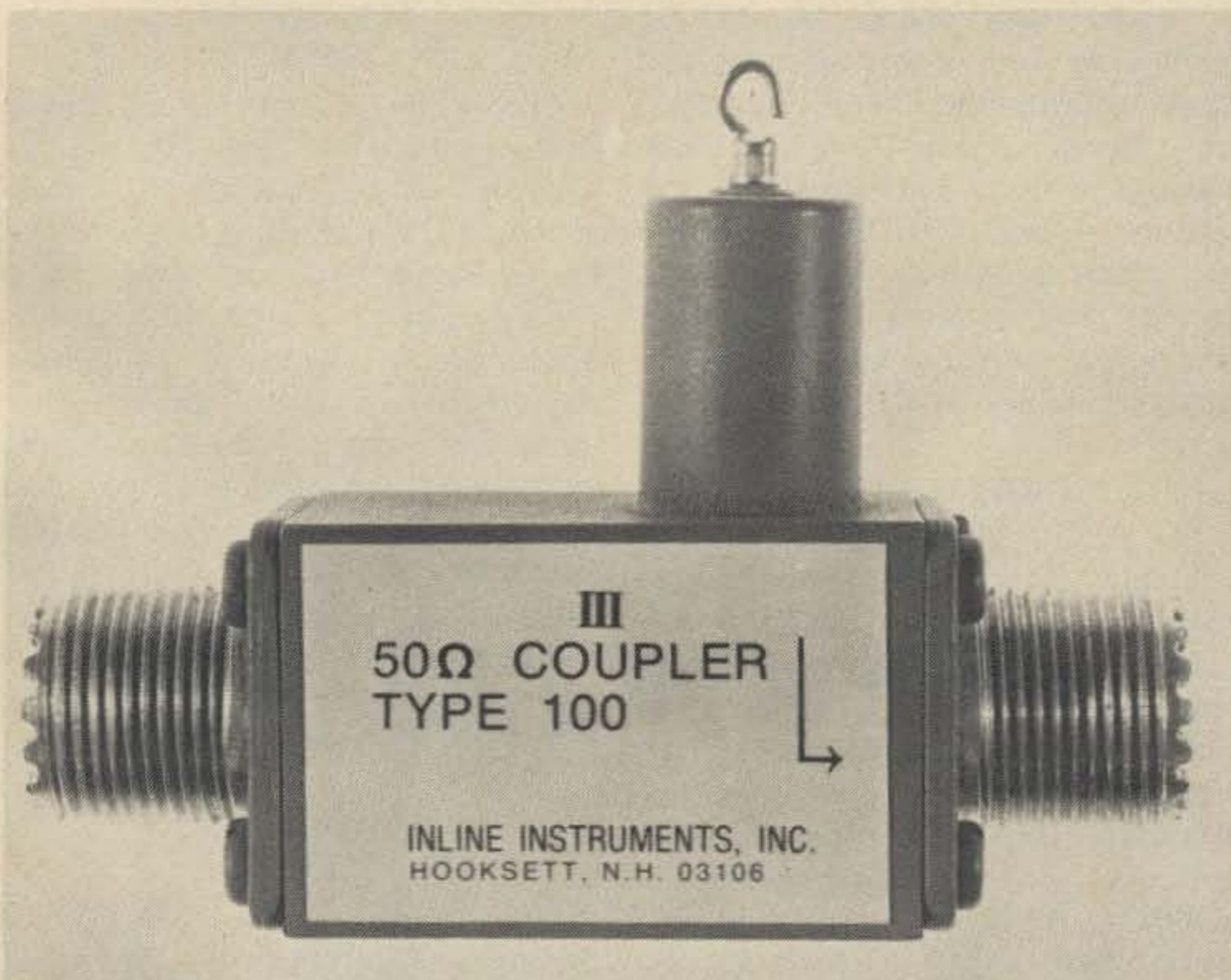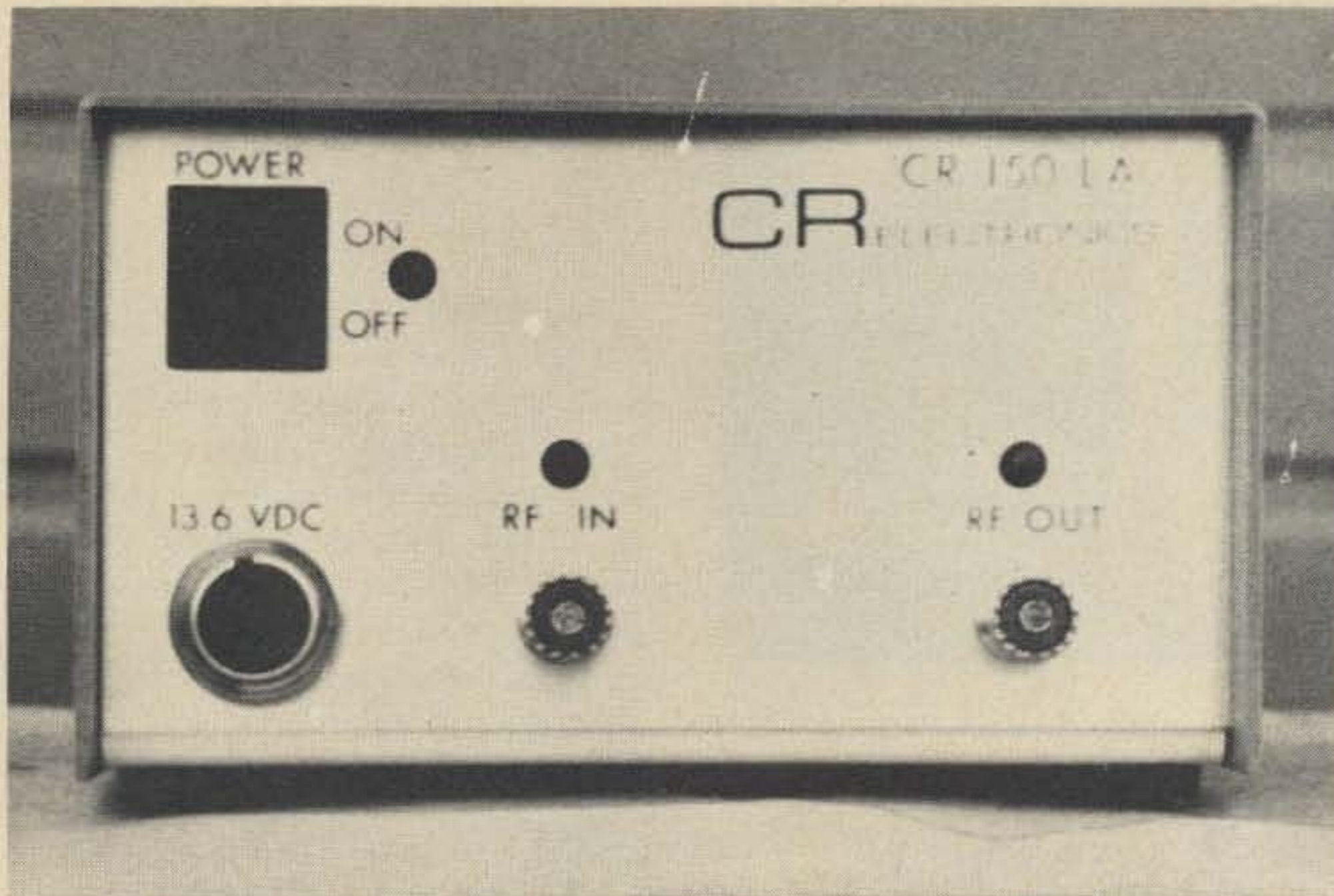

NEW LEADER 5" HORIZONTAL DUAL CHAN/DUAL TRACE SCOPE


The LBO-552 is a solid state dual channel/dual trace oscilloscope/vectorscope which provides a simultaneous left/right wave form display to make general purpose measurements and audio testing easier than ever, according to the manufacturer, Leader Instruments Corp., Plainview NY.

This new 20 mVp-p/cm sensitivity dual channel instrument permits the user to view 2 independent signals simultaneously — and side by side on a bright CRT display. It provides 2 separate vertical gain controls for independent and joint operation and also features a single channel display for conventional testing. Vertical bandwidth is dc or 2 Hz to 1.5 MHz. Sweep speeds are from 10 Hz to 100 kHz in 4 ranges, with an input impedance of 1 mΩ shunted by 40 pF. Phase differences on the X-Y axis are below 2° at 20 kHz and below 8° at 100 kHz. Left/right channel accuracy level is ±3%.

Among its many uses, the LBO-552 is said to be ideal for inspecting and aligning sophisticated stereo equipment including amplifiers, receivers and tape recorders as well as car stereos. It is also useful for on-line production and quality control testing. It measures 9-5/8"H x 6-7/8"W x 15"D and weighs approximately 15.5 lbs. Selling for \$399.95, it operates on 100, 115, 215 or 230 V power, as specified, 50/60 Hz; approximately 20 VA.

Continued on page 160



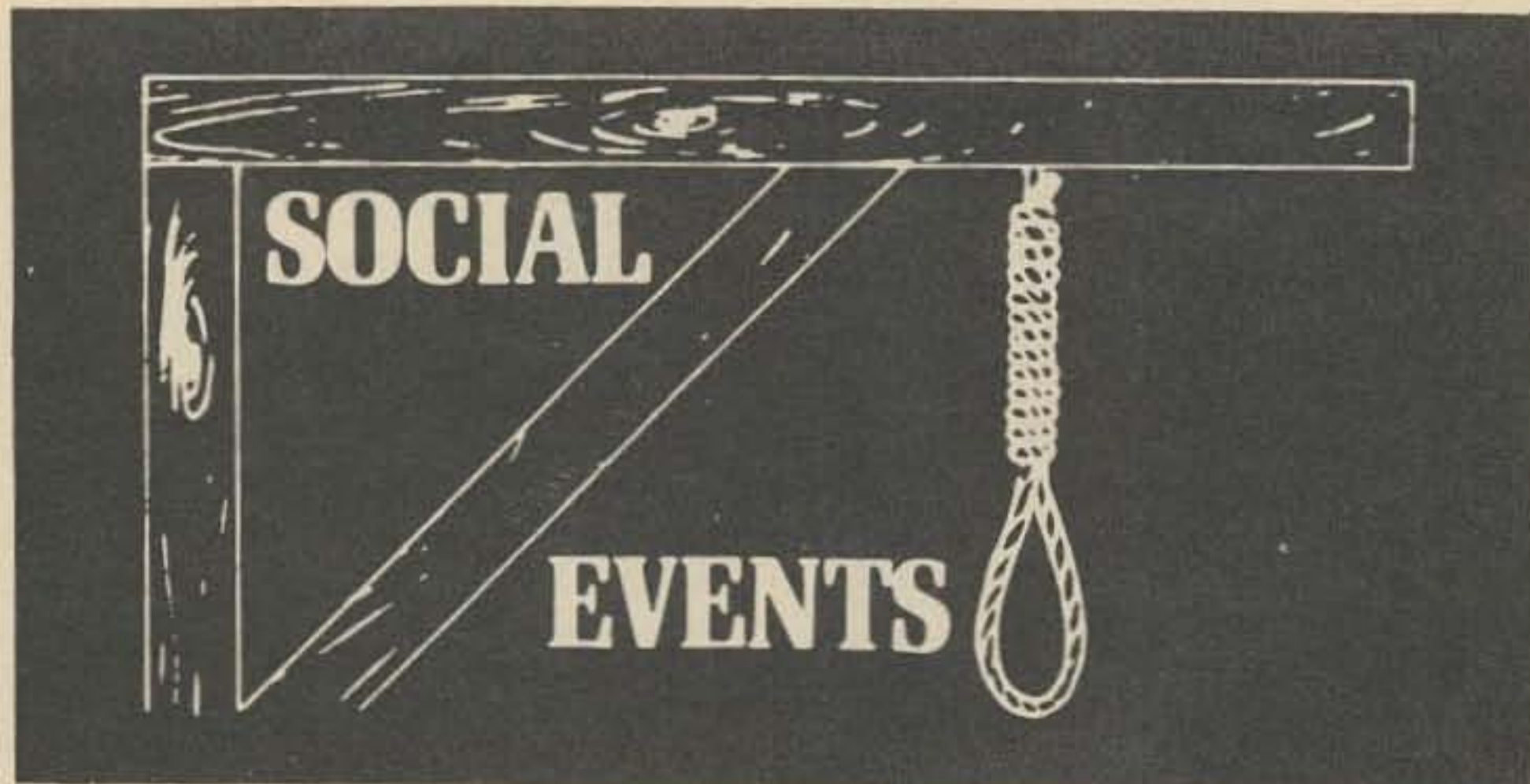

**MONCTON NEW BRUNSWICK
AUG 29-SEPT 1**

The Moncton Area Amateur Radio Club will sponsor the Atlantic Canada ARRL Amateur Radio Convention, August 29 - September 1, 1975 at the Hotel Beausejour, Moncton, New Brunswick. Exhibits, technical forums conducted by ARRL Headquarters personnel, VHF forum, swap shop, buffet Saturday night followed by dance, dinner and entertainment Sunday night, hidden transmitter hunt, etc. Talk-in on 146.28 - 88 and 146.52 simplex. For full information, write: Moncton Area Amateur Radio Club, P.O. Box 115, Moncton, N.B.

**SAN FRANCISCO CA
AUG 29-SEPT 1**

The Quarterly NORCAL DXers (Northern California DXers) gabfest will be held Labor Day weekend at the El Rancho Inn, 1100 El Camino Real, Millbrae CA 94030. \$1 reg. at door. Emphasis on SWL DXing. Technical sessions, displays, quiz, auction and free refreshments. Door prizes. For more info write NORCAL, Rick

Heald, 17412 Rolando Avenue, Castro Valley CA 94546.

**MELBOURNE FL
SEPT 6-7**

PCARs 10th annual Hamfest at Melbourne Auditorium, Saturday and Sunday, September 6 & 7, 9 am to 5 pm. Prizes galore, exhibits, swap-tables, auction, Floridora's, QCWA and much more. First prize complete 40' crank-up tower, tri-band beam, rotator and coax and many more prizes. For more info write Box 1004, Melbourne, Florida 32901.

**GRAYSLAKE IL
SEPT 6-7**

Radio Expo '75 will be held September 6-7 in Grayslake, Illinois at Lake County Fair Grounds, Intersection Rts. 45 & 120. Thousands of dollars in door prizes, state of the art displays by major manufacturers, spacious, all-weather flea market, informative technical movies and seminars. Acres of free parking, free camp area and full food service. Tickets - \$2 for both days, \$1.50 in

advance. Children under 12 free. Write to: Radio Expo Tickets, Box 1014, Arlington Hts. IL 60006.

**MENA AR
SEPT 6-7**

The Queen Wilhelmina Hamfest '75 is Saturday and Sunday, September 6 & 7 at Queen Wilhelmina State Park, Rich Mountain, Mena, Arkansas. Excellent accommodations and food at newly restored historic Queen Wilhelmina castle. Door prizes hourly, grand prize, new equipment displays, flea market, camping area with utilities and rest rooms, amusements for harmonics. Talk-in 146.52-3995. For more information write WB5GZR.

**MALAGA NJ
SEPT 7**

The 27th annual South Jersey Radio Association hamfest will be held on Sunday, September 7, starting at 10 am rain or shine at the Molia Farms Picnic Grounds, Malaga, N.J. (intersection of Routes 42 and 47). Swap shops, electronic equipment displays, prizes, ladies' games, swimming, you name it. Family picnic area with tables and outdoor grille; food may be purchased also. Free parking. Talk-in on 146.52 MHz FM Simplex. Advance reg. \$2.50; \$3.50 at the gate. For info or tickets write: Jack Koch K2MZP, 1980 Greentree Rd., Cherry Hill NJ 08003, SASE please.

**FINDLAY OH
SEPT 7**

The Findlay Hamfest will be held September 7, 1975 at Riverside Park, Findlay, Ohio. For advance drawing

additions
and
~~corrections~~
corrections

Please note these corrections on the item "Thirteen Billion Watts ERP?" which appeared on pages 4 and 5 of the July 1975 issue. They were pointed out to me by Lou Breetz, and have also been sent to *Auto-Call*.

The continuous rf power output should be 1 Megawatt, not 10 Mega-

watts, and the angular thickness of the fan pattern is 1.25 minutes from North to South, rather than 1-1/2 degrees.

Edwin P. Westbrook K3CS
Chairman, Publicity Committee
Naval Research Laboratory
Amateur Radio Club

Regarding my article, "How Gates Work" (July, 1975, page 113), many readers have spotted an error and brought it to my attention. On page 115, Table 9 *should* read as follows:

A	B	C	D	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
.
.
.

My only consolation (and a slight one at that) is that the readers apparently understood the article enough to find the mistake.

Larry Kahaner WB2NEL
4259 Bedford Ave.
Brooklyn NY 11229

tickets write Clark Foltz W8UN, 122 W. Hobart, Findlay OH 45840.

**PEORIA IL
SEPT 14**

The Peoria Area Amateur Radio Club's 18th Annual Hamfest will be held Sunday, September 14, at the Exposition Gardens, same place as last year. The site is located on Northmoor Road just west of University Avenue, at the northwest edge of Peoria. Lunch will be available, and there are activities for the entire family. Free swap session, parking, contests, cartoons for the children and many prizes. Advance registration \$1.50 (\$2 at gate). Banquet on Saturday, September 13, at V. Junction, \$6 per person. For banquet reservations, write Larry Pearsall W9FDY, 2224 W. Herold Avenue, Peoria, Illinois 61604. For Hamfest tickets, write Earl R. Kimzey WA9SCA, RFD 1, Hanna City, Illinois 61536.

**HARRISBURG PA
SEPT 14**

Hamfest, sponsored by the Central Pennsylvania Repeater Association, will be held Sunday, September 14, 1975 at the Park-n-shop Parking Garage, 200 Block Walnut Street, Harrisburg, Pa. Gates open 9 am. Registration: \$3 per ham — XYLs free — no charge for tailgating. Food available. Talk-in 146.16/.76 WR3ABV .94/.94. For more information contact W3ABF or WA3AVX.

**SHARON MA
SEPT 17**

The Sharon Amateur Radio Association is holding its annual auction on September 17, 1975 at 1 pm. At

the Sharon Community center. Free refreshments and doorprizes. 10% commission to club. For further info contact Ed Levine, 6 Carlton Road, Sharon MA 02067. Tel. 617 784-6033.

**HUDSONVILLE MI
SEPT 20**

The Grand Rapids Amateur Radio Association will hold its annual Swap & Shop Saturday September 20, 1975 at the fairgrounds in Hudsonville, Michigan. Food & prizes, \$2.00 at the gate — no charge for tables or trunk sales. Talk-in on 16/76 or 94/94. See you there!!!

**ITASCA IL
SEPT 20**

The 23rd Annual W9DXCC banquet will be held on September 20, 1975 at the Holiday Inn, Irving Park Rd., at I-90, Itasca IL, noon to ?? Contact the Indianapolis DX Assoc., 7008 W 71st St., Indianapolis IN 46278 for further details.

**HAMBURG NY
SEPT 20**

Hamburg International Hamfest will be held September 20, 1975 at the Erie County Fairgrounds. Features giant flea market, tech forums, displays, code contest, organization meetings, picnic facilities, FM hospitality room, women's programs, \$3000 in prizes. Free parking except rec vehicles \$2.50 for weekend. Admission \$2.50 advance, \$3 gate; flea market parking (set-up) \$1. Banquet separate. Directions: NY Thruway to Blasdell Exit 56. Rec vehicles turn right on Mile Strip Rd, then left on Rt 62 So. Follow signs to

fairgrounds. Other vehicles turn left on Mile Strip and right on McKinley Parkway. Talk-in WR2ABU 146.91, simplex 146.94, 7.255, 3.925. Other area repeaters WR2ACA (146.40) 147.00, WR2ADR 146.73. Info write Lin Brownell, 210 Buffalo St., Hamburg NY 14075; (716) 649-3106.

**EL PASO TX
SEPT 20-21**

The El Paso Hamfest will be held at the Vista Motor Hotel (special rates) on September 20-21. Special guest speaker and banquet Saturday night. For information write Charlie Wood WA5KYV, 10012 Suez, El Paso TX 79925. Talk-in on 28-88.

**CINCINNATI OH
SEPT 21**

Cincinnati Hamfest: 38th annual — Sunday, September 21, 1975 at the New Stricker's Grove on State Route 128, one mile west of Ross (Venice), Ohio. Flea market, contests, model aircraft flying, food and beverages all day. Advanced tickets \$7, covers everything; \$8 at gate. For tickets or further information: Carl J. Dettmar W8NCV, 8630 Cavalier Drive, Cincinnati OH 45231.

**TEWKSURY MA
SEPT 21**


The 19-79 Repeater Association's second annual Clambake Hamfest is being held Sunday, September 21, at the Tewksbury Rod and Gun Club, 11 Chandler St., Tewksbury MA (off route 38 across from the Tewksbury State Hospital). Talk-in 19-79 and 52 direct. Lobster dinner — \$8 per

Continued on page 76


I have had a lot of response from the article "Homebrew This SSTV Monitor," which appeared in *73 Magazine*, June 1975, page 22, and I would like to add a few comments to the article.

Circuit Error:

Was

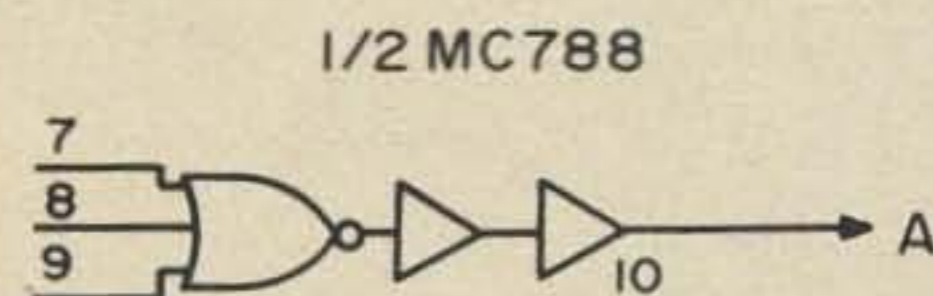

Change to

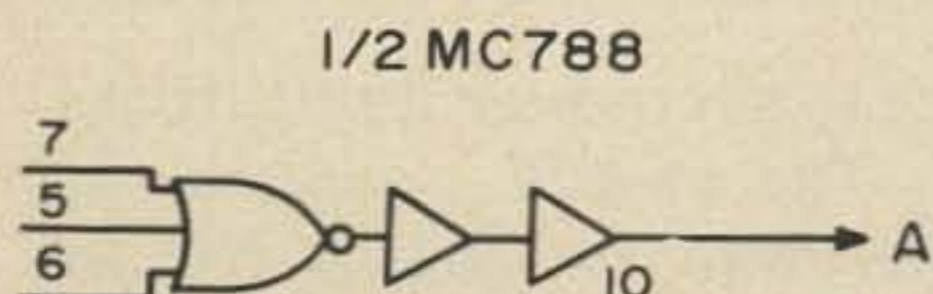

Transistors:

All transistors, NPN and PNP, are general purpose, silicon type, except where noted.

Diodes:


All small signal diodes are 1N914 or equiv. Power supply diodes are 1 kV type such as 1N4007.

Power Supply:

Add the 150 V supply —

The 7.5 kV transformer was a one of a kind type. However, suitable power supplies can be used that deliver 5 - 10 kV. For additional schematics I would suggest consulting the SSTV handbook published by *73 Magazine*.

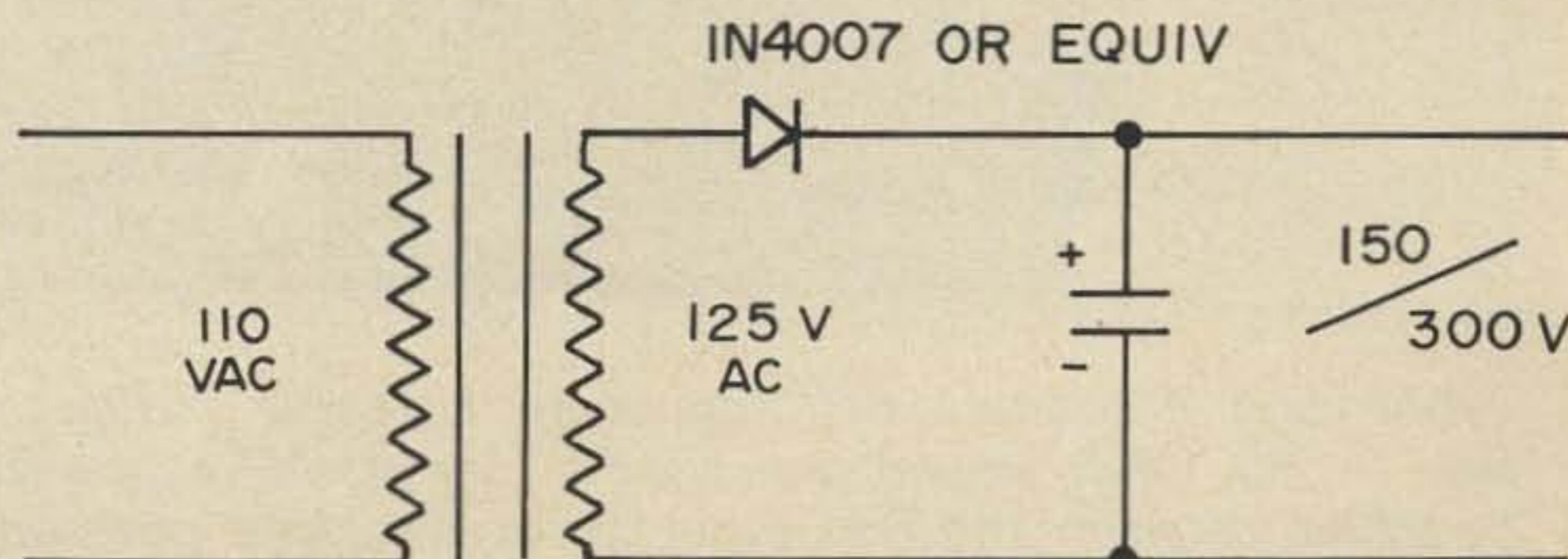Larry Pryor WA9MFF
5940 Carrollton Ave.
Indianapolis IN 46220




Robert Johnson
5707 - 101A Avenue
Edmonton, Alberta T6A 0L9
Canada

The Calculating Counter

And yet another electronic counter article? Yes, but with a difference. Traditional counters provide very limited resolution of audio frequencies associated, for example, with organ and piano tuning.

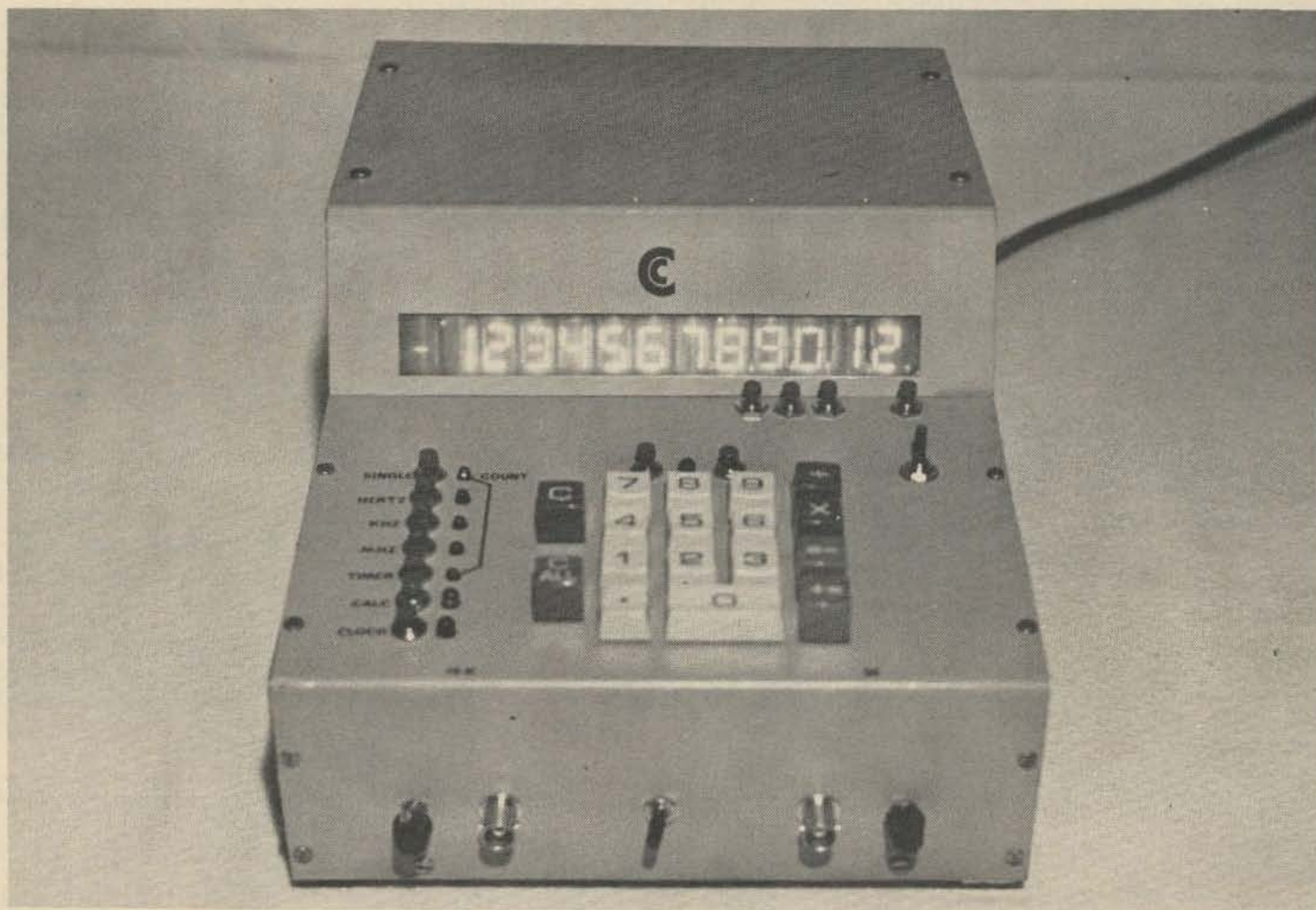The usual one-second gate time yields a reading varying between "59" and "61" for 60 Hz. To determine this frequency with any accuracy, you must measure the period of one cycle (16,666 microseconds), reach



Front view of counter. BNC inputs are: Left side – High impedance counter input; Right side – 50 Ohm impedance counter input, MHz prescaler. The switch transfers the prescaler between the two input jacks. The four push-buttons near the display are the decimal point setting controls.

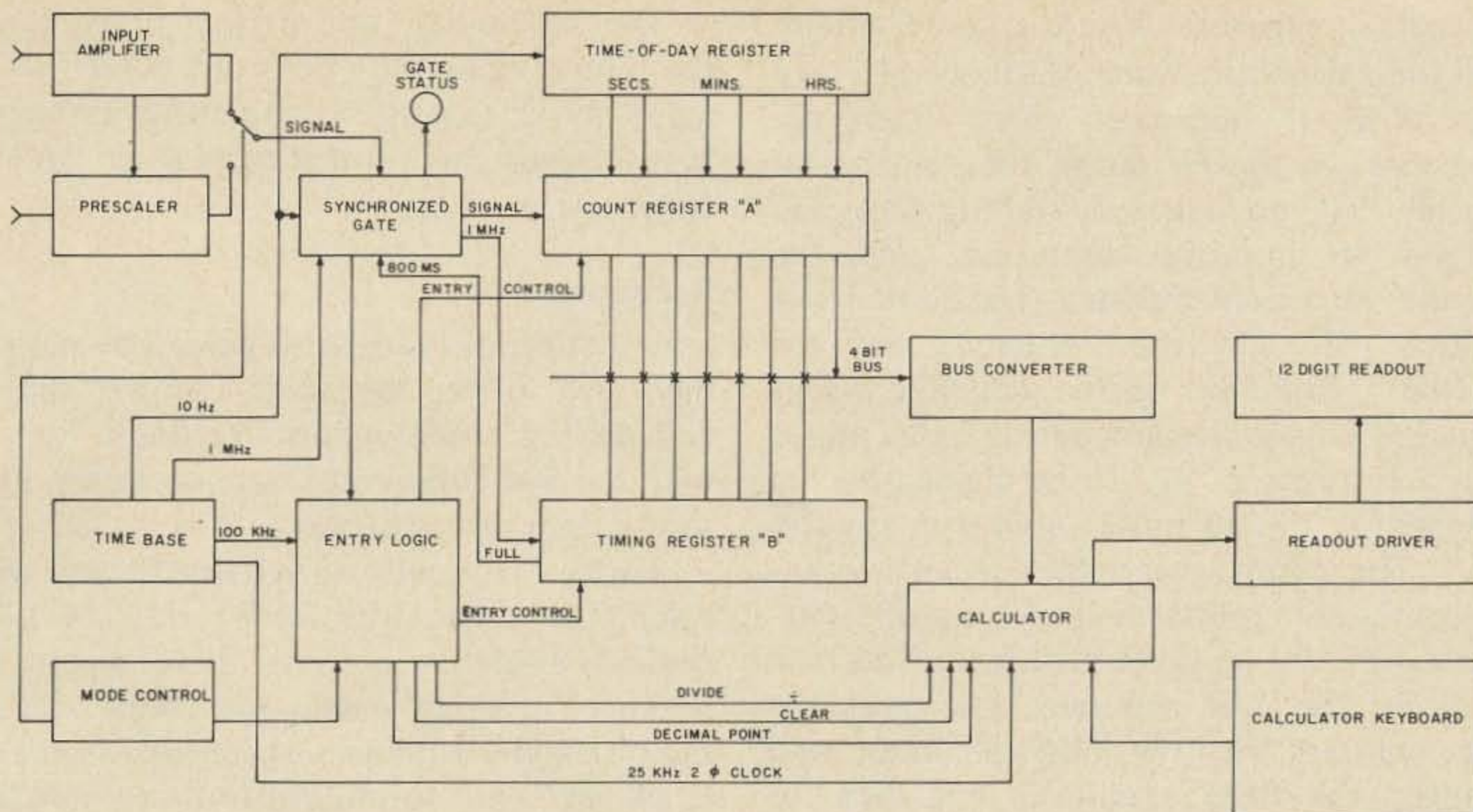


Fig. 1. Block diagram.

for your handy pocket calculator, and calculate the reciprocal (or wait 100 seconds perhaps!).

As our shack wasn't blessed with a handy pocket calculator, we decided to explore the possibility of teaching a counter to calculate frequencies from period measurements. It soon became apparent that designing a circuit to calculate reciprocals was no simple task. A ready-made solution to this dilemma presented itself in one of the "calculator chips" widely advertised at attractive prices. As a bonus, the problem of the missing "handy calculator" was solved as well. The "One-Chip Calculator" advertised as a type 5001 turned out to be both inexpensive and practical. The chip comes in one of two voltage ratings (for desk or pocket calculator use). While we used the low voltage model, which requires -8.5 and -13.5 volt power supplies, the higher voltage unit should be directly interchangeable, with minor power supply modifications.

We wished to construct an all-purpose counter, and our final design includes a basic 30 MHz counter, a high frequency prescaler, a reciprocal calculator, a desk calculator, a digital clock, an interval timer, and an incident counter. All logic circuits are TTL, except for the MOS calculator chip and ECL prescaler. Discrete devices are used for TTL/MOS interfacing and for driving readouts.

Design, construction and debugging of a project of this magnitude is virtually impossible without a test-breadboard facility. It is necessary to breadboard each function, and test it in turn. A suitable power supply is also essential, and we recommend construction of the power supply first, but note that use of different readouts or other components may require modification of the power supply.

Theory of Operation

Overall data and logic flow may be followed by reference to Fig. 1. The frequency to be counted is connected either to the input amplifier (high impedance) or directly into the prescaler (50 Ohms). The prescaler is automatically activated in the MHz mode. Note that the high impedance input may be used in all count modes, and it provides good sensitivity through the two meter band.

The synchronized input gate directs input pulses to register A, an 8 digit decade counter, and timing pulses to register B, a 6½ digit counter. Gate time in kHz and MHz modes is one second (plus or minus one input pulse period), and in the Hz mode varies between 800 milliseconds and 2 seconds (800 milliseconds plus one input pulse period).

When the input gate closes, entry logic is enabled, and in the kHz or MHz modes, the

contents of register "A" are entered serially into the calculator, which displays the entry just as if it had been made from the keyboard. In the Hz mode, the contents of register "A" are entered, trailing zeros are padded to improve resolution, and the "divide" function activated. The contents of register "B" are then entered, and the "divide" function again activated. This sequence causes the number of input pulses stored in register "A" to be divided by the number of timing pulses stored in register "B." The result (with the decimal point appropriately positioned) yields the frequency of the input (with up to 4 decimal places!). The bus converter interfaces the TTL registers with the MOS calculator, and changes the BCD coding of the TTL to conform to the 5001 chip's requirements.

The time-of-day register constantly contains the time, updated each second. Register "A" utilizes decade counters with preset inputs. In the time-of-day mode, once each second, the contents of the time-of-day register are strobed in parallel into register "A" and then serially entered into the calculator as in the kHz mode.

The accumulate and period modes cause the input gate to be controlled either manually or externally, and either timing or input pulses are routed to register "A" as appropriate.

Readouts

Selection of readouts is guided by desired digit size, price, availability, power supply and driving requirements. Readouts for use with the 5001 chip must have decimal points to the right of the digit.

Various readouts are suitable for use with calculator chips. The wide array of LED devices available suggests these would be preferred. Most calculator chips utilize multiplexed readouts, where like-segments of all digits are connected to a common bus line. Each digit is selected (turned on) for a brief period in turn. This driving method reduces wiring and driving hardware, because only eight segment drivers (including the decimal point) and one digit driver per digit are required.

LED readouts may be driven by the newly available 75491 and 75492 Darlington driver arrays; however, as they are NPN

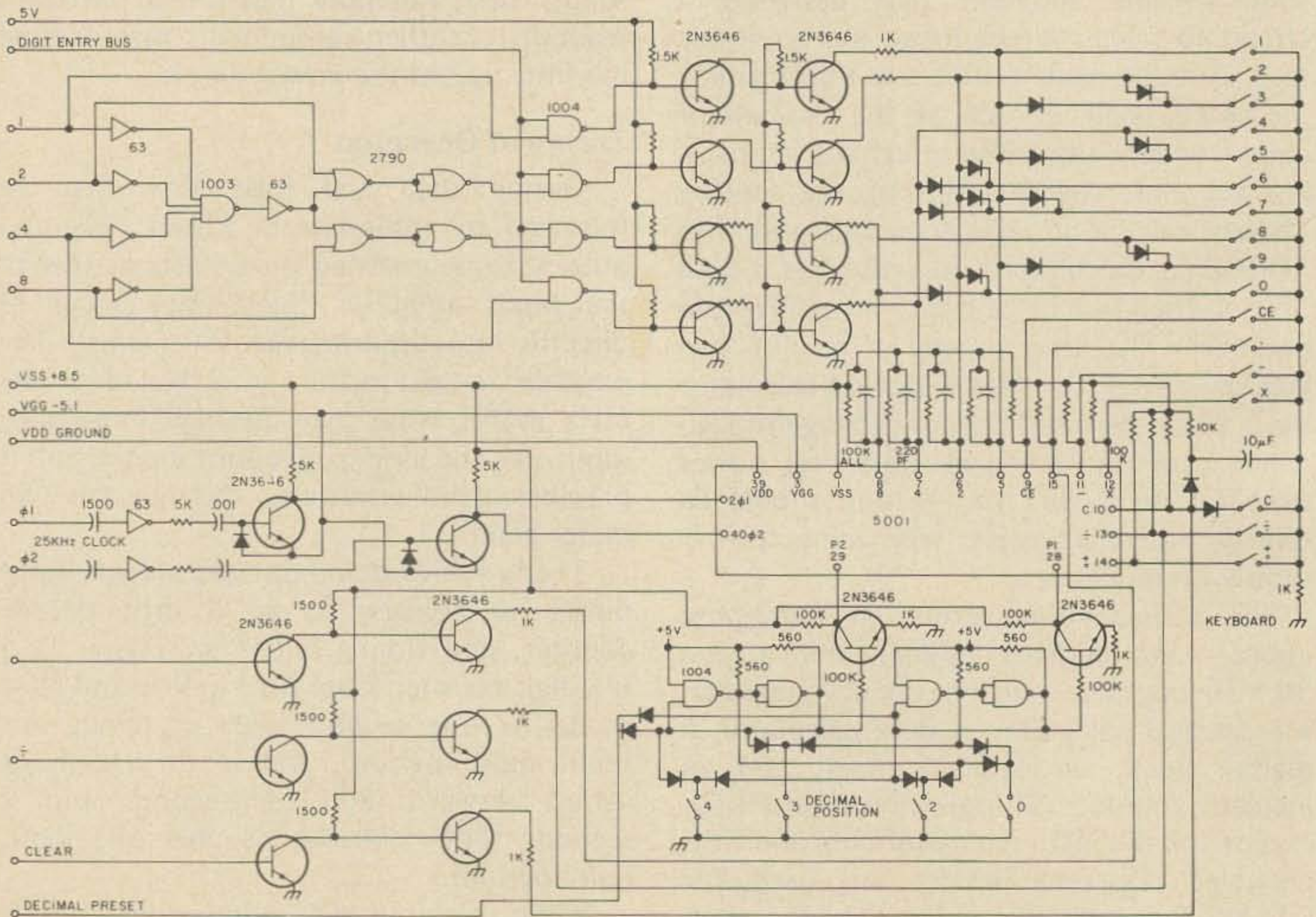


Fig. 2. Calculator Input Circuits.

devices, PNP predrivers may be required. Drivers shown in Fig. 3 are also suitable for driving LEDs, with the addition of limiting resistors.

Incandescent readouts require drivers capable of handling substantial inrush currents. Digit drivers should be selected to handle 500 mA. The author's choice of incandescent readouts was influenced by cost at the time, and size of display. Present LED prices make them much more attractive. Selection of the 2N3569 for drivers was influenced by our junkbox stock, but the 2N2905 (PNP) is probably more suitable. The calculator data sheet shows PNP drivers, and use of the 2N3569 (NPN) requires the circuits of Fig. 3 to make the NPNs think they are PNPs. Diodes are required for isolation between each segment and the segment bus. (This was rather painfully discovered by the author!)

Driving circuits for Nixie and Numitron type readouts are included with the calculator data sheet.

The 5001 chip provides 12 digits, which is handy for calculating, but not really needed for counting. Although fewer than 12 can be used, you must then either provide overflow detection or take a chance on errors. Note also that there are restrictions upon the size of the arguments that the 5001 can handle without overflow. These restrictions cause an overflow if you attempt to calculate the frequency to too many decimal places. (You have the choice of zero, 1, 2, or 4 decimals.)

The Calculator


The 5001 Cal-tex chip widely advertised is probably the most suitable for this application. Data input is modified BCD, and is readily driven from TTL Circuits. The 5005 and several others use multiplexed inputs, which require more complex input interfacing. Although no investigating was done, the 4016 CMOS switches should be suitable for use with multiplexed inputs. The 5001 is available in 2 voltage versions. If you are not sure which version you have, it would be sensible to use the lower voltage supply to test it. Mine turned out to be the 13 volt version. If yours works at the lower voltage, it is a low voltage unit and should not be

tested at the higher voltage. (Murphy's Law must have been temporarily repealed, as mine survived!)

Table 2 lists equivalents of various components used by the writer. We were fortunate to locate a supply of surplus boards, each carrying about 30 TTL NAND gates with open collectors. At about 2¢ per IC, these found favor with the pocket book. (Use of a soldering iron tip designed for their removal is recommended.)

TTL and ECL are devilish creatures unless adequate power supply by-passing is done. The surplus boards noted above also yielded some very handy power bus strips. These are composed of two 3/8" wide strips of copper foil separated by a thin dielectric. Feed terminals are provided at convenient locations which permit short leads to ICs. Even with use of these bus strips, 1.0 mF (miniature electrolytic) and .1 (miniature ceramic disc) capacitors were liberally distributed from +5 volts to ground. A .1 discap across the supply terminals of every TTL and ECL IC is recommended, if you don't use bus strips. Failure to provide these bypass capacitors will result in miscounts at best, and total non-operability at worst.

Fig. 2 shows the various input circuits required for the 5001 chip. Pins 5, 6, 7 & 8

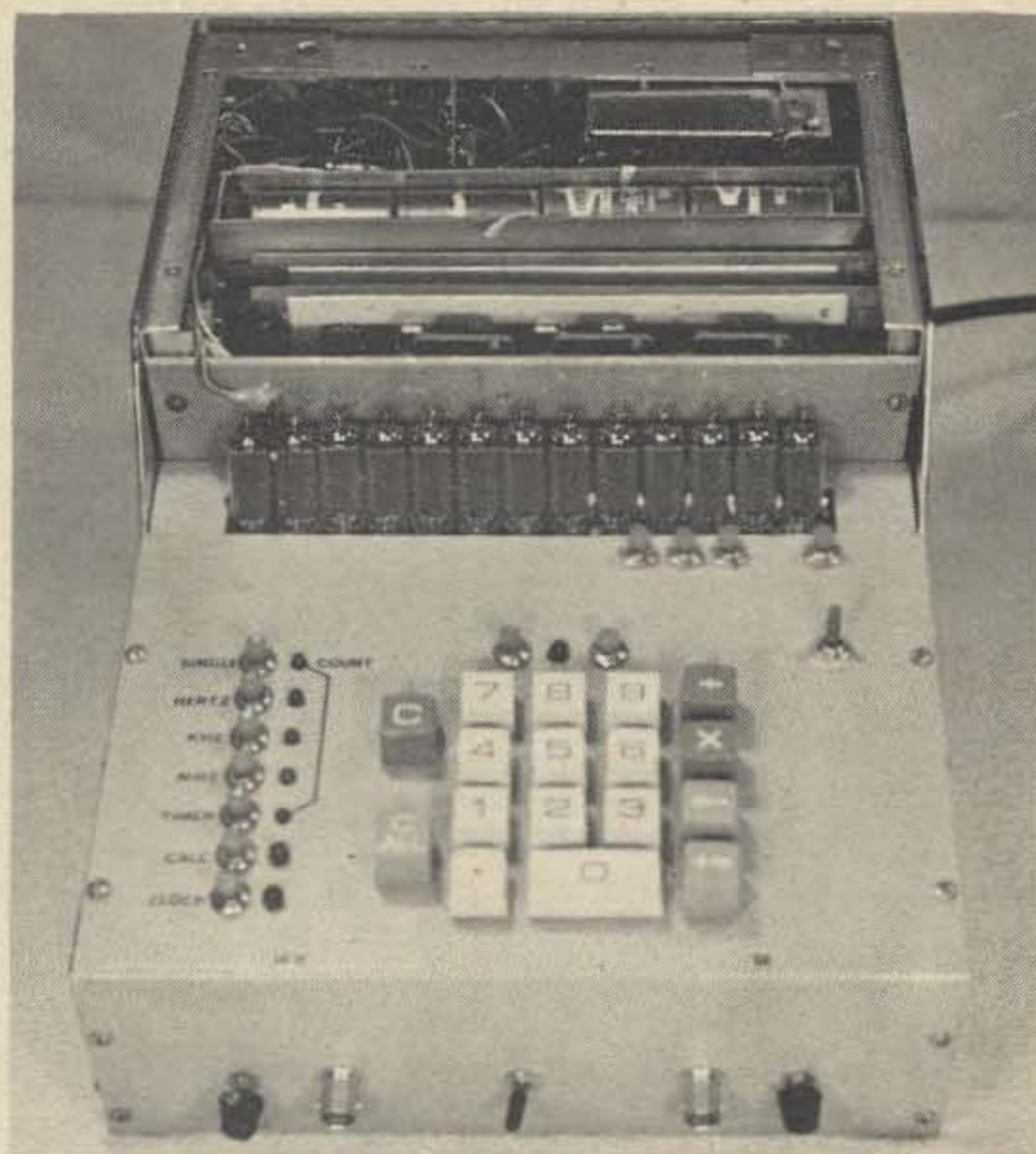

With the top cover removed, the incandescent readouts may be seen. The four Nicad batteries may also be seen.

are 1, 2, 4 & 8 BCD lines, with the exception that a zero is read in as a "10" (lines 2 & 8 low). A low reading on any line results in a digit entry. The "digit entry" converter at the top of the diagram converts a zero entry into a "10." The "digit entry" bus is driven high whenever a digit is to be entered, opening the 4 NAND gates to the 2N3646 level converters.

Level converters are also provided for the decimal point entry, divide function and the clear function. Although non-synchronous calculator clocking could have been used as shown on the 5001 data sheets, we chose synchronous clocking to minimize cyclic errors, and tapped a 25 kHz signal from the time-base countdown chain. Electronic, rather than mechanical decimal point switching, was chosen to permit automatic decimal point placement when selecting functions. (And after all, who wants a rotary switch in a project like this?)

Fig. 3 shows outputs from the calculator chip. A Quasi-Darlington connection is used for digit drivers. The digit drive transistors must be maintained in full saturation, other-

wise an "8" display will result in a dimmer digit than a "1," not to mention possible destruction of the transistor. Digits 3 & 6 (from right) are blanked in the time-of-day mode.

Segment drivers need not be high current devices as no more than one digit at a time is turned on (which means segment drivers only carry the load of one segment). Remember, however, the substantial inrush current if incandescent readouts are chosen.

Mode switching uses 8 NAND gates connected as 4 flip-flops. These gates serve as an instruction register and their outputs control the various logic circuits. LEDs are provided near each mode switch to indicate which mode has been selected.

Input Gating

A simple gate which opens for a fixed period of time is not adequate for use when calculating frequency from period measurements. The synchronized gate used here ensures only full pulses are counted, as opposed to a random gate which may open or close in mid-pulse. This substantially

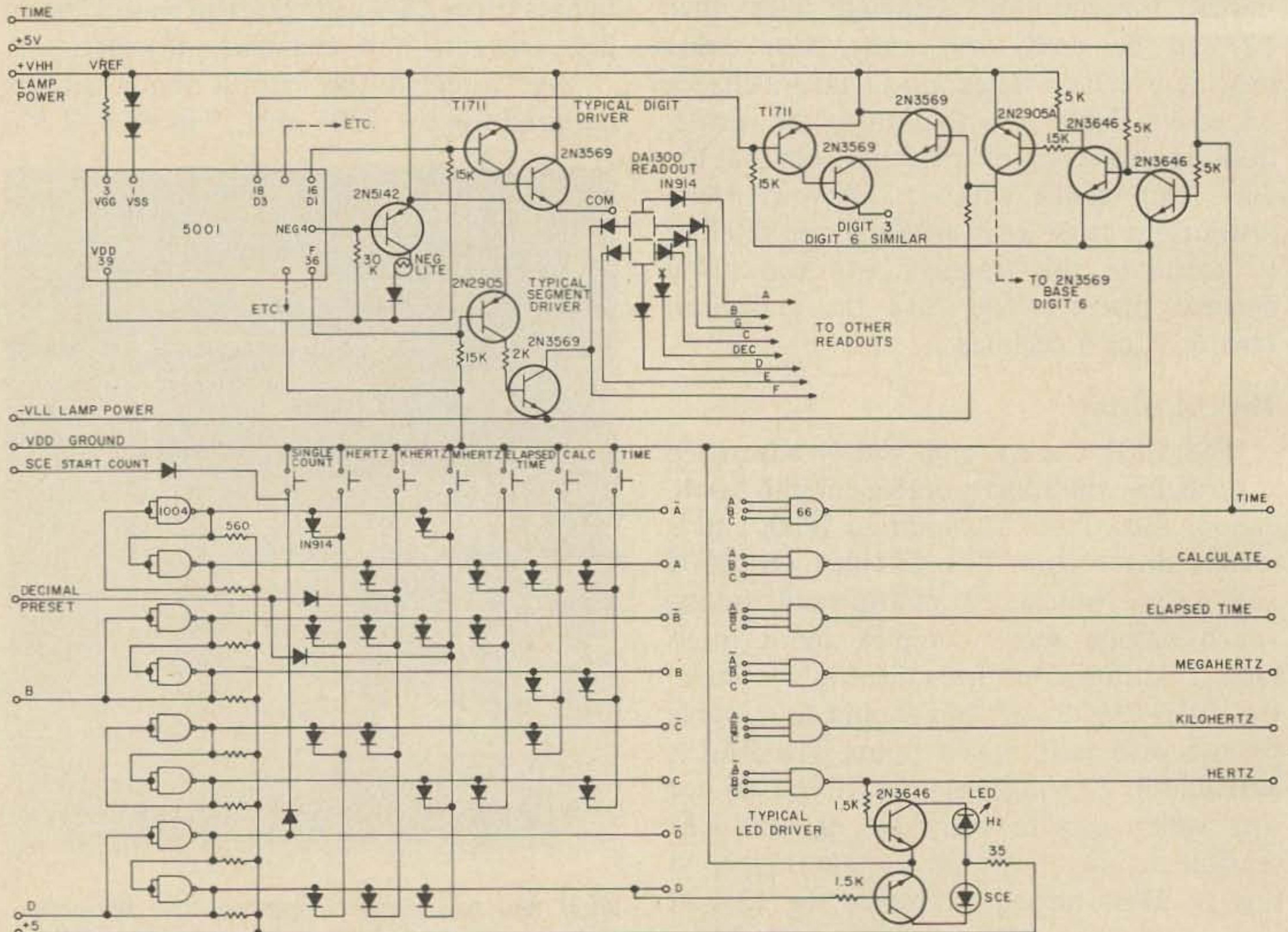


Fig. 3. Readouts and Mode Switching. The neg. light is the G-segment of the left-most readout.

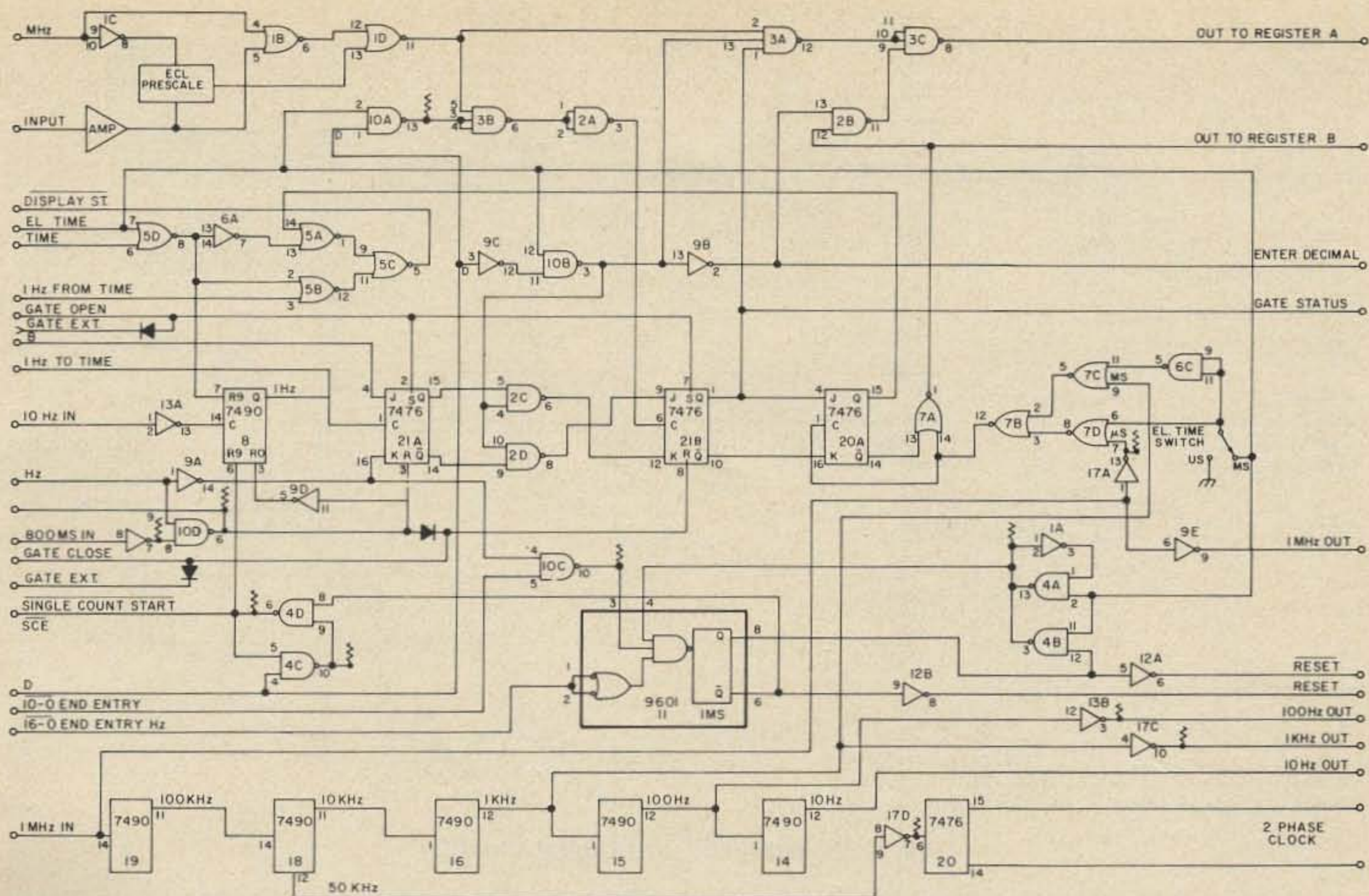


Fig. 4. Input Gate, Clock and Reset.

improves accuracy in the frequency calculate (Hz) mode, and reduces hunting of the last digit which is common to all counters.

The front end of the input board (Fig. 7) includes a wideband amplifier⁴ and a high speed prescaler², both described later. Gates in the signal path (1D, 2A, 3A, 3B, 3C), flip-flop 21, and the input divider of register "A" should be selected for high speed performance.

Assume for the moment that decade divider 8 is enabled (Fig. 4), and we are in the kHz (Standard Count) mode. The first 1 Hz pulse arriving at the count input of FF 21A causes the Q output to go high (gates 2C & 2D are enabled via gate 10B and the J & K inputs of FF 21B are conditioned to permit it to toggle "on"). The input signal is routed to the count input of FF 21B via gates 1B, 1D, 3B and 2A and the first subsequent input pulse causes FF 21B to turn on. Gate 3A is now enabled, and following input pulses are routed to register A via gates 3A and 3C. FF 20A was also set to toggle "on" by FF 21A and the first 1 MHz pulse at the count input of FF 20A causes it to turn on, and gates 5A and 5C cause the display-start line to go high. This readies the display entry logic. (1 MHz

pulses are routed to register "B," but are not used in this mode.)

After exactly 1 second, FF 21A switches off, and conditions FF 21B to switch off. The next input pulse causes FF 21B to switch off, and gate 3A closes. Register "A" now contains the count of input pulses during a one second interval. FF 20A promptly switches off (about 1 microsecond later), the display-start line is brought low, and the digit entry logic is initiated. When all digits have been entered (about 1/4 second), the 10/0 line goes low, and the one-shot generates a 1 ms reset pulse, which clears registers "A" and "B," and simultaneously sets decade divider 8 to a count of 9, through gate 4D. About one tenth of a second later (in the continuous count mode), divider 8 reaches a full count, transmits a pulse to FF 21A, and a new count cycle begins.

Single Count

When line D is high, after the count/display sequence, gates 4C and 4D are locked up by the reset pulse, and divider 8 is held at a count of 9. The start (SCE) line is brought down each time the single count

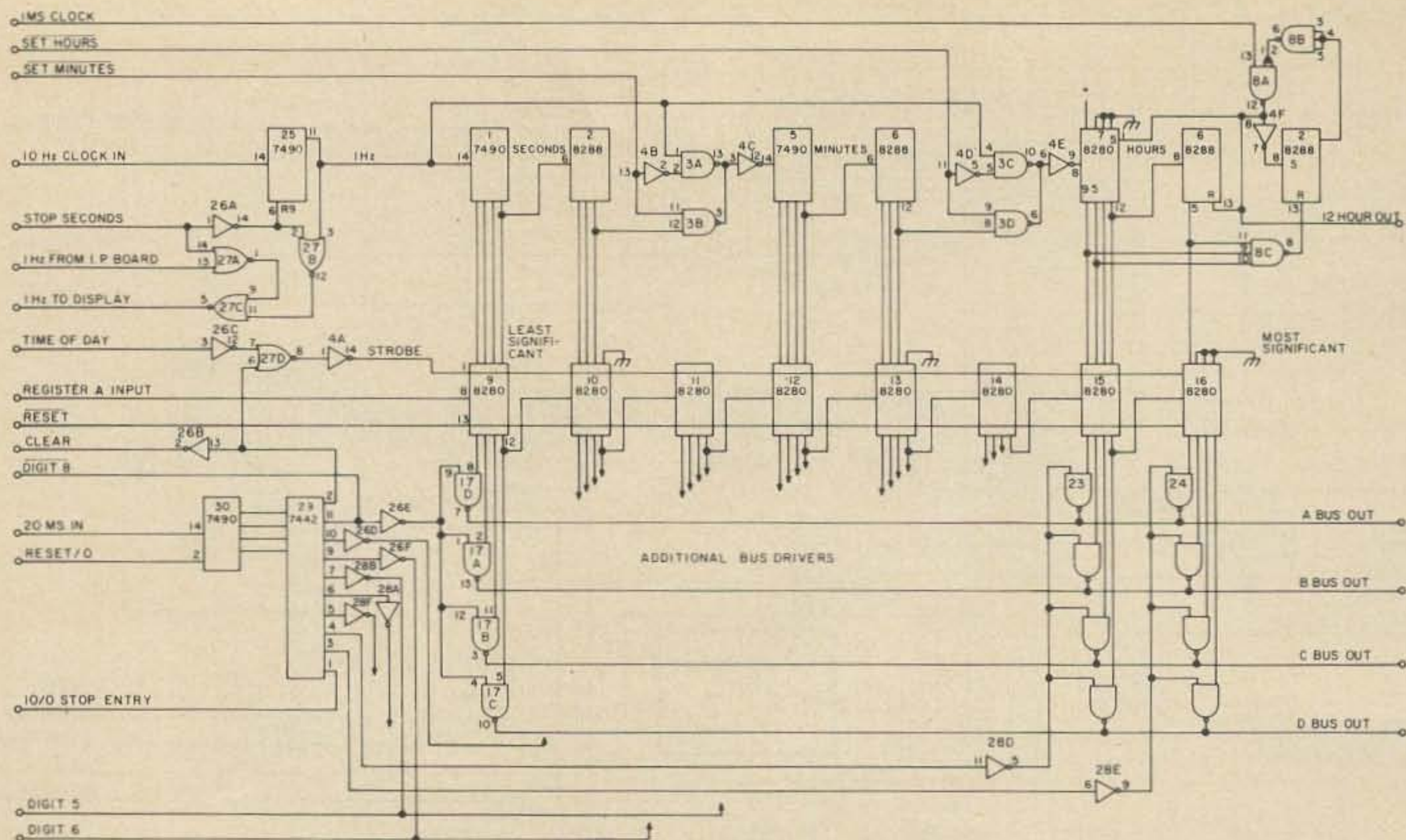


Fig. 5. Register "A" and Digital Clock.

push-button is operated, restarting divider 8, a new count, and resetting gates 4C and 4D.

Calculate Frequency (Hz) Mode

A logical 1 on the Hz line enables gate 10D, prevents FF 21A from resetting from its count input, and prevents (gate 10C) the 10/0 line from initiating a reset pulse. Gate 3A is enabled via FF 21A and FF 21B, similar to the kHz mode. It should be noted that FF 20A (which follows gate 3A by 1 microsecond) routes 1 microsecond pulses via gate 7A to register "B" in all count modes. In the Hz mode, when register "B" has counted 800 milliseconds, it sends a pulse via gate 10D to reset FF 21A. The next input pulse closes gate 3A via FF 21B, and gate 7A closes about 1 microsecond later. Register "A" now contains the number of input pulses which were counted during the time (in microseconds) stored in register "B." The display-start line causes entry of the number stored in register "A," a "divide" function, the period measurement in register "B," and a second divide (equals) function (which calculates the frequency), and initiates a reset pulse via the 16/0 line.

Elapsed Time and Event Counting Modes

When the elapsed time line is high, divider 8 is disabled via gate 5D, and either input

pulses or timing pulses are routed to register "A," depending upon the status of "D" (gates 9B, 9C and 10B). Microsecond or millisecond timing pulses may be selected by a back panel switch. In the elapsed time mode ("D" is low), the gate may be operated via the regular counter input, or via the manual or external gate inputs. Pressing "Single Count" and "Elapsed Time" together selects event counting, and input pulses are routed to register "A" when the gate is opened manually or externally. In these modes, display-start occurs once each second (gates 5D & 5B), and the reset generator is disabled via gates 1A, 4A and 4B. A single reset pulse is generated each time this mode is selected, which permits each count to start from zero.

Clock and Countdown Chain

In order to assure count accuracy, the clock oscillator must have high stability. The circuit chosen⁶ has proven to be very stable. There is little sense in providing 7 or 8 digits of readout unless the clock oscillator is stable to 10^7 or 10^8 or better.⁴ When the digital clock is adjusted to keep time to $\frac{1}{2}$ second in 10 days, accuracy is better than 10^6 . Methods of obtaining better accuracy are available, but are beyond the scope of this article.³ The oscillator is further discussed later.

All devices in the clock chain, and the time-of-day register are provided with battery standby. Interfacing between these devices and other logic devices was made via open collector buffers. Provision of pull-up resistors to the regular 5 volt line, and powering these buffers from the battery, avoids the possibility of glitches when the counter circuits are switched off.

Registers

Data registers and associated logic are diagrammed in Fig. 5 and 6. Referring first to Register "A," it can be seen that pulses presented to the input are counted during the interval the input gate is open. When the gate closes, counting stops and Data Entry Logic is enabled. Divider 30 (Fig. 5) is caused to count up, at a 20 millisecond rate, from "zero" through 8, and then resets to "zero." Decoder 29 changes the BCD output of divider 30 to a "one of ten" output. Each group of 4 gates to the data bus is enabled in turn, which causes the BCD output of the associated decade counter (high order first) to be presented to the BCD data bus (gate 24 presents divider 16, gate 23 presents divider 15, etc.). When divider 30 reaches the count of 8, a signal on the "stop entry" line stops further counting of divider 30, resets it to "zero," and in turn prevents further data entry.

At this stage, the calculator is displaying the contents of register "A." In the kHz and MHz modes, no further data entry occurs, and a new count cycle begins. Data Entry Control Logic will be discussed more thoroughly later.

The time-of-day register utilizes decade and divide-by-twelve dividers to determine the current time. Gates 26A, 27A, 27B, 27C and divider 25 are provided to permit setting the clock. Dividers 1 and 2 divide the 1 Hz pulses by 60, providing one minute output pulses, and storing the "seconds" of the time. Dividers 5 and 6 similarly divide by 60 providing "minutes", and an hourly output pulse. Divider 7 and the divide by 2 (flip-flop) portion of divider 6 provides a 12 hour count register. When a count of "13" is sensed by gate 8C, the hour register is preset to 1 through the action of FF2 and gates 8B and 8C.

The 8280 dividers used in register "A" have a very valuable feature. When the strobe input is raised to logic "1," the divider is preset to the value found on its BCD inputs. This feature permits parallel loading of time-of-day data into register "A" simply by strobing the 8280 dividers.

Time-of-day can then be entered into display, just as if it were a "count." Note that the digits between the "seconds" and minutes, and between the "minutes" and

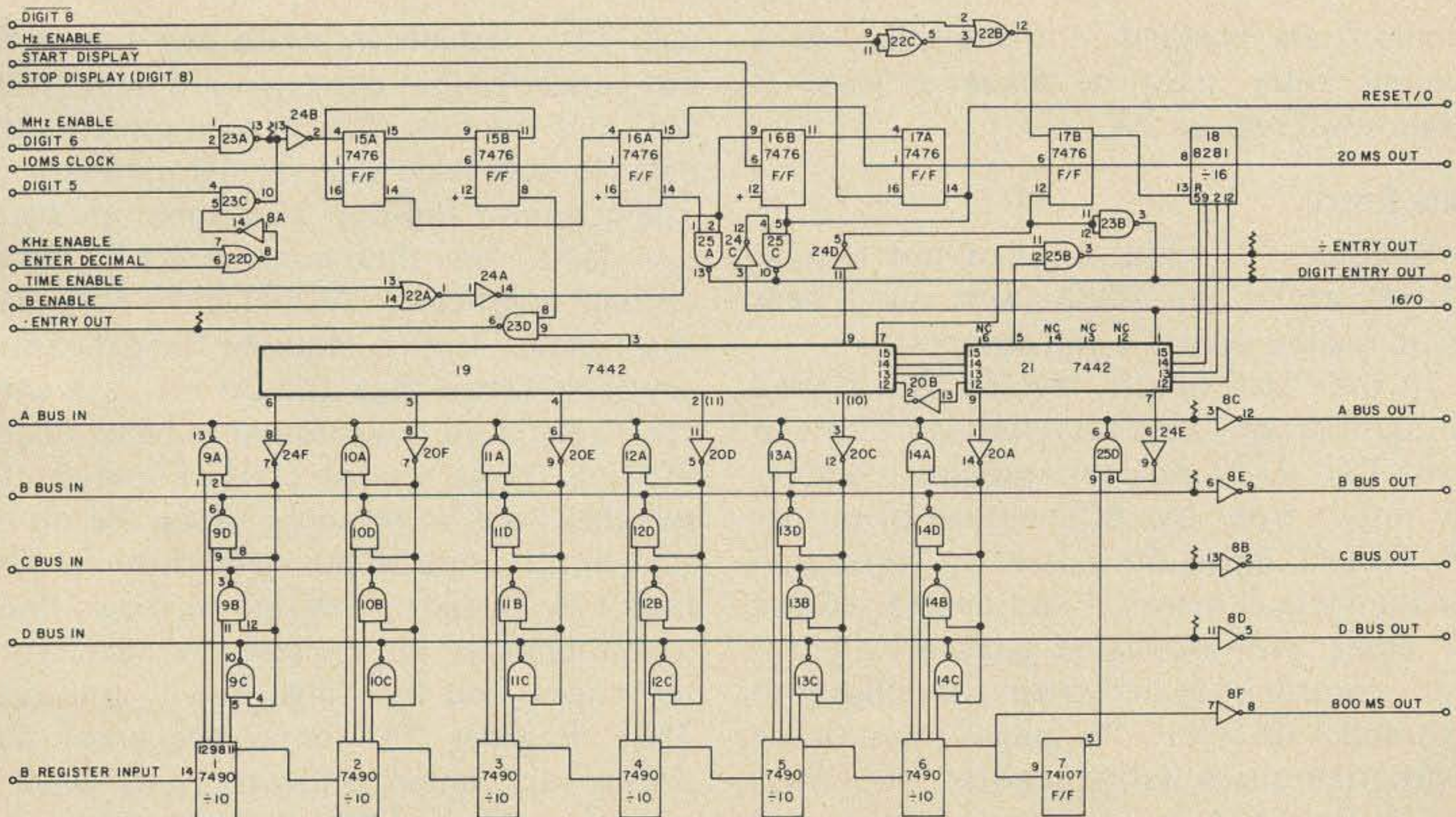


Fig. 6. Register "B" and Entry Logic.

Count Mode - kHz

Decimal Point Preset at "3"

1. Open Input Gate
2. Close Input Gate (1 second later)
3. Clear Display (CE)
4. Enter 5 High Order Digits From Register "A"
5. Enter Decimal Point
6. Enter 3 Low Order Digits From Register "A"
7. Clear Registers

Count Mode - MHz

Decimal Point Preset at "3"

Prescaler Activated

1. Open Input Gate
2. Close Input Gate (1 second later)
3. Clear Display (CE)
4. Enter 6 High Order Digits From Register "A"
5. Enter Decimal Point
6. Enter 2 Low Order Digits From Register "A"
7. Clear Registers

Count Mode - Hz

1. Open Input Gate
 2. Open Clock (Register "B") Gate
 3. Close Input Gate (When Register "B" Full)
 4. Close Clock Gate
 5. Clear Display (CE)
 6. Enter 8 Digits From Register "A"
 7. Enter Three Zeroes
 8. Enter "Divide" Command
 9. Enter 4 High Order Digits From Register "B"
 10. Enter Decimal Point
 11. Enter 3 Low Order Digits From Register "B"
 12. Enter "Equals" ("Divide") Command
 13. Clear Registers
- (Delay New Count Cycle to Provide 2 Second Update)

Elapsed Time Mode

- Route Clock (MS or uS) Pulses to Register "A" (gated)
Route Input to Control Input Gate
Update Once Each Second
Clear Register "A"
1. Clear Display (CE)
 2. Enter 5 High Order Digits From Register "A"
 3. Enter Decimal Point
 4. Enter 3 Low Order Digits From Register "A"

Accumulate Count Mode

- Route Input Pulses to Register "A"
Update Once Each Second
Clear Register "A"
1. Clear Display (CE)
 2. Enter 8 Digits From Register "A"

Time-of-day Mode

- Blank 2 Digits
Update Once Each Second
1. Clear Display
 2. Load Register "A" From Time-of-Day Register
 3. Enter 8 Digits From Register "A"

Calculate Mode

Lock Out Data Entry Sequencer
(Keyboard Always Live)

Continuous Count Mode (Hz, kHz, MHz)

Enable Automatic Count Restart (input gate) on Register Clear Signal

Single Count Mode (Hz, kHz, MHz)

Manual Count Restart (input gate)

Table 1. Calculate/Count Program.

"hours," are blanked in the display, so a dummy entry must be made in these 2 positions of register "A."

Data Entry

Register "B" (Fig. 6) does not require parallel entry, so 7490s were used here (more readily available and cheaper).

In the "Hz" modes, divider 18 is caused to count from "zero" up through "15" to zero. Two 7442 decoders provide a one-of-16 output from the BCD output of divider 18. Table 1 shows the data entry "program" for the various modes. Flip-flops 15, 16 and 17, along with associated gates, provide for entry control of both registers, and flip-flops 15A and 15B enter a "decimal" point in the appropriate place during register "A" entry.

Flip-flop 16A is normally enabled, and provides 20 millisecond pulses to the two

data entry sequencers. Gate 25A signals the bus converter that there is valid data on the bus, and the converter in turn presents this data to the calculator for 10 milliseconds. The action of flip-flop 16A is inhibited (and no digits are therefore entered) during decimal point entry. Although the 5001 data sheet states 4 ms is required for data entry, anything faster than the 20 ms data entry cycle rate chosen was found to be unreliable with my bargain price 5001. Flip-flop 16B switches "on" in response to a pulse on the start-display line (input gate closure). Flip-flop 17A is then permitted to toggle "on," which unlocks the register "A" data entry sequencer, and the "digit entry" line (gate 25C). Register "A" entry sequencer then counts up (entering digits), and when it reaches a count of "8" the stop-display line permits flip-flop 17A to toggle off, which

Build Your Own Computer

\$439

For complete information package including 24 page catalog, technical data, price list and sample Altair Users Group newspaper send \$2.00 to: Altair Package, MITS, 6328 Linn NE, Albuquerque, New Mexico 87108

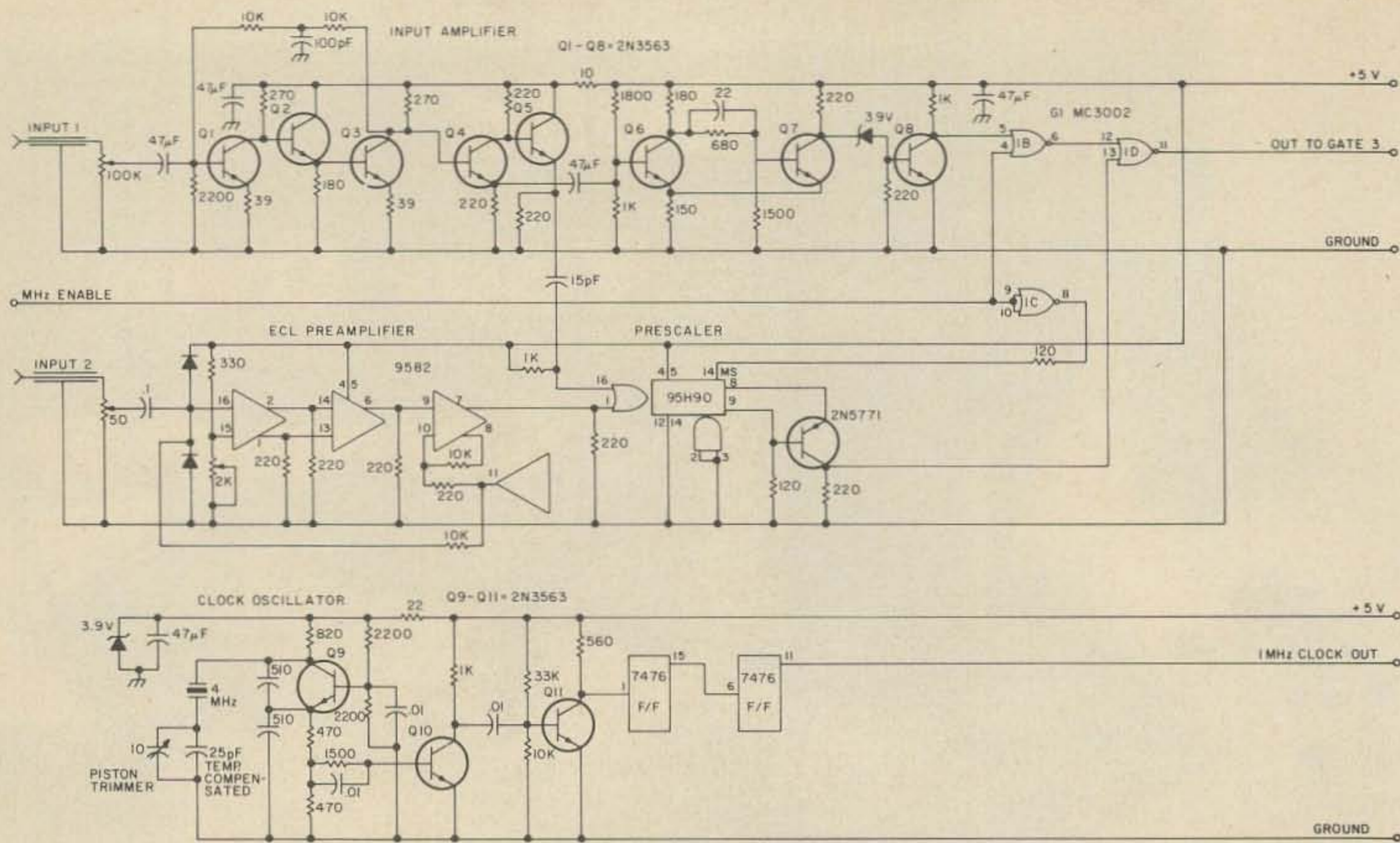


Fig. 7. Details: Input Amplifier, Prescaler, Clock Oscillator.

resets the entry sequencer to "zero" and stops further entry of register "A."

In the "Hz" mode, a count of "8" on the register "A" entry sequencer permits flip-flop 17B to toggle "on" which enables the 8281 register "B" entry sequencer (18) and unlocks the digit entry line at gate 25C. Register "B" entry sequencer then counts up, entering register "B," and at count 15 gate 24D enables the flip-flop 17B "K" input. The next count pulse causes sequencer 18 to return to a "zero" count, and simultaneously toggles flip-flop 17B "off," which disables divider 18.

Input Amplifier and Prescaler

Details of the input amplifier and prescaler are shown in Fig. 7. The input amplifier uses low-cost high speed 2N3563 transistors throughout. The input amplifier has a passband from 1/2 Hz through at least 150 MHz. This amplifier is described elsewhere⁴ and is highly recommended. (Some resistor changes were found necessary to optimize response.) The 9582 ECL pre-amplifier was found to have less sensitivity than the discrete preamp, and stability proved a problem. In retrospect, the writer would eliminate the ECL preamp, and use the discrete preamp for all input signals.

(Reference 14 discusses improvements to the prescaler.)

The 95H90^{2,11} prescaler functions exactly as expected. Again, power supply impedance is critical² and .01 discs must be used liberally to ensure stability. The output transistor as recommended is a 2N5771.

Clock Oscillator

Time base stability is very important if accurate counts are to be expected. The oscillator circuit⁶ was chosen after much experimentation. The crystal is a 4 MHz HA type (high accuracy) ordered for room temperature use. This frequency seems to be about optimum for thermal stability, and use of a series/parallel combination of NPO and negative temperature capacitors for the crystal series capacitor permits stability to be adjusted.³ The 10 pF capacitor is a glass piston trimmer and can be anything smaller than 10 pF (4 pF probably is about right if you can find one). Q9, Q10 and Q11 are 2N3563 or 2N4274. Use of this oscillator permits stability to 1 part in 10⁷ or better without an oven. The author's unit keeps time to better than 1/4 second to WWV over a two-month period. Only a very slight difference in time-keeping ability was noted when the unit was run "warm" for a similar period.

Mode Switching

Use of 8 open collector TTL 2 input NAND gates (or inverters) connected as 4 S/R flip-flops permits a completely electronic mode switching system. The configuration of these flip-flops is set by pressing one of the mode push-buttons. The flip-flops then "remember" what mode switch was last pushed.

Outputs at the first three flip-flops are decoded by six 3-input NAND gates. The fourth flip-flop is used to control the single count function, and also, together with the "elapsed time" mode, to provide an "accumulate" mode. LEDs indicate the mode presently in use. Operation of either the kHz or MHz button presets the calculator to 3 decimal places. This permits display of the decimal in the appropriate location. An extra decimal point LED was mounted between the 5th and 6th digits (from the right) and connected via a driver to the MHz function. This provides a reading of xx.xxx.xx in this mode. (Although it might appear that the MHz function should preset 2 decimal places, the decimal point is entered in the proper place by the data entry

logic.) Germanium diodes should be used in the "decimal preset" line to ensure that TTL inputs are brought below their switching thresholds.

Power Supply

In order to avoid loss of power to the digital clock, a battery standby has been provided for the clock circuits. Referring to Fig. 8, a constant current regulator, comprised of a 2N3055 and a 2N3569, maintains the Nicad battery in a fully charged state. The voltage regulator using another 2N3055 and a 2N3698 is somewhat unusual. A voltage doubler driven by G1 and G2 provides sufficient current to the 2N3055 to maintain it in saturation when the input voltage drops to 5.2 volts or less. This ensures adequate output voltage to drive the TTL clock circuits until the battery voltage drops to about 4.7 volts. At this point, zener diode Z1 (with diodes D5 and D6) reduces the base current to the 2N3055, which results in a drop in output voltage. Lowered voltage to the TTL countdown chain causes a loss of clock drive to the voltage doubler, and results in a complete shut-down of the voltage regulator. Deep discharge of a Nicad

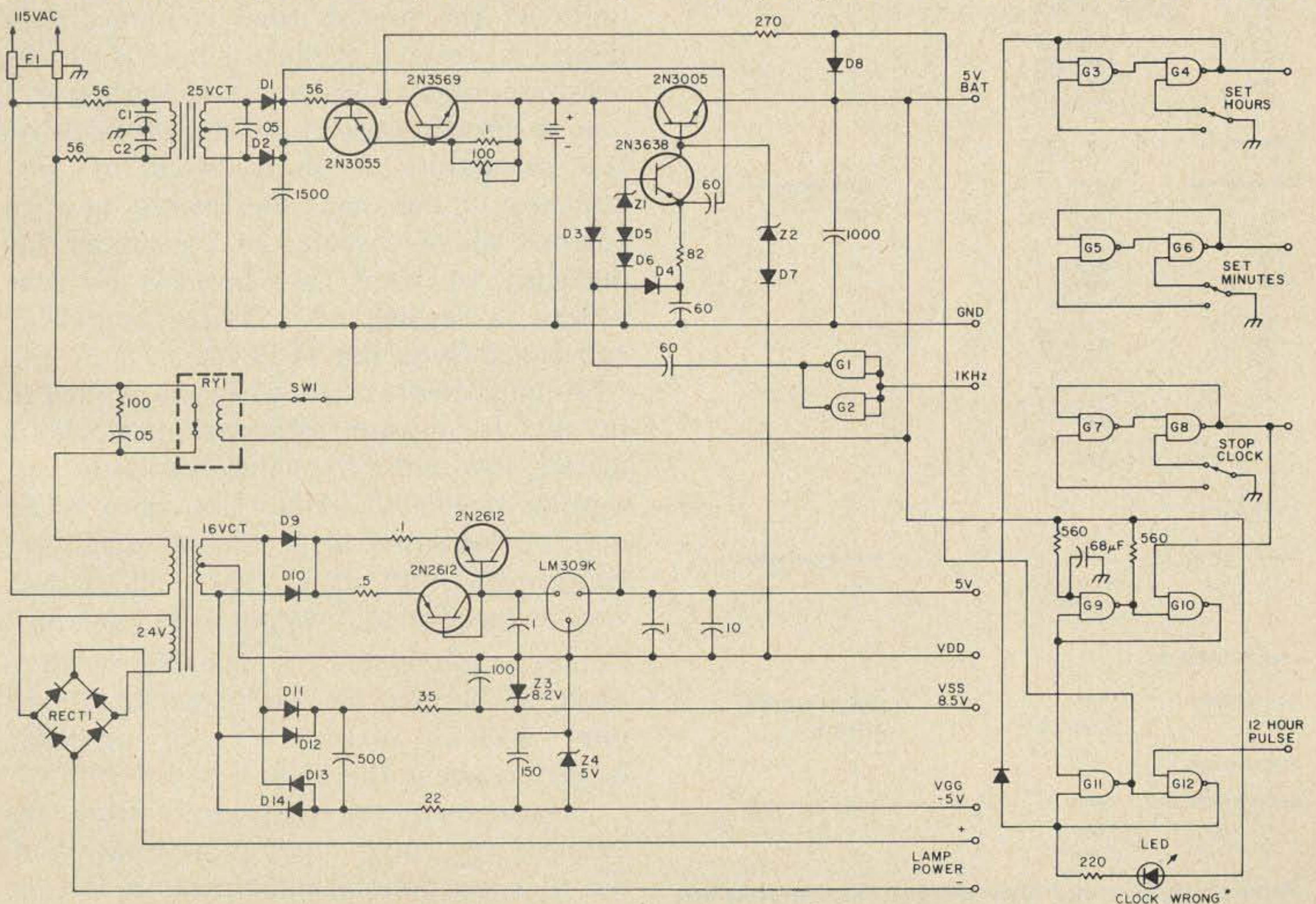


Fig. 8. Power Supply. *This LED signals a power off condition until the clock is reset.

battery would result in permanent cell damage.

Zener diodes Z1 and Z2 with their associated forward diodes must be chosen to provide about 5.7 volts at the base of the 2N3055, and about 5 volts at the base of the 2N3638. (Note that throughout this project transistors were chosen mostly for their ready availability in the writer's junkbox, and suitable substitutions are in order.)

REGISTER "A"

Device Number	Device	Similar Equivalent
1	7490	
2	Signetics 8288	74193, 74161
3	RM1004D	7401, 7403
4	F3005663	7404
5	7490	
6	8288	
7	8280	74160, 9310, 74192, 8310
8	7410	
9 - 16	8280	
17 - 24	RM1004D	
25	7490	
26	F3005663	
27	SN2790N/F3005664	7402
28	F3005663	
29	7442	
30	7490	

REGISTER "B"

Device Number	Device	Similar Equivalent
1 - 6	7490	
7	74107	
8	F3005663	
9 - 14	RM1004D	
15 - 17	7476	
18	8281	74161, 9316, 8316
19	7442	
20	F3005663	
21	7442	
22	SN2790N	
23	RM1004D	
24	F3005663	
25	RM1004D	

INPUT SYNC

Device Number	Device	Similar Equivalent
1	MC3002	7402
2	7400	
3	7410	
4	RM1004D	
5 - 7	SN2790N	
8	7490	
9	F3005663	
10	RM1004D	
11	MC9601	
12	7440	
13	RM1004D	
14 - 16	7490	
17	RM1004D	
18 - 19	7490	

READOUTS

Device Number	Device	Similar Equivalent
1 - 2	RM1004D	
3 - 4	F3005666	

INPUT CIRCUITS

Device Number	Device	Similar Equivalent
1	RM1003D	MC3007

POWER SUPPLY

Device Number	Device	Similar Equivalent
G1 - G8	7400	
G9 - G12	RM1004D	

Table 2. Devices and Equivalency. Duplications not listed.

The main 5 volt supply^{1 3} uses a PNP 2N2612 transistor to provide about 4 Amperes of regulated dc, controlled by the 1 Ampere LM309K. The second 2N2612 is diode connected to provide a voltage drop similar to the base-emitter drop of the pass transistor, and as it is mounted on a common heat sink, provides thermal stabilization. MOS voltage levels are provided by simple zener regulators. Note that Vdd is grounded, whereas the 5001 data sheet references voltage levels to Vss. Lamp power is unfiltered, which reduces readout brilliance changes with the widely varying readout load.

Three bounceless switches are provided for setting the time. Gates G9, G10, G11 and G12 increase the battery charge rate upon restoration of power after discharge. The high rate continues until first the "stop clock" (set seconds) switch is operated, and then a 12 hour pulse is received at midnight or noon. (That is, the high rate stops at noon or midnight after the time has been reset.)

Using the Calculating Counter

The completed counter has proven to be a very useful tool. By merely switching the unit on, the precise time is immediately displayed. Instead of those laborious parallel resistor computations with pad and paper, a precise calculation can be quickly made on the calculator. A short piece of wire attached to the input and placed near an antenna allows checking of transmitter frequencies. (A hand held business portable yielded a reading of 155.610.15 MHz — authorized frequency 155.610.)

As indicated earlier, while we wished to be able to measure frequencies through 2 meters, low audio frequency resolution was a prime target. All frequencies above 10 Hz may be measured to 5 or more significant figures. (A sixth digit shows, but as previously mentioned, hunting in the last digit cannot be eliminated.) Frequencies down to about 1/2 Hz may be determined to 3 (plus one) decimal places, if your obsession happens to be in this area.

Measurement of frequencies from the author's electronic organ proved easy with use of a microphone and a preamp, but the piano proved to be a little more challenging.

2 METER CRYSTALS IN STOCK

We can ship C.O.D. either by parcel post or U.P.S. Orders can be paid by: check, money order, Master Charge, or BankAmericard. Orders prepaid are shipped postage paid. Phone orders accepted. Crystals are guaranteed for life. Crystals are all \$5.00 each (Mass. residents add 15¢ tax per crystal). *U.S. Funds Only*

We are authorized distributors for: Icom and Standard Communications Equipment. (2 meter)

Note: If you do not know type of radio, or if your radio is not listed, give either fundamental frequency or formula and loading capacitance.

LIST OF TWO METER CRYSTALS CURRENTLY STOCKED FOR RADIOS LISTED BELOW:

- | | |
|------------------|--|
| 1. Drake TR-22 | 5. Ken/Wilson |
| 2. Drake TR-72 | 6. Regency HR-2A/HR212/Heathkit HW-202 |
| 3. Genave | 7. Regency HR-2B |
| 4. Icom/VHF Eng. | 8. S.B.E. |
| | 9. Standard |

The first two numbers of the frequency are deleted for the sake of being non-repetitive. Example: 146.67 receive would be listed as - 6.67R

- | | | | | | | | |
|----------|------------|-----------|-----------|-----------|-----------|-----------|-----------|
| 1. 6.01T | 9. 6.13T | 17. 6.19T | 25. 6.31T | 33. 6.52T | 41. 7.06R | 49. 7.18R | 57. 7.30R |
| 2. 6.61R | 10. 6.73R | 18. 6.79R | 26. 6.91R | 34. 6.52R | 42. 7.69T | 50. 7.81T | 58. 7.93T |
| 3. 6.04T | 11. 6.145T | 19. 6.22T | 27. 6.34T | 35. 6.94T | 43. 7.09R | 51. 7.21R | 59. 7.33R |
| 4. 6.64R | 12. 6.745R | 20. 6.82R | 28. 6.94R | 36. 7.60T | 44. 7.72T | 52. 7.84T | 60. 7.96T |
| 5. 6.07T | 13. 6.16T | 21. 6.25T | 29. 6.37T | 37. 7.00R | 45. 7.12R | 53. 7.24R | 61. 7.36R |
| 6. 6.67R | 14. 6.76R | 22. 6.85R | 30. 6.97R | 38. 7.63T | 46. 7.75T | 54. 7.87T | 62. 7.99T |
| 7. 6.10T | 15. 6.175T | 23. 6.28T | 31. 6.39T | 39. 7.03R | 47. 7.15R | 55. 7.27R | 63. 7.39R |
| 8. 6.70R | 16. 6.775R | 24. 6.88R | 32. 6.99R | 40. 7.66T | 48. 7.78T | 56. 7.90T | |

CRYSTALS FOR THE IC-230 SPLITS IN STOCK: 13.851111 MHz; 13.884444 MHz; 13.917778 MHz. \$6.50 ea.

SPECIAL

Buy the STANDARD 146/A W/T for ONLY \$298 and receive a \$60 MERCHANDISE CREDIT good for the following accessories:

- SR-CSA DESK TOP CHARGER \$43.00
- SR-C-AT19 RUBBER DUCKY ANTENNA \$6.00
- NI-CAD BATTERIES (10 REQUIRED) \$2.00 ea.
- CRYSTALS (UNIT COMES WITH 34/94 AND 94 DIRECT) \$5.00 ea.
- SR-C-PT3644 LEATHER CASE \$8.50

SPECIFICATIONS


Microphone:	Internal dynamic type	Frequency range:	143 to 149 MHz
Dimensions:	9" h x 3" w x 1-5/8" d	Number of channels:	5
Weight:	32 oz. max. (including batteries)	Channel spread:	2 MHz max.
Supplied with 2 channels:	146.94Tx/Rx (national calling channel)	Input voltage (negative ground):	12.5V dc ±20%
	146.34Tx/146.94 Rx (repeater channel)	Circuitry:	All solid state
	Internal 2" dynamic	Current drain:	15ma squelched max., 100ma receive max., 0.62A transmit max.

CASH, CHECK OR M.O. ONLY TO QUALIFY FOR W/T SPECIAL

STORE HOURS: MON-FRI: NOON-9 P.M. SAT: 10 A.M.-6 P.M.



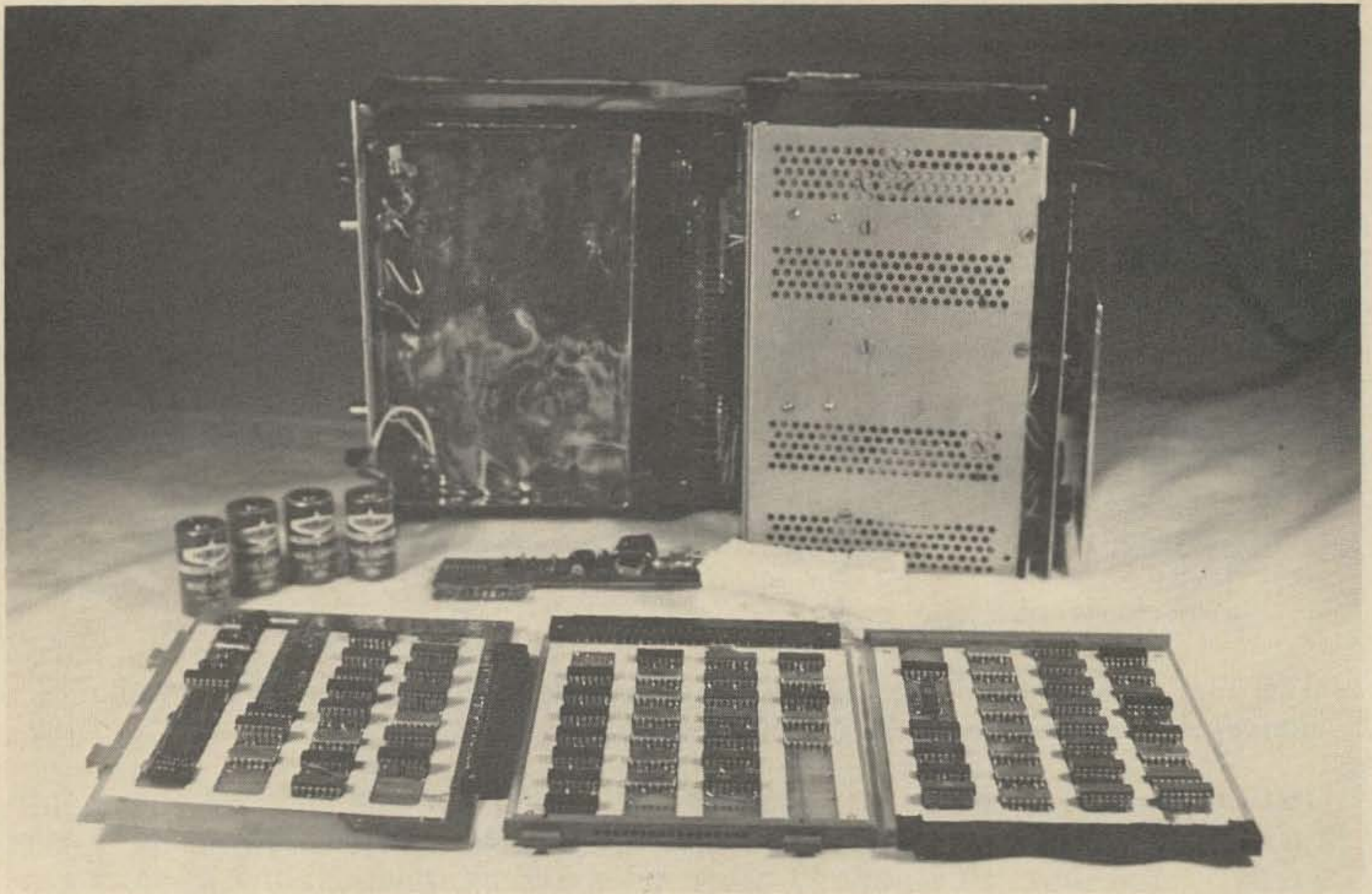Kensco 46 PEARL STREET PHONE (617) 471-6427
QUINCY MA. 02169
Communications INC.



Bottom view of counter. The shiny surface on the left is a copper shield between the input board and the calculator boards. The oscillator board is in the center. Left is the input board, and the other two boards contain the time-of-day register and the count logic and registers.

A recent article^{1 5} described a combination oscillator/tunable filter. When connected between a microphone preamp and the counter, the filter permitted a fundamental to be isolated from its harmonics. Furthermore, the high "Q" of the filter acts to sustain the note long enough to permit measurement. When a piano key is struck, and the single-count button operated immediately, a count may be accurately obtained before the note decays. It is said that a mechanical tuner cannot properly tune a piano, as octaves are not precise multiples, and multiple string notes have delicate differences in the tuning of the individual strings. One might nevertheless learn much by exploring a tuned piano.

It is the writer's hope that this article may evoke an interest in the many MOS devices currently on the market at most attractive prices.

References

¹"Advanced divide by ten frequency scaler", W6PBC, *HR*, Sept '72/ Oct '73. (Note - W6MGI, *HR*, Feb '73, page 57.)

²"A Modern VHF Frequency Counter", K2OAW, 73, May '72, July '72, Sept '72, correction Nov '72.

³"Mainline FS-1 Secondary Frequency Standard", W6FFC, *QST*, Nov '68.

⁴"Time-Frequency Measuring System", K5OUS, 73, Oct '72, Feb '73, March '73.

⁵"Digital Station Accessory", K6KA, *Ham Radio*, Feb '72, March '72, April '72.

⁶"Compact Frequency Counter", K4EEU, *Ham Radio*, July '70.

⁷"A 50 MHz Frequency Counter", *Cody Electronics World*, March '69.

⁸"Heath-Model 1B-101 Frequency Counter", *Techni-Guide, Electron*, Feb '71.

⁹"Introduction to Electronic Counters", Steinbach, *Electronics World*, Jan '71, March '71.

¹⁰"Low Cost Counting Unit", Lancaster, *Popular Electronics*, Feb '68.

¹¹"Divide-By-Ten Frequency Scaler", K4EEU, *Ham Radio*, August '70.

¹²"Popular Electronics Universal Frequency Counter", Lancaster, *Popular Electronics*, March '69, April '69.

¹³"Current Sharing Design Boosts Regulator Output", Vanderkoot, *Electronics*, March 29, '73.

¹⁴"Latest Counter Update" K2OAW, 73, Nov '74.

¹⁵"Build the Fil - Oscillator", Melen & Garland, *Popular Electronics*, May '71.

... JOHNSON

KENWOOD

*...Why settle
for less!*

There are several good transceivers on the market today. But if you compare them carefully . . . study the specifications, note the important features, and finally talk to some Kenwood owners, you will have to come to the same conclusion that thousands of others have come to . . . you can't buy a better rig for the money than a Kenwood. Every unit is built with pride and designed to give top performance year after year. Join the switch to Kenwood.



The TS-520 shown
with the VFO-520 and SP-520

The TS-520 is the final word in SSB transceivers . . . the "hottest little rig on the air." It is a compact, mostly solid state, all-in-one transceiver with built-in AC/DC power supply and speaker. It operates SSB and CW on 80 thru 10 meters. Features include 2-position ALC and double split frequency controlled operation.

Available at select Kenwood dealers throughout the U.S.

Distributed by



**TRIO-KENWOOD
COMMUNICATIONS INC.**

116 East Alondra / Gardena, California 90248

New Heath Ham Accessories



New solid state Heathkit Electronic Keyer...49.95

Sending code's easy with the HD-1410 whether you're operating base or portable. The dot and dash paddles' travel and tension are easily adjustable. When the two paddles are treated as one, the HD-1410 operates like a single-paddle keyer with dot and dash memories. Iambic operation forms most characters with reduced wrist movement. Dots and dashes are self-completing and always in proper proportion. During construction, you select the speed range you want up to 35 words per minute or up to 60 words per minute. Operates on 120 VAC or 12 VDC. Adjustable sidetone frequency, built-in speaker, headphone jack, weighted base. Styled to match our famous "SB" line.

Kit HD-1410, 5 lbs., mailable49.95*

HD-1410 SPECIFICATIONS — Keying Speed: Variable from under 10 to over 35 or from under 10 to over 60 wpm. Keying Output, Positive Line to Ground: max. voltage open circuit or spikes — 300 volts. Max. current — 200 mA. Keying Output, Negative Line to Ground: max. voltage open circuit or spikes — 200 volts. Max. current — 10 mA. Audio: internal speaker or jack for optional hi-Z (at least 500 ohms) headphones. Sidetone: adjustable from 500 to 1000 Hz. Internal Controls: sidetone frequency, paddle tension, paddle travel. Rear Panel Connections: AC power cord, 12-volt power input, keyer out, headphones, receiver audio in, ext. key. Temperature Range: 0°C to +40°C (typ. -10°C to +40°C) or approx. 50°F to 105°F. Power Requirement: 120/240 VAC (±10%), 60/50 Hz, 3.5 watts or 10-14.5 VDC, negative ground, 150 mA. Dimensions: approx. 3" H x 5" W x 7½" D. Net Weight: 3 lbs.

HEATHKIT ELECTRONIC CENTERS — Units of Schlumberger Products Corporation Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton) NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.



New solid state Heathkit Dip Meter...59.95

A better dip meter at lower cost. The Colpitts oscillator covers 1.6 to 250 MHz in fundamentals with MOS-FET paraphase amplifier and hot-carrier diodes for more sensitivity and better dip. Q-multiplier for greater detector sensitivity and responsive 150 μA meter movement for positive resonance indications. Phone jack for modulation monitoring. Solid-state design and 9-volt battery operation. Custom molded gray carrying case protects the meter and the 7 color-coded, pre-adjusted, plug-in coils in transit, and makes a handy storage place. Build it in one evening. Nearly everything mounts on two circuit boards. And when you finish, you'll have the best dip meter around — for a lot less money.

Kit HD-1250, less battery, 4 lbs., mailable...59.95*

Send for FREE Catalog

HEATH Schlumberger	Heath Company, Dept. 11-08 Benton Harbor, Michigan 49022	
<input type="checkbox"/> Please send my free 1975 Heathkit Catalog. <input type="checkbox"/> Enclosed is \$ _____, plus shipping. please send model(s) _____		
NAME _____		
ADDRESS _____		
CITY _____	STATE _____	ZIP _____
<small>PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE. *MAIL ORDER PRICES; F.O.B. FACTORY.</small>		
		AM-314

A Satellite Fax System You Can Build

Part One

One of the more persistent questions which I encountered in correspondence regarding my previous articles on weather satellite picture displays is why I didn't work up something for facsimile display of satellite pictures. I have always had a certain attraction to facsimile and the only thing that kept me out of that particular ball game was sheer mechanical ineptitude. I felt that I was at my limit using a simple chassis punch, and the thought of trying to construct a piece of "precision" facsimile equipment seemed a little more than I was willing to try. Prodding by Lindsay Winkler W6WMI, the author of the interesting article on an SSTV FAX machine (73, March 1973) was constant. Wink kept sending me some excellent pictures produced by Virgil Neher W6KT using a homebuilt photographic facsimile system and I finally had to give it a try — if only to retain my charter membership in the Lost Order of Home Brewers. The present project, which represents the illicit union of integrated circuits, some tried and tested tube circuits (you do remember tubes, don't you?), miscellaneous plumbing fixtures, and a kitchen rolling pin, was the final result. As it turns out, both CRT and FAX systems have strong points and shortcomings, which I will detail later. An active weather satellite station should have capability for both modes.

The circuit details described here assume

that you will be starting from scratch. The electronics are very straightforward, with the main challenge being the mechanical tinkering to arrive at optimum performance. No fancy machine tools are required — I don't have any and if I did I would probably only maim myself — so rest assured that you can Rube Goldberg yourself into the ballpark with nothing more than normal workshop tools. The project uses tubes in some parts of the circuit, so you will be able to justify having kept all that junk around if the XYL is still asking.

The first question that might occur is why build from scratch? Why not modify a commercial machine? The answer is that a photographic system, printing directly on photographic paper, is not only fast and cheap, but gives the best possible picture quality. Very few photographic facsimile machines are available and all would require extensive modification to the point where it's easier to start from ground zero. Similar systems can be worked up from machines using Teledeltos papers (Deskfax) or the better Alden machines and papers, but the results achieved, while adequate, will suffer in comparison to either a CRT or photographic facsimile system.

Principles of Operation

Fig. 1 shows a block diagram of the FAX system. There are two ways to look at the

NOAA satellite video format. It can be considered at 48 line per minute format, in which half the line represents IR data and half visible light data. Alternatively, the format can be viewed as a 96 line per minute system in which alternate lines of visible and IR data are displayed. On this run through we will use the first of these. If satellite video is arriving at the rate of 48 lines per minute, we have to rotate the drum of the facsimile recorder at 48 rpm, in order that one revolution of the drum corresponds to one line of video. A light gun, containing a high intensity modulated light source focused to a small spot, will paint the picture on the photographic paper as the drum rotates. The light gun must be slowly pulled (or pushed) along the length of the drum to provide "vertical" scanning as the image is built up. This is accomplished by a small slow speed motor operating a threaded rod which engages a nut on the carriage assembly for the light gun. Proper operation of the system requires that the drum operate at precisely the line rate of the satellite video, so a synchronous motor is required. Although there are 48 rpm synchronous motors, they are difficult to obtain so a 60 rpm motor is operated on 48 Hz ac (instead of the normal 60 Hz) to obtain 48 rpm output.

During reception of a satellite signal, the satellite video is recorded on the right channel of a stereo tape deck while an accurate 4800 Hz tone, derived by a digital countdown chain from a 4.8 MHz oscillator, is recorded on the left channel. During picture display the satellite video from the right channel of the tape deck is filtered and amplified, and routed to a high level video driver to modulate the light gun. Output

from the light gun is highest in black areas of the picture and lowest in white areas so the processed photographic paper will have a positive image. The 4800 Hz tone on the left channel is used to lock a phase locked loop (PLL) to 4800 Hz. The PLL output is divided to 48 Hz by a digital countdown chain and this 48 Hz signal is amplified by a high level class AB₁ amplifier to provide 48 Hz ac at 120 V to operate the drum motor at 48 rpm. Since the crystal controlled 4800 Hz tone was recorded simultaneously with the satellite signal, any variations in tape speed during playback will be "tracked" by the PLL and the ac driving the drum motor will shift in frequency to compensate, resulting in the maintenance of a stable sync condition despite flutter and wow in the recorder.

A word here about the recording process. Many of the earlier articles on satellite picture reception stated that "live" display was preferred to a recorded signal, in that the recorded signal was rarely equal to the "live" version. This may well have been the case several years ago but is no longer. Modern recorders of the "hi-fi" type, and integrated circuit PLL and digital countdown chains, result in a situation where there is no observable difference in quality between recorded and "live" picture display. Working from recordings is infinitely easier and will have no effect on picture quality.

Up until this point we have not mentioned picture phasing — alignment of the synchronized picture with the edge of the paper wrapped around the drum. The complete NOAA data display contains two areas of potential interest, the earth scan picture in the visible light channel and an identical

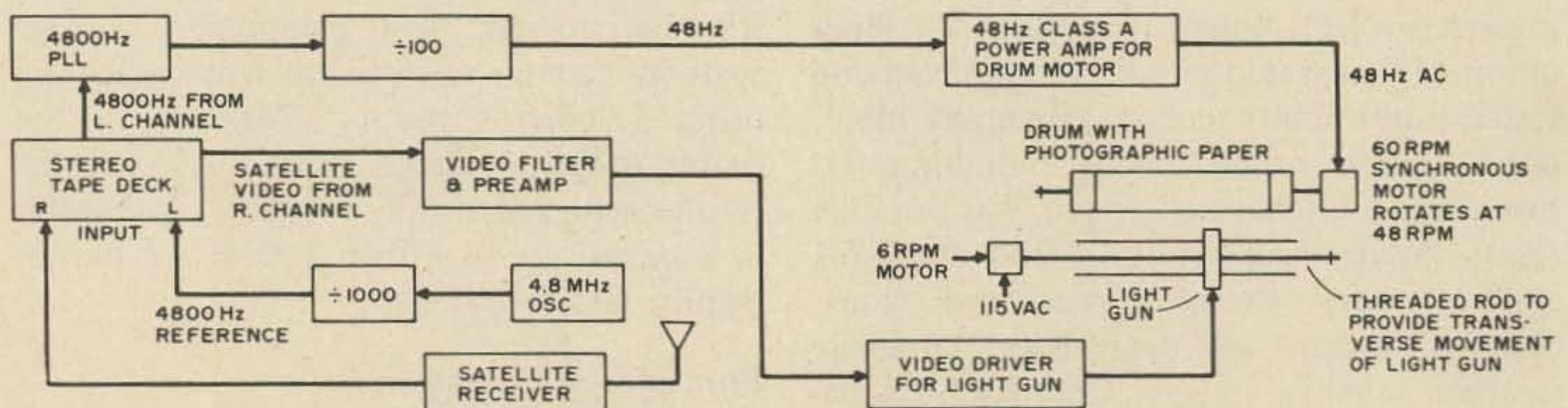


Fig. 1. A block diagram of the weather satellite facsimile system.

view as produced in the infrared waveband. Each of these earth scan images occupies 30% of the total length of the scanning line (circumference of the scanning drum). The remaining 40% of the line is taken up by space scan, telemetry, grey scale, instrument restore periods, and timing data, much of which is of little interest to us. At any given time we are usually interested in only one of the two images — visible channel during daylight passes and IR channel during evening passes. Thus, the image of interest on any particular pass occupies only 30% of the line length. This means that if we randomly slap paper on the drum, fire up the recorder, and print a picture, with no attention to phasing at all, the chances are 70% that the desired image will not fall on the point where the paper overlaps. This means that 70% of the time a usable picture could be printed with no attention to phasing. The other 30% represents situations where you would have to repeat runs or tape the complete picture from the overlapping paper ends.

There are two general situations where phasing is required. First, if you are a purist and want all the satellite data printed out neatly and uniformly, phasing will be required to correctly "place" the image on the photographic paper. Secondly, if you are using an oversize drum to increase picture size, and the stock paper size will not fit completely around the drum, you must phase to accurately align the desired part of the satellite image onto the portion of the drum which is covered by paper. The end of the construction phase will outline a very simple phasing system to accomplish precision alignment. The major disadvantage of phasing is that an external oscilloscope, or other CRT display, is required.

Solid State Module

The most critical functions in the system are performed by a simple module using ICs and other solid state devices. The circuit (Fig. 2) is simplified considerably by the use of several devices in more than one function,

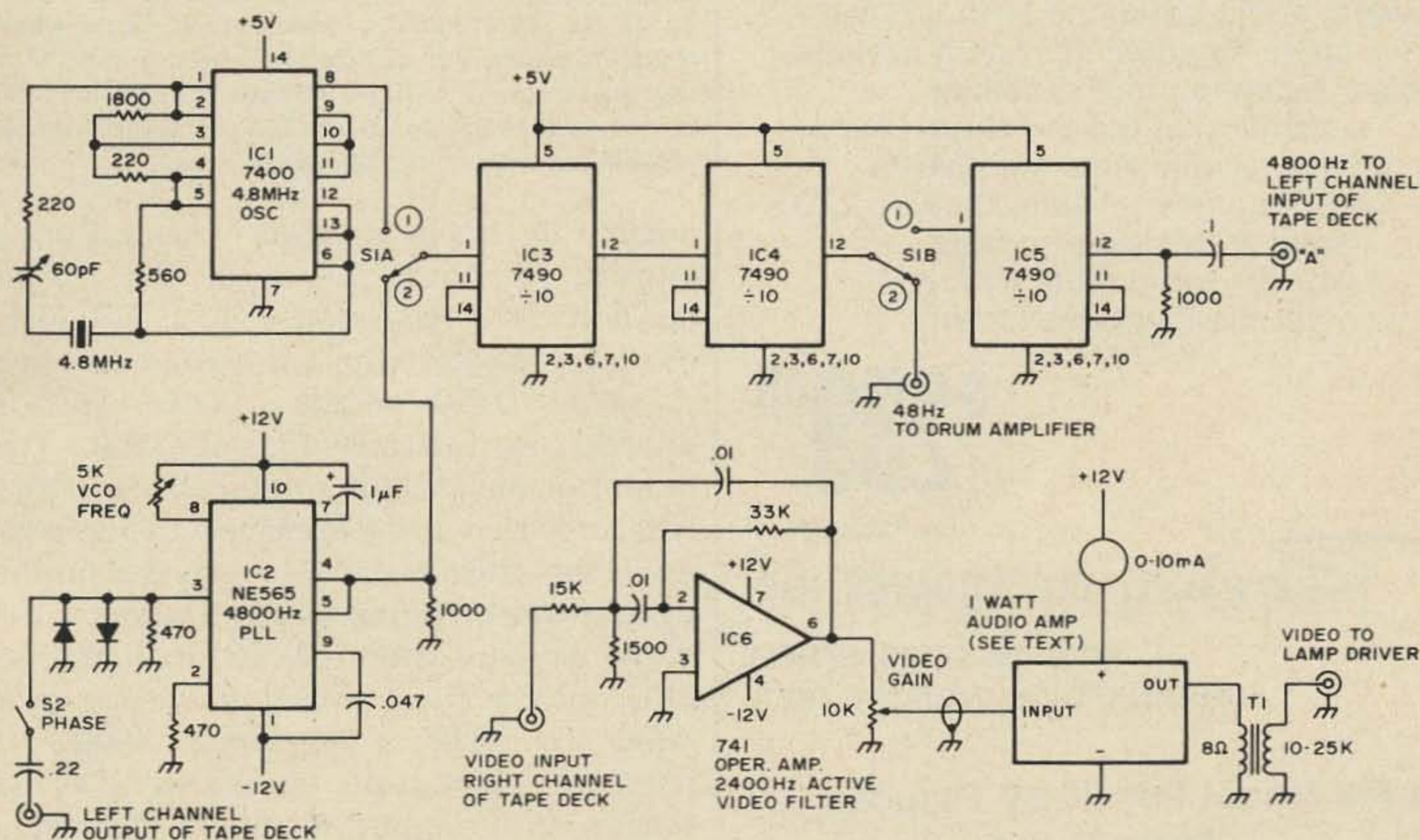


Fig. 2. Solid state module. All resistors $\frac{1}{4}$ - $\frac{1}{2}$ Watt; capacitors are 1 V mylar. S1 — DPDT; pos. 1 for receive, pos. 2 for display. S2 — SPST for phasing, open for phase, close for lock and run. VCO frequency adj. should be set for a free running frequency (S2 open) of 4700 Hz at pins 4 and 5 of IC2. The 60 pF capacitor in the 4.8 MHz oscillator circuit (IC1) should be set for an oscillator frequency of 4.8 MHz or exactly 4800 Hz at output jack A with S1 in position 1. The 4.8 MHz crystal should be a precision series resonant AT cut — send the oscillator schematic with the order. Surplus crystals might be suitable provided you can get them on frequency. The better the crystal the better the long term stability of the reference source.

Regency brings you the best
in 220 MHz transceivers

MODEL HR-220



American Made Quality at Import Price

Full 12 Channels with 10 Watts Power Out

Compactly designed for dash mount, this little transceiver gives you big signal power on the go . . . at low current drain. 3 watts audio equipped with a noise operated squelch system provides clear reception and excellent sensitivity of $0.4 \mu\text{v}$. High-Low power switch. American Made and Regency reliable, the HR-220's solid state design brings you tough, top quality circuitry at the low price of only

\$239⁰⁰

Amateur Net

Regency **ELECTRONICS, INC.**

7707 RECORDS STREET
INDIANAPOLIS, INDIANA 46226

An FM Model For Every Purpose . . .
Every Purse



HRT-2

5 Channel Hand-Held
2 Meter FM Transceiver



HR-2MS

8 Channel Transcan
2 Meter FM Transceiver



AR-2

2 Meter FM
Power Amplifier

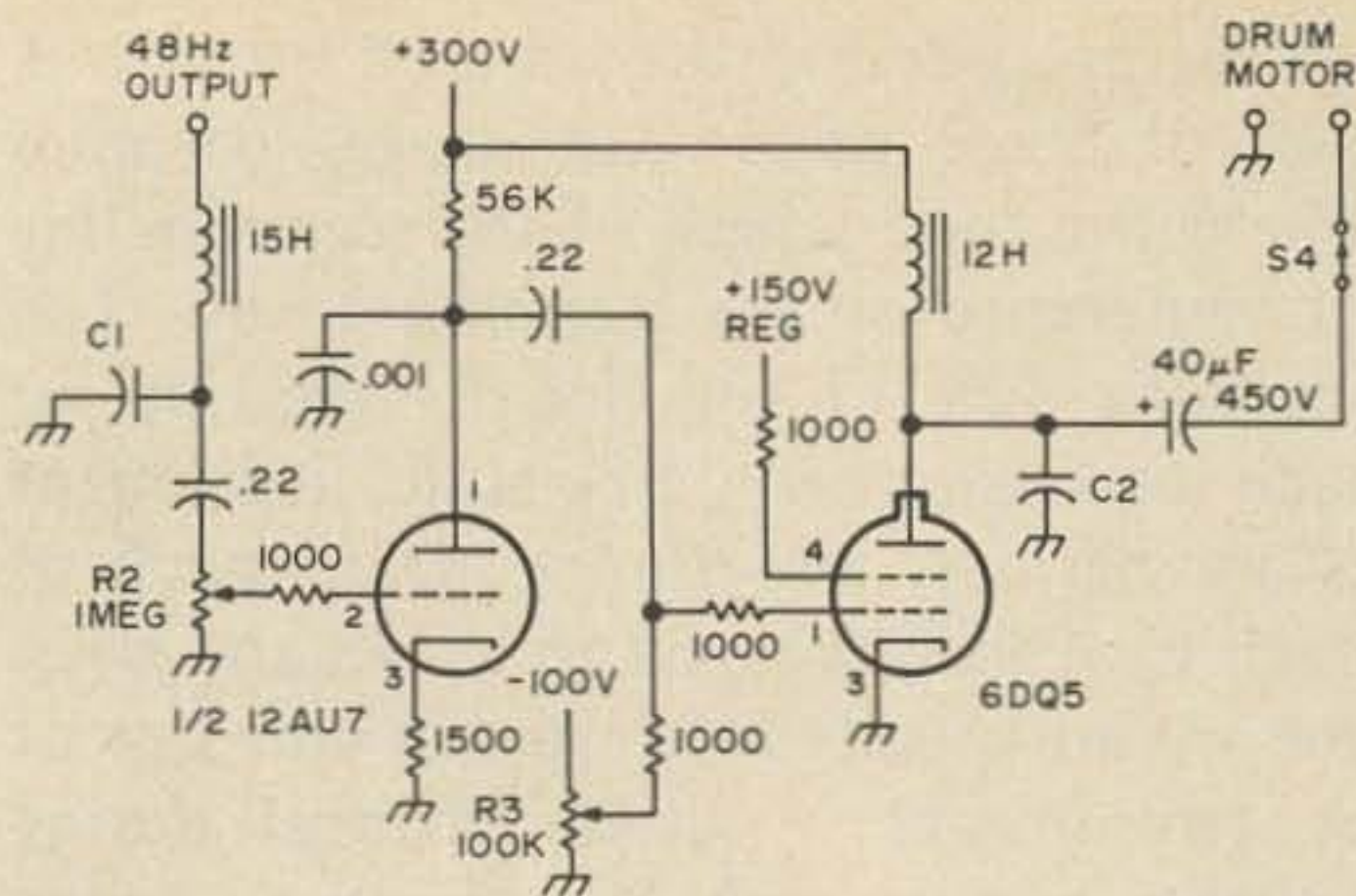


Fig. 3. Drum amplifier. Unless otherwise noted, fixed resistors are $\frac{1}{2}$ W 10%; capacitors are disc ceramic; pots are 2 W composition. Within reason, any inductance can be used with the input and output chokes, as long as a suitable value capacitor is used to bring the tuned circuit to 48 Hz resonance. C1 and C2 should be mylar units and the required capacitance can be obtained by paralleling smaller values. With the choke values shown, C1 should be 0.7 mF and the individual capacitors may be 100 V units. C2 should be 0.9 mF, and 600 V units should be used. If other chokes are used, an LC of 1.1×10^{-5} at 48 Hz may be used to calculate the value of the capacitor required. The input choke may be relatively high resistance but the output choke handles power and thus should be as low a resistance as possible. Adjust R2 for 120 V ac at the motor when driven by 48 Hz. S4 - SPST - open to stop motor while changing paper, etc. R3 should be set for -50 V at the center arm. A fixed voltage divider may be substituted; calculate on the basis of the fixed bias voltage available from the supply in use.

notably the ICs in the divider chains. During satellite reception, S1 is in the receive position (1). IC1 serves as a 4.8 MHz oscillator whose output is routed to three successive 7490 decade counters (IC3-5) providing a total division of 1000. The output of the chain is a 4800 Hz signal that is recorded on the left channel of the deck while the satellite signal is recorded on the right channel. During picture readout S1 is in the display position (2). IC2 is an NE-565 PLL with a free running frequency near 4800 Hz. The pre-recorded 4800 Hz reference signal locks up the PLL, whose square wave output is routed through a divide by 100 countdown chain (IC3 and 4), providing a phase locked 48 Hz output which will be used to drive the drum motor amplifier. Satellite video from the right channel of the tape deck is routed through IC6 which serves as a 2400 Hz bandpass filter with a bandwidth of 1000 Hz and


unity gain. The filtered video signal is then routed to a small IC or transistor amplifier which serves as a preamp to drive the video amplifier circuits for the light gun. Any small 1 Watt audio amplifier will work here, including any of the many small transformerless IC circuits. I use a small discrete component amplifier from Radio Shack. Very little output is required into the coupling transformer (T1), and a small 0-10 mA meter in either the + or - supply line to the amplifier will provide an indication of video level. Virtually all of the small amplifiers available, whether IC or discrete, are class B, drawing very little current when idling and, when driven, having current roughly proportional to the drive level. Few devices are required for this module, and the whole circuit can be assembled on a small piece of perf board with 0.1" hole spacing to accommodate the ICs. Sockets are recommended for the integrated circuits so they will not be damaged in wiring up the unit. I have my module mounted in a separate cabinet because it is part of the CRT system



The main chassis of the FAX unit. The 12AU7 and 6DQ5 in the drum amplifier circuit are toward the back of the chassis, with the lamp driver circuits (12AU7 and 6CL6) along the front edge. T2 in the lamp driver chain is mounted below the chassis. The front panel meter (M2) monitors lamp current. The three toggle switches on the front of the chassis control the on/off functions of the drum motor, traverse motor and lamp. The cable to the light gun plugs into the top of the chassis near the 6CL6, while the power cables for the FAX recorder motors plug into connectors on the rear apron.

THE LM-3 VOLKSMETER

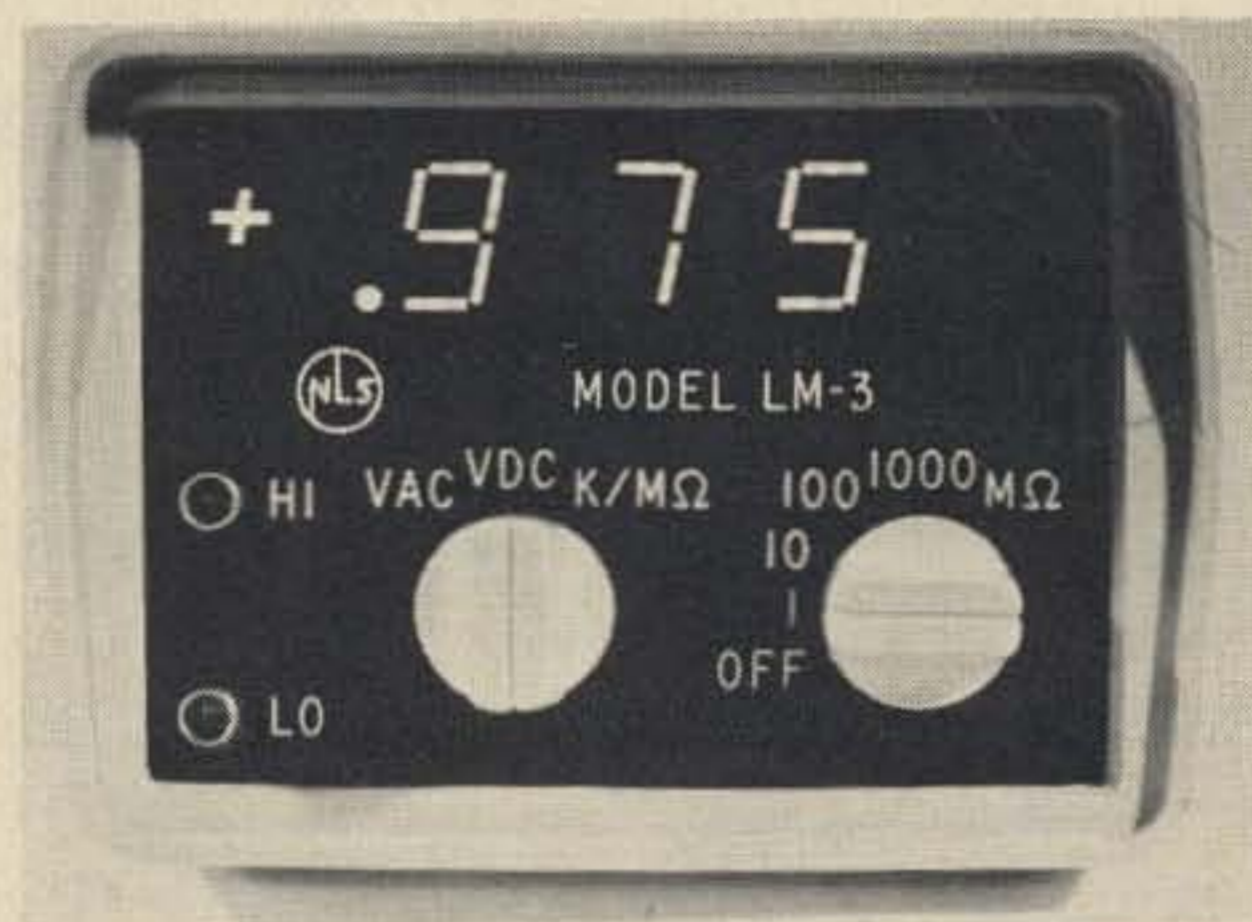World's lowest priced precision digital multimeter
-- more accurate and rugged than the old pointer
meter -- ideal for field service.



With rechargeable
batteries and charger unit

\$125

Now a multimeter with truly outstanding features.

- Super Rugged: Ideal for field service use - you don't have to recalibrate or replace if dropped.
- High Input Impedance: 10 megohms on all ranges; no more circuit loading.
- Automatic Polarity: No more test lead reversing or switching.
- Automatic Zero: No more adjustment of the zero when you change range, function or position; no more full scale ohms adjust.
- Full three digits without parallax or required interpolation; a 0.33" high LED display. A true one percent meter.
- 13 ranges: 4 vdc, 4 vac and 5 ohms.
- Measurements: Up to 700 vdc or 500 vac and up to 10 megohms.
- Small Size: 1.9" H x 2.7" W x 3.9" D.
- Versatile: Operates from standard 115V outlets or on self-contained rechargeable batteries.
- Fully Protected: No damage from overload on volts and ohms measurements.

Optional Features:

- Leather Case.
- High Voltage Probe: For measuring up to 30KV.
- Current Shunts: One percent accuracy from 1 μ A to 1A.

LM-3 basic meter also available in four digits with 0.02% accuracy. Ask for LM-4.

See your local distributor!

Distributor inquiries invited.



Non-Linear Systems, Inc.

Originator of the digital voltmeter.

Box N, Del Mar, California 92014

Telephone (714) 755-1134 TWX 910-322-1132

as well, but if FAX alone is desired it can be mounted on the same chassis as the tube circuits to be described.

Drum Motor Amplifier

Fig. 3 shows the class AB₁ amplifier used to power the drum motor. Although a solid state circuit could be used for this purpose, I decided to go the tube route and use an existing supply. There is nothing original about the circuit — it's cribbed from marginal notes on a letter from W6WMI. The circuit is straightforward and trouble free. A 15 H choke and capacitor, resonant at 48 Hz, distorts the square wave (from the solid state module) to a good sine wave, and drives ½ of a 12AU7 and a 6DQ5. The 6DQ5 output stage is resonant at 48 Hz and drives the drum motor windings through a 40 mF coupling capacitor. The input level to the 12AU7 is adjusted to provide 120 V ac to the motor windings. The filament voltage, bias voltage and 300 volts are obtained from my SB-102 power supply. You can build a separate supply of course, but if a suitable supply is already available a new power cable is certainly cheaper than what they are asking for power transformers these days. The regulated +150 volts can be obtained from the 300 volts via a 5k Ohm 8 Watt dropping resistor and an OA2 regulator.

Lamp Driver

Fig. 4 shows the lamp driver circuit which operates a glow modulator tube in the light gun. The circuit is a modified version of a

circuit described by Ruperto in a recent Amateur Scientist section of Scientific American (Jan. 74). The original circuit was designed by W6KT. In my version, the filtered hi-Z video from the solid state module is fed to a 12AU7 with its triode sections in parallel. The 12AU7 drives T2 with the full wave diode detector circuit in the secondary. The detected video is filtered to remove 4800 Hz components (resulting from full wave detection of the 2400 Hz satellite video subcarrier) by the 88 mH toroid and associated capacitors. The filtered waveform, now containing only video components, is fed to a 6CL6, which drives a Sylvania R-1168 glow modulator tube in the light gun. A meter in series with the lamp provides an indication of lamp current. The polarity of the video detector diodes results in maximum amplitude from the glow tube in black picture areas and minimum amplitude in white areas. The black level, maximum lamp current with no video input, is set by the 250 Ohm pot in the cathode circuit of the 6CL6.

Both the drum amplifier and the lamp driver can be assembled on a single chassis (see photo) along with the 150 volt VR tube. The modest power requirements of the unit are easily met with a transceiver power supply.

Drum Size and Motor Requirements

Synchronous motors are used in the facsimile recorder to achieve the required accuracy in all of the phases of picture display. Such motors are available in a

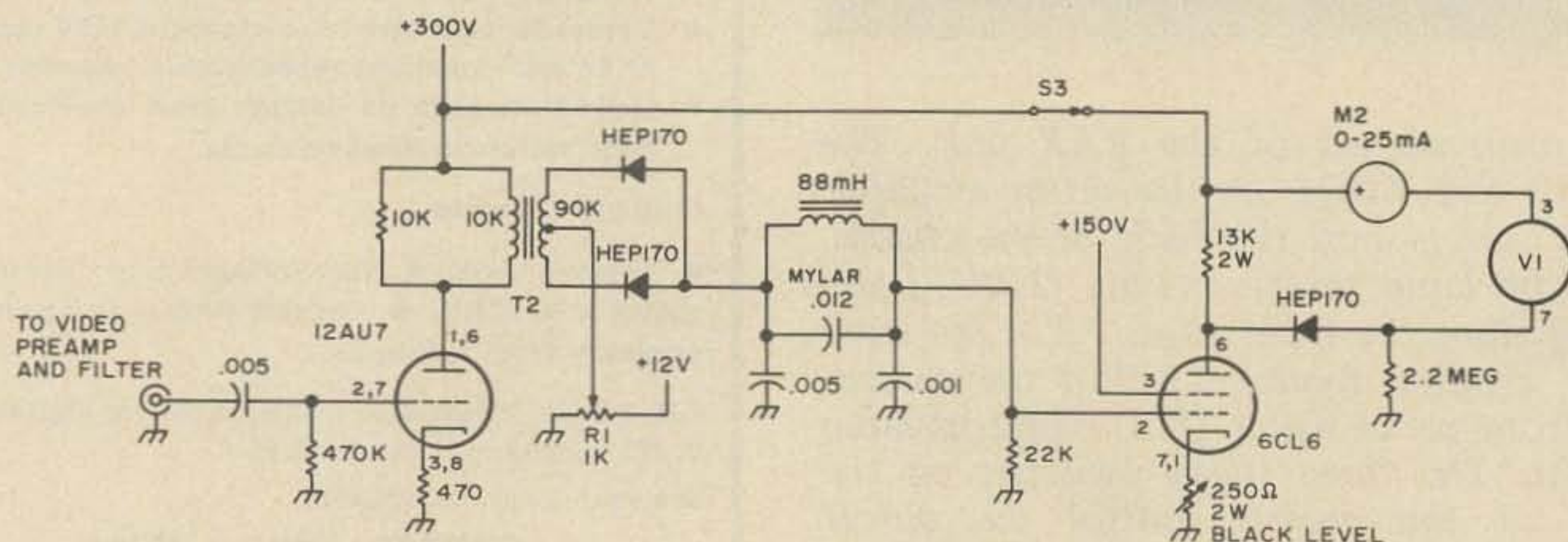


Fig. 4. The lamp driver circuit. Unless otherwise noted, all fixed resistors are ½ W 10%; capacitors are disc ceramic; pots are 2 W composition. R1 — start with +2.4 V on T2 centertap. Black level — adj. for 10-20 mA of lamp current (M2) with no video input. Exact level depends on paper used (see text). The 0.012 mF capacitor can be made up by paralleling 100 V mylar units of .01, .001, and .001 mF. See set up instructions for input level adjustment. S3 — SPST — turns off the lamp on standby.

Drum Diameter (inches)	Design rpm	Drive Motor Selection	Earth Scan Width (")	Picture Length (10 min. display)
2.0	6.9	6/60	1.9	3
2.25	7.7	8/60	2.1	4
2.5	8.6	8/60	2.4	4
2.75	9.5	12/48	2.6	4.8
3.0	10.6	10/60	2.8	5
3.25	11.0	10 or 12/60	3.0	5 or 6
3.5	12.0	12/60	3.3	6
3.75	13.0	12/60	3.6	6
4.0	13.8	12/60	3.8	6
4.25	14.7	20/48	4.0	8
4.5	15.5	20/48	4.3	8
4.75	16.4	20/48	4.5	8
5.0	17.1	20/48	4.7	8
5.25	18.0	20/60	5.0	10
5.5	18.9	20/60	5.2	10
5.75	19.8	20/60	5.4	10
6.0	20.6	20/60	5.7	10

Table 1. Traverse drive motor requirements and picture geometry for various drum sizes. The design rpm is the calculated rpm, driving a 20 turn per inch threaded rod, to achieve the proper aspect ratio. The drive motor selection shows the stock motor speed and drive frequency (Table 2) that comes closest to the design figure. The picture width indicates the width of the earth scan image in either the visible or IR channel, and the picture length is based on a ten minute pass. A 15 minute pass would result in an image 1.5 times longer, 20 minutes, 2x, etc.

variety of sizes from small units of 3 Watts or less, used for timing devices such as clocks, to very powerful units. We want motors with sufficient torque to carry out the operations required, but it doesn't pay to go to excessively large motors, particularly in the drum drive, since they would put too high a load on the drum amplifier. Motors rated between 100 and 150 inch/oz. of torque (ratings based on 1 rpm) are about right. It is also desirable to have motors that are reversible. With the recorder built according to the diagram in Fig. 5, if the drum motor turns the drum counterclockwise the light gun should move from the right end of the drum to the left in order to print out the picture. With a standard right hand thread on the lead screw rod this means the traverse motor should also turn

counterclockwise. If reversible motors are used, once the first picture is finished both motors can be reversed (clockwise) and a picture, with the correct orientation, can be printed out going back from the left end of the drum to the right. Once that picture is finished, the motors can be reversed again to print another picture in the same direction as the first. Hurst series DA synchronous motors, available from distributors such as Allied, are ideal since they are reversible with a SPDT switch and are rated at 150 inch/oz. torque. If a 60 rpm Hurst motor is operated on 48 Hz ac, the drum will turn once for every line of video, causing the visible and IR images to be displayed side by side. The drum size is all important in defining the remaining parameters of the system for in order for the picture to have the proper appearance the light gun must traverse the drum at a speed proportional to the drum diameter. If the traverse rate is too slow for the drum size in use, the picture will be too short in relation to its width, distorting clouds and other features. If the rate is too fast the picture will be "stretched" vertically, again distorting the proper aspect ratio. Since we standardize on the use of a 20 turn per inch threaded rod in the traverse assembly, the only variable in achieving the proper traverse speed with any

60 Hz rpm	48 Hz rpm
6	4
8	6.4
10	8
12	9.6
20	16
30	24
60	48 (use for drum drive)

Table 2. Standard Hurst DA series, 150 inch/ounce synchronous motors (reversible) showing their operating speeds (rpm) on 60 Hz (normal) and 48 Hz ac. When ordering, specify the 60 Hz speed.

particular drum size is the rpm of the traverse motor.

Without going into the calculations (which I will gladly supply to anyone who sends an SASE), Table 1 shows the design rpm required for different drum sizes so the resulting pictures will have the proper aspect ratio. Let's say you pick up a nice rolling pin from your local store and find that it measures 2.5" in diameter. According to Table 1, the proper rpm for the traverse lead screw would be 8.6. Fine, now just try to find an 8.6 rpm synchronous motor. As we can see in Table 2, the standard Hurst speeds (available from Allied) are 6, 8, 10, 12, 20, 30 and 60 rpm. No 8.6! The closest we can come is the 8 rpm unit (listed in the motor selection column of Table 1), which will do the job without producing enough distortion

to notice. Let's take another example. Assume a drum diameter of 2.75". The proper design value is 9.5 rpm. If we look at Table 2 we see that a 12 rpm motor, operated on 48 Hz instead of 60, will give an output speed of 9.6 rpm; the motor selection column in Table 1 thus calls for the 12 rpm motor operated on 48 Hz. We would simply hook the motor to the output of the drum amplifier, just as we do for the drum motor. If the motor selection column calls for the use of 48 Hz with any particular motor, the drum amplifier should be used as the ac source, while if 60 Hz is required the normal ac line may be used. Table 1 should be used to pick the proper traverse motor for the drum size you plan to use.

The additional factor which is determined by drum size is the final picture size. The

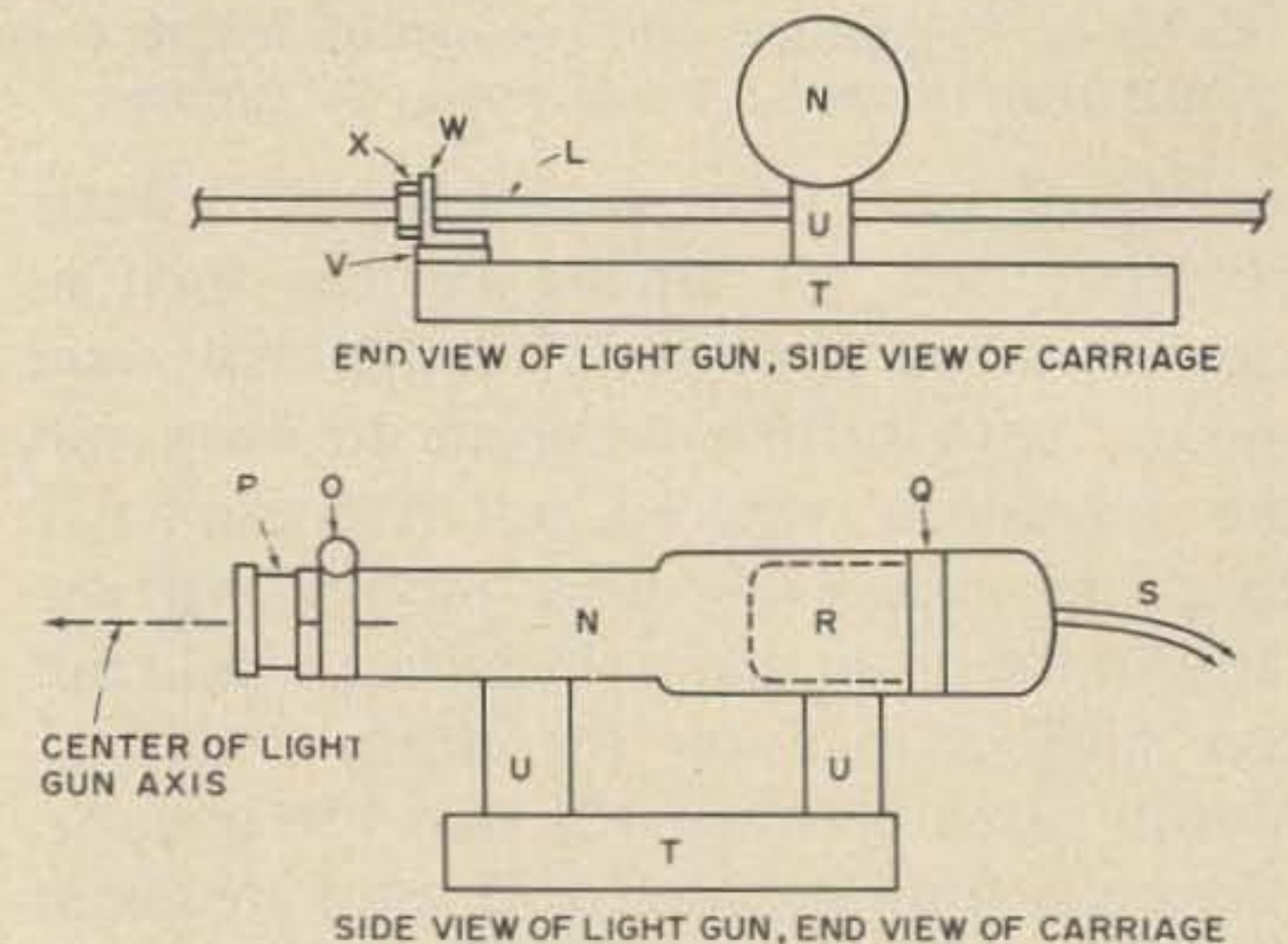
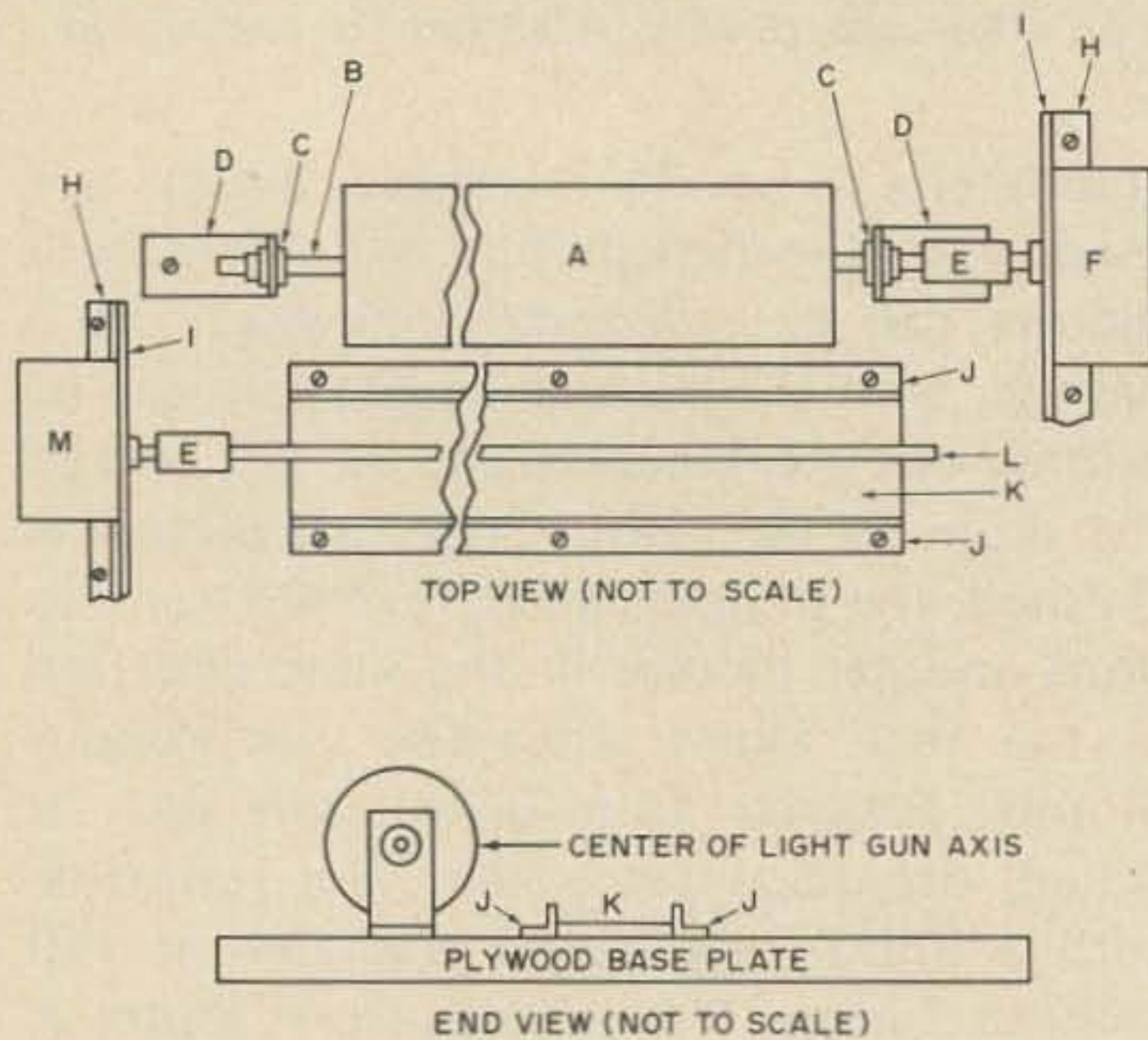


Fig. 5. General views of drum, motors and carriage track.



Fig. 6. Light gun and carriage details.

Key to elements of FAX diagram (Figs. 5 and 6):

- A — drum, plastic rolling pin, or other material.
- B — 1/4" steel rod — epoxied to drum.
- C — cut down (shortened) 3/8" panel bushing for 1/4" shaft, used as bearing.
- D — steel angle brackets mounted to base plate.
- E — stiff rubber coupling from drum shaft to drive motor.
- F — 60 rpm synchronous motor for drum drive.
- G — not used.
- H — 1/2" aluminum angle bracket to fasten motor mounting plate to base.
- I — 1/16" fiberglass PC stock for motor mounting plates.
- J — 1/2" aluminum angle stock screwed to base to form carriage track.
- K — glass plate epoxied to base between rails.
- L — 1/4" 20 threaded rod for carriage drive.
- M — synchronous motor for carriage drive (see text for speed).

- N — 1 1/4" flared plumbing fitting for body of light gun.
- O — hose clamp to lock lens into the slit end of the light gun.
- P — standard 1 1/4" telescope eyepiece for focusing light beam.
- Q — octal socket and shell for glow modulator tube.
- R — R-1168 glow modulator tube, slide fit into large end of flared tubing.
- S — flexible leads from glow tube socket to main chassis.
- T — wooden base of carriage assembly.
- U — wooden supports for light gun — epoxy to tube.
- V — double stick foam mounting tape.
- W — 1/2" aluminum bracket stock to support traverse nut.
- X — 1/4" 20 hex nut epoxied to support bracket.

the best slo-scan deal in town

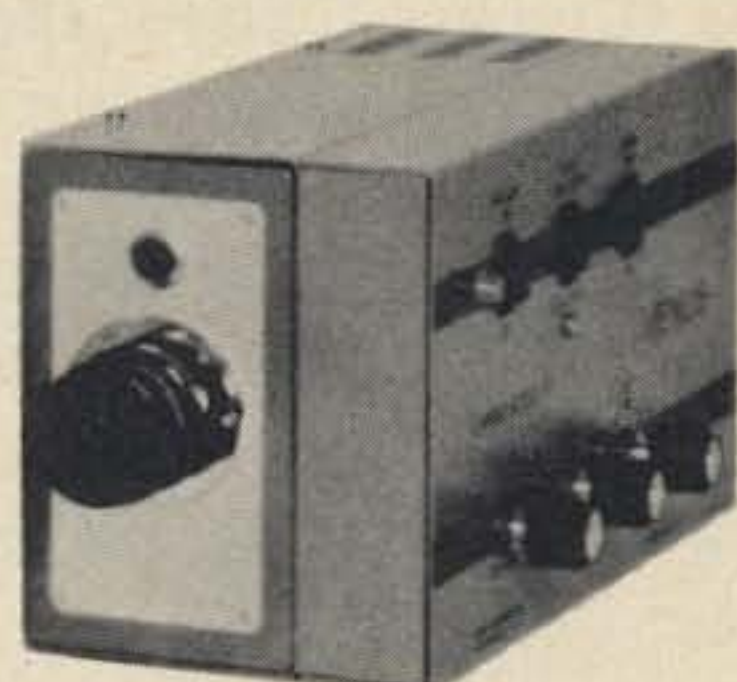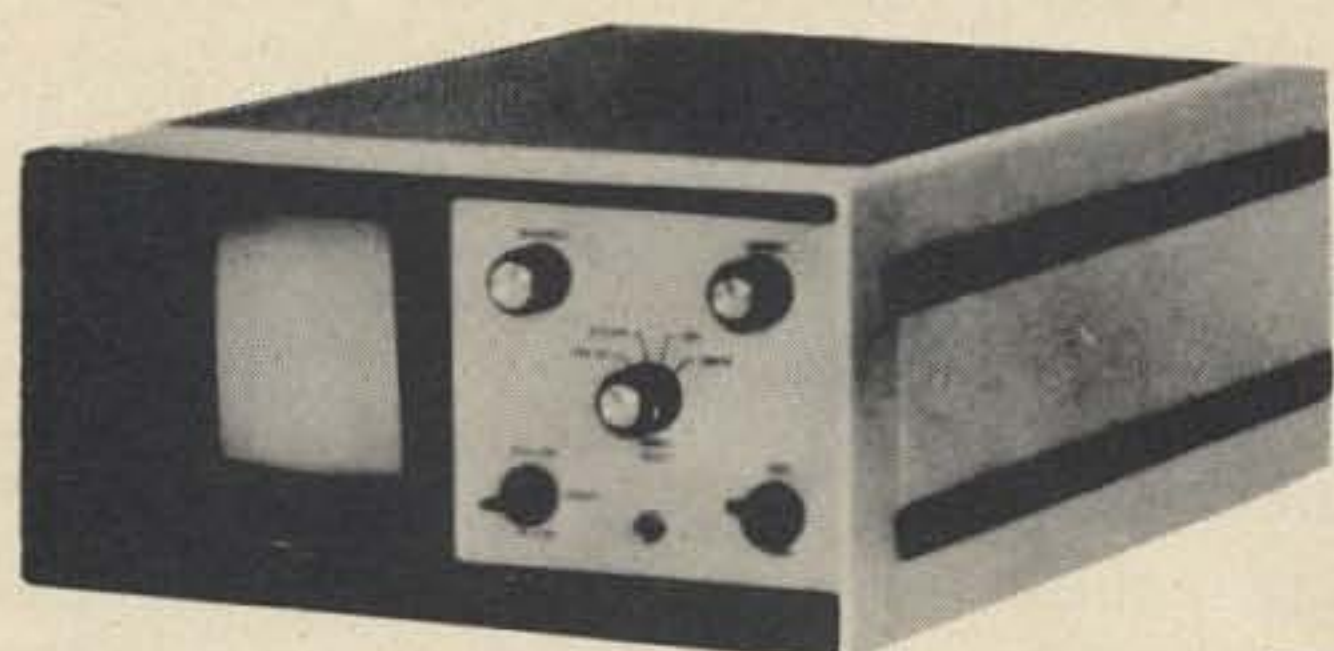

WIN
WITH



*** PRICE:**

SS2 MONITOR STILL ONLY \$349

*** KIT:**

THE VENUS SS2 IN KIT FORM FOR ONLY \$269

- 25 PAGE MANUAL
- TEST AND ALIGNMENT TAPE

*** PERFORMANCE:**

ACCUSYNC[™] OSCILLOSCOPE DISPLAY OF SSTV SIGNAL
FAST SCAN/SLO SCAN CAMERA

- USE CAMERA WITH YOUR HOME TV SET
- FOCUS ON POSTAGE STAMP

*** COMPLETE LINE:**

- SS2 MONITOR \$349
- SS2K MONITOR KIT \$269
- C1 FAST/SLO SCAN CAMERA \$469
- P1 POLAROID[™] CAMERA ADAPTER \$34.50
- V1 VIEWING HOOD \$14.50
- T1 TRIPOD \$24.95

*** LOCAL DISTRIBUTORS:**

VENUS SSTV AVAILABLE FACTORY DIRECT OR FROM
ONE OF THE FOLLOWING AUTHORIZED DISTRIBUTORS:

Aerocom LTD
Rua Henrique Martins 204
Manaus, Brazil

Argon Electronics
Miami Springs, Fla.

CFP Enterprises
Lansing, N.Y.

Harrison Electronics
Farmingdale, N.Y.

A-G Co., Inc.
Imperial, Pa.

A and W Electronics
Medford, Mass.

Electronic Distributors
Muskegon, Michigan

Henry Radio
Los Angeles, Calif.

Amateur Electronics Supply
Milwaukee, Wisc.
Cleveland, Ohio
Orlando, Fla.

Barry Electronics
New York, N.Y.

Goldstein's
Pensacola, Fla.

Hobby Industry
Council Bluffs, Iowa

Venus Scientific Inc.

The company that put high voltage on the moon, now brings you expanding amateur radio technology.

399 Smith Street
Farmingdale, N.Y. 11735
Phone 516-293-4100
TWX 510-224-6492

2.5" diameter drum mentioned previously will print out an earth scan image in both the IR and visible light channels that is 2.4" in width. The length of the image will depend on how much of the pass is displayed — Table 1 assumes 10 minutes. For a 10 minute pass with the 2.5" drum, both the IR and visible channel images would measure 2.4 x 4 inches — about the size of a Polaroid print. With the light gun system described, the images should be perfectly clear with well defined line structure under high magnification. Rolling pin style drums permit two passes (10 minutes each) to be displayed on a single 8x10" piece of photographic paper.

If you simply must have larger pictures, there are two ways to go about it. The first involves running the drum at 96 rpm (a 120 rpm motor on 48 Hz) and electronically blanking out alternate lines of video so that only the visible or IR image is displayed. The traverse motor speed for the lead screw must also be doubled for this approach but the picture comes out twice the size. If only visible channel data are desired, the line

blanking is not required due to the pronounced level difference between the visible and IR channels, and you will obtain a larger picture with the small drum format. The second method is simply to use a larger drum. The largest size covered in Table 1 is 6" in diameter. The image width in this case would be 5.7" and its length, for ten minutes, would be 10", about as much picture as can be packed in an 8x10" sheet of photograph paper. With a drum this large the paper will no longer cover the entire surface, so in effect, depending on how you phase the picture, you will be printing only the IR or visible image unless you use oversize paper. Larger drums can be made from almost any cylindrical material including metal juice cans, cardboard tubes, or custom fabricated assemblies. The height of the drum bearings and the height of the light gun must of course be adjusted to your drum size. The only requirement in fabricating a larger drum is that it must turn true when mounted on its shaft; otherwise, portions of the paper will be out of focus as the drum wobbles. Fig. 5 shows a diagram of

NEW! THE FINEST COMMUNICATIONS FILTER AVAILABLE

- WIDELY VARIABLE FREQUENCY AND SELECTIVITY!
- PEAK, NOTCH AND LOWPASS POSITIONS FOR SSB, CW, AM, FM & DIGITAL MODES!
- EXTREMELY STEEP SKIRTS (NOT A SIMPLE ONE-STAGE DESIGN).




AT LAST! An "infinitely-variable filter to combat any interference in any mode — our QF-1. • One knob adjusts its frequency from 250 to 2500 Hz, in all 3 positions. Zero-in on any signal without touching your rcvr. Optimize response instantly! • Peak CW, TTY, etc. with selectivity variable from 50 Hz to flat! Eliminate whistles, jammers, CW, etc. with a wide, deep (to 70 dB) notch. With variable width & frequency, it really works! • Reject SSB, Am, FM, etc. hiss & splatter in the sharp-cutoff lowpass position! • 8 IC op amps plus pwr. amp. 1 Watt peak to spkr or phones. Improves even the best \$2000+ rcvrs in all modes! Vastly superior to a 400 Hz IF CW filter, or any "fixed-frequency" filter. Use with any rcvr or xcvr made. Just plug into the phone jack!

Model QF-1. "The Finest" 115 VAC. 5x4x3 1/2". \$52.95
 Model QF-2. Basic circuit-board (2x4x3 1/4") version for custom installation. 5 minute hookup to receiver volume control. Requires 6 to 30 VDC. Less pwr amp, etc. 10" leads to 3 controls. Instructions. \$32.95.
 Add \$1.50 postage/handling in U.S. Add 6% tax in CAL. Add 10% outside N. America (airmailed). 1 yr warranty.

ISN'T IT TIME YOU INVESTIGATED WHAT AN ACTIVE FILTER CAN DO FOR YOU? SEND FOR FREE "TIPS FOR SELECTING AN ACTIVE AUDIO FILTER."

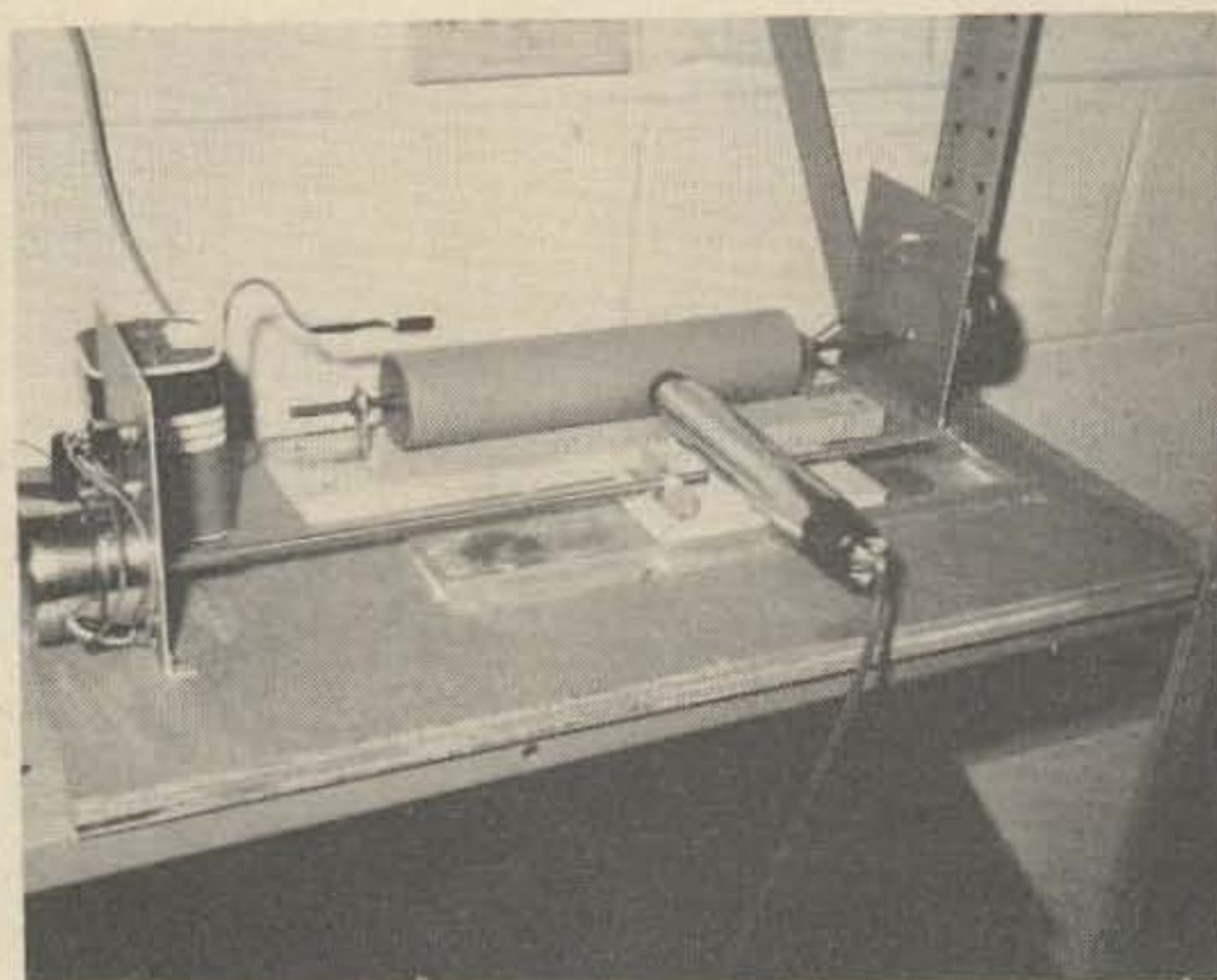**AUTEK RESEARCH
 BOX 5390F, SANTA MONICA CA 90405**



The author's FAX recorder. The relationship of the various parts should be clear. The reversing switches and capacitors for the Hurst motors are mounted on the motor mounting plates. The reed switch and battery used for picture phasing (see text) are also shown.

the drum and traverse assemblies and Fig. 6 the details of the light gun and carriage.

Next month: Construction and set up.

... WB8DQT

D. A. Bunday G3JQQ
 10 Smythe Road
 Swindon Village
 Cheltenham,
 Glos.
 United Kingdom

Where is your simplified, sensitive millivoltmeter?

Here's a practical instrument suitable for home construction which is based upon an integrated circuit (NATIONAL type LM 4250 C). Switched ranges of 5 mV to 500 V are provided.


Construction

Layout has not proved to be critical in the prototype but input leads and associated switching have been kept compact; 2% tolerance resistors have been used throughout. Initial zero adjustment on the 5 mV range is set by selection of R_b in association with potentiometer R_2 which is used for

fine control. No zero drift has been observed on the prototype even on the most sensitive range.

An internal calibration check is provided on the 5 V and 50 V ranges by a push-button connection to the positive supply rail. This facility is used to adjust the meter deflection initially to 1.4 V on the 5 V range by means of pre-set resistor R_m . The value of the associated fixed resistor r_f may also be varied if found necessary to suit the internal resistance of the meter used.

A miniature main switch serves to reverse the input polarity when required. The power

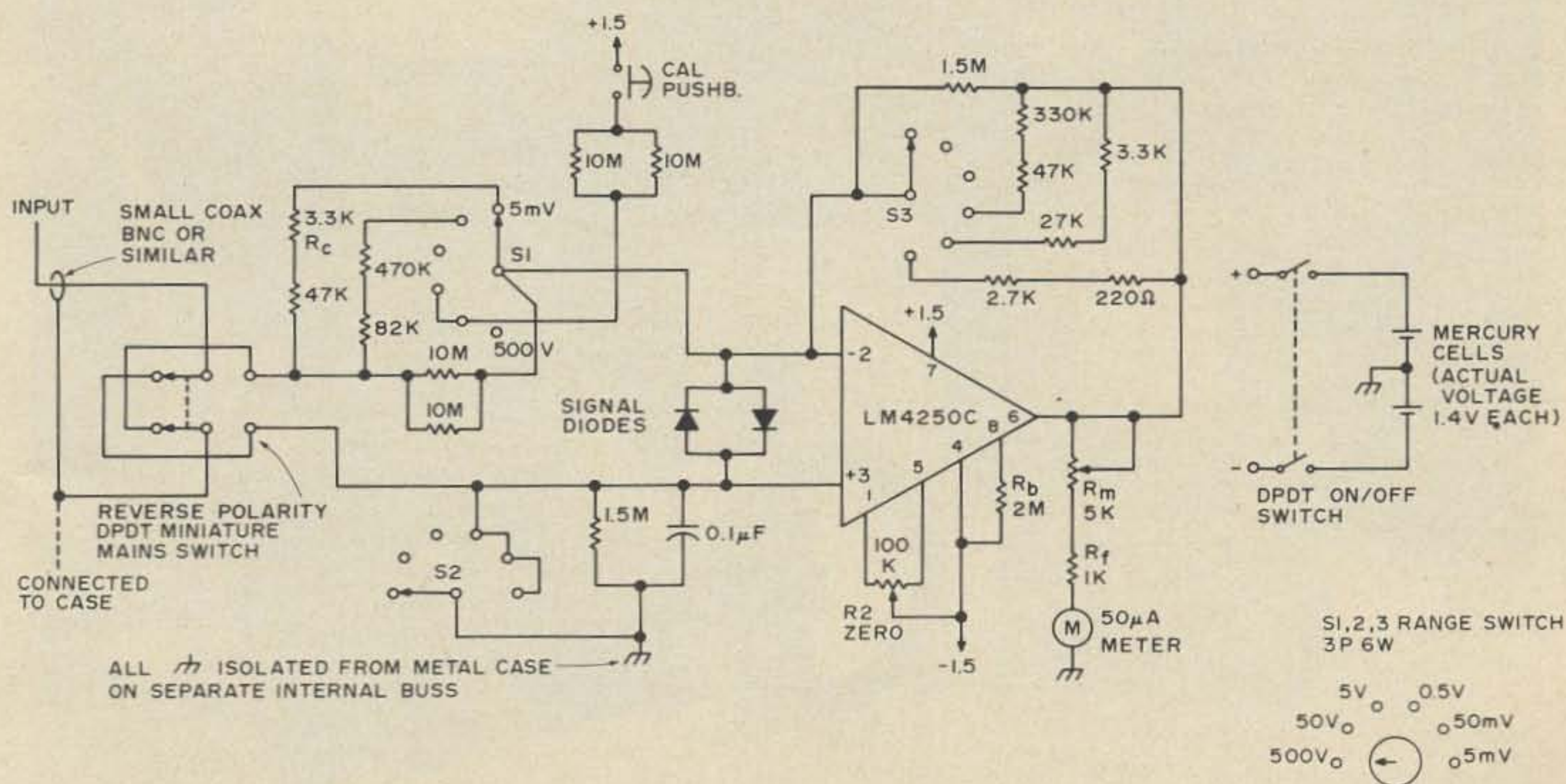

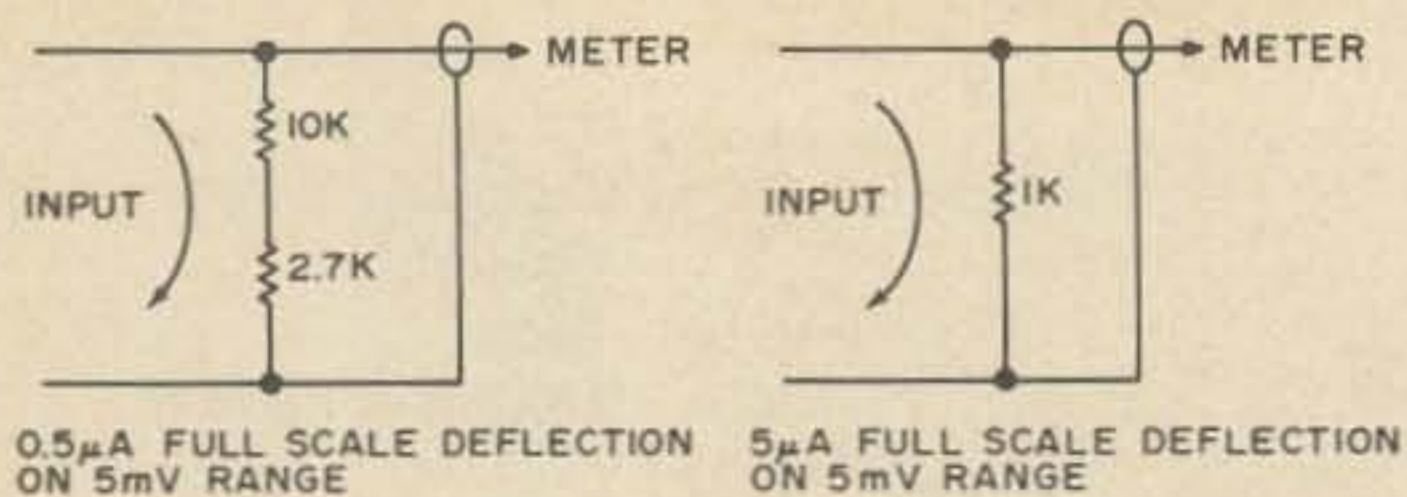


Fig. 2. External shunts.

supply comprises two mercury-button type cells (ER 675) contained within a small paxolin tube, spring loaded to maintain contact pressure. Other options are possible, of course. Consumption is minimal, being approximately 60 microamps for full-scale deflection. The unit is housed in an aluminum die-cast box.

Input impedance is approximately the value of R_c for the range concerned, shunted by the input-lead capacitance (approximately 50 k to 5 megohms, according to the range used). Overload protection is provided by two back to back signal diodes. Repeated application of 30 V dc on the 5 mV range has had no detrimental effect on the prototype. External shunt resistors may be used to monitor dc currents down to quite low values. Fig. 2 gives examples scaled for measuring 5 microamp and 0.5 microamp full scale deflection on the 5 mV range.

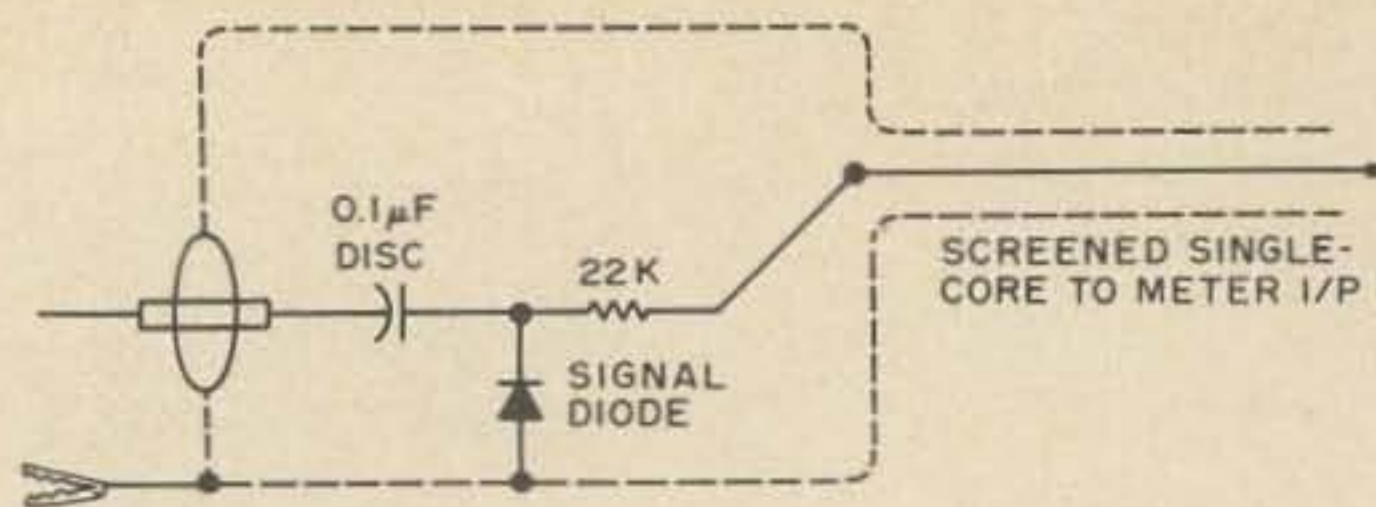


Fig. 3. Rf probe.


Rf may be measured by the use of a suitable probe (see Fig. 3). The approximate input impedance of this device is 6 k at 2 MHz falling to 1 k at 25 MHz. The probe is usable to about 100 MHz.

Application

Since the instrument is sensitive and self-contained, it lends itself to a variety of tasks, some beyond the means of conventional multimeters. The very low power consumption means that battery life is very near shelf life.

The ability to read currents of less than a microamp enables diode and semiconductor device reverse and leakage currents to be read. With the millivoltmeter suitably insulated EHT tube currents can be measured (CRTs).

...G3JQQ

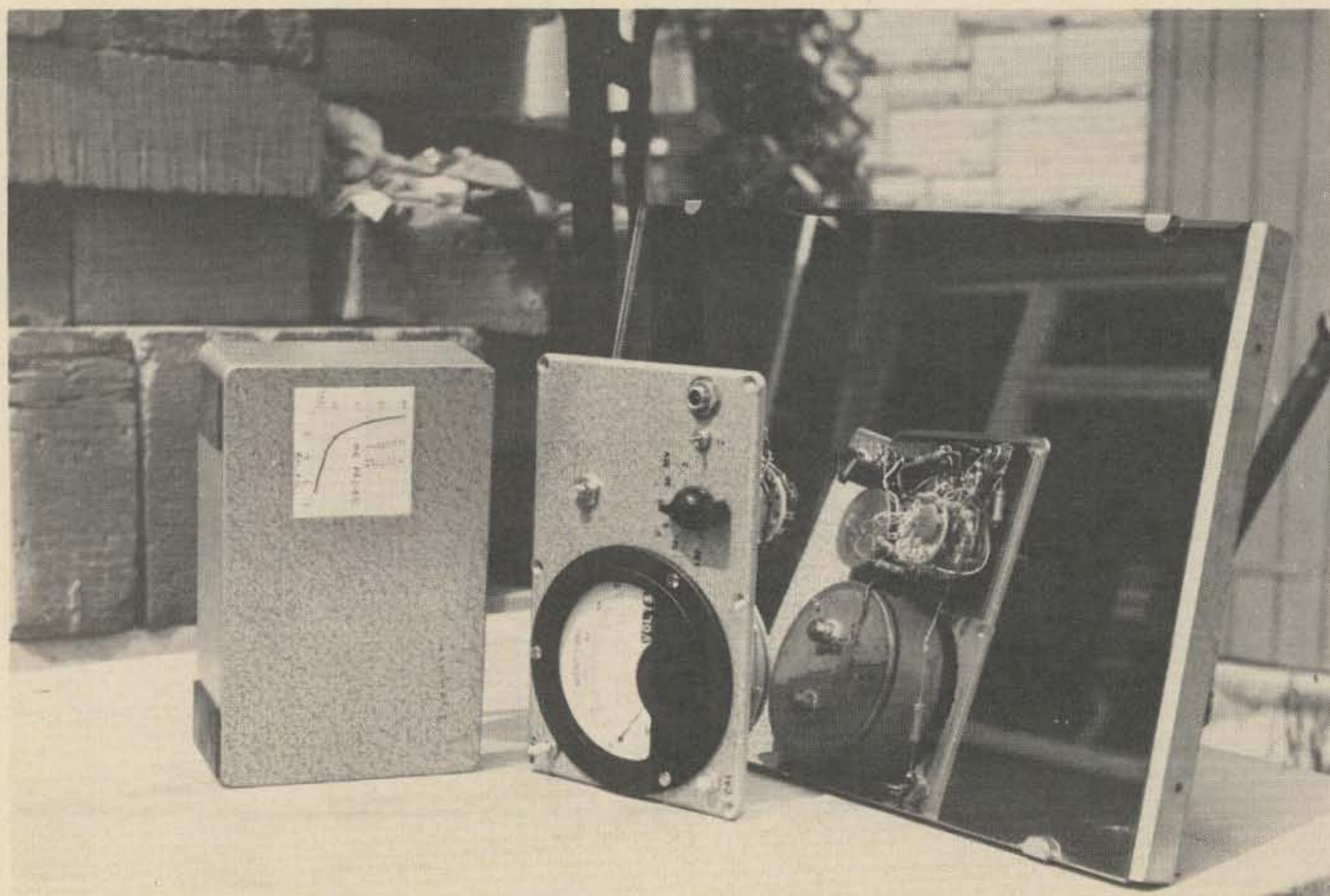

Wilson Electronics Corp.

**FACTORY DIRECT
SPECIAL SEPTEMBER SALE**



1402 SM - 2.5 Watt Hand Held FM Transceiver

SPECIAL INCLUDES:

- Rubber Flex Antenna
- Complete Set Nicad Batteries
- Leather Case
- 52-52 Crystal
- Your Choice of 2 Pair of Common Frequencies Only

Extra Xtals, \$4.50 ea.


**\$320 VALUE
\$199.95**

FEATURES

- 6 Channel Operation.
- Individual Trimmers on all TX and RX Xtals.
- All Xtals plug in.
- S Meter/Battery Indicator.
- 10.7 IF and 455 KC IF.
- 12 KHz Ceramic Filter.
- .3 Microvolt Sensitivity for 20 db Quieting.
- Microswitch Mike Button.
- Size 8 7/8 x 1 7/8 x 2 7/8 in.
- Weight 1 lb. 4 oz., Less Battery.
- Current Drain RX 14 MA TX 450 MA.
- 2.5 Watts Minimum Output - 12 VDC.

ACCESSORIES

SM1	Speaker Mike	\$ 29.95
BC1	Battery Charger	\$ 36.95
XF-1	10.7 Monolithic IF Xtal Filter (Installed)	\$ 10.00
TE-1	Continuous Sub-Audible Tone Encoder (Installed)	\$ 39.95
1410A	12 Watt Amplifier (Mobile)	\$109.00

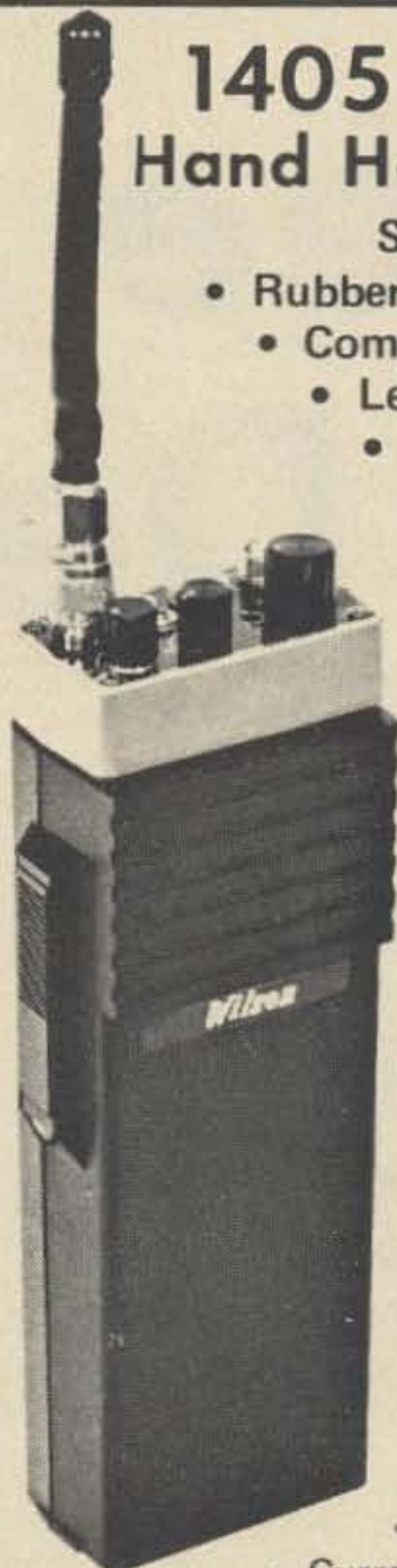

1405 SM - 5 Watt Hand Held FM Transceiver

SPECIAL INCLUDES:

- Rubber Flex Antenna
- Complete Set Nicad Batteries
- Leather Case
- 52-52 Crystal
- Your Choice of 2 Pair of Common Frequencies Only

Extra Xtals, \$4.50 ea.

**\$400 VALUE
\$279.95**

FEATURES

- 6 Channel Operation.
- Individual Trimmers on all TX and RX Xtals.
- All Xtals plug in.
- S Meter/Battery Indicator.
- 10.7 IF and 455 KC IF.
- 12 KHz Ceramic Filter.
- .3 Microvolt Sensitivity for 20 db Quieting.
- Microswitch Mike Button.
- Size 8 7/8 x 1 3/4 x 2 7/8 in.
- Weight 1 lb. 4 oz., Less Battery.
- Current Drain RX 14 MA TX 800 MA.
- Switchable 1 & 5 Watts Minimum Output - 12 VDC.
- High Impact Lexan® Case.

ACCESSORIES

SM2	Speaker Mike	\$ 29.95
BC2	Battery Charger	\$ 36.95
XF-1	10.7 Monolithic IF Xtal Filter (Installed)	\$ 10.00
TE-1	Continuous Sub-Audible Tone Encoder (Installed)	\$ 39.95

**TO: WILSON ELECTRONICS CORP., 4288 S. POLARIS AVE., LAS VEGAS, NEVADA 89103
(702) 739-1931**

SHIP ME _____ 1402 SM _____ 1405 SM _____ SEPTEMBER SPECIALS
PLUS SM1 BC1 SM2 BC2 XF-1 TE1 1410A

ENCLOSED IS _____ CHECK MONEY ORDER MC BAC
CARD # _____ EXPIRATION DATE _____
XTALS _____
NAME _____ ADDRESS _____
CITY _____ STATE _____ ZIP _____
SIGNATURE _____

Enclose additional \$4.50 for prepaid shipping & handling. Nevada residents add sales tax.
Sale ends September 30, 1975.

Three Button TT Decoder

In the process of designing a digital control system for our Touchtone entry repeater, it became necessary to come up with a simple system to recognize Touchtone groups. I decided upon a three button code for all functions as a compromise

between ease of "dialing" and number of operations possible. The system described here is very simple and allows automatic cancelling as well as security for the control functions.

The building block of this system is the TTL dual monostable multivibrator, SN74123. With only three external components each monostable yields a pulse of predetermined length for a short pulse initiated by the Touchtone decoding system.

Two of these monostable multivibrators (one IC package) plus two dual input NAND gates can be used to produce an output pulse upon the reception of the correct three Touchtone signals. My needs for the rest of the control circuits force me to include an inverter after each output yielding an output of a positive (TTL level) pulse whenever the correct combination is received.

There are 3 sets of decoders on each card in my control system. The whole card diagram is seen in the schematic diagram, Fig. 1. There were two dual input NAND gates leftover in the packages required so they are wired as an r/s flip flop. As shown in Fig. 1, the output from this flip flop will be positive upon receipt of a combination in the order of A-B-C and will remain positive until a combination in the order of

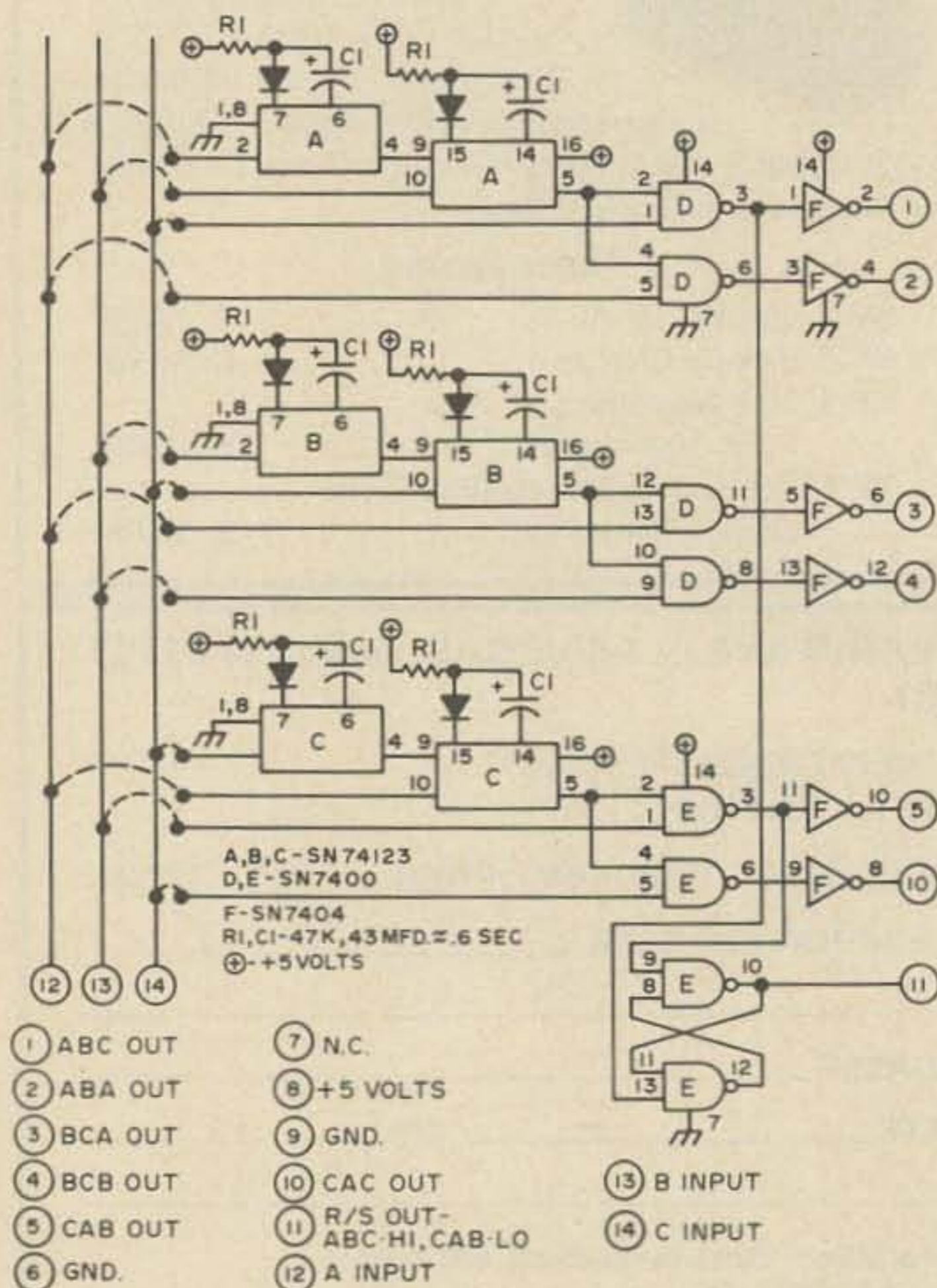


Fig. 1. Schematic.

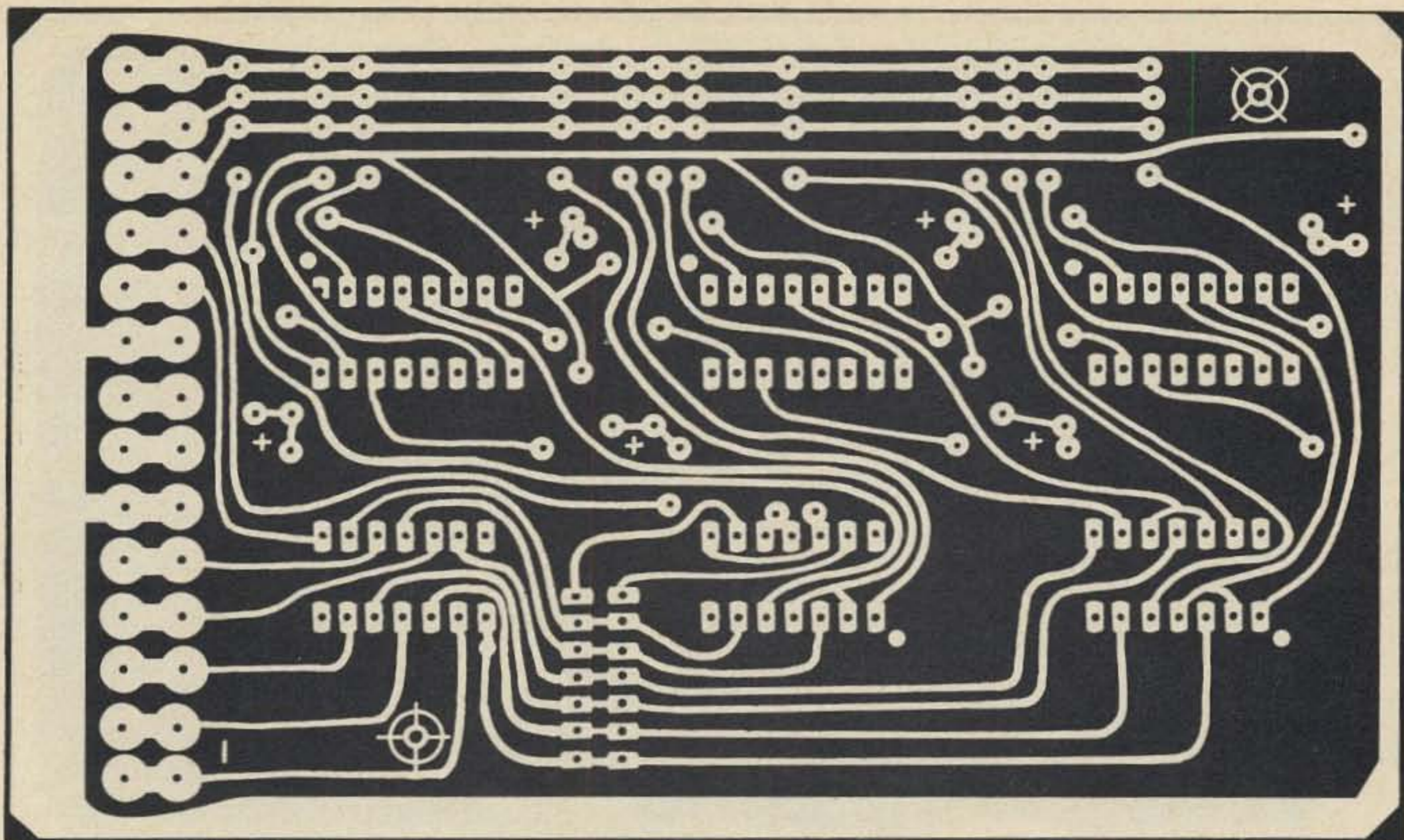


Fig. 2. PC board, foil side (full size).

C-A-B is received. Its state will then change to near ground and remain there until A-B-C is again received.

In our repeater system the tone entry is opened by transmitting 4-8-#. Therefore, the 4 = A, 8 = B, # = C. We can see from this that the r/s flip flop will give a positive output when the tone entry has been opened and will return to the ground state when #-4-8 has been transmitted. While the tone entry automatically closes after one minute of inactivity, it can also be manually closed using this code.

By changing the three inputs to this card and the jumpers to individual decoders, any combination of three may be selected with one exception, which is that no two adjacent inputs may be the same. In our example, #-#-8 would not be an acceptable combination, but #-8-# would be perfectly OK.

If we look at one of the sections of the decoder we may be able to get a better understanding of its operation. The monostable multivibrators, as mentioned before, will give an output for a predetermined length of time when they receive a change of state of their input. They have provided inputs of both polarities and outputs which are complementary. The first monostable, in this system, must give an output when a transition from ground to positive is received. Therefore, the inverting input to

the IC, pin 1, must be grounded and the non-inverting input, pin 2, is connected to the A input of the decoder. Pins 6 and 7 are connected to the timing components. The normally positive output, pin 4, is needed as an input to the next monostable. This output will remain low for a fixed period of time (about .6 second for the example shown). During this time the next input must have been selected. If it has not been, the process is automatically cancelled and must begin again if an output from this decoder is to be indicated.

If the second input, B, is selected during the low time, the inverting input, pin 9, of the second monostable is held low by this output from the first monostable and its non-inverting input, pin 10, is raised to positive by the B input. This will permit a change of state at its outputs. The timing components are the same as the first monostable. This output, the normally low one this time, pin 5, can only result when the first two numbers have been transmitted within the preset length of time. This output also will remain for only about .6 second. So the final tones must be transmitted within this time period or the operation is cancelled and must begin from the beginning.

If the C or A is received within this final period, its respective NAND gate will see

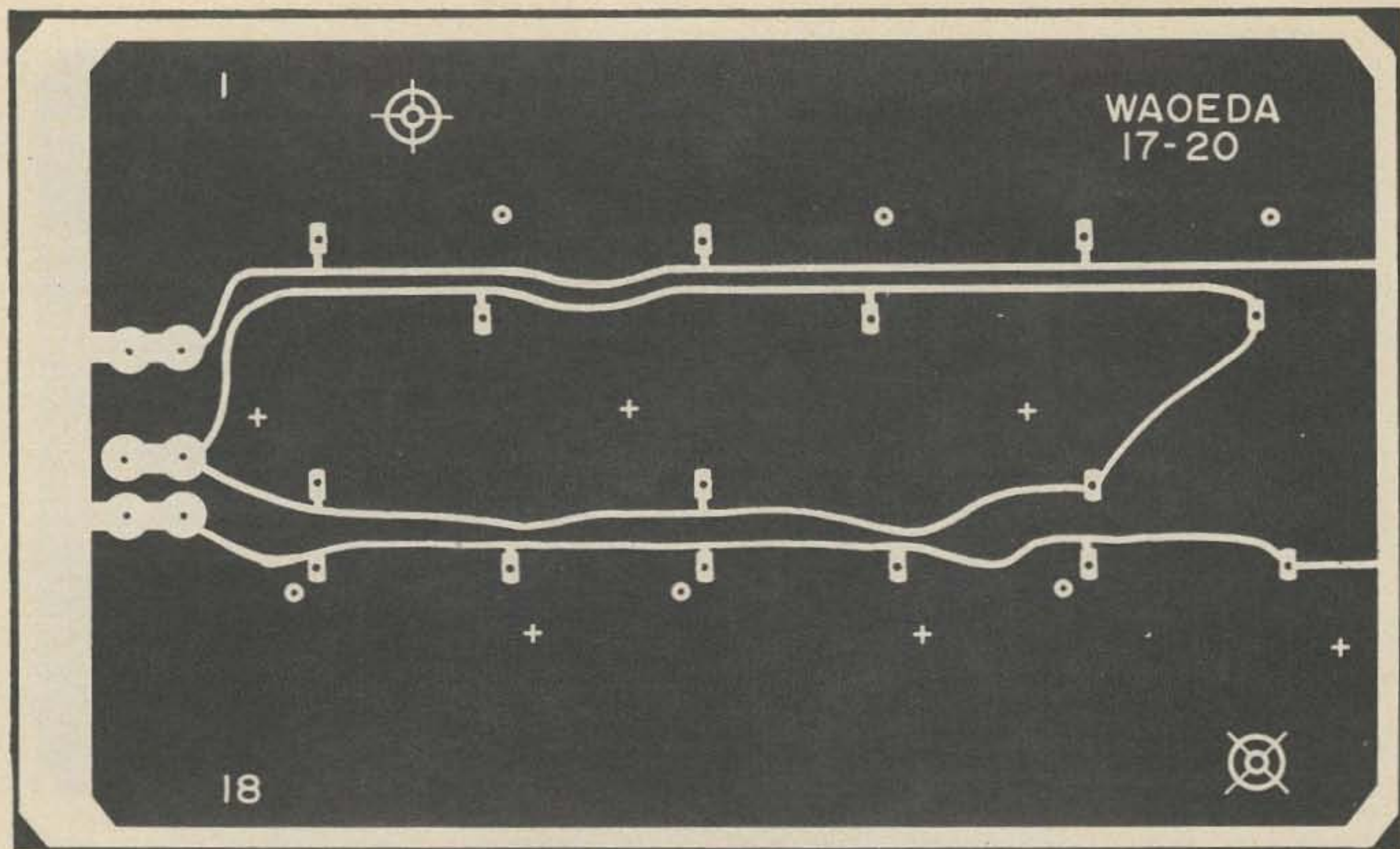


Fig. 3. PC board, component side (full size).

two positive inputs and will give a resulting low output while the second monostable remains in its ON state and the final input is being received. The second NAND gate was used as a cheap and easy way of getting two control functions with only the addition of one NAND gate. These outputs are inverted and are used to control the repeater functions.

This system was designed by me and has been in operation in our 13/73 repeater, WRØABO, since we received our license in July, 1973. It is the only part of the system which operated perfectly from the first and has developed no problems. The .6 second dialing requirement has caused few problems and is very convenient when a wrong number is pressed. The operator must only wait for a second and then begin to dial

again. The control functions which must remain secure are protected by the fact that anyone pushing buttons at random must press the correct combination in a very short period of time. Also, the system is easily changed to a different combination in case any unauthorized person learns the control codes.

A printed circuit layout is included and does require a dual sided circuit board. Many methods of decoding patterns of dialed digits exist but this seems to be the most practical for a reasonable number of functions. I would guess the price of components to decode two combinations (e.g., A-B-C and A-B-A) to be less than \$2. All components are readily available from distributors advertising in 73.

... WAOEDA

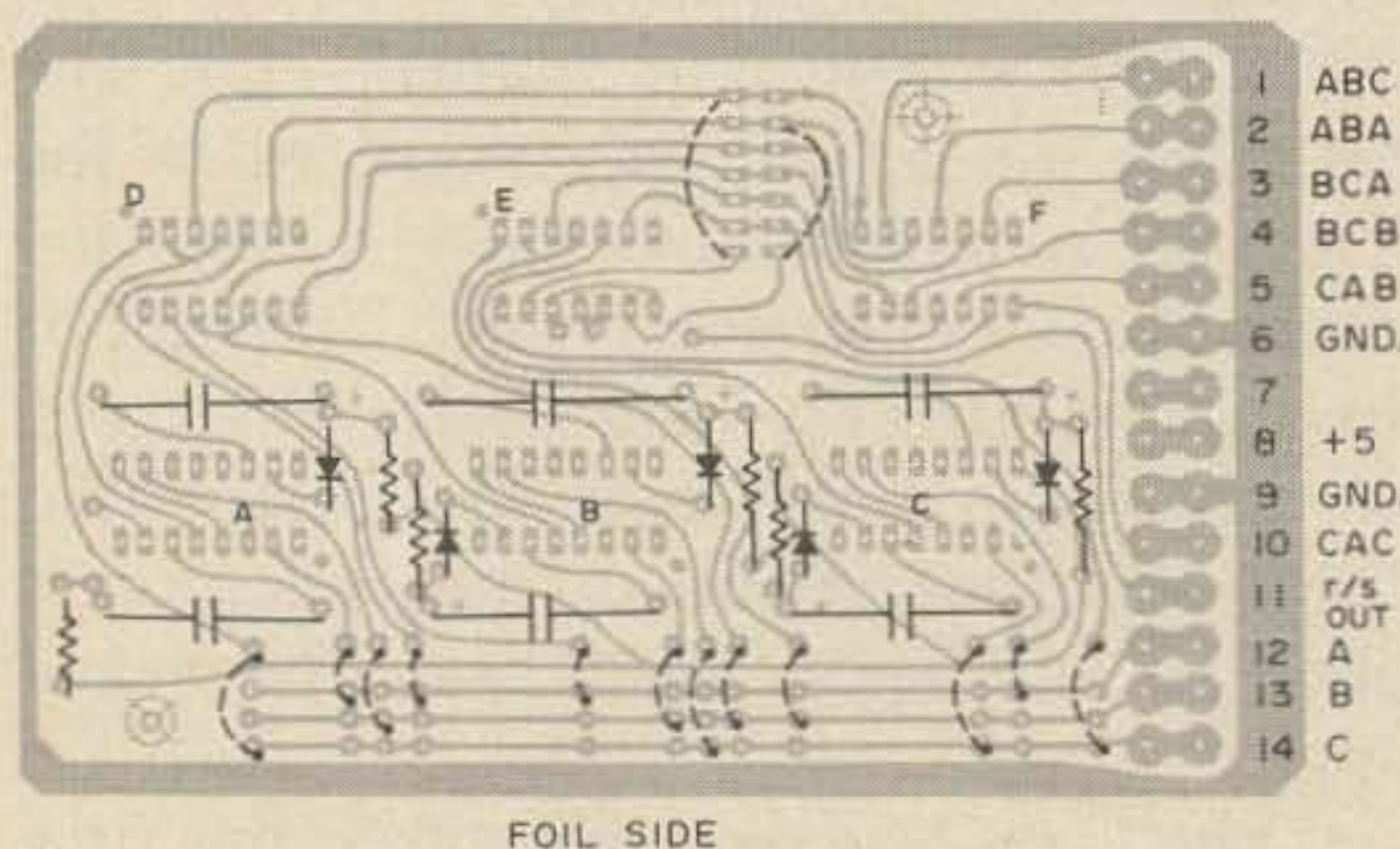


Fig. 4. Component layout, foil side.

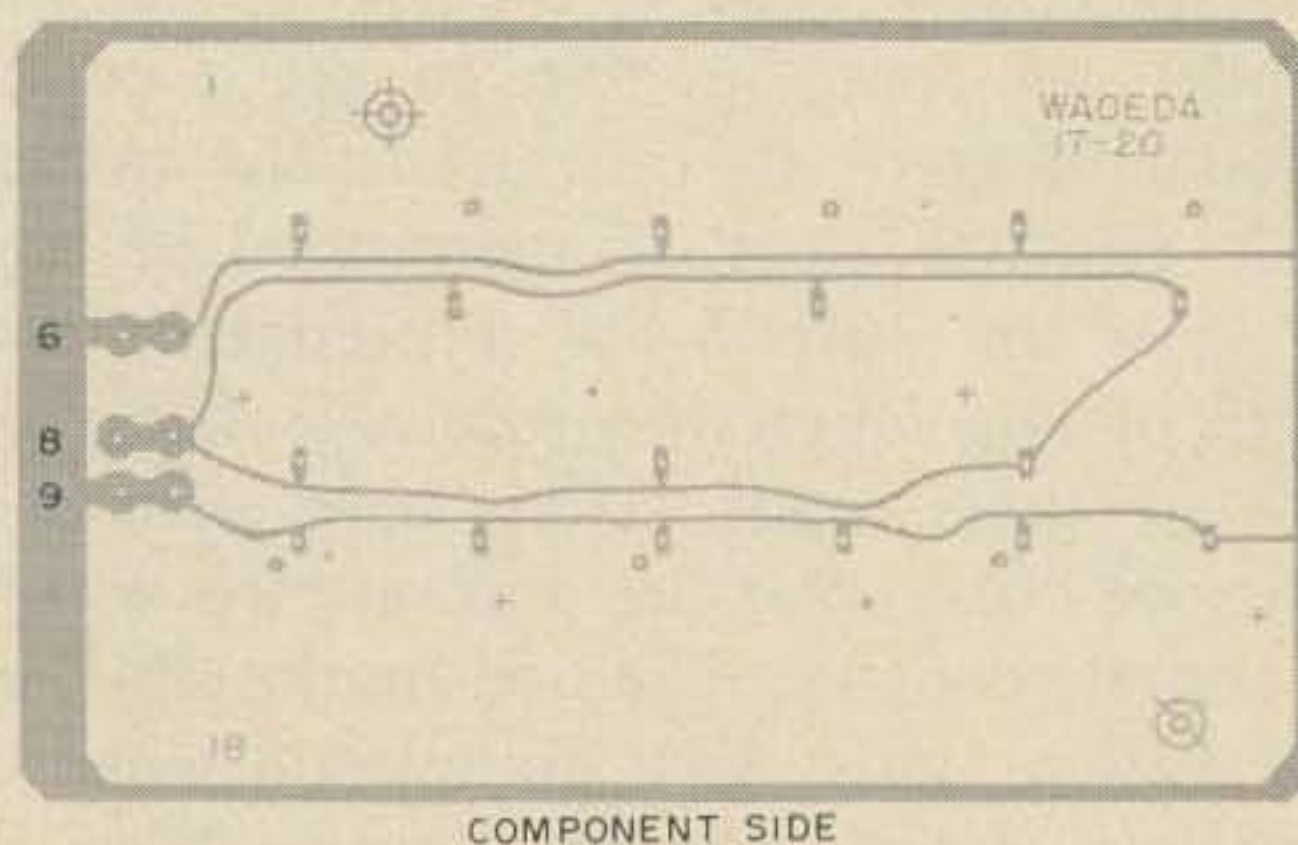


Fig. 5. Component layout, component side.

Clegg HT-146

New Factory Direct Prices Make
This The Best Value
Ever In 2 Meter Hand-helds!

Only \$197.25


Shipping included

*HT-146 Complete with
Heliflex Antenna (BNC)
Mercury Battery*

3 Pairs of Crystals

*146.52 Simplex and any two
pairs of your choice.*

Add \$20.00 for Nicad Battery.

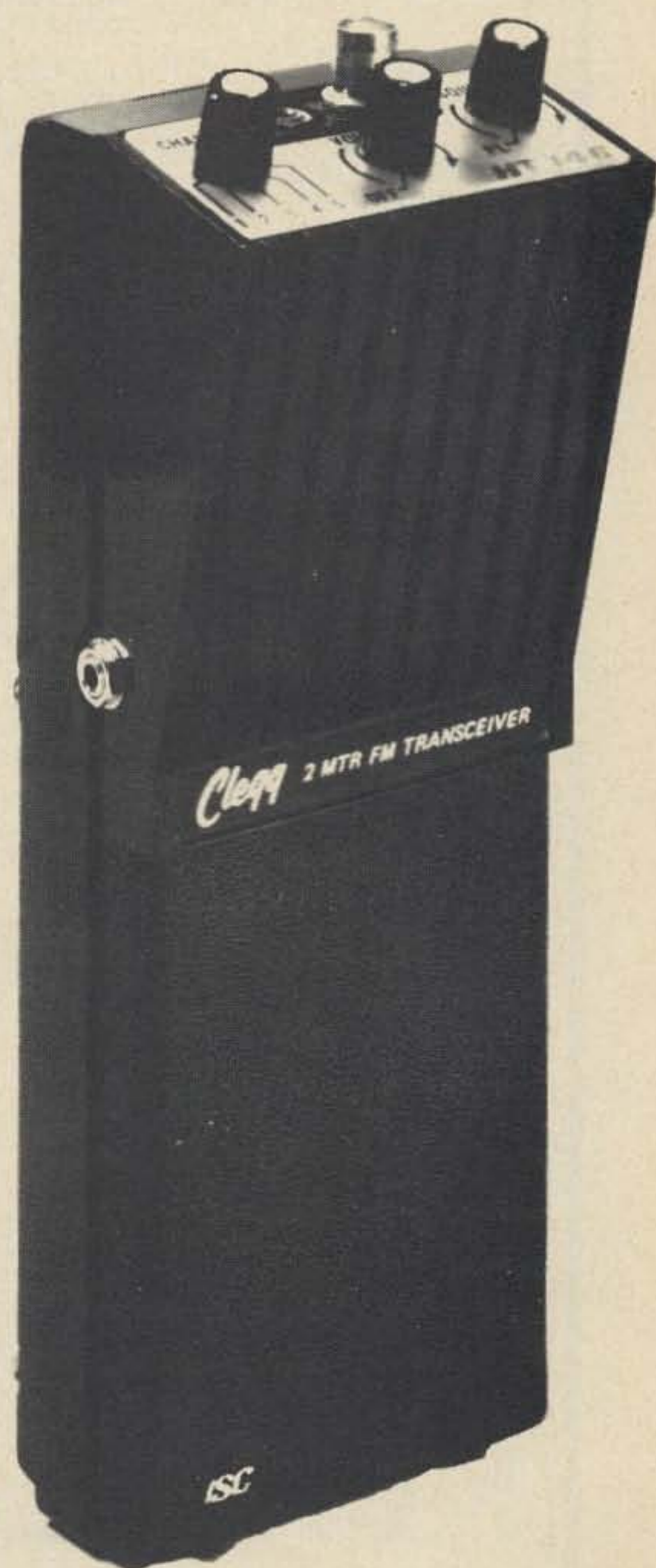

FOR MORE INFO

Phone toll free (800) 233-0250
in Pa. Phone (717) 299-7221 collect

Clegg

208 Centerville Road

Lancaster, Pa. 17603

mastercharge

BANKAMERICARD

For the Tops in Antennas see the Top Dealers

ALABAMA

Rickles Electronics
2800 W. Meighan Blvd.
Gadson AL 35904 547-2534

Rogers C. McCauley
2417 Penn St.
Huntsville AL 35801

ARIZONA

Apache Auto Machine & Parts
8825 N. Central
Phoenix AZ 602-992-8506

Eugene Kuklin
431 Lazy Horse Pl
Tucson AZ 602-297-2111

CALIFORNIA

Communication Devices
1211 Topper Ln.
El Cajon CA 92020

Gary Radio
8199 Clairmont Mesa Blvd.
San Diego CA 714-292-1440

Global America Corp.
P.O. Box 246
El Toro CA 714-533-4400

Ham Radio Outlet
999 Howard Ave.
Burlingame CA 415-342-5737

Henry Radio
931 N. Euclid Ave.
Anaheim CA 213-477-6701

L A Electronics
23044 S. Crenshaw Blvd.
Torrance CA 213-534-4456

M'Tron
2811 Telegraph Ave.
Oakland CA 415-763-6262

Quements
1000 Bascorn Ave.
San Jose CA 408-998-5900

Sequoia Stereo
773 8th St.
Arcata CA 707-822-0328

Teletronics
4175 San Felipe Rd.
San Jose CA 408-274-3100

Webster Radio
2602 E Ashlan
Fresno CA 209-224-5111

Westcom Engineering
Box 1020
Escondido CA 714-744-1395

Halted Specialties Co.
915 Kifer
Sunnyvale CA 415-969-1448

WMS Service Co.
14639 Maryton St.
Norwalk CA 213-921-1575

Chuck Oleson
Unit 54 12521 Centralia
Lakewood CA

Microcomm
14908 Sandy Lane
San Jose CA

Channel Island Communications
P.O. Box 99
Goleta CA

C.B. Radio
2515 So. H Street
Bakersfield CA

C and A Electronics Enterprises
P.O. Box 5232
Carson CA

COLORADO

Loc Electronics
P.O. Box 7515
Pueblo West CO

CONNECTICUT

Marcus Communications
134 E Center St
Manchester CT 203-646-1839

FLORIDA

Amateur Wholesale Electronics
8817 SW 129 Terrace
Miami FL 305-233-3631

Holmes Radio & TV
5057 North Dixie Highway
Pompano Beach FL
421-1880

Lasater Electronics
4617 Paxton Ave.
Tampa FL 813-839-5907

Help Radio
1055 Liberty St.
Jacksonville FL 32206
904-356-8545

GEORGIA

Stereo City, Inc.
481 Highland Ave.
Augusta GA 404-738-1058

Arthur P. Laws
2040 River North Pkwy.
Atlanta GA

HAWAII

Honolulu Electronics
819 Keeaumoku St.
Honolulu HI

ILLINOIS

Erickson Electronics
4135 W. Main St.
Skokie IL 312-677-2161

Hill Radio
212 Hammitt
Normal IL 309-452-6104

Global Research and Supplies
1020 S. Cornell
Villa Park IL 312-279-4658

IDAHO

United Electronics Wholesale
217 Second Ave. N
Twin Falls ID
208-733-7324

IOWA

Antenna Mart
P.O. Box 2
Rippey IA 515-436-7718

Hunter Sales
3621 Beaver Ave.
Des Moines IA
515-255-2186

KENTUCKY

Ramsey Mobile Home Sales, Inc.
P.O. Box 2747
Pikeville KY

LOUISIANA

Preston Electronics
611 Highland Dr.
Houma LA 504-868-2213

Electronics Parts & Supply
7214 Washington Ave.
New Orleans LA

MARYLAND

CQM Electronics
900 Crain Hwy. SW
Glen Burnie MD
301-768-2728

Tycol Communications
Rt. 3, Langdon Dr.
Mt. Airy MD 301-253-4376

MICHIGAN

Ray Liby
2112 South Burdick
Kalamazoo MI

MINNESOTA

Sub-Tronics Inc.
10129 Edon Prairie Road
Eden Prairie MN
612-941-3652

Robert D. Bliss
1440 Lakeview Ave.
Minneapolis MN

MISSISSIPPI

Morreville CB Radio Center
P.O. Box RR1
Morreville MS

MONTANA

Conley Radio Supply
101 S 31 St
Billings MT 59101
406-259-9554

NORTH CAROLINA

Speed Supply Company
P.O. Box 194
Stanfield NC

NEW YORK

J H Electronics
254 Captain's Dr.
West Babylon NY

South Fork Electronics
36 Hampton Rd.
So. Hampton NY
516-283-8686

Bratty Communications
1854 Colvin Rd.
Tonawanda NY

VHF Communications
915 N. Main St.
Jamestown NY

Westchester Comm. Spec. Div.
53 Hayward St.
Yonkers NY

NEW JERSEY

E. J. Narwid Electronics
61 Bellot Rd.
Ringwood NJ 201-962-4695

Radios Unlimited
86 Balch Ave
Piscataway NJ
201-752-4307

Hi-Fi & Photo Supply
P.O. Box 290
Toms River NJ

Curts BP Service
Rt 130 & Broad St.
Penns Grove NJ
609-299-9881

Spaford Communications, Inc.
883 Jaques Ave.
Rahway NJ 07065
201-382-7979

NORTH DAKOTA

CDS Electronics & Hobbies
3611 13th Ave. N.
Grand Forks ND
701-772-5480

OHIO

Challenger Electronics
1700 Central Ave.
Middletown OH
513-424-2475

Communications World
4788 State Rd.
Cleveland OH 216-398-6363

Queen City Electronics
1583 McMakin Ave.
Cincinnati OH

Kelly Schelmsberg
7379 Calmcrest Ct.
Dayton OH

Talley Electronics
8520 Winton Rd.
Cincinnati OH 513-931-1577

Advance Communications
1778 Adams Rd.
Loveland OH

OKLAHOMA

Larry Dillard
2624 S.W. 69th St.
Oklahoma City OK

Cal's Radio
3rd and Davis
Tipton OK

OREGON

Juniper Electronics
2648 S.W. 25th St.
Redmond OR

LJ Electronics
2075 S. Marylwood Ct.
West Linn OR

Silke Communications
680 Tyler
Eugene OR 97402
687-1611

PENNSYLVANIA

Hamtronics
4033 Brownville Rd.
Trevose PA 215-357-1400

SOUTH DAKOTA

J L Shaffer
Rt. 1, Box 13
Rapid City SD 605-343-8061

SOUTH CAROLINA

Greene's Electronics
Hwy. 15, So.—P.O. Box 626
St. George SC

TEXAS

Bolen Control Systems
5424 Ammons St.
Ft. Worth TX 817-485-1325

(Partial Listing)

KLM

ELECTRONICS

1600 Decker Avenue, San Martin CA 95046 408-683-4240

Larry Jack WA3AQS
3 Barry Avenue, Bay Ridge
Annapolis MD 21403

Underground Radio is Dirty Business

Can radio really work underground?

An underground radio system, one that can be used to communicate in caves, has fascinated me for a long time. Out of this fascination grew the basis for this unique experiment. A cave presents difficult barriers to overcome in its exploration. Tight crawl-ways, pits, mud and water are only a few. Many cave passages are measured in miles, with hours being required to explore them.

While many explorers or "cavers" will disagree as to their often masochistic reasons for enduring such sufferings required to explore caves, most will agree that one of these imposing barriers is isolation — isolation in the form of separation of an exploring party from the people back on the surface, or from another group within the

cave. It is a form of isolation hard to comprehend in an age of instantaneous communications, for in a cave communications is generally only as fast as an explorer can travel. Or at least it was until we began these cave-radio experiments. But before going on, let me give you an idea what exploring a "wild" cave is like, one without electric lights, pathways or guides.

An explorer pauses a moment to smile at his companions, and then silently rappels down a rope into a deep black hole. His miner's lamp is all that relieves the total darkness of the pit. While the others watch, the light grows smaller as he descends until it is no more than a speck far below. Several hours of tortuous climbing behind them, the summer sun blazes on a hot dusty afternoon.



Operating KA2XAR mobile unit 1 in the depths of a wet, muddy cave is Bill Madden. He's operating on 1545 kHz, 10 W input, AM modulation. (Photo by James McCloud)

But deep within the cave, the explorers quietly shiver as they wait in the cold mist of a waterfall for their turns to descend. Far below a voice calls out that he is safely down. Now another explorer prepares to enter the pit.

As you can see, in a cave man is the alien in an often hostile environment. Constructing a communications system that would both communicate through rock, and withstand this environment, is quite a challenge. In the past, the systems used in caves had been almost exclusively army-style field telephones. However, the difficulty of stringing wire made their use prohibitive in all but extensive, large group expeditions. Induction radios operating in the range of a few kilohertz have been used with a varying degree of success, but their range is severely limited. What I and others wanted was a system that could be used like a walkie-

talkie, one that could communicate up to several thousand yards between a "base station" on the surface, and portables located within the caves. The portable unit had to be idiot proof, for the last thing someone covered with mud and water wants to do is tune up a rig in the semi-dark. They also had to be designed to withstand being banged against rocks, pushed, dragged and tossed through mud and water as well.

In building up a system, the choice of a radio frequency was the main obstacle since experiments have shown that the lower the frequency, the better the range of a radio signal through the cave rock (in this case, limestone). Unfortunately the antenna size vs. efficiency of a portable unit makes some sort of compromise necessary. A few simple experiments convinced us that the .2 to 6 MHz region offered a good compromise frequency range in lieu of anything lower.

But just *how* good? How could the system be tested legally to see if it would work under actual field conditions?

Out of this curiosity was born KA2XAQ/KA2XAR. We were fortunate enough after exhaustive detailing of the proposed experiments to obtain an experimental license from the FCC under Part 5. We asked for and were given permission to operate on a number of frequencies from 185 kHz to 27 MHz during September and October, 1973. KA2XAQ was assigned as our "base station" call and KA2XAR was the call sign to be used by the portable units which would be carried into the cave. The FCC classified the equipment as experimental or "laboratory constructed." That is to say, homebrewed. Our surface units were conventional ham type tube equipment scrounged up and brought to operation on our new frequencies at the specified frequency tolerances. The in-cave portables were all solid state and built into surplus army 50 cal. ammo boxes to make them both rugged and waterproof. These portables ran between 2 to 10 Watts input into antennas that could vary in length from a few feet to over 60 feet in length.


The tests were carried out in a large West Virginia cave located in the northeastern part of that state. The results? Much better than expected. For one thing, it was found that the use of frequencies below 1 MHz was unnecessary. The desired communications distance could be achieved at higher frequencies, with the best between 1-2 MHz. Above 2 MHz, the distance drops off quickly until at 27 MHz it is only a hundred feet or so at best. It was also decided not to use .2 to 1 MHz range because of antenna tuning problems and general inefficiency of our portable units at these frequencies. Redesigning them might overcome this, but for the present the higher frequencies suits our purposes providing communications in excess of 1000 yards. The equipment proved to be rugged enough to withstand numerous abuses, simple enough for an inexperienced operator, and virtually 100% reliable up to its range-distance limit. We strongly feel that building more sensitive receivers and better portable antenna systems will increase the system's performance, but for now, the isolation factor in cave exploring isn't so pronounced as before.

... WA3AQS



Left to right are Gale Hiem and Lynn Wayshner, operating KA2XAR mobile unit 2 on 1545 kHz. (Photo by James McCloud)

WE'VE GIVEN IT A NEW LOOK!

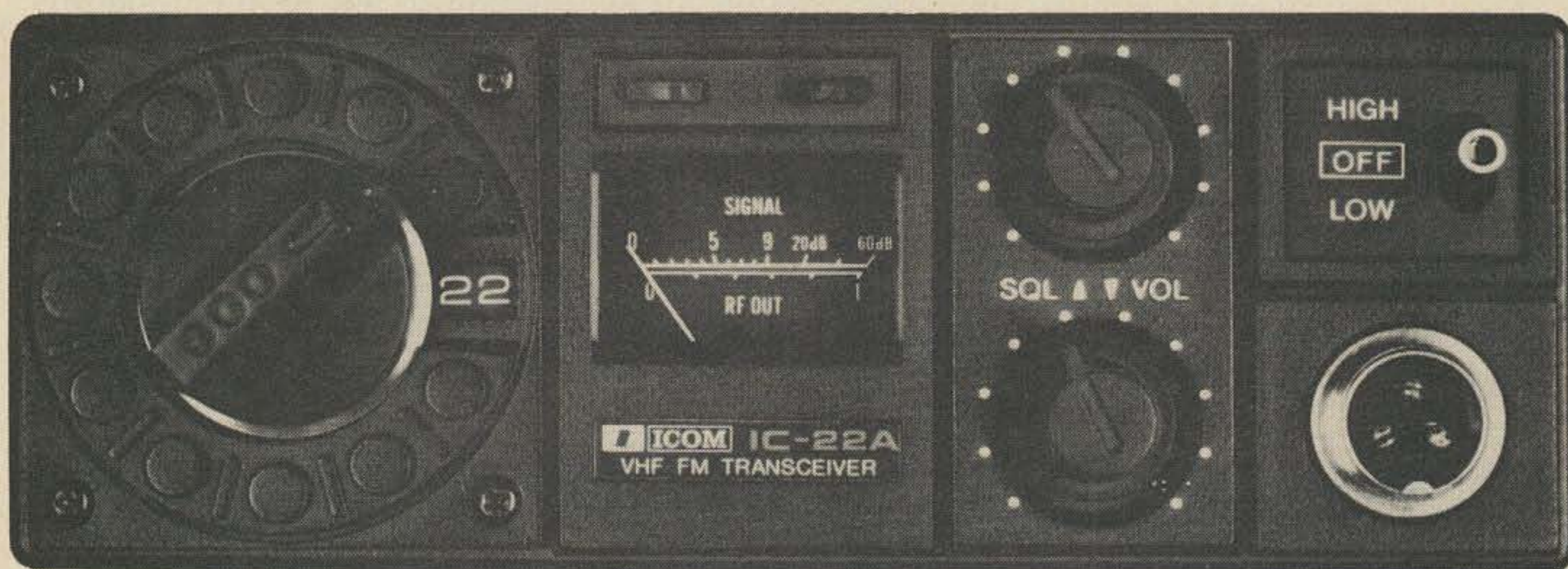

IC-22A

The front panel and control locations have been changed to make the IC-22A even better looking and easier to operate. The new design allows the use of larger channel numbers which may be

viewed from the left side or right side by reversing the window position and installing a new dial. (optional at nominal cost)

Inside is the same high quality radio construction and engineering that has made the IC-22 the most reliable, most popular two meter crystal controlled set on the market.

When you join 22 channels of capacity (five supplied) with the unexcelled performance of helical RF filtering in the receiver front end then add solid state T-R switching you get one great radio for your money. All the great features that made the IC-22 so desired are still there. Including, 1 watt/10 watt switch option, trimmer capacitors on both receiver and transmitter crystals plus a 9 pin accessory jack with the discriminator already wired for frequency calibration.

SEE ONE !! BUY ONE !! AT YOUR ICOM DEALER TODAY.

Distributed by:



ICOM

ICOM WEST, INC.
Suite 232--Bldg. 11
300-120th Ave. N.E.
Bellevue, Wash. 98005

ICOM EAST
Suite 307
3331 Towerwood Dr.
Dallas, Tx. 75234

IF YOU HAVE ALREADY GONE 450 ♦ ♦ ♦ ♦



GO ICOM 30A ♦ ♦ ♦ ♦ before you go bananas!

If you have been trying to resurrect something from the pre-transistor past that more closely resembles the mechanism used to keep large ships in place, or if the sound of bumble bees is keeping you awake at night--REJOICE!!! The ICOM 30A is here and working!

Consider these reasons for owning an IC-30A:

- (1) Despite the fact that the radio is completely solid state, it has output of ten watts
- (2) Receiver sensitivity is better than 0.6UV for 20 db of quieting and that means easy on the ears listening.
- (3) The IC-30A comes with five channels of the 22 channel capacity installed
- (4) Shielding is excellent because the unit is modularly constructed.
- (5) Your car tires will last long because the IC-30A weighs less than ten pounds.
- (6) Like its predecessors, the unit is equipped with a 9 pin plug in the side of the radio to provide you easy access to the discriminator and room for adding the necessary wiring for external accessories -- with all this and more, for only \$399.00.

SEE ONE !! BUY ONE !! AT YOUR ICOM DEALER TODAY

Distributed by:



ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue WA 98005

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas TX 75234

Dave Ingram K4TWJ
Rte. 11, Box 499
Eastwood Vil. #604 N.
Birmingham AL 35210

What's Wrong with my SSTV?

Slow Scan TV operators often have difficulty describing the various types of interference experienced in picture exchanges. This article is intended to fill that void and hopefully rectify reports of "your pictures were not very good" to more specific analysis like, "your pictures have perfect sync, but noise in the video is excessive." Also, I would like to suggest some references on picture quality so we will

be closer to an established system, like the RST system is for CW. Before discussing some picture specifics I would like to point out that photographs usually show up details the eye misses. Also, since we are dependent on the relationship of monitor dot intensity to camera F stops, photographs often reveal shadows and unequal illumination not noticed when viewing pictures on the monitor. These photos will also appear more



Photo 1.



Photo 2.

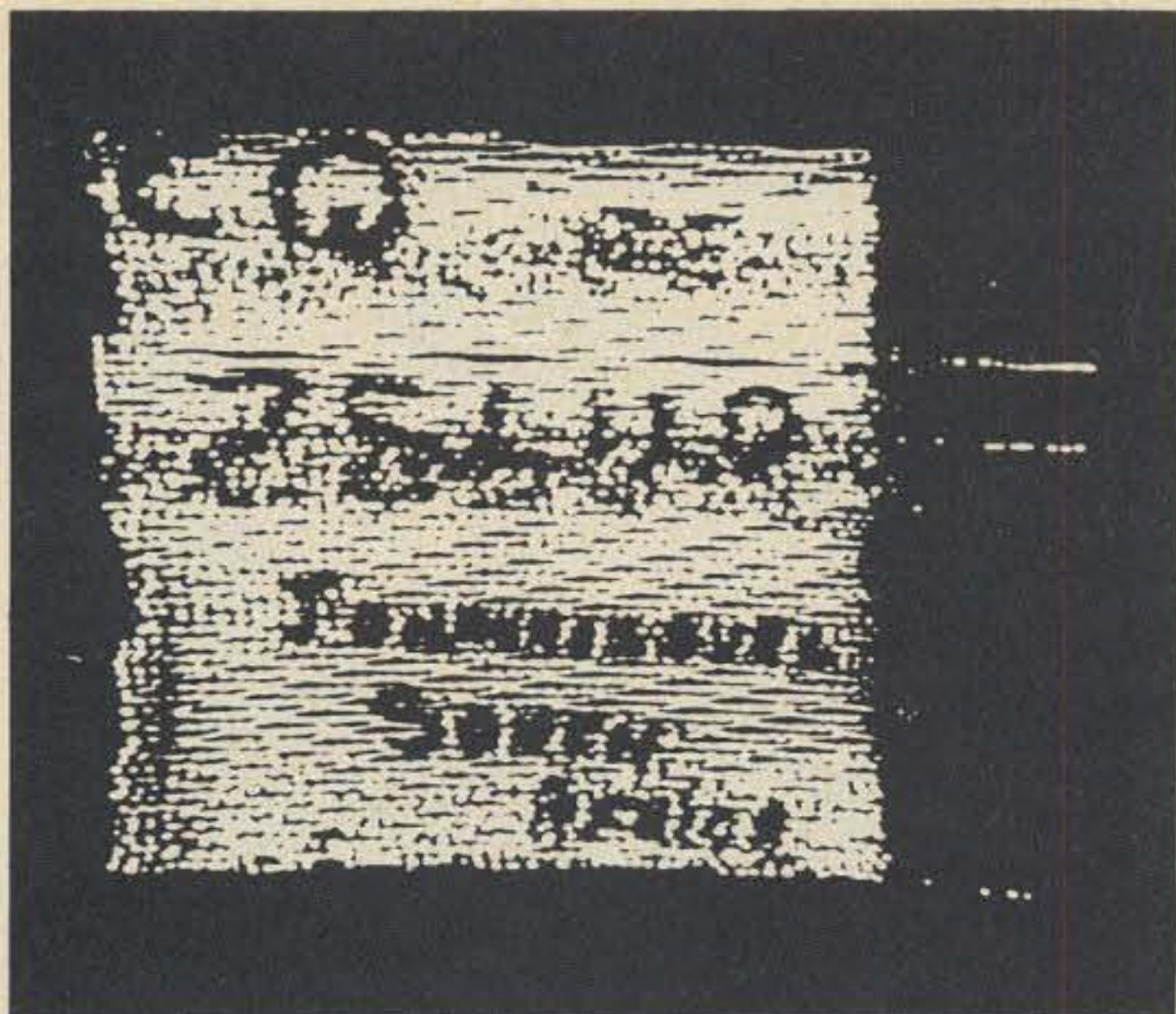


Photo 3.

natural on a monitor if you will view them at arm's length, rather than trying to "read" them closely.

Let's start our discussion with a solid "closed circuit" example as in Photo 1. Notice every line starts and stops exactly, resulting in a perfect raster. No interference of any type is evident and there are no skewed lines. The apparent gray scale limitation in the photo was only because monitor intensity was low to avoid "bleeding" on the photographs. When I made this shot, I was wearing photogray lens glasses which the monitor shows as regular glasses and the camera caught as sunglasses. (Pardon the bit of humor in the triple exposure picture.)

Next is Photo 2, which was received from FG7XT on Guadeloupe. This one may be considered very good and nearly closed circuit. There are a few missed lines right above the ID. These lost lines are due to intermittent QRM which overrode the sync pulses during that time period. Notice the otherwise perfect syncing and no noise in the video. If you look closely you'll see the circles are made up of the Slow Scan's 120 lines, not dots as one might think at first glance. The jiggled letters in "television" are due to a minute speed variation in my cassette recorder. The batteries were slightly weak and of course this is more noticeable with speeds like 1-7/8 ips (compare with Photo 1).

Now we move to Photo 3, which was received from ZS6UR in Johannesburg, South Africa, via 20m. He was only S3 and QRM was rough. QRM appears in the video as dots. This is noticeable immediately

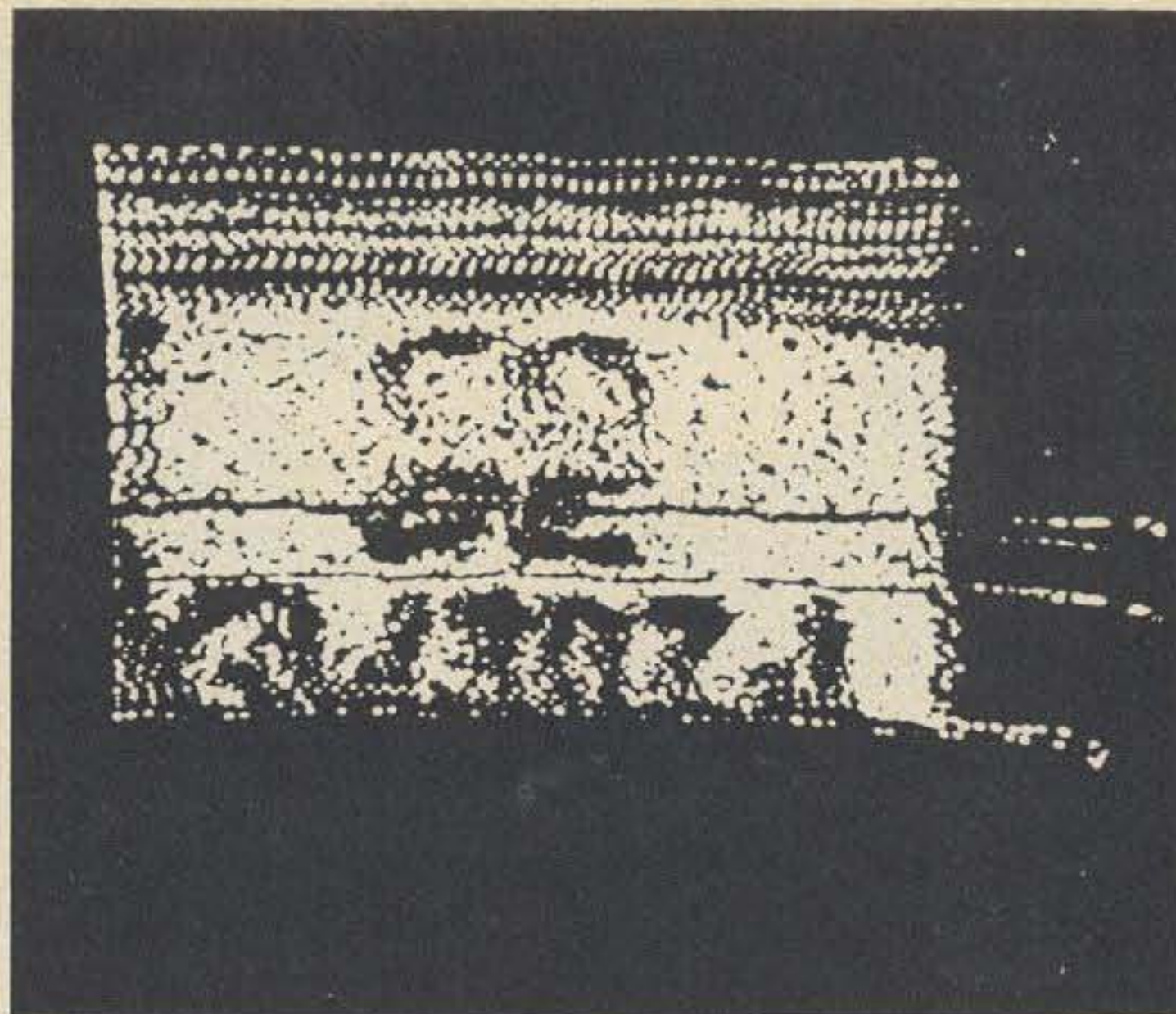


Photo 4.

below the CQ and around the UR in ZS6UR. Accurate syncing is still maintained, as noted by the neat right side. Although ZS6UR was readable on the monitor screen, the camera caught more of the white dots around the UR, making all the ID difficult to distinguish. Notice you can read the QTH, which shows fair resolution for a "long haul" QSO. This picture could probably be considered between fair and poor in picture quality.

Photo 4 is very close to nil. If you hold it back and study it carefully you can just make out CQ de GW3DZJ. QRM in the video is very predominant above CQ as are some missed lines (due to QRM causing loss of sync pulses). There are some missed lines also through the DE, and QRM completely overrode sync at the ID bottom, resulting in no trace for the remainder of that particular frame. Readable, but definitely a poor quality picture.

We should term Photo 5 an uncopiable

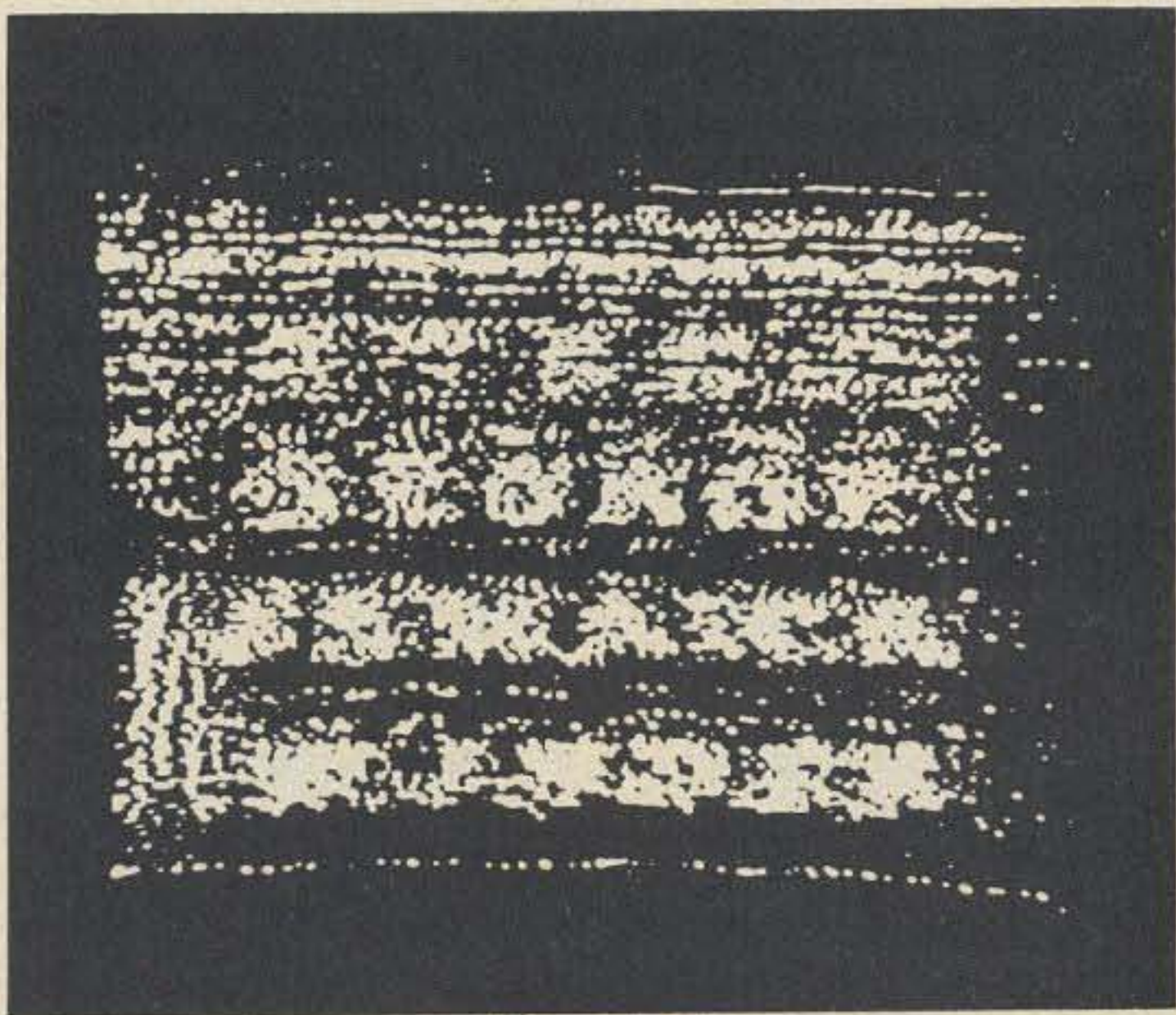


Photo 5.



Photo 6.

picture. If you study carefully the middle of the picture, you can make out George, Jamaica. However, everything else was lost in noise and QRM, both in sync and video. This picture does point up a slight advantage when using white letters on a black background. If conditions were slightly better the picture would have made it; however, a white raster with black letters would probably still have been indistinguishable.

Photo 6 is very interesting in the fact it exhibits (among other things) an unusual form of multipath propagation. Ordinary (?) additive multipath usually appears as "ghost" in the received picture while subtractive multipath may cause a loss of part or all of the picture . . . you might hear it but not see it. Subtractive multipath is similar to an out of phase situation. If the negative phase of a signal equals the positive phase, the two cancel and no signal remains. In Photo 6, the multipath appeared to



Photo 7.

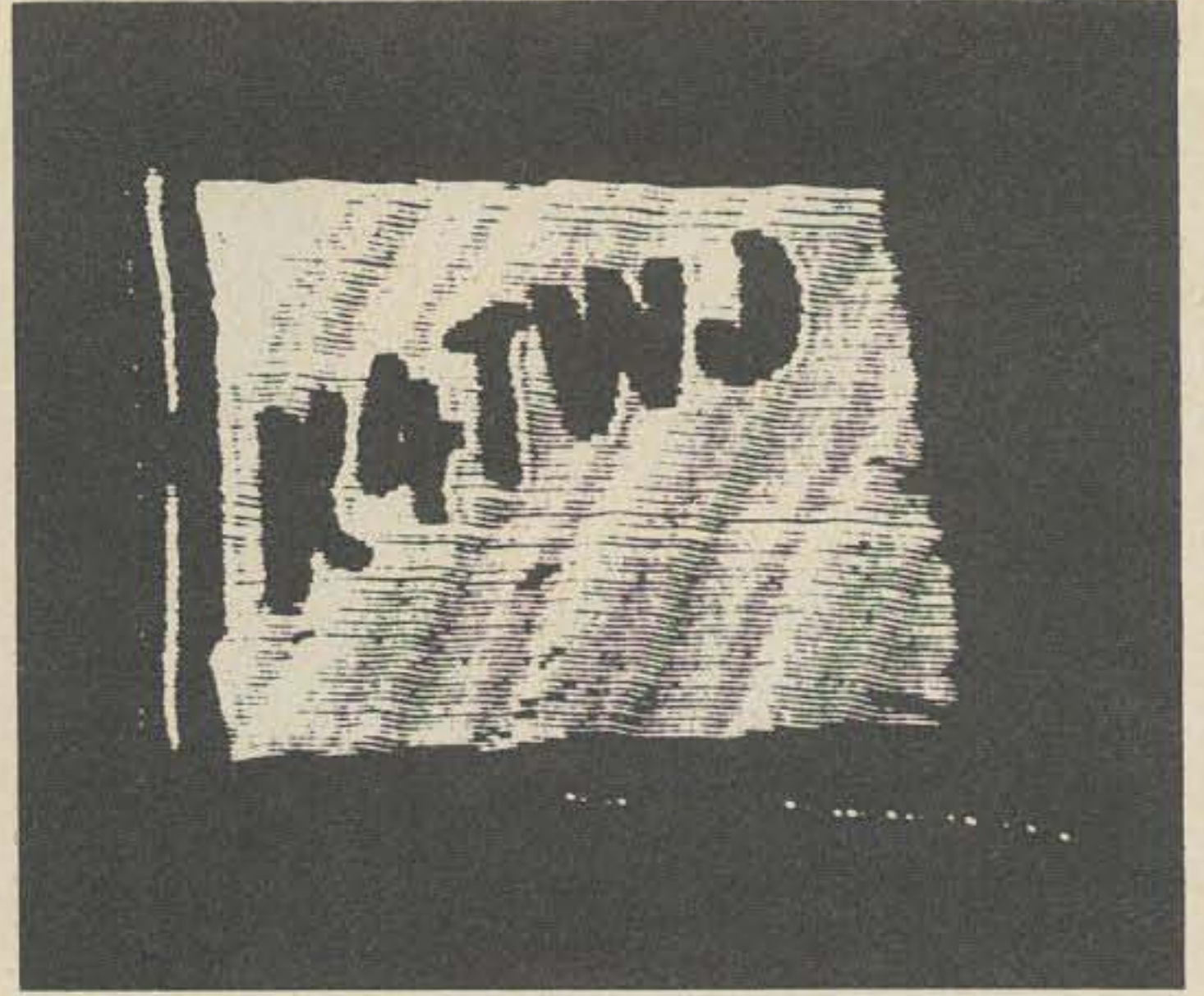


Photo 8.

manifest itself only in the higher video frequencies, causing partial cancellation in white. This is evidenced by "dots" in white (most noticeable near the bottom). This looks similar to QRM in the video. However, when this picture was received from ZS3B one night on 20m, he was the only station being heard (S8) and there was no QRM. His voice had a "DX echo" which denoted multipath, so this was the obvious answer.

Photo 7 is also "closed circuit" like Photo 1. Indeed there is nothing missing from this picture (!). Skewed lines are visible running from the top left to the bottom right and these are due to the playback tape recorder running slightly slower in speed than the recording tape recorder. If it had run faster, there would be skewed lines from top right to bottom left like Photo 8, and if the two speeds were identical, no skewed lines would be visible. If you will notice the absolute top line on your Slow Scan monitor you will see 4 very slight "waves." This is 15 cycle hum (60 cycles divided by 4). Now if speeds vary, these "hum bars" will displace on subsequent lines causing the "leaning" lines visible in Photos 7 and 8.

Photo 8 was accomplished by syncing the monitor externally to 15 cycles, then feeding in the Slow Scan picture. This resulted in the horizontal sync pulses being displaced just enough to be seen on the photo's left side. If you measure the sync pulse (although it is blacker than black, it only appears as black) which was approximately 6 ms wide, and then compare this with the picture's width, you will see it is approximately 1/11 the picture width, which means


the picture is 66 ms wide. The approximate 6 ms is the retrace, or flyback, period of horizontal sweep, while 66 ms is the "scan" period.

It is my sincere wish that the examples in this article will be of significant value for future Slow Scan understanding and, as a result, we will be closer to an established set of SSTV criteria.

I would especially like to thank Miss Beverly Taylor for the fine photography work in this article. Beverly had a good idea which deserves mention here. She placed a light meter in front of the monitor, got a reading off the initial trace as it scanned, set the camera's F stop accordingly and shot. Every picture came out fine, with good contrast and maximum definition. The room was very dim, the camera was 35mm and the film ASA400.

Finally, the DX shown in this article is typical of Slow Scan activity today. If you're not yet on SSTV, why not join in? It's really a great new mode of communications.

... K4TWJ

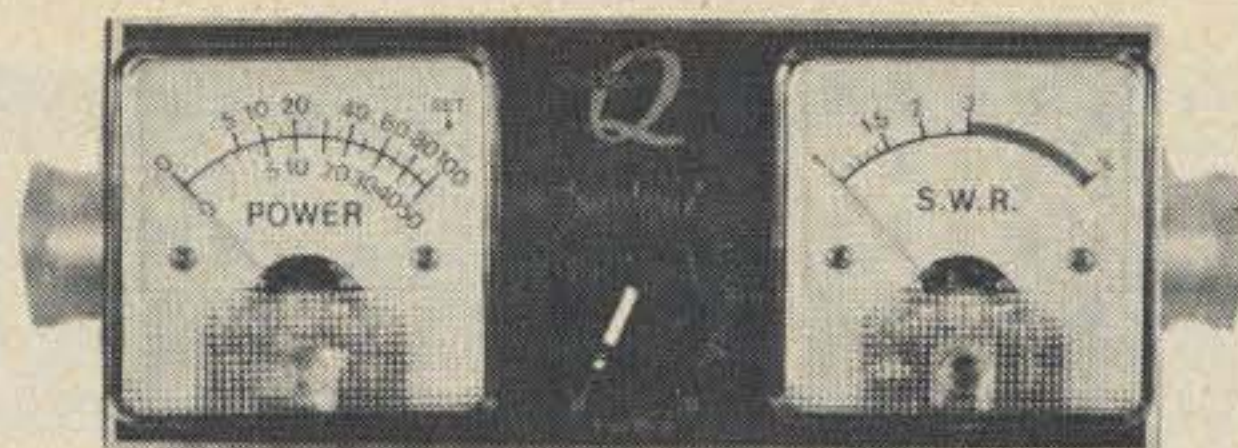

SWB-2 \$21.95*

SWR BRIDGE READS FORWARD & REFLECTED POWER SIMULTANEOUSLY

'EASY READ' METERS

DUAL 100-MICROAMP METER MOVEMENTS

LOW INSERTION LOSS

SIZE 5X2X2

MAY BE LEFT IN LINE UP TO 2,000 WATTS

3 TO 150 MHZ

ADD \$1.50 FOR POSTAGE

Calif. residents add Sales Tax.

* prices subject to change without notice ...

OUR BEST "HAM" BUY



QUEMENT ELECTRONICS
1000 SO. BASCOM AVE.
SAN JOSE, CA. 95128




For detailed technical information and pricing—write to:

APTRON

Dept. AMTV
P.O. Box 113A, R.R. 2
Bloomington, IN 47401

FAST SCAN Amateur TELEVISION

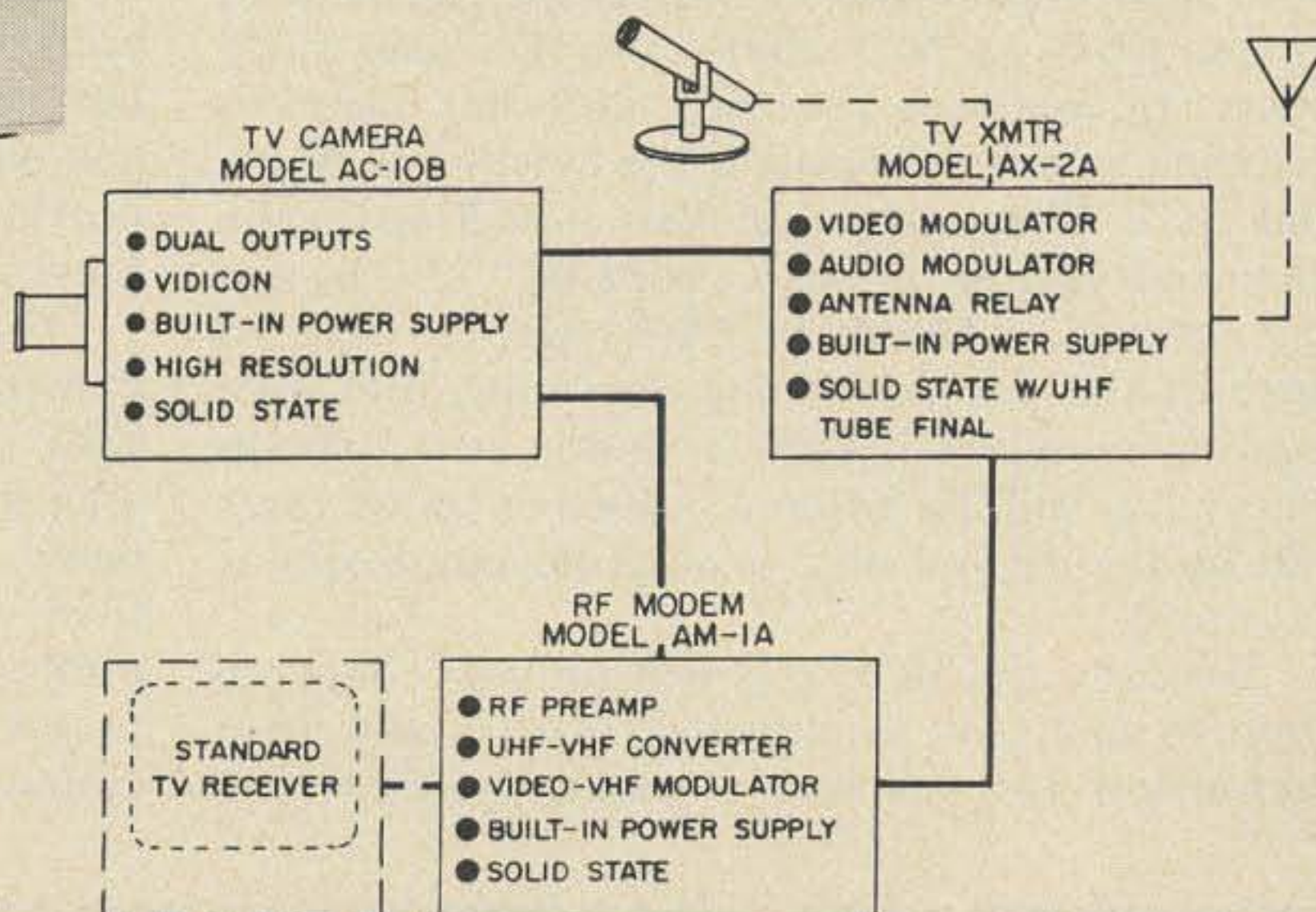NOW YOU CAN ENJOY FSTV
AT REASONABLE COST.



**Sumner Electronics
& Eng. Co. inc.**

P.O. BOX 572
HENDERSONVILLE, TENNESSEE 37075
TELEPHONE: 615-824-3235

Announcing Another Quality First From SEEC



(Production unit slightly
different in appearance)

Specifications - HCV-2CS

SLOW SCAN TO FAST SCAN AND FAST TO SLOW SCAN TELEVISION MONITOR

For the past 18 months SUMNER (SEEC) has been involved in the design of a Slow Scan to Fast Scan and Fast Scan to Slow Scan TV Monitor utilizing charge coupled devices (CCD) and digital circuitry. For well over a year the prototype unit has been in operation without a failure. We at SEEC feel that a complete monitor should be offered, rather than an assortment of "black boxes" and a separate TV set/video monitor. Furthermore the parts situation being what it is, a home brewer finds it very difficult to obtain parts for a 1 time unit at a reasonable price. In addition the HCV-2CS has been so designed as not to obsolete the existing HCV-2A and HCV-2B monitors, in that it will be in the same size cabinet as our current HCV-2A(B) and the owners of the HCV-2A(B) will be able to retro-fit the scan converting electronics into their existing monitors if they so desire, or a trade in allowance will be offered, which in most cases will be the desired way to go as the conversion is extensive.

Basically the HCV-2CS will provide complete slow to fast scan monitoring; fast to slow scan conversion for utilizing a standard CCTV fast

scan camera such as the RCA TC1000; interconnection to utilize the standard slow scan camera if desired; complete interconnections to connect the HCV-2CS into the existing or proposed slow scan system; auxiliary fast scan monitor output; tuning meter for sync (1200 Hz) signal tuning as well as LED tuning indicators for proper adjustment of Monitor Black and White Compression levels (1500 Hz and 2300 Hz), when tuning in the SSTV signal from the receiver and adjusting the monitor for proper black and white levels prior to receiving a picture from the receiver; tape recorder input and output jacks; telephone line input/output jack. A built-in viewfinder is provided for set up of a standard fast scan camera.

The slow to fast conversion will be based on a 256 line format displayed on a 9 inch rectangle CRT (cathode ray tube) being deflected at fast scan rates (composite fast scan video will be based on 15,750 Hz, horizontal, 60 Hz vertical field rate - 30 frames per second and a composite video amplitude of 1.4 volts pp being present at the auxiliary fast scan monitor output connector). Brightness of display will be similar

to the home TV set or standard fast scan video monitor. In addition 2 basic modes of reception/display will be provided as follows: 1. displayed as being received; 2. freeze display which will allow any picture to be frozen on the screen. The main memory will be a combination of CCD chips and digital shift registers to make up a total memory of some 80,000 bits. For those modifying current HCV-2A(B) monitors the display will be 6.5 inches, but all other functions will be as stated.

The fast scan to slow scan conversion will accept the standard composite fast scan video from a camera or video tape recorder (VTR), which is based on 15,750 Hz horizontal, 60 Hz vertical field and 1.4 volt pp video amplitude signal and convert this composite video to slow scan standards. ¼ and ½ frame rates, black-white (positive-negative) color reversal and a 4 shade vertical gray scale generator will also be provided in this section. Also a special feature to convert a frozen fast scan picture back to slow scan so that it may be retransmitted as slow scan will also be provided in this section. This feature allows picture that is being retransmitted to be reprocessed, before or during retransmission, if needed.

Front panel of the HCV-2CS will have all necessary controls for all modes of operation such as brightness and contrast for the fast scan monitor section; black and white compression controls for slow to fast and fast to slow converters; video/voice switch; slow scan and fast scan video selectors - Camera - Receiver - Tape; slow scan and fast scan video display selection; SS-FS RT switch for converting a frozen fast scan picture back to slow scan for retransmission; freeze switch. A total of 16 front panel controls to control all functions, in addition to tuning meter for sync tuning and LED indicators for black and white frequency, 1500

Hz and 2300 Hz, will be provided. Fast scan horizontal hold to be located on rear panel along with fast scan monitor video level control.

The HCV-2CS will measure approximately 14"W x 15½"D x 8½"H. All circuitry to be on gold flashed, glass epoxy, plug in printed circuit boards with ICs, Op Amps, transistors in plug in sockets. All of the system will be fan cooled via of ultra quiet fan mounted on rear panel.

Current delivery projection is scheduled for around September 30, 1975. Price: - \$925.00, F.O.B., Hendersonville, Tennessee. The HCV-2CS may also be purchased less the fast to slow scan converter, which could be installed at a later time, for \$795.00, F.O.B. Hendersonville, Tn. Conversion kits for the current HCV-2A(B) owners will be available about the same time for around \$400.00, or factory installed for \$600.00. Write for trade in allowance on HCV-2A(B) monitors stating serial number, date purchased, etc. The RCA TC1000 fast scan CCTV camera complete with lens and power supply is now in stock for \$245.00; GBC CTC4000 is available for \$225.00 and the JFD 604 with fast scan viewfinder built in is \$495.00 complete with F1.9-22 lens. We also have a full line of lenses, tripods, tape recorders (audio and video) and other accessories.

A complete brochure will be prepared shortly and mailed to you with ordering information on the HCV-2CS. To hold the HCV-2CS at the current price a deposit of at least 25% will be required (\$231.25 for standard HCV-2CS or \$198.75 for the HCV-2CS less fast to slow conversion). Note that the balance would be due prior to shipment of the unit. All prices and specifications are subject to change at our option without notice, except prices that are frozen with a deposit as mentioned above. All rights are reserved by SUMNER. **Write for more detailed specs and reserve yours now**

SUMMER SALE ENDS SEPT. 30, 1975

ALSO
AVAILABLE

HCV-1B SSTV camera, w/lens and power supply	\$380.
HCV-2A SSTV monitor	\$310.
HCV-2B SSTV monitor with built in fast scan viewfinder	\$415.
HCV-3KB SSTV keyboard	\$425.

Complete line of accessory items.



Five ways to purchase:

Cash with order - C.O.D. (20% deposit) - Mastercharge - BankAmericard - SEEC Financing (up to 36 months). Note: all credit cards pay regular price shown. All prices F.O.B. Hendersonville TN.



Sumner Electronics & Eng. Co. inc.


P.O. BOX 572
HENDERSONVILLE, TENNESSEE 37075
TELEPHONE: 615-824-3235

CRYSTALS are OLD FASHIONED


*Now in stock
The latest synthesized rigs available.*



ICOM 230 146-148
FM

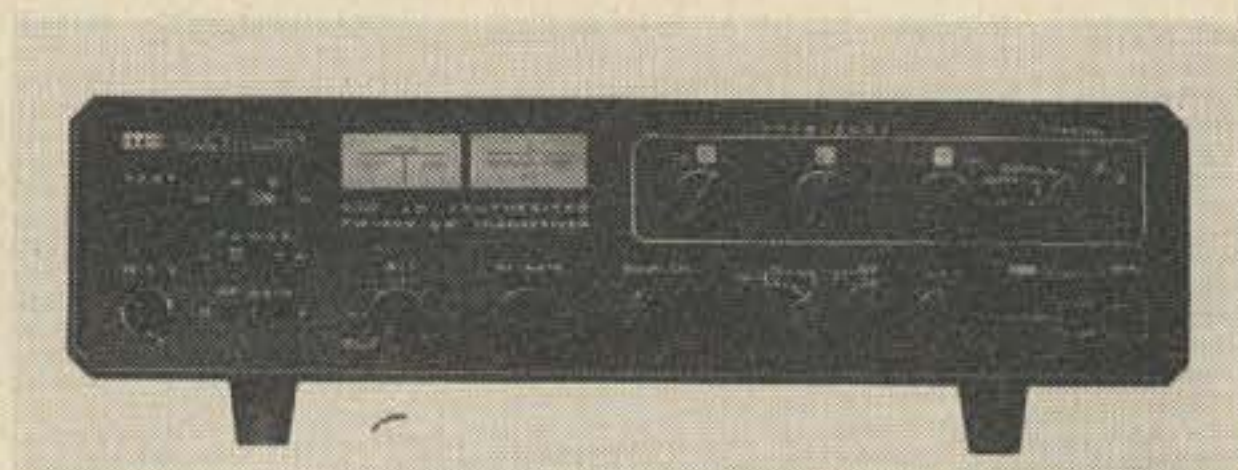

ITC Multi-2000 144-148
FM-CW-SSB

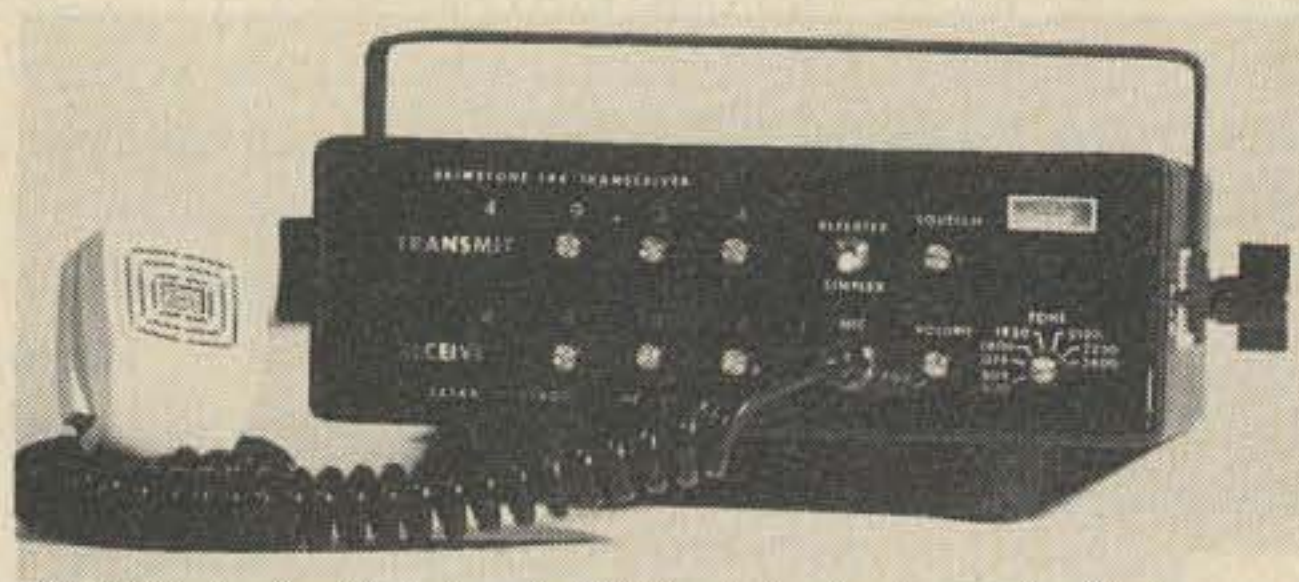


Brimstone 144 142-149
FM



EBC 144 Jr. 143.5-148.5
FM with priority



ICOM 21-A 146-148
ICOM DV-21

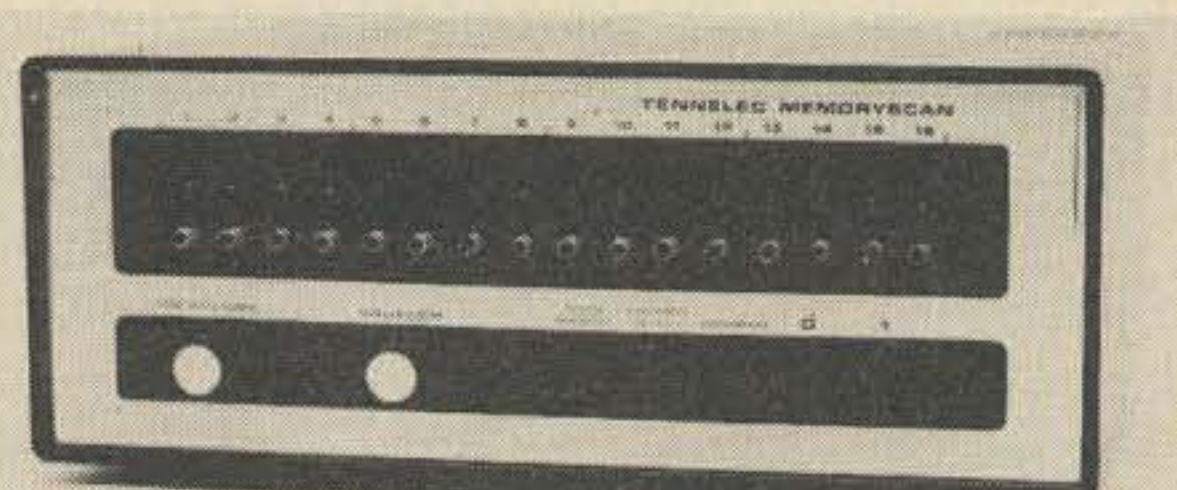

Tennelec Memory Scanner 30-50 146-170
450-510 MHz

AUDIO LAND is now offering high trade-in prices for your used equipment. Write for trade-in prices and price quotes. Now in stock – CUSHCRAFT – REGENCY – SBE – HAL COMMUNICATIONS – NEWTRONICS – HY GAIN – AMPHENOL – TURNER – E.V. – SHURE – STANDARD – TEMPO. 3000 xtals for most rigs. Rotors and cables. Stereo and Quad equipment – and much more. N.P.C. regulated power supplies. All major charge cards accepted. Several finance plans available. Write for our latest trade-in listing.


OUR HAMSSERVE YOU!

Sales: Earl K8BHP – Chris WB8OHK – Dave WB8TOB

Service: Jerry WB8OHJ – Jerry K8IDE

Audioland

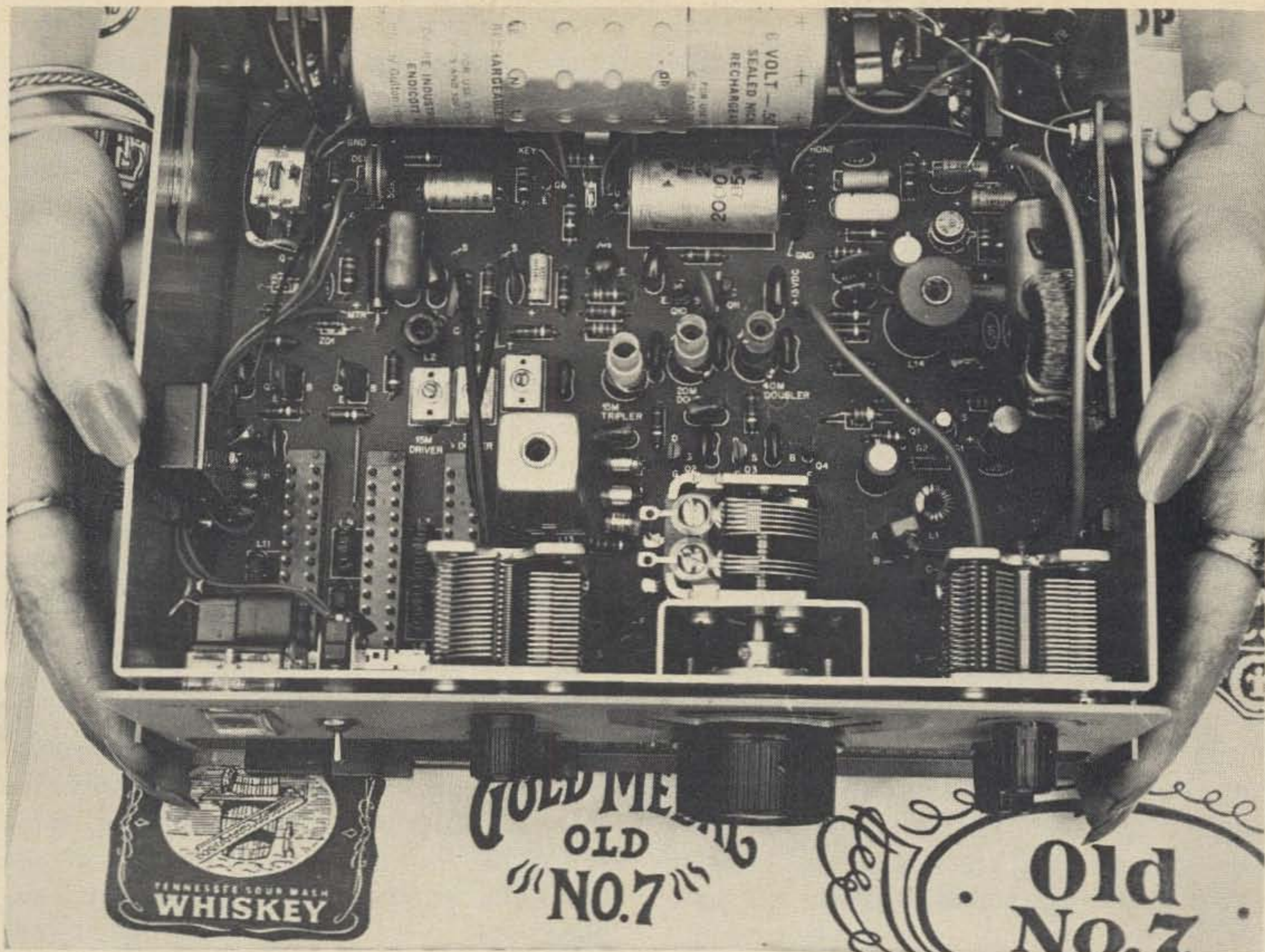36633 S. Gratiot
Mt. Clemens, Michigan 48043
(313) 791-1400



Ken Cole W7IDF
 P.O. Box 3
 Vashon WA 98070

Queen Roger Papa From Hotel Whiskey Seven

One of the many nice things about amateur radio is its eclectic layout.

We're all licensed eclecticians — and some of us are careless punsters. Put in proper English, hamming can be snuck up on from many directions: network with MARS or RACES, heavy DX or just hands-across-the-sea, teletyping, gigacycling with horns and dishes, roundtable socializing, repeaterwork, track-a-satellite, ATV, dreamy designing and build-it-from-scratch. The list is long and getting longer. And it's inclusive — once in the ring you can rattle with everybody.

Few of us settle down for good and all

with one mode or one band. Communication is dynamic, a lively art. The opportunities multiply as we exploit them. Tonight, in a little cottage in the west, a thoughtful W6 is putting dust covers on the RTTY gear to invest a few months in looking for YL's on Slow Scan. Soon he'll wonder about color.

A breakthrough in 3D may be the outcome. On a different tack, for more than a year I've been having a lot of fun with low power. The QRP fascination persists, but operating in miniature has lonely moments. It would be nice to have more company at eye-level, and that's why I'm writing this.

Homebrewers may recall that not very long ago it was so easy to end up with a (deleted) mess if you tried to design and build a transistor rig with a genuinely stable vfo, bandswitching and moderately useful power output.

Now, thanks to some of our bright and dedicated colleagues, and to the big-time R&D wizards of commercial electronics, impressive levels of solid-state rf power are within our reach. Stability is no longer a maddening problem, and components are available at prices that encourage building.

All it takes now is patient research, imagination, careful craftsmanship and lots of time. Or, if you just want to get in up to your ankles and have some QRP fun, there's this Heathkit.

The HW-7 is a three-band CW transceiver kit example of how ingenuity, careful engineering and economy can be teamed to turn out a novel and successful product targeted to a small market. Three, two and a half and two Watts on 40, 20 and 15, with sidetone and adjustable break-in. It's compact — four by nine by eight inches, plus fractions — and while the microsizing prizes may go to the two meter hand-helds, along with honors for giant-type repair and modification headaches, you don't need nerveless surgical dexterity to fiddle with the insides of the HW-7.

Every ham knows he can improve on any kit designed by the professional engineers . . .

Remove four screws, lift off the top half of the cabinet and every component is visible. Four more screws to drop the bottom shell and have at the circuit board. No cramping, layering or sequential disassembly tricks. A sturdy and attractive, truly portable, complete HF radio station for eighty dollars.

Today that's roughly the price of two steaks, a candle and a bottle of bubbly at a table the size of a bar stool — in a gloomy ambience of "Continental" fakery. By the time you read this you may have the privilege of choosing between an HW-7 and an evening of beer and pizza.

The simplicity of the front end of the receiver is breathtaking — one tuned circuit and one dual-gate MOSFET. One of the MOSFET gates looks at the vfo and the other at the antenna. You peak the tuned circuit with the "Preselector" control by tuning it to the vfo frequency, and you hear someone as the vfo is tuned to heterodyne with a signal. Audio I.F. With this type of reception selectivity and overall gain are uniquely dependent on the following audio circuitry, although somewhat less so if you want to get fancy with "Q" and amplification in an rf stage.

But simplicity and economy are important factors and the HW-7 is a workable compromise application of a clever concept. Of course there are problems, but in perspective they are acceptable. One is just a nuisance — the idling noise from the high gain audio IC — and another — microphonic sensitivity — is a real pain in the fulcrum.

If you turn up the audio (and only) gain control the footfalls of a fly on the cabinet sound like drumbeats. Well, almost. You can indeed talk to the Relative Power Meter and hear yourself clearly in the phones. More about this further down the log.

Every ham knows he can improve on any kit designed by professional engineers, and I suppose a philosophical detachment about this is common in kit factories, but if Heath sees the photo accompanying this article equal time may be demanded, so I'll explain the obvious haywiring.

On the left, fingered by a thumb, a 7,000 kHz crystal market oscillator, then clockwise on the rear panel a toggle switch in the ground return to the added batteries, and underneath it a coax socket paralleling the phono type supplied for the antenna connection.

Next, two six volt nicads and a mess that includes external power terminals, a fuse holder squinched into the hole that held Heath's rather outré (how you like that?) power socket, diode polarity protection (I'm human), ceramic by-passes for insurance and an extra phone jack.

On the right side is a junk box audio filter to take the edge off the IC hiss and microphonics mentioned earlier — an 88 mH toroid in parallel with .15 mF is connected

from ground to the midpoint of two .047 capacitors which are in series between the kit phone jack and the added jack.

If these additions do nothing else they demonstrate that Heath left a lot of room inside the HW-7. You can really fool around in there, and because of the wrap-around cabinet design mounting holes on the side won't show — they think of everything.

Wiring in a speaker amplifier is a temptation I've resisted so far. The manual mentions a nominal 1,000 Ohms output, so for this and other reasons I was surprised to find, after trying several sets, that the headphones I preferred are 8 Ohm (very nominal) and what you might call "bottom of the line" from Radio Shack's stereo salon. Labeled "Nova 10" and priced around four dollars, on strong signals they serve as speakers, not well, but better than you would expect.

Now about the vfo. It's stable enough that I spend too much time listening to sideband on 15, and I suppose someone will soon come up with a scheme to put the HW-7 on DSBSC. The dial is described as "virtually backlash-free" and that's close.

Good verniers are expensive. Although the catalog and manual show dial markings every 25 kHz, mine are every five. Incidentally, a later kit than mine showed another difference — heat sinks are included for the two output transistors. This is a wise precaution I've neglected to copy, although I will, and so far no dissipation problems.

After assembly, dial calibration is a simple synchrodyne two-step, about a minute per band. Checking the results around the dial with test gear did indicate gentle plate bending was in order, and this took a little patience, but once done the calibration stayed put.

It won't serve as a frequency standard, but the vfo's reliability turned out to be good enough to justify removal of that security-blanket low-edge marker oscillator on the port bulk head.

The adjustable timing on the break-in circuit works perfectly, but the sidetone had a rough edge and was uncomfortably loud. Tastes differ, but those readers who have an HW-7 and are unhappy with the sidetone can try the following: Connect a .01 ceramic

from base to collector of Q10; add a 47k resistor between C45 and R34; change R35 from 1,000 to 270 Ohms. This gave me a better note, smoother and suitably attenuated, which no one else may hear as an improvement. However, as noted, adding and subtracting from the circuit board is carefree fun.

When you have tuned in a signal with the vfo, peaking the preselector precisely can be a trial. With a tiny knob you are trying to come as close as you can to the best picofarad out of 393.

A vernier here would be nice, even a large knob would help, but out of respect for the aesthete who did a nice job on the panel I just try harder, combining delicacy and expletives. By the way, this control will also, when conditions are right, bring in short-wave broadcast stations — irresponsible elements of the synchrodyne front end, operating in diodyne mode as you tune segments between the ham bands. Fortunately it doesn't do this very well, but on the other hand you may think of it as a bonus.

Relative power output is indicated by the meter, which is driven by a diode connected to a safe point on an antenna to ground voltage divider. Hardly any levity is intended — a dummy antenna provided does indeed warm up when you test the transmitter. The psychological dividend is obvious.

A reminder now that should be unnecessary — Novices are a friendly bunch who couldn't care less about your final power.

A multimeter here would be a nice frill, but, again, UP is where the price would go. However, it's easy to modify the meter circuitry to indicate normal battery voltage and, by the difference between key-up and key-down readings, when charging or replacement is due.

I connected the hot side of the meter to the arm of a miniature SPDT toggler mounted just to the right of the meter — where it neatly replaces a panel bolt. One side of the switch then goes to the normal connection and the other through a 100k resistor to the battery buss.

When the switch is in battery position the meter reads slightly above midscale for

twelve volts. The simplest of mini-changes, but it's very nice to know the condition of your power source when you are operating tiny Watts.

In the beginning operating QRP instead of three or four hundred Watts was educational. It still is. The first revelation was that 40 kHz up from the bottom, a putative rallying point for minipower freaks, seemed to be a frequency with magnetic appeal for CW operators of whatever potency.

I've yet to identify a QRP station at this point on 40, 20 or 15. My fault, perhaps, for exposure atop a 2 Watt molehill tends to be diffident rather than determined.

On the other hand, as QRP experience accumulated it was cheering to find that courtesy was the rule and that, once tiny-mite status was confessed, the fellow on the other end would readily move me to a better spot, fine-tune, filter and listen harder. Courtesy is so common that the occasional put-down is only amusing.

Another lesson was that the relative quiet of the Extra-class CW slots isn't really all that promising for QRP. There's a lot of heavy artillery there, patiently awaiting DX targets of opportunity. One exotic yoo-hoo from Ruritania and you're wiped out.

A reminder now that should be unnecessary — Novices are a friendly bunch who couldn't care less about your final power. Most of them are trying to get their code speed up for the next exam, and working other novices isn't the most efficient way to do it. Working them with error-free CW just fast enough to stretch their mental muscles is of mutual benefit.

In the past I called on them fairly frequently, but not as often as a good neighbor should. The Novice bands are good places to give and get encouragement.

It's a fact of life in QRP country that you have to play your cards carefully. Just imagine throwing away 20 decibels or so of your current electronic pizzazz and then think of ways to compensate. Propagation conditions, antenna efficiency and applied psychology are suddenly very important. So is dumb luck.

The following surprises convinced me that sometimes perversity is well rewarded. Experimenting with supply voltages lower

than the 13 recommended in the HW-7 manual (nine turned out to be the low limit) resulted in a childish itch to make it on 20 with six "C" cells. I was still using a 14AVQ, a good vertical but hardly the best for QRP.

One string of CQ's on 14055 and JA7AME replied. We exchanged 559 reports and chatted for about 20 minutes despite a slow QSB and some competition on the frequency, mentioned by Kan but inaudible to me. Due credit to his three element beam. Nevertheless I found it astonishing that a more or less omnidirectional trap vertical, 10 feet above the ground, would lob across the Pacific a significant fraction of my Watt or so of input power.

Kung Fu: "It is easy to push needle into wooden wall. Try it with football and you go bananas."

Considering the efficiency figure of the final, whatever that is, the anomalous losses between it and the antenna, and the wasteful distribution in azimuth, the performance surpasseth human understanding. Mine, anyway.

Satisfactory reports come in from 6's and 7's in the opposite direction, so it doesn't seem likely that the vertical installation has a freak lobe favoring the Far East. Could it be that QRP really works?

Another surprise with the same antenna was SP9PT/VE8, a peak-climbing expedition packing a transceiver and gas-engine powerplant around in the Far North. En route to Mt. McKinley, they came back to a call with 579 from somewhere near Whitehorse.

Good reports are the rule from Alaska, with KL7MF's carrying extra emphasis since Hal — now retired, I believe — was the F.C.C. at Anchorage. For some reason I seem to work a lot of R.I.'s — is there a W.A.R.I. certificate? (How NOT to QSO an R.I. was described in the March, 1966 issue of this magazine.)

The day after the SP9/VE8 contact any remaining skeptical reactance was neatly tuned out by an exchange of identical reports with an 800 Watt powerhouse a hundred miles away on 40. He read his report from a meter and mine was just a guess, and perhaps his receiver had a hot

SPEC COMM 512/560 The New 5W 2M FM Portables With "Snap Pack" Modules

- **5 TIMES THE POWER** of the usual 1 Wt portables! But draws *only* 2x the current! While BP-1 Battery Module provides *3x the capacity* of the usual portable or HT batteries.
- **EXCLUSIVE HOT CARRIER DIODE MIXER** virtually eliminates intermods & receiver overload.
- **LARGE SCALE USE OF ICs IN RCVR. and XMTR.** for superior, more reliable performance at lower cost!
- Engineered and built in U.S. — Top Quality throughout.
- **FACTORY DIRECT SALES & SERVICE.** You deal direct with the experts.

FEATURES

*BP-1 Btry. provides apx. 8 hrs. norm. operation/chg. * LED Btry. voltage indicator * Super eff. xmtr — draws *only* 900 mA @ 5W. out * High quality Ceramic mic * Fantastic Squelch — fast & sensitive * Extremely sens. MOSFET front end, 0.3uV/20dB Qt. * Incredibly sharp IF, at least -80dB @ ±30 kHz * Single Conv. Rcvr. — *superior* to dual conv. designs for spurious resp. rejection! * Uses inexpensive TR22 xtals * 146.52 xtals supplied * Trimmers on *all* xtals * Reverse polarity protection * Final transistor fully protected * Large 3" spkr. for *unusually good sound* * Ext. spkr. jack * Front *and* rear antenna jacks * *Rugged* but *light* — 2 lbs. * Size 2¼X6X8" * Electronic T/R-no relay problems * Very easy to service.

See Review Article in April 73 Mag.
Send Card for Data Sheet.



SC512 W/BA-1 "Snap Pack"

A limited number of units are In Stock for Immediate Shipment.
(Allow 2 wks for personal checks to clear.)

- **USE IT PORTABLE — OVER THE SHOULDER** — with the Heavy-Duty BP-1 Nicad Battery "SNAP PACK"
- **USE IT MOBILE** with the BA-1 25 Wt. Amp "SNAP PACK"
- **USE IT FIXED** with the AC-1 AC Supply "SNAP PACK"
- **UNIQUE "SNAP PACK" MODULES** merely Snap-On and automatically interconnect — No messy wires or cables to hook-up. It only takes a few seconds!

SPEC COMM 512 \$199⁹⁵
5W 12 channels

SPEC COMM 560 \$179⁹⁵
5W 6 channels



SC512 W/BP-1 "Snap Pack"

Inquire about our:

- Package Deals
- SCR-100 Repeater Receiver Board
- SCT-100 Transmitter Board.



100% Moneyback Guarantee

100 Day Warranty

Please ship the following:

- SC512 @ \$199.95
- SC560 @ \$179.95
- MB-1 Mobile Mount @ \$7.95
- BP-1 Pkg. (Btry pack, chgr., ant., carrying stp) @ \$79.95
- BA-1 Amp @ \$84.95
- AC-1 Sply. @ \$44.95
- SCR100 @ \$89.95
- Precision Xtals ±0.001% @ \$4.95 (List on separate sheet)

Amt. Encl. \$ _____ M.O. CK.

M/C BAC Exp. Date _____

Card No. _____

M/C Interbank No. _____

Add \$3.50 Shipping/Handling
PA residents add 6% tax.

Name _____

Address _____

City _____ State _____ Zip _____

SPECTRUM COMMUNICATIONS

BOX 140, WORCESTER PA 19490 (215) 584-6469

front end and a low noise figure, but on 7 MHz the HW-7 is no slouch. So smile thank you and enter it in the log.

But there are hard lines too. In the beginning you find out how patient you can be. Call CQ and wait. Again, and wait. Gently rock the dial just to be sure and try again.

Oops, sounds like a station you couldn't hear has just finished a transmission — his contact is replying on the frequency but he doesn't mention any QRM. Bittersweet exculpation. Move and try again in vain.

In your mind an imp sketches cartoons: a fine mist of rf sprays out from your vertical about as far as it would go from the lawn sprinkler; a pingpong ball materializes from the Yagi, arcs gracefully and plops to the ground; electrons sliding back and forth on the long wire occasionally lose their grip and float to the grass. Images of a ruder nature bring a rueful smile. Just don't get discouraged.

If you aren't lucky with CQ's listen for some from a district at an optimal distance according to the time and band, and jump in feet first if you hear no replies. If there's

competition don't move away until you hear a contact made.

Playing it cool by opening with a careful search for CQ's that are reasonably strong and unanswered may be the smart way to begin your QRP log, but it's human nature to want to call to an empty corner of space and hear an acknowledging reply.

There are times when reality is a slippery concept and it's nice to be noticed. But however you shuffle the deck, the high cards in this game are patience, determination (stubbornness?) and lore of the art.

Getting results with expertise instead of KVA muscle purchased from a power company is, besides being good ecology manners, a challenging exercise bringing many rewards. Not the least being log entries sure to elicit gasps of admiration from your skeptical Watt-rich buddies.

Snorts of disbelief are equally satisfying, and to these you can reply with a reminder that the narrow edge of the hand has been proven more effective than the blunt fist by hundreds of TV scripts. (If not by the commercials.)

Kung Fu: "It is easy to push needle into wooden wall. Try it with a football and you go bananas."

Another benefit is that competing from a position of disadvantage does discipline the mind wonderfully. Little is taken at face value: ground systems are refurbished; old connections resoldered; everything that can be tightened profitably is; antennas are re-evaluated, lowered, raised, slewed and tipped; mismatches are analyzed and corrected; slipshod and make-do are sins of the past; test gear is put to work as dust motes rise from exhumed textbooks. All that neglected ham housework gets attention and in the process your smarts multiply and amateur radio benefits.

So operating low power on the dc bands is rewarding and instructive, besides being a lot of fun. But it hasn't been a wildly popular aspect of our hobby and I think the Heath Company deserves credit for taking a chance with the HW-7. How about a minute of meditative silence in congenial tribute? I could use that.

... W7IDF

ALUMA TOWERS

LOW PRICED

Made in Aluminum

- ★ TELESCOPING
- ★ WALL MOUNTED
- ★ GUYED

FOR:

**TV — CB — HAM
MARINE — MOBILE
RADIO TELEPHONE
COMMERCIAL**

Towers to 100 feet. Specials designed & made. See dealer or call.

ALUMA DIVISION

FRED FRANKE, INC.

Box 2806ST
Vero Beach, Florida 32960 U.S.A.
Phone (305)-567-3415
Cable: FREDFRANKE VEROBEACH FL.
Some Territories Available

What's All the Shouting About ?



It's the All New *Clegg* FM-DX

Amateur Net \$589.95 — Factory Direct Only

**Owners are shouting their praise
for all sorts of reasons
The ones we hear most often are ,**


- The operating simplicity, accuracy and stability of the Synthesizer and LED Frequency Readout.
- The unmatched receiver performance with super sensitivity and freedom from spurious responses.
- Those beautiful, clean 35 Watts of Transmitter Output.
- The rugged Modular construction.
- The 143.5 — 148.5 MHz coverage — opens a whole new world of SIMPLEX operation.

**UNTIL YOU TRY ONE YOU WON'T KNOW WHICH
FEATURE YOU WILL SHOUT ABOUT - PROBABLY
ALL THE ABOVE - AND MORE! CALL CLEGG'S TOLL
FREE NUMBER TODAY FOR DETAILS ON THE FM-DX.**

Clegg

208 Centerville Rd. Lancaster, Pa.
Toll free sales & services phone (800) 233-0250
In Pa. call (717) 299-7221 (collect)

MORE

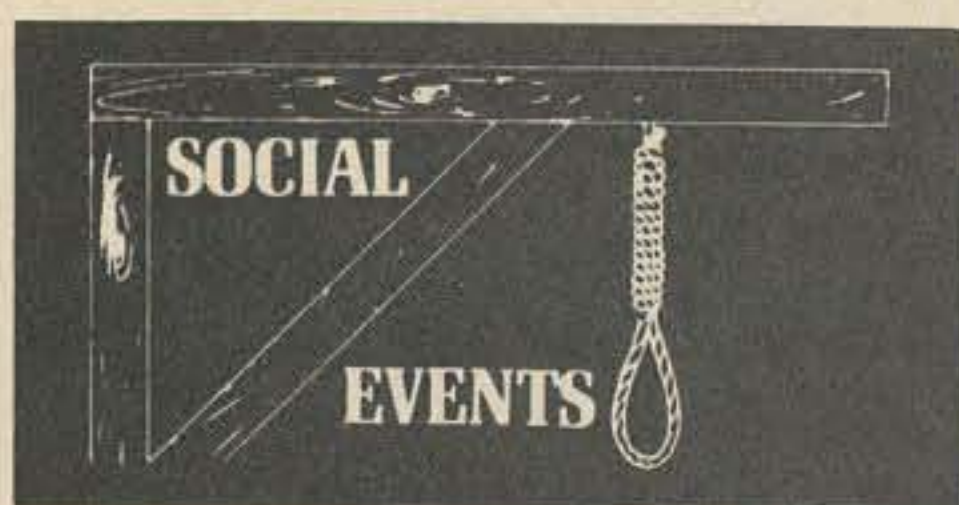

from page 21

person; chicken dinner \$6 per person. Activities begin at 10 am to sunset, dinner served 1 pm to 3 pm. Program: hidden transmitter hunt, horseshoe pitching contest, ARRL forum, radio control model airplane flying demonstration and fun and games for the kids. For tickets and program send your remittance (check or money order) to 19-79 Repeater Association, Box 221, Malden MA 02148.

BEREA OH SEPT 27

The Annual Cleveland Hamfest and Flea Market will be held Saturday, September 27th, at the Cuyahoga County Fairgrounds in Berea. Easy access from Hopkins Airport, Interstate I-71, I-90, and the Ohio Turnpike. Listen for the Buckeye Belles or Chix and "Talk In" from the East on 146.76, South on .82, West on .88, and locally on .52 and .94. Eastcars, Midcars on 40 and 80 M and 52.525 for farther out. Tickets \$1.50 before Sept. 25th — \$2.00 at 8:00 when gates open. Flea market parking earlier — bring your own tables. For early tickets and information on motels and campgrounds, send a check and SASE to: Cleveland Hamfest Association, Box 43413, Cleveland, Ohio 44143.

MADISON WI SEPT 28

3rd Annual Dane Co. Swapfest will be held in Madison WI, Sunday, Sept. 28, 1975 at the Dane Co. Expo Center Youth Bldg, rain or shine. Sponsored by Madison Area Repeater Association. Prizes, all you can eat pancake breakfast and beef bar-b-q luncheon, family fun, commercial exhibits. Adv tickets & tables \$1.50 — \$2 at door. For advanced tickets write M.A.R.A., Box 3403, Madison WI 53704.

LOUISVILLE KY SEPT 28

The Fifth Annual Greater Louisville Hamfest will be held on Sunday,

September 28, 1975 at the Kentucky National Guard Armory on Crittenden Drive at I-65. There will be a large indoor exhibitors area, large paved flea market area, club meetings, technical forums, prizes for the whole family and ladies' Bingo. Admission adults \$1.50 — under 12 free. Flea market pays admission plus \$1 per space. For info contact K4GOU, 2415 Concord Drive, Louisville KY 40217 (502 634-0619).

ADRIAN MI SEPT 28

The Adrian Amateur Radio Club, Inc., will hold its Fall Hamfest on Sunday, September 28 from 8 am to 3 pm at the Lenawee County Fairgrounds, Dean Street in Adrian. All buyers, sellers and visitors welcome. Cost \$1 in advance. \$1.50 at gate. Table size 8 ft. \$1.50 per half. Talk-in on 146.46 — .52 — .94 MHz. For more information write Adrian Amateur Radio Club, P.O. Box 26, Adrian MI 49221.

OTTAWA ONTARIO OCT 3-5

The 1975 Radio Society of Ontario Convention, hosted by the Ottawa Amateur Radio Club, will be held at the Skyline Hotel, Ottawa on October 3, 4 and 5, 1975. Programs include: 9 technical forums (including W2NSD/1, 73 Magazine's Wayne Green), commercial exhibits, flea market, technical displays, C.R.C. satellite display, major drawings and door prizes, and much more. The Skyline Hotel is located within walking distance of Parliament Hill, National Arts Centre, the Royal Canadian Mint and in a major shopping area.

EAST RUTHERFORD NJ OCT 4

The Knight Raiders VHF Club's auction and flea market will be held on Saturday, October 4th, at St. Joseph's Church of East Rutherford, Hackensack Street, East Rutherford. Free admission, free parking, refreshments available. Talk-in will be on 146.52 and 146.94. Flea market tables: \$5 for full table, \$3 for half table. Reserve your tables in advance by writing to The Knight Raiders VHF Club, Inc., K2DEL, P.O. Box 1054, Passaic, New Jersey 07055.

WAKEFIELD MA OCT 4

Quannapowitt Radio Association

annual auction, greatest and oldest in N.E., Saturday, October 4th, St. Joseph's Parish Hall, Wakefield, Massachusetts, 10 am to 4 pm, doors open 9 am, 10% commission, no minimum. Door prizes, special prizes. Talk-in 146.52.

MEMPHIS TN OCT 4-5

Memphis is beautiful in October! The Memphis Hamfest, bigger and better than ever, will be held at State Technical Institute, Interstate 40 at Macon Road, October 4 and 5. Demonstrations, displays, MARS meetings, flea market, prizes. Talk-in on 3980, .34-.94 and MARS. Contact Harry Simpson W4SCF, Box 27015, Memphis TN 38127 or telephone 901 358-5707.

LEAGUE CITY TX OCT 5

The Tidelands Amateur Radio Society's annual hamfest is Sunday, October 5, 1975, 9 a.m. 'til-? at the Galveston County Park, League City. Advance registration \$1.50; \$2 at door. Free parking, refreshments available. Main drawing for door prizes will be at 3:00 p.m. Swap booths available. For information, send a S.A.S.E. to Luke Sterling, 105 Seabreeze Drive, League City, Texas 77573.

WARRINGTON PA OCT 5

The Mt. Airy VHF Radio Club (the Packrats) are holding "Hamarama 75" at the Bucks County Drive-In Theater, Route 611 (Easton Rd), Warrington, Pa., on Sunday, 5 October 1975, 8 am to 4 pm. Registration \$1.00, tailgating \$2 — bring your own table. Parking for 1000 cars. Talk-in via W3CCX/3 on 52.525, 146.52 and 222.98/224.58 MHz. For information contact Lee Cohen K3MXM, 8242 Brookside Rd, Elkins Park, Pa. 19117. Phone (215) ME5-4942.

COLUMBUS OH OCT 10-11

On October 10 and 11, 1975, the ARRL Great Lakes Division Convention will be held in Columbus, Ohio. The actual site is on the north side of the Ohio State Fairgrounds just off 17th Avenue. There will be a number of well-known personalities among the amateur radio fraternity there both as guests and as speakers. For more information contact: Ira Bickham, Chairman, Industrial Displays, 1423 Thurell Road, Columbus, Ohio 43229.

CHARTER SUBSCRIPTIONS -


LAST CHANCE!

The first issue of BYTE is now out and it is going fast... so if you want to be sure to have a complete collection of this new experimenter's magazine, you'd better subscribe right now.

BYTE introduces you to the world of the small computing system... with loads of construction projects... evaluations of kits... news of new products of interest to the amateur and experimenter... sources of programs... and ways to use these inexpensive computers... the world's greatest toy.

Is it possible to have your own computer for well under \$1000? It is now, using newly invented techniques... it wasn't really possible just a year ago. And prices are coming down in this field faster than food prices are going up. Get into this now with BYTE and enjoy this whole new field for fun.

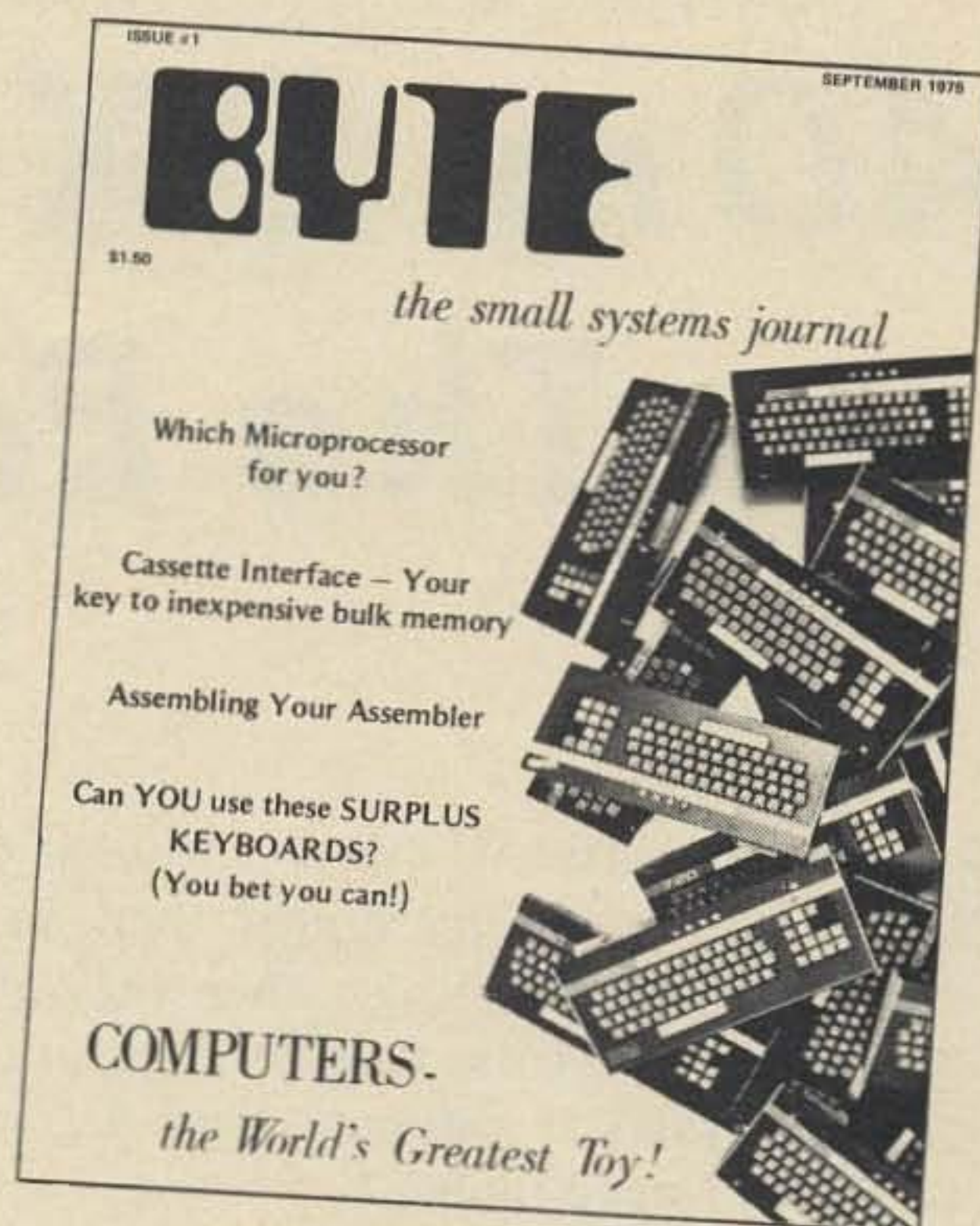Charter subscriptions are \$10 for one year... regular subscriptions will be \$12. The Charter subscription rate will hold until October 15th... but first issues of BYTE can only be sent out until the supply is exhausted.



BYTE Subscription - BYTE • Peterborough NH 03458

\$10 Charter Subscription one year

- Cash enclosed
- Check
- Bill me
- Master Charge
- BankAmericard

Card No. _____

Expiration date _____

Signature _____



Total enclosed \$ _____

Name _____

Address _____

City _____ State _____ Zip _____

40 m DX Antennas - The Easy Way

The trouble with 40 meter antennas is that they are usually longer than city lots, unless they are verticals. Then they are dependent on hard to dig radials. That is my problem. But what if antennas were half as long, and didn't need radials?

I have a 74 ft. wide lot, and was using 40 meter phased verticals to handle phone patches for the Antarctic stations during their winter, when no mail goes in or out. My yard is full of trees, most of which are as high as the verticals, and they are in leaf during this period, when it is summer here.

After several seasons, during which I handled a lot of traffic, I decided I needed to get a better signal from down there, and as well, put in a better signal to them.

I read an article on folded half wave radiators (by William Orr, *Ham Radio*,

March, 1970) and tried one out. However, a horizontal antenna must be nearly a half wave above ground, or its DX properties are no better than my verticals with no radials. Then it dawned on me that vertical dipoles need no radials, and sloping dipoles have gain off the front of the slope.

My towers are only 48 ft. apart — not a half wave, but I decided to try. I sloped one dipole from the top of my 35 ft. TV tower to the southwest corner fence post at the back of my yard, and the other from 35 ft. up on the 47 ft. ham tower to the southeast corner of the yard. The antennas were pulled up by pulleys, making them easy to adjust and tune. On the southeast antenna I was 10 dB stronger in Miami (167°) than in New Orleans (211°), and vice versa when I used the southwest antenna. When I used both of them I was better in both directions than with either one alone.

When I started to handle traffic to the Antarctic I was amazed. I pinned the meter on several occasions at South Pole Station, and was 10 over 9 at McMurdo Sound. That season I ran more patches during June, July, August and September than any other station and was told by McMurdo that I ran more than one fourth of all patches in spite of the fact that I used only 40 meters and they used both 40 and 20 and 20 meter MARS. Many nights I was running phone patches when the other two "regulars" were unable to even copy the Ice stations. Fig. 1 shows the layout of the antennas. It is

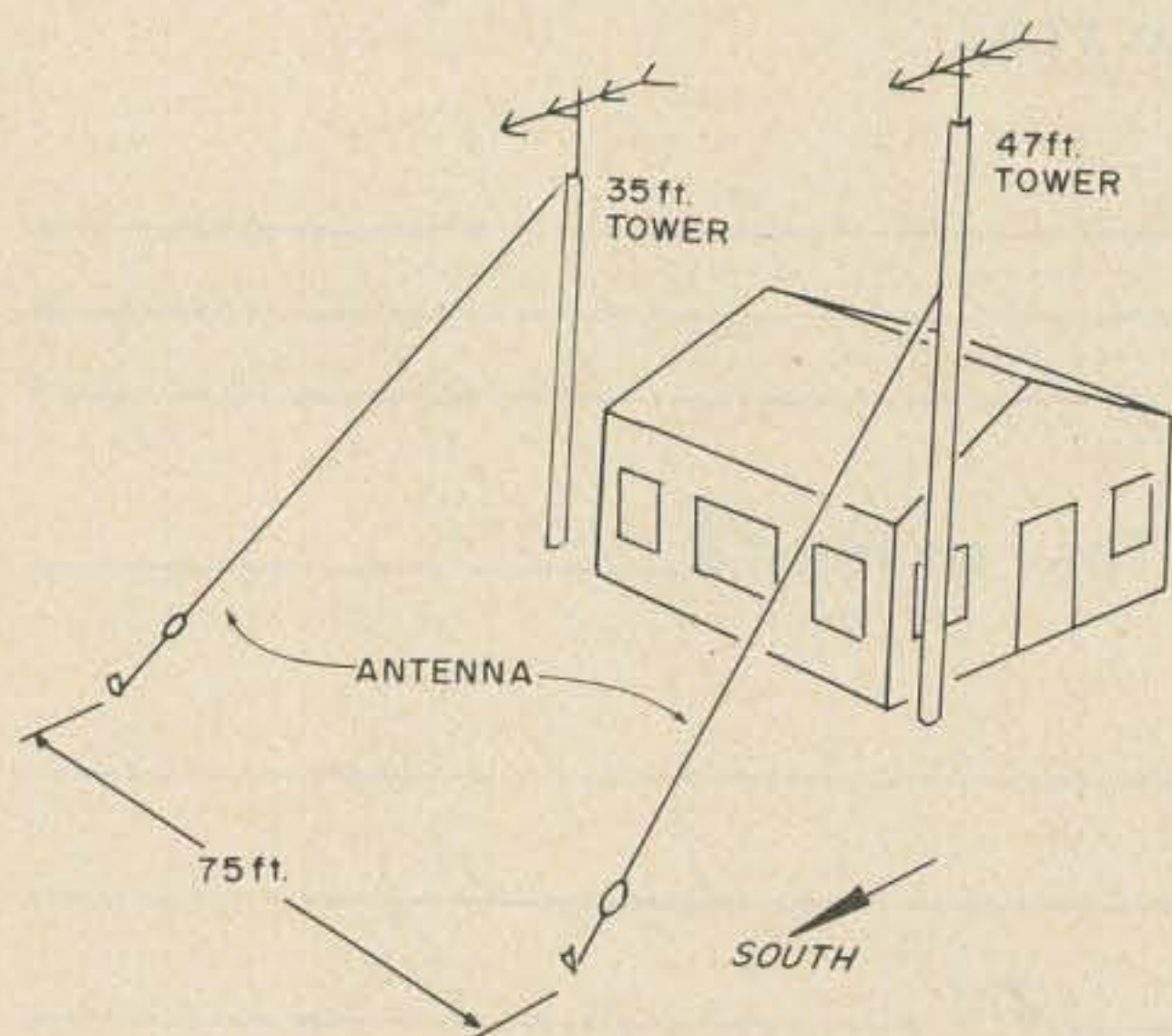


Fig. 1. Antenna layout.

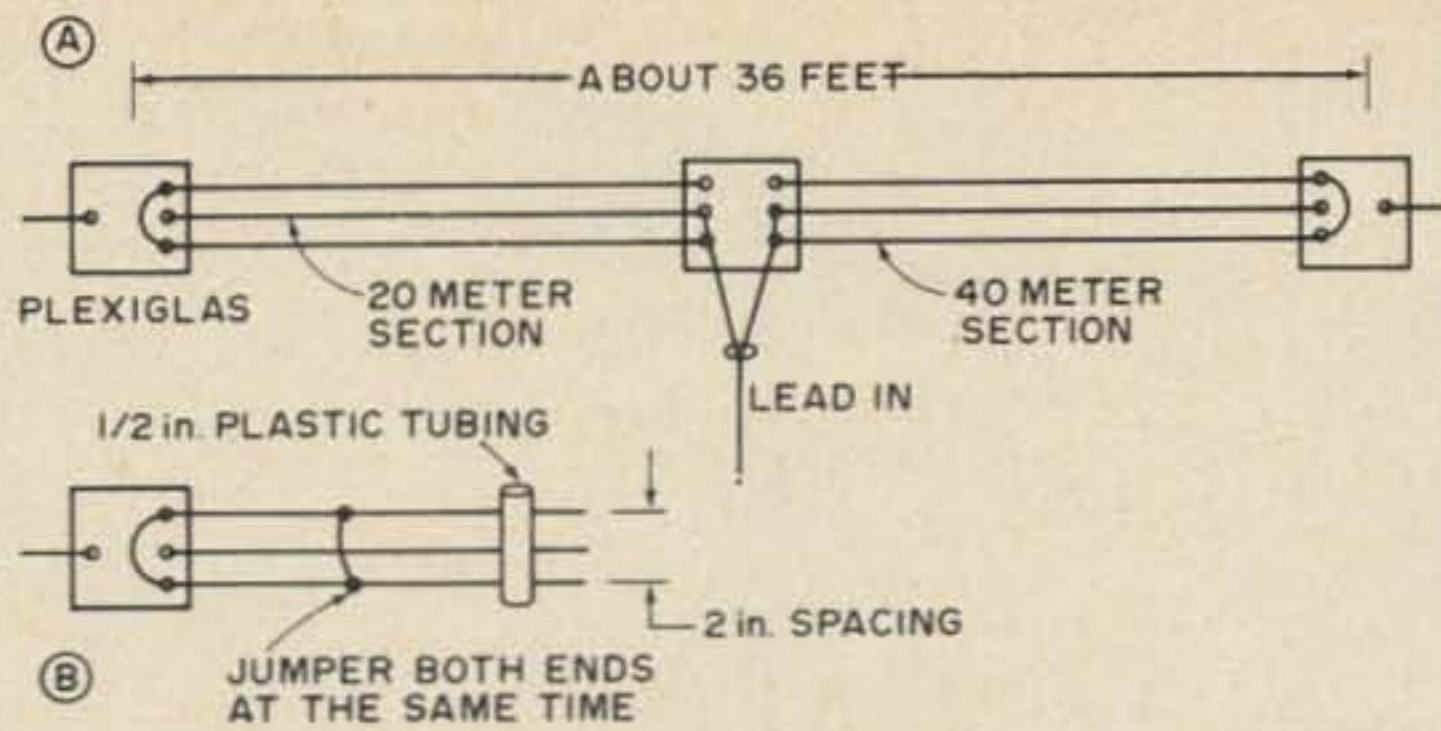


Fig. 2. (a) The design of the antenna. Cut the antennas for the low frequency of the band, and then, if necessary, tune by adding the jumper as shown. Then tune the higher frequency antenna by trimming at the ends. The antennas will cover quite a good band with low swr. (b) The 40m section can be tuned by moving the jumper.

important that both antennas be tuned to the same frequency for accurate phasing. By inserting a half wave of coax in one leg I can end fire into California and the East Coast, although the gain from the slope will be missing in these directions.

Fig. 2 shows the design of the antenna. The length of the dipole will be about the same as any other type of dipole and should be cut for the low end of the band. The 40 meter section can be tuned by moving the jumper as shown in Fig. 2b. Move both jumpers — one at each end — the same amount toward the center to shorten the antenna. To shorten the 20 meter section just trim both ends. There will be little

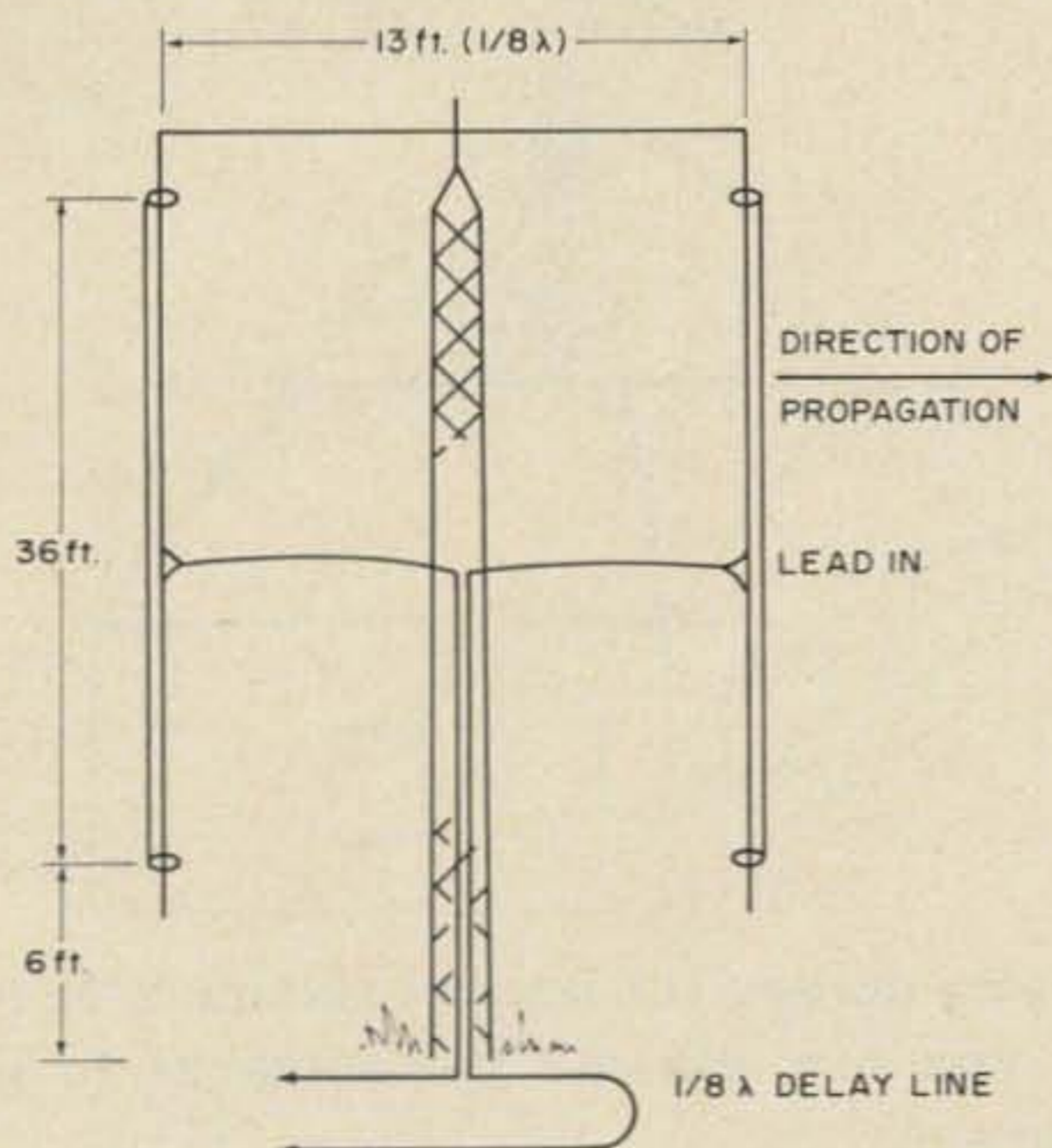


Fig. 3. Alternate antenna array for one tower. This array is 1/8 wave spacing on 40 meters and 1/4 wave spacing on 20 meters — a very good combination. A little imagination would show you that this could be made to rotate.

reaction between the antennas. The spreaders can be made of 3" lengths of 1/2" plastic tubing, with holes spacing the outside wires about 2" apart, and the other antenna between them. Space the spreaders about 6 ft. apart and fasten them either with epoxy cement or by making the holes slightly small so they won't slide. The wire can be #16 or #14, prestretched.

The tops of the antennas are about 33 ft. high, and the bottoms are about 6 ft. off the ground out of the reach of children.

Do not use a balun, and connect the coax shield to the lowest side of the dipole. It is easier to understand this antenna if you think of it as a ground plane with one radial.

A prominent antenna manufacturer told me that this array with the slope probably had a gain of about 10 dB.

I used RG59 for the lead in. The current is divided between two antennas, and RG59 has ample capacity for full legal power this way. I used 3/4 wavelength in each lead in. This makes a transformer match and gives me close to unity swr. Run the lead in at right angles from the antenna as far as possible. Keep the vertical angle less than 45° if possible to get maximum vertical polarization. You will be pleased with the absence of noise because of the nulls on the side of the array, and the lack of interference.

If you do not have two towers, try Fig. 3 for a one tower array. This is a cardioid array, with no slope, but takes advantage of the shortened antenna and phasing. By changing the delay section to the other lead in the direction of the array will be reversed.

There is one more array which this combination makes possible. This is shown in Fig. 4. Going back to my comments about the directive effect on my two antennas in different directions, a new idea comes up.

How about a rotating beam made of three or four antennas sloping from the top of a 35 ft. TV tower? You can either use separate feedlines or a Dow Key relay. If you use the relay, which grounds the unused lines, make the lead from the antenna to the relay 1/4 wave. This will open the center of the unused antennas and detune them. If you have a switch which leaves the lines ungrounded, then use half wave lines and they

FREE!

The All-New 1976 Lafayette Radio Electronics Catalog



The most comprehensive
consumer electronics
catalog available!

Hams, see the exciting new 1976 line of exclusive Lafayette Parts, tools and test equipment for do-it-yourself projects at Lafayette's traditionally value-packed prices. Stay tuned to the top amateur gear, name brand equipment and our huge selection of the latest in electronics. Send for your copy today!

- Stores Coast-to-Coast
- BankAmericard and Master Charge

- Transceivers • Antennas • Meters
- Transmitters • Rotators • Test Equipment
- Receivers • Masts • Parts, Cable

Lafayette

The Electronics Shopping Center
111 Jericho Turnpike Syosset, L.I., N.Y. 11791

Lafayette Radio Electronics
111 Jericho Tpke., Syosset, L.I. N.Y. 11791

Dept. 38095

Send me your FREE 1976 Catalog

Name _____ Apt. _____

Street _____

City _____ State _____

Zip


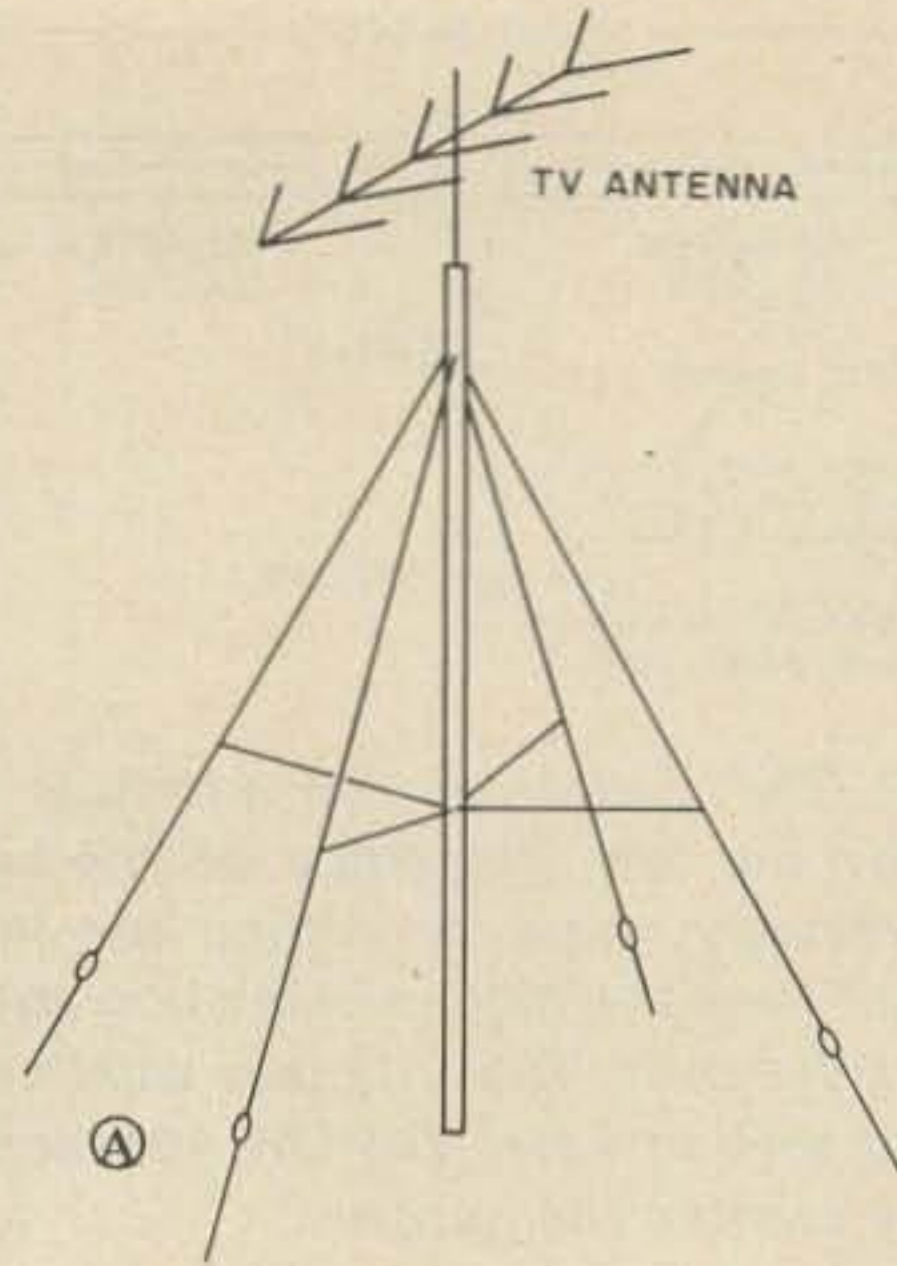


Fig. 4. (a) Rotating wire beam. You can either use four feedlines or use a relay. If you use a Dow Key relay, which grounds the unused lines, make the lead from the antenna one quarter wavelength to the relay. Then, when grounded, the antenna will be open in the center and detuned. If you use a coaxial switch, use half wavelengths from the antenna to the switch, and when the lead in is dropped from the switch the center of the antenna will be opened and thus detuned, by the rule that a half wave repeats the open impedance at the other end of the line. If you use a Dow Key relay with three positions, you can use just 3 antennas with nearly the same results. Naturally, you can also use the three antennas as guys for the tower. (b) Antenna mounted atop the TV tower.

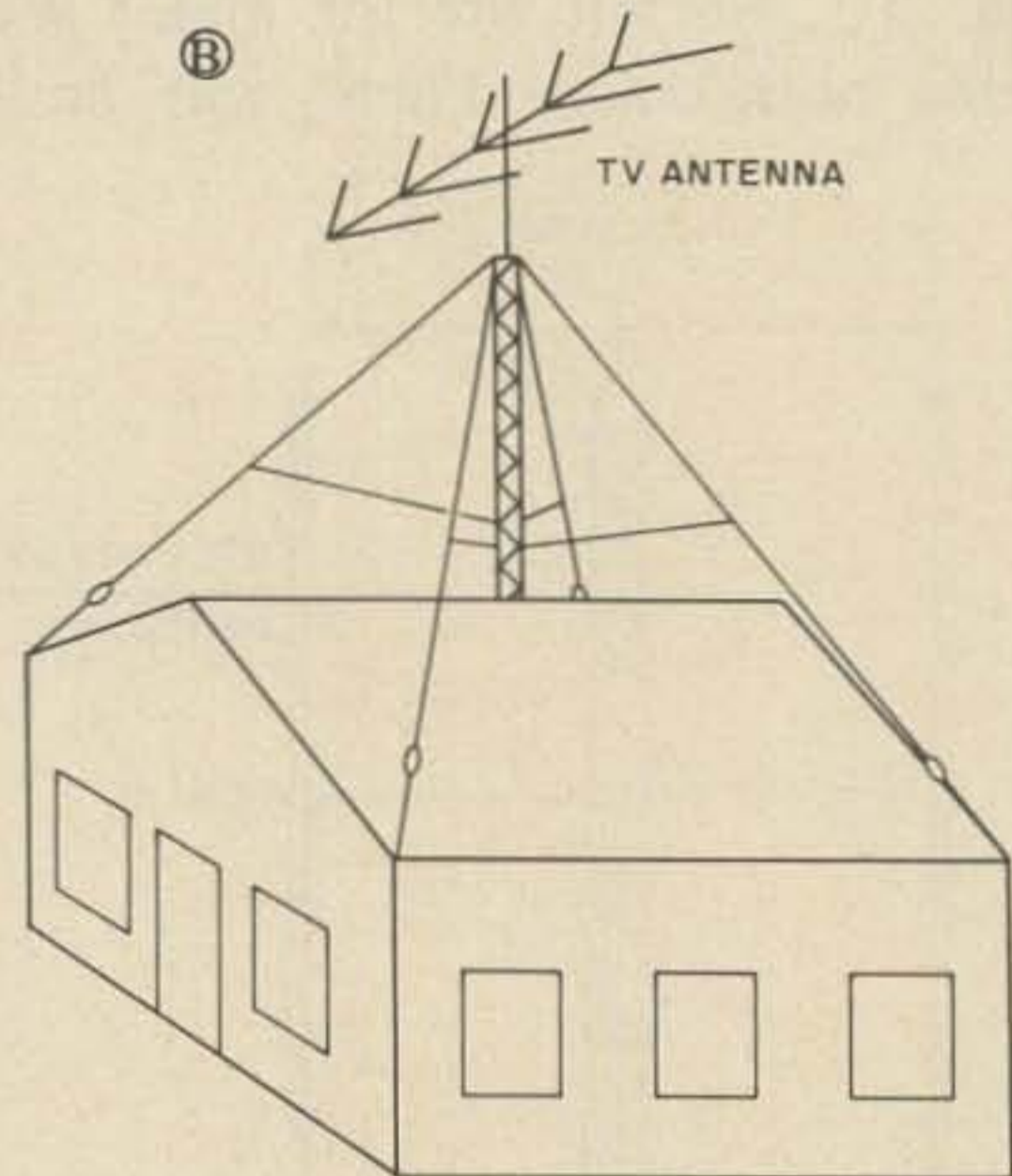

will also detune the unused antennas. Naturally, you can also use the antennas to guy the tower.

Last but not least, how about a tower on top of the house with antennas to each corner of the house, for a NO SPACE antenna array?

...W8HXR

Dentron introduces **MORE SKY OPENERS**

**NEW
4 V**



4 BAND 27' VERTICAL

Covers entire 10, 15, 20 & 40 meter band
Full 1/4 wave antenna on 20 meters
Self Supporting Heavy Seamless Aluminum
Weatherproof, wind survival, 80 mph
2 kW Power Capability
Factory Tuned & Sealed HQ Trap
Suitable For Ground, Roof or Tower Mounting
Radials are included

Dentron 4 V Four Bander \$84.50 ppd USA


**NEW
160M**

160 METER MOBILE ANTENNA

Now operate Top Band in your car, boat, plane or RV
10 kc Bandwidth without adjustment
Covers entire 160 meter band with adjustment
Slim, lightweight, factory-sealed, loading coil, 500 watt capability, 10 1/2 ft. Total Length, Standard Ball Mount Thread (3/8" - 24)

Mobile Top Bander 160 M \$59.50 ppd USA

NEW

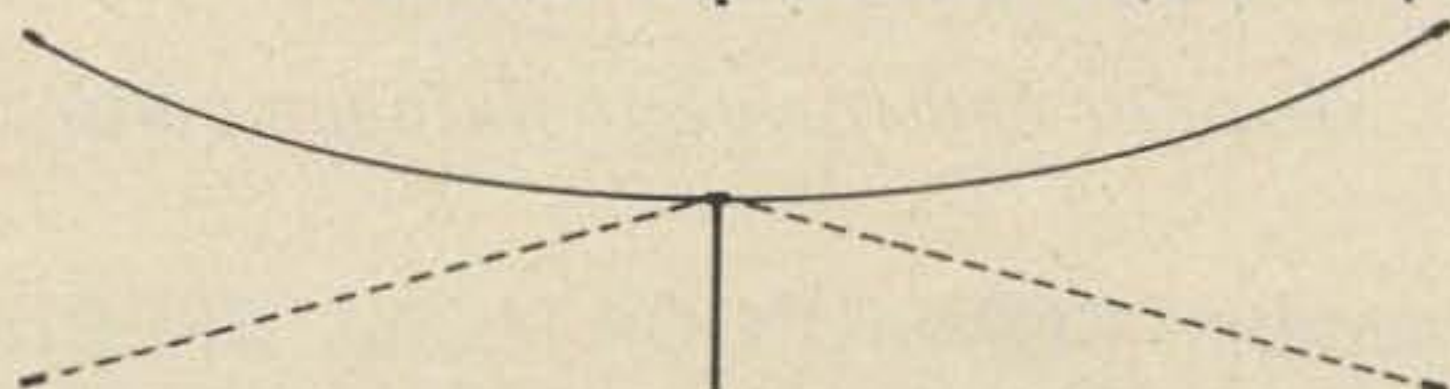

ALL BAND DOUBLET or Inverted Type 160-10 meters

- Center Fed Tuned Doublet • 130' Total Length — may be cut shorter if desired
- 100' 450 ohm open balanced Transmission Line
- 14 ga. stranded copper antenna wire
- Comes Assembled, just add rope to ends & pull up in the air and tune with the Dentron Super Tuner

Dentron All Band Doublet \$24.50 ppd USA

COMING ATTRACTIONS FROM DENTRON

- 160 meter solid state receiving converter
- "Dual-meter" in line wattmeter
- Audio Rectification Filters for RFI problems in HiFi, tape recorders, organs, intercoms, etc.

Write for full details



Dentron

RADIO CO., INC.
2100 Enterprise Avenue
Twinsburg, Ohio 44087
Phone: 216-425-8073

SATAN ELECTRONICS announces

a new dealer for **BRIMSTONE 144**

Communications Specialties

97 AMSTERDAM AVE., WARWICK RI 02889
401-738-3287



Write or call for your six page color brochure

Remember COMMUNICATIONS SPECIALTIES for two meter gear, HF transceivers automatic, electric touch-calling equipment.

Enclosure \$10.00


Pads \$26.00.

Also Ten Tec Keyers — regulated supplies
top antennas — HyGain — Mosely.

Free shipping

Call Chuck, K1HGB anytime

401-738-1887

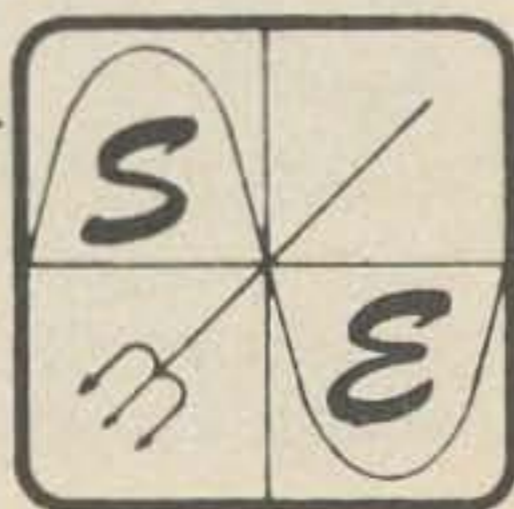

SATAN ELECTRONICS, INC.

R.R. 3 Box 38A
Salina, Kansas 67401

The Oscar Zapper

Conclusion

In beginning this project I felt that the helices would work very well and would yield a 12 to 15 dBi circular gain. I also thought that it was necessary to measure the gain as well as the antenna radiation pattern, so that the performance of the helices could be verified. Since I was a graduate student in physics at Georgia Tech, the antenna pattern was measured using the facilities that are available at the Georgia Tech Engineering Experiment Station and the Antenna Lab of the School of Electrical Engineering. I hoped to be able to perform the antenna measurements and actually see if the pattern (i.e. the beamwidth) and the gain of the antenna were comparable to the theoretical pattern and gain. Cliff Burdette WA8GRE, Research Scientist at the Georgia Tech Engineering Experiment Station, and I made the pattern measurements in April and May of 1974 (before the array was completed).


The 70 centimeter helix was measured on the outdoor antenna range located on the roof of the Electrical Engineering Building at Georgia Tech. Instrumentation consisted of a Scientific-Atlanta amplitude receiver, a series 1520 pattern recorder, a UHF oscil-

lator, and an antenna positioner control and turntable. A block diagram of the measurements setup is shown in Fig. 5. Using this configuration, patterns of the principal planes of the antenna were measured for both linearly and circularly polarized transmitting antennas. The antenna range is, however, not free from reflections. Nearby objects such as building corners and a crane prevented us from obtaining "free space" conditions. However, the far-field pattern can be measured since the far-field distance for the two antennas was only ten feet, as given by:

$$\text{Far-field Distance} = \frac{2(D_1 + D_2)^2}{\lambda}$$

where D_1 and D_2 are the largest aperture dimensions of the transmitting and test antennas, respectively. At this distance, the reflections should be approximately 40 dB below the maximum signal of the test antenna.

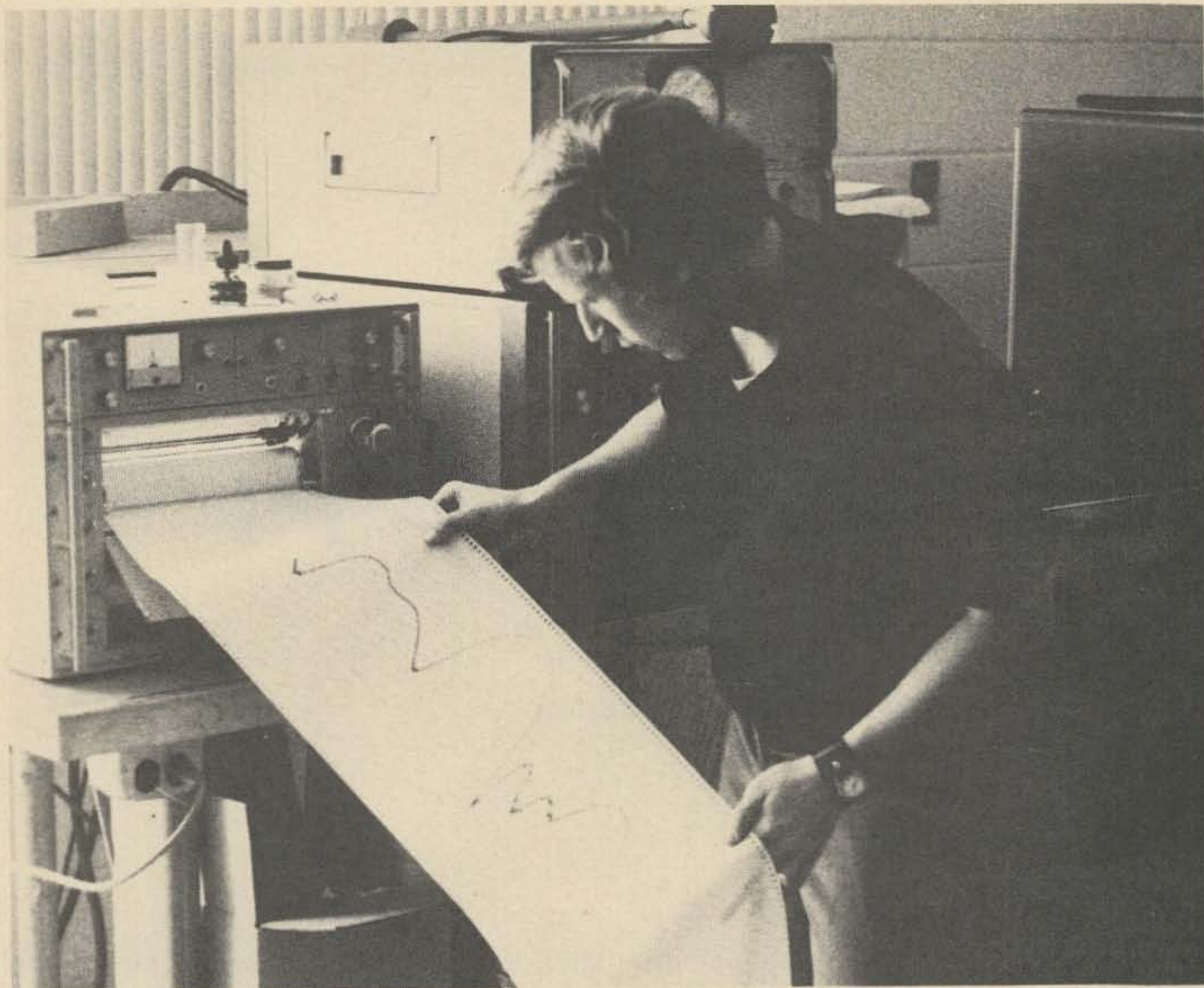The measurement of an antenna pattern (i.e. the far-field pattern) involves the test antenna, whose pattern is being measured, and another antenna located at a certain



Cliff Burdette WA8GRE observes one of the antenna patterns as it is generated by the recorder. Equipment used in the pattern measurements is located in the background.

distance away, that is, in the far-field region. The test helix is used as a receiving antenna and at the same time rotated about a vertical axis through the desired angles in measuring the pattern. The test antenna was operated in the axial mode with right circular polarization. Two different transmitting antennas were employed — a half-wave dipole and a 3 turn helix of the same polarization of the test antenna. Pattern cuts were taken using both transmitting antennas. The measured beamwidth of the test helix is approximately 39 degrees (and corresponds to the theoretical value). This represents an adequately directive antenna for amateur satellite communications. The pattern nulls are quite good and nearly symmetric. The patterns, shown in Figs. 7 and 8, do show a slight asymmetry or distortion. This might be due to the location of the feedpoint of the test antenna. The helix was fed approximately 2 inches to the left of the axial

center. This effectively produces a “tilt” in the pattern of the antenna. The level of the first lobe is approximately 16 dB below the level of the main beam of the antenna. However, this tilt is more likely to be a result of the antenna range itself as the reflections from the building and the crane and other factors can very easily cause such a tilt. The level of the first lobe cannot be pinned down because the pattern is slightly nonsymmetric. One lobe is 9 dB down, while the other is 16 dB down, as shown on the 40 dB plot of the pattern (Fig. 7). A minimum level of about 10 dB below the level of the main beam is desirable.

The gain measurements were made by direct comparison with a dipole, and the resulting gain was approximately 16 dB over a half-wave dipole. Since the gain measurements were made at 445 MHz, the gain at 432 MHz (the design frequency) would be less; nevertheless, the pattern results that

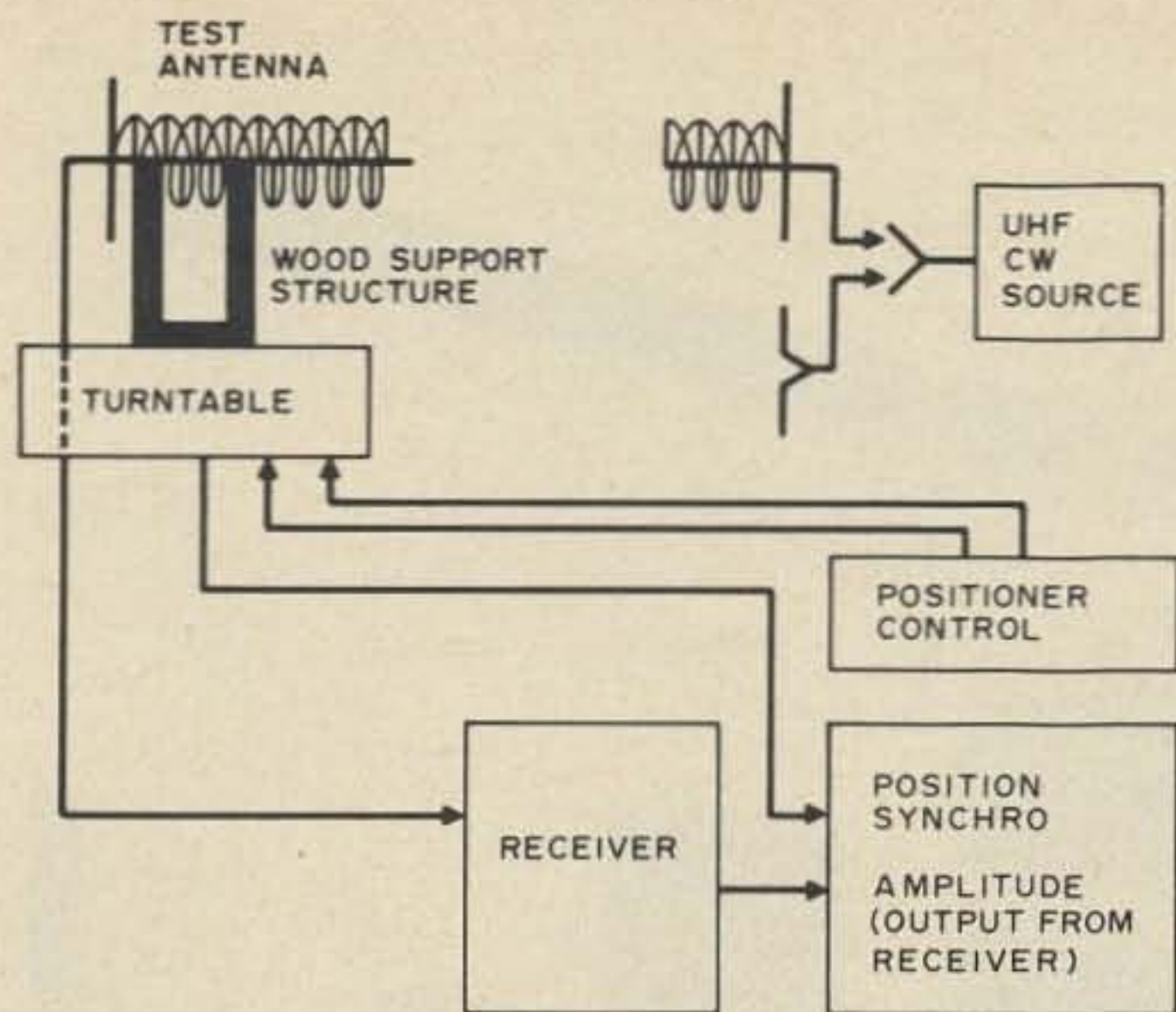


Fig. 5. Block diagram of antenna pattern measurements setup.

were obtained indicate that these antennas should be performing very well.

My results almost exactly correlate with Dr. Kraus's original graphs, i.e., the measured beamwidth and the theoretical beamwidth are practically the same. Since the center or design frequency is 432 MHz and since the gain depends on the circumference C , the number of turns n , and the spacing S , it can be easily seen that, as one goes to a higher frequency or frequencies above the design frequency, the gain will correspondingly increase [from $\text{Gain} = 11.8 + 10 \text{ Log}_{10}(C^2 n S)$]. Likewise, at frequencies below the center frequency the gain will decrease. Here the measured gain at 445 MHz corresponds to the correct increase, so at 432 MHz the gain should be about 14.7 dBi circular.

Another very important measurement is the axial ratio or ellipticity, especially where circularly polarized antennas such as helices are concerned. Here the axial ratio is the ratio of the major axis to the minor axis of the polarization ellipse. For the axial mode

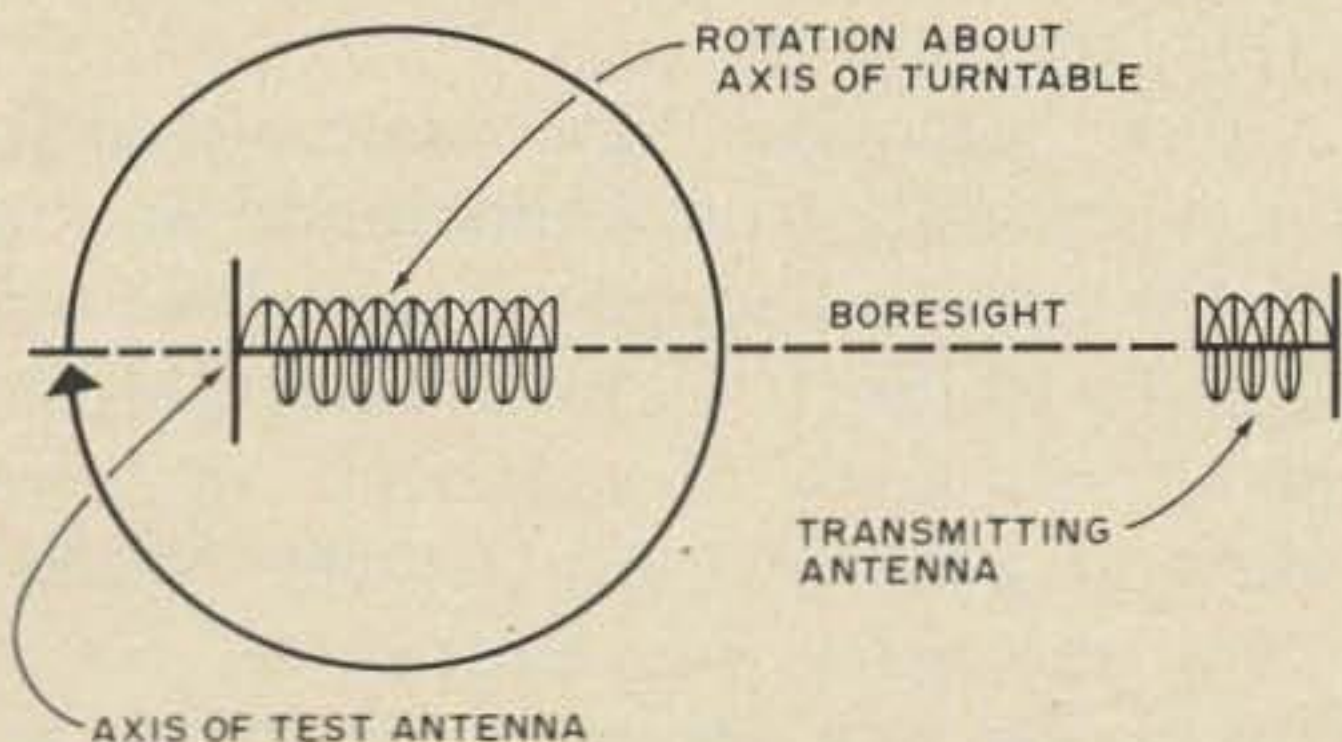


Fig. 6(a). Pattern measurement using test antenna for reception.

helix the axial ratio is described approximately by $AR = 2n + 1/2n$, where n is the number of turns. For n greater than 3, the axial ratio will be nearly unity.

I tried two different ways of determining the polarization. The pattern method utilizes a linearly polarized directional antenna and also a circularly or elliptically polarized test antenna. A polarization pattern is traced out in this method. Basically, a circle is generated for circular polarization.

The other method is the circular component method. In this case, it is necessary to use two circularly polarized antennas of opposite sense. One must compare the relative signals of the two helices, E_{lcp} and E_{rcp} , to find the axial ratio:

$$AR = \frac{E_{rcp} + E_{lcp}}{E_{rcp} - E_{lcp}}$$

If the axial ratio is positive, then the wave is right circularly polarized. For these helices, AR will be very nearly unity. In my radiation pattern measurements I used two three turn helices of opposite sense plus the eight turn test helix for 432 MHz. Suffice it to say that the 8 turn helix was right circularly polarized (AR approximately 1.07, as compared to 1.0555 theoretical).

Conclusion

A lot can be said about helices and their good characteristics, and how they can be successfully used on the amateur bands. I


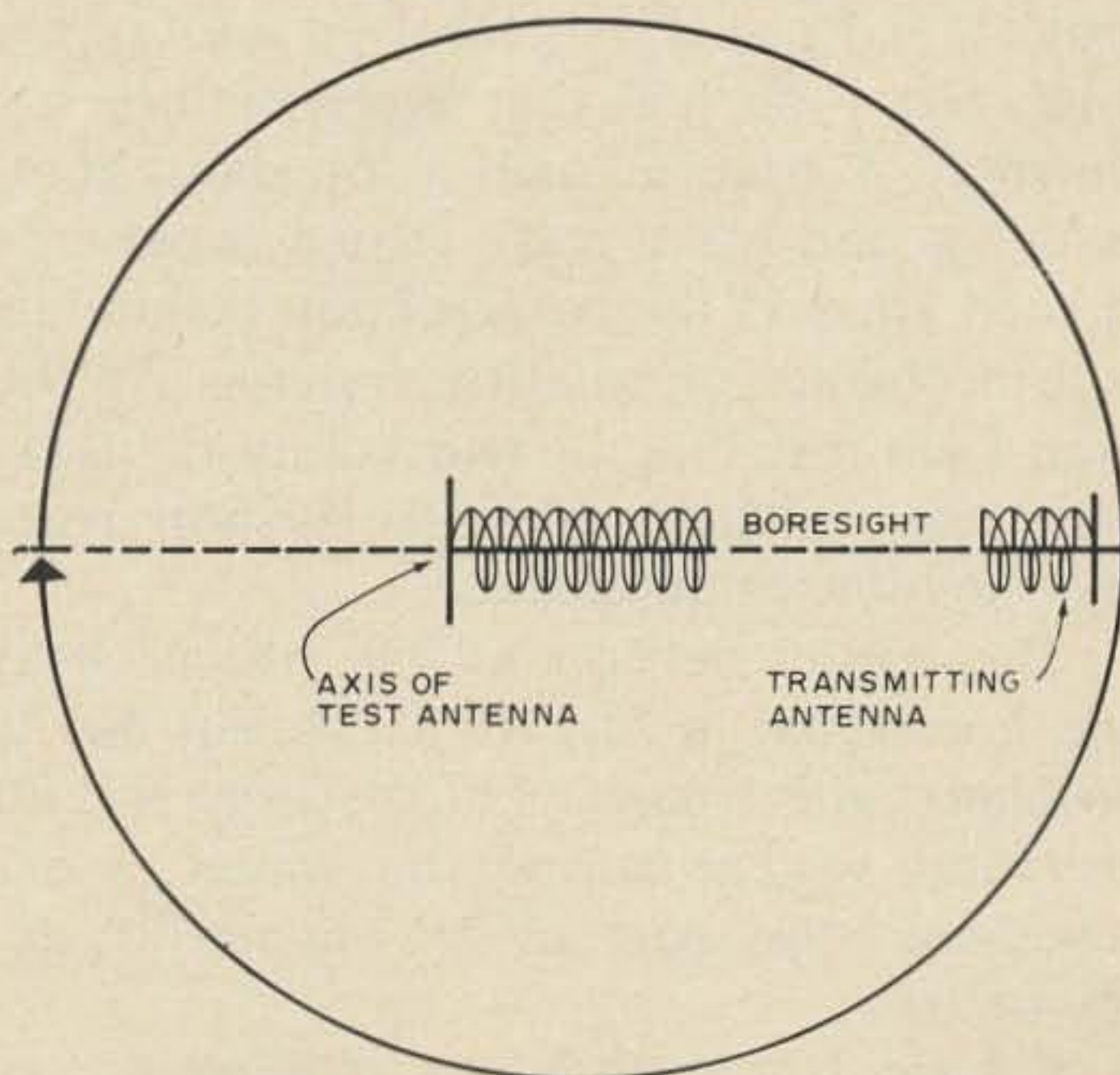


Fig. 6(b). Pattern measurement using test antenna for transmission.

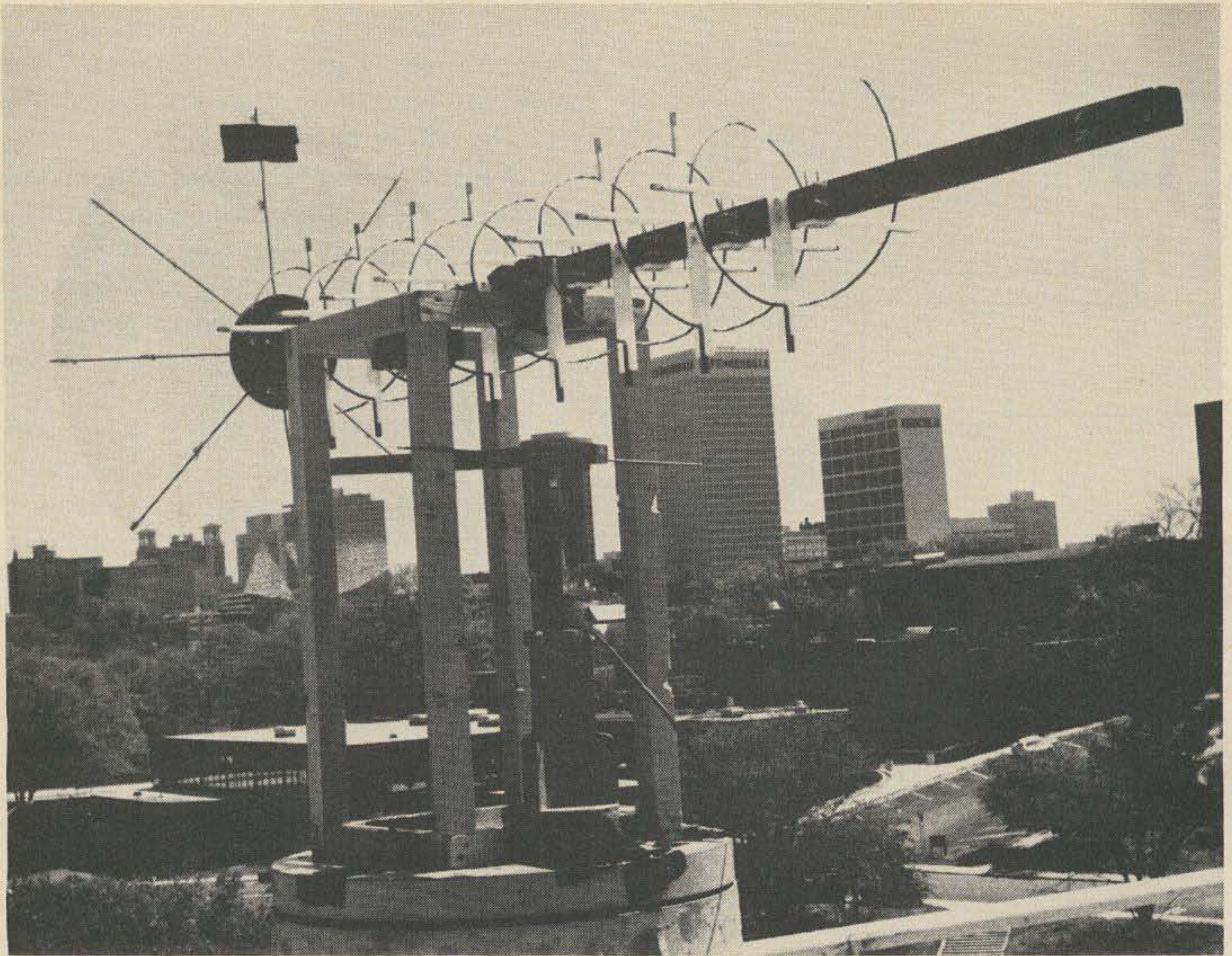

The test antenna used during antenna pattern and gain measurements was the 8 turn 70 cm helix shown here. The helix was mounted on a wooden structure and placed on top of the turntable. The half-wave dipole used during gain measurements is located toward the front of the helix in the center of the picture.

feel that these antennas deserve more attention than they have gotten, even though I do not expect everyone to rush out and build an array like the one that I have. The project, as I call it, has involved a lot of my time, but I do feel that every minute was worth it. I have learned a lot about these antennas and have really gained experience in such areas as the construction techniques and mechanics of rotating systems. At this time I am installing or reinstalling the array with the updated azimuth-elevation rotor and the remounted helices.

The earlier version of the helical array was completed in August, 1974, but due to problems with balancing of the array and the elevation system during the winter, I had redesigned this part of it — hopefully, for the better.

I have found that, by making use of surplus materials in putting the array back together, I could come up with both a small

investment and a mechanically sound antenna array. Also, in remounting the helices I decided that a counterbalance system should be installed, since I had found it very hard to balance the first array. Improper balance alone would cause rotor problems. By eliminating, in this updated version, the major stresses encountered with the elevation drive, the mechanical problems are solved, which means I can use the antennas more without having to keep working on the array.

Other “gleanings” have come out of the project, basically from building and working with the helices. I somehow found the time to build a 10 turn helix for 2 meters, which I entered in a home brew antenna measuring contest at a hamfest last October. Needless to say, this array was quite large, but its performance was what I expected and brought a first place in the “most gain” category of the contest. From this helix,

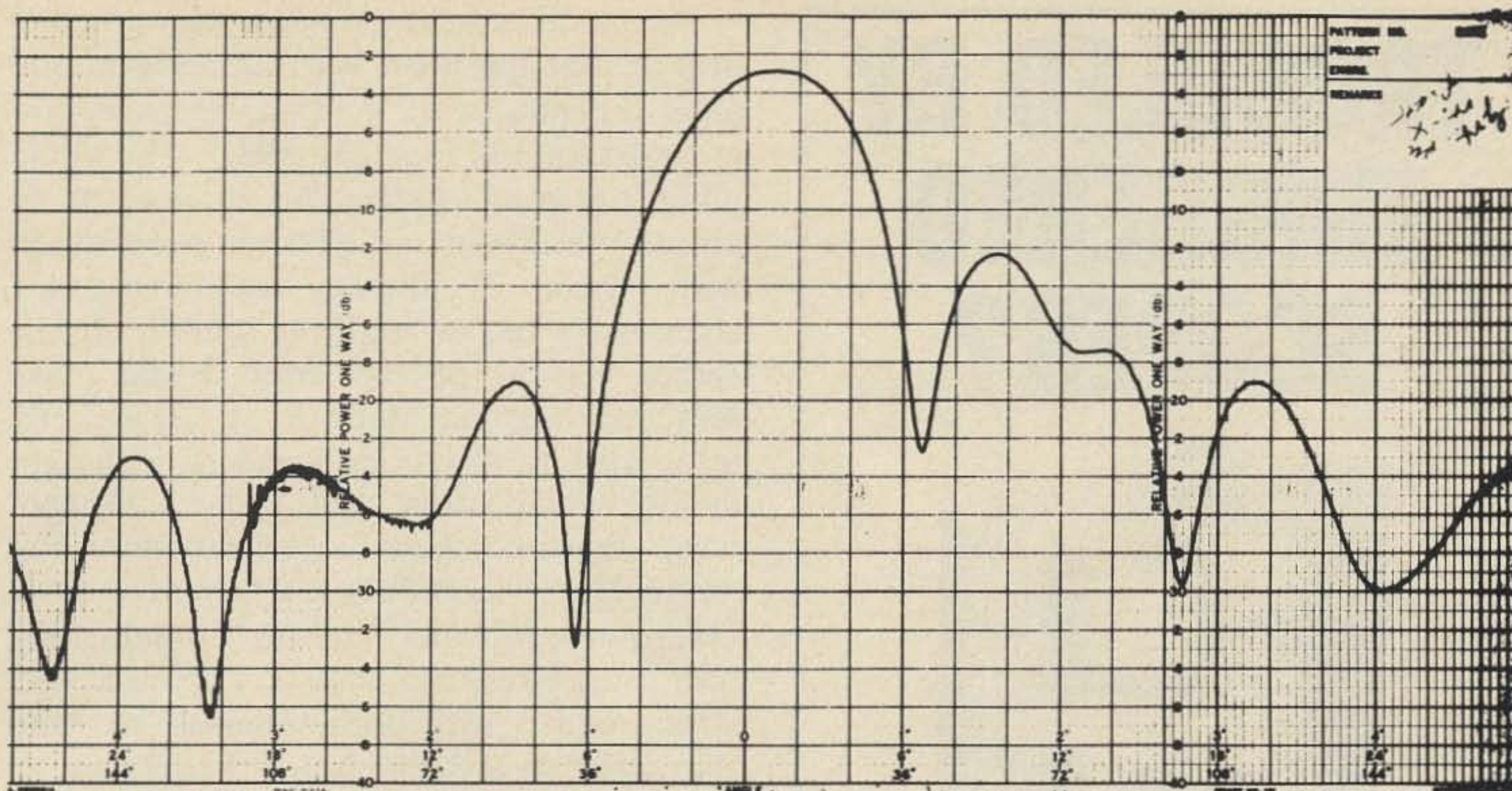


Fig. 7. Radiation pattern for 8 turn helix taken on a 40 dB rectangular recorder.

which was basically designed to be built and taken apart in less than an hour, I have found that a ground plane made of an aluminum plate with 8 radials will suffice. Here my original installation was too heavy and the ground plane for the 2 meter helix

was the major factor. So in redoing the array I have tried to reduce the weight where possible without sacrificing any of the performance of the antenna.

Another factor in putting together these antennas was utilizing materials available at the lowest possible cost. The plexiglass supports, which can be used up to 1000 MHz, were spaced at 90 degree intervals along the turns of the helix, even though other spacing could have been used. Also, 120 degree spacing on a triangular crossed sectioned boom could be used, depending upon the band of operation and the type of wire used for the conductor of the helix.

Fiberglass or aluminum can be used for the boom. Aluminum does not degrade the wide band characteristics of the helix when it is used primarily as a narrow band antenna, although the helix conductor must be insulated from the aluminum boom.

Since the helix is pretty broadbanded, i.e., a design at 160 MHz will operate well at 137 MHz and 220 MHz, so construction techniques depend on its basic use or application (Ref. 1, 2 — see 73 #178, page 64). For instance, a high performance array of helices could be built for working moon-bounce, possibly using 4 helices of about 20 turns to obtain about 24 dBi circular gain. (Or possibly more than four antennas could be stacked to get more gain, such as is done by W8JK's 96 helix array at Ohio State.)

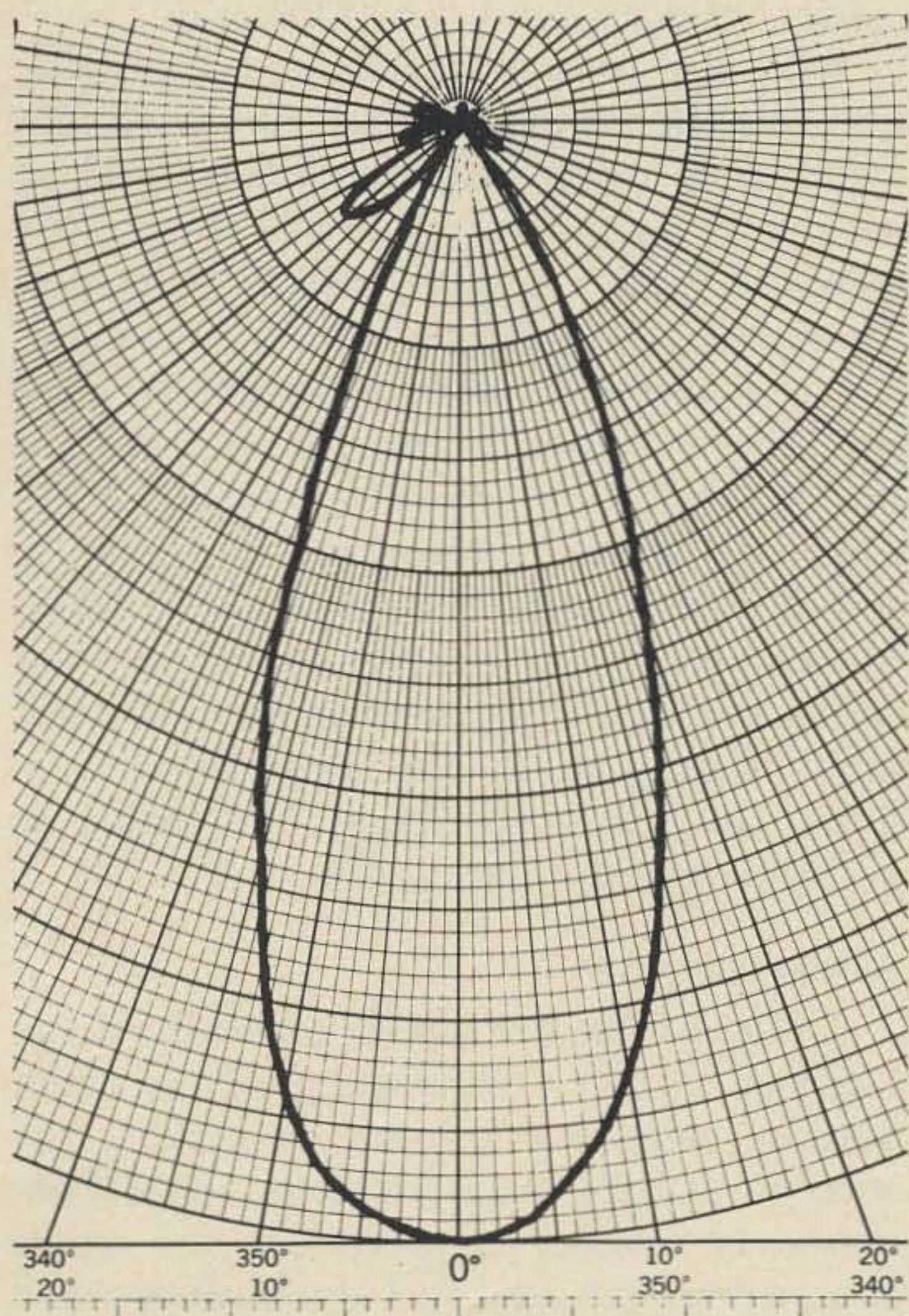


Fig. 8. Polar plot of radiation pattern of 8 turn helix.

TROUBLED BY TRIGGERED SCOPES?



The Hickok Model 512 Dual Trace Oscilloscope eliminates the set-up and precision problems you've had to accept using other triggered scopes.

It's easy to set up

- Simplified color-coded front panel controls.
- Beam finder quickly locates off-scale traces.
- Foolproof triggering to 15 MHz. It gives you superior performance
- 10 MHz response flat within 3dB. Excellent pulse response.
- 3% accuracy on vertical and horizontal ranger.

Hickok industrial lab quality and construction

Glass epoxy PC boards used throughout. Regulated power supply.

At your distributor **\$675⁰⁰**
complete with probes and accessories

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

As far as satellite work is concerned, I believe that the helix will out-perform any other antenna (with the possible exception of a parabolic dish at 432 MHz). The whole point in putting together this array was to be able to use antennas of different polarization with Oscar 7, thereby optimizing the chances for success with the satellite. In the earlier version of the array I did make receiving tests on Mode B of Oscar 7. By using the 6 turn helix on 2 meters, with right circular polarization, and also a 4 element yagi, I have compared signal fading on this mode. Here I used both a 2 meter converter (Microwave Modules) and my Gonset GSB-2 SSB transceiver on 2 meters. I received very strong signals with both antennas, but with the yagi I do get fading every 5 to 7 minutes or so. With the helix and the yagi both tilted at 30 degrees and only rotated in azimuth, I have found that the fading problem inherent in the yagi is not found with the helix. I did not really take any qualitative measurements or data on this, but when I do get this updated version I do plan to make some serious polarization measurements of both modes of Oscar 7 and also of Oscar 6.


With the rotor problems and re-installation of the array, I have not used the antennas as much as I should have. Making use of the tracking capability of the array, I plan to make some more polarization measurements, switching from right circular, left circular, and linear polarizations. Here also, the array will be diverse, as I can use the rcp helix for Mode B, the lcp helix for Mode A on 2 meters, and the lcp helix at 432 MHz for the beacon at 435, 1 MHz. By choosing the number of turns that correspond with just enough gain to work Oscar, and with the appropriate polarizations, this array will truly be capable of performing well in all respects.

Acknowledgments

I wish to thank WA8GRE, Cliff Burdette, Georgia Tech Engineering Experiment Station, who assisted me in making the antenna pattern measurements and collaborated in writing the section of the article concerning that subject. I also wish to thank WB4KUX for his help and suggestions.

... WB4VXP

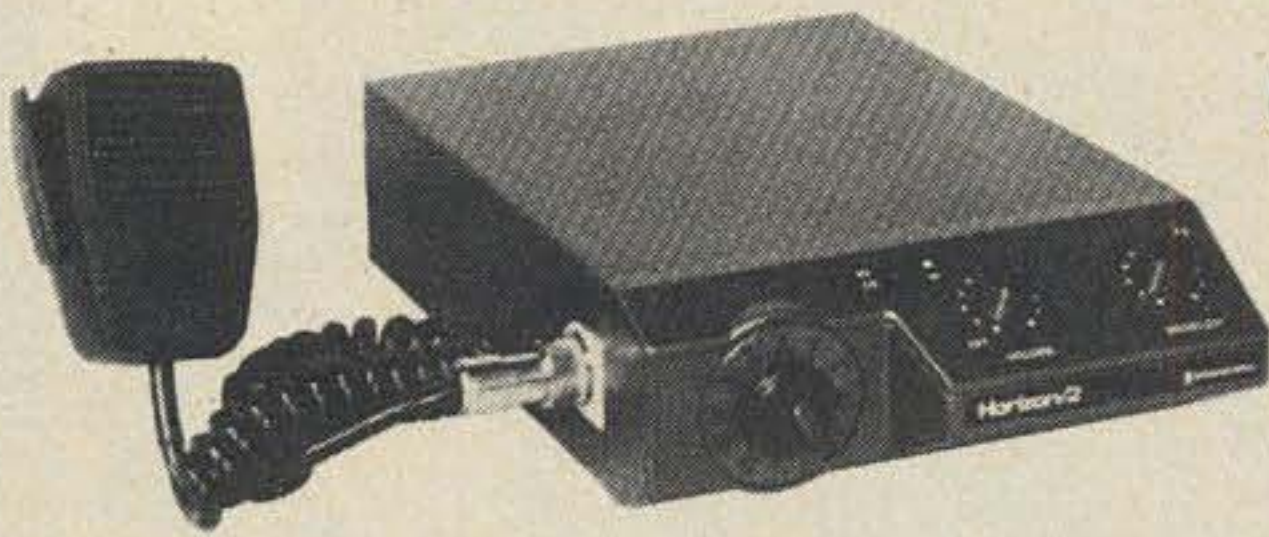**Get on the air NOW!
Let Tufts put you
there!**



by



**Standard
Communications**



**Horizon 2
25 Watts, 12 Channels**

**Walkie Talkie
146 A**

NEW ENGLAND'S FRIENDLIEST HAM DEALER

TUFTS Radio Electronics
386 Main St., Medford MA 02155
Phone: 714-222-8381

Penny Pincher 146A all XTALS (Specify three frequencies)\$298.00

34/94	94/94			
-------	-------	--	--	--

SCOTCH TREAT SPECIAL as above includes rubber ducky antenna.

Nicads with charger\$335.00

--	--	--	--	--

SCOTCH DELUXE as above plus Deluxe carrying case\$349.00

THE WORKS: all channels your choice spare Nicad Battery pak\$400.00

--	--	--	--	--

MOBILE DELIGHT HORIZON 2

6 channels your choice 5/8 wave gain antenna

Trunk lip or roof mount your choice\$295.00

--	--	--	--	--

MOBILE DELIGHT DELUXE as above but all channels your choice\$325.00

Send Check with order — Shipping postpaid
Mass. residents add 3% sales tax.

Name _____

Address _____

City _____ State _____ Zip _____

\$25.00 Free Gift Certificate if orders not shipped in 48 hours!
(excepting some XTALS — we have most all of 'em but. . .)



complete stock
of the following **lines:**

- ITC MULTI-2000
- ATLAS
- VHF ENGINEERING
- STANDARD
- REGENCY
- BOMAR CRYSTALS FOR 2MTR FM
- 73 MAGAZINE PUBLICATIONS
- QST PUBLICATIONS
- EMERGENCY BEACON
- NEWTRONICS
- TEN-TEC

Largest inventory of used equipment in the Boston area.

NEW ENGLAND'S FRIENDLIEST HAM DEALER

TUFTS Radio Electronics
386 Main St., Medford MA 02155

Digital SWR Computer

Conclusion

Once the swr computer is built, you should check its proper operation before connecting it to an swr directional coupler. At this time some minor adjustments may be necessary.

Whether or not adjustment is needed depends on the quality of the 741 operational amplifier ICs. Ideally, if an op amp receives an input of 0 volts (that is, its two inputs are shorted together), its output should also be 0 volts. In practice, however, this does not happen. Instead, in order to obtain a 0 volts output, a slight input voltage (either positive or negative) has to be applied between the two inputs; this is called the input offset. For good quality op amps, this input offset is very small, on the order of millivolts. However, many of the 741 op amps available to the amateur at low prices are of dubious origin — such as factory rejects. One common reason for being rejected is that a unit may have a high offset voltage requirement. Although such an amplifier may still be perfectly usable for ac amplification, the offset voltage introduces a

slight error in dc amplification applications. For this reason, we will check the operation of the 741 op amp ICs in this circuit, and if necessary introduce a slight amount of “offset compensation,” which will compensate for the high offset and produce normal operation.

As an initial check, connect the V_F input to a 1.5 volt dry cell as shown in Fig. 7; this puts about .26 volts dc on the V_F input. Turn both R1 and R2 to minimum, and turn on the ac power to the power transformer. At this time the decimal point on the center LED should light, and the display may or may not be on. If the center decimal point is not on, turn off power and check the power supply.

Now slowly turn R1 toward its maximum setting. As you begin, the display should start to flash on-off-on-off . . . , and the flashing speed should get faster and faster as you continue to turn the pot until eventually it looks as though the display is on continuously (it is still flashing on and off,

but so fast that you cannot see it). If this does not happen, refer to the troubleshooting section later in these instructions, and come back here after you find the problem.

Offset Compensation of IC2 and IC3. Now carefully turn R1 back toward its minimum setting. As you approach the minimum, the display should start to flash on-off . . . at a slower and slower rate, as slow as once every second or two, and should just *stop* flashing as you reach the minimum setting of R1. (As it stops flashing, it will either stay permanently on or stay off.) The important factor is that the flashing should stop just as R1 reaches its minimum setting, or else that the flashing should be *very* slow — not more than once a second or two. If this is so, IC2 and IC3 are OK; skip down to Offset Compensation of IC1, below. If not, simply interchanging the three 741 op amps (assuming that you used IC sockets or Molex pins) may produce good results.

On the other hand, if either the flashing stops *before* R1 reaches its minimum setting, or else the display still flashes fast although R1 is already at minimum, then compensate IC2 and IC3 as follows:

Obtain a 100k potentiometer, and temporarily connect it between pin 4 of IC3 (this is the -9 volt line) and *either* pin 1 of IC3 (if the display still flashes when R1 is at the minimum setting and you want to slow it down), *or* pin 5 of IC3 (if the display stops flashing before you get to the minimum setting of R1).

Adjust the 100k pot so that, with R1 at its minimum setting, the display is just on the verge of flashing at a very slow rate. When this is done, remove the 100k pot, carefully measure its resistance, and substitute an equivalent fixed resistor ($\frac{1}{2}$ to $\frac{1}{4}$ Watt) in its place.

Offset Compensation of IC1. After IC2 and IC3 are compensated, if needed, adjust R1 so that the display flashes fast enough to look as though it is permanently on. Now adjust R3 so that the display reads 01.0; as with any digital device, there may be a slight amount of flicker in the least significant digit, so adjust R3 until this flicker is at a minimum.

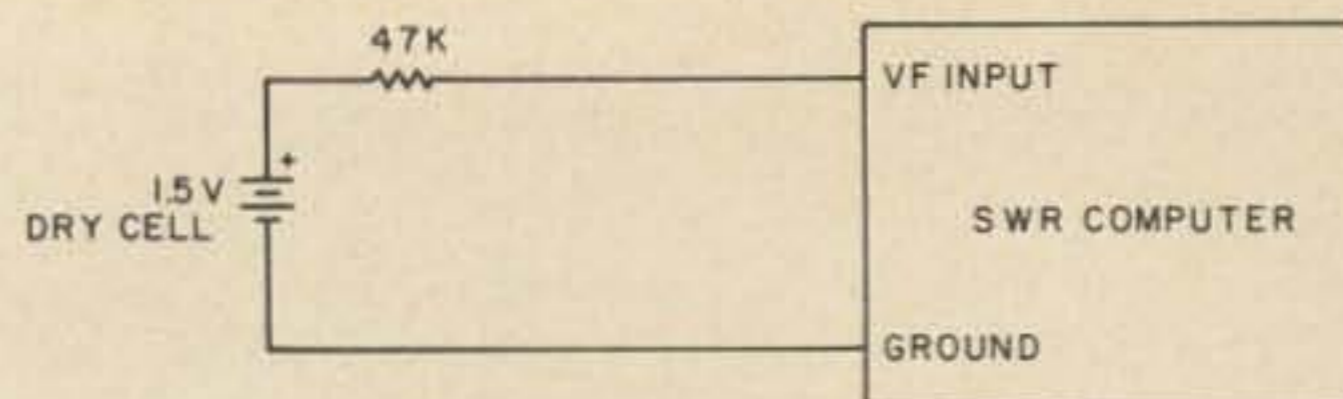


Fig. 7. Input test circuit.

Now turn R1 back toward its minimum setting. The display reading should stay between 00.9 and 01.1, and preferably at 01.0, as the display starts to flash more and more slowly. If it does, IC1 does not need compensation.

If compensation is needed, connect a 100k pot temporarily between pin 4 of IC1 and *either* pin 1 of IC1 (if the reading goes below 1 as R1 is turned lower), *or* pin 5 of IC1 (if the reading goes above 1 as R1 is turned lower).

Adjust the 100k pot so that the reading stays at 01.0 ± 0.1 as R1 is turned through its range. When finished, replace the pot by a fixed resistor of the same value. The offset compensation should be good for the life of your instrument.

Connection To Directional Coupler

A certain amount of discretion is needed in choosing an appropriate directional coupler (swr bridge) to use as the rf sensor. Though a coupler can easily be constructed using any of the variety of circuits given in ARRL publications and the ham magazines, the simplest and fastest solution is to connect into a commercially made swr bridge. The following description takes the latter approach, and describes the connection into a simple "Swr and Field Strength Meter" available from Lafayette Radio as their model 99-25371. To aid you in identifying this model, which is also available from other sources, a simple drawing is shown in Fig. 8. However, almost any swr bridge can be used as the sensing unit.

The internal circuit of the swr bridge is shown in Fig. 8.

In the particular sample of this swr bridge which we examined, forward voltage outputs for typical amateur powers were between about 0.2 and almost 10 volts, well within the range of the digital swr computer. (Incidentally, though this particular unit is

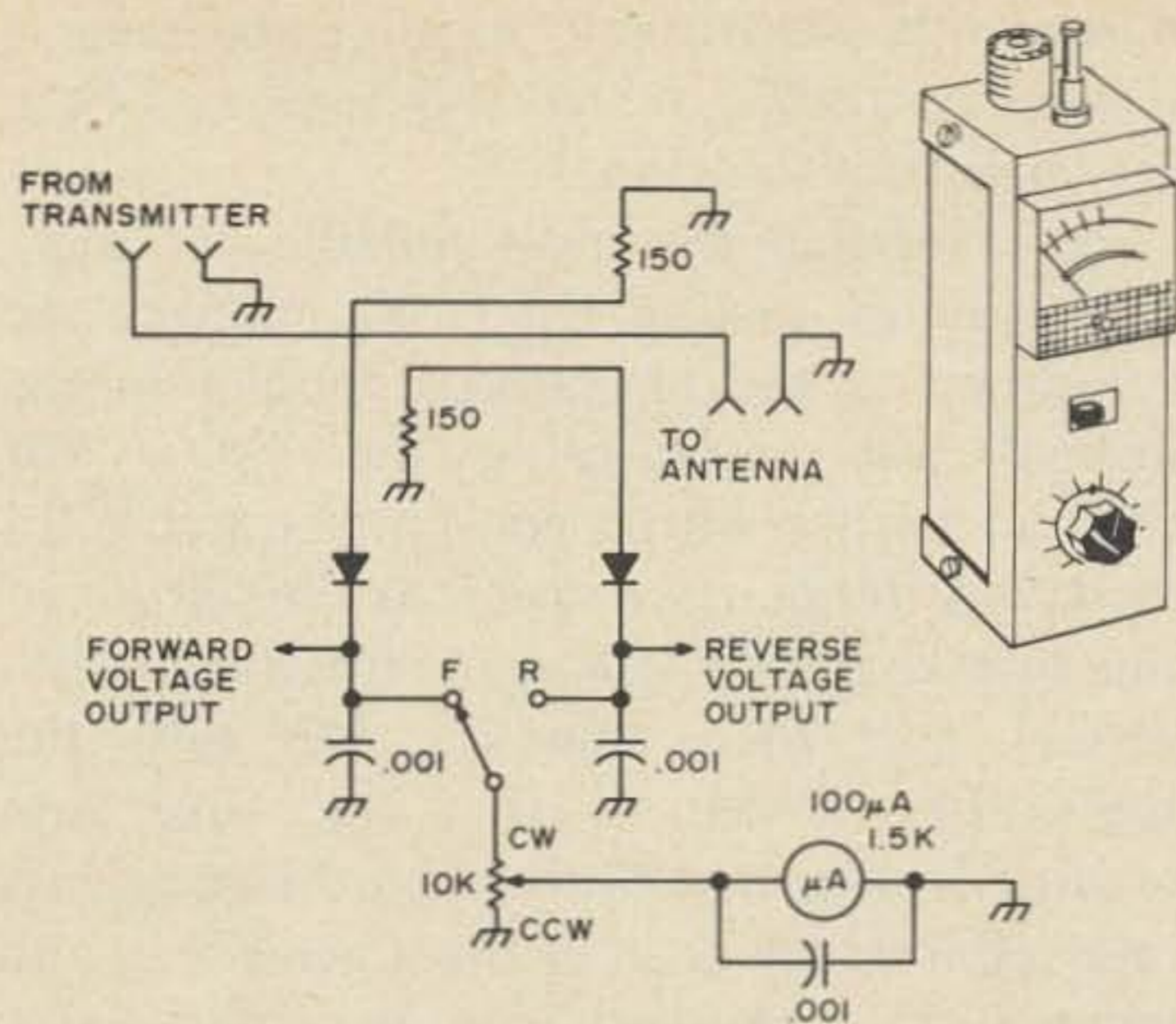


Fig. 8. Typical commercial swr bridge.

rated for use up to 30 MHz, we have in the past found it reasonably accurate even for use at 147 MHz, where a transmitter power of 10 Watts produced a forward voltage of about 4 volts.) In general, the higher the transmitter power or the higher the operating frequency, the higher the output voltage.

The connection to the swr computer consists simply of bringing out the forward and reverse voltage outputs as shown in Fig. 8.

Since the input resistance of the two swr computer inputs is approximately 10k, connection of the computer to the standard bridge does not upset the circuit operation; the swr bridge can still be used in its normal mode. This is of some use in checking the calibration of the computer.

On the other hand, the fact that the swr meter is connected to only one bridge output at a time can cause erroneous readings from the computer. For foolproof operation, the 10k pot in the bridge should ideally be disconnected from the switch. Actually, this is not necessary, as the computer can be calibrated to compensate for the 10k pot's existence, as long as the pot is in the fully counterclockwise position (to take the meter resistance out of the picture) and care is taken to leave the Forward-Reflected switch in the same position at all times.

If a different bridge or directional coupler is used, make sure that the two diodes are oriented as shown so that the bridge output voltage is positive, not negative.

Calibration

The voltage-to-frequency converters are quite linear over a range of more than 40 dB, that is, over a voltage range of 100 to 1, or a power range of 10,000 to 1. Hence adjustment of input levels is not too critical, with the only requirement being that the input level controls be adjusted so that, with the typical range of transmitter powers to be used, the circuitry operates within the linear range of operation.

At the upper limit of the usable range, operation of the circuit is quite linear up to the point where the voltage-to-frequency converter suddenly stops operating. This condition is quite obvious to the user. At the lower end of the range the accuracy drops before the voltage-to-frequency converter fails to function completely; however, a built-in safety device exists in that the display starts to flicker on and off at a noticeable rate when in the doubtful range, as a visual warning.

Calibration is done as follows:

1) *Adjustment of R1.* Connect a voltmeter across the 10k resistor labeled R4 (positive lead to ground). Connect the V_F input of the computer to your bridge, but temporarily leave the V_R input grounded. Now key your transmitter at your normal power and adjust R1 so that the voltmeter indicates about 1 volt. Then disconnect the meter.

Explanation: The voltmeter is measuring the applied voltage going to the voltage-to-frequency converter handling the $V_F + V_R$ signal; the range of fairly linear operation is from about 0.02 to about 2.5 volts. Our object here is to adjust the forward voltage input level to operate the converter in the linear portion of its range. With the normal V_F applying slightly less than one half of the full-range input allowed, we have enough headroom so that even with a very high swr (so that V_R is about the same as V_F , and their sum is twice as large as V_F) we are still in the linear range of operation. If you want to keep the calibration such that the swr computer will operate accurately, even though you vary your output power over a large range, the above information should prove sufficient for you to make your own

adjustment. Keep also in mind that the swr coupler is more sensitive at higher frequencies, and thus a 10 Watt 2 meter signal may provide a higher voltage output than a 500 Watt 80 meter signal.

2) *Adjustment of R3.* Still keeping the V_R input grounded, adjust R3 so that the LED readout reads 01.0 with the transmitter keyed.

Explanation: With V_R equal to zero, the swr is 1. This adjustment matches the two voltage-to-frequency converters so that, with the same input, they provide the same output frequency, which is indicated as an swr of 1 on the display.

3) *Adjustment of R2.* This can be done in several ways, depending on the accuracy desired. The more accurate methods are more tedious, so we will give several ways, starting with the least accurate.

(a) Connect both the V_F and the V_R inputs to the forward voltage output of your directional coupler or swr bridge. Starting with R2 at the grounded end, key the transmitter and slowly adjust R2 while observing the displayed swr get larger and larger. Eventually the display will start to flicker at a slower rate, and at some point will blank out altogether. Adjust R2 just at the point where the display disappears.

Explanation: With the forward and reverse voltages the same, the theoretical swr is infinite since the difference $V_F - V_R$ is zero. This adjustment sets R2 to the point where the difference voltage-to-frequency converter just stops working because it's getting zero input. This method of alignment does a good job at aligning the computer, but it ignores possible differences in coupler (bridge) sensitivity in the two directions. This might be a problem if the swr bridge's meter and 10k pot are left connected, as this loads down one output more than the other. This can be overcome by loading down the other side with an equivalent resistance (in this case 10k).

(b) An alternative method of setting R2 is to use another swr bridge to measure the swr in the line, and then adjust R2 so that the digital swr computer indicates the same value.

Explanation: No explanation for this is needed, but note that a high swr is needed

during this adjustment so that the reverse voltage is sizable; hence this may not be a very practical solution.

(c) Probably the most reliable yet practical way of setting R2 is to connect the computer to the directional coupler in the normal way, monitoring the $V_F + V_R$ channel (either with a good meter across R4 or with a frequency counter at the output of the sum channel's voltage-to-frequency converter) and then adjusting R2 with the transmitter keyed so that the same sum reading is obtained both when the coupler is inserted into the coax in the normal way and when it is connected into the coax backward.

Explanation: If the directional coupler is connected into the coax backward, the forward and reflected powers should be the same; hence the two output voltages out of the coupler should be the same except for the fact that they appear on the opposite lead. But their sum should be the same. If one of the two channels in the coupler has slightly lower sensitivity than the other, the adjustment of R2 will compensate for this fact. But the overall accuracy you should strive for in this adjustment depends on how well the two 27k resistors connected to IC1 (labeled "1" in Fig. 2) are matched, since they determine how well the sum signal $V_F + V_R$ is obtained.

4) *Overall calibration accuracy.* One popular commercial swr bridge rates its accuracy as ± 5 dB, whatever that means. Even if your swr computer is only matched to within 10%, or even worse, you can still see that this would be a tremendous improvement over the accuracy you can normally obtain with a commercial bridge.

Of much greater importance than the *absolute* accuracy, however, is the *incremental* accuracy. That is, we normally do not care whether the swr on a given line is 2.1 to 1, or 2.3 to 1. No reasonably priced method of measurement is going to guarantee the absolute accuracy of that number. But of prime importance is the change — or increment — in the swr as we make a small adjustment in the antenna or operating frequency. This is where the digital swr computer really outperforms the commercial bridge, since even a change in swr of .1 unit

is easily seen, and changes even of 0.05 unit or less can sometimes be observed, though not actually measured. The gist of this is that you should strive to match the 27k resistors and do the adjustment of R1, R2 and R3 as well as you can, but all is not lost even if you cannot do so because of lack of a good meter or other equipment. Even if the digital swr computer is only aligned to within 10% or worse, it is still a tremendous improvement over the conventional swr bridge.

Troubleshooting

Because the swr computer is built on a printed circuit board, construction is fairly foolproof. Most problems arise due to either bad solder joints or accidental shorts, or defective components.

After mounting all the components, check all your connections for solder bridges between adjacent pins for cold solder joints. Good wiring of printed circuit boards requires good thin solder (60% tin, 40% lead) with a rosin core, a small pencil iron of 25-40 Watt capacity with a very small tip, and great care.

Use the following procedure as a general guide for troubleshooting:

1. With no inputs except power, the decimal point on the center LED should light. If not, check the power supply. Check the +9 and -9 volt supplies, and check that the +5 volt supply is really very close to +5 volts.
2. Connect the VF and VR inputs to +1.5 volts from a dry cell. Starting with R1 and R2 both at the grounded side, pin 6 of IC3 should be near 0 volts, while pin 6 of IC1 and IC2 should be near -0.6 volts.
3. Turn R2; pin 6 of IC3 should go negative, and reach -1.5 volts when fully on. Turn it back to the grounded end.
4. Turn R1; pins 6 of IC1 and IC2 should both go more negative, down to at least -3 volts or more.
5. As you are doing step 4, the two voltage-to-frequency converters should be generating outputs whose frequency goes up as R1 is turned further away from ground. With a frequency counter, if you have one, you can monitor the frequency on either side of the 0.002 μ F capacitors. Most scopes

won't display the very short pulses here, but should show a nice triangular wave on the emitter of the appropriate unijunction transistor. Chances are that at least one of the two circuits will work properly, so you can then use it to tell you what should happen in the other one.

6. The output of IC4, pin 11, should be one-tenth the frequency of the input, pin 14.
7. The output of IC5b, pin 12, should be one-half of the frequency of the input, pin 1.
8. With IC7, IC9 and IC11 unplugged, the LEDs should display the number 888.
9. With IC5 unplugged and a temporary jumper between pins 5 and 9 in its place, and R1 near its ground end, the LEDs should count up, counting the output of the voltage-to-frequency converter.
10. IC5 pin 6 should be near +2.5 volts with barely visible pulses on it; IC6 pin 3 should be near ground, with barely visible positive pulses on it; IC7 pin 4 should be near ground when the LEDs are dark, and should be near +3 volts when the LEDs are lit.

The above operational checks will help you narrow down the cause of any problem, if necessary. Since the unit has four 7490 and three 7448 ICs, as well as three identical LEDs, interchange of these units should help to spot defective ones. A good reason for using IC sockets or Molex pins!

Modification

Exists there a ham who ever builds a project exactly as described? Here are a few possible parts substitutions and modifications which may occur to you.

1) T0-5 style 741 op amps can be used instead of the 8-pin DIP style for which the board is designed. The pin numbers on the T0-5 are the same as for the DIP package. 741 op amps are also available in a 14-pin DIP package, which has different pin numbers and would therefore require some changes. Dual 741 amps are available under the numbers 747 or 5558; however, again they do not fit the board layout and so some changes would be necessary.

2) The PNP and NPN transistor types specified can be easily substituted for. Instead of the 2N706 NPN transistor, you

may use any NPN silicon switching transistor, and others as well. This transistor is not at all critical, and even a 2N5172, which costs only some 15¢ or so (*list*) will do. For the 2N3638 you may substitute any PNP silicon low power transistor, but make sure that it has a good beta and low leakage, as a good quality unit is needed here — I used the 2N3638 only because it is cheap and I had some. But use the same type number in both voltage-to-frequency converters — matching is important here.

3) Other unijunction transistors can be used instead of the 2N4891 specified. I chose this one because it is a standard Radio Shack item and therefore easy to get. But again, make sure to use identical transistors in both circuits.

4) Common-cathode LEDs were used because their price is often slightly lower than common-anode LEDs. However, other LEDs can be substituted. Other common-cathode LEDs may require slightly larger resistors — check their spec sheets. Common-anode LEDs require the 7447 driver rather than the 7448, and a different connection. Other types of readouts, such as Numitron,

fluorescent, or several others, can also be used. Alternatively, a separate printed circuit board, originally designed for the K2OAW counter, may be used if you wish to use MAN-1 type common-anode LEDs (see the K2OAW counter articles in the May, July, September 1972 and November 1974 issues of 73 Magazine for circuitry). Obviously, using common-cathode LEDs is a cheaper and easier solution than trying to adapt the layout to common-anode LEDs.

5) If you already have the K2OAW counter, or are planning to build it, you can use the counter as the digital readout for the swr computer. This will significantly reduce the computer's cost.

If the counter is used, you may omit IC4 in Fig. 2, *all* of Fig. 3, and all except the two diodes and two capacitors used to produce -9 volts in Fig. 4.


The K2OAW counter power supply can provide +9 and +5 volts to the swr computer. Adding the four parts specified above to the counter power supply will produce -9 volts.

The *sum* output from Fig. 2 is fed into the counter input, that is, into the low frequency input, in the same way as an unknown signal.

The *difference* signal from Fig. 2, which would normally go to pin 14 of IC4 for division by 10, now goes to pin 14 of IC29 of the counter instead. A switch will have to be put into the counter to select whether the input to IC29 comes from IC28 or from the swr computer. In operation, this switch would be placed in the swr computer position, and the Hz-kHz switch would be placed in the Hz position.

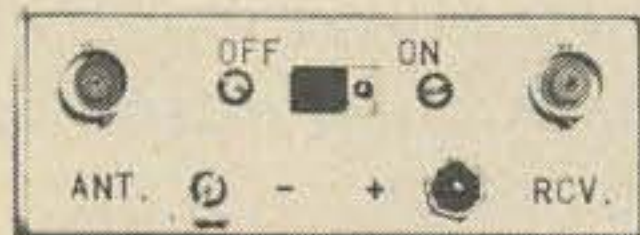6) For some applications, you may not need readouts as high as 99; let's face it, most commercial swr bridges are not calibrated for swr's above 8 or 10. If a maximum swr readout of 9.9 is quite satisfactory for your use, you may remove the most significant LED as well as IC10, IC11 and the seven 390 Ohm resistors associated with this digit, and place a jumper between pins 14 and 11 of the IC10 socket to connect the overrange circuit directly to IC8. This simplification can save you about \$5-6.

VANGUARD NOW HAS A "HOT" 2 METER CONVERTER at a price you can afford



MODEL C-144-A
ONLY \$39.95

Read the specifications and see why it's the best converter value available anywhere.

- Dual-gate MOSFET r.f. stage with diode protected input.
- Dual-gate MOSFET mixer for minimum cross modulation. Every converter tested for noise figure (2.5 — 3.0 dB max.) with Hewlett Packard noise measuring equipment.
- 6 tuned circuits.
- More than 20 dB gain. .1 microvolt sensitivity guarantee when used with receivers having 1 microvolt or better sensitivity.
- Complete with one .005% plug-in crystal to cover 144-146 or 146-148 MHz (be sure to specify which, or get both for only \$5.00 more). Standard output is for 28-30 MHz.
- 16 gauge aluminum case with BNC receptacles and antenna/power switch. Measures 3-1/2" x 2-3/4" x 1-1/4".

IN STOCK NOW FOR IMMEDIATE C.O.D. SHIPMENT. Call Monday through Friday 9 AM to 4 PM (212) 468-2720.

VANGUARD LABS

196-23 Jamaica Ave., Hollis, New York 11423

... K2OAW

Full Break-in at 60 wpm?

With this device you can, with every tap of the key, mute your receiver, key a transmitter, and activate a sidetone oscillator for monitoring your CW, to achieve true, quiet, full break-in CW to 60 wpm, without using a TR switch. The gadget will work well with any station using a separate transmitter and receiver, and separate antennas; it goes together easily in under an hour. The cost? Under \$1.50.

Parts needed for the device are: One cold chisel, about 30 feet of enameled magnet wire, and a \$1.29 package of four magnetic reed switches from the local Radio Shack store. (Catalog number 275-026, or whatever you can find there with ratings sufficient to handle the key circuit on your rig.)

Close-wind the magnet wire in one direction, one layer, the full length of the chisel (or other bar of steel or iron), leaving about six inches of lead wire on each end. Tape the coil ends to keep them from unwinding, then lay the coil on a piece of wood or cardboard and tape it in place.

Open the package of reed switches carefully, being sure not to ruin the plastic "bubble" on the package, as it is one of the components of the device. Cut out the ends of that bubble, place it over the coil, and tape it in place. See the photograph.

The schematic indicates the wiring of the coil, from a source of dc (6-20 V), through the station key. A simple rectifier-filter circuit is shown in the event you cannot tap

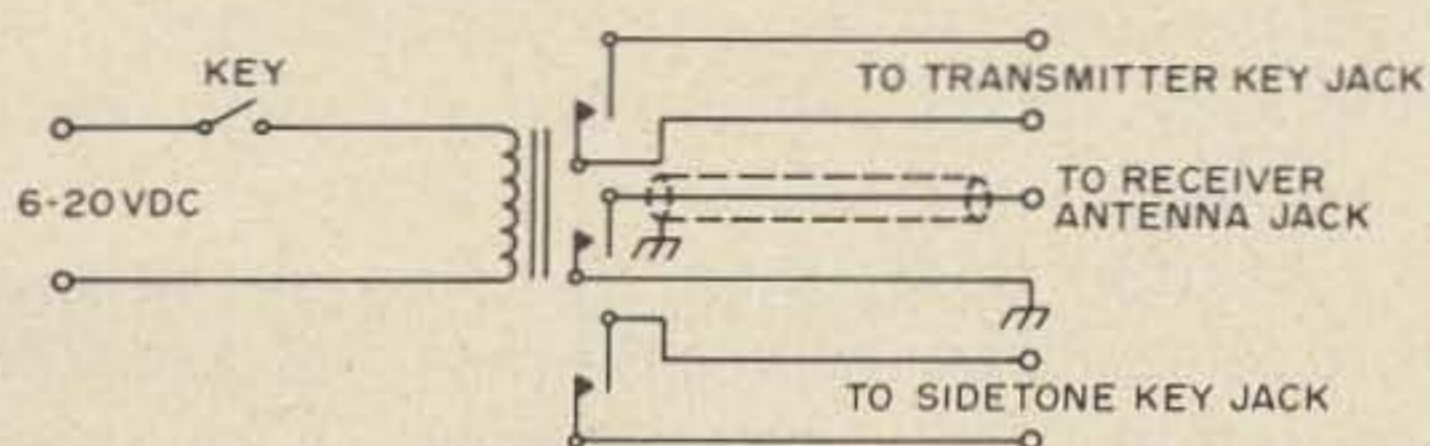


Fig. 1. Schematic.


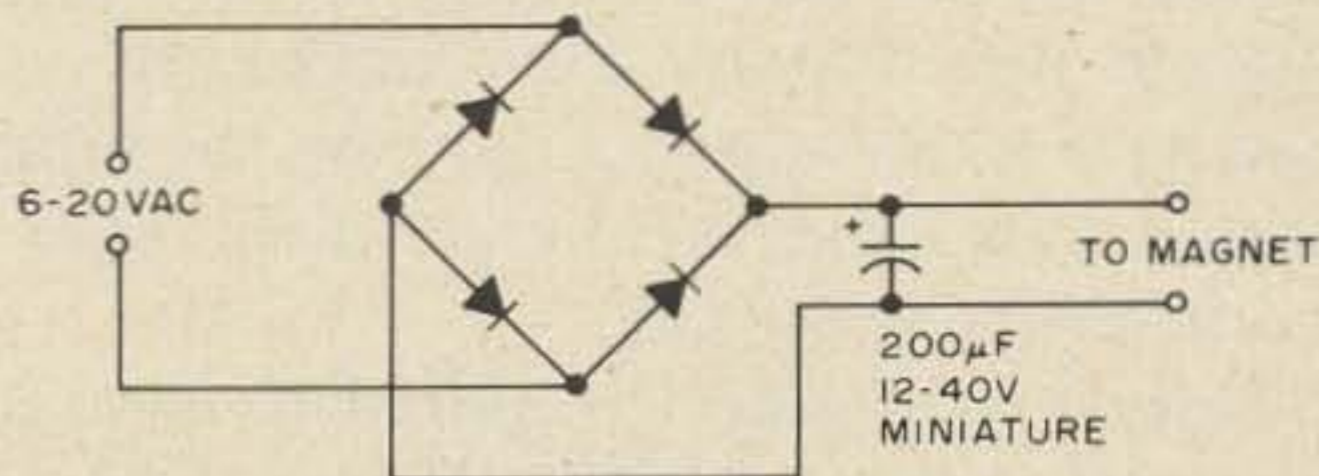


Fig. 2. Rectifier/filter for filament/panel lamp circuit use.

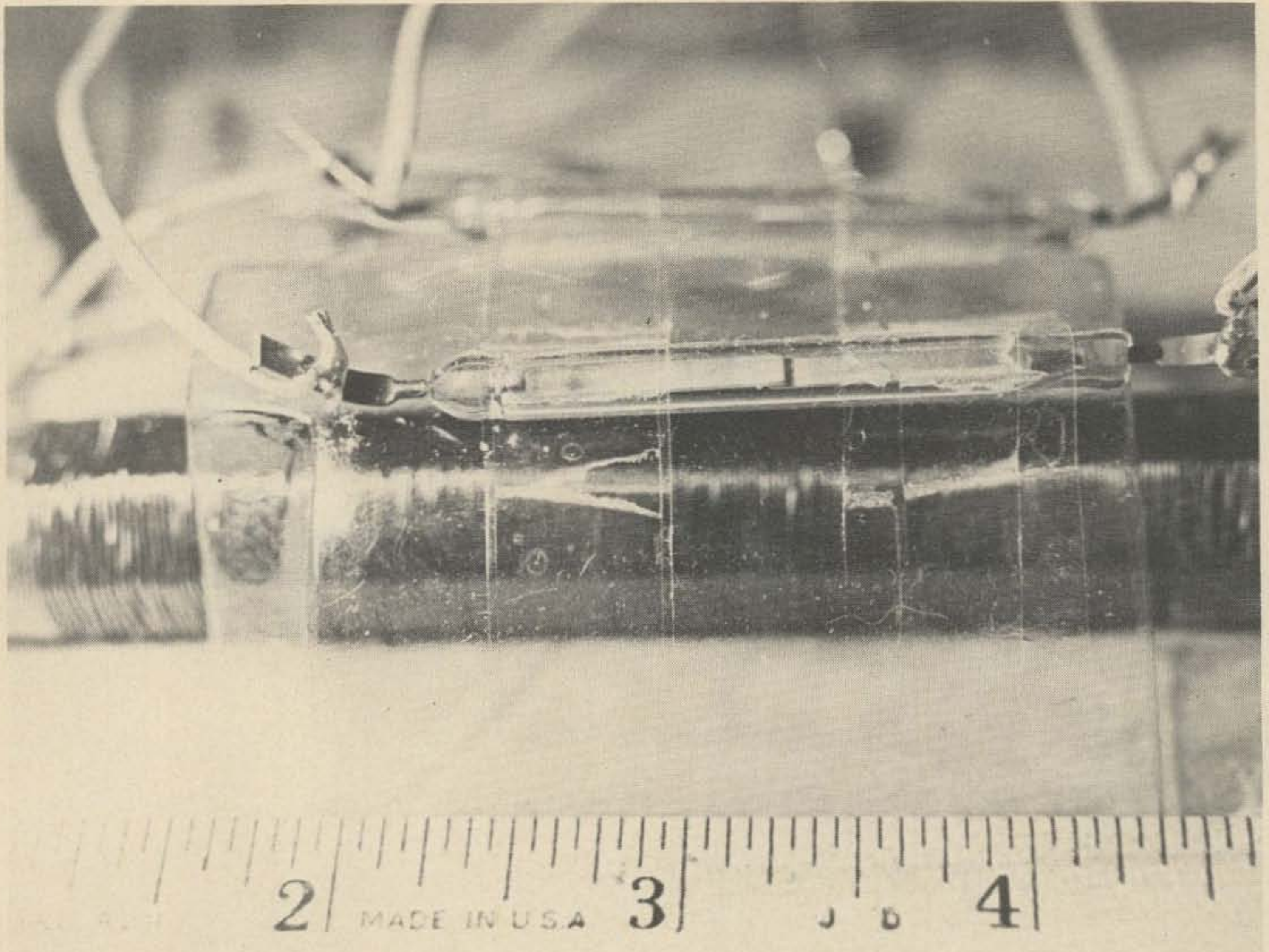

any dc, and must tap a filament or panel lamp circuit. Dc is a must. Granted, ac will produce a field around the coil, but reed switches will chatter in the vicinity of a rapidly changing field. A battery was tried, and worked well, but lasted only an hour. Portable operation with the device could be possible by keying the car battery to the magnet, through a resistor to eliminate the huge blue flash at the key that would occur without the resistor.

Once the magnet is wired, the bubble is in place over the coil, and a roll of cellophane tape is at hand, place the switches on the bubble one at a time while keying the coil. Find a spot where each switch pulls in every time you depress the key, and tape it on the bubble in that place. (Every switch in the package will respond a bit differently, and may have to be moved around on the bubble quite a few times before positive action is had from each switch.)

Note that the device cannot be mounted on metal, as metal will interfere with the magnetic field. Mount the device on a small board, on a wall, on a floor under the table,

or wherever you can get at least six inches clearance from metal.

All that is left is to connect the circuits you wish to activate, or ground, to the switch prongs. One can key the transmitter (mount a key jack on the leads from the switch, and plug it into the key jack on the rig); another switch can short the speaker leads; another can short the receiving antenna to chassis ground; and another switch can be used to key a simple code practice oscillator for monitoring your sending. The number of circuits you can activate by keying the gadget is limited only by the number of reed switches you can crowd around the coil. You could conceivably mount the coil in the cardboard tube accompanying bathroom stationery, and mount switches around the whole circumference of the tube, if you had need for that much switching.

At this QTH, three switches are in use, and have been giving flawless full break-in operation for seven months, following keying faster than you can say --... ..--.

...WB6OMT

CLIP OUT AND ORDER NOW

THIS PAGE IS YOUR ORDER BLANK!

ORDER NOW AND SAVE!

Specials at Unbeatable Prices




GENAVE, 4141 Kingman Dr., Indianapolis, IN 46226 (317+546-1111)

HEY, GENAVE! Thanks for the nice prices! Please send me:

NEW!  **GTX-200-T Operate Auto-Patch**
 2-meter FM, 100 channels. 30 watts (incl. 146.94 MHz) **Special Price \$259⁹⁵**

 **GTX-200**
 2-meter FM, 100 channels. 30 watts **was \$299.95** (Incl. 146.94 MHz) **NOW \$219⁹⁵**

 **GTX-100**
 1 1/4-meter FM, 100 channels, 12 watts **was \$309.95** (Incl. 223.5 MHz) **VERY SPECIAL \$199⁹⁵**

 **GTX-10** 2-meter FM, 10 channels, 10 watts **WOW! \$139⁹⁵** ~~\$169⁹⁵~~

 **GTX-2**
 2-meter FM, 10 channels. 30 watts **was \$299.95** (Incl. 146.94 MHz) **NOW \$199⁹⁵**

 **GTX-600**
 6-meter FM, 100 channels, 35 watts **was \$309.95** (Incl. 52.525 MHz) **SPECIAL NOW \$199⁹⁵**

- PSI-11 Battery Pack (with charger)** @ \$109.95 \$ _____
- ARX-2 2-M Base Antenna** @ \$29.95 \$ _____
- Lambda/4 2-M Trunk Antenna** @ \$29.95 \$ _____
- TE-I Tone Encoder Pad** @ \$59.95 \$ _____
- TE-II Tone Encoder Pad** @ \$49.95 \$ _____
- PSI-9 Port. Power Package (less batteries)** @ \$29.95 \$ _____
- PS-1 AC Power Supply** @ \$69.95 \$ _____

and the following **standard** crystals @ \$4.50 each: _____ \$ _____

Non-standard crystals @ \$6.50 each: _____ \$ _____

(allow 8 weeks delivery.)

For factory crystal installation add \$8.50 per transceiver.

IN residents add 4% sales tax:

CA residents add 6% sales tax:

All orders shipped post-paid within continental U.S.

Sub-Total: \$ _____

TOTAL: \$ _____

(minimum order \$12.00)

NAME _____ PHONE _____

ADDRESS _____ CITY _____ STATE & ZIP _____

Payment by: Certified Check/Money Order Personal Check C.O.D. Include

Note: Orders accompanied by personal checks will require about two weeks to process. **20% Down.**

20% Down Payment Enclosed. Charge Balance To:

BankAmericard # _____ Expires _____

Master Charge # _____ Expires _____ Interbank # _____

9
7
5

Prices and specifications subject to change without notice.

Byron H. Kretzman W2JTP
431 Woodbury Rd.
Huntington NY 11743



Odd Problems With an Old Antenna

You see, I have this summer place in the country, up-river, where I can escape from the rat race in the city. Actually, it is a year-round place, and I go up there just about every weekend, summer and winter. Built on the side of a hill, a big picture window in the den (ham shack, to you) looks out over the hill, sort of a plateau, covered with tall grass. After a week of the hustle and bustle of the city I can come up here, unwind, and really enjoy ham radio, in particular the chase of DX which has never paled for me.

Alongside the house a 75 foot telephone pole supports a full size five element rotary beam, a Yagi, for 20 meters. The receiver is highly sophisticated, and a chrome-plated linear amplifier permits the full gallon input on CW and 2 kW pep on sideband. It's CW that I enjoy the most, although I have more than 200 countries on phone. But, Asiatics have never come easy, phone or CW. Which brings me to this story.

One nice day, near the end of summer,

I'm sitting at a table out on the patio making out QSL cards when one of the local fellows, a farmer, drives up to tell me about a county hamfest he and some other locals are planning. I invited him to have a nice cool tall one and to sit down and chew the rag; about DX, of course. I was bemoaning the difficulty in working the Asian stations, in spite of my beam and chrome plate linear. He sort of smiled (I never did find out how many countries he had) and looked out over the hill in back. "You know, son," he says, "If I had that much unplanted acreage and if I wanted to work Asians that bad, I would put up a rhombic!"

All next week I thought about that suggestion. A rhombic antenna. What ham used a rhombic these days? There wasn't much about this kind of antenna in the Handbook. No constructional info, but this statement, "Antenna gains of the order of 10 to 15 dB can be obtained..." So I did a little research on rhombics. An old World War II Signal Corps technical manual gave

me the information I needed. Well, I spent the balance of the summer and most of fall building a pair of stacked three-wire rhombics, one behind the other, and pointed in the direction of central Asia. Seven telephone poles, each about fifty feet high, supported these monsters, $7\frac{1}{2}$ wavelengths long on each side. A weather-proof box on the rear pole housed a bank of high power terminating resistors. A two-wire transmission line, with a tapered transformer section to bring the 800 Ohm impedance of the antenna down to the 600 Ohm line impedance, led into the shack through two large bowl-type feed-through insulators in the middle of a glass window pane, which had been carefully drilled. A large ferrite balun transformed the 600 Ohm line to the 52 Ohm coax to the antenna relay in the linear.

At long last I was ready to try out this creation. An extra set of coax relays were connected to allow me to make an instant comparison with the five element Yagi. First I carefully tuned the low end of 20 with the Yagi, pointed towards Japan, switched in. The band was reasonably good. A fair complement of J's, KL7's and DU's were coming in S-4 to S-5. Then I switched to the rhombics. Looking at the panadapter, it appeared as if the ambient noise level had risen, but interestingly, the Asians heard just a few seconds ago on the Yagi had dropped down into the noise. Nothing from them could be heard. I continued to tune the band until I spotted a weak CW signal, barely above the noise. It was chirpy and it drifted quite a bit, but with the noise blanker switched on I copied him. He signed, "HS1RJ." I rapidly zeroed in the VFO and gave him a call. Nothing doing. He came back to a W6, giving his QTH as Siam. *Siam?* Then I lost him in the noise. I continued to tune. With the aid of the panadapter I found another weak signal, just above the noise, calling CQ. It signed MX3A. I gave him a short call but he came back to W8CRA and gave his QTH as Manchukuo. *Manchukuo?* Where the heck is that? Before the night was over I copied, and called, ZM1AA, PK1TT, XU6ST, KA8ZK and VS2AL. Not one came back to me! Dawn was breaking as I crawled wearily, frustrated into bed. Right after my

head hit the pillow, I sat bolt upright as a thought banged into my head: There were no pile-ups around any of these stations! I collapsed and fell asleep without further consideration of that one.

Next weekend I went at it again. This time I concentrated on the high end of 20. Underneath the quacking SSB phone level I dug out such goodies as VU2EU, XU4XA and VS7RF. Out of the band, above 14,350, I found UK8IA and J8CG. I hugged the band edge and called them. Neither one came back.

Since there was little agreement between the Call Book prefix QTH's and QTH's given by the DX, I decided to write the DXperts in Newington to see if they could explain this. Also, since none of the stations came back to me, I figured maybe I needed a little bit more power. That's when I remembered Big Bertha. Big Bertha was built about 10 years ago, when I was living with my folks in the city. It is very efficient, much more so than any linear, because it runs Class C. A pair of 4-1000A tubes in push-pull are in the final. (I moth-balled it because the ac power lines in the city were just not stiff enough. Lights dimmed for blocks every time I pressed the key.) At that point I decided to take a week's "vacation" and get Big Bertha up to the summer place where the ac came from a nice, stiff, REA line.

I won't go into the details of getting Big Bertha trucked up and moved into the shack. It wasn't easy. Neither was its installation, which took the rest of the week. But, there it was, on the other side of the room, across from the operating desk. Ducting and a ventilating fan was put in directly above the big cabinet to take the heat out through the roof. Input to the king-size plate transformer primary was controlled by a variac on the front of the rig, its knob as big as a steering wheel. The two-wire spaced feeders were now brought directly into the cabinet through a pair of big bowl insulators to a huge 2-pole antenna relay. Its transmit contacts went to the swinging link of the tank coil and the receive contacts were connected to the ferrite balun for the coax to the receiver, via the switching relays mentioned before.

It was late Sunday night before Big



CURTIS KEYER CHIP as low as \$7.95

8043; IC only, 50-up group rate	\$ 7.95
8043-1; IC, PCB, Manual	\$ 24.95
8043-2; Semi-kit	\$ 49.95
Add for air postage and handling ...	\$ 1.50
(See Feb 75 CQ and Apr 75 HR articles)	
KB4200 Keyboard Keyer (Oct 74 QST) ...	\$549.95
EK420/KM420 Keyer/Memory (Oct 73 QST)	\$439.90
EK430 CMOS Keyer (uses 8043 chip)	\$124.95
IK440 Instructokeyer (Jun 75 "73")	\$224.95

CURTIS ELECTRO DEVICES, Inc.

(415) 964-3136

Box 4090, Mountain View, Cal. 94040



KAUFMAN BALUN

new and improved
molded plastic

KAUFMAN
water tight
BALUN



with or
without
BALUN
1:1 impedance
match

Patent No. D219106 For dipoles,
beams, inverted "V", and quads

KAUFMAN Center Insulator with BALUN	\$12.50 postpaid USA
KAUFMAN Center Insulator without BALUN	7.50 postpaid USA
Dragon Fly antenna construction sheet and drawing	\$2.50 postpaid USA

3 Kw PEP
4 Ounces
Q1 Ferrite

KAUFMAN INDUSTRIES
BOX 817
REEDS FERRY, NH 03054

Bertha was ready to go. A storm was brewing in the west. Lightning was flickering on the horizon but when I turned on the receiver the QRN had not as yet built up. Nothing but noise was coming through on the rhombics. I tuned around for a long time. The storm was getting closer. The thunder, and the QRN, was building up. Then I heard it, weak but above the noise, calling CQ. AC4YN. Quickly I had the vfo on him, switched it into Big Bertha, and gave him a short call. The plate voltage meter read 3,300 volts. Nothing doing. Another short call, this time with 5,000 volts. Nothing doing. The storm was right overhead now. The thunder had become crashes. Another short call, this time with 6,500 volts. Then, *Whaap!* A ball of lightning came in on the feeders with the roar of a freight train, smashing into Big Bertha like a mortar round. Steel flew around the room like shrapnel, for the most part missing me because I was momentarily unconscious behind the desk. When I came to, the rig was a molten mass of glowing metal. Every light in the house was out. Through the picture window I saw that the center pole with its

yardarm was a flaming cross etched against the black stormy sky. Flames were also licking at the ceiling where the fan had been so I struggled to my feet, grabbed the CO2 extinguisher and cooled things down as quickly as I could. Then the rains came. With the aid of a flashlight I reset the house lighting breakers, all of which had been tripped.

The rain stopped as quickly as it started. I spent the balance of the night patching the roof and putting in a plywood panel where the feeders had come in through the window. And, occasionally squirting the fire extinguisher at the still hot pile of debris. The smell of burnt bakelite permeated the whole house.

In the morning I shoveled the mess that had been Big Bertha into a wheelbarrow and gave her a decent burial in the back 40. Walking out on the hill afterwards I found that not a scrap of wire was left, just broken and blackened insulators. The terminating resistor bank, and its dog house, were completely gone. The blackened center pole was still smouldering, in spite of the rain. A very disheartening sight. As I turned to go back down the hill I noticed the mail man's truck coming up the road.

There was just one letter that day. From Newington. Scrawled with a felt pen across my letter to them were these words, "*Who are you kidding? These stations haven't been active in 35 years! Most of the ops are Silent Keys!*" That did it. I cleaned up what was left of the mess, closed up the house and headed back to the city.

Epilogue

It wasn't until next Spring that I had the heart to go back up the river to the summer place. But, a ham is a ham is a ham. Over the summer I rebuilt the rhombics, this time with a big outside grounding switch and with underground coax feeder. The chrome plated linear was back on the desk. However exotic DX calls out of the past were never heard again. Those Keys were really silent now. What little Asiatic DX I did hear now and then was only one or two S-units better on the rhombics than on the Yagi; and, I *did* manage to work a few. . . . W2JTP


The Alligator Squelcher

This is a simple project which can be built in an hour or so and requires no exotic parts or bottomless junk box. If you buy every part new, the cost is less than \$6.00 at any electronics hobby store, such as Radio Shack, Lafayette, etc. The heart of the time-out timer is an NE555 timer, wired to turn on after the pre-set interval. After the transmitter has been keyed for the preset time, the indicator light (or bell, or cannon) will come on and let you know that your time is up, and you should now (1) let the repeater drop; (2) ID; (3) replace your sweep tube finals which have just gone west; or (4) all of the above. None of the component values are particularly critical, so you can substitute freely.

The purpose of the relay is two-fold: One set of contacts resets the timer at the end of each transmission; the other contacts apply voltage to the timer during a transmission, so the circuit will be completely off during receiving. C3 keeps transients from re-triggering the timer. C1 and R1 together determine the time interval. I used 10 microfarads and 5.6 megohms for a delay of about a minute and forty seconds. Most electrolytics are *not* the exact capacitance they are supposed to be. In fact, they may vary as much as minus 50% to plus 100% in an actual circuit. If you want this to be a ten-minute timer, then in theory a combination of 100 microfarads and 6 megohms would give a 600 second delay, but in practice you will have to fudge a bit. In any

event, when you try it for the first time, just push down the plate of the relay rather than key the rig. It saves wear and tear on the finals, and you won't be QRMing anyone while you're finding the correct setting of R1 for the time interval you want.

If you use a light emitting diode for the indicator, you will need a current-limiting resistor, R2, and a value of about 150-200 Ohms is OK for a 12 volt supply voltage. An incandescent bulb that draws up to about 100 milliamps will work also, and you won't need the limiting resistor R2. If you would rather have an audible alarm, most hobby stores stock a small code oscillator module manufactured by Carl Cardover for 98 cents.

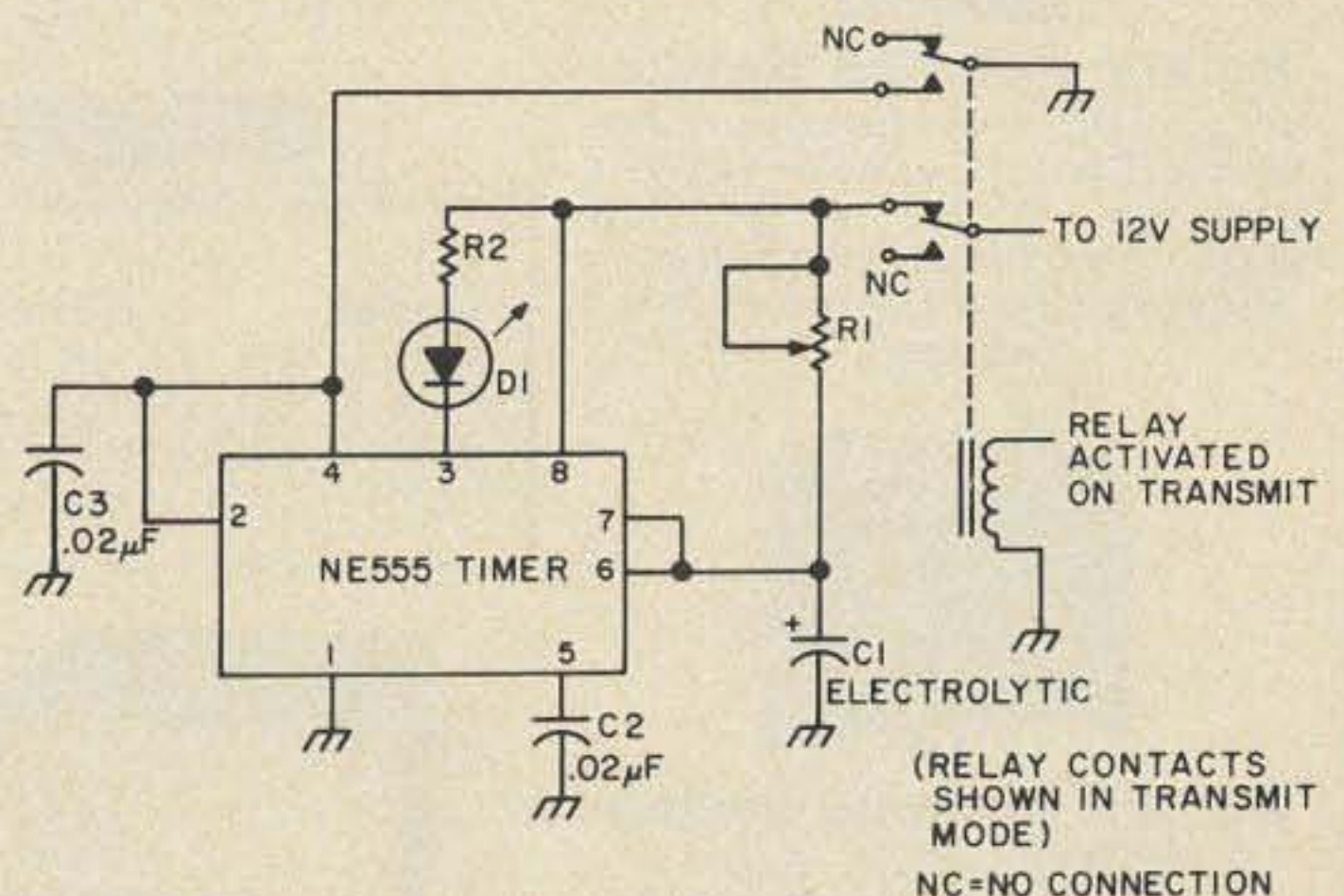

- R₁ — Miniature PC board potentiometer
- R₂ — 150-200Ω (not used unless an LED is also used at D₁)
- C_{2,3} — Disc ceramic
- D₁ — Light emitting diode, or incandescent bulb, such as #47 pilot lamp

Fig. 1.

— WE GOT 'EM —

CLEGG, COLLINS, DRAKE, SWAN, YAESU, TEN-TEC, and many more in stock. Large selection of used equipment. See us for quick courteous service. Established 1928.

FRECK RADIO & SUPPLY CO. Inc.
 P.O. Box 7287 W4WL
 Asheville NC 28802
 704-254-9551



ALDELCO SEMI-CONDUCTOR SUPERMARKET
INTRODUCTORY SPECIAL

5 741 Linear Op Amps 14 Pin DIP	\$1.98
10 1000 Volt 2 Amp Rectifiers	.99
10 Germanium Diodes 1N34	.99
10 Silicon Diodes 1N4148	.99
10 NPN Transistors 2N3904	.99
10 PNP Transistors 2N3906	.99
10 Power Transistors Assorted Germanium & Silicon	4.95
10 Zener Diodes Assorted Unmarked	1.98
10 Assorted ICs All Marked	1.98
100 Assorted Rectifiers 1 Amp Unmarked	3.95
100 Assorted Transistors Unmarked	6.95

POST PAID \$5.00 Minimum SEND FOR COMPLETE LIST

ALDELCO P.O. Box 341, Dept. 7
 Lynbrook, New York 11563

In place of a light, wire the module so the positive terminal goes to pin 8 of the 555 and the negative terminal goes to pin 3. As a last resort, if you're the type that ignores everything while you're talking, you could hook up another relay to pins 3 and 8 that would cut off power to the rig at the end of the time interval.

Layout of parts is not critical, so long as you keep the project down to a reasonable size. Just remember, having very long leads in a circuit near an operating transmitter is asking for rf pickup. I used a 14 pin integrated circuit socket as both a terminal strip and IC holder. The extra pins can be cut off, or used to attach the circuit to the rig.

Before trying my circuit out in the transmitter, I hooked everything together with clip leads, and cut and tried until I found the right value of resistance of R1. This done, the completed circuit worked right the first time when put in the rig, something I only dream of for most of my projects.

...WB8EQQ

APOLLO PRODUCTS by "Village Twig"



1500X-2

Rotary Antenna Switch

Single pole, 3 position Antenna Switch. Low SWR. Use up to 30 MHz. 500 Watt handling capacity. Sloping Front Console Cab.

\$14.95



450X-S Antenna Switch


3-Position Slide Switch Low Loss - Walnut-grain Finish Chassis - Gold Cover

\$7.95

700X-2 KW Wattmeter

Dummy Load Wattmeter for 52 Ohm Input. Measures RF in 4 ranges to 1000 watts. Measures modulation percentage on calibrated scale. Portable.

\$149.50

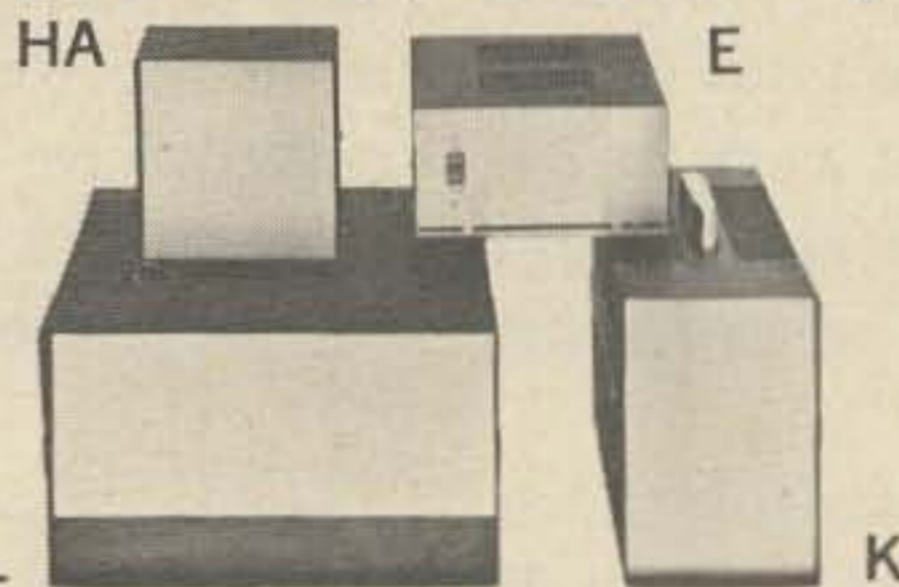

Model	Dimensions	Resale Net
"E"	6 1/2 x 3 15/32 x 7 1/16	9.25
"HA"	5 1/8 x 5 1/2 x 4 (Blank Panel)	8.95
"K"	4 3/4 x 7 3/8 x 11 W/Handle	13.50
"L"	11 1/8 x 6 1/8 x 12 3/4	22.95



Meter O-1 MA
 to fit "L" box
 ppd. \$7.00



"L" package enclosure "Shadow Box" machined with: 2-SO239, 1 - Pilot Light, 3 - Rocker Switches, and 2 - Knobs
 pkg. \$33.50

APOLLO PRODUCTS

BOX 245 - VAUGHNSVILLE, OHIO 45893 - Phone (419) 646-3495 - Evening Phone (419) 646-3495



2100X-2 SWR Bridge
 Large Meter -

Sloping Panel Cabinet - Rubber Feet - Keep in Antenna Line up to 1 Kilowatt

\$37.50



900X-2 Wattmeter

Measures RF in 2 ranges 25 and 250 watts. 52 Ohm input.

\$35.50

1700X-2 Vertical/Horizontal Antenna Switch


Allows operator to select any one of 3 antennas or dummy load. Two Antennas can be switched in simultaneously. New Sloping Front Console Cab.

\$14.95

WRITE FOR COMPLETE INFORMATION ON ANY OF THE ABOVE

You Don't Have a Power Failure Alarm?

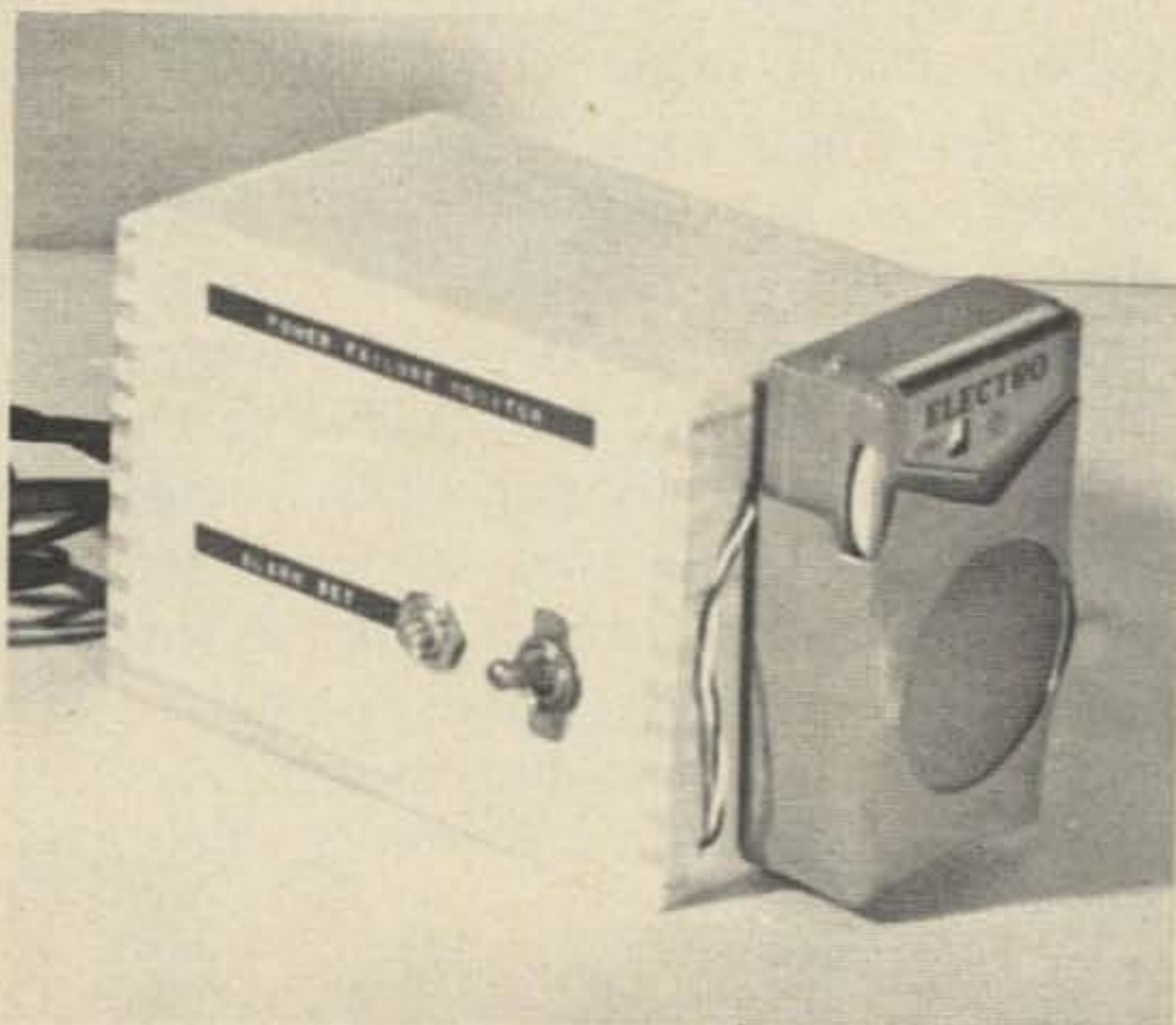You probably need a power failure alarm. Why don't you have one? You haven't seen one for sale? Then why don't you build one? You just don't think it's worth the trouble for one or two power failures each year. And after the lights come back on you just know it won't happen again for a long time.



Front view, PFA. A larger box would allow radio to be placed inside.

Well, that is exactly how I felt about PFAs (power failure alarms), until about six years ago when I found just the right assortment of parts to make one. This little warning device has done such a good job for me that I have not even "improved" it, and that is unusual at my shack.

What It Will Do

The device I built is somewhat different from others I have seen. Here's what it will do for you:

(1) If power fails while you are asleep it will gently awaken you with an audible signal so familiar sounding that it will not scare you out of your PJ's at 3 a.m. some morning. . . no bells, sirens, buzzers or whistles.

You can then set your trusty wind-up alarm clock or sit up and read some back issues of this magazine.

(2) If power fails during daylight it will warn your MYL (in case she was scrubbing floors instead of watching TV, which would have also warned her).

(3) If power fails while you are all away from home, you will know about it as soon as you return. The GENTLE alarm will be on, even though power has been restored in the meantime. Without the PFA you might have gone to bed and not noticed the electric alarm clock was 45 minutes slow.

(4) If your electric service never fails (you dreamer!) this project is still not a total loss because you can use this PFA as a spare radio. . .just flip the switch.

Here's what it will not do: (1) It will not sound an alarm every time the lights flicker in a storm. There is a three second delay before the alarm trips. (2) It will not recharge or replace its own battery. . .you have to do that about once a year.

Construction Notes

Now let's get on to some of the details of this PFA. The assortment of parts I mentioned before includes a wooden file box, a retired transistor radio that still works, a fresh 9 volt battery, a sensitive relay, a momentary contact push-button, and parts to make a small power supply. Throw them together as shown in Fig. 1. Construction can be plain or fancy according to your taste. A small purchased power supply will save you some labor but will raise the cost.

The radio used should be a 9 volt type; otherwise, you may have to modify the circuit. Prepare the radio by removing its battery and bringing out the power leads. The file box should be made of wood or plastic so the radio's antenna will not be detuned, and so the radio can be placed inside, if desired.

A cigar box might also be a suitable cabinet. I attached the radio to the outside of the file box as shown in the photo. The relay should be the small, sensitive type rated at 9 volts or less and drawing less than 20mA. This will keep power consumption to 200mW plus transformer losses. If the relay coil is rated lower than 6 volts, use an appropriate dropping resistor in series with it.

The power supply, if not a ready made item, should be enclosed in a metal case for safety. Use a 1/2 A fuse in the line and a UL

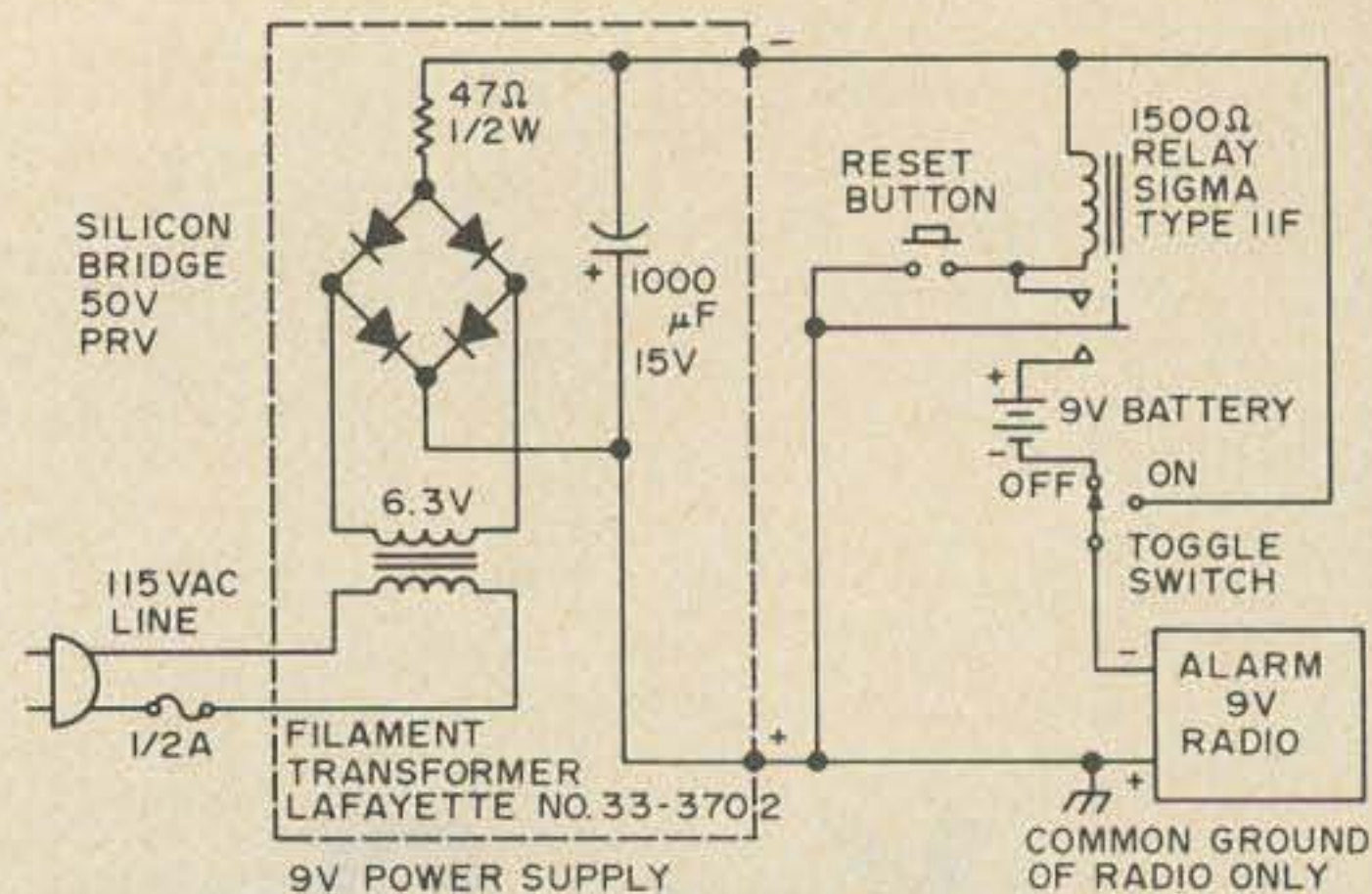


Fig. 1. Schematic of simple power failure alarm. The 1000 μ F electrolytic capacitor should be increased in value if a longer delay time is desired.


approved cord. Make certain your 115 volt wiring is well insulated! Remember, you are constructing a piece of equipment which will be connected to the power line 24 hours a day. It can be safer than a table lamp if it is built well.

By now you have probably figured out how it works. The relay is normally held energized by the 9 volt power supply. When 115 volt power is cut off, the filter capacitor will hold the relay energized for about three seconds. After this delay period the relay drops out, or de-energizes, and connects the 9 volt battery to the radio which has been carefully preset to your favorite 24-hour-a-day radio station at a GENTLE volume. In case you live where there is no dependable 24-hour-a-day station, set it to a station that comes on early enough to get you to work on time.

The battery problem is one of the drawbacks of this PFA. You can either buy a new battery for it once a year, or else keep rotating. When some other radio needs a battery, use the one from the PFA and put the new battery in the PFA. The PFA battery will usually not wear out unless you take long vacations. I used a large D6 size battery and actually the 2U6 would have done the job. The large batteries seem to deteriorate with age about as fast as the little ones. If you do insist on having a battery-less alarm, a clever one is described by Frank H. Tooker in *Popular Electronics*, February, 1968.

Operation

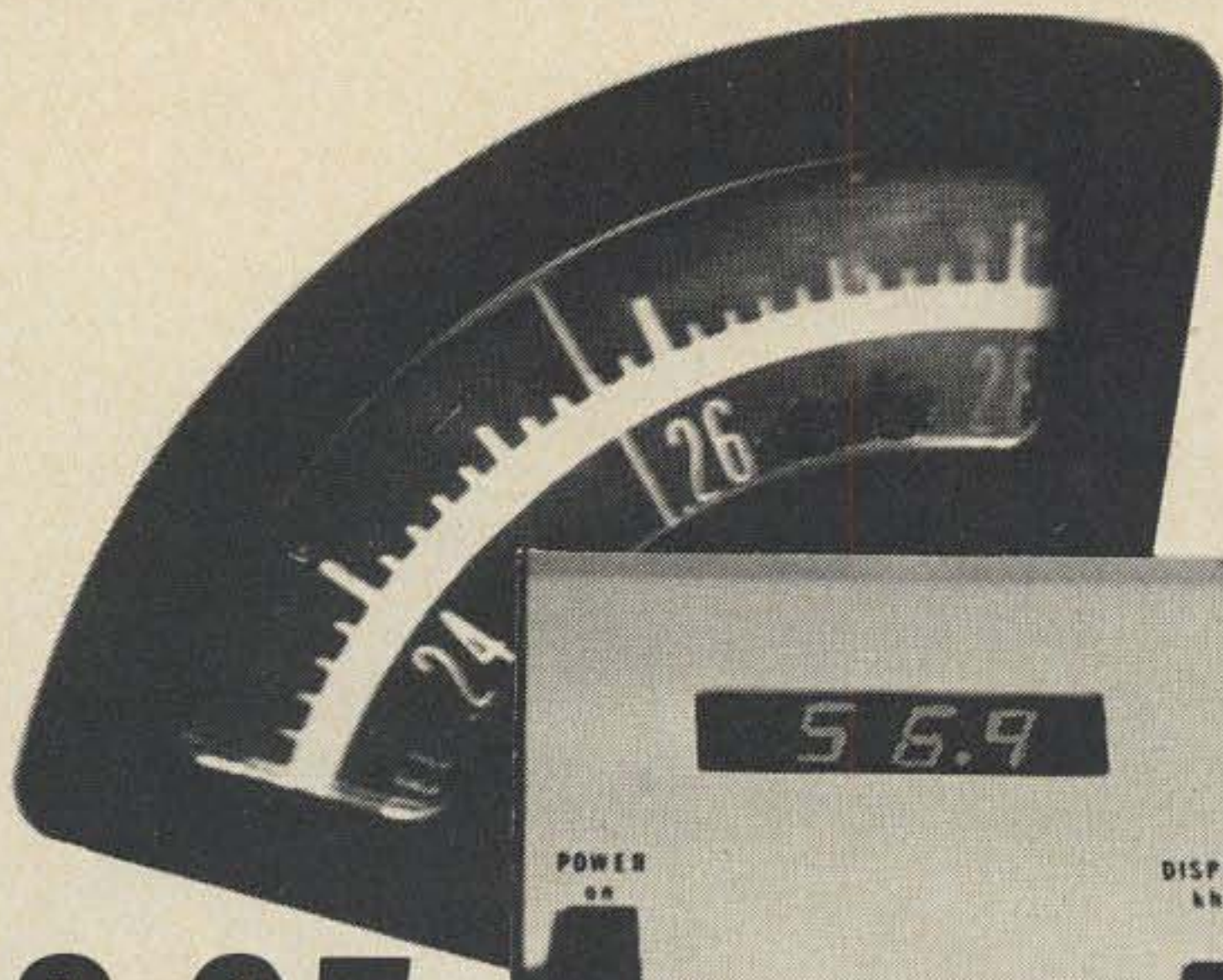Operation of the PFA is simple but confusing to write about. PFA unplugged




UPDATE

to

DIGITAL READOUT TUNING

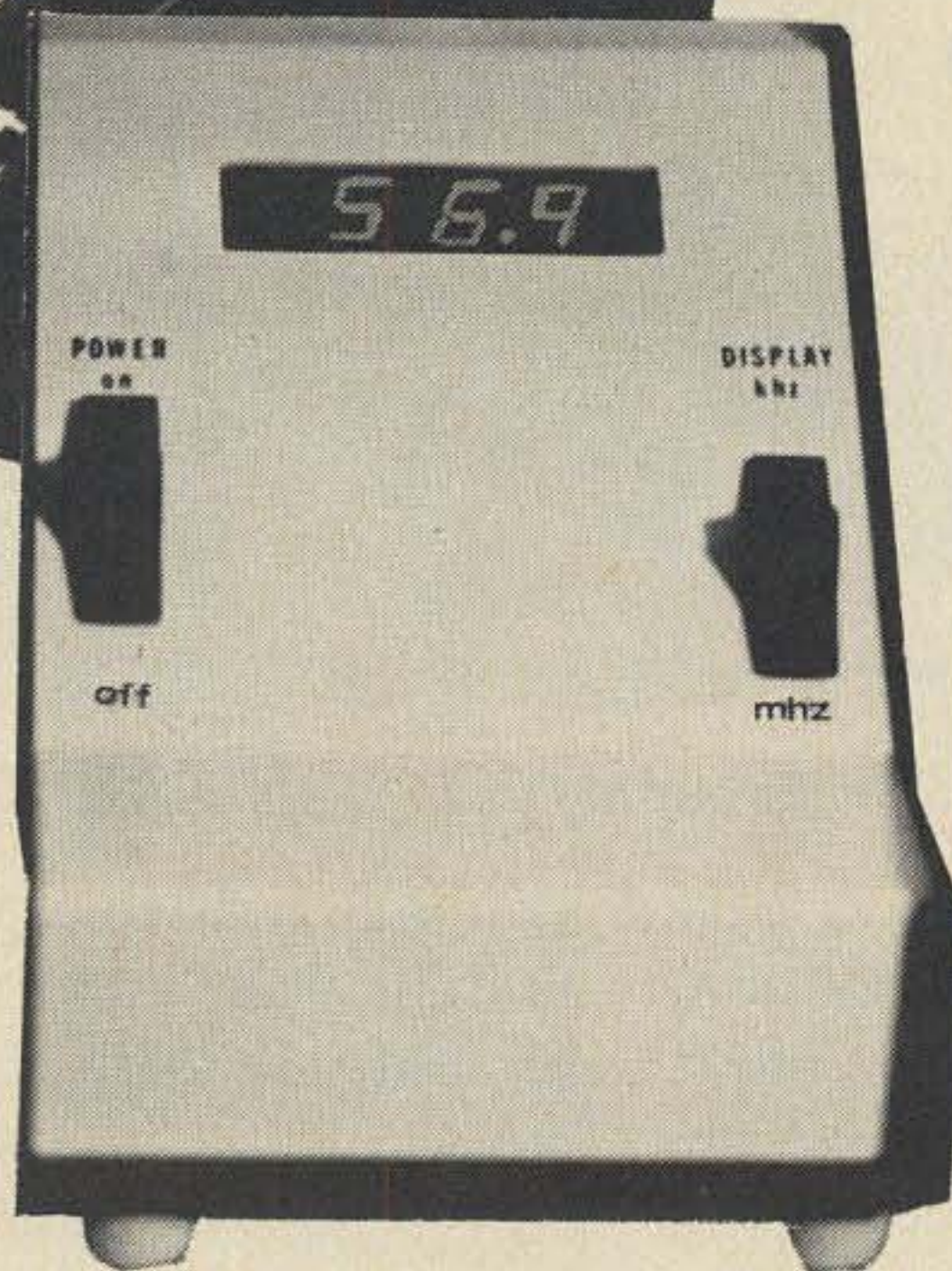42.95

Kit: includes;
Power Supply,
Display card,
Timing card,
Misc. parts, less
case.



**WORKS WITH ANY 160-20 METER TRANSMITTER OR
TRANSCEIVER WITH JUST A PICKUP LOOP**

- All IC
- Build it into your rig
- Converts to 15 and 10
- Even works with QRP rigs
- Mobile too
- MHz/KHz coarse/fine readout
- Frequency to 100 Hz
- Easy to build
- Power supply included
- Crystal controlled time base

BRING YOUR RIG TO THE STATE OF THE ART

HURRY, I don't want to lay out several hundred bucks for a new rig, but I gotta have digital readout (doesn't everyone?)

Here's a check for _____ for _____ unit(s). You pay shipping.

Name _____ Call _____


Address _____

City _____ State _____ Zip _____

TWS LABS

ATTENTION: IF YOUR RIG HAS 5-5.5MHZ
VFO YOU CAN HAVE FULL-TIME ALL BAND
READOUT IN TRANSMIT AND RECEIVE !!!

P.O. Box 357, Provo, Utah 84601

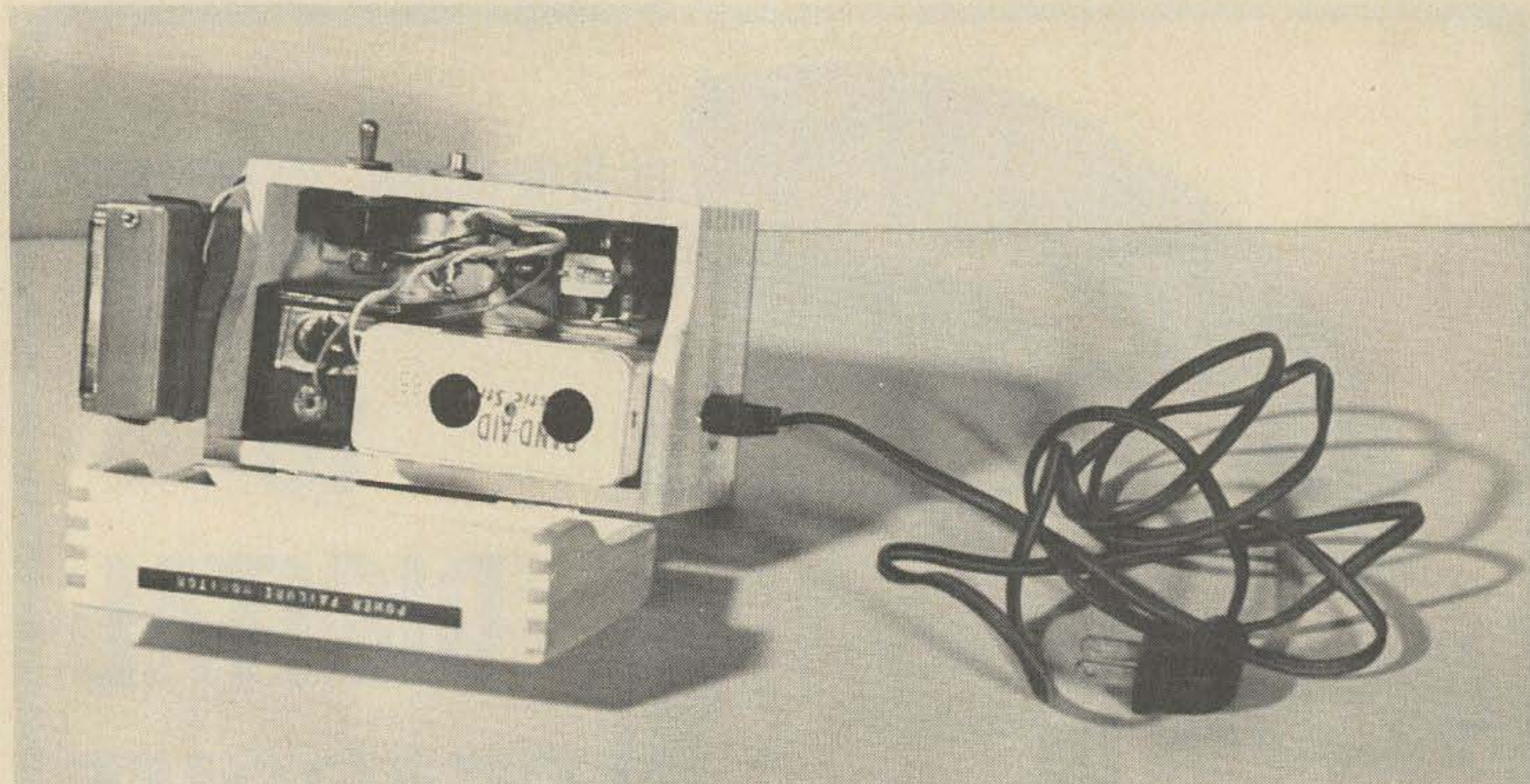

Inside of PFA. Power supply is in BAND-AID® can.

and switch "off" causes the radio to play from battery, which is the alarm condition. If you now plug PFA into a live 115 volt ac line, the radio should continue to play from the battery. Push the reset button. The relay should latch causing the radio to go off. This is the normal condition: power is on, switch is "off", and radio is off; the alarm is set.

Now test the PFA. Unplug the cord for two seconds and reconnect...nothing should happen. Unplug the cord again and in 2 to 5 seconds the radio should start to play. When you have the PFA working right, it is a good idea to tape the radio's volume control and tuning dial to prevent accidental misadjustment.

Let's take some actual situations. Electric service is interrupted for ten minutes while you are away. When you return the lights are working, the refrigerator is running and everything seems normal, except the PFA radio is playing.

Simply reset with the push-button, set all your electric clocks and wait for the next power failure. Let's say you are at home when that happens. It is daylight and you might not know that power is off. But the PFA warns you immediately.

If you want to be alerted when power is restored, flip the switch to "on." This now turns PFA radio off. When power returns

you will hear the radio again. Now turn the switch "off" and push the reset button. Should you want to catch a news or weather report while power is normal, just turn switch to "on" and now, believe it or not, the radio will play. But if you have a power failure now the radio will stop playing. See what I mean about confusing? It is really much simpler than it sounds. After all, with only two controls, it doesn't take long to try all the combinations.

After you install this PFA in some remote nook or cranny of your house, you should forget about it, and you will forget, just as my wife did. Her first experience with the PFA was about six months after I had placed it on a high shelf behind some pictures. One afternoon she was completely perplexed by mysterious music in the house. Cautiously tracing the sound to its origin brought her face to face with the PFA, clearly labeled: POWER FAILURE MONITOR. She then realized the electricity was off. But alas! She didn't shut off the PFA by turning the switch to "on." No, she very sensibly and simply turned the radio itself off. Now you know why I said to tape up the radio's volume control.

In six years of operation my PFA has never failed to signal a power failure. The situations mentioned before have all occurred in our household.

... W9DJZ

73 Where the Action Is!

Subscribe and Save — a lot
\$16 Today or \$60 Tomorrow?

*Subscribe today,
before the prices go up.
Your cost is only \$16.*

Wait for a few weeks and you've had it . . . the new cover price will be \$1.50 per issue (and worth it) . . . that's \$18 per year . . . plus \$2.00 extra for a giant secret bonus issue (no extra charge for subscribers) . . . \$20 per year newsstand cost . . . \$60 for three years (unless prices go up further, which they probably will, considering paper, printing and postage hikes).

(Outside North America — \$18.)

SUBSCRIPTION to 73 MAGAZINE *(Offer valid only until Oct. 15, 1975)*

Name _____

Address _____

City _____ State _____ Zip _____

Cash

Check

BankAmericard

Master Charge

Bill me

Charge No. _____

Expiration date _____

Signature _____



73 MAGAZINE • Peterborough NH 03458



Alan Smith W8CHK
3213 Barth Street
Flint MI 48504

Portable QRP Power Unit

One of the very attractive advantages of QRP operation is its built-in potential for ultra-portability. The easy way a 3 or 4 band CW transceiver fits into an underseat flight bag speaks volumes for the tote-ability of these little gems.


In truth, these rigs can be taken anywhere as handily as a lunch bucket or a briefcase. And with a little imaginative antenna work, you can be on the air as fast as you can say Wayne Green 73 times.

Maybe even faster.


Now these QRP transceivers don't require much in the way of fan cooling, but they still need a little punch from a friendly power source.

Most often, power is supplied at 12 volts dc. This is easy when 120 V ac is at hand, but the implication of QRP is that it may be used at a QTH many furlongs from a high line.

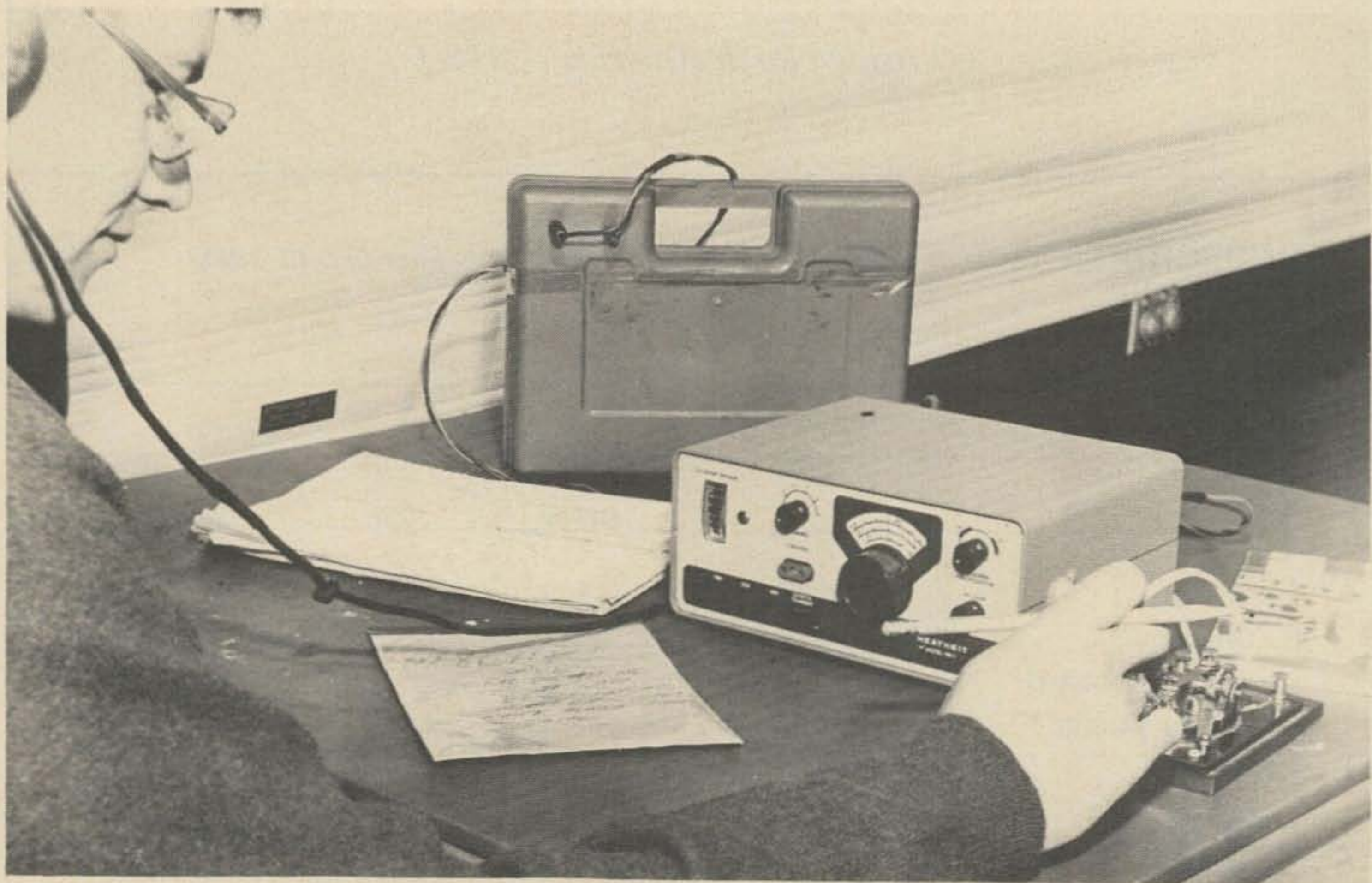Of course, 12 volts is also available wherever you can take a car, but when you are really out there, up there or down there, the choices all add up to batteries. And there



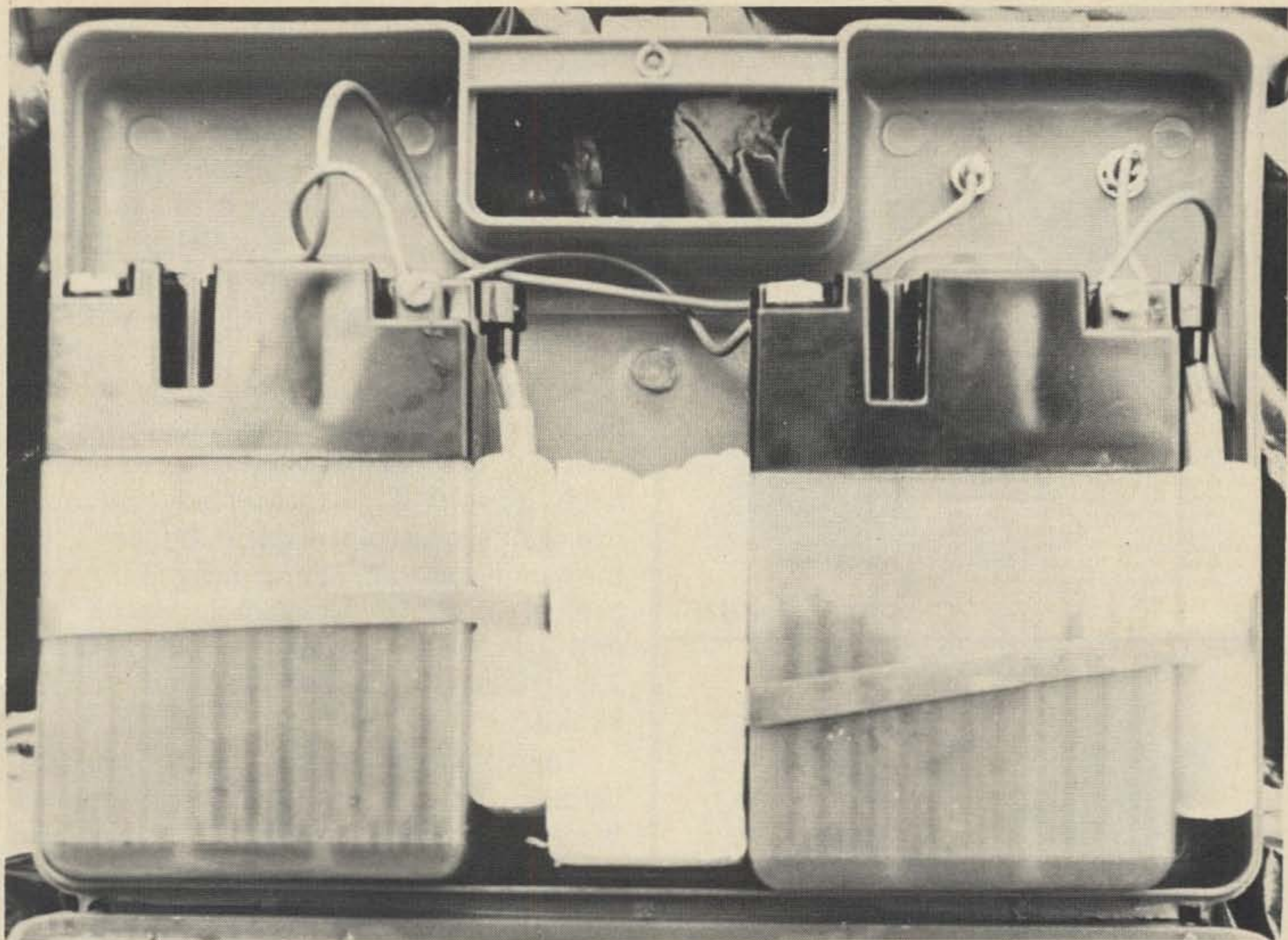Mark Smith WB8KKZ and battery pack get it all together.



12 volt battery pack.

are batteries and batteries. Some are cheap, some expensive. The rechargeable variety is usually the most costly, although the recharging angle brings the cost per hour down.

Dry cells are, as everyone knows, an easy answer to the portability question. But the right dry cells are not available just anywhere and when they are dead, you throw them away. There is, however, another way to go. What is needed is a compact, heavy duty rechargeable 12 volt supply obtainable without giving up your last Picasso in the process. It is really quite simple. All you have to do is assemble a small lead-acid storage battery pack from easily available parts.

First on the bill of material is a brace of the 6 volt miniature lead-acid batteries now being marketed at many electronic parts outlets. Olson sells one for a very reasonable price. The Olson battery measures $5\frac{1}{2} \times 4\frac{1}{2} \times 2\frac{1}{2}$ inches and is rated at 6 Ampere hours. Hook up two of these in series. Fit them into a cast-off plastic carrying case such as is

used to package certain brands of soldering guns (Weller and Montgomery Ward) and you are ready to go.


The Weller and Montgomery Ward cases are sized exactly right to house two Olson batteries plus a styrofoam spacer to keep everything snug. A couple of *color coded* pin jacks installed in one corner of the case provides easy access to the 12 volt output.

The battery pack pictured here is housed in a Wards soldering gun case. Starting with a full charge, it was used to power a Heath HW-7, also shown, during a 2 week Michigan camping trip. The rig was used off and on each day by two operators. At the end of the 2 weeks, good signal reports were still coming in although the batteries had not been recharged.

Electrolyte leakage, the curse of lead acid batteries, is well controlled in the Olson battery. During the 2 week camping trip the batteries remained perfectly dry on the exterior. And considering the generally rough treatment handed out, this is quite a feat.

NEW KITS! NEW KITS!

DIGITAL VOLTMETER

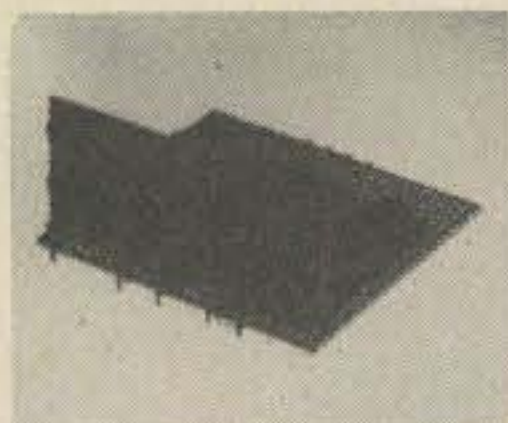

This is a 3 1/2 digit, 0-2 volt Digital Voltmeter, with a .5% full scale accuracy. It is based around the Siliconix LD110, LD111 DVM chip set. The voltmeter uses MAN7 readouts (.3" high) to provide a highly readable display. The unit requires the following supply voltages: 12, -12, 5. The unit comes complete with all components to build the unit pictured at the left, that is a complete DVM less power supply.

\$39.95 Per Kit

LOGIC PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families: TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (HI)-1 (LOW)-0 (PULSE)-P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.



\$9.95 Per Kit

DIGITAL COUNTER



This is a 4 digit counter unit which will count up to 9999 and then provide an overflow pulse. It is based around the Mostek MK5007 digital counter chip. The unit performs the following functions: Count Input, RESET, Latch, Overflow. The counter operates up to 250 kHz. The counter is an ideal unit to be used as a frequency counter, where the only extra components needed would be a timebase, divider chain and gate. The unit requires 5V, and -12V. The unit comes complete as shown on the left less power supply.

\$29.95 Per Kit

ONE KILOBYTE RANDOM ACCESS MEMORY

This memory card is for the most part a universal unit that can be used in almost any microcomputer from a HOMEBREW to an ALTAIR 8800. It uses an array of 2102 1k x 1 static random access memories to produce a 1024 x 8 memory compatible with most standard microcomputer systems. We provide everything from the super low noise vector logic card, to fine quality low profile sockets, to the eight 2102's. We even include timing diagrams and tantalum bypass capacitor.



\$69.95 Per Kit

5 VOLT 1 AMP T²L SUPPLY



5 VOLT 1 AMP T²L SUPPLY \$9.95 Per Kit

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only:

PLASTIC INSTRUMENT CASE

These cases are fine quality units made by a German manufacturing firm which fit to the dimensions of our DVM and COUNTER kit with room enough left for power supply or batteries. Excellent for many other projects as well. Dimensions 2" x 3-1/8" x 5-7/8".



\$5.95 Per Case

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. Add \$1.25 for Postage — Write for FREE 1975 Catalog California Residents — Add 6% Sales Tax

JAMES

P.O. BOX 822, BELMONT, CA. 94002
PHONE ORDERS — (415) 592-8097

Nickel-cadmium batteries of the same capacity are much more expensive. Although they have the advantage of not having free electrolyte to worry about spilling, they have their own private curse. This is the polarity reversal gremlin that almost always appears when a ni-cad is depleted until the voltage drops. This is an expensive curse because polarity reversal ruins the affected cell.

A new plastic carrying case for the batteries can of course be obtained, along with a soldering gun, wherever such battery items are sold. If you are already the proud owner of such a soldering gun, but can't find the case it came in, Montgomery Ward is the best place to try for a replacement. You might also try "The Cooper Group," PO Box 728, Apex NC 27502 (cat. no. PUC20, \$3.00).

This pack will quickly suggest other uses: lighting, rocketry, test bench and so forth. We even use ours to check out the trailer brakes before hitching up to the car.

Your list might be even more interesting.
... W8CHK

18" FACSIMILE RECORDERS FOR SALE

The leading manufacturer of 18" facsimile weather chart recorders is now updating an existing network to solid state equipment. This updating is making available a number of 18" weather map recorders ideally suited for anyone interested in experimenting with facsimile.

These recorders, with suitable receiver and FSK converter, can be used to monitor radio weather chart broadcasts as well as press wire photo transmissions. With some modifications, data from weather satellites can also be received.

These recorders are reasonably priced and available on a first come, first served basis.

Call or write Mr. Armand D. Bouchard:

ALDEN ELECTRONICS & IMPULSE RECORDING EQUIPMENT CO., INC.
Washington Street, Westboro MA 01581
617/366-8851

CATALOG GOVERNMENT SURPLUS ELECTRONIC EQUIPMENT For 1975

FREE UPON REQUEST! Write for Copy of Catalog WS-75 Now!
Address: Attention Dept. 73

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

the all-year Gift

Next time you're giving a friend a gift, give some thought to a gift subscription to 73. Each month they'll receive a lively new copy of 73 Magazine, packed with intriguing articles and ideas for the ham radio enthusiast. And most importantly, you'll be sharing a mutual interest in something you can both enjoy.

Just fill out the material below and we'll rush off an attractive gift card to the person of your choice . . . a distinctive gift card personalized with your name. It's the perfect gift for young or old, experienced or novice. And we promise (WE PROMISE!) to send your gift card out immediately. Do a friend a favor and order today.

OK! You promise to rush my gift card and gift subscription to:

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

Please send them a : 1 year (\$8.00) 3 year (\$16.00) subscription.

Master Charge BankAmericard Check Enclosed

Signature _____

Card No. _____ Expiration date _____

Total enclosed \$ _____

Bill me

Name _____

Address _____


City _____ State _____ Zip _____

Mail Today to:

GIFT SUBSCRIPTION Dept • 73 Magazine • Peterborough NH 03458

TECO has the newest from *Dentron*

The Brand New 160-V Vertical Antenna

Another eye opener from Dentron, this new vertical antenna will solve your 160, 80 and 40 meter problems. 

- Efficient Vertical Design
- Self Supporting
- Weatherproof
- Quick & easy one man installation
- Covers 160, 80 or 40 meter band with only one adjustment.

160-40V Antenna \$79.50 ppd. USA



Here is another Dentron first, a six band antenna tuner designed to solve virtually any matching problem you may have.

- Covers all bands 160 through 10 meters
- Handles maximum legal power
- Matches coax feed, random wire and balanced line
- Includes heavy duty balun for balanced line
- Black wrinkle finish cabinet

160-10 Super Tuner \$119.50 ppd. USA


Be ready for restructuring — Special Supertuner handles 3 KW PEP amplifiers —

\$229.50 ppd. USA

This is the low cost way to match almost any random length wire on the five most used HF bands.

- Covers 80 through 10 meters
- Handles maximum legal power
- Matches random length long wire antennas
- Features Dentron quality and value

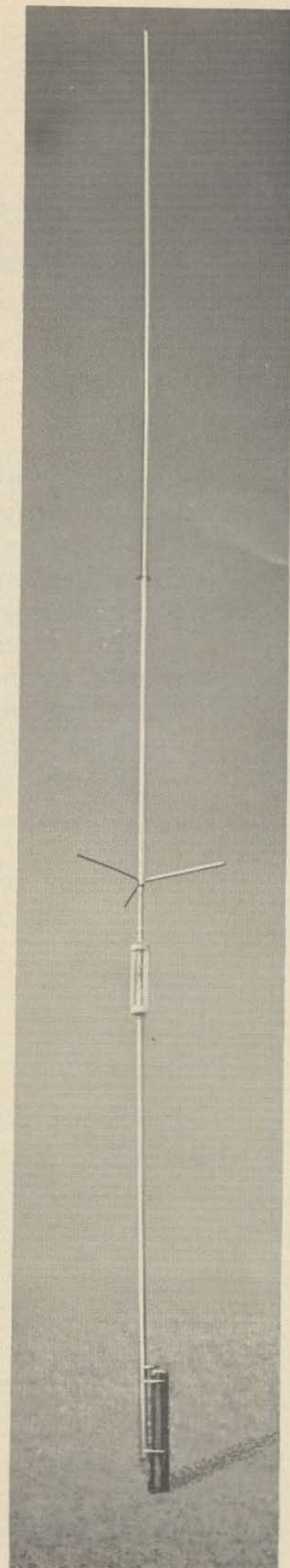Model 80-10 Antenna Tuner \$49.50 ppd. USA



TECO

P.O. BOX 1050


a subsidiary of Tucker Electronics Co.

1717 S. Jupiter Rd. GARLAND, TX. 75040

800-527-4642 toll free

In Texas Call 214-348-8800

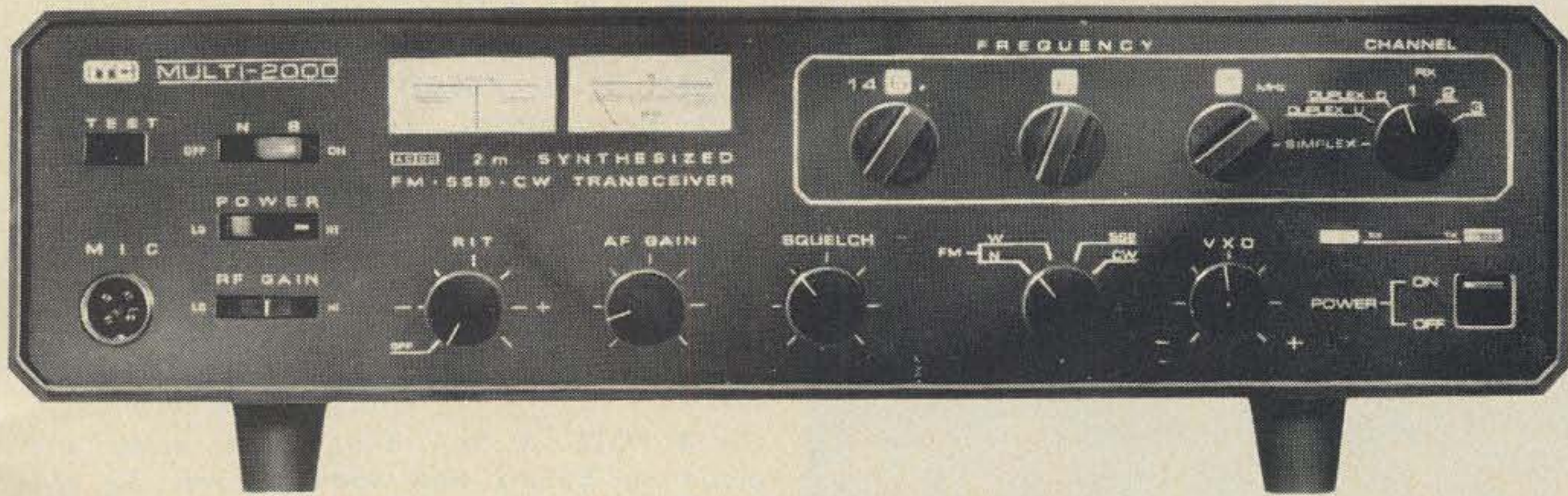MEET THE STATE OF THE ART ON 2 METERS... THE ITC MULTI-2000 CW/SSB/FM TRANSCEIVER



Whether your interest is simplex, repeater, DX or OSCAR the new ITC MULTI-2000 lets you get into all the action on all of the

band. Fully solid-state and employing modular construction, the MULTI-2000 enjoys features found in no other 2m transceiver.

FEATURES

- PLL synthesizer covers 144-148 MHz in 10 kHz steps
- Separate VXO and RIT for full between-channel tuning
- Simplex or ± 600 kHz offset for repeater operation
- Three selectable priority channels
- Multi-mode operation (CW/SSB/NBFM/WBFM)
- Built-in AC and DC power supplies, noise-blanker squelch and rf gain control
- Selectable 1W or 10W output
- Separate S-/power and frequency deviation meters
- Built-in test (call) tone and touch-tone provision
- Excellent sensitivity ($.3 \mu\text{V}$ for 12 dB SINAD)
- Superior immunity to crossmodulation and intermodulation
- Introductory price: \$695.



TECO

a subsidiary of Tucker Electronics Co.

P.O. BOX 1050 1717 S. Jupiter Rd. GARLAND, TX. 75040

214—348-1560

NEW
(A)



NEW
(B)




NEW
(C)



NEW
(D)



NEW
(E)

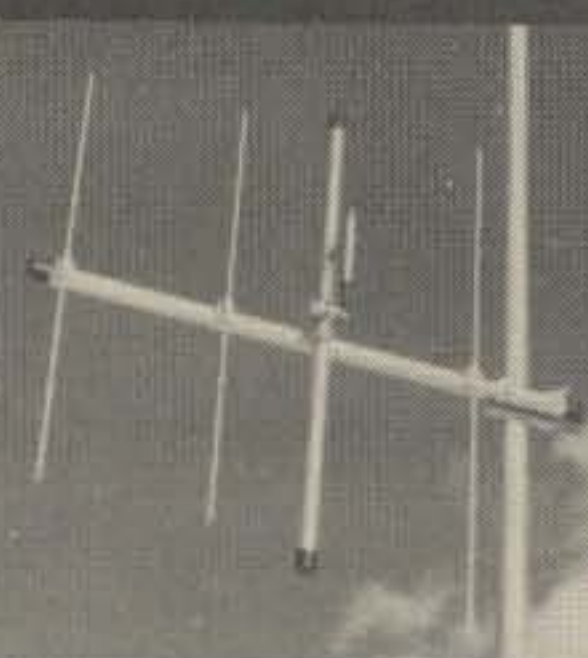

NEW
(F)



Cush Craft

2 METER FM ANTENNAS

NEW FROM THE WORLD'S LEADING MANUFACTURER OF VHF/UHF COMMUNICATION ANTENNAS

(A) **FM GAIN RINGO:** The most popular — high performance, half-wave FM antennas. Give peak gain, and efficiency, instant assembly and installation.

AR-2	100 watts	135-175 MHz
AR-25	500 watts	135-175 MHz
AR-220	100 watts	220-225 MHz
AR-450	100 watts	420-470 MHz
AR-6	100 watts	50-54 MHz

(B) **4 POLE:** A four dipole gain array with mounting booms and coax harness 52 ohm feed, 360° or 180° pattern.

AFM-4D	1000 watts	146-148 MHz
AFM-24D	1000 watts	220-225 MHz
AFM-44D	1000 watts	435-450 MHz

(C) **FM MOBILE: IMPROVED** Fiberglass 5/8 wave mobile antenna with new molded base and quick grip trunk mount. Superior strength, power handling and performance.

AM-147T 146-175 MHz mobile

(D) **POWER PACK:** A 22 element, high performance, vertically polarized FM array, complete with all hardware, mounting boom, harness and 2 antennas.

A147-22 1000 watts 146-148 MHz

(E) **4-6-11 ELEMENT YAGIS:** The standard of comparison in VHF/UHF communications, now cut for 2 meter FM and vertical polarization. 4 & 6 Element models can be tower side mounted.

A147-4	1000 watts	146-148 MHz
A147-11	1000 watts	146-148 MHz
A220-11	1000 watts	220-225 MHz
A449-6	1000 watts	440-450 MHz
A449-11	1000 watts	440-450 MHz

(F) **FM TWIST:** A Cush Craft exclusive — it's two antennas in one. Horizontal elements cut at 144.5 MHz, vertical elements cut at 147 MHz, two feed lines.

A147-20T 1000 watts 145 & 147 MHz



TECO

a subsidiary of Tucker Electronics Co.


P.O. BOX 1050 1717 S. Jupiter Rd. GARLAND, TX. 75040

214-348-1560

**A GREAT SCOPE-
AT A GREAT PRICE**

!

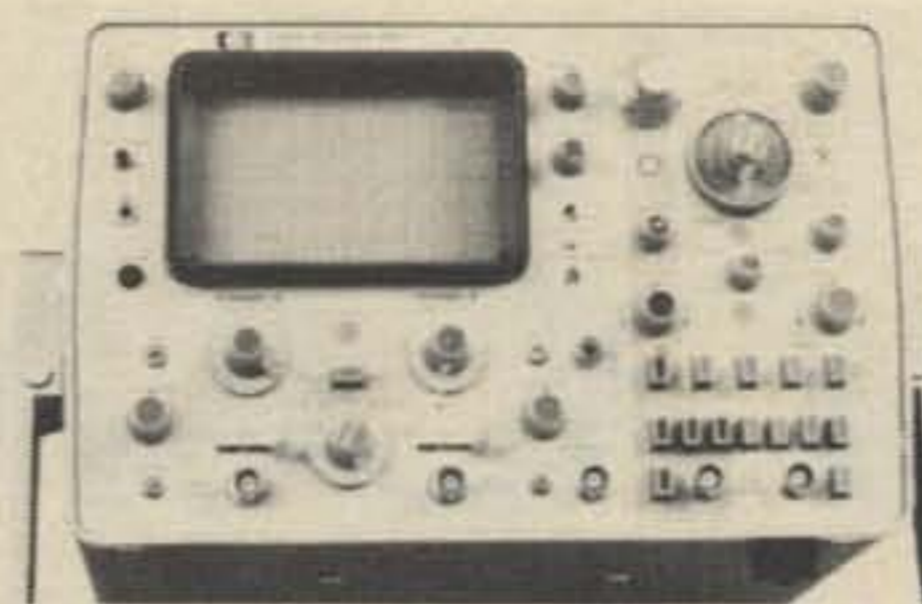\$1295 (Reconditioned)
WHILE THE SUPPLY LASTS



HEWLETT PACKARD 1707B

DUAL CHANNEL, 75 MHz BANDWIDTH, 10 mV/DIV SENSITIVITY, SWEEP SPEEDS FROM 0.1 μ SEC/DIV TO 2 SEC/DIV. DELAYED TIME BASE FROM 0.1 μ SEC TO 2 SEC DELAY. EXTERNAL HORIZ INPUT - DC TO 1 MHz. CHANNEL A OUTPUT - 100 mV PER DIV.

MANUFACTURED BY HEWLETT PACKARD - SOLD BY TUCKER
TUCKER ELECTRONICS has a limited quantity of reconditioned HEWLETT PACKARD 1707B OSCILLOSCOPES in like new condition. These units are complete with all standard accessories and instruction manual. The current list price on these scopes is \$1995 - by buying now from TUCKER ELECTRONICS you save \$700 (that's 35%) and get immediate delivery. The HP 1707B is covered by our famous 30 day, unconditional, money-back guarantee and our 90 day parts and labor warranty.

SOME INFORMATION ABOUT TUCKER ELECTRONICS -

Chances are you won't have any warranty problems, but it's reassuring to know that TUCKER ELECTRONICS is the nation's largest supplier of quality reconditioned test equipment. We also distribute 12 lines of new test equipment and also operate the Southwest's largest independent repair and calibration laboratory.

**HOW TO ORDER THE HEWLETT PACKARD
1707B OSCILLOSCOPE -**

It's easy. Just call our toll-free WATS line (800-527-4642) and ask for test equipment sales. Your area salesman will assist you in completing your purchase. He's a good man to know whenever you have test equipment requirements.

TOLL-FREE CALL 800-527-4642



TUCKER

ELECTRONICS • COMPANY

P. O. Box 1050 • Garland, Texas 75040

You CAN Fix It!

The rest of the family is in bed. You sit at the kitchen table soldering the last connections in place. You sigh, a little in relief at completing the project. But it is more in anticipation of seeing results from all the time last weekend and a couple of evenings this week, plus the wad of cash you put into that gadget in front of you.

You check the controls. The power switch is off. You connect the battery and reach for the switch. The moment of truth has arrived. It's time for those assorted parts so carefully assembled to spring to life. SNAP! goes the switch. Then nothing. No gurgles. No blurps. None of the squeals and howls for which hams are so well known. Thank goodness it didn't smoke.

You unplug the battery after turning off the power switch. A quick visual scan for loose wires or a bad solder joint gives no clues. Poking the wiring is just as fruitless. Sigh again. This time it is in disappointment bordering on disgust.

Every builder knows this scene. And engineering technicians report that hobbyists and experimenters do not have a monopoly on it. The simple fact is that few pieces of electronic equipment that have more than six or seven interconnecting parts operate

properly the first time they are turned on. This applies whether they are one-of-a-kind home built gadgets or assembly line produced consumer products. Texas Instruments has a large, well-equipped lab designed for fault detection and analysis in items ranging from single components and circuit boards to finished products. Other manufacturers surely have similar facilities.

If the pros have this problem too, the weekend homebrewer need not berate himself for his stupidity when he throws the power switch and nothing happens. But where does he go from there?

In order to answer that, let's back-track just a little. The builder assumed that he used parts that are in operating condition. As nutty as a bunch of us hams are, it is hard to imagine one intentionally installing defective parts in his own project. If he checked each part on a suitable instrument, his problems are a little different than if he did not test them.

A personal example will illustrate this principle. During the time since the original draft of this paper was written, the writer was asked to check out a transceiver for a friend. When one of the 6146s was found to be shorted, the owner decided it was a good



time to replace them both. New ones were purchased and installed, without being tested. Yep, you guessed it. The rig wouldn't work properly. Before tearing deeper to see if the original defective tube had caused other circuit damage, it was decided to put the tubes on a tester. Sure enough, one of them showed a heater to cathode short. The rig worked fine when two tubes that gave a proper indication on the tester were installed.

It will have to be assumed that each part has been checked before installation.

Step One: Carefully look over the wiring to spot poor connections. If there are none, trace the wiring carefully to be sure it matches that in the schematic of the project. However, if the project is a multi-stage affair, circuit tracing may be deferred until the faulty stage is localized as described below. In any case, circuit tracing is best delayed for at least 24 hours after wiring is completed. This gives the builder a chance to forget some of the details and approach his work with a mind not quite so cluttered with details he is sure are correct.

Step Two: Reread the discussion of "how it works" in the article from which the project was built. A knowledge of the theory behind the hardware will save much fruitless

1/2 KW WIND ELECTRIC GENERATOR



NEW KIT INCLUDES:

BLADES

SPECIAL ALTERNATOR

CONTROL UNIT

FABRICATION INSTRUCTIONS

BASIC KIT AS LOW AS:

\$ 147⁰⁰

STANDARD RESEARCH INCORPORATED

P. O. BOX 1291

EAST LANSING,

MICH. 48823

poking and prodding. It will give meaning to voltage and resistance measurements to be made later. If your project was built from a scrawled schematic supplied by a friend, try to locate something similar in a handbook or the annual index published by most electronics magazines. Time spent in this way not only can save time in the repair, it might also help you answer some of the questions next time you visit Fox Charlie Charlie.

Step Three: Bring out the test equipment. Exactly which instruments are needed depends on the nature of the project.

The homebrewer should have access to the best multimeter he (or his friends) can afford. He will probably choose to own it if he hopes to do a great deal of building his own or servicing of commercial equipment. "The best he can afford" does not necessarily mean buying the most expensive model in the catalog. A friend or ham club may have equipment he can rent or borrow. Digital instruments are nice, but a used volt-ohmmeter picked up at a flea market can often do the same job. It has the added advantage that there are fewer parts inside it

that might need fixing before checking out the latest project.

The following suggestions can serve as a general guide to troubleshooting and give a general feel for the procedure. In this type of presentation, it is not possible to give details required for a specific project.

One of the few things common to all electronic equipment is a power source. Check it to learn if it is producing the needed voltages at its output. To do this, set the range switch of the multimeter to the highest voltage expected. This might be the 10 or 15 volt dc range if a 9 volt battery is used as the power source. It would be the 150 volt dc range or next higher if rectified line voltage is used to supply the power. Connect the negative (-) probe, which is usually a black lead to the negative side of the power supply and the positive (+) to the positive output of the power source. A beginner should do this before turning on the power switch to avoid the shock hazard.

If there is no output voltage or it is quite low, the supply may be faulty or there may be a short in the load causing excessive

current drain. To determine which it is, disconnect the load (with power off, of course) and measure the output voltage in the same manner. A normal voltage will indicate a properly functioning power supply.

An important exception to the last statement is that a stale battery can show full voltage at no load, but drop to practically zero when put under even light loads. Most batteries can be checked by connecting only a thousand Ohm resistor across the terminals and measuring the voltage across it. If that voltage is more than half a volt below the rated voltage of the battery, it is best to replace it. Keep in mind that a short in the load could have caused the demise of the battery, so check before installing a replacement.

In the case of an ac supply with rectifiers, check the line input voltage. To do this set the multimeter on the 150 volt ac range and connect either probe to one side of the transformer primary and the other probe to the remaining primary lead. Then turn on the power. The meter should show a reading between 110 and 120 volts. This procedure

**A new
profit opportunity
for your Retail Store**

Seventy Three Magazine is always on the lookout for new magazine distributors. There are hundreds of retail stores currently selling 73 profitably, both nationally and internationally . . . and these hundreds of stores are just about every type you could imagine, from small to large, electronics stores, radio stores, newsstands, small family-run businesses, etc. etc. All of them are benefitting from our attractive magazine discount and unbeatable returns policy.

You'll find 73 Magazine to be another service feature to your customers that increases store traffic and provides you, the retailer, with a tidy profit. Interested? Send us a note on your letterhead and we'll rush off the materials you'll need to begin ordering 73. It's as simple as that.

Send to:

73

Magazine
Retail Sales Dept.
Peterborough, N.H. 03458
Attn: Kim Huegel, Business Manager

can be skipped if there is a pilot light in the circuit which lights as it should. No voltage indication means there is an open circuit which can be found by resistance checks of the line cord, power switch or solder connections. The most common point where a line cord develops breaks is at the junction of the plug structure and the wire cord. This is particularly true of molded plugs. More than one old-timer has asked this writer to repair equipment with nothing more seriously wrong with it and then asked him not to tell others of the incident.

At the risk of being tedious to those with some experience, a brief explanation of how to make a resistance check seems in order. Set the range switch to low Ohms scale for checking wire continuity. Disconnect all power. Connect either probe to either end of circuit to be tested and the other probe to the other end. The power cord will show a fraction of an Ohm even for many feet of wire. A switch should show zero Ohms, if good, and the primary windings of most power transformers have resistance running as high as 500 Ohms or so. An eight Ohm speaker coil seldom shows more than a

fraction of an Ohm at dc. Low voltage secondary of a transformer, both power and audio output, will show very low readings, usually less than a couple of Ohms. High voltage secondaries usually show several hundred Ohms of resistance. An extremely high Ohms reading in any of these circuits will indicate an open circuit. Transformer windings sometimes open at the point where wire from the outside connects to the smaller internal wire. At today's prices for transformers, it is worthwhile to carefully remove the outer insulation paper to check this point when an open winding is located.

To summarize on resistance measurements, the most important part is to know how to interpret the readings you obtain. This comes only with experience. Therefore, make measurements in operational equipment to gain a knowledge of what you should expect when you are working on malfunctioning equipment. Resistors are easy to measure, because the values are marked on them. On other components, it is worthwhile to make notes on values so they will be available for comparison at a later time.

Continued

CLOCK CASE

If you're into electronic kits — you're into clocks. Put the finishing touch on your clock with our beautifully designed solid walnut case. Styled to enhance any decor, this case comes with glare free Polaroid® filter installed.

D & N Gifts by Mail offers exceptional value and the finest quality. Display that clock you worked so hard to build in a case designed to give that professional look.


Postage pre-paid order shipped same day received.

15.95

D & N Gifts By Mail

P.O. Box 28502

Dallas, Texas 75228

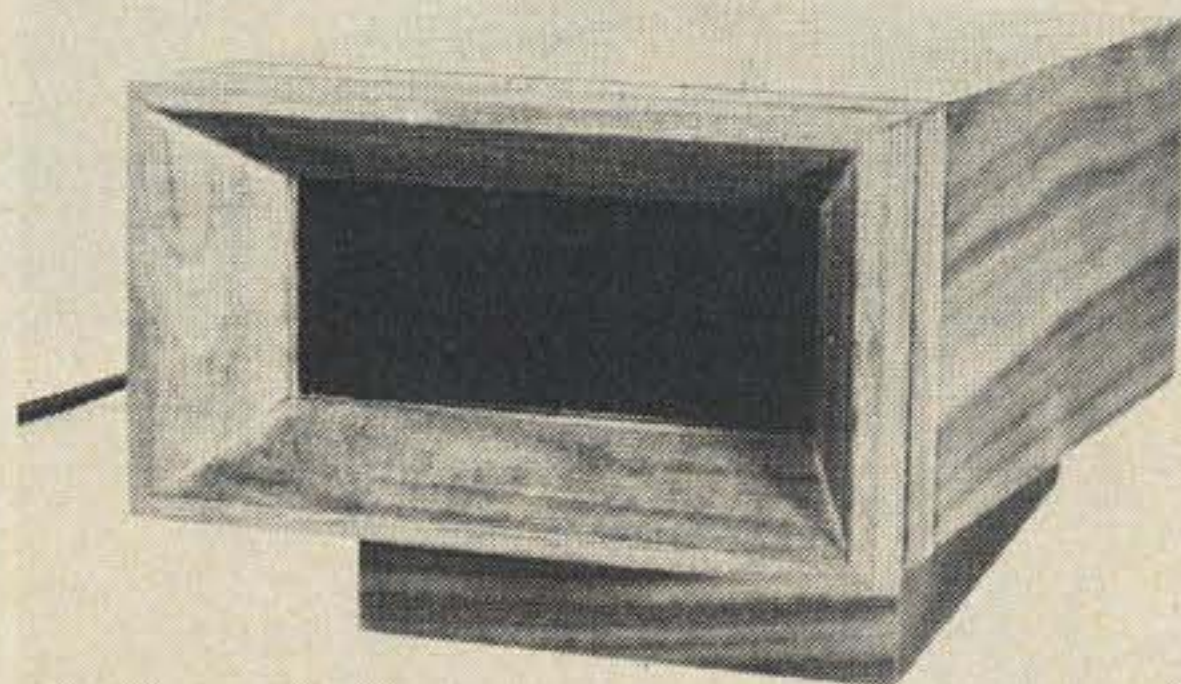

CFP ENTERPRISES IS MOVING

New facilities, new hours, and getting Jim Beckett (WA2KTJ) back all adds up to improved service for you! We expect to open our doors at the new store on Sept. 2!

607-533-4297 607-739-0187

CFP Communications

Division of CFP ENTERPRISES

211 N. Main St., Horseheads NY 14845

DELUXE QSL ALBUM Excellent for WAS + DXCC

These fine quality imported albums have following features:

- Provide maximum protection for treasured QSL cards
- Luxurious padded vinyl binder with index window
- Snap fastener mechanism
- 50 clear plastic pockets with black leaves holding up to 100 cards back-to-back
- Choice of 5 colors - black, blue, green, red, tan



No. 2 for most foreign cards

\$5.95 pp

No. 3 for all U.S. cards

\$5.45 pp

Out of US add 10% NYS add tax

SATISFACTION GUARANTEED OR MONEY REFUNDED

WA2UGO

P.O. Box 1189-Poughkeepsie, N.Y. 12602

KRP Open Wednesday Nights 'til 11 PM 200 MHz freq. counter kit

Range 60 cycles to 200 MHz. Sensitivity less than 100 MV. 50 ohm 8 digit LED readout boards, all parts except case. Complete kit - Bezel sockets etc. \$140.00 All TTL logic

ELECTRONIC SUPERMART, INC.

219 West Sunrise Highway, Freeport, LI, NY 11520, 516-623-3346-9

PARTS! CORNELL TUBES!

FREE Send For FREE

**CORNELL'S
New Color
Catalog**

48 Pgs. New Items

CORNELL

33¢ per tube

IN LOTS OF 100

36¢ per tube

ORDER FREE
IF NOT SHIPPED
IN 24 HOURS!

4215 S University Ave. San Diego, Calif. 92105

PL-259

SO-239

Either Plugs OR Sockets

5 for **\$3.50**

POST-PAID

N.J. residents add 18c Sales Tax

Send SASE for other Connectors.

COAKIT

P.O. Box 101-A, Dumont, N. J. 07628

Now back to power supply measurements. When a proper ac voltage is obtained at the primary input, the next step is to go to the various secondary outputs. Set up the meter for a full scale range slightly higher than you expect to read, connect the probes to the pair of wires coming from the winding, apply power, and note the reading on the meter. If there is none, check for open circuits. If it is too low, disconnect the load and check the voltage again. Check all secondary windings in this way. Lighted tube heaters or pilot light on a particular secondary show it is working, so don't bother measuring it.

Once you are sure the proper voltage is being produced by the power source, other parts of the circuit can be checked. However, if the output voltage is too low, it may be caused by a part of the load drawing too much current. Since most projects have several branches of the dc line, a logical procedure is to disconnect them one at a time, apply power with meter connected to read dc voltage at output of power source, and note if the voltage rises to normal. When it does with one branch disconnected, that branch should be checked for wiring errors or defective parts. This approach will save much time in comparison to tracing the wiring in the entire project.

Although the foregoing explanations are somewhat cumbersome, the tests, with exception of the previous paragraph, can be performed in less time than it takes to read about them. Experience has shown that these simple measures can put about 75 percent of home built projects into operation when no defective components have been installed. Another 20 percent require signal tracing or injection which will be discussed in a future article. Most of the remainder have a component damaged when power is switched on because of a wiring error.

In conclusion, do not be afraid to tackle the chore of finding where the problem lies in that newly built project. If you had knowledge enough to put it together, there is a good chance you can make it operate, even if it failed the smoke test.

... WØHMK

ICOM

IC-21A



Program any frequency you want... any frequency split you desire.
Scan... active or inactive frequencies... adjustable scan rate.
LED Digital readout on transmit and receive.
The ICOM IC-21A and the DV-21... a truly advanced and unique package well ahead of its time.

\$838.95

ICOM

IC-230



VHF FM PHASE LOCKED LOOP SYNTHESIZED TRANSCEIVER
PUT OVER 67 CHANNELS IN THE PALMS OF YOUR HANDS FOR JUST **\$489.00**

\$100.00 FREE MERCHANDISE
with purchases over \$800.00

\$50.00 FREE MERCHANDISE
with purchases over \$400.00

\$25.00 FREE MERCHANDISE
with purchases over \$200.00

SPECIAL LIMITED QUANTITY VARITRONIC'S AS-2HG

5/8 2 METER GROUND PLANE
3.5 db GAIN

\$22⁹⁵

ICOM **IC-22A**



10W in - 70W out

22 CHANNEL
2-METER FM
10 WATTS


ONLY \$249.00

READY TO GO ON:
1 94/94
2 34/94
3 22/82
4 28/88
5 52/52

REGULATED POWER SUPPLY

4 AMP
6 AMP MAXIMUM

\$49⁹⁵

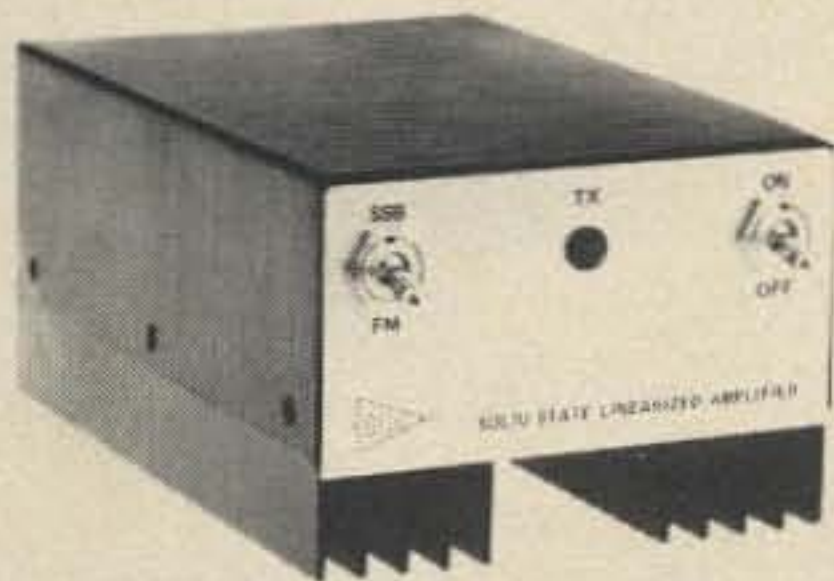

\$139.95
2 M10 - 70 L

2 METER AMPLIFIERS

1 WATT = 25 WATTS OUTPUT

THE GROWING LINE OF SCS AMPLIFIERS INCLUDE THESE NO COMPROMISE FEATURES:

Completely Solid State Broadband Design Requires No Retuning
Across Band Selectable Biasing For:
Class C-High Power FM at Peak Efficiency
Class AB-Linear for SSB or Low Power FM
Increased T-R Delay for SSB/CW Operation. Fully VSWR and Reverse Voltage Protected. One Year Warranty on Entire Amplifier. Under One DB Insertion Loss in Receive.



TOUCH TONE PAD
\$34.95

VEGA BEEP BOX

12 Button Tel Touch
Self-Contained Battery. Audible Coupled. No Wiring.



\$49.95 Kit
\$69.95 Assembled

AN AMPLIFIER FOR YOUR HAND-HELD

Carrier Operated Relay Can Be Driven From 180 mw. No Tuning. Output Short Circuit Protected. Easy to Install & Operate.



SCANNING MONITORS
\$139.95

Powerful, Crisp, Clear Speaker Performance!
Bearcat Scans 25-Channels-Per-Second... fewer missed signals! Built-in 12-Volt DC/117-Volt AC Power Capability! Made in Cumberland, Indiana, U.S.A.

VEGAS RADIO

1108 SO. 3rd STREET • LAS VEGAS, NEVADA 89101
Call or Write: Norm, W7IUC 702-382-4305

ORDER UNDER \$100 ADD \$2.50 FOR SHIPPING & HANDLING... NEVADA RESIDENTS ADD SALES TAX

Precision +10.000 V dc Voltage Reference Standard

This article describes a simple, easy to build dc voltage reference standard whose temperature coefficient (tempco) can be tailored to the ham's individual requirements. It can be used by itself or as an individual circuit element.

Design Considerations (see Fig. 1)

The circuit described uses an operational amplifier in a non-inverting circuit utilizing a single positive supply. The output of the reference standard supplies the zener reference diode current, providing a stable supply voltage for the zener and de-coupling from the positive supply voltage. The positive supply voltage should be regulated by either a three-terminal regulator or zener diode and should be from +15 to +18 volts.

Temperature stability is expressed in $\%/^{\circ}\text{C}$ or ppm (parts per million)/ $^{\circ}\text{C}$. (.0001 $\%/^{\circ}\text{C}$ is equivalent to 1 ppm/ $^{\circ}\text{C}$.) A 1 ppm/ $^{\circ}\text{C}$ change referred to an output of 10.000 volts is 10 $\mu\text{V}/^{\circ}\text{C}$. Both terms, $\%/^{\circ}\text{C}$ and ppm/ $^{\circ}\text{C}$, will be referred to in this article.

The zener reference diode, CR1, should not be confused with the more common zener regulator diode. The zener reference diode is intended for use in applications where it is important to maintain stable dc voltages under severe combinations of temperature, shock and vibration. The temperature stability of the zener reference diode is due in part to the combination use of reverse-biased and forward-biased silicon p-n

junctions, taking advantage of their opposing tempco characteristics. Application notes and design data sheets are available from the larger suppliers of zener reference diodes (e.g. Motorola, Dickson, Centralab) and are invaluable as reference material.

The 1N821 through 1N829 family of zener reference diodes is used for CR1. The diodes in this family exhibit tempcos from .01 $\%/^{\circ}\text{C}$ (1N821) to .0005 $\%/^{\circ}\text{C}$ (1N829) at a nominal zener current of 7.5 mA. The nominal zener voltage is 6.2 V $\pm 5\%$. R1, which sets the nominal zener current (7.5 mA in this case), should be a 100 ppm/ $^{\circ}\text{C}$ metal film resistor. Other families of zener reference diodes can be used, such as the 1N4565 through 1N4584, with a corresponding change in nominal voltage and current.

As a general rule, the gain resistors used in the reference standard should have tempcos similar to the zener reference diode selected. For example, if the 1N821 is selected, gain resistors R2 and R3 should have tempcos of .01 $\%/^{\circ}\text{C}$ (100 ppm/ $^{\circ}\text{C}$).

The overall tempco of the reference standard is dependent upon the tempcos of the reference zener CR1, gain resistors R2 and R3, and to some extent, the zener current resistor R1 (providing it has a 100 ppm/ $^{\circ}\text{C}$ tempco) and A1.

The gain required of the circuit is dependent upon the zener voltage. The nominal voltage of the 1N821 is 6.2 V, necessitating a gain of 1.613 for an output of +10.000

volts. The total resistance of R2 and R3 should be 5k to 10k, limiting the current through the gain resistors to from 1 mA to 2 mA.


If R1 is a 100 ppm/°C as suggested, here is an easy way to estimate the overall tempco of the completed reference standard: 1) Write down the tempcos of CR1, R2 and R3 in ppm/°C; 2) Square each one that you have written down; 3) Add the squares of R2 and R3 together, dividing the answer by seven; 4) Add the square of CR1 and the answer of step 3; and 5) Find the square root of the answer in step 4. Step 5 will be the approximate overall tempco of the reference standard in ppm/°C. This will give you a good idea if the components you have selected fit your tempco requirements. If CR1, R2, and R3 have the same tempco, just multiply the tempco of *one* of them by 1.1 to determine the overall tempco of the reference standard. The reason for the division by seven in step 3 is that the tempco of R2 and R3 is reduced a factor of approximately 2.7 (depending on the gain) by the low gain of the amplifier.

The output of the reference standard can be trimmed to +10.000 volts by paralleling a resistor across R2 and/or R3 as required. Tempco of the gain trim resistors, R4 and R5, is critical, and should not alter the tempco of the gain resistors. For example, if R2 was a 6.04k 25 ppm/°C resistor and a 62k ½ Watt carbon resistor was paralleled across it having a 1000 ppm/°C tempco (typical tempco of carbon resistors), the result would be the same as using a 5.5k 100 ppm/°C resistor. The effective tempco of the trim resistor in this case would be 1/10 its real tempco. A 620k ½ Watt carbon, in the same example, would have an effective tempco of 1/100 or 10 ppm/°C, and a 6.2 megohm would have an effective tempco of 1/1000 or 1 ppm/°C. Some discretion must be used when selecting the value and tempco of the trim resistors.

Practical Design

The next step is to build a working reference standard. The following components were selected for a reference standard having a calculated tempco of 22 ppm/°C and a measured tempco of 17

ppm/°C after assembly. An LM301A operational amplifier was selected for A1. The LM301A will supply approximately 20 mA and has a typical tempco of 1 ppm/°C. A 1N825 reference zener was selected for CR1 which has a 20 ppm/°C tempco and a nominal voltage of 6.2 volts at 7.5 mA. An RN55 100 ppm/°C 511 Ohm metal film resistor was selected for R1. The actual reference zener voltage at 7.5 mA measured 6.286 volts, necessitating a gain of 1.591 for +10.000 volts output. For a gain of 1.591, an RN55E 25 ppm/°C 6.04k metal film resistor was selected for R2 and an RN55E 25 ppm/°C 3.57k metal film selected for R3. A ½ Watt 2.2k 5% carbon resistor was

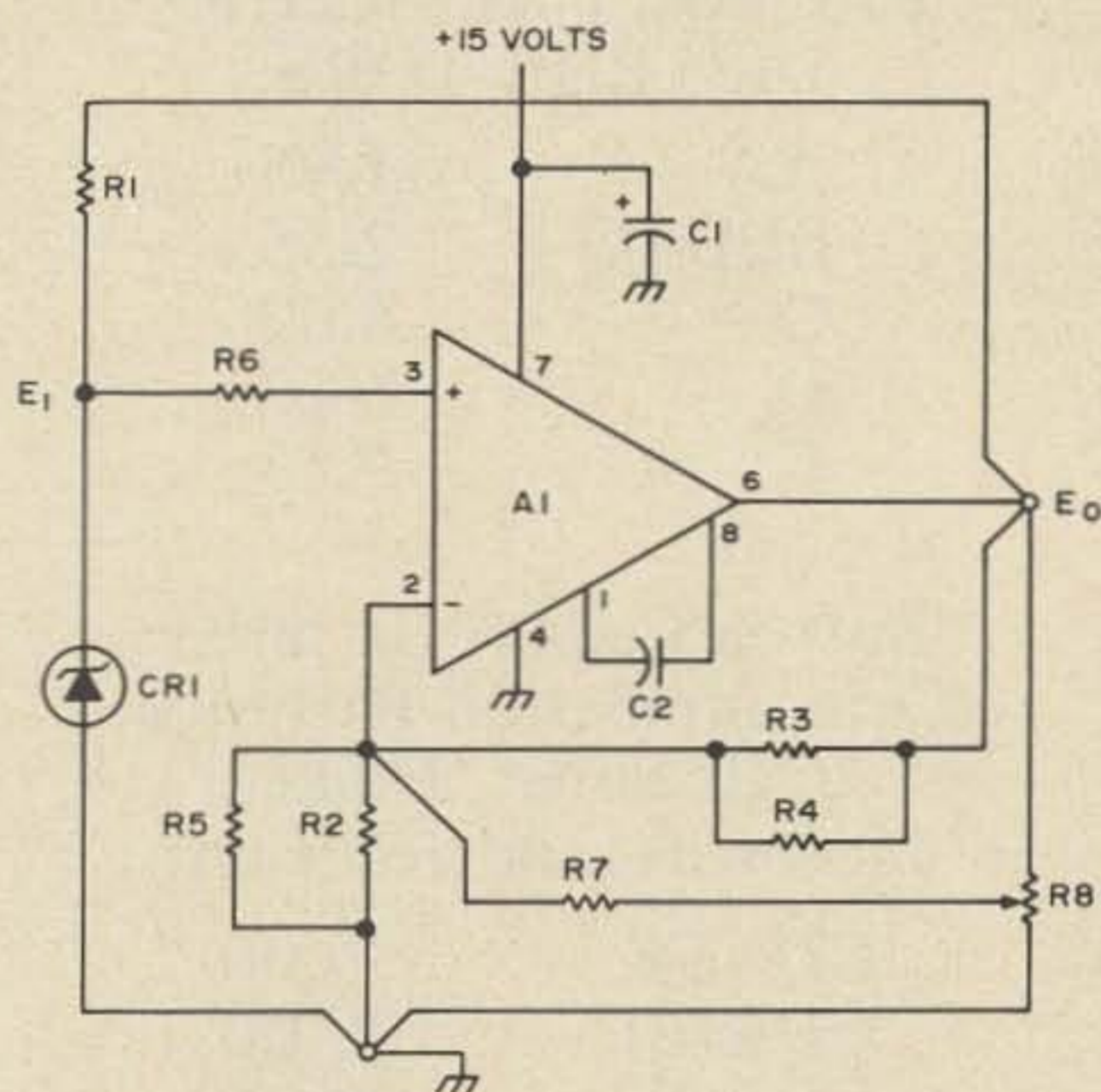

$$\text{Gain} = \frac{R2 + R3}{R2}$$

$$E_0 = E_1 \frac{R2 + R3}{R2}$$

- A1 — LM301A Operational Amplifier
- C1 — 1 mF electrolytic capacitor, 25 W V dc
- C2 — 30 pF ceramic disc capacitor
- CR1 — Reference zener diode, 1N821 family
- R1 — 100 ppm/°C metal film resistor (Select value for the nominal current of CR1.)
- R2,R3 — Gain resistors (Select for desired tempco.)
- R4,R5 — Gain trim resistors
- R6 — ½ Watt resistor (Value should be the parallel equivalent of R2 and R3.)
- R7* — Optional +10.000 volt trim resistor for use with R8 (Value can be 100k to 1 megohm, 5-10 ppm/°C.)
- R8* — 10k 89PR cermet pot or equivalent optional +10.000 adjust.

*with a 100k resistor at R7, the output can be adjusted about 10% if the sum of R2 and R3 is 10k. 1 megohm will provide about 1%.

Fig. 1. Voltage reference standard schematic.

GOULD NICAD®

RECHARGEABLE BATTERIES

FACTORY STOCKING DISTRIBUTORS

AA -	\$1.95
SUB-C -	2.55
C -	4.02
D -	6.13
F -	9.53

Button Cells & Batteries
Communication Batteries
to fit Sonar, Drake,
Motorola, and Johnson:

CD-64 -	39.00
CD6761 -	39.00
CD6682 -	30.90

GELYTE/LEAD - ACID BATTERY CHARGERS

We carry a full line of tools, tubes,
transistors and accessories.

WELLER * UNGAR * XCELITE
KLEIN * G.E. TUBES * MOT. HEP.

Minimum billing \$10.00.

*Shipping charges and sales tax where
applicable. Prices subject to change
without notice.*

ADVANCE Electronics

54 WEST 45th STREET
NEW YORK, N.Y. 10036

TEL: 212-687-2224 212-687-0720

selected for R6. After assembly, R3 had to be trimmed for an output of +10.000 volts.

The most difficult task after assembly for the average ham will be finding access to a 4 or 5 digit digital voltmeter so that the reference standard output can be trimmed to +10.000 volts. No special equipment is required up to the trimming operation. The accuracy of the reference standard will be as good as the equipment used to trim it.

Conclusion

It has been demonstrated that a precision reference standard can be constructed by utilizing available reference zener diodes and suitable gain resistors. This article was written primarily as a tool to enable some of those interested in acquiring a stable dc source to design their own. Different output voltages can be obtained by either changing the gain of the amplifier or adding a voltage divider across the output of the reference standard (current cannot be supplied in this mode). Layout is not critical, cost is minimal, and performance can be determined to some extent before assembly.

...WA6VVL

WANNA WORK MORE DX ?

Subscribe to THE WORLDS ONLY weekly DX Magazine. Strictly DX news in depth. I give you upcoming events, dates, times, freqs, DX QSL info, contest info, DX articles, etc. SUBSCRIBE NOW and WORK 'EM ALL ! DX NEWS GALORE ! \$ 6.00 for 6 mo. or \$ 12. per yr to W/K, VE, XE, First Class mail. THE DXERS MAGAZINE, (W4BPD), Drawer "DX", CORDOVA, S.C. 29039. DXING IS GREAT USING OUR INFO !


WORLD QSL BUREAU

5200 Panama Ave., Richmond CA USA 94804

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next county, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 6¢ each.

CMOS KEYER

ASSEMBLED PCB
\$24.95 ppd

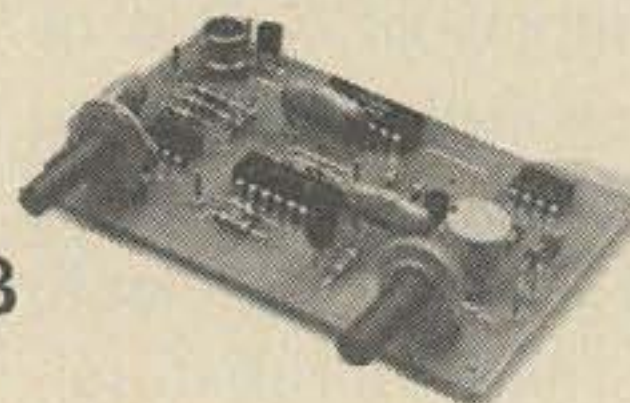

- *SELF-COMPLETING DOTS AND DASHES
- *INSTANT START WITH JAM PROOF SPACING
- *BUILT-IN SIDETONE
- *5-50 WPM
- *OPERATES ON 5-12 Vdc
- *FOR GRID-BLOCK AND CATHODE KEYING
- *SIZE: 2.3 x 3.5 INCHES

(WI residents add 4% sales tax)

DGM ELECTRONICS
787 Briar Lane, Beloit, WI. 53511

Building a 135 kHz i-f Strip

This article describes the use of the second surface of a baseboard for a 135 kHz i-f strip. I used the first side for the converter, 1.65 MHz to 135 kHz mixer, and the 1.785 MHz oscillator, which left the other side bare and ready for mounting the 135 kHz strip.

The first thing to do is the construction of the two terminal strips with their .021 diameter pins to hold the various components in place, such as the resistor tie points, capacitors, three pins for each transistor, interstage coupling capacitors, 12V bus, etc.

Fig. 1 shows placement details of these pins on the $3\frac{3}{4} \times \frac{1}{4}$ in. fiberglass strips which are .035 thick. As in my converter strip, 1/8W or 1/10W was used for resistors throughout, and small 10 mF electrolytics are also a must. There are two components

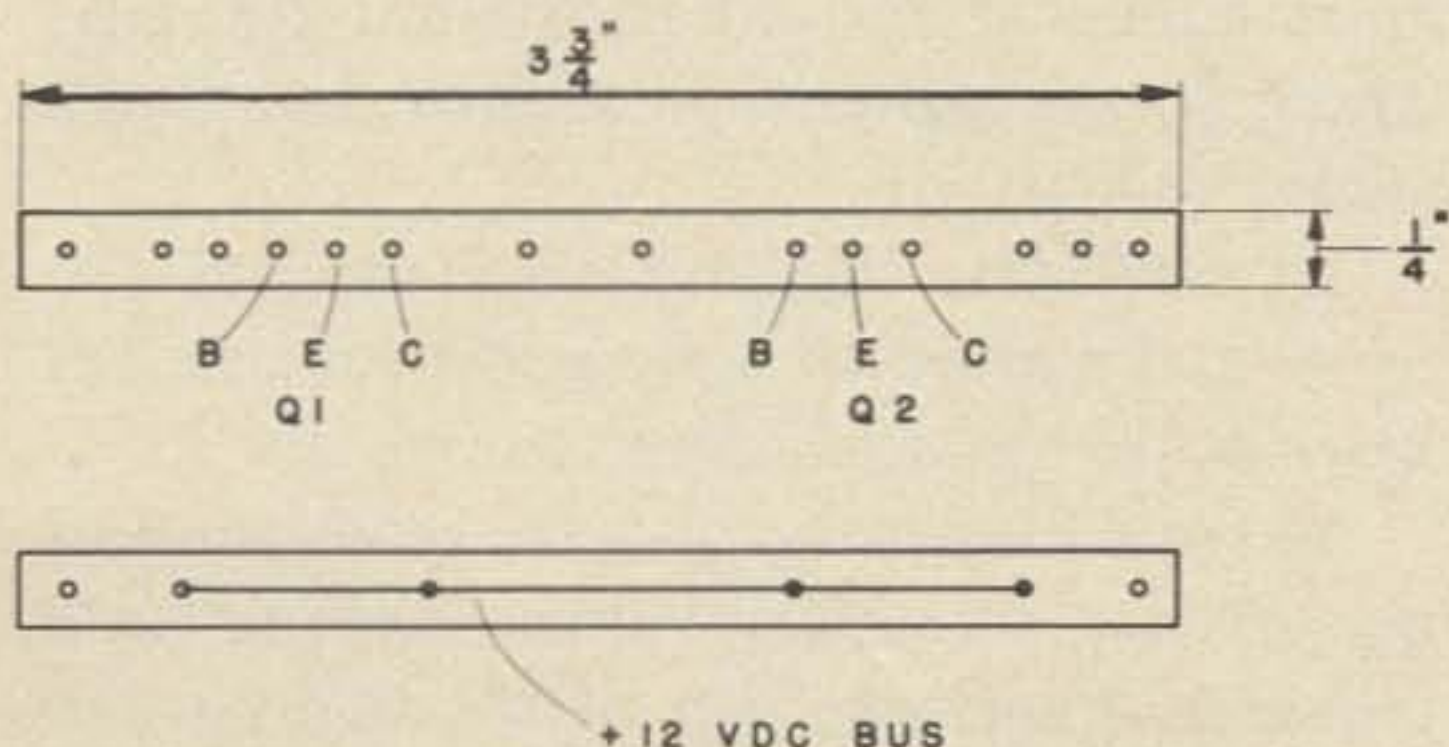


Fig. 1. Terminal pin layout.

which are still fairly large, the 135 kHz inductors and the mica compression trimmers, but even when these are mounted there is still lots of space available, as you can see in Figs. 5 and 6.

Be sure to use the narrow type trimmers which are only $\frac{3}{8}$ in. wide but still have 700 pF maximum capacity, which are the kind of values you need down at 135 kHz. As you can see, the 12V bus is interrupted at one end for the avc line, and on the other end has a 100Ω resistor for dc battery supply purposes.

The top line of terminals works out nicely with, from left to right, "S" meter connection, input to the base capacitor, base, emitter and connector pins, collector bus, interstage capacitor, second stage B, E, and C pins, diode one, and the output capacitor. Three more pins were needed for the avc diode and its associated avc components.

The HEP 55 Transistor

Practically in the middle of building and


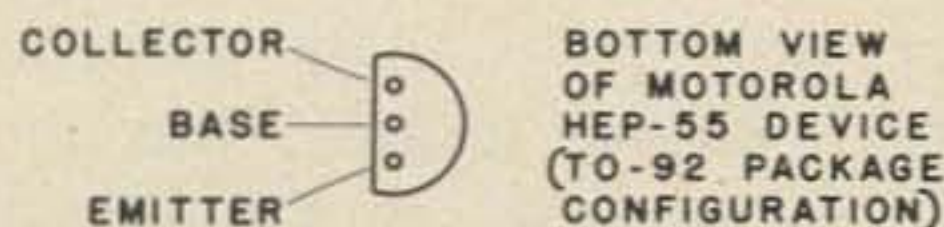


Fig. 2. HEP 55 pin connections.

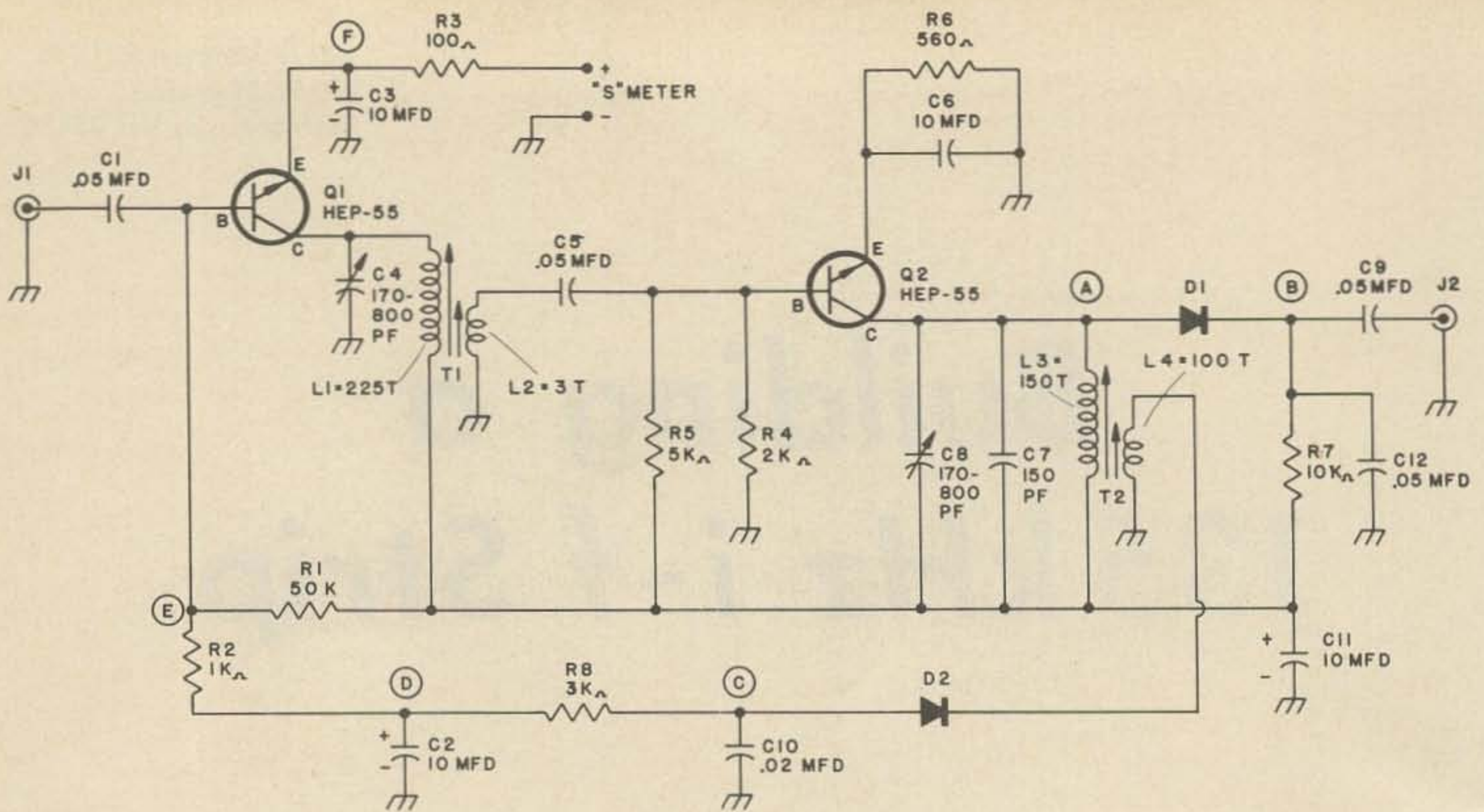

NOTE: ENCIRCLED LETTERS DESIGNATE TEST POINTS

Fig. 3. 135 kHz i-f circuit.

testing this unit I received a shipment of goodies from Motorola. There were a bunch of HEP 55s in the box, and these look like the answer for use in all the stages between (and including) 135 kHz up to two meters.

I tried one (HEP 55) right away in the 135 kHz strip against a 918 and the increased gain showed up quickly.

Tubes used to have a fairly simple parameter called "Gm," or transconductance, which gave a pretty good idea of what the tube would do, at least on lower frequencies, with other things being equal. There are, to start with, some 100 symbols in fairly current usage for transistor parameters, but fortunately there is one that helps a lot as a preliminary indication, again on the lower frequencies. It is known as *beta*, using the common emitter circuit, and is simply the ratio of the change in output current to the change in input current that caused it. In an HEP 55 for example, a one microampere change in the input can become a 350 uA change in the output. This therefore is a hot device! Testing a number of them against 918s, 3600s, and various others, the HEP 55 simply amplifies more at 135 kHz. Don't get me wrong about the 918s, though: They are of course made for UHF work

and the HEP 55 is listed for use up into VHF only.

The HEP 55 is good for 200 MHz, which is listed as Ft, the cutoff frequency, and so is good for nine stages in the 432er. These are the two at 135 kHz, mixer, oscillator, two i-f stages at 1.65 MHz, and the rf, mixer and oscillator of the tunable i-f at 28 to 30 MHz, otherwise known as the ten-meter-receiver section.

The terminal arrangement is not exactly ideal, but is satisfactory when mounted as in Fig. 2. It does have some good features for sure. For example, the base-emitter voltage is listed as five, which is better than the 918s which only can take three volts. Don't forget, almost any transistor can burn out a following one of the same type, so step down that impedance!

The dissipation of the 55 is 310 mW, which is alright in the receiver. The maximum collector current is listed at 200 mA, which seems higher than needed, but that's Motorola's affair.

At 200 MHz the beta is still around 250 or so and should thus be good for receiver work up to and including two meters.

As you know, if you have read many of my articles, I've always been looking for a universal transistor, out of the many thousands available, that can be used in almost every receiver stage up to two meters. This

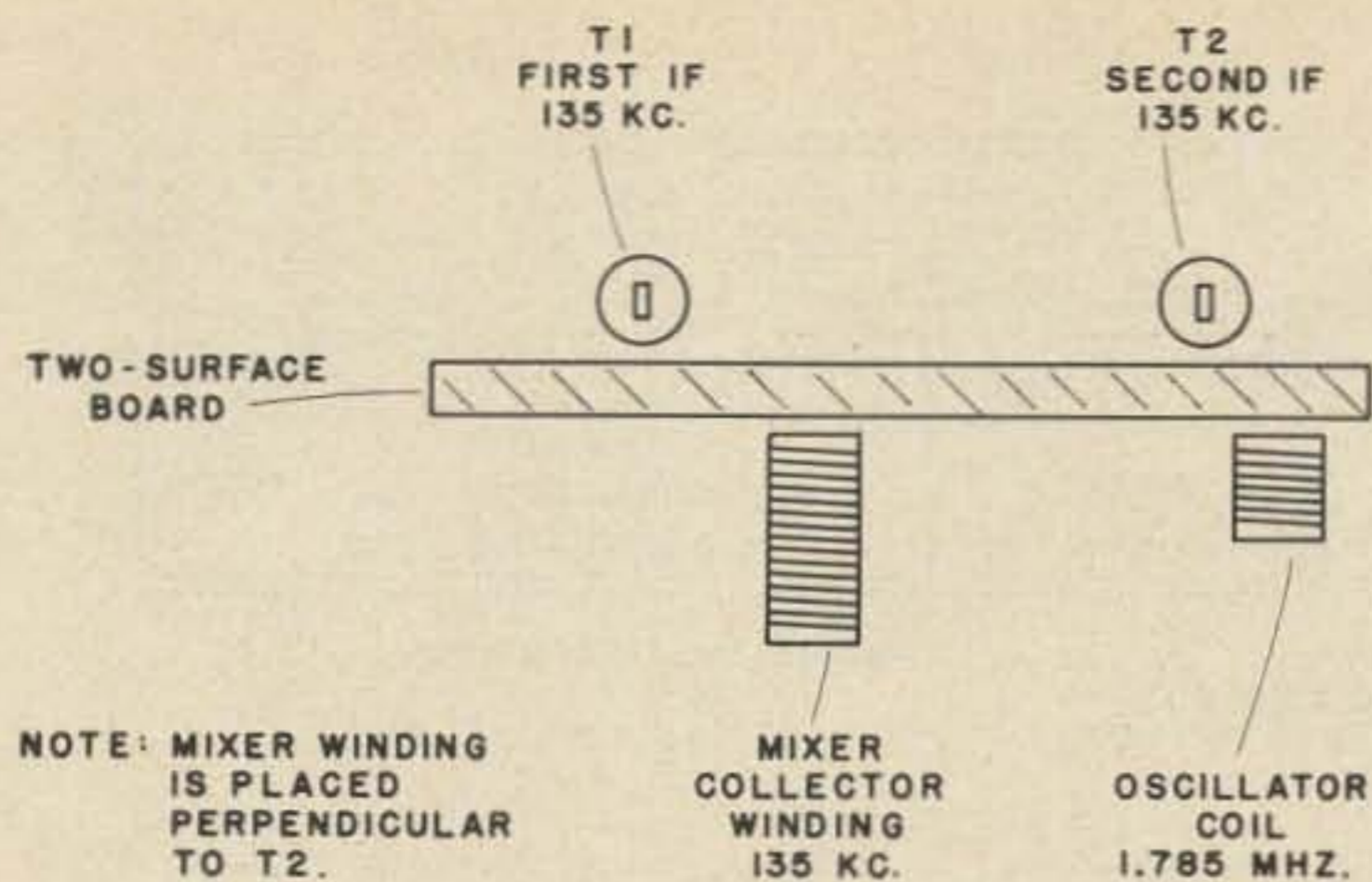


Fig. 4. Magnetic feedback prevention details.

does not include the low-noise rf stage or stages, for which you will have to pay a little more at present.

If further tests hold up, the HEP 55 may just be this universal device.

If you're going to de-breadboard a circuit and minibox it, go ahead, but *copy*, don't *change*! I did (change) and it cost me two extra days of hard work. I don't mind the time if you can profit by it, so here goes.

The final circuit is shown in Fig. 3, which looks almost like the one in my breadboard unit. It was supposed to be the same, but as soon as I turned it on — zilch! Insufficient avc action with af diode blocking on any signal over an S5. After hours of checking for proper avc voltage, milliamps of current with the signal generator on and off, I dismantled the original breadboard 135 kHz i-f and checked it for overloading. None — it was perfect. Alright, just what had I done, or changed?

After checking capacitors and resistors, diodes 1 and 2 were replaced. Still nothing. What remained? I had put in two of the higher gain HEP 55 devices for Q1 and Q2, so they were replaced with the original 918s. Still nothing. There remained only the "new" winding of 225 turns instead of the original 150. And that was it! As soon as I wound up another T2 using the original 150 turns, with 100 turns in the avc diode secondary for good measure instead of 80, bang, good avc again. Current in Q1, the avc controlled device, dropped to 10 uA with a good signal at the input.

So, once again, *don't* make changes when reducing the size, unless you're ready to do more experimentation, maybe several days of it, because the smaller you get the harder it is to change components.

More Avc Details

"Out of evil comes good," it says in the Good Book, so sure enough, while on the blocked avc trouble I was able to improve the avc circuit. Checking the circuit in Fig. 3, you will see R8 feeding the avc line. When only one diode is used for both af and avc, this resistor cannot be very small, but when a separate diode D2 is used, R8 can be of any value you want because it now serves just as a filter in the line and does not have to isolate the line from the af channel. The smaller you make it the more avc action you will have. You can see the balance needed between R8 and R1, the 50k resistor feeding plus voltage to the base of Q1. If you want more, or less, avc action with this circuit, you can juggle the values of these two resistors, R8 and R1.

The lower impedance of L1 with 150 turns instead of 225 also gives a better match for Q2 making it more of a current driver into D2.

Table 1 shows representative voltage readings at significant test points for avc action. Readings at these points will vary somewhat depending on your voltmeter, transistors, etc. I used a small VOM but of course a VTVM would be better.

The Final Circuit

Every value given in Fig. 7 is exactly as in the working model which is completely

Point	To Point	Volts	
		Sig. Off	Sig. On
A	B	0	about 1V
C	GND	+ .2	-.5
D	GND	+ .9	+ .3
E	GND	+ 1V	+ .5
F	GND	+ .5	close to zero volts.

Table 1. Avc voltage test points. Note: Signal "On" was the "Low" output from a Lafayette signal generator, output control full "On," through a 100:1 resistor attenuator, home brewed, frequency 1.65 MHz. No tuned circuit was used at 1.65 MHz — just a direct cable connection to C1.

enclosed in the 4 x 2 minibox and working well.

An output link on the 1.65 MHz to 135 kHz mixer comes through C1 to the base of Q1, an HEP 55 Motorola NPN. Base bias is obtained as detailed in the avc section above, with emitter current going out to the "S" meter on a pair of red and black flexible wires.

The secondary of T1 was changed to 3 turns to drop the gain a little and provide more selectivity.

The circuit of Q2 is almost identical to the breadboard one, with another HEP 55 being used. The avc secondary of T2 is now 100 turns instead of 80, to provide more avc action, and R7 is lower for the same reason. The idling current of Q1 is about 5 mils, dropping to as low as 10 uA on almost any good signal. Needless to say, there is plenty of af out of J2.

Figure 4 shows the final placement of the mixer collector winding in relation to the collector winding of the first stage i-f, T1. Note that Q1 has its collector in T1 and its base in the mixer winding. If any coupling is present between these two it could provide a feedback path and oscillate. It did!

The magnetic field went right through the copper baseboard (naturally enough) just as though it weren't there, and Q1 made like an oscillator. Adding four small pieces of flexible wire (you can do this at 135 kHz but *not* at VHF) to allow moving the coil around, it was rotated in several planes. Sure enough, when parallel to L1 it produced nice, clean (but unwanted) oscillation. When mounted perpendicular to L1 as in Fig. 4, no feedback and no oscillation.

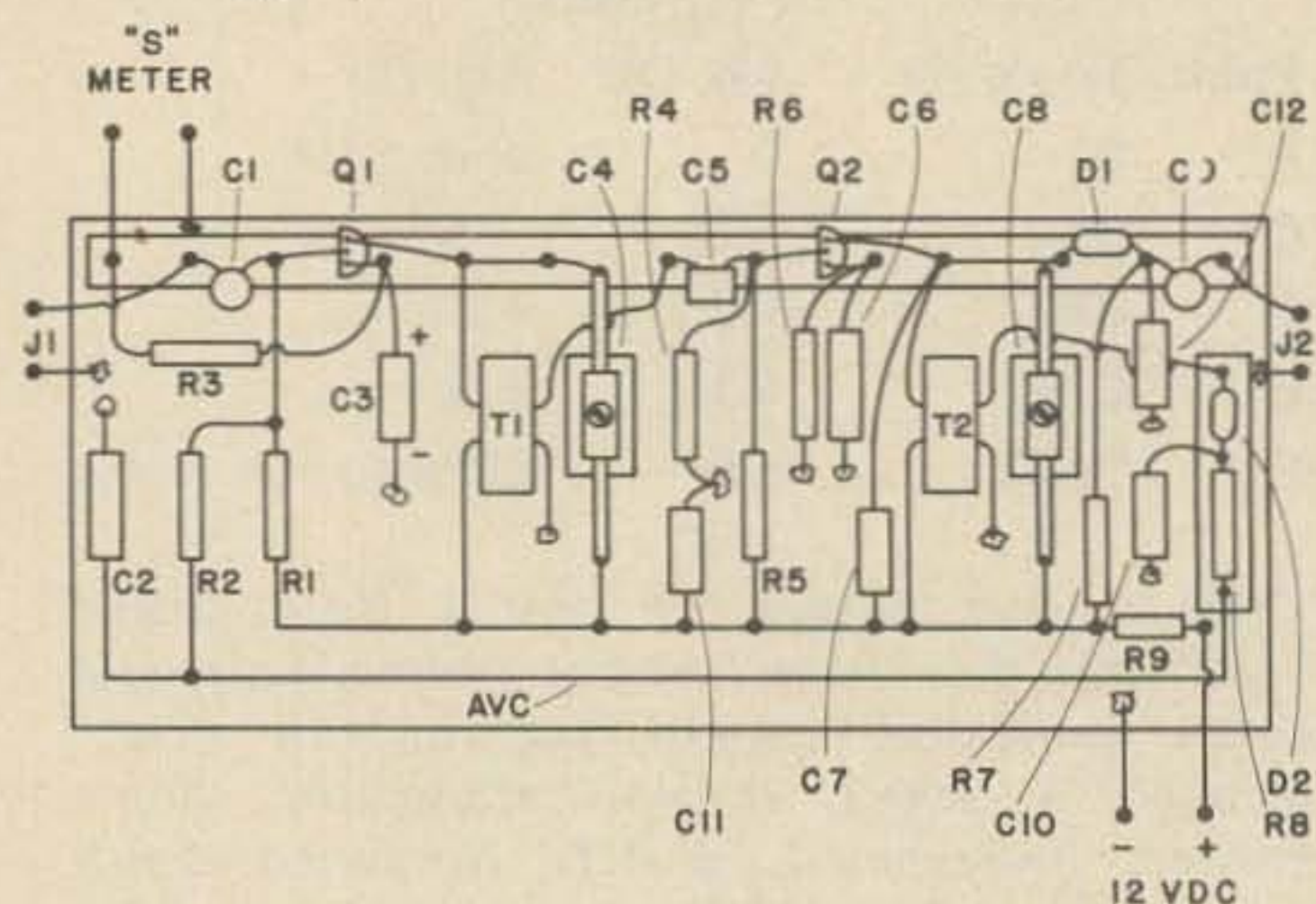


Fig. 5. Layout of the 135 kHz i-f strip.

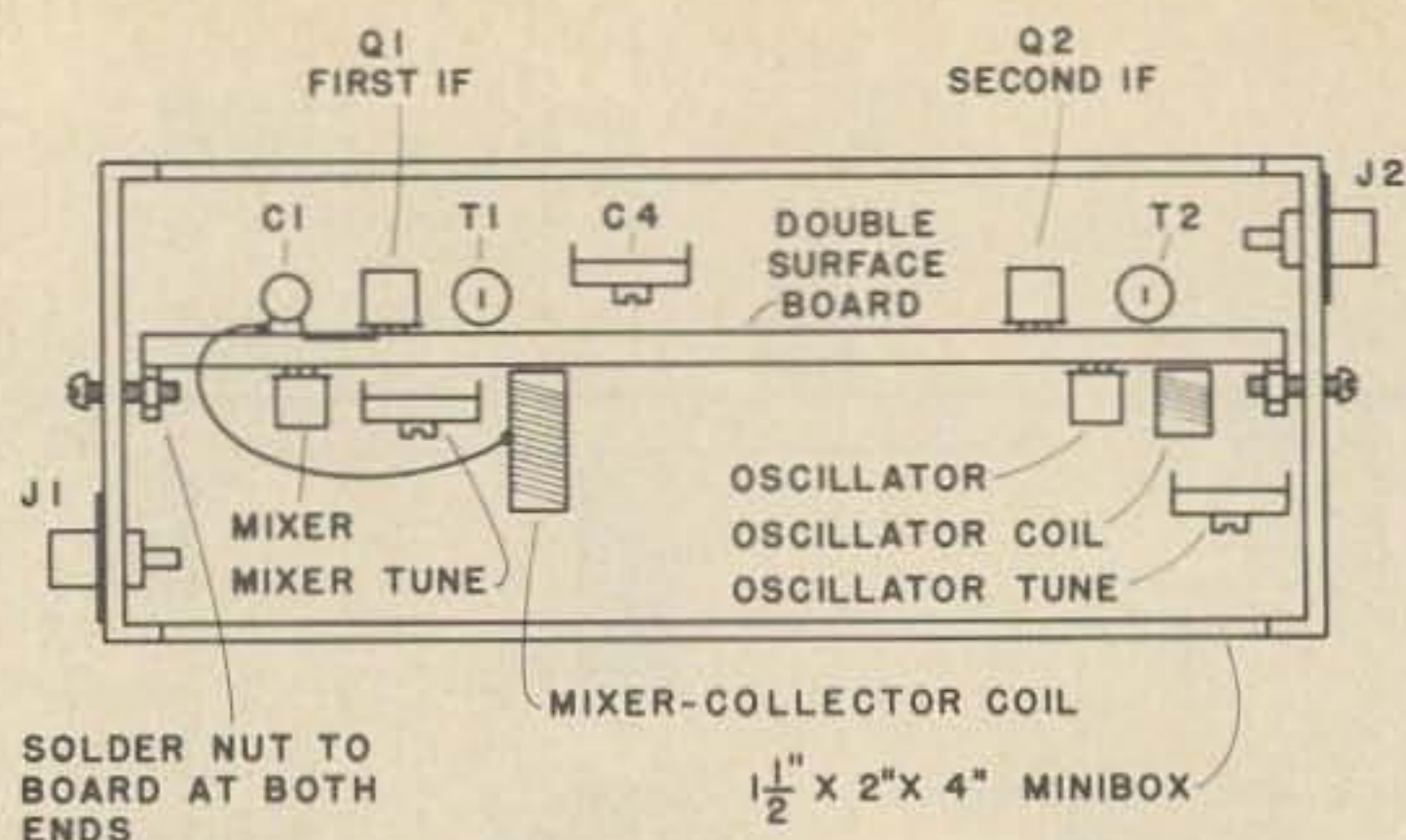


Fig. 6. Installation in a minibox, top view with cover off.

The Layout

Figure 5 shows the various components and how they are fitted onto the $3\frac{3}{4} \times 1\frac{1}{2}$ in. second surface of the baseboard. I clamped the board bare side up in a drill vise and proceeded with the entire assembly and tuneup on 135 kHz. I then brought just one wire over from the mixer transformer to Q1, and the 12V to the bus, and the two sides were in action together.

Looking onto this 135 kHz strip, you can see in Fig. 4 that there is still plenty of room left and so far nothing is covered up, with all the components in plain view. As mentioned, the transformers and trimmer capacitors loom rather large among the 1/10th watters and transistors, but I still can't believe the amount of empty space in that little box, even when I'm looking right at it.


Tuning Up

Referring to Fig. 3, the final circuit, the interstage transformer T1 tuned quite well over the range of 130 to 150 kHz with the mica trimmer C4, 170 to 600 pF. This inductor plus the mixer collector coil determines the 135 kHz center of the narrowband i-f. T2 is fairly broad with its close coupling to the af diode and also to the avc diode now with the 100 turn secondary. Both af demodulation and avc action are aided by this close coupling, so the sharp selectivity is left to the first two transformers.

With quite a bit more work and winding time you could add more tuned circuits, but this whole triple conversion receiver is enough of a project for now.

Mobile Amplifiers With Versatility

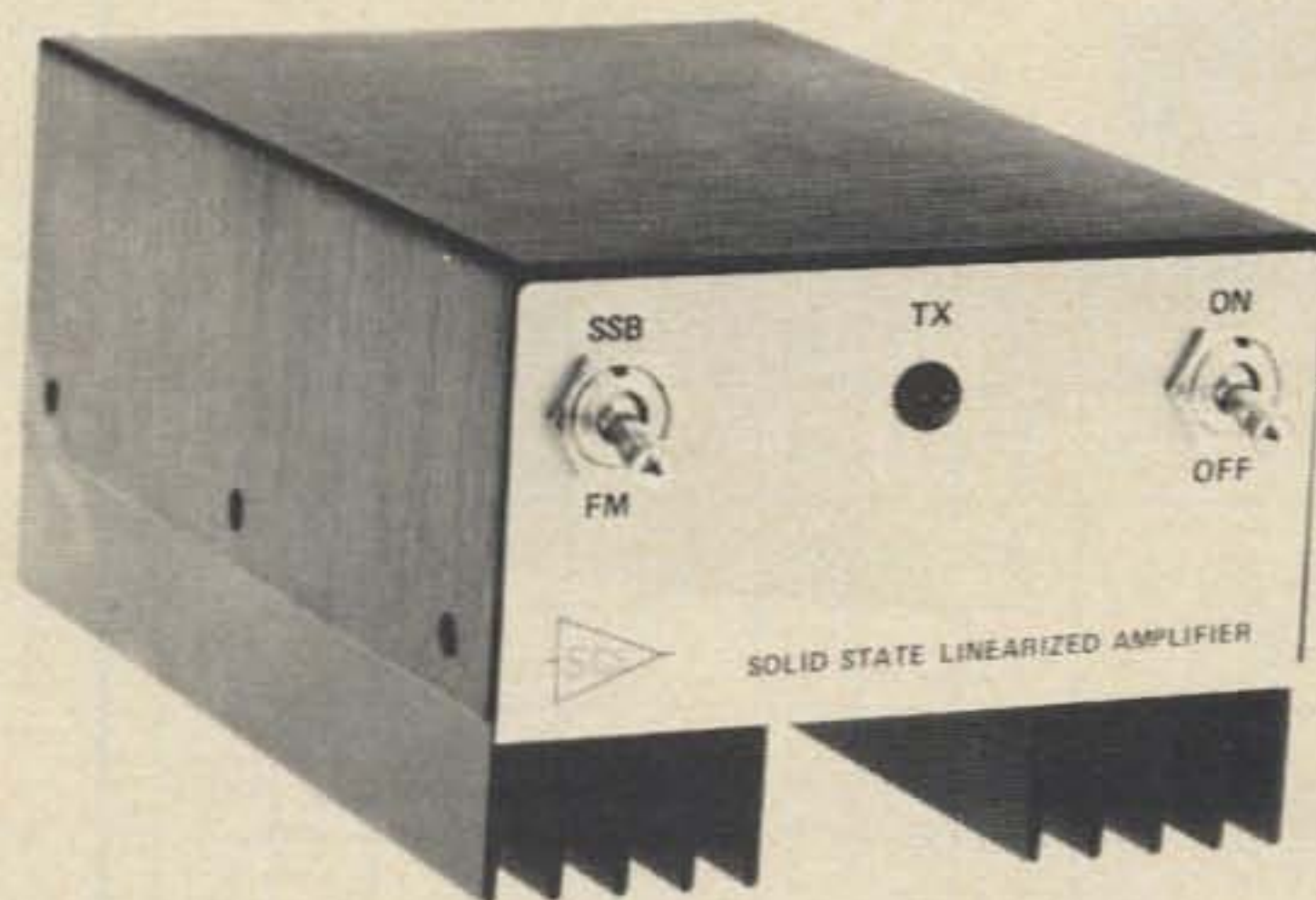-
- 2M10-70L \$139.95
10 W in – 70 W out 144-148 MHz amp
- 2M30-140L \$179.95
30 W in – 140 W out 144-148 MHz amp
- 2M10-140L \$199.95
10 W in – 140 W out 144-148 MHz amp
- 1.3M10-60L \$159.95
10 W in – 60 W out 220-225 MHz amp
- 1.3M30-120L \$199.95
30 W in – 120 W out 220-225 MHz amp
- 1.3M10-120L \$219.95
10 W in – 120 W out 220-225 MHz amp
-



\$2.50 shipping USA, CA residents add 6% tax.

- All Amps:
- Fully VSWR & reverse voltage protected
 - No tuning required across band
 - Switchable Class C or AB operation
 - Built-in TR switching, w/increased delay for SSB
 - Fully compatible with all 1-15W FM/SSB/AM/CW rigs
 - All solid-state and microstrip construction

Also available: 1–10W, 10–40W and 420–450 MHz linearized amps

*See your local dealer, or write for further information
Dealer inquiries desired*

... some of our dealers ...

Vegas Radio
1108 S. 3rd
Las Vegas NV 89101

James M. Homan W4DPH
PO Box 719
Clearwater FL 33517

Gary Radio Inc.
8199 Clairmont Mesa
San Diego CA 92105

SPECIALTY COMMUNICATIONS SYSTEMS

4519 Narragansett Ave., San Diego CA 92107

Louis N. Anciaux WB6NMT

TUFTS

"New England's Friendliest Ham Store"

INVITES YOU TO SEE THE ABOVE LINE

TUFTS Radio Electronics
386 Main St., Medford MA 02155
Phone: 714-222-8381

GATEWAY ELECTRONICS

8123 Page Blvd.
St. Louis MO 63130
(314)427-6116

2839 W. 44th Ave.
Denver CO 80211
(303)458-5444




IC SOCKETS

	8	14	16	18	24	28	36	40	
Commercial CS	.24	.28	.30	.36	.53	.67	.84	.89	Gold
Low Profile LS	.21	.25	.27	.35	.52	.64	.82	.86	Tin
Standard CA	.26	.34	.36	.40	.59	.70	.88	.94	Gold
	.23	.33	.35	.39	.58	.67	.86	.91	Tin
Standard Wire Wrap CA-WW	—	.36	.38	.42	.62	.74	.93	.99	Gold
	—	—	—	—	—	—	—	—	Tin
Standard Wire Wrap CA-WW	—	.39	.41	.45	.79	.95	1.08	1.14	Gold
	—	—	—	—	—	—	—	—	Tin

IC sockets may be assorted for quantity discounts. 1 to 9 pcs. NET, 10 to 24 pcs. LESS 5%, 25 to 99 LESS 10%, 100 to 499 LESS 20%. WRITE FOR LARGE QUANTITY QUOTATIONS, D.I.P. plugs and covers also available.

MINIATURE THUMBWHEEL SWITCHES

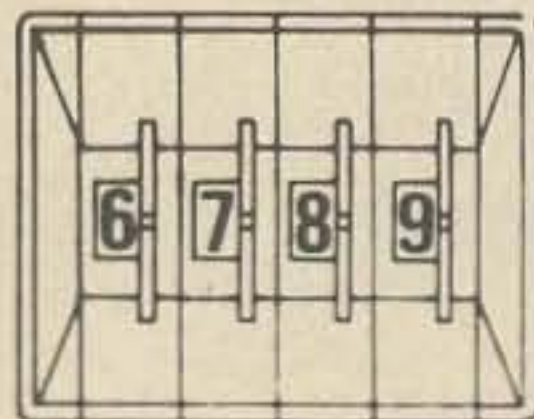

BCD ONLY	\$2.50
COMPLIMENT ONLY	2.75
BCD & COMPLIMENT	4.00
DECIMAL	2.50
END PLATES (PAIR)50
HALF BLANK BODY40
FULL BLANK BODY40
DIVIDER PLATE40

MINIATURE SIZE 0.315 X 1.3 X 1.78

All switches are black with white figures and snap-in front mounting.

\$5.00 minimum order —
Please include sufficient postage.

VISIT US WHEN IN ST. LOUIS OR DENVER

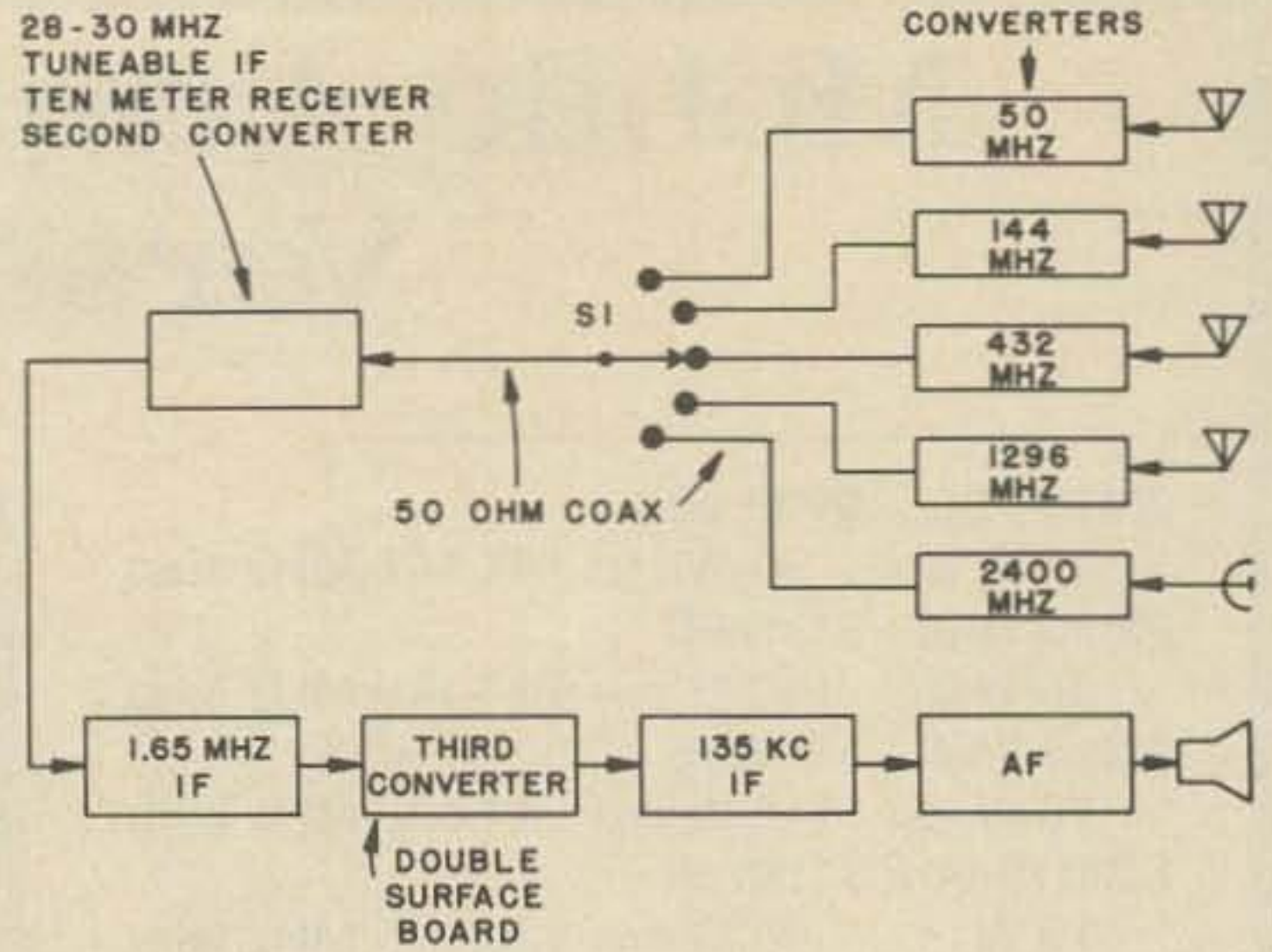


Fig. 7. Block diagram of an all-band VHF-UHF-S-Band receiving system.

The modular concept is still very evident. In fact, it's even more so now with each module consisting of an enclosed minibox instead of a breadboard. I'm getting quite curious to see just how small the whole receiver can be. Putting the entire rf section into closed boxes looms as the toughest size problem.

Installation in the Box

Fig. 6 shows a view looking down into the minibox with the cover off. You can see that with both sides of the box open, almost all the components are available for service if needed.

To remove the board from the box only two wires have to be unsoldered, one to J1 and one to J2. The layout of Fig. 5 shows all the detail needed for the 135 kHz side.

Now you have the narrowband i-f in a small minibox, so next in line, going backwards toward the antenna, are two 1.65 MHz stages which should go into an even smaller box, as long as there is room for a 1/2 in. control to set the i-f gain to your fancy. Using the two low noise rf stages and the battery-operated "ten-meter-receiver" section in front of the two i-f strips, you certainly don't need much i-f gain.

Note that these units, beginning with a 28 to 30 MHz tunable i-f, can be used on Six, Two, 432, 1296, and 2400 MHz to make up an all-VHF-UHF-S-Band receiving setup, as in Fig. 7, and that they can all operate from one battery.

... K1CLL

A True Tale of the Faked Fist

A ham or commercial radio operator's signature is his "fist." More than a dozen years ago when I was a Novice I worked a fellow named Ashley WA4AGT, in Valdosta GA on CW almost every afternoon. Ashley had a good fist, not perfect, but better than average. When I tuned across the 40m Novice band in search of a contact I would recognize Ashley's signal even before he finished a word or gave his call. Soon I recognized others by their fist alone, the staccato, machine-gun like Frank K4RAD, and John WA4BMG, with his dots almost as long as his dashes; and the perfectly spaced characters of Owen K4YXN. The "fist" is as much a part of an operator's being as his voice.

During World War II a trio of FBI agents used the characteristics of a man's keying hand to fool the Germans. A Dutchman named Albert Van Loop was sent to the United States to spy for the Germans and to set up a transmitter to send information back to Germany. But Van Loop, a 50 year old engineer and jeweler, defected to the United States. The FBI, however, thought it would be interesting if they kept the defection secret and set up the transmitter and sent back false information to Germany.

Van Loop, who told U.S. intelligence agents that he signed up for German spy school because he wanted to get out of Europe, showed up at the American consulate in Madrid in April 1942. He told an assistant ambassador that he had been sent by Germany to spy on U.S. troops and that

he had been instructed to set up a transmitter in the U.S. and send the information back to a station in Hamburg. He had microfilm of a radio transmitter schematic, parts list, assembly instructions, a secret code plus more than \$16,000 in cash. He was to buy an off the shelf receiver. The U.S. intelligence establishment, including the FBI, decided to play along.


Van Loop and his wife arrived on a Portuguese ship in New York and were immediately submitted to grueling questioning by the FBI.

From the questioning and research the FBI found that Van Loop had been a spy for the Germans during World War I and he had been convicted and spent time in jail for stealing \$7,000 in Holland.

The FBI agents didn't fully trust the little Dutchman, so they allowed him to rent an apartment in New York, but under the FBI's close watch. He got a job in a jeweler's shop. The FBI set up the transmitter on Long Island and made the first contact with Hamburg on February 7, 1943.

Van Loop did not operate the transmitter; instead, it was manned by FBI men who knew German and could send and receive CW, taking the place of the Dutch counterspy.

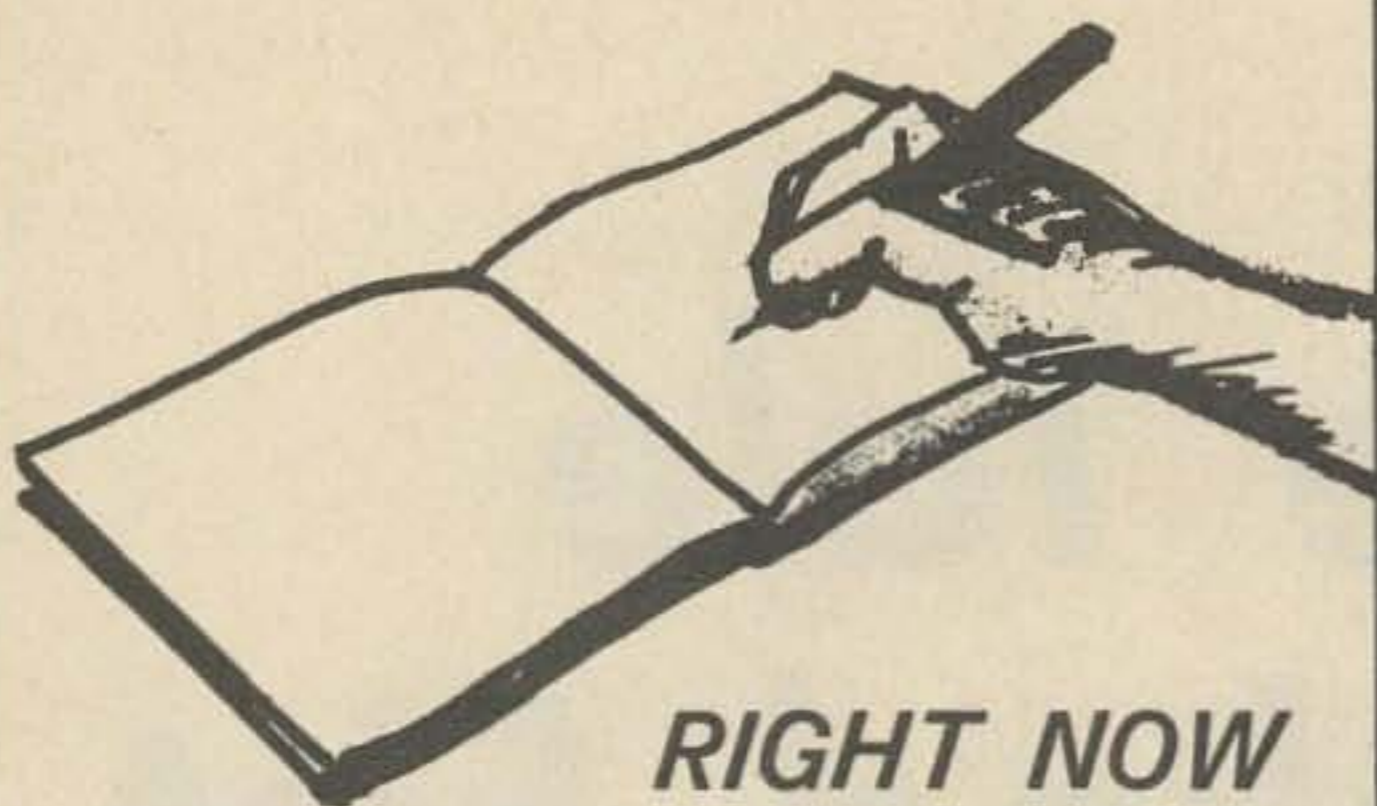Since this was before widespread use of magnetic tape, Van Loop recorded phonograph records of his fist and the agents played them back over and over trying to sound exactly like the counterspy. Actually it wasn't easy, for Van Loop had a very



RIGHT NOW

is the time to order your

75 callbook

Don't wait until 1975 is half over. Get your new **Callbooks** now and have a full year of the most up-to-date QSL information available anywhere.

The new **1975 U. S. Callbook** will have over 300,000 W & K listings. It will have calls, license classes, names and addresses plus the many valuable back-up charts and references you have come to expect from the **Callbook**.

Specialize in DX? Then you're looking for the new, larger than ever **1975 Foreign Callbook** with over 225,000 calls, names and addresses of amateurs outside of the USA.



**United States
Callbook**
All W & K Listings
\$12.95



**Foreign Radio
Amateur Callbook**
DX Listings
\$11.95

Order from your favorite electronics dealer or direct from the publisher. All direct orders add 75¢ shipping and handling per Callbook.

WRITE FOR RADIO AMATEUR
FREE BROCHURE  **callbook** INC.
Dept. B 925 Sherwood Drive
Lake Bluff, Ill. 60044

sloppy fist and his dots were far too long, but it would have been a mistake to try and correct the faults in his sending.

A German named Vizetun could identify anyone he had ever worked on CW and American agents knew that Vizetun had listened to Van Loop sending before the Dutchman left Germany just in case someone tried to call Hamburg saying they were the real German spy when they were not.

Also, the agents had to memorize the slang or oddities of a German speaking Hollander and use them in their reports back to Germany.

Most of the information sent back was of little importance, usually true material but just trivia. One day in May 1944 word came from Washington to the agents to transmit data about troops shipping out from New York to Iceland. The agents made up stories of a drunk sailor and drunk army officer making a remark about going to Iceland. Other false leaks about Iceland were transmitted. Within 78 hours the Germans sent a photo plane over Iceland and observed dozens of tents and barracks that had recently been put up.

Actually the barracks and tents were decoys so the Germans would think the D-Day invasion would take place in Norway instead of France. The fake barracks caused the Germans to believe the Iceland base was a staging area.


Because the Germans couldn't be sure where the invasion was coming from until a few days before the battle, many troops and much equipment was held in Northern Europe and not on the beaches of Normandy.

The agents continued sending in the sloppy fist of Van Loop until April 27, 1945, when the station in Hamburg was destroyed.

Van Loop opened a jewelry store in a large Eastern city after the war and became a citizen of the United States. If you have ever worked an old Dutchman with dots twice as long as they should be, he might have been the hero of Normandy who spent the day of battle in his New York apartment while special agents sent false information to the enemy using Van Loop's fist.

... W4ZBE

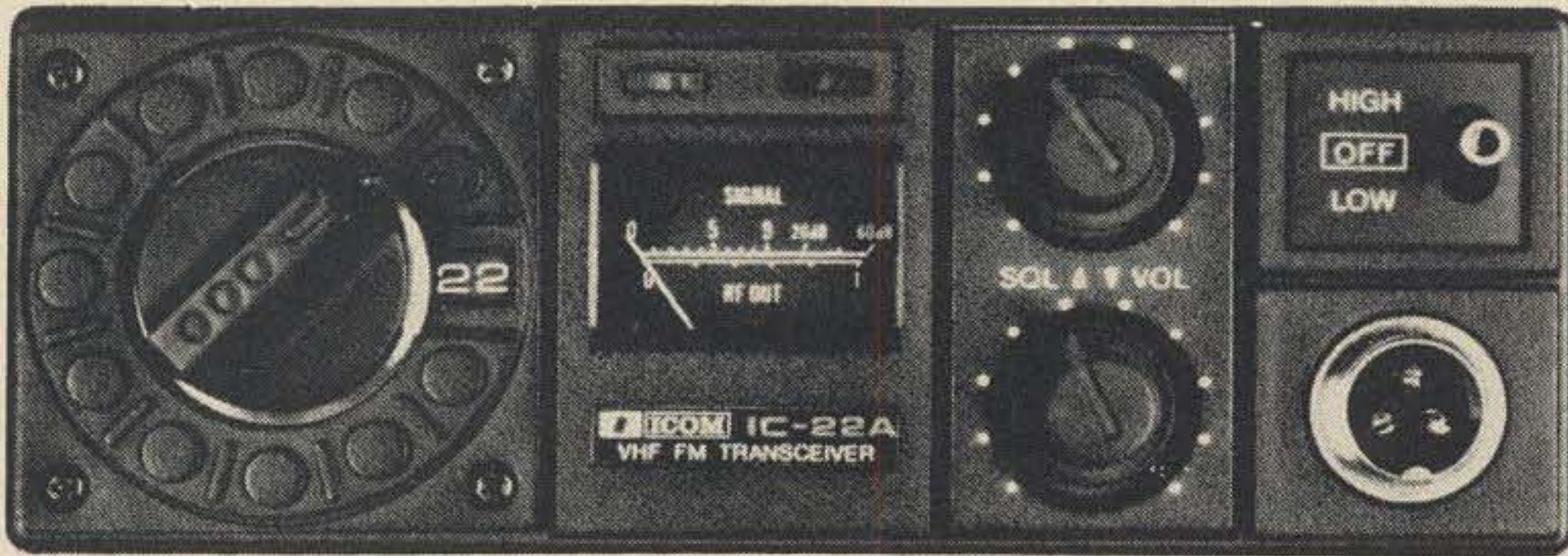Specializing in VHF-UHF FM & SSB Equipment



IC-22A \$249.00 ppd.

Supplied with
Seven channels
94/94 34/94
22/82 28/88
52/52

Plus TWO channels
of your choice.
Additional channels
\$9.95 installed

THE PREMIUM 2 METER FM TRANSCEIVER

IC-230 \$489.00 ppd.



IC-230

SAVE \$50.00!

Purchase an ICOM for \$489 with no-trade, and you may apply \$50 credit towards the purchase of accessories below.

For the Mobile —

KLM PA10-70B 70W 2M Ampl	\$129.95
KLM PA10-140B 140W 2M Ampl	\$189.95
Hustler CGT-144 5.2dB Colinear, trunk lip mount	\$39.95
Hustler CG-144 5.2dB Colinear, 3/8 thread	26.75
Larsen LM-150K 3dB 5/8 wave	\$28.35
Larsen LM-150 on Magnetic Mount	\$35.00

For the Ham Shack —

KLM 144-148-12 12el DX Beam	\$49.95
KLM 144-148-16 16el DX Beam	\$54.95
KLM Baluns (optional, recommended)	\$13.95
KLM 2 Antenna Combiner	\$19.95
Cushcraft ARX-2 Ringo Ranger	\$26.50
Cushcraft A147-11 11el Beam	\$23.95
Cushcraft A147-22 Stacked 11's	\$68.50

Allow \$3.00 shipping per antenna or amplifier.

We Ship!

Our in-depth stock assures filling orders the same day received. We ship UPS or best way. For fast shipment we suggest 1. Cashier's check or MO., 2. C.O.D. (\$15 deposit), 3. Bank-Americard, 4. Master Charge. California residents add 6% sales tax.

Westcom

831 GRAND AVE. • SAN MARCOS • CAL • 92069 • (714) 744-0700

RGS ELECTRONICS

008A MICROCOMPUTER KIT

8008 CPU, 1024 x 8 memory; memory is expandable. Kit includes manual with schematic, programming instructions and suggestions; all ICs and parts supplied except cabinet, fuses & hardware. Includes p.c. board. **\$375.00**

MANUAL ONLY, \$25.00
(no discount on manual)

008A-K ASCII keyboard input kit. **\$135.00**

008A-C Audio cassette adapter kit. **\$100.00**

Details on computer, peripheral kits in our flyer.

\$12.00 VALUE FREE

With each order of \$50.00 or more, a FREE subscription to *BYTE*, the new computer hobbyists' magazine. ASK FOR IT when you order; we won't include it unless you ask. (Offer open to residents of continental U.S. only.)

"THE CUBE" Fully assembled subaudible tone generator for small handheld or portable FM radios. 9-16 volts; no moving parts, set anywhere between 98 & 240 Hz with a trim resistor.

.5" x .6" x .8" **\$19.95**

Set on frequency by the factory, \$5.00 extra

PS 25-1 0 to 25v 1a lab type power supply with adjustable current limiting; remote sensing & remote programming for voltage & current. Instructions included. All parts except chassis, meter(s), p.c. board. Kit of parts with schematics **\$14.95**
P.C. boards available, No. 007 **\$3.00 ea.**

TTL

7400	\$.20	7485	\$1.40
7401	.20	7486	.50
7402	.20	7489	2.90
7403	.20	7490	.80
7404	.25	7492	.80
7405	.25	7493	.80
7406	.45	7495	.90
7407	.45	7496	.85
7408	.25	74107	.50
7409	.25	74121	.60
7410	.20	74122	.60
7411	.30	74123	1.10
7413	.85	74125	.65
7416	.45	74126	.65
7417	.45	74141	1.25
7420	.20	74150	1.70
7430	.20	74151	1.00
7432	.30	74153	1.40
7437	.50	74154	1.70
7438	.50	74157	1.40
7440	.20	75161	1.50
7442	1.10	74161	1.70
7446	1.45	74164	2.00
7447	1.45	74165	2.00
7448	1.45	74166	1.75
7450	.20	74174	2.20
7451	.20	74175	2.20
7453	.20	74176	1.60
7454	.20	74177	1.35
7473	.45	74181	3.90
7474	.45	74192	1.50
7475	.80	74193	1.45
7476	.50	74195	1.00
7483	1.10		

SOME NEW TRANSISTORS . . .

			1-99	100+
N1	T0-92	NPN Darlington	\$.35	.30
N2	T0-92	NPN lo-noise, lo-level	.15	.10
N3	T0-92	NPN medium purpose	.20	.15
N4	T0-92	NPN 2N3904 type	.15	.10
N5	T0-92	NPN UHF	.20	.15
N6	T0-92	NPN RF-IF	.15	.10
P2	T0-92	PNP lo-level	.15	.10
P3	T0-92	PNP medium power	.20	.15
P4	T0-92	PNP 2N3906 type	.15	.10
P7	T0-92	PNP high-voltage	.25	.20
P8	T0-92	PNP higher-voltage	.30	.25

AND SOME OLD TRANSISTORS . . .

		1-99	100+
2N2222	T0-18 NPN	\$.25	.20
2N2907	T0-18 PNP	.25	.20
NPN	T0-92 general purpose	.08	.0595
PNP	T0-92 general purpose	.08	.0595

Data on all transistors and JFETS is now in our flyer.

BRAND NEW ALUM. ELECTROLYTIC CAPS, RADIAL LEAD

	10wv	35wv	50wv
1mfd	\$.10	\$.12	\$.15
2mfd	.10	.12	
5mfd	.10	.12	
10mfd	.11	.13	.16
30mfd	.12	.20	.28
50mfd	.13		
100mfd	.15	.30	.45
200mfd	.20		.70
500mfd	.28	.75	
1000mfd	.50		

RGS ELECTRONICS

3650 Charles St., Suite K ■ Santa Clara, CA 95050 ■ (408) 247-0158

We sell many ICs and components not listed in this ad. Send a stamp for our free flyer. **TERMS OF SALE:** All orders prepaid; we pay postage. \$1.00 handling charge on orders under \$10.00. California residents please include sales tax. Please include name, address and zip code on all orders and flyer requests. Prices subject to change without notice.

DISCOUNTS: 10% OFF ORDERS OVER \$25.00; 20% OFF ORDERS OVER \$250.00

Adapting Telephone Handsets to FM Transceivers

Many hams are enjoying the benefits of using a telephone type handset in conjunction with their two meter FM equipment. There are several advantages to this type of microphone arrangement. The shape of the handset almost assures proper microphone technique; the earpiece frequently improves the readability of incoming signals by reducing the apparent amount of road noise; and the listener gains a bit of privacy, if desired, by not using the speaker in the set simultaneously.

At the top end of the spectrum are commercial handset assemblies such as the Shure model TH-100. It includes switching to mute the speaker in the set when the handset is in use, and is designed principally to be wired directly into the set, rather than to adapt to an existing microphone connector. At a lower cost, the ham can convert a handset designed for another purpose for use on an FM transceiver. Frequently surplus outlets offer handsets, usually manufactured by Stromberg-Carlson, which include a carbon microphone, a high impedance earphone, and a quality push-to-talk switch. Alternately, a small pushbutton can be installed near the earpiece end of a conventional handset from a telephone set in order

to provide for PTT operation.

In order to adapt a handset using a carbon microphone to most modern two meter FM transceivers it is necessary to change the microphone element and the coil cord. If your transceiver uses a low impedance microphone such as a Drake TR-22, the replacement cartridge for a Shure type 514B hand microphone is an excellent choice. While not the least expensive element, it delivers high output with superb audio quality, and readily fits in place of the original carbon type by simply wedging it from behind with a small pad of foam rubber. For sets like the Clegg or Regency which use a high impedance microphone, the replacement cartridge for a Turner model 360 hand microphone provides good audio quality and also is a snug fit in most handsets. The coil cord may be replaced with a Belden No. 8497 coil cord. This is necessary because the original cord does not have a shielded conductor which is required because of the low level of non-carbon microphones.

Most two meter transceivers employ a three circuit microphone connector. Since a ground, a switching lead, and a microphone audio lead are required for a conventional

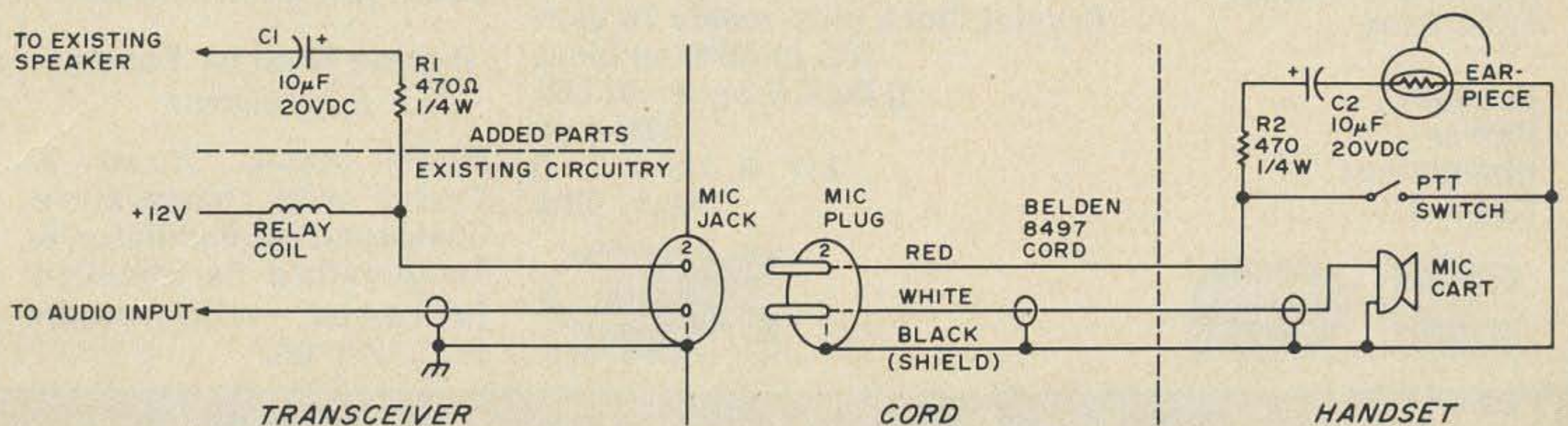


Fig. 1. Handset connection.

microphone, there is no conductor left to bring the receiver audio up to the earpiece. To avoid defacing a truly fine radio such as a Clegg FM-27B (mine in this case), an alternate solution to changing the type of microphone fitting was needed.

A little thought yielded an easy solution to the problem; simply superimpose the receiver audio on the push-to-talk conductor in the coil cord. This is a workable solution since the relay coil looks like a fairly large inductor at audio frequencies, and therefore will not short out the receiver audio. Conveniently, the PTT switch will short out the line to the earpiece, fully muting the receiver audio in the transmit mode. This is a nice plus, as some transceivers do not fully deactivate the receive audio in the transmit mode, resulting in a faint but annoying sound in the earpiece while transmitting.

A glance at Fig. 1 will show how it all goes together. The values of R1 and R2 were used successfully with both a Clegg FM-27B and a Regency HR-2A; however, they may be reduced to provide more audio to the earpiece, or increased to provide less should

a different balance between speaker and earpiece volume be desired. Most handset earpieces have a small beadlike device across the terminals. This is a varistor whose function is to level out variations in signal input. It is recommended that this be left in the circuit as it really does help.

A note of caution to anyone planning to disconnect the internal speaker in the set is in order. If you do remove the speaker, or install a switch to defeat it at will, be certain to substitute a resistor such as 10 Ohms at one or two Watts in place of it. This is important because failure to do this may result in reverse polarity appearing across C1 with certain types of transceivers. This is not good for electrolytics.

Several of the local hams have added the convenience of handset operation to their sets using the methods outlined here. All are reporting fine results. Naturally, the original microphone may be carried as a spare; its operation is of course not affected by the addition of the circuitry for the handset audio. See you on 88 or 61 or 94 or...

...WA8LEM



SPECIFICATIONS

Frequency Range	500 KHz—250 Mhz
Sensitivity	Less than 80 mV at 150 Mhz
Input Z...(500 KHz to 10 Mhz)	1 Meg.
Input Z...(10 Mhz to 250 Mhz)	50 ohms
Max. Input Voltage	15 V rms, 50 V dc
Time Base	Crystal Clock plus-minus 10 ppm 0°C to 40°C ambient
Readout	6 Digit 7 Segment LED
Power	120 V ac
Dimensions	2 1/4" H, 10" L, 7" D
Cabinet	Light Blue



Model 4x6 250 Mhz FREQUENCY COUNTER

250 Mhz for \$1.00 per Mhz
Wired and Tested

\$250


Price FOB Shawnee, Okla.

Include \$2.50 for Postage
& Insurance

Model 4x6-C Wired &
Tested with Temperature
Compensated Oscillator &
Temperature Certification
furnished with coun-
ter....\$270.00.



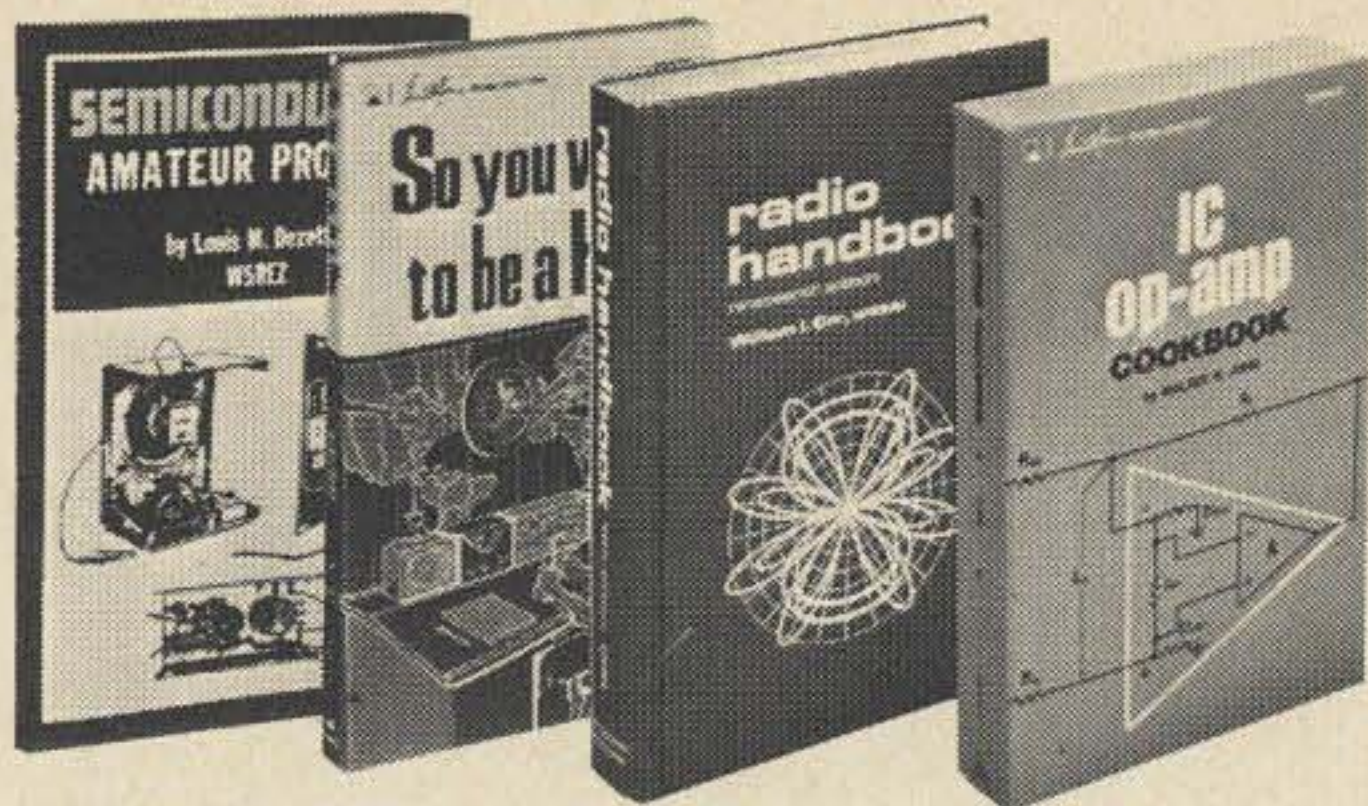K-ENTERPRISES 1401 E. Highland • Shawnee, Okla. 74801



AMATEUR RADIO BOOKS FROM HOWARD W. SAMS

RADIO HANDBOOK (19th Edition)

by William I. Orr, W6SAI. The standard work on practical and theoretical aspects of radiocommunication and electronics. Provides detailed construction information and a complete understanding of theory on modern circuitry of transmitters, receivers, transceivers, power supplies, and test equipment. Broad coverage of fm, rtty, ssb, and a-m, plus full data on workshop practices, radio math, and other fields of special interest to the engineer and advanced amateur. 978 pages; 6 1/4 x 9 1/4; hardbound.

No. 24030 \$16.95

ELECTRONICS FOR THE AMATEUR

by Louis M. Dezettel, W5REZ. Discusses radio-wave propagation as it applies to amateur band frequencies, reception and transmission as they pertain to the equipment "hams" use, and the special field of antennas and how to feed them. 272 pages; 5 1/2 x 8 1/2; hardbound.

No. 24022 \$7.95

HAM AND CB ANTENNA DIMENSION CHARTS

by Edward M. Noll, W3FQJ. Tabulates dimension information in feet and inches for all the popular antenna configurations. Gives data for dipole antennas, quarter-wave verticals, two-element beams, quads, triangles, inverted dipoles, and inverted vees. 64 pages; 6 x 9; softbound.

No. 24023 \$2.25

AMATEUR TESTS AND MEASUREMENTS

by Louis M. Dezettel, W5REZ. Contains the know-how the average amateur needs to perform almost all necessary performance tests and make adjustments to transmitters, receivers, and antennas. 208 pages; 5 1/2 x 8 1/2; softbound.

No. 24007 \$5.50

SO YOU WANT TO BE A HAM (6th Edition)

by Robert Hertzberg, W2DJJ. Learn what types of licenses are available and the requirements and procedures for obtaining them. Technical aspects of radio equipment are also discussed. 192 pages; 5 1/2 x 8 1/2; softbound.

No. 20977 \$5.50

SEMICONDUCTOR AMATEUR PROJECTS

by Louis M. Dezettel, W5REZ. Contains instructions for making 16 useful ham-radio accessories—all designed to make a ham station more efficient and more enjoyable to operate. 160 pages; 5 1/2 x 8 1/2; softbound.

No. 24025 \$4.95

SINGLE SIDEBAND: THEORY AND PRACTICE

by Harry D. Hooton, W6TYH. A one-source guide emphasizing basic principles and circuitry, rather than mathematics. Includes information about the origin of ssb, the derivation of ssb signals, carrier-suppression techniques, sideband selection, carrier generators, and more. 388 pages 5 1/2 x 8 1/2; hardbound.

No. 24014 \$6.95

ABC'S OF HAM RADIO (3rd Edition)

by Howard S. Pyle, W7OE. Includes all the study material necessary to obtain the novice-class amateur radio license. Covers FCC regulations. Gives helpful hints on how to learn the code and how to set up your first station. 144 pages; 5 1/2 x 8 1/2; softbound.

No. 20638 \$3.50

101 QUESTIONS AND ANSWERS ABOUT AMATEUR RADIO

by Kenneth M. Bourne, Robert M. Brown, and Leo G. Sands. Serves not only as an introduction for the beginner to the many facets of amateur radio but also as a valuable reference source for the old-timer. 112 pages; 5 1/2 x 8 1/2; softbound.

No. 20731 \$2.95

73 DIPOLE AND LONG-WIRE ANTENNAS

by Edward M. Noll, W3FQJ. Covers practically every type of wire antenna used by amateurs. Gives dimensions, configurations of noise bridges, line tuners, and more. 160 pages; 5 1/2 x 8 1/2; softbound.

No. 24006 \$4.95

73 VERTICAL, BEAM, AND TRIANGLE ANTENNAS

by Edward M. Noll, W3FQJ. Contains data on practically all types used by amateurs. The 73 different antennas have all been built and air-tested by the author. 160 pages; 5 1/2 x 8 1/2; softbound.

No. 24021 \$4.95

IC OP-AMP COOKBOOK

by Walter G. Jung. Covers not only the basic theory of the IC op amp in great detail, but also includes over 250 practical circuit applications, liberally illustrated. Organized into three basic parts: introduction to the IC op amp and general considerations, practical circuit applications, and appendixes of manufacturers' reference material. 592 pages; 5 1/2 x 8 1/2; softbound.

No. 20969 \$12.95

TTL COOKBOOK

by Donald Lancaster. Explains what TTL is, how it works, and how to use it. Discusses practical applications, such as a digital counter and display system, events counter, electronic stopwatch, digital voltmeter, and a digital tachometer. 336 pages; 5 1/2 x 8 1/2; softbound.

No. 21035 \$8.95

RTL COOKBOOK

by Don Lancaster. Explains the how and why of RTL (Resistor-Transistor Logic) and gives design information that can be put to practical use. Gives a multitude of digital applications ranging from the basic switch to the sophisticated counter. 240 pages; 5 1/2 x 8 1/2; softbound.

No. 20715 \$5.50

ABC'S OF SHORT-WAVE LISTENING (3rd Edition)

by Len Buckwalter. An easy-to-understand introduction to the exciting world of short-wave radio. Tells what programs are available and how to get the most out of short-wave listening. 96 pages; 5 1/2 x 8 1/2; softbound.

No. 20797 \$2.95

SAMS BOOK ORDER FORM

Please fill in your order below:

- | | | |
|------------------------------------|------------------------------------|------------------------------------|
| <input type="checkbox"/> No. 24030 | <input type="checkbox"/> No. 24025 | <input type="checkbox"/> No. 24021 |
| <input type="checkbox"/> No. 24022 | <input type="checkbox"/> No. 24014 | <input type="checkbox"/> No. 20969 |
| <input type="checkbox"/> No. 24023 | <input type="checkbox"/> No. 20638 | <input type="checkbox"/> No. 21035 |
| <input type="checkbox"/> No. 24007 | <input type="checkbox"/> No. 20731 | <input type="checkbox"/> No. 20715 |
| <input type="checkbox"/> No. 20977 | <input type="checkbox"/> No. 24006 | <input type="checkbox"/> No. 20797 |



CARD NO.



EXPIRATION DATE

NAME

ADDRESS

CITY

STATE

ZIP

SIGNATURE

CHECK OR MONEY ORDER
TOTAL AMOUNT ENCLOSED

MAIL ORDERS TO: RADIO BOOKSHOP/PETERBOROUGH, NEW HAMPSHIRE 03458

Atlanta 1975

The Atlanta Hamfest was a perfect way for the family to spend the Fourth of July holiday weekend, and the Atlanta Radio Club did a fine job of planning.

For the ham, there were many manufacturer and dealer exhibits, as well as a sheltered flea market. Fifteen forums and meetings were well attended, especially the ARRL and FCC ones. XYLs and YLs had a special hospitality suite — not to mention bus tours of Atlanta and vicinity. There was even a well equipped nursery for young harmonics.

Eighty persons took advantage of the special opportunity offered by the FCC to take a license exam on Saturday morning. Mr. Ditty, Atlanta District Engineer-in-Charge, and several other employees gave up their day off just to administer the exams! Who said the FCC has no heart?

Saturday night, Prose Walker was the featured speaker at the banquet, where he spoke to a "full house" of 300 persons on Docket 20282. Among his comments at the banquet and at the FCC forum the next day, Walker stated that restructuring is necessary


to increase the number of licensed amateurs in the United States. Less than 275,000 amateurs occupy 13% of the spectrum between 3 and 30 MHz, and this number is decreasing monthly. "The future of amateur radio demands that our ranks be increased," he asserted. "The average age of an amateur today is 43 years old."

The "Communicator" or "Basic Amateur" license class is inevitable. The unanswered question is, "How do we accelerate him into the mainstream of Amateur Radio?" Walker said that this must be done by education and training, in ham clubs and on the air. The FCC has no magic formula for best restructuring ham radio. They are reading the 2000 comments filed to date, trying to find the right direction, and claim the results of the ARRL membership poll should be of assistance.

The only thing I did not quite follow was the comparison of hams and CBers: Amateur radio is clearly defined in Part 97, while the purpose of CB radio is defined in Part 95. A ham is permitted to radiate a signal with 2000 Watts PEP with the intent of being



Display booth bedlam.

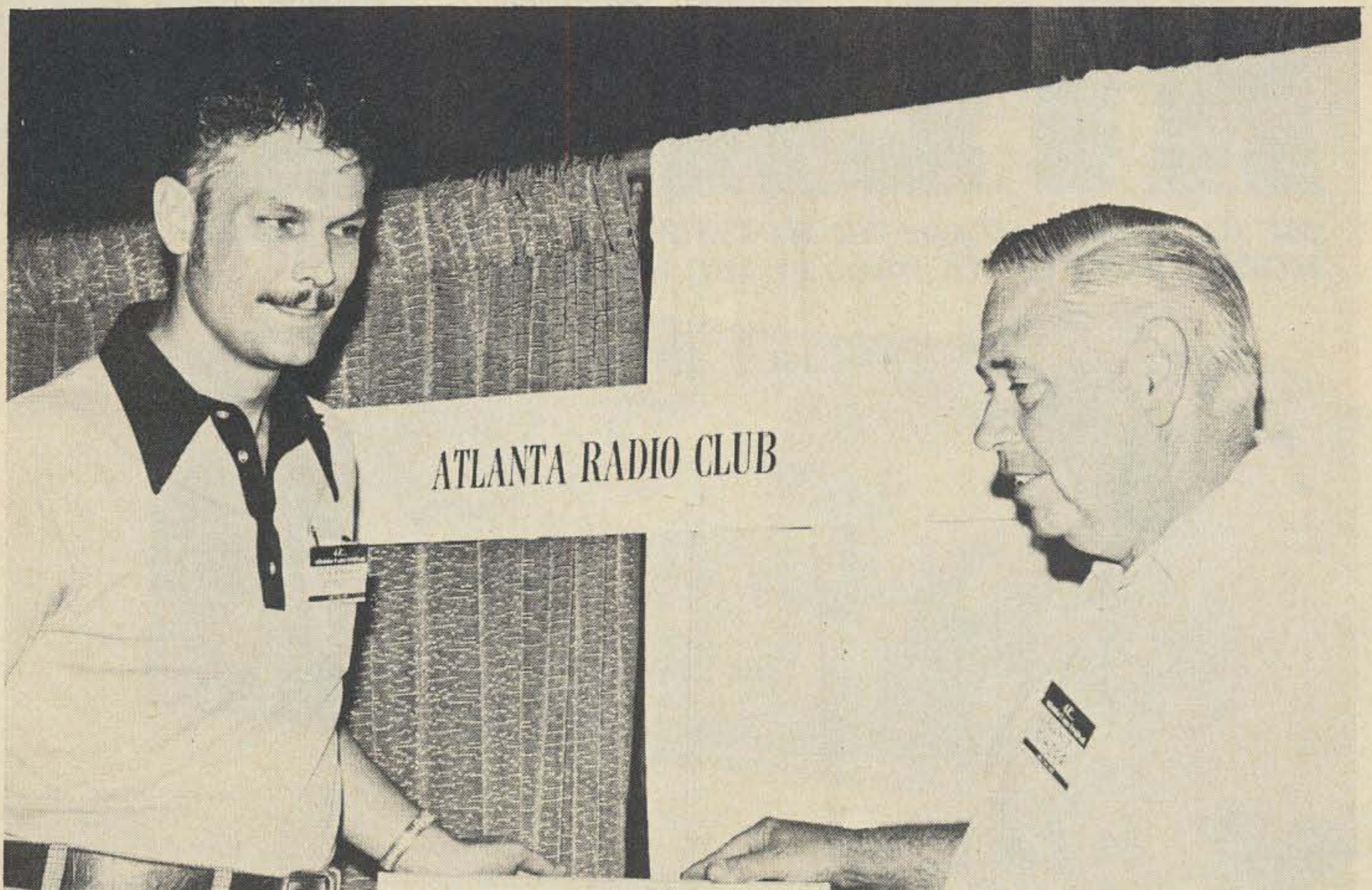

Dick Ehrhorne presents Alpha 374 2 kW linear to K4IOQ.

heard anywhere in the world. A CBer, in contrast, transmits a 5 Watt (12 Watt PEP)



Prose Walker at the podium.

signal for the purpose of short range (less than 150 mile) communications. How can these two very different services be compared only in terms of number of licenses of transmitters?

Another area covered was plans for the upcoming WARC '79; Walker received a standing ovation for his speech.

It is interesting that the only equipment reported stolen at the Hamfest was a walkie-talkie from a booth. No automobile or room burglaries were reported. Could it be that people in the southeast practice the golden rule?

Eight thousand dollars worth of prizes were given away, with K4IOQ the proud winner of the first prize, an Alpha 374 2 kW linear amplifier.

Sales were generally slow. Most exhibitors felt they had excellent exposure and most recovered their costs. Could be that southeastern hams are saving up for a rainy day.

Everyone did agree that the 1975 Atlanta Hamfest was well planned and coordinated, and we're looking forward to next year.

... W6LJU

ATLAS 210

for 10, 15, 20, 40 and 80 METERS AND THE COMPANION MODEL 215 FOR 15 through 160 METERS.



**ATLAS
RADIO INC.**

417 Via Del Monte Oceanside, CA 92054
Phone (714) 433-1983

Measuring only 0.18 cu. ft. and weighing less than 7 pounds, the Atlas 210/215 Solid State Single Sideband Transceiver is a real GIANT KILLER. It packs a hefty 200 watts P.E.P., offers 5 band coverage, and unprecedented selectivity (only 9200 cycles at 120 db down).

Priced at just \$599, it's the best transceiver value on the market today.

ATV on 450 with a T44

TV is presently enjoying a never before realized popularity. Much of the rf equipment now utilized for ATV has been 450 UHF commercial FM equipment with video modulators added.

The most popular of the present modified mobile equipment are the Motorola T44, the GE Prog line and the RCA Carphone. Each of these rigs possesses certain advantages and disadvantages. All of them do have the significant disadvantage of requiring relatively heavy, complex power supplies and consuming relatively large quantities of power.

In an effort to reduce the cast iron content of my shack along with a reduction

in power consumption, I decided to utilize already existent solid state equipment to simplify my TV system.

The first ingredient in the project was a newly purchased SB-450 transceiver. The second item was the dead T44 transmitter strip from the junk box. Last, a WØMZL video modulator was added to the stack. A liberal application of miscellaneous parts from the hidden recesses of the work shop yielded one hybrid (1 tube) television transmitter.

The total power drain was 90 W for a 30 W rf output! (Contrasted with more than 250 Watts for a T44 under similar conditions.)

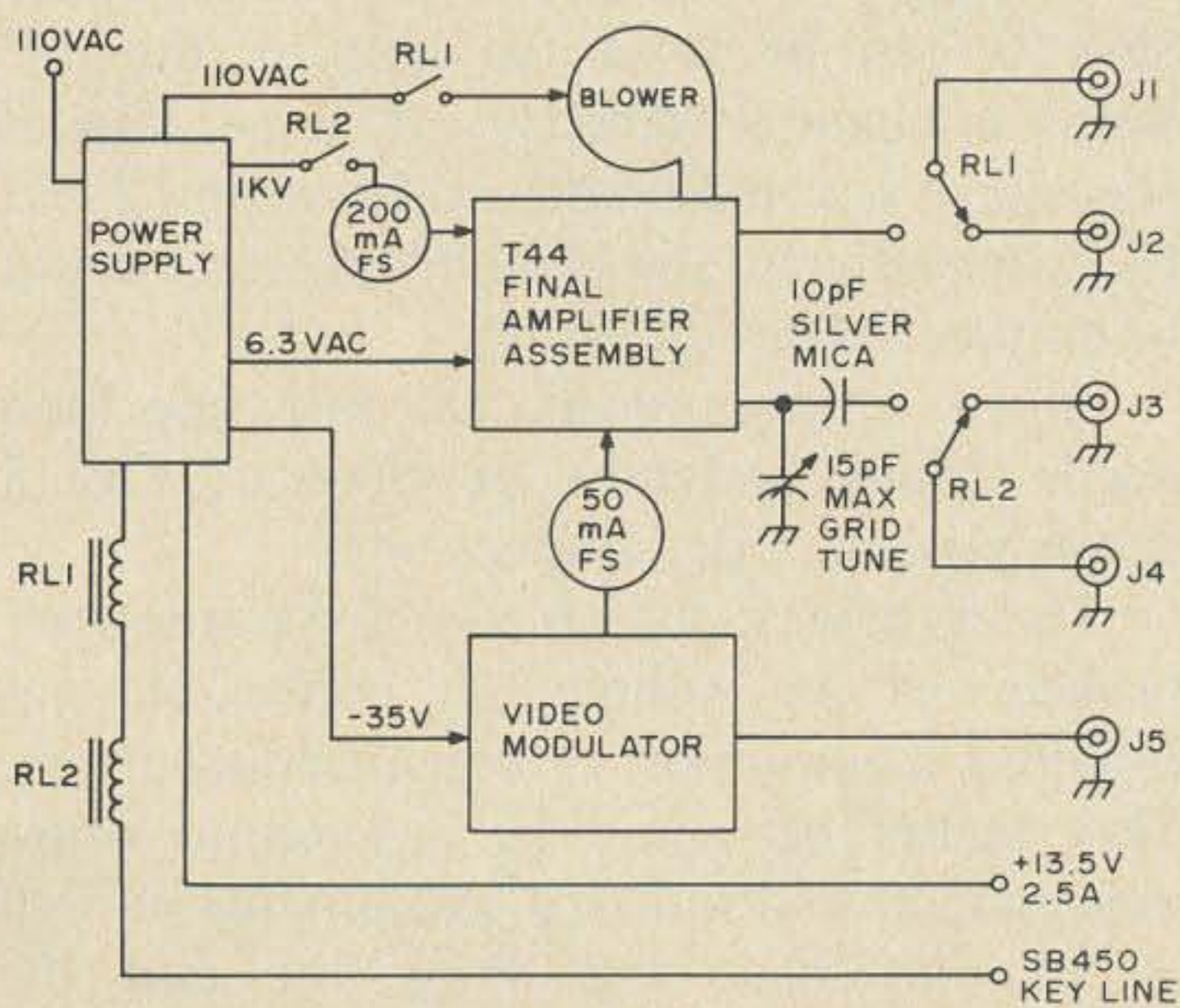


Fig. 1. System block diagram.

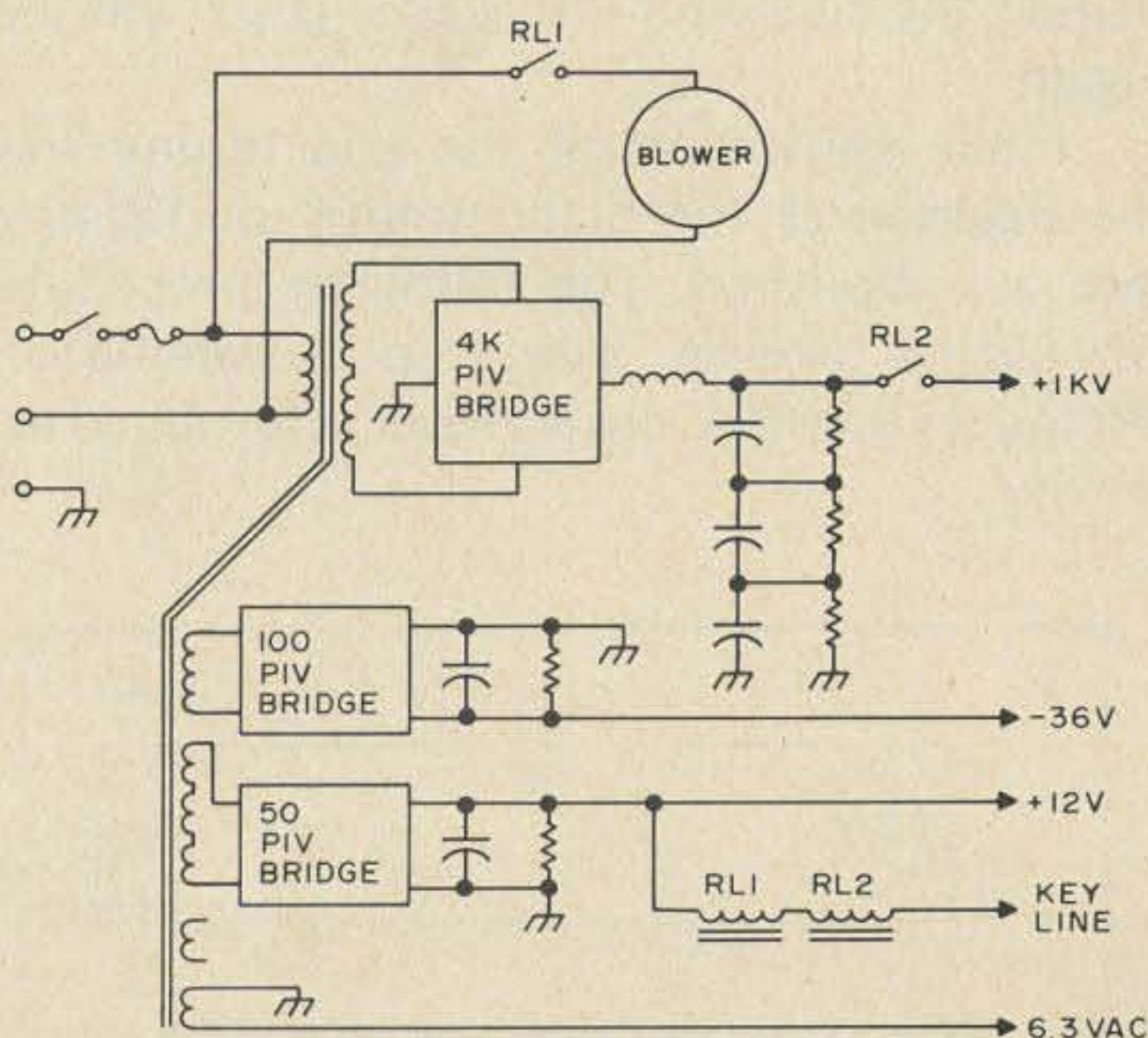


Fig. 2. Typical power supply.

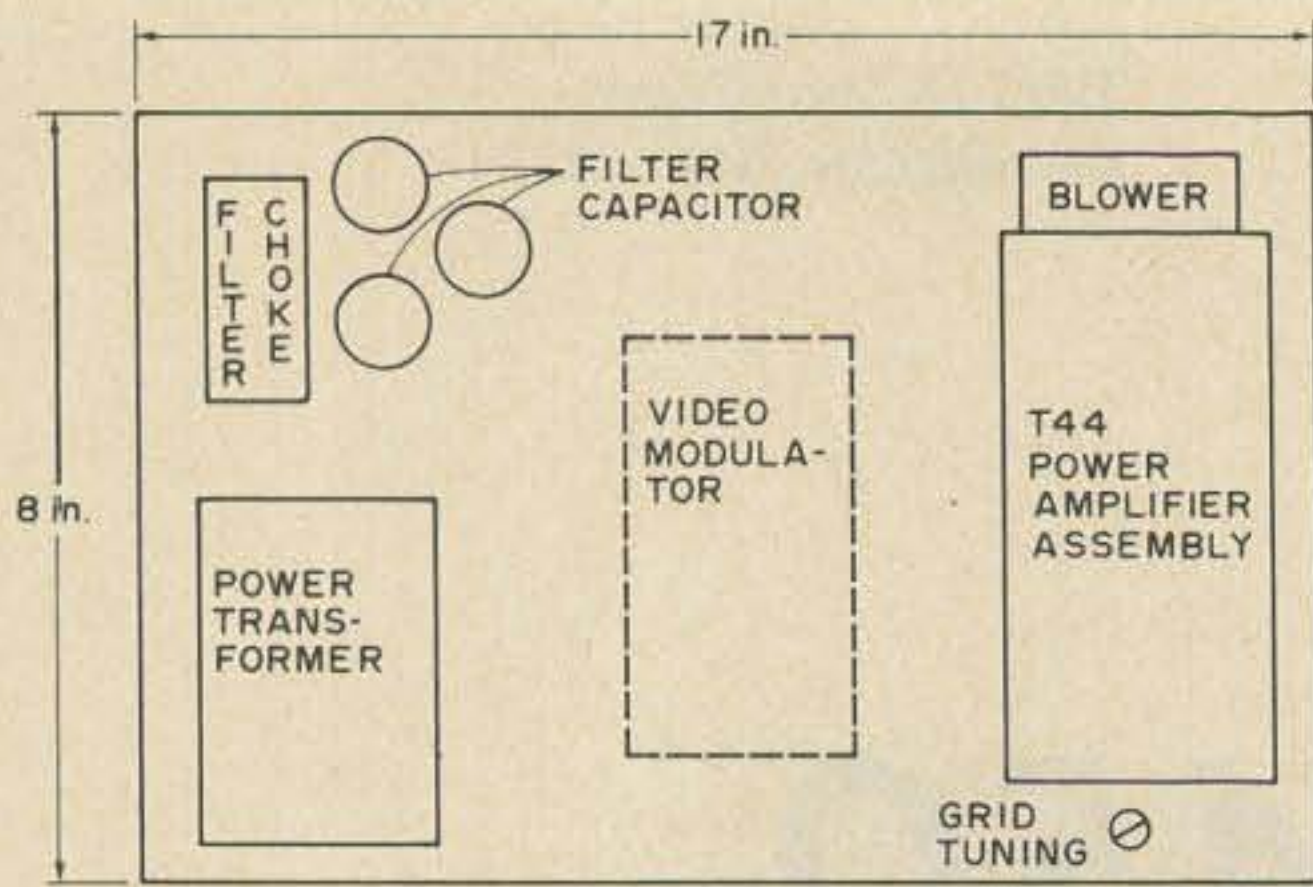


Fig. 3. Chassis layout.

Fig. 1 shows the block diagram of the hybrid transmitter. The power supply is left to your own devices. Fig. 2 shows the one that I used. A minimum of 800 V dc at 150 mA (max of 1 kV) is recommended for the high voltage. Relays RL1 and RL2 were salvaged from Motorola T44s also.

The layout of Fig. 3 is one of many possible arrangements. This particular arrangement divides the chassis into three nearly equal sections — power supply, video and rf — and is convenient.

Tune up of the amplifier is simple with only one possible hitch. The SB-450 possesses an swr protection circuit which turns off the transmitter. In order to reset the protection circuit, the SB-450 power switch must be turned off and then returned to the on position.

With this in mind it is important to preset the grid tuning capacitor to approximately 1/2 mesh. If the transceiver trips, reset and rotate the capacitor one way slightly and try again.

Final adjustment of the grid tuning will be made after the plate tuning and loading are accomplished. The following procedure should be used in setting up the amplifier. Remove the top cover from the amplifier cavity.

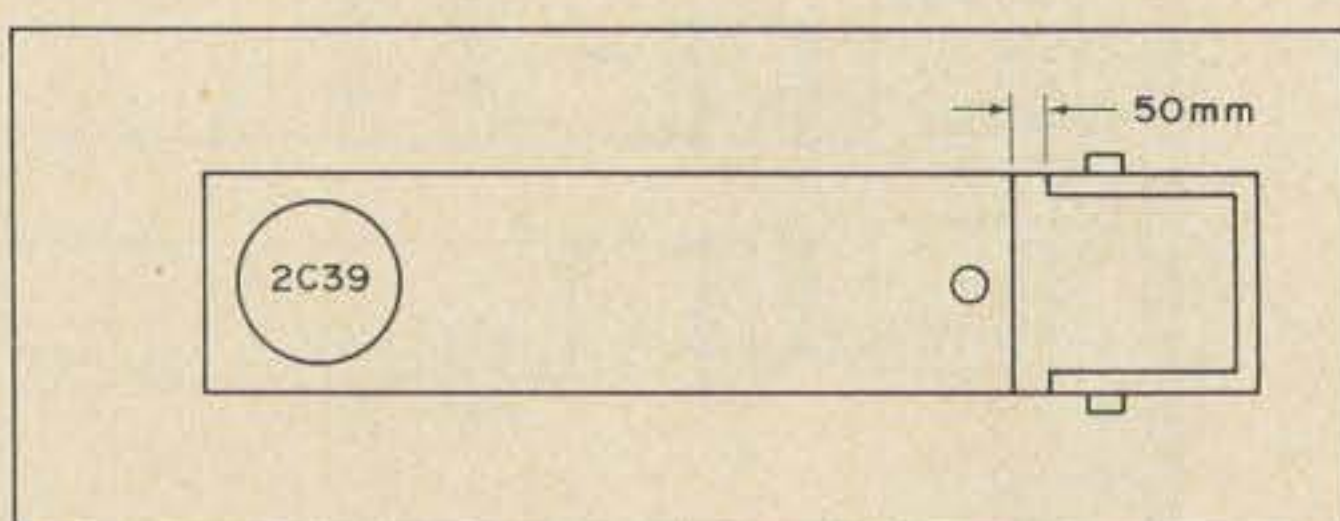


Fig. 4. Cavity amplifier — Interior.

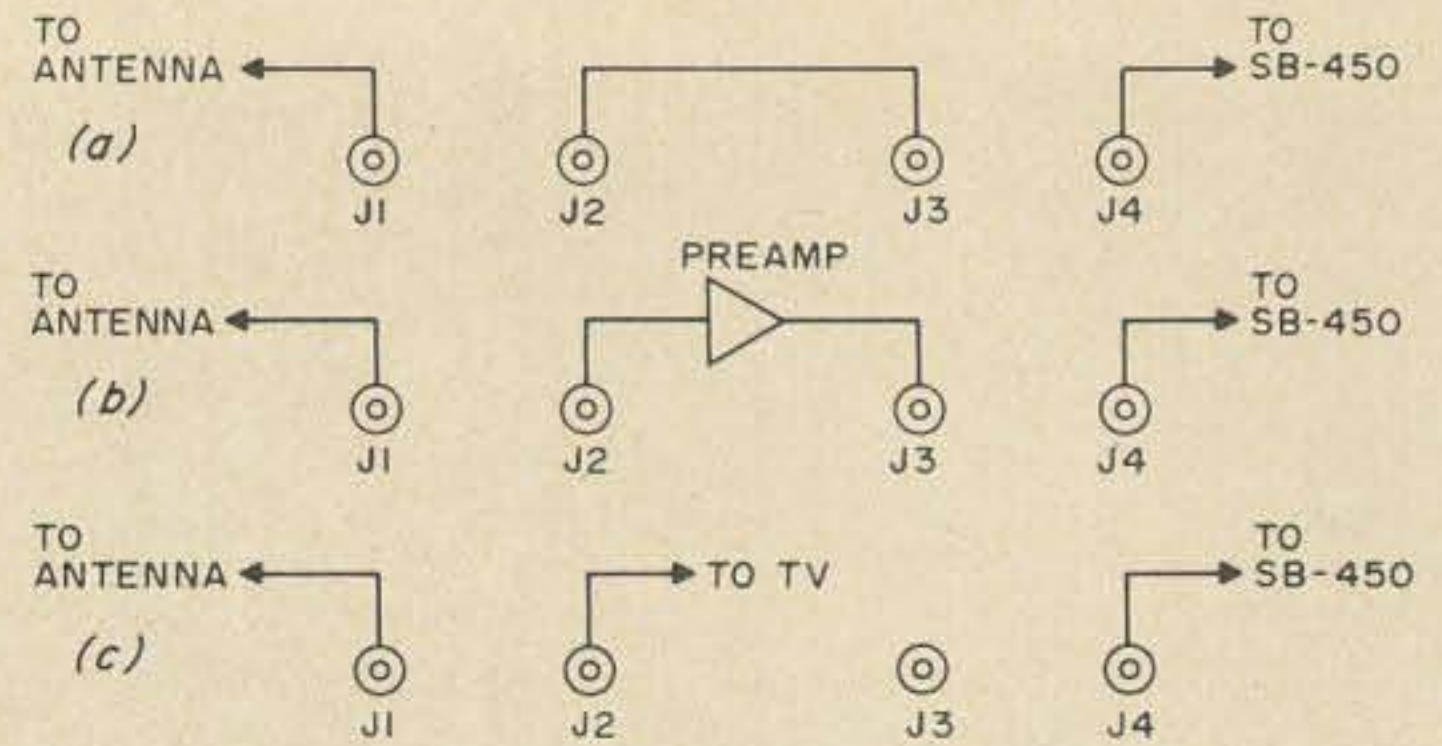


Fig. 5. Possible interconnection diagram.

The physical layout of the interior is shown in Fig. 4. Set the length of the line plate to the dimension shown. (50mm for 440 MHz.)

Apply drive to amplifier, and adjust plate tuning for a dip. The plate tuning control is the large screw-driven adjustment on top of the cavity. Then adjust the loading control using a non-metallic screwdriver for maximum power output, taking care not to exceed 100 mA average plate current. Grid bias should be about -25 V and power output should be about 35 W. Detailed tune-up procedure for video operation can be found in the December 1972 issue of QST.

The amplifier can be used for TV, FM and AM if desired. If desired for use only as an FM amplifier, the video modulator may be eliminated. For AM operation an external modulator may be used or the video modulator may be used simply by providing 1 V peak to peak audio to the input of the video modulator.

Several options are available for receiving. By placing a jumper between J2 and J3, the SB-450 can be used to monitor the TV simplex channel directly. If a preamp is necessary, it could be placed between J2 and J3. Alternatively, the Ham TV receiver could be connected directly to J2.

Other combinations to suit specified needs could certainly be devised. Fig. 5 shows possible interconnections.

The hybrid approach to a TV transmitter proved to be simple to construct and required a minimum of construction effort. This technique could be applied to other commercial and military equipments as well — in particular, GE Prog line and the AM-1178 military UHF amplifiers.

... KØMOC/WA4EMO

0-60 MHz Synthesizer


Part One

The design of a stable yet versatile frequency source has long been a central problem of amateur radio. And while great progress has been made over the years, VFOs still drift, and crystals still cost upwards of \$5. Operation in VHF and UHF is still largely crystal controlled.

The ideal solution to the problem is the frequency synthesizer, which combines the

versatility of the VFO with the stability of a crystal. Suitable synthesizers, such as the Hewlett-Packard HP-5100B, have been around for a long time, but a price tag of around \$10,000 put them far beyond reach of the amateur.

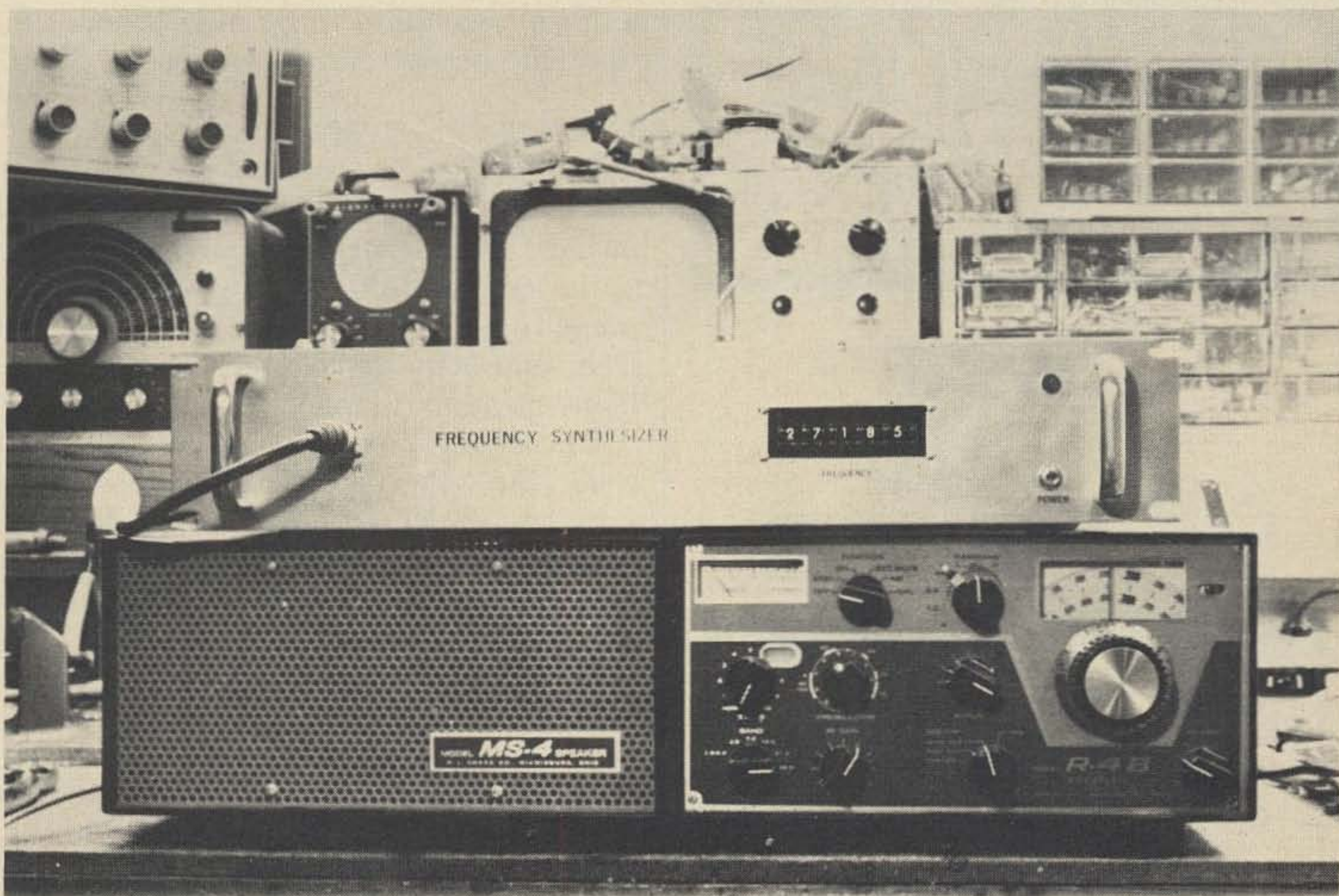However, the introduction over the past 2 years of a whole line of ICs specifically designed for phase locked loop (PLL) fre-



Front view.

NEW 500 MHz PRESCALER module

Only 35 mv. required at 500 MHz. 20 mv. at 150 MHz.

Miniature size: 1.5 x 1.5 x .4 inches. Fits right into existing equipment.

F/10 output, TTL compatible.

Overload Protected up to 2 volts input.

Requires 12 to 15 VDC at 100 mA max.

Measures a 1 watt transmitter from 6 feet using a 1/4 wave antenna at 500 MHz.

PS-M Prescaler Module wired and tested \$99.00.

Still available: Prescalers with 110 VAC power supplies, 150 mv. sensitivity, F/10 and F/100 outputs, 3 x 4 x 1.5 inches PS-K kit . . . \$89.00
PS-A . . . \$109.00

All orders please add \$.85 for shipping Calif. residents add 6% sales tax

LEVY ASSOCIATES
P.O. Box 961, Temple City, CA 91780

CASHAROONIE

Money! You can get top dollars now for U.S. surplus electronics, particularly Collins. Write or call now for your bigger than ever quote. Space Electronics Corp., 76 Brookside Ave., Upper Saddle River, N.J. 07458 (201) 327-7640.

STAMP-IT ETCH-IT



Reduces Printed Circuit Board Art Work From 2 Hours to 10 Min.

Simple as A.B.C.

A. Stamp Components on P.C. Board. B. Use Pen to Interconnect Lines. C. Etch Board.

SE-2 KIT CONTAINS:


- CONNECTOR FINGERS
- 18 PIN DUEL IN LINE IC SOCKET
- 10 PIN ROUND IC SOCKET
- 8 PIN ROUND IC SOCKET
- TO-3 TRANSISTOR SOCKET
- TO-18 TRANSISTOR SOCKET
- LARGE & SMALL DONUT PAD
- RESIST INK
- PLUS INK PAD
- RESIST PEN

ONLY \$9.95


ADDITIONAL STAMPS:

- Bread board stamps for all integrated circuits "Great" for experimenters.
- Only \$2.95 each four \$9.95
- # 1 DUAL INLINE
 - # 2 FLAT PACK
 - # 3 8-PIN ROUND
 - # 4 10-PIN ROUND

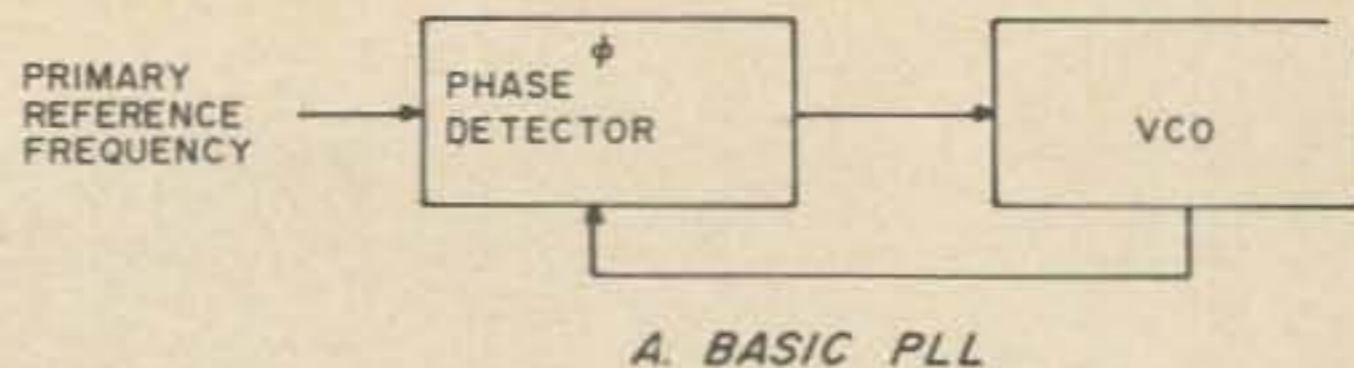
M-TECH
ENGINEERING, INC.
BOX C
SPRINGFIELD, VA. 22151



A. BASIC PLL

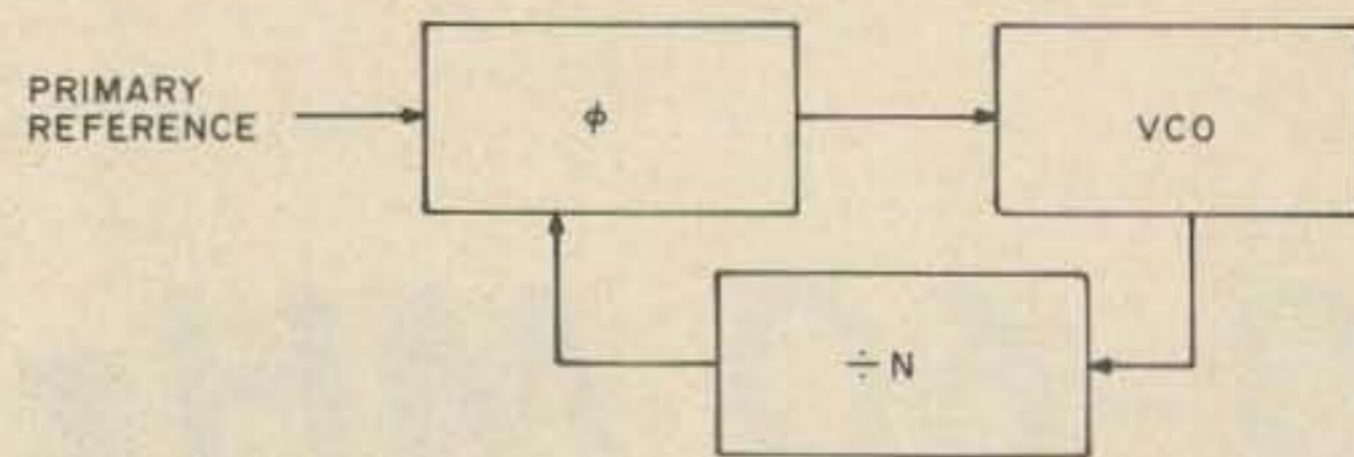

B. PLL WITH PROGRAMMABLE DIVIDER

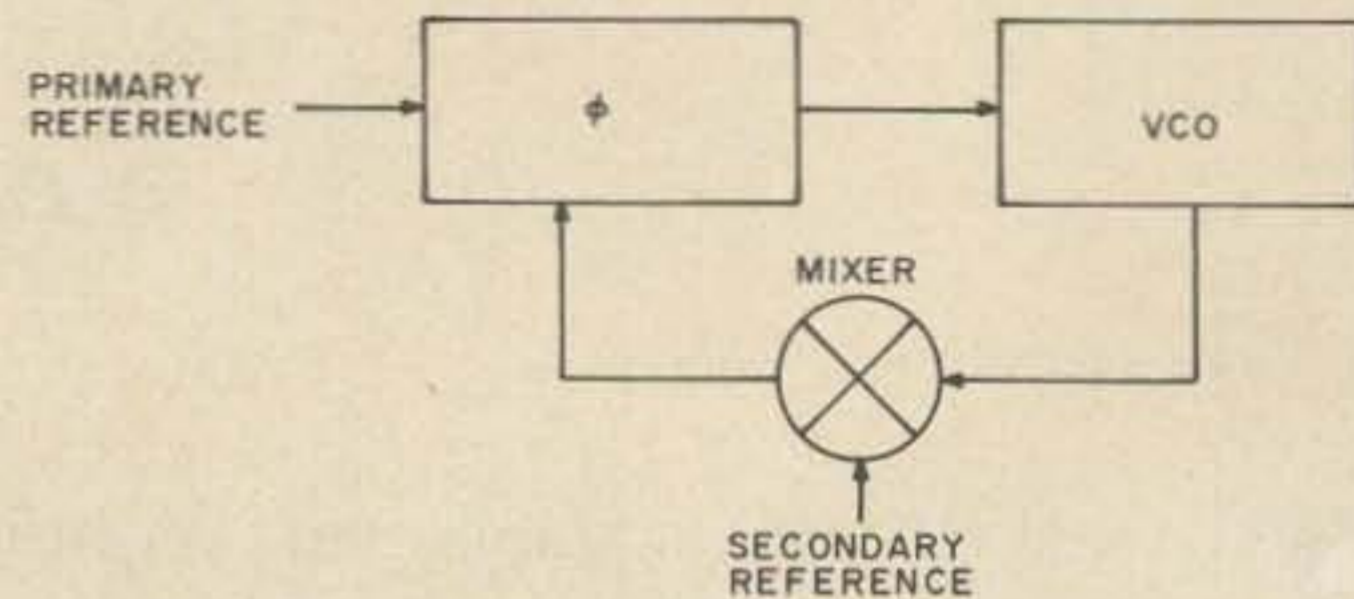

C. PLL WITH MIXER

Fig. 1.

frequency synthesizers has completely changed the picture. By using these ICs and the circuitry described in this article it is now possible for the amateur to build a frequency synthesizer offering 1 kHz (0.1 Hz optional) resolution to 60 MHz, along with excellent spectral purity, for around \$300.

A Word About Synthesizers in General

The frequency synthesizer described in this article works on the phase locked loop principle recently made famous by such ICs as the Signetics 565. There are, however, several other types of frequency synthesizers, and before going on I would like to briefly mention two of them.

The oldest principle, and the one on which the venerable HP-5100B is based, generates the desired frequency by performing arithmetic operations (addition, subtraction, multiplication, division) on a set of crystal-controlled primary standard frequencies. This method requires a large number of primary standards (20 or more), a highly complex system of mixers, multipliers, dividers, and filters — plus a sophisticated control section. It works very well, and can switch between channels extremely fast, but it is too involved and expensive to be worthwhile to the amateur.

Another principle in use today is that of direct digital synthesis. In this method some sort of digital counter is used to drive a ROM (Read-Only-Memory) which in turn drives a DAC (Digital-to-Analog Converter), which generates a sine wave (or other desired signal). This method is capable of high resolution and fast switching time, but the maximum frequency obtainable is limited by the ROM to 1 MHz.

This leaves the phase locked loop. In this method, Fig. 1(a), the output of a voltage-controlled oscillator (VCO) is compared to a reference frequency, and a correction voltage applied to the VCO to keep it precisely in phase with the reference frequency. The loop may be opened, as shown in Fig. 1(b), and a divider inserted, so that the VCO is locked to the n^{th} harmonic of the reference; or, as in Fig. 1(c), a mixer can be inserted, so that the VCO is locked to the secondary reference frequency plus or minus the primary reference.

When used with a programmable divider the resolution (minimum frequency difference between adjacent channels) of the PLL is the same as the reference frequency. When a mixer is used the VCO frequency is entirely determined by the two reference frequencies and the question of resolution doesn't arise.

Now we come to the basic disadvantage of the PLL. Because the signals involved are almost invariably digital, correction voltages can be generated no faster than once each cycle of the reference frequency. As a result, the loop can respond to changes, either external programming changes or internally generated noise, no faster than about one tenth the reference frequency. Here then is the problem; in order to achieve high resolution a low reference frequency must be used, while in order to achieve fast response time and a clean signal a high reference frequency must be used. Therefore high resolution and low noise are mutually exclusive goals for a single PLL, and we reach an impasse.

The way around it is to use several PLLs together.

A Practical Multi-PLL Design

The block diagram of the synthesizer is



Aha, the SECRET of PC Board success finally revealed. A perfectly balanced lighting tool combining magnification with cool fluorescence. Excellent for fine detail, component assembly, etc. Lens is precision ground and polished.

Regularly \$65.00. Now, over 30% discount (only \$46.00) to all licensed Hams, verified in Call-Book. Uses 22 watt fluorescent tube 8 inch diameter circle (not supplied).

Include \$3.00 U.S. postage, or \$4.00 in Canada, \$5.00 elsewhere. California residents include 6% sales tax. Or send stamped envelope for free brochure of other incandescent or fluorescent lamps suitable for all engineers, architects, students, etc

\$46.00 price assured until Jan. 1, 1976

D-D ENTERPRISES

Dept. B-3, P.O. Box 7776
San Francisco CA 94119

PRINTED CIRCUIT

EPOXY GLASS CIRCUIT BOARD STOCK;
CARBIDE DRILL BITS; TAPE RESIST;
ARTWORK; BUBBLE ETCHERS
SEND S.A.S.E. FOR FLYER

TRUMBULL

833 BALRA DR., EL CERRITO, CA. 94530

TRY SURE MASTER CODE CASSETTES!!

COMPUTER GENERATED RANDOM CODE PRACTICE MATERIAL

TAPE SPEEDS	#
401 5, 10, 15, 20 WPM	
201 5, 10 WPM	
202 10, 15 WPM	
203 15, 20 WPM	
101 25 WPM	
102 30 WPM	

EACH ONLY \$3.95 plus .25 handling
Ohio residents add 4% sales tax.

Each tape one hour in length


COMPCODE, P.O. BOX 13087,
Columbus, Ohio 43213

*Rush \$1 for exciting Surplus and Factory
Closeouts Catalog. Save Big Money.*

ETCO Electronics

Dept 73 Box 741
Montreal, Quebec H3C 2V2 Canada

DIPOLE ANTENNA CONNECTOR

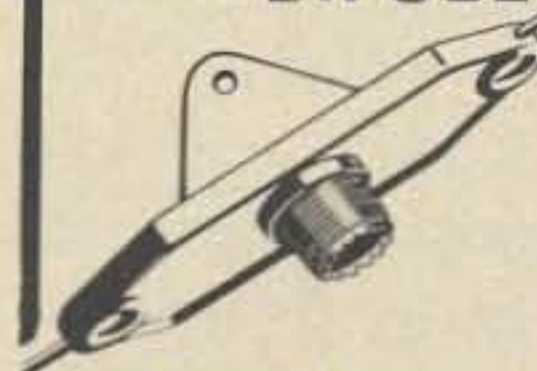

HYE-QUE (HQ-1) dipole connector has coax SO-239 socket molded into glass filled plastic body to accept coax PL-259 plug on feedline. Drip-cap keeps coax fittings dry. Instructions included. Guaranteed. At your dealers or \$3.95 postpaid. Companion insulators 2/\$.99.

BUDWIG MFG. Co. PO Box 97B, Ramona CA 92065

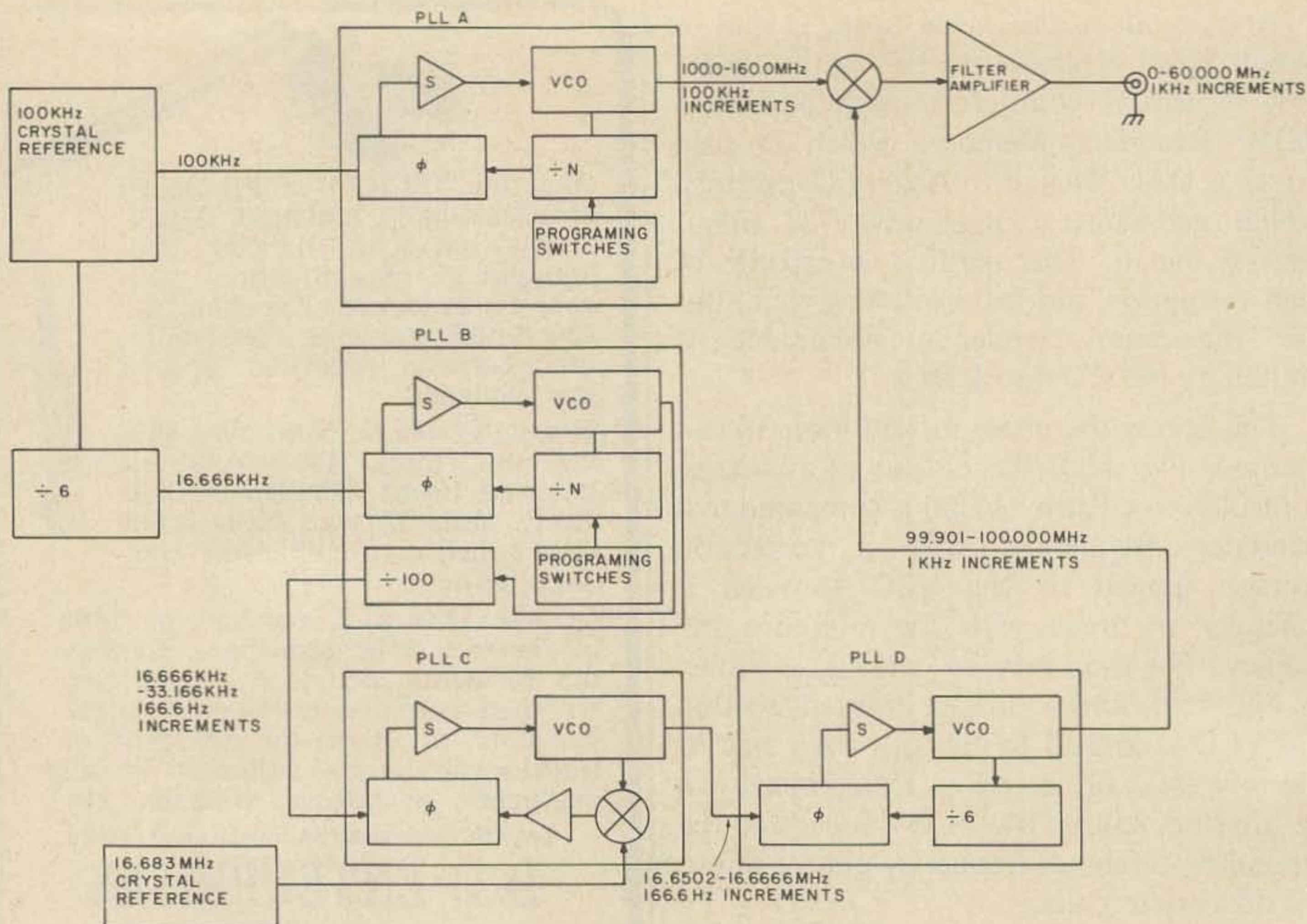


Fig. 2. Frequency Synthesizer.

shown in Fig. 2. It consists of four PLLs connected together.

The operation of PLLs A & B is straightforward. PLL A is programmed by the front panel programming switches to produce any multiple of the 100 kHz crystal reference between 100.0 MHz and 160.0 MHz. PLL B, also programmed by the front panel programming switches, produces any multiple of $16 \frac{2}{3}$ kHz between $1666 \frac{2}{3}$ kHz and $3316 \frac{2}{3}$ kHz.

The output of PLL B is then divided by 100 to produce 16.666-33.166 kHz in 166.6 Hz increments. This is fed into the primary reference input of mixing PLL C.

Instead of dividing the output of its VCO with a programmable divider, PLL C mixes the VCO output with a secondary crystal reference frequency and obtains the difference frequency. The difference frequency is then compared to the output of PLL B and a correction voltage generated to keep them in phase. The net result of this process is to subtract the output of PLL B from the 16.683 MHz secondary reference, giving 16.6502-16.6666 MHz in 166.6 Hz increments.

The output of PLL C is fed into PLL D, which simply multiplies it by six, thus producing 99.901-100.000 MHz in 1 kHz increments.

The output of PLL B is then subtracted from the output of PLL A, giving a final output of 0-60 MHz in 1 kHz increments.

The synthesizer is much more complex than a single PLL, but this is justified by major improvements in performance in three key areas.

The response time of a single PLL with 1 kHz resolution would be around 100 ms; the response time of the synthesizer is around 2 ms.

Noise, both sideband and white, in a PLL with 1 kHz resolution would be totally unacceptable. Noise in the synthesizer originates primarily in PLL A and PLL C. However, PLL A operates at a reference frequency of 100 kHz, which is high enough to get rid of all audible noise, and PLL C uses a special crystal controlled VCO which generates virtually no noise to begin with. The result is that noise is kept 80 dB down.

Finally, the resolution of the synthesizer can be extended to 10 Hz, or even 0.1 Hz,

with no increase in response time or noise. This is done by adding some more PLLs between PLL B and PLL C, as shown in Fig. 3.

The thing which more than anything else made the construction of the synthesizer possible was the introduction by Motorola of the PLL building blocks, especially the 4016 programmable divider, the 12012 prescaler, and the 4044 phase detector. These ICs compressed whole circuit boards into a few DIPs so easy to use that the actual circuit looks like a block diagram. This external simplicity combined with internal complexity can make their operation seem mysterious, so before going on I will give a very brief description of them. Complete descriptions are given in the Motorola data sheets listed at the end of Part Two.

Programmable Dividers

The Motorola set of programmable dividers consists of the 4016 presettable down counter, the 12012 variable modulus prescaler, and the 12014 control logic.

The 4016 counters are down counters with internal zero detection and a program

enable input. In operation they count downward from whatever they are preset to until they reach zero, when they reset themselves

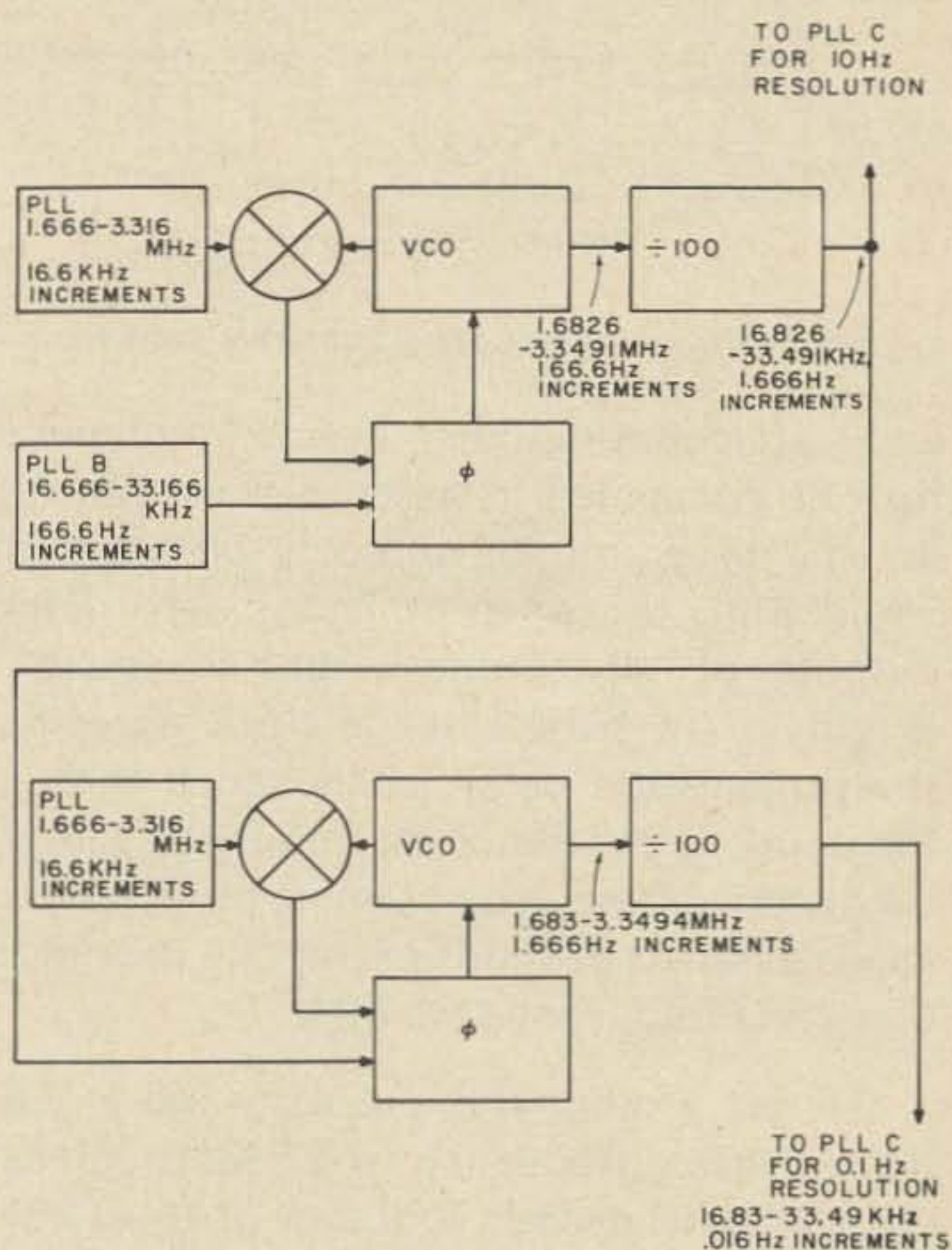


Fig. 3. Extending resolution of synthesizer.

Soon to be extinct . . .

Destined to follow the path of the dinosaur and low taxes . . . GONE FOREVER! Since 73 is going to the new 8½ x 11 format in January, no additional binders for the current 9 x 6 size are being ordered. That means, when the few we have on hand are gone, there will be no more available . . . EVER! They will probably become collector's items.

Keep your pre-1976 issues of 73 safe from being lost or damaged . . . in these handsomely appointed binders with rich red covers and gold lettering. Each binder holds 12 issues . . . making an excellent reference handbook . . . several binders form a quality library you can be proud of.

Order yours today . . . before they are gone . . . only \$4.95 each or 10 for \$45. SEND IN YOUR ORDER RIGHT NOW . . . DON'T MISS OUT ON THIS LAST CHANCE! Order right from this ad . . . by check, BankAmericard or Master Charge (include card number and expiration date).



Get 'em while they last!

LIMITED SUPPLY
ORDER TODAY!
\$4.95 ea. or \$45 for 10

name _____

address _____

city _____ state _____ zip _____

Check/Cash BankAmericard # _____ MasterCharge # _____

Expiration date _____ Signature _____

Send to: 73 MAGAZINE, Peterborough NH 03458

Note: Offer valid only until current supply is depleted.

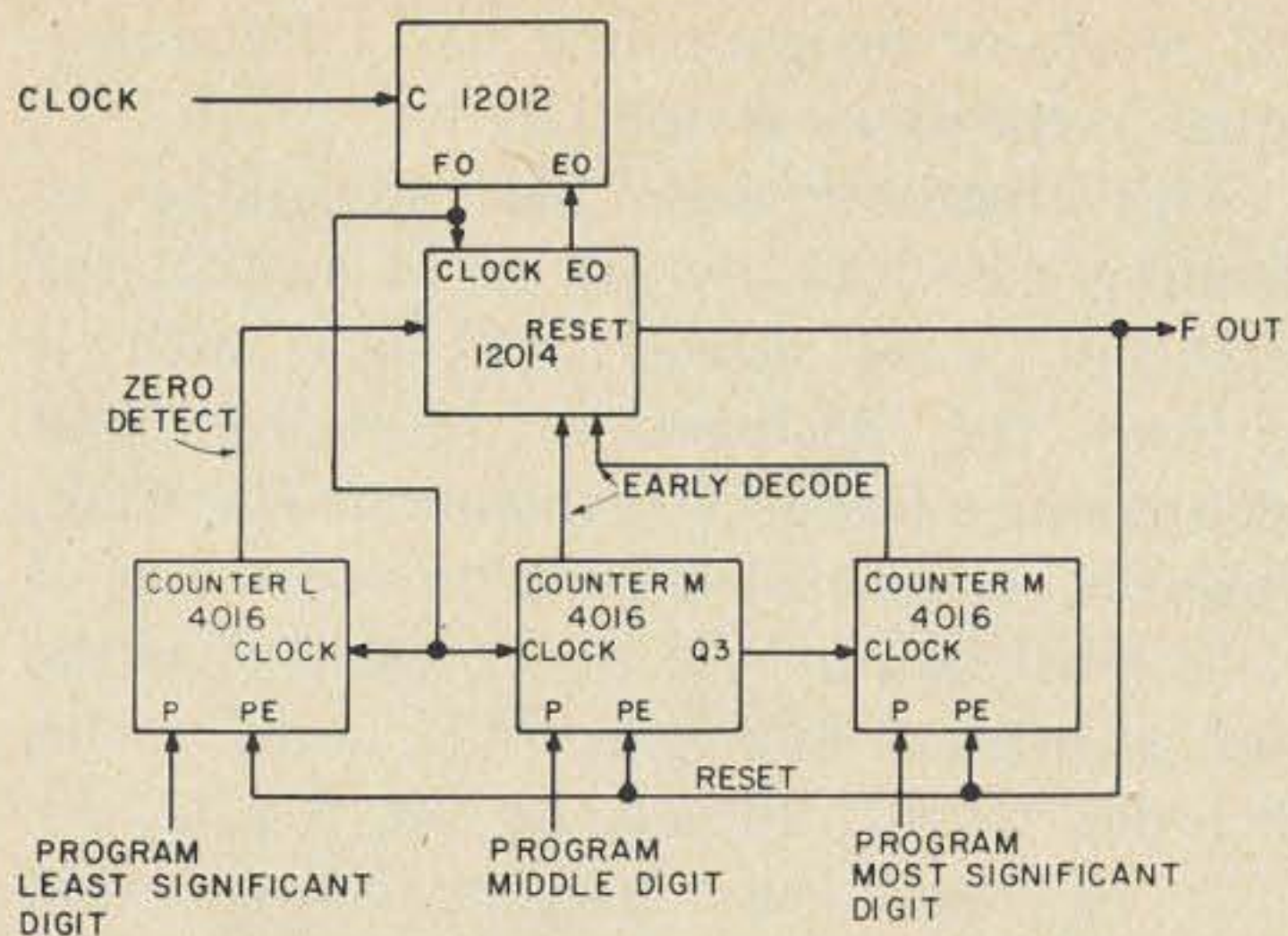


Fig. 5. Block diagram of variable modulus programmable counter.

7 times, a total of 77 counts. It then is reprogrammed to divide by 10, and counts 10 clock cycles M-L, or $38-7=31$ times, for a total of 310 counts. It now reprograms to divide by 11 and starts over, having counted exactly 387 counts, which is another way of saying that it has divided the clock frequency by 387.

This is precisely the way the Motorola 12012 high frequency variable modulus prescaler works. Programming is accomplished by holding the EO input low for divide by 11 and high for divide by 10. In combination with the 12014 control logic and some 4016 counters it forms a complete high frequency programmable counter capable of operating up to 200 MHz. A block diagram of a typical circuit is shown in Fig. 5.

The least significant digit of X is programmed into Counter L, while the remaining digits, M, are programmed into counter M. Let's take 387 again. Counter L is programmed to 7 and counter M to 38. The counter control logic senses that Counter L is not at zero, and programs the prescaler to divide by 11. Every time it counts 11 clock pulses it produces a single pulse which counts both the L and M counters down by one. When the L counter reaches zero, the control logic reprograms the prescaler to divide by 10. The prescaler now produces a single pulse for every 10 clock pulses, and the M counter, now down to M-L, or 31, continues to count down. When it reaches . . .02 the control logic as described earlier resets both counters, and the process begins again. The counters are reset once every $11L+10$ (M-L), or X pulses, and thus

PEN OR PENCIL HOLDERS

Approx. 8" long
1 1/4" wide 1 1/4" high

\$2.50

Plus postage and handling 50¢
50¢ extra for name on back



Also

Name Plates In Plastic \$1.25


HAROLD W. HASBROUCK

1157 Palms Blvd. Venice, CA. 90291

500 MHZ PRESCALER

Extend the range of your present frequency counter to measure through 500 MHz (typically 525 MHz). Works into any standard counter rated for 5 MHz or higher. A must for work on 2 meters, 432 MHz and commercial high bands.

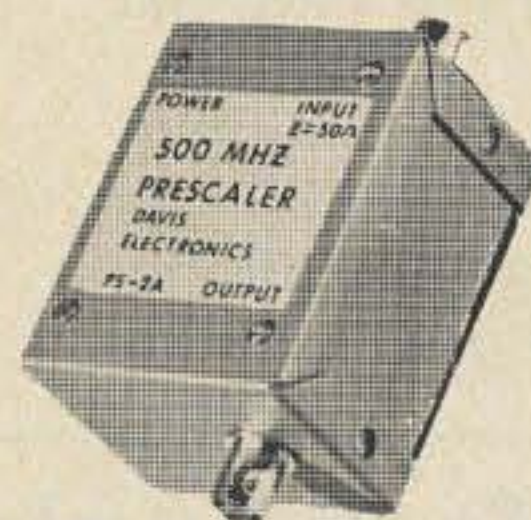- 150 mv sensitivity
- Input overload protected
- 50 ohm input Z
- Small size
2 3/4 x 2 1/8 x 1 5/8"
- BNC connectors
- Divide by 100 or 10
- Light blue case
- Model Ps 2A \$99.95



Prescaler is shipped assembled, tested and ready to operate. Complete with line cord power supply.

DAVIS ELECTRONICS

636 Sheridan Dr., Tonawanda, N.Y. 14150 716/874-5848-9

YOU ASKED FOR IT! ECM-5B FM Modulation Meter

ONLY \$132 less batteries and crystals

- 0-7.5 kHz deviation peak reading
Meets commercial requirements
- Operates 30-500 MHz
- Crystal Controlled for easy operation
- Telescopic antenna

- NEW OPTIONS**
- NICAD power pak \$20.46
 - Charger \$29.95
 - Audio/scope output with earphone \$12.95

Write or call for complete info.



Send check or money order for \$132.00 plus \$1.50 for shipping. Indiana residents add 4% sales tax. Crystals for 146.94 MHz \$3.95. All other freq. \$7.10.

ECM

ECM Corporation
412 North Weinbach Ave.
Evansville, Indiana 47711
812-476-2121

DIXIE TEC

Private tutoring for any
class FCC license

\$10.00

**DIXIE TEC Box 8352
Savannah, Georgia 31402**

TELETYPE

UT-4 - ASCII to BAUDOT CONV. - AUTO
CW IDER - AK-2 AFSK - XK-2 XTAL AFSK
- and LOTS MORE.

CALL OR WRITE FOR DETAILS AND PRICES

edi

Electronic Development, Inc., P.O.
Box 951, Salem, Oregon 97308 (503)
399-9660.

BE HEARD!



Put some real
MUSCLE
in your 2M FM signal.

P15A1
1-3 watts in
12-25 watts out
\$55

P50A10
2-18 watts in
14-60 watts out
\$98

P100A10
2-12 watts in
40-110 watts out
\$198

P100A20
18-35 watts in
90-120 watts out
\$155

*The finest state of the Art Class C
Power Amplifiers
One year warranty! ORDER TODAY!*

M-Tech Engineering, Inc.

Box C, Springfield VA 22151 (703) 354-0573

M-TECH . . . The Quality Company

POWER SUPPLY KITS

\$18.95 POSTPAID

±15v at 50ma Short Proof
+5 or +12 at 100 ma

IC REGULATED. All Parts Including -
Printed Circuit & Transformer. You
Supply Line Cord, Switch, & Case.

LIMITED SUPPLY SEND TODAY!

SPACE TIME
PRODUCTIONS

BOX 191
CARBONDALE, ILL
62901

DIGITAL FREQUENCY COUNTER

50 Hz to over 250 MHz - 8 digit LED display
less than 90 mV to 45 MHz - less than 250 mV
to 250 MHz - packaged 10 MHz clock - ± 1
PPM stability - AC or DC operation - wired
and tested. **CALL OR WRITE FOR DETAILS
AND PRICES**

edi

Electronic Development, Inc., P.O.
Box 951, Salem, Oregon 97308 (503)
399-9660.

73 GOT US COVERED?
is always looking for photos or art-
work suitable for cover use - and the
pay is good.

the reset, or program line has a frequency equal to the clock divided by X.

This method has the advantage of dividing the clock by 10 or 11 so that the relatively slow 4016s can deal with it without the decrease in resolution that accompanies fixed ÷10 prescaling. There are, however, some restrictions on the value of X. It must be possible to represent it as the sum of integral multiples of 10 and 11. This includes 10, 11, 20, 21, 22, 30, 31, 32, 33,99, and all integers above 100. Obviously this method is restricted to applications where X is larger than 100. In the synthesizer described here the minimum X is 1000, so this is no problem.

The 12012 prescaler is an ECL device, as indeed it has to be to operate at 200 MHz. However, in order to make it easier to use it contains on chip ECL-TTL and TTL-ECL translators on the FO output and EO input, which explains the apparent abandon with which it is connected to the TTL control logic. The clock input remains standard ECL 10k, and is best driven from an ECL line receiver such as the 10216.

Phase Detector

The 4044 phase detector consists of a digital phase detector and a charge pump. When used with an integrator it forms a near ideal PLL building block. The logic of the phase detector is quite complex, and, as a full description is given in the data sheet, I will give only a brief functional description here.

The phase detector has two inputs and two outputs. It accepts the reference fre-

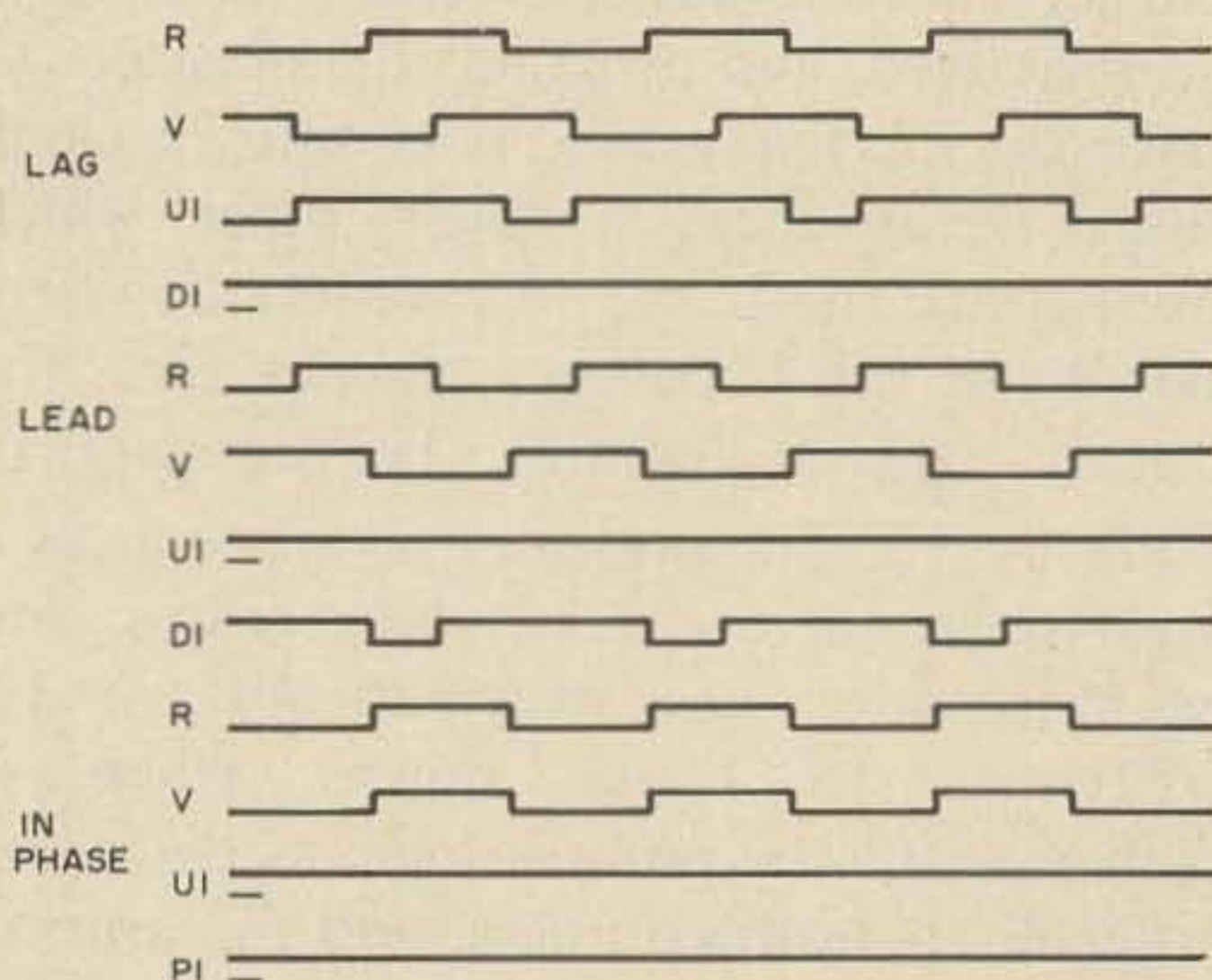


Fig. 6. Waveforms of 4044 phase detector.

quency at one input, and the output of the programmable divider, mixer, or VCO at the other input. It is sensitive only to the downward transitions of the inputs, so duty cycle is unimportant.

If the downward transitions of both inputs occur together, that is, if they are in phase, both outputs remain high. If one input lags behind the other, a pulse appears at the appropriate output, as shown in Fig. 6. The phase detector also prevents harmonic lockup. The outputs of the phase detector are fed into the charge pump, which consists of an inverter and a couple of diodes. The charge pump is connected to an integrator, and the output of the integrator is connected to the VCO, thus closing the loop. See Fig. 7.

Operation is as follows. If the VCO and reference are in phase, no pulses appear at the output of the phase detector, the charge pump neither pushes nor pulls current out of the integrator, and consequently there is no change in the output of the integrator or in VCO frequency. If the two are not in phase one of the outputs of the phase detector pulses, the charge pump pulls or pushes current out of or into the integrator, and the control voltage moves up or down to correct the error.

This system has the advantage that when in lock the only ripple appearing in the control voltage — which causes FM of the VCO, or sidebands — is the result of leakage in the integrator and charge pump, and these can be made very small.

The response characteristics of the loop are determined by the components used in the integrator. The values of these components are a compromise between low sideband-causing ripple and fast response time, and are rather critical. A full explanation of the equations used is given in the 4044 data sheet, so I will give only a highly

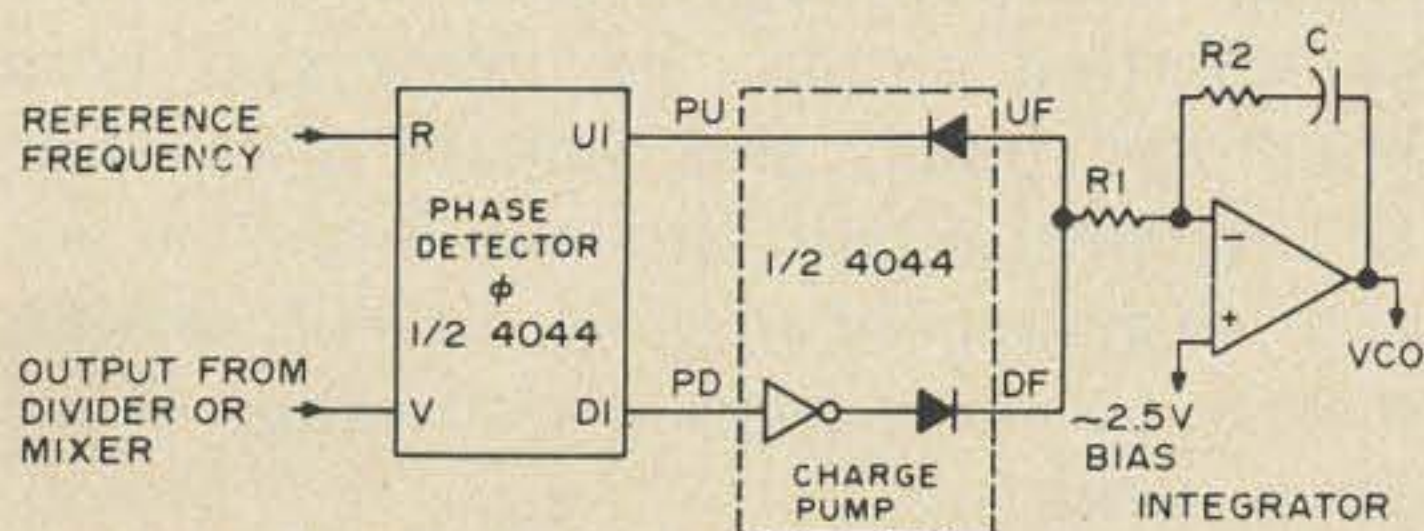


Fig. 7. 4044 phase detector.

ATTENTION METRUM II OWNERS

VANGUARD has a high quality synthesizer made for your rig. You get 2,000 thumbwheel selected channels from 140.000 to 149.995 MHz in 5 kHz steps at .0005% accuracy over the temperature range of -10 to +60 C and your cost is only \$159.95. With the Metrum, one Vanguard synthesizer covers both transmit and receive frequencies.

For complete details and photo see our half-page ad in this magazine.


VANGUARD LABS

196-23 Jamaica Ave., Hollis, New York 11423

ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sine wave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in

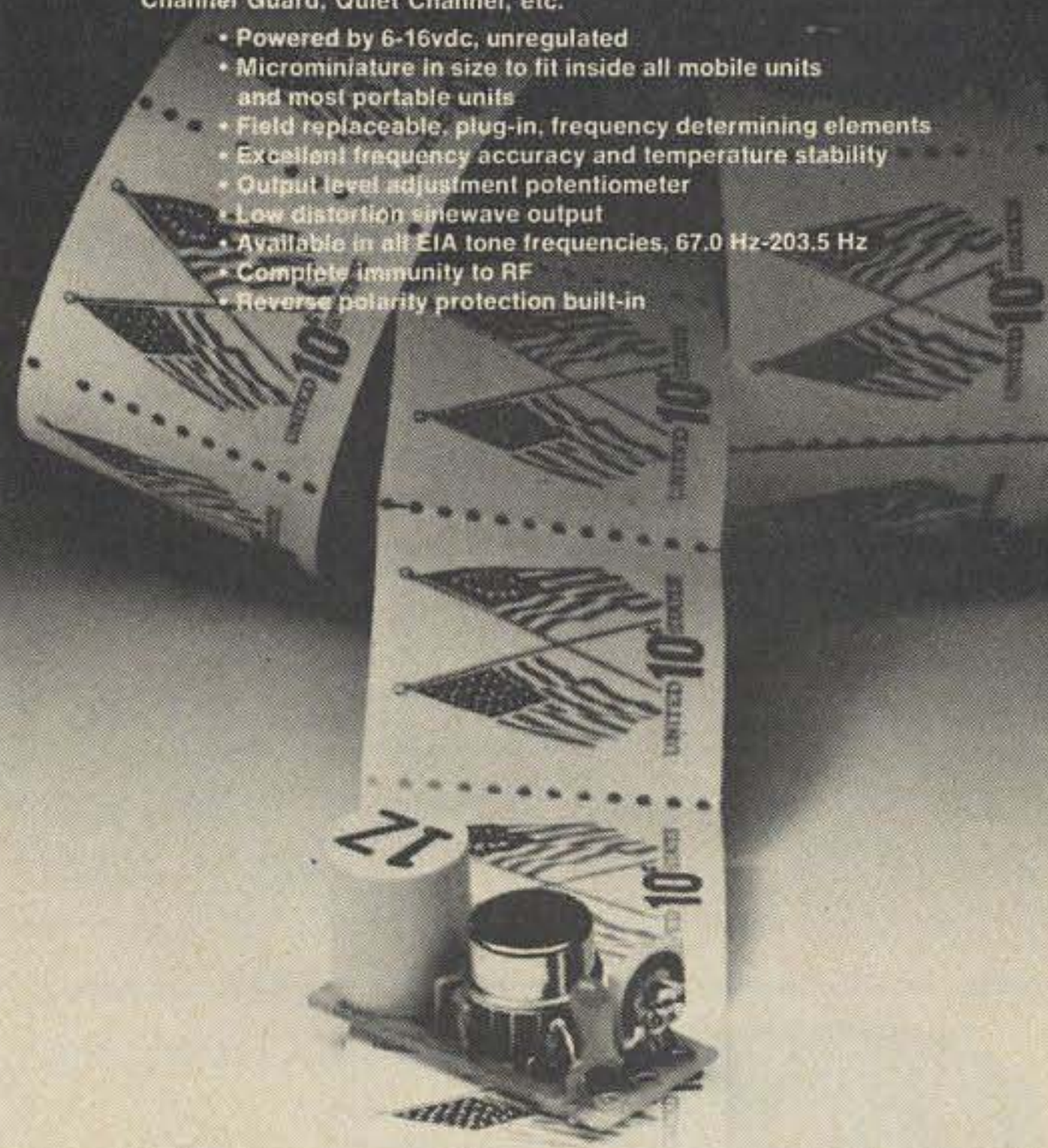

\$29.95 each

Wired and tested, complete with K-1 element

communications specialists

P. O. BOX 153
BREA, CALIFORNIA 92621
(714) 998-3021

K-1 FIELD REPLACEABLE, PLUG-IN, FREQUENCY DETERMINING ELEMENTS

\$3.00 each

CW FILTER



- New! Stereo enhancement.
- 8 pole IC filter.
- 80 Hz bandwidth.
- Steep skirts. No ringing.
- Simulated-stereo technique filters out QRM but lets you hear off-frequency answers to your CQ's. Great for contest ops, CW nets.
- 800 Hz center frequency. (Stereo headphones, 9-v battery not included.)
- Send for free brochure.
- Order direct. \$39.95 PPD U.S. and Canada. (Add sales tax in Calif.)

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

YOUR HAM TUBE HEADQUARTERS!

TUBES BOUGHT, SOLD AND TRADED
SAVE \$\$\$ - HIGH \$\$\$ FOR YOUR TUBES

MONTHLY SPECIALS

2K25	\$ 28.00	6146B	\$ 4.25
3-500Z	42.00	6360	3.75
3-1000Z	120.00	6883B	4.50
4-125A	42.00	6939	9.00
4-400A	45.00	811A	5.00
4CX250B	24.00	813	18.00
4X150A	19.00	7735A	38.00
572B	18.00	8236	22.00

BRAND NEW**FACTORY GUARANTEED**

TOP BRAND Popular Receiving Tube Types.
BRAND NEW 75%+ Off List*Factory Boxed.
FREE LIST Available - Minimum Order \$25.



COMMUNICATIONS, Inc.
2115 Avenue X
Brooklyn, NY 11235
Phone (212) 646-6300

SERVING THE INDUSTRY SINCE 1922

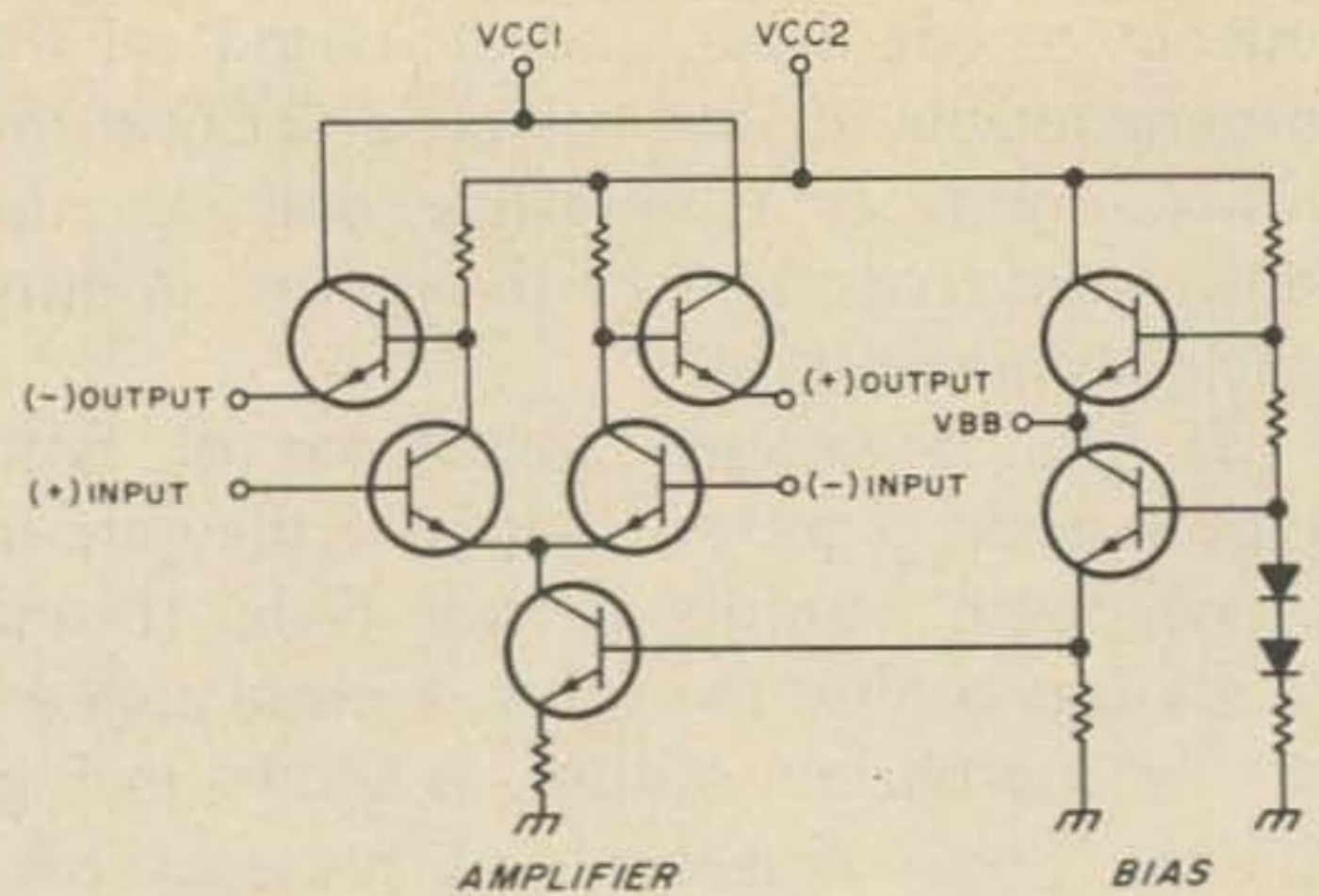


Fig. 8. 10216 amplifier.

abbreviated form below.

$$C = \frac{K}{N (F_{ref})^2 \cdot 25}$$

where

$$K = \frac{F_{MAX}^{VCO} - F_{MIN}^{VCO}}{V_{MAX}^{VCO} - V_{MIN}^{VCO}} \cdot 2\pi$$

$$N = \frac{F_{MAX}^{VCO}}{F_{ref}}$$

$$R_1 = 1k$$

$$R_2 \approx \frac{40}{F_{ref} \cdot C}$$

Line Receiver

The last IC I shall mention was not specifically designed for PLL applications, but it is nevertheless extremely useful. It is the 10216 MECL 10k triple line receiver. It contains three differential amplifiers, one of which is shown in Fig. 8. These amplifiers have a gain of 16 dB and are useful to well beyond 200 MHz. They are capable of 1/2 volt single ended output into 50Ω, and are of course compatible with ECL logic levels. They work well as buffers, amplifiers, and oscillators. Two rules should be observed. First, the gain from an input to the inverted output is much higher than that to the non-inverting output, so unless you need differential inputs and outputs, always use the inverting output. Second, always tie one input of an unused amplifier to VCC or VBB in order to maintain proper operation of the bias network.

Next month: Circuitry and design guidelines.
... CALVIN

Bridging the Information Gap

A recent QST article¹ pointed out how one amateur group identified the need for and then constructed a public relations program, largely by taking advantage of available resources. While the author describes a sound and effective approach to solving a problem, he touches on only one aspect of a profession which has been given the generic title of "public relations," and one which holds important ramifications for amateur radio.

There is much more to the process than trying to keep the general public informed of our activities, and in an age when amateur radio is rapidly undergoing an identity crisis of its own, it is to the advantage of ham radio clubs at all levels to think in terms of a total information program.

Unfortunately, the term "public relations" is overworked, negative in its connotation, and erroneous in its application. Replace the concept of a smooth-talking, glad-handing PR man with that of a well-organized director of information who is concerned with three broad program elements: public information, internal information, and community relations. While these three elements are designed to meet different objectives and it is frequently hard to determine where one ends and another begins, they all eventually come together to produce some rather effective results.

Internal Information

For years amateur radio groups have worried and fretted about getting their story told to the general public. This is important

and admirable, but in the rush to make certain that the local community knows all about the preparations for Field Day or how the local repeater club can serve the city rescue squad, we all too frequently overlook the information needs of amateurs themselves.

It shouldn't come as too much of a surprise to learn that not all hams are League members nor even belong to the local radio group. These individuals have a right to know what's going on in the amateur community and how it affects them, and there is probably no better way of getting the word out to everyone than through a newsletter or club newspaper.

Any internal publication should probably include at least three major sections:

- 1) a general section which includes news of wide relevance (meeting schedules, awards, hamfests, impending elections, etc.);
- 2) a special division which dwells on such specialized facets of amateur radio as repeater operations, VHF/UHF operating, and contests; and

- 3) a classified section in which hams can list items for sale or their individual needs. This last element might be expanded to include projects being worked on by club members. And, the classified section might be of some interest to electronic stores in the area who could be "talked into" spending a few dollars to advertise therein and thus provide the club with added revenue and a means to defray the cost of publishing the paper.

Your distribution list for the newsletter should probably include other organized amateur groups throughout the state on a reciprocal basis. It's always nice to know

¹Keith, Don, "Getting the Story Told!", *QST*, October, 1974, pp. 49-51.

what other clubs are doing, and many local problems can be solved from a lateral cross-feed of information.

From an internal standpoint, it's generally a good practice to know the names, calls, and addresses of all hams living and operating in your "sphere of influence." Why not purchase a copy of the Amateur Callbook at least twice a year and delegate someone to pore through the listings for your call area and compile a list of the local stations. Periodically you might send non-members a copy of the club newsletter, possibly generating enough interest on their part to drop by and attend a meeting.

Public Information

No matter how you view this function, perhaps the most important rule here is that in dealing with the local print and broadcast media you want to present your news story or feature in such a manner so as to not turn them off. In other words, don't make mountains out of molehills by exaggerating the importance of the story. You fool no one, least of all a harried city editor or news director who is already overworked.

The basic objective of the public information element is informing the local community — laymen — about a particular facet of your amateur radio operation that is or should be of some interest or relevance to them. I don't think the public audience is too interested in knowing the results of your routine meetings or who participated in the last VHF Party. But there may be an angle in the composition of your group (the butcher, the baker, the candlestick maker, who are all hams) or how the new two-meter repeater will benefit the community or how the club's TVI committee responds to complaints. Be honest with yourself in your appraisal of a story's news value.

If I had to recommend one step to take before doing anything else, it is to develop contacts at each newspaper, TV, and radio outlet in the community. In the case of the newspaper it's the city editor or science editor while at the broadcast media you'll want to know the news director. Introduce yourself, present a copy of your club's fact sheet, tell him you'll be contacting him periodically with stories, and ask what you

can do in preparing a story that will help in getting it published or put on the air. Don't become pushy or develop the attitude that you have a right to get publicity. Like every other special interest group in the area, you're competing for a piece of the pie and just how big that piece will be depends largely on how realistically you define your objectives, and the expertise you use in trying to accomplish them. You can succeed, but in addition to practicing the ABCs of basic journalism (accuracy, brevity and clarity) add honesty and tact.

Public information encompasses more than preparing a news release as the result of something happening or scheduled to happen; it should be continuing without being obtrusive. Information kits placed in strategic locations can accomplish this. A kit should include a fact sheet (a resume of the club's history and objectives), copies of recent articles concerning the club, an up-to-date list of officers, information about repeaters, and anything else that might be of interest to the non-amateur reader. Place copies of the kit with the local chamber of commerce and at information centers throughout the area.

As a final note about the public information aspect, I recommend strongly that if your group includes a member who has any experience at all in working with the media ask him to handle this task or go all the way and appoint him your director of information. His qualifications make him a natural for the job, and if he has any interest at all in amateur radio he'll find some way to accommodate the group's program in his schedule of activities.

Community Relations

The community relations element probably comes closest to the stereotype of the old PR concept, for the objective here is primarily one of fostering within the community an atmosphere friendly to the conduct of amateur radio operations. And after this atmosphere is established, we probably should want to capitalize on it by going one step further: proselytizing to seek new amateurs.

A comm rel project is generally designed to let the public know what we're up to in general and how this affects the community.

In this sense, comm rel approaches the public information function, except that the goal is not only to inform but to deliberately try to influence attitudes as well.

Three types of activities come to mind and ought to be included in your club's repertoire: a speaker's program, an open house, and participation in selected community-wide projects.

Service organizations (Kiwanis Club, Rotary International, Lion's Club, etc), church groups, Boy and Girl Scout meetings, high school science clubs, and women's clubs all need speakers; it isn't too presumptuous to think that each might be interested in hearing an informative presentation on amateur radio.


A club member who can speak in public, a well-written script, a 35mm slide projector, and possibly a tape recorder can be assembled to form a briefing that can highlight virtually any kind of club gathering.

Plan the briefing well, organizing in rhetorical fashion the major points you're going to cover by means of an introduction, a body, and a conclusion. Once you've introduced the topic by showing its relevance to the audience, you'll probably be speaking about two major points: amateur radio in general (what it is and a brief history) and how your club fits into the overall picture. At the end you'll summarize and point out that your club can provide more information to interested persons. This is only a very skeletal approach to developing a good briefing; there are others, but remember that the important thing is to organize the script logically and coherently.

Rather than attempt to bring an entire station to the scene of the speaking engagement (where "gremlins" invariably appear and destroy whatever measure of realism and authenticity you hope to achieve), capture on magnetic tape off-the-air QSOs as examples to work into your briefing. And while you're at it, you might as well take the extra step and shoot 35mm slides to accompany the entire briefing, including summaries of your important points (lettering kits are fairly inexpensive and easy to use) and plenty of shots of *people* operating equipment, erecting antennas, etc.

Plan for about a twenty-minute presenta-

FIBERGLASS ANTENNA CENTRAL INSULATOR

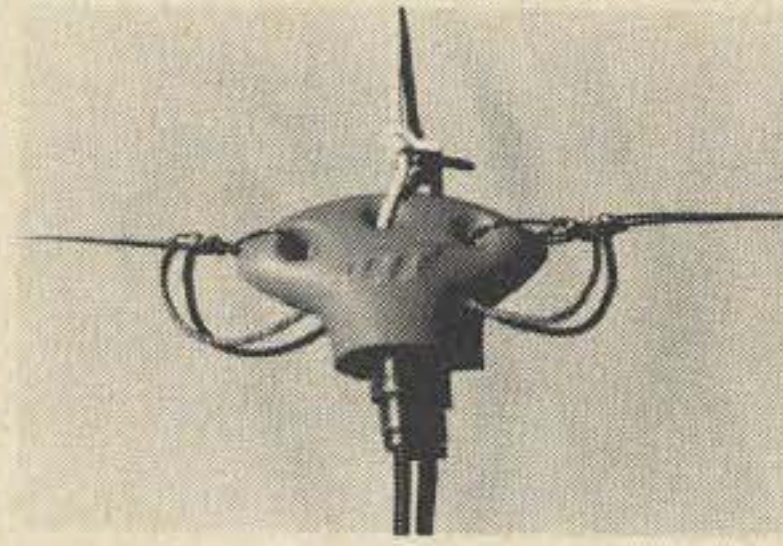

Completely watertight with SO 239 inside to prevent water going to coaxial line. Price \$5.95

Central insulator only without SO 239. Price \$1.95

Heavy duty 2KW PEP TRAP 80--40 tension resistant = 1000 LBS. could be used on guy system. Price \$15.95

Postpaid—Quebec residents add 8% tax

Jac Tenna Electronic
13850, Rte. Marie Victorin,
Tracy, Quebec Canada

5 square inches

That's the amount of space in this 1/8 page ad — more than enough to put your company's message into tens of thousands of homes around the world.

It pays
to advertise in

73

Keyer Module



\$40

This new, low-cost, two-ounce keyer module has full squeeze or normal operation, yet draws less than one ma., key down! Attach a 9v transistor battery and forget it! Has dot, dash and space memories. Use with any key lever and 4 to 15 vdc source. Write or call for brochure. (303)794-7234. Dealer inquiries invited.

CONTROL SIGNAL CO 5964 W. COLUMBIA PLACE
DENVER, COLORADO 80227

tion and allow approximately ten minutes for answering questions. And, make certain that the speaker is an individual who is both knowledgeable about his topic and capable of speaking before an audience.

Besides an active speaker's program, the radio club can open its doors to the community once a year, assuming, of course, that the group has available a building or room where equipment can be set up and which can accommodate a large number of visitors.

Are civic exhibitions held in the community periodically? If so, then seek permission to set up exhibits — attractive booths which graphically depict the role of amateur radio in the community. Use photographs and charts as visual aids.

And finally, from time to time various groups within the area sponsor projects in which amateur radio can make important contributions. Watch for such things as Leukemia Walkathons, parades, and other projects where FM repeaters can provide needed communications links. Volunteer your services — don't wait to be asked.

In summary, every amateur group, no matter how small, can only benefit from a systematic and organized information program. With our decreasing numbers and an ever-growing public service and CB group (with their associated manufacturers' lobbies), amateurs can no longer afford to rely solely on "PR" as a means of bridging the information gap.

Now, perhaps more than ever, we need to insure that amateur radio is known by as many people as possible for what it is, not necessarily to compete with citizens band and other public service operations *per se* but rather to make certain that our interests are protected. In order to do this, we need to have a friendly environment in which to operate as well as an informed community of fellow hams and laymen alike. "PR," as anachronistic as the butch haircut and the liquid-fuel rocket, no longer meets the demands of an information-oriented society. The triangular total information program, however, is geared to meet these demands, and while the development and implementation of such a program is going to require a certain amount of effort, dedication, and

even money, the results will certainly justify the expenditure.

Several Considerations for an Information Program

1) Appoint as director of information an individual who wants to succeed. While a background in advertising or journalism may certainly be helpful, it's more important that the director be well-motivated.

2) At the beginning of the year, compile a list of your information program objectives. Know what you want to do, why you need to do it, and how you'll go about doing it.

3) Meet personally with editors and news directors. Also include on your visit list the director of information for the local chamber of commerce.

4) Allow only one spokesman for your club; the group must speak with only one voice to preclude embarrassing contradictions.

5) A written story is usually more valuable to a newsman than a verbal description. The reporter can always rewrite the article, and he'll contact you if he needs more information.

6) Spend some money for a typewriter and letterhead stationery. If the club budget allows you to really splurge, invest in a decent camera and some photo supplies.

7) Publish a club newsletter on a periodic basis, sending copies to other clubs in the state and to non-members as well.

8) Develop an informative briefing about amateur radio and your club (preferably a 35mm slide presentation).

9) Actively seek out speaking engagements where you can present your briefing.

10) Don't make mountains out of molehills and expect to pass them off as legitimate news stories to the local media. Be factual, truthful, and to the point.

11) Avoid shouting matches with local CB groups; there's sufficient room for both activities, and bear in mind that while a stereotype of a CB operator has emerged, we have our own problem children.

12) Find projects that will benefit the local community — a massive campaign which tells what you can do in all types of future disasters is fine, but it's the present that counts.

...K3DSQ/4

Which would you rather be, jack-of-all-bands or master of one?

We make our SkyClaw™ vertical antennas for the ham who doesn't want to be a jack-of-all bands. Because no antenna can be all things to all people. You tune our SkyClaw™ to your choice of 160 (50kHz bandwidth), 80 (200kHz bandwidth), or 40 (the whole band). We don't fudge the tuning for multi-band performance. We put the materials into it that let you pump the legal limit through it. We build it to withstand more wind than you'll find in a QSO on 75.

And we deliver the whole thing for \$79.50, postpaid in the USA. Radial and phasing harness kits are available, too.

It's self-supporting. Weatherproof. You put it up yourself with just 4 tools. It stands

24'7". And you connect to an SO-239 in its base.

Now, then. Have you decided which kind of operator you want to be?

Yes, Master.



**It's faster than a speeding bullet!
More powerful than the legal limit!
And able to match long wires with a single bound!**

SuperTuner



Did we mention smaller than a breadbox?

This amazing visitor from far-off Ohio has powers and abilities far beyond ordinary mortal antenna tuners. Single-handedly, it matches coax feed, random wire, balanced or unbalanced line on any band, 160 through 10, up to the full legal limit. And Dentron's new Super SuperTuner handles a full 3 KW PEP—in case you-know-who passes you-know-what. SuperTuner and Super SuperTuner. Who, in black wrinkled finish, fight a never-ending battle for truth, justice, and juicier signals. Up, up and away. Just \$119.50 ppd. in the USA.

KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria IL 61614, Phone 309-691-4840
Cliff Morris W9GAO — Jim Plack WB9BGS

NEW PRODUCTS

from page 19

LSG-16 RF WIDE BAND SIGNAL GENERATOR

The LSG-16 wide band signal generator, pretty darn good for service, hobby, education or industrial use, is now being made available by Leader Instruments Corp. of Plainview, N.Y.

The new product features an FET oscillator circuitry for high stability performance, plus an accurately calibrated frequency dial. Frequency range is 100 kHz to 100 MHz, and up to 300 MHz on harmonics. Internal modulation is 1 kHz at 30% or higher, while external modulation is 50 Hz—20 kHz at less than 1 Vrms.

The LSG-16 is capable of functioning as a marker-generator when used in conjunction with a sweep generator, and will check and align rf and i-f circuits in TV, FM and communication-type receivers and transmitters. Use of the product is further extended by provisions to accommodate a 1—15 MHz crystal.

The LSG-16 offers a 115/230 V, 50/60 Hz, 3 VA approx. power supply. Measuring 6"H x 10"W x 5"D, and weighing 5.5 lbs, it sells for \$109.95.

HICKOK FUNCTION GENERATOR

So who needs a bunch of functions, you ask? Better yet, what is a function in the first place, and what

on earth do we need with 'em?

In olden days we had sine wave oscillators... a sine wave was one type of function. Then some smart guy came along and invented square waves... another function. Oscilloscope fans developed an insatiable need for sawtooth waves... still another function. The problem came when one piece of equipment could develop a lot of different types of waveforms... should they call it a sine-square-sawtooth-pulse-etc generator? No. So now we have function generators and they are getting pretty common... and the price has been going against the grain, being one of the few items to drop in cost.


Hickok, one of the older names in test equipment, has come out with a ham-priced function genera-

tor... model 270... weighing in at only \$166. This doohinky does not wash the dishes, but that's about its only limitation. From 1 Hz to 1/2 MHz in six push-button selected ranges, it will turn out sines, triangles, squares, and a variety of pulses, FM, AM/FM mixed, high/low combinations for testing filters, FSK for setting up RTTY gear and computer driven cassettes, AM, swept sine waves, etc.

Also built in is an attenuator going down to -60 dB for checking gain and filter action.

How much longer are you going to suffer along without a modern piece of test gear in your ham shack?

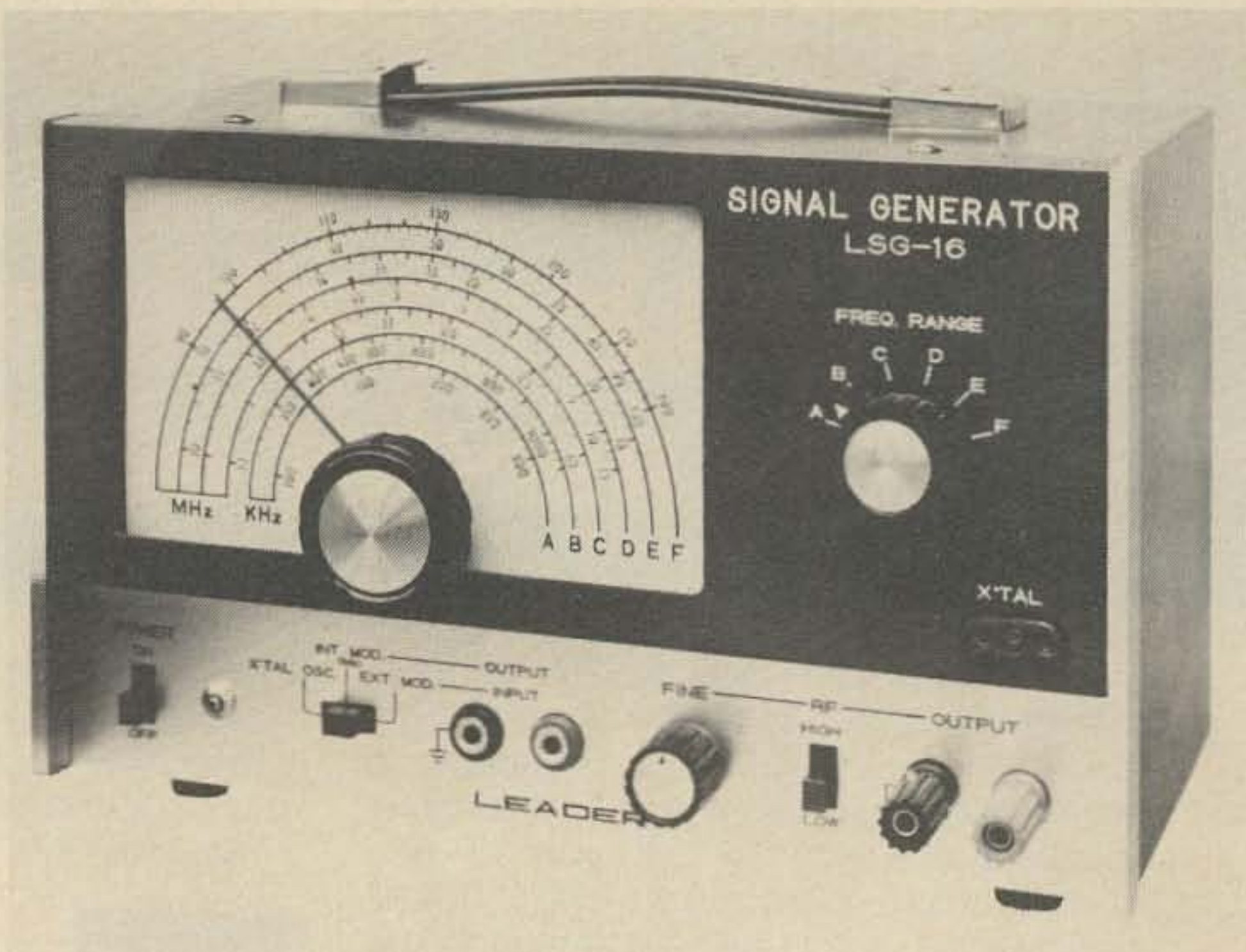Further details are available from Hickok, 10514 Dupont, Cleveland OH 44108.



NEW CODE SYSTEM

Now you can learn the code in a fraction of the time it used to take!



four speeds available

Plays on any cassette player so you can practice anywhere anytime!

5 WPM This is the beginning tape for people who do not know the code at all. It takes them through the 26 letters, 10 numbers and necessary punctuation, complete with practice every step of the way using the newest blitz teaching techniques. It is almost miraculous! In one hour many people — including kids of ten — are able to master the code. The ease of learning gives confidence to beginners who might otherwise drop out.

14 WPM Code groups again, at a brisk 14 per so you will be at ease when you sit down in front of the steely eyed government inspector and he starts sending you plain language at only 13 per. You need this extra margin to overcome the panic which is universal in the test situations. When you've spent your money and time to take the test you'll thank heavens you had this back breaking tape.

6 WPM This is the practice tape for the Novice and Technician licenses. It is made up of one solid hour of code, sent at the official FCC standard (no other tape we've heard uses these standards, so many people flunk the code when they are suddenly — under pressure — faced with characters sent at 13 wpm and spaced for 5 wpm). This tape is not memorizable, unlike the zany 5 wpm tape, since the code groups are entirely random characters sent in groups of five. Practice this one during lunch, while in the car, anywhere and you'll be more than prepared for the easy FCC exam.

21 WPM Code is what gets you when you go for the Extra Class license. It is so embarrassing to panic out just because you didn't prepare yourself with this tape. Though this is only one word faster, the code groups are so difficult that you'll almost fall asleep copying the FCC stuff by comparison. Users report that they can't believe how easy 20 per really is with this fantastic one hour tape. No one who can copy these tapes can possibly fail the FCC test. Remove all fear of the code forever with these tapes.

ONLY \$3.95! 73 is in the publishing business, not tapes, so these are priced much lower than anyone else could sell them. Have you ever seen one hour cassettes for under \$6?

ORDER NOW!

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

- 5 WPM 1 hr cassette \$3.95 14 WPM 1 hr cassette \$3.95
 6 WPM 1 hr cassette \$3.95 21 WPM 1 hr cassette \$3.95
 all four cassettes \$13.95

73 Magazine — Peterborough NH — 03458

Looking West

from page 11

It's funny, but there is a simple solution to this problem, and maybe because I am just an onlooker I can see it. First, for the record, I can and do hear WR6AJL here in the Van Nuys area of the San Fernando Valley, and with the spring-summer inversion with us, their signal strength measured on a Hammarlund HQ-110AC using an Ameco CN-144 converter and Antenna Specialists 1/4 wave Six Meter Vertical is S-8 to S-9 plus 10 dB since early May. Before approximately May 10th, I did not hear AJL at all though others claimed to have. As I said earlier, for my part I couldn't give a row of beans who uses .76 and for what, but if everyone would get off their damn ego trip and learn that it's not all that hard to cooperate with one another, then this whole mess could and would "go away" in record time.

It is a known fact in both commercial and broadcast radio that there are techniques available that will effectively "null" a signal from one area while totally saturating another: phased antennas, directional arrays, etc. By going to a directional system, AJL could survive and flourish along with L.A. simplex and the world could live happily ever after. AJL can serve an important purpose if its owners are willing to take the necessary steps toward that end and



SANDRA delegate responds to SCRA Technical Committee report and announces SANDRA's withdrawal from SCRA.



On tour of JPL after SCRA meeting, Bill Carpenter WA6QZY, SCRA Technical Committee Chairman, explains exhibit.

if, when the AJL signal disappears from LA on .76, so does the AKC signal on .16. All parties have the nation watching them at this moment. If action by either one of them causes failure within the SCRA, then I bid them both beware that such a failure here can and probably will have the most awesome consequences nationally. If the SCRA fails, then most probably it will be the lead for each individual who dislikes something within his area's coordinating body to work towards its destruction. Such would mean the quick end of relay type communication and a return to the "old days" where a VHF mobile could hardly work out of his backyard. I for one have no intention of sitting by and watching this happen.

It's about time we all realize that though we may not love one another as brother and sister, we are by federal decree neighbors in the same relay sub-band — repeater, simplex and remote. There is but one way for us to survive and that is through total open mutual cooperation. Mutual cooperation takes the form of area frequency coordinating groups such as SCRA and its counterparts throughout the nation. These are organizations built on naught more than a handshake, and if the handshake becomes a fist of rage, and each individual or group goes his own way because a decision made in the interest of all does not suit an individual, then all that we have worked for is lost and we might as well pack it in.

To all involved in the present confrontation, beware: The eyes of the nation are watching every move you make. There is a heavy burden on

your shoulders, that of risking the destruction nationally of relay type communications by your actions here. There will be no replay of the old days; this time every move is being watched and being reported. If either party destroys it for the rest of us, then the world will quickly know who is responsible.

A late note: It has been announced that some 15 San Diego Area systems have written to SCRA pledging their support of the organization. SCRA has also stated that it will continue to take whatever steps are necessary to insure a quick solution amicable to all parties.

Other matters covered at the recent SCRA meeting included setting definite jurisdictional boundaries for the organization to administer, action on docket 20282 and the SCRA proposal to the FCC to take part in repeater licensing for Southern California. As to the latter, in a letter exploring such possibilities sent to the FCC, the SCRA proposes that VHF repeater Form 610 applications would be pre-processed and sanctioned by the SCRA prior to FCC filing for a one year test period.

Finally, in answer to a load of mail that all but broke the back of our local postal delivery person, following the publication of my dissertation on split-split repeater systems, the following is the information that I have on where to get some narrower filters for radios using the Mu-Rata brand filters. The address I have is: Mu-Rata Corp. Ltd., Elmsford NY. Thanks to Lou K2VMR for supplying this information. Till next month, that's all there is for now from the "Hot" Southland.

... WA6ITF


GET TO THE FAST TOP!

NOW YOU CAN CHANGE, ADJUST OR JUST PLAIN WORK ON YOUR ANTENNA AND NEVER LEAVE THE GROUND!

ROHN manufactures towers that are designed and engineered to do specific jobs and that is why we have the FOLD-OVER TOWER . . . designed for the amateur. When you need to "get at" your antenna just turn the handle and there it is. Like other ROHN big communication towers, they're hot dip galvanized **after** fabrication to provide a maintenance free, long lived and attractive installation. ROHN towers are known and used throughout the world . . . for almost a quarter century . . . in most every type of operation. You'll be in good company. Why not check with your distributor today?



ROHN **MANUFACTURING**

® DIVISION OF 

P.O. Box 2000 / Peoria, Ill. 61601

Take off your shoes.



Hit the deck in shorts and a tee shirt. Or your bikini if you want.

You're on a leisurely cruise to remote islands. With names like Martinique, Grenada, Guadeloupe. Those are the ones you've heard of.

A big, beautiful sailing vessel glides from one breathtaking Caribbean jewel to another. And you're aboard, having the time of your life with an intimate group of lively, fun-loving people. Singles and couples, too. There's good food, "grog," and a few pleasant comforts...but there's little resemblance to a stay at a fancy hotel, and you'll be happy about that.

Spend ten days exploring paradise and getting to know congenial people. There's no other vacation like it.



Your share from \$245. A new cruise is forming now. Write Cap'n Mike for your free adventure booklet in full color.

SPECIAL HAM DISCOUNT



Windjammer Cruises.

A WINDJAMMER INTERNATIONAL SUBSIDIARY • OTC

Name _____

Address _____

City _____

State _____


Zip _____

Phone _____

P.O. Box 120, Dept. 121

Miami Beach, Florida 33139

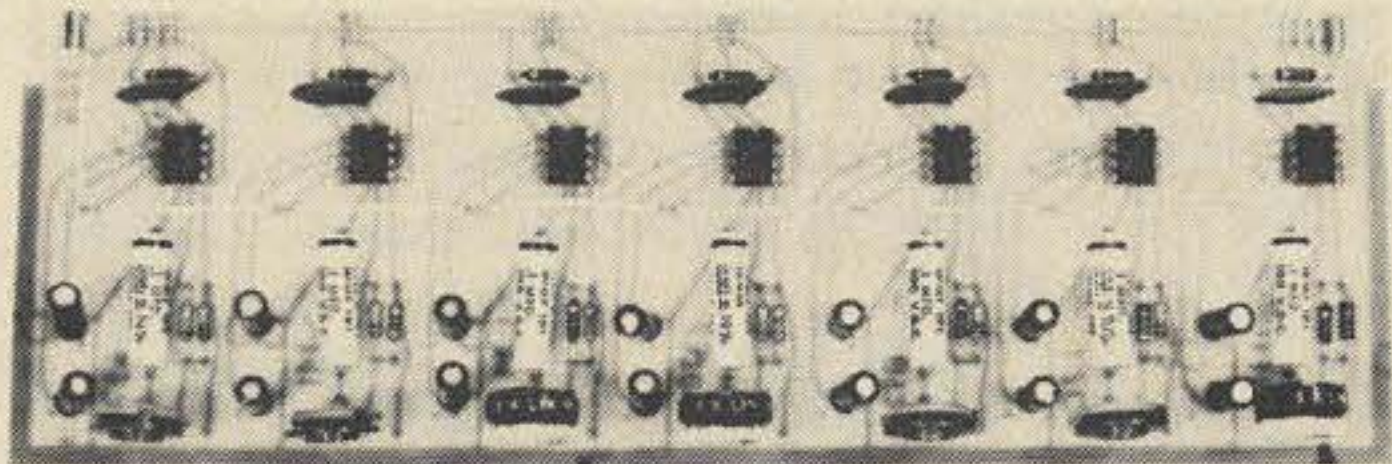watch this space for SPECTACULAR ANNOUNCEMENT WOW! SURPRISE! ZOWIE!



TDC (Tone Decoder Card)

Primary function: to detect touch-tone signals
(0 through 9 and the star & number keys)

A multitude of applications

- A. Touch-tone repeaters
- B. Electronic locks
(access to regenerators, base stations, auto-patch, repeater control, antenna control)

TDC comes completely assembled on a 9" x 3" PC Board. Each Tone Decoder is individually adjustable — easy calibration.

Electronics are centered around the NE567Z. Phase lock loop dip package for fast reliable tone detection. The output of each tone decoder is a logic low (zero volts) when the appropriate tone is detected.

Applications, literature, circuit descriptions, component layout drawing, specific circuits for various applications supplied with the card.

Factory calibrated. Power requirements +5 to +18.


\$139.00/each

TD MODULE (Tone Decoder Module)

The TONE DECODER MODULE is identical in circuitry with the TD Card, except that only one tone may be detected. The Module can be tailored to detect most any frequency.

Applications:

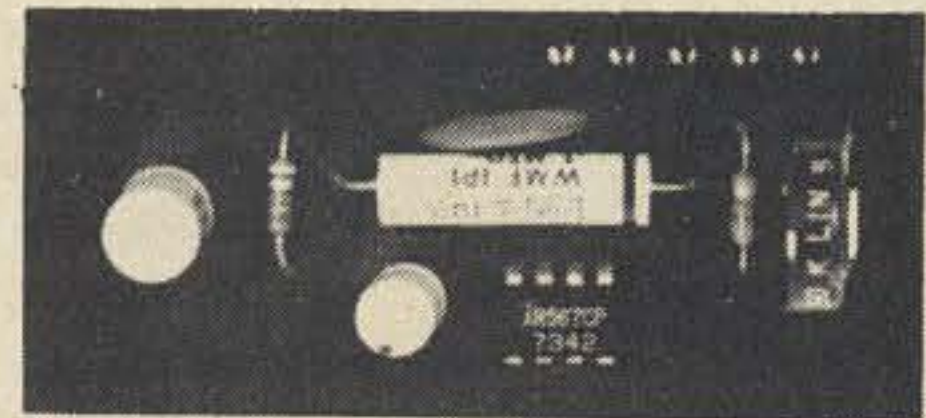- A. FSK detection
- B. Antenna Control
- C. Repeater control
- D. Tone detection
- E. In conjunction with the TDC a user can obtain full 2 x 8 touch tone detection (16 keys).




\$29.95/each

Telecommunication Control SYSTEMS

*Div. of Communications, Inc.
Haverhill and York Sts.
Andover, Mass. 01810*

CONTESTS

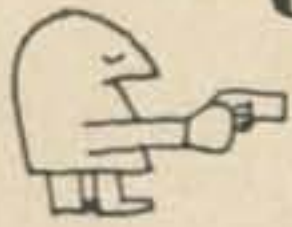

from page 15



316). DX stations may be worked, but do not count as multipliers.

AWARDS:

All amateurs contacting 5 amateurs in each of the 4 states comprising the Division will receive the Delta Achievement Award. Certificates will be awarded to the 3 highest scoring stations in each state in the Delta Division. Fourth and fifth place awards if warranted. Outside the Division, certificates will go to the high scoring station in each ARRL Section and country (second and third if warranted). A plaque will be awarded to the high scoring station both inside and outside of the Division. Plaques will also be awarded to the high scoring portable and mobile stations operating in the Division. A portable or mobile station is here defined as a station operating outside of his home county for the purpose of operating in the Delta QSO Party. Any station disrupting a working Delta Division traffic net or whose log exhibits obvious irregularities will be disqualified from award consideration.

LOGS:

Logs must include date/time, station worked, exchange, band, emission and multiplier. Logs must be postmarked no later than October 21, 1975, to be eligible for award consideration. Logs will be returned if requested. Send logs to Malcolm P. Keown W5RUB, 213 Moonmist, Vicksburg MS 39180.

1975 RTTY ART CONTEST

Contest period runs from
October 1st to end of
November

PRELIMINARY RULES:

Original RTTY art must have been transmitted during this two month period, with copies and prints being mailed on or before a deadline of November 30th. The contest is sponsored by the RTTY Journal. Mail entries to: Donald Royer WA6PIR, 16387 Mandalay Drive, Encino CA 91436.

CALIFORNIA QSO PARTY

Starts: 1800 GMT Saturday,
October 4
Ends: 2400 GMT Sunday,
October 5

The 1975 California QSO Party is sponsored by the Northern California Contest Club. Of the thirty hour period, the maximum operating time shall not exceed 24 hours. Times on/off must be clearly marked in the log. Each time off shall not be less than 15 minutes. All amateur bands may be used, and stations may be worked once on phone and once on CW on each band. A California station which changes counties is considered a new station and may be contacted again on each band and mode.

EXCHANGES:

California stations send QSO number and county. All others send QSO number and state, province or country. California stations may work each other.

FREQUENCIES:

CW: 1805, 3560, 7060, 14060, 21060, 28060. SSB: 1815, 3895, 7230, 14280, 21355, 28560. Novice: 3725, 7125, 21125, 28125. Try 10 meters on the hour and 15 meters on the half hour between 1800 and 2200 GMT.

SCORING:

Each completed QSO counts 2 points. California stations multiply QSO points by the total number of states and Canadian call districts (VE/VO 1-8; max. of 8). California stations may count the State of California as one multiplier and DX stations may be worked for QSO points but not multipliers. All other stations multiply total QSO points by the number of different California counties worked (58 maximum).

AWARDS:

Certificates will be awarded to the highest scoring station in each California county, state, province, and country. Second and third place awards may be made where justified. In addition, certificates also will be awarded to the highest scoring mobile station, portable station, multi-single, and multi-multi entries. A certificate will be awarded to the club submitting the highest aggregate score.

LOGS:

Log information should include date, time, band, mode, callsigns worked, and exchanges sent and received. Please number each new multiplier as worked. A summary sheet should be included showing your callsign, name, address, number of QSOs on each band and mode, total QSOs, total multiplier, claimed score, and whether

the entry is single or multi-operator. All entries must be sent to the NCCC, c/o John Minke W6KYA, 6230 Rio Bonito Drive, Carmichael CA 95608, and must be postmarked not later than October 31, 1975. A large, business-size SASE is requested with each entry. All comments and suggestions will be appreciated.

ROCKY MOUNTAIN QSO PARTY

Starts: October 4
Ends: October 5

The contest is sponsored by the Rocky Mountain Division of the ARRL. The states participating in this QSO Party are Colorado, New Mexico, Utah and Wyoming. Each state is having a separate QSO Party.

CONTEST PERIODS:

2100 GMT to 2400 GMT October 4
0100 GMT to 0500 GMT October 5
1800 GMT to 2100 GMT October 5

EXCHANGE:

Serial number, RST, state and county for stations in the Rocky Mountain Division, while others may omit the county. Stations may be contacted only once per band regardless of mode, except that mobiles may be contacted again if they change counties. Intradivision and intrastate contacts are valid for stations in the Rocky Mountain Division.

FREQUENCIES:

CW: 65 kHz up from the bottom. Phone: Near the edge between General and Advanced. Novice: Near the middle of each band. Stations from outside the division please refrain from calling CQ Contest near these frequencies.

SCORING:

Score 1 point per QSO. Multiplier for Rocky Mountain Div. stations is the sum of states, VE provinces, countries, and Rocky Mountain Div. counties. For all others, the multiplier is the number of counties worked in the state in whose party he is participating. There will be 4 different multipliers, one for each state, for those that enter all 4 contests.

AWARDS:


Appropriate awards will be given.

LOGS:

Send full log data, including exchanges, to Bill Wageman K5MAT, 35 San Juan, Los Alamos NM 87544, no later than November 1, 1975. Include SASE for awards and/or copies of the results.

DUPAGE FM

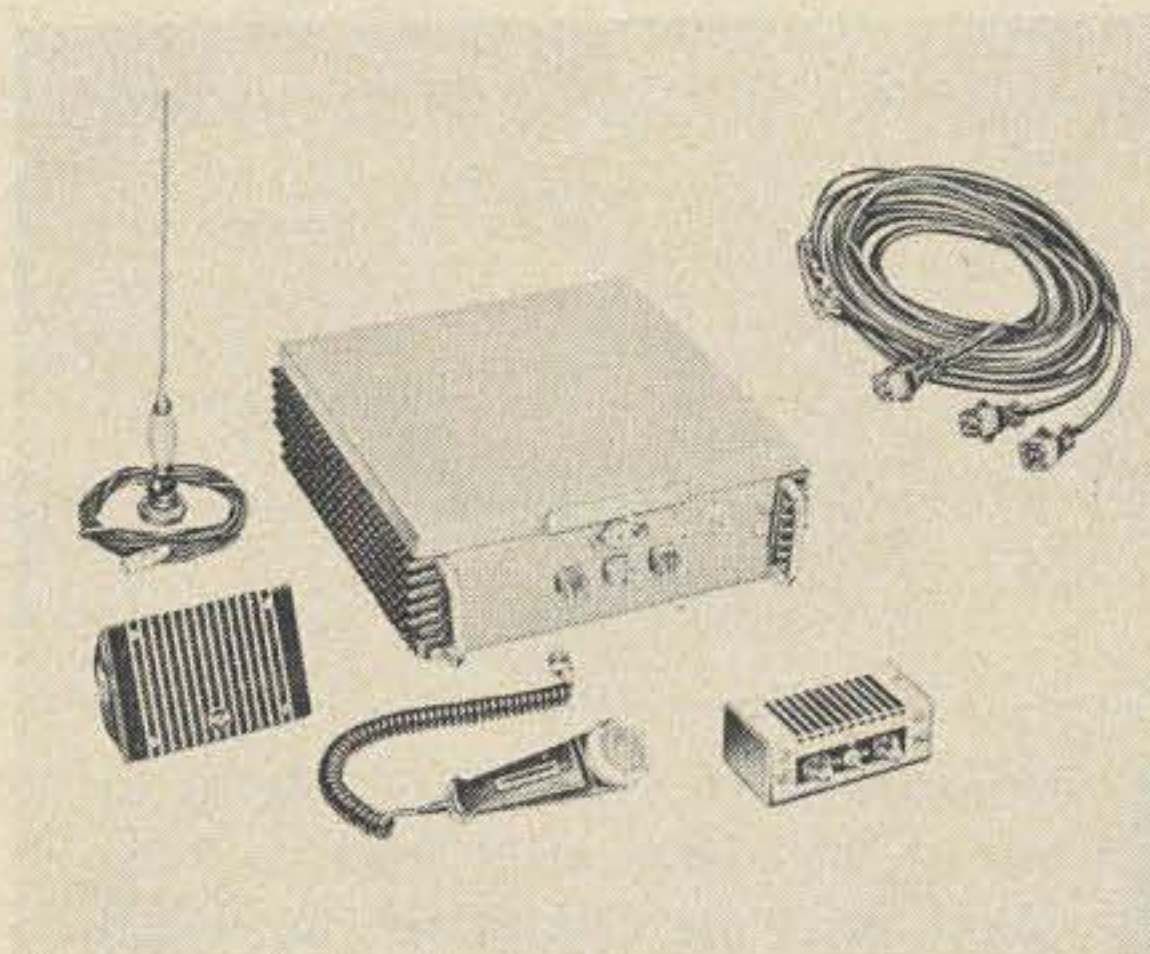WILL NOT BE UNDERSOLD!
A \$5.00 RADIO SALE repeated by
POPULAR DEMAND !!



RCA Model CMFT-50. Fifty Watts output — 30 to 54 mc — Tunes any segment of the band without coil changes. Transistor power supply, partially transistorized receiver with trunk mount, with accessories. Regularly \$125.00 each, buy two for only \$130.00.

RCA Model CMCT-30. Thirty Watts output on two meters. Transistorized power supply, partially transistorized receiver, trunk mount, with accessories — Regularly \$100.00 each, buy two for \$105.00.

General Electric MA/E-13N. Thirty Watts output in the 30 to 50 mc band. 6/12 volt vibrator power supply. Trunk mount, with accessories. Regularly \$90.00 each, two for \$95.00.

General Electric Model FA/E-16N. Sixty Watts output in the 30 to 50 mc band. 6/12 volt vibrator power supply. Front mount, accessories. Regularly \$100.00 each, two for \$105.00.

SEND A CHECK OR MONEY ORDER TODAY TO:

DU PAGE FM INC. P.O. Box 1 Lombard, Ill. 60148
(312) 627-3540

TERMS: All items sold as is. If not as represented return for exchange or refund (our option) shipping charges prepaid within 5 days of receipt. Illinois residents must add 5% sales tax. Personal checks must clear before shipment. All items sent shipping charges collect unless otherwise agreed. Accessories do not include crystals, relay or antennas.

2 Rigs in one!

Comcraft's **NEW** VHF Two-Band Transceiver for 2 and 1 1/4 meters with Digital Frequency Synthesis



Model CST-50

The new CST-50 Two-Band Transceiver provides coverage of two complete amateur bands with all the features needed by most operators. Imagine! The two most popular VHF bands in one rig with Phase Locked Loop frequency synthesis. In the CST-50 all frequencies are generated digitally by reference to one highly accurate and easily adjustable crystal. As soon as a new repeater is on you can use it, no waiting for crystals. Write for further information.

- Covers entire 2 meter and 1 1/4 meter bands
- Covers MARS, CAP and CD frequencies from 142 to 149.995 MHz
- Full digital frequency synthesis with 5 kHz steps
- Lighted thumbwheels for night mobile operation
- No crystals to buy — ever
- Built-in repeater offsets of 600 kHz, 1 Mhz and 1.6 MHz
- 25 watts output on each band
- No transmitter retuning across either band
- FM-AM receiver
- 8 pole crystal filter
- Front mounted speaker

- PTT microphone and mobile mount included
- Operates on 12 volts DC
- AC supply available
- Accessory connector for tone burst and tone coded squelch

CST-50 two-band transceiver \$869.95
CPS-6 AC power supply \$139.95



MADE IN USA by
COMCRAFT
P.O. BOX 266, GOLETA, CA 93017



EDITORIAL BY WAYNE GREEN

from page 12

73	223
QST	181
HR	128
CQ	77

That comes to about 23% more ads in 73 than the next magazine. This may be of interest to amateurs getting ready to start new companies in the ham field who are looking for the magazine which provides the lowest cost ads in terms of sales results... and that is the bottom line. It may also interest the sales managers of the few firms which are not advertising in 73 because they disagree with the editorial policy and hope to force a change with economic sanctions. Ads in 73 outsell anyone else... which is the reason there are more in 73.


YOUR PROTECTION

Another major firm has been kicked out of the 73 pages... for a variety of reasons. Since they are

threatening to sue us to force us to accept their ads, we'll have to keep mum on the situation for legal reasons. We really can't even tell you who they are... but if any readers have been having any problems with Emergency Beacon for any reasons it wouldn't hurt to drop us a line with the details... we may be able to help.

FREE PHONE CALLS

For a period of several years (alas, no more), those in the know were able to make long distance phone calls for free. It seems that when you put in a TWX system it came with a telephone connected to it, said phone having a solid cover on the mouthpiece since the teletype machine was to be used over the phone wires. Now it further appears that Bell was having a lot of trouble with TWX systems getting wrong numbers as a result of less than diligent servicing of the switching equipment, and the resulting mis-billing was cured by having the computer bill only for calls to TWX numbers. TWX users, upon discovering this cute system, unscrewed the solid part of the handset and put in a regular microphone, thus enabling them to make calls at will over the TWX line, knowing they would not

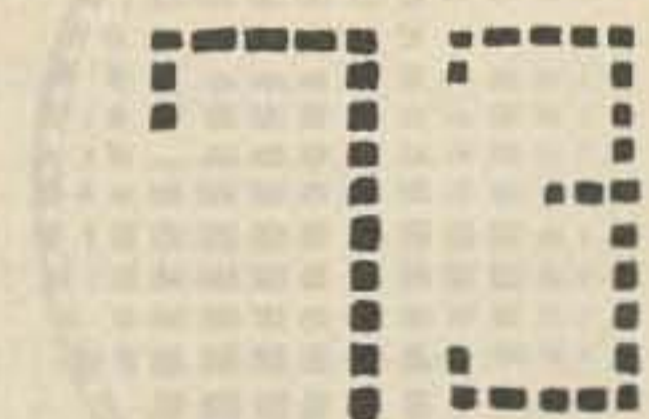

Ad In?

The big companies in amateur radio today were, for the most part, started by one or two amateurs... and many grew very rapidly as a result of the low ad rates in 73 and the wide circulation among active (buying) hams. We'll give you 10% of the first ad run by a new company if you let us know about them and they advertise first in 73. Do yourself and the new firm a big favor — drop a note to 73 Advertising, Peterborough NH 03458.

have to pay because the computer would reject the billing. This little game went on for several years, claim people who took advantage of it.

... W2NSD/1

Startling Learning Breakthrough



NOVICE THEORY TAPES
Set of 4 Tapes only \$13.95

You'll be astounded at how really simple the theory is when you hear it explained on these tapes. Three tapes of theory and one of questions and answers from the latest Novice exams give you the edge you need to breeze through your exam.

73 is interested in helping get more amateurs, so we're giving you the complete set of four tapes for the incredibly low price of ONLY \$13.95.

Scientists have proven that you learn faster by listening than by reading because you can play a cassette tape over and over in your spare time — even while you're driving! You get more and more info each time you hear it.

You can't progress without solid fundamentals. These four hour-long tapes give you all the basics you'll need to pass the Novice exam easily. You'll have an understanding of the basics which will be invaluable to you for the rest of your life! Can you afford to take your Novice exam without first listening to your tapes?

SPREAD
the
WORD!

RADIO AMATEURS!
TALK TO THE WORD!!
...ask me about it!

ONLY .50¢

Ham radio is too great a hobby for us to keep it to ourselves. Let's tell the whole world about it! And what better way than by sporting this attractive lime-green bumper sticker on your car! It's only 50¢ — and it's phosphorescent so you can see it even at night. Go ahead... SPREAD THE WORD! Order yours TODAY!

SOLID STATE PROJECTS

\$4

More than 60 projects of interest to anyone in electronics. The devices range from a simple transistor tester to a ham TV receiver. This collection will help you become more intimately acquainted with zeners, ICs and varactors, etc.



VHF PROJECTS FOR AMATEUR AND EXPERIMENTER

\$4

A must for the VHF op. Opening chapters on operating practices and getting started in VHF, both AM and FM, followed by 58 chapters on building useful test equipment, modifying existing and surplus gear.

2M FM HANDBOOK

hardbound \$7
softbound \$5

Contains almost every conceivable circuit that might be needed for use with a repeater. All circuits explained in detail. All aspects covered, from the operator to the antenna.



4 STUDY GUIDES
NOVICE — \$4 GENERAL — \$6
ADVANCED — \$4 EXTRA — \$5

FCC exams got you scared? Frustrated by theory fundamentals? There's no need to worry. 73's four License Study Guides will help you breeze through any of the four tough exams! They are the ONLY guides which cover ALL the material you will have to know. Many amateurs find that one quick reading through our guides is enough to get them through with no sweat.

LATEST RELEASES from 73 publications

RF and DIGITAL TEST EQUIPMENT YOU CAN BUILD

RF burst, function, square wave generators, variable length pulse generators — 100 kHz marker, i-f and rf sweep generators, audio osc, af/rf signal injector, 146 MHz synthesizer, digital readouts for counters, several counters, prescaler, micro-wavemeter, etc. 252 pages. \$5.95



PRACTICAL TEST INSTRUMENTS YOU CAN BUILD

37 simple test instruments you can make — covers VOMs, VTVMs, semiconductor testing units, dip meters, watt meters, and just about anything else you might need around the test lab and ham shack. \$4.95



DIGITAL CONTROL OF REPEATERS

softbound \$5 hardbound \$7
Here's a book for the FMer who wants to design and build a digital repeater control system. Contains sections on repeaters, basic logic functions, logic circuit design, control systems, support circuits, mobile installations, touch-tone, plus a special section on a "mini" repeater control system.



- Novice Theory Tapes \$13.95
- Bumper Stickers .50 ea.
- Solid State Projects \$4.00
- VHF Projects \$4.00
- 2M FM Handbook
 - Hardbound \$7.00
 - Softbound \$5.00
- Rf and Digital Test Equip. \$5.95
- Practical Test Instruments \$4.95
- Novice Class Study \$4.00
- General Class Study \$6.00
- Advanced Class \$4.00
- Extra Class Study \$5.00
- Digital Control of Repeaters
 - Hardbound \$7.00
 - Softbound \$5.00

Name _____

Address _____

City _____ State _____ Zip _____

Cash Check BankAmericard Master Charge

Card No. _____ Expiration date _____

Signature _____

Total enclosed \$ _____

Order from: 73 MAGAZINE, Peterborough NH 03458

NEXUS TRADING CO.

Box 3357 San Leandro, Ca 94578

6 digit AUTOMOTIVE CLOCK KIT complete with a CRYSTAL TIMEBASE accurate to .01 percent. 12 volts d.c. operation — built-in noise suppression and voltage spike protection. Readouts blank when ignition is off — draws 25 ma in standby mode. Has .3 in. readouts. Use it in your car or for all applications where a battery-operated clock is needed.

With black plastic case \$34.95 ppd.
Without case \$29.95 ppd.

60 Hz. CRYSTAL TIMEBASE KIT with .01 percent crystal. 5-15 v.d.c. operation. Draws only 3 ma at 12 volts d.c. Single I.C. — very small size — the P.C. board is 1½ in. by 2 in. 9 other output frequencies are available on the board. Ideal for use with the MM 5309 clock chip as a clock, timer, or stopwatch.

Complete parts kit \$10.95 ppd.
Wired, tested, & calibrated \$15.95 ppd.

Solid State Music's 4K X 8 MEMORY BOARD KIT. Directly Mark 8 compatible — Altair interface data provided. Complete kit includes double-sided, plated-through board, sockets, all necessary capacitors and resistors, and 32 new, factory tested, 1 microsecond 2102 memory chips. Seen elsewhere for \$130, we are selling the complete kit for \$100 ppd. An assembled and tested to one microsecond version is available for \$130 ppd. Add one week to delivery time.

MM 5320 TV CAMERA SYNC GENERATOR — this LSI chip supplies the basic sync functions for either color or monochrome 525 line/60 Hz. camera and video applications. The price is \$4.95 ppd. and includes the data sheet.

MM 5309 CLOCK CHIP — features reset, 4 or 6 digit operation, MULTIPLEXED seven segment or BCD output, leading zero blanking, 12 or 24 hour, operates over 11-19V range. Only \$5.95 ppd., includes data sheet.

FLYER AVAILABLE. WRITE FOR IT.

Kits include all electronic parts, instruction sheet, and etched and drilled P.C. board. Calif. residents add 6% sales tax.

EXCEPT FOR THE ASSEMBLED MEMORY BOARD, ALL ITEMS ARE SHIPPED WITHIN 24 HOURS.



from page 16

CALL LETTER LICENSE PLATES — still being collected by 73 Magazine for possible cover use. Please send in an old call letter plate — most treasured are out-of-district plates such as W2NSD/NH, etc. Got any real oldies? 73 Magazine, Peterborough NH 03458.

TECH MANUALS — \$6.50 each: R-220/URR, SP-600JX, USM-34, GRR-5, URM-25D. Thousands more available. Send 50¢ (coin) for large list. W3IHD, 7218 Roanne Drive, Washington DC 20021.

MANUFACTURERS, Distributors! The Memphis Hamfest will be bigger than ever. The dates are Saturday and Sunday October 4 and 5. Best location possible — State Technical Institute, Interstate 40 at Macon Road. Security. Contact Chairman, Harry Simpson W4SCF, Box 27015, Memphis TN 38127, phone (901) 358-5705.

RADIO ARCHIVES, amateur ANECDOTES (then & now) solicited for proposed (SASE subscription) monthly PR newsletter. Electronic Avocations, 3207 fourth St. N., Mpls., Mn. 55412.

HT220 HI-BAND 4 freq. universal \$250.00 D.M. Herlihy, 2338 Berry St., Lemon Grove, Calif. 92045.

POLICE AND FIRE Scanner Special — Regency ACT — R — 10 H/L/U 10 channel 3 bands, combined ac/dc 10 free crystals included \$169.00 pre-paid, dealer inquiries invited, Four Wheeler Communications 10-F New Scotland Avenue, Albany NY 12208.

NEW EBC 144 JR: The dream machine costs \$599.00. First cashier's check for \$495.00 gets it shipped the same day. Still under warranty. M. T. Henry, 5173 North Hampton Ridge, Norcross, Georgia 30071.

LOOKING FOR JAN 1961 issue 73 Magazine. Please write, stating price, only mint condition. All letters answered. R. H. Wilson, 4011 Clearview Drive, Cedar Falls IA 50613.

FOUNDATION FOR AMATEUR RADIO annual Hamfest Sunday, 19 October 1975 at Gaithersburg Maryland Fairgrounds.

FOREIGN LANGUAGE cassettes. 2 — 60 minute quality tapes per set. French, German, Italian, Spanish. \$6 a set, 4 sets \$20. Royal, Box 2174, Sandusky, Ohio 44870.

WANTED: CX-7 Dead or Alive, write price, condition, symptoms. **SELL: VRM26A**, manual, spare tube. Trade for 2 mtr or HF rig. Rob Pohorence, 2334 Regal Court, Lawrenceville, Ga. 30245. WB4RSK.

SSTV ZOOM LENS, 12-48 mm, F 1:8 focusing C mount, (Robot, Venus, HCV, etc.) brand new, closeout, \$64.95 each postpaid, UHF, Box 504, Huntington Station, New York 11746.


TWO PLASTIC HOLDERS FRAME and display 40 QSL's for \$1.00 or 7 holders enhance 140 cards for \$3.00 — from your Dealer, or prepaid direct: TEPABCO, Box 198M, Gallatin, Tennessee 37066.

WANTED: Mobile telephone equipment such as Delco, GE, etc. Also heads, decoders, duplexers. Greg Hyman, WA2OTG, 19 Sicard Ave., New Rochelle, New York 10804, (914) 636-2494.

FM RECEIVER, preamp, scanner, UHF converter kits. Hamtronics, Inc., 182 Belmont, Rochester NY 14612.

You KNOW you need QSLs!

Get some you can be proud of...

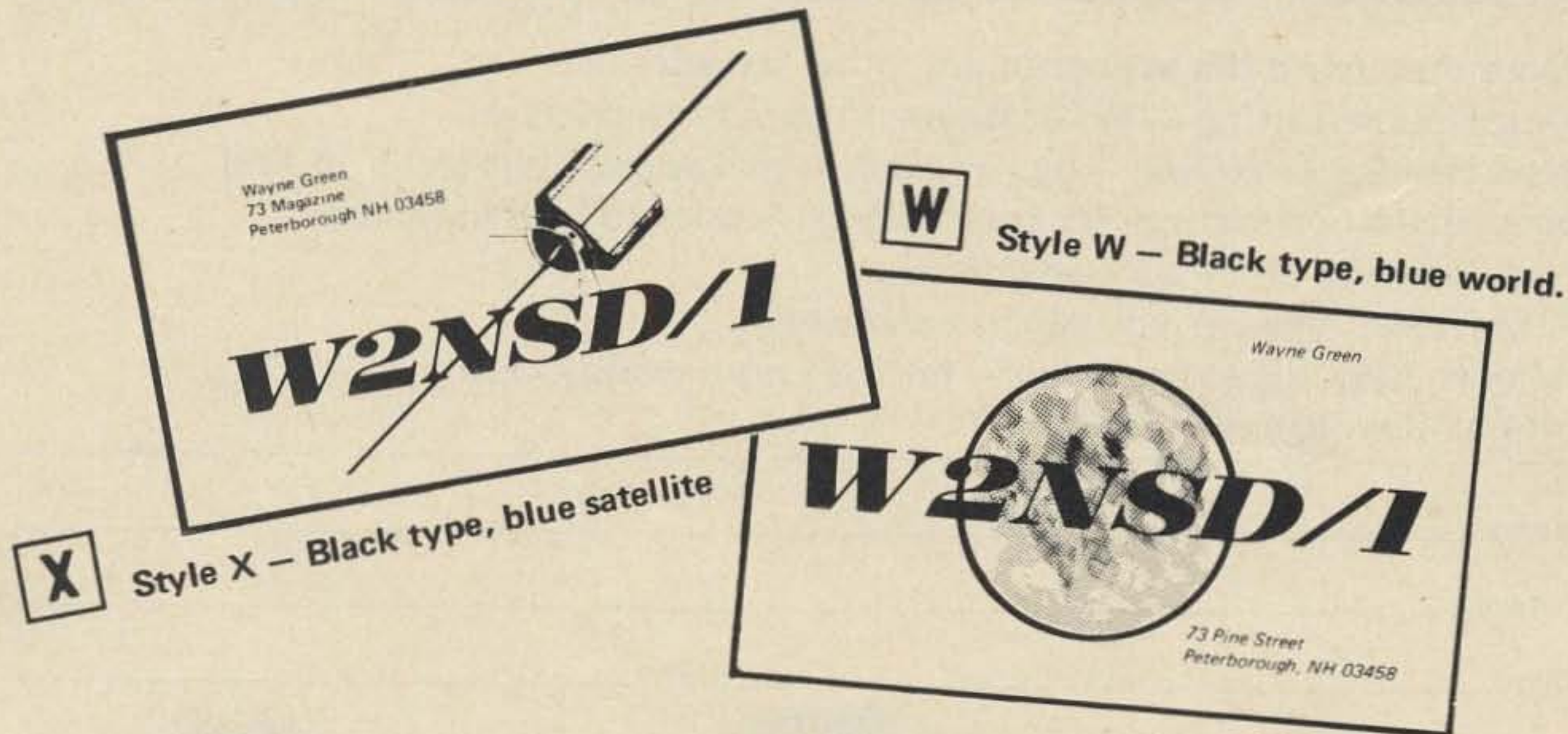

and—save money!

ONLY \$6 for 250, \$10 for 500, \$15 for 1,000, and \$20 for 2,000.

How can 73 make such beautiful cards, printed on the best coated stock, available for about half the regular cost? Our business is 73 Magazine and QSLs just help keep things going during slack days of the month. We do this at cost just to keep busy — you get the benefit. How many shacks have your QSL card proudly on display?

The world and satellite are printed in blue, your name, address and call are in black. The QSO information is a standard form on the back.

DOMESTIC ORDERS ONLY

QSL Dept. • 73 MAGAZINE • Peterborough NH 03458

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

Awards to be listed: _____

Cash Check



BankAmericard



MasterCharge

Style

- | | |
|----------------------------|--------------------------------------|
| <input type="checkbox"/> W | <input type="checkbox"/> \$6 — 250 |
| World | <input type="checkbox"/> \$10 — 500 |
| <input type="checkbox"/> X | <input type="checkbox"/> \$15 — 1000 |
| Satellite | <input type="checkbox"/> \$20 — 2000 |

Card No. _____

Expiration Date _____

Signature _____

NEW! Fall Edition

brand new edition of the **REPEATER ATLAS**

- More than twice the listings of any other repeater list.
- New Double Listing — by location and also by frequency.
- New Handier Grouping — by call areas — makes repeaters easier to find.
- New Simplified Listings for fast reading — easier to read in the car.
- New listing of all Pirate Repeaters.
- Know what repeater you can use and where.
- Almost 3,000 repeaters listed — for the entire world — not just ARRL affiliated repeaters.

Name _____

Address _____

City _____ State _____ Zip _____

Cash Check BankAmericard



Master Charge



Card Number _____ Expiration Date _____

Signature _____

Order now from:

RADIO BOOKSHOP, Peterborough NH 03458

ONLY \$1.95

HAM HELP

According to long-standing policy, *73 Magazine* makes a continual effort to match those in need of technical help or instruction with those who feel they can offer it. If you find yourself in one of these two categories, please do yourself and amateur radio a favor by contacting Ham Help, 73, Peterborough NH 03458.

Lawrence R. Harrington
1503 E. Walnut Avenue
El Segundo CA 90245

Steve Dobrenchuk WN3YQB
122 Grafton Street
Chevy Chase MD 20015
(301) 652-3150

Freeman Dodsworth
5302 Pooks Hill Road
Bethesda MD 20014
(301) 530-3674

James F. Reuter, Sr.
2595 Marlborough
Detroit MI 48215
(313) 821-0395

Edward A. Smith
55 East End Avenue (82nd St)
Apartment 4G
New York, NY 10028
(212) 879-6580

Add my name and address to your list of those willing and able to give constructive assistance to those that need help — W9EQG dates from 1954. I can help in amateur radio and basic and advanced electronics.

David R. Halliburton
WA3ZOR/ex-W9EQG
726 Tiffany Court
Gaithersburg MD 20760

The Hamburglar STRIKES AGAIN!

STOLEN: Two miniature GE portable radio transmitter/receivers; model number PE56RAS66, S/N 2210672 and 4351289. Contact John E. Dillon, LtCol, USAF, Chief, Security Police, Department of the Air Force, 3800th Air Base Wing (AU), Maxwell Air Force Base, Alabama 36112.

TAKEN: SB-144 was stolen from locked auto on June 28, 1975 at the "Tradewinds" Shopping Center at Barrington and Irving Park Road in

Hanover Park, Illinois. S/N 620952. Internal speaker is removed and a Data Engineering Pre-amp is installed in its place. Contact Mr. D. L. Holdeman W9HJL, 1510 Birch Avenue, Hanover Park, Illinois 60103. Phone: (312) 289-1919.

RIPPED OFF: Tempo One & AC PS and Drake TR-22 taken on June 14, 1975. Contact Dennis J. Gazak WA3SZD, 321 Stevens Street, Philadelphia, Pennsylvania 19111.



**WE DON'T HAVE
YOUR NUMBER
BUT YOU HAVE OURS**

Toll Free
(Cont. 48 States)

800-325-3636

(MO. cust call 314-993-6060 coll.)

**CALL
HAM RADIO CENTER
ST. LOUIS
FOR NEW AND USED
AMATEUR RADIO EQUIPMENT**

*We Trade on New or Used
Charge it on Master-Charge or BankAmericard*

HAM RADIO CENTER INC.

8342 Olive BL.
P.O. Box 28271
St. Louis, MO 63132

The New Hy-Gain 270 brings state-of-the-art design to 2 meter mobile.

The Hy-Gain 270 is specifically designed to solve the problems of gain 2 meter mobile antennas...hard tuning, high VSWR, poor pattern due to irregular ground plane, and fade from whip flex.

The all white fiberglass and chrome design develops 6 db gain through the use of 2 stacked 5/8 wave radiators with a self-contained 1/4 wave decoupling system. Because the Hy-Gain 270 operates independent of the car body ground, you get minimum pattern distortion for maximum range in all directions. Independence from the car body also means the end to tune-up problems. The fiberglass design solves the fading problem due to upper whip flex. Since the antenna and feedpoint are sealed in fiberglass, the Hy-Gain 270 will deliver top performance year after year without loss due to corrosion. The Hy-Gain 270 can be mounted anywhere...bumper, cowl, deck or mast...for fixed, land mobile or marine service using Hy-Gain mounts listed below.

- 6.0 db gain.
- 250 watt rated.
- 144-148 MHz.
- VSWR less than 1.5:1 at resonance, 6 MHz Bandwidth.
- 96" whip height.
- No pruning required, completely factory tuned!
- 50 ohm input.
- 3/8 x 24 standard mobile thread.
- Comes with 18' coax and PL-259 connector.

Order No. 270

Mounts — Universal No. 271

Flush Body No. 499

Bumper No. 415

Get maximum range...get a Hy-Gain 270!

For prices and information,
contact your local Hy-Gain
distributor or write Hy-Gain.



hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

WE'RE FIGHTING INFLATION NO PRICE RISE IN '75



FOR FREQUENCY STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us!

CRYSTAL SPECIALS

Frequency Standards

- 100 KHz (HC 13/U) \$4.50
- 1000 KHz (HC 6/U) 4.50
- Almost all CB sets, TR or Rec \$2.50
(CB Synthesizer Crystal on request)
- Amateur Band in FT-243 ea. \$1.50
..... 4/\$5.00
- 80-Meter \$3.00 (160-meter not avail.)

Crystals for 2-Meter, Marine, Scanners, etc. Send for Catalog.

For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please.



Div. of Bob Whan & Son Electronics, Inc.
2400 Crystal Dr., Ft. Myers, Fla. 33901
All Phones: (813) 936-2397

Send 10¢ for new catalog with 12 oscillator circuits and lists of frequencies in stock.

- AY5-1013A UART \$10.90, 2/\$19.95
- 8038 VCO \$4.95
- MK5002 4 Decade counter \$13.95
- 9374 7 Segment Decode, Quad Latch, LED Driver \$2.99
- MM5320N. T.V. Sync Gen \$18.80
- MM5322N. Color Bar Gen \$20.00
- MM5740 AAEN ASCII Keyboard Encoder \$17.99
- XR205 Function Generator \$8.40
- XR210 FSK Demod \$5.25
- XR320 Precision Timer \$1.55
- XR2206CP Monolithic Function Gen \$5.50
- XR2207CP VCO \$3.85
- XR2240CP Prog. counter timer \$4.85
- 100V/3A Epoxy Diodes SPECIAL 10/\$1.00
- 500µf/50V Electrolytics SPECIAL 10/\$2.50

All orders postpaid — please add insurance minimum order — \$5 U.S./\$15 foreign latest lists — 10¢ stamp



TRI-tek, inc.

P.O. BOX 14206, DEPT 7
PHOENIX, ARIZONA 85063

New!

COMPLETELY NEW!

VHF Antenna Handbook

The theory, design and construction of dozens and dozens of different VHF and UHF antennas . . . antennas for FM, for DXing, for repeaters, for mobiles, for emergencies, for contests, quickies, mammoth arrays . . . everything.

This is a practical book written for the average amateur, not full of formulas for the design engineer — this is a book for the amateur who takes joy in building — perhaps it is a brookstick and some coat hangers fashioned into an effective beam for some instant mountain top DX into far off repeaters during a vacation . . . perhaps it is a folding beam you can take with you on business trips, packed away in your suitcase . . . this book is packed full of fabulous antenna projects that you can build.

This book, which would normally sell for \$5 or \$6 is being offered for a short while at a pre-publication price of \$2.00 postpaid. Send cash, check, money order . . . or give your Master Charge or Bank Americard number

GREEN PUBLISHING, INC.

Peterborough NH 03458

Name _____ Zip _____

Address _____ State _____


City _____ Exp. date _____

BankAmericard or Master Charge No. _____

Signature _____


See you at Reston, Va. Big Antenna Deal from the Dealing Wheel

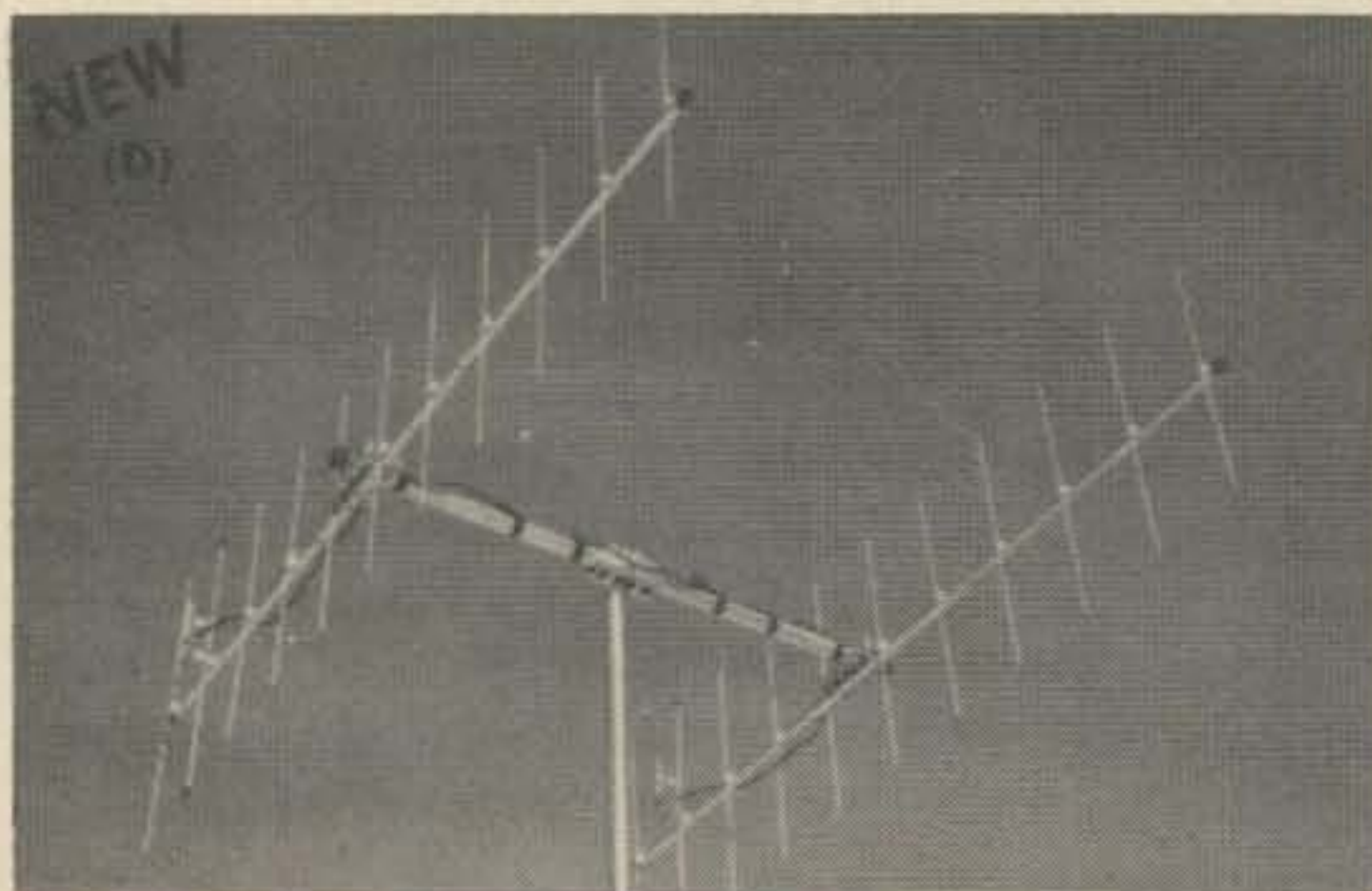Beam of Your Choice and HAM M2 for peanuts —
WRITE for the Deal of a Lifetime



POWER PACK: A 22 element, high performance, vertically polarized FM array, complete with all hardware, mounting boom, harness and 2 antennas.
A147-22 1000 watts 146-148 MHz

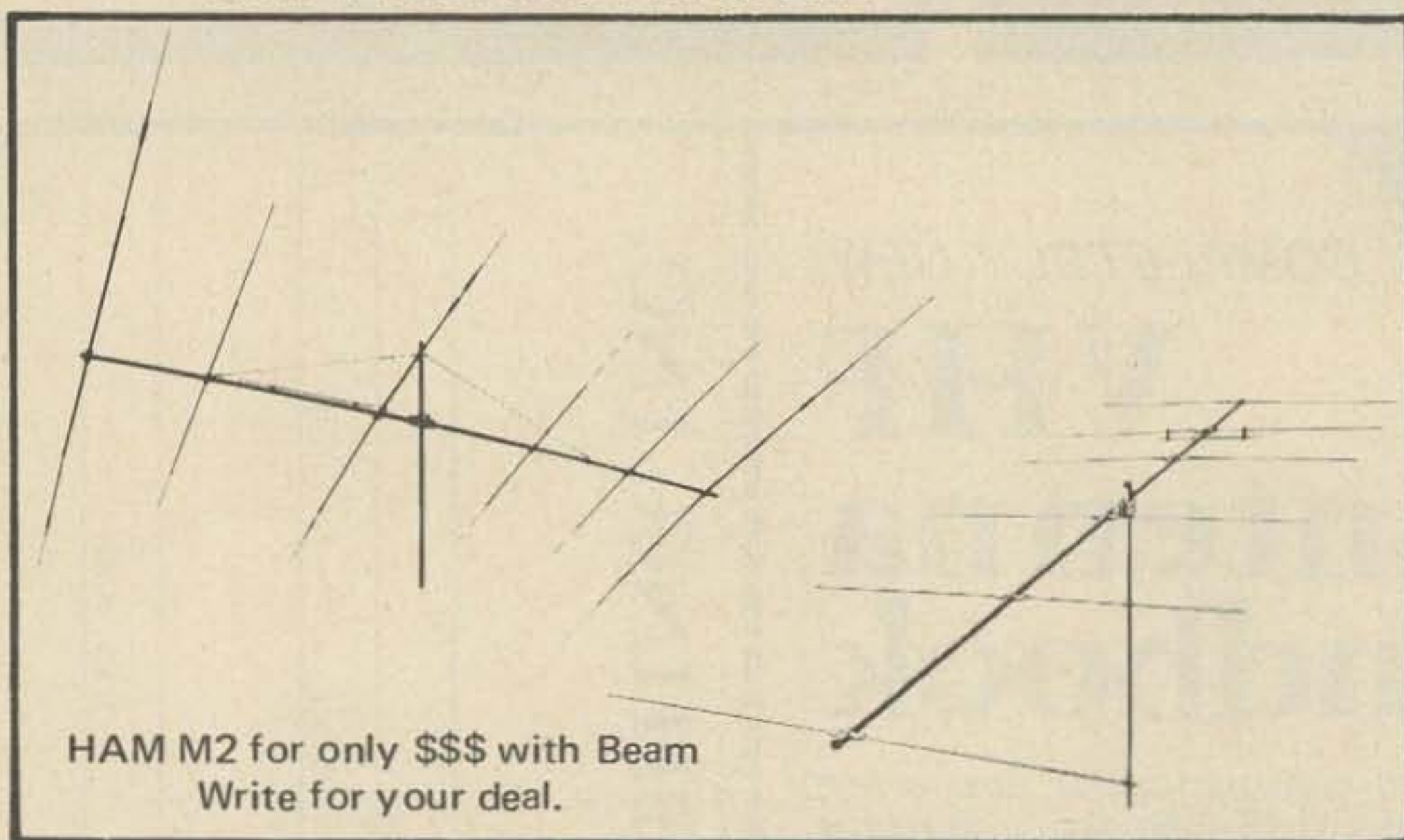- CUSH-CRAFT
- STANDARD
- CLEGG
- NEWTRONICS
- ANT. SPECIALISTS
- REGENCY
- DYCOMM
- DRAKE
- HY-GAIN
- GALAXY
- SONAR
- MOSLEY
- MIDLAND
- BIRD
- ICOM
- YAESU
- TEMPO
- KLM
- SWAN
- SBE
- AND MORE



HAM M2 for only \$\$\$ with Beam
Write for your deal.

- * huge inventory of New and Used Ham Gear
- * we trade any kind of Electronic Gear. **LARGEST** on the East Coast.
- * Use your Mastercharge, Bank Americard * SAVE GAS — BUY VIA U.P.S. —

HAMTRONICS

A DIVISION OF TREVOSE ELECTRONICS

4033 BROWNSVILLE ROAD, TREVOSE, PA. 19047

MEET THE STATE OF THE ART ON 2 METERS... THE ITC MULTI-2000 CW/SSB/FM TRANSCEIVER



Whether your interest is simplex, repeater, DX or OSCAR the new ITC MULTI-2000 lets you get into all the action on all of the

band. Fully solid-state and employing modular construction, the MULTI-2000 enjoys features found in no other 2m transceiver.

FEATURES

- PLL synthesizer covers 144-148 MHz in 10 kHz steps
- Separate VXO and RIT for full between-channel tuning
- Simplex or ± 600 kHz offset for repeater operation
- Three selectable priority channels
- Multi-mode operation (CW/SSB/NBFM/WBFM)
- Built-in AC and DC power supplies, noise-blanker squelch and rf gain control
- Selectable 1W or 10W output
- Separate S-/power and frequency deviation meters
- Built-in test (call) tone and touch-tone provision
- Excellent sensitivity ($.3 \mu\text{V}$ for 12 dB SINAD)
- Superior immunity to crossmodulation and intermodulation
- Introductory price: \$695.

Available ANYWHERE IN THE WORLD directly from

ELECTRONIC DISTRIBUTORS, INC.

— Communication Specialists for over 36 years —

1960 Peck Street, Muskegon, Michigan 49411 Tel.(616) 726-3196

Telex 22-8411

digital clock




1/2" LED DIGITAL Display

- 110 volt 60 Hz
- Size H3"1/8 x D 3 3/8 x 3 3/4 inches
- Color — Black, Red, Chrome

12 Hour 24 Hour
\$24.95 \$29.95

Specify 12 or 24 hour and 1st and 2nd color choices

		each	qty. of 10 (each)
NE567N	Tone Decoder	1.75	1.50
NE566N	Function Gen	1.75	1.50
7446	BCD to 7 seg	.85	.60
MC1550	RF OP AMP	1.50	1.00
TC430	Quad RC Tone gen	2.25	1.75
75491	Quad seg. driver	.80	.65
75492	Hex digit driver	.80	.65
2102	1024X1 RAM	4.50	3.75
1101	256X1 RAM	1.25	1.00
5314	Clock chip	4.95	3.95
5312	Clock chip	3.75	3.00

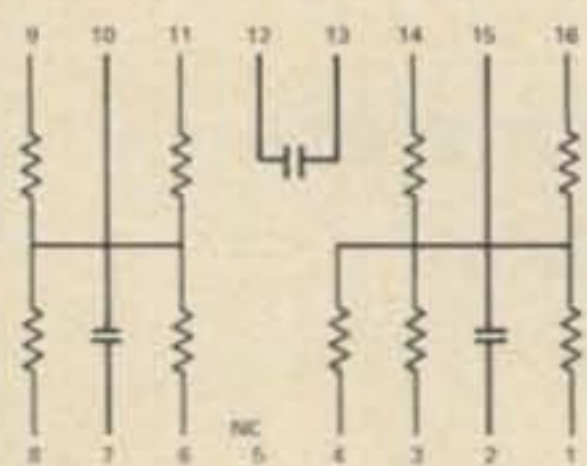

IC-DIP

resistor and cap array all resistors are 50Ω caps are .01

1 for \$1.00
 10 for \$6.50

liquid crystal display watch



... You never thought it could happen but it did, and you saw it first in 73. The digital timepiece for your wrist is finally available at the price of an ordinary wind-up watch. Yet this QUARTZ LIQUID CRYSTAL watch is the equal of those you've seen at two and three times our LOW PRICE.

- Pulsating dots show elapse of seconds
- Continuous Display
- Mfd. by American Micro Systems International (AMI)
- Guaranteed for one year by manufacturer
- Specify stainless or gold color
- Color coordinated leather watch band
- Crystals will not fade in sun like other liquid crystals
- PP in continental USA

● THIS IS NOT A KIT! \$55.00

AP's 14 pin Chipclip. A must for the IC troubleshooter
 1 for 3.75 10 for 35.00

Transformer
 120 Pri, sec 11.9V ac at 150 MA
 \$1.50 ea., qty. of 10 — \$1.00 ea.
 110/220 Pri, sec 12-15V ac at 10 amp
 \$12.00 ea., qty. of 10 — \$10 ea.

Push button switch spst normal open
 4 for \$1.00 25 for \$5.00

Computer logic diodes IN4148, same as IN914 tested prime units on tape
 min 25 for \$1.00 100 for \$3.00

100,000 uF cap. at 10v
 1 for \$2.75 10 for \$20.00

5.00 min. order. All under a 50¢ service charge
 We are a surplus house. All items are new unless otherwise stated and all are 100% guaranteed. If you have surplus send list or sample. All samples are accounted for.

Florida residents remit 4% state sales tax.
 All items PP in continental USA.

Marlin P. Jones & Associates

P.O. Box 9023 • Riviera Beach • Florida 33404
 305-848-8236

USED EQUIPMENT SALE: All used equipment is sold as is, FOB our warehouse. We guarantee that all items are either fully operational or require only minor repairs. We will gladly check it out and restore to perfect operating condx; call or write for a quote.

POWER SUPPLIES: All regulated, with outputs as indicated; LAMBDA Model 25; Bench model in cabinets, front mtd ctrl variable from 200-325VDC @ 150ma. **\$9.95**
 LAMBDA Model 28; Same as above except rack mtd and voltage control on rear deck . . . **\$9.95**
 LAMBDA Model 29; Same as Md1.28 except output is 100-200VDC @ 100ma. **\$8.95**
 LAMBDA Model C281 Rack Mtd; 125-325VDC @ 750ma. **\$14.95**
 LAMBDA Model LA-100-03B, a real beauty for solid state bench sply; 0-32VDC@10amps **\$29.95**
 HEWLETT-PACKARD Model 712-B; Well regulated lab type supply in cabinet; full metering and variable 0-500VDC @ 200ma., 0-150VDC @ 5ma (bias), in perfect condx **\$49.95**

OSCILLOSCOPES: All work, but need calibration and/or tube changes; CRT okay:
 TEKTRONIX 517. Wide band, fast risetime. High intensity blue phosphore. Complete w/P.S. and manuals **\$99.95**
 HEWLETT-PACKARD. Model 185A w/187A dual trace plug-in compl. w/dual hi imp.probes. In cab. **\$79.95**
 A.B.DUMONT 401AR. General purpose, rack mtd. 5" CRT **\$49.95**

MISCELLANEOUS: Some one-of-a-kind, mostly lab quality and most in good condx. May need minor repair SKL Fast Rise Pulse Generator — good for digital work **\$29.95**
 MEASUREMENTS CORP. Standard Pulse Gen. Mod.179; 30hx-100kHz, 0-100 volt output, width variable from .5-60 microsecs. **\$49.95**
 NEMS-CLARKE Panoramic Display Mdl.300-1: Input frequency of 21.4 MHz; 3" CRT, rack mounted, good for 21 MHz IF receivers used in satellite work **\$59.95**
 COMMUNICATIONS ELECTRONICS — Multi-coupler; Passband from 150kHz to over 28 MHz @ 15db; 117/230VAC built-in pwr.sply; 16 RCA 7586 Nuvistors gives 8 outputs from one input **\$29.95**
 Berkey COUNTER Mod. 7370 — 7 digit counter with crystal time base in oven. Operable. Good to more than 20 MHz **\$89.95**

USED HAM GEAR: Guaranteed operable, may need calibration (only if you're really fussy)
 HALLICRAFTERS — HT-46 80-10 SSB transceiver-150 Wpew, VFO all modes new final, checked out **\$149.95**
 HALLICRAFTERS — HT-41 1200 Wpew linear — same size and style as HT-37 exciter. Good condx, ckd out **\$179.95**
 EICO Model 753 TRI-BAND SSB Transceiver; 80-40-20M, 150Wpew less than 20 hours use. 6146s in final — complete with A/C Pwr. Supply and Spkr **\$149.95**

IC*IC*IC*IC*IC* DEAL. SIGNETICS DTL DIPs on boards. At least 50 various ICs on each board, gold plated fingers, several caps and so on. Some of each of ST616A, ST620A, ST659A, ST670A, ST680A — all good popular numbers including JK F.F., Buffer/drivers, quad NAND gates, etc. Use board as is, or remove for only ten cents per DIP — One board **\$4.95; 2/\$7.95 ppd.**

IC/OP AMP PWR SUPPLY XFRMR-(RFE)* BUILD YOUR OWN IC OR OP.AMP. POWER SUPPLY USING THIS RUGGED TRANSFORMER: Dual 117 VAC inputs, either 117VAC or 235 VAC OUTPUTS: Three secondaries - 22VAC @ 10AMPS; 30VAC @ 5AMPS; 12VAC @ 2AMPS; all center-tapped **\$5.95 FOB**

COMPUTER GRADE ELECTROLYTICS -(RFE)* 36,000 MFD @ 30WVDC w/mtg hardware **\$0.99 ea. ppd.**

VIDEO DISPLAY TERMINALS. We still have a few of the VDTs (as described in our August, 73 Magazine ad). The response has been tremendous and we're doing our best to keep up with the orders. Please bear with us. If you haven't ordered yours yet, please do so at once. We will not be able to offer this item again once our present supply is sold; don't be disappointed — place your order now — we ship on a first come, first served basis and we sure do hate to send out-of-stock letters. Runs up the overhead, you know!

RFE* — Removed from operational equipment.



On all postpaid orders, please ADD \$.50 to cover handling costs. Orders shipped same day in most cases. All prices subject to change without notice. F.O.B. warehouse. Send SASE for literature.



SUNTRONIX COMPANY

6 KING RICHARD DRIVE, LONDONDERRY, N. H. 03053
 603-434-4644

MICROPLEXER[®]

The Microstrip Duplexer

The Two Meter Microplexer has:


- 105 db of isolation
- less than 1.5 db insertion loss
- temperature stability

It's so good we guarantee it!

The price? Just \$350.00
\$385.00 with built in directional
cu coupler.

Microplexer is available for 2 meter, 1.5 meter and 70 centimeters.

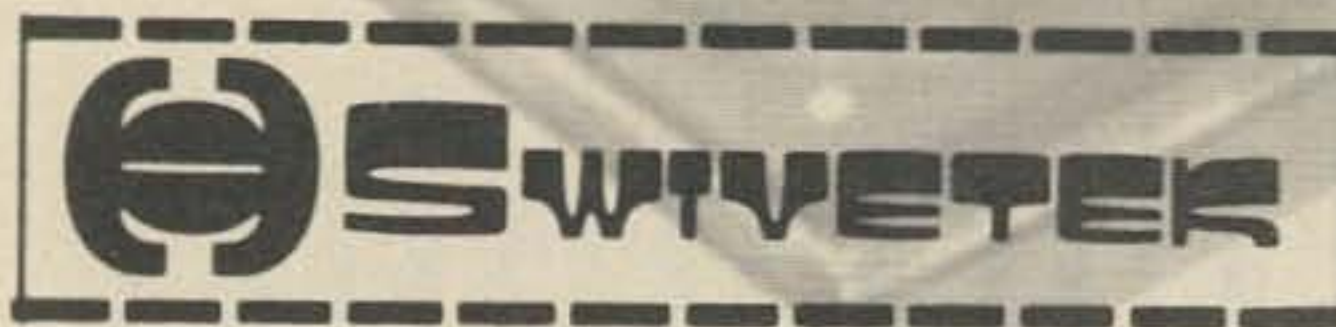See your dealer or call or write for our free catalog.



544 Lassen St.

Los Altos, Ca.

94022

(415) 941-2118

Win! Win! Win!



an Atlas Transceiver

ONE EACH MONTH UNTIL FURTHER NOTICE

You made S.D. SALES successful with your patronage and we want to say

Thank You

In cooperation with 73 Magazine, we will give an Atlas Transceiver complete with deluxe mobile mount, each month until further notice.

No Purchase Required

Send your name and address in a letter — tell us in 25 words or less — why you like S. D. SALES. The winner will be notified by Air Mail.

S. D. SALES CO.

P.O. Box 28810, Dallas TX 75228

S. D. SALES CO.

P. O. BOX 28810 DALLAS, TEXAS 75228

6 Digit Digital Clock Kit

Our Engineer said it would be "impossible" to sell a Six Digit kit for this price. But because of several special super buys we made on chips and displays we can offer this unbelievable bargain on our Clock Kit. Sure, this price is too good to be true, but rest assured, all parts in this kit are prime, first run units. Also, all kits are sold with an unconditional money back guarantee.

Here's What The Kit Includes:

- 1 — MM5314 National Clock Chip
- 6 — Common Cathode Led Readouts (.25 in. char.)
- 13 — NPN and PNP Driver Transistors
- 2 — Push Button Switches for time set
- 1 — Switch for time hold
- 1 — Filter Cap
- 4 — IN4001 Rectifiers
- 1 — IN914 Diode
- 2 — .01 Disc. Caps
- 9 — Carbon Resistors

Transformer for
this kit — \$1.50.

\$9⁹⁵
(KIT)
WITH SPECS.
POSTPAID

P.C. BOARD FOR ABOVE — \$3.00 each

All you need to add is a 12VAC Transformer, perfboard, and your choice of case. The above parts, if ordered separately from our competitors, could cost you as much as \$20. Buy from S.D. and you'll be happy with our quality parts and ultra fast shipment.

<p>NATIONAL 2K ERASEABLE PROM 2048 Bit, static units. U.V. light eraseable. MM5203. Factory prime new units. Special — \$14.95.</p>	<p>SUBMINIATURE TRIMMER CAPS Ultra stable. Range: 3.5 to 18 PF. 2 for \$1</p>
<p>DIGITAL CLOCK CHIPS BY NATIONAL FACTORY NEW UNITS! MM5314 — 4 or 6 digits. 24 pin DIP. Use with LED Readouts. With Specs. — \$3.95 MM5316 — Alarm chip. 40 pin DIP. \$4.44</p>	<p>FILTER CAPS Dual section, 2000 MFD and 1500 MFD at 30 WVDC. Twist Lock. 79c ea. 3 For \$2</p>
<p>TEXAS INSTRUMENTS 8 DIGIT CALCULATOR CHIP TMS0 103NC. Four function. Same style as used in TI pocket calculators. Factory new units, with specs. \$1.99 each.</p>	<p>NATIONAL VOLTAGE REGULATOR Like 7805. 5VDC — 1 AMP output. Has TO-220 plastic power tab — 99c</p>
<p>1AMP 1000 PIV SILICON RECTIFIERS IN4007. Factory prime devices. 10 for \$1.00.</p>	<p>IN4148 COMPUTER DIODES Same as IN914. Factory prime. 20 for \$1.</p>
<p>741C OP AMPS Prime, factory tested and marked. Full spec on all parameters. Not re-tested, functional only, units as sold by others. 741CH — TO-5 8 Lead Metal Can 3/\$1 741CV — 8 Lead Mini Dip 4/\$1</p>	<p>FULL WAVE BRIDGE By G.I. 1.5 AMP 800PIV — 75c</p>
<p>12VDC RELAY DPDT. Heavy gold plated 5 amp contacts. 300 OHM coil. Limited Qty. 99c</p>	<p>2N706A 400MHZ. TRANSISTORS Silicon NPN. 1 WATT. TO-18 Case. 5 For \$1</p> <p>723CH PRECISION VOLTAGE REGULATOR Build a circuit regulating the voltage from 2 to 37 volts. Complete specs included. One of the easiest to use regulators now on the market. S.D. Special Introductory Price 2 For \$1.00</p>

S. D. SALES CO.

P. O. BOX 28810 DALLAS, TEXAS 75228

FAST SERVICE — QUALITY MERCHANDISE
BARGAINS GALORE — NO BACK ORDERS

We are **SMALL** enough to give personalized service, but
LARGE enough to handle every order swiftly and efficiently!

<p>INTEL 1K 2102 RAM Factory prime, tested units. Factory selected for much faster speed than units sold by others. 650 NS. These are <i>static</i> memories that are TTL compatible and operate off + 5 VDC. The real workhorse of solid state memories because they are so easy to use. Perfect for TV typewriters, mini-computers, etc. With specs. \$3.95 ea. or 8 for \$30</p>	<p>FAIRCHILD LED READOUTS — 69c FND-70. Common cathode. Right hand decimal point. .25 inch character. Prime new units. Perfect for clocks, frequency counters, etc. 69c 10 For \$6 Best Readout Buy In USA!</p>																																																																								
<p>SIGNETICS 1K P-ROM 82S129. 256 x 4. Bipolar, much faster than MOS devices. 50NS. Tri-state outputs. TTL compatible. Field programmable, and features on chip address decoding. Perfect for microprogramming applications. 16 pin DIP. With specs. \$2.95 ea.</p>	<p>DO YOU NEED A LARGE, COMMON ANODE READOUT AT A FANTASTIC PRICE? S.D. presents the MAN-64 by Monsanto - .40 inch character. All LED construction - not reflective bar type, fits 14 pin DIP. Brand new and factory prime. Left D.P. \$1.59 ea. 6 For \$7.50</p>																																																																								
<p>LM324 — QUAD 741 OP AMP — \$1.50</p>	<p>DL747 JUMBO LED READOUTS By Litronix. .65 inch character. Common anode. Outperforms SLA-3. Perfect for giant digital clocks. Only 20 MA. per segment. Special — \$2.50 ea.</p>																																																																								
<p>NE555 — Timers — 69c or 10 For \$6</p>	<p>LARGE SIZE LED LAMPS Similar to MV5024. Prime factory tested units. We include plastic mounting clips which are very hard to come by. Special 4 For \$1</p>																																																																								
<p>709CH — OP AMPS — 4 For \$1</p>	<p>PC BOARD MATERIAL FR-4 blank epoxy boards. 2 oz. copper, 5 x 10 in. Single Sided. Limited Qty. — \$1.49</p>																																																																								
<p>GE SCR C106B1 4 AMP 200PIV. Sensitive Gate. 59c</p>	<p>MOTOROLA VOLTAGE REGULATOR MC1469R. TO-66 9 Lead package. For 3 TO 30V Outputs. Provides 600 MA direct output or more by using an external power transistor. Reg. catalog \$4 ea. With specs. \$1.95 ea.</p>																																																																								
<p>MOTOROLA POWER DARLINGTON — \$1.99 MJ3001 - NPN - 80 Volts - 10 Amps - HFE 6000 typ. To-3 Case. Ideal for power supplies, etc. We include a free 723 regulator w/schematic for power supply with purchase of the MJ3001. You get the two key parts for a DC supply for only \$1.99. Regular catalog price for the MJ3001 is \$3.82</p>	<p>MOTOROLA NEGATIVE VOLTAGE REG MC1463R — Like our 1469R above, except for negative voltage. Reg. catalog \$5. Our price \$1.95.</p>																																																																								
<p>TRANSISTORS</p> <table border="1"> <thead> <tr> <th>Type</th> <th>Mat.</th> <th>Pol.</th> <th>Vceo</th> <th>Ic</th> <th>Hfe</th> <th>Case</th> <th>Price</th> </tr> </thead> <tbody> <tr> <td>2N3904</td> <td>S</td> <td>N</td> <td>40</td> <td>100MA</td> <td>200</td> <td>TO-92</td> <td>6/1.00</td> </tr> <tr> <td>2N3906</td> <td>S</td> <td>P</td> <td>40</td> <td>100MA</td> <td>200</td> <td>TO-92</td> <td>6/1.00</td> </tr> <tr> <td>2N4401</td> <td>S</td> <td>N</td> <td>40</td> <td>250MA</td> <td>200</td> <td>TO-92</td> <td>6/1.00</td> </tr> <tr> <td>2N4403</td> <td>S</td> <td>P</td> <td>40</td> <td>250MA</td> <td>200</td> <td>TO-92</td> <td>6/1.00</td> </tr> <tr> <td>2N3638</td> <td>S</td> <td>P</td> <td>25</td> <td>150MA</td> <td>60</td> <td>TO-105</td> <td>6/1.00</td> </tr> <tr> <td>EN930</td> <td>S</td> <td>N</td> <td>45</td> <td>50MA</td> <td>300</td> <td>TO-106</td> <td>6/1.00</td> </tr> <tr> <td>2N2905</td> <td>S</td> <td>P</td> <td>40</td> <td>350MA</td> <td>200</td> <td>TO-5</td> <td>4/1.00</td> </tr> <tr> <td>2N4249</td> <td>S</td> <td>P</td> <td>60</td> <td></td> <td></td> <td></td> <td>6/1.00</td> </tr> </tbody> </table>	Type	Mat.	Pol.	Vceo	Ic	Hfe	Case	Price	2N3904	S	N	40	100MA	200	TO-92	6/1.00	2N3906	S	P	40	100MA	200	TO-92	6/1.00	2N4401	S	N	40	250MA	200	TO-92	6/1.00	2N4403	S	P	40	250MA	200	TO-92	6/1.00	2N3638	S	P	25	150MA	60	TO-105	6/1.00	EN930	S	N	45	50MA	300	TO-106	6/1.00	2N2905	S	P	40	350MA	200	TO-5	4/1.00	2N4249	S	P	60				6/1.00	<p>POWER TRANSISTOR PC BOARD Mfg. by Memorex Computer Corp. Board has 20 Power Transistors. 10-RCA 2N3585 TO-66 SILICON NPN. VCEO-300 IC-2AMPS. 10-MOTOROLA MJE-340. NPN Silicon. VCEO-300. Plastic power tab case. Also has 10-2N2222A TO-18 NPN transistors and 10-1N5059 1 AMP 200 PIV rectifiers, plus 32 resistors. LIMITED QTY. Board #103. \$3.99 ea.</p>
Type	Mat.	Pol.	Vceo	Ic	Hfe	Case	Price																																																																		
2N3904	S	N	40	100MA	200	TO-92	6/1.00																																																																		
2N3906	S	P	40	100MA	200	TO-92	6/1.00																																																																		
2N4401	S	N	40	250MA	200	TO-92	6/1.00																																																																		
2N4403	S	P	40	250MA	200	TO-92	6/1.00																																																																		
2N3638	S	P	25	150MA	60	TO-105	6/1.00																																																																		
EN930	S	N	45	50MA	300	TO-106	6/1.00																																																																		
2N2905	S	P	40	350MA	200	TO-5	4/1.00																																																																		
2N4249	S	P	60				6/1.00																																																																		
<p>RCA HIGH VOLTAGE POWER TRANSISTOR 100 Watts. 5 Amps. 300 VCEO. TO-3 case. Silicon NPN. Mfg. house numbered 2N5240. Regular catalog is \$6. Perfect for H.V. supplies or vertical and horizontal circuits. SPECIAL — 99c</p>	<p>48 HOUR SERVICE You deserve, and will get prompt shipment. On orders not shipped in 48 HRS., a 20% cash refund will be sent. We do not sell junk. Money back guarantee on every item. WE PAY POSTAGE. Orders under \$10 add 75c handling. No C.O.D. Texas Res. add 5% tax.</p>																																																																								
<p>HEAVY DUTY TRANSFORMER 36 VAC, 3.5 AMPS. 115VAC 60HZ. PRI. For power supplies or audio power amps. Best quality, fully enclosed. \$4.95</p>	<p>S. D. SALES CO. P.O. BOX 28810 DALLAS, TEXAS 75228</p>																																																																								
<p>Our 6 DIGIT CLOCK is not a CHEAP CLOCK KIT, only inexpensive. That's why we have sold several thousand in the last three months, without a single kit being returned for refund.</p> <table border="1"> <tr> <td data-bbox="65 2701 500 2853"> <p>ORDERS OVER \$15 CHOOSE \$1 FREE MERCH.</p> </td> <td data-bbox="500 2701 970 2853"> <p>FREE BONUS All clock or calculator chips are shipped with <i>free socket</i>.</p> </td> </tr> </table>		<p>ORDERS OVER \$15 CHOOSE \$1 FREE MERCH.</p>	<p>FREE BONUS All clock or calculator chips are shipped with <i>free socket</i>.</p>																																																																						
<p>ORDERS OVER \$15 CHOOSE \$1 FREE MERCH.</p>	<p>FREE BONUS All clock or calculator chips are shipped with <i>free socket</i>.</p>																																																																								



**6 digit
clock
kit**

KIT
COMES
WITH
CASE,
STAND,
AND ALL
ELECTRONIC
COMPONENTS.

VERSATILE AND DECORATIVE...\$19.95 +
2 LBS SHIPPING

.3"
READOUTS
FOR HRS &
MINUTES PLUS
SMALLER READOUTS
FOR SECONDS.



GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

HAPPY
ANNIVERSARY
TO US
2 YEARS!
THANK YOU SO MUCH

VECTOR

WIRE \$9.50
ppd.

PENCIL

A HAND HELD, UNDER 1 OZ. TOOL USED TO HELP GUIDE AND WRAP #36 INSULATED WIRE (FROM A SELF-CONTAINED BOBBIN) ONTO COMPONENT TERMINALS. MAKE CONNECTIONS BY SOLDERING: HEAT FROM THE IRON MELTS THE INSULATION, PERMITTING A GOOD SOLDER BOND. THIS IS A FAST WAY TO WORK WITH VECTORBOARD AND COMPONENTS. COMES WITH TOOL, AN INSTALLED BOBBIN OF 250 FT. GREEN WIRE, AND AN EXTRA BOBBIN OF RED WIRE AS WELL AS INSTRUCTIONS

**FIXED 1/2 AMP
POWER SUPPLY
KITS \$7.95**
plus 2 lbs. SHIPPING

- ** REGULATED
- ** SHORT PROOF
- ** THERMALLY LIMITED
- ** 1/2 AMP CONTINUOUS
- ** 1 AMP INTERMITTENT

SPECIFY 6, 8, OR 12 VOLTS,
POSITIVE OR NEGATIVE OUTPUT
VOLTAGE.

...AND WHILE WE'RE ON THE
SUBJECT OF POWER...

POWER TRANSFORMER: 24 VCT, 600
MA. USEFUL FOR A VARIETY OF
PROJECTS. \$1.95 + 1 LB SHPG.

★ HAM SPECIAL ★

FOR ORDERS POSTMARKED BY SEPTEMBER 30TH

INDUCTORS

THESE ARE PC MOUNT TYPE IN CERAMIC.
VALUES ARE COLOR CODED ON THE PARTS.
10 OF ANY ONE VALUE.....~~10~~ \$1.00

1.0 MICROHENRY	24 MICROHENRY
1.2 MICROHENRY	27 MICROHENRY
2.0 MICROHENRY	30 MICROHENRY
2.7 MICROHENRY	33 MICROHENRY
2.8 MICROHENRY	43 MICROHENRY
6.8 MICROHENRY	47 MICROHENRY
8.2 MICROHENRY	68 MICROHENRY
12 MICROHENRY	82 MICROHENRY
18 MICROHENRY	120 MICROHENRY
22 MICROHENRY	680 MICROHENRY

TWO
KIT ONE OF EACH ABOVE VALUES \$1.95

! THE SECRET IS OUT !

the SECRET MICROCOMPUTER Co! is ...

NATIONAL SEMICONDUCTOR

NATIONAL HAS HIT THE MICROCOMPUTER WORLD IN A BIG WAY WITH PACE, A REAL 16 BIT PARALLEL MICROPROCESSOR. THIS SINGLE 40 PIN DIP PROVIDES CAPABILITY FOR 45 CLASSES OF INSTRUCTIONS WITH UP TO 337 INSTRUCTIONS AND FEATURES DIRECT ADDRESSING UP TO 65K.....\$125

--- AND DON'T FORGET ---

5203 2K EAROM.....\$14.50 5203 4K (!) EAROM.....\$24.50
 8 BIT MICROCOMPUTER CHIP SET: 1-8008 & 8-2102s.....\$42.50

TERMS AND ALL THAT STUFF:
 ADD 50¢ TO ORDERS UNDER \$10.
 ITEMS POSTPAID EXCEPT WHEN NOTED.
 CALIFORNIANS + TAX.
 SORRY, NO COD ORDERS.


GODBOUT

CALL (415) 357-7007
 TO PLACE MASTERCARD[®]
 OR BANKAMERICARD[®] ORDERS,
 24 HOURS A DAY!

ROM PROGRAMMING -- ROM PROGRAMMING -- ROM PROGRAMMING -- ROM PROGRAMMING
 We can program your 5203s, 5204s, 1702s, and other ROMs for \$7.50 a piece or 10/\$35. Call our 24 hr phone line to request hexadecimal coding forms

MICROCOMPUTER 16 BIT KIT ... including

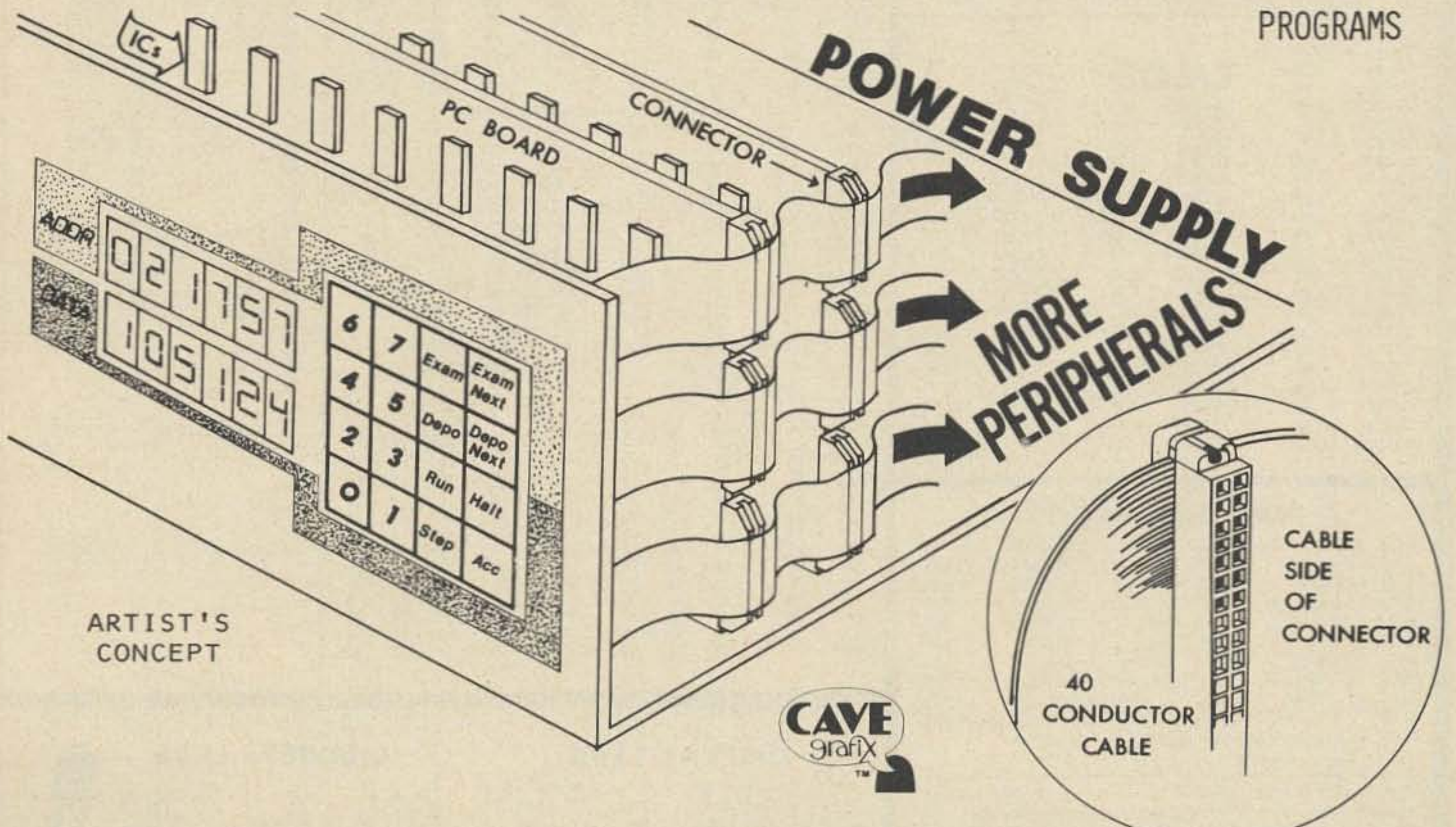CPU BOARD /// 1K X 16 INTEGRAL RAM /// SERIAL I/O INTERFACE /// POWER SUPPLY
 FRONT PANEL //// AUDIO CASSETTE I/O //// INTERFACE AND EDITOR & ASSEMBLER PROGRAMS



WRITE FOR DETAILS!

JAMES

DIGITAL COUNTER UNIT

- *Digit Latches
- *On Board Oscillator
- 4 Each - Man7 Displays
- * ± 10000 Counter
- *Complete with Board



\$29.95 Kit

DIGITAL VOLTMETER KIT

0-2 Volt, Auto Polarity 3½ digits (MAN7)
DVM MOS - LSI Design
Size: 2½" x 2¼" x 1½"



\$39.95

TTL Logic Probe Kit

Detects TTL levels, pulses, with man 3 readout



\$9.95 per kit

DVM Chip Set Siliconix

LD110 Digital A/D Processor 16.00
LD111 Analog A/D Processor 13.00

\$28.00 Set

DM8890N

Complete Horiz./Vert. Divider Chain for T.V. Type, Appl. 1.95 Each

PRIME INTEGRATED CIRCUIT ASSORTMENTS

ASST. 8	3 ea.	SN7400	7401	7402	7403	7404	SSI/TTL	\$5.95 ASST.
		SN7410	7430	7438	7440	7472		
ASST. 9	2 ea.	SN7447	7490	7491	74100	74121	MSI/TTL	\$9.95 ASST.
		SN74145	74175	74180	74191	74193		
ASST. 10	2 ea.	CD4001	4002	4011	4012	4013	CMOS	\$8.95 ASST.
		CD4016	4017	4019	4023	4030		
ASST. 11	2 ea.	LM301T	301N	302T	307T	309K	LINEAR	\$10.95 ASST.
		LM311T	565T	567T	741T	741N		

4' POWER SUPPLY CORDS

Black .59¢ ea.

THUMBWHEEL SWITCHES



Part No.	Description	Price
SF-12	Single Pole 10 Position	\$2.50
SF-12	Decade	3.00
SF-21	10 Position BCD only	3.50
SF-21		3.00

Snap together - No Hardware

SERIES SF Front Mount Assembly (S11.78)



Note: Picture to the left has the following:
4 ea. SF-12, 1 ea. SF-EP, 1 ea. SF-BB,
1 ea. SF-OP and 1 ea. SF-HB.

Part No.	Description	Price
SF-EP	End Plate (Pair)	.50
SF-OP	Divider Plate (each)	.40
SF-BB	Blank Body (each)	.40
SF-HB	Half Body (each)	.40

SERIES SR Rear Mount Assembly (S11.78)



Note: Picture to the left has the following:
4 ea. SR-12, 1 ea. SR-EP, 1 ea. SR-BB,
1 ea. SR-OP and 1 ea. SR-HB.

Part No.	Description	Price
SR-EP	End Plates (pair)	.50
SR-OP	Divider Plate (each)	.40
SR-BB	Blank Body (each)	.40
SR-HB	Half Body (each)	.40

Ordering: Order desired switch or switches and add necessary accessories for your particular application.

POCKET CALCULATOR KIT

5 function plus constant - addressable memory with individual recall - 8 digit display plus overflow - battery saver - uses standard or rechargeable batteries - all necessary parts in ready to assemble form - instructions included. 3" x 5¼" \$17.50 each

OPTIONS -
115VAC Transformer 4.95 each
6 each "N" Alkaline Batteries 2.50 lot

.394" DIAM. TRIMMER

MODEL	100Ω	500Ω	1K
2K, 5K, 10K, 20K, 100K, 200K, 1Meg			
RESISTANCE (OHMS)	1-8	10-34	
STD100Ω	.35	.30	
1 MEGΩ			

1/16 VECTOR BOARD

MATERIAL	STOCK NO.	LONG	WIDE	PRICES
PHENOLIC	84P44 022XXX	4.50	8.50	1.72 1.54
	180P44 022XXX	4.50	17.00	2.88 2.32
	84P44 062	4.50	8.50	2.07 1.88
EPOXY GLASS	84P44 062	4.50	8.50	2.58 2.31
	180P44 062	4.50	17.00	5.04 4.53
	180P44 062	8.50	17.00	8.72 8.20
EPOXY GLASS COPPER CLAD	180P44 062C1	4.50	17.00	8.80 8.12

WALL or T.V. DIGITAL CLOCK

12 or 24 Hour
25' VIEWING DISTANCE
Walnut Case-6" x 3" x 1"
Hr. & Min.-6" High
Seconds-3" High
KIT - All Comp. & Case
Wired & Assembled 115 Vac



\$39.95
\$44.95

NEW PROTO BOARD-100

Here's a low cost, big 10 IC capacity breadboard kit with all the quality of QT Sockets and the best of the Proto-Board series . . . complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.




COMPLETE KIT . . . \$19.95

50 PCS. RESISTOR ASSORTMENTS \$1.75 PER ASST.

ASST. 1	5 ea:	10 OHM- 12 OHM- 15 OHM- 18 OHM- 22 OHM 27 OHM- 33 OHM- 39 OHM- 47 OHM- 56 OHM	1/4 WATT 5% = 50 PCS.
ASST. 2	5 ea:	68 OHM- 82 OHM-100 OHM-120 OHM-150 OHM 180 OHM-220 OHM-270 OHM-330 OHM-390 OHM	1/4 WATT 5% = 50 PCS.
ASST. 3	5 ea:	470 OHM-560 OHM-680 OHM-820 OHM- 1K 1.2K 1.5K 1.8K 2.2K 2.7K	1/4 WATT 5% = 50 PCS.
ASST. 4	5 ea:	3.3K 3.9K 4.7K 5.6K 6.8K 8.2K 10K 12K 15K 18K	1/4 WATT 5% = 50 PCS.
ASST. 5	5 ea:	22K 27K 33K 39K 47K 56K 68K 82K 100K 120K	1/4 WATT 5% = 50 PCS.
ASST. 6	5 ea:	150K 180K 220K 270K 330K 390K 470K 560K 680K 820K	1/4 WATT 5% = 50 PCS.
ASST. 7	5 ea:	1M 1.2M 1.5M 1.8M 2.2M 2.7M 3.3M 3.9M 4.7M 5.6M	1/4 WATT 5% = 50 PCS.

IC'S EXAR KITS FUNCTION GENERATOR KIT

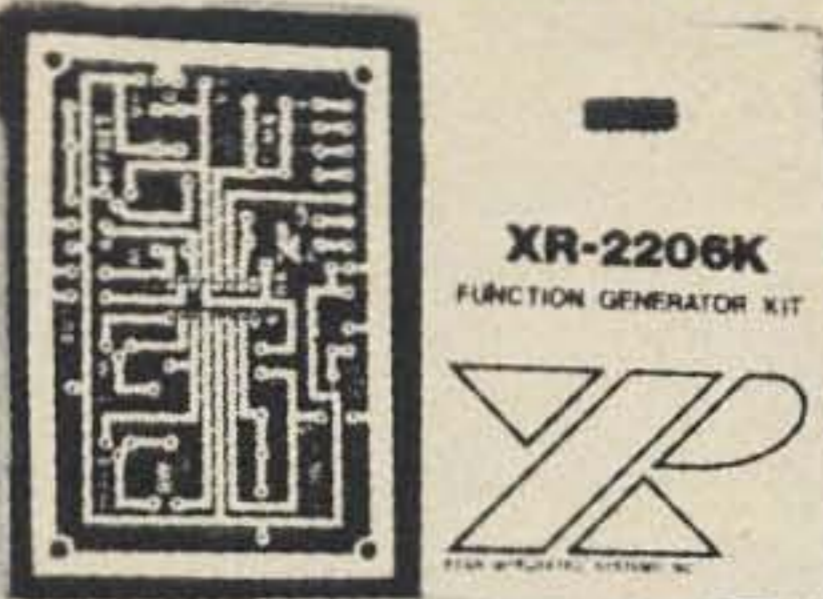

features sine, triangle and square wave; THD 0.5% typ.; AM/FM capability

XR-2206KA \$19.95
Includes monolithic function generator IC, PC board, and assembly instruction manual.

XR-2206KB \$29.95
Same as XR-2206KA above and includes external components for PC board.

TIMERS	PRICE
XR-555CP Monolithic Timer	\$ 1.10
XR-320P Precision Timer	1.55
XR-556CP Dual-555 Timer	1.85
XR-2556CP Dual Timing Circuit	3.20
XR-2240CP Programmable Counter/Timer	4.80
PHASE LOCKED LOOPS	
XR-210 FSK Demodulator	5.20
XR-215 High Frequency PLL	6.60
XR-567CP Tone Decoder (mini DIP)	1.95
XR-567CT Tone Decoder (TO-5)	1.70
STEREO DECODERS	
XR-1310P PLL Stereo Decoder	3.20
XR-1310EP PLL Stereo Decoder	3.20
XR-1800P PLL Stereo Decoder	3.20
WAVEFORM GENERATORS	
XR-205 Waveform Generator	8.40
XR-2206CP Monolithic Function Generator	5.50
XR-2207CP Voltage-Controlled Oscillator	3.85
OTHER EXAR IC'S	
XR-1468CN Dual + 15V Tracking Regulator	3.85
XR-1488N Quad Line Driver	5.80
XR-1489AN Quad Line Receiver	4.80
XR-2208CP Operational Multiplier	5.20
XR-2211 CP FSK Demodulator/Tone Decoder	6.70
XR-2261 Monolithic Proportional Servo IC System w/4 ea. Driver Transistor	3.79

Special Requested Items

RC4194 Dual Track V Reg	\$5.95	N8T97	\$3.00	2533	\$11.85
RC4195 * 15v Track Reg	3.25	4024P	2.25	8263	5.95
MC1741 High Slew Op Amp	4.00	2513	11.00	8267	2.75
MC4044P	4.50	2518	7.00	8288	1.15
CA3130 Super CMOS Op Amp	1.49	2524	3.50	8826	3.00
40410 3w PNP	1.75	2525	6.00	8880	1.35
40673 3w NPN	1.75	2527	5.00	7497	5.00

(Zener)				DIODES				(Rectifier)			
TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE	TYPE	VOLTS	W	PRICE
IN746	3.3	400m	4/1.00	IN4003	200 PIV	1 AMP	.10				
IN751A	5.1	400m	4/1.00	IN4004	400 PIV	1 AMP	.10				
IN752	5.6	400m	4/1.00	IN3600	50	200m	6/1.00				
IN753	6.2	400m	4/1.00	IN4148	75	10m	15/1.00				
IN754	6.8	400m	4/1.00	IN4154	35	10m	12/1.00				
IN965B	15	400m	4/1.00	IN4734	5.6	1w	.28				
IN5232	5.6	500m	.28	IN4735	6.2	1w	.28				
IN5234	6.2	500m	.28	IN4736	6.8	1w	.28				
IN5235	6.8	500m	.28	IN4738	8.2	1w	.28				
IN5236	7.5	500m	.28	IN4742	12	1w	.28				
IN456	25	40m	6/1.00	IN4744	15	1w	.28				
IN458	150	7m	6/1.00	IN1183	50 PIV	35 AMP	1.60				
IN485A	180	10m	5/1.00	IN1184	100 PIV	35 AMP	1.70				
IN4001	50 PIV	1 AMP	.09	IN1186	200 PIV	35 AMP	1.80				
IN4002	100 PIV	1 AMP	.10	IN1188	400 PIV	35 AMP	3.00				

TRANSISTORS					
MPS-A05	5/S1		2N3905	4/S1	
2N918	.25	2N2906A	4/S1	2N3906	4/S1
2N2219A	3/S1	2N2907A	5/S1	PN4249	4/S1
2N2221	4/S1	2N3053	2/S1	PN4250	4/S1
2N2222A	5/S1	2N3055	.95	2N4409	5/S1
2N2369	5/S1	2N3725A	2/S1	2N5129	.19
2N2369A	4/S1	2N3903	5/S1	2N5139	.19
2N2484	4/S1	2N3904	4/S1	C106B1-SCR	2/S1

JAMES Electronics

P. O. Box 822 - Belmont, Ca. 94002
PHONE ORDERS WELCOME
(415) 592-8097

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.
California Residents - Add 6% Sales Tax
Write for FREE 1975 Catalog - Data Sheets .25¢ each



Desk top calculator by well known mfr. These are rejects, 8 digit, 4 function, liquid crystal display. Fully assembled, some factory reject, some customer returns. Most are repaired in a few minutes. Sold "as is." Ship wt 3 lbs.

Battery portable model \$11 each
3 for \$30.00

SINGLE CHIP ASCII ENCODER

A hot item today. We furnish full data booklet with each order. \$10 each 3 for \$25.00

8 CHAN MULTIPLEX SWITCH

Solid state 16 pin IC MOS. 8 channel w/output enable control & one-of-eight decoder in chip. With data. Fairchild 3705. . . ~~\$5.00~~ \$3.00

RC OSCILLATORS

16 pin IC chip contains 4 RC osc. Ideal for touch tone encoder. TCA 430. . . ~~\$5.00~~ \$3.00

PHOTO-STROBE

Made for Instamatic but useful on any camera with instructions provided. Info also on trick uses, automotive strobe, slave strobe, automotive strobe, Psychedelic repetitive strobe, etc. Complete with charger & Nickel Cadmium batteries.

\$8.00, 3 for \$22.00

COLUMBIA 4 CHANNEL SQ

Solid state SQ 4 channel adapter, 2 amps built in. Decodes 4 channel or synthesizes 4 channel.
\$20.00

LED READOUTS 5/\$1.00!

The price is not a mistake. We have some hobby variety with some segments out. Ukinbuyem for as low as
5 for \$1.00

DUAL 16 BIT MEMORY

Dual 16 bit memory, serial MOS by Philco TO-5 case, brand new with 2 page specs.
#PLR 532 \$1.00 each \$10/12

AM-FM RADIO

For console installation, w/face plate, no knobs. Stereo amplifiers for tape or turnable playback.
\$15.00
Pair of matching speakers w/xfmrs for above
\$5.00

CALCULATOR CHASSIS

Fully assembled pocket calculator chassis less calculator chip. Uses LED readouts not included.
\$1.00 each, 6/\$5.00




Beautiful AM-FM Stereo Multiplex radios made to sell in the over \$100 range. Picture shows typical unit. Solid state. AC powered, made for famous US manufacturer. Ship wt 10 lbs.
\$35.00

BELLTONE PAGER

Genuine "Ma Bell" belt clip radio receiver beeper. Picks up specific radio signals in 35 MHz area, encoded by internal reed encoder. Seems to be a "natural" for construction jobs, in-plant calling. An interesting experimental gadget. Self contained antenna, adjustable coding by shifting wires on coding module.

#SP-125 \$5.00 each, 6/\$25.00

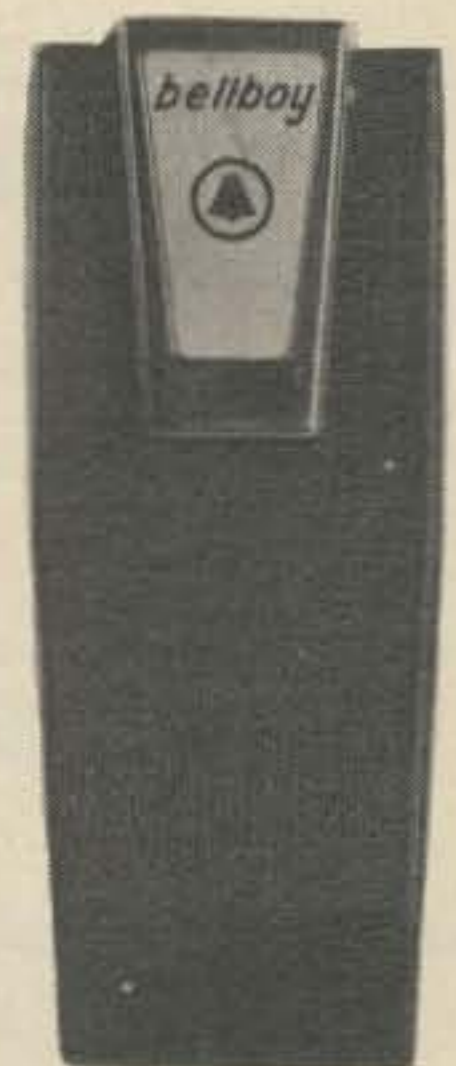

Please add shipping cost on above.

Meshna


P.O. Box 62
E. Lynn MA 01904

FREE CATALOG

KEYBOARD \$35.00

One of the nicest keyboards we've found. Mounted in modern design wood grained enclosure for desk-top use. Magnetic reed relay bounceless keyswitches, Encoder board mounted within. Fine Biz. for Morse Code Generators — TV Typewriter — computer terminals, etc.

7 lb #SP-153L \$35.00

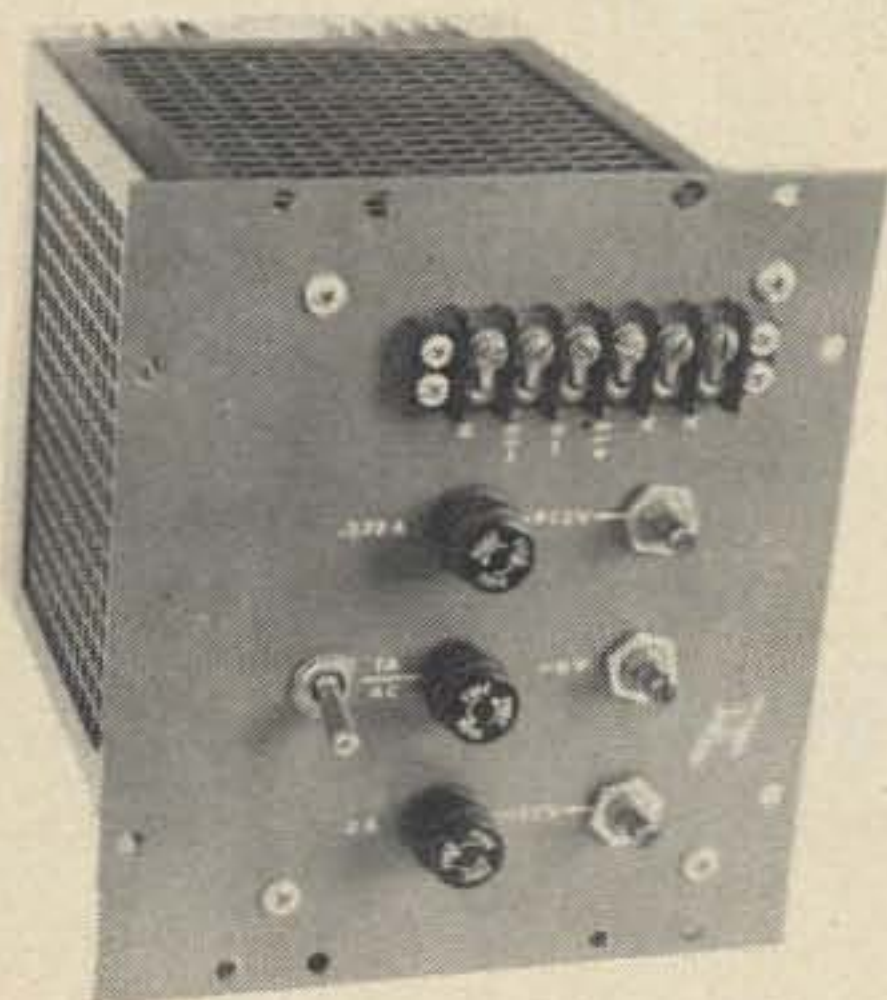

GENERAL PURPOSE POWER SUPPLY



Well designed transistorized, regulated power supply with many uses. Each voltage adjustable by pot. Each voltage fused. 115 volts ac input. Output (minus) 12 volts at 1/3 Amp, 12 volts (plus) at 3 Amps, 6 volts at 1 Amp. Three output voltages. Many uses . . . as battery charger, op amp (plus & minus 12 volts), 5 volt logic (adjust 6 volts to 5 volts), operate your car radio, tape player, CB set in the house, etc. A commercially built supply for less than the price of kit.

10 lb #SP-152L \$12.50 5/\$50

AIR COMPRESSOR \$19.00

Diaphragm compressor slightly used surplus from the computer industry. Built-in 115 volt ac motor ball bearing for long life. Puts out 17 PSI with volume 0.7 SCFM. For general paint spraying, air cleaning, bubble bath for PC etching tank, etc. Many uses in lab or home.

14 lb #SP-148L \$19.00

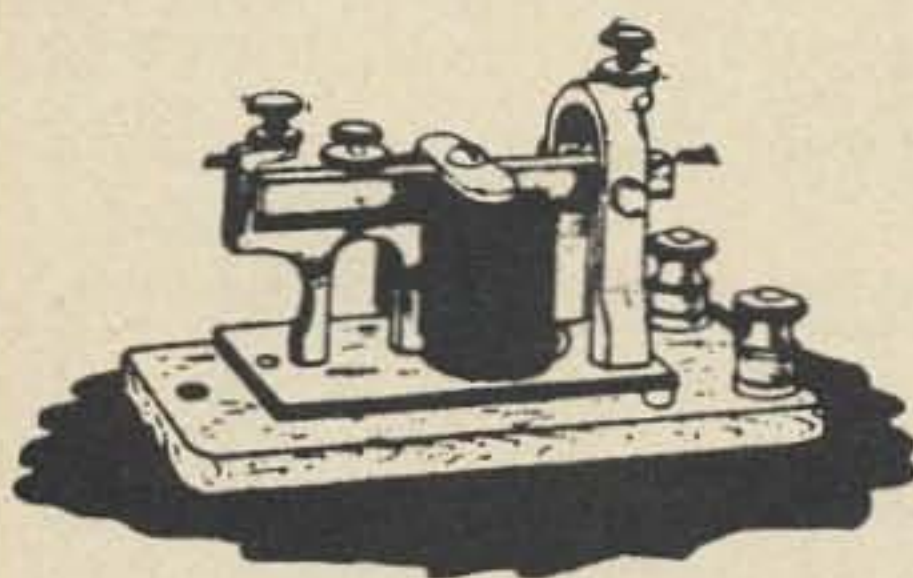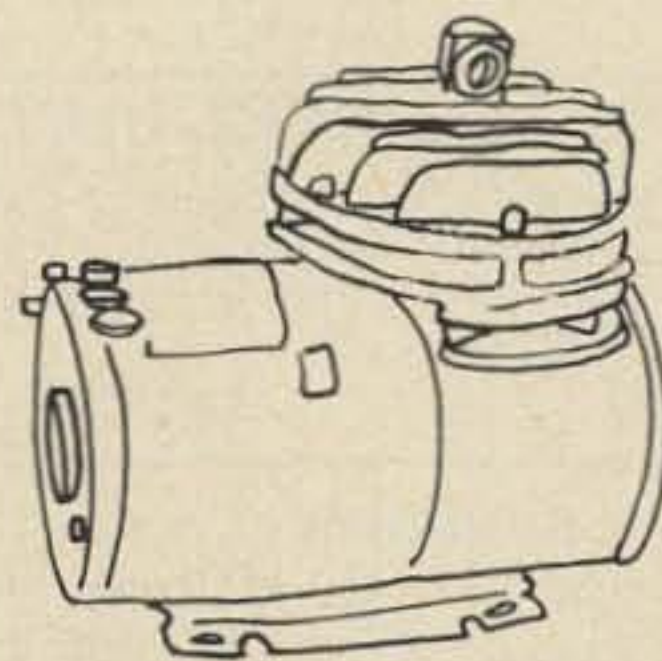

ANTIQUE SOUNDER

Takes you back to the Pony Express days. A genuine antique relic dating back to the old days. A real beauty, polished brass, wood base, bright and shiny new despite its age. In original packing as issued to the US Navy Dept. Already worth more than our asking price. Makes an unusual gift or desk top conversation piece for the man who has almost everything.

#SP-115 \$15.00 2/\$25.00

SPERRY 9 DIGIT DISPLAY \$2.50

180 volt 9 digit, 0.25 inch height character. Brand new and we include free with each, the \$1.50 mating socket. The price an astounding new low . . . \$2.50



#SP-145 \$2.50 5/\$10.00

Please add shipping cost on above.

Meshna

P.O. Box 62
E. Lynn, Massachusetts 01904

FREE CATALOG



7-Segment Readout 12-PIN DIP

Three digits with right-hand decimal
Plugs into DIP sockets
Similar to (LITRONIX) DL337
Magnified digit approximately .1"
Cathode for each digit
Segments are parallel for multiple
operation
5-10 MA per segment
EACH \$1.75 4 (12 DIGITS) \$6.00

RCA Numitron

EACH.....\$ 5.00

SPECIAL: 5 FOR \$20.00

DR2010



MOS MEMORY 2102-2

1024 Bit Fully Decoded Static MOS
Random Access Memory

- fast access 650ns
- fully TTL compatible
- n channel silicon gate
- single 5 volt supply
- tri-state output
- 1024 by 1 bit
- chip enable input
- no clocks or refreshing
required

Brand New Factory Parts
16 PIN DIP Each \$5.00
8 for \$34.95

Power Supply SPECIAL!

723 DIP variable regulator chip 1-40V,
+ or - output @ 150 MA 10A with external
pass transistor--with diagrams for
many applications.
EACH \$1.00 10 FOR \$8.95

5001 Calculator

40-Pin calculator chip will add, sub-
tract, multiply, and divide. 12-digit
display and calculate. Chain calcula-
tions. True credit balance sign out-
put. Automatic over-flow indication.
Fixed decimal point at 1, 2, 3, or 4.
Leading zero suppression. Complete
data supplied with chip.

CHIP AND DATA.....ONLY \$2.49
DATA ONLY (Refundable)... \$1.00
5002 LOW POWER CHIP AND DATA \$12.95

High Quality PCB Mounting IC Sockets

8-PIN, 14-Pin, 16-Pin and 24-Pin PCB
mounting ONLY--no wire wrap sockets.

8-Pin.....\$.22

14-Pin.....\$.26

16-Pin.....\$.30

24-Pin.....\$.75

40-Pin.....\$1.25



All IC's are new and fully tested. Leads
are plated with gold or solder. Orders
for \$5.00 or more will be shipped prepaid
Add \$.55 for handling and postage for
smaller orders; residents of California
add sales tax. IC orders are shipped
within 2 workdays--kits are shipped with-
in 10 days of receipt of order. \$10.00
minimum on C.O.D.'s.

Mail Orders to: Phone
P.O. Box 41727
Sacramento, CA (916) 334-2161
95841

BABYLON ELECTRONICS

Money back guarantee
on all goods!



Dale Trimmer

-12 turn trim pots which plug
into a DIP socket
-5K and 200K
- $\frac{1}{2}$ " x $\frac{1}{4}$ " x $\frac{1}{4}$ "
-4 leads spaced .3" x .2"
Each \$1.00 10 for \$8.95

1000 MHz Counter

11C05 Fairchild 1GHz Divide By Four

- DC to 1000 MHz operation
- AC or DC coupled
- Voltage compensated
- TTL or ECL power supply
- 50 ohm drive output
- Lead compatible with Plessey SP613
- True and complement ECL outputs
- 14 pin DIP
- Data and application notes

Each \$49.95

LED's

MV50 Red Emitting \$.20
10-4 MA @ 2V 10 FOR \$1.25

MV5024 Red TO-18 \$.35
High Dome 10 FOR \$2.95

MV10B Visible Red \$.30
5-7 MA @ 2V 10 FOR \$2.50

CMOS

CD4001 \$.45	CD4023 \$.45
CD4002 .45	74C20 .65
CD4011 .45	74C160 3.25
CD4012 .45	

3-Amp Power Silicon Rectifiers

MARKED EPOXY AXIAL PACKAGE

PRV	PRICE	PRV	PRICE
100.....	\$.10	800.....	\$.30
200.....	.15	1000.....	.40
400.....	.18	1200.....	.50
600.....	.23	1500.....	.65

DIODE ARRAY 10-1N914 silicon
signal diodes in one package. 20
leads spaced .1"; no common connec-
tions.
EACH.....\$.29
10 FOR \$2.50




7400 .20	74H51 .25
74H00 .30	7453 .20
7401 .20	7454 .20
74H01 .25	74L54 .25
7402 .25	74L55 .25
7403 .25	7460 .16
7404 .25	74L71 .25
74H04 .30	7472 .40
7405 .30	74L72 .60
7406 .40	7473 .35
7408 .30	74L73 .75
74H08 .30	7474 .45
7410 .20	74H74 .75
7413 .75	7475 .80
7417 .40	7476 .55
7420 .20	74L78 .70
74L20 .30	7480 .50
74H20 .30	7483 .70
74H22 .30	7489 3.00
7430 .20	7490 1.00
74H30 .30	7492 .65
74L30 .30	7493 1.00
7440 .20	7495 .65
74H40 .30	74L95 1.00
7442 1.00	74107 .35
7447 1.50	74145 1.25
7450 .20	74180 1.00
74H50 .30	74193 1.50
7451 .20	74195 .65

7400 Series DIP

25K Trimmer

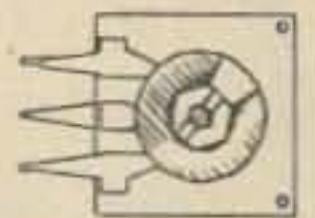PRINTED CIRCUIT BOARD TYPE
EACH \$.20 10 FOR \$1.50



Rectifiers

VARO FULL-WAVE BRIDGE




VS647	2A	600V	\$1.10
MR810 Rectifier	50V	1A	\$.10

Special 811: Hex Inverter

TTL DIP Hex Inverter; pin interchangeable with SN
7404. Parts are brand new and branded Signetics
and marked "811."

DATA	EACH	\$.16
SHEET	10 FOR	1.50
SUPPLIED	100 FOR	14.00
	1000 FOR	110.00

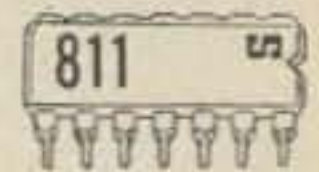


1 AMP RECTIFIER

1N4007 1KV PRV EACH \$.15
SALE 10 for \$1.00



MAN 4

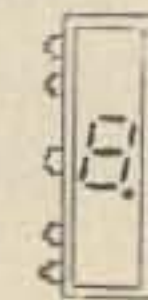7-Segment, 0-9 plus letters.
Right-hand decimal point. Snaps in 14-
pin DIP socket or Molex. IC voltage re-
quirements. Ideal for desk or pocket
calculators!




EACH \$1.20 10 OR MORE \$1.00 EACH

CD-2 Counter Kit

This kit provides a highly sophisticated display
section module for clocks, counters, or other nu-
merical display needs. The unit is .8" wide and
4 3/8" long. A single 5-volt power source powers
both the ICs and the display tube. It can attain
typical count rates of up to 30 MHz and also has
a lamp test, causing all 7 segments to light. Kit
includes a 2-sided (with plated thru holes) fiber-
glass printed circuit board, a 7490, a 7475, a
7447, a DR2010 RCA Numitron display tube, complete
instructions, and enough MOLEX pins for the ICs...
NOTE: boards can be supplied in a single panel of
up to 10 digits (with all interconnects); there-
fore, when ordering, please specify whether you
want them in single panels or in one multiple
digit board. Not specifying will result in ship-
ping delay.

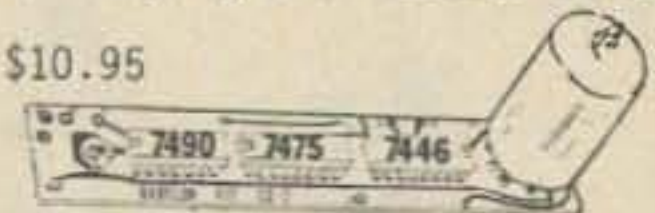COMPLETE KIT ONLY \$10.95
FULLY-ASSEMBLED
UNIT \$15.00



Boards supplied separately @ \$2.50 per digit.

LINEARS

NE555	Precision timer.....	.90
NE560	Phase lock loop DIP.....	2.95
NE561	Phase lock loop DIP.....	3.00
NE565	Phase lock loop.....	2.95
NE566	Function generator TO-5.....	3.50
NE567	Tone decoder TO-5.....	3.50
709	Popular Op Amp DIP.....	.40
710	Voltage comparator DIP.....	.60
711	Dual comparator DIP.....	.45
723	Precision voltage regulator DIP.....	1.00
741	Op amp TO-5/MINI DIP.....	.45
748	Op Amp TO-5.....	.80
CA3018	2 Isolated transistors and a Darling- ton-connected transistor pair.....	1.00
CA3045	5 NPN transistor array.....	1.00
LM100	Positive DC regulator TO-5.....	1.00
LM105	Voltage regulator.....	1.25
LM302	Op Amp voltage follower TO-5.....	1.25
LM308	Op Amp TO-5.....	2.00
LM309H	5V 200 MA power supply TO-5.....	1.00
LM309K	5V 1A power supply module TO-3.....	1.00
LM311	Comparator Mini.....	1.75
LM370	AGC amplifier.....	1.75
LM380	2-Watt Audio Amp.....	1.75
LM1595	4-Quadrant multiplier.....	1.70
MC1536T	Op Amp.....	1.35

LOWEST PRICES IN POLY PAKS SMASHES U.S.A.!

'CALCULATOR' PRICES

9-FUNCTION, 8-DIGIT MEMORY CALCULATOR KIT

It's the easiest multi-function kit today!

- DOUBLE MEMORY
- Percent, Constant, Display Restore

\$16.95



4-Function Arithmetic
• 22 KEYS!

EASY TO PUT TOGETHER! You bet it is... imagine no resistors, capacitors, but it **ONLY REQUIRES 2 CHIPS** and a **READOUT!** How's that for simplicity? The 2 Memory keys are MS Memory Storage and MR Memory Recall (requires very little soldering). The display restore key is to conserve battery life. Your display on panel shuts off 25 seconds after the last operation. By depressing "D" key, the display is restored! Uses 6 N cell batteries. Red decimal appears on left to show when batteries need replacement or charging. Has Decimal, Clear, Constant, Percent, and arithmetic key red, white and blue colors. Lightweight, pocket size 5 1/4 x 3 x (2" at back side) x 1 1/4" front side of angular display panel black case. Nifty unit for business, school, home, and for the youngsters. Slips into any pocket, briefcase with ease. Easy-to-understand pictorial instruction booklet and how-to-use-book.

AC/DC too!
KIT INCLUDES: case, 22-key keyboard kit, ON-OFF switch (part of keyboard) PC board, driver and memory calculator chips, 9-digit "bubble" magnifier-LED array, array cable, AC adapter jack & wires, battery case, 6 battery card display, instruction and pictorial step-by-step construction booklet.

MICROPROCESSORS! ROMS! RAMS! MEMORIES!

- 8008 Microprocessor \$39.95
- 8080 Super 8008 250.00
- 2102 1024 Static RAM 3.95
- 1101 256 bit RAM 1.50
- 1103 1024 bit RAM 2.95
- MM5260 1024 RAM 2.95
- MM5262 2048 bit RAM 6.50
- 2513 Character generator 12.50
- MM5203Q Erasable PROM 19.95
- MM5202Q Erasable PROM 19.95
- 1702A Erasable PROM 19.95
- 8223 Programmable ROM 2.95

'BLASTAWAY' ON 1N4000 RECTIFIER PRICES

- | Type | PIV | Sale |
|---------------------------------|---------|----------|
| <input type="checkbox"/> 1N4001 | 50 10 | for 45c |
| <input type="checkbox"/> 1N4002 | 100 10 | for 55c |
| <input type="checkbox"/> 1N4003 | 200 10 | for 65c |
| <input type="checkbox"/> 1N4004 | 400 10 | for 75c |
| <input type="checkbox"/> 1N4005 | 600 10 | for 85c |
| <input type="checkbox"/> 1N4006 | 800 10 | for 99c |
| <input type="checkbox"/> 1N4007 | 1000 10 | for 1.29 |

4 1/2 DIGIT DIGITAL VOLTMETER DVM CHIP

Type MM5330 by National utilizes P channel low-threshold enhancement mode devices and ion implanted depletion mode devices. Provides logic circuit for 4 1/2 digit DVM. All logic for four decade counters, a divide by four counter, a divide by two counter for over-range blanking, latches for all counter stages, an output ROM to generate BCD to 9's complement BCD of the latches and a module 4 counter to sequentially present each of decade latches thru ROM to the BCD outputs plus four outputs to indicate which decade is display. A reset for all counter stages, transfer pulse generator to set the latches. To 400 KHz operation. TTL compatible. With instruction sheets and diagram on "how-to-build a 4 1/2 digit DVM". Ideal with our Litronix 1/2" single, 1 1/2" and dual digits, 16-pin DIP.

\$14.95



Money-Back GUARANTEE on all items

LED Revolution!

MONSANTO! XCITON! LITRONIX! OPCOA!


5 for \$1

- | .340x.260 | .240x.200 |
|---------------------------------|---------------------------------|
| Jumbo | Medium |
| <input type="checkbox"/> Red | <input type="checkbox"/> Red |
| <input type="checkbox"/> Green | <input type="checkbox"/> Yellow |
| <input type="checkbox"/> Yellow | <input type="checkbox"/> Green |
| <input type="checkbox"/> Amber | <input type="checkbox"/> Amber |
| <input type="checkbox"/> Clear | <input type="checkbox"/> Clear |
| Micro | .210x.125 |
| <input type="checkbox"/> Red | <input type="checkbox"/> Yellow |
| <input type="checkbox"/> Green | <input type="checkbox"/> Amber |

- Micro (Axial) MV-50 style
- MV-50 Clear 10 for \$1.
 - MV-55 Red 6 for \$1.

Touch Tone KEYBOARD KIT \$4.95

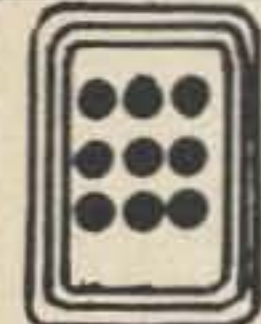Kit includes 4 x 2 1/2" G-10 glass etched pc board, with 10 OAK "smooth touch" white keys with black numerals, plus diagram on "touch tone encoder". Makes many "keyboard systems" readily available. 0-to-9



This unit is not advertised anywhere! Made for Motorola Communications at the original cost of \$4.50 each (for insertion in their Walkie Talkie Program). It's a 60-ohm imp MIKE. It's an excellent speaker

POSTAGE STAMP MOBILE SPKR MIKE \$1.98

too, covering broad range in sound. Extremely well-made.

555

Timer
2 for \$1

OR

558

Dual 741
3 for \$1

NATIONAL LM-340T VR's

* TO-220 Case * 1 Amp * POSITIVE VOLTAGE

\$1.75 Each

- Buy 3 - Take 10%
- | Type | Volts |
|-------------------------------------|-------|
| <input type="checkbox"/> LM-340-05T | 5 v |
| <input type="checkbox"/> LM-340-06T | 6 v |
| <input type="checkbox"/> LM-340-08T | 8 v |
| <input type="checkbox"/> LM-340-12T | 12 v |
| <input type="checkbox"/> LM-340-15T | 15 v |
| <input type="checkbox"/> LM-340-18T | 18 v |
| <input type="checkbox"/> LM-340-24T | 24 v |

7-SEGMENT READOUT SALE!

* Up to 20 mils per seg. at 5V. MAN-1
* All fit into 14-pin IC socket.

- | Type | Size | Color | Sale | 3 for |
|----------------------------------|------|--------|--------|--------|
| <input type="checkbox"/> MAN-1 | .27 | Red | \$2.50 | \$6.00 |
| <input type="checkbox"/> MAN-3MA | .12 | Red | .69 | 2.00 |
| <input type="checkbox"/> MAN-4AB | .27 | Red | 1.95 | 5.00 |
| <input type="checkbox"/> MAN-5 | .27 | Green | 1.50 | 4.00 |
| <input type="checkbox"/> MAN-6 | .6 | Red | 4.50 | 12.00 |
| <input type="checkbox"/> MAN-64 | .4 | Red | 3.50 | 9.00 |
| <input type="checkbox"/> MAN-7 | .27 | Red | 1.00 | 2.50 |
| <input type="checkbox"/> MAN-8 | .27 | Yellow | 1.50 | 4.00 |

ALL ABOVE BY MONSANTO

- | Type | Size | Color | Sale | 3 for |
|---------------------------------|------|--------|--------|--------|
| <input type="checkbox"/> SLA-1 | .33 | Red | \$1.95 | \$5.00 |
| <input type="checkbox"/> SLA-1 | .33 | Green | 1.95 | 5.00 |
| <input type="checkbox"/> SLA-1 | .33 | Yellow | 1.95 | 5.00 |
| <input type="checkbox"/> SLA-3 | .7 | Green | 4.95 | 12.00 |
| <input type="checkbox"/> SLA-3 | .7 | Yellow | 4.95 | 12.00 |
| <input type="checkbox"/> 707 | .33 | Red | 1.95 | 5.00 |
| <input type="checkbox"/> 704A | .33 | Red | 1.95 | 5.00 |
| <input type="checkbox"/> 701C | .33 | Red | 1.50 | 3.00 |
| <input type="checkbox"/> FND-70 | .25 | Red | 1.50 | 3.00 |

A—Common Cathode, others Common Anode
B—With bubble magnifier
C—Plus or Minus 1

LITRONIX "JUMBO'S"

* Singles size: 1 x 3/4 x 5/16
* Duals size: .8 x .9 x .29
* 7-Segment, 25-mils per segment

- | Type | Size | Color | Sale | 3 for |
|-------------------------------|------|-------|--------|---------|
| <input type="checkbox"/> 721D | .5 | Red | \$5.95 | \$15.00 |
| <input type="checkbox"/> 727E | .5 | Red | 5.95 | 15.00 |
| <input type="checkbox"/> 746F | .6 | Red | 3.95 | 11.00 |
| <input type="checkbox"/> 747 | .6 | Red | 3.95 | 11.00 |

D—Plus or Minus 1 plus a digit (1 1/2 digits)
E—Dual digits
F—Plus or Minus 1

Terms: add postage Rated: net 30
Phone Orders: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Del Carmine St., Wakefield, Mass.
(off Water Street) C.O.D.'S MAY BE PHONED

20c CATALOG Fiber Optics, 'ICs', Semi's, Parts
MINIMUM ORDER — \$4.00

POLY PAKS

P.O. BOX 942A LYNNFIELD, MASS. 01940

INDUSTRIAL SPEED CONTROL \$4.95

A \$30 item from G.E. Model 533A (made for Xerox) that controls home, shop and industrial lighting too! A very elaborate circuit for controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, etc. 115vac, rated at 1100 watts. With variable speed or dimming control in heavy-duty aluminum case. 3 x 2 3/4 x 2. With diagram and hookups.

Wow! INCREDIBLE PRICES

TW'S

BUY ANY 10 TAKE 15%

BUY 100 TAKE 25%

- | | | | | | |
|---------------------------------|------|----------------------------------|-------|----------------------------------|------|
| <input type="checkbox"/> SN7400 | .16 | <input type="checkbox"/> SN7489 | 2.45 | <input type="checkbox"/> SN74155 | .95 |
| <input type="checkbox"/> SN7401 | .16 | <input type="checkbox"/> SN7490 | .59 | <input type="checkbox"/> SN74156 | .95 |
| <input type="checkbox"/> SN7402 | .16 | <input type="checkbox"/> SN7491 | 1.10 | <input type="checkbox"/> SN74157 | .95 |
| <input type="checkbox"/> SN7403 | .16 | <input type="checkbox"/> SN7492 | .59 | <input type="checkbox"/> SN74158 | .95 |
| <input type="checkbox"/> SN7404 | .19 | <input type="checkbox"/> SN7493 | .59 | <input type="checkbox"/> SN74160 | 1.35 |
| <input type="checkbox"/> SN7405 | .19 | <input type="checkbox"/> SN7494 | .95 | <input type="checkbox"/> SN74161 | 1.25 |
| <input type="checkbox"/> SN7406 | .35 | <input type="checkbox"/> SN7495 | .79 | <input type="checkbox"/> SN74163 | 1.35 |
| <input type="checkbox"/> SN7407 | .35 | <input type="checkbox"/> SN7496 | .79 | <input type="checkbox"/> SN74164 | 1.50 |
| <input type="checkbox"/> SN7408 | .19 | <input type="checkbox"/> SN74100 | 1.40 | <input type="checkbox"/> SN74165 | 1.50 |
| <input type="checkbox"/> SN7409 | .19 | <input type="checkbox"/> SN74104 | .44 | <input type="checkbox"/> SN74166 | 1.50 |
| <input type="checkbox"/> SN7410 | .16 | <input type="checkbox"/> SN74105 | .44 | <input type="checkbox"/> SN74173 | 1.45 |
| <input type="checkbox"/> SN7411 | .25 | <input type="checkbox"/> SN74106 | .52 | <input type="checkbox"/> SN74174 | 1.39 |
| <input type="checkbox"/> SN7413 | .59 | <input type="checkbox"/> SN74107 | .44 | <input type="checkbox"/> SN74175 | 1.30 |
| <input type="checkbox"/> SN7414 | 1.65 | <input type="checkbox"/> SN74108 | .89 | <input type="checkbox"/> SN74176 | 1.20 |
| <input type="checkbox"/> SN7416 | .34 | <input type="checkbox"/> SN74112 | .89 | <input type="checkbox"/> SN74177 | 1.20 |
| <input type="checkbox"/> SN7417 | .34 | <input type="checkbox"/> SN74113 | .89 | <input type="checkbox"/> SN74180 | .95 |
| <input type="checkbox"/> SN7420 | .16 | <input type="checkbox"/> SN74114 | .89 | <input type="checkbox"/> SN74181 | 2.98 |
| <input type="checkbox"/> SN7412 | .45 | <input type="checkbox"/> SN74121 | .49 | <input type="checkbox"/> SN74182 | .74 |
| <input type="checkbox"/> SN7423 | .29 | <input type="checkbox"/> SN74122 | .48 | <input type="checkbox"/> SN74184 | 1.98 |
| <input type="checkbox"/> SN7425 | .29 | <input type="checkbox"/> SN74123 | .85 | <input type="checkbox"/> SN74185 | 1.98 |
| <input type="checkbox"/> SN7426 | .25 | <input type="checkbox"/> SN74125 | .59 | <input type="checkbox"/> SN74190 | 1.40 |
| <input type="checkbox"/> SN7427 | .29 | <input type="checkbox"/> SN74126 | .59 | <input type="checkbox"/> SN74191 | 1.40 |
| <input type="checkbox"/> SN7430 | .16 | <input type="checkbox"/> SN74132 | 1.75 | <input type="checkbox"/> SN74192 | 1.25 |
| <input type="checkbox"/> SN7432 | .25 | <input type="checkbox"/> SN74140 | 2.10 | <input type="checkbox"/> SN74193 | 1.25 |
| <input type="checkbox"/> SN7433 | .49 | <input type="checkbox"/> SN74145 | 1.05 | <input type="checkbox"/> SN74194 | 1.20 |
| <input type="checkbox"/> SN7437 | .34 | <input type="checkbox"/> SN74148 | 2.25 | <input type="checkbox"/> SN74195 | .85 |
| <input type="checkbox"/> SN7438 | .34 | <input type="checkbox"/> SN74150 | .98 | <input type="checkbox"/> SN74196 | 1.80 |
| <input type="checkbox"/> SN7440 | .16 | <input type="checkbox"/> SN74151 | .75 | <input type="checkbox"/> SN74197 | .90 |
| <input type="checkbox"/> SN7441 | 1.00 | <input type="checkbox"/> SN74153 | .90 | <input type="checkbox"/> SN74199 | 1.75 |
| | | <input type="checkbox"/> SN74154 | 1.35 | <input type="checkbox"/> SN74200 | 4.95 |
| | | <input type="checkbox"/> SN7442 | \$.70 | | |
| | | <input type="checkbox"/> SN7444 | 1.25 | | |
| | | <input type="checkbox"/> SN7445 | .89 | | |
| | | <input type="checkbox"/> SN7446 | 1.15 | | |
| | | <input type="checkbox"/> SN7447 | .99 | | |
| | | <input type="checkbox"/> SN7448 | .99 | | |
| | | <input type="checkbox"/> SN7450 | .16 | | |
| | | <input type="checkbox"/> SN7451 | .17 | | |
| | | <input type="checkbox"/> SN7452 | .17 | | |
| | | <input type="checkbox"/> SN7453 | .17 | | |
| | | <input type="checkbox"/> SN7454 | .17 | | |
| | | <input type="checkbox"/> SN7455 | .22 | | |
| | | <input type="checkbox"/> SN7460 | .17 | | |
| | | <input type="checkbox"/> SN7462 | .22 | | |
| | | <input type="checkbox"/> SN7470 | .29 | | |
| | | <input type="checkbox"/> SN7471 | .49 | | |
| | | <input type="checkbox"/> SN7472 | .29 | | |
| | | <input type="checkbox"/> SN7473 | .36 | | |
| | | <input type="checkbox"/> SN7474 | .36 | | |
| | | <input type="checkbox"/> SN7475 | .59 | | |
| | | <input type="checkbox"/> SN7476 | .39 | | |
| | | <input type="checkbox"/> SN7478 | .79 | | |
| | | <input type="checkbox"/> SN7480 | .52 | | |
| | | <input type="checkbox"/> SN7481 | .99 | | |
| | | <input type="checkbox"/> SN7482 | .89 | | |
| | | <input type="checkbox"/> SN7483 | 1.25 | | |
| | | <input type="checkbox"/> SN7485 | 1.25 | | |
| | | <input type="checkbox"/> SN7486 | .37 | | |
| | | <input type="checkbox"/> SN7488 | 3.95 | | |

73 reader service

Check appropriate boxes for desired company brochures, data sheets or catalogs and mail in to 73. Include your zip code, please. Send money directly to advertisers. **LIMIT: 25 requests.**

ADVERTISER INDEX

- | | |
|---|--|
| <input type="checkbox"/> Advance Elec. 126 | <input type="checkbox"/> James 112, 186, 187 |
| <input type="checkbox"/> Aldelco 104 | <input type="checkbox"/> Jan 175 |
| <input type="checkbox"/> Alden Elec. 112 | <input type="checkbox"/> Jones, Marlin P. 178 |
| <input type="checkbox"/> Apollo 104 | <input type="checkbox"/> Kaufman 102 |
| <input type="checkbox"/> Apron 65 | <input type="checkbox"/> Kensco 35 |
| <input type="checkbox"/> Atlas 142 | <input type="checkbox"/> K Enterprises 138 |
| <input type="checkbox"/> Audioland 68 | <input type="checkbox"/> Kenwood 37 |
| <input type="checkbox"/> Autek 48 | <input type="checkbox"/> Klaus 159 |
| <input type="checkbox"/> Babylon 190 | <input type="checkbox"/> KLM 56 |
| <input type="checkbox"/> Budwig 147 | <input type="checkbox"/> Lafayette 80 |
| <input type="checkbox"/> BYTE 77 | <input type="checkbox"/> Levy 146 |
| <input type="checkbox"/> CeCo 154 | <input type="checkbox"/> Meshna 188, 189 |
| <input type="checkbox"/> CFP 122 | <input type="checkbox"/> MITS 31 |
| <input type="checkbox"/> Clegg 55, 75 | <input type="checkbox"/> M-Tech 146, 152 |
| <input type="checkbox"/> Coakit 122 | <input type="checkbox"/> Newtronics CII |
| <input type="checkbox"/> Comcraft 168 | <input type="checkbox"/> Nexus 170 |
| <input type="checkbox"/> Comm. Specialists 153 | <input type="checkbox"/> Non-Linear Systems 43 |
| <input type="checkbox"/> Comm. Specialties 82 | <input type="checkbox"/> Palomar 154 |
| <input type="checkbox"/> Compcode 147 | <input type="checkbox"/> Poly Paks 191 |
| <input type="checkbox"/> Control Signal 157 | <input type="checkbox"/> Quement 65 |
| <input type="checkbox"/> Cornell 122 | <input type="checkbox"/> Radio Callbook 134 |
| <input type="checkbox"/> Curtis 102 | <input type="checkbox"/> Regency 42 |
| <input type="checkbox"/> Davis 151 | <input type="checkbox"/> RGS 136 |
| <input type="checkbox"/> D-D Enterprises 147 | <input type="checkbox"/> Rohn 163 |
| <input type="checkbox"/> Dentron 81 | <input type="checkbox"/> S. D. Sales 181-183 |
| <input type="checkbox"/> DGM 126 | <input type="checkbox"/> Sentry 9 |
| <input type="checkbox"/> Dixie Tech 151 | <input type="checkbox"/> Space Elec. 146 |
| <input type="checkbox"/> D & N Gifts 121 | <input type="checkbox"/> Space Time Prod. 152 |
| <input type="checkbox"/> DuPage 167 | <input type="checkbox"/> Specialty Comm. 131 |
| <input type="checkbox"/> DXers 126 | <input type="checkbox"/> Spectrum Comm. 73 |
| <input type="checkbox"/> ECM 151 | <input type="checkbox"/> Standard Comm 89 |
| <input type="checkbox"/> Electronic Devel. 151, 152 | <input type="checkbox"/> Standard Research 119 |
| <input type="checkbox"/> Electronic Distr. 177 | <input type="checkbox"/> Sumner 66, 67 |
| <input type="checkbox"/> Electronic Supermart 122 | <input type="checkbox"/> Suntronix 179 |
| <input type="checkbox"/> ETCO 147 | <input type="checkbox"/> Swivetek 180 |
| <input type="checkbox"/> Fair 112 | <input type="checkbox"/> Telecomm. Control 165 |
| <input type="checkbox"/> Franke 74 | <input type="checkbox"/> Tri-Tek 175 |
| <input type="checkbox"/> Freck 104 | <input type="checkbox"/> Trumbull 147 |
| <input type="checkbox"/> Gateway 132 | <input type="checkbox"/> Tucker 114-117 |
| <input type="checkbox"/> GENAVE 99 | <input type="checkbox"/> Tufts 90 |
| <input type="checkbox"/> Godbout 184, 185 | <input type="checkbox"/> TWS Labs 107 |
| <input type="checkbox"/> Green Publishing 175 | <input type="checkbox"/> Vanguard 96, 153 |
| <input type="checkbox"/> Ham Radio Center 173 | <input type="checkbox"/> Vegas Radio 123 |
| <input type="checkbox"/> Hamtronics 176 | <input type="checkbox"/> Venus Scientific 47 |
| <input type="checkbox"/> Hasbrouck 151 | <input type="checkbox"/> VHF Eng. CIV |
| <input type="checkbox"/> Heath 38 | <input type="checkbox"/> WA2UGO 122 |
| <input type="checkbox"/> Henry 13 | <input type="checkbox"/> Westcom 135 |
| <input type="checkbox"/> Hickok 88 | <input type="checkbox"/> Wilson 51 |
| <input type="checkbox"/> Hy-Gain 174 | <input type="checkbox"/> Windjammer 164 |
| <input type="checkbox"/> ICOM 60, 61 | <input type="checkbox"/> World QSL 126 |
| <input type="checkbox"/> Jac Tenna 157 | <input type="checkbox"/> Yaesu CIII |

73 STUFF

- | | |
|------------------------|--------------------|
| Subscriptions 109 | Back Issues 150 |
| Gift Subscriptions 113 | Code Tapes 161 |
| Reps 120 | 73 Bookshop 169 |
| Radio Bookshop 139 | QSLs 171 |
| Binders 149 | Repeater Atlas 172 |

This 73 was acquired through:

- NEWSSTAND SUBSCRIPTION

*Reader service inquiries not solicited. Correspond directly to company.

Reader's Service **SEPTEMBER 1975**
73 Inc., Peterborough NH 03458

Please print or type.

Name _____ Call _____

Address _____

City _____

State _____ Zip _____

Coupon expires in 60 days . . .

PROPAGATION CHART

J.H. Nelson

Good (open) Poor (0)

Fair (□)

September - 1975

Sun	Mon	Tue	Wed	Thu	Fri	Sat
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

EASTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	7A	7	7	7	3	3	3	7	7	7	14	14	
ARGENTINA	14	7	7	7	7	7	14	14	14	14	14A	14A	
AUSTRALIA	14	7B	7B	7	7	7	7	7	7	7	14	14	
CANAL ZONE	14	7	7	7	7	7	7A	14	14	14	14A	14A	
ENGLAND	7	7	7	7	7	7	7	14	14	14	14	7	
HAWAII	14	7B	7B	7	7	7	7	7	14	14	14	14	
INDIA	7	7	7B	7B	7B	7B	14B	14	14	7	7	7	
JAPAN	14	7B	7B	7	7	3	7	7	7	7	7	14	
MEXICO	14	7	7	7	7	3A	7	14	14	14	14	14	
PHILIPPINES	14	7B	7B	7B	7B	3B	7	7	7	7A	7B	14	
PUERTO RICO	7	7	7	7	7	3A	7A	14	14	14	14	14	
SOUTH AFRICA	7	7	7	7	7B	7A	14	14	14A	14	14	14	
U. S. S. R.	7	3	3	3A	3A	7	7	14	14	14	7	7	
WEST COAST	14	7	7	7	7	3A	7	7A	14	14	14	14	

CENTRAL UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7	7	3	3	3	7	7	7A	14	14	
ARGENTINA	14	14	7	7	7	7	7	14	14	14	14A	14A	
AUSTRALIA	14	14	7B	7	7	7	7	7	7	7	14	14	
CANAL ZONE	14	7A	7	7	7	7	7	14	14	14	14A	14A	
ENGLAND	7	7	7	7	7	7	7	14	14	14	14	7	
HAWAII	14	14	7B	7	7	7	7	7	14	14	14	14	
INDIA	7	7	7B	7B	3B	3B	7B	7	7A	7A	7	7	
JAPAN	14	7A	7	7	3	3	3	7	7	7	7	14	
MEXICO	14	7	7	7	7	3	7	7	14	14	14	14	
PHILIPPINES	14	14	7B	7B	3B	3B	3B	7	7	7	7B	14	
PUERTO RICO	14	7	7	7	7	3	7A	14	14	14	14	14A	
SOUTH AFRICA	7	7	7	7	7B	7B	7A	14	14	14	14	14	
U. S. S. R.	7	3	3	3	3	3B	7	7	14	14	7	7	

WESTERN UNITED STATES TO:

	GMT:	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14	14	7	7	3	3	3	7	7	7	7	7	7A
ARGENTINA	14	14	7B	7	7	7	7B	14	14	14A	14A	14A	
AUSTRALIA	14A	14A	14	7B	7	7	7	7	7	7B	14	14	
CANAL ZONE	14	14	7	7	7	7	7	14	14	14	14	14A	
ENGLAND	7	7	7	7	7	3B	7	7	14	14	14B	7	
HAWAII	14A	14	14	7	7	7	7	7	14	14	14	14	
INDIA	7	14	7B	7B	3B	3B	3B	7	7	7	7	7	
JAPAN	14	14	7A	7	7	7	3A	7	7	7	7A	14	
MEXICO	14	14	7	7	7	7	7	7	14	14	14	14	
PHILIPPINES	14	14	14	7B	7B	7B	3B	7	7	7	7B	14	
PUERTO RICO	14	7	7	7	7	3A	7	14	14	14	14A	14	
SOUTH AFRICA	7	7	7	7	7B	3B	7B	7A	14	14	14	14	
U. S. S. R.	7	3B	3	3	3	3B	3B	7	7A	7A	7	7	
EAST COAST	14	7	7	7	7	3A	7	7A	14	14	14	14	

A = Next higher frequency may be useful also.

B = Difficult circuit this period.



Amateur radio's new look.

The new look in amateur radio is digital readout. And in the FR-101 digital receiver from Yaesu, you can check frequency with just a glance. If you're searching for a whisper of a QSL from across the world, you can be sure you're on the right wave-length every time.


The FR-101 digital receiver is accurate to an incredible 100 Hz. And there's a provision for up to four crystal-controlled channels in each of eight band segments. Added options allow up to twenty-one 500 KHz frequency ranges from 1.8 MHz all the way up to 148 MHz with reception of SSB, CW, AM, RTTY and FM modes.

Whether you're interested in two-way communications or listening in on the world, hear it all with the receiver that sports amateur radio's new look — the FR-101 digital receiver. Backed by a solid warranty, a strong dealer and service network — from the world's leading manufacturer of amateur radio gear, Yaesu. See the FR-101 digital receiver at your nearest Yaesu dealer or write for our catalog. Yaesu Musen USA Inc., 7625 E. Rosecrans Blvd., No. 29, Paramount, California 90723.




YAESU
The radio.

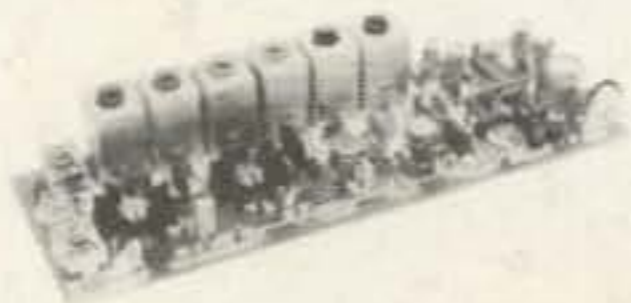The world's most complete line of VHF - FM kits and equipment



TX144B Kit . . .	exciter - 1 watt - 2 meters . . .	29.95
TX144B W/T . . .	factory wired	49.95
TX220B Kit . . .	exciter - 1 watt - 220 MHz	29.95
TX432B Kit . . .	exciter - NEW - 432 MHz	39.95

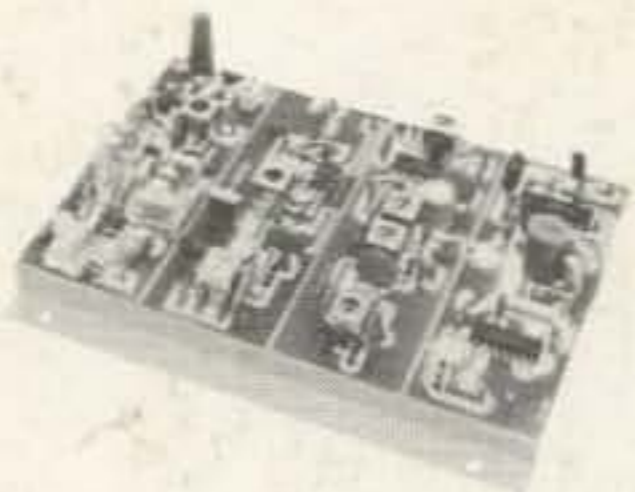

RX50C Kit . . .	30-60 MHz rcvr w/2 pole 10.7 xtal filter	59.95
RX144C Kit . . .	140-170 MHz rcvr w/2 pole 10.7 xtal filter	69.95
RX144C W/T . . .	factory wired / mounted	114.95
RX220C	210-240 MHz rcvr w/2 pole xtal 10.7 filter	69.95
RX432C Kit . . .	NEW - 432 MHz receiver	79.95
RXFL	70DB filter option for all RX-Recv (w/exch.)	9.50



HT144B Kit . . .	2 meter - 2w - 4 channel - hand held xcvr	129.95
------------------	--	--------



PA2501H Kit . . .	similar to above - 25w	59.95
PA2501H W/T . . .	factory wired	74.95
PA4010H Kit . . .	10w in - 40w out - relay switching	59.95
PA4010H W/T . . .	factory wired	74.95
PA144/15 Kit . . .	similar to PA1501H less case, connectors & switching	39.95
PA144/25 Kit . . .	similar to above - 25w	49.95
PA220/15 Kit . . .	similar to PA144/15 for 220 MHz	39.95
PA432/10 Kit . . .	NEW - similar to PA144/15 ex- cept 10w and 432 MHz	39.95
PA140/10	NEW - 10w in - 140w out 2 meter amp - factory wired . . .	179.95
PA140/30	NEW - 30w in - 140w out 2 meter amp - factory wired . . .	159.95



PS3 Kit	power supply regulator card	8.95
PS12C Kit	12 amp - 12 volt regulated power supply w/case	69.95
PS12C W/T	factory wired	85.95
PS24C Kit	24 amp - 12 volt regulated power supply w/case	99.95
PS24C W/T	factory wired	114.95



RPT144 Kit	2 meter - 15w - complete	364.95
RPT220 Kit	220 MHz - 15w - complete	364.95
RPT432 Kit	NEW - 10 watt - 432 MHz repeater	399.95
RPT144	NEW - 15 watt 2 meter repeater - factory wired	595.95
RPT220	NEW - 15 watt - 220 MHz repeater - factory wired	595.95
RPT432	NEW - 10 watt - 432 MHz repeater - factory wired	649.95

OTHER PRODUCTS BY VHF ENGINEERING

CD1 Kit	10 channel receive xtal deck w/diode switching	\$ 6.95
CD2 Kit	10 channel xmit deck w/switch and trimmers	14.95
COR2 Kit	complete COR with 3 second and 3 minute timers	19.95
CWID-1 Kit	NEW - code identifier - 160 bits, field programmable diode matrix . . .	39.95
SC2 Kit	10 channel auto-scan adapter for RX	19.95
Crystals	we stock most repeater & simplex pairs for 146.0-147.0	5.00
*DPLX-144	2 meter, 6 cavity, close spaced duplexer - tuned to frequency	399.95
*DPLX-220	220 MHz, 6 cavity duplexer tuned to frequency	399.95

SHIPPING INFORMATION: All shipments are F.O.B. Binghamton, N.Y. 13902. Shipments will be made by the most convenient method. Please include sufficient funds to cover shipping and handling. Figure shipping charges on a minimum weight of 2 pounds per unit with the exception of the following: PS 12C - 13 lbs., PS 24C - 25 lbs., Repeaters - 25 lbs.



320 Water St. • PO Box 1921-S • BINGHAMTON, NY 13902 • 607-723-9574
DIVISION OF BROWNIAN ELECTRONICS CORP.