

75 cents

hr

focus
on
communications
technology ...

ham **radio**

magazine

MARCH, 1971

a
PHASE-LOCKED

**local
oscillator**

this month

- 6-meter transverter 12
- RTTY signal generator 23
- fm repeaters 38
- rating tubes for linear amplifiers 50

STATE OF THE WATT...



...a la *ALPHA SEVENTY*

The *ALPHA SEVENTY* high power linear amplifier incorporates components heretofore available only in equipment designed for military or industrial applications. The result — a new standard of performance and convenience.

- EXTRA HEAVY DUTY TRANSFORMER WITH TAPE-WOUND CORE OF GRAIN-ORIENTED SILICON STEEL is 60% smaller and lighter than conventional laminated units.
- VACUUM VARIABLE CAPACITOR combines low minimum and high maximum capacitance, very small size, and excellent flashover resistance.
- VACUUM T/R RELAY is extremely fast, quiet and compact. It closes in milliseconds with a barely audible "tick," handles maximum power with ease.
- CERAMIC-METAL POWER TUBES are rugged and compact. The revolutionary vapor-cooled *ALPHA SEVENTY* delivers uncompromising maximum legal power in all modes. It runs whisper-quiet, thanks to the Eimac 3CV1500A7 shown above and ETO's integral recirculating heat exchanger system. The *ALPHA SEVENTY* is also available with a 3CX1000A7 tube in a thermostat-controlled air cooling system. The two models are otherwise electrically and mechanically identical.

The *ALPHA SEVENTY* ...

Air-cooled model PA70-A \$1595

Vapor cooled model PA70-V \$1775




EHRHORN TECHNOLOGICAL OPERATIONS, INC.

BROOKSVILLE, FLORIDA 33512

(904) 796-8400

IF YOU'VE
EVER
USED
A
REPEATER,

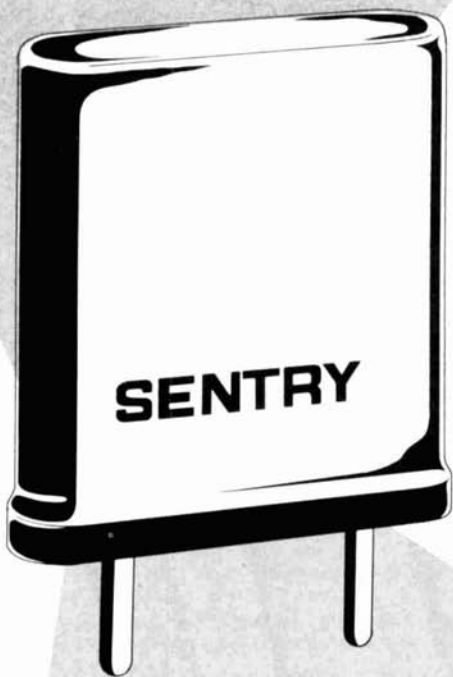

YOU'VE USED A
SENTRY CRYSTAL

If you haven't
already received
a copy of our **NEW**
1971 Catalog of Precision
Quartz Crystals & Electronics
for the Communications Industry,
SEND FOR YOUR COPY TODAY!

Somewhere along the line, in virtually every ham repeater in the world, you'll find a couple of Sentry crystals.

Repeater owners and FM "old-timers" don't take chances with frequency—they can't afford to. A lot of repeater users depend on a receiver to be on frequency, rock stable...in the dead of winter or the middle of July. The repeater crowd took a tip from the commercial "pros" a long time ago—and went the Sentry Route.

That's one of the reasons you can depend on your local repeater to be there (precisely there) when you're ready to use it. FM'ers use the repeater output as a frequency standard. And for accuracy, crystals by Sentry are THE standard.

**IF YOU WANT THE BEST,
SPECIFY SENTRY CRYSTALS.**

*Do the World's Best
Who don't Repeaters!*



SENTRY MANUFACTURING COMPANY
Crystal Park, Chickasha, Oklahoma 73018

PHONE: (405) 224-6780

TWX-910-830-6425

Versatility plus!... in a 2 Meter FM Transceiver

... IN THE FIELD
IN THE CAR
IN THE HOME ...



DRAKE MODEL TR-22

\$199⁹⁵ Amateur Net*

The TR-22 is a 2-meter VHF-FM completely transistorized, compact, portable transceiver with capacity for six channels. It can be used over the shoulder, mobile, or in your home. Has a built-in telescoping antenna, and SO-239 connector provided for external antenna. May be used barefoot or with accessory two-way amplifier. Operates on external 12 VDC or on internal rechargeable nickel-cadmium batteries. Has built-in 120 VAC 50-60 Hz battery charger.

SPECIFICATIONS

GENERAL • Frequency Coverage: 144-148 MHz • 6 channels, 3 supplied: (1) Rcv: 146.94 MHz, Xmit: 146.34 MHz; (2) Simplex: 146.94 MHz; (3) Rcv: 146.76 MHz, Xmit: 146.34 MHz • Frequency modulation • Push-to-talk Xmit Control • DC Power Drain: Rcv: 45 mA, Xmit: 450 mA • Power Source: 12 VDC \pm 20%; 120 VAC 50-60 Hz (for recharging nickel cadmium batteries only.) • Size: 5 $\frac{3}{8}$ " x 2 $\frac{3}{16}$ " x 7 $\frac{1}{8}$ ", Wt: 3 $\frac{3}{4}$ lbs.

RECEIVER • Completely transistorized crystal controlled double conversion superheterodyne circuit. • 1st IF 10.7 MHz • 2nd IF 455 KHz • Antenna Input Impedance: 50 ohms • Sensitivity: 1 microvolt or less for 20 dB S+N/N ratio • Audio Output: 0.7 watt at 10% or less distortion • Built-in speaker.

TRANSMITTER • RF Output Power over 1 watt • Frequency Deviation adjustable to 15 kHz maximum; factory set to 5 kHz.

*PRICE OF TR-22 INCLUDES: Dynamic Microphone, Over-the-Shoulder Carrying Case, 120 VAC and 12 VDC Power Cords, Speaker/Headphone Plug, and 10 Nickel-Cadmium Batteries.

AT YOUR DEALER'S!

R. L. DRAKE COMPANY



AA-22

Model AA-22 Accessory Amplifier \$149.95. Improves receiver sensitivity and rejection of undesired signals. Provides at least 25 watts output with $\frac{1}{2}$ to 3 watts drive. Fully automatic.

Model MNK-22 Mobile Mount for TR-22 \$6.95



540 Richard Street
Miamisburg, Ohio 45342

March, 1971
volume 4, number 3

staff

James R. Fisk, W1DTY
editor

Nicholas D. Skeer, K1PSR
vhf editor
J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Jean Frey
art director
Wayne T. Pierce, K3SUK
cover

T. H. Tenney, Jr. W1NLB
publisher

John B. Morgan, K1RA
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology Inc.
Greenville, New Hampshire 03048

Subscription rates, world wide:
one year, \$6.00, three years, \$12.00.
Second class postage
paid at Greenville, N. H. 03048
and at additional mailing offices

Foreign subscription agents:
United Kingdom:
Radio Society of Great Britain,
35 Doughty Street, London WC1, England.

All European countries:
Eskil Persson, SM5CJP, Frotunagränd 1,
19400 Upplands Vasby, Sweden.

African continent:
Holland Radio, 143 Greenway,
Greenside, Johannesburg,
Republic of South Africa

Copyright 1970 by
Communications Technology, Inc.
Title registered at U. S. Patent Office.
Printed by Wellesley Press, Inc.
Wellesley, Massachusetts 02181, U.S.A.

ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind,
221 Rock Hill Road, Bala Cynwyd,
Pennsylvania 19440

Microfilm copies of current
and back issues are available
from University Microfilms,
Ann Arbor, Michigan 48103.

Postmaster: Please send form 3579 to
ham radio magazine, Greenville,
New Hampshire
03048



ham
radio
magazine

contents

6 phase-locked local oscillator

J. A. Koehler, VE5FP

12 six-meter transverter

Louis E. Savoie, K1RAK

23 RTTY signal generator

Victor G. Shinsel, W7ZTC

30 tabulated characteristics of vacuum-tube and transistor amplifiers

Carl C. Drumeller, W5JJ

38 plain talk about repeater problems

Vern Epp, VE7ABK

44 audio-oscillator module

John A. Houser, WB2GQY

50 rating tubes for linear amplifiers

William I. Orr, W6SAI

Robert I. Sutherland, W6UOV

56 sweep-response curves for low-frequency i-f's

Larry Allen

4 a second look

94 advertisers index


85 flea market

64 ham notebook

72 new products

94 reader service

56 repair bench

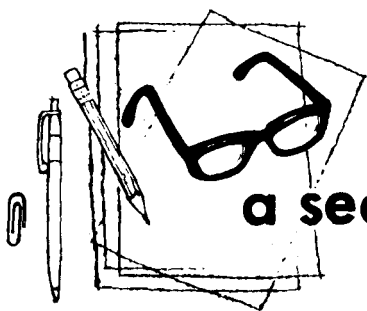

a second look

by jim
fisk

Within the next 20 years the world's power needs may be supplied by huge solar power stations in synchronous orbit around the earth. Diminishing fossil-fuel reserves, doubts about the practicality of nuclear power and problems of air and water pollution have led scientists to develop a plan for a system of orbiting solar-power stations.

The satellites would collect solar energy with huge arrays of solar cells, and convert the resulting dc into microwave energy for transmission to the earth. On the earth large rectifier-antennas (rectennas) would convert the received microwave energy back to direct current for distribution to the user.

Each power satellite in the system would consist of a solar array about five-miles square, a parabolic transmitting antenna 1.5 miles in diameter and 10,000 microwave transmitting tubes, with an output of 1000 kW each. The transmitting antenna and solar array would be connected with a super-conducting cable 2 miles long. Total power of the proposed system is 100-million kilowatts.

A large rectenna on the earth, several miles square, would convert the received microwave energy back into dc power for distribution. Each element of the large receiving array would consist of a half-wave dipole with its own four-diode bridge. Since the individual dipole-diode combinations (dipodes) are independent, the overall beam pattern is essentially

nondirectional, so it eliminates the necessity for precise aiming at the satellite.

An operating frequency of 3000 MHz was chosen to minimize the effects of atmospheric attenuation. Higher frequencies would be attenuated by the troposphere while lower frequencies suffer from ionospheric attenuation. In addition, in complete cloud cover and moderate rainfall attenuation is lowest around 3000 MHz.

Many people, when first hearing of this plan, imagine that the microwave beam would virtually be a death ray that could cause great damage. Actually, with the proposed 100-million kW system, power density within the beam would only be 10 mW per square centimeter near the earth. This is the official Air Force maximum exposure level, and is a conservative limit with a built-in buffer factor, so it should not be hazardous for living things.

Although 20 years is a reasonable estimate for getting the satellite solar power system into operation, some scientists predict that the system could be working in 10 years if the government were willing to initiate a crash program similar to the nation's moon-landing program. In any event, this is the kind of planning we need to solve the increased demands for electric power in the future.

Jim Fisk, W1DTY
editor



New FM for '71 Standard's SR-C826M

**professional quality, solid state, two-way radio,
designed and sold exclusively for amateur use
in the United States and Canada.**

Standard Communications Corp., the world's largest manufacturer of marine V.H.F. equipment, has just developed a new industrial quality, high performance 2-meter unit. This rugged, compact transceiver is available only in the U.S. and Canada thru an authorized Standard dealer. The "826" is so compact that it makes mobile installation practical in almost any vehicle or aircraft, it becomes fully portable with the addition of Standard's battery pack.

GENERAL

Freq. Range — 143 to 149 MHz, 2 MHz spread
Supply voltage — 11 to 16 VDC. Negative Ground 13.8VDC nominal
Current Consumption — .15 amp receive standby. 2.4 amp transmit
Number of channels — 12-
Supplied with 4 channels

- 1) 146.94 Simplex
- 2) 146.34/94
- 3) 146.76 Simplex
- 4) 146.34/76

Microphone — Dynamic
Dimensions — 6 $\frac{7}{8}$ " w x 2 $\frac{1}{2}$ " h x 9 $\frac{7}{8}$ " d

Weight — 4 $\frac{1}{2}$ lbs. max.
Frequency stability—.001%
(-10 to +60°C)

TRANSMITTER

RF power output — .8 or 10 watts
Output impedance — 50 ohms nominal
Deviation — Internally adjustable to ± 10 kHz min. factory set to ± 7 kHz
Spurious and harmonic attenuation — 50dB below the carrier power level
Type of modulator — Phase
RECEIVER
Sensitivity — .4 or less microvolts for 20 dB quieting

Squelch sensitivity —
Threshold — .2 microvolts or less

2 MOSFET RF Amplifiers
1 MOSFET Mixer

Deviation acceptance —
Up to ± 15 kHz deviation
Spurious and image attenuation — 65 dB below the desired signal threshold sensitivity

Adjacent channel selectivity (30 kHz channels) — 60 dB attenuation of adjacent channel


Type of receiver —
Dual conversion superheterodyne
Audio output — 5 watts
For external speaker

\$339.95 (complete as shown with microphone, built-in speaker and external alternator whine filter.)



**STANDARD
COMMUNICATIONS CORP.**

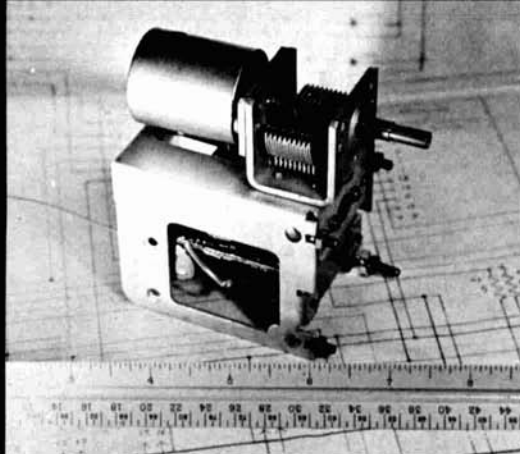World's largest manufacturer of marine V.H.F. equipment
P. O. Box 325, Wilmington,
Calif. 90744 (213) 775-6284



phase-locked local oscillator

A practical solid-state
phase-locked
local oscillator
that covers the range
from 14 to 50 MHz

J. A. Koehler, VE5FP, 2 Sullivan Street, Saskatoon, Saskatchewan, Canada

This oscillator was built to satisfy the requirement for the first local oscillator in a receiver. The design called for a number of stable frequencies separated by exactly 1 MHz over as wide a frequency range as possible — at least 30 MHz. One obvious solution would have been to use separate crystals for each frequency. However, this was not economical because of the large number of frequencies. An alternative would have been to build a frequency synthesizer using somewhat fewer crystals (twelve in this case), and produce the required outputs by mixing. I have gone this route before and it is extremely difficult to get all the frequencies precisely where required. The problem of suppressing unwanted mixing products is also formidable. For these reasons I decided to build a variable-frequency oscillator which covered the desired frequency range and which could be phase locked to the harmonics of a 1.0-MHz crystal-controlled oscillator.

Although phase-lock systems are not uncommon in commercial equipment, there has not been a great deal written about them in the ham literature; probably because a rigorous analysis of the process is mathematically complex. However, it is relatively easy to understand their operation and to build systems which work.

The phase-lock system is basically a servo system where the difference between the variable-oscillator frequency and a *reference* frequency produces an

error signal which is used to alter the frequency of the variable oscillator. The process is similar to automatic frequency control (afc) except for one major difference which makes it far superior.

phase-lock operation

A conventional afc system is shown in block form in fig. 1. The discriminator produces an output which is proportional to the difference between the frequency of the voltage controlled oscillator (vco) and a reference frequency (the center frequency of the discriminator). The system is designed so that the overall feedback is negative. For example, if the discriminator output is zero volts for the desired frequency, positive for higher frequencies, and negative for lower frequencies, and if the vco moved up in frequency for positive control voltages and down for negative control voltages, then the amplifier must invert as well as provide gain. Then, if the vco drifted up in frequency for some reason, the discriminator output would become positive; the amplifier would amplify this voltage and would make it negative. This negative voltage, applied to the vco, would cause its frequency to decrease, thus counteracting the drift. The problem

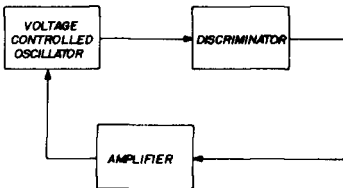


fig. 1. Basic parts of the automatic frequency control circuit.

with an afc system is that frequency drift cannot be compensated for exactly; there is *always* some frequency error.

This can be proved by the following argument. Suppose the vco were originally set exactly at the desired frequency. And furthermore, at that frequency, the discriminator output were exactly zero volts. Therefore, the control voltage to the vco would also be exactly zero volts.

Now suppose that the vco drifted slightly upward in frequency. To bring it back to the original frequency requires a negative control voltage. This control voltage could only be produced if the discriminator output were somewhat more positive than zero; i. e., the vco frequency could not be exactly its original value.

This requirement for an error signal is characteristic of any servo system. The error can be reduced by tightening the control loop; in the case of afc this is done by increasing the gain of the amplifier so the control output would be very sensitive to small frequency changes.

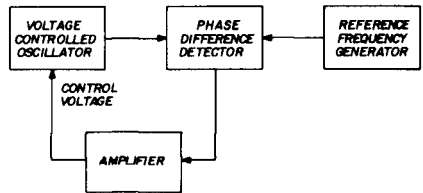


fig. 2. Block diagram of the basic phase-lock system.

However, the frequency error cannot be eliminated entirely. In practice, the vco would be designed to be very stable so that frequency drift would be small. The afc system would then reduce drift even further.

A phase-locked system (pls) can produce an output frequency which is exactly the same as the reference frequency. This is done by deriving the error signal not from a frequency difference but from a phase difference. The block diagram of a pls is shown in fig. 2. Note that the afc discriminator has been replaced by a phase-difference detector. A reference frequency oscillator is also required, the discriminator performed this function in the afc system.

Fig. 3 shows a hypothetical time sequence of two input voltages (one at the reference frequency and the other at the vco frequency) and the output of the phase-difference detector. Initially the two voltages are in phase (the phase difference was zero) so the output of the phase detector is zero. However, because

the two frequencies are different, the phase difference increases steadily with time until it reaches 360° . At that point the output of the phase difference drops back to zero since 360° phase difference is equal to zero phase difference.

Now suppose the output of the phase detector were connected to the vco control line. The ramp voltage would sweep the vco frequency. For the system to work properly, the control-voltage would sweep the vco frequency in a direction so as to decrease the frequency difference. Then, as the vco frequency approached the reference frequency, the rate of change of phase difference would decrease, and the vco would sweep more slowly. When the vco exactly reached the reference frequency, the phase difference between the two would be constant in time, so the vco frequency sweep would stop; the vco frequency would be phase-locked to the reference frequency.

The error signal in this loop is due to the phase difference between the vco and the reference frequency while they are locked together. This phase difference can be made arbitrarily small, just as the frequency difference in an afc can be reduced, but it cannot be entirely eliminated. However, for purposes of frequency control it is immaterial because the frequency error will be zero regardless of the phase error. If the vco frequency tended to drift, the phase detector would produce an output voltage which would

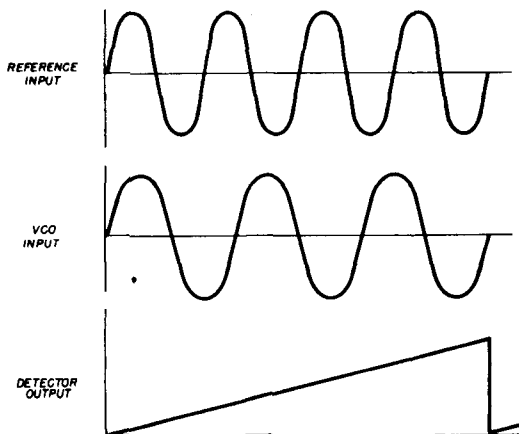


fig. 3. Waveforms in the phase-difference detector.

keep the vco locked to the reference frequency. After the drift, the phase difference between the two oscillators would, of course, be different from its original value, but the two frequencies would still be identical.

In practice, it is difficult to build a phase-difference detector with characteristics exactly as outlined above, and the devices used are called phase-sensitive detectors. The output of phase-sensitive detectors are usually only approximately

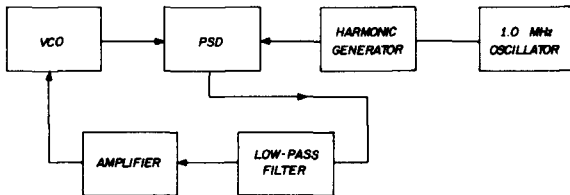


fig. 4. Proposed phase-locked oscillator for receiver local oscillator.

proportional to phase difference, and then only over a restricted range of phase difference. Also, there will also be a low-pass filter of some sort following the detector.

The lock-in range of the system, the range of vco frequency variation over which it can be locked onto the reference frequency, depends in a complicated way upon total loop gain and low-pass filter band-width. If you are interested in pursuing the topic, there are a surprising number of papers in technical journals on the subject. One of the more readable explanations I have seen appeared in the *Proceedings of the IRE*¹.

practical phase-locked oscillator

For my requirements, the vco had to have as wide tuning range as possible. Fair Radio has been selling a surplus tuning unit with a ganged capacitor and slug-tuned coil that covers the frequency range from 14 to 50 MHz, and I bought one of these.* I wanted to use this mechanism as the basis for a variable oscillator for this frequency range and

*\$1.25 from the Fair Radio Sales Company, Post Office Box 1105, Lima, Ohio 45802. Order RT-45 tuner. Shipping weight: 1 pound.

phase lock it to the harmonics of a 1-MHz oscillator.

The system is shown in **fig. 4**. The surplus tuning unit was made into a Hartley oscillator using an fet. With no padding capacitor, the frequency range extended from about 15 to 80 MHz — this was more than adequate, and a padding capacitor was added to reduce the range somewhat, and to lower the low-frequency limit to a bit lower than 14 MHz. Frequency stability was quite

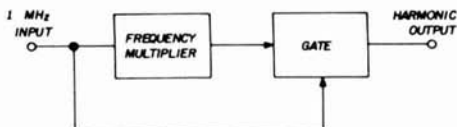


fig. 5. Harmonic generator.

good. Normally the oscillator should be as stable as possible so that it does not readily drift out of the lock-in range. A varicap across the tank circuit was to be used as the frequency controlling element.


The 1-MHz crystal-controlled oscillator also used an fet. The harmonic generator was more complicated than the type usually seen in the amateur magazines. A phase-lock system requires that some power must be supplied to the reference frequency input to the phase detector at all frequencies where phase lock is required. To lock at 50 MHz, for example, requires appreciable amplitude of the 50th harmonic of the 1-MHz oscillator. Harmonics were originally generated by squaring the 1-MHz waveform and applying it to a diode — and later, other non-linear devices.

However, after a few experiments, it was apparent that the amplitudes of the higher harmonics generated in this way were too small. Step-recovery diodes probably would have been excellent; however, I didn't have any, so I built the harmonic generator outlined in **fig. 5**.

The output of the multiplier was keyed on and off at a 1-MHz rate by the gate. Assume that the frequency multiplication factor were ten and that it was

somewhat non-linear; the output of the multiplier would then contain energy not only at 10 MHz, but also its harmonics, 20, 30, 40 MHz, etc. The gate can be thought of as a modulator which overmodulates. Consider for example the signal from the multiplier at 10 MHz. This would be modulated at a 1-MHz rate so the output of the gate would contain the carrier at 10 MHz as well as sidebands 1 MHz to each side of it (9 MHz and 11 MHz).

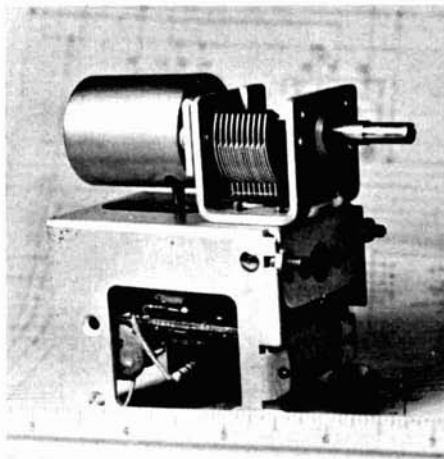Because of overmodulation, there would also be other sidebands 2, 3, 4, and 5 MHz on either side of 10 MHz. The output of the gate would contain all the carriers (spaced at 10 MHz intervals) plus all the sidebands (spaced at 1 MHz



Miniature phase-locked local oscillator.


intervals) between the carriers. This type of harmonic generator can be very efficient. The simple version I built produced sufficiently strong harmonics up to 70 or 80 MHz.

Since any mixer is, in fact, a phase-sensitive detector of sorts, my phase detector was a simple diode double-balanced mixer. I didn't have any hot-carrier diodes, so four 1N270s were selected by matching them on a curve tracer. The low-pass filter was an RC type, and the amplifier was a μ A741 integrated circuit.

Unfortunately, when the system was built, it would not work properly over the entire range of the vco. Despite careful diode matching, the double-balanced mixer was not well enough

been to provide some amplitude limiting of the vco output. However, the system was beginning to get too complicated, and the whole approach was abandoned.

After considerable experimentation,

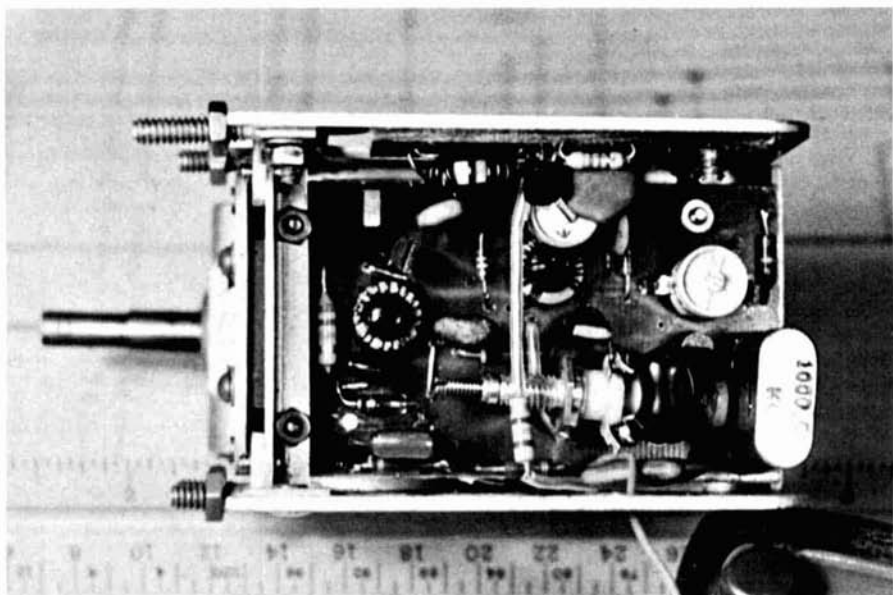

Complete phase-locked oscillator circuit is built on small board that is mounted in the surplus LC tuner.

balanced. The output of the mixer must be coupled directly to the amplifier input. Ideally, the output of the mixer should be at zero volts dc when the two inputs are not harmonically related. However, due to diode unbalance, there will always be a small dc component as well as the desired signal which offsets the amplifier input.

The problem was that the offset depended on vco amplitude. The system could, for example, be adjusted to work near 14 MHz by compensating for dc offset. However, when the vco was tuned to higher frequencies, the output amplitude changed, causing the dc offset to change and saturate the amplifier. If the gain of the amplifier were reduced so that it did not saturate anywhere over the vco range, then the lock-in range became unacceptably small at the higher frequencies. A possible solution might have


the final solution required very few components. The oscillator fet itself was used as a mixer by coupling the harmonic generator output into the oscillator tank circuit with a varicap. The signal at the gate of the fet contained the oscillation frequency as well as all the 1-MHz harmonics. The instantaneous voltage at the gate depended on the phase difference between the oscillation frequency and the harmonics. Because the varicap was connected to the gate, the oscillation frequency therefore depended on this phase difference — thus satisfying the requirement of a phase-locked loop.

This system worked very nicely when I used a 1N914, a silicon planar switching diode, for the varicap. Normal varicaps with capacitance of 10 pF at 4 volts resulted in lock-in ranges which were too large, and which overlapped. With the 1N914, the lock-in range was about 100

kHz at 14 MHz and somewhat lower at the higher frequencies.

The final circuit is shown in fig. 6. The oscillator transistor was mounted on small terminal strips next to the coil. The

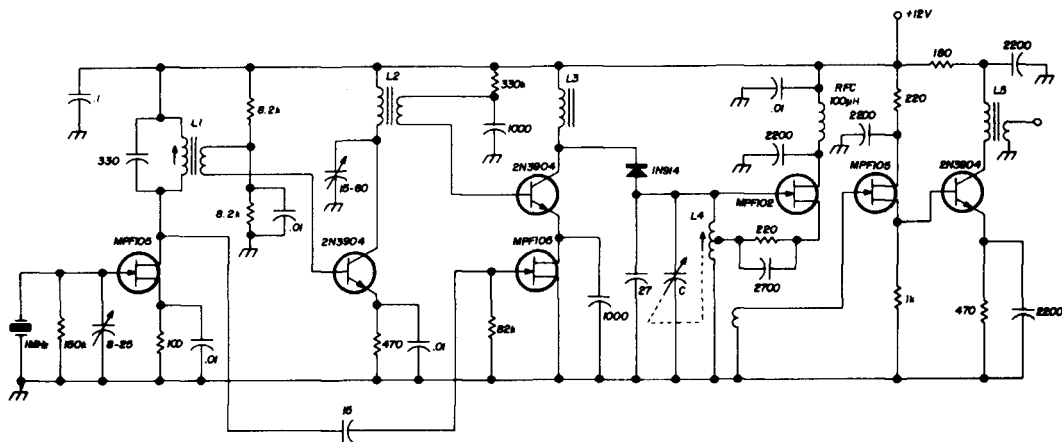factory, and it is anticipated that when the system is incorporated into the receiver, it will not be necessary because considerable wideband noise will be generated when the system is not locked.



C1, L4 Part of surplus tuner, Fair Radio RT-45 (see text)

L1 100 — 125 μ H (J. W. Miller 42A104CB1) with 20-turn link

L2 25 turns no. 28 on Phillips 2P65347 toroid core, 7-turn link

L3 18 turns no. 28 on Phillips 2P65347 toroid

L5 15 turns no. 28 on Phillips 2P65347 toroid, 4-turn link

Phillips toroids are 0.375 inch in diameter. Ferroxcube 266CT125 toroids made of 4C4 material are identical to the Phillips units; Indiana General type CF102-Q1 are virtually the same.

fig. 6. Circuit of the practical phase-locked oscillator that tunes from 14 to 50 MHz.

1-MHz oscillator and harmonic generator was built on a printed-circuit board which fit nicely inside the framework of the surplus capacitor-coil framework as shown in the photograph. The smaller board on the side of the frame is the output buffer amplifier.

The frequency multiple in the harmonic generator need not be ten but can be any multiple. In the final version, it was sixteen.

The only remaining detail was to determine whether the vco was free running or whether it was phase locked at any point on the dial. This was done by connecting a diode detector and audio amplifier in parallel with the output. As the vco was tuned through its range, it was possible to hear it snap in and out of lock.

This method is not particularly satis-

As an interesting side effect I found that it was possible to lock the vco on to harmonically related frequencies other than the 1-MHz points. For example, the vco could be locked to exactly 14.3333 MHz because the mixer detected the phase difference between the third harmonic of the vco at 43 MHz and the 43rd harmonic of the 1-MHz oscillator with sufficient amplitude to cause locking. However, the lock-in range for these frequencies is quite small and there is no difficulty in determining whether or not the output frequency was on one of these points or on the desired frequency.

reference

1. H. T. McAleer, "A New Look at the Phase-Lock Oscillator," *Proceedings of the IRE*, June, 1959, p. 1137.

ham radio



TR-50 customized six-meter transverter

A compact 300-watt
transverter
featuring
high efficiency
and a low-noise
mosfet front end

Louis E. Savoie, K1RAK, 29 Hillsdale Road, Holbrook, Massachusetts 02343

The 50-MHz transverter described in this article was built to satisfy a specific purpose: to provide a medium power, tabletop transverter which was compatible, both electronically and in styling, to the Drake TR-3. A secondary object was cost. The result is a 300-watt ssb transverter that uses a low-noise mosfet receiving converter, and includes built-in solid-state power supplies. Efficiency of the output stage is 64%.

cabinet

My first order of business was to select a suitable enclosure for the unit. The Drake TR-6 cabinet matches the TR-3 in styling and offers the advantage of not having additional cutouts as do other cabinets of the TR-4 line. Cabinet measurements indicated a 10-1/2 x 13-1/4-inch chassis and 10-1/2 x 5-1/4-inch front panel were optimum. Considering the weight of the power-supply components, 0.047 steel was chosen for the chassis to provide strength and rigidity.


The chassis and front panel were purchased from a local metal shop for \$9. This included bending and corner welding. The chassis, front panel and cabinet were then mated, and the chassis drilled

for the captive hardware I wanted to use to hold the system together. The captive nuts should be riveted in place to provide a smooth, flush outside surface.

circuit

In the next phase of the design I considered both the mechanical and electrical requirements of the transverter. I have found it useful to first decide upon the circuit and power-tube requirements, and then search the literature for com-

A recent article by K2ISP¹ described printed-circuit transmitting mixers for both six and two meters. Local experience with the two-meter unit suggested similar possibilities for the six-meter mixer. K2ISP's mixer features a conventional 6U8 buffer/amplifier that feeds a push-pull 5763 mixer/driver stage; the low-frequency ssb signal is injected at the cathodes of the 5763s. Although the original circuit was designed for a 43-MHz local oscillator and 7-MHz ssb, it seemed

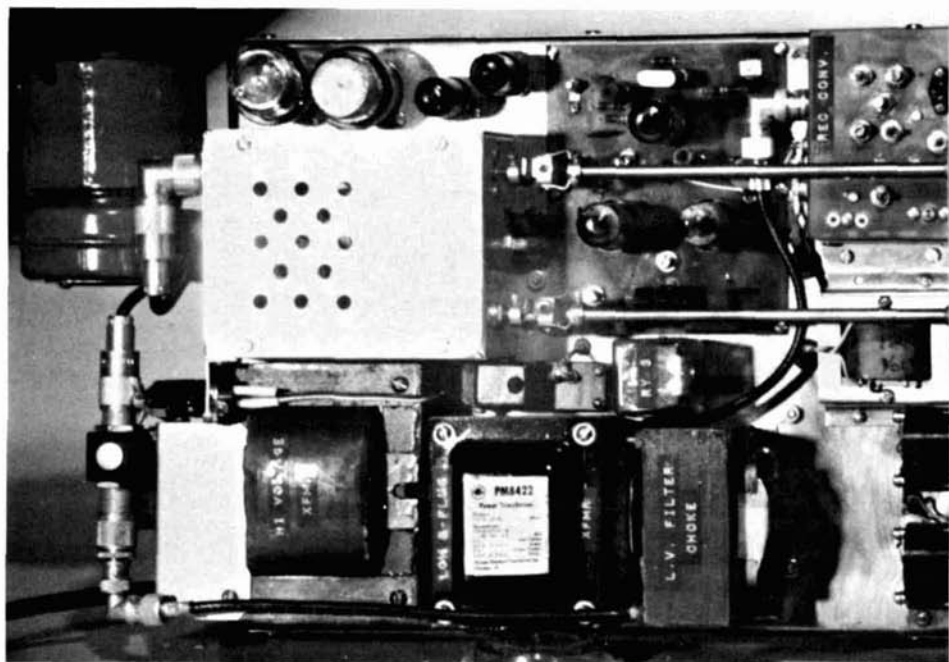


Top view of the TR-50. The coaxial cable on the bottom goes to the receiving converter.

mercial transformers that will do the best possible job. Since I wanted the design to be as close to the state-of-the-art as possible, I decided on printed-circuit construction; solid-state would be used where feasible.

reasonably easy to convert to the more popular 36-MHz local oscillator, 14-MHz ssb system (fig. 1).

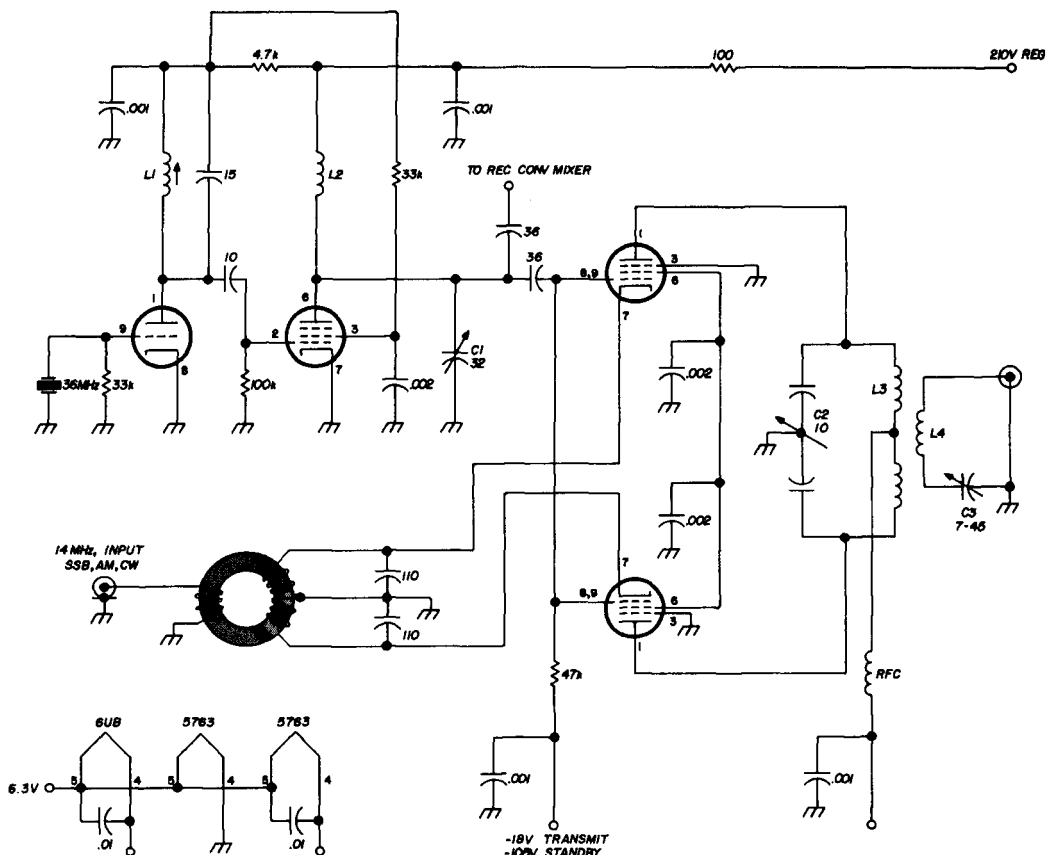The printed-circuit board used in the K2ISP transverter, shown in fig. 3, can be used in the TR-50 without modifica-



C1 32-pF variable (E. F. Johnson 160-110)

C2 10-pF butterfly (E. F. Johnson 160-211)

C3 7 — 45 pF ceramic trimmer

L1 12 turns no. 24, close wound on 1/4" slug-tuned form

L2 12 turns no. 20, air wound, 1/4" diameter, 1/2" long

fig. 1. Six-meter transmitting mixer uses 14-MHz ssb input.

L3, L4 7 turns no. 20, air wound, 1/2" diameter, 9/32" long

L5 4 turns no. 20, air wound, 1/2" diameter, 5/32" long

RFC Ohmite Z-50

Xtal 36-MHz third overtone

tion — although a few component values must be changed to accommodate the new mixing frequencies. The oscillator and buffer coils were re-designed to cover 36 MHz, and the input toroid was wound for 14-MHz injection.

After all the components were mounted on the printed-circuit board, the unit was tested on the bench. Using a TR-3 for injection, through a 10-dB pad,

the transmitting mixer worked well into a 50-ohm load. A Heath Monitorscope indicated good quality ssb. Power output was calculated to be slightly more than 1.5 watts — more than enough to drive a

power amplifier

The available chassis space dictated a power tube that would combine ef-

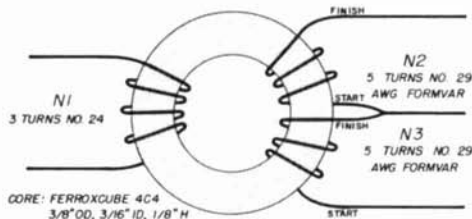


Fig. 2. Toroid transformer for 14-MHz input. Core is Ferroxcube 4C4 3/8" OD, 3/16" ID, 1/8" thick. Winding N1 is 3 turns no. 24 enameled; Winding N2 and N3 are each 5 turns no. 29 enameled. Windings N2 and N3 must be wound in same direction. Primary and Secondary winding should use full circumference of the core.

ficiency with small size. The 4X150/4CX250B power tetrodes offer a power-output-to-size ratio that seemed ideal for this application. These tubes require forced-air cooling, but commercial squirrel-cage blowers are available in small sizes and at low cost. A schematic of the six-meter power amplifier is

shown in **fig. 4.**

Rough sketches indicated that the pi-network coil, variable capacitors, plate choke and bypasses would easily fit into a 3x4x5-inch aluminum utility box. This made a suitable rf compartment which would fit into the vertical space between the cabinet and the top of the chassis.

The grid compartment box was made from 0.047-inch steel and mounted upside down under the chassis. By mounting this box against the back edge of the chassis, and including a rubber-gasketed cover, a plenum chamber was created. Cooling air is provided by a Dayton 21-cfm blower mounted to the chassis and sealed with rubber gaskets. A 1½-inch diameter hole through the back of the chassis and the grid compartment provides for air flow.


All power and filament connections are fed to the grid compartment through, .001 μF feedthrough capacitors. Coupling

fig. 3. Full-size printed-circuit board for the transmitting mixer.



from the mixer output link is fed to the 4CX250B grid through a ceramic feed-through connector. I believe this setup provides the input-output isolation which resulted in an exceptionally stable power

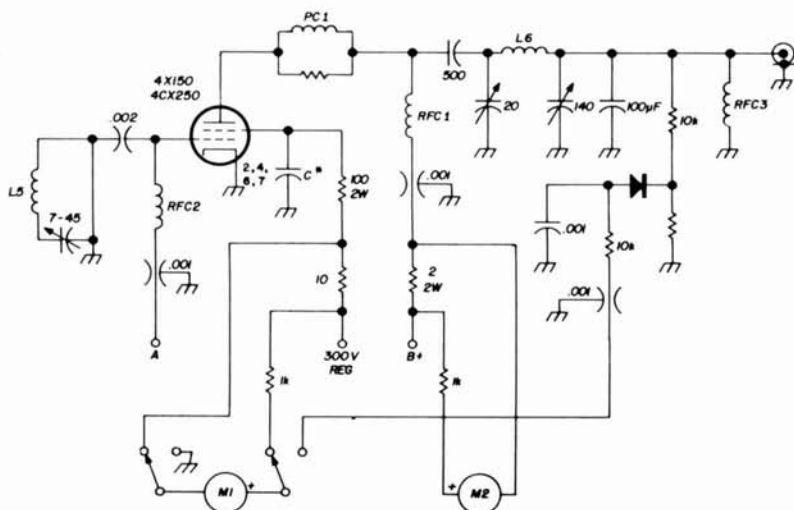provided power for the miniature coaxial relay and 15-volt zener-regulated receiving-converter power supply.* Power supply circuits are shown in figs. 9, 10 and 11.



C1 Eimac SK600 socket bypass capacitor

L5 Link on transverter board (L4 in fig. 1)

L6, 5 turns 1/8" copper tubing, 1" diameter


PC1 3 turns no. 14 around 47-ohm, 2-watt resistor

RFC1,2,3 Ohmite Z-50

fig. 4. 4X150 power amplifier stage operates at 64% efficiency and requires no neutralization.

amplifier that needs no neutralization.

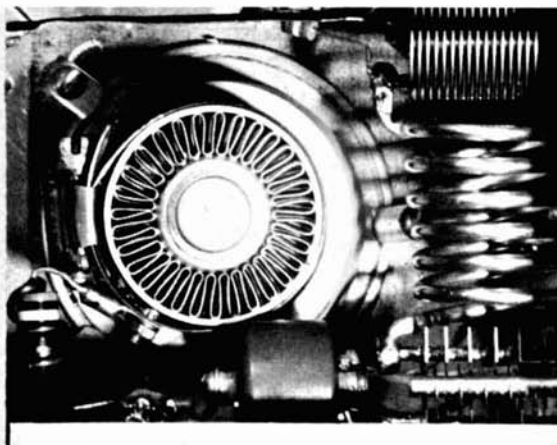I used low-cost surplus transformers and chokes for the various power supplies, although suitable commercial transformers are available. Separate transformers were fused for the high- and low-voltage supplies. A Stancor PS8415 was used for the bias supply, and a small 24-volt electric-train transformer pro-



Power-amplifier compartment. The 4CX250B is mounted to the rear of the compartment. Tube clamp is a stainless-steel heater-hose clamp.

*Shortly after completing this project, I uncovered a small bonanza. Jim Reeves, WA9HKE, 2207 Columbus Avenue, Anderson, Indiana purchased the closing stock of an electronics manufacturer, and included in this stock were a number of multiple-winding power transformers yielding 1100 to 1200 volts, 300 volts, 130 volts, 6.3 volts and 5 volts. The price is \$12 each. These transformers are ideal for transverter projects such as the TR-50; I bought several for future projects.

switching and controls

Since the power output of the TR-3 is much higher than that needed for the 5763 mixer circuit, it must be attenuated. The 10-dB pad shown in **fig. 5** is somewhat over-designed, since the resistors specified will permit 220 watts dissipation. It is built into a 3x4x5-inch minibox and connected to the transverter input with short length of RG-58/U coaxial cable.

The switching relays consist of one three-pole, double-throw unit (K3), a standard Dow-Key antenna changeover relay (K1), and a miniature surplus coaxial relay (K2). K3 is the main control relay and is actuated by extra contacts in the ssb exciter (**fig. 6**); it actuates K1 and K2, and grounds the two bias lines. One multiple-pole relay would probably do the job, but these three relays were already in my junkbox.

metering

The meter circuits were designed with two factors in mind: low cost and easy-to-calculate meter shunts for the scales I wanted. By using low-cost imported meters in series with 1000-ohm resistors, all shunts are multiples or submultiples of 10 ohms. For example, with a 1-ohm

shunt, this system will read 1 ampere full scale: for 500-mA full scale a 2-ohm shunt is required, and for 100-mA full scale, a 10-ohm shunt.



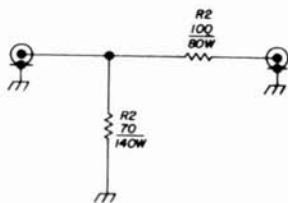


fig. 5. 10-dB pad must be used to lower output of ssb exciter. 100-ohm resistors consist of six parallel-connected 600-ohm 14-watt resistors (Sprague 459E7015). 70-ohm resistor consists of 7 parallel-connected 700-ohm, 14-watt resistors (Sprague 459E6015).

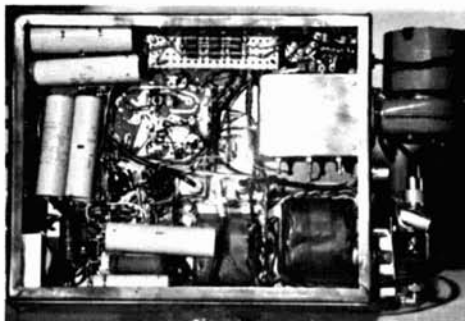

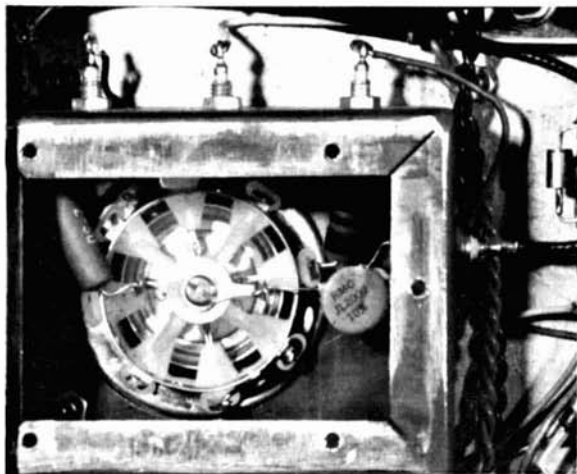Bottom view of the TR-50. Bias transformer is mounted in lower left corner. Diodes in upper center are the high-voltage bridge rectifiers. BNC fittings in center are from the miniature coax relay.



Power-amplifier grid compartment. All connections are fed through .001 μ F feedthrough capacitors.

The meters are used in the plate and screen circuits of the power-amplifier stage; these are the most critical measurements in 4X150 tetrodes. In addition, the screen-current meter is switched to read relative power output. The scale numbers on the original Micronta* meters were erased and replaced with press-on numbers to indicate the desired ranges.

*Micronta meters are \$2.98 from Radio Shack.

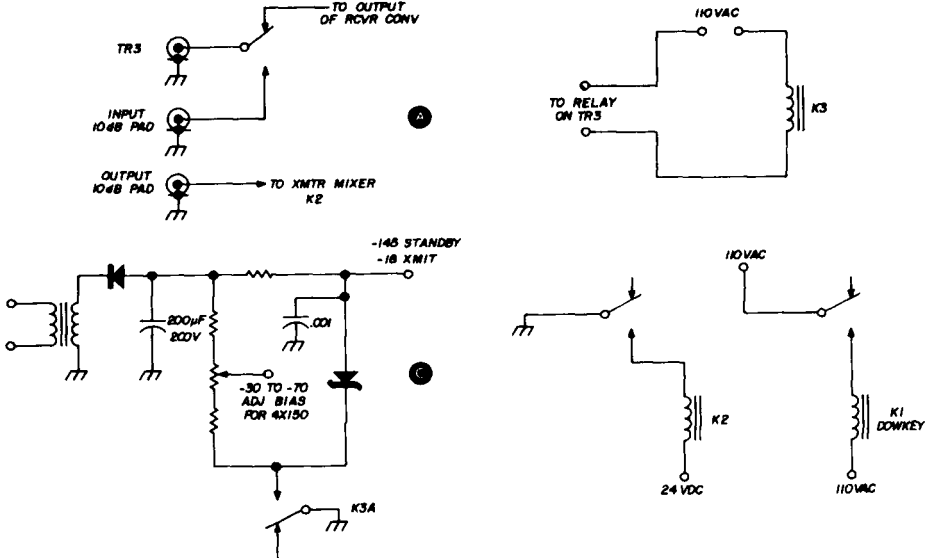


fig. 6. Switching and control circuitry. Relay K3 is a multiple-contact unit actuated by TR relay in the exciter. K2 is a miniature coax relay. K1 is a Dow-Key antenna changeover relay.

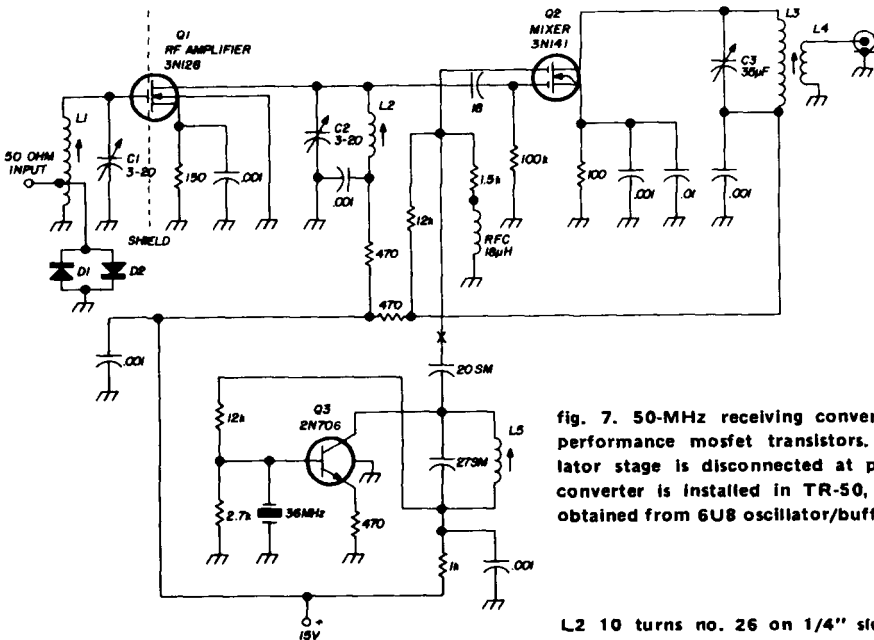


fig. 7. 50-MHz receiving converter uses high performance mosfet transistors. 2N706 oscillator stage is disconnected at point X when converter is installed in TR-50, and injection obtained from 6U8 oscillator/buffer.

L2 10 turns no. 26 on 1/4" slug-tuned form (J. W. Miller 20A000-2 form)

L3 24 turns no. 26 on 1/4" slug-tuned form, secondary 3 turns no. 26 (J. W. Miller 20A000-2 form)

L4 9 turns no. 26 on 1/4" slug-tuned form (J. W. Miller 20A000-2 form)

RFC 18 µH (J. W. Miller 9310-42)

C1,C2 3-20 pF air variable

C3 7-35 pF air variable

D1,D2 1N100 or equivalent

L1 10 turns no. 30 on 1/4" slug-tuned form, tap at 3 turns (J. W. Miller 20A000-2 form)

receiving converter

The receiver converter is based on a design by WB2EGZ originally published in *ham radio*.² The modified converter in the TR-50 uses a high-gain single-gate 3N128 mosfet as an rf amplifier; the mixer is a dual-gate 3N141 mosfet. To provide full transceive ability, oscillator injection is taken from the transmitting mixer. This circuit exhibits an excellent noise figure, and has high resistance to cross modulation.

I had originally planned to build the receiving converter into a commercial cast-aluminum box. However, there was not enough space between the top of the chassis and the final-amplifier tuning shafts to accommodate the commercial box. The box I finally used was made from double-sided printed-circuit board. The top and sides of the box were fixed in a holding jig and joined by solder fillets on all interior seams. This chassis is mounted next to the transmitting mixer board for direct capacitance coupling to the output of the 36-MHz oscillator/buffer.

Placing of components in the receiving converter is not critical with the exception of the interstage shield in the 3N128 rf amplifier. The transistor socket should be mounted so the shield can be soldered across the width of the box, isolating the input to a small compartment on one end of the chassis. Ceramic feedthrough con-

nectors are used for oscillator injection and i-f output. A BNC coaxial connector is used at the input.

The converter circuit shown in fig. 7

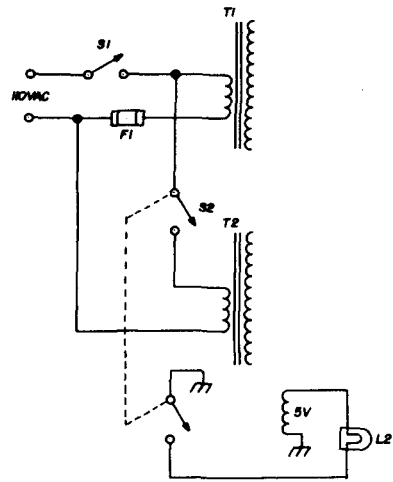


fig. 8. Ac control wiring for the TR-50. Fuse F1 is a 5-amp slo-blow unit.

nectors are used for oscillator injection and i-f output. A BNC coaxial connector is used at the input. The converter circuit shown in fig. 7 has a 36-MHz oscillator stage that was included so the converter could be bench tested before putting it into the TR-50. When the receiving converter is installed in the transverter, the oscillator injection line is disconnected from the 20-pF capacitor and connected to the output of the transmitting-mixer buffer. The built-

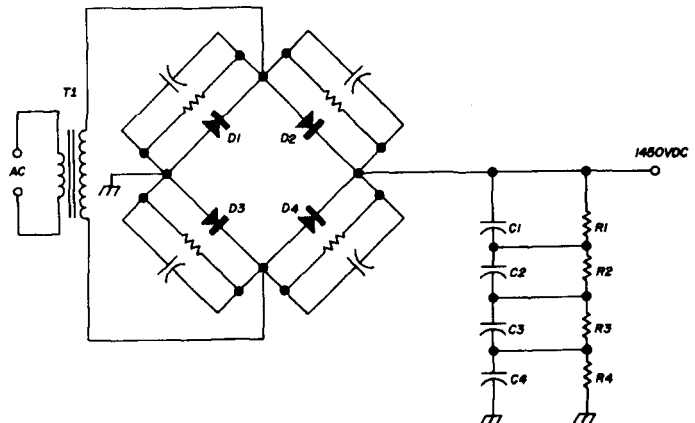


fig. 9. High-voltage power supply for the TR-50.

in receiving-converter oscillator stage is left on the board for future troubleshooting and maintenance.

alignment and test

After all the wiring and assembly were completed, the unit was given a good shaking out and cleaning to remove all the bits of wire that had become lodged in the crevices. Next, I carefully inspected all the tube sockets, tie points and cable terminations for miswiring, shorts and undersoldered joints. This is time well spent, and it pays to do some careful circuit tracing. Do not short change yourself – a simple wiring mistake can become very costly when the power is turned on.

Before applying power for the first time, remove all the tubes from their sockets. Then turn on the power and measure the voltages. The voltages will tend to be on the high side, but will confirm that connections have been made to the right places.

Test the transmitting mixer first. Connect the output of the exciter through the pad to the mixer. Plug the mixer tubes in, along with the OB2 regulators and relay keying circuit. Adjust all tuned circuits to the correct frequency with a grid-dip meter. Temporarily connect a 51-ohm, 2-watt resistor from the output link of the mixer to ground; *do not* install the 4X150 yet.

Tune the ssb exciter for normal output, and using the grid-dipper as a wavemeter, adjust the 6U8 tuned circuits for

maximum output to the 5763. Adjust the 5763 tuned circuits for maximum indication at 50 MHz. Be careful not to exceed the tune-up limitations of the exciter.

Turn off the exciter, disconnect power, discharge all the filter capacitors and install the 4X150. Remove the 51-ohm resistor from the mixer output. Connect a 50-ohm non-inductive load to the output of the power amplifier. Apply power and allow a normal warm-up

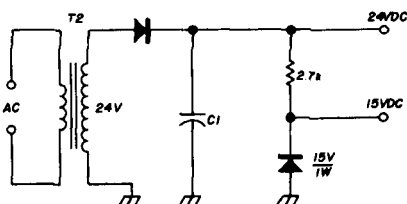


fig. 11. Receiving-converter and relay power supply.

period. Turn the exciter gain control down, key the exciter and adjust the bias on the 4X150 for resting current of 50 mA.

Now turn up the exciter gain control and resonate the final. With 1400 volts on the plate, I could load my unit to 200 mA plate current; screen current was 30 mA. This corresponds to 280 watts dc input – power output, measured with a Bird thru-line wattmeter, was 178 watts, representing 64% efficiency.

Although I have not experienced any

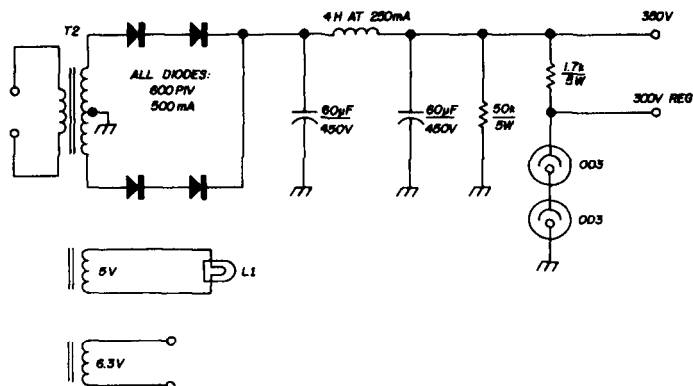


fig. 10. Low-voltage power supply.

instability in my unit, if you should run into this problem, conventional stub neutralization should cure it.

Alignment of the receiving converter is simple and straightforward. Since the mosfets are high-impedance devices, the resonant circuits can be dipped before the transistors are put in their sockets. When the converter is installed in the TR-50, only slight touchup is required to peak all the tuned circuits for maximum output.

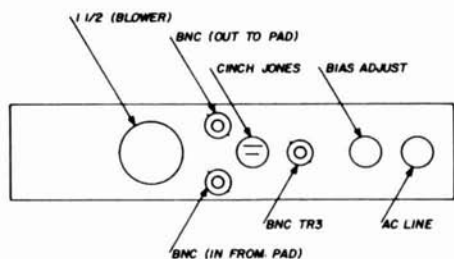


fig. 12. Rear panel layout of the TR-50.

painting

After all the checks and tests were completed and the transverter was fully checked out on the air, the front panel was removed. The steel panel was sanded with fine sand paper using *only* horizontal strokes, followed by a thorough cleaning with a degreasing solvent. *Rust-O-Leum* Dove Gray and Equipment Gray enamel were chosen as the closest match to the Drake TR-3 panel colors. A 3/16-inch wide piece of masking tape on the bare steel divided the panel into vertical halves. Each half was alternately masked while the other half was sprayed. Repetitive light coats of paint are preferred over one heavy coat.

Each color was baked for 30 minutes in the hot-air plenum chamber of a forced hot-air home furnace. After each half of the panel was baked, the 3/16-inch masking strip was carefully removed, leaving a bright steel dividing line that matches the decorative strip on the TR-3.

For lettering on the front panel I used *Prestype* transfers — black letters on the light gray upper half, and white lettering

on the lower dark-gray half. Three coats of clear acrylic lacquer spray, baked for 30 minutes, protect the lettering.

The elevation legs for the TR-50 were made from 1-inch dowel rod, capped with rubber crutch tips.

conclusion

The original design was recently modified when I acquired a 4X250R from a friend. The 4X150 was replaced, and the bias readjusted for 125 mA idling current. No other modifications were necessary. An immediate increase of 20 watts was noted in output power. This tube, although expensive, is designed specifically for class-AB linear service, and the increase in power and efficiency was well worthwhile.

The pleasure I have derived from designing and building the TR-50 has been multiplied many times by the excel-



Rear view of TR-50 shows blower and Dow-Key antenna changeover relay.

lent on-the-air reports I have received. The excellent results have spurred me to begin another project — a TR-144 using K2ISP's printed-circuit two-meter mixer.

I would like to express my thanks to Dick McGinn, WA1IMS, for providing the excellent photographs of the TR-50.

references

1. D. W. Bramer, K2ISP, "Heterodyne Transmitting Mixers for Six and Two Meters," *ham radio*, April, 1969, p. 8.
2. D. W. Nelson, WB2EGZ, "Six-Meter Mosfet Converter," *ham radio*, June, 1968, p. 22.

ham radio

The latest word in Heathkit® receivers: “Solid-State”



the Heathkit® SB-303... \$319^{95*}

The "303"... a new performance standard for receivers. The renowned Heathkit "300" & "301" are a tough act to follow because of their obvious performance superiority and value. But the Hams at Heath have come up with the last word again in the new solid-state SB-303, already a standard-setter for the industry.

Advanced solid-state design using 27 silicon transistors & 1 IC delivers instant warmup, 100 Hz stability in 10 minutes and better LMO linearity. The exclusive Heath factory assembled solid-state LMO with 1 kHz readout gives the smooth, linear tuning that the SB-series is famous for. A dual-gate MOSFET front end provides greater dynamic range and large signal handling capability with low distortion.

Features built-in, not added on...no costly options in this rig. Compare the "303": full transceive capability with the "400" or "401"...3-position AGC...25 kHz calibration...antenna & power connection for two VHF converters...15 MHz WWV reception. Check the specs: 2.1 kHz selectivity...less than 0.25 uV sensitivity...60 dB image rejection.

Send for a free spec sheet, then order your "303"... and learn what hundreds of owners call their new "303": the hottest one yet from the Hams at Heath.

Kit SB-303, 19 lbs.\$319.95*
SBA-301-1, optional 3.75 kHz AM Xtal filter \$20.95*
SBA-301-2, optional 400 Hz CW Xtal filter...\$21.95*

SB-303 SPECIFICATIONS - Frequency Range: (MHz) - 3.5 to 4.0, 7.0 to 7.3, 14.0 to 14.5, 15.0 to 15.3, 21.0 to 21.5, 28.0 to 30. Intermediate Frequency: (IF) - 3.395 MHz. Frequency Stability: Less than 100 Hz drift per hour after 10 minutes warmup under normal ambient conditions. Less than 100 Hz drift for ±10% line voltage variation. Fre-

quency Selection: Built-in Linear Master Oscillator. Modes of Operation: SSB - Single sideband (suppressed carrier, with selectable upper or lower sideband). CW - Keyed continuous wave. AM - Amplitude modulated continuous wave. RTTY - Radio teletype (frequency-shift keyed continuous wave). Sensitivity: Less than 0.25 uV for 10 dB S+N/N for SSB operation. Overall Gain: Less than 1.5 uV input for 0.5 audio output (single tone SSB). AGC Characteristics: Blocking - Greater than 3.0 V CW/SSB/RTTY. Dynamic Range - Greater than 150 dB CW/SSB. RF Attenuator: Variable 0-40 dB nominal. Selectivity: SSB - 2.1 kHz @ 6 dB down, 5.0 kHz maximum @ 60 dB down (crystal filter supplied). CW - 400 Hz at 6 dB down, 2.0 kHz maximum at 60 dB down (crystal filter available as an accessory). AM - 3.75 kHz at 6 dB down, 10 kHz maximum at 60 dB down (crystal filter available as an accessory). RTTY - 2.1 kHz at 6 dB down, 5.0 kHz maximum at 60 dB down (uses SSB crystal filter). Image Rejection: 60 dB or better. IF Rejection: 3.395 - greater than 55 dB. 8.595 - greater than 50 dB. Spurious Response: All below 1 uV equivalent signal input. Temperature Range: 10° C ambient. Dial Accuracy: Electrical - Within 400 Hz after calibration at nearest 100 kHz or 25 kHz point. Visual - Within 200 Hz. Calibration: Every 100 kHz or 25 kHz. Dial Backlash: No more than 50 Hz. Antenna Input Impedance: 50 ohm nominal unbalanced. Power Requirements: 105 to 125 or 210 to 250 VAC, 40 W max. Dimensions (with knobs & feet installed): 12¼" W x 7¼" H x 14" D. Net Weight: 15¾ lbs.

HEATHKIT

HEATH COMPANY, Dept. 22-3
 Benton Harbor, Michigan 49022
a Schlumberger company

Enclosed is \$ _____, plus shipping


Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____ State _____ Zip _____

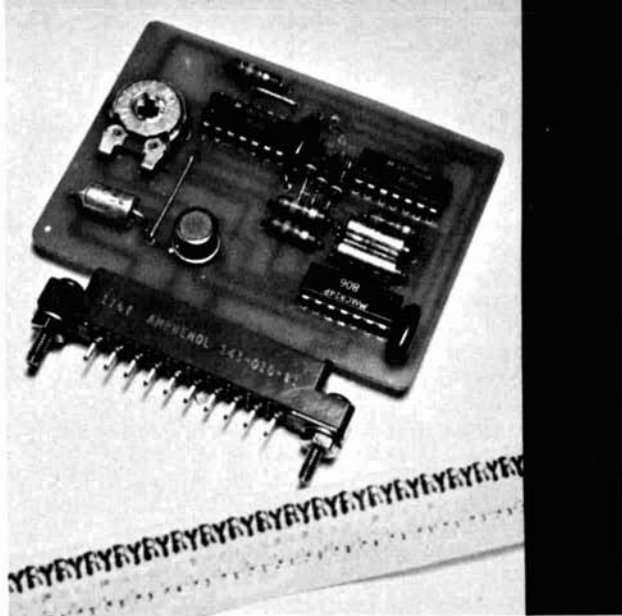Prices & specifications subject to change without notice.
 *Mail order prices; F.O.B. factory. AM-243R



RTTY signal generator

This integrated-circuit
RTTY reversal generator
produces an RYRYRY
signal for testing
teleprinters

Vic Shinsel, W7ZTC, 2116 Oak Street, LaGrande, Oregon 97850

Teleprinter range adjustments and other performance checks are usually made while the machine is printing the standard RY test signal. R signals select even mark and odd space pulses, then Y signals reverse everything and select even space and odd mark. The result is a maximum amount of slipping and sliding of adjacent parts within the machine, and conditions which are likely to cause misprint are readily observed.

Bias and distortion measurements are ordinarily taken during reception of *reversal* square-waves or continuous space-bar signals. Reversal signals alternately open and close the machine loop, simulating a succession of mark and space pulses. Space-bar signals perform the same job if a keyboard of known quality is available. Use of the reversal square-wave or keyboard space-bar signal to a questionable RTTY transmission unit promptly turns up any bias distortion — as evidenced by alteration of the

pulse duty cycle. This is the electronic counterpart of the *mechanical slipping and sliding check*.

Here's a low-cost reversal generator which also sends repetitive, zero-bias, RYRY test signals to the printer or transmitter loop. An electronic clutch is included, making the unit a self-contained solid-state transmitter-distributor. A *clutch keyer* circuit may be added later if desired. This enables the generator to send "...RY (pause) RY (pause) RY..." leaving both hands free for stubborn machine adjustments. A multi-purpose RTTY bias and loop test meter will also be described.

In order to be useful in distortion tests, reversal square-wave pulses must be of accurate length, with reasonably fast rise and fall times, and of especially

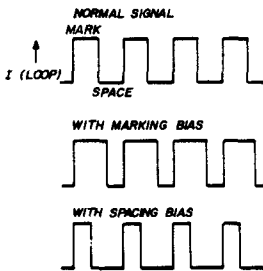


fig. 1. Bias distortion.

accurate duty cycle. The square-wave works out to be 22.5 Hertz for the 45.5 baud (60 wpm) standard system. Mark and space pulses are of equal duration, so the duty cycle is exactly 50 percent.

theory of operation

Consider a defective demodulator or terminal unit which changes the duty cycle by lengthening the mark pulses and shortening the space pulses. The demodulator is said to cause "marking bias" and it degrades system performance according to the severity of the condition. This kind of distortion (fig. 1) may be one reason why two teleprinters are unable to communicate through a radio system, while

both print fine on local loops. The effects of bias distortion may be additive.

Quantitative bias measurements are expressed as percentages. Distortion which lengthens a 22-millisecond mark

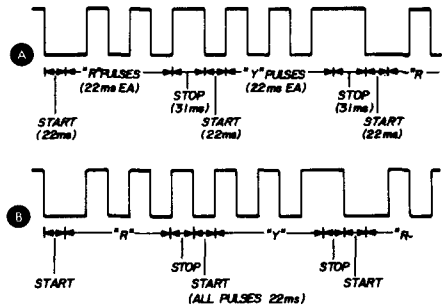


fig. 2. Teletype Corporation RY signal is shown in A; Western Union RY signal is shown in B.

pulse by 11 milliseconds is described as 50% marking bias.

The RY generator takes advantage of a compatibility scheme to develop a signal which prints RY while maintaining the perfect 50% duty cycle of the reversal square-wave. As such, this generator can be a very useful standard for RTTY system tests.

Fig. 2A shows the waveform of a Teletype Corporation model-14 distributor sending RY at the usual 61.3 words per minute. Fig. 2B shows the waveform of a surplus Western Union distributor sending RY at the compatible speed of 65 words per minute. Both machines are usable in the amateur bands, but 65 wpm is right at the upper speed tolerance limit set by FCC.

Note that the only difference between the two signals is the duration of the stop pulses. The Western Union machine sends a shorter (22 millisecond) stop pulse. The two machines operate compatibly because the *selecting* pulses are all the same length, i. e. both units use a 45.5 baud code.

Even with the shorter stop pulse, synchronization is assured. The nominal (420 rpm) receiving shaft speed of the Teletype machine is still faster than the

(390 rpm) transmitting shaft speed of the Western Union machine.

The Western Union RY signal in fig. 2B may be used as a reversal signal, because each mark has a space counter-

from the ic logic. The remainder of the circuit is used to invert two out of every fourteen square-wave pulses to form the RY test signal.

Flip-flops A, B, C and D form a

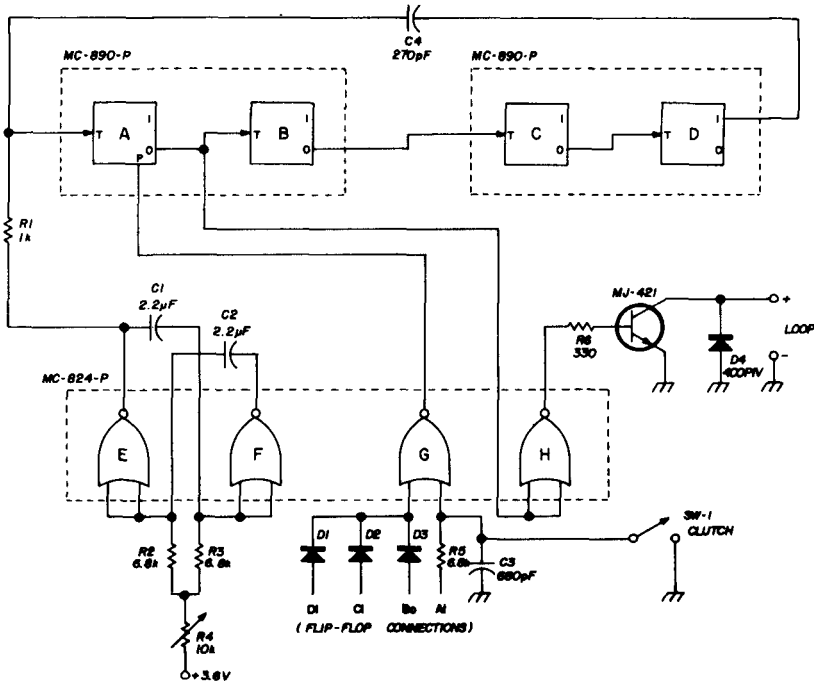


fig. 3 Solid-state RY generator. Diodes D1, D2 and D3 are germanium computer types. Silicon diodes may be used with higher supply voltage (3.5 to 4.5 volts). Resistor R4 is a Mallory MTC1414.

part of equal duration. The duty cycle is exactly 50 percent.

circuit

The circuit of fig. 3 generates the RY waveform of fig. 2B. Gates E and F of the MC824P quadruple-two-input gate are connected as an astable multivibrator. The negative slopes of the multivibrator output trigger flip-flop A (MC890P) to form a perfect square-wave. Gate H is used as a buffer to drive the base of the Motorola MJ421 transistor with the square wave. The MJ421 is rated at 350 volts V_{cb} and makes an excellent loop driver. Diode D4 is for inductive transient suppression. Resistor R6 (not shown on the photo) was added to decouple transients

scale-of-sixteen counter. Feedback capacitor C4 inverts one pulse by causing count 2 to be skipped. This occurs during the decay of the positive pulse fed through the capacitor from flip-flop D, which retriggers A and causes an immediate advance to count 3. Gate G inverts the other pulse by presetting count 15 to count zero. In other words, count 15 is also skipped. The truth table of fig. 4 summarizes generator operation.

When S1 is closed, the circuit advances to the mark pulse of count 14. Gate G recognizes this count because all inputs are zero. The output of gate G goes positive and presets flip-flop A to mark. The circuit holds the mark as long as S1 remains closed, because the preset line

will not allow flip-flop A to toggle. This provides the clutch action for the generator.

When S1 is opened, the positive voltage at R5 (from A1) pulls down the

G rapidly reactivates the preset line and forces the circuit on to count zero. Gate G has no further influence until count 15 is reached again, (or count 14 if S1 gets closed). Capacitor C3 adds a delay of 0.5

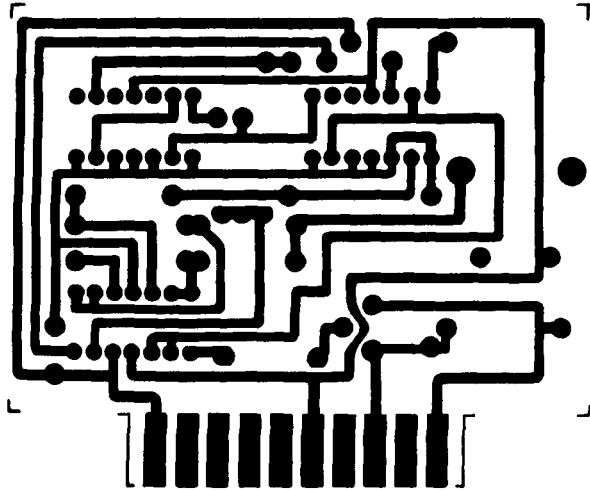


fig. 5. Full-size printed-circuit board layout for the RTTY generator.

output of gate G and removes the preset condition from the first flip-flop. The next trigger from the multivibrator momentarily advances the circuit to count 15. Then the positive voltage disappears from R5, causing the output of gate G to rise. The positive output from

microsecond to ensure that the preset pulse is of sufficient duration to do its job.

The overall effect is that only complete RYs are sent. The circuit action is always stopped in the proper state to begin another RY. If S1 is opened, then closed, a single RY will be sent. If S1 is opened, and remains open, a continuous train of RYs is sent. If S1 is eventually closed, the unit finishes its last RY, then stops ready to send another.

fig. 4 Truth table for RTTY generator.

Count	Ao	Bo	Co	Do	Output
0	0	+	+	+	Mark (Stop)
1	+	+	+	+	Space (Start)
2	0	0	0	0	Space pos. transient — 0.5 μ sec.
3	+	0	0	0	Space
4	0	+	0	0	Mark
5	+	+	0	0	Space R
6	0	0	+	0	Mark
7	+	0	+	0	Space
8	0	+	+	0	Mark (Stop)
9	+	+	+	0	Space (Start)
10	0	0	0	+	Mark
11	+	0	0	+	Space
12	0	+	0	+	Mark Y
13	+	+	0	+	Space
14	0	0	+	+	Mark
15	+	0	+	+	Space neg. transient — 0.3 μ sec.
0	0	+	+	+	

construction

Construction of the RY-reversal generator is simplified by the full-size etched-circuit layout of fig. 5. Component locations are given in fig. 6. This is a compact board, and every caution must be taken to avoid solder bridges and excessive heat. It is recommended that all hole locations be dimpled with a sharp scribe, then drilled out to no. 60 holes. Enlarge the pot mounting holes to no. 40 and 50, as required. Brighten the copper with steel wool or SOS pad just prior to soldering.

Surplus flatpack ics worked fine on

the original breadboard, but layout clearances were bothersome. This board uses popular plastic dual-inline RTL ics. The pattern was designed to match an Amphenol 143-010-01 connector. Three to

multivibrator. Use 60-Hz line sweep and set the speed pot for minimal motion of the Lissajous pattern. This will be a slight adjustment! The Lissajous ratio is 22.5 : 60, or 3/8.

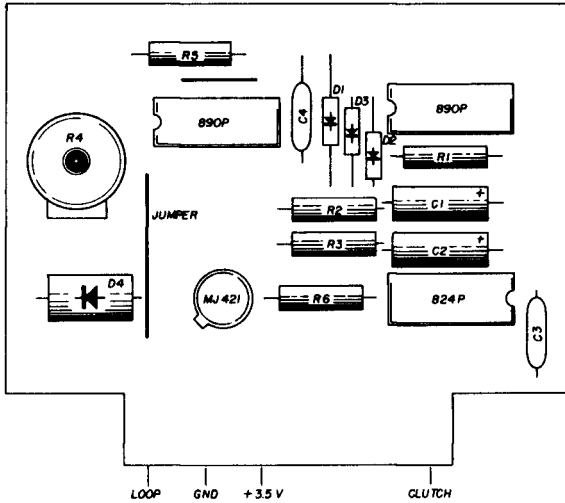


fig. 6. Component placement on the printed-circuit board.

four volts at about 75 milliamperes are required to power the unit; two flashlight cells are fine!

Ham printer loops are capable of some pretty wild transients. Some may develop spikes as high as 800 volts. Avoid ground loops and long leads common to the loop and board supply. A particularly noisy loop may require an 0.1 μ F disc-ceramic capacitor from the board +3V to ground right at the Amphenol connector. This was not required on the original unit. Be sure to observe polarity when connecting the generator into a loop, or it will fail to print. No damage should result from a reverse connection.

adjustment

Only one adjustment is necessary. Open S1 and set the speed control (R4) for an approximate 22.5 Hz square-wave at the output of the multivibrator. The printer will start typing RYRY as the proper frequency is approached. Then, for precise adjustment, connect an oscilloscope probe to the output of the

Other speeds may be set on the pot for local machine tests, but it is wise to observe the FCC limits of 55-65 wpm for on-the-air tests.

There is a certain comfort in having nice, clean zero-bias RYs available at the flick of a switch. Automatic carriage-return shows its worth with this unit slamming out continuous RYs.

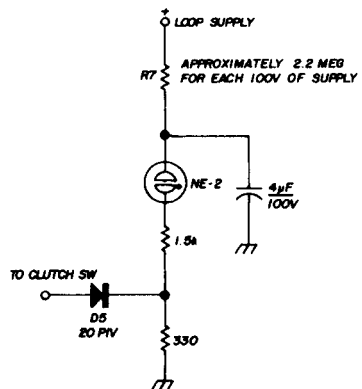


fig. 7. Clutch-keyer circuit.

clutch keyer

The clutch keyer of **fig. 7** was an afterthought. Note that the RY generator's clutch-control line is grounded

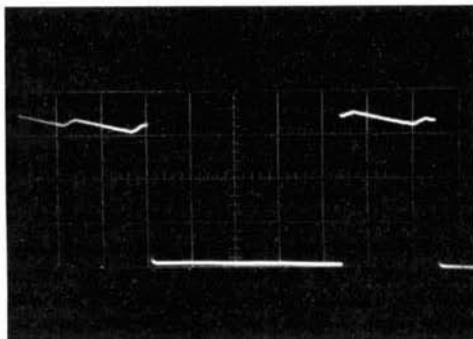


fig. 8. Poor regulation of loop current into resistive load. Droop above 60-mA value looks like marking bias to milliammeter. (Vertical scale, 20 mA per division; horizontal scale, 10 msec per division.)

through the diode and 330-ohm resistor. The ground inhibits generator operation. Every few seconds the neon relaxation oscillator fires and momentarily reverse-biases the diode, which effectively removes the ground from the clutch. As a result, one single RY is sent at a time — every two seconds. R7 is about 2.2 meg for each 100 volts of loop supply.

measuring distortion

A common scheme for measuring bias distortion is as follows. First, close the loop (steady mark) and measure the loop current. Then apply reversal signals to the unit under evaluation, and again measure loop current. Since the reversal signal is half mark and half space, the meter will flutter slightly — but its average indication should be exactly half of the closed loop reading. This corresponds to zero bias, and any variation indicates the presence of gremlins. This seems to be a popular method because just about any loop milliammeter is suitable for the test. But there is a pitfall.

The regulation of the loop supply may influence the bias reading. This difficulty

popped up in my Mainliner. The mark pulses had a high instantaneous current when first keyed on. Then the current drooped slightly to the steady-mark value. **Fig. 8** shows the loop current

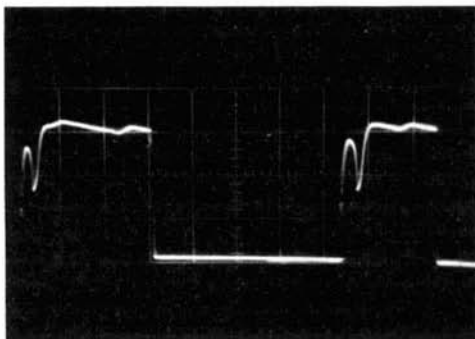



fig. 9. Inductive transients from selector magnet may also fool the bias milliammeter. (Vertical scale, 20 mA per division; horizontal scale, 10 msec per division.)

waveform through a resistive load. With this condition, the meter errantly indicated a duty cycle change. The triangular “droop” portion of the signal above the steady-mark (60 mA) value appeared as marking bias. In this particular case, adjustment of a slicer or polar relay to reduce the apparent bias would have introduced about 8% distortion.

The situation worsens as inductive loads are switched into the loop. **Fig. 9** shows the effect of switching in a model-26 selector magnet.

A better bias measuring scheme is given in **fig. 10**. The zener diode clips at 5 volts and standardizes the mark pulses. Now the meter shows true duty cycle, and the reading is not appreciably affected by poor regulation, loop transients, loop resistance or supply voltage.

fig. 10. Bias meter measures true duty cycle.

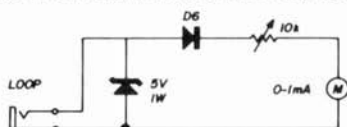

D6 = SILICON COMPUTER DIODE, 20 PIV

The pot is set once and for all at full scale on steady mark. Diode D6 assists in transient suppression.

The meter may be calibrated directly in bias percentage if desired. Zero current

for the Western Union machine. Potentiometer R8 translates a compromise duty cycle of 33% to center scale on the multimeter for bias-distortion measurements where no reversal generator is

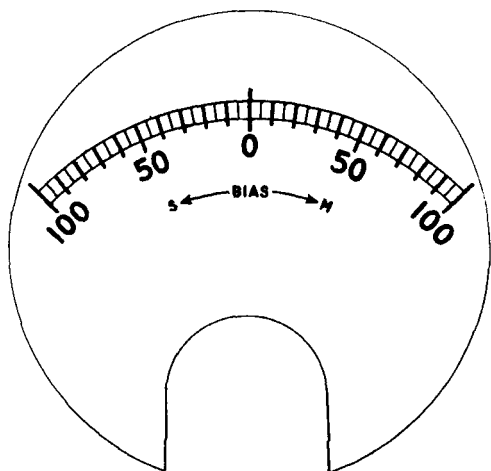


fig. 11. Full-scale bias scale for 3-inch Simpson meter.

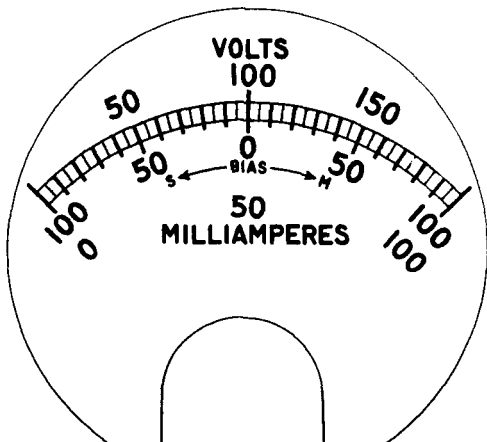


fig. 12. Full-scale RTTY multi-meter scale for 3-inch Simpson meter.


corresponds to 100% spacing bias; half scale is zero bias; and full scale is 100% marking bias. Fig. 11 is a suitable scale for a three inch Simpson movement. The scale of fig. 12 was developed for the multi-purpose RTTY meter shown in fig. 13. It measures loop current, loop supply voltage and bias.

A steady stream of keyboard-space signals has a duty cycle of 31% for the standard Teletype equipment, and 35%

available. If the distributor is known to be free of bias, simply send successive keyboard-space signals at full speed. Read the bias at the printing end for an overall check.

For calibration: Set R7 to full scale on steady mark. Then set R8 to 66% of the resistance or R7. As an alternative, R8 may be set to zero bias on a good, synchronous transmitter-distributor. When R7 is in the circuit, the meter reads bias from reversal signals. When R8 is in the circuit, the meter reads bias from keyboard-spaces.

fig. 13. Circuit for RTTY multimeter.

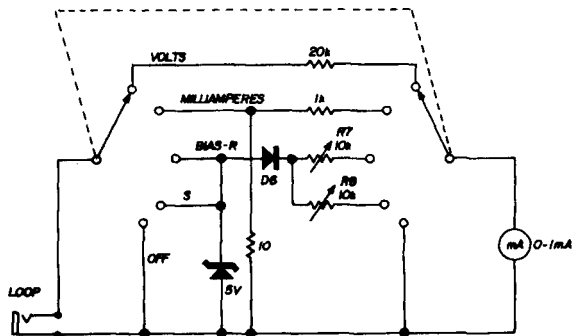

bibliography

1. Irv Hoff, "Operating the Teleprinter," *QST*, February, 1965, p. 29.
2. Charles Teeters, "Teletype Reversal Generator," *CQ*, March, 1958, p. 41.
3. Durward Tucker, "RTTY From A to Z," *CQ*, August, 1964, p. 27.
4. John Connors, "Photographic Printed Circuit Process," *73*, August, 1968, p. 14.
5. Hank Olsen, "Micro-logic for Non-Logical Users," *73*, June, 1967, p. 58.

ham radio

tabulated characteristics

of vacuum-tube and transistor amplifiers

Although there are many active devices that are used for generating or amplifying af and rf signals, only two, vacuum tubes and transistors, are of great interest to radio amateurs. These two can be split into many sub-categories. However, only the conventional vacuum tube in the common-cathode configuration and the bipolar transistor in the common-emitter configuration will be considered in this article.

Transistors are finding great favor among both manufacturers and amateurs for use in receivers and low-level stages of transmitters. The vacuum-tube amplifier, however, still ranks as the best choice for moderate and high-power stages in radio transmitters.

Intelligent use of either device requires that the user have a clear concept of the device's capabilities, especially the limitations of these capabilities. Then, too, the FCC likes to ask rather searching questions concerning both vacuum tubes and transistors in its amateur license examinations. With the upsurge of interest in qualifying for higher-grade licenses, these

active devices are having a new and inquiring look taken at their characteristics and capabilities.

Many books and magazine articles have been published on the characteristics and applications of vacuum tubes; almost as many have been written on transistors. Most of these are very good for the study of a particular aspect of the subject. A tabulation of the relative characteristics of the three major classes (A, B, and C) of amplifier operation has not had the emphasis that interest demands. This aspect must be understood clearly if an amateur is to make knowledgeable use of such amplifiers, whether in equipment of his own design or in the correct adjustment of manufactured equipment.

This article is written to provide a simple but complete comparison of the operating characteristics of class-A, class-B, and class-C amplifiers, listed under one heading for vacuum tube amplifiers and under another for bipolar transistors. Class AB1 and class AB2 operation may be interpolated between class A and class B.

This tabulation makes no pretense of being an in-depth exposition of the behavior of vacuum-tube amplifiers, and most certainly, not of transistor amplifiers. The facts, however, concisely state the more important factors that determine the use to which we put such amplifiers, and how we operate them in those applications.

Carl C. Drumeller, W5JJ, 5824 N. W. 58th Street, Warr Acres, Oklahoma 73122

table 1. Characteristics of vacuum-tube amplifiers.

Class-A Operation

Distinguishing property	Ability to amplify signals without distortion.
Desired effect	To have the waveform of the output signal be identical, except for amplitude, to the waveform of the input signal.
Method	<p>Quiescent grid-bias voltage is set to establish the operating point midway on the straight portion of the $E_c I_b$ characteristic curve.</p> <p>Grid signal voltage is limited so it never goes beyond the straight portion of the $E_c I_b$ characteristic curve in either the negative- or positive-going extremes of signal voltage.</p> <p>For triode vacuum tubes, for maximum undistorted output, the plate load resistance is set at twice the dynamic plate resistance of the tube.</p> <p>Plate voltage is limited to a value that will ensure the tube's rated plate dissipation will not be exceeded.</p>
Distinguishing characteristics	<p>Voltage gain is very high</p> <p>Power gain is very high</p> <p>Grid drive power requirement is extremely low</p> <p>Plate current, as measured with a dc meter with signal present, remains constant</p> <p>Plate current flows 360° during an input signal cycle</p> <p>Input impedance is very high</p> <p>Output impedance is not critical; however, distortion increases more for too-low than for too-high mismatch</p> <p>No grid current flows</p> <p>Grid-bias voltage source does not have to have low impedance or good voltage regulation</p> <p>Plate voltage source does not need to have good voltage regulation</p> <p>The stage may be used either single-ended or push-pull for either af or rf signals</p> <p>Stage can not be used as a frequency multiplier</p> <p>Oscillators can be forced, by limitation of grid swing, to operate in this class</p> <p>Efficiency is approximately 20%</p>

Class-B Operation

Distinguishing property	Ability to amplify amplitude-modulated signals without distortion of the modulation characteristics.
Desired effect	To have the output signal power vary as the square of the input signal voltage.
Method	<p>Quiescent grid-bias voltage is set to establish the operating point just short of the cut-off point on the $E_c I_b$ characteristic curve.</p> <p>Grid signal voltage may be great enough to drive the grid into the positive region. The less it is driven into the positive region, the lower will be the distortion of the output signal.</p> <p>Plate load resistance is adjusted to the value required to attain the desired effect. Normally, it is adjusted for very heavy plate current loading.</p> <p>Plate voltage is limited to a value that will ensure the tube's rated plate dissipation not being exceeded even when the plate current is set high to attain the desired effect.</p> <p>Vacuum tube is selected to have ample cathode emission to meet heavy peak current demands.</p>
Distinguishing characteristics	<p>Voltage gain is moderate</p> <p>Power gain is moderate</p> <p>Plate current, as measured with a dc meter with signal present, may vary in relation with signal voltage amplitude. This is the condition when amplifying af or ssb rf signals. When amplifying a-m (double sideband with carrier), fm, or key-down cw signals, the plate current remains constant</p> <p>Plate current flows for approximately 180° during an input signal cycle</p> <p>Input impedance varies from high, when the grid is not excited into the positive region, to low, when the grid is driven into conduction</p> <p>Output load impedance is quite critical, as its optimum adjustment is an important factor in achieving the desired effects</p> <p>Grid current may flow; when it flows, it varies in the same manner as does the plate current</p> <p>Grid-bias voltage source needs low internal impedance and good voltage regulation</p> <p>Plate voltage source needs good voltage regulation</p> <p>Stage makes a moderately good frequency multiplier</p> <p>Stage must have push-pull configuration for af use but may be either single-ended or push-pull for rf</p> <p>Oscillators can be forced to operate in this class</p> <p>Efficiency is approximately 30% to 33% for steady-state rf (double sideband with carrier, fm, or key-down cw) and may go as high as 66% for af or ssb rf</p>

Class-C Operation

Distinguishing property	Ability to respond linearly to amplitude modulation of the plate circuit
Desired effect	To have the plate current vary directly with the plate voltage. (The plate current, for example, will double when the plate voltage is doubled)
Method	<p>Quiescent grid voltage is set to establish the operating point at approximately two-and-one-half times the negative potential required to cut off plate current flow. A portion of this voltage may come from a fixed source; part, however, must come from the IR drop across a grid resistor</p> <p>Grid signal voltage must be great enough to drive the grid far into the positive region, preferably into saturation</p> <p>Plate load resistance is not critical; it usually is set by complying with the requirement for moderate plate loading</p> <p>The vacuum tube is selected to have ample cathode emission to meet heavy peak current demands</p> <p>Plate voltage is limited to a value that will hold the plate dissipation to well within its rated capabilities, preferably to not over 60% of the rate capability; also, the plate voltage must not exceed one-half the flash-over voltage rating for the tube</p>
Distinguishing characteristics	<p>Voltage gain is very low</p> <p>Power gain is low, averaging about 10</p> <p>Grid drive power requirement is high</p> <p>Plate current, as measured with a dc meter under modulation conditions, remains constant</p> <p>Plate current flows between 60° and 90°, depending on bias and drive, during an input signal cycle</p> <p>Input impedance is low</p> <p>Output impedance is not critical; generally it is established by the requirement that the plate current should not exceed about 60% of the tube's rated capability</p> <p>Heavy grid current flows</p> <p>Grid-bias voltage source does not need good voltage regulation</p> <p>Plate voltage source needs good voltage regulation</p> <p>Efficiency is approximately 65% to 75%</p> <p>The stage may be used in either single-ended or push-pull configuration</p> <p>The stage makes an excellent frequency multiplier</p> <p>Oscillators normally operate in this class</p>

table 2. Characteristics of bipolar transistor amplifiers.

Class-A Operation

Distinguishing property	Ability to amplify signals without distortion
Desired effect	To have the waveform of the output signal to be identical, except for amplitude, to the waveform of the input signal.
Method	<p>Quiescent base current is set to establish the operating point midway between the cut-off and saturation points on the ac loadline</p> <p>Base signal voltage is limited to produce equal variations of collector current for both positive- and negative-going excursions of base-emitter signal voltage</p> <p>Load resistance is made equal to the value of the collector-emitter voltage divided by the collector current</p> <p>Collector-emitter voltage is limited to a value that will not permit the transistor's dissipation to exceed the rated power under any condition of signal voltage</p>
Distinguishing characteristics	<p>Voltage gain is very high</p> <p>Power gain is high</p> <p>Base-emitter drive power is moderate</p> <p>Collector current, as measured with a dc meter with signal present, remains constant</p> <p>Collector current flows 360° during an input signal cycle</p> <p>Input impedance is quite low</p> <p>Output impedance is not critical</p> <p>Base-emitter current flows 360° during an input signal cycle</p> <p>Collector voltage source does not need good voltage regulation</p> <p>The stage may be used either single-ended or push-pull for either af or rf signals</p> <p>The stage cannot be used as a frequency multiplier</p> <p>Oscillators can be forced, by limitation of base-emitter voltage swing, to operate in this class</p> <p>Efficiency is low, running from 20% to 30%</p>

Class-B Operation

Distinguishing property	Ability to amplify amplitude-modulated signals without distortion of the modulation characteristics
Desired effect	To have the output power vary as the square of the input signal voltage
Method	<p>Quiescent base-emitter current is set to establish the operating point just short of collector current cutoff</p> <p>For rf linear-amplifier service, a transistor is selected to have:</p> <ol style="list-style-type: none">1. A flat beta curve2. Multiple emitters, each with an integral bias resistor3. High second-breakdown characteristic4. Power dissipation at least twice the power at which it will be operated <p>For rf linear-amplifier service, the peak collector current swing is limited to only 30% of the rated maximum current</p> <p>Collector load resistance is adjusted to the value required to attain linearity; normally, it is adjusted for very heavy collector current loading</p>
Distinguishing characteristics	<p>Voltage gain is moderate</p> <p>Power gain is moderate</p> <p>Collector current, as measured with a dc meter with signal present, may vary with signal voltage amplitude</p> <p>Collector current flows for approximately 180° during the input signal cycle</p> <p>Input impedance is low</p> <p>Output impedance is quite critical, as its optimum adjustment is an important factor in achieving the desired results</p> <p>Base-emitter current will flow during slightly over 180° of the input signal cycle</p> <p>Base-bias source must have low internal resistance</p> <p>Collector voltage source must have good voltage regulation</p> <p>The stage makes a good frequency multiplier</p> <p>The stage must have push-pull configuration for af use but may be either push-pull or single-ended for rf use</p> <p>Oscillators can be forced to operate in this class</p> <p>Efficiency varies from 30% to 66%</p>

Class-C Operation

Distinguishing property	Ability to respond linearly to amplitude modulation of the collector circuit
Desired effect	To have the collector current vary directly with the collector voltage. (The collector current, for example, will double when the collector voltage is doubled)
Method	<p>Quiescent base-emitter current is zero; the base-emitter voltage is biased so that a small signal voltage is required to cause base-emitter (and collector-emitter) current to flow</p> <p>Input signal voltage must be great enough to drive the transistor to collector saturation. Because of the decreasing efficiency of a transistor under high excitation, the input signal also must be amplitude modulated. This serves two purposes: it supplies the extra peak excitation to keep the output power up during upward modulation peaks, and decreases the excitation to lessen feed-through during downward modulation swings</p> <p>Collector load resistance is not critical</p> <p>Collector voltage must be limited to not over one-half, and preferably not over one-fourth, the rated maximum voltage</p>
Distinguishing characteristics	<p>Voltage gain is very low</p> <p>Power gain is low, from 3 to 10 dB</p> <p>Base-emitter drive power is quite high</p> <p>Collector current, as measured with a dc meter under voice modulation conditions, remains constant</p> <p>Collector current flows between 90° and 160°, depending upon base bias and drive, during an input signal cycle</p> <p>Input impedance is very, very low</p> <p>Base-emitter current is high under signal conditions</p> <p>Base-bias source does not need good regulation</p> <p>Collector voltage source requires good regulation</p> <p>Efficiency is approximately 65% to 75%</p> <p>The stage is useful only in rf service and may be used either single-ended or push-pull</p> <p>The stage makes an excellent frequency multiplier</p> <p>Oscillators normally operate in this class</p>

ham radio

KENWOOD

IS THE *ValueLine*



COMPARE FEATURES... COMPARE PRICES...

In fact, we defy you to find a better value for your equipment dollar. The R-599, pictured above, boasts features, specifications and styling you won't find in any other receiver. So, whichever is more important — quality or price — the Kenwood R-599 wins hands down. Look at these features... they're standard! ① **MODE** — Permits reception of CW, LSB, USB, AM, AM with noise limiter, or FM. ② **FUNCTION** — Selects receiver position between: Standby, Monitor signal from T-599, Slow AGC, Fast AGC, 100 KHz or 25 KHz calibrator. ③ **DIAL** — 1/2 KHz readout, 25 KHz on subdial. ④ **PRESELECTOR** — Adjusts R-599 for maximum gain on desired receiving frequency by tuning for maximum s-meter reading. ⑤ **BAND** — 160, 80, 40, 20, 15, 10 meters (2 & 6 meters with accessory converters). ⑥ **RIT** — Allows off-set tun-

ing of receiver when Kenwood units are operated in transceiver configuration. ⑦ **VFO SELECT** — Chooses VFO of either unit in transceiver operation or allows each VFO to operate independently. ⑧ **SELECTIVITY** — Automatically selects appropriate filter for selected mode or choose 2.5 KHz filter for LSB and USB, 500 Hz filter for CW, 5 KHz filter for AM (and AM with noise limiter), and 25 KHz filter for FM.

The S-599 speaker \$14.50 • CC-29 2 meter converter \$29.50 • CC-69 6 meter converter \$29.50.

The Kenwood T-599 hybrid transmitter, the perfect match, offers the same degree of perfection... SSB, AM and CW, all amateur bands 3.5 MHz to 29.7 MHz. Only \$345.00.

ORDER YOURS TODAY... FROM ANY OF THESE FINE DEALERS:

HENRY RADIO • 11240 W. Olympic Blvd. • Los Angeles, Calif. 90064 • (213)477-6701 □ Butler 1 Mo. 64730 • (816)679-3127 □ 931 N. Euclid • Anaheim, Calif. 92801 • (714)772-9200

FRECK RADIO & SUPPLY CO. • 38 Biltmore Ave. • Asheville, North Carolina 28801 • (704) 254-8637

HAM RADIO OUTLET • 999 Howard Ave. • Burlingame, Calif. 94010 • (415)342-5757

ELECTRONIC CENTER • 117 Third Ave. N. •

Minneapolis, Minn. 55401 • (612)338-8461

ELECTRONIC DISTRIBUTORS • 11324 Fern St. • Wheaton, Md. 20902 • (301)949-2262

ELECTRONIC DISTRIBUTORS • 1960 Peck St. • Muskegon, Mich. 49441 • (616)726-3196

MADISON ELECTRONICS SUPPLY • 1508 McKinney Ave. • Houston, Texas 77002 • (713) 224-2668

WORLD RADIO • 3415 W. Broadway • Council Bluffs, Iowa 51501 • (712)328-1851

plain talk about repeater problems

Intermodulation
and desensitization
are the two most
serious problems faced
by repeater users —
here is a discussion
of some solutions

Vern Epp, VE7ABK, 203 View Street, Nelson, British Columbia, Canada

There are presently over 300 vhf amateur repeaters in use in the USA and Canada. Although a number of articles have been written on the subject, very little has been published about some of the problems. Basically, a repeater receives a signal on one frequency and transmits it on another. A carrier-operated relay is normally used to turn on the transmitter with an incoming signal. One of the biggest repeater problems is desensitization intermodulation and transmitter noise in the receiver. With proper design this problem can be alleviated.

The transmitter interferes with the receiver in two ways. First, the high signal power overdrives the grids of the receiver rf mixer or i-f tubes and causes grid current to flow. This grid current produces bias voltages which reduce receiver gain; this is desensitization. Secondly, the output of the transmitter consists of a carrier, sidebands and noise. Since the noise spreads to either side of the carrier, a portion of this noise spectrum falls on the receiver frequency, causing further receiving problems.

For successful operation, the following items must be kept in mind when designing a repeater: frequency spacing, antenna separation and transmitter power.

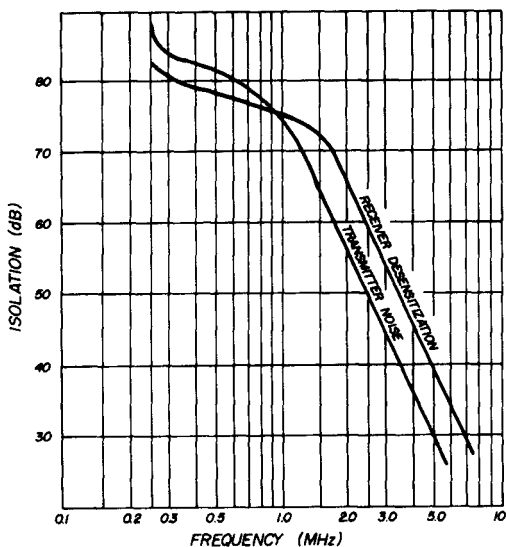


fig. 1. Isolation between transmitter and receiver to protect the receiver from transmitter noise and desensitization.

ceiver desensitization. With very little separation, the effect of transmitter noise is predominant. At greater frequency separations, the effect of receiver desensitization becomes greater (fig. 1).

It is generally agreed that the minimum frequency spacing should be 550 kHz if equipment is physically in one location and two antennas are used. The most common amateur repeater receives on 146.34 MHz and transmits on 146.94 MHz, a separation of 600 kHz. An even larger frequency separation is desirable to reduce the problems discussed.

antenna separation

Antenna separation is a very important factor. Most repeaters use vertical polarization since the mobile stations use vertical antennas. One solution to this problem is shown in fig. 2A where the transmit and receive antennas are physically remote from each other. An inter-

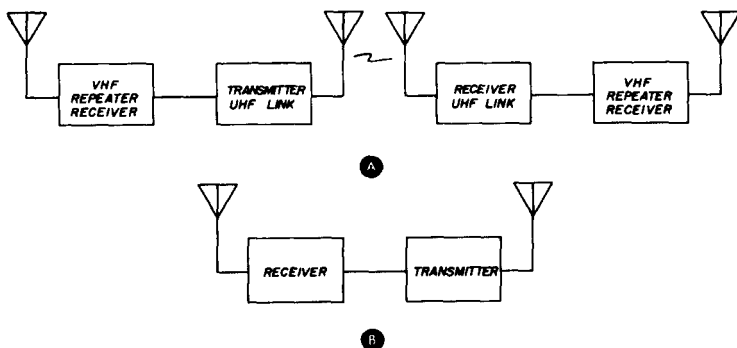


fig. 2. Use of separate antennas for transmitter and receiver.

frequency spacing

The closer the frequency of the transmitter is to the receiver, the more severe the effects of transmitter noise and re-

ceiving link on 220 or 450 MHz connects the units together. This system is expensive but antenna isolation is nearly ideal.

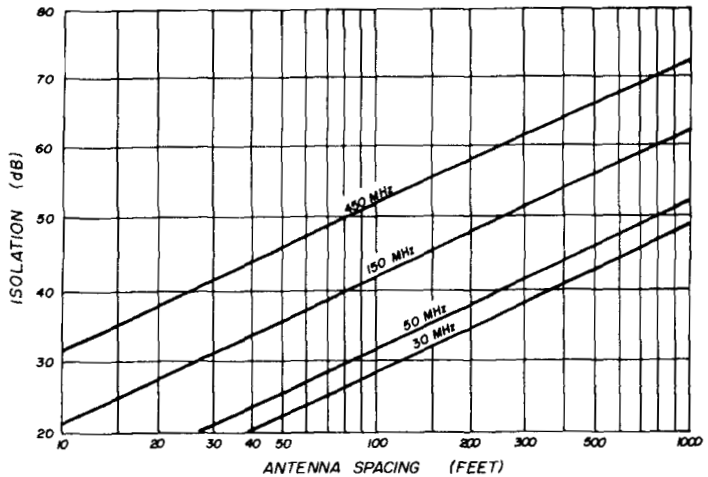


fig. 3. Attenuation provided by horizontal separation of dipole antennas.

The more common, less expensive method uses one location (fig. 2B). The antennas are separated vertically or horizontally from each other. Figs. 3 and 4 show relative attenuation using vertical or horizontal separation. Vertical separation provides better isolation and is recommended for repeater operation. The top antenna is normally used for receiving while the lower one is used for transmitting.

transmit power

Interference problems increase as the power is increased. Most repeaters oper-

ate in the 25 to 50 watt range since mobiles use about the same power outputs. There is no point in running high power unless the mobile and base stations are also high powered. Obviously, a repeater gains little with a transmit range that is much greater than its received range.

cavity filters

Cavity filters are excellent devices for reducing interference problems. Loops are used to insert and extract energy from the cavity. The degree of coupling can be controlled by rotating the loops; this

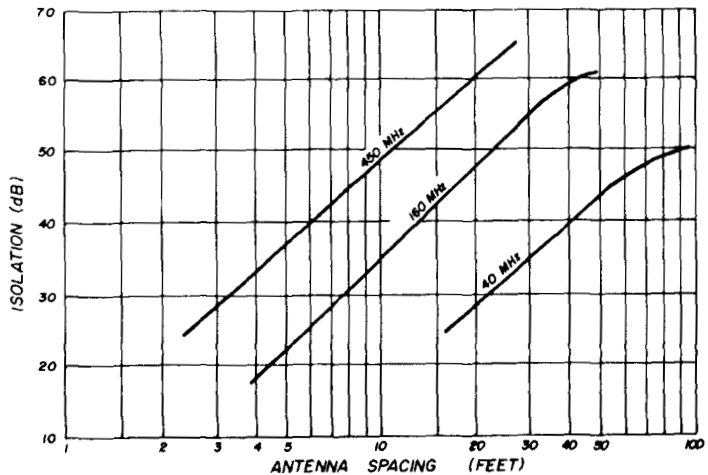


fig. 4. Attenuation provided by vertical separation of dipole antennas.

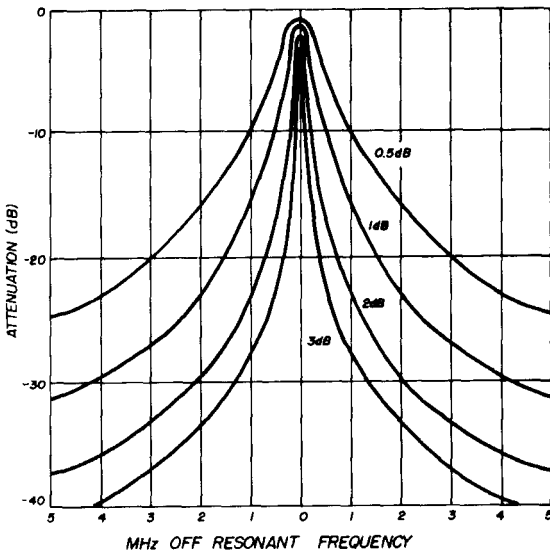


fig. 5. Selectivity curve for Decibel Products DB-4001 single cavity.

determines cavity insertion loss and selectivity. The more selective the cavity, the higher the insertion loss.

When a bandpass cavity is installed in the output of a transmitter it will pass the carrier and sidebands and attenuate nearly all other frequencies. The amount of attenuation depends on the frequency spacing between the undesired frequency

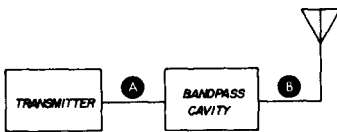


fig. 6. Using a bandpass cavity with a transmitter. Cable length A should be an odd multiple of a quarter wavelength.

and the carrier frequency. A typical bandpass cavity frequency vs attenuation curve is shown in fig. 5, and a typical application is shown in fig. 6.

The cavity presents an impedance of approximately 50 ohms at resonance but the off-resonance impedance of the cavity loop is very low. This makes coaxial cable length (A in fig. 6) very important. If the electrical length between the cavity loop

and the transmitter output circuit is any multiple of a half wavelength, the cavity, if not tuned to resonance, will present a short circuit to the transmitter.

To remedy this, cable length should be an odd multiple of a quarter-wavelength. The transmitter will then see a high impedance when the cavity is off resonance, and danger of transmitter damage is much smaller. Cable length B in fig. 6 is not critical.

bandpass cavities in receivers

Fig. 7 shows a cavity installed between the antenna and receiver. Coaxial cable length is not critical. The frontend selectivity of the receiver is improved by rejection of off-frequency signals that would otherwise desensitize the receiver or cause intermodulation interference. If greater selectivity is required, two or more cavities can be connected in series.

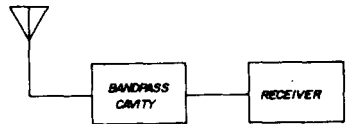


fig. 7. Using a bandpass cavity with a receiver.

checking for interference

1. Switch on the transmitter while receiving a weak signal and watch the limiter current. If it decreases, the receiver is being desensitized. Try additional attenuation in the receiver by adding a cavity.

2. With no signal input, switch on the transmitter. If limiter current increases, transmitter noise is being received. Try additional attenuation in transmitter by adding a cavity.

other items to consider

The coax cables between transmit and receive antennas should never be run together physically. The shielding of RG-8/U, for example, is only about 80%

efficient, and some coupling will result. Also, the transmitter and receiver should be physically separated in the mounting bay. Both units should be well grounded and may require shielding if a problem exists locally and not by the antennas.

Another good method of reducing receiver desensitization was described by W5KPZ.¹ He places a crystal across the antenna coil of the receiver. The crystal is an overtone type that is resonant at the frequency of the interfering signal (fig. 8).

duplexers

A duplexer is used to permit operation of a transmitter and receiver on one antenna. It uses a number of resonant cavities to provide sufficient isolation between units. At close frequency spacings duplexer adjustment is very critical to obtain sufficient isolation. Duplexers for close spacing (0.5 to 1 MHz) commercially cost anywhere from \$500 to \$1000.

rf interference

Rf interference is occurring more frequently since the frequency spectrum is becoming more and more crowded. Many mountain-top sites have many repeaters located near each other and using the same power levels. As a result many interference problems exist.

Rf interference can be defined as, "rf power which interferes with the reception of the desired signal thus causing reduced intelligibility." Receiver selectivity is of the utmost importance since an off-frequency signal can enter the front end of a receiver even though it is rejected later by i-f selectivity. A number of problems can occur, including desensitization, intermodulation and receiver spurious response. Most commercial manufacturers use high-Q rf filters to obtain better rf selectivity.

intermodulation

Intermodulation products (IM) are generated when two or more frequencies are mixed. They can occur in the transmitter, usually in the power amplifier

table 1. Calculating intermodulation products.

Order	Formulas for Calculating Possible Intermodulation Products
2nd	$A \pm B$
3rd	$A \pm 2B, 2A \pm B$
4th	$A \pm 3B, 2A \pm 2B, 3A \pm B$
5th	$A \pm 4B, 2A \pm 3B, 3A \pm 2B, 4A \pm B$

stage, or in the receiver, usually at the first converter. IM products can be reduced by using bandpass or band-reject cavity filters that are tuned to the interfering signal.

Table 1 shows the new frequencies which can be produced by intermodulation. The third- and fifth-order products are the ones most likely to cause trouble. And, when a number of transmitters are

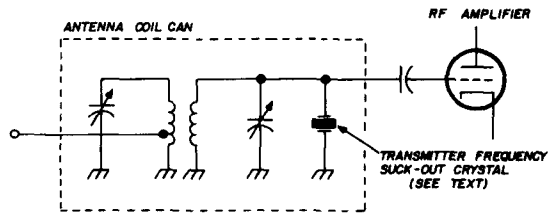


fig. 8. Installation of a suck-out crystal to reduce receiver interference. Crystal is same frequency as that of the interfering signal.

located in the same general location, the IM problem becomes very difficult and complex.

spurious responses

Spurious receiver responses fall into three general categories, i-f response, local-oscillator spurious response and image response.

1. I-f response results when interference at the i-f frequency enters the receiver.

2. Local oscillator spurious response occurs when an off-frequency signal enters the receiver and mixes with a harmonic of the local oscillator to produce an i-f frequency.

3. Image response; the image is twice the i-f frequency plus or minus the desired signal (depending on whether the local oscillator is above or below the incoming signal).

spurious radiation

Transmitters can cause interference to nearby receivers even if it is within the FCC or DOT requirements of 60 or 70 dB down. Interference can come from several sources, including the spurious of a transmitter crystal oscillator, second and third harmonics of the operating frequency, or from the 150-MHz energy in the tripler stage of a 450-MHz transmitter.

intermodulation tests


transmitters If a receiver is interfered with when two transmitters are on the air, place a pad between one of the transmitters and the antenna. If the interference level decreases by twice the dB value of the pad, the undesirable frequency mix is taking place in the transmitter with the pad. This is because the signal from the second transmitter is attenuated on entering the first transmitter, and the intermodulation products are attenuated on the way out. If the intermodulation is taking place in the transmitter without the pad, the interfering signal will be reduced only by the dB value of the attenuator.

receivers If intermodulation is suspected in a receiver, install an attenuation pad in the receiver antenna circuit. For each dB of attenuation in the pad, 3rd order products will be reduced by 3 dB, and fifth-order products by 5 dB. If the interfering signal is generated outside the receiver it will be reduced by the value of the pad.

references

1. D. Baxter, W5KPZ, and J. Douglas, W50BV, "Two-Meter Repeater," 73, September, 1966, p. 58.
2. R. C. Trott, "Considerations in the Use of Cavities and Duplexers," Decibel Products, Inc., Dallas, Texas.
3. General Electric Datafile bulletins 10002-2, 10007-2 and 10007-4.

ham radio

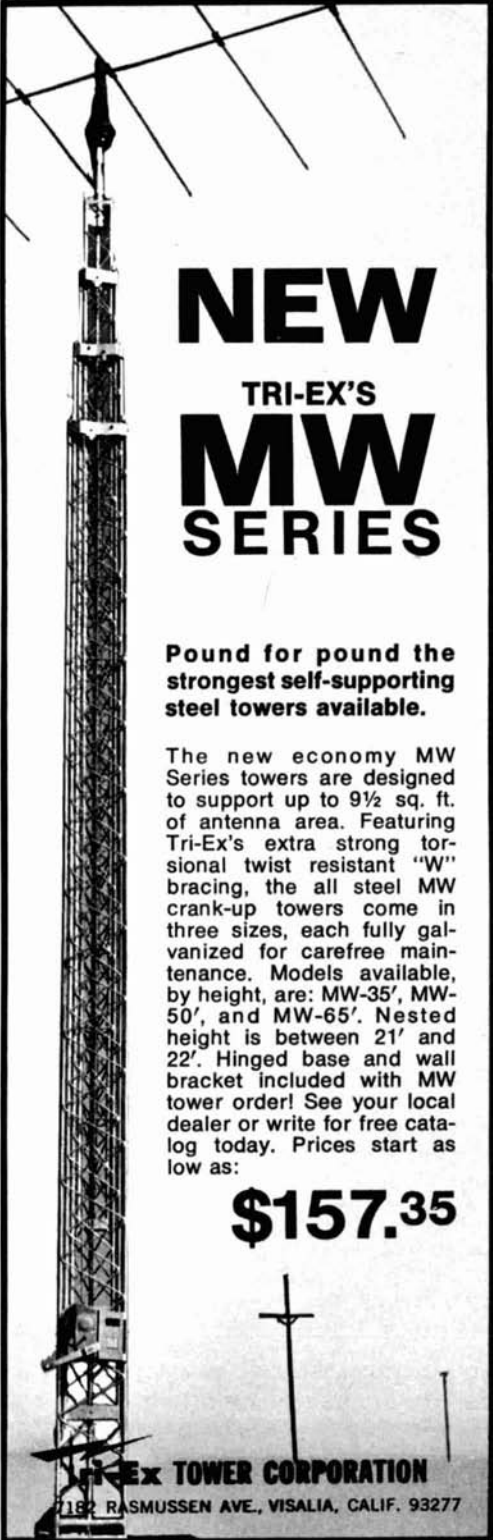

NEW

TRI-EX'S

MW

SERIES

Pound for pound the strongest self-supporting steel towers available.

The new economy MW Series towers are designed to support up to 9½ sq. ft. of antenna area. Featuring Tri-Ex's extra strong torsional twist resistant "W" bracing, the all steel MW crank-up towers come in three sizes, each fully galvanized for carefree maintenance. Models available, by height, are: MW-35', MW-50', and MW-65'. Nested height is between 21' and 22'. Hinged base and wall bracket included with MW tower order! See your local dealer or write for free catalog today. Prices start as low as:

\$157.35

Tri-Ex TOWER CORPORATION
182 RASMUSSEN AVE., VISALIA, CALIF. 93277

the cordover audio-oscillator module

Introducing
a completely assembled
circuit board
that has many
amateur applications —
for less than
a dollar!

J. A. Houser, WB2GQY, 23 Washington Street, Rensselaer, New York 12144

The circuit shown in fig. 1 is undoubtedly one of the best bargains available when one considers the many uses to which it can be adapted.

Known as the Cordover module,* the circuit is designed as an audio oscillator. A pnp low-power audio driver is coupled to an npn 5-watt output stage. The only other parts of the complete module are a 33k resistor and a .02 μ F capacitor. As no heat sink is provided, full power can't be obtained without ruining the output transistor. An advantage (or disadvantage, depending on how you look at it) is that the module is designed to work directly into the voice coil of any speaker from 3 to 16 ohms without a matching transformer. Only 3 volts (two size D cells) are needed for efficient operation. Terminals are provided for an on/off switch or key. The circuit will switch with a bug set at its fastest speed.

Audio output is sufficient for most applications; but if greater output is desired, 6 volts may be used at considerably greater battery drain and consequent shorter battery life. I measured the current at 3 volts, and it varies between 50-60 mA over the whole audio range of oscillation. Dc input measures 0.18 watt.

*Available from Allied Radio Shack, bubble-packed with instructions, for 98¢. Listed in their 1971 catalog as no. 20-1155.

The efficiency seems to be close to 50% with just under 100 mW output available.


changing audio frequency

Because many beginning hams or experimenters may not have an audio generator to calibrate the module, and may

spot-frequency applications

Table 2 shows the effect of changing the value of the resistor supplied with the module. Various values of resistance were connected in parallel with the 33k unit. The data in the table was obtained with a .25 μF capacitor in the circuit, which

fig. 1. Schematic of the bargain audio oscillator module. Unit comes completely assembled and wired, ready for numerous amateur applications.

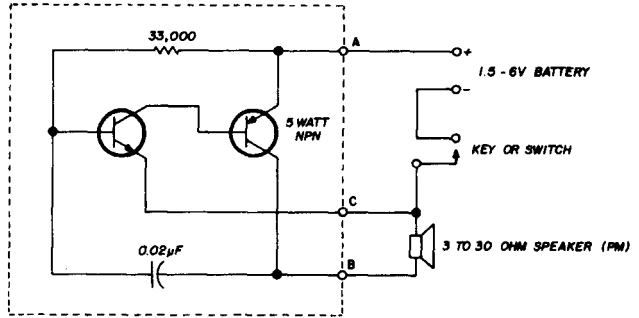

desire to use it at a frequency other than that at which it's set, I made up table 1 so anyone may choose the desired frequency and substitute the designated capacitor for the one supplied. The tone will be within a few Hz of that specified in the table, allowing for variation in transistors and components. Although specifications mention 1000 Hz (as supplied with the .02- μF capacitor installed), I measured 960 Hz on all modules tested, which seems close enough.

ssb testing

I use these modules for tone-testing an ssb transmitter. Two are used for a 2-tone test at full modulation. (An article is in preparation on this use of the module.) Although the observed audio waveform is closer to a square wave than a sine wave, no difficulty was encountered in evaluating ssb transmitter performance.

other uses

The module can be used as part of an off-the-air monitor;¹ as the subcarrier source for a voice scrambler;² and, with an integrator circuit, as a pulse timing source.

produced the basic (nominal) frequency of 250 Hz. This experiment was made to show how the basic module frequency can be changed by a few Hz to hit a spot frequency between those afforded by various capacitor changes. Five-percent-

table 1. Module frequency as a function of capacitor value. Capacitors shown were substituted for the .02 μF unit supplied with the module. Measurements were taken with 3 Vdc at 50-60 mA.

Capacitor Value (μF)	Measured Frequency (Hz)
40 (electrolytic)	.5
10 (electrolytic)	10
.5	160-170*
.25	280*
.1	400-450*
.05	690
.02	890-960
.01	1440
.005	2800-2900 (harmonic 5700)**
.0025	4400 (harmonic 14,000)**
.001	7000***

* varied with capacitor tolerance.

** harmonic as strong as fundamental.

***out of hearing range but strong.

table 2. Module frequency change as a function of resistor value. Value shown in first column was connected in parallel with the 33k unit supplied.

Resistance (kilohms)	Observed Frequency Increase (Hz)	Measured Frequency (Hz)
1000	5	255
560	10	260
330	15	265
180	25	275
100	50	300
56	105	355
33	175	425

tolerance resistors were used, so a deviation may be found in the numbers given if you use resistors with different tolerances. The frequency can deviate from 1 Hz with a 1 megohm resistor to perhaps 5 Hz with 33k.

harmonic output

Unless the module is fully loaded with a speaker, harmonics and subharmonics can develop at the higher-frequency ranges. This condition can be detected by an increase in current from the nominal (50-60 mA) to 90-100 mA. I ran into this problem when using matching transformers as loads when the transformers were not sufficiently loaded to reflect a low (3-30 ohm) impedance to the transistor output.

fm applications

The information in the paragraphs above suggests the possibility of using these modules for tone-frequency-controlled keyers to actuate two-way frequency-shift mechanisms in certain fm transmitters. Another possibility is their use as function (tone) controls to actuate fm repeater transmitters.

In tests, the Cordover module frequencies were as stable as those obtained in touch-tone telephones. With a little juggling of components, exact zero-beats to these frequencies could be obtained.

No frequency shift was noticeable in any of the ranges when fresh batteries were used. As a matter of fact, fre-

quencies were so stable it occurred to me that eleven of these little modules might be used to construct an inexpensive electronic organ. If more than 1 octave were desired, the modules could be followed with one or more "times two" ICs. The keyboard would probably cost more than the electronics.

Just one of these modules furnishes an excellent audio source for testing mono or stereo amplifiers, from the pickup right through the speakers; PA amplifiers ditto — from microphone or phono input to speakers. An inexpensive 6-ohm to high-impedance miniature transformer comes in handy in such applications.


For 98¢, the Cordover audio oscillator module is hard to beat.

references

1. J. A. Houser, WB2GQY, "A CW Monitor," 73, March, 1970, page 76.

2. J. Pina, "A Subcarrier Source for a Voice Scrambler," *Popular Electronics*, March, 1970, page 42.

ham radio

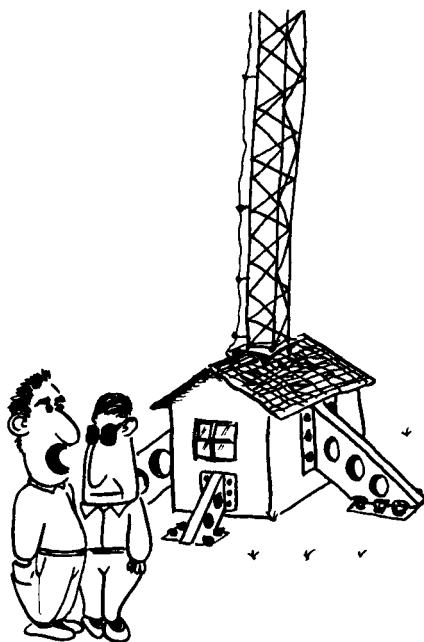

Yeah — the QTH used to rotate about 20° until I put in the shack clamps!

in
1931



SW-3

Way back in 1931, when the Model A was in its heyday, the SW-3 was the amateur's vehicle in the communications field. The SW-3, the receiver that started nine out of ten old-timers in amateur radio, pioneered the SW series, which was soon followed by the NC and HRO series. Each of these famous series found favor with the knowledgeable amateur, and achieved a world-wide reputation for excellence. In keeping with the modern amateur's spirit of adventure, NRCI is now leading the field with the already world-famous HRO-500. As to the future . . . we'll keep you posted!



NCX-1000, the transceiver of the 70's, is NRCI's latest product for the amateur. It is NRCI's answer to an engineering challenge to combine in a single package: a solid-state receiver of unparalleled performance, an exciter of exceptional capability, an outstanding linear amplifier, and a superior power supply. The challenge has been met head-on, with a top-performance, high-reliability, amateur radio station.

CHECK THESE OUTSTANDING FEATURES:

- solid state except for driver and linear amplifier
- five bands -- 80 through 10 meters
- SSB-CW-AM, with FSK capability and selectable sideband
- rugged 8122 final amplifier for ultimate in efficiency and reliability (400W plate dissipation)
- modular construction
- 1000 watts PEP output on SSB, 1000 watts CW (normal duty cycle), and 500 watts AM or FSK
- rf speech processor for effective 2 KW PEP talking power
- built-in 117/234 VAC power supply

The NCX-1000 is the one transceiver that offers, in a single desk-top equipment, a high-performance, one-kilowatt, amateur station.

In 1971, as in 1931, NRCI is providing you, the radio amateur, with the best gear on the market in its price range. NRCI salutes your many contributions to the field of communications. We invite you to stop by today to

in
1971



NCX-1000

AMATEUR NET \$839.95

see and perhaps operate the NCX-1000 at your local distributor. He is one of the best friends you have.

NATIONAL RADIO COMPANY, INC.

37 WASHINGTON STREET, MELROSE, MASSACHUSETTS 02176



R S G B



RADIO COMMUNICATION HANDBOOK

\$12.95 postpaid

amateur radio's most
complete handbook — the one that
sets the standards for all the others.

Complete Chapters On . . .

Basic Principles
Tubes
Semiconductors
HF Receivers
VHF & UHF Receivers
HF Transmitters
Power Supplies
Keying & Break-in
Modulation Systems
Single Sideband

RTTY
Propagation
HF Antennas
VHF & UHF Antennas
Noise
Mobile Equipment
VHF & UHF Transmitters
Interference
Measurements
Operating Techniques

832 pages — Beautifully hardbound

NEW!
3rd EDITION

AMATEUR RADIO TECHNIQUES

J. Pat Hawker, G3VA

Do you have the time to review all the dozens of amateur and commercial magazines which are brought out each month to collect the best of their many good new ideas.


Here it has already been done for you in this very complete collection of material taken from a number of periodicals. It is presented in a most useful and well organized manner.

Chapter headings include Semi-conductors, Receivers, Transmitters, Oscillators, Antennas, Power Supplies and Test Equipment.

Over 200 pages ONLY \$3.75

COMTEC BOOKS • BOX 59

PUBLICATIONS

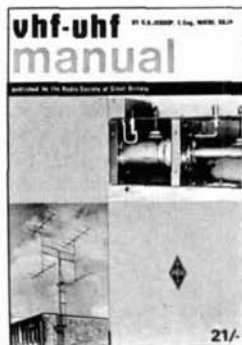

VHF - UHF MANUAL G. R. Jessop, G6JP

If you have any interest in the frequencies above 30 MHz then you need this book. It is probably the most comprehensive work of its kind ever produced. Included is simple material for the beginner in VHF and advanced material to satisfy the most experienced and critical reader. A wide range of information is included covering such topics as propagation, tuned circuits, mobile equipment, single side-band and antennas. There are 62 pages devoted exclusively to receivers and 58 pages to transmitters. This book has set a high standard in this field for a long time to come.

ONLY \$4.00 POSTPAID

RADIO DATA REFERENCE BOOK

G. R. Jessop, G6JP

Here in a 148 page book is one of the most complete compilations of radio and electronic charts, nomographs, formulas and design data available anywhere. Included are sections on General Formulas, Pi-Network Design, Wideband Couplers, TVI Filters, Baluns, Antenna Design Charts, Coil Design, Frequency Allocations and much much more.

Here is a book that will probably pay for itself the first time you use it. Whether you design, build or operate, this volume definitely belongs very close to your workbench or operating table.

148 pages Hardbound

ONLY \$3.00 POSTPAID

AMATEUR RADIO CIRCUITS BOOK

G. R. Jessop, G6JP

Have you ever spent half an hour or so going through all kinds of literature looking for a good basic amplifier or oscillator to put into that new design of yours? In this collection you will find several examples (using both semi-conductors and vacuum tubes) of each type of circuit you might need.

Typical headings include Antenna Matching, T-R Switches, Preamplifiers, Converters, I.F. Stages, Noise Limiters and Blankers, Power Amplifiers, Linear Amplifiers, Audio Amplifiers, Keyers, Oscillators, Power Supplies, Test Equipment and many more.

All of this is offered in a rugged little book which has a spiral binding permitting it to lie flat while being used.

120 pages

ONLY \$2.50 POSTPAID

RADIO COMMUNICATION & RSGB MEMBERSHIP

This is the oldest and most widely read British amateur radio magazine. Published monthly it provides complete coverage including such popular features as: Technical Topics, a monthly survey of the latest ideas and circuits, Four Meters and Down, a run-down of the latest in VHF and UHF and much more.

It includes numerous technical and construction articles in addition to a complete run-down on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$9.60 a year.

\$9.60 per year

2 • AMHERST, N. H. 03031

rating tubes

for linear amplifier service

Peak envelope power
and
intermodulation
distortion

are important parameters
when selecting tubes
for linear amplifiers —
here's what they mean
and how they are measured

The power-handling capability of a given tube in single-sideband service depends upon the nature of the signal being transmitted and the tube's power dissipating capability. The method of establishing single-sideband service ratings should be such that relatively simple test equipment can be used to determine whether or not a tube is operating within its maximum ratings.

It is impractical to establish a rating based on voice-signal modulation because of the irregular waveforms and the varying ratios of peak-to-average signal power found in different voices. The most convenient rating method, and probably most practical, uses a single-tone audio signal to modulate the ssb transmitter. By using this test signal at its full modulation capability, the amplifier will operate under steady, maximum-signal conditions which are easily duplicated and observed.

When a single sine-wave tone modulates a single-sideband transmitter the rf output appears as a steady, unmodulated signal on an oscilloscope (see fig. 1A). This is because the output is a continuous signal having a frequency removed from that of the carrier by the modulating frequency, as shown in fig. 1B.

two-tone tests

Consequently, the operation of a linear amplifier under single-tone modulation is comparable to that of a cw transmitter under key-down conditions. As such, the performance of the power-amplifier stage at maximum signal (or peak) conditions can be determined from meter readings. However, this simple test lacks information on the linearity of the

Robert I. Sutherland, W6UOV, William I. Orr, W6SAI, Eimac division of Varian


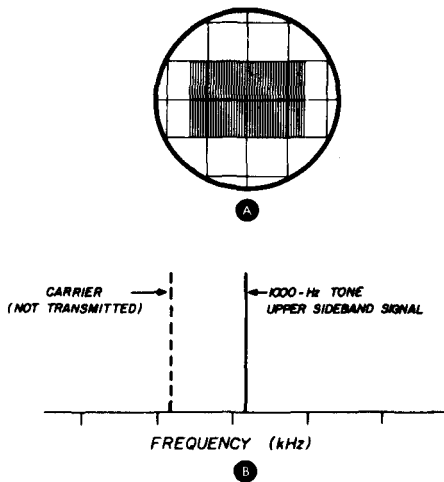


fig. 1. Rf output of ssb transmitter with single-tone modulation. Oscilloscope pattern is shown in A; spectrum is shown in B.

stage. To study linearity by observing amplifier output, some means must be provided to vary the output signal level from zero to maximum with a regular pattern that can be easily interpreted. A simple means is to use two equal-amplitude audio tones to modulate the ssb transmitter. This is termed a *two-tone* test. With this procedure the transmitter emits two steady signals separated by the frequency difference of the audio tones (fig. 2).

In some ssb generators, the two-tone signal is obtained by impressing a single tone at the audio input and injecting the carrier (by unbalancing the balanced modulator) to provide the second equal amplitude rf signal (fig. 3). The resultant beat between the two rf signals produces

fig. 2. Spectrum of ssb transmitter modulated by a two-tone test signal containing 400- and 2500-Hz tones and transmitting upper sideband.

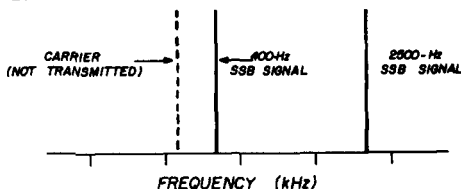

a scope pattern which has the appearance of a carrier 100 per cent amplitude-modulated by a series of half sine waves as shown in fig. 4.

When using the two-tone technique to measure the distortion of a linear rf amplifier it is sometimes more expedient to use two rf signal sources (separated in frequency by the desired number of cycles) and to combine them in a manner which will minimize the interaction between them. The two rf signals represent the two equivalent sideband frequencies generated by the two-audio-tone system and produce exactly the same scope pattern.

A linear amplifier is usually rated at peak envelope input or output power level. *Peak envelope power* (PEP) is the root-mean-square (rms) power generated at the peak of the modulation envelope. With two-tone or single-tone test signals the approximate relationships between single- and two-tone meter readings, peak envelope power and average power (class B or AB operation) can be determined from the formulas shown in appendix 1. Although the equations for average power output are different for the two tests, the PEP formulas are identical.

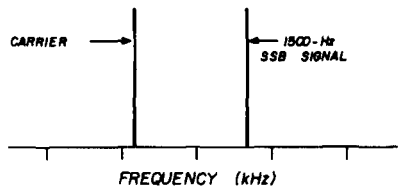


fig. 3. Spectrum of ssb transmitter modulated by 1500-Hz tone and injecting carrier to obtain second rf signal equal in amplitude to the tone.

multitone relationships

The approximate equations given in appendix 1 are for single- and two-tone conditions, the most common test situations. However, in some multi-channel transmitter applications many more tones are used. The following method can be used to determine the peak-envelope-

power to average-power ratio. (For the purposes of this explanation it is assumed that all the tones are equal.)

The following examples demonstrate two important relationships between

one-half that of the single-tone case, so the resultant peak envelope power ratings are identical.*

The two test frequencies (f_1 and f_2) are equal in amplitude but slightly dif-


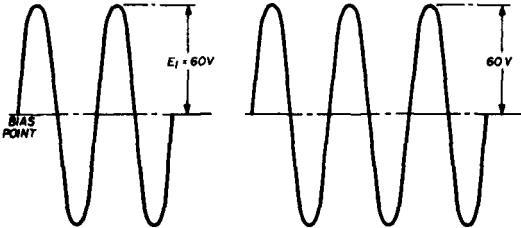


fig. 5. Single-tone condition.

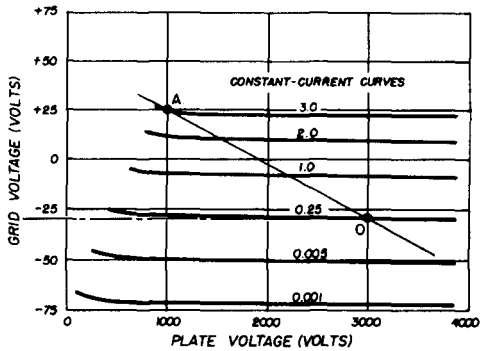

single and multitone signals amplified by a linear system.

Assume the amplifier is set up for a single-tone driving signal and a Point "A" on the operating line is established (see fig. 5). A definite PEP output is developed under this condition. To drive this linear amplifier to the same PEP output with a multitone signal, the drive signal voltage for each tone must be 1/nth (n = number of tones) the amplitude of the single-tone signal.

By assuming a perfectly linear amplifier where the input waveshape is exactly reproduced in the output load, these grid waveshapes can be used to demonstrate the relationship of PEP to Average Power.

For the single-tone case, PEP = Average Power; for the two-tone case, PEP = twice Average Power. However, in the two-tone case the average power is

ferent in frequency. As a result, when they are exactly in phase the two crest voltages add directly to produce the crest of the two-tone envelope. When the two frequencies are exactly out of phase the

*This is best illustrated with two practical examples.

single-tone

$$\text{Average power} = \frac{E_1(\text{rms})^2}{R_L} = \frac{\left(\frac{60}{\sqrt{2}}\right)^2}{R_L} = \frac{1800}{R_L} \text{ W}$$

$$\text{PEP} = \frac{E_1(\text{rms})^2}{R_L} = \frac{\left(\frac{60}{\sqrt{2}}\right)^2}{R_L} = \frac{1800}{R_L} \text{ W}$$

Therefore, PEP = average power


two-tone:

$$\begin{aligned} \text{Average power} &= P_{1\text{avg}} + P_{2\text{avg}} = \frac{E_1(\text{rms})^2}{R_L} + \frac{E_2(\text{rms})^2}{R_L} \\ &= \frac{\left(\frac{30}{\sqrt{2}}\right)^2}{R_L} + \frac{\left(\frac{30}{\sqrt{2}}\right)^2}{R_L} = \frac{450}{R_L} + \frac{450}{R_L} = \frac{900}{R_L} \text{ W} \end{aligned}$$

$$\begin{aligned} \text{PEP} &= \frac{(E_{1\text{rms}} + E_{2\text{rms}})^2}{R_L} = \frac{\left(\frac{30}{\sqrt{2}} + \frac{30}{\sqrt{2}}\right)^2}{R_L} \\ &= \frac{\left(\frac{60}{\sqrt{2}}\right)^2}{R_L} = \frac{1800}{R_L} \text{ W} \end{aligned}$$

Therefore, PEP = 2 x P_{avg}

fig. 4. Scope pattern of ssb transmitter modulated by two-tone test signal.

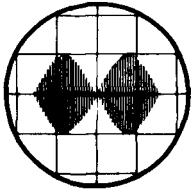

cusps of the two-tone envelope results (see fig. 6).

Note that the voltage amplitude at the crest of the resultant two-tone envelope is equal to that of the single-tone envelope


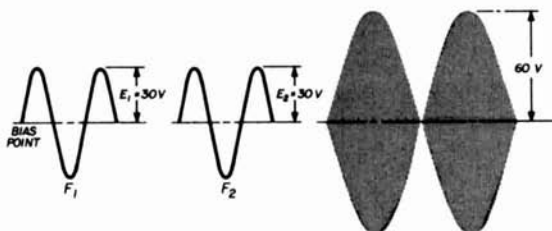


fig. 6. Two-tone condition.

and therefore the tube is driven to the same point on the operating line in each case. If the tube is driven to the same peak plate current and the same peak plate voltage swing by different excitation signals, then the peak envelope power output for both signals is the same.

the single- and two-tone examples.

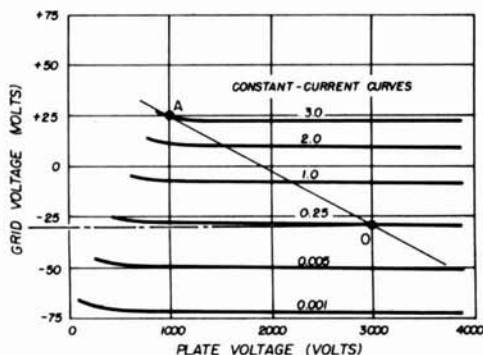These results (equal amplitude tones) may be summarized by the following expressions:



$$PEP = n P_{avg}$$

$$PEP = n^2 P_t$$

Where P_{avg} is the average power of the composite signal, P_t is the average power in each tone, and n is the number of tones.


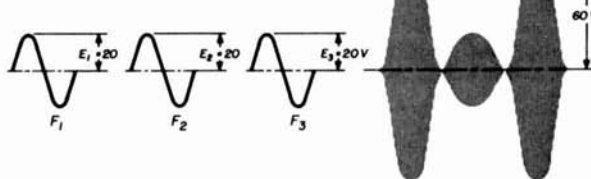


fig. 7. Three-tone condition.

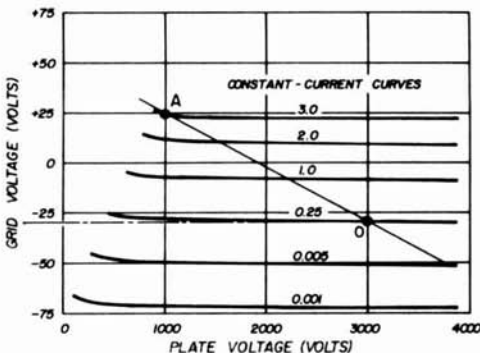The same holds true for a three-tone test signal. Note that the sum of the three individual tone-crest exciting voltages add in phase to drive the tube to the same peak current and peak plate voltage swing as that of the single-tone case (see fig. 7) so the PEP output is the same as




example

An fm repeater is to be designed to simultaneously rebroadcast one to eight channels. Each channel must have an average power output of 100 watts. How much peak envelope power must the linear amplifier deliver?

Each channel can be considered to be a single-tone signal. Therefore, the PEP of each channel is equal to the average power of each channel. The *maximum power output* requirement of the ampli-

Peak envelope power is the root-mean-square power at the crest of the envelope. This term is usually shortened to PEP. Idling plate current determined by the operating point is called the *zero-signal*

fig. 8. Graph showing intermodulation distortion products. As drive is increased, the various IMD products pass through maxima and minima. Misleading conclusions can be drawn if the equipment is tested near a cusp on the IMD curve where a particular IMD product drops to an extremely low level.

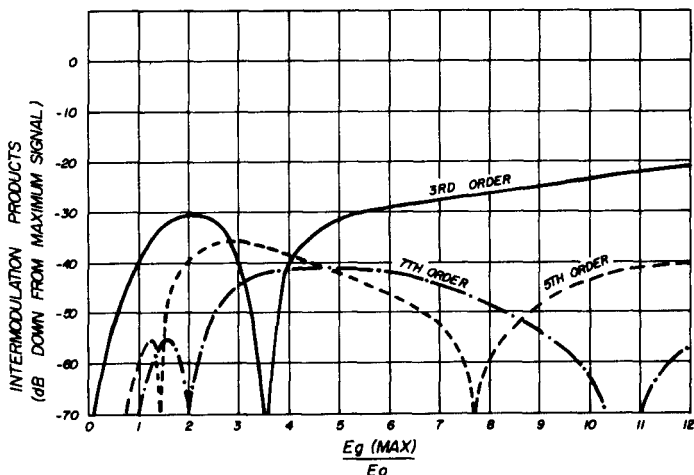

fier will be under the 8-tone condition. The average power output for the composite 8-tone signal will be 8 times the 100 watts-per channel power. Therefore, the linear amplifier must be capable of 800 watts of average power output.

The peak envelope power will be eight times the average power of the composite signal ($PEP = nP_{avg}$) or 6400 watts. A tube must be selected to deliver this peak-envelope and average power at an intermodulation distortion level compatible with the degree of interchannel cross-talk that can be tolerated.

measurement standards

To describe adequately the performance of a tube in single-sideband linear service, it is necessary to determine many parameters. The normal electrode voltages and currents must be specified as well as the two-tone currents, the operating point, peak envelope power and the magnitude of the intermodulation-distortion products. These parameters are defined as follows:

appendix 1

Approximate relationships between meter readings, peak envelope power and average power for class B or AB operation with one- and two-tone tests.

parameter	single-tone	two-tone
dc plate current	$I_b = \frac{I_{pm}}{\pi}$	$I_b = \frac{2I_{pm}}{\pi^2}$
plate input (watts)	$P_{in} = \frac{I_{pm}E_b}{\pi}$	$P_{in} = \frac{2I_{pm}e_p}{\pi^2}$
average output (watts)	$P_o = \frac{I_{pm}e_p}{4}$	$P_o = \frac{I_{pm}e_p}{8}$
PEP (watts)	$P_o = \frac{I_{pm}e_p}{4}$	$P_o = \frac{I_{pm}e_p}{4}$
plate efficiency	$N_p = \frac{\pi e_p}{4E_b}$	$N_p = \left(\frac{\pi}{4}\right)^2 \frac{e_p}{E_b}$

definition of symbols:

I_{pm} = peak of the plate current pulse (plate current pulse is not sinusoidal)

e_p = peak value of plate swing, assumed to be sinusoidal when tank-circuit has sufficiently high Q.

E_b = dc plate supply voltage

plate current and is designed I_{b0} .

The other two plate current values of significance are the *single-tone plate current* and the *two-tone plate current*. The ratio of single- to two-tone current is 1.57:1 in a true class B amplifier (180° plate conduction angle). For other classes of linear operation and for different zero-signal plate currents, this ratio varies from 1.1 to 1.57:1.

The standard method of specifying the magnitude of the distortion products is to specify the reduction in decibels of one product from one tone of a two-equal-tone signal.

For example, assume that a particular tube under a given set of operating conditions has third-order distortion products of -35 dB and fifth-order distortion products of -50 dB. This means that the third-order product has an amplitude of 35 dB below one of the two test tones and the fifth-order product has an amplitude 50 dB below one of the two test tones. (It is also correct to add the amplitudes of the two third-order products and compare them to the *sum* of the two tones. The decibel ratio is still the same as the example.)

It is *not* correct to compare one distortion product to the sum of the two tones; that is to say, the PEP value of the signal. The resulting distortion figure would be 6 dB better than the correct example (-41 dB rather than -35 dB and -56 dB rather than -50 dB).

Normally the tube under test is adjusted to the full drive condition, and all the pertinent parameters are measured. The drive signal is then reduced. At each test point, all the parameters are measured again. The resulting data can then be plotted as a function of drive voltage.

It should be noted that maximum intermodulation distortion does not necessarily occur at maximum drive level, and it can be shown mathematically that an intermodulation characteristic like fig. 8 can be expected. In practice there is very good correlation between mathematical prediction and actual test results.

ham radio


DIODES

400 VOLT PIV @ 1.5A Epoxy	14¢
600 VOLT PIV @ 1.5A Epoxy	16¢
800 VOLT PIV @ 1.5A Epoxy	20¢
1000 VOLT PIV @ 1.5A Epoxy	24¢

CAPACITORS

ALL NEW FULL AXIAL LEADS

1 MFD @ 25 VOLT	5 for \$1.00
3 MFD @ 6 VOLT	5 for \$1.00
5 MFD @ 15 VOLT	5 for \$1.00
10 MFD @ 6 VOLT	5 for \$1.00
30 MFD @ 15 VOLT	5 for \$1.00
80 MFD @ 2.5 VOLT	5 for \$1.00
100 MFD @ 50 VOLT	5 for \$1.00
500 MFD @ 15 VOLT	40¢ ea.
800 MFD @ 20 VOLT	3 for \$1.00
1000 MFD @ 12 VOLT	3 for \$1.00
1000 MFD @ 50 VOLT	2 for \$1.00
1500 MFD @ 25 VOLT	2 for \$1.00
3000 MFD @ 16 VOLT	2 for \$1.00

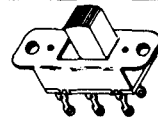

Beautiful American made UL Approved DPDT Slide Switches 3 Amp rating. Your choice Red or Black. 20¢ ea. 6 for \$1.00 ppd USA



6 Foot Gray Line Cord. UL Approved. Very nice. 40¢ ea. ppd

CDE Type WMF Tubular Mylar Capacitors. All 100 Volt.

.033	8¢ ea. 14 for \$1.00
.22	10¢ ea. 12 for \$1.00
1.0	25¢ ea. 5 for \$1.00



2N3055 NPN Silicon Power Transistor \$1.50 ea. 3 for \$4.00

TI 1N914 Silicon Diode 16 for \$1.00

1N4007 1000 V PIV @ 1 A Diode 28¢ ea.


Assorted Carbon Resistors. 1/2-1.2 Watts. 100 for \$3.00

Assorted Silver Mica Capacitors 100 for \$3.00

.001 @ 2 KV Disc Ceramic Capacitors. 20 for \$1.00

SEND STAMP FOR BARGAIN LIST
Pa. Residents add 6% State sales tax
ALL ITEMS PPD. USA

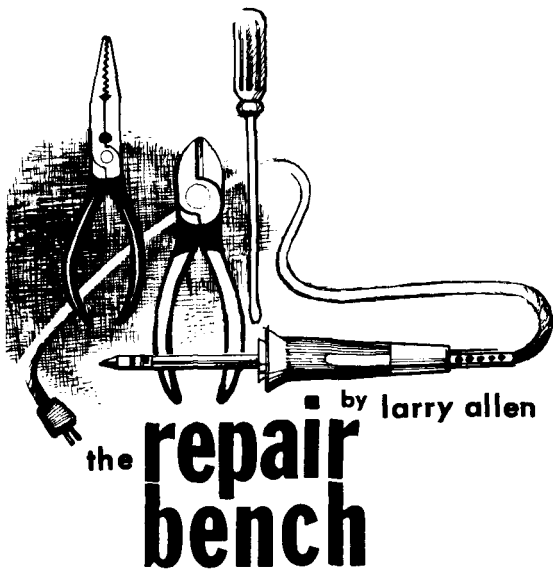M. WEINSCHENKER K3DPJ
BOX 353 · IRWIN, Pa. 15642



sweep response curves for low-frequency i-f's

You've been reminding me. Some months ago I promised to show you how to display a sweep response curve for low-frequency i-f stages. This month, I keep that promise.

As you know, test equipment people have quit making sweep instruments that can be used at 60 kHz, 455 kHz, and other low intermediate frequencies. Electronically-swept rf generators of today have two drawbacks at those frequencies. First, their center frequencies seldom go below 4 MHz. Second, their sweep doesn't swing the frequency wide enough at the low end to reach that far below 4 MHz.

What's worse, not all present-day sweep generators even go down that far. Instead, they're designed exclusively for television sweep alignment. A few include a 10.7-MHz center frequency for sweeping i-f strips in commercial fm receivers.

There is a way you can generate a sweep curve centered on ham i-f frequencies. You can do it with a sweep generator that doesn't go near those low frequencies; all you need is an rf generator to use with the sweep instrument.

The secret, as you may have guessed, is heterodyning. Let's review some of the fundamentals of "beat frequencies" and be sure you understand what's happening in the method I'm about to describe.

one and one make four

If you mix two rf signals together in some kind of nonlinear stage, they beat together in a process known as heterodyning. The output of this nonlinear mixer stage is four signals. Two of them are the same as the original signals, one is the sum of their frequencies, and one is the difference.

For example, suppose you mix a 10-MHz and a 9-MHz signal in the nonlinear mixer stage. The outputs are: 1 MHz (the difference), 9 MHz, 10 MHz, and 19 MHz (the sum). Which output you use depends on your purpose. In a superhet receiver, you might pick the difference — to form an intermediate frequency. In a sideband transmitter, you might pick the sum — the 19-MHz — to raise the signal to a communications frequency.

For the purpose I'm describing in this *repair bench*, you approach this same principle from another direction. What you need to do is convert a high frequency to whatever is used in the i-f stages. To do that, you mix in a signal whose frequency is displaced from the available sweep signal by exactly the i-f.

Let me cite an example. Suppose the sweep signal is at 10 MHz, and the i-f strip you want to sweep operates at 1 MHz. You can mix a plain rf signal of 9 or 11 MHz with the sweep rf signal. Either frequency produces a difference heterodyne of 1 MHz (1000 kHz). They also produce sum heterodynes, but the i-f tuned circuits reject any but the 1-kHz frequency.

heterodyned sweep signals

If you saw my earlier *repair bench* about sweep alignment in ham gear (April, 1970 issue), you know how a sweep signal is made up. It has a center frequency, which is the frequency at which the sweep generator dial is set.

Here's what this means: A sweep signal that is 1 MHz (1000 kHz) wide swings 500 kHz above and 500 kHz below the center frequency. If the center is 10 MHz, the frequency swings from 9.5 MHz to 10.5 MHz, and does it back and forth 60 times every second.

That frequency is swept upward and downward from center. How far up and down depends on the setting of the *Sweep Width* control. The sweep rate of most generators today is 60 times per second.

Modern Sweep and rf equipment, although not really made for low-frequency sweep, can produce it. Chief secret is homemade mixing device in fig. 1, and what you do with the instruments.



Visualize what happens when this same sweep signal is converted to some other frequency. The arithmetic is simple. Imagine it's being heterodyned with an 11-MHz signal. At the instant the sweep signal passes through center frequency at 10 MHz, the difference heterodyne is 1 MHz or 1000 kHz. That's center frequency for the "new" sweep signal. At the instant the sweep signal reaches its bottom frequency, at 9.5 MHz, the difference is 1.5 MHz or 1500 kHz. Then, when the frequency is swept up to its topmost value, at 10.5 MHz, the difference is 0.5 MHz or 500 kHz. So, by mixing a 10-MHz signal, which is swept 500 kHz each way, with a plain unmodulated 11-MHz rf signal, you generate a 1000-kHz signal swept 500 kHz up and 500 kHz down.

The thing about this idea is that you can make the center frequency of the "new" sweep signal whatever you want it to be merely by choosing the unmodulated rf signal you mix with the original sweep signal.

using what you have

You can use almost any sweep generator. Best results come from using the lowest sweep frequency you have available. Just be sure the sweep width is usable.

As it happens, my newest sweep generator is a B&K model 415. It's solid state, and intended primarily for television alignment. I could use a tv i-f sweep frequency, in the 44-MHz range. However, this generator also produces a sweep at 10.7 MHz, for aligning the i-f strips of fm receivers. And there's a nice marker right in the middle — precisely at 10.7 MHz. (More about markers later.) That's lower than the tv sweep frequencies, so I use the 10.7 MHz for heterodyning down to low sweep frequencies.

The source of unmodulated rf at my bench is a new B&K model E-200D. It's a modern version of the Old Precision Apparatus model E-200. Old-timers will remember that once-popular unit. The dial settings are reasonably accurate. But more important, the E-200D is stable once it's warmed up. That's a requirement of whatever generator you use.

The calculations for using this pair of instruments are easy. They apply to any

sweep and rf generators you use. To create the low-frequency sweep I want from the fixed 10.7-MHz sweep signal, I either subtract or add the frequency of the i-f strip I'm checking.

A common i-f is 455 kHz. That's what's in the receiver I'm using for this demonstration. With a 10.7-MHz sweep signal, a 455-kHz beat can be obtained by adding 11.155 MHz or 10.245 MHz. Either one is okay, but I choose 10.245.

device that produces the heterodyning between the two signals.

Of course, you need a scope. Any ordinary servicing scope will do. Mine is a modern wideband scope, but for this purpose yours needn't be.

The model 415 sweep/marker generator uses post-injection for the marker, as most recent instruments do. The block diagram in fig. 2 shows the equipment hookup. Here are the steps:

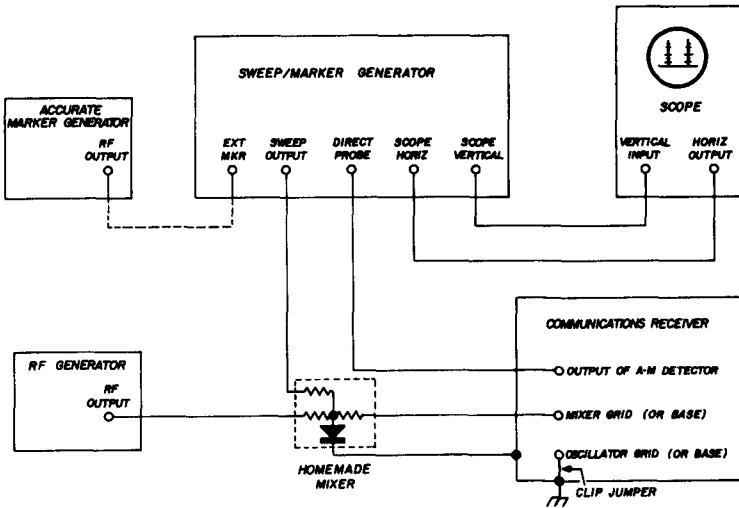


fig. 2. Equipment hookup. It is slightly different if sweep generator doesn't have the post-injection marker arrangement.

If the i-f were 60 kHz, another common one in ham receivers, an rf signal at 10.64 MHz would do the job.

You have to build a little mixer stage yourself. The simple one in fig. 1 is adequate. The diode is the nonlinear

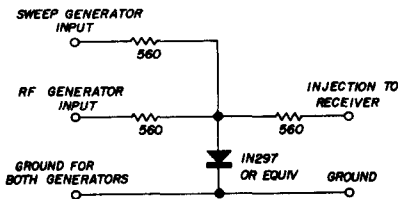


fig. 1. Four parts make up mixing device used for creating low-frequency i-f sweep signal.

1. Let everything warm up at least 15 minutes.
2. Set scope sweep to External Input.
3. Set scope vertical-input attenuator to whatever setting gives a 1-inch deflection for about 5 volts of signal input.
4. Connect scope vertical input to Scope Vertical jack of sweep/marker generator.
5. Connect scope horizontal input to Scope Horizontal jack of sweep/marker generator.
6. Connect rf outputs of the two generators to the inputs of your homemade mixer device. Connect ground cables to receiver chassis.

7. In the receiver, clip the mixer-device diode lead to ground and the output lead to the grid (or base) of the receiver's mixer stage.
8. Clip a shorting jumper from the receiver oscillator grid (or base) to ground (or to emitter), thus disabling the receiver's oscillator.
9. Connect the direct-probe lead from the sweep/marker generator to the output of the receiver's a-m detec-

sweep just right on the scope trace.

Here's how. Leave the rf generator output control at zero for now. Turn the sweep rf output wide open. Set the *Sweep Width* control as low as it goes; it'll still be wide enough for communications receiver i-f coils. Turn up the *Marker Amplitude* control on the generator just slightly.

Now roll the *Center Frequency* dial back and forth until the marker comes

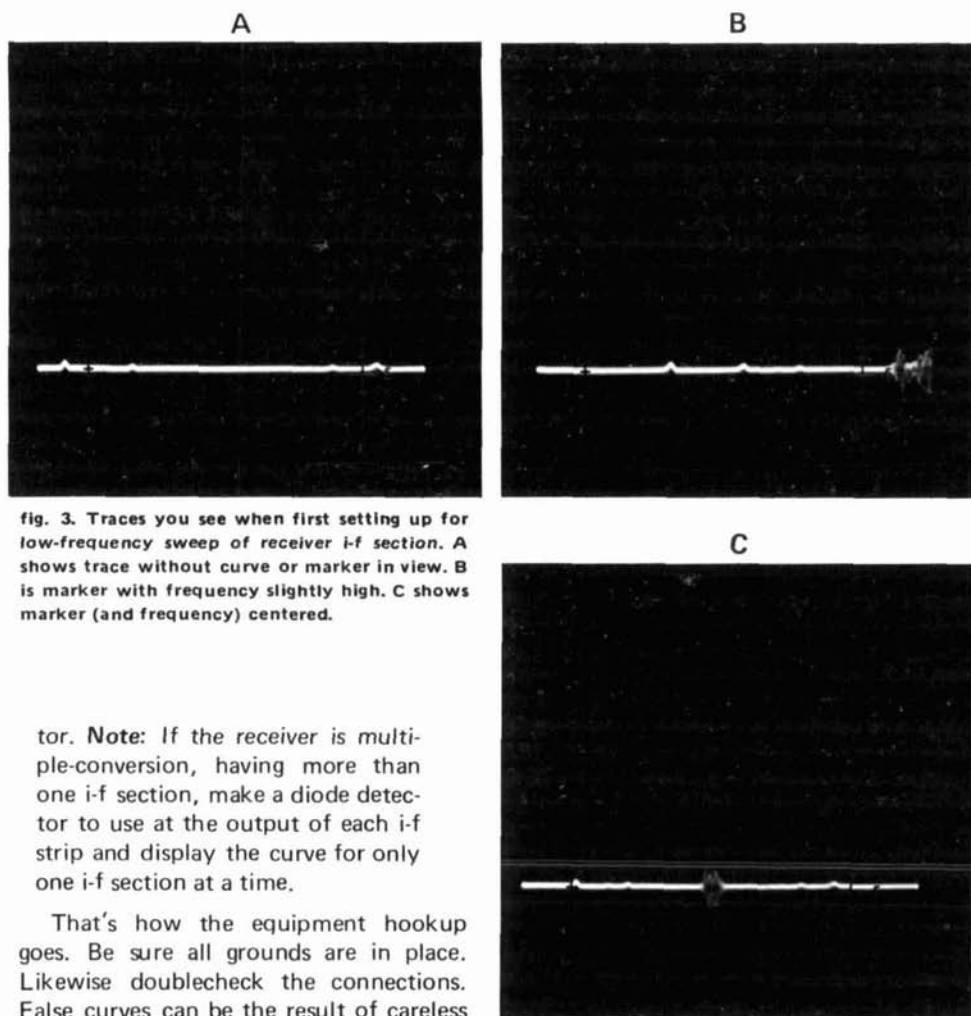


fig. 3. Traces you see when first setting up for low-frequency sweep of receiver i-f section. A shows trace without curve or marker in view. B is marker with frequency slightly high. C shows marker (and frequency) centered.

tor. **Note:** If the receiver is multiple-conversion, having more than one i-f section, make a diode detector to use at the output of each i-f strip and display the curve for only one i-f section at a time.

That's how the equipment hookup goes. Be sure all grounds are in place. Likewise doublecheck the connections. False curves can be the result of careless hooking-up.

getting the curve

The 10.7-MHz sweep in the model 415 has a center-frequency marker. That offers a convenient way of situating the

into view along the scope trace. The photo in fig. 3A shows the trace before you get the center frequency just right. This is sort of a fine-tuning control. Fig. 3B shows the marker just coming into

view. Turn the *Center Frequency* control to put the marker exactly in the center of the scope trace, as in **fig. 3C**.

The object of this step is to put the

rf signal is added.

Now set the frequency dial of the rf generator as near 10.245 MHz as you can. Turn up the output controls. If your

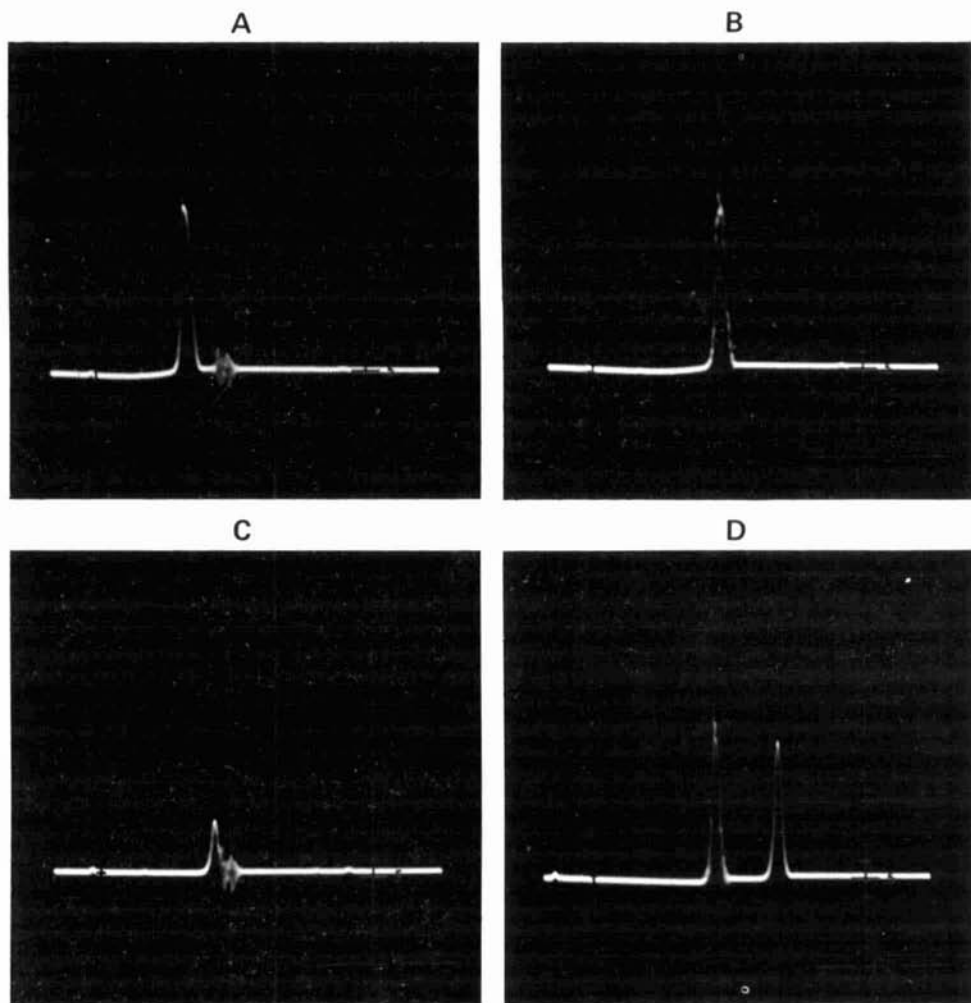


fig. 4. Curve appears when rf generator signal is added. Curve in **A** not exactly at i-f center marker. Curve in **B** moved to coincide with marker by returning i-f coils or rf generator. In **C** some of i-f coils detuned. Two curves in **D** mean the receiver oscillator hasn't been disabled.

marker in a position that enables you to use it as the center of the curve you will presently display. The marker is at 10.7 MHz, but it is added to the scope trace from within the sweep generator. It therefore remains as a center reference for the 455-kHz sweep signal developed when the

hookup is correct and the i-f strip is reasonably normal, you'll see the curve rise somewhere along the scope trace, as in **fig. 4A**. Just how far it is from the center marker depends on how near the rf generator is to 10.245 MHz and how accurately tuned the i-f coils are.

(The ideal is a *calibrated* 10.245-MHz signal, such as from a heterodyne frequency meter that has been checked against WWV. I've used a BC-221 for this, as well as a Lampkin model MFM frequency meter. For this demonstration, I calibrated the vernier of my rf generator against a frequency meter. That way, I know the i-f stages are slightly off-frequency when I see the curve displaced from the marker as it is in **fig 4A**.)

The photo in **fig. 4B** shows the curve right on the marker. You can put it there by adjusting the dial of the rf generator. Since I knew my rf generator was precisely accurate, I readjusted the six i-f coil cores (two per i-f can) to move the curve over to the marker.

The technique is not difficult. I just turn each core a small amount in the same direction, then peak all six at the new position of the curve. The curve in

Be sure the receiver oscillator is cut off. I told you how, in **step 8** of the equipment hookup. Otherwise, you may get the double curve shown in **fig. 4D**. The correct curve is identified by the marker, but it's best not to have the extra curve.

You may wonder how to determine bandwidth. With another generator of high accuracy, you can put a movable marker into the sweep generator through the *External Marker* jack. Record the frequencies when the marker is at the upper skirt (**fig. 5A**) and at the lower skirt (**fig. 5B**). Bandwidth is roughly the difference between them. The two markers in **fig. 5** are at 10.235 and 10.255 MHz. The difference is 20 kHz, the bandwidth at the bottom of the skirts. That means bandwidth at the half-points on the curve is 10-12 kHz. That's not bad for a general-purpose

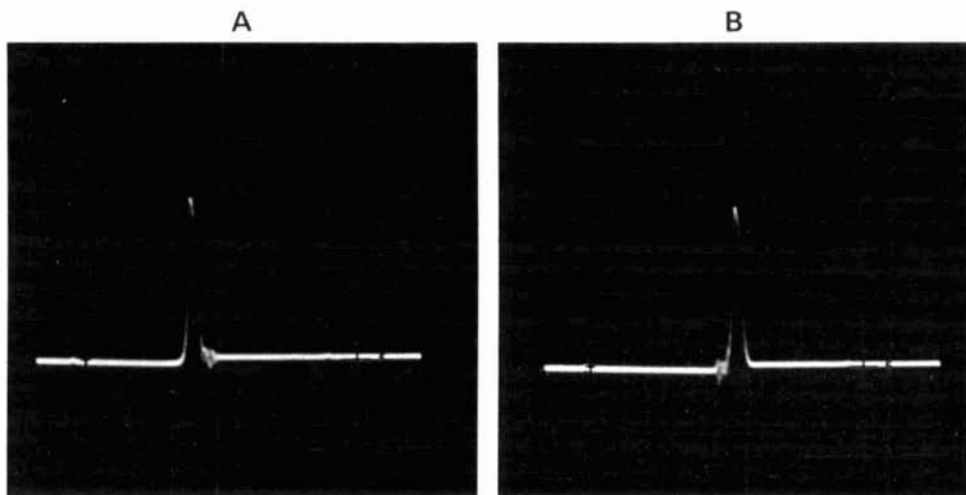


fig. 5. Movable markers show bandwidth in terms of kHz between upper skirt A, and lower skirt, B.

fig. 4B results. The curve in **fig. 4A** was down-frequency from the marker. I therefore backed all six cores out about one-half turn. At first, it looked as though I was destroying the curve. (**Fig. 4C** shows how it looked when only three slugs were turned to the new setting.) But as all six were turned near the new frequency, the curve got tall again.

receiver, but a little wide for a selective communications receiver.


Another way I estimate bandwidth is with the built-in 100-kHz markers that are part of my model 415 sweep generator. **Fig. 6** shows the trace with the 100-kHz markers activated. You may have to increase *Sweep Width* slightly to get both markers on the scope trace.

The 100 kHz beats with the 10.7-MHz marker and puts one at 10.6 and another 10.8 MHz. Converted in the homemade mixer, this means markers at 355 kHz and 555 kHz. Of course the main 10.7-MHz marker still makes the 455-kHz

other uses of sweep curve

You can see the effect of a crystal selectivity filter on the i-f response. Fig. 7A shows the curve with the *Selectivity* switch of the receiver set for *Crystal - Broad*. Turning the *Crystal Phasing*

A

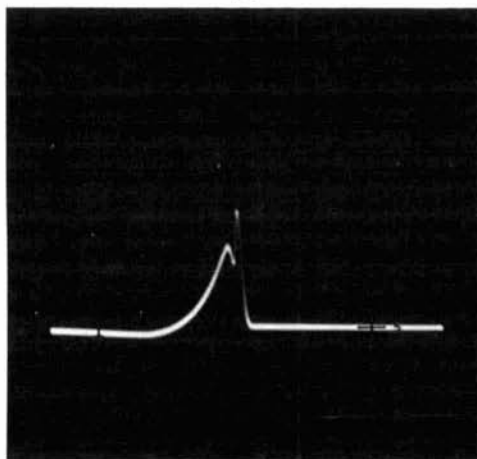

B

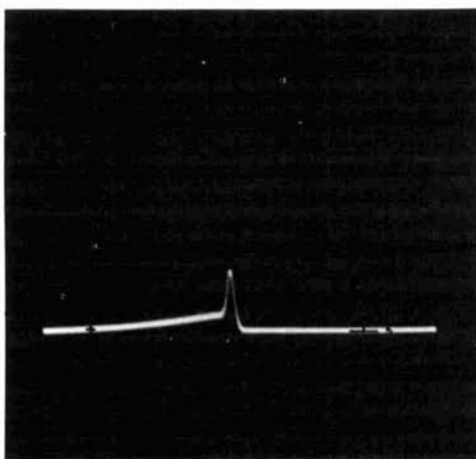


fig. 7. Selectivity switch of receiver changes response of i-f strip, as shown by the curve. Broad response, A, with crystal phasing set at one spot. Sharp crystal position, B, reduces gain but sharpens curve peaking.

center marker. The distance between the two outside markers is 200 kHz. From that you can estimate the bandwidth of the curve being displayed.

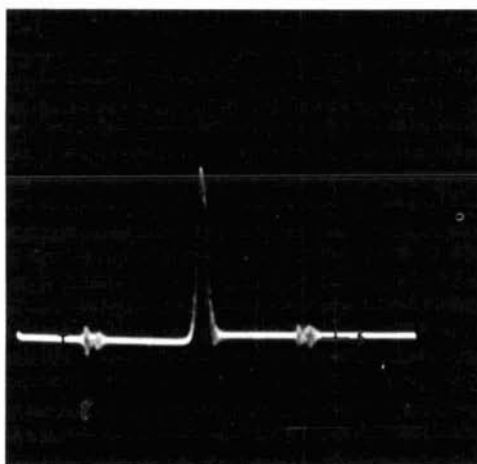


fig. 6. 100-kHz markers on each side of main center marker also can help estimate bandwidth.

capacitor knob changes the curve shape somewhat.

Switching to *Crystal - Sharp* reduces the gain of the i-f strip, but sharpens the curve. You can see the result in fig. 7B. You can alter the *Crystal Phasing* to virtually eliminate the i-f curve.


A sweep curve generated as described here can be used for testing any rf or i-f stages. Without the gain provided by amps in the receiver, you'll need a more sensitive setting of the scope's vertical input. Or, you can build an untuned transistor amp to follow the homemade mixer. That'll give you enough signal to be useful with unamplified tuned circuits. You'll have to add a diode detector for stages that don't end with an a-m detector.

With a little practice and imagination, you can find a lot of other uses for this method of generating a low-frequency sweep signal.

ham radio

TEN-TEC
 SEVIERVILLE, TENNESSEE 37862

TEN-TEC PM2B Transceiver

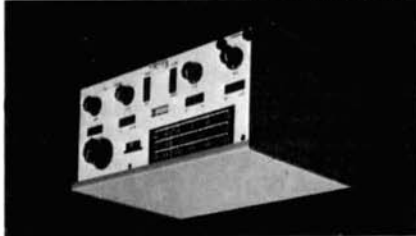

WHAT WE SAY ABOUT OUR MODULES

These modules or a factory built, ready-to-operate Ten-Tec transceiver can be yours at a modest cost. Then, soon, you may be sending us a letter detailing your own amazing QSOs. If your distributor does not stock these units, use the coupon below to order direct from Ten-Tec.

Ten-Tec modules about they're saying


Dear Sirs, I have not often written to manufacturers: however, this time I feel obliged to let you know how pleased I am with your low power building blocks. Several months ago I obtained the AC 3 (15m converter) and basic modules MR 1 (40/80m), the AC 6 (20m transceiver) and built into a small aluminum housing. . . . the result is a thoroughly pleasing piece of equipment, which gave me many hours of fun in the "field". . . . Many QSOs have been made during the summer and fall months and "unbelievable", regularly followed by the question "what antenna do you use?". Obviously the chap on the other end thinks I have some big array and is even more puzzled to hear that I only use a G.P. I worked so far more countries of Europe, several VAs (over 3000KM away) and a 4x4 (all during the daylight hours). Even a Hb9 and a OHM have been worked through some pile-ups! The comments on frequency stability and tone quality are always excellent. To me, the most surprising thing is the sensitivity of the receiver, considering the utmost simplicity of the design: even weak DX stations can be well received. . . . Congratulations and compliments to you for a fine and inexpensive job!


Dr. Gunther Hauenberger, OB1HGW
 Vienna Austria

Name _____
 Address _____
 City _____ State _____ Zip _____

- Satisfaction guaranteed or money back. Dept. FI
- I enclose my personal check money order in full (Tennessee residents add 3% sales tax)
- 64.95 Complete PM2B Transceiver (all modules above) assembled, ready-to-operate.
- 7.95 all bands transceiver operation with side-tone for AC6 Extend MR1 module group to 20 meter
- 7.95 TX1 Crystal oscillator and power amplifier
- 7.95 VO1 40-80 meter oscillator-buffer
- 7.95 A41 IC audio amplifier
- 7.95 MX1 Synchronyne detector-converter
- 37.90 MR1A Module Group (MX1, A41, VO1, TX1, AC6)
- \$29.95 MR1A Module Group (MX1, A41, VO1, TX1)

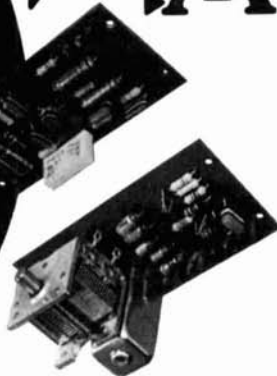Please ship the following, prepaid, immediately:



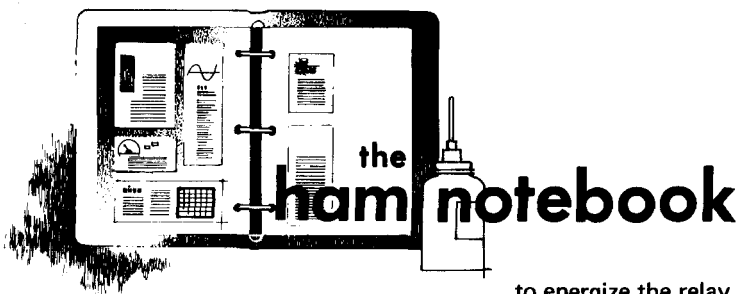

safer suicide cord

Most electronics experimenters have an ac-plug-to-clip-lead adapter (better known as a "suicide cord") on their workbench. Unfortunately, too many experimenters fail to take a few simple safety precautions — precautions that can save much embarrassment or worse!

First of all, always use a fused ac plug such as the EI Menco along with 5- to 10-amp fast-blow fuses. For the cord itself use about 6 feet of no. 16 heavy-duty lamp cord. For the clip-lead end, Mueller no. 60 alligator clips are a good bet, but be sure to insulate each alligator clip with a Mueller no. 62 rubber cover.

Bruce Clark, K6JYO

using undervoltage relays

Although many forms of undervoltage relays are on the market, it sometimes happens (as in my case) that a quick and dirty substitute can be found. Most standard relays exhibit a very wide difference in pickup and dropout current, typically three to one. Therefore, it's often impossible to use a single relay for a specific application.

I needed a relay that had to drop out within approximately 10% of the normal running voltage. Available relays were Allied Control type BO6-D 184VDC. These units have a 13500-ohm coil. Pickup is at approximately 10 mA, but dropout occurs at about 3 mA.

As shown in fig. 1, R1 is proportioned

to energize the relay (RY 1) at about 20% below the operating voltage. R4 is then set to pull in RY 2 at a point a little higher — say 10% below the operating voltage. The 100k composition pot is then set to drop out RY 1 at a point 10% below the operating voltage.

This arrangement was run in a bench setup for eight hours to determine if relay heating would result in any variation of the dropout point. The maximum variation in dropout point was approximately 2% of the operating voltage.

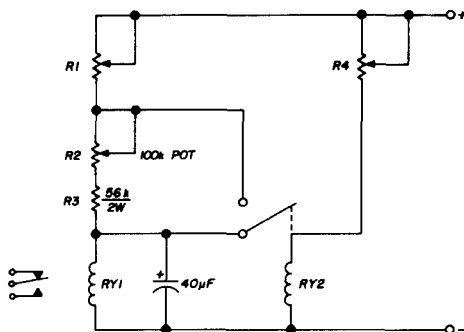


fig. 1. Method for controlling relay dropout voltage. Resistors can be proportioned to cause pull-in and dropout over fairly wide current range.

caution

Don't try to use a variation in dropping resistance as shown in fig. 2, or instability will result. Also, don't try to use an extra set of contacts on RY 1 to perform the function of contacts on RY 2; i. e., to switch in R2 and R3. Oscillation or instability will result.

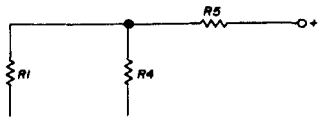


fig. 2. An example of dropping-resistor arrangement that will cause instability.

A solid-state circuit would have been preferable, except that this particular equipment was to be subjected to a radioactive environment, which precluded the use of solid-state devices.

Bill Wildenhein, W8YFB

simple resistance standard

As many amateurs know, ohmmeter readings taken with a vom can be notoriously inaccurate. However, there are times when you need an accurate resistance measurement of a higher order than that obtainable with an ordinary multimeter. Higher accuracy generally requires a Wheatstone bridge or similar laboratory-type equipment. For occasional use such expense cannot be justified.

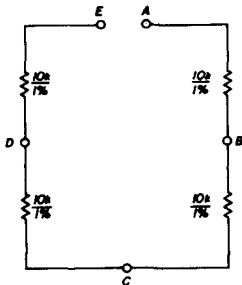


fig. 3. Simple resistance standard provides accurate checkpoints from 2500 to 40,000 ohms. Connections are shown in table 1.

The inexpensive "resistance checker" shown in the photograph and in fig. 3 is a simple and direct solution to this problem. Four 1% resistors are wired as shown; it is apparent that there will be resistance check points at 10k, 20k, 30k and 40k ohms. If your volt-ohmmeter has not been grossly abused, you can set the

table 1. Parallel connections required for resistance values from 2500 to 40 kilohms.

desired resistance value	connect together	read ohms between
2500	A-C B-D C-E	A-B
3333	A-C B-D	A-D
5000	A-C	A-B
6667	A-D	A-C
7500	A-E	A-D
10,000	—	A-B
13,333	A-C B-D	A-E
15,000	A-C	B-D
16,667	A-D	C-E
20,000	—	A-C
25,000	A-C	B-E
30,000	—	A-D
40,000	—	A-E

meter to 10k ohms when connected across one leg of the standard — merely adjust the "zero ohms" knob so the meter coincides with the selected resistance value. Thereafter you may read resistance values with good accuracy up to 10 or 20 percent removed from the check point.

In addition to the multiple 10k check points, parallel connections will result in resistor standards at 2,500, 3,333, and 5,000 ohms (see table 1). Other standard values may be obtained through suitable interconnection of the various resistors. The chart is provided since most of us don't want to get out the slide rule when a quick resistance check is needed. Obviously other decade values may be selected but the above setup provides resistance checkpoints at more than one dozen intervals throughout the range from 2.5k to 40k ohms.

Neil Johnson, W20LU

cleaning printed-circuit boards

If you work with printed-circuit boards you probably have had difficulty removing solder from the holes when removing resistors, capacitors or other components. A cutting-torch cleaner — available from a welder's supply house — is a very useful aid. The cutting-torch cleaner comes with 12 different-sized steel rods which can be pushed through the solder holes. About one-quarter inch back from the smooth tip of each rod there's a machine-cut rasp surface which may be used to enlarge the holes, if necessary. The rods are usually furnished with a small metal case for easy storage.

Felix W. Mullings, W5BVF

Heath HW-17 modifications

After using the Heath HW-17 for some time, I decided that the receiver in the little rig lacked sufficient gain. The front-end seemed quiet and relatively sensitive, but overall receiver response was low. When WB2EGZ's article appeared in the August issue I built the mosfet pre-amplifier. It did give the receiver more gain, but didn't help much with weak-signal reception. In fact, the preamp

quiet and sensitive I thought that the receiver needed a little more i-f gain. From a quick check of the diagram it appeared that the 40673 mosfet and associated components would fit the HW-17 like a glove. It was wired into the set between the i-f output and the second mixer. This can be done very easily without drilling any holes.

Solder is removed from the i-f output pin of the tuner where it connects to the board; a vacuum de-soldering tool is very handy here. A small piece of spaghetti is slipped over this pin to keep it from touching the foil. Gate 1 of the transistor is soldered directly to the pin, and the drain lead is soldered to the foil nearby. The transistor is mounted perpendicular to the board and the rest of the components are soldered to the transistor leads. Although the additional i-f stage is very stable, and no combination of lead placement will cause it to oscillate, use short leads.

The modification requires re-alignment of T1 (in the tuner) and L6. Adjust them for maximum signal strength as indicated on the S-meter while rocking the main tuning dial across a weak signal.

Since adding this modification, the familiar background hiss of most vhf receivers is present, and ignition and atmospheric noise can be easily heard. With the antenna disconnected, the noise is

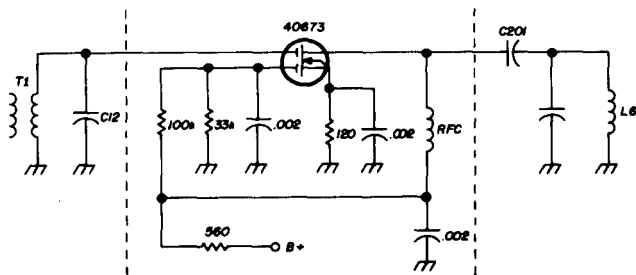


fig. 4. Added stage of i-f amplification for the HW-17. RFC is not critical.

seemed to degrade the noise figure of the HW-17's own frontend.

Since I already had the 40673 transistor and its bias and load resistors, it was decided to try to use those parts if possible. Since the frontend seemed to be

very low, indicating the frontend is quite quiet. The S-meter is much livelier because of improved agc action. Also the squelch will open with weaker signals than before.

Ed Ranson, WA5PWX

noise limiter for heathkits

Since I live in a noisy area and own one transceiver with a noise limiter and one without, the advantages of a noise limiter are very apparent to me. With some component value changes to match the resistance of the original audio-gain control in my transceiver, a very satisfactory noise-limiter circuit evolved for the Heathkit SSB line. The components for this circuit cost less than \$3.00, and the time involved is approximately one hour. The circuit is shown in fig. 5.

The switch on my HW-12 is mounted as low as possible and centered on the front panel. I used a miniature switch that mounts with two screws. These screws are used to support two 4-conductor tie points.

If the af gain-control in your transceiver is a 500k pot, R1 and R2 will be 1 megohm and R3, 150k. If the af gain-control is a 1-megohm pot, then R1 and R2 will be a 2.2 megohm, and R3, 270k. All resistors are 1/2 watt.

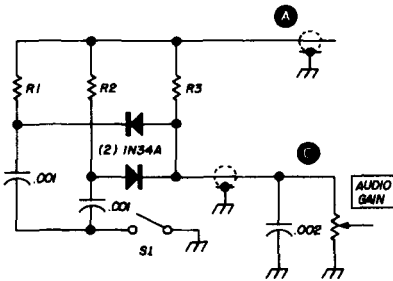


fig. 5. Simple noise limiter for Heathkit sss transceivers. Values for R1, R2 and R3 are given in text.

Remove the shielded audio-input lead from point C of the af gain-control and connect it to the input of noise limiter at point A. Connect the output of the limiter to point C on the af gain control. You will find there is very little loss with

this limiter and no noticeable distortion until the audio is too loud for comfortable listening.

Jim Welborn, W7CKH

increasing the versatility of the comdel speech processor

The Comdel speech processor can be made more versatile by the simple modification shown in the diagram. A miniature potentiometer is mounted on the rear plate of the unit and connected into the output circuit so the output level may be

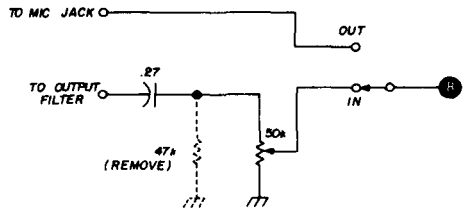


fig. 6. Gain control for Comdel CSP-11 adds versatility to the unit.

adjusted to be equal in peak amplitude to the level encountered when the unit is switched out of the circuit.*

Gain through the speech processor, without the potentiometer, is greater than unity and "in-out" checks can only be made with difficulty because of change in gain level. With the addition of the potentiometer, processor output level may quickly and easily be set to the proper amount. The output circuit potentiometer is substituted for a 47k resistor (shown in dotted lines) which is removed from the circuit board.

William I. Orr, W6SAI

*With high-level microphones, such as the D104, the peak microphone output is considerably higher than the limited 70-to 100-mV peak level available from the processor; in this case the output potentiometer should be mounted in the microphone line.

NOW

The Quality Leader In Amateur FM At A Competitive Price



Deluxe 2 Meter FM Transceiver

Always the quality leader, (see December and January 73 Magazine, and reviews in January QST and March CQ) the IC-2F remains the same — superb performance, deluxe features, 1 year warranty . . .

TRANSMITTER: RF input power — 20 watts; RF output — 10 watts minimum; maximum frequency deviation — 15KHz (adjustable); Automatic Protection Circuit (APC) — NEW! Not offered in any other transceiver on the market. Absolute assurance of final PA protection from shorted or high VSWR antennas by instantaneous transmitter disabling; Electronically switched — no relays; Sealed low pass filter to eliminate spurious radiation.

RECEIVER: Double conversion superheterodyne; Sensitivity better than $0.4\mu\text{V}$ @ 20 db of quieting; FET front end; ceramic filters for excellent bandpass shaping; Integrated Circuit IF; built-in speaker on front panel.

GENERAL: Six channels (six transmit and six receive crystals) selectable from the front panel; large RF/"S" meter and easier to read controls; power requirements 12 to 15 volts DC.

The Deluxe IC-2F comes complete with high impedance microphone, three-position chrome mobile mounting bracket, crystals installed for two channels (Ch. 1, 146.34/146.94; Ch. 2, 146.94/146.94), power cables and plugs and manual. **Amateur Net \$299.95**

Optional AC Power Supply with built-in Discriminator Meter, Model IC-3P. **Amateur Net \$42.50**

PA-50A 50 watt solid state AFTERBURNER for more power mobile. **Amateur Net \$129.95**

Available at your dealer


VARITRONICS INCORPORATED

2321 EAST UNIVERSITY DRIVE • PHOENIX, ARIZONA

for the experimenter!

INTERNATIONAL EX CRYSTAL & EX KITS

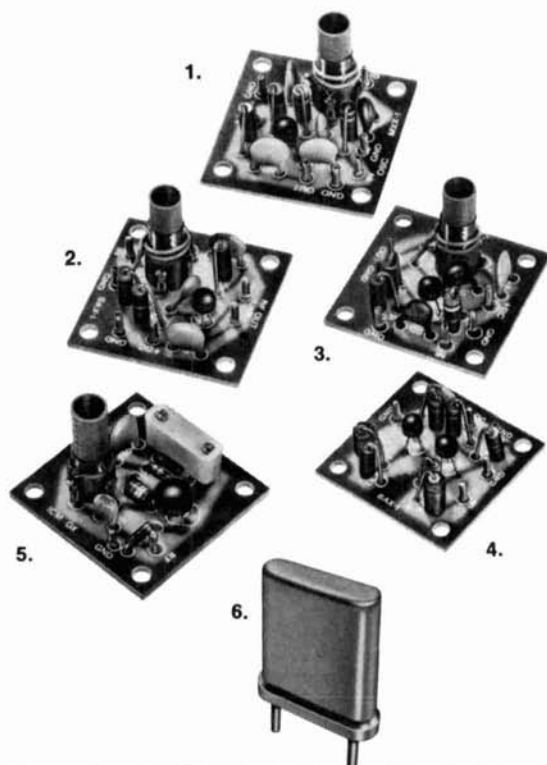OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50

2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50

3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....\$3.75

4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur.....\$3.75

5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....\$2.95

6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency).....\$3.95

for the commercial user

INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

CRYSTAL TYPES: (GP) for "General Purpose" applications
(CS) for "Commercial Standard"
(HA) for "High Accuracy" close temperature tolerance requirements.



WRITE FOR CATALOG.



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

HAL DEVICES



**HAL 311BC
ELECTRONIC
KEYER
\$53.00**

THE most versatile keyer available. Send for full details on the **HAL 311BC** and the complete line of **HAL** electronic keyers. There is a model to fit your requirement and budget from \$16.50 to \$53.00. Shipping extra. Now available in kit form for even greater value.




HAL MAINLINE ST-6 RTTY TU

Complete parts kit for the **W6FFC ST-6** now includes all parts except cabinet. Only 7 **HAL** circuit boards (drilled G10 glass) for all features. Plug-in IC sockets. Custom transformer by Thordarson for both supplies, 115/230V, 50-60Hz. \$135.00 kit. Wired units available. Shipping extra. Write for details.



**HAL
TOUCHCODER II
KIT
\$55.00**

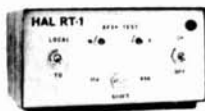Complete parts kit, excluding keyboard, for the **W4UX CW** code typer. All circuitry on one 3 x 6" G10 glass PC board. Plug-in IC sockets. Optional FM repeater ID, contest ID, and RTTY features available. Keyboard \$25.00. Shipping extra. Write for full details.



**HAL RT-1
TU/AFSK
KIT
\$51.50**

All TU and AFSK generator circuitry, including PS, on 3x6" G10 PC board. 850, 170, and CW ID shifts. Zener protected transistor loop switch. High and low impedance audio output. Price \$45.00. Shipping extra. Write for full details. **HAL** Designer Cabinet for the above \$6.50. 3 pole Butterworth filter drilled PC board \$3.00.

HAL DIP BREADBOARD CARD

Drilled G10 glass PC board accepts 6 16 pin DIP IC's in plug-in sockets. Each IC pin fanned out to two pads. Plugs into standard 22 pin edge connector (.156" finger spacing). \$5.50

DOUBLE BALANCED MODULATOR KIT

For the DBM in March 1970 Ham Radio 7/8 x 2" drilled G10 glass PC board
4 HP-2800 hot carrier diodes matched by **HAL**.
2 Indiana General CF102-Q1 toroids.
Wire and instructions included. \$6.50

TTL INTEGRATED CIRCUITS

HAL is now stocking NEW 7400 series TTL IC's. Available are 7400, 7401, 7402, 7404, 7405, 7410, 7420, 7430, 7440, 7441, 7442, 7473, 7475, 7490, and 7493. Write for prices and complete catalog.

HAL MAINLINE ST-5 RTTY TU

ST-5 kit now includes drilled G10 glass boards, custom Thordarson transformer, meter and metering components. Boards accept both round and DIP 709 IC's. \$50.00. Less boards, meter & meter components \$37.50. Boards only \$6.00. Shipping extra.

HAL MAINLINE AK-1 AFSK OSC

HAL now offers a parts kit for the AK-1 AFSK osc. Drilled G10 glass PC board plugs into 12 pin edge connector for compatibility with the **HAL ST-6**, or for ease of use alone. Requires 12vdc. \$27.50. Shipping extra. Write for parts list.

HAL FM REPEATER IDENTIFIER

TTL logic. Power line frequency counter for 3 minute or less timing and control. Easily reprogrammable diode ROM uses only 27 diodes (depending on call) to send DE "any call". Low impedance audio with volume and tone control. All circuitry including PS on small G10 glass PC board. Write for full details.

ORDERING INFORMATION

Postage is not included in the prices of **HAL** products. Please add 50¢ on small parts orders, and \$2.00 on larger kits. Shipping is via UPS when possible, and via insured parcel post otherwise. Please give a street address.

HAL DEVICES, Box 365H, Urbana, IL 61801


Hot Carrier Diodes: HP2800..... 90¢, 12/\$10.00 Matched by **HAL**..... 4/\$4.25
IC's: 1 µL 900, 914..... 60¢ 1 µL 923..... 90¢
MRTL MC790P, MC890P..... \$2.00, 10/\$19.50
MC724P, MC789P, MC792P, MC725P..... \$1.05, 10/\$9.50
Also available: MC723P, MC788P, MC890P, MC767P, MC9760P.
OP AMP: SN72709N (DIP), SN72709L (TO-5)..... \$1.25

TOROIDS: Indiana General CF102-Q6, CF102-Q1, CF101-Q2..... \$0.40
CINCH IC sockets, 14-DIP, 8-ICS..... 80¢ **HAL DEVICES**
Add 50¢ Postage, send for complete list. Box 365 Urbana, Illinois 61801



TFME POWER SUPPLY FOR Regency HR-2

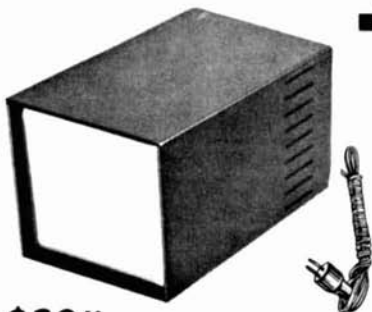Over 2 amps fully REGULATED with short circuit protection and low ripple content. Suitable for use with other similar transceivers. HF-144 RPS



\$39⁵⁰ add \$3.00 for shipping

Regency	HR-2	\$ 229 ⁰⁰
Crystal	146.34 MHz	6 ⁵⁰
TFME	HF 144RPS	39 ⁵⁰
TFME	HF 144RW	16 ⁵⁰
	pre-amp installation	3 ⁵⁰
	shipping	3 ⁰⁰
Total	Value	\$ 298⁰⁰

Includes 1 pair of 146.94 MHz crystals



TFME SPECIAL

\$ 269⁹⁹

For



TFME 2 METER PRE-AMPS

Put a NEW RECEIVER in your old hi-band set for less than \$17.00 (or the next best thing).



HF - 144 U* MOS FET RF Preamplifier

NEW from your old set

PERFORMANCE

SUPERIOR from your 1971 model

Typical 18db gain 3db noise figure
Lo Intermod/Hi burn-out threshold

	Kit	Wired
HF - 144 DGK	-----	\$9.50
HF - 144 U for Universal use	--	\$11.50 \$16.50
HF - 144 M for Motrac radios	-----	\$16.50
HF - 144 R for Regency HR-2	--	\$10.50 \$16.50

PLEASE ADD 60¢ FOR POSTAGE AND HANDLING

NEW

HF - 144 RPS \$39.50
Regulated DC power supply for HR-2



GAIN ANTENNAS
by LARSEN



Cush
craft

WRITE TODAY FOR OUR FLYERS WITH DETAILED INFORMATION AND PRICING OF PRODUCTS SHOWN.

HIGH PERFORMANCE VHF YAGIS

TOPEKA F M ENGINEERING
3501 CROCO ROAD
TOPEKA, KANSAS 66605
(913) 233 7580

new products

new linear amplifiers



The new Delta 70 linear amplifier is externally identical to the Alpha 70 except for the plate-tuning control; it uses a vernier drive to an air-variable capacitor. Internally, the only difference between the Delta and Alpha models is the use of an air-cooled 3-1000Z in place of the Alpha 70's vapor-cooled system. The two amplifiers are almost identical electrically and handle much the same. Power ratings are identical.

While the Alpha 70 features continuous coverage from 3 to 30 MHz, the Delta is specified for the amateur bands, 10 through 80, although it too is almost continuous tuning. The Delta 70 linear amplifier is initially priced at \$1195.00.

For more information on the Alpha 70 or Delta 70 linear amplifiers, write to Ehrhorn Technological Operations, Inc., Post Office Box 1297, Highway 50 East, Brooksville, Florida 33512, or use *check-off* on page 94.

mosley 75 and 80-meter conversion kit

The new Mosley RV-8C conversion kit is designed for amateurs who already own the Mosley 4-band vertical, the RV-4C, or for those who are considering the purchase of a 5-band vertical antenna system for operation on 10 through 80 meters. The 5-band antenna stands only 22-feet high and requires no guying or concrete footing.

The conversion kit includes a loading coil rated at 750 watts a-m or CW, and 2000 watts PEP ssb. Tuning is accomplished by sliding the U-shaped matching-section along the vertical element until a match is obtained at the desired operating frequency.

A plexiglass coil housing, closed at one end with a polyethylene cap, assures protection against the most severe weather conditions. Easy-to-follow instructions are included with the kit. For more information, write to Mosley Electronics, Inc., 4610 N. Lindbergh Boulevard, Bridgeton, Missouri 63044, or use *check-off* on page 94.


50-watt mobile amplifier

Varitronics has just announced a new power amplifier that should appeal to all mobile fm operators.

The Varitronics PA-50A is a completely solid-state class-C rf amplifier designed for use in mobile amateur fm applications. Because of internal rf

switching, the PA-50A can be used with any two-meter transmitter with 5 to 15 watts output when used with the IC-2F transceiver (nominal 12-watts drive). Balanced-emitter semi-conductors insure complete insensitivity to high vswr—even no load conditions. This handsome and ruggedly built amplifier is styled like the Varitronics IC-2F, features a calibrated output meter and comes complete with a mobile-mounting bracket and dc power cord. \$129.95 amateur net. For more information, use *check-off* on page 94, or write to Varitronics Incorporated, 2321 East University Drive, Phoenix, Arizona 20665.

two-meter fm transceiver

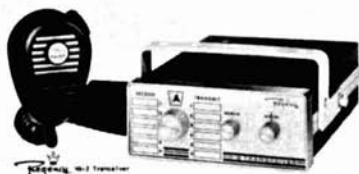

Regency Electronics has announced a compact mobile fm transceiver for operation in the 144-MHz band. The solid-state model HR-2 features a 10-watt power output with operation on any of six transmit and receive channels in the band. Simple operator modification, however, can enable the radio to transmit and receive on any of 12 different duplex combinations.

The receiver is a double-conversion superhetrodyne with a highly selective ceramic filter for operation on both wide- and narrow-band signals. Sensitivity is rated at $0.35 \mu\text{V}$, 20 dB quieting and audio output at 5 watts.

The transmitter features phase modulation for exacting carrier stability. Individual trimmer capacitors enable frequency setting optimum performance in point-to-point or repeater applications. Built-in swr load mismatch circuitry protects against open or shorted antenna conditions.

The modern integrated circuitry operates on 13 Vdc with low current drain. The package comes complete with plug-in ceramic microphone, built-in speaker and mobile-mounting bracket. One pair of factory installed transmit and receive crystals on 146.94 MHz are included in the \$229.00 amateur net price. An ac power supply and linear amplifier will soon be available as optional equipment.

For more information, write to Regency Electronics, Inc., 7900 Pendleton Pike, Indianapolis, Indiana 46226, or use *check-off* on page 94.

short-wave listening

A new, well-illustrated, multi-page primer on short-wave listening has been written by The Hallicrafters Company, and is being offered free to the interested reader, DXer, short-wave listener, hi-fi buff, hobbyist and amateur radio enthusiast.

Aptly titled "short-wave puts you where it's at," the multi-colored brochure takes the interested reader through the many adventures he can experience with short-wave; explains graphically and in simple terms "what is short-wave;" tells the reader what can be heard on short-wave (i.e., amateur bands, overseas marine radio, aeronautical bands, international broadcasting, military and clandestine stations, standard time signals, public safety and many others); provides a complete radio frequency spectrum in a unique and copyrighted graphic illustration; and points out what to look for when choosing a quality short-wave receiver.

Also included in the center fold of the primer is Hallicrafters' complete line of a-m and fm general-coverage short-wave receivers, special frequency monitor radios and amateur transceivers and accessories. For a free copy of the multi-page, short-wave primer, "short-wave puts you where it's at," write to The Hallicrafters Company, Dept. PR, 600 Hicks Road, Rolling Meadows, Illinois 60008, or use *check off* on page 94.

THE RADIO CONSTRUCTOR

Vol. 22 No. 11

JUNE 1968

THREE SHILLINGS

Top Band "Quartet" Transmitter



Special
IN THIS ISSUE

A New Magazine?

Not really. New in the U.S.A. perhaps, but very well known in Great Britain and now being offered to you here.

RADIO CONSTRUCTOR is almost exclusively construction material. Clearly written, concise articles give you full details on:

- Audio Construction Projects
- Receiver Construction Projects
- Transmitter Construction Projects
- Test Equipment Projects
- Radio Control Projects
- ... and much more

Try a subscription to this interesting magazine, we are sure that you will not be disappointed.

ONE YEAR SUBSCRIPTION — \$6.00

Write
RADIO CONSTRUCTOR
Greenville, N. H. 03048

Name

Address

City State

Zip

new allied catalog

Allied Electronics' new 1971 catalog of electronics parts and supplies, considered by many as the bible of the industry, is now available. The catalog lists over 70,000 separate stock items from more than 700 manufacturers. Detailed specifications, descriptions and illustrations cover a vast array of parts and components including: semiconductors, integrated circuits, tubes, relays, timers, transformers, resistors, capacitors, connectors, coils, chokes, sockets, plugs, jacks, switches, fuses, batteries, clips, lamps, wire and cable, and much more.

Other major sections of the catalog feature test instruments, recording equipment, sound equipment, intercoms and business communications gear, power supplies, electronic counters, chemicals, hardware, technical books, tools and solder equipment. Allied Electronics Catalog No. 710 sells for \$2.00 (or no charge with order) and is available from Allied Electronics, 2400 W. Washington Boulevard, Chicago, Illinois 60612.

solid-state rtty demodulator



The new Space One RTTY demodulator from J&J Electronics has a number of interesting features, including heavy-duty loop supply, regulated power supply, electronic keyer stage supplying plus and minus voltages with provisions for adjusting to 1 mA when driving diodes, as well as both 850 and 170 shifts, selectable from the front panel. The solid-stage circuitry uses integrated-circuit amplifiers

and high-voltage transistors for keying the loop supply.

The Space One uses standard tones of 2125 and 2975 Hz, has metered tuning (indicator lamps available as option), and provides a spare socket for the addition of a three-pole Butterworth bandpass input filter if local conditions warrant it. The basic unit is completely self contained, including loop supply and fsk driver, and is ready to connect between your receiver and printer.

Several extra features are available at optional extra cost, including receive and standby indicator lamps, auto receive without motor-control relay, and auto-start plus motor control relay. Basic unit, less options, is \$124.95. For more information, write to J&J Electronics, Windham Road, Canterbury, Connecticut 06331, or use *check-off* on page 94.

video/rf selector-control center



The new Alco CCV3 is a three-position control center that has many uses in video or rf layouts. Although it is suitable for switching *low-power* antenna systems it is designed primarily for controlling tv cameras and monitors. The unique push ON and push to RELEASE switches allow the operator to select equipment optionally at will. The unit uses standard type-UHF coaxial connectors, and no external power is required for operation. Crosstalk between adjacent channels is negligible. Price is \$19.95. For more information use *checkoff* on page 94, or write to Alcoswitch Division of Alco Electronic Products, Inc., Post Office Box 1348, Lawrence, Massachusetts 01842.

Digital Frequency Meter



- Monitors your "transmitted" signal
- Measures kHz and MHz
- Operates with any exciter-transmitter (1 to 600 watts — up to 30 MHz)
- Large-bright "Nixie" display
- Now - 100 Hz (.1 kHz) Readout through 35 MHz

FM-6 Kit . . . \$139.50

(170 MHz Prescaler - \$45.00 extra)

Micro-Z Co.

Box 2426 Rolling Hills, Calif. 90274

HAL DEVICES

FOREIGN HAMS

DO YOU NEED AMERICAN CONSTRUCTION COMPONENTS?

Send us a list of your needs and we will give you a quotation on any standard American parts which you may require.

No longer need you avoid construction projects in **Ham Radio** or any other U. S. amateur publication because of hard to find parts. We'll find them and send them to you.


Send 4 IRC's for catalog.

HAL DEVICES

BOX 365 HF
URBANA, ILLINOIS 61801 U.S.A.

SERIOUS ABOUT VHF?

432 MHz DUAL GATE MOSFET
CONVERTER

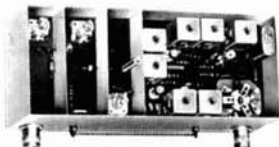

All solid state. Silverplated, brass enclosure. Stripline 432 MHz circuits. Noise figure: 3.2, cross mod. 80 mV min., gain 5-20 db, T-match output attenuator.

I.F. 144-146 MHz. Model DGTC 1702. \$69.00
I.F. 28-30 MHz. Model DGTC 1710. \$71.50

DUAL GATE MOSFET CONVERTER
FOR TWO METERS



Noise figure: 2 or less. Excellent cross modulation and image rejection (116 MHz xtal oscillator.) IF 28-30 MHz. All inductors shielded. Model DGTC 22. \$35.00

ALSO:


144/432 MHz VARACTOR TRIPLER
Model LVV 270. \$75.00

144/432 MHz TRANSVERTER
Model TTV 1270. Spec. introductory offer: \$37.50

si

SPECTRUM
INTERNATIONAL
BOX 87C TOPSFIELD
MASSACHUSETTS 01983

radio amateur callbook

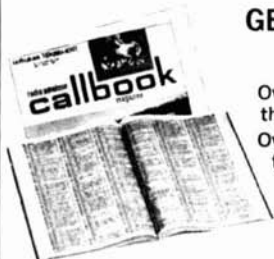

GET YOUR NEW
ISSUES NOW!

Over 285,000 QTHs in the U.S. edition **\$8.95**

Over 165,000 QTHs in the DX edition **\$6.95**

NEW EDITION EVERY:
MARCH 1 - SEPT. 1
JUNE 1 - DEC. 1

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Prefixes by Countries!
- Zips on all QTH's!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

See your favorite dealer or order direct (add 25c for mailing in U.S., Possessions & Canada. Elsewhere add 50c).

WRITE FOR
FREE
BROCHURE!




RADIO AMATEUR
callbook INC

Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

two-meter fm antenna

Varitronics has recently introduced the *Redhead*, a two-meter groundplane antenna with 3.4-dB gain. This sturdily built, commercial quality antenna is adjustable for low SWR over the entire two-meter band. Radials and radiator are made from heavy-gauge aluminum tubing, and the loading coil is well protected by a metal shield which is painted red (hence the nickname). The model AS-2HG *Redhead* antenna is rated at 250 watts cw, a-m or fm, and 500 watts PEP ssb. \$18.95 from your local dealer. For more information, write to Varitronics Incorporated, Post Office Box 20665, Phoenix, Arizona 85036, or use *check-off* on page 94.

keyer memory kit

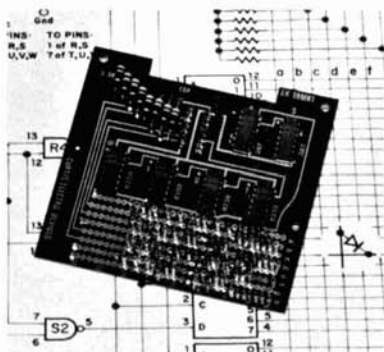

For hams who like to roll their own, Curtis Electro Devices has introduced a do-it-yourself diode-matrix message memory for their EK-39M, a combined keyer and message generator. The kit is an exact plug-in equivalent to the custom integrated-circuit memory which Curtis supplies individually pre-programmed per user instructions. It consists of six integrated circuits, a pre-drilled circuit board and 150 diodes plus other components and hardware. Complete instructions are provided.

Assembly requires no knowledge of logic techniques or Karnaugh maps. If you can send Morse, you can program the matrix. Programming and assembly time is three or four hours. The memory kit

yields three programs. A typical contest set are:

5NN03 DE W1DTY
CQ TEST CQ TEST DE W1DTY
DE W1DTY

In addition to operating convenience, the new message generator is expected to raise cw contest scores by boosting operator efficiency. The EK-39MK Diode Memory Kit is available now from dealers or direct from the manufacturer and is priced at \$49.95. (The EK-39M is \$179.95.) For more information write Curtis Electro Devices, Box 4090, Mountain View, California 94040, or use *check-off* on page 94.

motorola semiconductor kits

Two new construction kits with special "how to" project brochures have been introduced by Motorola HEP through its nationwide network of semiconductor distributors. The HEK-3 Radio Amateur Hobby Kit, retailing for \$5.95, contains two rf/i-f linear integrated circuits and an RTL integrated circuit in addition to an HMA-36 special project brochure. Circuits in the brochure include a 6-meter preamp, 6-meter a-m modulator, 40-meter transmitter, video amplifiers and a microphone amplifier.

The HEK-4 Home Handyman Hobby Kit, retailing for \$4.95, contains a silicon-controlled rectifier, a unijunction transistor, a silicon rectifier, a photo transistor and a silicon npn transistor. Special project brochure HMA-37 that comes with this kit shows 11 applications including a light dimmer, electronic timer, burglar alarm and code-practice oscillator.

The project brochures are free at HEP semiconductor distributors. HEP is Motorola's sales program for making semi-conductor devices readily available to the experimenter through a nationwide network of authorized suppliers.

TWO METER SSB TRANSMITTER



Time to get ready for the next Oscar satellite repeater!

Audio amplifier, 9 MHz USB oscillator, balanced modulator, 9 MHz amplifier with crystal filter, mixer, driver and linear amplifier 144 - 146 MHz. Output 12 Watts PEP at 24 Volts. Oscillator injection 135 - 137 MHz.

Glass-epoxy, silverplated p.c. board (3½" x 9") plus complete construction, assembly and alignment instructions (including construction data for 135 - 137 MHz VXO or phase-locked oscillator).

\$4.95


plus 25¢ shipping

si

SPECTRUM
INTERNATIONAL
BOX 87C TOPSFIELD
MASSACHUSETTS 01983

GEM-QUAD FIBRE - GLASS

ANTENNA FOR 10, 15, and 20 METERS.

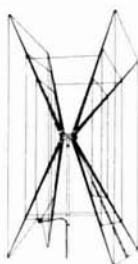

Two Elements \$87.00
Extra Elements \$50.00 ea.

Submit Payment with Order
Shipped Freight collect.

Price includes
Canadian Federal Sales Tax
or U.S. Customs Duty.

KIT COMPLETE WITH

- SPIDER
- ARMS
- WIRE
- BALUN KIT
- BOOM WHERE NEEDED

SEE OUR FULL PAGE IN MAY ISSUE

Buy two elements now - a third and fourth may be added later with little effort.

Enjoy optimum forward gain on DX, with a maximum back to front ratio and excellent side discrimination.

Get a maximum structural strength with low weight, using our "Tridetic" arms.



MANITOBA DESIGN INSTITUTE
AWARD WINNER

Structural Glass
LIMITED

Canadian Patent No. 794506
U.S. Patent No. 3532315

20 Burnett Avenue, Winnipeg 16, Manitoba, Canada

CIRCUIT BOARDS in 10 Minutes ?

with
just a pair
of scissors



try Cir-kit

Pressure Sensitive Copper Foil
Tape and Sheet

- No Chemicals — No Mess
- No Layout Restrictions
- Full Instructions
- Simple Circuit Changes
- Flexible — Conforms to any surface shape
- Use for Crossovers — Either insulate with Teflon or Mylar or use other side of board.

A revolutionary new material for the construction of experimental and prototype "printed" circuit boards.

Cir-Kit is high purity .002" copper protected by lacquer and coated with an exclusive heat resistant pressure sensitive self adhesive. Just remove backing paper and place in selected position. Press down firmly. If modifications are necessary just rip it up and start over.

Cir-Kit can be used for modifying existing boards or building up new ones. The perfect answer for small quantity applications or one of a kind amateur projects.

5 feet 1/16" or 1/8" wide \$.60
100 feet 1/16" or 1/8" wide \$9.95
Sheets 6" x 12" — \$2.50 each
or 5 for \$9.95

Order Now

Cir-kit

Box 592
AMHERST, N. H. 03011

Dealer Inquiries
Invited

The World's Most
Versatile Circuit Building System

mobilink



The Mobilink is a unique new product that will have wide acceptance among two-way radio users in the commercial field, CB, amateurs, and other operators who require constant monitoring of their mobile receivers. The Mobilink is helpful when out of the car or out of hearing range while on business calls, coffee breaks or lunch.

Mobilink is a low powered a-m transmitter used with a pocket receiver as an accessory for mobile communications, base stations, paging and intercom extensions. All calls and the exact content of messages will be heard up to 1/4 mile away on the small receiver. This is a great improvement over the systems that blow the car horn, or turn on the car lights. Mobilink has a greater usable distance, will not disturb others and will not discharge the car battery.

The Mobilink features easy installation — only connection needed is a pair of wires to the speaker; the internal 9-volt battery has shelf life in standard service due to the vox circuit that turns on the Mobilink transmitter only when a signal is received on the communications receiver. It can be used with all code, scramble and squelch systems without modification because it uses audio instead of an rf signal.

The Mobilink has 75 milliwatts input power, an antenna that adjusts from 5 to 18 inches, small size, weighs only 11 ounces, frequency of 27.263 MHz or any CB channel on request, crystal controlled, input impedance of 3 to 8 ohms, heavy aluminum construction, all solid-state

devices and made in U. S. A. Price is \$44.95 complete with crystal, battery, connecting wire and antenna.

The Mobilink receiver is a small pocket size portable transistor circuit with 18-inch collapsible antenna, rf tuned circuit, crystal controlled, speaker, ear-phone, agc performance, 9-volt battery and carrying case. Comes complete ready to use with crystal for \$24.95 postpaid. Mobilink transmitter and receiver set is \$69.90 postpaid. Units and information are available from Herbert Salch & Co., Marketing Division of Tompkins Radio Products, Woodsboro, Texas 78393, or use *check-off* on page 94.

continuous-tone encoder




Automatically activated signal-tone encoders for use with two-way radio equipment have been announced by the Ross and White Company. Keyed by closing the transmitter microphone switch, the encoder generates a short duration tone burst which modulates the transmitter, and automatically activates tone-access repeaters, tone-operated receiver squelch circuits or other signalling devices.

The two models are the TE-2, with two switch-selected output tones, and the TE-5, with five tones. Frequency range is field adjustable from 1600 to 2800 Hz. The 0.5 second output tone burst is a 6-V p-p open-circuit sine wave, with output impedance adjustable in three steps. The all solid-state circuit uses commercial-

AT LAST a SPEECH COMPRESSOR that REALLY WORKS

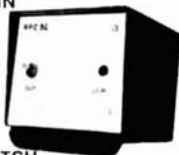- LOW DISTORTION CIRCUIT
- 5-10 DB IMPROVEMENT IN TALK POWER
- FULLY WIRED & TESTED NOT A KIT
- SEVERAL MODELS TO CHOOSE FROM
- WORKS WITH PHONE PATCH
- Quality construction includes Silicon transistors, FETs Glass circuit boards
- FULL WARRANTY—ONE YEAR
- Performance second to none
- INTRODUCTORY LOW PRICES — \$22.50 to \$34.95 (Illinois residents add 5% sales tax)



Write for specifications and information sheets (free)

Rp Electronics

Demonstration Tape cassette available (\$2.00 deposit)

BOX 1201H
CHAMPAIGN, ILL.
61820

WIRED AND TESTED INTERDIGITAL PRE-AMPLIFIERS

by CADCO

Factory wired and aligned 6, 2 and 1-1/4 meter state of the art ultra low noise Interdigital Pre-amplifiers and filters - as featured this month in HAM RADIO!

INTERDIGITAL PRE-AMPLIFIERS

50 MHz Model IPA-50 \$29.00*
144 MHz Model IPA-144 \$29.00*
220 MHz Model IPA-220 \$29.00*

INTERDIGITAL BANDPASS FILTERS

50 MHz IS-BPF-50 \$19.00*
144 MHz Model IS-BPF-144 \$19.00*
220 MHz Model IS-BPF-220 \$19.00*

*Plus \$0.50 postage

Allow 3 weeks for receipt of order

BOB'S DISCOUNT ELECTRONICS

720 N. Hudson, Oklahoma City, Okla. 73102

(405) 232-1384

NEED CRYSTALS?



We can supply crystals from 2KHz to 80 MHz in many types of holders.

SPECIALS

Color TV crystal (3579, 545KHz) wire leads	\$1.60	4 for \$5.00
100 KHz frequency standard crystal (HC 13/U)	4.50	
1000 KHz frequency standard (HC6/U)	4.50	
Any CB crystal, trans. or rec. (except synthesizer crystals)	2.50	
Any amateur band crystal in FT-243 holders (except 80-160 meters)	1.50	4 for \$5.00
80 meter crystals in FT-243 holders	2.50	

We have in stock over six million crystals which include types CRIA/AR, FT243, FT241, MC7, HC6/U, HC13/U, HC25/U, HC18/U, etc. Send 10¢ for our 1970 catalog with oscillator circuits, listing thousands of frequencies in stock for immediate delivery. (Add 10¢ per crystal to above prices for shipment 1st class mail; 15¢ each for air mail.)




Special Quantity Prices to Jobbers and Dealers.

ORDER DIRECT
with check or money order to

2400H Crystal Drive
Fort Myers, Florida 33901

... THE BEST 2 METER CONVERTER

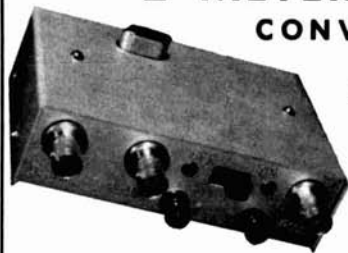

Model 407
\$42.95
ppd.

144-146 MHz in, 28-30 MHz out
or 146-148 MHz with a second crystal
available for \$5.95 each

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of thousands of satisfied users) that it's the best. The reason is simple - we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$42.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

VANGUARD LABS

Dept. R, 196-23 Jamaica Ave., Hollis, N.Y. 11423

grade American-made components and silicon semi-conductors on an epoxy-fiberglass circuit board.

The encoders and their 9-V batteries are housed in 2-1/8 x 1-1/8 x 3-1/4-inch plastic cases, and are connected to the transmitter microphone circuit with a 15-inch shielded cable. Installation typically requires 20 minutes or less. An aluminum bracket is provided for mounting the encoder.

The price of the TE-2 is \$29.95, and for the TE-5, \$39.95. For further information, contact Ross and White Company, 50 West Dundee Road, Wheeling, Illinois 60090, or use *check-off* on page 94.

QRPP magazine

Ade Weiss, K8EEG, long time QRP enthusiast, has launched a new bi-monthly, now in its second year, for the QRPP amateur radio operator. To the uninitiated, QRPP is an extension of the Q-signal QRP which is applied to amateur operation of less than five watts. The new magazine, *The Milliwatt: National Journal of QRPP*, is devoted exclusively to under-five-watt amateur radio, and has featured technical articles, construction projects, operating news, QRPP WAS standings and QRPP log selections. The first volume includes construction projects for transistor transmitters and receivers for 3.5, 7 and 14 MHz, QRPP wattmeters, dummy loads and SWR meters, articles on propagation, operating procedures and other applications of general theory to the specific requirements of very low power operation. *The Milliwatt* is published six times a year; subscriptions are \$3.00 annually, \$3.40 first-class mail. A reprint of the entire Volume I is available, \$4.00 postpaid. Subscriptions and general queries to Wes Mattox, K6EIL/2, 115 Park Avenue, Binghamton, New York 13903. Articles and operating news to Adrian Weiss, Editor, *The Milliwatt*, Meckling, South Dakota 57044.



NOW...you can have the complete line of Swan amateur equipment at **FACTORY DIRECT PRICES**

Our value engineering and advanced methods of production are not restricted to our manufacturing efforts alone. One of the bases for our success has been our ability to market products equal or superior to other makes, at a lesser cost to the amateur.

The introduction of foreign made products, sold on a direct basis, has offered an interesting new challenge to our marketing department, and we believe they have developed the ideal solution.

Introducing Swan's new **SALES PROGRAM**

You can now buy any Swan equipment

direct from our factory at substantially reduced prices. If you wish to trade, or desire individual financing, purchase your Swan equipment from one of our authorized Swan dealers, at a price slightly higher than the factory price. Either way, you are now able to have proven, American made amateur radio equipment, at prices competitive with any foreign made products.

Write for our 1971 Swan catalog. It contains photos, descriptions, specifications, and the new Factory Direct Prices for every piece of equipment we make. (Did you know Swan manufactures over 50 different pieces of amateur radio equipment?)



SWAN ELECTRONICS

A Subsidiary of Cubic Corporation

SWAN Factory
305 Airport Road
Oceanside, CA. 92054
Phone: (714) 757-7525

Eastern Office
P. O. Box 151
Freehold, N.J. 07728
Phone: (201) 431-0707

SWAN Electronics, 305 Airport Road,
Oceanside, CA. 92054 Phone: (714) 757-7525

Gentlemen:

Please send me the 1971 Swan catalog.


Name _____

Street _____

City _____

State _____ Zip _____

Call _____

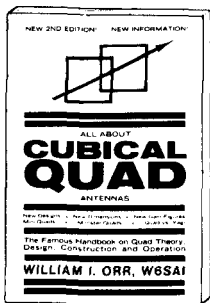

NEW!

SECOND EDITION

Long considered "THE" book
on Quads
this latest edition has

- New** — Revised gain figures for Quads
- New** — Delta Quad, Swiss Quad, Birdcage Quad
- New** — Analysis of Quad vs. Yagi — which is best?
- New** — Miniature Quad construction and performance
- New** — Monster Quads — power gains up to 14!
- New** — Correct dimensions for single and multiband Quads, 6 thru 80 meters
- New** — Improved Tri-Gamma match feeds triband Quad efficiently with one line
- PLUS . . .** The exhaustive detail which made the 1st edition so popular.

Listen to these famous DX'ers

KH6IJ: "A storehouse of valuable new information. W6SAI Quads land that Sunday punch in a pile-up."

W6AM: "A tremendous help to new and old alike. Packed with useful, accurate data."

VS6AZ: "a must for every DX-minded ham! Makes Quad building and adjustment easy."

Still only \$3.95 Postpaid

4th EDITION — Just released

For many years the "Bestseller" on beam antennas, this handbook covers all areas of the subject, both theory and practice. This new fourth edition has been updated to insure that the reader has the very latest information available.

It includes many special features such as:

- Correct dimensions — 6 thru 40 meters
- Are 40 meter compact beams worth the effort?
- Exclusive 25 year bibliography of important beam antenna articles

Whether you plan to build or buy — DX or rag chew — you need this book.

What Famous DX-er's Say:

W4BPD: "I've listened to W6SAI beams from all over the world and they work. The Beam Antenna Handbook is my bible."

5Z4ERR: "Vital for DX-er's who want results."

W9IOP: "Top beam performance separates the men from the boys in pile-ups. This book tells you how to achieve it."

W4KFC: "The most Borrowed publication on my bookshelf!"

Only \$4.95 Postpaid


Order from

comtec

BOOKS

BOX 592

AMHERST, NEW HAMPSHIRE 03031

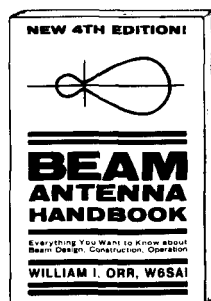

At last—Drake quality in a VHF FM Transceiver



Marker Luxury



The best of the Japanese, the Marker Luxury VHF FM Transceiver is built for and distributed and backed by the R. L. Drake Co.

- Exceptional receiver
- Backed by R. L. Drake
- Complete package for . . .

\$329⁹⁵

Includes transceiver, two channels supplied, mobile mount, microphone, coax cable, Hustler antenna, and built-in AC-DC power supply.

SPECIFICATIONS

General

Frequency Coverage	144-148 MHz
Number of Channels	12 Channels, 2 supplied Channel 1 Receive 146.94 MHz Transmit 146.34 MHz Channel 2 Simplex 146.94 MHz
Modulation	Frequency Modulation
Transmitter Control	Push-to-Talk
Power Drain	AC: Receive 6 Watts Transmit 50 Watts DC: Receive 0.5 Amps Transmit 4 Amps
Power Source (Built-in)	AC: 117 Volts 50-60 Hz DC: 13.5 Volts \pm 10%.
Dimensions	7 $\frac{7}{8}$ " W x 2 $\frac{3}{4}$ " H x 10 $\frac{1}{4}$ " D.
Weight	8 $\frac{3}{4}$ lbs.
Standard Accessories	Dynamic Microphone, Hustler Antenna, Antenna Connector Plug, AC/DC Cord, Speaker Plug.

Transmitter—transistorized with 6360 output tube

RF Output Power	Greater than 10 Watts
Frequency Deviation	Adjustable to 15 kHz maximum
Frequency Stability	\pm .001% or less
Spurious Radiation	Greater than -80 dB below Carrier
Output impedance	50 ohms

Receiver — completely transistorized

Receiver Circuit	Crystal-controlled Double Conversion Superheterodyne
Intermediate Frequencies	1st 10.7 MHz, 2nd 455 kHz
Input Impedance	50 to 75 Ohms
Sensitivity	0.5 μ V or less for 20 dB quieting. 1 μ V or less (30 dB S+N/N ratio at 10 kHz deviation with 1 kHz modulation)
Spurious Sensitivity	Greater than -60 dB.
Audio Output	0.5 Watt with 10% or less distortion.

See at your distributor, or write for details . . .



R. L. DRAKE COMPANY

540 RICHARD ST., MIAMISBURG, OHIO 45342

DRAKE SPR-4

Solid-State-Programmable COMMUNICATIONS RECEIVER



The SPR-4 outperforms the best tube receiver, and has all advantages of solid state design . . . low power consumption, high stability and reliability.

Model SPR-4 \$499⁹⁵
Amateur Net

ACCESSORIES: Noise Blanker, 100 kHz Calibrator, MS-4 Speaker, AL-4 Loop Antenna for .15-1.5 MHz, Transceiver Adaptor (T-4XB), DC Power Cord, Crystals.

PROGRAMABLE for any interest . . . SWL, Ham, lab, BC, marine, etc. • Only FETs in signal path • Linear VFO with 1 kHz readout • Covers 150-500 kHz plus any 23 ranges (500 kHz wide) .500-30 MHz • 10 ranges furnished, others \$5.00 each • Coverage easily changed • 3 band-widths: 0.4, 2.4 and 4.8 kHz for CW, SSB and AM • Built-in sprk • Notch filter • 115 or 220 VAC, or 12 VDC • Dimens: 10¾" W x 5½" H x 12¼" D, Wt. 14 lbs.

Available at your local distributor.

R. L. DRAKE COMPANY



540 Richard Street
Miamisburg, Ohio 45342

BOOKS

COMPONENTS

TRY QRP

"SOLID-STATE QRP PROJECTS"
by Ed. Noll W3FQJ

FET Rigs	Xtal & VFO
BIPOLAR Rigs	CW & AM
IC Rigs	DSB
QRPP Rigs	½, 1, 2, 10 Watters
Antennas	And more

PRICE \$4.25 (\$5.00 Foreign) 128 Pages

QRP FET'S

TWO 1.8W POWER FET'S
SILICONIX 2N3970

For Experimental Use
Plus Complete Circuits and Instructions

Crystal Osc. & Amp
Push-Pull Xtal Osc.

PRICE \$10.75 (Pa. res. add 6% Sales Tax)

TRY A TRIANGLE

"73 VERTICAL, BEAM AND
TRIANGLE ANTENNAS"
by Ed. Noll W3FQJ

¼ & ⅝ Verticals	Low-Band Triangles
Phased Verticals	Triangle & Parasitic
Phased Horizontals	Turnstile
Yagi's	Double Triangle
Quads	Three-Band Triangle

PRICE \$4.95 (\$5.95 Foreign) 160 Pages

40M

TURNSTILE TRIANGLE

DOES A FINE JOB ON
10, 15 and 20 TOO

Parts and Complete Instructions
(does not include mast or line)

PRICE \$12.75 (Pa. res. add 6% Sales Tax)

TRIANGLE ANTENNAS

BOX 276 • WARRINGTON, PA. 18976

flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be type-written or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

LISTING SERVICE — Gear to sell? Need Rig? Sellers - \$1.00. Lists information year. Buyers - Free. SASE brings details. Listing Service, Box 1111, Benton Harbor, MI 49022.

WANTED: SELF-SUPPORTING crank-up tower. At least 50'. Von Stafford, K4VUY, 8316 Denise Drive, Louisville, Ky. 40219. 502-969-5414.

ORIGINAL EZ-IN DOUBLE HOLDERS display 20 cards in plastic, 3 for \$1.00, 10 for \$3.00 prepaid. Guaranteed. Patented. Free sample to dealers. Tepabco, John K4NMT, Box 198R, Gallatin, Tenn. 37066.

WANTED. Will pay \$15 for following set of unutilized Ham Radio. April, June, July, Sept., Dec. 1968; Jan., April, July 1969. John Gibson, 1305 Tevlin, Berkeley, Calif. 94706. Phone TH9-1051.

HEATH HX-30 6M SSB/AM/CW xmtr \$135, Gonset 6M linear model 3063 with extra output tubes \$45, Motorola 6M 60W FM xtal controlled receiver and xmtr (PA8671A) strips \$50. Paul Sobel, WA6HMV, 755 E. Pine, Altadena, Calif. 91001.

ASK FOR FREE LIST of used Ham gear or for prompt personal attention on any new gear. Mail your order direct to VanSickle Radio, W9KJF, Indianapolis, Indiana 46205. 40 years experience.

CODE PRACTICE TAPES - Novice - General - Extra Class - Specify - \$8.00 each. W9CJJ, 1105 Schaumburg Road, Schaumburg, Illinois.

PHOTORESIST: Make professional PC boards at home with no special equipment. 10¢/board. Send 25¢ for information and instructions or \$2.00 for 1 oz. of photoresist. Information included. S&H Electronics, Dept. A, P. O. Box 286, Corvallis, Ore. 97330.

MOTOROLA FM — 2 meters; U43GGT, 40 watts output, transistor supply, very clean, with cables and control head, less crystals - \$145.00. 80D Transmitter strip - \$15.00. Sensicon A Receiver - \$20.00. Complete 80D, Dynamator supply with cables and head - \$40.00. WA1INO, P. O. Box 587, Manchester, Conn. 06040.

MECHANICAL FILTERS: 455 Khz. 2.1 Khz \$18.95. 300 Hz \$22.95. J. A. Fredricks, 314 South 13th Ave., Yakima, Washington 98902.

CANADIANS — Racal RA17-C12 C/W RA63SSB and RA137-B-LF components. 10KC thru 30MC. RX. Details contact G. Stewart, 26 Dominion Bay, Thompson, Man. 677-5802.

RADIO CONTROLLED GARAGE DOOR OPENER. Om's! Be kind to your XYL and your car. Now the car will be where it belongs; in the garage. Not a kit. Shipped ready for installation with easy to follow instructions. Write for free brochure and price information. You'll be pleasantly surprised. Radio Door Co., P. O. Box 282, Pomona, New York 10970.

QSLs. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

TOROIDS! Lowest price anywhere. 40/\$10.00 POSTPAID (5/\$2.00). center tapped, 44 or 88mhz. 32KSR page printer, reconditioned, perfect \$225. MITE UG41KSR page printer, reconditioned, \$250. Mod28 Sprocket to friction kit, \$25. 28LBD TD, \$70. 28LPR repert with gear shift, \$170. Model 15KSR, \$65. Matching RA87P.S. Unused, \$7. Lorenz 15KSR, \$75. Sync motors, \$7. 14TD, \$20. DPE punch, \$14. HP200CD Oscillator, \$95. R390/URR, \$550. 11/16" tape, 40/\$10.00. 33ASR, complete, \$700. Stamp for listing. Van W2DLT, 302H Passaic, Stirling, N. J. 07980.

"HOSS TRADER ED MOORY" says he will not be undersold on Cash Deals! SHOP around for your best price and then call or write the "HOSS" before you buy! **NEW EQUIPMENT:** New "Demo" Galaxy GT-550 with warranty, \$389.00; New Rohn 50 Ft. Foldover Tower prepaid, \$219.00; New Mosley Classic 33 and Demo Ham-M Rotor, \$205.00; Waters 335 Coaxial Switch, \$8.75; New YAESU Fdx400 VFO, \$79.00; New Swan 270B Cygnet, \$405.00 freight prepaid; **USED EQUIPMENT:** Drake TR-4, \$449.00; R4-B, \$349.00; T4XB, \$365.00; Ham-M Rotor, \$85.00; 2A, \$125.00; SPR-4, \$369.00; Swan 250 (6 meter), \$225.00. Moory Electronics Co., P. O. Box 506, Dewitt, Arkansas 72042. Phone (501) 946-2820.

WANTED R390, R390A, R389, 51J4, 51S1, Racal, Nems, Clarke, Marconi receivers. SWRC, P. O. Box 10048, Kansas City, Missouri 64111.

DON'T BUY QSL CARDS from anyone until you see my free samples. Fast service. Economical prices. Little Print Shop, Box 9848, Austin, Texas 78757.

"DON AND BOB" NEW GUARANTEED BUYS. Dealer Tempo, Kenwood. Write specifications. Monarch KW SWR-Relative Power Dualmeter Bridge, now 14.95; Regency HR2 2M. FM (reg. 229.00) 195.00; Hygain TH6DXX 139.00; Hyquad 104.00; Swan 500CX 470.00; Mosley Classic 35 134.00; Ham-M 99.00; TR44 59.95; RCA 6LQ6 3.50; Motorola HEP 170 2.5A 1000PIV Epoxy diode 39¢; Amperex 8802 300Z 32.00; 6146B 4.45; Write quote Drake SPR4. Prices FOB Houston. GECC finance. Madison Electronics, 1508 McKinney, Houston, Texas 77002. (713) 224-2668.

TRANSCEIVER SR-150 and P-150C, complete with crystals for five bands and calibrator, excellent condition. Also Turner SSB mike, new. \$300 plus shipping. McFolIn, WA4WRU, 710 Dellwood Road, Huntsville, Alabama 35802.

WAB CONTEST. The Cannock Chase Amateur Radio Society is hosting several contests for certificate hunters looking for the Worked All Britain (WAB) award. These contests include all bands from 1.8 to 28 MHz, with both cw and phone sections. Frequencies are divided in'to two groups: HF 14, 21 and 28 MHz, and LF, 1.8, 3.5 and 7 MHz. HF phone contest is 14 March; HF cw contest is 28 March; LF phone contest is 4 April; LF cw contest is 11 April. For more information, write to C. J. Morris, G3ABG, 24 Walhouse St., Cannock, Staffs., England.


SURPLUS MILITARY RADIOS, Electronics, Radar Parts, tons of material for the ham, free catalogue available. Sabre Industries, 1370 Sargent Ave., Winnipeg 21, Manitoba, Canada.

TELL YOUR FRIENDS about Ham Radio Magazine.

NEW G&G CATALOG! MILITARY ELECTRONICS

24 PAGES, crammed with Gov't Surplus Electronic Gear - the Biggest Bargain Buys in America! It will pay you to for your copy - Refunded with your first order. **SEND 25¢**

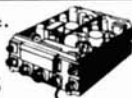BC-645 TRANSCEIVER 15 tubes, 435 to 500 Mc. Easily adapted for 2 way voice or code on Ham, Mobile, Television Experimental, and Citizens bands. With tubes, less power supply in factory carton, BRAND NEW..... **\$16.95**



TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7
RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7
RECEIVER I.F.: 40 Megacycles
SIZE: 10-1/2" x 13-1/2" x 4-1/2". Shpg wt 25 lbs.

SPECIAL PACKAGE OFFER: BC-645 Transceiver, Dynamotor and all accessories, including mounting, UHF Antenna Assemblies, control box, complete set of connectors and plugs. Brand New **\$26.95**

AN/APR - 4Y FM & AM RECEIVER "FB" for Satellite Tracking! High precision lab instrument, for monitoring and measuring frequency and relative signal strength, 38 to 4000 Mc. in 5 tuning ranges. For 110 v 60 cycle AC. Built-in power supply. Original circuit diagram included. Checked out, Perfect. LIKE NEW..... **\$88.50**



TG-34A CODE KEYS, self-contained, automatic, reproduces code practice signals from paper tape. 5 to 12 WPM Built-in speaker. Brand new with tech manual, takeup reel and AC line cord. ... **\$24.50**
Code practice tapes for above P.U.R.



WILLARD 2-VOLT STORAGE BATTERY Rated at 20 Amp.-Hours. Model 20-2. Rechargeable. Compact nonspill construction. Lightweight polystyrene container, 3x4x5 1/2". Shipped dry, uses standard electrolyte. Shipping Weight 3 lbs. NEW, each..... **\$2.79**



HEADSET Low impedance. With large chamois ear cushions. 4-ft. cord and plug. Reg. \$12.50. OUR SPECIAL PRICE..... **\$2.95**
High impedance adaptor for above 69¢



SCR-274-N, ARC-5 COMMAND SET HQ!

FREQ. RANGE	Type	Exc. Used	Like New	BRAND NEW
RECEIVERS.	Complete with Tubes			
190-550 Kc.	BC-453	\$16.95	\$23.50	\$27.50
3-6 Mc.	BC-454	\$16.50	\$19.50	\$22.50
6-9.1 Mc.	BC-455	\$14.95	\$17.95	\$21.50
1.5-3 Mc.	R-25		\$19.50	\$21.50
TRANSMITTERS.	Complete with Tubes			
4-5.3 Mc.	BC-457	\$ 8.95		\$11.95
5-3.7 Mc.	BC-458	\$ 8.95		\$11.95
7-9.1 Mc.	BC-459			\$23.50

ARC-R11A Modern Q-5 Receiver 190 - 550 KHz **\$10.95**
ARC-R22 540 - 1600 KHz Receiver with tuning graph **\$15.95**
R-4/ARR-2 Receiver 234-258 Mhz, 11 tubes, NEW **\$8.95**

SCR-625 ARMY MINE DETECTOR Complete **\$32.50**
EE-8 SIGNAL CORPS FIELD PHONES..... **\$16.95**
T-30 THROAT MIKE, NEW..... 59¢ USED, checked out \$4.95
T-17 MICROPHONE, NEW.....\$8.50 USED, checked out \$4.95
BC-605 INTERPHONE AMPLIFIER, NEW \$3.45 EXC. USED..... **\$1.95**
TELEPHONE HANDSET, W.E. type..... LIKE NEW **\$2.95**
SCR-522 TRANSMITTER-RECEIVER, with 18 tubes. LIKE NEW \$32.50

AM-300/AIC PUSH-PULL AMPLIFIER 4-tube PP power amplifier with dynamotor, works on 28 VDC. Automatic gain control. Shpg wt 15 lbs. LIKE NEW..... **\$4.95**



FREQUENCY METER MODEL LM Fine general purpose Navy unit, range 125 to 20,000 Kc. Operates on 12/24 VDC & 200V 10 Ma DC. Complete with tubes, crystal, calib. book. Checked out, EXCELLENT USED..... **\$59.50**
As above, less book \$24.50 AC Power Supply, \$19.50



McELROY AUTOMATIC KEYS for keying transmitter or for code practice. Photoelectric cell & sensitive relay. Variable speed motor 110V 60 cy. Complete with tubes, EXC. USED **\$11.25**



BC-733 RECEIVER Receives radio signals being transmitted by US satellite on approx. 108 Mc. AM, crystal-controlled on 6 preset freqs. in 108.3 to 110.3 Mc range. Operates on 12/24 V DC & 220 VDC 80 Ma. Complete with 10 tubes. Can be converted to FM Receiver
80 to 108 Mc, Exc. Used..... **\$5.95**
BC-732A Control Box for above, NEW.... 1.75



T-41 / APS - 18 TRANSMITTER ANTENNA UNIT designed for 115 V 800 to 1400 cps. Tubes included are two 15E and one 15R. Complete with shock mounts and blower motor. 7x8x18", NEW.... **\$7.45**



RADIO SET AN/ APR-21 TRANSMITTER & RECEIVER . Freq. modulated 152 to 174 Mc. Operated on any preset frequency within VHF range 152-174 Mc FM. Reliable voice communication over moderate distances. Includes antenna, handset H-33 and two carrying straps. Size 12x8-1/4x5-3/4. Wt 15 lbs. LIKE NEW, complete **\$69.50**



AM-26/AIC PHASE INVERTER AMP. 4-tube pushpull power amplifier. Carbon mike input, hi-lo imp. output. Works on 24VDC. Easily converted to dandy 9-watt amplifier. Complete with tubes and dynamotor LIKE NEW **\$6.95**



DUAL AMPLIFIER has two input circuits each feeding a single 6SN7GT twin triode amplifier. Complete with 115V 60 cy. power supply using 6X5GT rectifier. NEW..... **\$5.95**



IP-69A/ALA-2 INDICATOR 3" scope. Front panel controls: Vertical Pos., horizontal pos. intensity, focus, gain, width, center freq. Pan. Operates on 115 V 380 to 1000 cps. Complete with tubes..... **\$24.50**



BC-929 US GOVT SCOPE INDICATOR Compact radar display unit uses 3BP1. A favorite with TTY fans as foundation for converter with cross-line scope presentation. Also for Hams: Modulation-monitor foundation. Complete with all tubes. LIKE NEW..... **\$16.95**



TG-5B TELEGRAPH SET for code communications or code practice. Portable, with hinged lid. Two or more units operate up to 25 miles apart. Bell call system, 1000 cycle howler, key, headpiece, canvas case, book. Size 5-1/2x5-1/2x10". NEW..... **\$8.95**



TS-100AP TEST OSCILLOSCOPE Small portable instrument used to test and calibrate range measuring circuits of radar systems. Used for viewing short video pulses on 3" screen. Power supply: 115 or 230 V 50-1200 cps. Complete with plugs, cables..... **\$59.50**



TS-126/AP RANGE CALIBRATOR TEST SCOPE Top quality 2" scope with all positioning, focus, gain and intensity controls. Complete with tubes and cables, NEW. **\$24.50**
Demilitarized, like new..... **\$13.75**



TELEPHONE TYPE RELAY Made by J.H. Bunnell, has adjustable sensitivity. 150 ohm coil. NEW..... **\$3.45**



T-28 / APT TRANSMITTER radar jamming covering freq. 140 to 210 Mc. Osc. Amp. Plate, Grid Plate & Mixer Plate controls on front panel. Complete with tubes. 7-1/2x10x20" Wt 40 lbs. NEW..... **\$32.50**



TERMS: 25% Deposit with order, balance C.O.D. -or- Remittance in full. Minimum order \$5.00 F.O.B. NYC. Subject to prior sale and price change

G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. [2nd Fl.] New York, N.Y. 10007 Ph. 212-267-4605

QSL'S — BROWNIE W3CJI — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cut catalogue 25¢.

VIRGINIA STATE ARRL CONVENTION — May 22-23. War Memorial Building, Vinton, Va. Largest Flea Market in the Roanoke Division. All dealers invited. All space free. Saturday night Round & Square Dance. \$1.00 per person. Registration: \$1.50 ea, 4 for \$5.00. Write: Roanoke Valley ARC, Van Wimmer, WA4BIX, Rt. 4, Box 446, Salem, Va. 24153

STOLEN from Red Cross emergency communications truck in Wichita, Kansas: Drake R-4B Receiver serial #11125G; Drake T-4XB transmitter serial #16428R; Gonset "Communicator II" 2M Transmitter-receiver; Gonset 2M VHF Power Amplifier. Anyone with information contact the Wichita Police Dept., 114 E. William, Wichita, Kansas 67201, phone 316-262-2611.

MICHIGAN — 24,000 square ft. for the Blossomland Amateur Radio Association 4th annual auction and Swap-Shop at Shadowland Ballroom, St. Joseph-Benton Harbor, Mich. Sunday, March 14th 9:00 a.m. to 4:00 p.m. Hot food. Prefer to do your own selling? Rent one of our swap tables. If that fails let our skilled auctioneer put your gear on the block. Direct inquiries to B.A.R.A., Box 175, St. Joseph, Michigan 49085.

TELETYPE #28 LRXB4 reperforator-transmitter "as is" \$100; checked out \$175. Includes two 3-speed gearshifts. Alltronics-Howard Co., Box 19, Boston, Mass. 02101. 617-742-0048.

UHF BASE STATION Antenna for sale. Comm. Products #541-509 7db omni 10db offset. With clamps, like new. Andrew Mueller, Germantown, Wisconsin 53022.

HRO-60. "B" slicer, manuals, A,B,C,D,AC coils and case, headphones, some spare tubes, excellent condition. 8 40m. xtals, 6 position xtal switch, \$35, best offer. You ship. Jon Ahlquist, 205 Bender, University of Northern Iowa, Cedar Falls, Iowa 50613.

SELL: SB-101 with 400 Hz filter, SB-600 and HP23A \$370; SB-500 2M transverter 28 MHz IF \$169; Hallicrafters HA-6 6M transverter wth supply \$150; Eico 753 transceiver and 751 supply \$150; beautiful homebrew 6M linear, single 7034 \$50 less HV supply. James Coulter, K8HKQ, 191 Union, Hillsdale, Michigan 49242.

GREENE — center of dipole insulator with or without balun . . . also the GREENE DRAGON FLY antenna . . . send for free flyer GREENE, Box 423, Wakefield, R. I. 02880. WICPI.

826 TUBES wanted for cash. C. Hutnan, 308 Hickory Street, Kearny, N. J. 07032.

IMPORTANT — ROCHESTER location for W.N.Y. Hamfest and VHF Conference, May 15th, has been changed. Send for map and program. Write WNY Hamfest, Box 1388, Rochester, N. Y. 14603.

THE CHICAGO SUBURBAN RADIO ASSOCIATION will hold its annual "Hamboree" on March 21, 1971 at the Operating Engineers Hall, 9200 West Joliet Road, La Grange, (Countryside) Illinois. All Hams and the public are invited. The latest amateur radio equipment will be on display. All Hams are invited to come out and display or sell any products or items they wish free of charge. The exhibit hall has 10,368 square feet of exhibit space. Ample padded parking space will also be available at no added charge. Drawings for three grand prizes valued at \$1000 plus a number of lesser value prizes will be held during the one-day Hamboree. All those who attend will be eligible for the drawings. A donation of \$1.50 per person at the door. Advance tickets for only \$1.00 may be purchased from: Mr. Wilson Thomas (W9KWA), 4017 Vernon Avenue, Brookfield, Illinois 60513.

AM PREPARING an article on busy and creative persons over 65. Would like to get in touch with any who are hams. L. H. Dick, R. D. 3, Box 374, Newton, N. J. 07860.

NOVICE CRYSTALS: 40-15M \$1.38, 80M \$1.83. Free flyer. Nat Stinnette Electronics, Umatilla, Florida 32784.

BOOKS: Don't miss our ad on pages 48 and 49 Comtec.

See your
DEALER
for
DRAKE
products



**MONARCH
SWR AND
POWER
METER**

Reads output and reflected power simultaneously. May be left in line up to 2000 watts. Low insertion loss. Size 5x2x2. Good to 175 Mhz.

PRICE \$14.95 Insured Postage & Handling \$1.50

MADISON ELECTRONICS SUPPLY

1508 MCKINNEY — HOUSTON, TEXAS 77002

(713) 224-2668

radio amateur
callbook

Radio Amateur
Emblems engraved
with your call letters.



Charm

Gold
 Rhodium
call letters
\$6.00 Ea.



Tie Bar

Gold
 Rhodium
call letters
\$6.00 Ea.



All illustrations
are actual size.

Lapel Pin

Gold
 Rhodium
call letters
\$6.00 Ea.

Two or more emblems at the same time \$5.00 each.

Rush Order To: RADIO AMATEUR CALLBOOK, Inc.
Dept. E. 925 Sherwood Drive, Lake Bluff, Ill. 60044

BARRY

COAXIAL DUMMY LOAD B & W Waters CDL-1K. 1500 Watt Ohm Dummy Load. DC to 150 Mhz. Brand new with built-in Fan (115 VAC) Orig. \$280.00 net. **Sale \$80.00**

B&W/WATERS TPC-120 W Transistor Power Supply. 120 Watt 12 V. Input 500/250/660 Volts out at 120 Watt total. Brand new. (2 lbs.) Reg. \$57.80 **Sale \$36.00**

WATERS MODEL 346 Nuverter. 2 & 6 M VHF converter. New. Orig. \$175.00 net. **Sale \$80.00**

B & W BBC-3.5 K PLATE CHOKE. 2 to 30 Mhz, 5 KV and 2 amperes. Brand new. Orig. \$25.00 plus. **Sale \$6.00**

COLLINS — 75A1 Receiver \$195.00
COLLINS — 75A4 Receiver \$350.00

COLLINS — 32V2 Xmtr \$175.00
TMC — GPR-90 RDX w/TMC GSB-1 — (a \$2000. net value) \$495.00
HP-415B SWR METER, good @ \$89.95
HP-5214L PRESET COUNTER, xInt @ \$495.00
HP-491A TWT AMPLIFIER, 2-4 GHZ @ \$125.00
HP-492A TWT AMPLIFIER, 4-8 GHZ @ \$125.00
HP-430CR BOLOMETER BRIDGE, good @ \$89.95
HP-200AB AUDIO OSCILLATOR, needs work @ \$75.00
HP-X810B SLOTTED SECTION, good @ \$39.95
HEATH IO-18 5" LAB SCOPE new, wired @ \$95.00

SILICON BRIDGE RECTIFIER. Tested at 6000 volts and 1 Amp. (4 separate rectifiers mounted on Nylon card.) 2 oz. **Sale \$4.95**

RAYTRACK DX 2000L. 2000 W. PEP Linear Amplifier. 10 thru 80 meters. (115 V or 230 aAC @ 50/60 Hz.) Uses pair of Eimac 3-500Z's. \$699.00 with separate 42 lb. supply.

ROTRON HIGH-POWER BLOWER. 110/220V. 50/60 Hz, 3350 RPM. 6" Dia. wheel. 1 1/4" x 2 3/4" (r/e) **\$17.95**

COLLINS CHOKES: 4 Hy @ 500 Ma. 2.5 KV at 9.95; 12 Hy @ 500 Ma. 12 KV at \$19.95

D.P. TRIPLE THROW HEAVY DUTY R.F. SWITCH. 2 KW. Ceramic insul. Sil. plated contacts. \$6.95

4 SECTION 4 POLE MULTI-POSITION SWITCH. Ceramic insul. Silver plated contacts **\$9.95**

1000 WATT INLINE WATT METER. 1000 Watts continuous, 2-30 Megahertz, Dummy Load Position, 3 scales: 0-10, 0-100, 0-1000 Watts, VSWR Function, 50 Ohm impedance. This 1000 Watt wattmeter absorbs negligible power; continuously monitors radiated power. A two-way load switch permits rapid change from dummy load to antenna, or between two antennas. **NEW. Only \$39.95**

WIDE-VUE 4" PRECISION METER, 0-1 MA, brand new @ \$4.99

HALLICRAFTERS SX-73, SIMILAR TO SP-600 @ \$295.00

HUNTER BANDIT 2000B, with (4) new 572B tubes @ \$275.00

HATFIELD (ENGLISH) DELUXE BALUN MODEL B60 (52 to 75 ohm) @ \$9.95

HATFIELD (ENGLISH) DELUXE BALUN MODEL B61 (75 to 75 ohm) @ \$9.95

RCA 1000.000 Khz CRYSTAL. Only \$3.50

ROHN GROUND OR ROOF MODEL #25G (40 foot) COMMUNICATIONS TOWER finest heavy guage 1 1/4" steel tubing, hot-dip, galvanized, complete with hardware. **\$207.00**
 (Specify grnd. or roof mount.) FOB factory, Ill.

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LNI. We Buy!

We ship all over the World. DX Hams only. See Barry for the new Alpha 70. (See front inside cover of this magazine.)

Send 35¢ for 104 page catalog #20.

BARRY ELECTRONICS
 DEPT. H-3 — PHONE A/C 212-925-7000
 512 BROADWAY, NEW YORK, N. Y. 10012

DRAKE C-4

Station Console puts you in COMPLETE CONTROL



Puts complete station control at operator's fingertips . . .

Model C-4 \$299⁹⁵
 Amateur Net

- 24 hour digital clock—lighted, shows correct time to the second
 - Solid state resettable timer flashes light at identification intervals
 - Station power control with eight 120 VAC and two 240 VAC receptacles, front panel controlled heavy duty power contractor
 - Equipment control switch for changing exciters, rcvrs., etc.
 - Directional RF wattmeter with 200 or 2000 W full scale
 - Built-in rotor control for Ham-M
 - Electronic phone patch gives const. xmtr input, works PTT, meets phone co. requirements
 - Remote motor-driven coax switch selects from 5 antennas
- Dimens:** 10 3/4" W x 5 1/2" H x 12 1/4" D., **Wt.** 24 lbs.

Available at your local distributor.

R. L. DRAKE COMPANY



**540 Richard Street
 Miamisburg, Ohio 45342**

THE ONLY AUTHORITATIVE QRPP handbook: The Milliwatt: National Journal of QRPP, 125 pages, 10 QRPP transmitters, 2 receivers, accessories; Operating News, Log Selections, QRPP WAS/DXCC standings; articles on technical subjects for the QRPP operator. Volume I, \$4.00. SASE for table of contents. Ade Weis, K8EEG/O, The Milliwatt, Meckling, SD 57044.

THE MAARC ANNOUNCES the 1971 ARRL Great Lakes Division Convention. Date: March 27, 1971. Place: Muskegon Community College, Quarterline Road, Muskegon, Michigan. Advance tickets \$2.00, at the door \$2.25. Large swap & shop, meetings for all MARS programs, VHF repeater program, net & traffic meetings, RTTY forum program, Ham TV program, races-CD program, midcars program, QWCA meeting, and many more. Complete luncheon facilities, parking for over one thousand cars. Easy access: Interstate 196 & US-31 to Muskegon; Junction of US-31 & Michigan 46. Complete new and comfortable facilities. Muskegon Area ARC, Box 691, Muskegon, Michigan 49443.

TRADE, SELL: Used receivers. Trade for new amateur equipment. Available HQ-180C, R-4A, HQ-200, NC-190, SX-110, 2B, HW-16, GPR-90, SX-130, Eimac 4-1000A, PL 8160/4-1000A, S-Line, Nems-Clarke 1456A, S-36. Send for current list. Steven Kullmer, Evergreen Hatchery, Dysart, Iowa 52224.

SETH THOMAS DIGITAL CLOCKS with seconds indication reg. \$27.95 value only \$13.95 postpaid while they last. Laboratory clear, for sale or trade: Singer Metrics Spectrum Analyzer SPA#3 200CPS-15M R/mount \$800.00 new cost \$3500.00, HP520A 10 MC scaler R/mount \$75.00, GR805C sig. gen. 500KC-50MC cal. output \$250.00, ME74/U AC VTVM like new \$50.00, TS375A/U AC-DC VTVM like new \$50.00, SP 600 JX rec. 500KC-54MC retubed recal. our lab. \$275.00, manuals are included all units. Want HP608D,E,F, or 390A series rec. Wawasee Electronics Co., P. O. Box 36, Syracuse, Indiana 46567.

ELECTRONICS YOUR BAG? Looking for an electronics course . . . that you can pay for by the subject AND take ONLY the subjects you NEED? . . . that you can change into ANY PHASE of electronics after completion of basics WITH NO PENALTY? For full information, write: EDCO ENTERPRISES INC., P. O. Box 432, Sparks, Nev. 89431.

TOROIDS 44 and 88 mhy. Unpotted, 5 for \$1.50 ppd. W. Weinschenker, Box 353, Irwin, Pa. 15642.

WORLD QSL BUREAU — See ad page 90.

PLEASE, need type H coil for old HRO receiver. Also want J & G, Cash or trade. W2IMB, P. O. Box 721, Westfield, N. J. 07090.

WANTED: JOHNSON VIKING NAVIGATOR transmitter. WA9WGT, tel: 715-623-3107.

MANUALS — R-390/URR, R-390A/URR, BC-639A, URM-25D, CV-591A/URR, TS-497B/URR, FR-5/U, TS-587B/U, UPM-45, USM-24C, SP-600JX, \$6.50 ea. S. Consalvo, 4905 Roanne Drive, Washington, DC 20021.

WANTED — DUPLEXER for 148.01 MHz receive and 143.99 MHz transmit. State manufacturer, condition, model and price. WA4VNN, 1013 Pecan Drive, Monroeville, Alabama 36460.

COLLINS KILOWATT linear amplifier 30S-1 excellent condition, \$500. K2GW, 100 Webb Ave., Ocean Grove, New Jersey 07756.

VHF NOISE BLANKER — See Westcom ad in Nov., Dec. '70 and Mar. '71 Ham Radio.

THE SPRING AUCTION OF THE ROCKAWAY ARC will take place Friday evening April 23, 1971 at 8:00 p.m. at the American Irish Hall, Beach Channel Drive at Beach 81st St., Rockaway Beach, N. Y. Come to the best auction in the New York Area. For further info write to Al Smith, WA2TAQ, Auction Chairman, P. O. Box 341, Lynbrook, N. Y. 11563.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

See your DEALER for DRAKE products



ANTENNA MATCHING TRANSFORMERS

- 50 ohm co-ax to 50 ohm balanced load (for doublets & inverted vee's) **\$14.95**
 - 50 ohm co-ax to 75 ohm balanced load (for doublets and quads) **\$14.95**
 - 50 ohm co-ax to 75, 120, and 140 ohm load (for single feed three band quad) **\$18.95**
 - Other impedance ratios available on request
- All units are rated at full legal power and shipped post paid. Calif. residents add 5% sales tax.

H & H ENGINEERING

P. O. Box 68, La Mirada, Calif. 90638



Radio Amateurs Reference Library of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables . . . postpaid **\$1.25**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities: Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. . . . postpaid **\$1.25**

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 150 United States and other Countries. . . . postpaid **\$1.25**

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 1/4" x 12" postpaid **\$2.00**

Complete reference library of maps — set of 4 as listed above postpaid **\$3.50**

See your favorite dealer or order direct.

**WRITE FOR
FREE
BROCHURE!**

RADIO AMATEUR
callbook INC.

Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

Extended "SAROC" Bonus



Galaxy GT-550

- More Power
- More Sensitivity
- More Stability
- More for Your Money

GALAXY GT-550 TRANSCEIVER \$550.00
 GALAXY AC-400 AC POWER SUPPLY 99.95
 HY-GAIN TH3MK3 TRI-BAND BEAM No Charge
 (Regular Ham Net \$144.95)

Complete Package Only \$649.95
 (\$794.90 Value)

L.A. Electronix Sales

"Home of L. A. Amateur Radio"

23044 CRENSHAW BLVD., TORRANCE, CALIF. 90505
 213-534-4456 — 213-534-4402

Add just \$25.00
 to replace AC-400 with
G-1000 DC Supply

U.S.A. Coin Guide

Show the value of over 1400 United States coins. Only \$1.00.

BELLS COIN SHOP

Box 276
 Tolleson, Arizona 85353

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 4¢ each.

5200 Panama Ave., Richmond, CA USA 94804

NEW! REPEATER IDENTIFIER!

The black box you've been asking for...

- YOUR MCW OR CW ID EVERY 3 MINUTES
- ALL SOLID STATE, -12 TO -28VDC
- 100VA CARRIER RELAY, AUDIBLE MONITOR
- MEETS FCC REQUIREMENTS, -40 TO +140°F

Complete, programmed (DE YOUR CALL).

\$129.95 plus shipping (4 pounds)

Box 4090, Mountain View, California - 94040

CURTIS ELECTRO DEVICES



SURPLUS CRYSTAL FILTERS

6 XTAL-11.5 MHZ-36 KHZ 6DB BW-MOD EL-3A \$14
 60 DB BW 100 KHZ MAX - 50 OHM TERMINATIONS
 MATCHING XTAL DISCRIMINATOR - MOD. AL-1 \$10
 TO ±15 KHZ DEVIATION-DOPE SHEET INCL.

10.7 MHZ-13 KHZ 6 DB BW - 8 XTAL-MOD. F8-5M \$19
 60 DB BW 25 KHZ MAX - 1000 OHMS IN & OUT

10.7 MHZ-30 KHZ 6 DB BW - 6 XTAL-MOD. 10-MA \$14
 60 DB BW 75 KHZ MAX - 2000 OHMS IN & OUT

10.7 MHZ-XTAL DISCRIMINATOR - MODEL AB-1C \$16 L. 2 3/8
 TO ±15 KHZ DEVIATION-TEST CKT INCL. W. 1.0

FREE CATALOG-FILTERS AND CORES-NEW & SURPLUS H. 1/32

TOROID CORES

CARBONYL "E" TOROID CORES
 2" DIA. T-200-2 EACH \$2.75 OR 3 FOR \$7.00
 .69 DIA. T-68-2 EACH 50¢ OR 7 FOR \$2.75
 .50 DIA. T-30-2 EACH 45¢ OR 8 FOR 2.75

MINIMUM POSTPAID ORDER 2.75 TOTAL

J. T. McCULLOUGH, W0BHG

E. S. Electronic Labs
 301 AUGUSTUS, EXCELSIOR SPRINGS, MO. 64024



QSO W¹ T^H W2CFP

IS HEARD OVER
WHCU
 IN ITHACA, NEW YORK
 EVERY SATURDAY

For further information, contact Dave Flinn, W2CFP, 10 Graham Rd. W., Ithaca, N. Y. 14850, (607) 257-2424. Watch for Dave and his tape recorder at Hamfests and Conventions throughout the country.

20th Anniversary DAYTON HAMVENTION 24 April 1971

Wampler's Hara Arena

Technical Session • Exhibits • Ladies Program • Hidden Transmitter Hunt • Flea Market • Awards • Banquet

Dept: Box 44, Dayton, Ohio 45401

WE PAY **HIGHEST**
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS

H & L ASSOCIATES

ELIZABETHPORT INDUSTRIAL PARK
ELIZABETH, NEW JERSEY 07206
(201) 351-4200

FIRE & BURGLAR ALARMS

1971 Handbook & Catalog



Save
Hundreds
of
Dollars

Professional equipment from famous manufacturers. Easy step by step illustrated instructions, no special tools required. Save up to 75%. This handbook is a must for every homeowner and businessman. Just \$1 cash, check or M.O.


**ALARM COMPONENT
DISTRIBUTORS**

33 NEW HAVEN AVE., DEPT. HR
MILFORD, CONN. 06460

See your
DEALER
for
DRAKE
products

TYMETER[®]

"Time At A Glance"

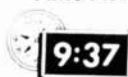

**24
HOUR
CLOCK**



= 100-24H

\$16

Made in
U.S.A.

At Your Dealer, or
DIRECT FROM

Walnut or ebony plastic case.
4" H, 7 3/4" W, 4" D. 110V 60
cy. Guaranteed One Year.

PENNWOOD NUMECHRON CO.

TYMETER ELECTRONICS

7249 FRANKSTOWN AVE. PITTSBURGH, PA. 15208

AMATEUR LUNCHEON CLUB
SSB ANNUAL DINNER
at the ENGINEERS CLUB
32 West 40th Street, New York City

MARCH 23, 1971, Noon
Limited Seating
Tickets available through W2PF



ELECTRONIC FIST ... THE PROFESSIONAL KEYSER

Every feature you need for easy, accurate CW

- IAMBIC FOR SQUEEZE KEY'ers
 - VARIABLE WEIGHTING FOR DX'ers
 - MESSAGE GENERATOR FOR CONTEST'ers
 - COLORS TO MATCH YOUR RIG
- KIT OR WIRED. PRICES START AT \$69.95
WRITE FOR SPECIFICATIONS

CURTIS

ELECTRO
DEVICES

Box 4090, Mountain View, California - 94040

5 India Pennies \$1.00
100 Foreign Coins \$3.95

BELLS COIN SHOP

Box 276
Tolleson, Arizona 85353

**A HANDSOME PAIR
MATCHING
BOUND VOLUMES and BINDERS**

Binders \$3.95

1969 & 1970

Bound Volumes each \$14.95

HAM RADIO MAGAZINE

GREENVILLE, N. H. 03048

Hi-Sensitivity Wide-Band AM / FM RCVR

38-1000 MHz: AN/ALR-5 consists of brand-new Tuner/Converter CV-253/ALR in original factory pack and an exc., used, checked OK & grtd. main rcvr R-444 modified for 120 v, 50/60 hz. Packed with each tuner is the factory checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.3 mhz, 0.9 at 133 mhz, 5 at 538 mhz, 4 1/2 at 778 mhz, 7 at 1 ghz.

With book & pwr-input plug, all for **275.00**

30 MHz Panadapter for the above **97.50**

R-390/URR Rcvr: Collins xtl-zero-beating, driftless rcvr, grtd 100% perfect, w/book **795.00**

R-390A/URR has mech. filters, grtd. perfect **995.00**

SP-600-JX1 0.54-54 MHz perfect, w/book **375.00**

Nems-Clarke 1302B 55-260 MHz AM/FM/CW **495.00**

Regul. Pwr Sply for Command, LM, Etc.

PP-106/U: Metered. Knob-adjustable 90-270 v up to 80 ma dc; also select an AC of 6.3 v 5A, or 12.6 v 2 1/2 A or 28 v 2 1/2 A. With mating output plug & all tech. data. Shpg. wt. 50 lbs. **19.50**

BARGAINS WHICH THE ABOVE WILL POWER:
LM(-) Freq. Meter: 125-200 MHz, .01%, CW or AM, with serial-matched calib. book, tech. data, mating plug. Shipping wt. 16 lbs. **57.50**

Same, less calib. book **12.95**

TS-323 Freq. Meter: 20-480 MHz .001% **169.50**

A.R.C. R22: 540-1600 kHz rcvr, shpg. wt. 9 lb. **17.95**

A.R.C. R32: 108-132 MHz rcvr w/knob and data, shpg. wt. 9 lb. **13.95**

Versatile Plate & Filam. Transformer

Depot Spares for SP-600 JX: Pri. 95/105/117/130/190/210/234/260 v 50/60 hz. Sec. 1: 305-0-305 v. 150 ma. Sec. 2: 5 v 3 A. Sec. 3: 6.3 v 5A. Sec. 4 7 1/2 v, 3/4 A. Sec. 5; 7 1/2 v, 1 1/4 A. Legend for pins is plainly marked. Herm. sealed. Add postage for 13 lbs. **3.95**

Our warehouses are bursting with good OSCILLOSCOPES, Digital Counters, Aeronautical Test Sets, Audio Test Sets, Oscillators, VTVM's, Precision Meters, Pulse Generators, Signal Generators, Differential Voltmeters, Regulated Power Supplies, Ham Receivers, Wattmeters, Line-Voltage Regulators, etc. etc. We can't possibly begin to list every thing in these ads. We have separate Catalogs for each Category of Equipment . . . so please ask for your needs by the type of equipment you need! Thanks!

WE ALSO BUY! WHAT DO YOU HAVE?

R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

NOISE BLANKER

Designed for the serious VHF operator requiring effective suppression of interference generated by auto ignitions, power lines, appliances, radars, etc. Models available for both VHF transmitter and receiver-converter systems.



Model TNB-250, for Swan 250 transceivers. Features include modern solid state design techniques utilizing dualgate MOSFET transistors and a special gain controlled amplifier circuit yielding excellent cross modulation characteristics in strong signal locations. Simplified installation requires twenty minutes without drilling holes.

TNB-250 (for Swan 250) **\$32.95**
TNB-250C (for Swan 250C) **\$32.95**

Model TNB Noise Blanker, designed to operate with VHF converters by connecting in the coax between converter and receiver.



Noise suppression characteristics are similar to those of the TNB-250. Choice of 14 dB, 100 dB, or 125-160 dB. RCA phono or BNC connectors. Specify for 10 or 20 meter converter output.

Model TNB **\$29.95**

Prepaid orders shipped postpaid. For Air Mail add 80¢ COD orders require \$1.00 deposit. All products are warranted for one year and offered on a satisfaction-guaranteed or return basis. Technical brochure available.

WESTCOM

ENGINEERING COMPANY

P. O. Box 1504

San Diego, Calif. 92112

METERS

BIGGEST STOCK IN THE COUNTRY

All are standard AMERICAN made, all BRAND NEW, bought at the NATIONAL VIDEO auction, at exceptional prices. These very large savings passed on to you. These were bought in partnership, with PACER ENGINEERING, Inc. and may be ordered from either address below.

2" square-choice-\$2.50 each

0-25 ma DC 0-300v DC 0-15v AC

2 1/2" square

0-500v DC

2 1/2" round-choice-\$3.00 each

0-50 ma DC 0-25 ma DC 0-10v AC

3" square-choice-\$3.50 each

mix or match-4 for \$13.00

0-10v AC	0-150v AC	0- 1 ma DC
0-15v AC	0-250v AC	0- 3 ma DC
0-50v AC	0-300v AC	0- 5 ma DC
0-1 Amp. AC	0- 50v AC	0- 10 ma DC
0-2 Amp. AC	0- 15v DC	0- 25 ma DC
0-3 Amp. AC	0- 50v DC	0-200 ma DC
	0-150v DC	

micro-ammeters-\$4.00 each

0- 25 ua DC 0- 50 ua DC 0-500 ua DC
0-100 ua DC

center scales-\$5.00 each

100-0-100 ua DC 50-0-50 ua DC

3 1/2" round-choice-\$4.00 each

mix or match-4 for \$15.00

0- 10v AC	0-100v DC	0- 5 ma DC
0- 15v AC	0-10 Amp. AC	0- 6 ma DC
0- 25v AC	0-20 Amp. DC	0- 10 ma DC
0-150v AC	0- 1 ma DC	0- 25 ma DC
0- 15v DC	0- 3 ma DC	0-100 ma DC

4 1/2" square-\$5.50 each

mix or match-4 for \$20.50

0-10v AC	0- 10v DC	0- 1 ma DC
0-15v AC	0- 50v DC	0- 3 ma DC
0- 1 Amp. AC	0-100v DC	0- 5 ma DC
0- 3 Amp. AC	0-150v DC	0- 10 ma DC
0-15 Amp. AC	0-300v DC	0- 50 ma DC
0-25 Amp. AC	0-750v DC	0-250 ma AC

micro-ammeters-\$6.00 each

0- 15 ua DC 0-100 ua DC 0-200 ua DC
0- 25 ua DC 0-500 ua DC

center scale ua meters-\$7.50 each

15-0-15 ua DC 100-0-100 ua DC

Other meters, just received, also terrific bargains.

10-0-10 ua DC, CONTROL METER, with dual adjustable settings for control, 5 terminals on back. 3 1/2" square, wide view plastic. Made by API, taut band. Take-outs, in excellent, guaranteed condition. 4 for \$57.50 \$15.00 each

10-0-10 ua DC. 3 1/2" ROUND SIMPSON. BRAND NEW. 4 for \$32.00 \$8.50 each

0-1 ma DC. White figures on black background. Scales: Final plate 0-500 ma; grid 0-10 ma; output RF 0-10. No shunts or therocouple. 5000 ohm internal resistor. 2 1/2" wide view, square, plastic case. JAP. MADE. 4 for \$10.35 \$2.75 each

All items subject to prior sale. Prices are NET, FOB store. PLEASE — include sufficient for postage. Any excess returned with order.

PACER ENGINEERING, INC.

13911 LINCOLN AVE.
DOLTON, ILLINOIS 60419
312-841-6663

BC ELECTRONICS

1249 W. ROSEDALE AVE.
CHICAGO, ILLINOIS 60626
312-334-4463 & 784-4426

NEW from **BLULYNE**



Model SG-10 Function Generator

- ULTRA LINEAR RAMP GENERATOR
- SQUARE WAVE GENERATOR
- PULSE GENERATOR (width adjustable 0-100%)

Frequency Range 0.1 Hz to 100 kHz with continuous control

Variable Amplitude Control

Rise times less than 200 nanoseconds

Excellent stability on all ranges

Reliability and Quality Without High Cost

Model SG-10 Function Generator Only \$69.00



BLULYNE

WILLIAMSTOWN • MASS. 01267



VHF COMMUNICATIONS

A PUBLICATION FOR THE RADIO AMATEUR
ESPECIALLY COVERING VHF, UHF AND MICROWAVES

VHF COMMUNICATIONS is the only truly international publication devoted entirely to VHF and UHF amateur radio technology.

VHF COMMUNICATIONS is written for and by amateurs interested in modern VHF/UHF technology and equipment construction. Each issue contains at least sixty pages of complete and carefully detailed construction articles on VHF and UHF receivers, converters, transceivers, transmitters, transverters, antennas and test equipment. Solid state devices and printed circuit techniques are used extensively in the designs featured in the magazine.

To facilitate home-construction of the equipment described, VHF COMMUNICATIONS makes available all special components such as p.c. boards, complex metal work, etc. Also offered are complete equipment kits. Thus, even those with limited fabrication and testing facilities will be able to duplicate the designs and attain the same high performance.

VHF COMMUNICATIONS also brings theoretical articles and reports on new technological developments of interest to the VHF/UHF amateur.

VHF COMMUNICATIONS is published in February, May, August and November. It is mailed directly from West Germany. Subscriptions are by calendar year, \$3.50 (U.S.) for surface mail, \$4.50 for air mail delivery. Single issues and back issues are \$1.10 each. A sample copy of the November 1970 issue is available for \$0.50.

Why not send us your subscription now?

Write to:

VHF COMMUNICATIONS

BOX 283

FORESTDALE, MASSACHUSETTS 02644

Advertisers check-off

... for literature, in a hurry —
we'll rush your name to the companies
whose names you "check-off"

INDEX

- | | |
|----------------|--------------------|
| —Alarm | —LA |
| —Alco | —Madison |
| —Allied | —Micro-Z |
| —BC | —Milliwatt |
| —Barry | —Mosley |
| —Bell's | —Motorola |
| —Blulyne | —National |
| —Bob's | —Pennwood |
| —Cir-Kit | —R P |
| —Comtec | —Callbook |
| —Curtis | —Radio Constructor |
| —Dayton | —Regency |
| —Drake | —Ross & White |
| —E-S | —Salch |
| —Ehrhorn | —Sentry |
| —Eimac | —Spectronics |
| —Flinn | —Spectrum |
| —Goodheart | —Standard |
| —H & H | —Structural |
| —H & L | —Swan |
| —HAL | —Ten-Tec |
| —Hallicrafters | —Topeka |
| —Ham Radio | —Tri-Ex |
| —Heath | —Triangle |
| —Henry | —VHF Communication |
| —International | —Varitronics |
| —J & J | —Vanguard |
| —Jan | —Weinschenker |
| | —Westcom |
| | —World QSL |

March 1971

Please use before April 30, 1971

Tear off and mail to

HAM RADIO MAGAZINE — "check-off"
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....


CITY.....

STATE..... ZIP.....

Advertisers iNdex

Alarm Component Distributors	91
BC Electronics	92
Barry Electronics	88
Bell's Coin Shop	90, 91
Blulyne Electronics Corp.	93
Bob's Discount Electronics	79
Cir-Kit	78
Communications Technology, Inc.	48, 49, 82
Curtis Electro Devices	90, 91
Dayton Hamvention	90
Drake Co., R. L.	2, 83, 84, 87, 88, 89, 91
E-S Electronic Labs	90
Ehrhorn Technological Operations	Cover II
Eimac Division of Varian Associates.....	Cover IV
Flinn, David G.	90
G & G Radio Electronics Co.	86
Goodheart Co., Inc., R. E.	92
H & H Engineering	89
H & L Associates	91
HAL Devices	70, 75
Ham Radio Magazine	91
Heath Company	22
Henry Radio	37
International Crystal Manufacturing Co.	69
Jan Crystals	80
LA Electronix Sales	90
Madison Electronics Supply	87
Micro-Z Co.	75
National Radio Co., Inc.	47
Pennwood Numechron Co.	91
RP Electronics	79
Radio Amateur Callbook, Inc.	76, 87, 89
Radio Constructor	74
Sentry Manufacturing Co.	1
Spectronics	95, 96, Cover III
Spectrum International	76, 77
Standard Communications Corp.	5
Structural Glass Ltd.	77
Swan Electronics	81
Ten-Tec, Inc.	63
Topeka FM Engineering	71
Tri-Ex Tower Corp.	43
Triangle Antennas	84
VHF Communication	93
Varitronics, Inc.	68
Vanguard Labs	80
Weinschenker, M.	55
Westcom Engineering Co.	92
World QSL Bureau	90

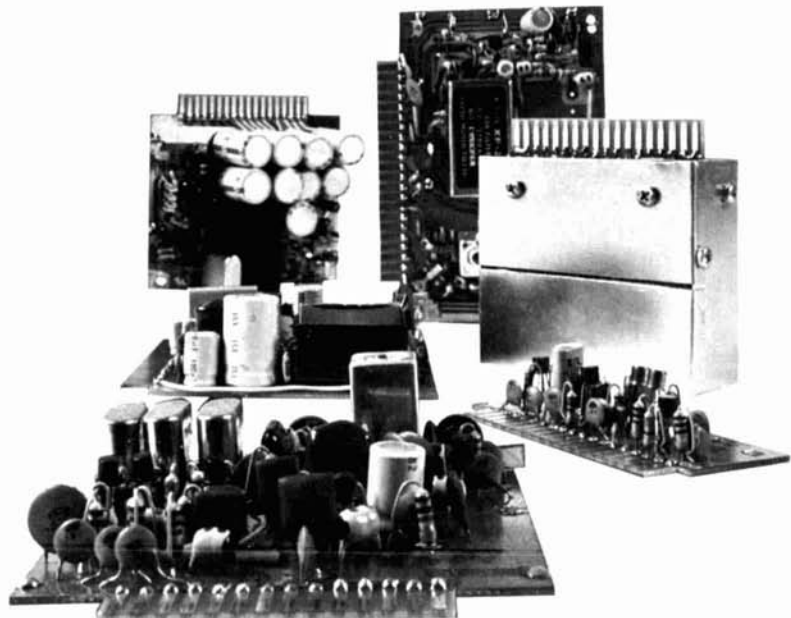Here's just half a dozen reasons why the Yaesu FT-101 is the world's best portable rig.



Those six computer-type plug-in modules hold most of the FT-101's 10 FET's, 3 IC's, 31 silicon transistors and 38 silicon diodes. Being solid-state, they're built to give you years of superior performance. But if any one of them ever gives you trouble, you simply mail it back to us for a factory-new replacement module.

Not that you should expect trouble. What you should expect — and what you get — is the most

The FT-101 is a thirty-pound package of DX punch, air-ready when you are, wherever you are. Just add an antenna, feed it 12 or 117 volts, and you're ready to work the world.

So sure are we of the 101's solid-state reliability, we guarantee it for one year from date of purchase. And we guarantee you that it will be a very good year . . . the first of many to come. The FT-101 — only \$499.95.



sensational portable rig ever offered to the American amateur. With features like these: a built-in VOX, 25 KHz and 100 KHz calibrators, the WWV 10 MHz band, a high Q permeability tuned RF stage and a 5 KHz clarifier. And 260 W PEP, 180 W CW and 80 W AM. With 0.3 microvolts receiving sensitivity — for a 10 db signal-to-noise ratio.

Not to mention a built-in 12 VDC and 117 VAC power supply. Plus an in-motion necessity — a noise blanker that picks out noise spikes, leaving only clean noise-free signal copy behind.

SPECTRONICS WEST

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

SPECTRONICS EAST

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ _____

Please send model(s) _____

Name _____


Address _____

City _____ State _____ Zip _____

All prices F.O.B. Signal Hill, Ca.

Now you don't have to pay twice the price to get twice the rig.

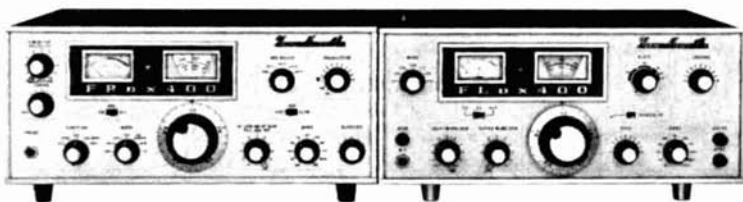Picture this pair in your shack. The Yaesu FLdx 400 transmitter and the FRdx 400 receiver. Loaded with power. Loaded with sensitivity. Loaded with features. Loaded with value. Read on, and discover how you can have the most up-to-date receiver-transmitter rig in the world... and at an unbelievably low price.



The FRdx 400 Receiver

Get a big ear on the world with complete amateur band coverage from 160 meters through 2 meters, including WWV and CB reception. Four mechanical filters do it—they provide CW, SSB, AM and FM selectivity. Separate AM-SSB-FM detectors are included, along with squelch and transmit monitor controls. Plus a noise limiter and a variable delay AGC. And a built-in notch filter with front panel adjust for notch depth.

The FRdx includes calibration markers at 100 KHz and 25 KHz, with accurate calibrator checks verified by WWV. A solid-state FET VFO for unshakable stability. And a direct-reading 1 KHz dial affords frequency read-out to less than 200 Hertz.

The FRdx 400 sells for \$359.95.

The FLdx 400 Transmitter

Here's how to set yourself up with dual receive, transceive or split VFO operation. The FLdx 400 with its companion receiver brings you the ultimate in operational flexibility. Flexibility like frequency spotting, VOX, break-in CW, SSB, AM and even an optional FSK circuit.

The completely self-contained FLdx 400 features a built-in power supply, fully adjustable VOX, a mechanical SSB filter, metered ALC, IC and PO. A completely solid-state FET VFO provides rock-solid frequency stability.

We rate the FLdx 400 very conservatively. That rating guarantees you 240 W PEP input SSB, 120 W CW and 75 W AM. The FSK option will go all day at a continuous 75 W. And you get full frequency coverage on all amateur bands—80 meters through 10

meters—with an optional provision for certain other bands that you can personally specify. For all that, you pay just \$299.95.



FL2000 B Linear Amplifier.

Ideal companion to the Series 400, this hand-crafted linear is another example of Yaesu's unbeatable combination of high quality and low cost. Designed to operate at 1500 watts PEP SSB and 1000 watts CW, this unit provides superb regulation—achieved by a filter system with 28 UF effective capacity.

Other features include dual cooling fans (one for each tube), individual tuned input coils on each band for maximum efficiency and low distortion, and a final amplifier of the grounded grid type using two rugged carbon-plate 572 B tubes. Ready to operate at only \$299.95.

SPECTRONICS WEST

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

SPECTRONICS EAST

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ _____

Please send model(s) _____

Name _____

Address _____

City _____ State _____ Zip _____

All prices F.O.B. Signal Hill, Ca.

The Yaesu FTdx 560 is a great rig, but it's no bargain.

At \$450, it's a steal.

Considering all the FTdx 560 offers, you might think its \$450 price tag was for a kit. But it isn't.

You get a powerful, air-ready station. A handsome, completely hand-crafted transceiver that's fully guaranteed for one year.

You'll have maximum input of 560 watts PEP in the SSB mode or 500 watts CW. And except for speaker, mike and antenna, you'll have nothing else to buy. Power supply, WWV, calibrators, VOX, warranty and all the other items you usually have to pay extra for are included.

One more point: About 90% of the amateur stations in the Orient are Yaesu; in Europe, it runs about 80%. They're good. It is quite likely Yaesu is the best transceiver made anywhere in the world.

Send for our free information packet that tells the Yaesu story and gives you facts, specifications and schematics for the FTdx 560. The radio you can steal.



SPECTRONICS WEST

Dept. H, 1491 E. 28th, Signal Hill, Ca. 90806 / (213) 426-2593

SPECTRONICS EAST

Dept. H, Box 1457, Stow, Ohio 44224 / (216) 923-4567

Please send new color catalog of all Yaesu products.

Enclosed find \$ _____

Please send model(s) _____

Name _____

Address _____

City _____ State _____ Zip _____

All prices F.O.B. Signal Hill, Ca.

EIMAC's new 8873 family covers the electromagnetic spectrum from DC to 500 MHz.

No need to compartmentalize your thinking when you contemplate EIMAC's new 8873 family of zero bias triodes. This tube for all seasons has three interesting configurations that allow you unprecedented design freedom: conduction cooling to heat sink (8873), axial cooling (8874) and transverse cooling (8875). Your choice to overcome today's design constrictions.



8873
CONDUCTION COOLED
ANODE



8874
AXIAL COOLED
ANODE



8875
TRANSVERSE COOLED
ANODE

Consider that the 8873 family provides up to 1000 watts PEP input or 500 watts continuous duty input per tube to 500 MHz. Low grid interception allows low drive power to be combined with low intermodulation distortion in linear service.

Observe that while the 8873 family performs in superior fashion as a linear amplifier in SSB service, it is also ideally suited for high gain, class-C FM or AM service in the VHF/UHF range. Electron control by EIMAC's new segmented, self-focusing cathode and unique aligned grid structure provide the key to this improved performance. The grid, moreover, is terminated in a low inductance contact ring about the base of the tube, permitting very effective intra-stage isolation to be achieved up to the outer frequency limit of operation.

Note that these rugged triodes are exceptionally well suited for class-B audio service as well as for pulse operation demanding high peak current capability at modest drive power.

Remember the 8873 family of triodes covers the electromagnetic spectrum from DC to UHF with ease, meeting widely divergent requirements in a package you can hold in the palm of your hand. Use these compact tubes in table-top design where space is a scarce commodity or where high density packaging is imperative.

Write EIMAC today for details and circuitry on the 8873 family of grounded grid triode tubes. Another example of EIMAC's ability to provide tomorrow's tubes today. EIMAC, 301 Industrial Way, San Carlos, California 94070. Phone (415) 592-1221.

