

one dollar


ham **radio**

magazine



DECEMBER 1976

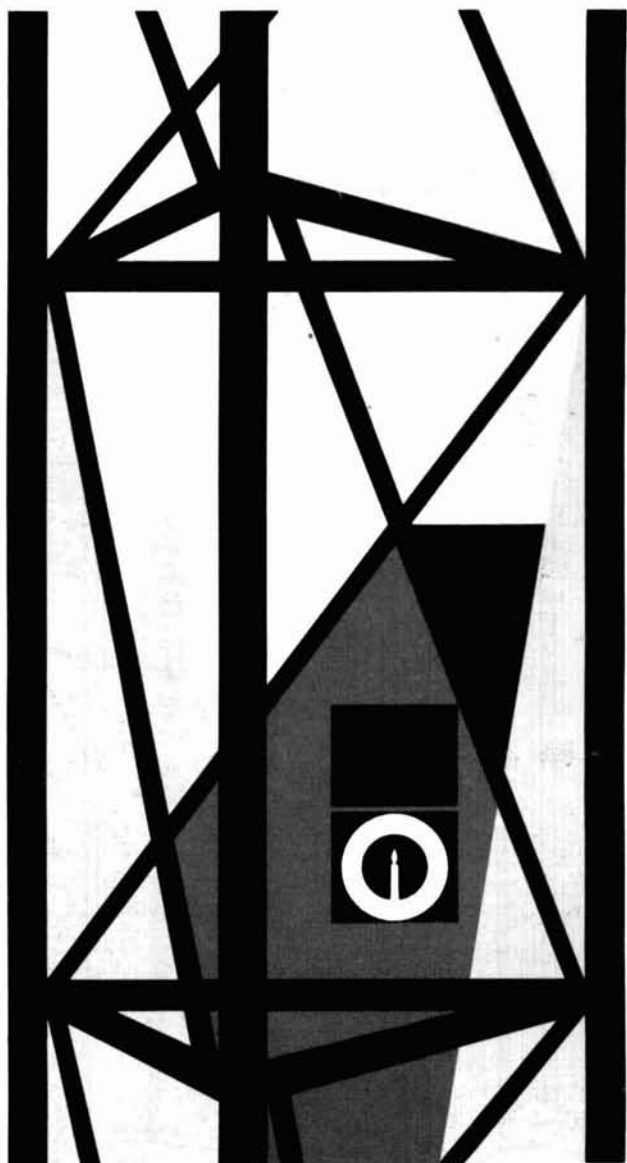- high-frequency communications receiver 10
- loop antennas 18
- broadband mospower amplifier 32
- ASCII-to-Morse code translator 41
- microprocessors 66
- and much more . . .



Now...more than ever--- the TEMPO line means solid value

Tempo VHF/ONE

the "ONE" you've been waiting for

No need to wait any longer — this is it! Whether you are already on 2-meter and want something better or you're just thinking of getting into it, the VHF/ONE is the way to go.

- Full 2-meter band coverage (144 to 148 MHz for transmit and receive).
- Full phase lock synthesized (PLL) so no channel crystals are required.
- Compact and lightweight — 9.5" long x 7" wide x 2.25" high. Weight — About 4.5 lbs.
- Provisions for an accessory SSB adaptor.
- 5-digit LED receive frequency display.
- 5 KHz frequency selection for FM operation.
- Automatic repeater split — selectable up or down for normal or reverse operation.
- Microphone, power cord and mounting bracket included.
- Two built-in programmable channels.
- All solid state.
- 10 watts output.
- Super selectivity with a crystal filter at the first IF and E type ceramic filter at the second IF.
- 800 Selectable receive frequencies.
- Accessory 9-pin socket.

TEMPO SSB/ONE

SSB adapter for the Tempo VHF/One

- Selectable upper or lower sideband.
- Plugs directly into the VHF/One with no modification.
- Noise blanker built-in.
- RIT and VXO for full frequency coverage.



TEMPO fmh

So much for so little! 2 watt VHF/FM hand held 6 Channel capability, solid state, 12 VDC, 144-148 MHz (any two MHz), includes 2 pair of crystals, built-in charging terminals for nicad cells, S-meter, battery level meter, telescoping whip antenna, internal speaker & microphone.

\$199.00



F.M.H. MC for Marine & Commercial service also available



TEMPO CL146A

... a VHF/FM mobile transceiver for the 2 meter amateur band. It is compact, ruggedly built and completely solid state. One channel supplied plus two channels of your choice FREE

144 to 148 MHz coverage • Multifrequency spread of 2 MHz • 12 channel possible • Metering of output and receive • Internal speaker, dynamic microphone, mounting bracket and power cord supplied. A Tempo "best buy" at \$239.00.



TEMPO 6N2

The Tempo 6N2 meets the demand for a high power six meter and two meter power amplifier. Using a pair of Eimac 8874 tubes it provides 2000 watts PEP input on SSB and 1000 watts input on CW and FM. Completely self-contained in one small desk mount cabinet with internal solid state power supply, built-in blower and RF relative power indicator.

\$895.00

The Tempo 2002... 2 meters only \$745.00
The Tempo 2006... 6 meters only \$795.00




TEMPO POCKET RECEIVERS

MS-2, 4 channel scanning receiver for VHF high band, smallest unit on the market. MR-2, same size as MS-2 but has manual selection of 23 channels, VHF high band. MR-3, miniature 2-channel VHF high band monitor or paging receiver. MR-3U, single channel on the 400 to 512 UHF band. All are low priced, extremely compact and dependable.

TEMPO 100A110

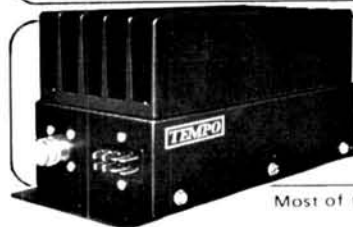SOLID STATE VHF LINEAR AMPLIFIER. 144-148 MHz. Power output of 100 watts (nom) with only 10 watts (nom) in. Reliable and compact.



TEMPO

VHF and UHF Amplifiers

Solid state power amplifiers for use in most base/mobile applications. Increase the range, clarity, reliability and speed of two-way communications.

Low Band VHF amplifiers available in 100W out with 2, 10 & 30W in. High Band VHF amps available in 30, 50, 80 & 130W out with 2, 10 & 30W in. UHF amps available in 10, 25, 40 & 70W out with 1, 2, 10 & 30W in. Call or write for spec sheet and prices.

Most of the above products are available at dealers throughout the U.S.

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Prices subject to change without notice

Call toll-free 800-647-8660 for products by MFJ ENTERPRISES

(Want MFJ products for Christmas? Mark your choice and show your XYL this ad.)

400% MORE RF POWER PLUGS BETWEEN YOUR MICROPHONE AND TRANSMITTER



\$ 49⁹⁵



\$ 59⁹⁵

LSP-520BX. 30 db dynamic range IC log amp and 3 active filters give clean audio. RF protected. 9 V battery. 3 conductor, 1/4" phone jacks for input and output. 2-3/16 x 3-1/4 x 4 inches.

LSP-520BX II. Same as LSP-520BX but in a beautiful 2-1/8 x 3-5/8 x 5-9/16 inch Ten-Tec enclosure with uncommitted 4 pin Mic jack, output cable, rotary function switch.

SUPER LOGARITHMIC SPEECH PROCESSOR

Up To 400% More RF Power is yours with this plug-in unit. Simply plug the MFJ Super Logarithmic Speech Processor between your microphone and transmitter and your voice is suddenly transformed from a whisper to a **Dynamic Output**.

Your signal is full of punch with power to slice through QRM and you go from barely readable to "solid copy OM".



\$ 27⁹⁵

CWF-2BX Super CW Filter

By far the leader. Over 5000 in use. Razor sharp selectivity. 80 Hz bandwidth, extremely steep skirts. No ringing. Plugs between receiver and phones or connect between audio stage for speaker operation.

- Selectable BW: 80, 110, 180 Hz • 60 dB down one octave from center freq. of 750 Hz for 80 Hz BW
- Reduces noise 15 dB • 9 V battery
- 2-3/16 x 3-1/4 x 4 in. • CWF-2PC, wired PC board, \$18.95 • CWF-2PCK, kit PC board \$15.95



\$ 49⁹⁵

CMOS-8043 Electronic Keyer

State of the art design uses CURTIS-8043 Keyer-on-a-chip.

- Built-in Key • Dot memory • Iambic operation with external squeeze key • 8 to 50 WPM • Sidetone and speaker • Speed, volume, tone, weight controls • Ultra reliable solid state keying +300 volts max. • 4 position switch for TUNE, OFF, ON, SIDETONE OFF
- Uses 4 penlight cells • 2-3/16 x 3-1/4 x 4 inches



\$ 39⁹⁵

NEW

MFJ-16010 Antenna Tuner

Now you can operate all band — 160 thru 10 Meters — with a single random wire and run your full transmitter power output — up to 200 watts RF power OUTPUT.

- Small enough to carry in your hip pocket, 2-3/16 x 3-1/4 x 4 inches • Matches low and high impedances by interchanging input and output • SO-239 coaxial connectors • Unique wide range, high performance, 12 position tapped inductor. Uses two stacked toroid cores



\$ 29⁹⁵

SBF-2BX SSB Filter

Dramatically improves readability.

- Optimizes your audio to reduce sideband splatter, remove low and high pitched QRM, hiss, static crashes, background noise, 60 and 120 Hz hum
- Reduces fatigue during contest, DX, and ragchewing
- Plugs between phones and receiver or connect between audio stage for speaker operation
- Selectable bandwidth IC active audio filter
- Uses 9 volt battery • 2-3/16 x 3-1/4 x 4 inches



\$ 27⁹⁵

MFJ-200BX Frequency Standard

Provides strong, precise markers every 100, 50, or 25 KHz well into VHF region.

- Exclusive circuitry suppresses all unwanted markers • Markers are gated for positive identification. CMOS IC's with transistor output. • No direct connection necessary
- Uses 9 volt battery • Adjustable trimmer for zero beating to WWV
- Switch selects 100, 50, 25 KHz or OFF
- 2-3/16 x 3-1/4 x 4 inches



\$ 49⁹⁵

MFJ-1030BX Receiver Preselector

Clearly copy weak unreadable signals (increases signal 3 to 5 "S" units).

- More than 20 dB low noise gain • Separate input and output tuning controls give maximum gain and RF selectivity to significantly reject out-of-band signals and reduce image responses
- Dual gate MOS FET for low noise, strong signal handling abilities • Completely stable • Optimized for 10 thru 30 MHz • 9 V battery
- 2-1/8 x 3-5/8 x 5-9/16 inches



\$ 27⁹⁵

MFJ-40T QRP Transmitter

Work the world with 5 watts on 40 Meter CW.

- No tuning • Matches 50 ohm load • Clean output with low harmonic content
- Power amplifier transistor protected against burnout
- Switch selects 3 crystals or VFO input • 12 VDC
- 2-3/16 x 3-1/4 x 4 inches

MFJ-40V, Companion VFO \$27.95

MFJ-12DC, IC Regulated Power Supply,

1 amp, 12 VDC \$27.95



\$ 15⁹⁵

NEW

CPO-555 Code Oscillator

For the Newcomer to learn the Morse code.

For the Old Timer to polish his fist.

For the Code Instructor to teach his classes.

- Send crisp clear code with plenty of volume for classroom use
- Self contained speaker, volume, tone controls, aluminum cabinet • 9 V battery
- Top quality U.S. construction • Uses 555 IC timer
- 2-3/16 x 3-1/4 x 4 inches

TK-555, Optional Telegraph Key \$1.95

OUR OFFER TO YOU

Dear Fellow Ham,

Try any MFJ products and if you are not completely satisfied, return it within 30 days for a full prompt refund (less shipping). Call us today toll free 800-647-8660 and charge your BankAmericard or Master Charge, or mail your order in today with your check or money order (or use your BAC or MC). Please add \$2.00 for shipping and handling. Order now and avoid the Christmas rush.

73, Martin F. Jue, K5FLU

P.S. Solve your XYL's Christmas problem. Mark your choice and show her this ad.

ORDER TODAY. MONEY BACK IF NOT DELIGHTED. ONE YEAR UNCONDITIONAL GUARANTEE.


Order By Mail or Call TOLL FREE 800-647-8660 and Charge It On



MFJ ENTERPRISES

P. O. BOX 494
MISSISSIPPI STATE, MISSISSIPPI 39762

Stay tuned for future programs.

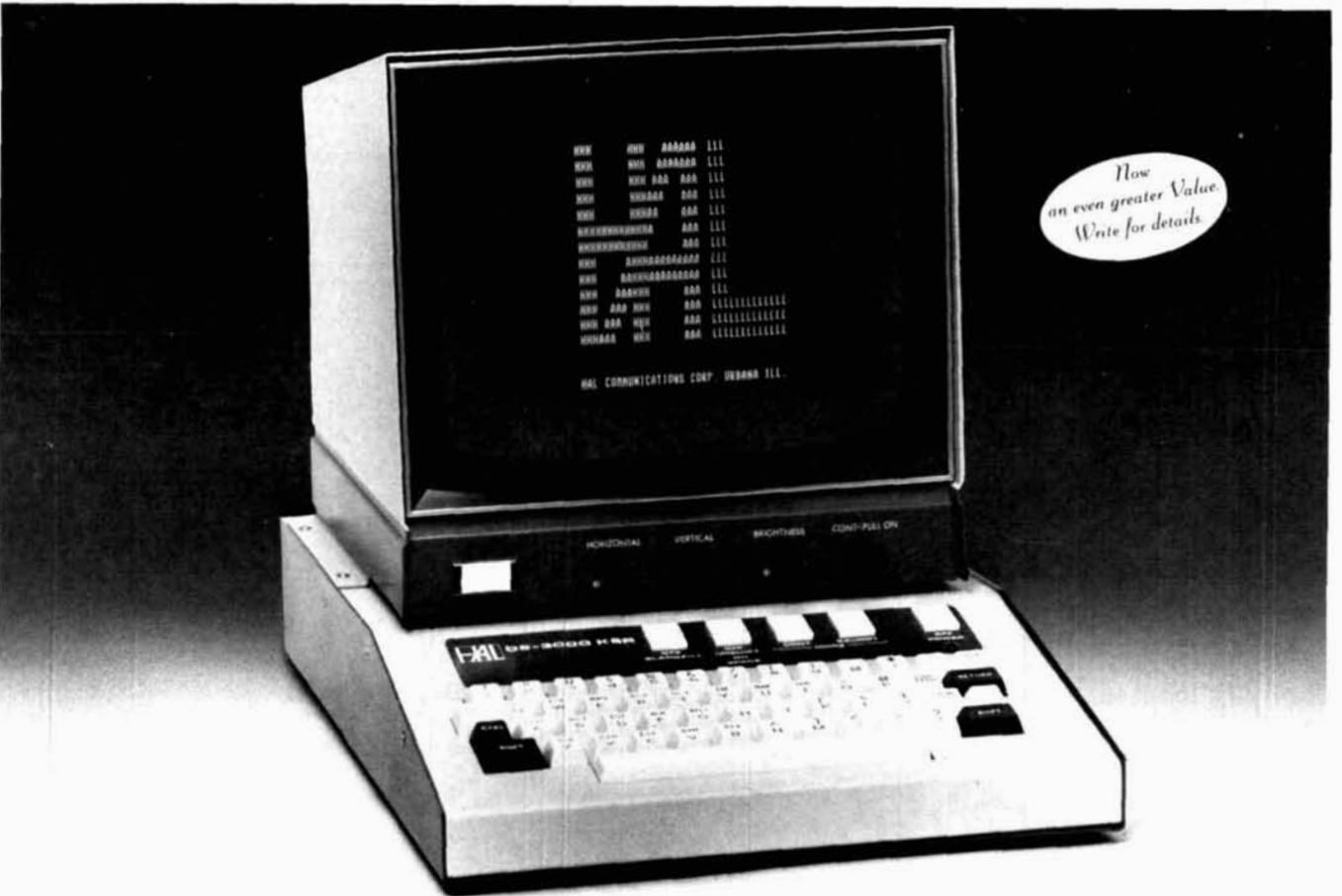

The HAL ST-6000 demodulator/keyer and the DS-3000 and DS-4000 KSR/RO series of communications terminals are designed to give you superlative TTY performance today—and in the future. DS series terminals, for example, are re-programmable, assuring you freedom from obsolescence. Sophisticated systems all, these HAL products are attractively priced—for industry, government and serious amateur radio operators.

The HAL ST-6000 operates at standard shifts of 850, 425, and 170 Hz. The tone keyer is crystal-controlled. Loop supply is internal. Active filters allow flexibility in estab-

lishing different tone pairs. You can select AM or hard-limiting FM modes of operation to accommodate different operating conditions. An internal monitor scope (shown on model above) allows fast, accurate tuning. The ST-6000 has an outstandingly high dynamic range of operation. Data I/O can be RS-232C, MIL-188C or current loop.

The DS-3000 and DS-4000 series of KSR and RO terminals provide silent, reliable, all-electronic TTY transmission and reception, or read-only (RO) operation of different combinations

of codes, including Baudot, ASCII and Morse. The powerful, programmable 8080A microprocessor is included in the circuitry to assure maximum flexibility for your present needs—and for the future. The KSR models offer you full editing capability. The video display is a convenient 16-line format, of 72 characters per line.

These are some of the highlights. The full range of features and specifications for the ST-6000 and the DS series of KSR and RO terminals is covered in comprehensive data sheets available on request. Write for them now—and tune in to the most sophisticated TTY operation you can have today... or in the future.



HAL Communications Corp., Box 365, 807 E. Green Street
Urbana, Illinois 61801 • Telephone: (217) 367-7373

ham radio

magazine

DECEMBER 1976

volume 9, number 12

editorial staff

James R. Fisk, W1DTY
editor-in-chief
Thomas F. McMullen, Jr., W1SL
managing editor
Charles J. Carroll, W1GQQ
James H. Gray, W2EUQ
Patricia A. Hawes, WN1WPM
Alfred Wilson, W6NIF
assistant editors
J. Jay O'Brien, W6GO
fm editor
Joseph J. Schroeder, W9JUV
associate editor
Wayne T. Pierce, K3SUK
cover

publishing staff

T. H. Tenney, Jr., W1NLB
publisher
Harold P. Kent, WN1WPP
assistant publisher
Fred D. Moller, Jr., WN1USO
advertising manager
Cynthia M. Schlosser
assistant advertising manager
Therese R. Bourgault
circulation manager

ham radio magazine is published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048
Telephone: 603-878-1441

subscription rates

U.S. and Canada: one year, \$10.00
three years, \$20.00
Worldwide: one year, \$12.00
three years, \$24.00

foreign subscription agents

Ham Radio Canada
Box 114, Goderich
Ontario, Canada, N7A 3Y5
Ham Radio Europe
Box 444
194 04 Upplands Vasby, Sweden
Ham Radio France
20 bis, Avenue des Clarions
89000 Auxerre, France
Ham Radio Holland
Postbus 3051
Delft 2200, Holland
Ham Radio Italy
STE, Via Maniago 15
I-20134 Milano, Italy
Ham Radio UK
Post Office Box 64, Harrow
Middlesex HA3 6HS, England
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa

Copyright 1976 by
Communications Technology, Inc
Title registered at U.S. Patent Office

Microfilm copies
are available from
University Microfilms
Ann Arbor, Michigan 48103

Second-class postage
paid at Greenville, N.H. 03048
and at additional mailing offices

contents

10 high-frequency communications receiver
Ovidiu N. Florea, WB2ZVU

18 low-frequency loop antennas
John R. True, W4OQ

26 QRP 7-MHz CW transmitter
Si Marians, W4LPW
Howard J. Stark, WA4MTH

32 broadband amplifier uses mospower fet
Ed Oxner

38 electronic meter amplifier
Norman J. Foot, WA9HUV

41 ASCII-to-Morse code translator
David Scharon
Robert Morley

48 ladder network analysis
Walter van B. Roberts, W2CHO

52 resurrecting old receivers
Joseph J. Carr, K4IPV

58 increase flexibility for MFJ CW filters
Howard M. Berlin, K3NEZ


62 signal-to-noise performance of
low-frequency shift RTTY
Leland E. Thompson, K6SR

66 microcomputer interrupts
David G. Larsen, WB4HYJ
Peter R. Rony
Jonathan A. Titus

4 a second look
142 advertisers index
116 cumulative index
101 flea market
86 ham mart
66 microprocessors

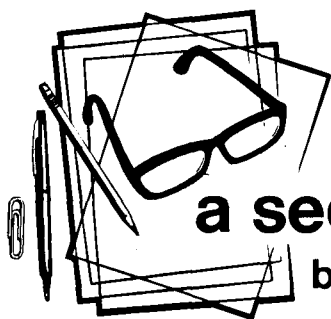68 new products
52 novice reading
6 presstop
142 reader service
52 repair bench





a second look

by Jim Fisk

In looking back over the advances in IC technology that have occurred during the past several years, it's hard to realize that integrated circuits actually celebrated their 18th birthday this past summer. It was during the summer and fall of 1958 that Jack S. Kilby of Texas Instruments built the first integrated circuit. Other semiconductor companies had been working on ways to miniaturize solid-state electronic circuits, but most of these techniques used miniature components of one kind or another; Kilby was the first to use semiconductor material for both the active (transistors) and passive elements (resistors and capacitors) to build a complete circuit on a single piece of germanium.

His first circuits, a phase-shift oscillator and multivibrator, demonstrated the feasibility of this approach. Since, at that time, germanium was well established as a semiconductor material, and silicon was not, Kilby used germanium. On top of the germanium wafer were the contacts of the diffused transistors, junction capacitors, and resistors. A gold-plated metal frame protruded from the lower surface of the substrate, and thermally-bonded gold wires were used for connections between those elements not linked by the wafer itself.

Kilby's first circuits were large and irregular — at least by today's standards — and were considerably different from the precision ICs that are presently on the market. The photo masks and resists necessary to IC manufacturing were yet to be developed, so the patterns were hand painted on the semiconductor chip with black wax. Needless to say, the end product was rather crude looking (and huge by today's standards), but it worked.

About the same time Kilby was working on his first integrated circuits, Fairchild Semiconductor developed the *Planar* process — an innovation that is generally conceded to be the foremost semiconductor discovery of the 1960s. This process made semiconductors more reliable and cheaper to produce, as well as accelerating IC progress and acceptance.

Since these early developments, the number of circuits per unit area has increased and prices have plummeted. In 1962, a typical IC flip-flop chip was about 0.1 inch (2.5mm) square; by 1970 a similar circuit was one-tenth that size, and today the same circuit is even smaller. At the same time circuit size (and unit cost) were decreasing, circuit speed increased from audio to 1 MHz or so, then to 5 MHz, 15 MHz, and on up the scale. It was only a few short years ago that a 30-MHz frequency counter was only a dream — today 600-MHz counters are commonplace, and even higher count frequencies are available if you're willing to pay a small premium for the capability.

It wasn't all that long ago that I reported on this page that, "... you can now buy a dual flip-flop for a couple of dollars or a complete decade counter for about seven." And these were RTL devices, with maximum counting speeds in the low MHz range. The same issue carried ads for 709 op amps at \$3.98 and 711 dual comparators for \$4.98. A low-current voltage-regulator IC, if you could find one, cost ten dollars or more. Scanning through the ads in the back of this issue, you can now buy a 30-MHz decade counter for about 45 cents, a 709 op amp for 29 cents, and a 711 dual comparator for 39 cents — about one-sixteenth of their 1968 prices. Considering that the consumer price index has increased nearly 70 per cent during the same period of time, ICs have to be among the best buys of all time.

Although I've said it before, it's worth saying again that, with the sophisticated, low cost ICs that are on the market, it's possible for amateurs to build exotic electronic equipment that only large laboratories with big budgets could afford a few years ago — and some they couldn't afford at any price because the technology just wasn't available!

Jim Fisk, W1DTY
editor-in-chief

ICOM INTRODUCES THE REVOLUTION IN VFO TECHNOLOGY



Introducing the IC-245, 144-148 MHz FM Transceiver

The VFO Revolution goes mobile with the unique, ICOM developed LSI synthesizer with 4 digit LED readout. The **IC-245** offers the most for mobile on the market. The easy to use tuning knob moves accurately over 50 detent steps and assures excellent control as easily as steering the vehicle. With its optional adapter, the **IC-245** puts you into all mode operation on 12V DC power with a compact dash-mounted transceiver. In FM, the synthesizer command frequency is displayed in 5 KHz steps from 146 to 148 MHz, and with the side band adapter the step rate drops to 100Hz from 144 to 146 MHz. For maximum repeater flexibility, the transmit and receive frequencies are independently programmable on any separation. The **IC-245** even comes equipped with a multiple pin Molex connector for remote control.

The **IC-245** is a product of the revolution in VFO design, from its new style front panel, to its excellent mechanical rigidity and Large Scale Integrated Circuitry. Your **IC-245** will give you the most for mobile.

SPECIFICATIONS

GENERAL

Frequency Coverage Modes	*144.00 to 148.00 MHz FM (F3)
Supply Voltage	*SSB (A3J), CW (A1) DC 13.8V ±15%
Size (mm)	90H x 155W x 235D
Weight (kg)	2.7

TRANSMITTER

TX Output	F3 10W *A3J 10W (PEP), A1 10W
Carrier Suppression	40 dB or better
Spurious Radiation	-60 dB or less below carrier
Maximum Frequency Deviation	±5 KHz
Microphone Impedance	600 ohms

RECEIVER:

Sensitivity	*A3J, A1 0.5 microvolt input gives 10 dB S+N/N or better F3 0.6 microvolt or less for 20 dB quieting S+N+D/N at 1 microvolt input, 30 dB
Squelch Threshold	-8 dB or less (F3)
Spurious Response	-60 dB or better

SYNTHESIZER:

Frequency Range	144 MHz to 148 MHz
Step Size	5 KHz for FM *100 Hz or 5 KHz for SSB
Stability	per C in the range of -10 to +60 C, ±0.0000145% per C

* Valid with SSB Adapter only

THE BEGINNING OF THE ICOM VFO REVOLUTION!

VHF/UHF AMATEUR AND MARINE COMMUNICATION EQUIPMENT

Distributed by:



ICOM

ICOM WEST, INC.
Suite 3
13256 Northrup Way
Bellevue, Wash. 98005
(206) 747-9020

ICOM EAST, INC.
Suite 307
3331 Towerwood Drive
Dallas, Texas 75234
(214) 620-2780

ICOM CANADA
7087 Victoria Drive
Vancouver B.C. V5P 3Y9
Canada
(604) 321-1833



"N" PREFIXED TWO-LETTER CALLS are now available to any Amateur eligible for a 1x2 callsign. The release of N prefixes applies only to 1x2 callsigns at this time, though presumably the N prefix will also continue to be available when requested for special events stations.

"X" Suffix Callsigns, released in late October, increases total pool of 1x2 calls in each district by 676. Although the X suffix has traditionally indicated an experimental station in the United States, 1x2 X calls have not been issued since well before World War II so are not expected to cause any great confusion. Who's first for W1XX, Whiskey one Double Cross?

AMSAT'S ANNUAL MEETING drew about 75 people to Goddard Space Flight Center in October. JAIANG brought the prototype 2-meter to 70-cm transponder from JAMSAT, and reported about 500 Japanese Amateurs are users of OSCARs 6 and 7. The AMSAT 2-10 meter transponder for OSCAR A-OD is now ready for test.

OSCAR 6's Birthday was October 15 and AMSAT's longest lived bird is over four years old and still going strong. As the launch anniversary ended OSCAR 6 began its 18,300 orbit, a lot of miles and many thousands of contacts to its credit.

OSCAR 7 Also celebrated a birthday; it was a healthy two-years old November 15. N6V's Operation by the Jet Propulsion Laboratory's Amateur Radio Club was seen by millions of viewers on NBC's Today show. Featured during the outstanding segment was N6V's relaying of Mars photographs throughout the world via Amateur slow-scan TV.

The European Space Agency has announced approval of an Amateur Radio satellite launch on its experimental Ariane launch vehicle. A German-built OSCAR is scheduled to go aloft with Ariane's test flight B during December, 1979.

EXCELLENT RFI/EMI SURVEY article appeared in the September 20, 1976 issue of Electronic Design, should be "must" reading for any one seriously interested in the subject. Interference to as well as by communications equipment is included, and there's strong emphasis on FCC's increasing role in the problem area.

CB Is A Major cause of TVI/RFI complaints, of course, and in a recent discussion with FCC Chief Engineer Ray Spence he made the interesting observation that by far the majority of complaints of CB-caused interference was found to involve illegal power!

ITU SECRETARY-GENERAL MILI was the top brass at the dedication of United Nations' club station K2UN on October 21st. WIAW and 4U1ITU in Geneva joined in the inaugural ceremony, though K2UN's current antennas toward Europe leave much to be desired.

ARRL'S BICENTENNIAL CONTEST could become an annual affair, though under a different name. So many participants said they liked its format that League Communications Manager W1NJM has asked for comments.

AMATEUR NOVICE TRAINING PROGRAM currently has more than five times the enrollment it had last year - nearly 35,000 vs 6,000 in 1975. Unlike previous years, established classes continue growing with nearly zero dropout while newcomers appear after hearing about them from friends or on 27 MHz.

CARF WILL HAVE a headquarters office complete with Amateur station thanks to a grant of \$10,000 to the Kingston (Ontario) Old Timers' Amateur Radio Association. The office and Amateur station (VE3VCA) will be located at 370 King Street, West, in Kingston, but the mailing address will remain Box 356.

CANADIAN CB WILL EXPAND to 40 channels following the U.S.'s lead, but the General Radio Service operators won't be able to use their new channels until April 1. 40 channel radios for the Canadian market must be tested to tighter specs, but they can't be submitted for testing until after January 1. Commercial users presently operating on the new frequencies have the option of staying put or applying for a new assignment.

Whether A U.S. CBer entering Canada with a shiny new 40 channel radio before April 1 would have problems remains to be seen.

SEVERAL THOUSAND CB LICENSES issued around the beginning of 1976 apparently never reached the applicants. Areas affected include Zip Codes beginning with 0 through 8, and the problems ran from December through April. New licenses for the affected blocks are being printed and mailed; however, any licensee receiving one as a duplicate should discard it.

AMATEUR RADIO RELATED articles have been showing up in non-Amateur Radio publications with increasing frequency, but those not written by Amateurs often suffer from distracting inaccuracies. Ham Radio's editorial staff volunteers its services in reviewing future Amateur Radio articles for any non-Amateur publication that wishes to take advantage of the offer.

Does Your Transmitter Love Your Antenna?



If you're fighting the constant battle of limited band width, high SWR ratios, inefficient low-pass TVI filter operation due to high SWR you're not alone.

DenTron makes the Problem Solvers.

The DenTron tuners give you maximum power transfer from your transmitter to your antenna, and isn't that where it really counts?

Our Super Tuners (A. B. & E.) are the only tuners on the market that match everything between 160 and 10 meters. Whether you have balanced line, coax cable, random or long wire the DenTron Super Tuners will match the antenna impedance to your transmitter.

NEW: The Monitor Tuner (E.) was designed because of overwhelming demand. Hams told us they wanted a 3 kilowatt tuner with a built-in wattmeter, a front panel antenna selector for coax, balanced line and random wire. So we engineered the 160-10m Monitor Tuner. It's a life time investment at \$299.50

The DenTron 80-10 AT (D.) is a random wire, 80-10 meter tuner which is ideal for portable operation or apartment dwellers.

Every serious ham knows he must read both forward and reverse wattage simultaneously for that perfect match. So upgrade with the DenTron W-2 Dual in line Wattmeter. (C.)

The flexibility we build into our Tuners make any previous tuner you might have owned obsolete.

- A. Super Tuner 1KW PEP \$129.50
- B. Super Super Tuner 3 KW PEP \$229.50
- C. W-2 Wattmeter \$ 99.50
- D. 80-10 AT 500 W PEP \$ 59.50
- E. Monitor Tuner 3 KW PEP \$299.50

All DenTron products are made in U.S.A.

DenTron
Radio Co., Inc.

2100 Enterprise Parkway
Twinsburg, Ohio 44087
(216)425-3173

Dedicated to Making Amateur Radio MORE FUN!



- Advance Registration \$12.50 per person; with Hotel Sahara Late Show and two drinks \$23.00 per person or with Hotel Sahara Congo Dinner Show (entree Cornish Hen), no drinks \$30.00 per person. Tax and Gratuity included.
- Totie Fields and Bert Convy are scheduled entertainers in Hotel Sahara's Congo Room.
- Advance Registration must be received by **SAROC** on or before January 1, 1977.

The NATION'S TWELFTH ANNUAL LAS VEGAS PRESTIGE CONVENTION



HOTEL SAHARA'S CONVENTION SPACE CENTER

January 6-9, 1977

- **SAROC** Registration includes: registration tickets, admission to technical sessions, Friday cocktail party hosted by T. P. L. Communications and TRI-EX Tower Corp. with **SAROC**; Saturday cocktail party hosted by Ham Radio Magazine with **SAROC**; Hotel Sahara Buffet Brunch on Sunday, Tax and Gratuity.
- Hotel Sahara room rate for **SAROC** registered delegates \$17.00 per night plus room tax, single or double occupancy.
- Hotel Sahara room reservation request card will be sent to **SAROC** registered delegate.



Send your check or money order to **SAROC**, P. O. Box 945, Boulder City, NV 89005

KENWOOD'S TS-520

...worth waiting for!



Why wait any longer for a rig that offers top performance, dependability and versatility... the TS-520 has proven itself in the shacks of thousands of discriminating amateurs, in field day sites, in DX and contest stations, and in countless mobile installations.

Superb craftsmanship is evident throughout... in its engineering concepts as well as its construction and styling... craftsmanship that is a Kenwood hallmark.

Maybe the Kenwood TS-520 is the one you have been waiting for.

Kenwood offers accessories guaranteed to add to the pleasure of owning the TS-520. The TV-502 transverter puts you on 2-meters the easy way. (It's completely compatible with the TS-520.) Simply plug it in and you're on the air. Two more units designed to match the TS-520 are the VFO-520 external VFO and the model SP-520 external speaker. All with Kenwood quality built in.



TS-520 Specifications

MODES: USB, LSB, CW
POWER: 200 watts PEP input on SSB, 160 watts DC input on CW
ANTENNA IMPEDANCE: 50-75 Ohms, unbalanced
CARRIER SUPPRESSION: Better than -45 dB
UNWANTED SIDEBAND SUPPRESSION: Better than -40 dB
HARMONIC RADIATION: Better than -40 dB
AF RESPONSE: 400 to 2600 Hz (-6 dB)
AUDIO INPUT SENSITIVITY: 0.25 μ V for 10 dB (S+N)/N
SELECTIVITY: SSB 2.4 kHz (-6 dB), 4.4 kHz (-60 dB) CW 0.5 kHz (-6 dB), 1.5 kHz (-60 dB) (with accessory filter)
FREQUENCY STABILITY: 100 Hz per 30 minutes after warmup
IMAGE RATIO: Better than 50 dB
IF REJECTION: Better than 50 dB
TUBE & SEMICONDUCTOR COMPLEMENT: 3 tubes (2 x 6146B, 12BY7A), 1 IC, 18 FET, 44 transistors, 84 diodes
DIMENSIONS: 13.1" W x 5.9" H x 13.2" D
WEIGHT: 35.2 lbs.
SUGGESTED PRICE: \$629.00

VFO-520

Provides high stability with precision gearing. Function switch provides any combination with the TS-520. Both are equipped with VFO indicators showing at a glance which VFO is being used. Connects with a single cable and obtains its power from the TS-520. Suggested price: \$115.00.

SP-520

Although the TS-520 has a built in speaker, the addition of the SP-520 provides improved tonal quality. A perfect match in both design and performance. Suggested price: \$22.95.

TV-502

TRANSMITTING/RECEIVING FREQUENCY: 144.145.7 MHz, 145.0, 146.0 MHz (option).
INPUT/OUTPUT IF FREQUENCY: 28.0, 29.7 MHz
TYPE OF EMISSION: SSB (A3J), CW (A1)
RATED OUTPUT: 8W (AC operation)
ANTENNA INPUT/OUTPUT IMPEDANCE: 50 Ω
UNWANTED RADIATION: Less than -60 dB
RECEIVING SENSITIVITY: More than 1 μ V at S/N 10 dB
IMAGE RATIO: More than 60 dB
IF REJECTION: More than 60 dB
FREQUENCY STABILITY: Less than ± 2.5 kHz during 1.60 min after power switch is ON and within 150 Hz (per 30 min) thereafter.
POWER CONSUMPTION: AC 220/120V, Transmission 50W max., Reception 12W max., DC 13.8V, Transmission 2A max., Reception 0.4A max.
POWER REQUIREMENT: AC 220/120V, DC 12-16V (standard voltage 13.8V)
SEMI CONDUCTOR: FET 5, Transistor 15, Diode 10
DIMENSIONS: 6 $\frac{1}{2}$ " W x 6" H x 13 $\frac{1}{4}$ " D
WEIGHT: 11.5 lbs.
SUGGESTED PRICE: \$249.00

CW-520

500 Hz CW Crystal Filter. \$45.00.

Prices subject to change without notice



DX receiver

for the hf bands

This design features
four selectable front ends
and excellent dynamic range
to help you dig out
the weak ones

Today's erratic propagation conditions together with the tremendous increase in the number of amateur stations make DX operating much more difficult than, say, ten or fifteen years ago. In my case, using an SB220 linear amplifier and a four-element quad antenna, I had fair response to directional CQ DX calls only to become frustrated by adjacent-channel overload or interference in my receiver by strong local or short-skip stations.

The answer to this problem is a receiver with characteristics such as those in the design described in this article. Tests made on the 20- and 40-meter front ends of this design produced the data shown in **table 1**. Note that the dynamic range is 100 dB for both test conditions on 40 and 20 meters.

receiver front-end design

Conflicting requirements and tradeoffs were necessary to obtain a receiver with a wide dynamic range. Recent articles, studies, and experiments indicated that balanced mixers, together with selective rf tunable filters ahead of the first active device, represented effective means for diminishing third- through fifth-order intermodulation (IMD) and cross-modulation products.

I tried hot-carrier diode mixers using discrete diodes (monolithic packages weren't available) in both ring and cross configurations. It was an unsuccessful attempt, since low input-output impedances created matching problems and these mixers seemed to have an insatiable hunger for oscillator power.

The overall receiver noise factor is interrelated with the receiver passband; and in the mathematical formula, one term shows that it is also inversely proportional to the mixer gain. With the diode mixer, the receiver lacked sensitivity because of a conversion loss of almost 9 dB.

Without discrediting the hot-carrier diode mixer, better results were obtained by using the Motorola C6050G double-balanced integrated circuit and also selected pairs of the RCA 40673 dual-gate mosfet.

Occasionally, at certain antenna bearings, the combination of galactic, ionospheric, atmospheric, and man-made noise is below predicted levels; therefore an "in-out" rf amplifier would be justified. For higher-frequency bands, extremely good sensitivity is possible by using a balanced amplifier as in some vhf receivers.

Theoretically, this kind of arrangement should have a better noise factor, as somewhat more than 50% of internally generated random noise would be rejected in the common-mode operation, being cancelled in the balanced output circuit. The rf amplifier becomes a nuisance when the bands become crowded with strong signals exceeding S9+40 dB levels. Receiver gain compression occurs, along with numerous intermodulation products, indicating that it's time to turn off the rf amplifier! This is accomplished in this design by means of miniature reed relays.

Another unwanted phenomenon in mixers is so-called "reciprocal mixing." This mixing is a direct consequence of oscillator noise modulation. When a large interfering signal appears at the mixer input, the signal will mix with oscillator noise and, although the interfering signal may be out of the i-f passband, the noise so produced will be within the i-f passband.

Reciprocal mixing is measured by the amount of noise introduced by a closely spaced interfering signal;

By Ovi Florea, WB2ZVU, 76 Whitson Road, Huntington Station, New York 11746

i.e., when the level of the interfering signal, expressed in dB above 1 μV and spaced 20 kHz away from the desired signal produces a reduction of signal-to-noise ratio by 10 dB.¹ Oscillator noise reduction is possible by a) careful elimination of unwanted spurious generation

Ultimately, reciprocal mixing reduces mixer dynamic range by raising its equivalent noise floor. As stated above, inherent oscillator noise modulation is also dependent on oscillator power; therefore, mixers working at high injection levels will be more affected.

table 1. Measured characteristics of the DX receiver 20- and 40-meter front ends.

receiver characteristic	40-meter band		20-meter band	
	rf ampl off	rf ampl on	rf ampl off	rf ampl on
Sensitivity for 10-dB s/n	0.5 μV (-119 dBm)	0.1 μV (-133 dBm)	0.2 μV (-127 dBm)	0.07 μV (-136 dBm)
third-order intercept point (dBm)	+23	+6	+15	+3
gain compression (dBm)	+10	-10	0	-15
dynamic range (dB)	100	100	100	100

on other frequencies, b) good dc filtering, c) good stability, and d) reducing oscillator power and narrowing oscillator bandwidth. Recommended low-noise oscillators are those consisting of differential amplifier integrated circuits with balanced output circuitry.

Front end. Four separate front ends are selected by rotary switch S1 (fig. 1). In this design resistors in the signal path were kept to a minimum as they are noise devices. Despite the cumbersome appearance, this setup allows individual band optimization and eliminates


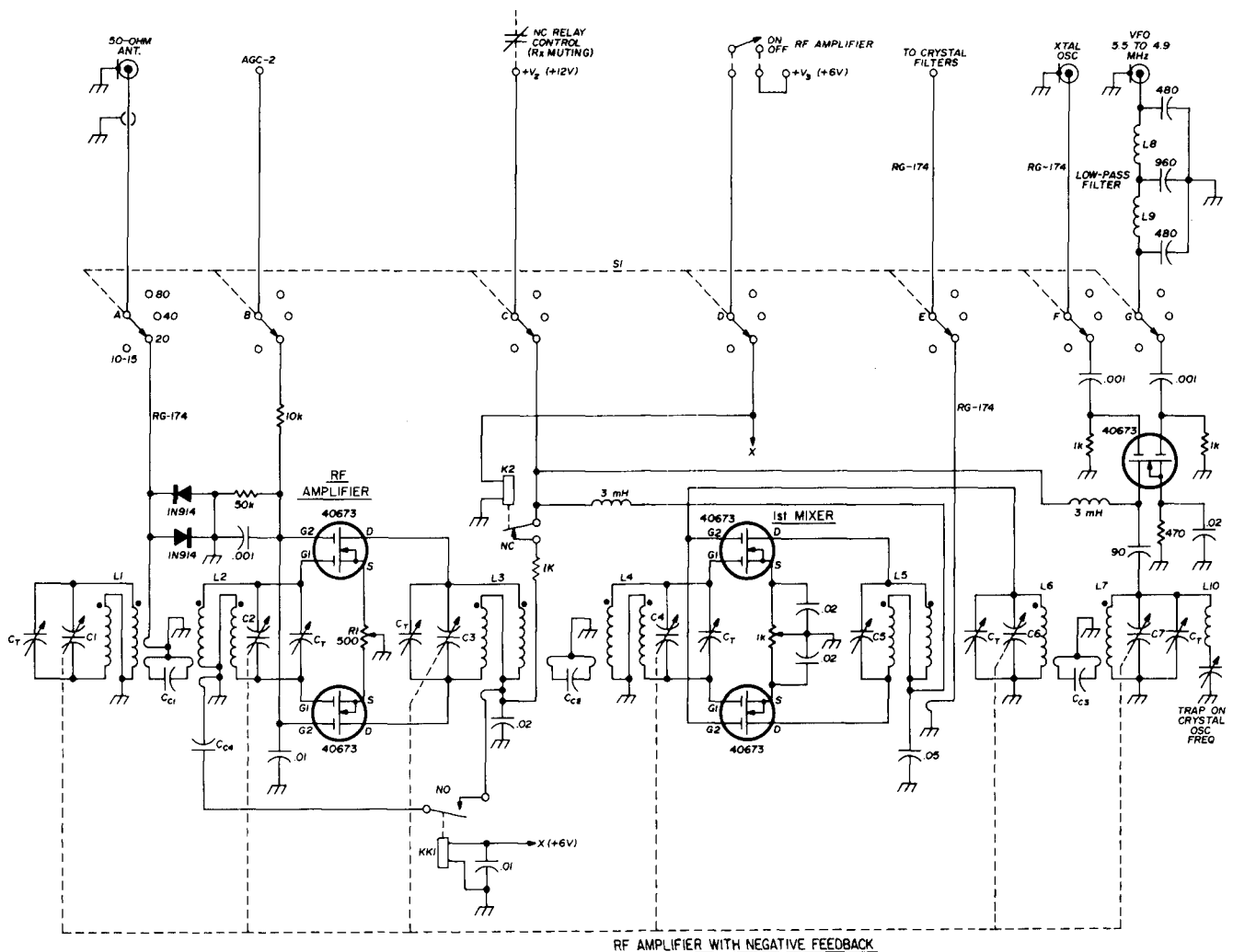


fig. 1 Schematic of the DX receiver front end, first mixer, and vfo. All links are one turn for an impedance of approximately 50 ohms. All trimmer capacitors are mica, 20 to 130 pF. L8, L9, 17 turns no. 24 AWG (0.5mm) on Amidon T-50-6 core. L5, 44 turns no. 28 AWG (0.3mm) wound 2 x 22 on Amidon T-50-6 core. The i-f is 3395 kHz.

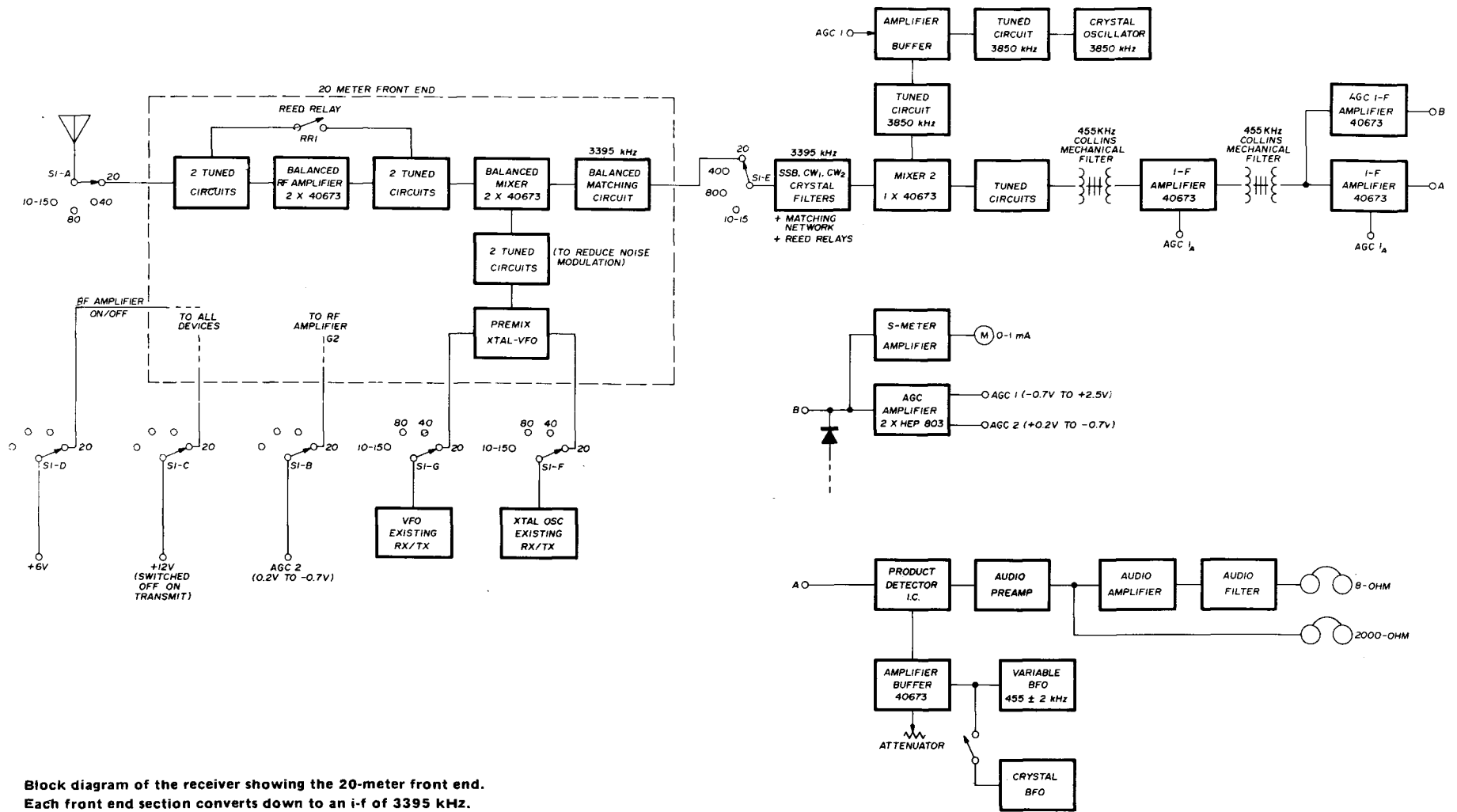

Block diagram of the receiver showing the 20-meter front end. Each front end section converts down to an i-f of 3395 kHz.

problems related to balanced circuitry switching. I was fortunate enough to obtain some surplus vhf six-gang split-stator variable capacitors. To prospective builders of this front end, I suggest the use of smaller units of the kind having a shaft extension on both sides, which could be mechanically ganged. A good substitution would be a matched set of varactors for an unbalanced arrangement.

Good tracking between rf input and pre-mixer output circuits is imperative since the 4-pole rf filter is very selective, particularly on the lower bands. On the

low values of CC3), while the upper quad could be saturated or unsaturated (our signal port). Recommended external biasing is:

$$(V6, V9) - (V7, V8) \geq 2 \text{ V}$$

$$(V7, V8) - (V1, V4) \geq 2.7 \text{ V}$$

$$(V1, V4) - (V5) \geq 2.7 \text{ V}$$

Filters. In accordance with modern receiver design practice, an ssb filter and two CW crystal filters are

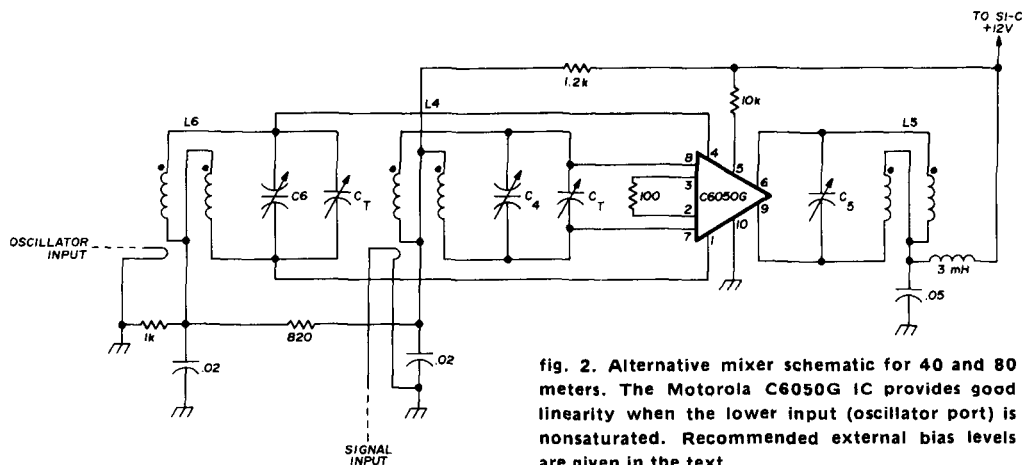


fig. 2. Alternative mixer schematic for 40 and 80 meters. The Motorola C6050G IC provides good linearity when the lower input (oscillator port) is nonsaturated. Recommended external bias levels are given in the text.

20-meter band with the rf amplifier off, measured filter response was 50 kHz wide at 20-dB down, which means that an unwanted signal 25 kHz away from the receive frequency is attenuated 20 dB. The frequencies shown in table 2 would be applicable to Kenwood or Heathkit lines, but the principle could be extended to other makes.

Mixer. The dual-gate 40673 mosfet mixer has lower third- and fifth-order products in its output when gate G2 remains nonbiased; however, gain is definitely lower. For best performance oscillator injection level was set at 300 mV.

Fig. 2 shows the 40- and 80-meter alternative mixer configurations. The Motorola C6050G double-balanced differential amplifier with emitter degeneration has good linearity when the lower input (i.e., our oscillator port) is nonsaturated (maximum 27-mV oscillator level — see

placed at the first mixer output through a matching network. Filter selection is accomplished by using remotely controlled miniature reed relays. Interelectrode capacitance of these reed relays is so minute that, when dc switching voltage is removed, signal feedthrough was measured at 120 dB down.

Fig. 3 shows the crystal filter arrangement. To obtain the above attenuation figure, filters were placed against a ground plane (double-clad printed circuit board, the face next to the filter grounded on one spot only). The second mixer is of classic design, and the local oscillator operates in a very stable mode. The second i-f strip is on 455 kHz and uses two Collins ssb mechanical filters.

Agc. An elaborate amplified agc system is derived from a separate uncontrolled i-f amplifier. One branch of this fast-rise, slow-decay agc system controls the i-f stages along with the local oscillator amplifier-buffer by

table 2. Coil and capacitor values for coverage between 3.5-28 MHz.

band (MHz)	frequency coverage (MHz) circuit 1 to circuit 4	circuits 6 and 7	vfo	xtal osc	L1 = L2 = L3 = L4 (turns)	coils and capacitors*				
						L6 = L7 (turns)	C1 = C2 = C3 = C4 (pF)	C6 = C7 (pF)	CC1 = CC2 (pF)	CC3 (pF)
3.5	3.5-4.0	6.895-	5.5-	12.395	2 x 20	2 x 16	10-30	8-20	800	90
		7.395	4.9		T-50-6					
7	6.9-7.9	10.295-	5.5-	15.895	2 x 14	2 x 12	10-30	8-20	470	51
		11.295-	4.9		T-50-6	L7 = 24T				
14	13.9-14.9	17.295-	5.5-	22.895	2 x 7	12T	10-30	8-20	350	330
		18.295	4.9		T-50-6	T-50-10				
21-28	20.5-30.0	23.895-	5.5-	29.895	2 x 5	8T	10-100	8-90	250	220
		33.395	4.9	36.895	T-50-10	T-50-10				
				37.395						

*No rf amplifier on 3.5 MHz. Rf amplifier on 7 MHz is unbalanced

Notes:

455 kHz i-f transformer:

A&B — primary impedance	$Z_p = 35k$	Radio Shack
secondary impedance	$Z_s = 6k$	"black core"
C — primary impedance	$Z_p = 60k$	"yellow core"
secondary impedance	$Z_s = 500k$	
D — primary impedance	$Z_p = 40k$	"white core"
secondary impedance	$Z_s = 1k$	

SSB crystal filter Trio 4 pole 2.2 kHz at -6 dB

CW-1 crystal filter Trio 4 pole .5 kHz at -6 dB

CW-2 crystal filter Heathkit .4 kHz at -6 dB

(CF = 3395.4 kHz)

Reed relays 6V miniature for PC board mounting

(Electronic Applications Co. 1A3A-H)

All resistors 1/4 watt

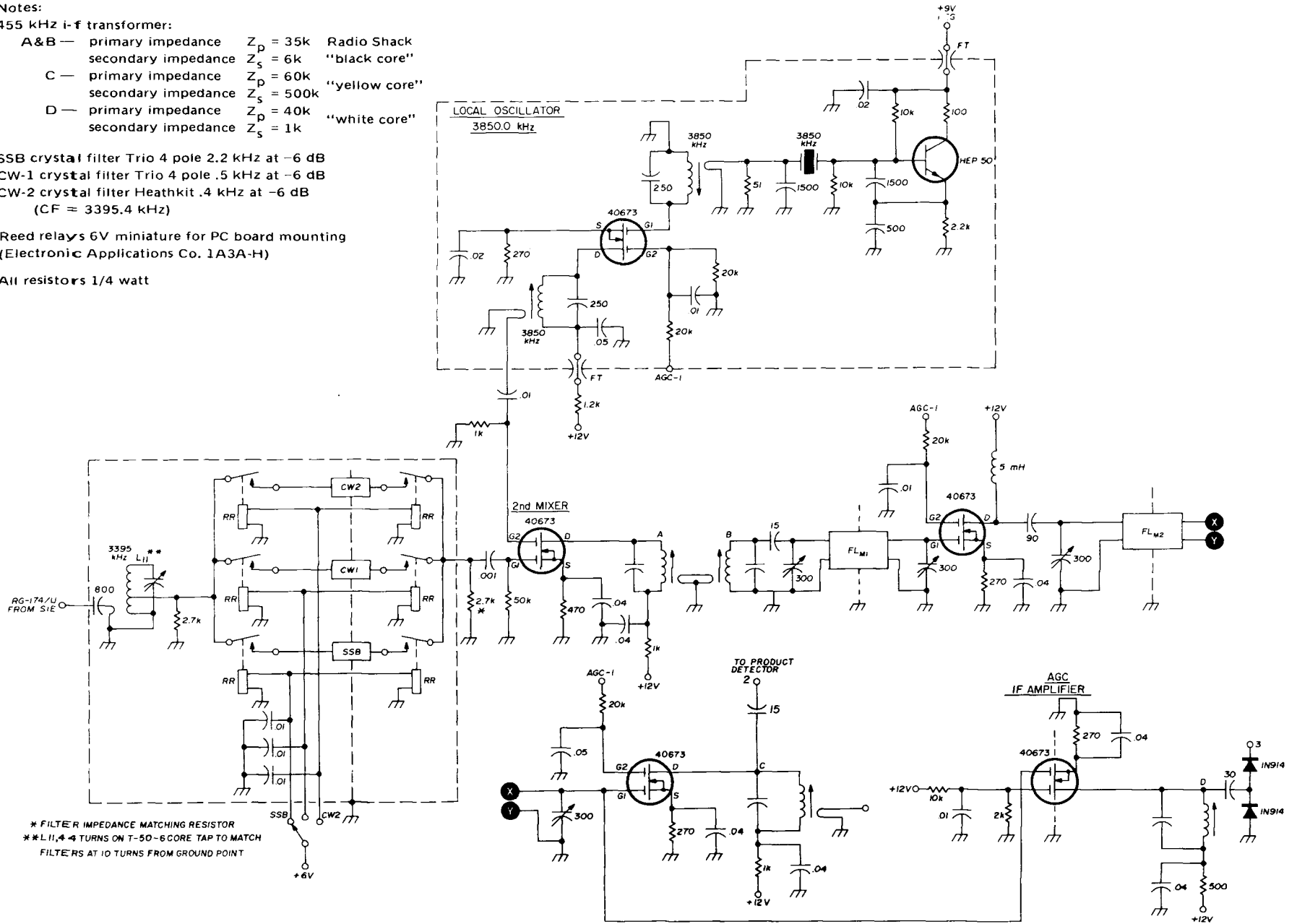


fig. 3. Crystal filter, local oscillator, second mixer, and agc amplifier schematic. Filter sections are selected by remotely controlled reed relays.

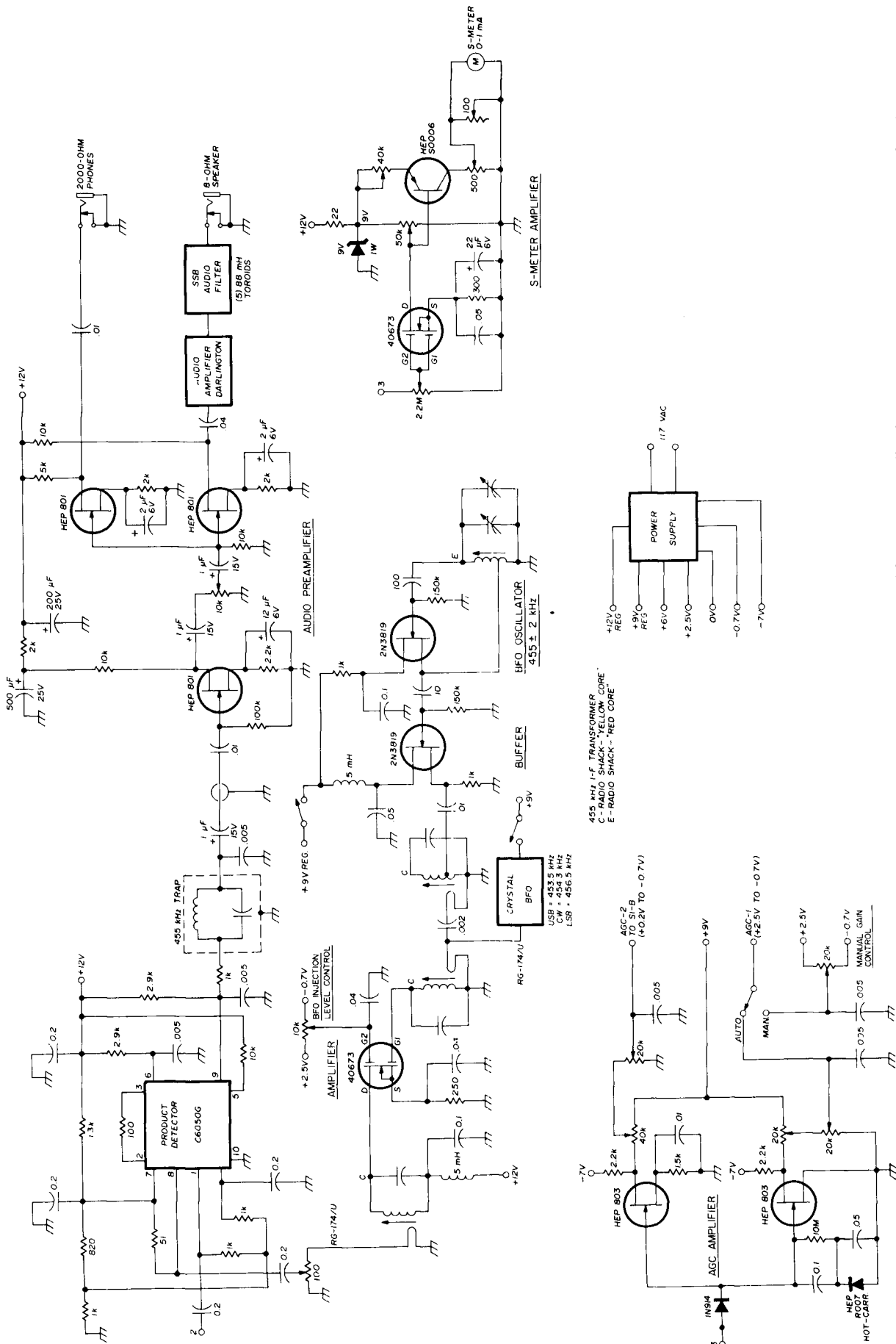


fig. 4. Product detector, bfo, agc, and audio circuits. The Motorola C6050G is used for the product detector, which produced excellent strong-signal rejection with decreased bfo injection voltage.

swinging voltages from +2.5 V (weak signals) to -0.5 V (strong signals). The second agc branch is threshold-biased and applied only to the rf amplifier over a restricted range, so that front-end linearity is not impaired. The receiver has a separate S-meter amplifier as shown in fig. 4. Minipotentiometers are used to calibrate the meter. Accuracy is within 3 dB, or one-half S-point.

Detector and bfo. The product detector and bfo are of particular interest. A very sensitive Motorola C6050G double-balanced IC makes a good product detector and requires a maximum of 300 mV bfo injection for the strongest signals.

The beat-frequency oscillator is variable within 455 \pm 2 kHz. Its output is amplified and filtered to supply the required maximum of 300 mV into a 50-ohm load at the product detector.



Theory says that, for minimum distortion a product detector requires carrier injection at least 10 times the level of the incoming signal at the input port. What would happen upon lowering that injection level? Decreasing the bfo level caused strong perturbing signals to become unreadable, while weak DX signals were still crystal clear. One helpful finding was that the audio output versus bfo level dropped about 10 dB faster for the stronger signal compared to the weak one.

A crystal bfo was incorporated for good transceive operation. This crystal bfo is used to calibrate the variable bfo. At times, the output from the product detector is extremely low; henceforth, a noiseless audio preamplifier is required. The receiver also employs a 5-toroid audio filter to alleviate inherent noise pickup when using an audio amplifier.

construction hints

This is an experimental receiver; appearance was secondary to conveniences such as avoiding stray noise pickup, rf feedback, and audio hum. It was constructed by degrees starting with the front end for the 20-meter band. Mosfet devices were first tested with respect to dynamic transconductance and dc for matching purposes. Each device was set up in an amplifier with a plug-in socket and identical rf signal levels were applied

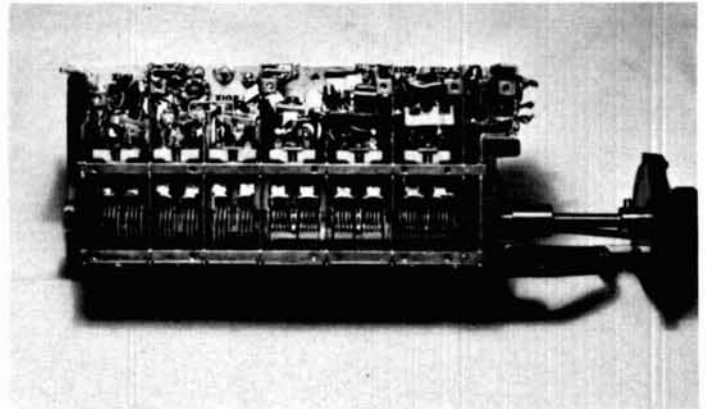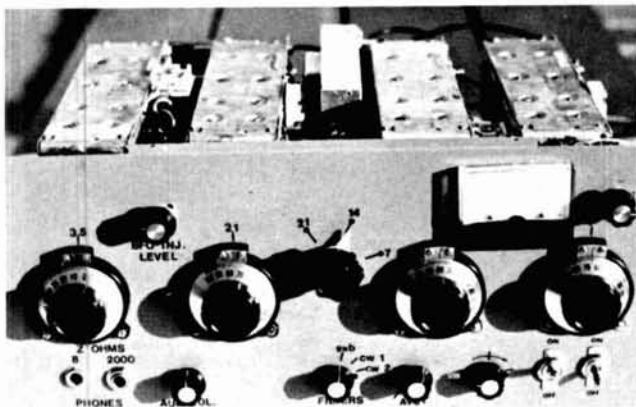Front view of the DX receiver with cabinet removed.



Typical receiver front-end arrangement. Capacitor stator plates are easily removable so that proper maximum-minimum capacitance is obtained for band coverage and precise tracking.

to both gates from a signal generator, while a vtvm was used to measure output level on a tuned circuit. A table was compiled, and devices showing close characteristics were paired. From 40 available devices I could select only three closely matched pairs, which leads to the conclusion that integrated mosfet circuits would be a far better choice.

tests and results

The 20- and 40-meter front ends were tested for sensitivity, IMD, gain compression, and dynamic range (table 1). Two powerful signal generators (most signal generators are not capable of delivering more than 100 mV into a 50-ohm load) were used, tuned 10 kHz apart, each at a level of +12 dBm, which becomes +6 dBm after the hybrid combiner. The spectrum analyzer indicated at this level an IMD of 35 dB on the 40 meter band.

acknowledgement

I wish to express gratitude to Serge Costin, WB2ZWJ, for his continuous technical advice in the design and construction of this receiver.

reference

1. B.M. Sosin, "HF Communication Receiver Performance Requirements and Realization," *The Radio and Electronics Engineer*, Vol. 41, July, 1971, pages 321-329.

bibliography

1. F.E. Terman, *Electronic and Radio Engineering*, New York, 1955, page 440.
2. W. Hayward, W7ZOI, "Receiver Dynamic Range," *QST*, July, 1975, page 15.
3. S. Maas, K3WJQ, "The Meaning of Sensitivity," *QST*, June, 1975, page 20.
4. R. Moore, "Modern RF Amplifiers," *ham radio*, September, 1974, page 42.
5. *Specification and Application Information*, Motorola Semiconductor Products, Inc., 1972.
6. Jim Fisk, W1DTY, "Receiver Sensitivity and Dynamic Range - What the Numbers Mean," *ham radio*, October, 1975, page 8.

ham radio

The one you've been waiting for!



Shown with optional Micoder™

HEATHKIT SYNTHESIZED 2-METER TRANSCEIVER!

\$269⁹⁵
With Standard
PTT Microphone

The new Heathkit 2-meter frequency-synthesized transceiver...

combines state-of-the-art technology with operating ease, convenience and versatility in an easy-to-build kit that's about **HALF THE COST** of comparable synthesized transceivers. It's the one to buy and build for real 2-meter PERFORMANCE!


Operation is easier than ever! The front panel lever switches select any frequency in any 2 MHz segment of the 143.5 to 148.5 operating bands. You select the last four digits, three with lever switches which display the frequency directly and the last with a 5 kHz toggle switch which makes ALL 2-meter frequencies in the band available. If you inadvertently dial up an out-of-band frequency, the transmitter simply will not key.

And the signal is solid! The HW-2036 puts out a minimum 10 watts at 25° C and 13.8 VDC. And it operates into an infinite VSWR without failure. The transmitter output is extremely clean (see spectrum analyzer photos above). True FM circuitry means you transmit and receive with excellent audio quality too.

The receiver is hot! Sensitivity is an outstanding 0.5 μ V for 12 dB SINAD. An 8-pole IF crystal filter provides an ideally shaped bandpass for excellent adjacent channel rejection and its superb selectivity characteristics make it the one to have for crowded signal areas.

Prices & specifications
subject to change without notice

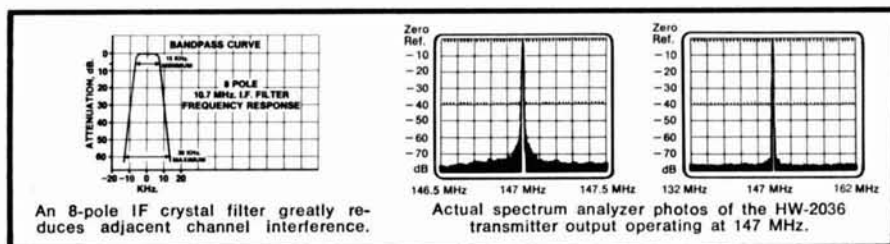Heath Company, Dept. 122-24
Benton Harbor, Michigan 49022



Complete operating versatility! A built-in continuous tone encoder — with three tones selectable on the front panel accesses most repeaters. Built-in simplex, + and - 600 kHz offsets, and an Aux. position that lets you add a crystal for any other frequency gives you all the offset capability you'll ever need. And, if you order the HW-2036 with the Heathkit Micoder combination microphone/auto patch encoder, you'll be able to make phone calls through repeaters equipped with auto patch input!

The HW-2036 operates from its built-in 12 VDC power supply, or you can use the optional HWA-2036-3 AC power supply, and operate it from a fixed station.

The HW-2036 is our best 2-meter transceiver. Check it out for yourself and you'll see it's the one to have for years of reliable 2-meter communications. Read more about the HW-2036 and all the other superb Amateur radio products in new Heathkit catalog. Mail card or send coupon today!



Nearly 400 fun-to-build, practical and money-saving electronic kits!
Send coupon today!

FREE Heathkit Catalog
Send coupon today!

HEATH
Schlumberger Heath Company, Dept. 122-24
Benton Harbor, Michigan 49022

Please send me my FREE Heathkit Catalog.
I am not on your mailing list.

Name _____

Address _____

City _____ State _____

AM-340 _____ Zip _____



loop antennas

A discussion of small
loop receiving antennas
and details on
their construction
for the
low-frequency bands

Most amateurs use the same antenna for both receiving and transmitting. This makes a lot of sense on vhf, and on 10, 15 and 20 meters, but at the lower frequencies which are more susceptible to noise interference entering via the antenna (160, 80 and 40 meters), the small loop receiving antenna has some advantages in reducing the susceptibility to certain types of noise. This article will attempt to explain the loop's operation in the simplest possible terms and will describe several practical loop antennas which are suitable for amateur use.

The electric- and magnetic-field components of an incoming electromagnetic wave are at right angles to each other. The plane formed by these components is at right angles to the direction of wave arrival. With the wave polarization and the direction of wave travel shown in fig. 1, both the electric and magnetic field components excite current flow in the vertical portions of the simple unshielded loop. The current induced by the electric field is due to the difference in charge impinging along the length of the vertical elements, while the current due to the magnetic field is because of the motor-generator action of the vertical conductors cutting the lines of force in the magnetic field as it moves past the conductors.

The currents due to both field components are mutually in phase, and although neither the electric nor the magnetic field components can exist without the other in the radiated electromagnetic field, the loop antenna behaves identically with excitation from either or both field components.¹

While the voltage available at the terminals of a dipole is simply proportional to the current induced in the dipole, the voltage available at the terminals of a small loop is proportional to the *difference* between the

By John R. True, W40Q, 10322 Georgetown Pike,
Great Falls, Virginia 22066

currents induced in the two opposite vertical loop elements. No currents are *induced* in the top or bottom horizontal conductors connecting the vertical elements.

When the *axis* of the loop is pointing toward the signal source as in **fig. 1A**, the two vertical elements of the loop are excited at the same phase point of the wave front. Thus the current induced in both elements is of the same amplitude and phase, and flow in the same absolute direction (see **fig. 2**). However, the two currents are actually flowing in opposite directions with respect to a continuous, one-way travel around the loop, and therefore cancel each other, producing zero net voltage.

On the other hand, when the *plane* of the loop is pointing toward the signal source, as in **fig. 1B**, maximum voltage is produced because the two vertical elements are now in positions of maximum *difference* in phase relationship with the wave front, with the resulting difference between the currents induced in the vertical elements producing a maximum voltage. In fact **fig. 1B** shows that during the portion of the wave cycle when the field is changing most rapidly, the currents in the two elements are flowing in *opposite* absolute directions (one flowing upward and the other downward), with the result that both currents are actually flowing in the *same* direction around the loop, and are therefore mutually aiding instead of opposing as in **fig. 1A**. For orientations of the loop at angles in between the two just described, and in general, the voltage produced is proportional to the cosine of the angle formed between

Junction box for the square loop antenna containing 80/40 bandswitch, balun and tuning capacitor.

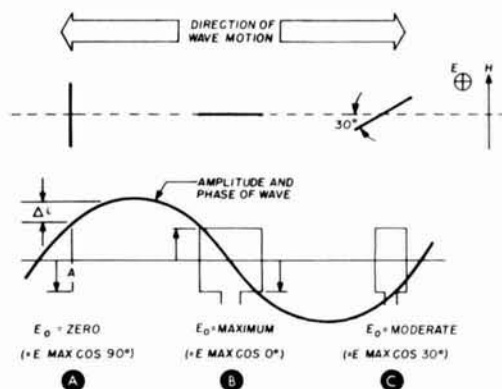
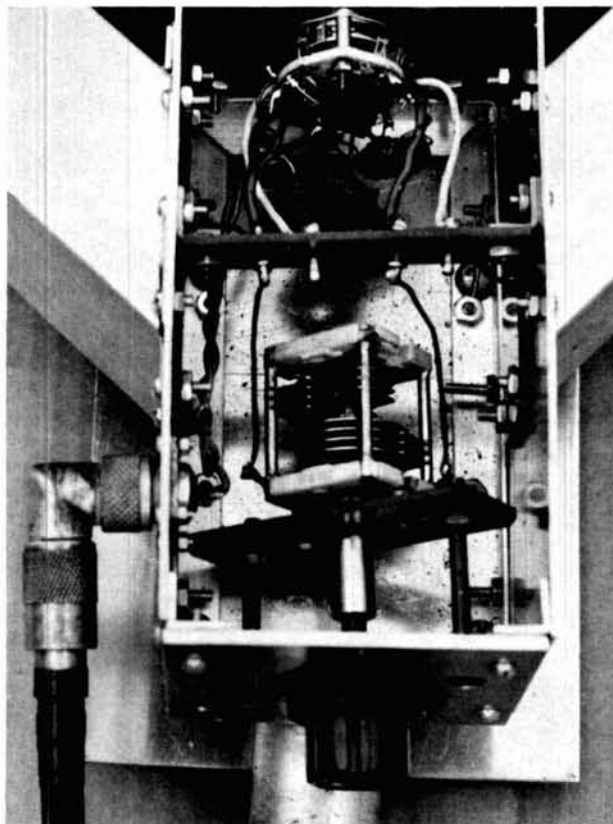



fig. 1. Directivity of the loop arises from the interception of the wavefront by each half of the antenna. In (A) the currents are of equal amplitude and phase, producing no net voltage difference at the output. In (B) the currents are at maximum amplitude and phase difference, producing maximum output voltage. In (C) the current difference between loop halves is moderate, producing a corresponding voltage difference at the output terminals. Voltage output is small for angles larger than 60 degrees.

the loop plane and direction of the wave propagation, as in **fig. 1C**. The resulting figure-eight radiation pattern is thus a perfect pair of circles tangent to one another as shown in **fig. 3**.


For several basic reasons, nearly all practical loop antennas are electrostatically shielded by means of an open-turn shield. One reason is that electrostatic shielding is a convenient way of achieving a capacitance balance between the two opposite halves of the loop and ground. Without this balance the figure-eight pattern would be distorted and the nulls misplaced and obscured. Second, the open-turn shield shown in **fig. 3** forms a balun, permitting the loop to feed an unbalanced load without upsetting the loop-to-ground balance. And third, electrostatic shielding renders the loop insensitive to the electric component of a passing wave. This has an insignificant effect on the reception of a wave propagated in the far field (radiation field). However, in the case of several types of man-made noise interference, the effect is to reduce the reception of the noise.

If the electrical disturbance producing the interfering noise is confined primarily to the *induction* field (as many such noise disturbances are), the electric compo-

fig. 2. Electric (E) and magnetic (H) components of a wavefront impinging upon a loop antenna, showing current flow in the loop. When the plane of the loop is parallel to the wavefront, as shown here, output voltage is minimum (see **fig. 1A**).

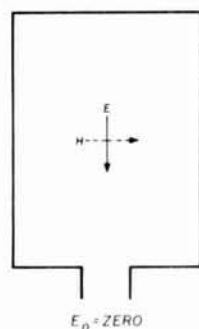

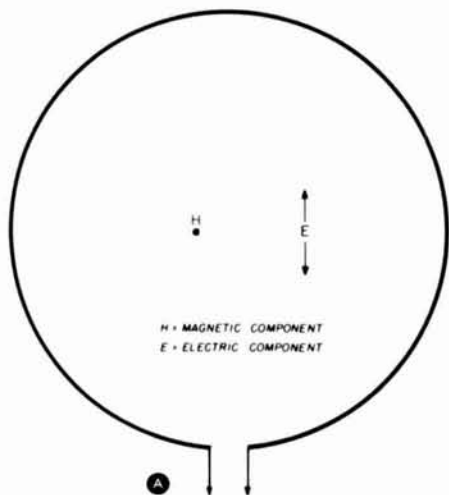ment generally predominates over the magnetic field. Since the shielded loop is sensitive only to the magnetic field, there's a noticeable reduction in noise pickup as compared to that of a vertical dipole. Providing the desired signal is not arriving from the same direction as



out the loop of relatively equal amplitude and phase. This condition will produce the figure-eight pattern illustrated, but lengths in excess of this criteria will cause some pattern distortion. Reference 4 states that loops as large as 0.1 wavelength in diameter (0.314 wavelength


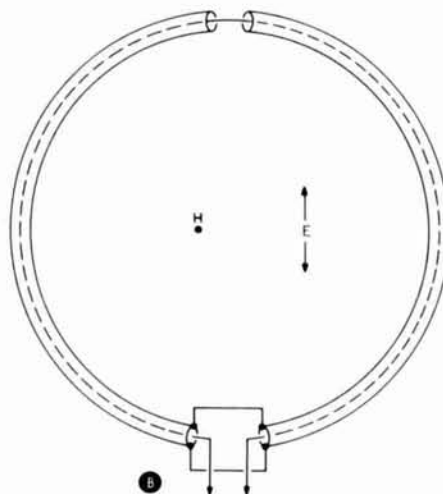


fig. 3. Unshielded loop antenna (A) and shielded loop antenna (B). There is no difference in the radiation patterns of the unshielded or shielded loop (C) if the output is balanced and if the capacitance to ground from both sides of the loop are equal. Loop pattern distortion results from these types of imbalances, and shielding the loop is one way of achieving the desired balance.

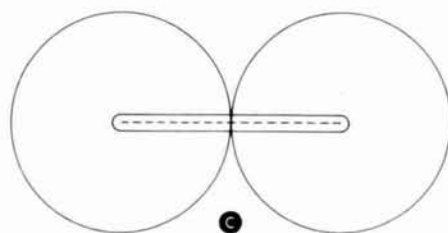

the noise, some additional reduction in noise interference level is also available due to the directivity of the loop radiation pattern. Simply pointing the axis of the loop in the direction of the noise will minimize the noise pickup, while the desired signal still arrives from a favorable angle on the directivity pattern.


In general, atmospheric noise is propagated as a *radiation* field, generated by the electrical discharges that attend thunderstorms, both locally and throughout the world. Noise from an electrical storm concentrated in a single direction may be reduced by the directive properties of a shielded loop, but not by its insensitivity to the electric field. On the other hand, interference from precipitation static will be effectively reduced by the shielding properties of the loop because precipitation static is caused by an *induction* field localized directly around the receiving antenna.

The illustration of fig. 1 is greatly exaggerated. When a loop 6½ feet (2m) between legs is used on 80 meters, the maximum wavefront intercepted represents only a small fraction of the energy intercepted by a half-wavelength dipole. However, such a small antenna is still adequate for good signal reception.

References 2 and 3 state that a maximum wire length of about 0.08 wavelength will produce currents through-

circumference) can be used without serious pattern distortion. However, this reference is confined to aperiodic loops, while reference 2 deals with loops that are tuned, providing higher Q. The higher Q changes the current and phase difference in the loop wire, resulting

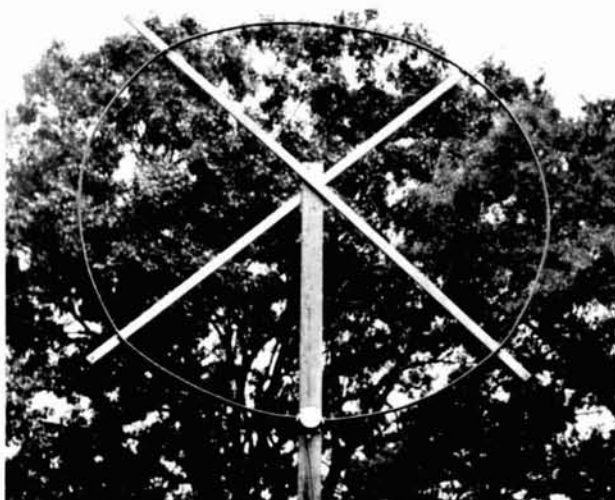The coaxial loop of fig. 4 as built by the author.



in the shorter specified loop lengths (0.08 wavelength maximum).

The advantage of dual-band reception from a single loop further compromises the design criteria. For those who wish to retain the criteria of references 2 and 3,

towers and guy wires, etc., signals will be injected into a loop antenna from both the direct signal and re-radiation from these nearby structures. If such structures have high Q and are at or near resonance at the frequency of the exciting signal, their energy may approach that of

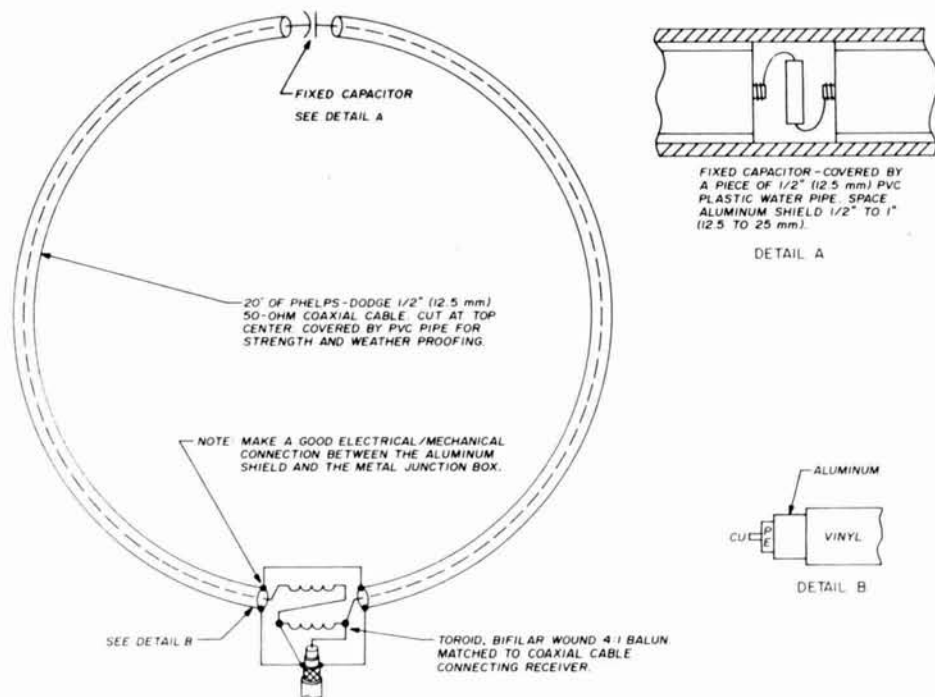


fig. 4. Single-turn coaxial loop antenna suitable for use on 80 and 160 meters. The toroid transformer balances the loop output to ground, whether shield is present or not. Typical dimensions are listed in table 2.

table 1 has been included. Corrections to table 2 must be made to compensate for this altered construction. Single-band designs would do well to follow the referenced design for maximum performance.

effects of nearby re-radiation


If there are metallic structures near the loop antenna of ample conductivity and size, such as power lines, homes with electrical wiring, water and furnace air-conditioning ducts and piping, as well as antennas,

the direct signal and cause appreciable deviation to the true bearing of the signal source. The resultant voltage induced into the loop will be the vector sum of the amplitude and phase of the multiple sources. Since the amateur is not generally interested in obtaining accurate bearings of signal sources, such deviation is relatively unimportant. What is of prime importance is the amplitude of the desired signal and, secondarily, the depth of

table 1. Maximum wire length for direction-finding loops as specified in references 2 and 3 (0.08 wavelength).

frequency (MHz)	wavelength (meters)	maximum wire length
1.8	166.7	43' 7" (13.28m)
1.9	157.9	41' 4" (12.60m)
3.5	85.7	22' 6" (6.86m)
3.6	83.3	21' 10" (6.67m)
3.7	81.1	21' 4" (6.49m)
3.8	78.9	20' 9" (6.32m)
4.0	75.0	19' 8" (6.00m)
7.0	42.9	11' 3" (3.43m)
7.1	42.3	11' 1" (3.38m)
7.2	41.7	10' 11" (3.33m)
7.3	41.1	10' 9" (3.28m)

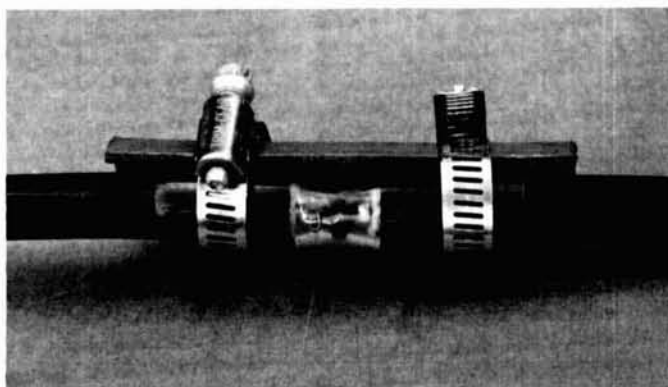Detail of the break in the coax at top of loop. See detail B in fig. 4.



the null available to reduce the strength of an interfering signal.

If installed with the axis of the loop horizontal, only signals from the horizon i.e., low angle or ground wave, will produce the deep nulls shown. Signals from higher vertical angles will not have their wave front parallel to

lated covering that will provide strength to this point of the loop will be satisfactory, but it should also provide a weatherproof seal to keep moisture out of the break. Before placing the cover on the break, check for peak performance on your desired portion of the band. I used a grid dipper in the shack and tuned its signal in on the

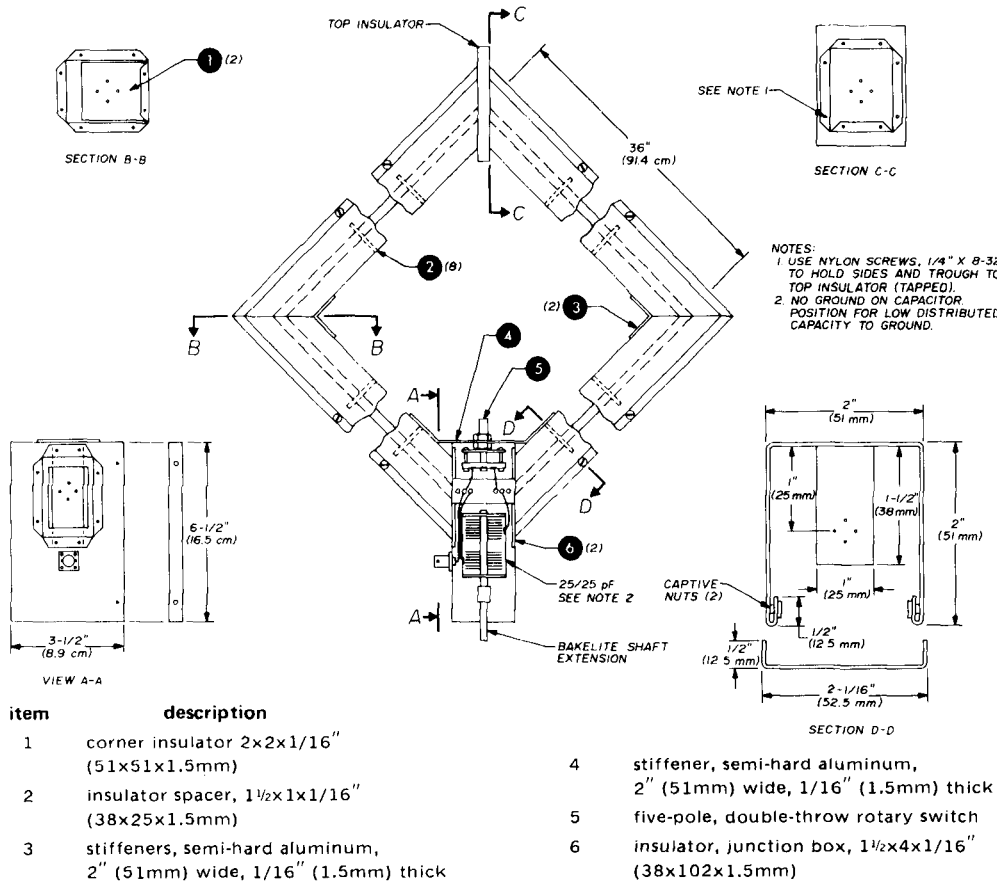


fig. 5. Double-turn, square-loop antenna for 40, 80 and 160. Typical loop dimensions and tuned-circuit components are listed in table 2.

the plane of the loop and even though the azimuth is correctly set, the signal received will still be appreciable.* Therefore, do not expect many signals to show an extremely sharp null unless provision is made to tilt the loop axis in elevation as well as azimuth.

As shown in fig. 4, a practical loop antenna may be built from a single turn of coaxial cable. The shield must be broken as previously explained to remove the "shorted turn" effect. A loop so configured will almost completely shield the electric component of the wave. To insure retention of the figure-eight pattern the two halves of the loop must maintain symmetry as closely as possible.

Detail B of fig. 4 shows the method used to insert a capacitor between the ends of the inner conductor as well as providing spacing of the outer shield. Any insu-

receiver. I noted each frequency for S-meter reading, then substituted various fixed capacitors (and combinations) to center the required bandpass.

An alternate construction method is shown in fig. 5. This illustration should provide most of the required construction details. The stiffeners at the junction box, J, and the two side corners were added to reduce the floppiness that existed without them. An even number of turns is required for symmetry since both the inductor and the capacitor are located in the junction box. Two turns (33 inches or 83.8cm on a side) are adequate for 80 and 160 meter operation. For 40 and 80 meters, two turns (16 inches or 40.6cm on a side) would comply with the design criteria of reference 1. For single-band operation, the lengths given in table 2 provide an optimum signal-to-noise ratio and should result in maximum performance.

The tuneup procedure for the square loop is similar to that for the circular loop. Using a length of coaxial cable with a loop at the end attached to the output

*This feature of the loop enhances its ability to null out interfering signals, particularly local ground waves or electrical noise, while still maintaining reception of skywave signals. Editor

connector, the grid dipper is used to get the resonant frequency of the system near that required. (Caution: The grid dipper will also show a dip at the resonant length of the coaxial cable used.) Vary the number of turns on the primary of the toroid and the fixed paralleling capacitor until the loop shows peak pickup

I have substituted an alternate coupling network shown in fig. 6 that provides slightly better pickup and higher loaded Q. It has been incorporated in all loops shown in figs. 4, 5 and 6. Table 3 lists the required components.

The Hula-Hoop was separated, and the twinlead inserted. The loop is then spirally covered with folded

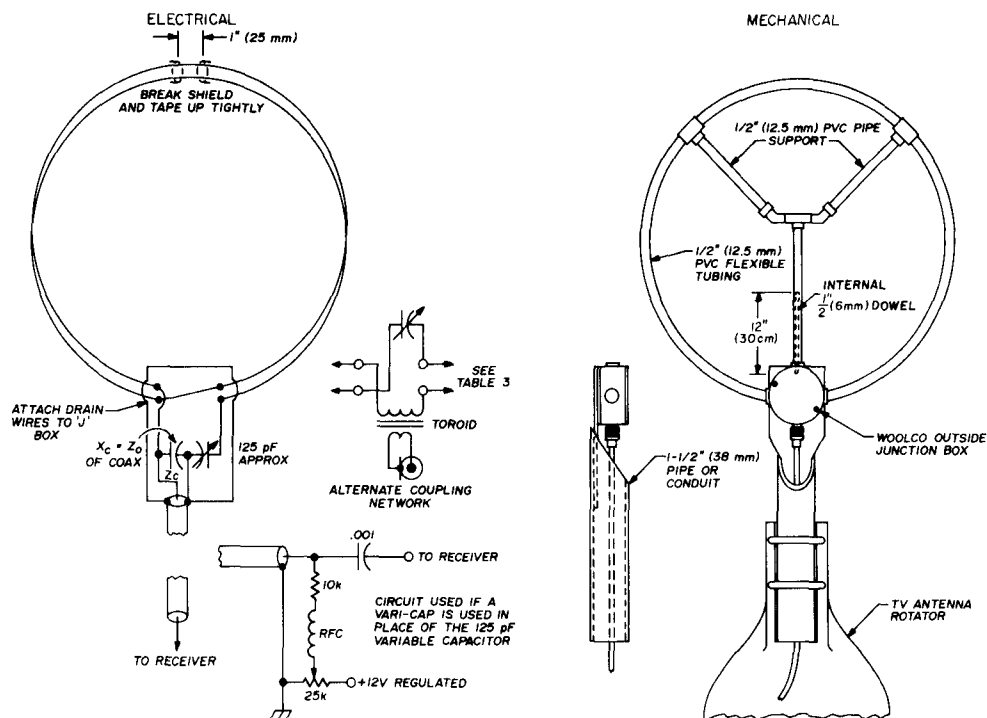


fig. 6. The Hula-Hoop designed by W5DS. The alternate coupling network is suggested. Component values for the coupling network are given in table 3.

near your favorite spot in the band. Then position the loop where it is to be permanently mounted, with the required length of coaxial cable to connect it to the receiver, and inject a grid dipper signal into it. Plot the S-meter reading for each frequency. Adjust the inductor and capacitor until the bandpass is centered on the desired frequency.

(two layers, 3-inches or 76mm wide) heavy-duty aluminum foil with a number-15 (1.5mm) aluminum drain wire to provide connection for the foil shield. This was then continuously taped with vinyl electrical tape for weatherproofing. The aluminum wire is connected to the junction box to provide a path to ground for currents induced by the electric component of the wave.

table 2. Wire lengths and tuning capacitors used in the loops of figs. 3 and 4.

	frequency (MHz)	loop size	wire length	number of turns	toroid turns		capacitor (pF)	
					primary	secondary	variable	fixed
coaxial cable loop	1.8 MHz	8'3" (2.5m)	26' (7.9m)	1	20/20 balun		0	500
	3.8 MHz	6'3" (1.9m)	20' (6.1m)	1	10/10 balun		0	125
square loop	1.8 MHz	36x36" (91x91cm)	48' (14.6m)	4	40	8	15-15	0
	3.5 MHz	36x36" (91x91cm)	24' (7.3m)	2	24	6	15-15	40
	7.0 MHz*	36x36" (91x91cm)	24' (7.3m)	2	12	7	15-15	75

*This loop built before reading references 2 and 3 so wire is considerably longer than 0.08 wavelength. Although it works fine, the design criteria of those references is recommended.

A third arrangement is shown in fig. 6. It was suggested by Bob Edlund, W5DS, who has named it the "Hula Hoop Loop" due to the basic material used to support the loop wires. A single-turn of TV twinlead is used to provide a two-turn loop when series connected.

I used a 10-foot (3-meter) length of 1/2 inch (12.5mm) PVC tubing in place of the Hula-Hoop. This in turn is supported by 1/2 inch (12.5mm) PVC water pipe and fittings to form a Y-shaped support for the loop. A 1/2-inch (12.5mm) wooden dowel, boiled in beeswax, was

inserted into the vertical member of the Y support, terminating in the junction box to increase strength against wind torque at this point. The coupling networks shown will provide a good match between the loop and the coaxial line to the receiver.

In an attempt to remotely tune the loop a voltage-

In all loop configurations and couplers I tested there is a loss of about two S-units of signal pickup with respect to the vertical radiator I use for transmitting on 40 and 80 meters. Some of the weaker signals are then below the noise level of the receiver. A low-noise front-end preamplifier/preselector, similar to that described


table 3. Components for the alternate coupling network shown in fig. 5.

frequency	twinlead length	loop diameter	approximate capacitance		toroid primary turns	secondary turns
			(pF)	type		
1.8 MHz	20' (6.1m)*	3'3" (99.1cm)	150	T106-2	14	8
3.5 MHz	10' (3.0m)	3'3" (99.1cm)	110	T68-2	12	7
7.0 MHz	5' (1.5m)	1'7" (48.2cm)	75	T56-2	10	6

*Two turns (be sure capacitor is centered in loop).

variable capacitor (varicap) was substituted for the capacitor in the loop-coax coupling network. John Venters, K4UR, suggested, and provided, a silicon planar epitaxial diode (ITT type BA163) which, when reverse biased with 1 to 12 volts dc, provides a capacitance range of 10 to 260 pF. However, when feeding the varicap via the rf coaxial line with the required rf chokes to isolate the dc from the rf, the loaded Q dropped to about 10 (indicating the introduction of some form of undesired loss resistance). The convenience such a device would provide is worth further investigation; however, still to be found is a way to use the varicap and retain high Q. With the coupling networks shown, the loaded Q is in the vicinity of 75. This provides a 50-kHz bandwidth (at the 6 dB points) which is adequate on 80 meters if you operate near one spot most of the time.

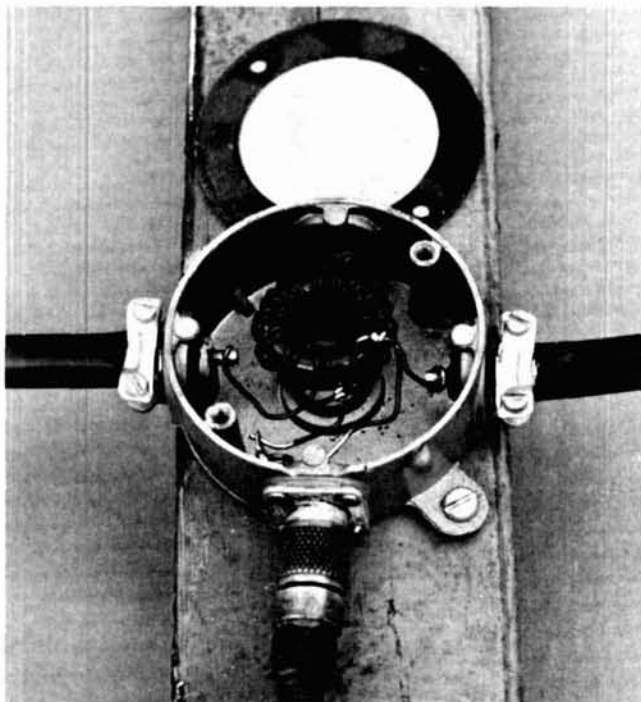The 4:1 balun for the coaxial loop, mounted in the Woolco junction box.



recently in QST⁵ provides about 20 dB gain and puts the signal back up where the receiver can detect even the weakest signals.

conclusions

Comparing the loops against my "Five Band, Tower Antenna System"⁶ for receiving, I get about five S-units reduction of man-made noise and precipitation static,* with only a loss of a couple of S-units of signal pickup.

Since the radiation resistance of such a small loop on the wavelengths involved is less than one ohm, it would make a very poor transmitting radiator.

*Atmospheric noise is propagated entirely by the radiation field so it cannot be reduced by using a shielded loop antenna. Precipitation static which is due to wind-blown rain, on the other hand, is an induction field and can be reduced by using a shielded loop.

Editor

references

1. H. H. Skilling, *Fundamentals of Electric Waves*, John Wiley & Sons, New York, 1942, page 150.
2. *ARRL Antenna Handbook*, 11th Edition, ARRL, Newington, Connecticut, 1968, page 64.
3. R. Landee, D. Davis, and A. Albrecht, *Electronic Designer's Handbook*, McGraw-Hill, New York, 1957, page 21-20.
4. John D. Kraus, *Antennas*, McGraw-Hill, New York, 1950, Chapter 6, "Loops," page 161.
5. D. DeMaw, W1CER, and L. McCoy, W1ICP, "Learning to Work with Semiconductors," *QST*, September, 1974, page 38.
6. J. R. True, W4OQ, "Grounded Vertical-Tower Antenna System," *ham radio*, May, 1973, page 56.

bibliography

1. D. S. Bond, *Radio Direction Finders*, McGraw-Hill, New York, 1944, "Loop Antennas," page 87.
2. H. Jasik, *Antenna Engineering Handbook*, McGraw-Hill, New York, 1961, "Single Loops," page 28.5.
3. R. Keen, *Wireless Direction Finding*, Iliffe & Sons, London, 1946.
4. R. King, H. Mimno, and A. Wing, *Transmission Lines, Antennas and Wave Guides*, Dover Publications, New York, 1965, "Loop Antenna for Reception," page 230.
5. R. L. Nelson, K6ZGQ, "Receiving Antennas," *ham radio*, May, 1970, page 56.
6. P. C. Sandretto, *Principles of Aeronautical Radio Engineering*, McGraw-Hill, New York, 1942, "The Loop Receiving Antenna," page 110.

ham radio

Open the door to a new world...

of continuous-tuning short wave!

Combine synthesized general coverage flexibility...

...with the selectivity, stability, frequency readout and reliability of the world-famous Drake R-4C or SPR-4 Receivers, and you're on your way... the new solid state Drake FS-4 Synthesizer writes your ticket...



**DRAKE FS-4
GENERAL COVERAGE
FREQUENCY SYNTHESIZER**

- Interfaces with all R-4 series receivers and T-4X series transmitters: (R-4, R-4A, R-4B, R-4C, SPR-4, T-4, T-4X, T-4XB and T-4XC), without modification.
- MHz range is set on FS-4, with kHz readout taken from receiver dial.
- Complete general coverage—no range crystals to buy.
- T-4/T-4X series transmitters transceive on any FS-4 frequency, when used with R-4 series receivers.
- For use with SPR-4, order Interface Kit Model 1523.
- **Model FS-4 Amateur Net... \$250.00**



R-4C/FS-4

Continuous coverage from 1.5 MHz through 30 MHz with Passband Tuning, Notch Filter, optional Selectable 8-pole Crystal Filter for optimum selectivity, and 1 kHz readout from the famous Drake PTO.



SPR-4/FS-4

Continuous coverage 150 kHz-30 MHz. • Built-in L/C Filter for selectivity on AM, CW, USB and LSB. • Versatile combination when your needs include low frequency Marine and Broadcast band coverage. • Readout 1 kHz with Drake PTO • All solid state.

Now available at your Dealer


To receive a FREE Drake Full Line Catalog, please send name and date of this publication to:

R. L. DRAKE COMPANY



540 Richard St., Miamisburg, Ohio 45342
Phone: (513) 866-2421 • Telex: 288-017

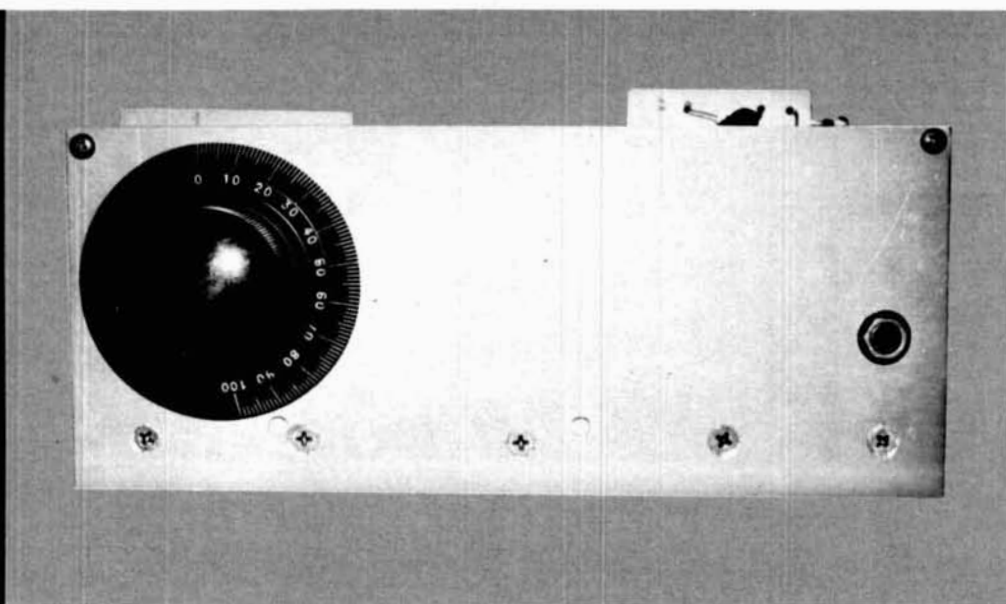Western Sales and Service Center, 2020 Western Street, Las Vegas, Nevada 89102 • 702/382-9470



QRP transmitter for 7-MHz CW

This little rig
is still in
the low-power class,
but it will make
a big difference
on the crowded
40-meter band

The amateur radio literature over the past several years has described numerous solid-state QRP transmitters. Most of these transmitters have been in the power range of milliwatts, some a little higher and a few as high as 5 or 10 watts. These articles have made significant contributions to the development of better solid-state transmitters and have also kept interest high in building and testing such transmitters. The authors wish to thank all who have published their circuits and designs, thus enabling others to experiment and build designs of their own.

The CW transmitter described here is not just another low-power rig. It has some features that make it interesting, very inexpensive to build and, using a twenty-cent transistor in the final stage, it provides 20 to 30 watts input. The CW note is a pure delight to hear. All the transistors, which cost from twenty to fifty cents, are easily obtainable from Poly Paks, Radio Shack, and many surplus radio parts dealers.

The transmitter can be duplicated easily as it contains no critical circuits. It is built on five pieces of perf board, although etched PC boards would be the best construction approach. One such transmitter, built into a transceiver, has worked into most of the U.S., parts of Europe, and Australia.

power supplies

Before discussing the transmitter circuits, we'll talk about power requirements. A power supply must deliver

By Col. H. J. Stark, WA4MTH, 9231 Caribbean Boulevard, Miami, Florida 33189 and Dr. Si Marians, W4LPW, 6261 Collins Avenue, Miami Beach, Florida 33141

the quality and quantity of current and voltage required by the transmitter or problems will occur such as instability, poor performance, burned-out transistor, chirps, and key clicks.

This transmitter uses two separate power supplies. The first is a 12-volt, well-filtered and regulated supply capable of delivering up to 1 ampere. The transmitter will require about 250 mA from this supply. Reference 1 describes the power supply we used. The second supply powers the final amplifier transistor. It's a very useful power supply for transistor experimentation and test work, providing a well-regulated output to about 3 amperes at variable voltages between 5-30 volts. Its three transistors can be purchased for less than a dollar each. This power supply could be updated with an IC voltage regulator, but the circuit of reference 2 was used and is recommended.

circuit description

The transmitter has five stages, fig. 1. The vfo and doubler run continuously when the transmitter is keyed. The keyed stage, buffer amplifier Q5, Q6, operates in class C. Although collector voltage is present on this stage during operation, it has no rf output until the key is closed. Power to the vfo, doubler, buffer, amplifier, and driver is supplied by the 12-volt supply. The final


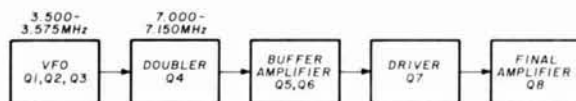


fig. 1. QRP transmitter block diagram. Eight low-cost transistors provide 2-30 watts input power for beefing up your CW signal on 40 meters.

amplifier, which also operates in class C, is powered by the variable 5 to 30 volt supply. Voltage to the other stages must be turned off during receive so you can hear the other fellow in your receiver.

Variable-frequency oscillator. The vfo (fig. 2) is straightforward, using an fet in a Colpitts configuration followed by an amplifier stage and an emitter follower for isolation. The vfo tunes 3.5-3.575 MHz. If you wish, you can make it tune the entire 75-meter band and have as much bandwidth as desired. This circuit has little bandwidth, however, as we're concerned with only 125 kHz of the 40-meter band, including the Novice portion.

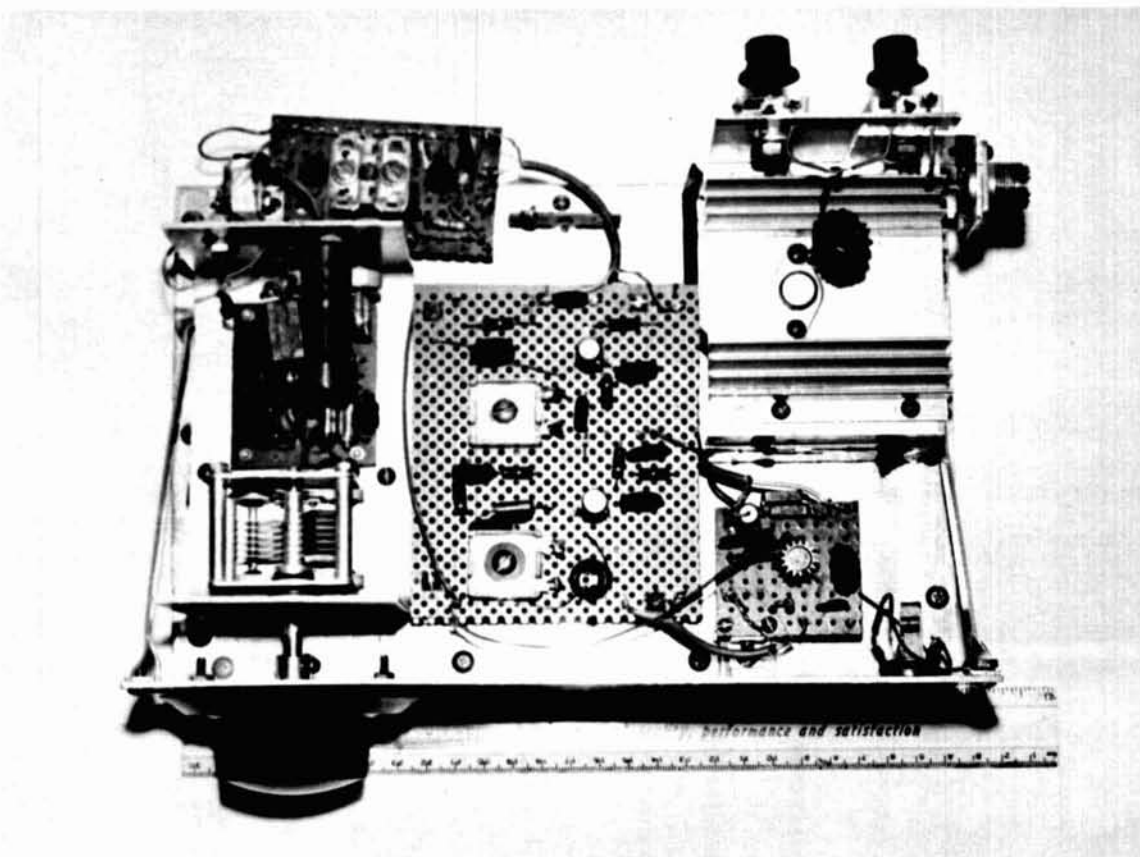The significant feature of this vfo is that frequency doubling from 3.5 to 7 MHz is used. This technique avoids pulling effects on the vfo frequency when keying the transmitter. The note you hear is the note that goes out over the air — crisp, clean, and chirpless. A 6.8-volt



The completed QRP 7 MHz CW transmitter. Vfo section is at left with the frequency doubler mounted at its rear. Buffer amplifier and doubler are shown at right, with the final amplifier removed from the chassis.

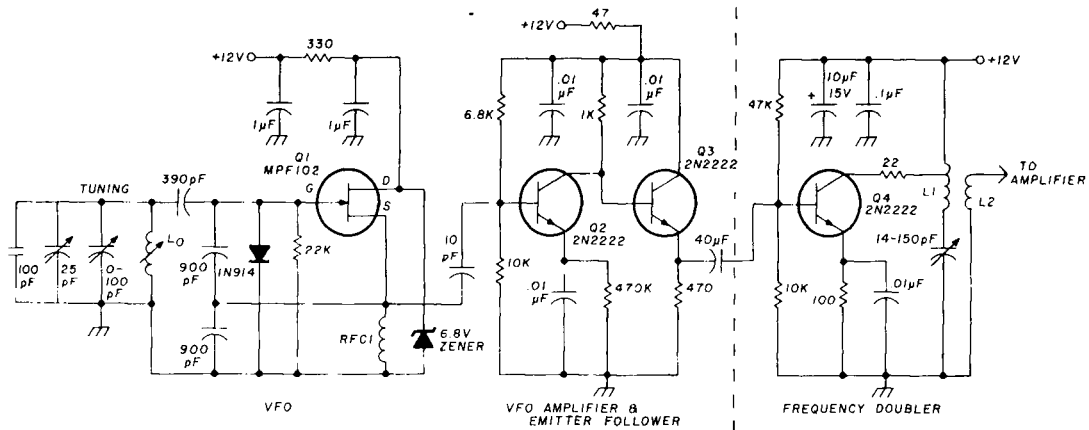


fig. 2. Vfo and frequency-doubler schematic. Circuit provides a stable, harmonic-free output to drive succeeding stages.

zener in the drain of Q1 and a high-speed switching diode in its gate ensure low harmonic content in the vfo output. The 1N914 acts as a clamp on the positive-going half cycle of the oscillator signal, thus preventing Q1 from reaching an operating point where high harmonic content may occur. Although many other transistors could have been used for the vfo amplifier, emitter-follower and doubler, the 2N2222 was chosen on the basis of performance and low cost.

Buffer amplifier. In this stage we begin to get a lift in rf output. Fig. 3 shows the circuit, which uses two 2N3053s in class B. The 2N3053 will easily dissipate the power, provided it has a proper heatsink. The 12-volt supply to the collector must be well bypassed, and ferrite-bead chokes must be used on the collector leads. This is the keyed stage: the 2N3053 emitters aren't grounded until the key is closed. The component values shown in fig. 3 will permit this stage to function as a

stable amplifier. Neutralization wasn't found to be necessary.

Driver. The driver is the simplest of all the stages. It operates as a class-C amplifier. The reliable 2N3053 is also used here, and it *must* be installed in a heatsink, otherwise it will be zapped. If this occurs, the 12-volt power supply will draw excessive current.

Final amplifier. So far we've been concerned with stages resonant at 3.5 or 7 MHz. In the final amplifier stage, however, we must think not only of having a 7-MHz resonant output circuit but must obtain an output impedance close to 50 ohms to match the antenna feedpoint impedance.

The final amplifier (fig. 3) also operates in class C. The input circuit to Q8's base uses a tuned-T network, and the collector output circuit uses a pi network so that the amplifier output impedance will be near 50 ohms. Rf

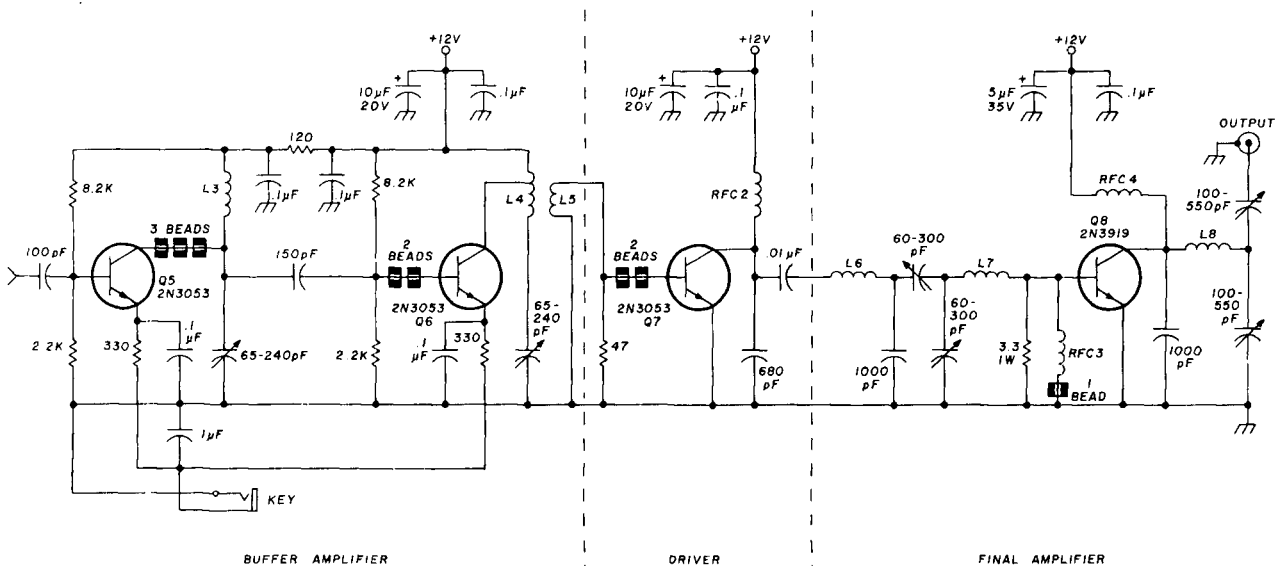


fig. 3. Buffer amplifier, driver, and final amplifier schematic. Note the use of toroid coils for resonant circuits and liberal use of ferrite beads for decoupling.

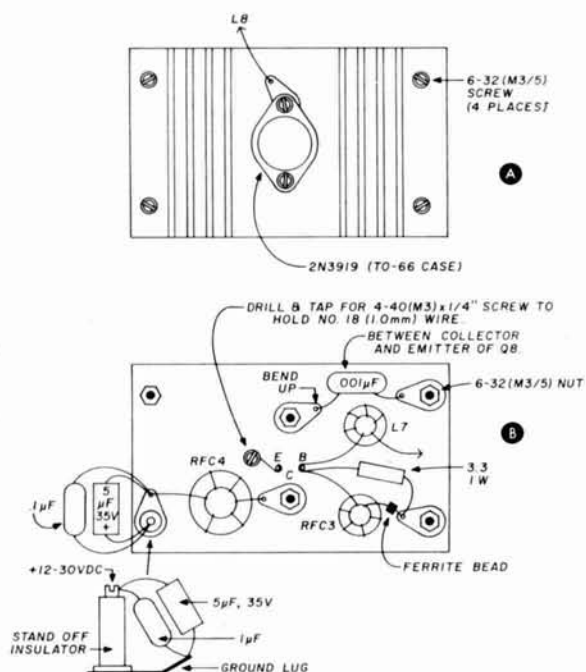



fig. 4. Construction details for the final amplifier. Sketch A shows mounting of the 2N3919 in its heatsink; B shows under-chassis wiring and parts location.

bypassing and rf chokes are important. This stage is built on a heavy aluminum heatsink, so the transistor barely gets warm while dissipating nearly 30 watts. It's hard to find a low-cost transistor on today's market to beat this one (Fairchild 2N3919 or Poly Paks 92CU1234). One word of caution: when testing you *must* use a 50-ohm dummy load. Adequate drive must be provided to this stage before it will function. References 3 and 4 are suggested for further reading.

construction

As mentioned earlier, the transmitter is built on five perf boards. Prepunched boards may be obtained from

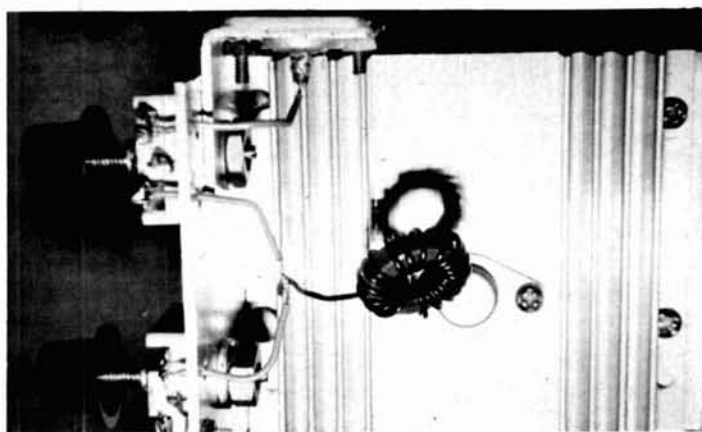Close-up view of the final amplifier. L8 is shown wound on the toroid.



such as Vector T-28 or flea clips (Lafayette Radio 198302) work well on this board. Arrange the parts on the board for a symmetrical layout, bearing in mind the necessity for short rf leads and adequate bypassing. Avoid crowding and try to keep dc voltage wiring isolated physically from circuits carrying rf voltages. Install a wire around the board periphery to serve as a ground plane for connecting all circuits to be grounded; this will avoid ground loops and feedback problems. The nice thing about perf-board construction is that you can rearrange parts until you're satisfied with the layout without touching a soldering iron.

table 1. Construction data for the inductors used in the QRP transmitter.

RFC 1	1 mH (not critical)
RFC 2	60 or 70 turns no. 28 (0.3mm) enamelled wire on T50-2 toroid core (Amidon). Fill core with wire.
RFC 3	25 turns no. 28 (0.3mm) enamelled wire on T50-2 toroid core (Amidon)
RFC 4	75 turns no. 28 (0.3mm) enamelled wire on T68-2 toroid core (Amidon)
L0	40 turns no. 26 (0.4mm) enamelled wire close wound on 1/2 in. (12.5mm) O.D. slug-tuned coil form
L1	27 turns no. 28 (0.3mm) enamelled wire on T50-2 toroid core (Amidon), tapped 7 turns from plus end of coil
L2	3 turns no. 22 (0.6mm) enamelled wire over L1
L3	21 turns no. 28 (0.3mm) enamelled wire on T50-2 toroid core (Amidon)
L4	27 turns no. 28 (0.3mm) enamelled wire on T50-2 toroid form (Amidon), tapped 7 turns from plus end of coil
L5	3 turns no. 22 (0.6mm) enamelled wire over L4
L6	14 turns no. 22 (0.6mm) enamelled wire on T50-2 toroid core (Amidon)
L7	14 turns no. 22 (0.6mm) enamelled wire on T50-2 toroid core (Amidon)
L8	17 turns no. 22 (0.6mm) or no. 18 (1.0mm) enamelled wire on T68-2 toroid core (Amidon)

Plastic transistor sockets are used for all devices except the final-amplifier transistor, which is packaged in a TO-66 case and mounted directly on a heavy heatsink. Coil data is provided in table 1. Fig. 4 shows parts layout for the final-amplifier stage. Note that this stage is built on a separate chassis, which includes the heatsink for the 2N3919 (fig. 5). The sketches in fig. 5 also provide overall dimensions for the frame that contains the five chassis.

test equipment

A few essential instruments will be needed for testing and making measurements. A vtvm with an rf probe capable of measuring up to 25-30 volts will be needed. The Heath Company stocks one that is a good buy, or if you want to build one a description appears in reference 5. Another useful item is the absorption frequency meter, also described in reference 5. A grid-dip meter is needed to determine resonant frequencies of toroid coils

and LC circuits. To save headaches later on, all toroid LC circuits should be tested before wiring them into the stages to ensure they are resonant and cover the proper frequencies.

A dummy load capable of handling about 8 watts is needed. It can be made by paralleling four 200-ohm, 2-watt resistors or some other combination of resistors

can in one or two more steps obtain an input of 25-30 volts at 700-850 or more mA. Thus at 30 volts at 850 mA you are putting 25.5 watts into the final transistor and will obtain 8 or more watts output. You can calculate your output power from E^2/R by measuring the rf voltage across the 50-ohm dummy load — pretty good performance for a few inexpensive transistors.

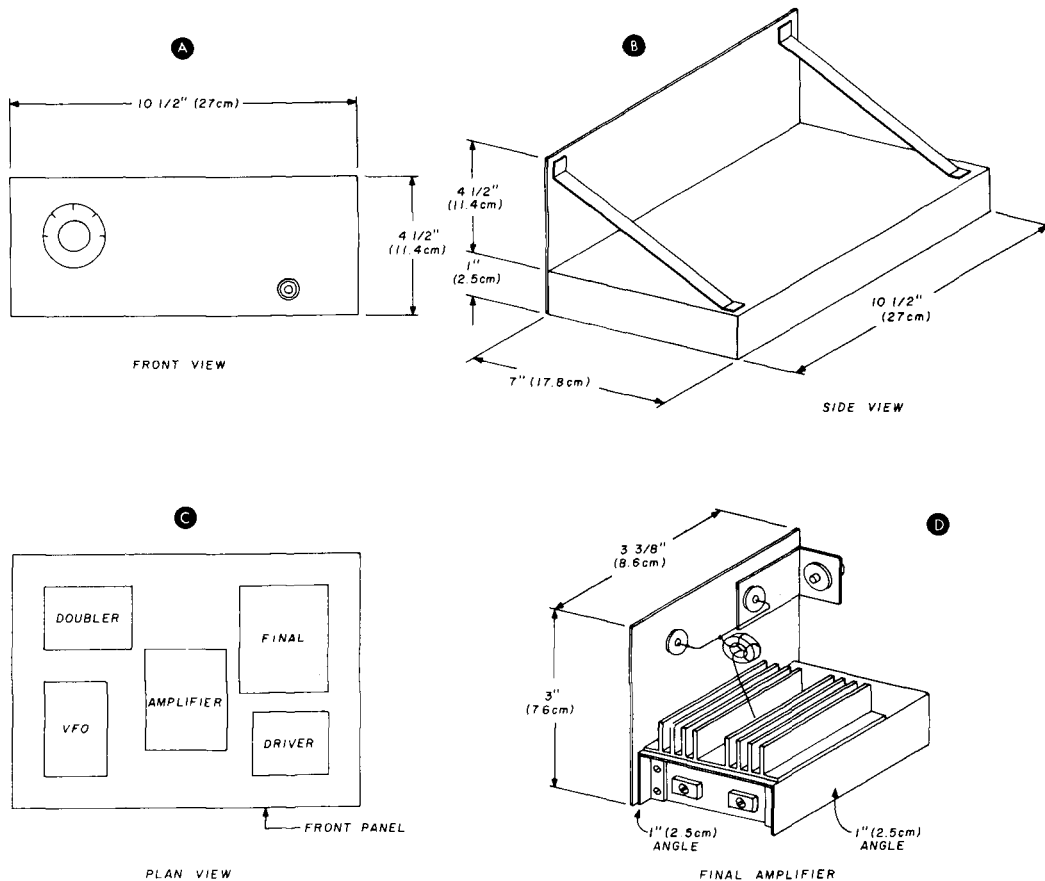


fig. 5. Dimensions and layout of the QRP transmitter. Sketches A through C show details of the main chassis; D shows the final amplifier arrangement.

to give 50 ohms and a power capacity of 8 watts or more.

When you complete construction of a stage, it should be tested with respect to the preceding stage. When you reach the last stage, be sure it has adequate rf drive. Connect the 8-watt dummy load to the SO239 output connector. You are now ready to test the completed transmitter.

Starting with 12 volts on the final-amplifier transistor, key the transmitter and tune all stages for maximum rf output using the vtm probe. Two precautions: be sure your rf probe will handle 30 volts and *don't* test without dummy load. It's best to peak the final amplifier stage first, work back to the vfo, then repeak the final stage. Now you can release the key and advance the final-amplifier voltage to 20 volts. Key the transmitter and peak the four capacitors in the final. By working incrementally and peaking the final stage each time, you


When you connect the transmitter to the antenna, all you'll have to do is peak the capacitors in the final pi network for a maximum output. A tuning indicator is required here, such as an swr indicator. If there is a high swr, better antenna efficiency will be obtained with an antenna tuner.

references

1. Wes Hayward, W7ZOI, "A Second-Generation Mosfet Receiver," *QST*, December, 1970, page 17.
2. R.M. Mendelson, W2OKO, "A Power Supply for Transistor Circuits," *Ham Tips*, Vol. 27 No. 1, June, 1967, RCA Electronic Components and Devices Division.
3. "Matching Network Design and Computer Solutions," *Motorola Application Note AN267*.
4. Wes Hayward, W7ZOI, "Increased Power for Solid-State Transmitters," *QST*, May, 1972, page 19.
5. "Rf Probe for Electronic Voltmeters," *The Radio Amateur's Handbook*, ARRL, 1975, pages 535-536.

ham radio

VHF DX


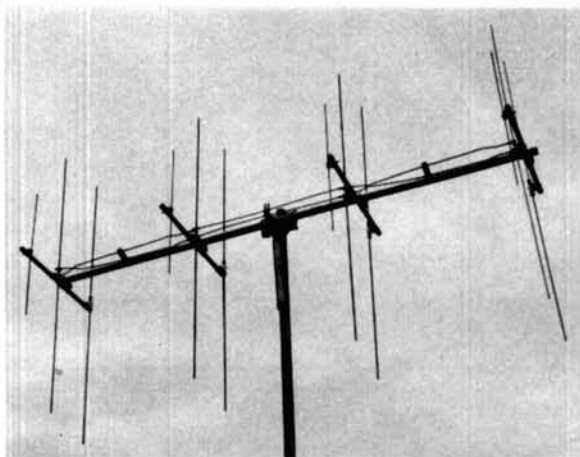


FM —

Enjoy the thrill of dependable long distance contacts on simplex or thru remote repeaters. The 20 element co-linear DX-Array offers a precise pattern with large capture area. This vertically polarized, horizontally stacked array provides a narrow beamwidth for the discriminating FM user. Wide impedance and gain bandwidths make the DX-Array a natural choice for the serious FM'er. A vertical polarization bracket, model DX-VPB, is required (support boom and mast not supplied). Seek out new horizons with DX-Array!

SSB/CW —

Discover reliability in long-haul communications with VHF SSB and CW. The Cush Craft DX-Array also gives low angle, high gain performance for many exotic propagation modes — tropo, aurora, sporadic-E, and meteor scatter. Horizontally polarized DX-Arrays may be used singly or combined in pairs (twice Effective Radiated Power) or quads (4 x ERP). Each DXK stacking kit is complete with stacking frame and phasing harness (vertical mast not supplied). This year has seen some spectacular VHF band openings — Don't miss the next one!

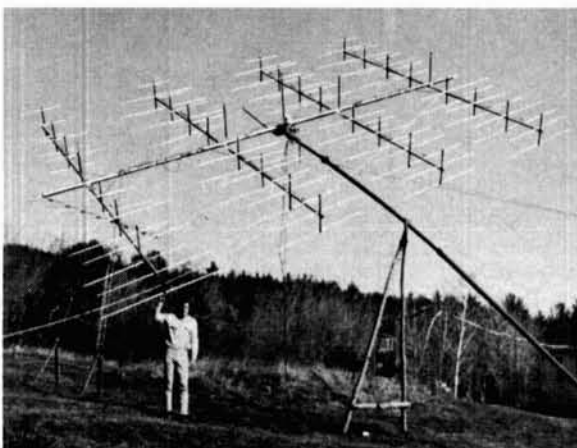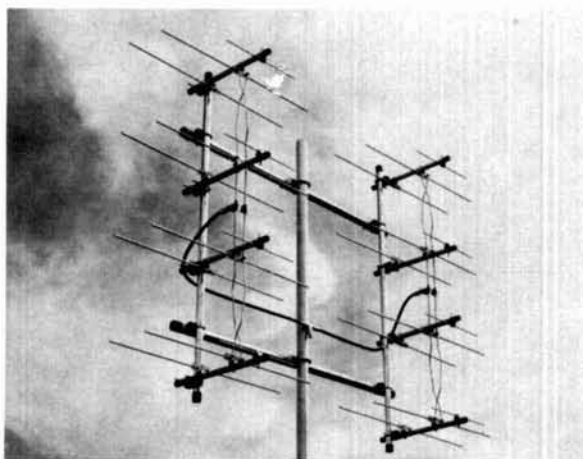

Dave Olean, K1WHS, with his 160 Element DX-Array and Polar Mount EME System

EME —

Many VHF experimenters have found excitement in conquering the formidable Earth-Moon-Earth (EME) path. 2-meter moonbouncers have achieved outstanding success using eight stacked DX-Arrays. Impedance and gain characteristics of this antenna permit stacking without the critical detuning problems inherent in large arrays of Yagis. Enlarging system size will yield a more uniform gain increase with DX-Arrays than with many other large antennas. The physical configuration alleviates mounting and phasing/tuning problems. EME enthusiasts are setting new records — So can you!


DX-ARRAY LEADS THE WAY!

Description:	144 MHz.		220 MHz.		432 MHz.	
	Model:	Price:	Model:	Price:	Model:	Price:
20 Element DX-Array	DX-120	\$39.50	DX-220	\$32.50	DX-420	\$29.50
Frame & Harness (40 E.)	DXK-140	\$52.50	DXK-240	\$49.50	DXK-440	\$36.50
Frame & Harness (80 El.)	DXK-180	\$100.00	DXK-280	\$85.00	DXK-480	\$70.00
1-1 52-ohm Balun	DX-1BN	\$10.95	DX-2BN	\$10.95	DX-4BN	\$10.95
Vert. Pol. Bracket (20 El.)	DX-VPB	\$8.95	DX-VPB	\$8.95	DX-VPB	\$8.95

IN STOCK WITH
DISTRIBUTORS WORLDWIDE



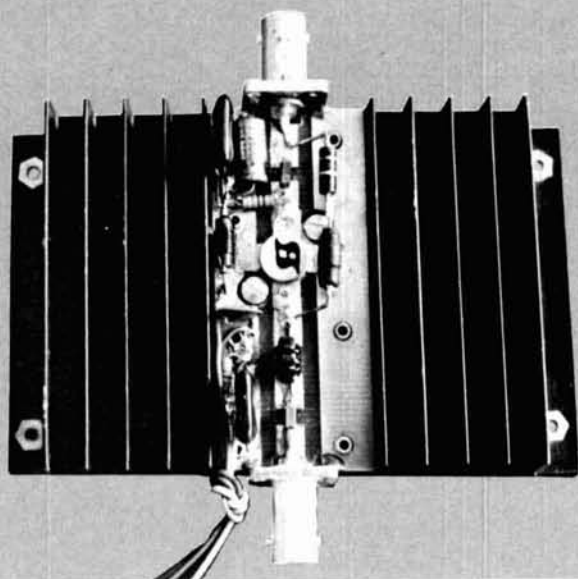cushcraft
CORPORATION
P. O. BOX 4680, MANCHESTER, N. H. 03108



mospower fet as a broadband amplifier

A new type of
power transistor provides
linear performance
over three vhf bands
without switching

The *Mospower* fet introduced by Siliconix* in late spring, 1976, is undoubtedly the most revolutionary semiconductor in decades and one that will open up exciting new applications heretofore impossible with bipolar transistors. Switching of 1-ampere in less than 4 nanoseconds is commonly accomplished with this new power mosfet. Among the many new features is one in particular that will interest those who seek wide dynamic range: a linear transfer characteristic! Imagine too a transistor that can double for either a linear power amplifier or a wide dynamic range, low noise, small-signal, front-end transistor!

Other features of the *Mospower* device are typical for field-effect transistors and would be especially desirable for bipolar transistors. As with all fets, there is no

thermal runaway nor secondary breakdown, and no minority-carrier storage time. The latter opens up interesting applications for class-D (switching) amplifiers. Additionally, the *Mospower* fet can accept any vswr — open or short — at any phase angle without debilitating effects. This enhancement mode, N-channel, mosfet can be operated in any class (A, AB, B, or C) without requiring a bias supply.

Unlike the usual mosfet, which is *planar* in construction, the *Mospower* fet is a four-layered vertical structure shown in **fig. 1**. This drawing compares, somewhat oversimplified, the fundamental differences between MOS, DMOS and VMOS — which is the generic name for the *Mospower* structure. Common to both MOS and DMOS (but not VMOS) is the singular disadvantage which affects their power handling capabilities: the geometry requires massive area to handle the necessary current. A further disadvantage of MOS and DMOS lies in their inability to accept high voltages. In the *Mospower* fet the current travels vertically, the source being on top while the drain is the bottom of the chip. In this vertical structure there are four layers whose dimensions are controlled by diffusion processes rather than by the less precise photolithographic methods common to planar (MOS) technology.

VMOS construction offers high current densities, high source-to-drain breakdown capability, and low gate-to-drain feedback capacitance, which makes the *Mospower* fet a great device for hf and vhf applications. Probably the most attractive aspect of this revolutionary semiconductor is its inherent linear transfer characteristic. In conventional mosfet (and jfet) devices this transfer characteristic is closely identifiable to a square-law

By Ed Oxner, Siliconix, Inc., 2201 Laurelwood Road, Santa Clara, California 95054

*Mospower is a trademark of Siliconix, Incorporated.

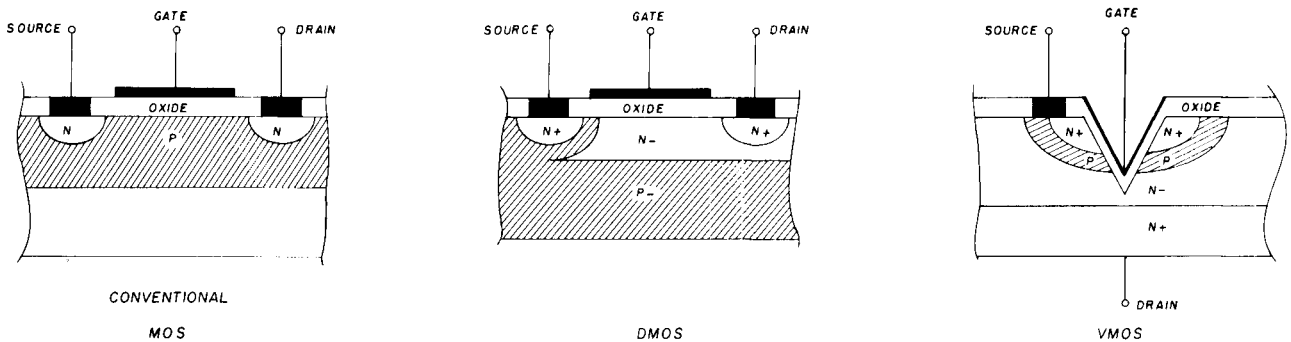


fig. 1. Fundamental differences in enhancement-mode MOS structures.

response; that is, the drain current is proportional to the square of the gate-to-source voltage. However, in the VMOS structure the short channel causes the drain current to be linearly proportional to the gate-to-source voltage. Fig. 2 is a transfer characteristic which shows this effect.


mospower vhf fet

The Siliconix VMP4 is packaged in the popular flange-mount, "opposing-emitter" (in this case, opposing-source) stripline configuration. This transistor is capable of saturated output power approaching 20 watts at 160 MHz. The performance shown in fig. 3 represents the available *saturatc.* output power versus frequency when both the input and output impedances of the VMP4 are conjugately matched (but *not* in the circuit described in this article). The input and output impedances (in the common-source configuration) are particularly well-suited for wideband amplifier service with *complete stability*. Unlike bipolar power semi-conductors these impedances are affected very little by drive levels.

the circuit

Simplicity is an understatement for the wideband

fig. 2. Transfer characteristic of the VMOS structure.

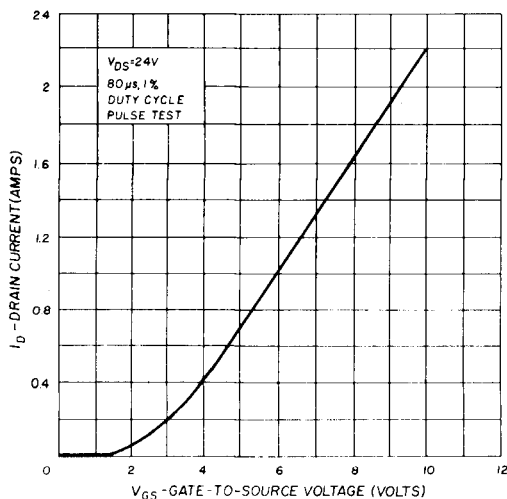

power amplifier shown schematically in fig. 4 and in the photo of the finished amplifier. Unlike many claims for broadband performance, this amplifier, by virtue of a negative feedback circuit, performs with flat gain response (± 0.5 dB) over its entire operational bandwidth.

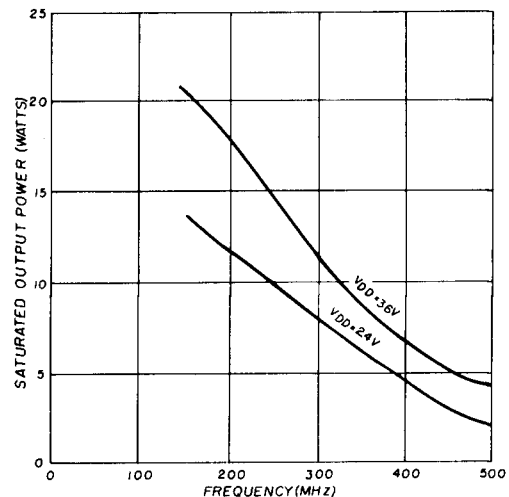


fig. 3. Showing the output power (saturated) versus frequency of the Siliconix VMP4. This assumes that the input and output impedances are matched. Drive power is 1 watt, drain current is 0.8 amp.

Two interesting features are immediately apparent in the circuit diagrams: first, the simple 4:1 transformer for broadband input matching and, second, effectively no matching circuit at the output. My philosophy is, "Why use parts if they're really not necessary?" The drain circuit needs no further complication. Some readers may question the wisdom of such an over-simplistic design, especially in light of the familiar equation

$$R_o = \frac{(V_{cc} - V_{sat})^2}{2P} \quad (1)$$

where R_o = output impedance, V_{cc} = drain supply voltage, V_{sat} = saturated drain-to-source voltage, and P = output power.

However, using this formula and making a few first-order assumptions, we can arrive at some near 50-ohm values

for the drain load impedance; for example

$$R_o = \frac{(25 - 3)^2}{2 \times 4} = 60.5 \text{ ohms}$$

To reach the lowest operational frequency requires a ferrite core with reasonably high permeability, but in this design 6 meters was my low-end goal and the 220-MHz band uppermost, so an operational bandwidth extending from 40 to 265 MHz was chosen. Only one circuit trick was required to reach the upper frequency objective and in reality it wasn't so much a circuit trick as a careful selection of component. I do not recommend the use of a commercially available molded 0.15 μH feedback inductor — manufactured inductors appear to exhibit too much distributed capacitance for this application. I used 6 to 8 turns of no. 30 AWG (0.25mm) enameled wire on a $\frac{1}{2}$ -watt, 1-megohm resistor. If you have an inductance bridge you can wind the choke to 0.15 μH , otherwise you may need to experiment. Using a commercially molded choke will severely reduce the upper-frequency limit.

About the only difficult aspect in building this circuit is preparing the double copper-clad board to accept the flange-mounted stripline transistor. Careful layout and cutting is required. As with any rf layout be sure to connect both copper foils (top and bottom) together, either with small eyelets or what-have-you. Additionally, remember that the *Mospower* fet is MOS and has an unprotected gate, so don't handle it without first being absolutely sure that you are not carrying a static charge. Stay off rugs and out of crepe-sole shoes until you've got the transistor soldered into your circuit. Once in the circuit you're free to do anything you want to with your amplifier.

Since this transistor operates with healthy currents it is absolutely necessary to mount the flange to a suitable heatsink. The large one shown in the photo is an over-design but it does emphasize that a heatsink is necessary. As is typical with any heatsink, you should use a suitable silicon grease or thermal compound between the flange and the sink.

A second precaution common to any high-current load is to avoid current-carrying molded chokes that may vaporize when the power is applied. I have found, quite by accident, that generally speaking, values of inductance *less than* 0.22 μH will hold up with currents of 1.5 amp or less. Further proof of reliability in regard to this construction is that I have built four identical amplifiers and all performed equally well.

An interesting aspect of this wideband amplifier is that performance does not seem dependent upon whether you use it for a small-signal amplifier, say in the microwatt area of a front-end receiver design, or for medium power (1 to 2 watts) amplification, possibly to excite a linear final amplifier.

Of special interest to those advocates of wideband amplifiers will be the observation that in a *Mospower* fet amplifier the wideband noise is literally unmeasurably low! For an example, this VMP4 (and any other VMP device) offers excellent small-signal noise figures. A typical value of 2.4 dB at 146 MHz is easy to achieve

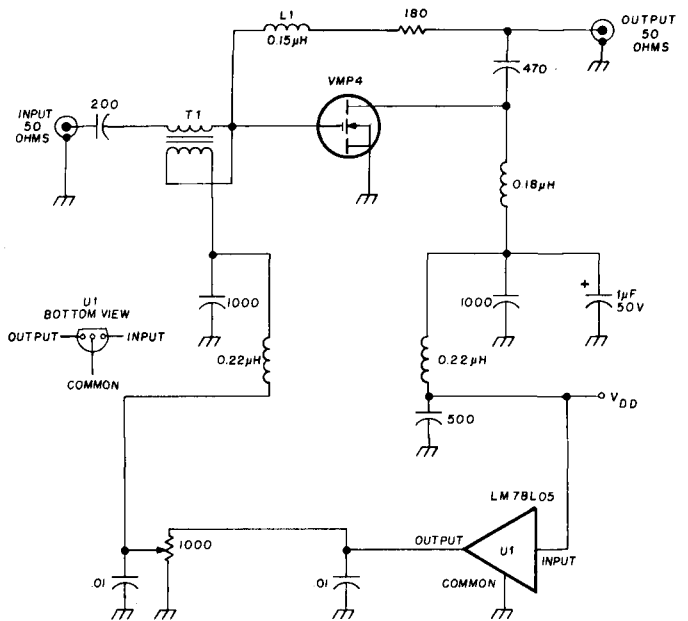


fig. 4. Simplicity is the keynote in this broadband amplifier. L1 should not be a molded choke; see text for winding information. T1 is 4 turns no. 22 AWG (0.6mm) twisted pair on an Indiana General F625-9Q2 toroid core.

with a properly matched input circuit. However, it should be pointed out that this particular circuit using the 4:1 matching transformer is *not* properly matched for optimum small-signal noise figure; that was *not* the objective in the first place. Bandwidth for two power levels is shown in fig. 5. With 1-dB compression occurring at an input level of +23 dBm, the +27 dBm input level is understandable under compression, hence the lower gain figure.

Two-tone, third-order intermodulation performance at both the 100-mW and the 1-watt output levels is displayed in fig. 6 as intercept point (IP). This point was calculated with reference to a single-tone output, using the formula

$$IP (dB) = P_{out} (dB) + \frac{P_{imd} (dB)}{2} \quad (2)$$

When calculating the intercept point, or when comparing specifications between devices, care must be

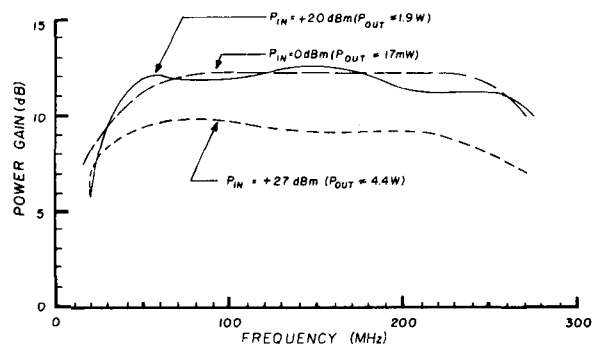


fig. 5. Power gain versus frequency curves at different levels of drive. The +27 dBm curve is above the compression point, therefore the gain is lower.

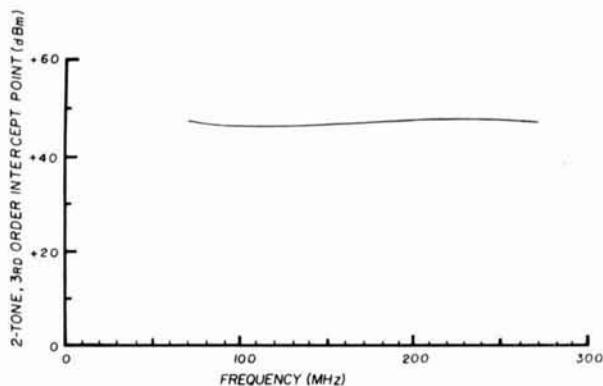


fig. 6. Two-tone, third-order intercept point for the Siliconix VMP4 power fet. V_{dd} is 26V, I_d is 0.4A. Intercept point was referenced to a single tone. Power levels were 100 mW and 1 watt.

taken to know how the numbers were obtained. Some manufacturers may use the PEP output as a reference; others may use average power. A more conservative rating may be obtained by using the single-tone output as a reference, as in fig. 7.

Another interesting feature of the VMP4 *Mospower* fet is that it is not sensitive to load mismatch; there is no need to panic if you disconnect the output cable during testing or tuning. Should a slip occur during a tweaking session, sparks may fly from the metal tool, but when things have calmed down again, the fet will still be ready for action. *Mospower* fets appear to have three funda-

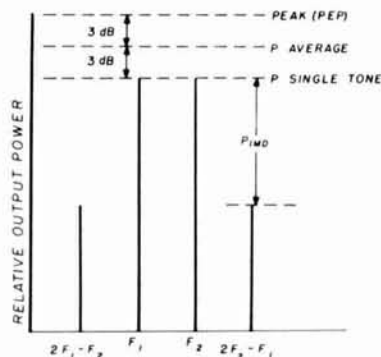


fig. 7. Three common methods of rating IMD performance. The most conservative uses a single-tone output as a reference.

mental advantages; very easy to match; extremely rugged; and can be operated in parallel without complications.*

The VMP1 is available for \$7.85 each; the VMP4 is priced at \$20 each (plus postage and handling charge). California residents please add 6% sales tax. For complete ordering information, write to Ed Oxner, Siliconix, Incorporated, 2201 Laurelwood Road, Santa Clara, California 95054.

ham radio

*Circuits for using *Mospower* fets (VMP1) in single and parallel configurations were given in the September, 1976, issue of *ham radio*, page 10.

State
of the art



by
K.V.G.

CRYSTAL FILTERS and DISCRIMINATORS

9.0 MHz FILTERS

XF9-A	2.5 kHz	SSB TX	\$31.95
XF9-B	2.4 kHz	SSB RX	\$45.45
XF9-C	3.75 kHz	AM	\$48.95
XF9-D	5.0 kHz	AM	\$48.95
XF9-E	12.0 kHz	NBFM	\$48.95
XF9-M	0.5 kHz	CW	\$34.25
XF9-NB	0.5 kHz	CW	\$63.95

9.0 MHz CRYSTALS (Hc25/u)

XF900	9000.0 kHz	Carrier	\$3.80
XF901	8998.5 kHz	USB	\$3.80
XF902	9001.5 kHz	LSB	\$3.80
XF903	8999.0 kHz	BFO	\$3.80
F-05	Hc25/u Socket		.50

9.0 MHz DISCRIMINATORS

XD9-01	± 5 kHz	RTTY	\$24.10
XD9-02	± 10 kHz	NBFM	\$24.10
XD9-03	± 12 kHz	NBFM	\$24.10

Export
Inquiries
Invited

Shipping
\$1.25
per filter

144 MHz SSB TRANSVERTER, MM144

Use your HF Transceiver on the 144 MHz band with the addition of the MM144 linear Transverter. The MM144 operates on all modes; SSB, CW, AM, FM. It contains BOTH the linear transmit up-converter and the receive down-converter. An internal PIN diode T/R connects to your Transceiver T/R line. The MM144 is FT101 and similar rig compatible. Add the J-Beam 8XY/2M crossed Yagi's and operate horizontal, vertical or circular polarization into the OSCAR satellite. (8XY/2M \$39.95) Write for free application note.

Specifications:

Output Power	10 W peak
Drive, 10 meters	1/2 W max
Receiver N.F.	3.0dB max
Receiver gain	30 dB typ
Bandwidth	4 MHz
Prime Power	12 V D.C.

Price: \$199.95
Shipping: \$3.50



50 MHz FREQUENCY METER MMd 050 500 MHz DECADE PRE-SCALER MMd 500P



MMd 050



MMd 500P

Measure frequencies to 50 MHz
6 digit digital display
High sensitivity 50 mV RMS
Internal crystal reference
Price: \$164.95

Extend your freq. meter to 500 MHz
Sensitivity 200 mV RMS
Input impedance 50
Output TTL compatible
Price: \$74.95

Power 12 V D.C. Size 4 1/2" x 2 1/2" x 1 1/4"
Send for free data sheet. Shipping \$2.50 each

Send 26¢ (2 stamps) for full line catalogue of KVG crystal products and all your VHF & UHF equipment requirements.

Pre-Selector Filters Pre-Amplifiers Converters
Varactor Triplers Transverters Antennas
Decade Pre-Scalers Digital Counters Crystals

NEWS ITEM: All Microwave Modules, J-Beam prices reduced, due to the low exchange of the Pound!

si

Spectrum
International, Inc.
Post Office Box 1084
Concord, Mass. 01742, USA

FAIRCHILD

ANNOUNCES THE

FAIRCHILD


SOLID STATE TECHNOLOGY KIT

- FOR THE EXPERIMENTER WITH TASTE FOR "STATE OF THE ART" PRODUCTS
- COMPLETE SPECIFICATIONS ARE PRINTED ON THE BACK OF EACH TECHNOLOGY KIT

FTK0020

FTK0020

FTK0106

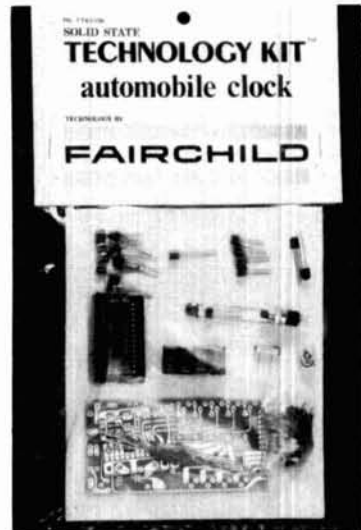

CARD FRONT

CARD BACK

CARD FRONT

DIGITS

FTK0001	0.5" High Common Cathode Digit	\$1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	.357" High Common Cathode Digit	.75
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

0.8" HIGH DISPLAY ARRAYS

FTK0010	12 Hour, 3 1/2 Digit Clock Display	7.00
FTK0011	24 Hour, 4 Digit Clock Display	8.00

LED LAMPS

FTK0020	10 Red LED Lamps	1.00
FTK0021	5 Mixed Colored LED Lamps	1.00
FTK0022	10 LED Mounting Clips	1.00
FTK0023	5 Three Piece LED Mounting Adapters	1.00

PHOTO TRANSISTORS

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

PHOTO ARRAYS

FTK0040	9-Element Tape Reader Array	16.00
FTK0041	12-Element Card Reader Array	24.00
FTK0042	Reflective Opto Coupler	4.00

COUPLERS

FTK0050	3 General Purpose Opto Couplers	1.00
FTK0051	Darlington Opto Coupler	1.00

MOS CLOCK CIRCUITS

FTK0400	Digital Clock/Calendar Circuit (FCM7001)	7.00
FTK0401	Digital Clock/Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with DC Output (FCM3817D)	5.00
FTK0405	Direct Drive Digital Clock/Calendar Circuit (FCM7015)	6.00

KITS

FTK0106	Automobile Clock Kit	40.00
---------	----------------------	-------

- THESE PRODUCTS ARE PACKAGED FOR OUTSTANDING WALL DISPLAY APPEARANCE

• FULL **FAIRCHILD** PRODUCT LINE TO FOLLOW


Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.
 California Residents — Add 6% Sales Tax
 Send a 24¢ Stamp (postage) for a Free 1977 Catalog

NOW OPEN SATURDAYS

JAMES

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
 PHONE ORDERS WELCOME — (415) 592-8097

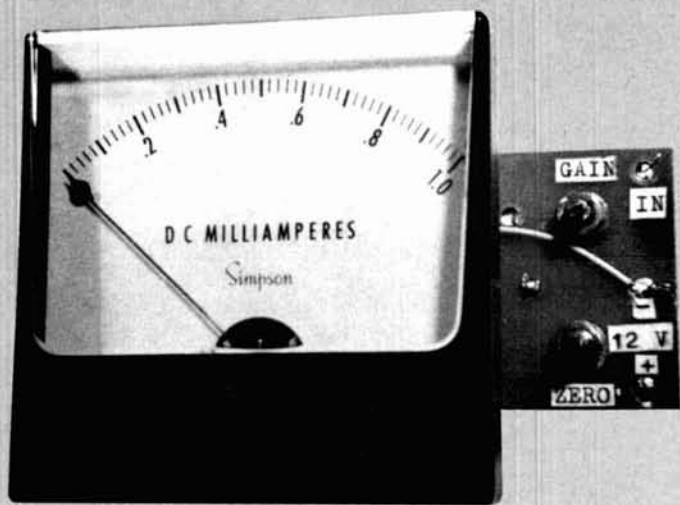- DEALER'S AND WHOLE-SALER'S INQUIRIES INVITED — PRICE LIST AVAILABLE.
- BUY WITH PRIDE THE PRODUCTS BUILT BY THE INDUSTRY'S LEADER — **FAIRCHILD**



electronic meter amplifier

Junction fet
in simple circuit
turns dc milliammeter
into dc microammeter

My ham radio budget was seriously threatened recently when circumstances called for use of a 0-100 μ A microammeter. Reference to the radio wholesale catalog immediately discouraged the purchase of a new meter. However, a 0-1 mA milliammeter recently acquired at a reasonable price was available from the parts cabinet. The question was, could a 0-1 mA meter, with the aid of a dc amplifier, substitute for a 0-100 μ A microammeter?

The following description answers the question in the affirmative.

circuit description

A Motorola MPF102 junction fet is used as the active element of a dc amplifier, as illustrated in **fig. 1**. There are many other types of fets that can be used, including mosfets, depending upon what is available in the junk box. The MPF102 is inexpensive and can provide current gains of over 50 dB in this meter bridge circuit. The maximum full-scale sensitivity of the circuit is approximately 2.0 microamperes. For example, two volts fed to the circuit through a 500k source impedance provides a full-scale meter reading. The 500k gain control is used to set the circuit sensitivity to the desired value.

Parts for the meter amplifier are assembled on a piece of 3/32-inch (2.5mm) thick epoxy fiberglass board. The assembly is attached directly to the rear of the meter by the two meter terminals. I used 1/4-inch (6.5mm) brass eyelets equipped with solder lugs and spaced to match the meter terminals. All other terminals are 1/8-inch (13mm) brass eyelets, mounted in 1/8-inch (13mm) holes drilled in the fiberglass board and rolled over with the aid of a center punch and a hammer. Location of the

By Norman J. Foot, WA9HUV, 293 East Madison Avenue, Elmhurst, Illinois 60126

holes is not critical, but the general layout shown in the photographs can be followed.

Allen-Bradley type-G potentiometers are used for gain and zero-set purposes, primarily because they were available, but standard size potentiometers can be used just as well. The potentiometers are mounted on the right-hand side of the board for accessibility. After the meter and amplifier assembly have been mounted behind a panel, adjustments are made through screwdriver access holes.

adjustment

Adjustment of the meter amplifier is relatively simple. First, with no signal at the input, adjust the


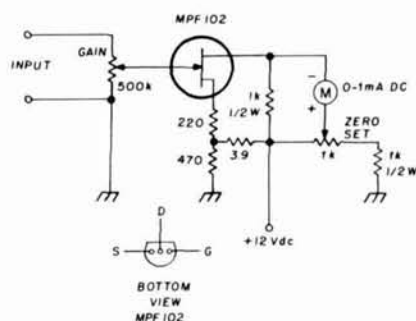
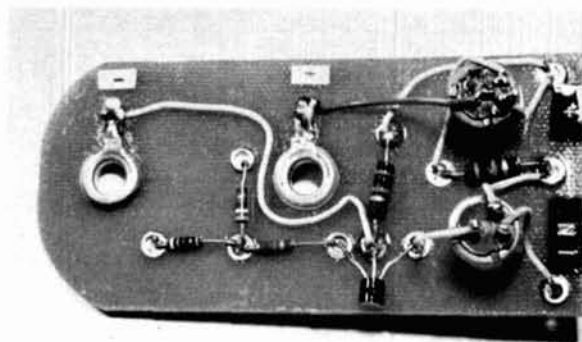


fig. 1. Schematic diagram of the meter amplifier circuit. All resistors are 1/4 watt unless otherwise noted.

zero-set control for zero meter current; then connect the signal to the input and adjust the gain to the desired value. If the source includes a dc offset voltage, it is possible to compensate by properly offsetting the zero-set control.

At my station, the dc meter amplifier is used in conjunction with an rf detector attached to the forward-coupled arm of a 20 dB directional coupler. Since the detector operates in its linear region, the 0-1 mA meter reading is approximately proportional to the

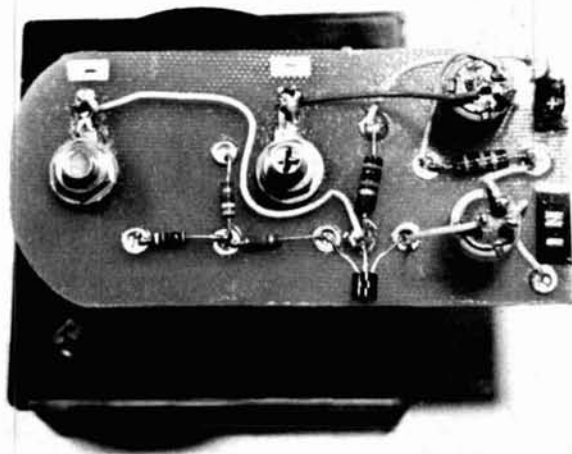B. Finished circuit board shown mounted to back of meter, held in place by the meter terminals. Neat, simple.



C. Circuit board uses eyelets for component-mounting and convenient tie-points for wiring. Large eyelets are for meter terminals.

current flowing in the main line of the coupler (except at the bottom end of the scale). The meter was calibrated by comparing its reading with an rf power meter borrowed for the purpose. The power meter was connected to the output end of the directional coupler, as shown in fig. 2.

Once the scale is calibrated there is no further need for the wattmeter, and antenna power may be read directly from the meter scale with the aid of a calibration chart. In the example given in fig. 2, the full-scale power reading is 1.0 watt. Higher power levels can be monitored with the same setup by using directional

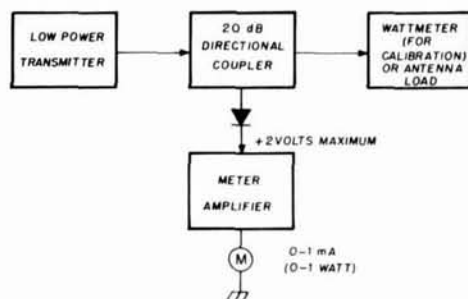


fig. 2. Block diagram showing application of the dc meter amplifier as a sensitive rf wattmeter. In this case 0-1 mA meter reads out 0-1 watt with 20 dB directional coupler (see text).

couplers having higher coupling values. For example, the full-scale power reading would be 100 watts if a 40 dB directional coupler were used.

The dc meter amplifier can also be used as a high impedance dc voltmeter, with a range of 0-1 volt, for example. If the meter amplifier is connected to the avc line in a receiver, it can serve as an S-meter.

references

1. Norman J. Foot, WA9HUV, "Fet Tone Keyer," *QST*, October, 1969, page 103.
2. *Motorola Semiconductor Handbook*, 5th edition, Motorola Semiconductor Corporation, Phoenix, Arizona, page 7-465.

ham radio

ALPHA POWER

IS IN ~~THREE~~ **FOUR** CLASSES BY ITSELF

WITH THE ADDITION OF ... VOMAX



ALPHA 77D IS 'THE ULTIMATE'

- Runs cold and whisper-quiet at maximum legal power, any mode, with No Time Limit [NTL] and lots of reserve.
- Tunes 10-160 meters (3-30 MHz continuous).
- Full vacuum relay QSK (CW break-in) standard.
- Basic design...

ALPHA 374 IS SUPER CONVENIENT

- The smallest and lightest of all true [NTL] kilowatts at only 0.9 cubic ft. and 52 pounds.
- No-tune-up operation 10-80 meters, thanks to factory-pretuned bandpass filters, yet built-in manual...

ALPHA 76 SETS THE VALUE STANDARD

- An honest, rock-crusher [NTL] kilowatt in all modes, like the ALPHA 374. You can lock the...

"VOMAX" IS FOR EVERYONE WHO USES SSB, FM, AM - HF, VHF, UHF - AMATEUR, COMMERCIAL, OR CB. Your signal can now have that distinctively clean and penetrating audio characteristic that heretofore was achievable only by carefully integrating a custom rf clipper right into the exciter rf circuitry. After years of investigation, ETO's specialists in big clean signals have finally found - in VOMAX - a speech processor of such excellence as to deserve the ALPHA name. This new "split band" processor is equivalent in performance to the best rf clippers, yet it works on virtually any transmitter and is extremely easy to install and use. VOMAX plugs into the mike line, requires almost no operator attention, and can boost "talk power" as much as a 10 dB power increase under marginal conditions! If you're already using an ALPHA linear, VOMAX is one of a very few legitimate ways [other than a much bigger antenna!] to further improve your signal. Operating "barefoot" or mobile? Then you need VOMAX even more. Either way, VOMAX is probably the least expensive major improvement you can make in your signal. ETO warrants every VOMAX for a full year against defects, and offers a 10 day money-back guarantee of satisfaction. Like a famous ALPHA linear, VOMAX delivers capability you just can't get elsewhere... it's in a class by itself. VOMAX [12 VDC], \$179.50; AC adapter, \$10; shipping in USA, \$2; ALPHA 76, \$985; ALPHA 76P, \$1095; ALPHA 374, \$1395; ALPHA 77D, \$2995. Contact ETO for detailed literature, personal consultation, and prompt delivery of all models. (U.S.; factory stock.

... modern, rugged ceramic grounded-grid features that's available in no other true... silver-plated copper tubing... full-cabinet, ducted air cooling; • self-contained desk-top service is conveniently available in the Midwest and in Southern California. Write or phone ETO direct for full information, illustrated brochure, and personal service.

ETO

EHRHORN TECHNOLOGICAL OPERATIONS, INC.
BROOKSVILLE, FLORIDA 33512 (904) 796-1428



ASCII-to-Morse code translator

Sit back and type
near-perfect Morse
with this interface
between keyboard
and transmitter

I suppose every amateur at one time or another has wanted an easy way to send perfect code. The bug, and later the electronic keyer, have to a large degree solved the problem of sending good code. The ultimate way, however, would be to bang out the letters on a typewriter keyboard at any speed while the code is being sent out at some preselected speed. Not only is this nice and easy for you, but the fellow on the other end


probably wouldn't complain when he hears your good code. This idea certainly isn't new, but if you've checked lately you know that a commercially produced unit with memory costs about \$400, and that's just about out of everyone's price range. This project may just change all that since its unit with memory and keyboard should cost about \$120.

code conversion

The initial problem is changing the ASCII code to Morse, but that by no means is the end because Morse characters vary in length from 1 to 6 bits. Since programmable read-only memories (ROMs) are readily available, they're used in this circuit to convert the 6-bit ASCII keyboard output to a special code that includes the Morse letter and its bit length in binary code. The actual code in the memories is not terribly important and is not discussed as most amateurs have no easy way of programming the memories.

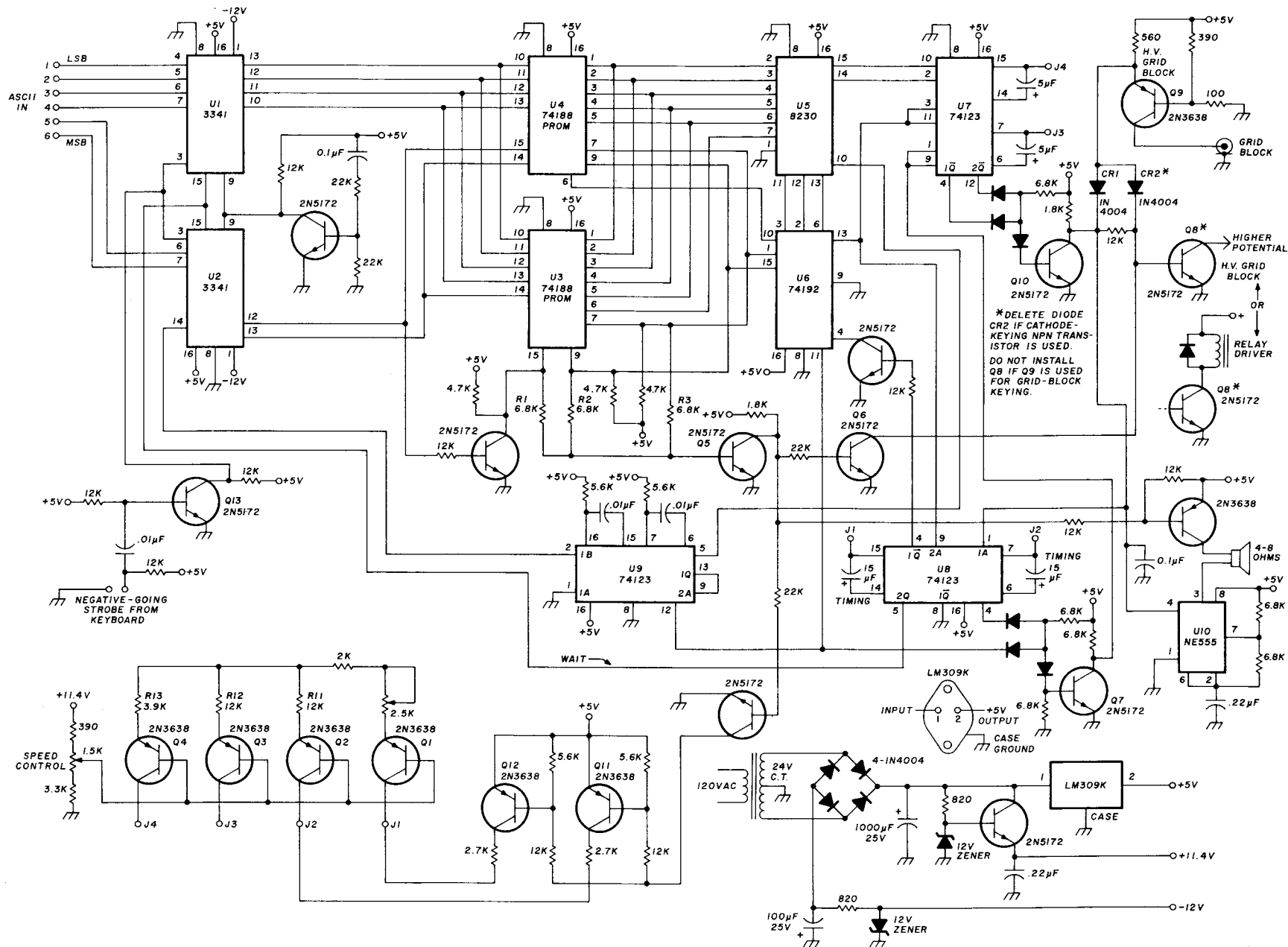Example: The letter R appears at the outputs of the PROMs as (110)00010, where the binary number in parentheses is the bit length (3) of the letter and the right-hand portion is the letter, starting from right to left. Zero is a dot; 1 is a dash. Even though the PROMs can be programmed, I recommend they be purchased

By Robert Morley and Dave Scharon, 2145 East Drive, St. Louis, Missouri 63131



*DELETE DIODE CR2 IF CATHODE-KEYING NPN TRANSISTOR IS USED.
DO NOT INSTALL Q8 IF Q9 IS USED FOR GRID-BLOCK KEYING.

fig. 1. ASCII-to-Morse code translator schematic. U3 is the numeric memory; U4 is alphabetic memory. U1 and U2 are Fairchild 3341 FIFO memories. All resistors are 1/4 watt, 10%. Capacitors larger than 1 µF are electrolytics. All diodes not otherwise marked are 1N914 or equivalent.

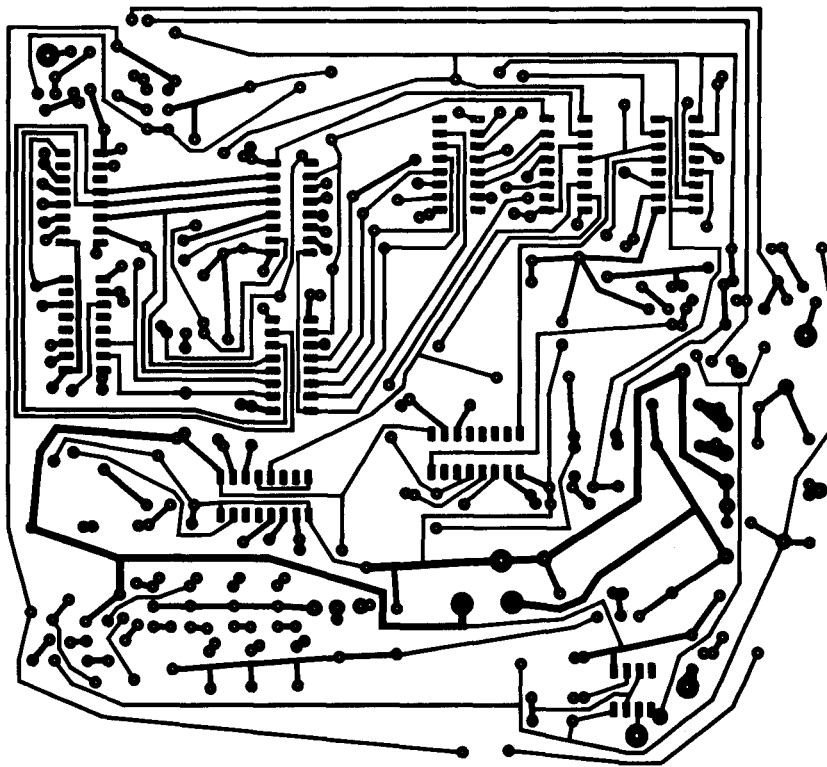


fig. 2. Printed-circuit board layout.

preprogrammed from the supplier listed in the article, because if one mistake is made, that's it. The supplier guarantees correct preprogramming.

The circuit (fig. 1) contains two PROMs. One includes all the alphabet (U4) and the other the numbers and punctuation (U3). Most of the Morse code is represented on a regular ASCII keyboard by its equivalent key except as follows:

key	Morse
<	end of message
>	end of work
=	wait
() either key	parentheses

This is done because all letters have the 6th bit of ASCII data low and numbers and punctuation high. The 6th bit is used to switch from one PROM to the other. The first 5 bits of both PROMs (U3 and U4) are wired together and connected to U5, an 8230, which is an 8-line to 1-line multiplexer. The last bits address U6, a 74192 up/down counter, which clocks through the bits of Morse letter by selecting the proper lines into U5. The output of U5 determines if a dash or dot is to be fired. The dash or dot is formed by U7, a 74123 dual one-shot. After the dash or dot is formed, the falling edge of the NEEDED \bar{Q} outputs fires a space one-shot, U8, whose timing is equivalent to a dot. U8 clocks the counter on the pulse rising edge, which selects the next bit of the letter and triggers the dot or dash on the falling edge.

This trigger circle continues until U6 reaches the 000 state. At this time the borrow line of U6 (pin 13) is used to inhibit the dot-dash one-shot, U7, and also fire one-shot U8 to produce a wait between characters equivalent to a dash. This one-shot output is used to bring up the next piece of data in the first-in, first-out (FIFO) memories, U1 and U2.

speed control

It is obviously desirable to have some means to vary the speed of the device, and for simplicity's sake we have chosen one-shots for our dots-dashes and wait timing. Tracking control of the speed would be nearly impossible with variable resistors, as it would take a 4-ganged pot and the control would be nothing close to linear. Current sources, however, make control easy as well as fairly linear. The current sources are controlled by one pot and feed each of one-shots, U7 and U8, at points J1, J2, J3, and J4. These current sources are made up of pnp transistors Q1, Q2, Q3, Q4, in a sort of upside-down emitter follower arrangement. Current control results in good 10:1 speed control.

input buffer

This portion consists of some very interesting circuits, which are the FIFO memories. The input and output are completely asynchronous, which means that data may be entered at any rate independent of the rate at which data is being clocked out by the code generator. As the data is clocked out of the FIFO memory, it is entered

into the two PROMs consisting of U3 and U4. If the keyboard has inverted ASCII, a 7404 ahead of U1 and U2 can be used.

keying circuit

The \bar{Q} outputs of U7, the dot-dash one-shot, are NEEDED through a discrete-component NAND gate including Q10. This circuit also drives a high-voltage npn

will normally occur at the end of the last character and the end of the H that the space sends, will equal seven dots. This was done by eliminating the space time and one wait time: much greater current is switched in through Q12 and Q11 to the space and wait one-shots while the H is being sent. This action eliminates the time taken up by the three spaces and one wait, which very nearly equals seven dots of time between words.

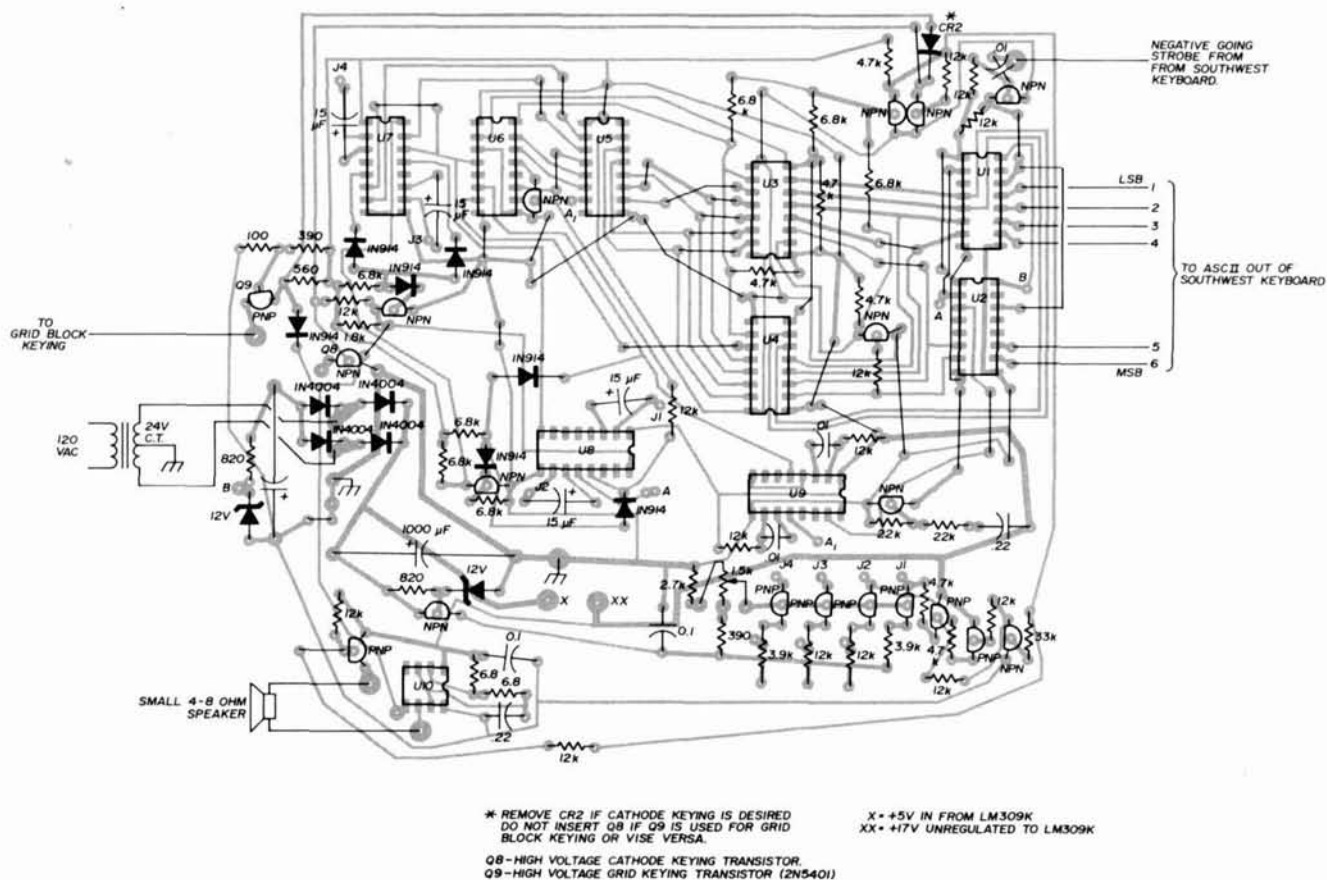


fig. 3. Component side of PC board.

transistor, Q8, for cathode keying and a pnp, Q9, for grid-block keying. The transistors selected here must handle the voltage and current of your transmitter. (This information can be found in the transmitter manual.) Grid-block keying will probably be the most widely used. A good value for the transistor would be 200 volts at 100mA. The NAND output, collector of Q10, also switches a sidetone oscillator made from a NE555, IC10.

space timing

One function that required a trick was the space timing, which is a necessity when the buffer memory is used. This problem required a resistor-transistor OR gate consisting of R1, R2, R3, Q5, Q6, which allows the circuit to function but inhibits the output and sidetone oscillator to simulate the proper space length. When the space bar is hit, a Morse H will be sent. Since good code requires 7 dots between words, something must be done to this H so that its time, plus the two wait dashes that

Any ASCII keyboard will do the job, but be sure it has a bounceless stobe that appears after the data is set up. A good keyboard for this purpose is available.* The circuit is set up for a negative-going strobe into Q13's base. An error key was considered, but when using the buffer chances are you'll be a few characters ahead before you realize an error has been made, and an error signal here would be meaningless. The unit won't make an error itself, so errors should be very rare.


construction

Point-to-point wiring could be used, but a PC board would make assembly easier.† If you prefer to make

*South West Technical Products, 219 West Rhapsody, San Antonio, Texas 78216. (Keyboard kit about \$40.00.)

†Circuit boards, 3341 FIFOs, the 8230 and PROMs are available for \$60.00 from Scharon Fabricators, 2145 East Drive, St. Louis, Missouri 63131.

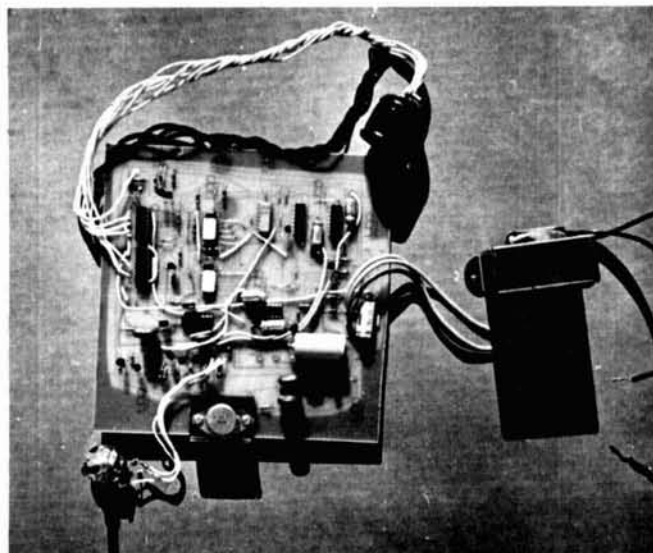your own, fig. 2 provides a full-size etched board layout; the component side of the board is shown in fig. 3. Wiring isn't critical, but care should be taken to ensure proper wiring so none of the integrated circuits will be damaged when the power is turned on. This advice applies particularly to the ROMs and FIFO memories, as they are more expensive than regular TTL integrated circuits.



Printed circuit board for translator chassis showing parts arrangement.

Earlier, the type of possible keying was mentioned. An npn transistor in the Q8 position can be used to key a relay (fig. 1). A diode should be placed in reverse across the relay coil to prevent voltage spikes.

The transistors in the circuit aren't critical except for the high-voltage transistors mentioned earlier. The 5-volt power supply is an LM309K. The 3341 FIFOs are MOS integrated circuits, and even though they're internally protected, care should be taken when handling them.

testing and operation

The capacitors used to set the timing on the one-shots for creating the dots, dashes and spaces will never have exact values, therefore resistors R10, R11, R12, R13 may have to be trimmed to get perfect dot-to-dash ratios. Points are available on the board to add these resistors, but in most cases this should not be necessary.

Connect a speaker to the sidetone oscillator and apply power to the unit after the keyboard has been properly attached. (See fig. 1 for the LSB-MSB keyboard locations.) At this point hit one of the keys on the keyboard and listen for the proper code from the sidetone oscillator. If the proper code isn't heard, check the circuit carefully and if an error is found, try again. Set the speed control as slow as possible, type in a message, then sit back and listen to the code; it should now be ready to put on the air.

ham radio

POWER PLUS PERFORMANCE



depend on BLACK CAT® Linear Amplifiers

The Black Cat® JB 2000 10/80 linear amplifier delivers the power you need and rugged performance you can count on. Designed and built with the same quality craftsmanship and pride that backs every Black Cat® product, the JB 2000 10/80 lets you stay up as long as you like, whenever you like.

Containing a 120VAC — 240VAC, Solid State self contained power supply, with a power input of 2000 watts PEP SSB, the JB 2000 10/80 linear amplifier greatly increases your signal. Whether building a new station or renovating an old, the Black Cat® JB 2000 10/80 is the perfect addition to any ham operator's equipment roster.

Also included in the Black Cat® line of durable and dependable ham accessories is the test equipment to insure that you stay on the air: the JB 1000 Dummy Load, JB 1000 SM Oscilloscope/RF Wattmeter/SWR Bridge, and JB 2000 SW Power Meter/SWR Bridge.



For complete information on all Black Cat® products, contact your nearest Black Cat® dealer, or write:

WAWASEE ELECTRONICS

"HOME OF BLACK CAT® PRODUCTS"


Wawasee Electronics Co., Inc.

P.O. Box 36 • Syracuse, Indiana 46567

Phone: (219) 457-3191

Wilson Electronics Corp.

HAND HELDS

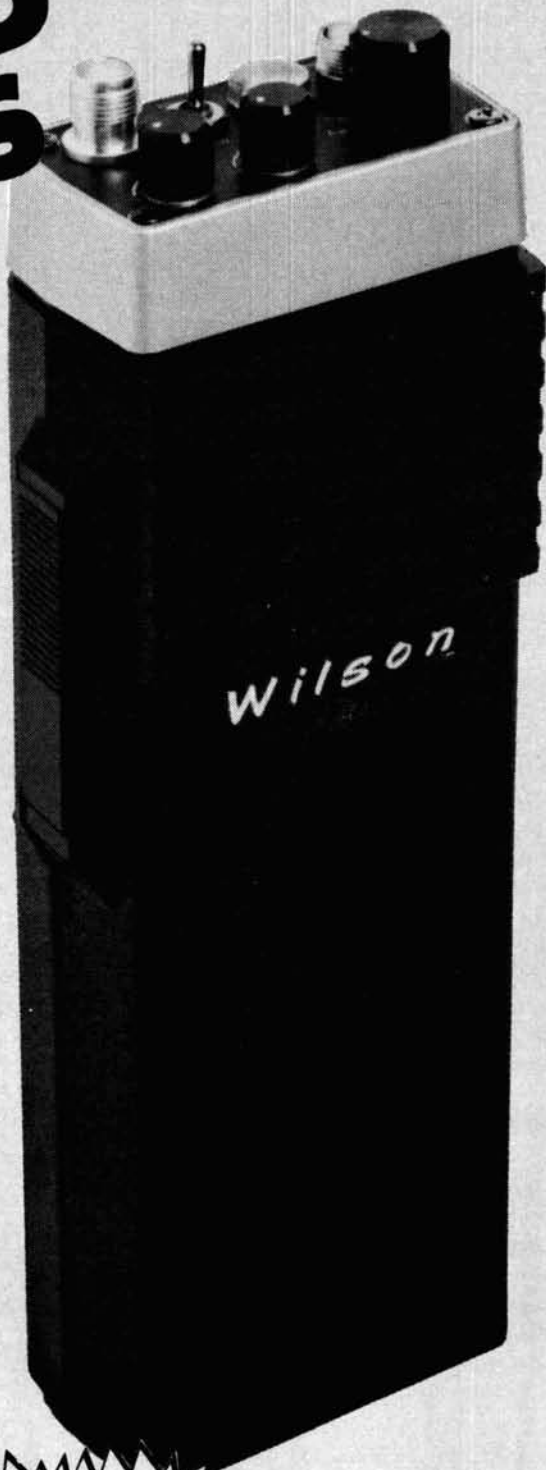

450

FREQUENCY RANGE 420 - 450 MHz

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 21.4 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 1.8 Watts Output @ 12 VDC
- Current Drain: RX 14 MA, TX 500 MA
- Microswitch Mike Button
- Unbreakable Lexan® Case

USES SAME ACCESSORIES AS 1405

INCLUDES

1. 4502 SM
2. Flex Antenna
3. 446.00 Simplex Installed

~~\$279⁹⁵~~

XMAS SPECIAL
\$269⁹⁵

220

FREQUENCY RANGE 220 - 225 MHz

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 2.5 Watts Output @ 12 VDC
- Current Drain: RX 14 MA, TX 500 MA
- Microswitch Mike Button
- Unbreakable Lexan® Case

USES SAME ACCESSORIES AS 1405

INCLUDES

1. 2202 SM
2. Flex Antenna
3. 223.50 Simplex Installed

~~\$239⁹⁵~~

XMAS SPECIAL
\$219⁹⁵

ACCESSORY SPECIALS

DESCRIPTION	SPECIAL PRICE
BC1 BATTERY CHARGER	\$34.95
BP1 10 EA. AA GOULD NICAD BATTERIES . . .	14.95
BT1 EXTRA BATTERY TRAY	5.00
LC1 LEATHER CASE 1402	12.95
LC2 LEATHER CASE 1405, 2202, 4502	12.95
SM1 SPEAKER MIKE FOR EARLY MODEL 1402 9 PIN CONNECTOR	24.95
SM2 SPEAKER MIKE FOR ALL NEW HAND HELDS WITH ROUND 6 PIN CONNECTOR	24.95
TE-1 SUB-AUDIBLE TONE ENCODER INSTALLED	34.95
TTP TOUCH-TONE PAD	49.95
INSTALLATION AT TIME OF RADIO PURCHASE	FREE
INSTALLATION AT LATER DATE, ADD	15.00
XF-1 10.7 KC MONOLITHIC XTAL FILTER	9.95
CRYSTALS TX or RX (Common Frequency Only)	3.75



BC-1 BATTERY CHARGER

XMAS SPECIAL

"FACTORY
DIRECT
ONLY"

XMAS SPECIAL

**1402SM HAND HELD
2.5 WATT
TRANSCIVER**

144-148 MHz

~~\$164.95~~

**XMAS SPECIAL
\$159.95**



Shown With
Optional
Touch-Tone Pad

**1405SM HAND HELD
5 WATT
TRANSCIVER**

144-148 MHz

~~\$289.95~~

**XMAS SPECIAL
\$229.95**



FEATURES

1402 SM

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 IF and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- 5-Meter/Battery Indicator
- Size: 8 7/8 x 1 7/8 x 2 7/8
- 2.5 Watts Minimum Output @ 12 VDC
- Current Drain RX 14 MA TX 500 MA
- Microswitch Mike Button
- High Impact Plastic Case

1405 SM

- 6 Channel Operation
- Individual Trimmers on all TX/RX Crystals
- All Crystals Plug In
- 12 KHz Ceramic Filter
- 10.7 and 455 KC IF
- .3 Microvolt Sensitivity for 20 dB Quieting
- Weight: 1 lb. 14 oz. less Battery
- Battery Indicator
- Size: 8 7/8 x 1 3/4 x 2 7/8
- Switchable 1 & 5 Watts Minimum Output @ 12 VDC
- Current Drain: RX 14 MA TX 400 MA (1w) 900 MA (5W)
- Microswitch Mike Button
- Unbreakable Lexan® Case

**SPECIAL
ON EACH RADIO
INCLUDES:**

Flex Antenna
52/52 Simplex Xtal

90
Day
Warranty

10 Day
Money Back
Guarantee

Can be Modified
for
MARS or CAP

**OVER 35,000
XTALS
IN STOCK**

**OVER 2000
UNITS IN STOCK
FOR XMAS SALE**

XMAS SPECIAL DIRECT SALE ORDER BLANK

TO: WILSON ELECTRONICS CORP., 4288 S. POLARIS AVE., LAS VEGAS, NEVADA 89103
(702) 739-1931

- ___ TTP @ \$49.95
- ___ XF1 @ \$9.95
- ___ TX or RX XTALS @ \$3.75 ea.
Common Frequencies Only.
- ___ FACTORY XTAL INSTALLATION/
NETTING @ \$7.50/Radio
- ___ MARS or CAP XTALS @ \$10.00 ea.

EQUIP TRANSCIVER AS FOLLOWS:

XTALS TX	RX	XTALS TX	RX
A. 52	52	G.	
B.		H.	
C.		I.	
D.		J.	
E.		K.	
F.		L.	

- ___ 1402SM @ \$159.95
- ___ 1405SM @ \$229.95
- ___ 2202SM @ \$219.95
- ___ 4502SM @ \$269.95
- ___ BC1 @ \$34.95
- ___ BP1 @ \$14.95
- ___ BT1 @ \$6.00
- ___ LC1 @ \$12.95
- ___ LC2 @ \$12.95
- ___ SM1 @ \$24.95
- ___ SM2 @ \$24.95
- ___ TE1 @ \$34.95

(SPECIFY FREQUENCY _____)

- CHECK MONEY ORDER
- MASTER CHARGE
- BANKAMERICARD

ENCLOSED IS _____

CARD # _____

EXPIRATION DATE _____

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

SIGNATURE _____

SHIPPING & HANDLING PREPAID FOR XMAS SPECIAL
NEVADA RESIDENTS ADD SALES TAX

HR VALID ONLY NOV. 1 THRU DEC. 31, 1976

the ladder network

An analysis of the ladder network using the method of "continued fractions"

If you happen to have an old three-gang tuning capacitor lying idle, the addition of a few resistors and a couple of inexpensive transistors will produce a phase-shift oscillator such as shown in fig. 1: no coils, no fixed capacitors, no variable resistors. This is no precision signal generator but is useful as a handy source of rf signals and has a large tuning range. With 2500-ohm resistors in the ladder network it covers about 250 kHz to 2.5 MHz. With higher resistances the range will be less. Transistors such as the 2N4996 or 2N4274 work well, with 3000 or 4000 ohms between ground and the second collector.

analysis

The main purpose of this article, however, is to show how any ladder network (including the one in the oscillator of fig. 1) can be analyzed in a purely routine fashion by the use of a not-too-familiar branch of mathematics called "continued fractions." The analysis applies to ladders composed of any number of elements, each of which can be anything you want. By suitably choosing these elements, the ladder can be made to become not only a phase shifter but also a bandpass, lowpass, or highpass filter; an impedance matching network; an attenuator; or a lumped-constant transmission line.

The input end of the ladder can be a series element to which a constant voltage, E , is applied or a shunt element fed by a constant current, I . The final element can be a shunt element across which the output voltage, e , is taken, or it may be a series element, the current in which i is the output.

For the moment, however, let us concentrate on the case of six elements arranged as shown in fig. 2 where the z s are the impedances of the series elements and the y s are the admittances of the shunt elements. For this network there are two elegantly simple formulas: the output voltage, e , is $\frac{E}{p_6}$ and the input impedance is $\frac{p_6}{q_6}$.

Of course these formulas are useful only when p_6 and q_6 have been expressed in terms of the various impedances and admittances in the ladder. How this is done in a systematic manner requires quite a bit of explanation, but proofs will be omitted so that only

what is necessary to operate the mathematical mechanism will be explained. We start by putting all the elements of the ladder in this peculiar-looking form:

$$z_1 + \frac{1}{y_2 + \frac{1}{z_3 + \frac{1}{y_4 + \frac{1}{z_5 + \frac{1}{y_6}}}}}$$

This expression is called a "simple continued fraction" containing six quantities. Its value is the input impedance of the ladder, although you may not be able to see it offhand. Any such continued fraction can be reduced to the ratio of two expressions involving the z s and the y s, the numerator of this ratio being called p with appropriate subscript, while the denominator is called q . If there had been only one element in the ladder we would have $p_1 = z_1$ and $q_1 = 1$. If there had been two elements we would have $p_2 = z_1 y_2 + 1$ and $q_2 = y_2$. But when there are quite a few elements, the reduction to p s and q s would be very laborious were it not for the fact that the theory of simple continued

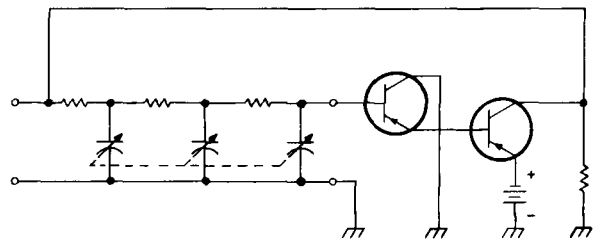


fig. 1. Phase-shift oscillator using ladder-network principle. Capacitor is a three-gang variable; transistors can be types such as the 2N4996 or 2N4274. Oscillator covers about 250 kHz to 2.5 MHz frequency range.

fractions gives us a rule for building up from one p to the next and from one q to the next. The rule is that every new p is equal to the previous p multiplied by the element having the same subscript as the new p , plus the p which is two places behind the new p . Thus, $p_3 = p_2 z_3 + p_1$ and $p_4 = p_3 y_4 + p_2$ and so on. By the use of this rule a table of p s can be built up without any real thinking. And the same rule applies to the q s starting with the two q s given above. It is not difficult, merely somewhat lengthy, to find the value of p_6 in general terms. But it becomes much easier if we don't make all the elements different. For example if we choose all the z s in fig. 2 to be equal resistances, R , and all the y s to be equal susceptances j/x , where X is the capacitive reac-

By Walter van B. Roberts, K4EA, 6330 Manasota Key Road, Englewood, Florida 33533

tance of one section of the tuning capacitor, then p_6 works out to be

$$\left(1 - 5 \frac{R^2}{x^2}\right) + j \left(6 \frac{R}{x} - \frac{R^3}{x^3}\right)$$

From this it is evident that when $R/X = \sqrt{6}$ the imaginary part vanishes and the value becomes -29 . In other words, the phase has been shifted 180 degrees and the output voltage is 1/29 of the input. Hence if the output voltage is amplified 29 times or more and then fed back to the ladder input, oscillation will occur, as in fig. 1.

the general case of n elements

The foregoing seems sufficient explanation to make the transition to the general case of n elements obvious. Fig. 3 gives all the information needed to grind out a solution for any ladder with any number of elements of any kind, provided the rule for building up the p s and q s is remembered. But it must be emphasized that the present method does not get around the necessity for writing out lengthy expressions when many different

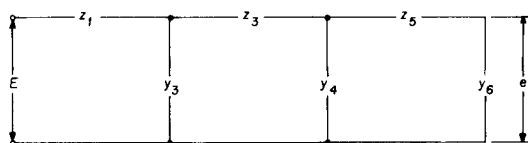


fig. 2. Ladder model using six elements. Network analysis is made in terms of impedances and admittances of the series and shunt elements.

elements are used. What it does do is provide a routine that can be followed without any brainwork other than to be careful not to make simple mistakes.


example

Before attempting to use the material of fig. 3 for anything complicated, however, it's a good idea to get the feel of the mechanism by trying it out on something easy, which can be checked by other methods. For example, in fig. 2 if all the elements are equal resistors, R , it will be found that the output voltage is 1/13 of the input voltage, regardless of the size of R , and that the input impedance is 13/8 times R . Incidentally it may be of interest to note that if the number of resistors is increased much beyond six in the network just discussed, the input impedance approaches a constant value

$$\frac{1 + \sqrt{5}}{2} R$$


Finally, although it should be obvious, the reason that no consideration has been given to ladders with constant voltage applied to a first shunt element, or with constant current fed into a series first element, is that in both these cases the first element becomes functionless. In the first case the input shunt element would merely draw useless extra current from the source of constant voltage, while in the second case the series first element

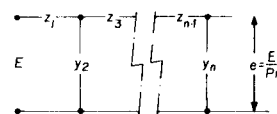INPUT TO SERIES ELEMENT
INPUT IMPEDANCE = p_n/q_n



The impedance fraction:
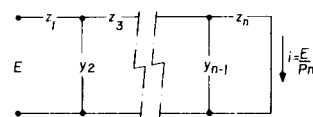
$$z_1 + \frac{1}{y_2 + \frac{1}{z_3 + \frac{1}{y_4 + \text{etc.}}}}$$



Its p s and q s are:


$$\begin{aligned} p_1 &= z_1 \\ p_2 &= y_2 z_1 + 1 \\ p_3 &= z_3 y_2 z_1 + z_3 + z_1 \\ p_4 &= y_4 z_3 y_2 z_1 + y_4 z_3 + y_4 z_1 + y_2 z_1 + 1 \end{aligned}$$

and so on

$$\begin{aligned} q_1 &= 1 \\ q_2 &= y_2 \\ q_3 &= z_3 y_2 + 1 \\ q_4 &= y_4 z_3 y_2 + y_4 + y_2 \end{aligned}$$


and so on

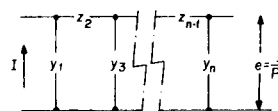INPUT TO SHUNT ELEMENT
INPUT ADMITTANCE = p_n/q_n



The admittance fraction:
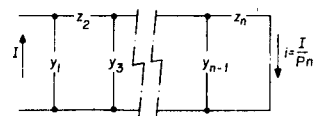
$$y_1 + \frac{1}{z_2 + \frac{1}{y_3 + \frac{1}{z_4 + \text{etc.}}}}$$



Its p s and q s are the same as at left with z and y interchanged:

$$\begin{aligned} \text{so } p_1 &= y_1 \\ p_2 &= z_2 y_1 + 1 \end{aligned}$$

and so on

fig. 3. Data for solving any ladder network of n elements using the method of "simple continued fractions."

would merely require more voltage in the source of constant current. In neither case would the first element play any part in the performance of the ladder. That would be determined solely by elements beyond the first. Thus fig. 3 covers all actual performance possibilities.

ham radio

Everything you put into ham radio comes together at your antenna. That's why we put everything we've got into making Swan antennas the best you can buy.

Swan beam antennas are precision engineered to give you a full 2000-watt P.E.P. rating. They're designed for a VSWR of 1.5:1 or better at resonance. They'll give you optimum gain and they're built tough, and rugged to stand up to some of the meanest environments.

Don't lose it right where it all comes together. Get one of these Swan beam antennas and top off your rig with a winner. Use your Swan credit card. Applications at your dealer or write to us.

TB-4HA



Heavy-duty, four-working-element antenna for 10, 15 and 20 meters. \$249.95

TB-3HA



Heavy-duty, three-working-element antenna for 10, 15 and 20 meters. \$189.95

TB-2A



Light-weight, two-working-element antenna for 10, 15 and 20 meters. \$129.95

MB-40H



Heavy-duty, two-working-element antenna for 40 meters. \$199.95

Ask about our 1040V trap vertical for 10 thru 40 meters with optional 75-meter add-on kit.


SWAN BEAM ANTENNA SPECIFICATIONS. For 52-ohm coaxial feedlines.							
ANTENNA MODEL NUMBER	BOOM LENGTH & DIAMETER	LONGEST ELEMENT	TURNING RADIUS	MAXIMUM WIND SURVIVAL	WIND LOAD @ 80 MPH	WIND SURFACE AREA	NET WEIGHT
TB-4HA	24' x 1.5"	28'-10"	18'-6"	100 mph	148 lbs.	6 sq. ft.	54 lbs.
TB-3HA	16' x 1.5"	28'-2"	16'	100 mph	110 lbs.	4 sq. ft.	44 lbs.
TB-2A	6.5' x 1.5"	27'-8"	14'-3"	80 mph	60 lbs.	1.8 sq. ft.	18 lbs.
MB-40H	15.75' x 1.5"	30'-4"	17'-6"	100 mph	80 lbs.	2.5 sq. ft.	40 lbs.

(Prices FOB Oceanside, CA)

Dealers throughout the world or order direct from

 **SWAN[®]**
ELECTRONICS
 A subsidiary of Cubic Corporation
 305 Airport Road, Oceanside, CA 92054
 (714) 757-7525

DON'T LOSE IT HERE.

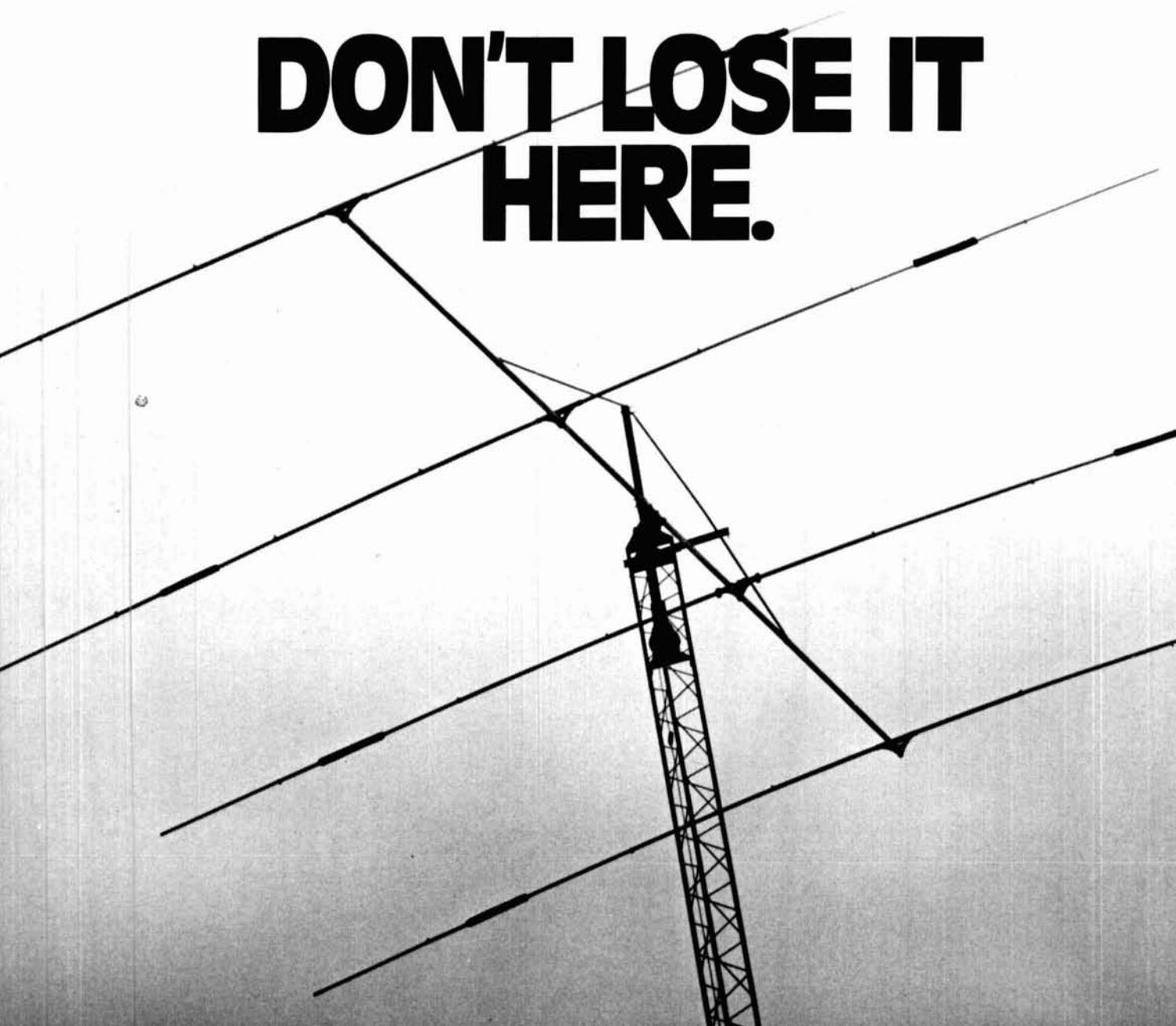

There's only one power reading in single sideband operation that means anything: true peak envelope power of your voice modulated signal.

And that's exactly what our precision WM-3000 peak/RMS wattmeter gives you.

You get flat frequency response from our new direc-

tional coupler that lets you read forward or reflected power from 3.5 to 30 MHz with more accuracy than you'll ever need. And you can read it on 200, 500, 1000 and 2000-watt scales in RMS as well as peak at the flip of a switch.

Get a Swan WM-3000 meter today and find out what's hap-

pening with your single sideband rig. Only \$66.95. Use your Swan credit card. Applications at your dealer or write to us.




SWAN
ELECTRONICS[®]

A subsidiary of Cubic Corporation
305 Airport Road, Oceanside, CA 92054
(714) 757-7525

(Price FOB Oceanside, CA)

SWAN PEAK READING WATTMETER

tells it like it is on SSB.

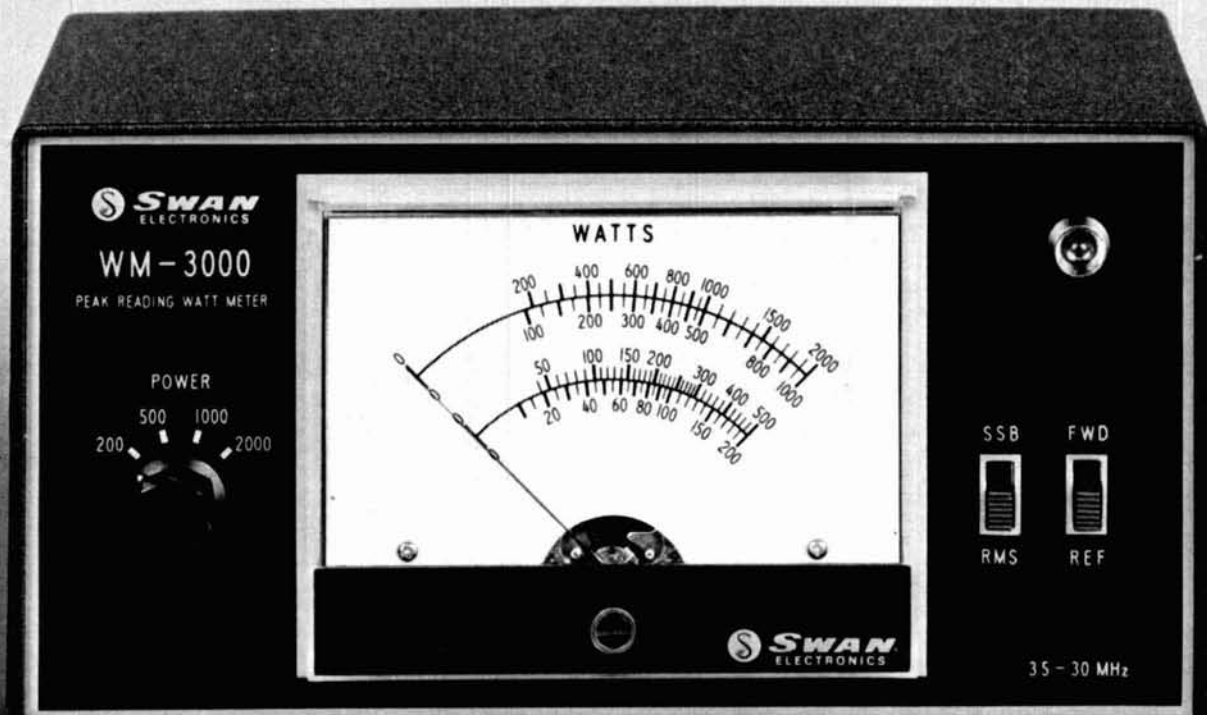

repair bench



Joe Carr, K4IPV

resurrecting the old war horse: new hope for the old receiver

If you walk through the flea market of any reasonably sized hamfest, it's likely that you will turn up any number of middle age receivers, often at bargain-basement prices. Models such as the venerable Hallicrafters SX-28A (which WA4EPI toted up the side of Bull Run Mountain on Field Day), SX99, SX-100, SX-101, and any of a long series of HQ-series Super Pro receivers by Hammarlund seem to be in evidence. Receivers, especially general-coverage types, manufactured prior to the late 1960s are in poor favor among hams because they lack the gloss of the newer technologies, may be a little troublesome when tuning single sideband (but not necessarily), and don't seem to fit well into the decor of our current transceiver-oriented radio stations. If, however, you are a new novice, a pre-novice wanting W1AW code practice and something to fiddle with, a young adult with a family budget battered by kids, mortgage and a car payment or two, or even an oldtimer with a luxury station, such old war-horse receivers can be a real bargain for use as a standby receiver, the main station receiver, or something to putter around with to learn some shirt sleeve electronics. The kicker is that — they frequently don't work properly.

As I pointed out in my troubleshooting article in the June issue, in most cases receiver troubleshooting is not the terrible chore it is made out to be. To be sure, there are some terrific problems that require a good technician and a lab full of equipment to solve but the vast majority are of a more mundane nature. In this article, I will address those problems that are peculiar to reworking or repairing old, supposedly worn-out, radio receivers which were the big guns of another era. After all, one person's trash may well be another's treasure.


By Joseph J. Carr, K4IPV, 5440 South 8th Road, Arlington, Virginia 22204

Consider my own case. After ten years of apartment living, my wife and I bought a little duplex house and settled into suburban living. While Bonnie fiddled with draperies and furniture placement, Yours Truly was scheming to erect something that had been denied me for all those years: *an antenna*. The next requirement to be met was an old DX-60B belonging to a co-worker and the purchase of a new receiver — until the prices made it apparent that I wasn't going to have a new receiver for a long while. An old friend who never really got into amateur radio was more than willing to part with his old Hammarlund HQ-145X which he had purchased new when Eisenhower was President. It only partially worked, but the price was well below its apparent market value. A decade and a half of improper storage had taken its toll.

The first thing to do when "auditioning" a receiver of this vintage is to make an operational check, preferably before making the purchase. Turn it on and operate the controls. Determine exactly what is, or is not, working properly. Keep in mind that most receivers which have been in storage for any length of time will not be in the best of working order. If the radio works on *any* band, then the set is a good candidate for resurrection. If, on the other hand, it does not work on any band, it is a lesser candidate but that doesn't mean it should be completely ruled out. To be sure, it may require a more extensive evaluation, but the fact that nothing goes "beep" when you tune across the ham bands should reduce the price quite a bit.

Once you have acquired the monster it may have to be repaired. But first, let it run (*not* unattended) for several hours a day over the course of a few days to a week. The heat from the filaments tends to drive out any accumulated moisture, and turning the receiver on for short periods allows the electrolytic capacitors to wake up and start working again. My own HQ-145X had a rather bad audio hum when I first inspected it, but the

fig. 1. The chassis of a reclaimed communications receiver, such as this HQ-145X, may have several points with lethal potentials — unplug the receiver before working on it. Examine the electrolytic capacitors for bulges or a swollen appearance. Make sure the variable capacitor plates are fully meshed before you begin working.

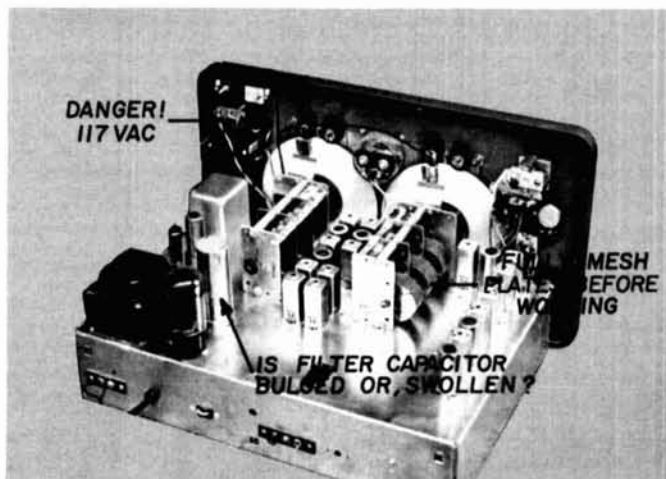

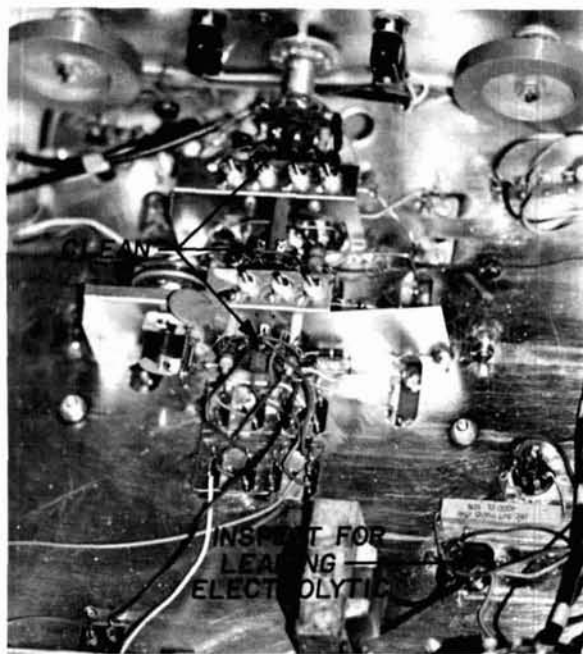


fig. 2. The bandswitch is a main area of difficulty and may need cleaning with a degreaser or a pencil eraser. Examine the bottom of the electrolytic filter capacitor for signs of electrolyte leakage.

hum disappeared in a few days after the electrolytics had reformed. In addition to the audio hum there were a number of other problems:

1. No high band (10 to 30 MHz) and only a scratching sound was heard on these frequencies when the main tuning dial was turned.
2. Occasional oscillation and a rather constant microphonic condition. Oscillation seemed frequency dependent and was at its worst on the special 20 BS band (a modified 10 to 30 MHz band unique to the HQ-145X series).
3. Noisy control potentiometers.
4. Noisy bandswitch.
5. All other rotary switches noisy and/or intermittent.

After the receiver had been burned in for almost a week, I was ready for the next step: cleaning and an additional inspection of the innards. Fig. 1 shows the HQ-145X with the cabinet removed. At this point I feel it's important to caution you that lethal voltages exist on several points inside the receiver. Raw 117 Vac, direct from the power mains, is present on the clock motor in the upper lefthand corner. Unplug the receiver until power is actually needed and discharge the filter capacitors. Also, at this point, be sure to fully mesh the capacitor plates (tune receiver to low end of the dial) so that they will not be damaged as you work. If the capacitor plates are left unmeshed as those in fig. 1, then damage is almost certain.

The first step in cleaning the receiver is to remove the layer of dust that inevitably collects on any electronic chassis. Use either a 1- to 2-inch (2.5 to 5cm) paint brush

or an air gun, if available. Don't ever use steel wool on an electronic chassis — the small particles can really gum up the works. Although aesthetic considerations and your early training may dictate that you clean every nook and cranny don't be too vigorous in the vicinity of the main tuning capacitor. Dust between the plates can cause trouble and is hard to completely remove.

The next phase of the job is to replace any burned-out lamps, then clean the potentiometers and the rotary switches. The switch wafers and pots can be cleaned with almost any of the spray-can electronic contact cleaners, even the cheapies sold through mailorder and walk-in retail outlets. Be sure to spray each switch wafer separately and try to get spray inside each potentiometer. Immediately after spraying it is wise to vigorously operate the control or switch through its entire range for several seconds. In many cases, though, badly neglected rotary switches, especially those that have been totally unused for years, will have corrosion bad enough (it's black and the spray doesn't cut it) that the spray treatment is insufficient. For switch wafers in that condition I recommend an ordinary pencil eraser applied directly to the contact surface. It is usually best, especially in the vicinity of the bandswitch where moved wires can mean changed alignment, to hold the eraser steady and move the contacts underneath it. Don't forget the portion of the wiper contact surface directly underneath the fixed contacts (see fig. 3). That is, after all, where most of the trouble is.

The initial cleaning just described completely solved problems 3, 4 and 5 on my list and made a dent in problem 1 and now I could hear activity on 20 meters and 15-MHz WWV! The 20BS oscillations remained, as did the scratching on 10 through 30 MHz as the main tuning dial was turned. I also noted that a frequency dependent oscillation had appeared on the 10 to 30 MHz band. This can be a little frightening. If you are cognizant of receiver problems you probably agree that troubleshooting *tunable* oscillations is a lot like trying to



fig. 3. Be sure to clean the portion of the switch wiper contact surface that is underneath the fixed contacts. This can be done by rotating the switch while holding the eraser between two contacts.

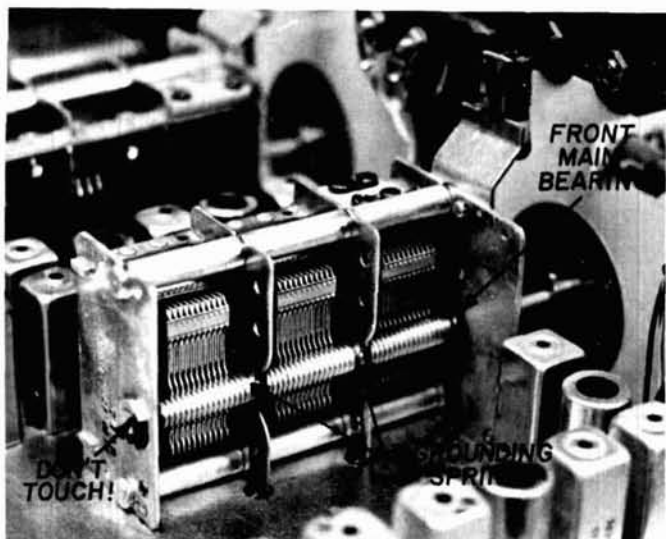


fig. 4. Instability and oscillation results from dirt and corrosion under the rotor ground springs and front main bearing. Clean and relubricate. See text for precautions.

skin an amoeba. I have seen amateur and professional technicians alike (including myself) work for hours, and even days, on such problems. Before looking for open suppressor grids, open screen bypass capacitors, or agc capacitors, you must consider other causes that are peculiar to the neglected receiver.

There are two general causes of oscillation and microphonic conditions on such receivers and they are both spelled *CRUD*. In some cases, it is found that crud on the chassis forms undecoupled feedback paths between stages. Use a Freon-based degreaser or, as an undesirable alternative if you must, that popular concoction consisting of a quart of *Lestoil* with a pinch of ammonia and acetone added, to clean the chassis. Be sure to concentrate on the underside of the chassis and take care not to slop that concoction inside i-f/rf transformers and on to the variable capacitors. The second type of crud is dirt and dried grease in the main bearing and underneath the rotor grounding springs of the main tuning capacitor (see fig. 4). The cleaning should be done with a tiny jeweler's screwdriver or a relay cleaning tool. Carefully burnish the frame and the spring until clean.

The front main bearing race is a circular track filled with ball bearings. Clean this out using a virgin solvent

such as Freon TF (I use Miller - Stephenson MS-180). *Do not* use foam contact cleaners or any television type cleaner that leaves a residue. Also, do not trust the labels on some products. Actually test the spray for a residue. Even with a cleaner such as MS-180 use it sparingly and avoid hitting the capacitor plates if possible (it *is*). After the bearing race is clean, re-lubricate it with a white grease such as Lubriplate (available at most electronic supply houses). Use a single dab on the main race and a microdab underneath each grounding spring. Clean the spring over the rear main bearing but otherwise leave that bearing alone. Under no circumstances should you attempt to adjust the tension screw associated with the rear bearing. It is unlikely that the capacitor will ever work properly if you do. Cleaning the main tuning capacitor and the bandspread tuning capacitor (in a similar manner) completely cured problem 2 and what was left of problem 1.

Once all of the cleaning is done you may worry about replacing components. Of course, if the radio does not work up to snuff then some troubleshooting may be in order. Chances are good, though, that the cleaning will restore normal operation, assuming that the radio had been retired in good working order.

Examine all electrolytic capacitors. If any are bulged out or appear swollen, replace them. Also examine the electrolytics for signs of electrolyte leakage. Look for fluid, either a loose, clear stuff or a thick syrup-like type or (more often) a dry powder that will be some color between off-white and dusky brown. Any of these symptoms mark the capacitor for replacement — don't leave a bad electrolytic in the set! If only one section of the multisection power supply filter capacitor is open do not be tempted by the poor advice, given by some people, to bridge a good capacitor across the bad section. That is only a diagnostic tool and is such poor practice that it ought to be scorned. That open section may short someday (sooner than you might think) and then you can kiss your filter choke and rectifier goodbye.

Examine all of the other capacitors in the set. On paper types look for the wax end plugs being either missing or in poor shape. On the types with a black plastic body look for fluid and cracks in the plastic. Ceramic capacitors may be chipped or cracked but, for the most part, survive well. Replace paper capacitors with a good grade of dipped mylar capacitor such as the

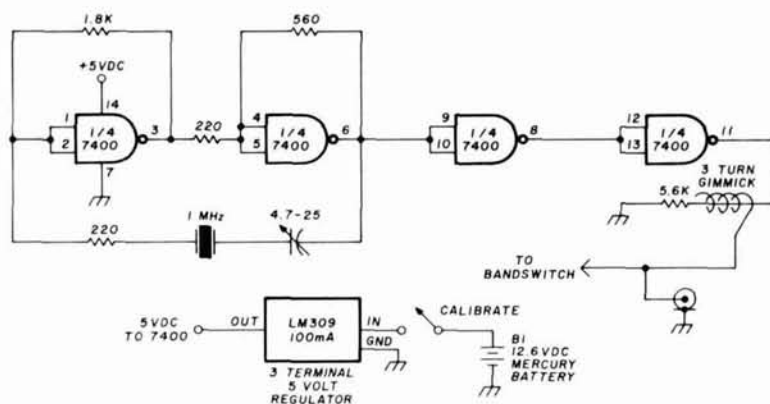


fig. 5. 1-MHz crystal calibrator using TTL logic. The regulator is in the TO-5 can, a 100 mA version of the LM309.

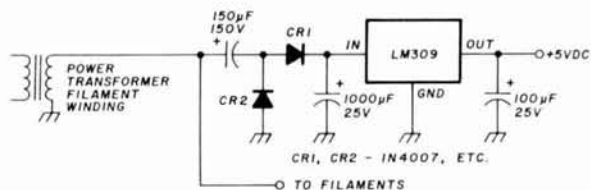


fig. 6. Suggested power supply for the crystal calibrator using the receiver's filament supply.

Sprague Orange Drop. Ceramic and mica types should be replaced with identical units.

Examine all of the carbon composition resistors for signs of overheating, burning, or cracking. Use only a good, new replacement. In this present context let me pass along some advice from my own experience: patronize a quality dealer and buy some good, new, replacement parts. This advice comes from trying bargain, hamfest castoff or surplus parts in one too many circuits! They are good for pittering around, but receiver servicing is really serious work. Incidentally, it won't cost over \$10 to \$15, even if almost all of the capacitors and resistors in the set are bad, which is unlikely.

You will also want to test the tubes from your reclaimed treasure. Use a tube tester, even if it is in a drug store or supermarket. These are simple emission testers but will quickly spot the gross loss of gain and internal shorts. Replace bad tubes with either new tubes recently acquired or those hamfest types known to be new military or commercial surplus. I have used a lot of new, surplus JAN tubes over the past two decades and honestly believe that the number of "bad-off-the-shelf" was actually less than those purchased at commercial outlets.

Once your receiver has been repaired and everything works properly, you may want to turn your attention to adding to (or changing) the instrument to fit your own needs. In my case, I activated an old irritation and replaced the three-screw terminal strip used as an antenna connector with a SO-239 coaxial connector. Also added was a binding post connected directly to chassis ground. The receiver which I had acquired lacked a crystal calibrator so one was added. Since I couldn't find a Hammarlund calibrator designed for the HQ-145, one had to be built. You have several alternatives here. You could duplicate the original and plug it into the appropriate socket or hard wire it to the socket. That has the advantage of using the front-panel *calibrator* switch to turn it on. After an inspection of my junk box I chose a 1-MHz TTL calibrator shown in fig. 5. Although mine is battery powered, you could power it from the receiver power supply as shown in fig. 6. The filament drain of the tube in the optional Hammarlund calibrator was about 300 mA and that is more than sufficient reserve to run the TTL integrated circuits.

After all else is done and you know that the radio is going to work, take some mild, soapy, household cleaner and gently clean the front panel. That "new" appearance will give you a psychological boost that is well earned.

ham radio

THE COMPUTER ROOM

SMALL COMPUTER SYSTEMS • SOFTWARE • AMATEUR RADIO EQUIPMENT

1455-B So. 1100 E. Salt Lake City, Utah 84105 Phone: 801-466-7911

"WE TAKE THE
MYSTERY OUT OF THE MICRO"



One Of The Nations Largest
Full-Service Computer Stores.

Over 1600 Square Feet Of Sales
And Service Facilities.

WHEN YOU WRITE FOR OUR CATALOG AND ENCLOSE \$1 TO HELP DEFRAY THE COST OF HANDLING AND MAILING, HERE'S WHAT YOU GET:

1. A CERTIFICATE GOOD FOR \$2 ON YOUR NEXT PURCHASE

2. THE **COMPUTER ROOM** EASY TO UNDERSTAND CATALOG COVERING

IMSAI
THE DIGITAL GROUP
POLYMORPHIC SYSTEMS
SOUTHWEST TECHNICAL PRODUCTS CORPORATION
TECHNICAL DESIGN LABS
PROCESSOR TECHNOLOGY
ETC.

3. THE **COMPUTER ROOM** "EASY GUIDE" TO HELP YOU PICK THE RIGHT SYSTEM, PERIPHERALS, COMPONENTS, AND SOFTWARE FOR

THE BEGINNER
THE ADVANCED
THE EXPERT
THE SMALL BUSINESS

4. A CURRENT LISTING OF PRESENTLY AVAILABLE

SOFTWARE
PUBLICATIONS
PERIPHERALS

5. INFORMATION ON REPAIR SERVICE, LOW COST CUSTOM PROGRAMMING AND OTHER SPECIAL SERVICES.

AT THE **COMPUTER ROOM** YOUR WRITTEN QUESTIONS ARE HAPPILY RECEIVED AND PROMPTLY ANSWERED

WE ALSO STOCK A COMPLETE
LINE OF AMATEUR RADIO EQUIPMENT

BANKAMERICARD MASTERCHARGE

From INFO-TECH's Advanced Technology in Digital Electronic Systems:



New Model 90 RTTY Terminal Unit

Features Tunable Active Filter Mark and Space Selection allowing any frequency shift combination. Dual meters allow easy tuning. Limiter & Autostart are standard features of this receive-only TU.

Priced at only \$259.50



Model 10 Morse Keyboard

(Shown with optional Buffer Capacity Meter)
Lowest priced, full feature C.W. Keyboard on the market today. Designed for the newcomer and advanced operator alike. 8-80 W.P.M. speed range with 64 character running buffer memory. (Options include dual message memory and buffer capacity meter)

Priced at only \$239.50



Model 30 — Morse to Video Converter

The most complete morse to video converter on the market today. Simply connect to your receiver's audio output and your video monitor and enjoy C.W. copy from 8 to over 80 W.P.M. Features word spacing control and automatic speed adjustment.

Priced at only \$324.95



Model 60 RTTY To Video Converter

Converts the output from the Model 90 or similar TU into Video for inexpensive, quiet RTTY reception on your video monitor. Features selectable speeds of 60, 66, 75 & 100 W.P.M.

Priced at only \$324.95

- All systems include prepaid UPS delivery in continental USA
- Master Charge Welcome
- Send for Data Sheets on any of these products as well as the Model 66C ASCII Computer Terminal

INFO-TECH **INCORPORATED**

Specializing in Digital Electronic Systems

20 Worthington Drive,

St. Louis, Missouri 63043

Phone: 314-576-5489

We have the perfect mobile/portable HF SSB Transceiver for you.



Seven pounds of dynamite
measuring only 9½ in. wide, 3½ in. high, 9½ in. deep.

The Atlas 210x/215x

The Atlas 210x or 215x measures only 9½" wide x 9½" deep x only 3½" high, yet the above photograph shows how easily the Atlas transceiver fits into a compact car. And there's plenty of room to spare for VHF gear and other accessory equipment. With the exclusive Atlas plug-in design, you can slip your Atlas in and out of your car in a matter of seconds. All connections are made automatically.

BUT DON'T LET THE SMALL SIZE FOOL YOU!

Even though the Atlas 210x and 215x transceivers are less than half the size and weight of other HF transceivers, the Atlas is truly a giant in performance.

200 WATTS POWER RATING!

This power level in a seven pound transceiver is incredible but true. Atlas transceivers give you all the talk power you need to work the world barefoot. Signal reports constantly reflect great surprise at the signal strength in relation to the power rating.

FULL 5 BAND COVERAGE

The 210x covers 10-80 meters, while the 215x covers 15-160 meters. Adding the Atlas Model 10x Crystal Oscillator provides greatly increased frequency coverage for MARS and network operation.

HELP WANTED

Technicians with Solid State and SSB experience. If you are a really sharp technician who would enjoy working in the amateur radio field, we have excellent opportunities with a bright future. Send your resume to Atlas Radio. No phone calls please.

NO TRANSMITTER TUNING OR LOADING CONTROLS

with Atlas' total broadbanding. With your Atlas you get instant QSY and band change.

MOST ADVANCED STATE OF THE ART SOLID STATE DESIGN

not only accounts for its light weight, but assures you years of top performance and trouble free operating pleasure.

PLUG-IN CIRCUIT BOARDS

and modular design provides for ease of servicing.

PHENOMENAL SELECTIVITY

The exclusive 8 pole crystal ladder filter used in Atlas transceivers represents a major breakthrough in filter design, with unprecedented skirt selectivity and ultimate rejection. This filter provides a 6 db bandwidth of 2700 Hertz, 60 db down of only 4300 Hertz, and a bandwidth of only 9200 Hertz at 120 db down! Ultimate rejection is in excess of 130 db; greater than the measuring limits of most test equipment.

EXCEPTIONAL IMMUNITY TO STRONG SIGNAL OVERLOAD AND CROSS MODULATION.

The exclusive front end design in the receiver allows you to operate closer in frequency to strong neighboring signals than you have ever experienced before. If you have not yet operated an Atlas transceiver in a crowded band and compared it with any other receiver or transceiver, you have a real thrill coming.

ATLAS TRANSCEIVERS

Model 210x or 215x Transceiver \$679
With noise blanker installed \$719

ACCESSORIES

AC Console 110/220V \$149
With VOX \$195
Portable AC Supply 110/220V \$100
Plug-in Mobile Kit \$48
Auxiliary VFO Model 206
Includes Digital Dial \$299
Model DD6-B Digital Dial only \$229
10x Osc. less crystals \$59
Matching Transformer MT-1 \$27
Model VX-5M Self-contained VOX \$55

NEW FROM ATLAS

DL 200 Dummy Load
200 watt intermittent or 60 watt continuous power rating. Housed in a compact one quart can \$9
Same Dummy Load as above, but with dual range Wattmeter reading 0 to 50, and 0 to 200 watts. \$24

For complete details see your Atlas dealer, or drop us a card and we'll mail you a brochure with dealer list.



417 Via Del Monte • Oceanside, CA 92054 Phone (714) 433-1983
Special Customer Service Direct Line (714) 433-9591

Season's Greetings from the gang at Atlas

increased flexibility for the MFJ Enterprises CW filters

Simple circuit changes
you can make to the
CWF-2 or CWF-3 filters
to permit rapid changing
of center frequency
or bandwidth or both

Perhaps the most popular active audio filters used to improve CW reception are those manufactured by MFJ Enterprises.* The CWF-2 model is an 8-pole filter with selectable fixed bandwidths of 80, 110, and 180 Hz around a center frequency of 750 Hz, as shown in fig. 1. MFJ's other filter, the CWF-3, is a smaller version of the CWF-2, providing a 4-pole filter with 110 and 180 Hz bandwidths.

After using the CWF-2 unit for awhile, I wanted to vary the filter center frequency and bandwidth independently to suit my own preferences. In addition, an article by W6AGW outlined the minimum criteria for the filter bandwidth and center frequency as a function of code speed.¹ Although several articles have described the design and construction of CW filters, I decided to

modify my unit rather than build a new one, since the components of the individual stages are already matched to give the same center frequency.

This article describes several modifications that can be made to either the CWF-2 or -3 to permit rapid changing of filter center frequency, bandwidth or both.

basic design

Although W7EIJ² and WA1JSM³ have presented the design steps for such a filter, it is nevertheless worthwhile to briefly summarize their results to better understand what components may be changed. Since each op-amp section (a 2-pole bandpass) is identical to the others, it is only necessary to present the basis for a single stage, as shown in fig. 2, used for Q_s less than 10 to minimize ringing. Calculation of component values begins with the selection of C and the choice of center frequency, f_o ; stage gain, A_o , at the center frequency; and Q , so that

$$R_3 = \frac{Q}{\pi f_o C} \quad (1)$$

$$R_1 = \frac{R_3}{2A_o} \quad (2)$$

$$R_2 = \frac{R_1 R_3}{4Q^2 R_1 - R_3} \quad (3)$$

For the basic filter section, $f_o = 750$ Hz, $A_o = 1.32$, and $Q = 4.24$, so that the input impedance is R_1 . The bandwidth, Δf , is the frequency difference between the upper and lower -3 dB points, or

$$\Delta f = f_h - f_L \quad (4)$$

where

f_h = frequency of the upper -3 dB point

f_L = frequency of the lower -3 dB point

*MFJ Enterprises, P.O. Box 494, Mississippi State, Mississippi 39762

By Howard M. Berlin, K3NEZ, 2 Colony Boulevard, Apartment 123, Wilmington, Delaware 19802

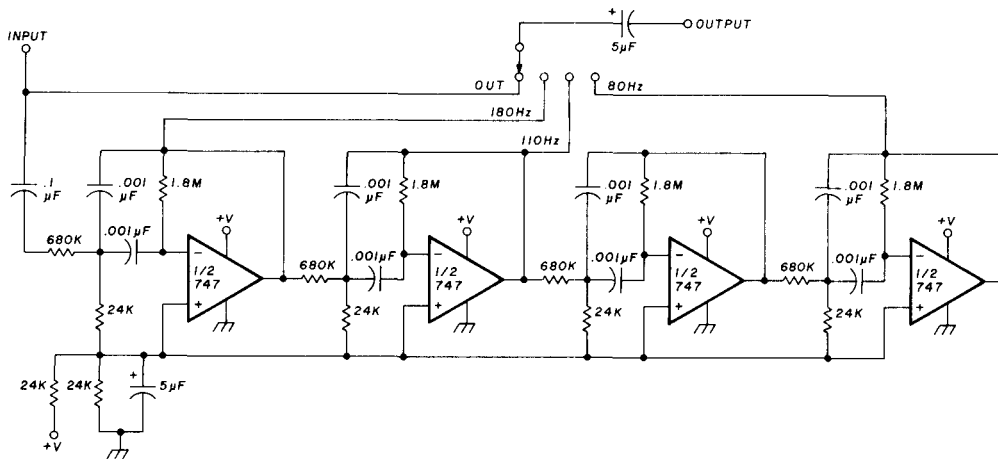


fig. 1. Schematic of the MFJ Enterprises Model CWF-2 CW filter featuring selectable bandwidths of 80, 110, and 180 Hz centered on 750 Hz.

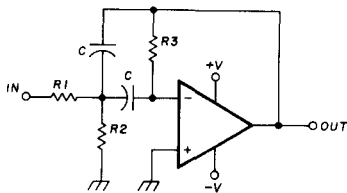


fig. 2. A single-stage, 2-pole bandpass filter section. The calculations of component values for changing filter center frequency and bandwidth are based on this circuit.

The center frequency, in terms of f_h and f_L , is thus

$$f_o = \sqrt{f_h f_L} \quad (5)$$

and

$$Q = \frac{f_o}{\Delta f} = \frac{\sqrt{f_h f_L}}{f_h - f_L} \quad (6)$$

The main disadvantage with the circuit of fig. 2, as well as most op-amp circuits, is the need for a dual-polarity power supply. To permit operation with a single-polarity supply, the circuit shown in fig. 3 is used, with two resistors of equal value for proper biasing. For the MFJ filters 24k resistors are used, and it's only coincidental that they are numerically equal to R2. In fact, other values could have been used for R.

modification 1

From eqs. 1 through 3, it can be shown that the center frequency of the single-stage circuit can be changed to a new frequency, f_o' , without changing A_o or Q by merely changing R_2 to R_2' , so that

$$f_o' = f_o \sqrt{\frac{R_2'}{R_2}} \quad (7)$$

Therefore, by using a dual-element potentiometer with series resistors, each combination being equal to R_2' , it is then possible to smoothly vary the filter center frequency with two fixed bandwidths using the CWF-3 model. With the components shown in fig. 4, the center frequency could be varied from 280 to 1590 Hz with only a 1% variation in either A_o or Q. If the CWF-2 unit is used, a quad-element potentiometer is required for the three selectable bandwidths.

modification 2

If it's desired to smoothly vary the filters bandwidth without varying center frequency, the feedback circuit of fig. 5, as suggested by MFJ, can be used with either unit. Only the first stage (180-Hz bandwidth) is held intact while rewiring one of the other op-amp sections. With the component values shown, it was possible to vary the bandwidth from 75 to 150 Hz at the 750-Hz center frequency. Consequently, the filter Q changed from 5 to 10.

modification 3

This final modification is a combination of the previous two and permits the greatest degree of flexibility. You can now select either fixed bandwidths of 180 and 110 Hz or a variable bandwidth with both bandwidths

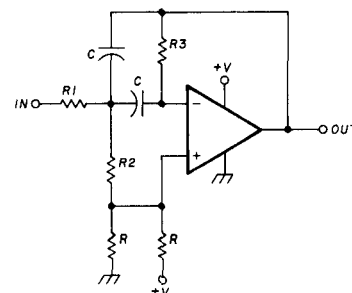


fig. 3. Alternative form of the basic filter stage for use with a single-polarity power supply.

having adjustable center-frequency capability. Using the CWF-2 unit the first two sections are untouched, while one of the remaining op-amp sections is changed. The final circuit is shown in fig. 6.

helpful hints

When soldering on the MFJ printed circuit board, be extremely careful not to overheat the copper laminate, otherwise the copper will separate from the board.

As pointed out by Lancaster in his recently published *Active Filter Cookbook*,⁴ ordinary multiple-element potentiometers, particularly the snap-together types,

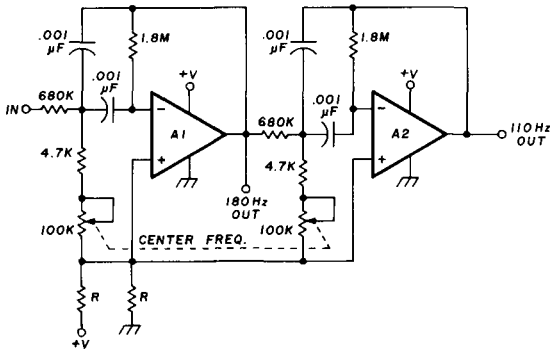


fig. 4. Schematic of the variable center frequency filter with fixed bandwidth. A variation between 280-1590 Hz of center frequency is possible with the two 100-k pots.

have problems. The first is that the resistance behavior is very uncertain at the extremes of pot rotation, since the electrical rotation is somewhat shorter than the mechanical rotation. Also, tracking between the elements should be 5 percent or better.

One inconvenience is linearity; that is, a linear center frequency vs pot rotation change. This is also a problem

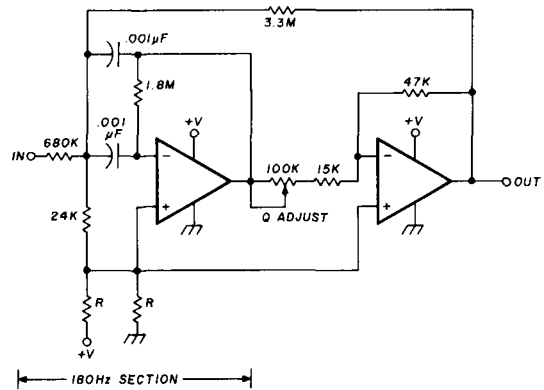


fig. 5. Circuit for varying the MFJ filter bandwidth without varying center frequency. The 180-Hz section is kept intact; the other section is changed as shown to provide bandwidth variation between 75-150 Hz at the 750-Hz center frequency. Filter Q is thus changed from 5 to 10.


with most integrated-circuit keyers.⁵ If a linear taper pot is used, the center frequency will change drastically at one end with very little pot rotation. A reverse-log taper should be used for best results; however, multiple-element reverse-log types are both hard to find and expensive.

references

1. A.F. Stahler, W6AGX, "Optimum CW Filter Design," *73*, December, 1973, page 107.
2. Don Kesner, W7EIJ, "An Introduction to Active Filters," *CQ*, April, 1975, page 32.
3. N.J. Nicosia, WA1JSM, "A Tunable Audio Filter for CW," *ham radio*, August, 1970, page 34.
4. D. Lancaster, *Active Filter Cookbook*, Howard W. Sams & Co. Inc., 1975.
5. H.M. Berlin, K3NEZ, "RAM Keyer Update," *ham radio*, January, 1976, page 60.

ham radio

fig. 6. The CWF-2 filter incorporating modifications to permit the greatest degree of flexibility. Circuit features either fixed bandwidths of 180 and 110 Hz or optional variable bandwidth with adjustable center frequency.

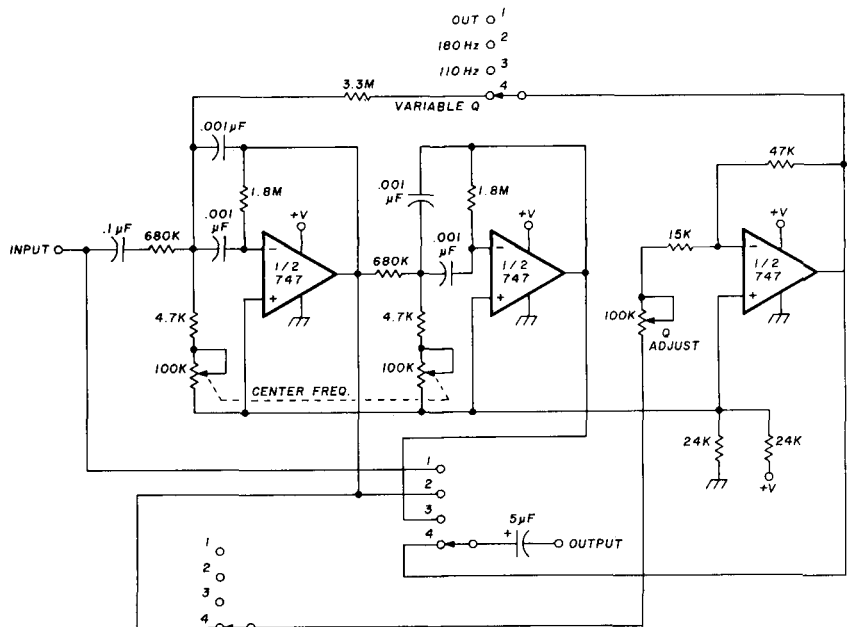

if the 4-BTV weighs 39% more... what do others leave out?

HUSTLER FIXED STATION FOUR BAND VERTICAL

The 4-BTV is longer for greater aperture, larger in diameter for strength and bandwidth, heavier traps for precision and safety factor. Individually, each subassembly weighs more to collectively give you an antenna designed for convenience of assembly and installation, a wide margin in mechanical stability and far superior electrical performance.

- **Lowest SWR—PLUS!**
 - Bandwidth at its **broadest!** SWR 1.6 to 1 or better at band edges.
 - Hustler exclusive trap covers "Spritz" extruded to otherwise unattainable close tolerances assuring accurate and permanent trap resonance.
 - Solid one inch **fiberglass trap forms** for optimum electrical and mechanical stability.
 - Extra heavy duty aluminum mounting bracket with **low loss—high strength** insulators.
 - All sections **1 1/4" heavy wall**, high strength aluminum. Length 21'5".
 - **Stainless steel clamps** permitting adjustment
- without damage to the aluminum tubing.
 - Guaranteed to be **easiest assembly** of any multi-band vertical.
 - Antenna has **3/8"-24 stud** at top to accept RM-75 or RM-75-S Hustler resonator for **75 meter operation** when desired.
 - Top loading on 75 meters for broader bandwidth and **higher radiation efficiency!**
 - Feed with **any length** 50 ohm coax.
 - Power capability—**full legal limit** on SSB and CW.
 - Ground mount with or without radials; roof mount with radials.

one setting for total band coverage! 40 THROUGH 10 METERS

HUSTLER ANTENNA PRODUCTS—for sixteen years—original designs—created and manufactured by American ingenuity, labor and materials—used by communicators throughout the world.

Hustler designs are patented under one or more of the following assigned to New-Tronics Corporation: 3287732, 3513472, 3419869, 3873985, 3327311, 3599214, 3582951


HUSTLER

Available from all distributors
who recognize the best!

MODEL
4-BTV
15 POUNDS

new-tronics corporation

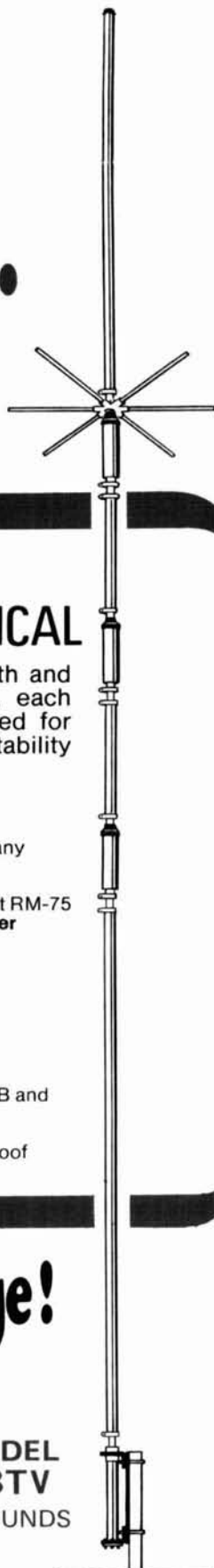15800 commerce park drive,
brook park, ohio 44142
Exporter: Roburn Agencies, Inc., New York, N. Y.



RTTY performance

and signal-to-noise ratio

A good case is presented for using low-frequency shift in amateur RTTY systems

Although most RTTY systems on the high-frequency amateur bands use the low-frequency shift of 170 Hz, a few use a shift of 850 Hz. In addition to more mutual interference with CW stations, performance with regard to signal-to-noise ratio (s/n) is not as good with the wider frequency shift. When selective fading is present, the lower-frequency shift will also perform better, as is well known.

The signal-to-noise performance can be shown by using the following formula:

$$\frac{s}{n} = 1.73 \frac{D}{f} \cdot \frac{C}{N} \sqrt{\frac{B}{2f}} \quad (1)$$

where s = signal voltage at output of discriminator and lowpass filter

n = rms noise voltage at output of discriminator and lowpass filter

D = deviation of the carrier from the center to one side (one-half the frequency shift)

f = audio frequency range following the discriminator and lowpass filter

By Leland E. Thompson, K6SR, 14851 Devonshire Avenue, Tustin, California 92680

B = frequency band preceding the limiter (it is assumed that a bandpass filter is used)

C = carrier voltage in frequency-band B before limiter

N = rms noise voltage in band B

Assuming a speed of 60 words per minute, the following values can be placed in eq. 1:

$$B = 250 \text{ Hz}$$

$$f = 28 \text{ Hz}$$

$$D = 85 \text{ Hz (total frequency shift is 170 Hz)}$$

Then $s/n = 31.2 \text{ dB}$ (when C/N is 10 dB).

Threshold in wideband fm systems is considered to exist when C/N is 10 dB. In narrowband systems such as those considered here, the threshold is not as sharply defined, and good performance can be obtained with this ratio several dB lower. The s/n of 31.2 dB is 11 or 12 dB more than necessary for satisfactory performance.

The following values can be used in eq. 1 for wide-shift systems:

$$B = 850 \text{ Hz}$$

$$f = 28 \text{ Hz}$$

$$D = 425 \text{ Hz (850 Hz total shift)}$$

The $s/n = 50.2 \text{ dB}$ (when C/N is 10 dB). This value of s/n is far higher than necessary, and it decreases fast as C/N drops below 10 dB. Since N is 5.3 dB higher because of the wider frequency band, C must also be 5 dB higher. With a fading signal, the wideband system will start producing errors before the narrow system will.

Although there may be a slight advantage in reducing the shift below 170 Hz, band B would have to be reduced by using a narrower filter, and stability would then become more of a problem.

Equal performance should be obtained with the phase-locked RTTY terminal unit described by Webb.^{1,2} In this case, band B is determined by the phase-locked-loop bandwidth and f is determined by the low-pass filter, as in the previous system.

references

1. P. Edward Webb, W4FQM, "A Phase-Locked Loop RTTY Terminal Unit," *ham radio*, January, 1972, page 8.
2. P. Edward Webb, W4FQM, "Optimization of the Phase-Locked RTTY Terminal Unit," *ham radio*, September, 1975, page 22.

ham radio

DON'T BROADCAST THE FACT THAT YOU'VE GOT A HAM RIG.



Now you don't have to let everyone know that you've got a mobile ham transceiver. Our model ASPR798 gain disguise antenna looks and acts just like a normal Ford antenna, operating on AM and FM broadcast* as well as the 2 meter band. We know the disguise is effective because we've been making them for law enforcement agencies for years. Antenna Specialists has an entire line of disguise antennas to prevent the theft of your VHF FM rig. Exact replacements for Chrysler and Ford products and universal mounts for everything else on wheels.

When it comes to choosing the right amateur antenna, don't settle for less than the best. Look for the Stripes of Quality. At your Antenna Specialists Dealer.

*When used with corresponding antenna coupler.



® Stripes of Quality

the antenna specialists co.

a member of The Allen Group Inc.
12435 Euclid Avenue, Cleveland, Ohio 44106
Export: 2200 Shames Drive, Westbury, L.I. New York 11590
Canada: A. C. Simmonds & Sons, Ltd.

© 1976 by The Antenna Specialists Co





New!

SOTA

"STATE - OF - THE - ART"

SSB

TRANSCEIVERS

\$395⁰⁰

MADE IN U.S.A.
SIZE: 3½ x 7 x 8½

MOBILE MONOBANDERS

MODEL 160	1.8 – 2.0 MHz.	LSB
MODEL 80	3.5 – 4.0 MHz.	LSB
MODEL 40	7.0 – 7.3 MHz.	LSB
MODEL 20	14.0 – 14.35 MHz.	USB

COMPLETELY SOLID STATE • Mosfet mixers for excellent I.M. and cross modulation performance. J-Fet oscillators for stability. I.C.'s used in digital frequency counter, balanced modulator, receiver I.F. amplifier, and audio output for functional simplicity. No relays.

DIGITAL DIAL • Frequency can be read at a glance. 0.3 inch L.E.D. displays are easily visible. Frequency counter offers 100 Hz. accuracy.

SPEECH COMPRESSOR • Increases average output power approximately 6 db. Level set by mic control.

NOISE BLANKER • Noise pulses are blanked ahead of the crystal filter for optimum reduction of interference.

100 WATTS INPUT • P.E.P. or C.W. 50 watts output (minimum).

BROADBAND OUTPUT • Infinite VSWR protection. Multiple pi-section low-pass filter for minimum spurious output.

RECEIVER FRONT END DESIGN • AGC controlled pin diode R.F. attenuator for low distortion large signal handling capabilities. Triple tuned preselector offers superior R.F. selectivity.

QUALITY CONSTRUCTION • Utilizing glass epoxy P.C. boards and commercial grade components. All electrical connections soldered for reliability. P.C. boards accessible for easy servicing.

STANDARD ACCESSORIES • Mobile mounting bracket and power connector with 8 foot battery cable are supplied with unit.

WARRANTY • Full one year warranty on all parts and workmanship with exception to damage incurred by abuse. Our customer service offers one week turnaround time on repairs.

SPECIFICATIONS

GENERAL

MODES: S.S.B. and C.W. with Sidetone
POWER REQUIREMENTS: 12-14 volts D.C. negative ground only. 12 amps maximum. Reverse polarity protection.
WEIGHT: 5.4 lbs.

RECEIVER

SENSITIVITY: Less than 0.5 microvolt for 15 db. signal-plus-noise/noise ratio.
SELECTIVITY: 2.1 KHz @ -6 db., 3.8 KHz @ -60 db.
IMAGE REJECTION: Better than 60 db.
AUDIO OUTPUT: 2 Watts at less than 5% distortion into 4 ohm load.

TRANSMITTER

POWER INPUT: 100 watts P.E.P. or C.W., nominal.
POWER OUTPUT: 50 Watts P.E.P. or C.W., minimum.
OUTPUT IMPEDANCE: 52 ohms, nominal.
UNWANTED SIDEBAND: -40 db or better.
CARRIER SUPPRESSION: -60 db or better.
THIRD ORDER DISTORTION: -30 db. or better.
SPURIOUS OUTPUTS: -30 db or better.
AUDIO RESPONSE: 400 to 2,500 Hz., ± 2 db.
MIC INPUT: High impedance dynamic or crystal microphone.

EXTERNAL AMPLIFIER CONTROL: Open collector to 100 volts @ 1 amp., maximum.

OPTIONAL ACCESSORIES:

MODEL MMB-1

Plug-in mobile mounting bracket making all connections to the transceiver at once, providing quick and easy installation or removal from the car.
Price \$45.00

MODEL PS-1

Matching A.C. power supply with built-in speaker. Supplies 13.8 VDC regulated at 12 amps. maximum. 110/220 VAC, 50-60 Hz. Price \$125.00

ORDERING INFORMATION:

All Prices F.O.B. factory plus shipping. California residents add 6% sales tax. To order now, send a deposit (\$25.00 minimum) to secure a delivery position. Fully refundable at any time. Payment in full required prior to shipment.

SOTA

Industries

308 ENCINAL STREET
SANTA CRUZ, CA. 95060
TELEPHONE: (408) 426-8161



DIGITAL DATA RECORDER

for Computer or Teletype Use

Up to 4800 Baud

Uses the industry standard tape saturation (NRZ) method to beat all FSK systems ten to one. No modems or FSK decoders required. Loads 8K of memory in 17 seconds. This recorder enables you to back up your computer by loading and dumping programs and data fast as you go, thus enabling you to get by with less memory. Great for small business bookkeeping. Imagine! A year's books on one cassette.

Can be software controlled. Comes complete with a software program used to test the units in production (8080). Manual includes software control hook up data and programs for 8080 and 6800.



SPECIFICATIONS — MODEL CC7:

- A. Recording Mode: Tape saturation binary (NRZ). This is not an FSK or Home type recorder. No voice capability. No Modem. Runs at 2400 baud or less Asynchronous and 4800 baud Synchronous. Runs at 3.1"/sec. Speed mechanically regulated $\pm .5\%$ or better.
- B. Two channels (1) Clock, (2) Data. Or two data channels providing four (4) tracks on the cassette. Can also be used for Bi-Phase, Manchester, etc.
- C. Inputs: Two (2). Will accept TTY, TTL or RS 232 digital.
- D. Outputs: Two (2). Board changeable from TTY, RS232 or TTL digital.
- E. Erase: Erases while recording one track at a time. Record new data on one track and preserve three or record on two and preserve two.
- F. Compatibility: Will interface any computer using a UART or ACIA board. (Altair, Sphere, IMSAI, M6800, etc.)
- G. Other Data: 110-220 V - (50-60) Hz; 3 Watts total; UL listed; three wire line cord; on/off switch; audio, meter and light operation monitors. Remote control of motor optional. Four foot, seven conductor remoting cable provided.
- H. Warrantee: 90 days. All units tested at 300 and 2400 baud before shipment. Test cassette with 8080 software program included.

Also available — MODEL CC7A with variable motor speed which is electronically regulated. Runs 4800 baud Synchronous or Asynchronous. Recommended for quantity users who require tape interchangeability. Comes with speed calibration tape to set exact speed against 60 cycle line.

\$169.95

NEW — 8080 I/O BOARD with ROM

Permanent Relief from "Bootstrap Chafing" This is our new "turnkey" board. Turn on your Altair or Imsai and go (No Bootstrapping). Controls one terminal (CRT or TTY) and one or two cassettes with all programs in ROM. Enables you to turn on and just type in what you want done. Loads, Dumps, Examines, Modifies from the keyboard in Hex. Loads Octal. For the cassettes, it is a fully software controlled Load and Dump at the touch of a key. Even loads MITS Basic. Ends "Bootstrap Chafe" forever. Uses 512 bytes of ROM, one UART for the terminal and one USART for the Cassettes. Our orders are backing up on this one. #2SIO (R)

Kit form \$140.00

Fully assembled and tested \$170.00

Fill out form and send check or money

Mailing Label — PRINT

NATIONAL MULTIPLEX CORPORATION


3474 Rand Avenue, Box 288
South Plainfield, New Jersey 07080
SHIP TO:

201-561-3600

CARD NO. _____ ZIP _____
EXPIRATION DATE _____

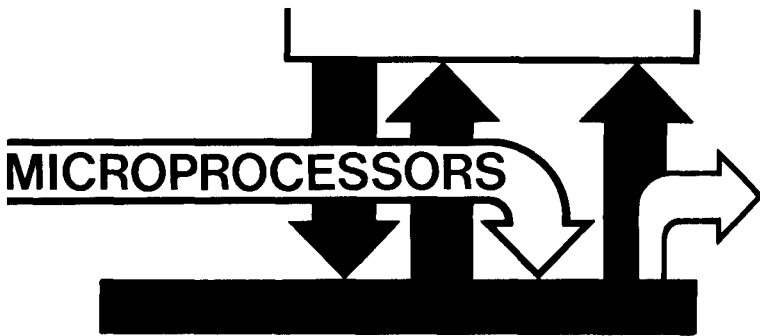..... Data Recorder CC-7 @ \$149.95
..... Data Recorder CC-7A @ \$169.95
Please enclose \$2.00 Shipping & Handling
on each Recorder or I/O Board.
..... Operating & Technical Manual
(Schematics) Includes Software
& Hookups for 8080, 6800, and
I/O. \$2.00
N. J. Residents add
5% Sales Tax





microcomputer interrupts

This month's column is the first of several that will focus upon the concept of an *interrupt*. When used in the context of a computer, an interrupt can be defined as the suspension of normal program execution in order to handle a sudden request for *service*, i.e., assistance, by the computer. At the completion of interrupt service, the computer resumes the interrupted program from the point where it was interrupted.¹ This specific use of interrupt is consistent with the general meaning of the term: to stop a process in such a way that it can be resumed.

A given computer will typically communicate with a variety of external I/O "devices." If a minicomputer is used, it may communicate with a teletype or alphanumeric keyboard, a CRT display, a printer, a floppy disk, and perhaps one or more laboratory instruments. If it is a microcomputer, it may communicate with smaller devices — (motors, solid-state relays, push-button switches, display lights) within a larger machine or instrument. When used as a replacement for discrete logic devices in a complex digital circuit, a microcomputer may communicate with other TTL integrated circuit chips such as latches, flip-flops, and three-state buffers.

When communicating with external I/O devices,² microcomputers can operate in two general modes, *polled* and *interrupt*. Polling is the periodic interrogation of each I/O device that shares a communications link to a microcomputer to determine whether it requires servicing. A microcomputer sends a poll that has the effect of asking the selected device, "Do you have anything to transmit?", "Are you ready to receive data?", and similar questions. When a microcomputer services a polled device, it simply exchanges digital information with the device in a manner that is prescribed by software in a subprogram or subroutine called a *software driver*.

By Peter R. Rony, Jonathan A. Titus, and David G. Larsen, WB4HYJ

Mr. Larsen, Department of Chemistry, and Dr. Rony, Department of Chemical Engineering, are with the Virginia Polytechnic Institute and State University, Blacksburg, Virginia. Mr. Jonathan Titus is President of Tychon Inc., Blacksburg, Virginia.

In a polled operation, the microcomputer sequences through the devices tied to the microcomputer, looking for individual devices that need servicing. When it finds a device that requires service, sequencing stops and a software driver services the device. Once it is finished, the microcomputer continues checking the devices. Polled operation is most useful with relatively slow devices that do not require frequent service, do not require attention from the microcomputer for excessive periods of time, or can wait to be serviced. Advantage is taken of the difference in speed of operations in the microcomputer and operations in the I/O device. Most common I/O devices are much slower than microcomputers. For example, in 100 ms (teletypewriter response time) an 8080A-based microcomputer can execute approximately 20,000 instructions when operated at a clock rate of 2 MHz. Although a microcomputer may give you the impression that it is doing several things simultaneously, this is only an illusion since it can manipulate data much faster than most I/O devices can respond to changes in data. *A single computer can perform only one task at a time.*

In interrupt operation, the microcomputer juggles the demands of the external I/O devices. There is a distinction between slow devices that require infrequent servicing and high-speed devices that demand the attention of the microcomputer for most of the time. The most appropriate description for interrupt operated systems is that they are *asynchronous*, i.e. they lack a common synchronizing signal and therefore give rise to generally unexpected or unpredictable program execution within the microcomputer. An *asynchronous device* is a device in which the speed of operation is not related to any frequency in the system to which it is connected.³ The use of asynchronous devices is the rule rather than the exception.

There can exist *priority* in interrupt operation. All I/O devices can be ordered in importance so that some devices take precedence over others. In contrast, there is usually no priority in polled operation. Once a device is serviced, it waits its turn until all other devices are sequenced and, if necessary, also serviced. The time between the interrupt request by a device and the first instruction byte of the software that services it is known as the *interrupt response time*. For a high-speed device that has high priority, the response time can be very short, less than a millisecond. For a low-speed device that has low priority, the response time is variable, since it depends upon the demands placed upon the microcomputer by all higher priority devices.

Three commonly used microcomputer interrupt techniques are the *single-line interrupt*, the *multilevel interrupt*, and the *vectored interrupt* (fig. 1). In the

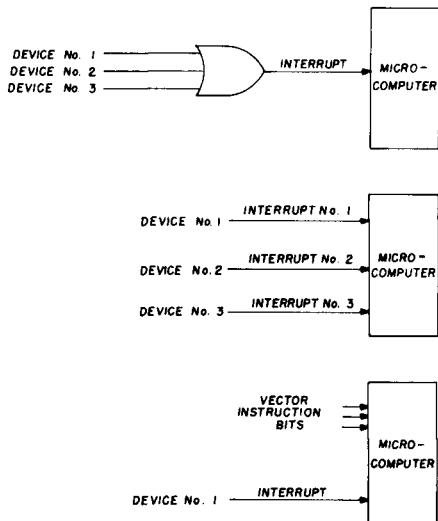


fig. 1. Schematic diagram of three different interrupt techniques, the polled interrupt (top), multilevel interrupt (middle), and vectored interrupt (bottom).

single-line interrupt technique, multiple devices must be OR connected to a single interrupt line to the microcomputer. Once an interrupt signal is received, all of the interrupt devices are polled to determine which one caused the interrupt. It is possible to assign software priorities to the various interrupting devices, so that the first device polled that needs service is the one that receives the attention of the microcomputer. A common term used for the part of a program that polls interrupt devices is a *flag checking routine*. We shall discuss the concept of a flag in a subsequent column. At the moment, consider a flag to be a single-bit memory that indicates when an operation has been completed or when a condition has been attained.

In the multilevel interrupt technique, there are several interrupt lines to the microcomputer, each line being tied to a separate I/O device flag. The microcomputer does not need to poll the devices to determine which one caused the interrupt. This is done internally within the microprocessor chip. Depending upon the nature of the microprocessor chip, this can be a very fast interrupt technique, but it is somewhat difficult to expand.

vectored interrupt

A vectored interrupt causes a direct branch by the microcomputer to that part of the program that services the interrupt. This interrupt technique requires external integrated-circuit chips to supply the memory address of the *interrupt service routine* as well as to set the priority. With the 8080A microprocessor chip, eight different service routine addresses can be readily specified, although one of these addresses coincides with the reset address for the microprocessor, location zero. If you are interested in vectored interrupts, we encourage you to

Reprinted with permission from *American Laboratory*, July, 1976, copyright © International Scientific Communications, Inc., Fairfield, Connecticut 1976.

consider the Intel 8259 programmable interrupt controller, which became available commercially in July, 1976.

The use of interrupts should be considered very carefully. More complicated software is invariably required. For example, you will generally have to save the status of the microprocessor chip at the time that the interrupt occurred. This means placing the contents of the accumulator, the flags, and the registers into a specified region of memory from which they can be retrieved at a later time, after the interrupting device has been serviced. Pay attention to priorities. Make certain that devices that require high priority and need immediate servicing are given the highest priority. Other devices, such as teletypes, should be low priority. Also, if you attempt to do too much with an interrupt system, you might find that your microcomputer becomes "interrupt bound," which means that the microcomputer is only working on the main task, which it should be doing while only infrequently servicing interrupt requests.

To end this column, we would like to provide one example of an interrupt system. Assume that your microcomputer is performing mathematical computations on 7-bit ASCII numbers that are entered via a UAR/T chip⁴ that is connected to a Teletype operated at 110 Baud, or ten ASCII numbers per second. The exchange of data between the microcomputer and the UAR/T can be performed in 20 to 30 microseconds, which leaves 99.97 ms left for the microcomputer to do other things. With the Intel floating point package, for example, each floating-point multiplication or division can be performed in 2 to 5 ms with an 8080A-based microcomputer operating at 2 MHz. Sixteen-bit binary multiplications and divisions can be performed even faster. Therefore, it is appropriate for you to consider that the main task of the microcomputer is to perform such computations, and that 0.05 to 0.10 percent of the time the microcomputer can devote its attention to servicing the interrupting teletype. The less attractive alternatives are for the microcomputer to either poll the UAR/T or else to wait for a change of state of the UAR/T data ready or transmitter buffer empty flags.

Interrupts are also effective for use with devices that provide data to a microcomputer but which have no buffer of their own to store it. Existing data must be removed from the device and stored in the microcomputer quickly before a new data word can be generated by the device. One example of such a device is an analog-to-digital converter (ADC) in which the conversions are clocked by an external clock at repetitive time intervals.

references

1. Schweber Electronics, *Microprocessor Buzz Words*, Schweber Electronics Marketing Services, Westbury, New York 11590.
2. D. G. Larsen, P. R. Rony, and J. A. Titus, "What is a Microprocessor Input/Output Device?" *ham radio*, February, 1976, page 50.
3. R. F. Graf, *Modern Dictionary of Electronics*, Howard W. Sams & Co., Inc., Indianapolis, 1972.
4. J. A. Titus, "The Universal Asynchronous Receiver/Transmitter (UAR/T), and How it Works," *ham radio*, February, 1976, page 58.

ham radio



NEW products

antenna mount thrust bearing



Unarco-Rohn has just introduced a new thrust bearing (TB-3) for mounting antennas. Manufactured from heat-treated cast aluminum for extra strength, the TB-3 incorporates 30 stainless-steel ball bearings in a race that is protected from the elements and permits free movement at all times. Three lock-nuts fasten the antenna mast securely to the thrust bearing, relieving the weight of the antenna on the rotor and allowing an exceptionally free turning movement.

For additional information, write Rohn Products Advertising Agency, Box 2000, Peoria, Illinois 61601 or use *check-off* on page 142.

low- and medium frequency radio scrapbook

Ken Cornell's new scrapbook fills a huge gap with good, basic, hard-core information. The gap? That range of radio frequencies extending from the bottom of the broadcast band down to about 10 kHz — nearly audio!

There's another gap, too: a gap in knowledge and information about regulations, communications capabilities, equipment, and "personalities" of those bands below the broadcast.

To all but a mere handful of dedicated experimenters such as Ken and his fellow "LFers," the low and medium frequencies today are nearly as much of a "no-man's band" as they were 50 years ago. *The Low- and Medium-Frequency Scrapbook* not only bridges that gap, but tends to fill it with circuits for practical receivers, transmitters, converters, antennas, and neat little doodads that you will find indispensable for your experiments.

Like any good scrapbook, this one presents the material in such a way that you can find what you need in chapters about communications bands where no license is needed, about coils and coil-winding techniques, and many other comparable "goodies." Tables, charts, nomographs and schematic diagrams are liberally sprinkled throughout its pages.

Even better, the pages are loose-leaf and already punched for three-ring binders so that your scrapbook can be a growing, personal and up-to-date source reference with pages of your own experiments and results added where appropriate. You need this book! Soft cover, 114 pages, \$6.95. With custom loose-leaf binder, \$8.95. Order from Ham Radio Books, Greenville, New Hampshire 03048.

binaural synthesizer for audio signals



Hildreth Engineering Company announces its new Binaural Synthesizer, a device for producing a stereo audio output from a monaural audio input.

The synthesizer may be plugged into the headphone or speaker jack of a receiver or other monaural audio signal source and provides outputs for stereo headphones, power amplifiers, or speakers.

The model 400 Binaural Synthesizer is available as a complete unit (less batteries) for \$29.95, as a partially assembled unit including an assembled and tested PC board for \$17.95, or as a kit which includes a predrilled, plated, glass-epoxy PC board with instructions for \$6.95. All prices postpaid.

The model 400 provides a sharp 24 dB per octave channel separation, four poles in each channel, for a good stereo effect. The unit employs 741 integrated-circuit op amps rather than multiple units for simple, easy-to-find attachment points. The PC board contains extra traces for resistor trimming, if desired. The cross-over frequency is 750 \pm 50 hertz, input impedance is 2000 ohms, and the unit may be powered from any supply that will provide negative or positive voltage between 4 and 15 volts dc. In operation, the synthesizer typically draws 5 to 10 milliamperes.

Additional information may be obtained by writing to Hildreth Engineering Company, Post Office Box 3, Sunnyvale, California 94088, or by using the *check-off* on page 142.

utility case for test instruments

Continental Specialties Corporation (New Products, July, 1976, *ham radio*) makes available to the custom designer a matching blank utility case that will accommodate CSC's line of test instruments. The DM-C *Design Your Own Mate* case is molded from flame-retardant ABS plastic which can be easily drilled, routed, sawed, filed, or reamed. The blank box incorporates a bottom plate with mounting screws and features a sloping front panel which allows easy custom design and provides a modern, utilitarian appearance. The DM-C is 6.75 inches (17.2cm) long, 7.5 inches (19cm) wide and 3.25 inches (8.3cm) high with a nominal wall thick-

Introducing the 2-meter hand-held that gives you high performance. Without high cost.

It's the new Hy-Gain 3806 2-meter, 6-channel hand-held FM transceiver (144-148 MHz). The 2-meter hand-held that takes the high cost out of performance.

The Hy-Gain 3806 is built to out-perform. Out-last. And out-class every other 2-meter hand-held.

It's built tough. Water, dirt and corrosion are sealed out by the specially gasketed case. The speaker/microphone grill is engineered to prevent direct entrance by water. Even changing the power pack in the field won't diminish case integrity. The power section is separately sealed. So you never expose the circuitry.

The high-impact ABS case is extra tough. And ribbed for a sure, non-slip grip. The controls are up front. And easy to operate. There's volume. Squelch. 6-position channel selector. Transmit LED indicator. A meter that indicates battery condition on transmit, signal strength on receive. And a separate power switch for positive on-off.

There's a telescoping antenna that collapses completely into the case. Or you can use our 269 flexible antenna for extra convenience. And there are jacks for use with external antenna. Earphone. And external 12 VDC.

The 3806 has the kind of guts that have made Hy-Gain products famous throughout the world. Its receiver section is superior



to everything else for the money. It has sharply tuned, on-frequency selectivity in the RF amplifier circuit. Two MOS-FET RF amplifier stages. Plus MOS-FET's in the 1st and 2nd mixers. They make the 3806 virtually immune to out-of-band signals. Intermodulation distortion. And cross-modulation. So you get truly incredible

dynamic range. For superb adjacent channel rejection, the 1st mixer is followed by a monolithic crystal filter. And the 2nd mixer by an 8-pole ceramic filter.

A frequency multiplication factor of 12 allows you to use thicker, high stability crystals (one set of 146.52 simplex crystals supplied). Audio is enhanced through use of separate speaker and microphone elements. And there's an internally adjustable mic preamp. Something you won't find anywhere else.

The Hy-Gain 3806 hand-held is backed by a complete line of superb accessories. Including AC and DC chargers. Carrying case. External antenna adapter cable. And a Nicad power pack that's so over-engineered you won't over-extend it. Even in the most adverse conditions.

The pack is completely sealed in its own tough ABS case. Protected against over-charging. And contact shorting. It has 30-40% more in-use capacity than competitive units.

Soon we'll have a Touch-Tone™ pad available for the 3806. It'll fit flush in the back panel. Because we designed it specifically for the 3806.

The Hy-Gain 3806 2-meter, 6-channel FM hand-held. It gives you the performance you want. Without costing a lot. Available locally through your Hy-Gain dealer. See it and our more than 300 other fine products soon.

hy-gain
We keep people talking.

Hy-Gain Electronics Corporation 8601 Northeast Highway Six; Lincoln, NE 68505

ramsey electronics



new mobile clock kit \$25.95

6 Digit .33" LED - 12 or 24 Hour

Here's a completely self-contained handsome digital clock for any 12 volt dc application. Small size (4 1/4"x2"x2") and rugged extruded aluminum case makes this clock ideal for mobile usage. Unique features such as ceramic resonator .01% accuracy, Polaroid lens filter and display blanking contribute to the value of this kit.

Colors available: Black, Gold, Silver, Bronze, Blue (specify)

110 Volt Version (uses 60 Hz line) \$22.95
 110 Volt Alarm (12 HR only) \$24.95
 Time base only (use with any clock) \$4.95

FM WIRELESS MIKE KIT

Transmit up to 300' to any FM broadcast radio. Sensitive mic. input requires crystal, ceramic or dynamic mike. Runs on 3 to 9V. Small one inch square size.
Complete Kit \$2.95

LED BLINKY KIT

A great attention getter which alternately flashes 2 Jumbo LEDs. Use for name badges, buttons, or warning type panel lights. Runs on 3 to 9 volts.
Complete Kit \$2.95

SIREN KIT

Produces police-type wail of siren at toy volume. Runs speaker from 3-45 Ohms to 200 mW output. Requires power source of 3 to 6 volts. A neat toy for the kids.
Complete Kit \$2.95

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with most any counter. Completely assembled and tested. Choice of ± 10 or ± 100 , specify with order.
\$59.95



POWER SUPPLY KIT ± 15 V, +5 V

A complete bench supply! Dual tracking regulator provides adjustable ± 6 to 15 Volts at 100 mA, while a stable 3 terminal regulator produces 5 V at 1 Amp. Novel 2 transformer design permits 110/220 V operation. Complete with all parts except case and cord.
PS-3 Power Supply Kit \$14.95

TRANSFORMER SALE

LINE CORD TYPE

12 V ac 175 mA
 short cord (6-10") ... 99¢
 long cord (72") \$1.69



PC LUG MOUNT 10V, 400mA
 ideal for home brew clocks \$1.49

5 VOLT REGULATORS

Both feature: 7 to 30 V input range, thermal shutdown and short circuit protection.

7805/340-5 98¢
 1 Amp T0-220
 LM-309K.....\$1.19
 1 Amp T0-3

741 OP-AMP SPECIAL 10 for \$2.00

Take advantage of a special one time deal on factory prime mini-dip op-amps. These were house numbered for Xerox Corp., but also have the 741 number printed on them. This is the LOWEST price in the USA!

DECADE COUNTER \$2.95 PARTS KIT

● 7490A ● CURRENT LIMIT RESISTORS
 ● 7475 ● .43" LED READOUT
 ● 7447 ● HOOK-UP INSTRUCTIONS

LM-567 decoder ... \$1.75
 LM-565 PLL75
 MC-145875
 7490A59
 744785
 74143 3.50
 MC4024VCO 1.95

FERRITE BEADS with info and specs 15/\$1.00
 6 hole Balun beads 5/\$1.00
 SLIDE POT-10 K Linear taper 4/\$1.00
 1000 uF 15 V FILTER CAP 5/\$1.00

ramsey electronics

P.O. Box 4072A, Rochester NY 14610
 SEND 25 ¢ FOR ILLUSTRATED CATALOGUE



48 HOUR SERVICE

Satisfaction guaranteed or money refunded. NO COD. Orders under \$10.00 add \$.75; NY residents add 7% tax.

ness of 0.085 inch (2mm) and sells for only \$5.50. Write Continental Specialties Corporation, 44 Kendall Street, Post Office Box 1942, New Haven, Connecticut 06509, or Box 7809, San Francisco, California 94110, or use check-off on page 142.

range of HP counter extended to vhf and uhf



Designed with the needs of the communications industry in mind, this new Hewlett-Packard Model 5305B Frequency Counter plug-on covers frequency bands from 50 Hz to 1300 MHz. In addition to all mobile communications bands, the counter's range includes TACAN/DME and ATC radar transponders as well as am and fm broadcast bands and vhf and uhf television bands.

The 5305B operates with the 8-digit 5300B mainframe. Sensitivity is 20 millivolts rms in both channels over the full bandwidth. A high resolution mode for tone measurements to 10 kHz improves resolution by 1000. Automatic gain control is included on both channels, plus a manual attenuation control on the high frequency channel.

A first for a counter is a probe power output to drive an accessory preamplifier. The Hewlett-Packard Model 10855A Preamp boosts sensitivity of the counter by 22 dB (x10). Adding an antenna and tunable filter to the preamp lets the user receive "on-the-air" signals for carrier measurements.

U.S. price of the Hewlett-Packard Model 5305B is \$900, the Model 5300B mainframe is \$460, and the Model 10855A Preamp is \$225. Delivery for any of these units is 30 days.

For additional information contact Inquiries Manager, Hewlett-Packard Company, 1501 Page Mill Road, Palo Alto, California 94304; telephone (415) 493-1501, or use check-off on page 142.

KENWOOD

...the Pacesetter in Amateur Radio



**Discover
the luxury
of 4 MHz**

TS-700A

Kenwood's TS-700A offers the ultimate promise of 2-meters... more channels, more versatility, tunable VFO, SSB-CW... and Kenwood quality.

Operates all modes: SSB (upper & lower), FM, AM and CW • Completely solid state circuitry provides stable, long lasting, trouble-free operation • AC and DC capability (operate from your car, boat, or as a base station through its built-in power supply) • 4 MHz band coverage (144 to 148 MHz) • Automatically switches transmit frequency 600 KHz for repeater operation. Simply dial in your receive frequency and the radio does the rest... simplex repeater reverse • Or accomplish the same by plugging a single crystal into one of the 11 crystal positions for your favorite channel • Transmit/Receive capability on 44 channels with 11 crystals.



TR-7400A NEW...AVAILABLE IN DECEMBER

KENWOOD'S EXCITING NEW 2-METER MOBILE TRANSCEIVER •
All solid state • Synthesized phase lock loop (PLL) • Power output: 25 or 10 watts (high or low selectable) • 6 digit LED frequency display • Full coverage 144-148 MHz, 800 channels in 5 KHz steps • 600 KHz repeater offset • Continuous tone-coded squelch (CTCS) for transmit and receive or transmit only with tone elements optional • Tone burst (tone elements optional) • Kenwood dependability and value built in.

TR-2200A

Kenwood's high performance portable 2-meter FM transceiver... completely transistorized, rugged and compact. 12 channel capacity • Telescoping removable antenna • External 12 VDC or internal ni-cad batteries • 146-148 MHz frequency coverage • 6 channels supplied • Battery saving "light off" position • Hi-Lo power switch (2 watts-400mW).



TR-7200A

Kenwood's superb 2-meter FM mobile transceiver. Designed to withstand the most severe punishment while providing consistently excellent performance. Packed with features like the PRIORITY function... Put your favorite crystals in channel 7, and the 7200A switches there with the push of a button... no matter what channel you are on. 146-148 MHz coverage, 22 channels, 6 supplied. Completely solid state.

The perfect companion to the TR-7200A is the PS-5 AC/DC power supply. Together they provide an efficient and handsome base station. Complete with a digital clock and automatic time control feature built in.

KENWOOD'S TS-820 *the Pacesetter*

Kenwood's well deserved reputation for fine craftsmanship and superb performance has never been more evident than in the TS-820. As a result of a host of innovative features being brought together, the 820 offers a degree of versatility, performance and pleasure second to none.

The Kenwood TS-820 is destined to be the world's new standard of excellence in amateur radio for years to come... a true "Pacesetter".



VFO-820

The VFO-820 is a solid state remote VFO designed exclusively for use with the Kenwood TS-820 Pacesetter. The VFO-820 has its own RIT circuit and control switch. It is fully compatible with the optional digital display in the TS-820. The perfect extra to any Pacesetter station.

RF MONITOR • Built-in monitor circuit allows you to hear your own voice by sampling the RF signal. Especially useful for adjusting the RF Processor.

NOISE BLANKER • The TS-820 uses an efficient noise blanker circuit, another Kenwood exclusive. A special crystal filter assures unsurpassed efficiency in eliminating unwanted pulse noises.

DIGITAL HOLD • A single pushbutton switch offers the operator unprecedented versatility. The digital hold circuit will lock the counter and display at any frequency, but will allow the VFO to tune normally. Ever wanted to return to a certain spot on the band and forgotten the frequency? That won't happen again with the new digital hold feature on the Kenwood TS-820.

SPEECH PROCESSOR • An HF circuit provides quick time constant compression using a true RF compressor as opposed to an IF clipper. Amount of compression is adjustable to the desired level by a convenient front panel control.

IF SHIFT • The IF SHIFT control varies the IF passband without changing the receive frequency. This "IF shift" control is located on the front panel and provides excellent unwanted signal reject control or "pass band tuning." The 820 moves the signal across the IF pass band not the pass band across the signal.

RF ATTENUATOR • Easy, one touch activation of the attenuator supplies 20 dB of padding on receive.

VOX • A voice-activated microphone circuit is built into the TS-820 with VOX GAIN, ANTIVOX, and VOX DELAY controls placed on the front panel for convenient adjustment any time.

Features

160 METERS • Full band coverage

PLL • The TS-820 employs the latest phase lock loop circuitry. The single conversion receiver section performance offers superb protection against unwanted cross-modulation. And now, PLL allows the frequency to remain the same when switching sidebands (USB, LSB, CW) and eliminates having to recalibrate each time.

RF NEGATIVE FEEDBACK • The linearity of the TS-820's final amplifier stage is now one of the best on the air. Third order intermodulation products are 35 db or greater below the output signal. RF Negative Feedback from the PA plate circuit to the driver cathode permits a high degree of linearity at the high power level of the final tubes.

FULL METERING • During receive, an easy to read meter functions as an S-meter. The same meter displays ALC level, plate current, RF output, and plate voltage during transmit. Includes COMP setting for adjusting the compression level of the built-in speech processor.

FINAL AMPLIFIER • The TS-820 is completely solid state except for the driver (12BY7A) and the final tubes. Rather than substitute TV sweep tubes as final amplifier tubes in a state of the art amateur transceiver, Kenwood has employed two husky S-2001A (equivalent to 6146B) tubes. These rugged, time-proven tubes are known for their long life and superb linearity. The input power of the TS-820 is conservatively rated at 160 W DC, 200 W PEP. Tubes run cool with the aid of a noiseless fan (standard) mounted on the rear panel. The above tube and power combination minimizes the possibilities of TVI and helps to maintain the Kenwood reputation for excellent audio quality.

DIGITAL READOUT DG-1 • (optional) A digital counter display can be employed as an integral part of the VFO readout system. Counter mixes the carrier, VFO, and first heterodyne frequencies to give exact frequency. Figures the frequency down to 10 Hz and digital display reads out to 100 Hz. Both receive and transmit frequencies are displayed in easy to read, Kenwood Blue digits.

DRS DIAL • Includes the same satin-smooth planetary drive found on other fine Kenwood models plus special, high-precision gears to add a new "monoscale" feature for easier frequency readout. LSB, USB, and CW operating frequencies can be accurately read from the same pointer.

HEATER SWITCH • The filaments of the three vacuum tubes may be turned off during periods of "receive only".

CW AUDIO CHARACTERISTICS • During CW reception, a special filter is used to alter the audio frequency response to provide a more comfortable, easy to copy tone.

HIGH STABILITY VFO • The VFO, heart of any SSB transceiver, is an exclusive Kenwood design using FET technology.

Other features include:

- Built-in 25 kHz calibrator*
- Built-in speaker*
- CW Sidetone and semi-break in*
- Rear panel terminals for linear amplifier, IF OUT, RTTY, and XVTR.
- Handy phone patch IN and OUT terminals



the TS-520

Why wait any longer for a rig that offers top performance, dependability and versatility... the TS-520 has proven itself in the shacks of thousands of discriminating amateurs, in field day sites, in DX and contest stations, and in countless mobile installations. Superb craftsmanship is evident throughout... in its engineering concepts as well as its construction and styling... craftsmanship that is a Kenwood hallmark.

Maybe the Kenwood TS-520 is the one you have been waiting for.



*Fine accessories
designed to increase
the versatility of your*

TS-520

SP-520

The SP-520 is an external speaker designed for use with the Kenwood TS-520. The SP-520 can be used in place of the transceiver's built-in speaker for better readability. The speaker's cabinet matches the TS-520 front panel to provide a clean looking integrated station.

VFO-520

The VFO-520 is a solid state remote VFO designed to match the TS-520 perfectly. It allows VFO controlled cross channel operation when connected to the transceiver. A built-in RIT circuit, with an LED indicator, permits receiver incremental tuning.

TV-502

The TV-502 transverter puts you on 2-meters the easy way. Simply plug it in and you're on the air. Operates in the 144.0-145.7 MHz frequency range with a 145.0-146.0 MHz option. The TV-502 is completely compatible with the TS-520 and the TS-820.

KENWOOD'S *"Twins"*



Kenwood developed the T-599D transmitter and R-599D receiver for the most discriminating amateur.

The R-599D is the most complete receiver ever offered. It is entirely solid-state, superbly reliable and compact. It covers the full amateur band, 10 through 160 meters, CW, LSB, USB, AM and FM.

The T-599D is solid-state with the exception of only three tubes, has built-in power supply and full metering. It operates CW, LSB, USB and AM and, of course, is a perfect match to the R-599D receiver.

If you have never considered the advantages of operating a receiver/transmitter combination... maybe you should. Because of the larger number of controls and dual VFOs the combination offers flexibility impossible to duplicate with a transceiver.

Compare the specs of the R-599D and the T-599D with any other brand. Remember, the R-599D is all solid state (and includes four filters). Your choice will obviously be the Kenwood.



*The newest
and best
in world listening*

KENWOOD'S **R-300**

Dependable operation, superior specifications and excellent features make the R-300 an unexcelled value for the shortwave listener. It offers full band coverage with a frequency range of 170 KHz to 30.0 MHz • Receives AM, SSB and CW • Features large, easy to read drum dials with fast smooth dial action • Band spread is calibrated for the 10 foreign broadcast bands, easily tuned with the use of a built in 500 KHz calibrator • Automatic noise limiter • 3-way power supply system (AC/Batteries/External DC)... take it anyplace • Automatically switches to battery power in the event of AC power failure.

HS-4

The Kenwood HS-4 headphone set adds versatility to any Kenwood station. For extended periods of wear, the HS-4 is comfortably padded and is completely adjustable. The frequency response of the HS-4 is tailored specifically for amateur communication use. (300 to 3000 Hz, 8 ohms).



MC-50

The MC-50 dynamic microphone has been designed expressly for amateur radio operation as a splendid addition to any Kenwood shack. Complete with PTT and LOCK switches, and a microphone plug for instant hook-up to any Kenwood rig. Easily converted to high or low impedance. (600 or 50k ohm).

TRIO-KENWOOD COMMUNICATIONS INC.
116 EAST ALONDRA/GARDENA, CA 90248

 **KENWOOD**
...pacesetter in amateur radio

SAVE UP TO 50% ON PARTS.

Hobbyist or professional, there are probably a lot of circuits you build just for the fun of it. And a lot you'd like to build, but never get around to.

* One reason is the cost of parts. Parts you buy for one project, but can't re-use... because you haven't time to take them carefully apart. Or because of heat and mechanical damage that occur when you do.

Now, there's an easier way that can save you big money on parts and hours on every project, as well: *Proto-Board® Solderless Breadboards.*

Now, assembling, testing and modifying circuits is as easy as pushing in—or pulling out—a lead. IC's, LED's, transistors, resistors, capacitors... virtually every kind of component... connect and interconnect instantly via long-life, nickel-silver contacts. No special patch

MODEL	NO. OF TIE-POINTS	14-PIN DIP CAPACITY	SUGG LIST *	OTHER FEATURES
PB-6	630	6	\$15.95	Kit — 10-minute assembly
PB-100	760	10	19.95	Kit — with larger capacity
PB-101	940	10	29.95	8 distribution buses, higher capacity
PB-102	1240	12	39.95	Large capacity, moderate price
PB-103	2250	24	59.95	Even larger capacity, only 2.7¢ per tie-point
PB-104	3060	32	79.95	Largest capacity, lowest price per tie-point
PB-203	2250	24	75.00	Built-in 1% regulated 5V, 1A low-ripple power supply
PB-203A	2250	24	120.00	As above plus separate 1/2-amp +15V and -15V internally adjustable regulated outputs

*Manufacturer's suggested list
Prices and specifications subject to change without notice

cords or jumpers needed—just lengths of ordinary #22-30 AWG solid hookup wire.

Circuits go together as quickly as you can think them up. And parts are re-usable, so as your "junk box" builds, you build more and more projects for less and less money.


Before you invest in your next project, invest in a CSC breadboard. See your dealer or order by phone: 203-624-3103 (East Coast) or 415-421-8872 (West Coast)—major charge cards accepted. You've got nothing to lose... and a lot to gain.

CONTINENTAL SPECIALTIES CORPORATION



44 Kendall Street
Box 1942, New Haven, CT 06509
203-624-3103 TWX 710-465-1227
West Coast office: Box 7809, San Francisco, CA
94119 • 415-421-8872 TWX 910-372-7992

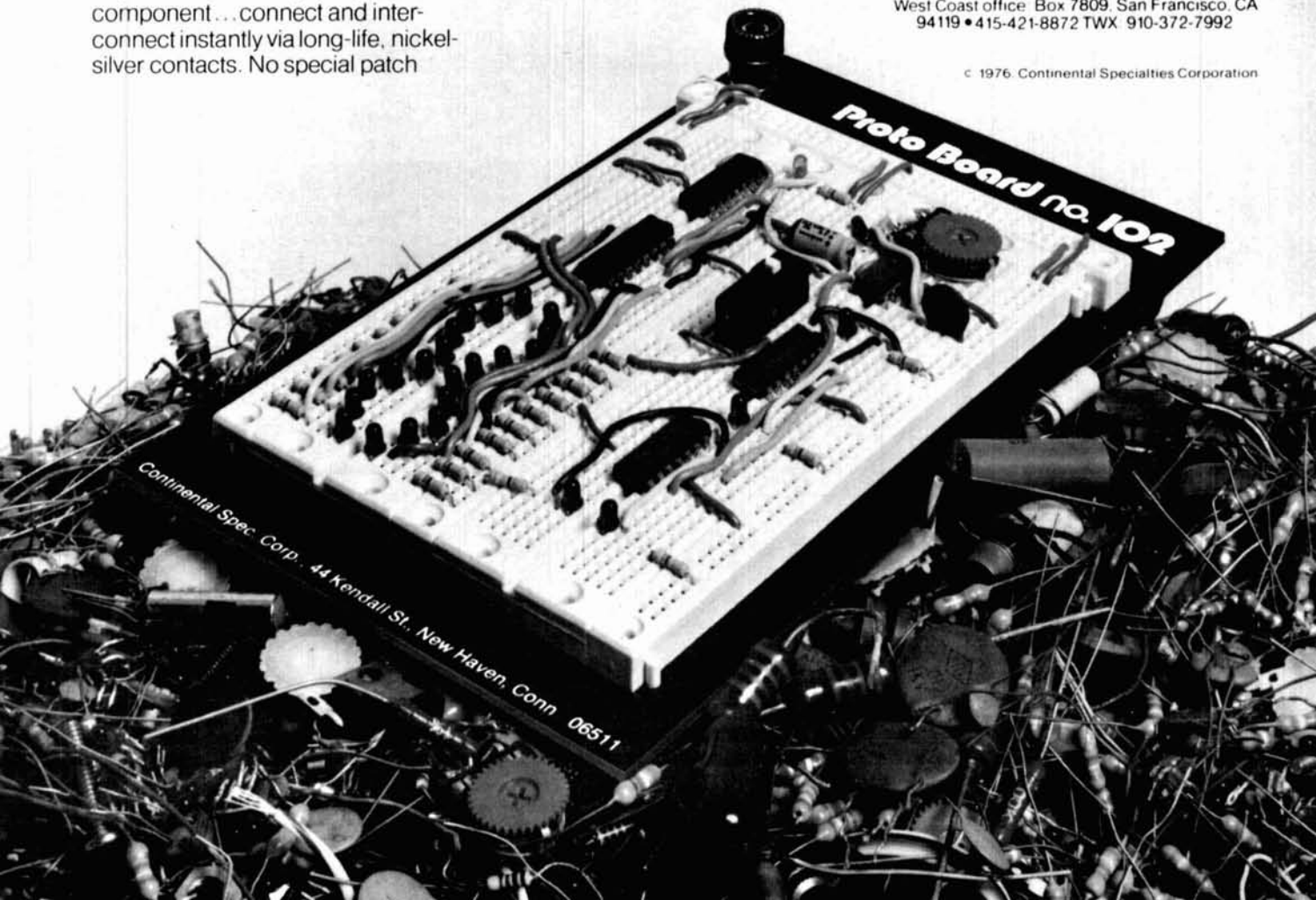© 1976, Continental Specialties Corporation






Regency
 the first name in solid state[®]

**INTRODUCES THE
VERSATILE
NEW**



HR-312

⊙ **More Channels...at the flip of a switch**

Unlock the unique mode switch and 12 channels become 144

⊙ **More Sensitivity, Less Interference.**

.25 μ V Sensitivity plus 75 db adjacent channel selectivity and 70 db image rejection

⊙ **More Power Out**

35 watts nominal with a minimum of 30 watts across the band

... for a lot less

\$269⁰⁰

Amateur Net



ELECTRONICS, INC. 7707 Records Street
Indianapolis, Indiana 46226

THE FM LEADER →


2 METER 

220 MHz 

6 METER 

440 MHz 

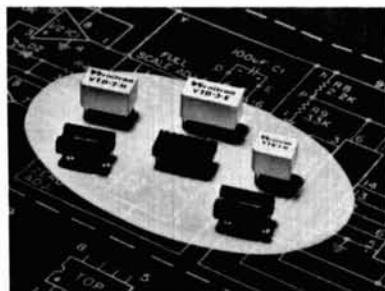miniature ceramic filter for communications receivers



Vernitron Piezoelectric Division recently introduced a new series of low-cost miniature VTD ceramic ladder filters designed to meet the needs of modern double conversion systems.

The small size of the VTD filters and their high stopband rejection, make them particularly suitable for hand-held transceivers, CB equipment, police scanners and commercial two-way radios.

These compact, highly sensitive ceramic filters are fully compatible with transistorized amplifier circuitry, as well as with ICs in am and fm sets. They plug into 14- or 16-pin DIP sockets or mount directly on PC boards, and provide maximum design flexibility.

Vernitron has designed the new VTD Series of ceramic ladder filters in three model groups. VTD-1 models offer 40 dB bandwidth and stopband of 25 to 27 dB; VTD-2 models offer 50 dB bandwidth and stopband of 30 to 40 dB; and VTD-3 models offer 60 dB bandwidth and stopband of 40 to 45 dB. The VTD-1 and VTD-2 filters plug into a 14-pin dip socket and the VTD-3 filter plugs into a 16-pin dip socket.

For more information and Data Sheet 940 write Mark Rickman, Vernitron Piezoelectric Division, 232 Forbes Road, Bedford, Ohio 44146; telephone (216) 232-8600, or use *check-off* on page 142.

Sinclair offers free brochure for amateurs

Sinclair Radio Laboratories — the company known for quality and innovation in the radio antenna systems equipment market for over 25 years —

6 Digit LED Clock Kit - 12/24 hr.

\$995 QTY. 12
ea. OR MORE

\$1095 QTY.
ea. 6-11

\$1195 QTY.
ea. 1-5


- KIT INCLUDES**
- INSTRUCTIONS
 - QUALITY COMPONENTS
 - 50 or 60 Hz OPERATION
 - 12 or 24 HR OPERATION

6-LED Readouts (FND-359 Red, com. cathode)
1-MM5314 Clock Chip (24 pin)
13-Transistors
3-Switches
6-Capacitors
5-Diodes
9-Resistors
24-Molex pins for IC socket

LARGE .4" DIGITS!
ORDER KIT #850-4
AN INCREDIBLE VALUE!

"Kit #850-4 will furnish a complete set of clock components as listed. The only additional items required are a 7-12 VAC transformer, a circuit board and a cabinet, if desired."

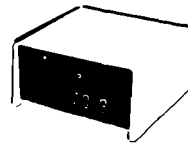Printed Circuit Board for kit # 850-4 (etched & drilled fiberglass)\$2.95
Mini-Brite Red LED's (for colon in clock display) pkg. of 5 1.00
Molded Plug Transformer 115/10 VAC (with cord) 2.50
NOTE: Entire Clock may be assembled on one PC Board or Board may be cut to remote display.
Kit # 850-4 will fit Plexiglas Cabinet II.



PLEXIGLAS CABINETS

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.

Black, White or Clear Cover

CABINET I
3"H, 6 1/4"W, 5 1/2"D

CABINET II
2 1/2"H, 5"W, 4"D


ANY SIZE / COLOR **\$6.50** ea. **2/*12.**

RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS

3"x6"x1/8" **95¢** ea. **4/*3**

MOBILE LED CLOCK

12 OR 24-HOUR OPERATION
12 VOLT AC or DC POWERED FOR FIXED OR MOBILE OPERATION.
SIX JUMBO .4" DIGITS!
KIT OR ASSEMBLED

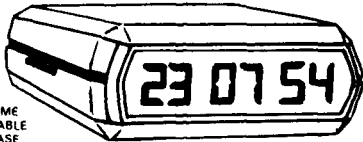

MODEL 2001

ACCURATE TIME WITH ADJUSTABLE XTAL TIME BASE

Approx. Size:
1 1/4" H x 4" W x 4 1/2" D

BATTERY BACK-UP FOR POWER FAILURE OR TRANSPORTING FROM HOUSE TO CAR, ETC.

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM.
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOULDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY - TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
- TOP QUALITY PC BOARDS & COMPONENTS - EXCELLENT INSTRUCTIONS

KIT #2001: COMPLETE KIT (Less V. Battery) **29⁹⁵** EA. 3 OR MORE **\$27⁹⁵** EA. 115 VAC Power Pack #AC-1 **\$2⁵⁰** EA.

ASSEMBLED UNITS W/ WIRING & TESTED (LESS V. BATTERY) **\$39⁹⁵** EA. 3 OR MORE **\$37⁹⁵** EA. Assembled Units May Be Mixed With Kits for Qty. Price

JUMBO RED LED'S 12/\$1.00 50/\$3.95

6 Digit-LED Clock-Calendar-Alarm Kit

This is a complete, top of the line, Kit for the person that wants the best. Some of the many features and options are: 12/24 time, 28-30-31 day calendar, alternates time (8 sec) and date (2 sec) or can display time only and date on demand, 24 hr alarm - 10 minute snooze, alarm set indicator, 50/60 HZ. line operation or use with Xtal time base (#TB-1), built in OSC for battery back-up / AC failure, Aux. timer. Large digits.

Kit #7001B 6-.4" Digits Man-64 **\$39.95**
Kit #7001C 4-.6" Digits & 2-.3" (seconds) **\$42.95**

Kits are complete (less cabinet) including PC boards, power supply, IC socket, 9 switches, 16 transistors and all parts required for above features and options (Ideal fit in Cabinet I above).

60 HZ.

XTAL TIME BASE KIT

Will enable Digital Clock or Clock-Cal. Kits to operate from 12VDC. Uses MM5369 and 3.58MHz. XTAL. Req. 5-15VDC/2.5 MA. 1"x2" PC Board. Easy 3 wire hookup Accuracy: +- 2 PPM

#TB-1 [adjustable] Complete kit \$4.95 ea
Wired & Cal. \$9.95 ea

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout. Specify for #7001B or #7001C (Set of 2) \$7.95

JUMBO DIGIT CLOCK KIT

A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC, 12/24 Hr. time, 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts. (Ideal Fit in Cabinet II) **\$19⁹⁵** 2/*38.
Kit #5314-5

JUMBO DIGIT CONVERSION KIT

Convert small digit LED clock to large .5" displays. Kit includes 6-.5" LED's, Multiplex PC Board & easy hook-up info. Kit #JD-1CC For common Cathode **\$9⁹⁵** ea. 2/*19.
Kit #JD-1CA For common Anode

Fairchild Super Digit FND-359

4" Char. Ht. 7 segment LED. RED Com. Cath. Direct pin replacement for popular FND-70. **95¢** ea, **10/\$8.50**
100/\$79.00

SET OF 6 FND-359 WITH MULTIPLEX PC BOARD **\$6.95**

25 AMP BRIDGE **\$1.95** ea.
3/\$5.00

100 PIV


TELEPHONE FORMAT KEYBOARD BY Chomerics

2-1/4"x3" 5/32" thick **\$4.95**

6/*28.

SEE THE WORKS CLOCK KIT Clear Plexiglas Stand

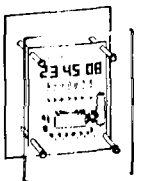- 6 Big .4" digits
 - 12 or 24 hr. time
 - 3 set switches (back)
 - Plug transformer
 - All parts included
- Plexiglas is Pre-cut & drilled. Size: 6"H, 4 1/4"W, 3"D



A SUPER LOOKING CLOCK!

Kit #850-4-CP **\$23⁵⁰** ea. 2/*45.

7-SEG LED COMMON CATHODE

COLOR	HT. DEC PT. PR. EA.
FND-359 RED	4" RHDP \$.95
FND-503 RED	5" RHDP \$1.35
DL-750 RED	6" LHDP \$2.95
XAN-654 GREEN	6" NDP \$2.95
XAN-664 RED	6" NDP \$2.95

COMMON ANODE

DL-747 RED	6" LHDP \$2.95
XAN-72 RED	3" LHDP \$1.25
XAN-81 YELLOW	3" RHDP \$1.75
XAN-351 GREEN	3" RHDP \$1.50
XAN-361 RED	3" RHDP \$1.50
XAN-362 RED	3" LHDP \$1.50
XAN-662 RED	6" NDP \$2.50
XAN-692 RED	6" NDP \$2.50

Form Inexpensive Sockets 100 for \$1.25 Reel of 1000 - \$8.50

MOLEX PINS

SCHOTTKY TTL		UART		EXAR		OP AMPS	
74S00 \$.35	300 \$.09	AYS-1013 \$ 6.95		XR 2556 \$ 1.75	3/10 DIP		
74S01 .40	932 .09			XR 2567 \$ 1.95	301 DIP		
74S04 .55	937 .09				709 DIP		
74S05 .60					741 DIP		
74S09 .55					741 M DIP		
74S10 .40	7447 \$.95				741 TO 5		
74S15 .55	7449 .95				747 DIP		
74S20 .50	75491 .65				748 TO 5		
74S22 .45	75492 .65						
74S40 .45							
74S50 .45							
74S51 .55							
74S60 .85							
74S64 .55	LM 309 H TO-5 \$.95						
74S73 1.25	LM 309 K TO 3 1.25						
74S74 .85							
74S75 1.75	7805 TAB .95						
74S78 1.50	7812 TAB 1.25						
74S86 .95	7815 TAB 1.25						
74S107 .95	7815 TAB 1.25						
74S112 .95	78L15 TO-5 .75						
74S113 1.40	7824 TO 3 1.25						
74S114 .95	723 DIP .75						
74S121 .95	723 TO-5 .75						
74S133 .75							
74S134 .75							
74S138 1.75							
74S139 1.50							
74S151 1.95	MM 5312 \$ 4.95						
74S153 1.95	MM 5314 3.95						
74S165 1.95	MM 5375 AB 3.95						
74S196 1.95	CT 7001 7.95						
74S197 1.90	CT 7002 13.95						
74S158 2.50	50380 3.95						
74S174 2.50	MM 5369 2.50						
74S175 2.50							
74S181 2.95							
74S182 1.95							
74S251 2.75	3 579545 MHZ. \$ 1.95						

BUY 100 OR MORE IC'S [Any Mix] TAKE 10% DISCOUNT.

OPTOELECTRONICS, inc.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056



ORDER BY PHONE OR MAIL
COD ORDERS WELCOME
(\$1.00 CHG.)
Orders Under \$15 Add \$1.00 Handling
Fla. Res. Please Add 4% Sales Tax.

WE PAY ALL SHIPPING IN CONTINENTAL USA — OTHERS ADD 5% [10% FOR AIRMAIL]

MICROPROCESSOR BOOKS

FROM ADAM OSBORNE

INTRODUCTION TO MICROCOMPUTERS —

Volume I Basic Concepts

by Adam Osborne

Takes you by the hand from elementary logic and simple binary arithmetic through concepts shared by all microcomputers. You learn how to take an idea that may need a microcomputer and create a product that uses one. This book is complete. Every aspect of microcomputers is covered: the logic devices that constitute a microcomputer system; communicating with the external logic via interrupts, direct memory access, and serial or parallel I/O; microprogramming and macro-programming; assemblers and assembler directions; linking and relocation — everything you need to know to start selecting or using a microcomputer.

Order AO-2001

Just \$7.50

INTRODUCTION TO MICROCOMPUTERS —

Volume II Some Real Problems

by Adam Osborne

Covers real microcomputers in considerable detail. Every major micro-computer: 4-bit, 8-bit or 16-bit is described including some soon to be announced products. Major chip slice products are also covered; more than 20 microcomputers in all.

Included is material on the following:

- 8259 Priority Interrupt Control Unit from Intel
- 8253 Programmable Counter Timer from Intel
- 8257 Direct Memory Access control devices from Intel
- 6028 Priority Interrupt Controller from Motorola
- 6875 USART from Motorola
- M6700 single chip microcomputer from Motorola
- 10800 family of chip slice logic from Motorola
- Single chip F-8 from Fairchild
- EA9002 microprocessor from Electronic Arrays

Plus others

Order AO-3001

900 pages in this giant volume Only \$7.50

8080 PROGRAMMING FOR LOGIC DESIGN

by Adam Osborne

A completely new book on a totally new subject: implementing digital and combinatorial logic using assembly language within an 8080 micro-computer system. What happens to fan-in and fan-out? How do you implement a one-shot? This book simulates well known digital logic devices using assembly language. Next it shows you how to simulate an entire schematic, device by device, keeping the assembly language simulation as close to the digital logic as possible. But that is the wrong way to use a microcomputer; the book explains why. Then shows you the correct way.

Order AO-4001

Just \$7.50

Order From

HAM RADIO, Greenville, NH 03048


announces that radio amateurs are now able to obtain a *free* "Equipment for Amateur Radio Service" brochure.

Sinclair is the originator of the *Excaliber* mobile antenna and the tunable *Mirage* antenna, and is responsible for developing the two-meter 100 dB hybrid ring duplexer, the Q-circuit[©] duplexer and the popular Q-filter.[©]

Now amateur radio organizations and individuals may obtain all Sinclair products at generous professional discounts.

To obtain the new brochure with price list, discount structure and order form, write: Amateur Brochure, Sinclair Radio Laboratories, Inc., 675 Ensminger Road, Tonawanda, New York 14150; or use *check-off* on page 142.

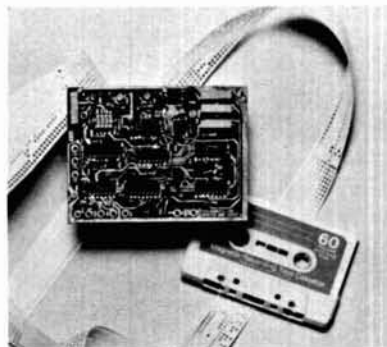low-cost audio cassette/tty/crt adapter for microprocessors



Electronic Product Associates announces the availability of a new, low-cost audio cassette/TTY/CRT adapter which allows any serial TTL or MOS output to simultaneously interface a low-cost audio cassette player via frequency shift keying (Byte Standard) up to 300 Baud and to a standard RS232 CRT and a 20 mA current loop TTY. The adapter also simultaneously decodes Byte Standard fsk data from low-cost audio cassette players and from 20 mA current loop TTY and RS232 CRT. Audio cassette information is decoded by a proprietary phase-locked-loop system developed by EPA which is said to be the most reliable method available for transferring digital data to and from low-cost audio cassette players. The Model TCC3 is 4½x3¼ inches

HERE'S A HOT NUMBER

800-325-3636

(Toll Free)

CALL

HAM RADIO CENTER

ST. LOUIS

FOR NEW AND USED AMATEUR RADIO EQUIPMENT
 MASTER-CHARGE BANKAMERICARD

TRADE ON NEW OR USED

Hours 9 A.M. - 5 P.M. (Central)

Closed Sun. & Mon.

THE HAM-KEY

NOW 5 MODELS


- Iambic circuit for squeeze keying.
- Self completing dots & dashes
- Dot memory.
- Battery operated with provision for external power.
- Built-in side-tone monitor.
- Speed, Volume, tone & weight controls.
- Grid-block or direct keying.
- Use with external paddle such as HK-1.



NEW
 MODEL HK-5
 ELECTRONIC KEYSER
\$69.95




MODEL HK-1
\$29.95

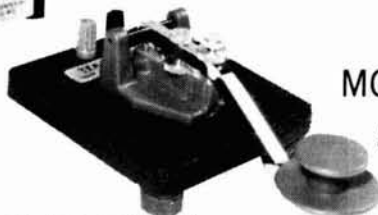


MODEL HK-3
\$16.95

- Dual lever squeeze paddle.
- Use with HK-5 or any electronic keyer.
- Heavy base with non-slip rubber feet.
- Paddles reversible for wide or close finger spacing.

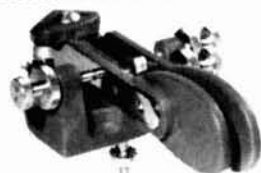- Deluxe straight key.
- Heavy base, no need to attach to desk.
- Velvet smooth action.



MODEL HK-2
\$19.95

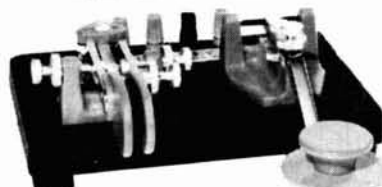

MODEL HK-4
\$44.95

- Same as HK-1, less base for those who wish to incorporate in their own Keyer.

- Combination HK-1 & HK-3 on same base.

Available from your local dealer or order direct.

HAM RADIO CENTER, INC.

8340-42 OLIVE BLVD. • P. O. BOX 28271 • ST. LOUIS, MO. 63132

How You Can Convert Your Rohn 25G Tower to a FOLD-OVER

**CHANGE, ADJUST OR JUST
PLAIN WORK ON YOUR
ANTENNA AND NEVER LEAVE
THE GROUND.**

If you have a Rohn 25G Tower, you can convert it to a Fold-over by simply using a conversion kit. Or, buy an inexpensive standard Rohn 25G tower now and convert to a Fold-over later.

Rohn Fold-overs allow you to work completely on the ground when installing or servicing antennas or rotors. This eliminates the fear of climbing and working at heights. Use the tower that reduces the need to climb. When you need to "get at" your antenna . . . just turn the handle and there it is. Rohn Fold-overs offer unbeatable utility.



Yes! You can convert to a Fold-over. Check with your distributor for a kit now and keep your feet on the ground.

AT ROHN YOU GET THE BEST



Unarco-Rohn

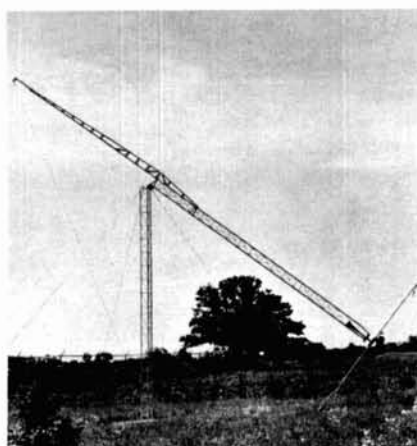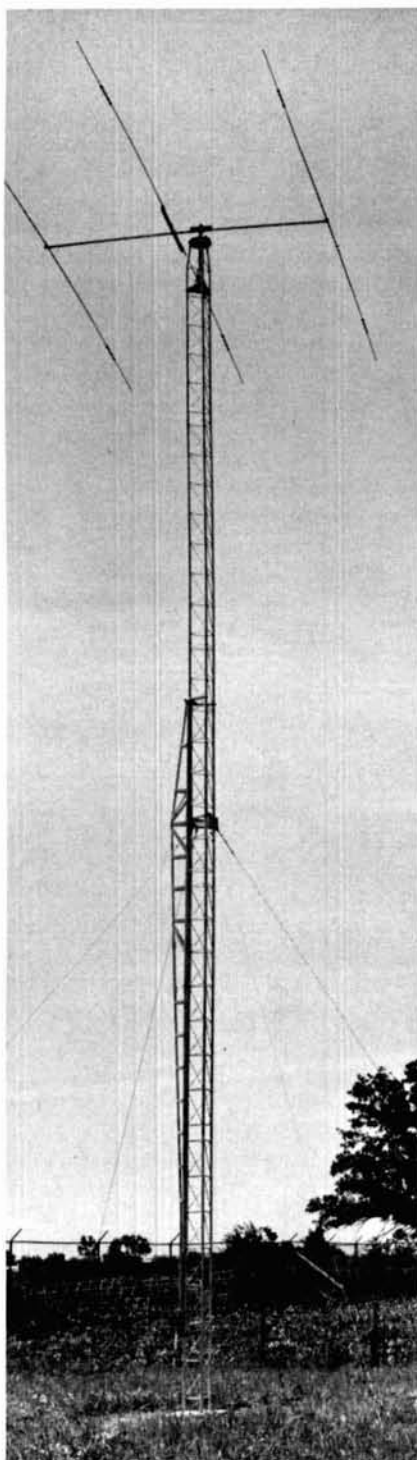Division of Unarco Industries, Inc.
P.O. Box 2000, Peoria, Illinois 61601



(11.5x8cm) and mounts piggy-back on the EPA Micro-68 development computer. The TCC3 price is \$129.00 in singles, completely assembled and tested. Delivery is from stock.

For additional information, write Electronic Product Associates, Inc., 1157 Vega Street, San Diego, California 92110; telephone (714) 276-8911 or use *check-off* on page 142.

IC Zener has one-ohm dynamic impedance

National Semiconductor Corporation recently announced a new reference diode with a dynamic impedance two orders of magnitude less than that of discrete Zener diodes. The LM129 linear IC, 6.9-volt, reference diode operates over a 0.5 to 15mA current range, allowing it to replace a wide variety of discrete devices and improve circuit performance. An important feature of the LM129 is that all operating characteristics of the reference are essentially independent of operating current.

The heart of the linear integrated circuit is a new sub-surface-breakdown Zener that yields a very low noise and highly stable breakdown. Long-term stability is typically 20 ppm while noise is guaranteed to be less than 20 μ V. Active circuitry around the Zener buffers external current changes to give a one-ohm dynamic impedance.

According to Robert C. Dobkin, inventor of the LM129, this new IC Zener will greatly simplify bias circuitry needed to make a reference. Normally, a precision current source is needed to bias reference Zeners; however, with the LM129, only a single resistor is needed.

The new reference is available in selected temperature coefficients from 0.001% to 0.01% per degree C for use in a zero to 70 degree C, or -55 to 125 degree C temperature range. The new IC is packaged in either a TO-46 hermetic transistor package or a plastic TO-92 package.

Pricing for the LM129AH (0.001% per degree C, -55 to 125 degree C) reference is \$15.00 in quantities of one hundred, and the LM329DZ (0.01% per degree C, zero to 70 degree C) reference is \$0.75. Delivery of both IC reference

From *Barry* The Outstanding New GOLD LINE FT-301D



ALL SOLID STATE

200W PEP

DIGITAL DIAL TRANSCEIVER



- 6 - Digit Readout
- All Modes - SSB/CW/AM/FSK
- 160 thru 10 Meters
- TX & RX Clarifier
- RF Feedback
- 3 - Position AGC
- Rejection Tuning (Tuneable IF Crystal Filter)
- Built-in DC Power Supply
- Optional AC Power Supply & Speaker Unit with 12 or 24 Hr. Digital Clock
- Noise Blanker
- RF Speech Processor
- Computer Type Plug-In Module Construction
- Size: 11 in. (w) x 5 in. (h) x 13½ in. (d)
- Light Weight: 22 lbs.

The Model FT-301D is a precision-built, all solid-state, compact high performance transceiver of advanced design. All circuits are fully transistorized with ICs and FETs for reliability. A wide-band tuning system with preset pass band tuning combined with wide-band amplifier eliminates final amplifier tuning for band change. Also available as an option is an automatic CW identifier (programmable).

Whether you judge it on price, performance or operational features, the FT-301D comes out a winner!

YAESU

Available at:

Barry Electronics

WORLD-WIDE AMATEUR RADIO SINCE 1920

512 Broadway, N. Y., N. Y. 10012 - Phone: 212-925-7000 - Telex: 12-7670

MICROPROCESSORS ANYONE?

Here are those fabulous BUGBOOKS® that everyone has been talking about. These are probably one of the best selling series of technical books we have ever handled.

What are BUGBOOKS? Each book is an excellent text plus complimentary experiments designed to introduce you into the exciting new world of microcomputers. They start right at the beginning and give you everything you'll need to start designing your own interface systems.

This is the first good microprocessor information featuring hardware and experiments. Hurry, Hurry, Hurry and get 'em while they're hot.

BUGBOOKS I and II

by Peter R. Rony, David G. Larsen, WB4HYJ

Sold as a set these two books outline over 90 experiments designed to teach the reader all he will need to know about TTL logic chips to use them in conjunction with microprocessor systems. You'll learn about the basic concepts of digital electronics including gates, flip-flops, latches, buses, decoders, multiplexers, demultiplexers, LED displays, RAM's, ROM's, and much, much more.

Order BB-12

Only \$17.00 per set

BUGBOOK IIa

by Peter R. Rony, David G. Larsen, WB4HYJ

This volume will introduce you to the fabulous UART chip — that all important interface between data terminals, etc., and your microcomputer. It also covers current loops, and the RS 232C interface standard. Particularly recommended for any RTTY enthusiast.

Order BB-2A

Only \$5.00

BUGBOOK III

by Peter R. Rony, David G. Larsen, WB4HYJ, Jonathan A. Titus

Here is the book that puts it all together. Besides having much valuable text there are a series of experiments in which the reader completely explores the 8080 chip pin by pin and introduces you to the Mark 80 microcomputer, a unique easily interfaced system. It is recommended that you have the background of the BUGBOOKS I & II before proceeding with BUGBOOK III.

Order BB-3

Only \$15.00

THE 555 TIMER APPLICATIONS SOURCEBOOK WITH EXPERIMENTS

by Howard M. Berlin

The first book in a new series of texts and experimental manuals to be issued by E & L Instruments, Inc. in cooperation with Larsen & Rony, authors of the famous Bugbooks.

Since its inception, the 555 IC timer has been shown to be popular and versatile. This book is the first of its kind and shows you what the 555 timer is and how to use it. Included are over 100 various design techniques, equations and graphs to create "ready-to-go" timers, generators, power supplies, measurement and control circuits, party games, circuits for the home and automobile, photography, music and Amateur Radio. In addition, experiments are included to gain experience with the timer, demonstrating many features and applications, most of which can be constructed in a few minutes on one of the recommended breadboarding devices.

Order BB-555

\$6.95

Order From

HAM RADIO, Greenville, NH 03048

diodes is from stock. For additional information, including typical circuit applications and wiring diagrams, write Roy Twitty, National Semiconductor Corporation, 2900 Semiconductor Drive, Santa Clara, California 95061; telephone (408) 737-5287, or use *check-off* on page 142.


B&K-precision issues new 40-page catalog

A new 40-page catalog describing B&K-Precision test instruments has just been released.

Among the new "cost effective" instruments in this catalog are a 30 MHz scope, a 15 MHz scope and a 5 MHz scope. A new low-cost 3-1/2 digit multimeter is also being introduced for the first time. Other devices described in the catalog include frequency counters, signal generators, semiconductor and transistor testers and numerous other test instruments.

The catalog is available without charge by writing directly to Mr. Paul Mangione, B&K-Precision, Dynascan Corporation, 6460 W. Cortland, Chicago, Illinois 60635; telephone (312) 889-9087, or use *check-off* on page 142.

Touch-tone pad

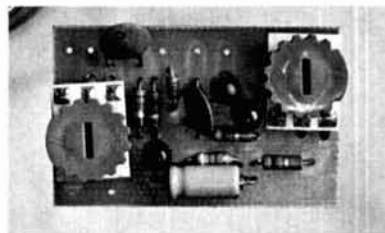


Touch-toners, if you've been looking for a neat way to interface a touch-tone pad with your two-meter rig, Trevor Industries may have just the device you need. The "Trevorface" has an adjustable audio output level and, each time a tone button is depressed, automatically keys your transmitter for any desired period of time up to several seconds. The printed-circuit board with components is small enough to find a home inside the enclosure of any but the smallest hand-held rig and measures only 3/8x1 1/2x2 inches (10x32x51mm). The design was developed nearly four years ago for the TR-22 by W2EUP who

BULLET ELECTRONICS

P. O. BOX 19442
DALLAS, TEXAS 75219
(214) 823-3240

- NO COD'S
- SEND CHECK or M.O.
- BANKAMERICARD OR M.C.#
- ADD 5% FOR FIRST CLASS
- FOREIGN ORDERS ADD 10% (20% FOR AIRMAIL)
- TEXAS RESIDENTS ADD 5% SALES TAX
- ADD 60c FOR HANDLING ON ORDERS UNDER \$10.00

POWER SUPPLY KIT

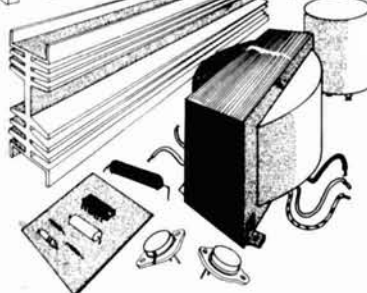


FEATURES:
Output adjustable from 3 to 30 Volts DC
Adjustable Current Limiting to 15 Amps
Special Pre-Regulator Circuit eliminates need for massive heatsinks
Better than 1% Load & Line Regulation from 0 to 15 Amps
Low Ripple Output
Heavy Duty 10 lb. transformer

KIT INCLUDES:
Transformer
Heatsink (drilled)
Semiconductors (diodes, transistors, etc.)
All Components (resistors, caps)
Transistor mounting hardware and insulators
Drilled & Plated P.C. Board
Wire

NOT ONLY IS THE PS-12 ABLE TO SUPPLY A CONTINUOUS 15 AMPS OF LOW RIPPLE, REGULATED DC VOLTAGE, BUT IT IS ALSO VARIABLE FROM 3 TO 30 VOLTS! USE IT AS A BUILDING BLOCK FOR A FANTASTIC BENCH SUPPLY. THE CHASSIS WORK IS UP TO YOU - GO FANCY WITH METERS AND LIGHTS; OR GO PLAIN WITH A METAL PLATE. EITHER WAY WE GET YOU OUT WITH A QUALITY KIT AT A SUPER LOW PRICE AND WE GUARANTEE YOUR SATISFACTION.

\$49.95
add \$3.70
postage.

MASSA AIR ULTRASONIC TRANSDUCER

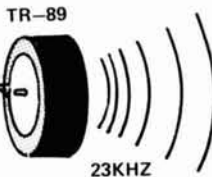


TR-89
23KHZ
BUILD YOUR OWN ULTRASONIC MOTION DETECTOR FOR USE IN INTRUSION DETECTORS, DOOR OPENERS, OBJECT COUNTERS, ETC. WE INCLUDE COMPLETE SPECS AND RECOMMENDED CIRCUITS.

\$2.49 4/9.00



49

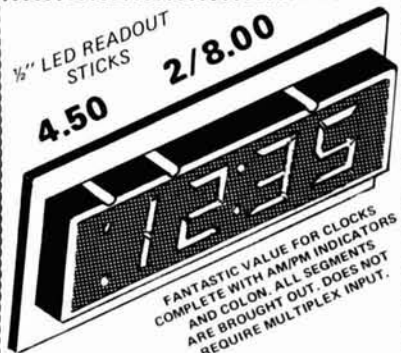
1 HY TOROID POT CORE COILS
ULTRA STABLE FOR LOW FREQUENCY OSCILLATORS, FILTERS, etc.



1/2" LED READOUT STICKS
4.50 2/8.00

FANTASTIC VALUE FOR CLOCKS COMPLETE WITH AM/PM INDICATORS AND COLOR. ALL SEGMENTS ARE BROUGHT OUT. DOES NOT REQUIRE MULTIPLEX INPUT.

MINI GRANDFATHER CLOCK KIT

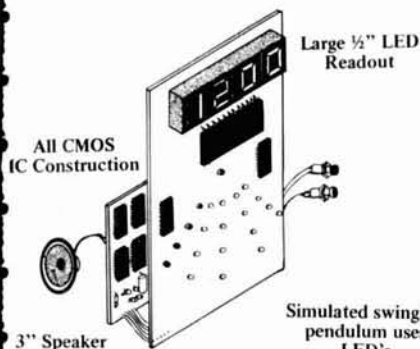

- 4 Digit LED Readout
- Simulated Swinging Pendulum
- Tick-Tock sound matches pendulum swing
- Electronic Tone Chimes the Hour (ie: 3 times for 3 o'clock)
- Quality Components & P.C. Boards
- Transformer for 115 VAC included.

\$44.00

The most novel and fascinating kit we have ever offered!


NO CASE INCLUDED, LET YOUR IMAGINATION RUN WILD AND DESIGN YOUR OWN. WE SUPPLY ALL THE ELECTRONICS.

MOBILE CLOCK KIT

COMPLETE WITH PRE-PUNCHED CUSTOM CASE AND MOUNTING BRACKET. CASE IS HEAVY GAUGE ALUMINUM WITH A BLACK WRINKLE FINISH TOP AND WHITE FRONT.
12 HOUR FORMAT ONLY.
CLOCK HAS ALARM CAPABILITY (extra parts needed).

\$25.00

COMPLETE!

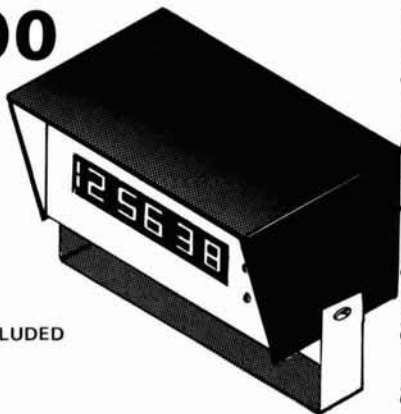


MK-04

- 6 DIGIT LED
- 4" READOUT
- TIMEBASE INCLUDED

10 WATT WARBLE ALARM KIT

A REAL SCREAMER! Emits a piercing dual tone blast that is impossible to ignore. Great for burglar alarms, signal devices or just a toy. Complete with drilled and plated pc board. Does not include a speaker or power switch. (3-15 volts) \$2.50

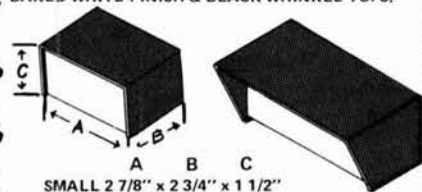METAL PROJECT CASES
CASES ARE HEAVY GAUGE ALUMINUM WITH BAKED WHITE FINISH & BLACK WRINKLE TOPS.



SMALL 2 7/8" x 2 3/4" x 1 1/2" \$1.60
MEDIUM 4 1/4" x 2 3/4" x 1 7/8" \$2.15
SHADOW FRONT 4 13/16" x 3 3/4" x 2" \$3.50

Rubber feet included

GUARANTEED!



RETESTED
UNMARKED
FUNCTIONAL
DEVICES

POSITIVE REGULATOR 500ma
VARIABLE FROM 3 TO 30 VDC

7560 - 50c

NEG. REGULATOR (same as 7560 but for negative) 7563 - 40c

DUAL REGULATORS +/- 500ma

7568 - 69c

AUDIBLE CONTINUITY TESTER

Code Practice Oscillator
Continuity Checker
Transistor, diode or LED checker
Tone varies with resistance

\$1.95 (kit)

MEASURE CONTINUITY & RESISTANCE TO 2K TEST LED'S, DIODES, AND TRANSISTORS. LESS SPEAKER.

Requires 3 to 6 volt batteries (not included)

PHONE ORDERS ACCEPTED ON BAC OR MC CARDS
ALL COMPONENTS AND KITS GUARANTEED.

48 HOUR FAST SERVICE

CATALOG INCLUDED WITH EACH ORDER, OR SEND A STAMP
ORDERS OVER \$50.00 TAKE 10% DISCOUNT

Sensational price! Superb quality!

69⁹⁵ 119⁹⁵
(30MHz Kit) (250 MHz Kit)

**6-DIGIT FREQUENCY
COUNTERS**



A counter-offer you can't refuse! It's rock-bottom price and sky-high quality make it your best buy! We've proved it to thousands. Let us prove it to you!

- 100MHz Readout
- Ham, CB, & Commercial Bands
- 1Hz Optional
- Master Chg./B. Americard OK
- Crystal Time-Base
- Add \$2 Shipping

All counters can be factory wired and tested.

Hufco

Write or call today!
P.O. Box 357, Dept. 54,
Provo, UT 84601 (801) 375-8566

QUALITY KENWOOD TRANSCEIVERS ... from KLAUS RADIO

The **TS-820** is the rig that is the talk of the Ham Bands. Too many built-in features to list here. What a rig and only \$830.00 ppd. in U.S.A. Many accessories are also available to increase your operating pleasure and station versatility.



**TS-820
160-10M TRANSCEIVER**



**TS-700A
2M TRANSCEIVER**

Super 2-meter operating capability is yours with this ultimate design. Operates all modes: SSB (upper & lower), FM, AM and CW. 4 MHz coverage (144 to 148 MHz). The combination of this unit's many exciting features with the quality & reliability that is inherent in Kenwood equipment is yours for only \$700.00 ppd. in U.S.A.

Guess which transceiver has made the Kenwood name near and dear to Amateur operators, probably more than any other piece of equipment? That's right, the **TS-520**. Reliability is the name of this rig in capital letters. 80 thru 10 meters with many, many built-in features for only \$629.00 ppd. in U.S.A.



**TS-520
80-10M TRANSCEIVER**

Send SASE NOW for detailed info on these systems as well as on many other fine lines. Or, better still, visit our store Monday thru Friday from 8:00 a.m. thru 5:00 p.m.

The Amateurs at Klaus Radio are here to assist you in the selection of the optimum unit to fulfill your needs.

KLAUS RADIO Inc.

8400 N. Pioneer Parkway, Peoria, IL 61614
Jim Plack WB9BGS — Phone 309-691-4840

made "GLB" famous, and a large number of these tiny units have been used successfully by amateurs in the Buffalo, New York area for several years. Five simple attachments to B+, ground, PTT line, and audio make hook-up to almost any pad simple and fast, and the unit even includes a 10-volt Zener diode to eliminate alternator "whine." Priced at only \$7.95 plus \$.45 for postage and handling (New York State residents please add 7% sales tax), the "Trevor-face" fills a definite need. Want one? Write or call Gary Ketch at Trevor Industries, Inc., Box 102, Getzville, New York 14068; telephone (716) 834-1639, or use *check-off* on page 142.

ham radio operating guide

Most amateurs like to be known as good operators, and The American Radio Relay League has just introduced a new book that will help the newcomer and brush up the old timer's operating habits. *The ARRL Ham Radio Operating Guide* is an easy-to-read manual for introducing the reader to the many and varied operating practices that exist throughout amateur radio.









The book is written by experts in each of the fields covered and answers questions faced by beginners in any phase of ham radio: What's the best Novice daytime DX band? What crystal frequencies should you order for your new fm transceiver? In the 75-meter phone band, where are Australian stations most likely to be found? When will an amateur satellite be in range of your station? What is the WAJA award? How long should you make each transmission when trying to call another station by meteor scatter?

The guide contains ten chapters: Getting Started, Message Handling, Contests, DX, Awards, Repeaters, Flea Power, Communicating Visually, VHF/UHF, Searching for New Horizons, Oscar.

The manual contains 128 pages and measures 8-1/4 by 11 inches. Price: \$4.00 in the United States and its possessions and \$4.50 elsewhere. Order your copy today from Ham Radio Books, Greenville, New Hampshire 03048.

Vhf engineering

THE WORLD'S MOST COMPLETE LINE OF VHF-FM KITS AND EQUIPMENT

RECEIVERS 		RECEIVERS RF28 Kit . . . 10 meter RF front end 10.7 MHz output . . . 12.50 RF50 Kit . . . 6 meter RF front end 10.7 MHz output . . . 12.50 RF144D Kit . . . 2 meter RF front end 10.7 MHz output . . . 17.50 RF220D Kit . . . 220 MHz RF front end 10.7 MHz output . . . 17.50 RF432 Kit . . . 432 MHz RF front end 10.7 MHz output . . . 27.50 IF 10.7F Kit . . . 10.7 MHz IF module includes 2 pole crystal filter . . . 27.50 FM455 Kit . . . 455 KHz IF stage plus FM detector . . . 17.50 AS2 Kit . . . audio and squelch board . . . 15.00
RX28C . . . 28-35 MHz FM receiver with 2 pole 10.7 MHz crystal filter . . . 59.95 RX50C Kit . . . 30-60 MHz rcvr w/2 pole 10.7 MHz crystal filter . . . 59.95 RX144C Kit . . . 140-170 MHz rcvr w/2 pole 10.7 MHz crystal filter . . . 69.95 RX144C W/T . . . same as above - factory wired and tested . . . 114.95 RX220C Kit . . . 210-240 MHz rcvr w/2 pole 10.7 MHz crystal filter . . . 69.95 RX220C W/T . . . same as above - factory wired and tested . . . 114.95 RX432C Kit . . . 432 MHz rcvr w/2 pole 10.7 MHz crystal filter . . . 79.95 RXCF . . . accessory filter for above receiver kits gives 70 dB adjacent channel rejection . . . 8.50	TRANSMITTERS 	TRANSMITTERS TX432B Kit . . . transmitter exciter 432 MHz . . . 39.95 TX432B W/T . . . same as above - factory wired and tested . . . 59.95 TX150 Kit . . . 300 milliwatt, complete 2 meter transmitter, less crystal and mike . . . 19.95
TX144B Kit . . . transmitter exciter - 1 watt - 2 meters . . . \$ 29.95 TX144B W/T . . . same as above - factory wired and tested . . . 49.95 TX220B Kit . . . transmitter exciter - 1 watt - 220 MHz . . . 29.95 TX220B W/T . . . same as above - factory wired and tested . . . 49.95	POWER AMPLIFIERS 	POWER AMPLIFIERS PA144/25 Kit . . . similar to PA144/15 kit except 25w out . . . 49.95 PA220/15 Kit . . . similar to PA144/15 for 220 MHz . . . 39.95 PA432/10 Kit . . . power amp - similar to PA144/15 except 10w and 432 MHz . . . 49.95 PA140/10 . . . 10w in - 140w out - 2 meter amp - factory wired and tested . . . 179.95 PA140/30 . . . 30w in - 140w out - 2 meter amp - factory wired and tested . . . 159.95
PA2501H Kit . . . 2 meter power amp - kit 1 w in - 25w out with solid state switching, case, connectors . . . 59.95 PA2501H W/T . . . same as above - factory wired and tested . . . 74.95 PA4010H Kit . . . 2 meter power amp - 10w in - 40w out - relay switching . . . 59.95 PA4010H W/T . . . same as above - factory wired and tested . . . 74.95 PA144/15 Kit . . . 2 meter power amp - 1w in - 15w out - less case, connectors and switching . . . 39.95	POWER SUPPLIES 	POWER SUPPLIES O.V.P. . . . adds over voltage protection to your power supplies, 15 VDC max 12 volt - power supply regulator card with fold back current limiting . . . 9.95 PS3A Kit . . . 12 volt - power supply regulator card with fold back current limiting . . . 8.95 PS3012 . . . new commercial duty 30 amp 12 VDC regulated power supply w/case, w/foldback current limiting and over voltage protection wired and tested . . . 239.95
PS15C Kit . . . 15 amp - 12 volt regulated power supply w/case, w/fold-back current limiting and overvoltage protection . . . 79.95 PS15C W/T . . . same as above - factory wired and tested . . . 94.95 PS25C Kit . . . 25 amp - 12 volt regulated power supply w/case, w/fold-back current limiting and overvoltage protection . . . 129.95 PS25C W/T . . . same as above - factory wired and tested . . . 149.95	REPEATERS 	REPEATERS RPT144 . . . repeater - 15 watt - 2 meter - factory wired and tested . . . 695.95 RPT220 . . . repeater - 15 watt - 220 MHz - factory wired and tested . . . 695.95 RPT432 . . . repeater - 10 watt - 432 MHz - factory wired and tested . . . 749.95 DPLX144 . . . 2 meter, 600 KHz spaced duplexer, wired and tuned to frequency . . . 399.95 DPLX220 . . . 220 MHz duplexer, wired and tuned to frequency . . . 399.95
RPT28 Kit . . . repeater - 10 meter . . . TBA RPT28 . . . repeater - 10 meter, wired & tested . . . TBA RPT50 Kit . . . repeater - 6 meter . . . TBA RPT50 . . . repeater - 6 meter, wired & tested . . . TBA RPT144 Kit . . . repeater - 2 meter - 15w - complete (less crystals) . . . 465.95 RPT220 Kit . . . repeater - 220 MHz - 15w - complete (less crystals) . . . 465.95 RPT432 Kit . . . repeater - 10 watt - 432 MHz (less crystals) . . . 515.95	TRANSCIEVERS 	OTHER PRODUCTS BY VHF ENGINEERING CD1 Kit . . . 10 channel receive xtal deck w/ diode switching . . . 6.95 CD2 Kit . . . 10 channel xmit deck w/switch and trimmers . . . 14.95 CD-3 Kit . . . UHF version of CD-1 deck, needed for 432 multi-channel operations . . . 12.95 COR2 Kit . . . complete COR with 3 second and 3 minute timers . . . 19.95 SC3 Kit . . . 10 channel auto-scan adapter for RX with priority . . . 19.95 Crystals . . . we stock most repeater and simplex pairs from 146.0-147.0 (each) . . . 5.00 CWID Kit . . . 159 bit, field programmable, code identifier with built-in squelch tail and ID timers . . . 39.95 CWID . . . wired and tested, not programmed . . . 54.95 CWID . . . wired and tested, programmed . . . 59.95 Microphone . . . 2,000 ohm dynamic mike with P.T.T. and coil cord . . . 9.95
TRX 144 Kit . . . case and all components to build 15 watt 10 channel scanning 2 meter transceiver (less mike and crystals) . . . 219.95 TRX 220 Kit . . . same as above except for 220 MHz . . . 219.95 TRX 432 Kit . . . same as above except 10 watt and 432MHz . . . 254.95	SYNTHESIZERS 	
SYN II Kit . . . 2 meter synthesizer, transmit offsets programmable from 100 KHz - 10 MHz, (Mars offsets with optional adapters) . . . 169.95 SYN II . . . same as above, wired and tested . . . 239.95	WALKIE TALKIES 	
HT 144B Kit . . . 2 meter, 2w, 4 channel, hand held receiver with crystals for 146.52 simplex . . . 129.95 NICAD . . . battery pack, 12 VDC, 1/2 amp . . . 29.95 NICAD . . . battery charger . . . 5.95 Rubber Duck . . . 2 meter, with male BNC connector . . . 8.95		



VHF ENGINEERING
 DIVISION OF BROWNIAN ELECTRONICS CORP.
 320 WATER ST. / BINGHAMTON, N.Y. 13901 / Phone 607-723-9574



HAM MART

Ham Radio's guide to help you find your local

Alabama

LONG'S ELECTRONICS
3521 TENTH AVE. NORTH
BIRMINGHAM, AL 35234
800-633-3410
Call us Toll Free to place your order

California

COMMTECH ENTERPRISES
13754 VICTORY BLVD.
VAN NUYS, CA 91401
213-988-2212
Headquarters for Yaesu, Kenwood,
Drake, Icom, Collins, Atlas.

HAM RADIO OUTLET
999 HOWARD AVENUE
BURLINGAME, CA 94010
415-342-5757
Northern California's largest
new and used ham inventory.

HENRY RADIO
931 N. EUCLID AVE.
ANAHEIM, CA 92801
714-772-9200
The world's largest distributor of
Amateur Radio equipment.

HENRY RADIO CO., INC.
11240 W. OLYMPIC BLVD.
LOS ANGELES, CA 90064
213-477-6701
The world's largest distributor of
Amateur Radio equipment

M-TRON
2811 TELEGRAPH AVENUE
OAKLAND, CA 94609
415-763-6262
We service what we sell.

QUEMENT ELECTRONICS
1000 SO. BASCOM AVENUE
SAN JOSE, CA 95128
408-998-5900
Serving the world's Radio Amateurs
since 1933.

Colorado

C W ELECTRONIC SALES CO.
1401 BLAKE ST.
DENVER, CO 80202
303-573-1386
Rocky Mountain area's complete
ham radio distributor.

Florida

GRICE ELECTRONICS
320 EAST GREGORY
PENSACOLA, FL 32502
904-434-2481
Gulf Coast dealer for Atlas, Drake,
Icom, Kenwood.

Illinois

ERICKSON COMMUNICATIONS, INC.
5935 NORTH MILWAUKEE AVE.
CHICAGO, IL 60646
312-631-5181
Headquarters for all your Amateur
Radio needs.

KLAUS RADIO, INC.
8400 NORTH PIONEER PARKWAY
PEORIA, IL 61614
309-691-4840
Let us quote your Amateur needs.

SPECTRONICS, INC.
1009 GARFIELD STREET
OAK PARK, IL 60304
312-848-6777
Chicagoland's Amateur Radio
leader.

Indiana

HOOSIER ELECTRONICS
P. O. BOX 2001
TERRE HAUTE, IN 47802
812-238-1456
Ham Headquarters of the Midwest.
Store in Meadow Shopping Center.

Kansas

ASSOCIATED RADIO
8012 CONSER P.O.B. 4327
OVERLAND PARK, KS 66204
913-381-5901
Amateur Radio's Top Dealer.
Buy — Sell! — Trade.

Kentucky

COHOON AMATEUR SUPPLY
HIGHWAY 475
TRENTON, KY 42286
502-886-4535
Ten-Tec dealer — Call 24 hours
for best deal

Maryland

COMM CENTER, INC.
9624 FT. MEADE ROAD
LAUREL PLAZA RT. 198
LAUREL, MD 20810
301-792-0600
New & Used Amateur Equipment.
All Inquiries Invited.

Massachusetts

TUFTS RADIO ELECTRONICS
386 MAIN STREET
MEDFORD, MA 02155
617-395-8280
New England's friendliest
ham store.

Michigan

AUDIOLAND
36633 SOUTH GRATIOT
MT. CLEMENS, MI 48043
313-791-1400
All major brands, new/used
equipment & accessories.

PURCHASE RADIO SUPPLY
327 E. HOOVER
ANN ARBOR, MI 48104
313-668-8696 or 668-8262
We still sell Ham parts!

RADIO SUPPLY & ENGINEERING
1203 WEST 14 MILE ROAD
CLAWSON, MI 48017
313-435-5660
10001 Chalmers, Detroit, MI
48213, 313-371-9050.

Minnesota

ELECTRONIC CENTER, INC.
127 THIRD AVENUE NORTH
MINNEAPOLIS, MN 55401
612-371-5240
ECI is still your best buy.

Missouri

HAM RADIO CENTER, INC.
8342 OLIVE BLVD.
P. O. BOX 28271
ST. LOUIS, MO 63132
800-325-3636
Call toll free.

MIDCOM ELECTRONICS, INC.
2506 SO. BRENTWOOD BLVD.
ST. LOUIS, MO 63144
314-961-9990
At Midcom you can try before you
buy!

Dealers - You should be here too! Contact Ham Radio today for complete details.

Amateur Radio Dealer

New Hampshire

EVANS RADIO, INC.
BOX 893, RT. 3A BOW JUNCTION
CONCORD, NH 03301
603-224-9961
Icom & Yaesu dealer.
We service what we sell.

New Jersey

ATKINSON & SMITH, INC.
17 LEWIS ST.
EATONTOWN, NJ 07724
201-542-2447
Ham supplies since "55".

New York

ADIRONDACK RADIO SUPPLY, INC.
185 W. MAIN STREET
AMSTERDAM, NY 12010
518-842-8350
Yaesu dealer for the Northeast.

CFP COMMUNICATIONS
211 NORTH MAIN STREET
HORSEHEADS, NY 14845
607-739-0187
Jim Beckett, WA2KTJ, Manager
Dave Flinn, W2CFP, Owner

GRAND CENTRAL RADIO
124 EAST 44 STREET
NEW YORK, NY 10017
212-682-3869
Drake, Atlas, Ten-Tec, Midland,
Hy-Gain, Mosley in stock

HARRISON
"HAM HEADQUARTERS, USA"
ROUTE 110 & SMITH STREET
FARMINGDALE, L. I., N. Y. 11735
516-293-7990
Since 1925 . . . Service, Satisfaction,
Savings. Try Us!

Ohio

UNIVERSAL SERVICE
114 N. THIRD STREET
COLUMBUS, OH 43215
614-221-2335
Give U.S. a try when ready to buy.

Oklahoma

RADIO STORE, INC.
2102 SOUTHWEST 59th ST.
(AT 59th & S. PENNSYLVANIA)
OKLAHOMA CITY, OK 73119
405-682-2929
New and used equipment —
parts and supply.

Oregon

OREGON HAM SALES
409 WEST FIRST AVENUE
ALBANY, OR 97321
503-926-4591
Yaesu dealer for the Northwest.

Pennsylvania

ARTCO ELECTRONICS
302 WYOMING AVE.
KINGSTON, PA 18704
717-288-8585
The largest variety of crystals
in N. E. Penn.

ELECTRONIC EXCHANGE
136 N. MAIN STREET
SOUDERTON, PA 18964
215-723-1200
New & Used Amateur Radio
sales and service.

"HAM" BUERGER, INC.
68 N. YORK ROAD
WILLOW GROVE, PA 19090
215-659-5900
Communications specialists.
Sales and service.

HAMTRONICS, INC.
4033 BROWNSVILLE ROAD
TREVOSE, PA 19047
215-357-1400
Same location for 25 years.

South Dakota

BURGHARDT AMATEUR CENTER
124 FIRST AVE. N.W. P.O. BOX 73
WATERTOWN, SD 57201
605-886-7314
America's most reliable Amateur
Radio Dealer — Nationwide!

Texas

ALTEC COMMUNICATIONS
1800 S. GREEN STREET
LONGVIEW, TX 75601
214-757-2831
Specializing in ham equipment for
the Ark-La-Tex.

HARDIN ELECTRONICS
5635 E. ROSEDALE
FT. WORTH, TX 76112
817-461-9761
You bet Ft. Worth has a ham store!

TECO ELECTRONICS SUPER STORE
1717 S. JUPITER ROAD
GARLAND, TX 75040
800-527-4642
Call Toll Free for Service Today!

Virginia

ARCADE ELECTRONICS
7048 COLUMBIA PIKE
ANNANDALE, VA 22003
703-256-4610
Serving Maryland, D.C., and Virginia
area since 1962.

Washington

AMATEUR RADIO SUPPLY CO.
6213 13TH AVE. SO.
SEATTLE, WA 98108
206-767-3222
Amateur center of the
Northwest.

Wisconsin

**AMATEUR
ELECTRONIC SUPPLY, INC.**
4828 WEST FOND du LAC AVENUE
MILWAUKEE, WI 53216
414-442-4200
Open Mon & Fri 9-9, Tues, Wed,
Thurs, 9-5:30, Sat, 9-3.

Apollo Products-Little Giant Trans Systems Tuner Kit — \$122.50

Designed and engineered after "Apollo" — "Little Giant" 2500X-2, for an "engineered performance" Trans Systems Tuner and Adaptations of the Lew McCoy Transmatch, with power handling at the KW plus level!



Kit includes:

1 200 pfd wide-spaced variable with isolantite insulation rated 3,000 volts
1 200 pfd dual section parallel condenser isolantited
2 finger-grip pointer knobs 2" diam. white indented
1 pvc insulated shaft couplings 1/4 to 1/2
3 SO-239 coax chassis connectors. Tunes 52 ohm or 52-300-600* or random wires

1 heavy inductance for 10-15-20-40-80 meters
6 pvc stand-offs, 4 for condensers and 2 for inductance
1 HD switch for band catching 10 thru 80 meter coverage
1 pig 12-gauge tinned round wire
Cabinet included — Apollo "Shadow Boxes" M Kit includes schematic. Recommend parts layout.
INFO NOTE *377 OHM and **600 OHM "Open wire spaced ladder line" air dielectric. *53 x wire diam. **84 x wire diam. info only — not supplied.

Apollo Products, Box 245, Vaughnsville, Ohio 45893 419-646-3495
Subsidiary "Little Giant Antenna Labs"

INTRODUCING THE ALL MODE LINEAR AMPLIFIER FOR 2 METERS



For use with the many new all-mode 2 meter transceivers, typified by the Kenwood TS-700A.

SPECIALTY COMMUNICATIONS SYSTEMS MODEL 2M10-70L

SCS's AMPS ARE BUILT FOR ALL MODES OF OPERATION!

Want more power on FM? You've got it with the SM10-70L. Want more power on SSB? Just flip the switch on the 2M10-70L and you've got it.

A TRUE 70 WATT P.E.P. OUTPUT with 10 watts input.

WITH LOWER INPUT POWER, THE 2M10-70L GIVES APPROXIMATELY A 10 dB GAIN.

SCS's ALL MODE LINEAR AMPS ARE FULL CAPACITY PRODUCTS!

Noteconomy lines. The Model 2M10-70L is the finest linear amplifier for 2 meters that can be purchased. Components are of the highest quality.

- All solid state—microstripline design.
- Broadband—requires no tuning across band.
- Variable T-R delay for SSB/CW operation.
- Full VSWR and reverse voltage protection.
- Under 1 dB insertion loss in receive or bypass mode.
- Harmonics levels typically -40 dB or better.
- Measures only 7.1 x 10.2 x 16.5 cm. Wt. 1 kg.
- One year warranty on entire unit.

\$139.⁹⁵

If not available at your dealer, tell him to get up to date, and call the SCS factory for name of your nearest SCS dealer.

SCS SPECIALTY COMMUNICATIONS SYSTEMS, INC.

8160 Miramar Road, San Diego, CA 92126 • Louis N. Anciaux • WB6NMT


appliance noise filter



Cornell-Dubilier has announced a new and efficient filter, the CBBS-1, for electrical interference produced by hot combs, blenders, electric shavers and similar appliances. Simply plug the Cornell-Dubilier CBBS-1 into the wall socket and then plug the noisy appliance into the CBBS-1. All annoying electrical noise which hampers radio and TV reception is removed. The unit is lightweight, highly reliable, (handles 5 amperes), and is built to resist the effects of heavy household usage.

For additional information, contact William Carlson, Cornell-Dubilier, 150 Avenue L, Newark, New Jersey 07101, or use *check-off* on page 142.


new repeater time-out timer

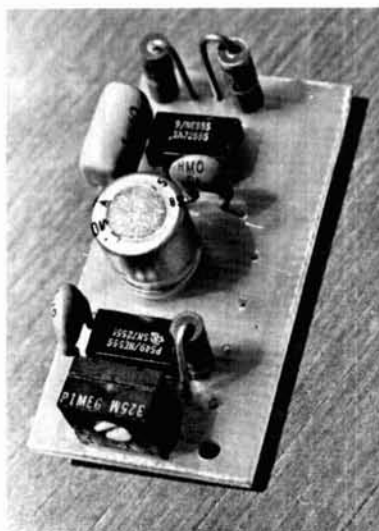

A new integrated circuit timer for repeater time-out use has been announced by Timekit.® All circuitry of Timekit's Model TG970 time-out timer is on a printed-circuit board measuring only 1x2 inches (25.4x50.8mm) that should fit inside most transceiver enclosures. External

CHRISTMAS GOODIES

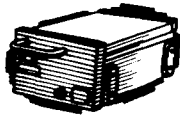1976 HAS BEEN A GOOD YEAR FOR BOTH HAM RADIO AND SPECTRONICS. WE WOULD LIKE TO THANK YOU ALL FOR YOUR SUPPORT. RATHER THAN USING A WHOLE PAGE OF PICTURES OF OUR STAFF AND SYMBOLS OF THE HOLIDAYS WE THOUGHT YOU WOULD LIKE A CHANCE AT BEING YOUR OWN SANTA AT DOWN TO EARTH PRICES. SO HERE GOES THE LIST OF GOODIES THAT WE PROMISED YOU LAST MONTH.



MOBILES


T43GGV...WB..w/accs	\$48.00
T43GGV...NB..w/accs	54.00
T43GGV...WB..no accs	35.00
T43GGV...NB..no accs	39.00
T41GGV...WB..w/accs	45.00
T41GGV...NB..w/accs	49.00
T41GGV...WB..no accs	35.00
T41GGV...NB..no accs	39.00
T51GGV...WB..w/accs	45.00
T51GGV...NB..w/accs	45.00
T51GGV...less accs	35.00
T51AGD...less accs	29.00
D33CMT...w/accs	149.00
R43HHT...RR Trac, less accs.	79.00
CMUA6...Super Carfone, less Accs, w/tone	149.00

NOTE: Accs consist of Control Head, cable and housing



STRIPS

Hi Band "G" Trans	\$7.00
Hi Band "G" Rcvrs	20.00
Hi Band "H" Rcvrs, Solid State, 12vdc	49.00
Hi Band "H" Trans	19.00
Hi Band "A" Trans	10.00
Lo Band "G" Rcvrs	20.00
Lo Band "G" Trans	10.00
Lo Band "A" Rcvr	17.00
Lo Band "A" Trans	10.00
UHF "B", 2F, Tone, NB	15.00
Hi Band 1.4W SS Trans	30.00
UHF 5W Amp for HT220	7.00
AC Supply for 80D	25.00
T Supply for GGV	10.00

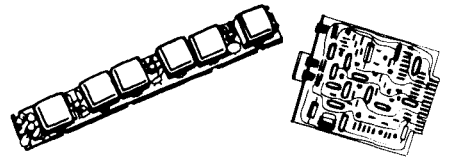

MISCELLANEOUS

Motrac housings	\$5.00
RR Motrac housings	7.00
Cable for 15" MOT	7.00
Motrac "H" audio bds	3.00
4 pin ovens for GGV	1.00
Multi tone head for TRAC	7.00
Solid State Termination panel for remote	15.00
Pulsar RX/TX Audio Bd with 2805 notch filter	5.00
PTT Handsets (Turquoise)	5.00
PT400 D cell packs	7.00
NPN6012 AC Sup. for 23BAC series portables	25.00
HT220 Mobile rapid chargers for omni	75.00
Dayton blowers SQ cage	10.00
Bud Boxes fit R390 Rcvr	15.00
Hartman Secall enc/dec	15.00
Video Tape, 1/2 hr. spools	8.00

CHANNEL ELEMENTS

1081, cool blue	\$6.00
1083, cool blue	6.00
8968A, piggy back	9.00

UPRIGHT CABINETS

New style, 5 foot racks, outdoor style, with locking doors \$75.00

CHART RECORDERS

Texas Inst, 10 speed strip chart.
Dual 1 ma Galvanometers \$70.00

HT200 HOUSINGS

These are for UHF HT200s and come with wiring harness and controls. Unused, less back covers \$25.00

VOICE COMMANDERS

Tech specials with nicad pack. VCIII's. Ideal for tinkering or spare parts. \$19.95

NOTE: Prices FOB Oak Park, Ill. Please include enough to cover shipping.

... If you have been having difficulty locating the Wattmeter or element just right for you. . . . You may have been looking in the wrong places. Our large inventory of most common elements lets you get what you want when you need it. Give us a call first for your BIRD needs.

HAVE A HAPPY & SAFE HOLIDAY SEASON. WE HOPE TO MEET YOU AT SAROC . . . IF YOU WON'T BE THERE SEND FOR YOUR FREE COPY OF OUR BUYERS GUIDE AND SHOP WITH CONFIDENCE FROM YOUR OWN HOME.



SPECTRONICS, INC.

1009 GARFIELD
OAK PARK, IL. 60304
312-848-6777
TELEX 72:8310

HOURS


STORE HOURS:

Mon-Thurs 9:30-6:00, Fri. 9:30-8:00
Sat. 9:30-3:00, Closed Sun. & Holidays.



This is easy- anyone can solder- WITH KESTER SOLDER

**KESTER
SOLDER**

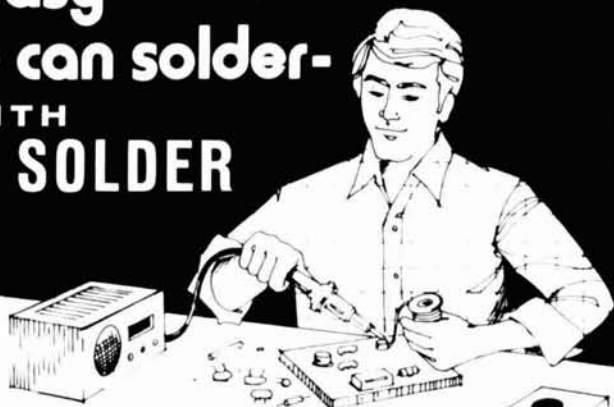

Handymen! Hobbyists! DO-IT-YOURSELFERS!

Let Kester Solder aid you in your home repairs or hobbies. For that household item that needs repairing — a radio, TV, model train, jewelry, appliances, minor electrical repairs, plumbing, etc. — Save money — repair it yourself. Soldering with Kester is a simple, inexpensive way to permanently join two metals.


When you Solder go "First Class" — use Kester Solder.

For valuable soldering information send self-addressed stamped envelope to Kester for a FREE Copy of "Soldering Simplified".



KESTER SOLDER
Litton 4201 WRIGHTWOOD AVENUE/CHICAGO, ILLINOIS 60639

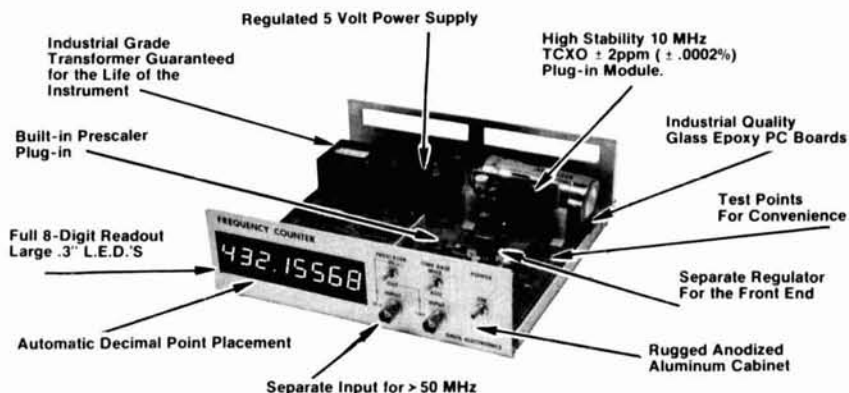(the outside looks nice) BUT IT'S WHAT'S INSIDE THAT COUNTS



DAVIS FREQUENCY COUNTER

- 500 MHz • $\pm .0002\%$ ACCURACY
- UNBEATABLE LOW COST

500 MHz Kit \$249.95
Kits include all parts, drilled and plated PC boards, cabinet, switches; hardware and a complete instruction manual with calibrating instructions.
All parts are guaranteed for 90 days. Factory service available for \$25.

Instruction and Calibrating Manual \$3.00 (refundable with purchase)
500 MHz Factory Assembled ... \$349.95

Factory assembled units are tested and calibrated to specifications, and are guaranteed for 1 year.

DAVIS ELECTRONICS

Dept. F, 636 Sheridan Drive, Tonawanda, New York 14150

(716) 874-5848



connections to the TG970 are 13 volts dc, PTT, ground and output.

When the microphone button is pressed (or when the COR is energized) a timing cycle continuously variable from 10 seconds to 30 minutes is activated. At the conclusion of the cycle, that is, at time-out, the TG970 produces a 13-volt, 2 Hz pulse train which can be used to flash an LED, activate a beeper or excite a Timekit Model TG3 oscillator designed for attachment to the TG970 board. The oscillator will pulse an external speaker at 2 Hz with a 1000 Hz note. Timer reset is immediate with no false triggering, and is immune to rf.

The TG970 is priced at \$7.95 wired and tested, or \$6.50 in kit form. The TG3 is priced at \$4.50 wired and tested, or \$4.00 in a kit.

For additional information, write Timekit, 23715 Mercantile Road, Cleveland, Ohio 44122; telephone (216) 464-3820, or use *check-off* on page 142.

solderless coaxial connector

The Bunker Ramo RF Division has introduced a PL-259-type Amphenol connector that provides instant and simple termination of RG-58A/U coaxial cable without solder, special tools, or adapters. Designated Amphenol 85-58FCP (for field crimp plug), the new, reusable connector has application in both fixed and mobile stations wherever coaxial cable termination must be made.

To complete a termination, the user simply strips the coaxial cable and pushed the connector parts onto the center conductor and braid. The contact is squeezed at the tip to secure the center conductor; but, if reuse is desired, the contact can be soldered. No braid soldering, braid combing, special crimping tools, or special adapters are needed. The result is a fail-safe, fast termination that eliminates faulty interconnections. Another advantage of the solderless termination is the absence of overheating during assembly and consequent damage to the cable itself. The Amphenol 83-58FCP offers performance equal to that provided by standard Amphenol 83-1SP-type uhf connectors, and at the same price.

At the heart of the solderless connecting mechanism is a body assembly featuring a hollow barrel with a barbed

Whatever Santa Says . . . Will be Sharper, Clearer and VALUE PACKED! With the Incredible

This
Holiday
Season
look for value,
look for performance.
Then buy the
Worlds Finest
Amateur Transceiver.
GENAVE!



**GTX-1 or
GTX-1T
HAND-HELD
2-Meter FM
Transceiver**

CHECK THESE FEATURES:

- All Metal Case
- American Made
- Accepts standard plug in crystals
- Features 10.7 MHz crystal filter
- Trimmer caps on TX and RX crystals
- 2.5 watts output
- Battery holder accepts AA regular, alkaline or nicad cells
- Mini Handheld measures 8" high x 2.625" wide x 1.281" deep
- Rubber ducky antenna. Wrist safety-carrying strap included
- 6 Channels
- Factory direct to You

Accessories Available:

- Nicad Battery Pack
- Charger for GTX-1 battery pack
- Leather carrying case
- TE-III Tone Encoder for auto patch

GTX-200-T



2-meter FM, 100 channel combinations, 30 watts with factory installed tone encoder (Incl. 146.94 MHz)

\$249⁹⁵

GTX-200



2-meter FM, 100 channel combinations, 30 watts (Incl. 146.94 MHz)

\$199⁹⁵

GTX-10-S



2-meter FM, 10 channels, 10 watts (Xtals not included)

\$149⁹⁵

GTX-2



2-meter FM, 10 channels, 30 watts with pushbutton frequency selector (Incl. 146.94 MHz)

\$189⁹⁵

2-meter FM, 6-channel, 3.5 watts Hand-Held

***\$249⁹⁵**



**TO
NE
ENCODER PAD**
Plug in installation on most amateur transceivers

Same as GTX-1, plus factory installed Tone Encoder
*(Bat. not incl.)

***\$299⁹⁵**

TE-II

\$49⁹⁵

TE-I
\$59⁹⁵

**GTX-I
GTX-IT**



HURRY!

Use This
Handy
Order
Form



4141 Kingman Dr., Indianapolis, IN 46226
Phone-in orders accepted (317+546-1111)

NAME _____
ADDRESS _____ CITY _____
STATE & ZIP _____ AMATEUR CALL _____

Payment by:
 Certified Check/Money Order Personal Check
C.O.D. Include 20% Down

Note: Orders accompanied by personal checks will require about two weeks to process.
20% Down Payment Enclosed. Charge Balance To:

BankAmericard # _____ Expires _____
 Master Charge # _____ Expires _____
 Interbank # _____ Expires _____

IN residents add 4% sales tax: \$ _____
CA residents add 6% sales tax: \$ _____
HR All orders shipped post-paid within continental U.S.

- GTX-200-T **\$249⁹⁵**
- GTX-200 **\$199⁹⁵**
- GTX-10-S **\$149⁹⁵**
- GTX-2 **\$189⁹⁵**
- GTX-1 **\$249⁹⁵**
- GTX-IT **\$299⁹⁵**
- Ringo Ranger ARX-2 6db 2-M Base Antenna **\$299⁹⁵**
- Lambda/4 2-M and 6-M Trunk Antenna **\$299⁹⁵**
- TE-I Tone Encoder Pad **\$59⁹⁵**
- TE-II Tone Encoder Pad **\$49⁹⁵**
- PS-1 AC Power Supply for use with all makes of transceivers 14 VDC—6 amp and the following standard crystals @ \$4.50 each _____
Non-standard crystals @ \$6.50 each: _____

ACCESSORIES FOR GTX-1 and GTX-1T

- PSI-18 Optional Nicad battery pack **\$29⁹⁵**
- PS-2 Charger for GTX-1(T) battery pack **\$39⁹⁵**
- GLC-1 Leather carrying case **\$12⁹⁵**
- TE-III Tone Encoder (for use with GTX-1) **\$49⁹⁵**

Add \$4 per Radio for Shipping, Handling, and Crystal Netting.

PRESTO!

Your counter becomes a digital display!

Like magic, Hufco's Digi-Dial Adaptor turns any frequency counter into an absolutely accurate digital display! Inexpensively! With continual display of both transmit and receive frequencies — as fast as you turn your transceiver dial!

With the Digi-Dial Adaptor your counter easily adapts to Yaesu, Tempo, Drake C Line, Collins, Kenwood and other transceivers. (Tell us which other brand you have. We'll tell you if the adaptor fits.)

Operation requires only a connecting cable to the transceiver VFO plug. Translates VFO output to 2 through 2.5 MHz. No internal connection or modifications necessary! Complete instructions included.


No frequency counter? Get both the Digi-Dial Adaptor and a frequency counter from Hufco. We have counters starting as low as \$45.95!

DIGI-DIAL ADAPTOR

39.95

kit form

\$49.95 assembled

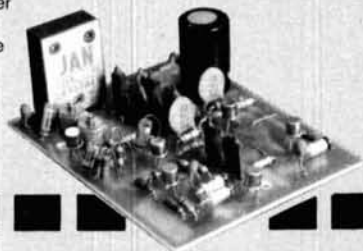

Quick!
Order yours today!

Please rush me:

Digi-Dial Adaptor

\$39.95 kit form - \$49.95 assembled

Check or money order enclosed.

Complete data on Hufco frequency counters

Name _____

Address _____

City/State/Zip _____

Hufco

Box 357, Dept. 70,
Provo, Utah 84601 801/375-8566

JUST IN TIME FOR CHRISTMAS

SENSITIVE DUAL GATED MOSFET — TWO-METER PRE-AMP

High S/N Ratio
Small & Compact
Works on 12 volts
D.C. and can be
mounted inside
transceiver



EASY TO INSTALL!

Brings in those weak signals.

\$11.99

KIT

\$15.99

ASSEMBLED

HW-202 SCANNER



\$29.95 Assembled

ELECTRONIC KEYS



\$16.97

Assembled

\$12.97

Kit

(ALL PRICES POSTPAID IN U.S.)



SANDLIN ELECTRONICS ENGINEERING


P. O. Box 909 • Jackson, Tennessee 38301

(Tennessee Residents Add Sales Tax)

end. After the cable is stripped, the slotted outer ferrule and coupling nut are slid onto the cable. Then the body assembly is pushed onto the cable dielectric but under the braid. The coupling nut is then slid over the body assembly, and the outer ferrule is pushed forward until it traps the cable braid against the rear flange of the body assembly. The ferrule then seats automatically. The resulting termination passed a 35-pound pull test.

For additional information about Amphenol 83-58FCP solderless connectors, contact Bunker Ramo RF Division, 33 East Franklin Street, Danbury, Connecticut 06810, or use *check-off* on page 142.

Bird Wattcher monitors rf power

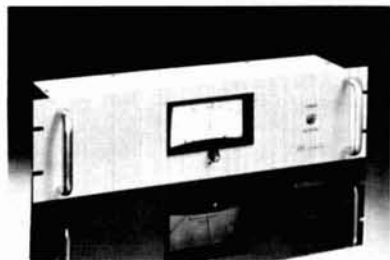

Bird Electronic Corporation recently announced its new Series 3162 rf power monitor/alarm Wattcher,® designed to warn of rf power drop-off below a set level to conform with FCC part 21.107 requirements. This fast-acting (50 millisecond) unit can be used, for example, at a mobile terminal site to measure forward power, reflected power (with a momentary-contact front-panel switch), and to obtain VSWR and optimum system data during routine maintenance. It is then left in the line to feed back a signal in response to the transmitter being keyed, indicating whether it is on the air and with sufficient power.

The series 3162 is available for operation at all telephone company communications frequencies and power levels; for example, 2-512 MHz and 1-500 watts. It is available in either a 12-volt dc model or a 117-volt ac model. A typical 12-volt model is priced at \$595.00.

For additional information, write Bird Electronic Corporation, 30303 Aurora Road, Cleveland (Solon), Ohio 44139; telephone (216) 248-1200, or use *check-off* on page 142.

The proof of the pudding is in the eating.



The proof of Triton IV is in owner satisfaction.

Here's some of the proof . . .

K4EME — This is my second TRITON IV. They are excellent xceivers! **WA8ICK** — Luv it. Dynamite! **W9NXU** — I am very thrilled with this unit, it is great. I think you have scooped the field. **WA0AYA** — I like CW and full break-in. (Beautiful) **K3TFU** — I love the unit. **WA3VEZ** — Rig is just great. Combined with your service makes a super transceiver. **WN0SED** — Beautiful radio to use. Magnificent CW filter! Just a pure joy. **W8IIT** — I have had my TRITON IV for two months and am delighted with it. **YN1MBV** — It is a very nice rig. **W3GTX** — New features very welcome. **W0BYC** — Bought one of the first TRITON II, like it so well I updated it with a TRITON IV. **W2TBK** — It is absolutely fantastic. **W800PI** — I am pleased with the rig. **WA3GJA** — Very-very-nice. Good audio quality. **W5ZBC** — The most outstanding rig I have ever used. **K8CJQ** — Excellent rig, Good filters. **W7BKK** — Very happy . . . getting excellent quality reports. **W2CET** — Power-signal reports good. **WB2UEH** — I like the compactness and appearance. **VE3IBK** — An excellent rig with superior receiving quality. **K4IVM** — I think it is tops. **WA4LOG** — I've become so used to dip, peak and adjust, this TRITON is a beautiful new experience. **KL7IHW** — Easy to set up—works great. **K4JXD** — Seems to be very FB rig. **WA7KHE** — Fantastic performance. Thanks for a fine rig. **WB4BPG** — No problems—fine rig. **VE1BZ** — Good work. **W9HQT** — Receiver better than expected, CW break-in is super. **WOAP** — Tremendous transceiver. I appreciate your engineering. **WA2ZRO** — Wonderful. **K0SFV** — Real nice rig. You thought of almost every feature and built it in. **KQ9DQ** — Beautiful. **W80JQ** — Beautiful radio; however, your ads do not do justice to the radio. **WN5SOH** — Very sophisticated—Easiest tuning rig ever. Very glad I bought it. **K30JV** — Very impressed. **W4LZP** — Very good results. Put out 100 watts as good as 300 watt rigs. **WA4DQY** — I think the TRITON IV is great. **W6QXN** — Appreciate full CW break-in. **W0INH** — Enjoy light weight. **VE3CYK** — I am extremely pleased with the clarity of receiver and after putting rig on the air, received unsolicited compliments on the audio quality of the transmitter. **K4PHY** — Was 3rd in USA, first in fourth district in WWCQ contest. **W8RYU** — Own Argonaut. Both fine rigs. **W4CDA** — Compact, light weight, good engineering. **WB2WZG** — TRITON IV is the most versatile CW/SSB radio I have ever used. **WB2FMV** — Outstanding. Highly pleased with performance. **WA8ACZ** — A real nice rig. I have owned about every other make. **W5EKG** — Works nicely. **WB4ECO** — I tried this rig, a pleasure to operate. **WA4YRK** — Excellent reports on audio. **WB8NKB** — Wonderful. **W9QPQ** — An excellent rig. Love it. **W8SOP** — Makes running SSB nets a real breeze. Also good on CW nets. **WL7IRT** — Fantastic rig. **W4MDB** — Has rekindled my interest and enthusiasm in Amateur Radio to an extent I hadn't thought possible. It far out distances any competitive product at any price. **W6EYR** — Very nice. Been a ham for 45 years and now solid state perfection. **W2RPH** — Excellent rig. **WN0TDK** — TRITON IV is a fabulous piece of equipment. **W5VIW** — Very nice rig **WB2LQF** — Wow! **W9JCV** — Tnx for giving us a FB piece of equipment made in the USA. **W8GHO** — Very pleased. **K4KXB** — Seems to have everything desired. **W4SZ** — A pleasure to operate. **W2FKF** — Greatest rig I ever had. So far in a month 34 QSO's without one miss. Been a ham since 1922. **W4GVC** — Nothing but complements. **WB9EZE** — Well pleased with performance and simplicity of operation. **K4ETI** — Rig is great. **WB8CNV** — Man—! what a rig. I've had this call since 1929. Never saw anything like it and I've seen them all! **WB2MZU** — Seems like everything the S----- O--- was supposed to be at one third the price. **WN0VHE** — I think it is a very good rig. **WB9FTD** — Break-in CW is very impressive. **K0CBA** — I believe it is one of the finest HF transceivers on the market. I can't tell you how pleased I am with the noise blanker. I can get on the air from my home station again for the first time in a few years. Other rigs with noise blankers just didn't hack it. **WA7YHW** — I am very pleased with this equipment. It is certainly of high quality. **W7IIA** — Excellent equipment. **WBORWA** — Couldn't be more pleased with it. It certainly has performed beautifully and is all I expected and more. **WB4QJT** — Like it very much — keep up the good work. **WN1YVX** — Really impressed with looks and performance. **W0NC** — Very FB rig. Performs up to specifications, an excellent design. **K8PBZ** — Already have TRITON II and IV. **W7KD** — This little "T-4" is smooth as silk . . . I've received some very flattering reports about transmitter voice quality and the CW operation is the greatest. **WN8TTO** — I found that the TRITON IV was the best rig on the market for around \$800. I love it! **W2JBK** — It is absolutely fantastic. **W8FEI** — Am amazed at receiver performance. I thought I had a top notch receiver with the H-----! **W1FYM** — Your guarantee is refreshingly proper. **W8MOK** — Sure makes a guy look twice at his old tube type gear. **W1TFS** — Finest CW ever, CW selectivity very good. **WB6IVR** — Very satisfied with TRITON IV. Just what I was looking for to use on my yacht. Thanks. **WA8ONP** — Also have a TRITON II. I am pleased that Al Kahn and the good guys at TEN-TEC thought of the CW operator! **W2EMX** — Excellent Amateur gear meets and exceeds advertised claims. **W0AMJ** — It looks like there is nothing left to be desired. It is beautiful. **W6SE** — The receive function is outstanding. It is superb in transmit. **W1BV** — In love with this fantastic gem. It's so easy and a pleasure to operate. **W6ASH** — Very happy with performance. Particularly impressed with full break-in and light weight. **WA0IMS** — By far the best rig I have ever operated. I am glad I decided on the TRITON IV and not one of the other transceivers on the market. **WA8HQO** — Thank you gentlemen.

Add your name to the growing list. See your TEN-TEC dealer or write for full details.



TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862
EXPORT: 5715 LINCOLN AVE., CHICAGO, ILL. 60646

TS-1 MICROMINIATURE ENCODER-DECODER


- Available in all EIA standard tones 67.0Hz-203.5Hz
- Microminiature in size, 1.25x2.0x.65" high
- Hi-pass tone rejection filter on board
- Powered by 6-16vdc, unregulated, at 3-9ma.
- Decode sensitivity better than 10mvRMS, bandwidth, ± 2 Hz max., limited
- Low distortion adjustable sinewave output
- Frequency accuracy, ± 25 Hz, frequency stability ± 1 Hz
- Encodes continuously and simultaneously during decode, independent of mike hang-up
- Totally immune to RF

Wired and tested, complete with K-1 element

\$59.95

K-1 field replaceable, plug-in, frequency determining elements

\$3.00 each

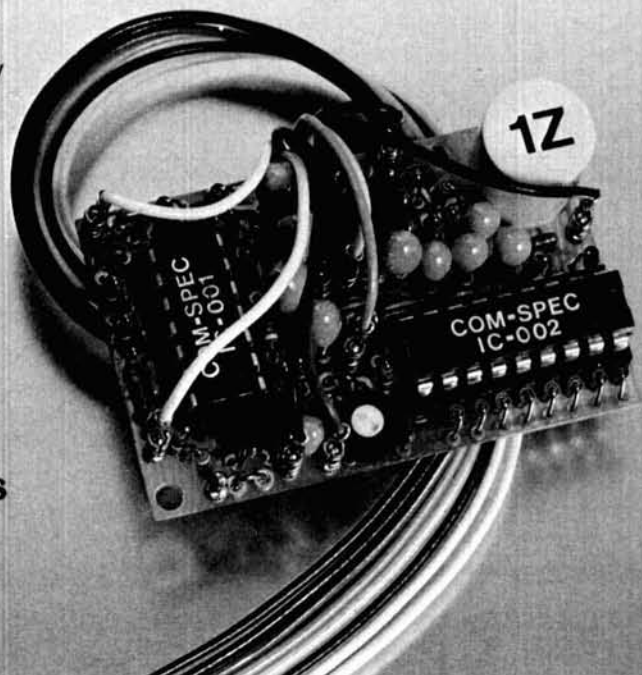

COMMUNICATIONS SPECIALISTS

P.O. BOX 153
BREA, CALIFORNIA 92621
(714) 998-3021

**some people
talk power-
we
deliver it.**



VHF Class C
Power Amplifiers

- Superb Craftsmanship
- State of the Art Performance
- Full One Year Warranty

MODEL P15A1 — 1-3 W input 12-25 W output. 13.6 V at 2 Amps, 100% duty cycle, solid state switching for only \$55 ppd.

MODEL P50A1 — 1-3 W input 40-60 W output. 13.6 V at 8 Amps, 85% duty cycle, COR switching w/LED indicator, spurious output filter. All for just \$139.

MODEL P50A1OC — 2-18 W input, 14-60 W output. 13.6 V at 7 Amps, 100% duty cycle, COR switching w/LED indicator, spurious output filter. It's yours for \$98 ppd.

Contact any of the following dealers for complete information on the M-Tech Engineering line:


Spectronics, Inc., Oak Park, Ill. 312-848-6778
Hobby Industries, Council Bluffs, Iowa 712-323-0142
Universal Service, Columbus, Ohio 614-221-2325
Adirondack Radio Supply, Amsterdam, N. Y. 518-842-8350
Arcade Electronics, Annandale, Va. 703-256-4610
Electronic Exchange, Souderton, Pa. 215-723-1200
Williams Radio Sales, Colfax, N. C. 919-993-5881
VHF Communications, Jamestown, N. Y. 716-664-6345
Electronics Int'l Svc. Co., Wheaton, Md. 301-946-1088

M-Tech Engineering, Inc.

Box C, Springfield VA 22151 (703) 354-0573

M-TECH . . . *The Quality Company*

K-ENTERPRISES

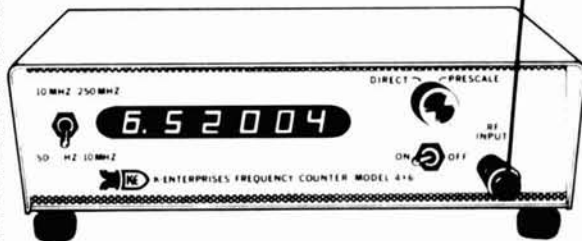

MODEL 4X6

50 HZ—250 MHZ \$270.00

300 and 500 MHZ PRESCALERS

FREQUENCY STANDARDS

MARKER and PEAKING GENERATORS

POWER SUPPLIES AMPLIFIERS

WRITE FOR FREE CATALOG



Phone:
918-676-3752



K-ENTERPRISES

Box 410 (N.W. of town)

FAIRLAND, OK 74343

We thought you might be interested in a 2-meter, synthesized, VHF-FM transceiver featuring 800 frequencies in 5KHz steps, variable RF output from 1 to 25 watts, 4 front panel selectable splits, a discriminator meter, and a price tag below five hundred dollars.

TRANSMITTER SPECIFICATIONS

Frequency Range: 144 to 148MHz. **Front Panel Frequency Splits:** Simplex, +0.6MHz, -0.6MHz, +1MHz, -1MHz. **Frequencies:** 800 (5KHz separation). **Modulation:** 16F3 \pm 5KHz for 100% at 1,000Hz. **RF Power Output:** 1-25 Watts, variable. **Frequency Stability:** Within \pm 0.001% from -20°C. to +60°C. **Hum & Noise:** Better than -30dB 2/3 rated system deviation at 1,000Hz. **Antenna Impedance:** 50 Ohms. **Switching:** Solid-state type. **Spurious & Harmonic:** At least 60dB below rated carrier power. **Microphone:** Tumer, low impedance. **Audio Frequency Response:** 300Hz to 3,000Hz, referred to +1, -8dB of 6dB/Octave de-emphasis curve. **Audio Distortion:** Less than 7% at 1,000Hz, 2/3 system deviation. **Frequency Display:** 6 digit, 7 segment HP LED. **Optional Accessory:** Plug in touch-tone encoder - \$50.

RECEIVER SPECIFICATIONS

Frequencies: 143 to 148.995MHz. **Usable Sensitivity (12dB sinad):** 0.35uV @ 50% audio. **Quieting Sensitivity (20dB):** 0.5uV minimum. **Squelch Threshold Sensitivity:** 0.25uV minimum. **Squelch Limit Sensitivity:** 2.0uV or less. **Modulation Acceptance Bandwidth:** \pm 7.5KHz minimum. **Adjacent Channel Selectivity:** 70dB minimum. **Spurious Response Attenuation:** 70dB minimum. **Intermodulation Attenuation:** 60dB minimum. **Local Oscillator Frequency Stability:** \pm 10 parts per million. **Audio Output Power:** 4.0 Watts into a 4 Ohm load @ less than 10% distortion. **Audio Frequency Response:** +2dB to -8dB from the standard 6dB per Octave de-emphasis from 300Hz to 3,000Hz. **Hum & Noise:** -50dB squelched and -30dB unsquelched. **Chassis Size:** 7 $\frac{1}{8}$ "W x 2 $\frac{5}{8}$ "H x 10"D.

SO, WE BUILT ONE FOR YOU.



Face plate also available in black.

The S 225 by AMCOMM[®]
An American Communications Corporation.

730 WEST McNAB ROAD · FORT LAUDERDALE, FLORIDA 33309

a revolutionary concept in kit building...

THE PROGRAMMABLE CLOCK KIT! \$27.95



SYSTEM 5000 is the first full-feature timepiece available in programmable form. After the circuit has been assembled and tested, all that is necessary is to add the appropriate switches and jumpers to easily program the system for the desired functions. The system may be expanded or reprogrammed at any time.

This represents a revolutionary concept in adaptability and flexibility. Build an Alarm/Clock/Calendar or a full feature Desk or Radio Station clock. Use the DUPLICATE TIME REGISTER to monitor GMT, another time zone, or as an elapsed timer. Add the optional relay to control AC or DC accessories. The possibilities are limited only by your imagination.

features

TIME OF DAY REGISTER • DUPLICATE TIME REGISTER • FOUR YEAR CALENDAR - month/day or day/month format • ALARM WITH SPEAKER TONE OUTPUT • ADDITIONAL ALARM - use for "his and hers" alarm or activate an accessory at a preset time • 10 MINUTE SNOOZE & "ID" REMINDER • 3 FUNCTION ALARM OUTPUT SELECT - tone, relay, or relay then tone • ONE HOUR DOWN COUNTER • BRIGHT FLUORESCENT DISPLAY - 5" blue or green digits with AM/PM • AUTOMATIC DISPLAY DIMMING • POWER FAILURE INDICATION • 12 & 24 HOUR DISPLAY • BLINKING OR STEADY COLON • SIMPLE FORWARD AND REVERSE TIME SETTING •

DIRECT DRIVE ELIMINATES RFI • SINGLE 9 VOLT BATTERY BACKUP • DISPLAY SECONDS CONTROL • HOLD AND RESET CONTROLS • 50/60 HZ OPERATION • 700 WATT RELAY OUTPUT OPTIONAL

SYSTEM 5000 includes all components, 2 time setting switches, and complete assembly and programming manuals. Switches for additional functions and relay are not included but are available as options. Case not included. Specify blue or green display.

RELAY OPTION - \$4.00

Includes 700 watt relay and all interface components. Will control AC or DC accessories such as appliances, stereos, etc.

SWITCH OPTION - \$3.75

Contains 4 black SPST pushbuttons, 2 black DPDT pushbuttons, and 2 black SPST slide switches. Programs all major features.

Send your check or money order today for fast delivery. Add \$1.00 per clock to cover shipping and insurance. Money back guarantee on all products if not fully satisfied. N.J. residents add 5% sales tax. Use your Master Charge or BankAmericard. Phone orders accepted.

add a new dimension to time itself... SERIES 2000 Decorator Clocks



A bright Fluorescent display provides easy to read numbers that brighten and dim automatically according to the light. The clear Acrylic tube with Acrylic or Hardwood end blocks gives these clocks a unique look of simple elegance. AM/PM & power failure indication. Seconds display button. 3 1/2" x 3 1/2" x 5 1/4". 50/60 HZ

Specify blue or green display, 12 or 24 hour time, and choice of Hardwood - Walnut, Zebrawood, or Rosewood.

FACTORY ASSEMBLED - 1 YEAR WARRANTY
EC 2001 Solid Acrylic "Time Capsule" \$59.95
EC 2002 Acrylic & Hardwood \$49.95

COMPLETE KITS - 90 DAY WARRANTY
EC 2001 K Solid Acrylic NEW! \$34.95
EC 2002 K Acrylic & Hardwood SPECIAL! \$29.95

 digital concepts

DIGITAL CONCEPTS CORPORATION
249 Route 46, Saddle Brook, N.J. 07662
201/845-7101

talk power by **TPL**
Econo-line



- Quality for an Economy Price
- Solid State Construction
- Linear Switch (FM/SSB)
- Broad Band

Model	Input	Output	Typical	Frequency	Price
702	10W-20W	50W-90W	10W in/70W out	143-149MHz	\$139.00
702B	1W- 5W	60W-80W	1W in/70W out	143-149MHz	\$169.00

Now get TPL COMMUNICATIONS quality and reliability at an economy price. The solid state construction, featuring magnetically coupled transistors and a floating ground, gives you an electronically protected amplifier that should last and last.

The Linear Bias Switch allows you to operate on either FM or SSB. The 702 and 702B are exceptionally well suited for 2-meter SSB. Typical power output levels as high as 100W PEP can be achieved with the proper drive.

The broad band frequency range means that your amplifier is immediately ready to use. No tuning is required for the entire 2-meter band and adjacent MARS channels on TPL's new *Econo-line*.

See these great new additions to the TPL COMMUNICATIONS product line at your favorite radio dealer.

TPL

Call or write for prices and information on TPL's complete line of amateur and commercial amplifiers.

COMMUNICATIONS INC.

1324 W. 135TH ST., GARDENA, CA 90247 • (213) 538-9814

Canada: A.C. Simmonds & Sons Ltd., 285 Yorkland Blvd., Willowdale, Ontario M2J 1S8
Export: EMEC Inc., 2350 South 30th Avenue, Hallandale, Fla. 33009



PORTA-PAK

MODELS IN STOCK INCLUDE:

BTL 8TH MT 25 MT15
GENAVE: ALL MODELS
ICOM 230 AND 22A AND 22 S
REGENCY HR6 HR28
MICRO-COM LINE
HEATHKIT HW 202
STANDARD SR-C826-MA


A GREAT IDEA FOR CHRISTMAS! WE'VE BEEN TOLD THAT THE DIFFERENCE BETWEEN A MAN AND A BOY IS THE PRICE OF HIS TOY. IF THIS IS TRUE, PORTA-PAK IS A MAN'S TOY WITH THE BOY'S TOY PRICE! PORTA-PAK MAKES YOUR MOBILE FM TRANSCEIVER A POWERFUL PORTABLE. THE PORTA-PAK IS A TOTALLY PORTABLE PERFORMANCE PACKAGE THAT WILL KEEP YOU IN TOUCH WITH WHAT IS HAPPENING. WHETHER YOUR COMMUNICATIONS NEED IS FOR BUSINESS OR PLEASURE PORTA-PAK WILL DO THE JOB. DELUXE PORTA-PAK HAS A 4.5 AHR CAPACITY AND THE SUPER PORTA-PAK HAS A 9 AHR CAPACITY.

THE PORTA-PAK INCLUDES THE CASE, BATTERY, AND CHARGER. GEL-CELL IS THE POWER SOURCE. GG-1245 IN STOCK FOR SAME DAY SHIPMENT: DELUXE \$67.50 + \$1.75 SHIPPING. THE SUPER. \$88.00 + \$2.75. GEL-CELL BATTERY ONLY \$29.20 + \$1.75. RUBBER DUCKIE ANTENNAS \$1.00. L.E.D. BATTERY CONDITION INDICATOR \$5.00.

PORTA-PAK, INC.
P.O. BOX 67
SOMERS, WI. 53171

the BRIMSTONE 144

2 METER FM TRANSCEIVER

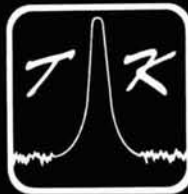

THE FIRST AND STILL THE ONLY 2 METER TRANSCEIVER THAT OFFERS IT ALL!




Size 9 1/2" x 10 1/2" x 3 1/4"

- No crystals to buy.
- Complete band average 143 to 149.99 MHz, 142 MHz optional.
- Independent transmit/receive frequency control, yet simplex with the flip of a switch.
- Autopatch, tone burst and sub-audible tone capability by simply plugging in the desired module.
- Very low transmitter spurious output. Some manufacturers have demonstrated their inability to eliminate unwanted spurious outputs. The Brimstone has demonstrated that non-harmonic spurious output at least - 70dB below the

- rated power output is possible when the radio is properly designed and constructed.
- The Brimstone 144 is designed for an unprecedented degree of component accessibility and plug-in modularity.
- The only amateur 2 meter FM transceiver with a TWO YEAR WARRANTY.

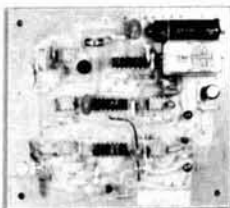We have changed our company name to **TEC-KAN, Inc.** and at this time we are offering a special Fall Sale Price on the Brimstone 144. Check with your dealer on the Fall Special and ask for the 6 page full color brochure.



REPEATER AND AUTOPATCH CONTROL MODULE RPT CM-4

If you are planning a repeater and need a control circuit, we have just what you need! Complete control of repeater as well as the autopatch. Local or remote control. If you are using telephone line control for your repeater the RPT CM is ideal because it uses an opti-coupler for complete line isolation and low voltage, low current control.

If you are using the TKI SCAP-3D, you can call your autopatch line number and the RPT CM will automatically answer and connect you allowing you to send tones over the phone to turn the repeater on or off, or access the autopatch and communicate through the repeater over the autopatch phone line.


When calling the repeater on the autopatch line, you have 20 seconds to either access the autopatch or turn the repeater off or on. If the proper codes are not sent within 20 seconds the RPT CM automatically disconnects.

If you call the autopatch number, hang up, wait 30 seconds and call the number again, the repeater transmitter will be keyed and a tone sent each time the phone rings, thus signaling a mobile operator to access the autopatch. If there is no one available to access the patch, it will automatically disconnect after 30 seconds of ringing.

It also features a COR "Hold" circuit, which is adjustable from 1 to 5 seconds, and automatic "time out" timer, that resets each time the receiver COR drops. No need to wait for the repeater to drop out to reset the timer.


If you are planning a repeater, all you need is a good transmitter and receiver and the TKI RPT CM Control Module.

Price \$79.95

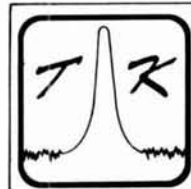

TEC-KAN, Inc.
2916 ARNOLD AVE.
BUILDING NO. 317
SALINA, KANSAS 67401
Tel. 913-823-2235

HANDI-TALKIE SCANNER KIT SK1402

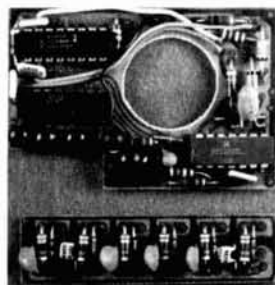


Six Channel Cmos Scanner Kit has provisions to include Mostek Touch-Tone Encoder Chip. Features dwell and normal operation. "Dwell" mode monitors each channel that has a signal on it for 8 seconds. "Normal" monitors in conventional manner. Manual operation locks out the scanner.

Includes LED channel indicators, schematic and installation instructions. Designed for Wilson 1402SM Talkie.

Scanner Kit Model SK1402 \$49.95
Includes Touch-Tone Encoder Chip Model SK1402TE \$58.95

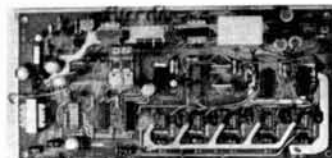Digi-Tran Pad, when ordered with Scanner Kit \$7.50




Size 9 1/8 x 4 1/8

AUTOPATCH SCAP-3D FEATURES

- 3 Digit access, single digit disconnect.
- 4 sec. time limit on access.
- Anti-falsing tone decoders.
- AGC with 30 Db dynamic range on all inputs and outputs.
- 3 digit on-off control of repeater or other devices.
- Remote inhibit or disconnect of autopatch as well as remote "off" function.
- Monitor amplifier allows monitoring all signals going into and out of the repeater.
- Adjustable level controls on all inputs and outputs.
- Jumpers on circuit board and frequency control pots on tone decoders allow field programming of access codes.
- Adjustable time out function. Patch will automatically disconnect in 30 to 90 seconds after it is accessed if no carrier is received.
- 90 days warranty.
- High quality tantalum and polyester capacitors used in tone decoder circuits to provide reliable low drift performance.
- Rugged G10 glass epoxy circuit board.
- High output level allows transmitter to be modulated through a dedicated phone line.
- Provisions for connecting LEDs for status indication at the local control point.
- Reverse polarity protection on supply line.
- Easily connected and adjusted.

Price \$199.95

ADVA

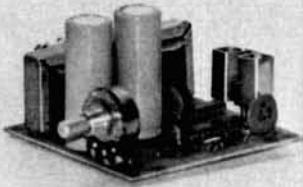

KIT \$11⁹⁵

ASSEMBLED \$17.95
ADD \$1.25 FOR
POSTAGE/HANDLING

VARIABLE POWER SUPPLY

- Continuously Variable from 2V to over 15V
- Short-Circuit Proof
- Typical Regulation of 0.1%
- Electronic Current Limiting at 300mA
- Very Low Output Ripple
- Fiberglass PC Board Mounts All Components
- Assemble in about One Hour
- Makes a Great Bench or Lab Power Supply
- Includes All Components except Case and Meters

OTHER ADVA KITS:

LOGIC PROBE KIT - Use with CMOS, TTL, DTL, RTL, HTL, and most MOS IC's. Built in protection against polarity reversal and overvoltage. Draws only a few mA from circuit under test. Dual LED readout. Complete kit includes case and clip leads. **ONLY \$7.95**

FIXED REGULATED POWER SUPPLY KITS - Short-circuit proof with thermal current limiting. Compact size and typical regulation of 0.5% make these ideal for most electronic projects. Available for 5V @ 500mA, 6V @ 500mA, 9V @ 500mA, 12V @ 400mA, 15V @ 300mA. Specify voltage when ordering. **\$8.95 ea.**

These easy to assemble kits include all components, complete detailed instructions and plated fiberglass PC boards. Power supply kits do not include case or meters. Add \$1.25 per kit for postage and handling.

MAIL NOW! FREE DATA SHEETS supplied with many items from this ad. **FREE ON REQUEST:** 741 Op Amp with every order of \$5 or more - 749 Dual Op Amp or two £100 FET's with every order of \$10 or more, postmarked prior to 3/31/77. One free item per order. **ORDER TODAY!** All items subject to prior sale and prices subject to change without notice. All items are new surplus parts - 100% functionality tested.

WRITE FOR FREE CATALOG #76 offering over 350 semiconductors carried in stock. Send 13¢ stamp.

TERMS: Send check or money order (U.S. funds) with order. We pay 1st Class postage to U.S., Canada and Mexico (except on kits) \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax. Foreign orders add postage. COD orders - add \$1.00 service charge.

MORE SPECIALS:

RC4195DN - 15V @ 50mA VOLTAGE REGULATOR IC. Very easy to use. Makes a neat Highly Regulated 15V Supply for OP AMP's, etc. Requires only unregulated DC (18-30V) and 2 bypass capacitors. With Data Sheet and Schematics. 8 pin MDIP **\$1.25**

LM741 FREE COMPENSATED OP AMP. μ A741, MC1741, etc. mDIP 5/S1 **3/51**

MC1468 DUAL 741 OP AMP mDIP **3/51**

RC4558 DUAL 741 OP AMP mDIP **3/51**

2N3904 NPN TRANSISTOR AMPLIFIER/SWITCH to 50 mA @100 **6/51**

ZENERS - Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2 400mW 4/S1 00
9.1, 10, 12, 15, 16, 18, 20, 22, 24, 27, or 33V (-10%) 1 Watt 3/S1 00

- MONEY-BACK GUARANTEE
- ALL TESTED AND GUARANTEED

ADVA

ELECTRONICS
BOX 4181 J, WOODSIDE, CA 94062
Tel. (415) 851-0455


FREE

IC or FET's WITH
\$5 & \$10 ORDERS.†
DATA SHEETS
WITH MANY ITEMS.

DIODES	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC's
ZENERS & RECTIFIERS	2N706 50.24	2N4901 3/51	2N5638 2/51	LM3404-5 \$1.75
1N450 10	2N718 24	2N4902 50.75	2N5640 2/51	LM3407 5 1.7.
1N458 10	2N720 48	2N4121 3/51	CP643 54.00	LM3407 8 1.75
1N458 10	2N719 3/51	2N4122 3/51	CP650* 55.00	LM3407 12 1.75
1N483 10	2N713 20.28	2N4124 5/51	CP651 54.00	LM3407 15 1.75
1N486 6/51	2N711 20	2N4248 5/51	E100 4/51	LM3407 24 1.75
1N746 10	2N1890 38	2N4249 5/51	E101 3/51	LM3706* 55
1N758 10	2N1893 38	2N4250 4/51	E102 3/51	LM3706 2.50
1N914* 15.5/51	2N2219 24	2N4274 5/51	E175 3/51	LM3800 1.29
1N962 10	2N2222 6/51	2N4302 50.29	MPF102 3/51	NE555V* 2/81
1N974 10	2N2222A* 5/51	2N4303 29	MPF104 3/51	NE568A 50.90
1N2064 6/51	2N2369 5/51	2N4338 51	MPF112 4/51	LM7900CN 29
1N3800 6/51	2N2906 10	2N4360M 2/51	MP9515 3/51	LM7900CN 29
1N4001* 12/51	2N2909 52	2N4381 51	SE1001 4/51	LM723H 2/81
1N4002 12/51	2N2905 50.24	2N4392 50.90	SE1002 4/51	LM723N* 3/51
1N4003 12/51	2N2906A 24	2N4416 51	SE2001 4/51	LM737N 51.00
1N4004 12/51	2N2907* 5/51	2N4486A 50.80	SE2002 4/51	LM741CN 3/51
1N4005 10/51	2N3553 51.50	2N4856 51	SE5001 3/51	LM741CN* 4/51
1N4006 10/51	2N3563 4/51	2N4861 51	SE5002 3/51	LM741CN14 34
1N4007 10/51	2N3564 4/51	2N4867 2/51	SE5020 53.00	LM741CN 35
1N4148 15/51	2N3565 10	2N4888 2/51	T1573 3/51	74BC2 DIP 05
1N4154* 25/51	2N3568 6/51	2N4881 52.50	T1575 3/51	74BC2 DIP 100
1N4370 10	2N3638 6/51	2N4889 51		74BC2 DIP 800
1N4372 10	2N3638A 5/51	2N4955 3/51	DIGITAL IC's	LM1304N 1.15
1N4454 15/51	2N3641 5/51	2N5087 4/51	MM5520N 52.55	LM1458N* 3/51
1N4728 10	2N3642 5/51	2N5088 4/51	SN7400N 16	LM2110 51.00
1N4753 3/51	2N3643 6/51	2N5138 10	SN7410N 16	KR2506CP 5.5
1N5231 10	2N3644 4/51	2N5135 6/51	SN7420N 16	72400E 1.95
1N5236 4/51	2N3646 4/51	2N5138 5/51	SN7451N 18	CA3028A 1.75
	2N3688 10	2N5139 5/51	SN7451N 18	CA3046 5.5
	2N3690 3/51	2N5163 3/51	SN7473N 38	LM3090N 1.45
	2N3691 10	2N5197 55.00	SN7475N 48	CA3086* 5.5
1N5139 10	2N3692 4/51	2N5199 2.50	SN7490N 44	LM3900N 55
1N5144	2N3821 50.80	2N5210 3/51		LM3090N 1.50
OS 1454MHz	2N3822 70	2N5308 2/51	LINEAR IC's	RC4195DN* 5.50
F 432MHz	2N3823 40	2N5397 51.50	LM100H 57.50	RC4195DN* 1.25
MV220 10	2N3866 75	2N5432 1.90	LM301AN 27	RC4195TR* 2.25
MV232 10	2N3903 10	2N5457 3/51	LM307H 27	LM2596CN 2.00
MV1620 10	2N3906 6/51	2N5458 50.38	LM3080N 18	RC4558DN 55
MV1634 5/51	2N3919 55.00	2N5484 3/51	LM309K 1.25	NE555V 95
MV1866 10	2N3922 5.00	2N5486 2/51	LM311N 90	NE558V 50
MV1872 10	2N3924 3.20	2N5543 52.00	LM320K 1.35	A7805UC 1.25
MV2201 10	2N3958 1.15	2N5544 2.50	LM320K-12 1.35	8038 DIP* 3.75
MV2205 5/51	2N3970 1.00	2N5561 12.00	LM320K-15 1.35	DM75482 89

*SUPER SPECIALS:

1N914 100V/10mA Diode	20/51	MPF102 200MHz RF Amp	3/51
1N4001 100V/1A Rect.	15/51	40673 MOSFET RF Amp	\$1.75
1N4154 30V 1N414	25/51	LM324 Quad 741 Op Amp	94
BR1 50V 1/4A Bridge Rect	4/51	LM376 Pos Volt Reg mDIP	55
2N2222A NPN Transistor	6/51	NE555 Timer mDIP	2/51
2N2907 PNP Transistor	6/51	LM723 2.37V Reg DIP	3/51
2N3055 Power Xistor 10A	69	LM741 Comp Op Amp mDIP	4/51
2N3904 NPN Amp/Sw @100	6/51	LM1458 Dual 741 mDIP	3/51
2N3906 PNP Amp/Sw @100	6/51	CA3086 5 Trans Arry DIP	56
CP650 Power FET 1/2Amp	55	RC4195DN - 15V/50mA mDIP	1.25
RF391 RF Power Amp Transistor 10.25W @ 3-30MHz TO-3			\$5.00
555X Timer 1/2 1hr Different pinout from 555 (w/data)			3/51
RC4194K Dual Tracking Regulator 10.2 to 30V @ 200mA TO-66			\$2.50
RC4195TK Dual Tracking Regulator 15V @ 100mA (TO-66)			\$2.25
8038 Waveform Generator 1/2A Wave With Circuits & Data			\$3.75

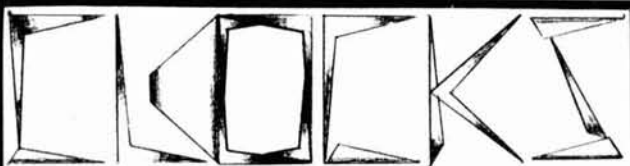

6 digit AUTOMOTIVE CLOCK KIT complete with a CRYSTAL TIMEBASE accurate to .01 percent. 12 volts d.c. operation - built in noise suppression and voltage spike protection. Readouts blank when ignition is off - draws 25 mA in standby mode. Has .3 in. readouts. Use it in your car or for all applications where a battery-operated clock is needed. Approximate size 3" x 3.5" x 1.75"

WITH BLACK PLASTIC CASE \$34.95 ppd.
WITHOUT CASE \$29.95 ppd.
ASSEMBLED AND TESTED \$45.95 ppd.

CMOS CRYSTAL TIMEBASE KITS with .01 percent accuracy. 5-15 v.d.c. operation. Draws only 3 mA at 12 volts. Single I.C. - very small size - the P.C. board is 7/8" x 1-5/8". Choose a main output of 50 or 100 Hz., 60 Hz., 500 or 1000 Hz., or 1 Hz. Several related frequencies are also available on each board, in addition to the main ones listed above. Be sure to specify the Frequency you want. All kits are \$10.95 ppd.

Flyer available -

NEXUS

TRADING CO.

Box 3357 San Leandro, Ca 94578

EMPLOYMENT OPPORTUNITIES FOR TECHNICALLY ORIENTED HAMS

as
Engineer, Technician, or Trainee

Degree Not Required

Work in suburban Washington, D.C.

Personnel sought with training or skills in

- circuit design
- module testing
- prototype fabrication
- troubleshooting
- RF interference analysis
- technical reports

Openings at all levels.

Write or call Personnel Department

ATLANTIC RESEARCH CORPORATION
5390 Cherokee Avenue
Alexandria, Virginia 22314
(703) 354-3400 X501, 502

It's New! It's from Midland with...

4,000

FREQUENCY CAPABILITY

144-148 MHz,
P.L.L. Synthesized

400 frequencies
in 10 KHZ steps

+

400 more frequencies
with 5 KHZ shift-up

+

3,200 more with 4 available offsets

Midland introduces a practical 25-watt, 2-meter mobile transceiver with operation programmed throughout the 144-148 MHz band...at a practical price. In operation, a large-scale L.E.D. digital readout displays the frequency selected through the advanced Phase Lock Loop tuning circuit. Duplex operation with any of four transmitter offsets is available at a touch of a button...or operate simplex. There is a full-range variable squelch control, a large lighted S/RFO meter, duplex and TX indicator lights.

Inside, the dual conversion superheterodyne receiver has active automatic gain control, multiple FET front end with high Q resonator filter and ceramic filters in both RF stages. The transmitter delivers an honest 25 watts

output power, switchable to 1 watt low power. There's automatic polarity protection and an APC circuit guarding final output transistors. A connector is provided for tone burst and discriminator meter.

All this is contained in a rugged, all-metal cabinet 2 $\frac{5}{8}$ " high by 6 $\frac{3}{4}$ " wide by 9 $\frac{5}{8}$ " deep, designed with a forward-projecting speaker housing for improved sound quality in mobile installation.

Midland's new MODEL 13-510 is supplied complete with push-to-talk microphone, crystals for +600 and -600 offsets, mobile mounting bracket, power cord and hardware. You'll find it at your Midland Amateur dealer.



MIDLAND
INTERNATIONAL®
Communications Division



Write for Midland's Amateur
Catalog: Dept. HR, Box 1903,
Kansas City, MO 64141

flea market



RATES Non-commercial ads 10¢ per word; commercial ads 40¢ per word both payable in advance. No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing). Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of second preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

HAM RADIO HORIZONS, a super new magazine for the Beginner, the Novice and anyone interested in Amateur Radio... What it's all about, How to get started, The fun of ham radio. It's all here and for just \$7.00 per year until January 1st. Then it will be \$10.00. **HURRY! HURRY!** Ham Radio HORIZONS, Greenville, NH 03048.

NEW ADJUSTABLE THREE OUTPUT REGULATED POWER SUPPLY, plus 900 parts worth \$400.00 list. Solid state TV recorder electronic unit. Schematics, parts cross reference. Free brochure. \$17.95 plus \$3.50 S&H, USA. Master Charge, BankAmericard. Satisfaction guaranteed. Madison Electronics Company, Incorporated, Box 369, D77, Madison, Alabama 35758.

SWAN CYGNET 260 (built-in AC-DC supplies) . . . Super rig in excellent condition with best of Swan's modifications, manual, and Swan mobile mike. \$260. HQ-180AC . . . Excellent, with noise immunizer, matching speaker; manual. For those who appreciate a premium receiver. \$365. WA9RAQ, Morrie Goldman, 5815 N. Christiana, Chicago, 60659.

STOP don't junk that television set. ASE manufactures the world's most complete line of television picture tubes. Over 1700 types. Most types immediate delivery. Tubes for Old or New TV's, black & white and color. 2 year factory warranty. Lowest prices anywhere. Allied Sales & Engineering, Inc., Dept. 22, Pimento, IN 47866. Telephone 812-495-6555.

NOT C.B. decals, 1 x 2 inches, black over white, plastic, weatherproof, peel and stick. Great for load coils, radios, control heads, etc. Stop having your radio gear mistaken for C.B. radio. 10 for \$1.00, with SASE 12 for \$1.00, 100 for \$7.00. WA4SGI, Ronald P. Pitts, 2113 Lester Lane, Birmingham, AL 35226.

TELETYPE EQUIPMENT for beginners and experienced operators. RTTY machines, parts, supplies. Beginner's special: Model 15 Printer and demodulator \$139.00. Dozen black ribbons \$6.50; case 40 rolls 11/16 perf. tape \$17.50 FOB. Atlantic Surplus Sales, 3730 Nautilus Ave., Brooklyn, N. Y. 11224. Tel: (212) 372-0349

WANTED: Rohn 25 or 45. Will take down if it's in the New England area. Write WIGOO, c/o HAM RADIO Magazine, Greenville, NH 03048.

VARIABLE CONDENSORS, Johnson 154-3, 19-488pt, 2KV, used, excellent condition, \$12 each or 3 for \$30, postpaid. KP4DSD, Box 297, Sabana Seca, P. R. 00749.

VERY in-ter-est-ing! Next 4 big issues \$1. "The Ham Trader," Sycamore, IL 60178.

HRO-500 GENERAL COVERAGE RECEIVER. Factory overhauled 1975, with speaker, mint condition. \$1200. HAL RVD-1002 visual display for RTTY. Art Levy, WBØDJX, 4900 Deertrail Court, Ft. Collins, Colo. 80521. (303) 484-1600.

SYNTHESIZER. See Ham Radio, July 76, pg. 20-23, figures 21 to 24. Kit for \$115, assembled and tested, \$140. Power supply to run from 117 volts additional \$15.00. CTD, P. O. Box 708, Cambridge, MA 02139.

BUY — SELL — TRADE. Write for free mailer. Give name, address and call letters. Complete stock of major brands, new and reconditioned equipment. Call for best deals. We buy Collins, Drake, Swan, etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Ks. 66204. 913-381-5901.

SAVE! Bomar FM, xtals \$4.00 ppd. Dentron, Hustler, CushCraft, W. M. Nye, Ameco. Used gear. Complete catalog - write Ferris Radio, 308 E. Harry, Hazel Park, Mich. 48030.

AMAZING! The "Electronics Sourcebook" reveals how, where to obtain 101 free samples, manuals, publications. \$3.75 ppd. Brochure free. Technical Publications, 1405A Richland, Metairie, LA. 70001.

RECONDITIONED TEST EQUIPMENT for sale. Catalog \$5.00. Walter, 2697 Nickel, San Pablo, Ca. 94806.

TENNELEC MEMORYSCAN sixteen channel VHF/UHF frequency synthesized receiver/scanner. Used, mint condition, \$250 or best offer. Raymond Glueck, 1 Rutledge Road, Pine-Brook, N. J. 07058. 201-227-5361.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines. Many other suppression accessories. Literature. Estes Engineering, 930 Marine Dr., Port Angeles, WA 93862.

TRAVEL-PAK QSL KIT — Send call and 25¢; receive your call sample kit in return. Samco, Box 203, Wyantskill, N. Y. 12198.

LOOKING FOR USED GEAR? Buyers & Sellers radio brokerage has the equipment you want at the right prices. Call our Ham Gear Hotline 617-536-8777 Monday-Friday, 9-9.

NAMEBADGES \$1.50 — Name and Call Sign \$2.00. Engraved plastic with pin, clutches, or adhesive. Black, white, red, blue. Include payment with order. Special prices on club badges and Hamfest plaques. Donan Engraving, P. O. Box 07155, Lakewood, Ohio 44107.

FREE Electronics Surplus Catalog. Electronic Specialties, 1659 Wetmore, Tucson, AZ 85705.

MOBILE BONDING STRAPS under 50¢ each. Literature. Estes Engineering, 930 Marine Drive, Port Angeles, Wash. 98362.

COMPLETE LINE KLM, CushCraft, Covercraft dust covers, SCS amplifiers, Regency, Trix Towers. Call or write Radios Unlimited, 86 Balch Ave., Piscataway, N. J. 08854. 201-752-4307.

ETCH IT YOURSELF PRINTED CIRCUIT KIT, Photo-Positive Method — All the supplies for four P.C. boards, direct from magazine article in less than 2 hours. Only \$19.95. S.A.S.E. for details. Excel Circuits, P. O. Box 891, Troy, Michigan 48099, 313-549-0440.

DIRECT CONVERSION RECEIVER KITS for AM or CW. Write WB9MBH, 3132 North Lowell Avenue, Chicago, Illinois 60641.

HW-101 W/AC PS \$250 like new. Ranger I \$75. HA-800 3.5-50GHz solid state rcvr \$75. Will ship Greyhound collect. Hal W6TU, (805) 644-4871.

YAesu EQUIPMENT OWNERS — Present or Prospective — Join the five-year-old, 2000-member, 40-country, International Fox-Tango Club. Members receive valuable monthly Newsletter, money-saving purchasing service, technical committee consultation, free ads, FT net, more. Back issues of Newsletter available from 1972. To join, send \$5 for calendar year (includes all 1976 issues of Newsletter) or \$1 creditable towards dues, for complete information and sample Newsletter. Milton Lowens, WA2A0Q/4, 248 Lake Dora Drive, W. Palm Beach, Fl. 33411.

MODERN CODE PRACTICE. 0-22 wpm on four 60 min. cassettes \$10. Royal, P. O. 2174, Sandusky, Ohio 44870.


TECH MANUALS for Govt. surplus gear - \$6.50 each: SP-600JX, URM-25D, OS-8A/U, PRC-8, 9, 10. Thousands more available. Send 50¢ (coin) for 22-page list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

FIGHT TVI with the RSO Low Pass Filter. For brochure write: Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada. MIS 3B4.

TELL YOUR FRIENDS about Ham Radio Magazine!

5 KW PEP INPUT

WITH THIS NEW BALUN

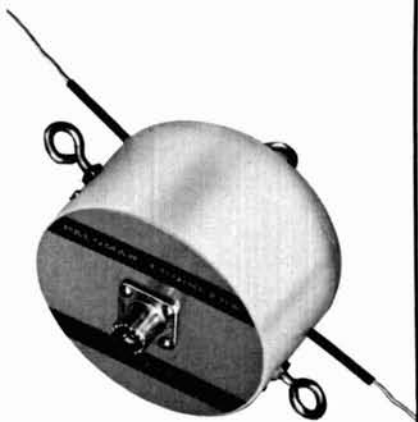

On all bands 160 to 10 meters.

Runs cool as a cucumber at its CCS rating of 2 KW (Continuous output power through the balun at matched load).

4" dia. Wt. 24 oz. \$32.50 PPD.

AND FOR FULL LEGAL POWER

the time tested Model 1K balun is still available. Rated at 1 KW CCS (3 KW PEP input).

2 1/2" dia. Wt. 9 oz. \$16.95 PPD.

ONLY PALOMAR BALUNS HAVE ALL THESE FEATURES

- Toroidal core for highest efficiency.
- Teflon insulated wire to prevent arc-over. OK for tuned feeders.
- Stainless steel eyebolts take antenna tension. Won't rust, won't pull apart.
- Epoxy filled case. Absolutely waterproof.
- Lightning protection built-in.
- Wideband 1.7 to 30 MHz.
- Hang-up hook provided.
- Now available in either 1:1 or 4:1 ratio. 1:1 ratio matches 50 or 75 ohm coax to 50 or 75 ohm balanced load (dipoles and inverted Vees). 4:1 ratio matches 50 or 75 ohm coax to 200 to 300 ohm balanced load.

Free descriptive brochure on request. Order direct.

Model 2K \$32.50 Model 1K \$16.95
Center insulator without balun \$7.95

Postpaid U.S. & Canada.

Specify ratio 1:1 or 4:1


California residents add 6% tax.

Send check or money order to:

PALOMAR ENGINEERS
BOX 455, ESCONDIDO, CA 92025
Phone: (714) 747-3343

DUPLEXER & CAVITY KITS...

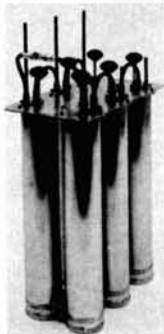Now available for you fully assembled and tuned!



• UPGRADE YOUR REPEATER WITH A RF TECHNOLOGY DUPLEXER.

• ALL DUPLEXERS AND CAVITIES ARE TEMPERATURE COMPENSATED WITH INVAR® AND MEET ALL COMMERCIAL STANDARDS

• ONLY TOP QUALITY MATERIALS GO INTO OUR PRODUCTS.

• BOTH KITS & ASSEMBLED DUPLEXERS AND CAVITIES ARE AVAILABLE TO YOU AT A SAVINGS TO YOU.

Mod. 62-3...6 cav., 2 mtr., insertion loss 0.6 db with isolation 100 db typical; pwr. 350 w. Kit \$349 ea.-Assembled \$439.

Mod. 4220-3...4 cav. 220 MHz insertion loss 0.6 db with 80 db isolation typical; pwr. 350 w. Kit \$249 ea. - Assembled \$329.

Mod. 4440-3...4 cav. 440 MHz, insertion loss 0.6 db with 80 db isolation typical; pwr. 350 w. Kits \$249 ea. - Assembled \$329.

Mod. 30 Cavity Kits: 2 mtr. \$65 ea., 220 MHz \$65 ea., 440 MHz \$65 ea.; 6 mtr. \$115 ea. Add \$15 for Assembled Kit.

Also available: 6 mtr., 4 cav. Kit \$399-Assembled \$499, 2 mtr. 4 cav. Kit \$249-Assembled \$329, 440 MHz TV Repeater Duplexer

Only hand tools are necessary to assemble Kits!

Send your order to: Distributor: **TUFTS RADIO**, 386 Main St., Medford, Mass. 02155. Phone (617) 395-8280.

(Prices F.O.B. Medford, Mass. All units can be shipped U.P.S.-C.O.D. orders require \$50 deposit. —Mass. residents add 5% sales tax.)

flea market

TOWER AND ACCESSORIES FOR SALE: Tri-Ex LM-354, TA-54L tilt over, CO-3 coax standoffs, thrust bearing, heavy duty mast, Ham-M rotor complete. New cost over \$1700.00. Take best offer. You pick up, Los Angeles area. Allen White, (415) 854-4771, 6 p.m. - 8 p.m.

RUBBER STAMP, name/call/QTH \$2.50 ppd. (CA residents add tax). LWM Press, Box 22161, San Diego, CA 92122.

TELETYPEWRITER PARTS, gears, manuals, supplies, tape, toroids. SASE list. Typetronics, Box 8873, Ft. Lauderdale, Fl. 33310. Buy parts, late machines.

PORTA-PAK the accessory that makes your mobile really portable. \$67.50 and \$88.00. Dealer inquiries invited. P. O. Box 67, Somers, Wisc. 53171.

DON'T READ THIS AD Unless you want a good deal and good service on your next ham radio or hi-fi purchase. Thousands of satisfied customers nation-wide have made us the largest volume communications and hi-fi dealer in the country. We are factory-authorized dealers for Kenwood, Drake, Collins, ICOM, Tempo and over 100 other brands of amateur radio and hi-fi gear. We have something for you! Call or write us today for our quote and become one of the many happy and satisfied customers of **HOOSIER ELECTRONICS, INC.**, P. O. Box 2001, Terre Haute, Indiana 47802. (812)-238-1456.

LARSEN ANTENNAS (our specialty) 2,432 magnetic, trunk-lip 5/8 \$33.00, 5/8 ground plane \$45.00. BankAmericard and Mastercharge accepted. 201-962-4695. Narwid Electronics, 61 Bellot Road, Ringwood, NJ 07456.

SURPRISES GALORE! Projects, ham radio, music synthesizers, etc. IC's, pots, hardware, crystals, keyboards, resistors, etc. Send 13¢ stamp for catalogue. UTEP, Box 26231A, Salt Lake City, Utah 84125.

QRP TRANSMATCH for HW7, Ten-Tec, and others. Send stamp for details to Peter Meacham Associates, 19 Loretta Road, Waltham, Mass. 02154.

VHF G.E. MASTR PRO 80 W xmtr, 4 chnl, UHS rcvr cg in xmtr 186.2. 1969 model. .22-.82 .28-.88, .34-.94, .76-.76. WA7PUD, 1720 N. E. 9th, E. Wenatchee, Washington 98801. \$350.00. 509-884-3891.

SYNTHESIZER, see Ham Radio, July 76, pg. 20-23, figures 21-24. Kit for \$115. Assembled and tested, \$140. Power supply to run from 117V additional \$15. CTD, P. O. Box 708, Cambridge, MA 02139.

FREE CATALOG. Calculators \$4.95 each, Ultrasonic Devices, Digital Thermometers, Strobe Light Kits, Memories, Photographic Electronic Flash Units, Rechargeable Batteries, LEDs, Transistors, IC's, Piezoelectric Crystals, Toroidal Cores, Unique Components. Chaney's, Box 27038, Denver, Colo. 80227.

WANTED: Car telephones and mobile telephone parts, heads, cables, etc. Greg Hyman, 87 Yonkers Ave., Yonkers, N. Y. 10701. 914-476-4330.

SELL — Touch Tone Pad, Solid State, Subminiature size, great for HT's, \$33 shipped. Regency HR2A, excellent condition, unmodified, \$150 shipped. Knight VOM KG-640, mint, \$20 shipped. WA9WDB/P5, John Teles, 10511 Tencoco, Houston, Texas 77099.

MANUALS for most ham gear, 1939/70. List \$1.00. Send SASE (or 25¢) for one specific model quote. Hobby Industry, W4JJK, Box H864, Council Bluffs, Iowa 51501.

PLEASE! Will pay for interconnection diagram for the 3 units — IMD, TDC, ACU — sold by PINON Electronics. Units sent to European ham. Want to save face for U.S. mfr. W4SXX, Rt. 3, Box 930, Merritt Island, Fla. 32952.

SIDSWIPER only \$13. Airmailed USA. Kungsimport, Box 257, Kungsbacka, Sweden.

RTTY DEMODULATORS — Immediate delivery. New ST-5's with auto-start and AK-1 AFSK audio oscillator. \$185 or \$25 and balance UPS COD. David Tancig, 618 W. White St., Champaign, Ill. 61820.

MOTOROLA HT220, HT200, Pageboy, and other popular 2M FM transceiver (Standard, Regency, etc.) service and modifications performed at reasonable rates. WA4FRV (804) 320-4439 evenings.

MERRY XMAS and HAPPY NEW YEAR from W0CVU. On the air since 1913. The Worlds finest hobby.

HQ-180A-C Hammarlund Rcvr for sale. Exc. cond. \$249, you pick up or pay shipping. Loren Jones, WA3JUN, 224 W. Willow Grove Ave., Phila, Pa. 19118. Phone 215-242-1435.



Aha, the SECRET of PC Board success finally revealed. A perfectly balanced lighting tool combining magnification with cool fluorescence. Excellent for fine detail, component assembly, etc. Lens is precision ground and polished.

Regularly \$70.00. Now, over 30% discount (only \$49.00) to all licensed Hams, verified in Callbook. Uses T-9 bulb (not supplied).

Include \$3.00 U.S. postage, or \$4.00 in Canada. \$5.00 elsewhere. California Residents include 6% sales tax. Or send stamped envelope for free brochure of other incandescent or fluorescent lamps suitable for all engineers, architects, students, etc.

Mastercharge and BankAmericard accepted

D-D ENTERPRISES

Dept. A, P. O. Box 7776
San Francisco, CA 94119

test for resonant resistance with an omega-t antenna noise bridge



The Omega-t Noise Bridge is an inexpensive and flexible testing device that can effectively measure antenna resonant frequency and impedance. This unique piece of test equipment does the work of more expensive devices by using an existing receiver for a bridge detector. There is no longer a need for power loss because of impedance mismatch. Get more details or order now!

Model TE7-01 for 1-100 MHz Range \$29.95
Model TE7-02 for 1-300 MHz Range \$39.95

ELECTROSPACE SYSTEMS, INC.

320 TERRACE VILLAGE
RICHARDSON, TEXAS 75080
TELEPHONE (214) 231-9303

Sold at Amateur Radio Dealers
or Direct from Electrospace Systems, Inc.

SPECIALS FROM

MHz electronics

Fairchild VHF Prescaler Chips

11C01FC	High Speed Dual 5-4 Input no/nor	15.40
11C05DC	1 GHz Counter Divide by 4	74.35
11C05DM	1 GHz Counter Divide by 4	110.50
11C06DC	UHF Prescaler 750 MHz D Type flip/flop	12.30
11C24DC	Dual TTL VCM same as MC4024P	2.60
11C44DC	Phase Freq. Detector same as MC4044P	2.60
11C58DC	ECL VCM	4.53
11C70DC	600 MHz flip/flop with reset	12.30
11C83DC	1 GHz 248/256 Prescaler	29.20
11C90DC	650 MHz Prescaler Divide by 10/11	16.00
11C90DM	same as above except Mil. version	24.00
11C91DC	605 MHz Prescaler Divide by 5/6	16.00
11C91DM	same as above except Mil. version	24.00
95H90DC	350 MHz Prescaler Divide by 10/11	9.50
95H90DM	same as above except Mil. version	16.50
95H91DC	350 MHz Prescaler Divide by 5/6	9.50
95H91DM	same as above except Mil. version	16.50

GIAY-3-8500 Gain Chip	29.95
T.I. TMS4060/C2107, 4K RAM	19.01

Batteries

NI-CAD's AA cells 1.25 volts at 500 mahr.	\$0.49
Gel-Cell 12 volts at 1.5 Amp Hr. #GC-1215	\$19.95

Crystals

1.000000 MHz	4.95	JUST ARRIVED! These radios have just been pulled out of service. Set up for approx. 150 MHz.
5.000000 MHz	4.95	Clean. All tubes included. No accessories. Prices FOB Phoenix.
10.000000 MHz	4.95	
3579.545 KC	2.95	Motorola U43 GGT \$49.95
		GE TPL \$99.95
		GE MT-33 \$39.95
		G.E.L. FM Broadcast Exciter (Stereo) contains the following: 1 ea. Model FM100, FM200, FM400A, FM600, FM800A, and SC200 \$299.00

NEW

Motorola, Motorcycle Radio — Model T33BAT \$39.95 FOB Phoenix
R390A (Not working but repairable) \$199.00 FOB Phoenix

Motorola MC14410CP CMOS tone Generator uses 1 MHz Crystal to produce standard dual frequency telephone dialing signal. Directly compatible with our 12 key Chomeric pads. Kit includes the following.

- 1 MC14410CP
 - 1 Touch Tone Pad
 - 1 1 MHz Crystal
 - 1 Printed Circuit Board (From Ham Radio Sept. 1975)
- And all other parts for assembly. **\$19.95**

Fairchild 95H90DC Prescaler divide by 10 to 350 MHz. Will take any 35 MHz Counter to 350 MHz. Kit includes the following.

- 1 95H90DC
 - 1 2N5179
 - 2 UG-88/u BNC's
 - 1 Printed Circuit Board
- And all other parts for assembly. **\$29.95**

Fairchild 11C90DC Prescaler divide by 10 to 650 MHz. Will take any 65 MHz Counter to 650 MHz or with a 82590 it will divide by 10/100 to 650 MHz. This will take a 6.5 MHz counter to 650 MHz. Kit includes the following.

- 1 11C90DC
 - 1 2N5179
 - 2 UG-88/U
 - 1 MC7805CP
 - 1 Bridge
 - 1 Printed Circuit Board and all other parts for assembly. 82590 add \$5.70 to total.
- \$59.95**

10.7 MHz Narrow Band Crystal Filter \$7.95
Bandwidth 13 kHz
Type 2194F
Input & Output Impedance 2700 ohms.
Two Filters in series gives steeper sides & a 30dB Bandwidth of ± 15 kHz.

Johanson Trimmer Capacitors		Ferrite Beads	
.6 to 6 pf.	\$1.95	12 for .99 or	120 for 9.99
.8 to 10 pf.	\$1.95		
1 to 14 pf.	\$1.95		
1 to 20 pf.	\$1.95		

FET's

2N3070	1.50	2N5460	.90	MFE3002	3.35
2N3436	2.25	2N5465	1.35	MPF102	.45
2N3458	1.30	2N5565	5.45	MPF121	1.50
2N3821	1.60	3N126	3.00	MPF4391	.80
2N3822	1.50	MFE2000	.90	U1282	2.50
2N4351	2.85	MFE2001	1.00	MMF5	5.00
2N4416	1.05	MFE2008	4.20	40673	1.39
2N4875	1.75	MFE2009	4.80	40674	1.49

TUBES

2E26	4.00	572B/TJ160L	25.00	8072	32.00
3B28	4.00	811A	7.95	8156	3.95
4X150A	15.00	931A	11.95	8908	9.95
4X150G	18.00	5849	32.00	8950	5.50
4CX250B	24.00	6146A	4.75	3-1000Z	135.00
4X250F	25.00	6146B/8298A	5.75	4-250A	24.95
4CX250K	27.00	6907	35.00	4-125A	20.95
4CX350A/8321	35.00	7377	40.00	4-65A	15.95
DX415	25.00	7984	4.95		

TRANSFORMERS

F-22A	6.3vct at 20 amps	\$7.91
F-21A	6.3vct at 10 amps	\$5.77
F-18X	6.3vct at 6 amps	3.56
F-93X	6.5v to 40v at 750 ma.	3.53
F-92A	6.5v to 40v at 1 amp	4.59
F-91X	6.5v to 40v at 300 ma.	2.72
N-51X	Isolation 115vac at 35va.	2.80
Model D-2	6.5v at 3.3 amps	4.95
	6.5v at 3.3 amps	
C-912-034	22vct at 200 ma.	
	11v at 250 ma.	1.49
BE-12433-001	30v at 15 ma.	.49
C-404-024	18vct at 400 ma.	1.49
BGH-9	6.3vct at 10 amps	
	115 vac at 100va Isolation	6.95
F-107Z	12V @ 4A or 24 V @ 2A	7.80

Erie High Voltage Power Supply

TSK-209-000
Input 24vdc
output #1 100 vdc — 12.95
#2 400 vdc +
#3 15000 vdc
Size: 3 1/2" x 2" x 2 3/4"
This power supply was used in a CRT Terminals

DIODES

1N270 Germanium Diodes \$7.95/c
HEP170, 2.5A, 1000 PIV \$4.95/20
Semtech SFMS 20K, 20KV, 10 ma, fast recovery \$1.26 ea.

METERS

General Electric DC Volts 0-80 vdc Catalogue #50-152011 10.44

RF TRANSISTORS

2N1561	15.00	2N3866 JAN TX	4.85	2N5590	6.30
2N1562	15.00	2N3924	3.20	2N5591	10.35
2N1692	15.00	2N3925	6.00	2N5635	4.95
2N1693	15.00	2N3927	11.50	2N5636	11.95
2N2631	4.20	2N3948	2.00	2N5637	20.70
2N2857	1.80	2N3950	26.25	2N5643	20.70
2N2876	12.35	2N3961	6.60	2N5641	4.90
2N2880	25.00	2N4072	1.70	2N5643	20.70
2N2927	7.00	2N4073	2.00	2N5764	27.00
2N2947	17.25	2N4135	2.00	2N5841	11.00
2N2948	15.50	2N4427	1.24	2N5842/MM1607	19.50
2N2949	3.90	2N4470	20.00	2N5849/MM1622	19.50
2N2950	5.00	2N4440	8.60	2N5862	50.00
2N3287	4.30	2N4957	6.30	2N5942	49.50
2N3300	1.05	2N5070	13.80	2N5922	10.00
2N3302	1.05	2N5090	6.90	2N6080	5.45
2N3307	10.50	2N5108	3.90	2N6081	8.60
2N3309	3.90	2N5109	1.55	2N6082	11.25
2N3375/MM3375	7.00	2N5177/MRF5177	20.00	2N6083	12.95
2N3553	1.80	2N5179	.68	2N6084	14.95
2N3571	4.10	2N5180	.83	2N6094	5.75
2N3818	6.00	2N5184		2N6095	10.35
2N3824	3.20	2N5216	47.50	2N6096	19.35
2N3866	1.09	2N5583	5.60	2N6097	28.00
2N3866 JAN	4.14	2N5589	4.60	2N6166	85.00

RF TRANSISTORS

MRF207	2.00	Kertron KB6008	5.50	MM3002	1.65
MRF208	10.20	Amperex BLY90	22.50	MM3009	1.80
MRF209	12.35	Amperex A209	8.60	MM3375	7.00
MRF237	1.85	MSC 2001	20.00	MM3904	1.50
MRF238	8.55	MSC 3000	20.00	MM3906	1.43
MRF450	16.55	MSC 3001	20.00	MM4000	1.24
MRF453	19.55	MSC 3005	20.00	MM4001	1.39
MRF504	6.75	MSC 80205	20.00	MM4003	1.85
MRF509	5.50	MSC 80206	20.00	MM4036	1.60
MRF511	8.60	MSC 80255	20.00	MM4044	3.00
MRF620	27.00	Fairchild SE7056	3.00	MM4545	3.00
MRF621	30.50	MM1051	2.00	MM8006/2N5842	2.15
MRF8004	1.90	MM1500	32.20	MM1552	50.00
HEPS3013/75	2.95	MM1550	10.00	MM1553	56.50
HEPS3014/76	4.95	MM1601	5.50	HEPS5026	2.48
HEPS3002	11.03	MM1602	7.50	MSC 80256	20.00
HEPS3003	29.88	MM1607/2N5842	8.65	CTC D1-28	20.00
HEPS3005	9.55	MM1614	2.75	CTC D10-28	20.00
HEPS3006	19.90	MM1620	17.50	CTC E1-28	20.00
HEPS3007	24.95	MM1622/2N5849	19.50		
HEPS3008	2.18	MM1661	15.00		
HEPS3010	11.34	MM1669	17.50		
RCA TA7994	50.00	MM1943	3.00		
RCA 40290	2.48	MM2605	3.00		
Kertron K2126	5.50	MM2608	5.00		

MHz electronics

2543 N. 32nd STREET
PHOENIX, ARIZONA 85008
PH. 602-957-0786

C.O.D.

OR



2 METER FM

and HF too . . .

**Chicago
Area
Hams!**

Come in or call for the

**ERICKSON
COMMUNICATIONS**

Cash or trade deal on:

- Ameco • ASP • Atlas
- Belden • Bird • CDE
- CES • Collins • Cushcraft
- Data Signal • Dentron
- Drake • ETO • HAL
- Hy-Gain • Icom • KLM
- Kenwood • Larsen • MFJ
- Midland • Mosley • NPC
- Newtronics • Nye
- Regency • Shure • Swan
- Standard • TPL • Tempo
- Ten-Tec • Yaesu . . .



Hours: 9:30-9 Mon. & Thurs,
9:30-5:30 Tues, Wed. & Fri.
9-3 Sat.



**ERICKSON
COMMUNICATIONS**
5935 N. Milwaukee Ave.
Chicago, IL 60646
(312) 631-5181

CANADIAN JUMBO SURPLUS and Parts Catalogs. Bargains Galore. Send \$1. ETCO-HR, Box 741, Montreal "A" H3c 2V2.

125-Hz CHYSTAL FILTER for Drake R-4C receivers. Ideal for DX and contest work, \$125.00. Sherwood Engineering, Inc., Dept. G, 1268 So. Ogden St., Denver, CO 80210.

RTTY — NS-1A PLL TU (HR 8/76). Wired/tested \$29.95 ppd. Board \$4.75 ppd. SASE for info. Nat Stinnette Electronics, Tavares, FL 32778.

"GRINCH" offers parts, service, calibration and custom or prototype fabrication. Send S.A.S.E. for data: "GRINCH", 307 Jane Road, Cinnaminson, N. J. 08077.

QSL'S — **BROWNIE W3CJI** — 3035B Lehigh. Allentown, Pa. 18103. Samples with cut catalog 50¢.

EXCLUSIVELY HAM TELETYPE 21st year, RTTY Journal, articles, news, DX, VHF, classified ads. Sample 35¢. \$3.50 per year. Box 837, Royal Oak, Michigan 48068.

OSCAR 7, SSB-CW TRANSMIT CONVERTERS. For 28 or 50 MHz input at 20 mw. 432 MHz output at 1 watt. Solid state, for 12 volt supply. 35 watt solid state amplifier available for this converter. Units designed and built by WØENC. Write for information. UHF-VHF Communications, 53 St. Andrew, Rapid City, S. D. 57701.

VARIABLE AND TRIMMER CAPACITORS — Milen, Johnson, Hammarlund, Erie, Arco. In stock for immediate shipment, write for free price list "A". D & V Radio Parts, 12805 W. Sarle Rd., R#2, Freeland, Mich. 48623.

500 MHz PRESCALER Divide by 10 or 100 \$59.95. Free information. CBS Enterprise, P. O. Box 1356, Cocoa Beach, Fla. 32931.

Coming Events

NEW YORK: The Kings County Repeater Association, will hold an indoor flea market on Sunday, December 19, 1976 from 9 a.m. to 4 p.m. Located at 910 Union St., Brooklyn, N. Y. (at Grand Army Plaza). Sellers \$3, buyers \$1. Children free. Refreshments available. Talk in on 146.43 and 146.52.

S O W P CHRISTMAS QSO PARTY. The Society of Wiretess Pioneers will conduct a membership on-the-air QSO Party on the weekend of December 18 and 19, 1976. The Party will cover the full 48-hour GMT period and will be the first "voice" Party scheduled by the Society. The purpose of the affair will be to give members an opportunity to meet one another and to pass along their season's greetings, etc. There will be no formal exchange requirements and no need to submit logs. All members with a phone capability are encouraged to participate. The call will be CQ SOWP. While there will be no certificates awarded, everyone who takes part will be a winner by having an opportunity to renew old friendships, establish new ones and to continue a camaraderie developed over the years. Suggested frequencies for the affair are 25 kHz (±) 5 kHz up from the low end of the general class phone portion of each amateur band.

Stolen Equipment

STOLEN on 8-20-76 in a San Francisco parking lot, one Tempo VHF 1-2 meter transceiver #5728 one Western Electric Touch Tone pad. Reward — contact K6RMM, Shel Kurtzman, 1-213-344-0878, 19436 Topham St., Tarzana, CA 91356.

ONE Collins 75A-3 SN#910, one Heathkit (Apache). Stolen from: Robert E. Kelley W5VFU, 3400 Brook Dr., Oklahoma City, OK 73119.

DRAKE TR-22 2 meter transceiver SN. 640139. Beige trimline, TT Handset. Magnet mount quarter wave antenna. Stolen from Rick Simpson, KØUZP, 303-471-2059, 2723 Rigel Drive, Colorado Springs, Colo. 80906.

WILSON T1402 S/M 2 meter handi-talky SN OR6427. Stolen from: James Hettle, PSC #1, PO Box 2493, Peterson AFB, Colo. 80914.

YAESU FR-101SDIG, HF Digital Receiver. SN. 6C31339. Yaesu FL101, HF Digital Transmitter. SN. GE306276. Stolen from: Associated Electronics Service, 303-475-7050, 404 Arrawana, Colorado Springs, Colo. 80909.

STOLEN FROM GENAVE RADIO Expo '76 booth in Chicago, Sept. 18-19, 1976: One GTX-1T Handie-Talkie S/N 10-59. Anyone with information is requested to contact Genave, 4141 Kingman Drive, Indianapolis, Ind. 46226. 317 546-1111.

ALUMA TOWERS

LOW PRICED

MADE IN ALUMINUM

★ TELESCOPING
(CRANK UP)

★ GUYED

★ TILT OVER MODELS

QUALITY MADE

Excellent for

**HAM
COMMUNICATIONS**

10 MODELS MFG.

Towers to 100 feet. Specials designed & made. See dealer or send for free catalog.

ALUMA TOWER DIVISION

FRED FRANKE, INC.

BOX 2806HR
VERO BEACH, FLA. 32960
PHONE (305) 567-3415

TEST EQUIPMENT

All equipment listed is operational and unconditionally guaranteed. Money back if not satisfied—equipment being returned must be shipped prepaid. Include check or money order with order. Prices include UPS or motor freight charges.

BECKMAN 7570A Counter Freq conv
10 1000mHz 2/5
BOONTON 190A Q mtr 30-200mHz 3/25
BOONTON 202B AM-FM sig gen
54-216mHz 2/5
DEI TDU 2 30mHz video display 5/5
GR546C Audio microvoltage 6/5

HP160B (USM105) 15mHz scope with
norm horiz, dual trace vert plugs 3/75
HP166B (Mil) Delay sweep for above 1/30
HP185A Sampling Scope 1gHz 186B
xstr rise plug 3/35
HP202B LF Osc .5Hz-50kHz 10v. out 7/5
HP205AG Lab Audio Gen .02 20kHz 1/95
HP212A Pulse Gen .06-5kHz PRR 2/5
HP430CR Microwave Pwr Mtr 4/0
HP540B Transfer Osc to 12.4gHz for
use with HP524 type counters 1/15
HP571B-561B Digital clock/rcdr 2/45


HP616 Sig gen 1.8-4gHz FM CW 3/85
HP686 Sweep Gen 8.2-12.4gHz Sweep
range 4.4mHz-4.4gHz 5/95
HP803A VHF Ant bridge 50-500mHz 9/5
SINGER SSB4 Sideband spec anal
0-40mHz, res. to 10Hz 6/85
TEK 181 Time mark scope calib. 4/5
TEK 190 Sig gen (const ampl) 50mHz 1/25
TEK 551 Dual beam 27mHz scope
less plug-ins 7/35
TEK 565 Dual beam 10mHz scope
less plug-ins 5/25
TS 505 Std VTVM (rf to 500mHz) 6/5

For complete list of all test equipment
send stamped, self addressed envelope

GRAY Electronics

P.O. Box 941, Monroe, Mich. 48161
Specializing in used test equipment.

SPECIAL OF THE MONTH

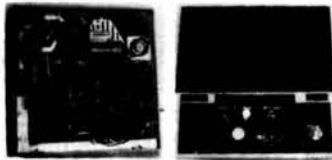

MADE FOR HOTEL ROOM SERVICE WAKE UP SERVICE

Here's a parts list- All new not used, just installed in the board.
 1-LM309K, heat sink, 2-2N5137,
 5-2N3904, 2-7400, 7402, 1-7403,
 3-7410, 1-7413, 2-7430, 9-7474,
 1-7486, 1-74151, 1-74154, 1-4001,
 2-741CT, 5-TIP29 & 30, 1-LM38C
 AN (14), 3-MDA942-1 Bridges, 1-
 555 Timer, 1-OnOff 10K Vol Con
 1-Fuse Block with 1 A SloBlo
 1-4" Speaker 3.2 Ohm 1 Watt,
 1-Transformer 16V Pri 5V-12V
 1-Thumbwheel Switch 2 Digit
 12 Positions, 40 other Misc.
 Weight 4 lbs

USE FOR: 5V DC Power Supply
 P. A. or Music Outlet

Price: \$12.95


TTL IC'S

7400 .18	7441 .75	7496 .65
7401 .20	7442 .44	7497 2.00
7402 .20	7443 1.20	74100 1.25
7403 .20	7445 .89	74107 .26
7404 .20	7446 .87	74109 .35
7405 .20	7447 .69	74110 .50
7406 .39	7448 .81	74116 2.00
7407 .39	7450 .20	74120 1.25
7408 .20	7451 .20	74121 .34
7409 .24	7453 .20	74122 .39
7410 .20	7454 .20	74123 .50
7411 .20	7460 .20	74125 .45
7412 .24	7470 .20	74126 .45
7413 .35	7472 .23	74128 .65
7414 .70	7473 .26	74132 .95
7416 .33	7474 .29	74136 .50
7417 .33	7475 .39	74141 .80
7420 .20	7476 .31	74142 4.00
7422 .50	7479 2.40	74143 4.00
7423 .28	7480 .69	74144 4.00
7425 .24	7482 .72	74145 .70
7426 .24	7483 .75	74147 2.50
7427 .24	7485 .90	74148 1.75
7428 .40	7486 .25	74150 1.00
7429 .40	7488 3.50	74151 .70
7430 .20	7489 1.50	74153 .70
7432 .28	7490 .39	74154 .90
7433 .34	7491 .65	74155 .70
7437 .28	7492 .39	74156 .90
7438 .28	7493 .39	74157 .70
7439 .36	7494 .70	74158 1.75
7440 .20	7495 .50	74159 2.25


VIDEO GAME KIT NOW 6 GAMES TO PLAY

A CHALLENGE TO BUILD,


A CHALLENGE TO PLAY.

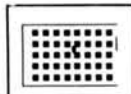


WIPE OUT I

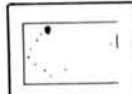


HANDBALL

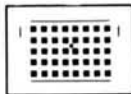


WIPE OUT II

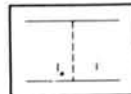

GRAVITY MATCH

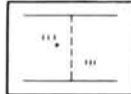

PRO MATCH

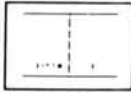

MATCH

WIPE OUT the squares — 7 serves from center — 40 squares — 10 pts each square hit by ball. On each serve square disappears when hit by ball. For 1 or 2 players.

HANDBALL — You may not win but you get alot of practice.

GRAVITY MATCH — You never know how high it will bounce when returning this one.

PRO-MATCH — You have 3 paddles to return a ball almost as fast as a hockey puck.

MATCH — The game that started the action.

Also a curve button while depressed sends the ball off at a new angle.

On screen scoring between automatic serves. 4 different sounds.

VK-2-A wt 4# 130.00
 P.C. Board with 78 IC's,
 PROMS's (programmed),
 resistors, capacitors to
 stuff board for game
 Requires 5V + DC 2 Amp

VK-3 wt 2# 17.50
HARDWARE KIT
 Controls, switches,
 speaker, 22 pin edge
 connector

VK-4 wt 1# 22.50
R.F. MODULATOR KIT
 To convert video signal
 to TV signal. Eliminates
 internal T.V. wire-in

VK-5-A wt 5# 17.50
POWER SUPPLY KIT
 for P.C. board mounting
 transformer, high current
 Voltage Reg. capacitor
 heat sink

VK-4-A Antenna-Game Switch 9.50



CLOCK KIT \$12.95
 MM5316, pc bd., display tubes
 switches, etc., instructions.

CLOCK CHIPS MM5375, CT7001, MM5369
 Your choice \$4.95

FTK1016 Auto Clock Kit 40.00
 Jade Co will include case
 when you buy from us.



FAIRCHILD TECHNOLOGY KITS

Jade Co offers all other Fairchild Technology Kits at published retail prices.

SOLAR CELLS

Build your own solar powered projects — Silicon photo voltaic cell wafers unmounted or encapsulated with output wires attached — Each cell has 0.45 volt output — Current varies with size and light intensity — Cells can be quartered for voltage build-up —

Single 3" dia Encapsulated with wire	
0.45 volt 0.8 to 1.2 amp	7.50
32 ea 3" dia Encapsulated in 1 unit	
14 volt 0.8 to 1.2 amp	195.00
32 ea halved 3" dia Encapsulated in 1 unit	
14 volt 0.4 to 0.6 amp	135.00
32 ea quartered 3" dia Encapsulated in 1 unit	
14 volt 0.2 to 0.3 amp	75.00
Unmounted in multiples of 11 only	
11 ea 3" dia wafer	
0.45V 0.8 to 1.2 amp	75.00
11 ea quartered 3" dia	
0.45V 0.2 to 0.3 amp	27.50
11 ea 2 cm x 2 cm	
0.45V 0.1 to 0.12 amp	22.50

SMOKE DETECTOR

PHOTO ELECTRIC TYPE

NOT A KIT

But a complete unit ready to install. U.L. approved
 Listed by Cal. Fire Code
 \$29.95

MICROPROCESSOR COMPONENTS

8008-1	8 Bit CPU	18.95
8080	Improved 8008	24.95
8080A	Super 8080	34.95
	DYNAMIC RAMS	
311L01	64 Bit low pow	4.45
1103	1024xl	2.50
2107B-4	4096xl	8.00
8225B	16x4	1.50
93407	16xl	4.85
	STATIC RAMS	
1101	256xl	1.75
2102	1024xl	2.00
2501B	256xl	1.75
3107	256xl	4.00
7489	64 Bit R/W	2.00
74200	256 Bit R/W	5.75
	PROMS	
1702A	256x8 Eras	12.00
1702AL	256x8 low pow	12.00
8223B	32x8	3.50
74S 287N	256x4	6.95
	SHIFT REGISTERS	
MM5058	1024xl Static	4.75
TMS3002LR	Dual 50	4.00
TMS3132NC	Dual 144	3.00
	COMPARES TO	
2107B4	TMS4060	
2102	AMD9102, ISL7552-1, TMS4033	
MM5058	AMD2533, FSC3355, TMS3133	
TMS3002	SIG2509	
TMS3132	MM40601, FSC3346	

NATIONAL MA1001A DIGITAL ALARM CLOCK MODULE



FEATURES:

- Bright 4 Digit 0.5" LED Display
- Assembled & Tested Module
- You only need compact transformer & switches
- 12 Hour Format with PM Indicator
- 30 or 60 Hz Operation
- Power Failure Indication
- Brightness Control Capability
- Alarm and Snooze Timers
- Compact 3.0"x1.75"

\$9.95



JADE Co

ELECTRONICS DISTRIBUTION

2007 W. CARSON (213) 320-1250
 P.O. BOX 4246 TORRANCE, CA. 90510

TERMS:

Add \$1.00 for shipping plus \$.85 if COD
 California Residents add 6% Sales Tax
 \$20 minimum on BoFA & M.C.

Orders from Foreign countries add appropriate postage



KEYBOARD

wt 6# 35.00

EDGE CONNECTORS

22 Pin dual Read Out .156 Sid 2.25
 50 Pin dual Read Out .125 WW 5.00

LED'S

TIL302 0.27 ChHt 1.00
 MAN4 0.187 ChHt 2/1.00



SPEAKERS



SQUARE — 3" - 4Ω - .3W, 4 mtg holes.
\$1.45 ea. ppd., 2/\$2.75 or 4/\$4.80 ppd.

PIONEER — Round 2 3/4" x 7/8" - 16Ω - .3W, 4 hole mtg.
\$1.55 ea., 2/\$2.85 or 4/\$5.20 ppd.


OVAL — 2" x 4" x 1 1/4" deep - 8Ω - .1W, 4 Hole Mtg. \$1.75 ea. ppd., 2/\$3.15 or 4/\$5.75 ppd.



Round #5P585A 2" x 3/4" - 8Ω - .1W \$1.35 ea. ppd.
2/\$2.55 or 4/\$4.75 ppd.

NOBLE 100K Dual Slide Potentiometer, 2 7/8" x 3/4" x 3/4" with 1 1/4" lever.
\$1.45 ea. or 10 for \$12.00 ppd.

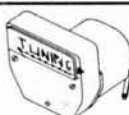1/8 WATT — Just Arrived — NEW Full Leads — Imported Resistors. 5% Resistors — 75 - 220 - 390 - 430 - 1.5K - 2K 18K - 22K - 39K - 82K - 3.9K - 4.3K - 10K - 15K - 220K - 270K. 10% Resistors, 10K - Both tolerances 33 for \$1.66 ppd. (You choose One Value — 100/\$4.15 ppd. values) Assorted — 100/\$4.55 ppd.



TUNING METERS — Blue tinted plastic body, 0 to left, graduated scale, 200μA, 1 1/2"W x 1 1/4"H x 3/4"D. Scale can be rear lighted. Sylvania #18148-1 \$2.25 ea. or 4/\$6.95 ppd.



3000 MFD @ 30 Volt Capacitors.

Size 1" Diameter x 3" Long. 90¢ Each or 3 For \$2.25 ppd.

3000 MFD @ 20V Capacitors. Same size as above. 80¢ ea. or 3 for \$2.00 ppd.

ALSO 3000 MFD @ 50V, 3" x 1 1/2" dia. 95¢ ea. or 3/\$2.65 ppd.

ELECTROLYTIC CAPACITOR — PHILCO



4" x 1 3/8" dia.


Quad section 100x150 MFD @ 400V and at 350V D.C. and 20x50 MFD @ 250V — TWISTAB MTG. A very nice unit for Transceiver Power Supplies etc.
Price is only \$1.10 ea. or 3/\$2.95 ppd.

DUAL Electrolytic 1000 & 500 MFD. 15V, long leads. 3/4" dia. x 2 1/4" long.
55¢ each 3/\$1.50 ppd.

CRL Disc Capacitors. .1 MFD, 10V 3/8" dia., long leads. 10 for \$1.00 ppd. 100/\$8.40, 500/\$36.60 (U.P.S. Only)

UNPOTTED TOROIDS — center tapped 88MHY Limited Qty's 44 MHY 5/\$2.95 5/\$3.95 ppd.

NEW

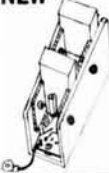

Transistor and Relay Assembly — consists of (2) MJE3055 and (2) MJE2955 transistors (10 amp, 90w, 60v complementary pairs) mounted in "U" channel heat sink 2 1/2" x 1 1/2" x 1 1/2". (2) XTAL CAN RELAYS, DPDT, 28v, 8000Ω, 5.8 ma DC, 1 amp contacts mounted on PC board with resistors. \$2.85 ea. ppd.

400 PIV BRIDGES — 1.5A Gen. Instr. P.C. Bd type. 60¢ ea. or 3/\$1.75 ppd.

SEMTECH BRIDGES



Heat sink w/center hole mtg. 10 Amp — Tested — 200V P.I.V. \$1.75 ea. ppd. 400V P.I.V. \$1.95 ea. ppd. 600V P.I.V. \$2.15 ea. ppd.



25 AMP — TESTED
200V P.I.V. \$2.25 ea. ppd. 400V P.I.V. \$2.50 ea. ppd. 600V P.I.V. \$2.85 ea. ppd.

SEND STAMP FOR BARGAIN LIST PENNSYLVANIA RESIDENTS - ADD 6% ALL ITEMS PPD. USA

Canadian orders for less than \$5.00 add \$1.00 to cover additional mailing costs. UPS requires your street address.

m. weinschenker
electronic specialties-BOX 353, IRWIN, PA 15642

HAM IT UP AROUND SOUTH AMERICA.

Prudential Lines is offering a special Mobile Expedition Cruise for HAM radio operators on our 100-passenger Santa Mercedes. So here's your chance to have a great 56-day cruise around South America and become a Maritime Mobile Operator, too. Sail from San Francisco on April 26 or join us at any of our 14 ports along the way. You'll get expert instruction in code classes and license upgrading from host Clarence Seid, W2KW and KV4AB. You can operate a special hi-powered Maritime Mobile Station with Chief Radio Officer Jack Lachelle. What's more, you can take part in a DX contest while cruising the fabulous Strait of Magellan. For more information, phone collect or write Prudential Lines.

Ships of U.S. Registry.



PRUDENTIAL LINES


One California St., San Francisco, CA 94106 • (415) 781-3800

We're Fighting Inflation No Price Rise for '76



FOR FREQUENCY STABILITY

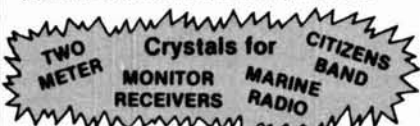Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us!



CRYSTAL SPECIALS

Frequency Standards
100 KHz (HC 13/U) \$4.50
1000 KHz (HC 6/U) 4.50
Almost all CB sets, TR or Rec \$2.50 (CB Synthesizer Crystal on request)
Amateur Band in FT-243 ea. \$1.50
..... 4/\$5.00
80-Meter- \$3.00 (160-meter not avail.)

For 1st class mail, add 20¢ per crystal. For Airmail, add 25¢. Send check or money order. No dealers, please.



Div. of
Bob Whan & Son Electronics, Inc.
2400 Crystal Dr.,
Ft. Myers, Fla. 33901
All Phones: (813) 936-2397
Send 10¢ for new catalog

NEW from NRI

Home training in AMATEUR RADIO

NRI, leader in Communications, Television, Electronics and TV-Radio home training, now offers the first in Amateur Radio courses, designed to prepare you for the FCC Amateur License you want or need.

Don't lose your favorite frequency

The FCC has said "either-or" on licensing, but to pass Advanced and Extra Class exams, you need the technical guidance as offered by NRI. NRI Advanced Amateur Radio is for the ham who already has a General, Conditional or Tech Class ticket. Basic Amateur Radio is for the beginner and includes transmitter, 3-band receiver, code practice equipment. Three training plans offered. Get all the facts. Mail coupon. No obligation. No salesman will call on you. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.



..... **MAIL NOW**

NATIONAL RADIO INSTITUTE 46-076
Washington, D.C. 20016

Please send me information on Amateur Radio training.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL


Performance...

your choice for
under \$299*

Standard's 146-A Handheld outclasses them all!

Check these "ASTROPOINT" features:

- 146-A** A deluxe 2 Meter FM transceiver in a Hand-held package
- 146-A** 2 watts RF output nominal
- 146-A** Compact size: only 1 5/8 x 3 x 9 inches
- 146-A** Separate internal mike for superb audio
- 146-A** Epoxy PC board mounted in a superior diecast frame
- 146-A** Provision for Private Channel (CTCSS) external mike or speaker mike
- 146-A** Myriad of available accessories for outstanding flexibility

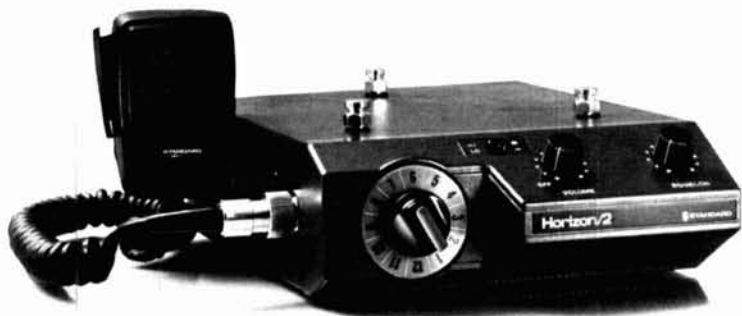


Because no two transceiver applications are exactly alike Standard also makes the rugged HORIZON "2" 25 watt output 2 meter FM transceiver for HAM, CAP, and MARS. The Horizon "2," like the 146-A, is also available for under *\$299. Both of these rugged radios offer you exceptional quality and outstanding performance at a price that's right.



**Standard
Communications**

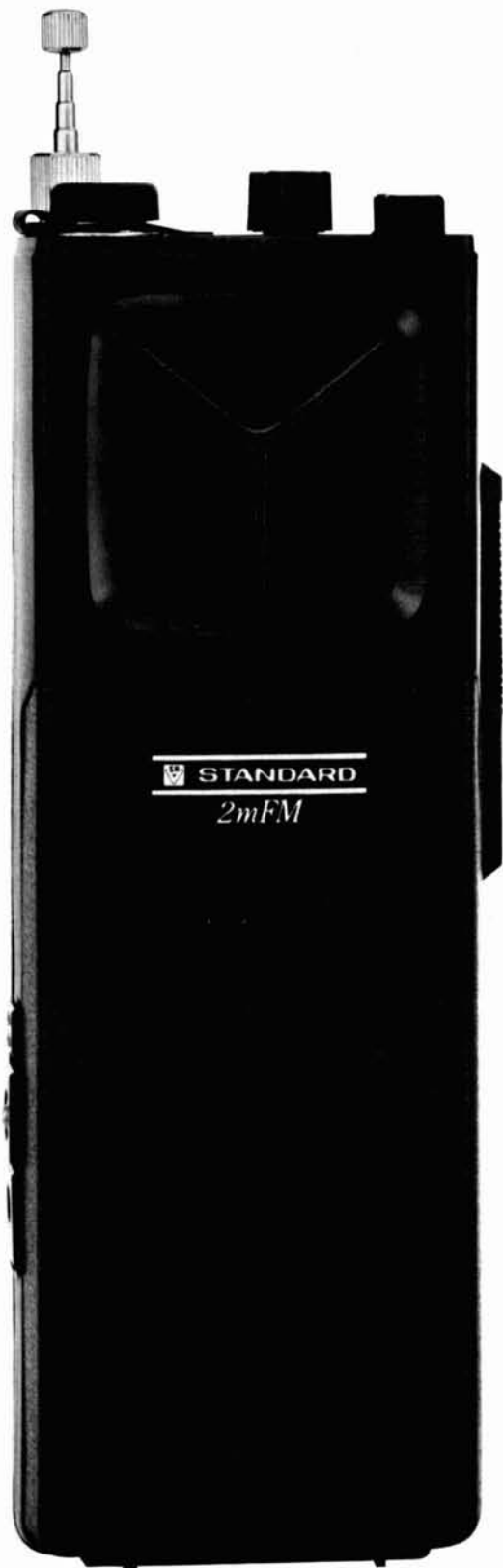Standard Communications Corp. P.O. Box 92151 · Los Angeles · Ca · 90009



SWAN METERS HELP YOU GIVE IT YOUR ALL

SWR Bridge for 21.95

Our little dual meter SWR bridge indicates relative forward power and SWR.

The Unit is capable of handling up to 1000 watts and will indicate 1:1 to infinity

VSWR from 3.5 MHz to 150 MHz on 100 microampere meters. Ideal for mobile or home operation with low in-line insertion loss.

Use your Swan credit card. Applications at your dealer or write:

SWAN[®]
ELECTRONICS

A subsidiary of Cubic Corporation

305 Airport Rd. Oceanside, CA
92054 (714)
757-7525



(Prices FOB Oceanside, CA)

— CLEAN SIGNAL —
— ALL CHANNELS —



ONLY RP GIVES YOU BOTH
PLUS

- SUPER ACCURACY (.0005%)
- FULL 2M FM COVERAGE

144-148 MHz

WORKS WITH MOST FINE AMATEUR
OR COMMERCIAL GRADE RADIOS

MFA-22 SYNTHESIZER

NOW SAVE 20%

MFA-22	\$260.00
with 5kHz Steps	\$300.00
Shipping (UPS)	\$3.00

Fully wired, tested, 1 yr. warranty

Factory direct
only

RP Electronics

SEND
FOR
FULL
DETAILS



BOX 1201H
CHAMPAIGN, ILL.
61820

IF WE WERE YOU



MODEL 6154 TERMALINE[®]

I'D BUY FROM US

YOUR INQUIRY OR ORDER WILL
GET OUR PROMPT ATTENTION

AUTHORIZED

BIRD DISTRIBUTOR

WEBSTER COMMUNICATIONS

115 BELLARMINE
ROCHESTER, MI 48063
313-375-0420

Out of Band



Barlow XCR-30

Shortwave Listening

Our only business is supplying everything needed to tune outside the Amateur Radio bands and identify what you hear. Our mini-catalog details Barlow Wadley, Drake and Yaesu receivers, WORLD RADIO TV HANDBOOK, logs, antennas, calibrators, CONFIDENTIAL FREQUENCY LIST, receiving antenna tuners, FM or TV station guides, AM pattern maps, audio filters, special ITU lists, QSL albums and every book published on "listening."

GILFER ASSOCIATES, INC

P.O. Box 239, Park Ridge, NJ 07656

ALDELCO SEMI-CONDUCTOR SUPERMARKET

RF DEVICES

2N3375 3W 400 MHz.....	5.50	2N6080 4W 175 MHz.....	5.40
2N3866 1W 400 MHz.....	.99	2N6081 15W 175 MHz.....	8.45
2N5589 3W 175 MHz.....	4.75	2N6082 25W 175 MHz.....	10.95
2N5590 10W 175 MHz.....	7.80	2N6083 30W 175 MHz.....	12.30
2N5591 25W 175 MHz.....	10.95	2N6084 40W 175 MHz.....	16.30

HEAVY DUTY RECTIFIERS

200 Volt 100 Amp D08.....	8.50
200 Volt 250 Amp D09.....	12.50
1000 Volt 2 Amp Silicon Rectifier RCA.....	10 for .99
10,000 Volt Silicon Rectifier Erie, 65 mA.....	2.95

ALDELCO KITS

Digital Clock Kit, Hours, Minutes & Seconds, Large Half Inch LED readouts, Elapsed time indicator, 12 hour format with 24 hour alarm, Snooze feature, AM, PM indicator, Power Supply, power failure indicator. Complete with wood grain cabinet. \$23.95

NOW OPEN - ALDELCO COMPUTER CENTER - books, magazines, kits, boards & support chips.

MOS Time Base Kit 50/60 Hz.....\$5.95

DISCRETE LEDS

Jumbo Reds, Long or Short bulb.....	6 for \$1.00
Jumbo Orange, Green, Clear, Red or Green.....	5 for \$1.00
209 Series, Green, Orange, Yellow or Red.....	5 for \$1.00
RL2 or Micro Red.....	5 for \$1.00

ZENERS

1N746 to 1N759 400 Mw ea. .25	1N4728 to 1N4764 1 w.....	.35
C1068.....	CA 3028A Dif. Amp.....	\$1.50
MPSA14.....	LM301 OP Amp.....	.55
2N3055.....	LM309K Volt. Reg.....	1.10
MPF 102 FET.....	LM380N Audio Amp.....	1.75
2N3904 or 2N3906.....	NE540L Power Driver.....	5.95
2N5496 or 2N6108.....	NE561B PLL.....	4.95
MJE 340 (2N5655).....	NE562B PLL.....	4.95
40673 RCA FET.....	NE565A PLL.....	2.50
741 or 709 14 Pin DIP.....	LM709 Min DIP OP Amp.....	.45
555 Timer.....	LM741CE TO5 OP Amp.....	.45
556 (Dual 555).....	14 or 16 Pin IC Sockets.....	.30
200 Volt 25 Amp Bridge.....	We have 7400 series IC's send stamp for catalog.	
1N914 - 1N4148.....	10 for .99	
1N34 - 1N60 - 1N64.....	10 for .99	

We quote on any device at any quantity. All items postpaid in USA. Min. order \$6.00. Out of USA send Certified Check or Money Order. Include postage.

ALDELCO

2281H Babylon Tnpk., Merrick, NY 11566
(516) 378-4555



Radio Amateurs Reference Library of Maps and Atlas

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country... DX zones, time zones, cities, cross referenced tables **\$1.25**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities: Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. **\$1.25**

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus useful information on each of the 50 United States and other Countries **\$1.25**

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. Size 8 3/4" x 12" **\$2.50**

Complete reference library of maps — set of 4 as listed above **\$3.75**

See your favorite dealer or order direct.

Mail orders please include \$1.25 per order for shipping and handling.

RADIO AMATEUR

callbook INC.

WRITE FOR FREE BROCHURE!



Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

UNIVERSAL
TOWERS

FREE STANDING
ALUMINUM TOWER
10' to 100'

Prices from \$110.00 (30')

MOST

POPULAR

HAM TOWER

EVER MADE!

REQUEST

NEW CATALOG

OF

TOWERS &

ANTENNAS

Midwest Ham Headquarters

For Over 38 Years

HAMS! Write For Free Catalog

and Wholesale Prices!

ELECTRONIC DISTRIBUTORS, INC.

1960 Peck Muskegon, MI 49441

Tel: 616-726-3196 TELEX: 22-8411

NEW

a digital frequency counter you can count on



New 300/600 Mhz Digital Frequency Counters are in a class by themselves when it comes to reliability, accuracy and performance.

Quality features include full 7 digit display panel with large LED readouts, resolution to .1HZ, high input sensitivity, automatic limit on input, controlled time base, selectable gate times .1 sec., 1 sec. and 10 sec. and high stability time base options available.

Complete Kit includes all parts, drilled and plated PC boards, cabinet, switches, hardware and a complete Instruction Manual including calibration instructions.

SPECIFICATIONS

Input Impedance:	Direct HI-Z, Pre-scaled 50
Sensitivity:	Ω 50 mv/20MHZ 150 mv/200MHZ 200 mv/600MHZ
Time Base:	10 Mhz crystal oscillator
Stability:	
Standard	10ppm 25 to 40 C
TXCO*	2ppm 15 to 55 C
Frequency Range:	Model 300 1HZ to 300 Mhz Model 600 1HZ to 600 Mhz
Resolution:	0.1 second gate 1.0 second gate 10.0 second gate*
Power:	120 VAC 25 Watts 12 VDC*
Cabinet Size:	8" x 8" x 2 1/2"

*Optional

TO ORDER

Send check or money order HR-12
\$129.00 for Model 300 Kit (1 HZ to 300Mhz)
\$179.00 for Model 600 Kit (1 HZ to 600Mhz)
 For preassembled and tested units
\$199.00 Model 300
\$249.00 Model 600

NAME _____
 ADDRESS _____
 CITY _____
 STATE _____
 ZIP _____
 (CALL) _____






Send check or money order to:

Crescent Wire & Cable Inc. ... for all your wire & cable needs






Bldg. 13 Euclid Ave., Newark N.J. 07105 (201) 589-4647

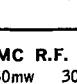SEMICONDUCTORS & MORE!

Motorola R.F. Power Transistors . . .

	2N2857	F	30mw	10Vcc	1000MHz	\$.95
	2N2947	G	15W	25Vcc	50MHz	\$ 8.00
	2N3375	A	11.6W	40Vcc	400MHz	\$ 3.50
	2N3818	A	20W	60Vcc	150MHz	\$ 4.50
	2N3866	B	1W	28Vcc	400MHz	\$.65
	2N3866JAN	B	1W	28Vcc	400MHz	\$ 2.00
	2N3866JANTX	B	1W	28Vcc	400MHz	\$ 3.00
	2N3925	I	5W	13.6Vcc	175MHz	\$ 2.50
	2N3948	B	1W	20Vcc	200MHz	\$ 1.25
	2N3950	A	50W	28Vcc	50MHz	\$10.00
	2N4072	E	.25W	13.6Vcc	175MHz	\$ 1.00
	2N5179	E		6Vcc	900MHz	\$.50
	2N5177	K	30W	38Vcc	400MHz	\$10.00
	2N5637	D	20W	28Vcc	400MHz	\$ 9.00
	2N5643	D	40W	28Vcc	175MHz	\$12.00
	2N5842	E		4.0Vcc	1700MHz	\$ 9.00
	2N6097	J		13.6Vcc	175MHz	\$15.00
	MM8006	E	3.8db	6Vcc	1000MHz	\$ 1.25
	MRF621	E	45W	12.5Vcc	470MHz	\$16.00

Transistors . . .

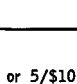	2N2431K	5/\$1.00
	2N2907A	5/\$1.00
	2N3250A	2/\$1.00
	2N3567	5/\$1.00
	2N2638	5/\$1.00
	2N3640	5/\$1.00
	2N3644	5/\$1.00
	2N3702	5/\$1.00
	2N3703	5/\$1.00
	2N4001	\$1.00
	2N4291	2/\$1.00
	2N5192	\$.75
	2N5194	\$.75
	MM3002	\$.75
	MM4000	\$.75
	MM4003	\$.75
	MM4049 (R.F.)	\$5.00
	2SC458	5/\$1.00
	2SD235	2/\$1.00
	MJE800	\$.75
	MJE1093	\$1.50
	MMT74	3/\$1.00
	MMT2857 (R.F.)	\$1.00
	MPSA13	3/\$1.00
	2N2369A	10/\$1.00
	2N3013	10/\$1.00

RF TRANSMITTER MODEL T-400
MICROCOM CORP. 26VDC 410.5MHz
\$12.50 each

RF POWER AMPLIFIERS

ACRODYNE INDUSTRIES, INC.
VHF 172MHz 15 Watts \$25.00
UHF 400MHz 15 Watts \$35.00

Feather Fans USED BUT TEST GOOD
AND LOOKS NEW MODEL 113 115
VAC \$6.00
ROTRON 3380 RPM 270 CMF

(NICAD BATTERIES) AA, 1.25 Volts
29¢ each

MUFFIN FANS USED BUT TEST
GOOD AND LOOKS NEW ROTRON
115VAC \$4.00

CAN TYPE ELECTROLYTIC CAPACI-
TOR 3000MFD @ 200VDC NEW
SANGAMD \$2.00

SILICONIX I.C.
G115BX 6X PMOS SW ARRAY \$2.00
DG200BA 2XSPST CMOS ANALOG
SW \$1.00

DIODES
1N2061 8/\$1.00 1N4002 6/\$1.00
1N2070A 8/\$1.00 1N4006 4/\$1.00
1N4001 8/\$1.00 1N540 8/\$1.00

KMC R.F. TRANSISTOR. TYPE K6008

450mw 3000MHz BVcbo 20 BVco 12 BVcbo 3.0 ICma 100 \$2.50 each or 5/\$10.00

Fairchild R.F. TRANSISTORS

SE5015 \$1.00
SE7056 \$2.00

Motorola 4-LAYER DIODES

1N5160/M4L3054 \$1.00

Motorola S.C.R. & TRIAC'S

2N4171	\$1.50	MAC21-3	100V 25 Amps	\$2.00
2N5060	\$.45	MAC21-5	300V 25 Amps	\$2.50
MAC21-1	\$1.00	MAC21-6	400V 25 Amps	\$3.00
MAC21-2	\$1.50			

Triad Transformers

F-18X PRI. 115V FIL. 6.3VCT @ 6 Amps \$3.00
F-93X PRI. 115V 6.5V to 40V @ 750ma \$3.00


I.C.s

N7473A	@ 35¢	N74193	@ 65¢	UA741C	@ 20¢
N7493A	@ 45¢	N74H11A	@ 40¢	DM5400D	@ 45¢
N74151A	@ 75¢	N74H11F	@ 45¢	DM7490N	@ 65¢
N74157A	@ 75¢	N74H21A	@ 40¢	DM74368N	@ \$1.00
N74174B	@ 75¢	1103P	@ \$1.00	DM8098N	@ \$1.00

SEMICONDUCTOR SURPLUS

3001 NORTH 32 ST., APT. 212 (602) 956-9893
PHOENIX, ARIZONA 85018

PRE-AMP

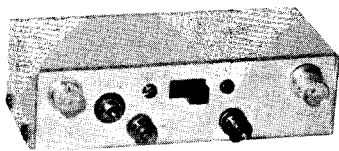

HIGH GAIN • LOW NOISE

35dB power gain, 2.5-3.0 dB N.F. at 150 MHz 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4 3/8" x 1 7/8" x 1 3/8" aluminum case with power switch and choice of BNC or RCA phono connectors (be sure to specify). Available factory tuned to the frequency of your choice from 5 MHz to 250 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order.

N. Y. State residents add sales tax.


Model 201 price: 5-250 MHz \$29.95

Vanguard Labs

196-23 JAMAICA AVE.
HOLLIS, N. Y. 11423

SUB-AUDIBLE GENERATOR for FM

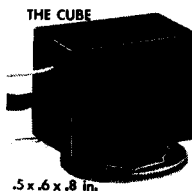- Inexpensive multi tone encoder
- Compatible with PL-CG-QC
- Low distortion sinewave
- Input 8-18 VDC unregulated
- Rugged, plastic encased with leads
- Adjustable frequency (98-250 Hz), Lower available
- Excellent stability



Price \$19.95

Freq. set at factory \$5.00 extra

Calif. res. add 6%


lyle Products

Dept. hr P.O. Box 2083 Santa Clara, CA. 95051

TONE ENCODER PAD

MODEL TTP-03

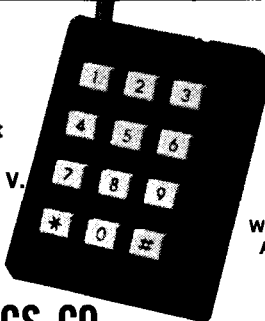- A Better Keyboard
- Output Level Set Pot
- Crystal Controlled-Digitally Synthesized Tones
- Strapping for Hi-Low Z Output
- Internal 5 V. Regulator Supply Voltage Range 7 to 24 V.
- RFI Suppression
- Velcro and Case Included
- Size 2.80 - 2.00 - 0.60 Inches



\$54.95

POSTPAID IN U.S.A.


TEXAS RESIDENTS ADD 5% SALES TAX

CHECK OR M.O.
WRITE FOR BROCHURE ON AUTOMATIC UNIT ATD-30

CLENG ELECTRONICS CO.

BOX 12171 — DALLAS, TEXAS 75225

PREVENT THEFT

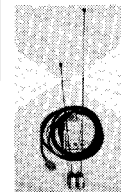

Gutter mount Antenna System has quick disconnect 1/4 wave element to resist theft. Resilient, vinyl-clad element and stressed aluminum mount to resist weathering. Available for 146 or 220 MHz. Elements are interchangeable.

VERY POPULAR AT HAMFESTS!

GUTTER MOUNT* PLUS ELEMENT

FM-146	\$15.95	FME-146	\$4.95
FM-220	\$15.95	FME-220	\$4.95

*Includes 10 feet of low loss RG-58 coax. Prices include postage in continental U.S.A. Penn. residents: Add 6% Sales Tax.

HamLine Electronics

Box 52, Sweet Valley, Pennsylvania 18656

CALL TOLL FREE 800-521-4414

SAVE \$80,000.00 IN CRYSTALS

LISTEN TO 16,000 DIFFERENT FREQUENCIES WITH NO CRYSTALS
FREE NO OBLIGATION 7 DAY TRIAL



BEARCAT 101

16 channels
30-50 MHz
146-174 MHz
416-512 MHz
CE's Price - \$296.95



TENNELEC

MCP 1
16 channels
31.18 - 51.655 MHz
151.18 - 171.655 MHz
451.18 - 471.655 MHz
CE's Price - \$339.95



Regency

WHAMO-10
10 channels
30-50 MHz
146-174 MHz
440-512 MHz
CE's Price - \$278.95



SBE

OPTISCAN
10 channels
30-50 MHz
150-170 or 140-160 MHz
450-470 MHz
490-510 MHz
CE's Price - \$296.95



Toll free U.S.A. 24 hour order & information line 800-521-4414. Outside U.S.A. & Michigan 24 hour phone 313-994-4441. Certified check or charge card on mail orders for immediate shipment. Dealer inquiries invited. Michigan residents add tax. Foreign orders invited. Call toll free or write for your free complete catalog & specifications. Satisfaction guaranteed or your money back. For engineering advice, call after 6:00 P.M. E.S.T.

COMMUNICATIONS ENGINEERING
P.O. BOX 1002
ANN ARBOR MI 48106

CALL TOLL FREE
800-521-4414
or
313-994-4441

DON & BOB'S SUPER BUYS



HY GAIN TH6DXX	\$192.00
TH3MK3 3 ELEMENT BEAM, 20, 15, 10	\$160.00
MOSLEY CLASSIC 33	\$179.00
MOSLEY TA-33	\$168.00
MOSLEY S-402, 40M BEAM	\$225.00
HY GAIN 204BA	\$144.00
HY GAIN 402BA	\$160.00
HY GAIN DB 10/15 A	\$120.00
2 BDQ 80/40 TRAP DOUBLET	\$39.95
CDE HAM-II ROTOR	\$129.00
CDE CD 44 ROTOR	\$104.00
CDE BIG TALK ROTOR + 100 FT. OF CABLE	\$100.00
KLM (MODEL KR400) ROTOR + 100 FT. OF CABLE	\$100.00
HY GAIN HY-QUAD	\$179.00
18HT HY TOWER	\$218.00

HY GAIN 18AVT/WB + 100 FEET OF RG8/U	\$100.00
SOLID ALUMINUM T-6 MAST 1 1/8" OR 1 7/8" x 12 FEET	\$25.00
CABLE CLAMPS 3/16" (MALLEABLE)	25¢ EACH
BELDEN 8214 RG-8/U FOAM COAX	23¢/FT.
BELDEN 8237 RG-8/U	19¢/FT.
BELDEN 8 WIRE ROTOR CABLE #8448	14¢/FT.
BELDEN 8210, 72 OHM KW TWINLEAD \$19 PER 100 FT.	
AMPHENOL PL-259	59¢
CALL FOR QUOTES — TS-520, TS-820, TS-700A, 210X.	
TEMPO 2020 & MULTI 2700	Call or Write
TECHNICAL BOOKS IN STOCK	
SWAN-SILTRONIX SWR-1	\$18.95
ELECTRA BEARCAT 101	\$289.00
RAYTHEON 811A, SEALED BOXES	\$15 per pair
ETO, DENTRON & DRAKE AMPLIFIERS	Call for Quote

ALL PRICES FOB HOUSTON. CALL TODAY FOR ITEMS NOT LISTED

OUR STAFF: W5GJ, K5AAD, W5M8B, W5ZNY, W5UUK, W5JJS, K5QHQ, W5HVU, W5TGU, W5AB, K5BGB

MADISON ELECTRONICS SUPPLY, INC.

1508 MCKINNEY AVENUE, HOUSTON, TEXAS 77002

713/658-0268

CALL US!

Nites 713/497-5683

FREE NEW CATALOG




NOW'S THE TIME to request your free new catalog on many, many exciting Amateur products including:

- Data-Tone Keyboards
- Data-Tone Encoders
- Handheld Encoders
- Automatic Data-Tone Dialers
- CW Keyers
- CW Memories
- Auto Patches
- Receiver Preamps
- Single Tone Encoders
- Single Tone Decoders
- Tone to Pulse Converters



DATA SIGNAL, INC.
2403 COMMERCE WAY
ALBANY, GA. 31707
912-883-4703

125 Hz CRYSTAL FILTER FOR DRAKE R-4C

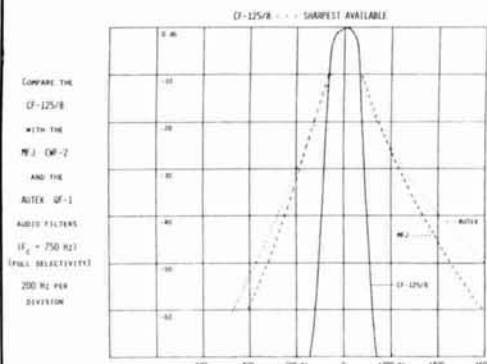

SHARPEST AVAILABLE



Cuts QRM. Ideal for DX and Contest Work. Does what no audio filter can do. A must for CW operators who want the best. 125 Hz @ -6 db, 325 Hz @ -60 db, 8 poles.

CF-125/8

\$125.00

Money back if not satisfied

Sherwood Engineering, Inc.

Dept. A
1268 South Ogden St.
Denver, Colo. 80210
(303) 722-2257

2 METER CRYSTALS IN STOCK

FOR THESE RADIOS ON
STANDARD ARRL REPEATER
FREQUENCIES

Clegg HT-146
Drake TR-22
Drake TR-33 (rec only)
Drake TR-72
Genave
Heathkit HW-2021

(rec only)
Heathkit HW-202
Icom/VHF Eng
Ken/Wilson
Lafayette HA-146
Midland 13-505
Regency HR-2
Regency HR-212
Regency HR-2B
Regency HR-312
Regency HR-2MS
S.B.E.
Sonar 1802-3-4, 3601
Standard 146/826
Standard Horizon
Swan FM 2X
Tempo FMH
Trio/Kenwood
Trio/Kenwood TR2200
Trio/Kenwood TR7200

**KENSCO
COMMUNICATIONS**

Dept.
30776

Box 469
Quincy, MA 02169
(617) 471-6427



FREE 12 red L.E.D.'S
with purchase of PB-100

**CONTINENTAL
SPECIALTIES
PROTO
BOARD 100**



A low cost, big 10 IC capacity breadboard kit with all the quality of QT sockets and the best of the Proto Board series . . . complete down to the last nut, bolt and screw. Includes 2 QT-35S Sockets; 1 QT-35B Bus Strip; 2 5-way binding posts; 4 rubber feet; screws, nuts, bolts; and easy assembly instructions.

\$19.95

Postpaid — Continental U.S.A.
Use "Check-Off" for complete product catalog.

**HOSFELT
ELECTRONICS**
2610 SUNSET BLVD.
STEUBENVILLE, OHIO 43925
Phone 614 264-6464

IF YOU DON'T HAVE OUR
CATALOG YET, SEND SASE!

**PREAMP, CONVERTER, FM RCVR &
XMTR KITS, CUSHCRAFT & LARSEN
ANTENNAS, STANDARD XCVRS.**


FAST MAIL & PHONE SERVICE

hamtronics, inc.

182 BELMONT RD., ROCHESTER, NY 14612

WANT SOMETHING REALLY SMALL AND EFFICIENT?

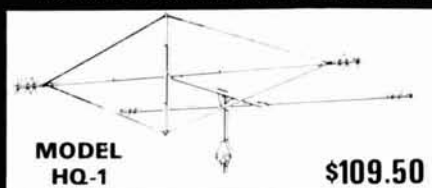Then you want the antenna that's known around the world for it's small size and superior performance . . . The Mini-Products Multiband HYBRID QUAD



MODEL
HQ-1

\$109.50

- ELEMENT LENGTH - 11 ft.
- BOOM LENGTH - 54 INCHES
- WEIGHT - 15 POUNDS
- WIND SURVIVAL - 75 MPH
- BANDS COVERED - 6, 10, 15 & 20
- 1200 WATTS P.E.P.
- FEED LINE - 50 OHMS

If not stocked by your dealer order direct. We pay shipping in USA. Send for free catalog of other models and more data.

Mini-Products, Inc.

1001 W. 18th St. Erie, Pa. 16502



A Christmas MESSAGE TO ALL...

Did you miss the mark again? Do you have trouble understanding where you fit in?
 In the beginning, God created us to have fellowship with Him and to love Him as our heavenly Father. If you are a parent, you experience what it means to love your children and for them to love you. Whether they are right or wrong, you still love them because they are part of you. When your children disobey and disappoint you, your fellowship together is broken. If your children disobey and want them to return to your plan for their lives. You continue to love them and say, "Dad, I'm sorry for missing the mark that you desired for me, please forgive me.", you would open your arms and welcome them back into your fellowship.

The Bible says in Romans 3:23, "All have sinned and come short of the glory of God." Isn't that just like us? We try to do our own thing and forget what our Father has planned for us.
 The Bible also says in I John 1:9, "If we confess our sins, He is faithful and just to forgive us our sins, and to cleanse us from all unrighteousness." Isn't it great to know that we can come home and have the desired fellowship with our Father in heaven.
 Jesus commented, "I am come that they might have life, and that they might have it more abundantly." (John 10:10b)
 Make your heavenly Father happy this Christmas and come home.
 Wishing you a meaningful Christmas,
 Lee, Andy, Jane, Denny, Don, Bill, Denny
 Rick, Linda, Barb, Lee, and Crissa



RD-1 • BOX 185A • FRANKLIN, PA. 16323

Webster says:
radio, inc.

You can really "ham" it up with our great line of transceivers!



The FT-101E YAESU Transceiver with new RF Speech Processor. Solid state 160 thru 10 meters. **\$749***
 * FT 101EE (less processor) \$659
 * FT 101EX (less accessories) \$599



The TS-700 **KENWOOD** Transceiver. Solid state 2 meters SSB/FM/CW/AM. **\$700.**

CTC: UHF/VHF
POWER TRANSISTORS FOR AMATEUR USE
J101 UNDERWOOD CAPACITORS

Order Direct 1. Check or M.O. with order.
3 E-Z Ways 2. Bank Americard or Mastercard.
3. C.O.D. (20% deposit, please)

Write for FREE brochures and particulars on all models.
Webster radio, inc.
 2602 E. Ashlan
 Fresno, CA 93726
 Phone (209) 224-5111

SUPER VALUE!

- ICS Socketed
- Push button Switches on Main PC Board
- Open chassis for Easy Assembly

2 IN 1 DMM-COUNTER



FCM-6
6 DIGIT
40 MHz KIT
\$179⁹⁵
 FCM-8
8 DIGIT
150 MHz KIT
\$219.95

Size 10W x 3-1/2H x 9D

Meter: Auto polarity and overrange indicator. 11 Meg. Ohm input impedance. Four overlapping ranges on AC-DC volts and current to 1KV and 1 AMP and five ranges on ohms to 1 Meg. Ohm. 500% overrange capability, except current. Accuracy: $\pm 1\%$, ± 1 count DC, $\pm 1.5\%$, ± 1 count AC and Ohms. Counter: Same as FCC-8.

CAPACITANCE COUNTER



NOW, IT IS A DREAM TO MEASURE YOUR CAPACITORS.
\$79⁹⁵ KIT
ASSEMBLED \$99.95

Size 7W x 3H x 8D

$\pm 1\%$ ± 1 count (± 1 pfd. below 100 pfd.)
 Four ranges from pico farads to several thousand microfarads. Features crystal timebase reference for stability. Auto-cycling.

- Deluxe Metal Cabinet
- Complete Step-by-step Instruction & Diagrams
- .3 in. 7-Seg. LED Readouts


FREQUENCY COUNTER



FC-6
30 MHz KIT
\$89⁹⁵
 FC-6H
150 MHz KIT
\$109.95

Size 7W x 3H x 8D

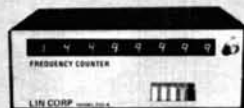Perfect for CBers, hams, hobbyists, technicians. Hi Z input, 100MV sensitivity. Frequency 10 Hz to over 30 Mhz. (FC-6) and 100 Hz to over 150 Mhz. (FC-6H). Crystal timebase. 5 ppm.



FCC-8
8 DIGIT
150 MHz KIT
\$149⁹⁵

Size 10W x 3-1/2H x 9D

Hi Z input. Sensitivity 100 millivolts at 150 Mhz. Readout Hz., Khz., or Mhz. Resolution 1 Hz. to 10 Mhz. and 10 Hz above Crystal time base - 5 ppm.

Add \$2.50 Shipping/Handling Each
 California Residents Add 6% Sales Tax
 Mastercharge and BankAmericard

Low Cost Assembled and Tested Modules for Stopwatch, Freq. Counter and Multimeter Available. Write or Call.

LIN CORP. 15311 S. Broadway, Gardena, California 90248 (213) 532-8809

NEW! IC KEYER

The World's Greatest
Sending Device



Adjustable to Any
Desired Speed

Now available from Palomar Engineers - the new Electronic IC KEYER. Highly prized by professional operators because it is EASIER, QUICKER, and MORE ACCURATE.

It transmits with amazing ease CLEAR, CLEAN-CUT signals at any desired speed. Saves the arm. Prevents cramp, and enables anyone to send with the skill of an expert.



SPECIAL RADIO MODEL

Equipped with large specially constructed contact points. Keys any amateur transmitter with ease. Sends Manual, Semi-Automatic, Full Automatic, Dot Memory, Squeeze, and Iambic - MORE FEATURES than any other keyer. Has built-in sidetone, speaker, speed and volume controls, BATTERY OPERATED, heavy shielded die-cast metal case. FULLY ADJUSTABLE contact spacing and paddle tension. The perfect paddle touch will AMAZE you.

Every amateur and licensed operator should know how to send with the IC KEYER. EASY TO LEARN. Sent anywhere on receipt of price. Free brochure sent on request.

Send check or money order. IC KEYER \$87.50 postpaid in U.S. and Canada. Add \$10.00 for HEAVY NON-SKID BASE. IC KEYER LESS PADDLE \$67.50. Add 6% sales tax in California.

Italy write I2VTT, P.O. Box 37, 22063 Cantu. Elsewhere send \$92.00 (U.S.) for IC KEYER or \$72.00 (U.S.) for IC KEYER LESS PADDLE for air parcel post delivery worldwide.


Fully guaranteed by the world's oldest manufacturer of electronic keys. ORDER YOURS NOW!

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025
Phone: (714) 747-3343

FAST SCAN AMATEUR TELEVISION EQUIPMENT

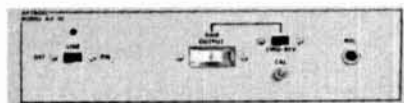- SOLID STATE
- BROADCAST QUALITY PERFORMANCE
- FOR TECHNICAL DATA AND PRICING, WRITE TO:



AX-10 TRANSMITTER



AM-1A RCVR MODEM

APTRON LABORATORIES BOX 323, BLOOMINGTON, IN 47401


! HELP !



MIXED VALUES.
DISC CERAMIC CAPACITORS
\$5.00/LB. PPD. IN U.S.A.

If you don't like the pound you get — call or write and we'll send another pound FREE. (And you keep the first pound.)

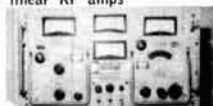.7-9pF Glass Piston Trimmer, JFD, VC-1 \$2.25 ea
10 for \$17.5 ea
4.7 MFD/10V Sprague 158D \$7.50/Hundred
COLLINS 635V-1 Bandpass filter, 2-29.999 MHz,
tunes in 1 kc increments. Sharply selective filter
w/integral linear RF amps \$175.00



Great Repeater Receiver. 215-265 MHz Plug in front-end & video unit with BW 1.5 KC — 1 MC built-in deviation meter. Defense Electronics Model TMR-5A. Only 1 in stock. SPECIAL \$215.00



RCVR 2 to 30 MHz depending on the plug-in front end. Provision for XTAL control. Makes a fine single-channel H.F. RCVR. \$125.00
100 kHz solid state standard frequency oscillator. Complete in oven. Size: 4 1/4" x 2" x 1 1/2". James Knight's part #JKT0-23. Octal plug-in. Hermetically sealed. \$25.00

WE ARE BUYERS as well as sellers. What have you? We don't have a catalog, by the time we'd publish it the merchandise would be gone.

DISC-CAP, 19075 BRAEMORE RD.
NORTHRIDGE, CA. 91326 213-360-3387

GROTH-Type

COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

PRICES

TC 2 — \$8.00
TC 3 — \$8.75
Spinner (\$) — \$1.00
Add \$0.75 for Air or UPS

Model TC2: Skirt 2-1/8";
Knob 1-5/8"
Model TC3: Skirt 3";
Knob 2-3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

WANTED: TECHNICIANS WITH SOLID STATE AND SSB EXPERIENCE

If you are a really sharp technician who would enjoy working in the Amateur Radio field, we have excellent opportunities for a bright future. No phone calls please.

Send your resume to: Atlas Radio,
417 Via Del Monte, Oceanside,
CA 92054.

FEATURING COMPLETE YAESU LINE



FT-101E TRANSCEIVER

ORDER TODAY
WRITE OR CALL

Mail Orders accepted. N. Y. residents add sales tax. See us for all your Amateur Radio needs. SASE will get our list of used Amateur Equipment.

Jim Beckett
WA2KJT

C F P COMMUNICATIONS

Store Hours
Tues. to Sat.
10-6 p.m.

Bryant Hozempa
WB2LWV



211 NORTH MAIN STREET
HORSEHEADS, N. Y. 14845
PHONE: 607-739-0187



Fri. & Sat. subject to
Hamfest weekends
Closed Sun. & Mon.

Performance... your choice for under \$299*

Horizon "2" outclasses them all! 25 watt output 2 Meter FM transceiver for HAM, CAP, and MARS • Full 12 channel capability • All solid state • Compact size: 6¼ x 2¾ x 9 inches • Weighs less than 4 pounds • Dynamic microphone • Built-in speaker • External speaker jack for 3 watts of crisp audio • Unique quick release/locking bracket and key included.

Because no two transceiver applications are exactly alike, Standard also makes the rugged 146-A. An action Handheld for 2 meter FM, the 146-A, like the Horizon "2", is also available for under *\$299. Both of these rugged radios offer you exceptional quality and outstanding performance at a price that's right.



Standard Communications

Standard Communications Corp. P.O. Box 92151 • Los Angeles • Ca • 90009

Cramped for Antenna space?



The answer to your problem is here!!!

The McKay DYMEK DA 100.

The DA 100 is a compact, wide dynamic range, broadband, untuned, omni-directional receiving antenna covering the frequency range of 50 kHz to 30 MHz.

The exterior module, a small weather-proof box with a 56 inch (142 cm) whip delivers the signal to the power supply unit through a supplied 50' coaxial cable.

The power supply locates near your general coverage receiver and attaches with a supplied patch cord.

The DA 100 antenna is small, but will equal or outperform a 100' long wire antenna, and is priced within reach of everyone!

Order factory direct. Call toll free today! Money-back guarantee. Rent/own plan available. Complete specs and details on request. In Canada, contact Ro-Bar Electronics, 140 Doncaster, Thornhill, Ontario (416) 881-2331.

Nationwide 800/854-7769

California 800/472-1783



MK McKay Dymek Company
675 N. Park Ave., P.O. Box 2100
Pomona, Calif. 91766

Incredible counter! Incomparable price!

A 500MHz (6-Digit) FREQUENCY COUNTER for under 40 cents per mHz! Figure it out. It adds up to unheard-of savings! With guaranteed quality to match and exceed overpriced brands. Let us prove it to you now!

(6-DIGIT/500MHz KIT) FREQUENCY COUNTER



169⁹⁵

\$199.95 assembled

Perfect for: CBers, Hams, Service Techs, & Experimenters!

• HAM, CB, & COMMERCIAL BANDS • WIRED & TESTED AVAILABLE • 100HZ READOUT • 6 DIGITS • CRYSTAL TIME-BASE • 1Hz OPTIONAL • MASTER CHG. / B. AMERICARD OK • ADD \$2 SHIPPING

Hufco

Incredible counters starting at \$45.95 are also available!

All counters can be factory wired and tested. Write or call today!

Box 357, Dept. 61, Provo, UT 84601 (801) 375-8566

ham radio

cumulative index

1968-1976

antennas and transmission lines

general

Antenna control, automatic azimuth/elevation for satellite communications
 WA3HLT p. 26, Jan 75
 Correction p. 58, Dec 75

Antenna dimension (HN)
 WA9JMY p. 66, Jun 70

Antennas and capture area
 K6MIO p. 42, Nov 69

Antenna and control-link calculations for repeater licensing
 W7PUG p. 58, Nov 73
 Short circuit p. 59, Dec 73

Antenna and feedline facts and fallacies
 W5JJ p. 24, May 73

Antenna design, programmable calculator simplifies (HN)
 W3DVO p. 70, May 74

Antenna gain (letter)
 W3AFM p. 62, May 76

Antenna gain, measuring
 K6JYO p. 26, Jul 69

Antenna switching, solid-state
 W2EEY p. 30, Nov 68

Anti-QRM methods
 W3FQJ p. 50, May 71

Bridge for antenna measurements, simple
 W2CTK p. 34, Sep 70

Cubical quad measurements
 W4YM p. 42, Jan 69

Dipole center insulator (HN)
 WA1ABP p. 69, May 69

Diversity receiving system
 W2EEY p. 12, Dec 71

Dummy load and rf wattmeter, low-power
 W2OLU p. 56, Apr 70

Dummy loads, experimental
 W8YFB p. 36, Sep 68

Dummy load, low-power vhf
 WB9DNI p. 40, Sep 73

Effective radiated power (HN)
 VE7CB p. 72, May 73

Feedpoint impedance characteristics of practical antennas
 W5JJ p. 50, Dec 73

Filters, low-pass, for 10 and 15
 W2EEY p. 42, Jan 72

Gain vs antenna height, calculating
 WB8IFM p. 54, Nov 73

GDO, new uses for
 K2ZSQ p. 48, Dec 68

Grounding, safer (letter)
 WA5KTC p. 59, May 72

Ground rods (letter)
 W7FS p. 66, May 71

Ground systems, vertical antenna
 W7LR p. 30, May 74

Headings, beam antenna
 W6FFC p. 64, Apr 71

Hook, line 'n sinker (HN)
 WA4NED p. 76, Sep 68

Horizontal or vertical (HN)
 W7IV p. 62, Jun 72

Impedance measurements, nonresonant antenna
 W7CSD p. 46, Apr 74

Insulators, homemade antenna (HN)
 W7ZC p. 70, May 73

Isotropic source and practical antennas
 K6FD p. 32, May 70

Lightning protection (C&T)
 W1DTY p. 50, Jun 76

Line-of-sight distance, calculating
 WB5CBC p. 56, Nov 76

Measurement techniques for antennas and transmission lines
 W4OQ p. 36, May 74

Measuring antenna gain
 K6JYO p. 26, Jul 69

Mobile mount, rigid (HN)
 VE7ABK p. 69, Jan 73

Power in reflected waves
 Woods p. 49, Oct 71

Reflected power, some reflections on
 VE3AAZ p. 44, May 70

Reflectometers
 K1YZW p. 65, Dec 69

Rf current probe (HN)
 W6HPH p. 76, Oct 68

Rf power meter, low-level
 W5WGF p. 58, Oct 72

Sampling network, rf — the milli-trap
 W6QJW p. 34, Jan 73

Smith chart, how to use
 W1DTY p. 16, Nov 70
 Correction p. 76, Dec 71

Standing-wave ratios, importance of
 W2HB p. 26, Jul 73
 Correction (letter) p. 67, May 74

Time-domain reflectometry, practical experimenter's approach
 WAØPIA p. 22, May 71

T-R switch
 K3KMO p. 61, Apr 69

Voltage-probe antenna
 W1DTY p. 20, Oct 70

high-frequency antennas

All band antenna portable (HN)
 W2INS p. 68, Jun 70

All-band phased-vertical
 WA7GXO p. 32, May 72

Antenna, 3.5 MHz, for a small lot
 W6AGX p. 28, May 73

Antenna potpourri
 W3FQJ p. 54, May 72

Antenna systems for 80 and 40 meters
 K6KA p. 55, Feb 70

Army loop antenna — revisited
 W3FQJ p. 59, Sep 71
 Added notes p. 64, Jan 72

Beam antenna, improved triangular shaped
 W6DL p. 20, May 70

Beam for ten meters, economical
 W1FPF p. 54, Mar 70

Beverage antenna
 W3FQJ p. 67, Dec 71

Big beam for 10 meters
 VE1TG p. 32, Mar 68

Bobtail curtain array, forty-meter
 VE1TG p. 58, Jul 69

Coaxial dipole antenna, analysis of
 W2DU p. 46, Aug 76

Coaxial dipole, multiband (HN)
 W4BDK p. 71, May 73

Collinear, six-element, for
 WØYBF p. 22, May 76

Compact antennas for 20 meters
 W4ROS p. 38, May 71

Converted-vee, 80 and 40 meter
 W6JKR p. 18, Dec 69

Corner-fed loop, low frequency
 ZL1BN p. 30, Apr 76

Cubical quad antenna design parameters
 K6OPZ p. 55, Aug 70

Cubical-quad antennas, mechanical design of
 VE3II p. 44, Oct 74

Cubical-quad antennas, unusual
 W1DTY p. 6, May 70

Cubical quad, improved low-profile, three band
 W1HXU p. 25, May 76

Cubical quad, three-band
 W1HXU p. 22, Jul 75

Curtain antenna (HN)
 W4ATE p. 66, May 72

Dipole, all-band tuned
 ZS6BT p. 22, Oct 72

Dipole antennas on non-harmonic frequencies (HN)
 W2CTK p. 72, Mar 69

Dipole beam
 W3FQJ p. 56, Jun 74

Dipole pairs, low SWR
 W6FPO p. 42, Oct 72

Dipole sloping inverted-vee
 W6NIF p. 48, Feb 69

Double bi-square array
 W6FFF p. 32, May 71

Dual-band antennas, compact
 W6SAI p. 18, Mar 70

DX antenna, single-element
 W6FHM p. 52, Dec 72
 Performance (letter) p. 65, Oct 73

Folded mini-monopole antenna
 W6SAI p. 32, May 68

Four-band wire antenna
 W3FQJ p. 53, Aug 75

Ground-plane, multiband (HN)
 JA1QIY p. 62, May 71

Groundplane, three-band
 LA1EI p. 6, May 72
 Correction p. 91, Dec 72
 Footnote (letter) p. 65, Oct 72

High-frequency amateur antennas
 W2WLR p. 28, Apr 69

High-frequency diversity antennas
 W2WLR p. 28, Oct 69

Horizontal-antenna gain at selected vertical radiation angles
 W7LR p. 54, Feb 76

Horizontal antennas, optimum height for
 W7LR p. 40, Jun 74

Horizontal antennas, vertical radiation patterns
 WA9RQY p. 58, May 74

Inverted-vee antenna (letter)
 WB6AQF p. 66, May 71

Inverted-vee antenna, modified
 W2KTW p. 40, Oct 71

Inverted-vee installation, improved low-band (HN)
 W9KNI p. 68, May 76

Inverted V or delta loop, how to add to tower
 K4DJC p. 32, Jul 76

Large vertical, 160 and 80 meters
 W7IV p. 8, May 75

Log-periodic antenna, 14, 21 and 28 MHz
 W4AEO p. 18, Aug 73

Log-periodic antennas, 7-MHz
 W4AEO p. 16, May 73

Log-periodic antennas, feed system for
 W4AEO p. 30, Oct 74

Log periodic antennas, graphical design method for
 W4AEO p. 14, May 75

Log-periodic antennas, vertical monopole, 3.5 and 7.0 MHz
 W4AEO p. 44, Sep 73

Log-periodic beams, improved (letter)
 W4AEO p. 74, May 75

Log-periodic beam, 15 and 20 meters
 W4AEO p. 6, May 74

Log periodic feeds (letter)
 W4AEO p. 66, May 74

Log-periodic, three-band
 W4AEO p. 28, Sep 72

Long-wire multiband antenna
 W3FQJ p. 28, Nov 69

Loop antennas
 W4OQ p. 18, Dec 76

Loop receiving antenna
 W2IMB p. 66, May 75
 Correction p. 58, Dec 75

Lopp-yagi antennas
 VK2ZTB p. 30, May 76

Low-mounted antennas
 W3FQJ p. 66, May 73

Mobile antenna, helically wound
 ZE6JP p. 40, Dec 72

Mono-loop antenna (HN)
 W8BW p. 70, Sep 69

Multiband dipoles for portable use
 W6SAI p. 12, May 70

Phased array, electrically-controlled
 W5TRS p. 52, May 75

Phased vertical array, four-element
 W8HXR p. 24, May 75

Quad antenna, multiband
 DJ4VM p. 41, Aug 69

Receiving antennas
 K6ZGQ p. 56, May 70

Satellite antenna, simple (HN)
 WA6PXY p. 59, Feb 75

Selective antenna system minimizes unwanted signals
 W5TRS p. 28, May 76

Shunt-feed systems for grounded vertical radiators, how to design
 W4OQ p. 34, May 75

Simple antennas for 40 and 80
 W5RUB p. 16, Dec 72

Simple 1-, 2- and 3-band antennas
 W9EGQ p. 54, Jul 68

Sloping dipoles
 W5RUB p. 19, Dec 72
 Performance (letter) p. 76, May 73

Small-loop antennas
 W4YOT p. 36, May 72

Stub bandswitched antennas
 W2EEY p. 50, Jul 69

Suitcase antenna, high-frequency
 VK5BI p. 61, May 73

Tailoring your antenna, how to
 KH6HDM p. 34, May 73

Telephone-wire antenna (HN) K9TBD	p. 70, May 76
Three-band ground plane W6HPH	p. 32, Oct 68
Triangle antennas W3FQJ	p. 56, Aug 71
Triangle antennas W6KIW	p. 58, May 72
Triangle antennas (letter) K4ZZV	p. 72, Nov 71
Triangle beams W3FQJ	p. 70, Dec 71
Tuning aid for the sightless (HN) W6VX	p. 83, Sep 76
Unidirectional antenna for the low-frequency bands GW3NJY	p. 61, Jan 70
Vertical antenna radiation patterns W7LR	p. 50, Apr 74
Vertical antenna, low-band W4IYB	p. 70, Jul 72
Vertical antenna, three-band W9BQE	p. 44, May 74
Vertical antennas, improving performance of K6FD	p. 54, Dec 74
Vertical antennas, performance characteristics W7LR	p. 34, Mar 74
Vertical beam antenna, 80 meter VEITG	p. 26, May 70
Vertical dipole, gamma-loop-fed W6SAI	p. 19, May 72
Vertical for 80 meters, top-loaded W2MB	p. 20, Sep 71
Vertical radiators W4OQ	p. 16, Apr 73
Vertical, top-loaded 80 meter VEITG	p. 48, Jun 69
Vertical-tower antenna system W4OQ	p. 56, May 73
Whips and loops as apartment antennas W2EY	p. 80, Mar 68
Windom antenna, four-band W4VUO	p. 62, Jan 74
Correction (letter)	p. 74, Sep 74
Zepp antenna, extended W6QVI	p. 48, Dec 73
ZL special antenna, understanding the WA6TKT	p. 38, May 76
160-meter loop, receiving K6HTM	p. 46, May 74
160-meter vertical, shortened (HN) W6VX	p. 72, May 76
160 meters with 40-meter vertical W21MB	p. 34, Oct 72

vhf antennas

Antennas for satellite communications, simple K4GSX	p. 24, May 74
Circularly-polarized ground-plane antenna for satellite communications K4GSX	p. 28, Dec 74
Collinear antenna for two meters, nine-element W6RJO	p. 12, May 72
Collinear antenna (letter) W6SAI	p. 70, Oct 71
Collinear array for two meters, 4-element WB6KGF	p. 6, May 71
Collinear antenna, four element 440-MHz WA6HTP	p. 38, May 73
Collinear, six meter K4ERO	p. 59, Nov 69
Corner reflector antenna, 432 MHz WA2FSQ	p. 24, Nov 71
Cubical quad, economy six-meter W6DOR	p. 50, Apr 69
Feed horn, cylindrical, for parabolic reflectors WA9HUV	p. 16, May 76
Ground plane, 2-meter, 0.7 wavelength W3WZA	p. 40, Mar 69
Ground plane, portable vhf (HN) K9DHD	p. 71, May 73
J-pole antenna for 6-meters K4SDY	p. 48, Aug 68
Log-periodic, yagi beam K6RIL, W6SAI	p. 8, Jul 69
Correction	p. 68, Feb 70
Magnet-mount antenna, portable (HN) WB2YYU	p. 67, May 76
Matching techniques for vhf/uhf antennas W1JAA	p. 50, Jul 76
Microwave antenna, low-cost K6HIJ	p. 52, Nov 69
Mobile antenna, magnet-mount W1HCI	p. 54, Sep 75
Mobile antenna, six-meter (HN) W4PSJ	p. 77, Oct 70
Moonbounce antenna, practical 144-MHz K6HCP	p. 52, May 70
Oscar antenna, mobile (HN) W6OAL	p. 67, May 76
Parabolic reflector antennas VK3ATN	p. 12, May 74
Parabolic reflector element spacing WA9HUV	p. 28, May 75
Parabolic reflector gain W2TQK	p. 50, Jul 75

Parabolic reflectors, finding the focal length (HN) WA4WDL	p. 57, Mar 74
Parabolic reflector, 16-foot homebrew WB6IOM	p. 8, Aug 69
Quad-yagi arrays, 432- and 1296-MHz W3AED	p. 20, May 73
Short circuit W3AED	p. 58, Dec 73
Simple antennas, 144-MHz WA3NFW	p. 30, May 73
Switch, antenna for 2 meters, solid-state K2ZSQ	p. 48, May 69
Two-meter antenna, simple (HN) W6BLZ	p. 78, Aug 68
Two-meter fm antenna (HN) WB6KYE	p. 64, May 71
Two-meter mobile antennas W6BLZ	p. 76, May 68
Vertical antennas, truth about $\frac{1}{8}$ -wavelength KØDOK	p. 48, May 74
Added note (letter)	p. 54, Jan 75
Vhf antenna switching without relays (HN) K2ZSQ	p. 76, Sep 68
Whip, 5/8-wave, 144 MHz (HN) VE3DDD	p. 70, Apr 73
Yagi, 1296-MHz W2CQH	p. 24, May 72
7-MHz attic antenna (HN) W2ISL	p. 68, May 76
10-GHz dielectric antenna (HN) WA4WDL	p. 80, May 75
144-MHz vertical, $\frac{1}{8}$ -wavelength K6KLO	p. 40, Jul 74
144-MHz antenna, $\frac{1}{8}$ -wavelength built from CB mobile whip (HN) WB4WSU	p. 67, Jun 74
144-MHz colinear uses PVC pipe mast (HN) K8LLZ	p. 66, May 76
144-MHz vertical mobile antennas, $\frac{1}{4}$ and $\frac{1}{8}$ wavelength, test data on W2LTJ, W2CQH	p. 46, May 76
144-MHz, $\frac{1}{8}$ -wavelength vertical W1RHN	p. 50, Mar 76
144-MHz, $\frac{1}{8}$ -wavelength, vertical antenna for mobile K4LPQ	p. 42, May 76
432-MHz high-gain Yagi K6HCP	p. 46, Jan 76
Comments, WØPW	p. 63, May 76
432-MHz OSCAR antenna (HN) W1JAA	p. 58, Jul 75
1296-MHz Yagi array W3AED	p. 40, May 75

matching and tuning

Antenna coupler for three-band beams ZS6BT	p. 42, May 72
Antenna coupler, six-meter K1RAK	p. 44, Jul 71
Antenna impedance transformer for receivers (HN) W6NIF	p. 70, Jan 70
Antenna matcher, one-man W4SD	p. 24, Jun 71
Antenna tuner adjustment (HN) WA4MTH	p. 53, Dec 75
Antenna tuner, automatic WAØAQC	p. 36, Nov 72
Antenna tuner, medium-power toroidal WB2ZSH	p. 58, Jan 74
Antenna tuner for optimum power transfer W2WLR	p. 28, May 70
Antenna tuners W3FQJ	p. 58, Dec 72
Antenna tuning units W3FQJ	p. 58, Jan 73
Balun, adjustable for yagi antennas W6SAI	p. 14, May 71
Balun, Simplified (HN) WAØKKC	p. 73, Oct 69
Baluns, wideband bridge W6SAI, WA6BAN	p. 28, Dec 68
Broadband Antenna Baluns W6SAI	p. 6, Jun 68
Couplers, random-length antenna W2EY	p. 32, Jan 70
Dummy loads W4MB	p. 40, Mar 76
Feeding and matching techniques for vhf/uhf antennas W1JAA	p. 54, May 76
Gamma-match capacitor, remotely controlled K2BT	p. 74, May 75
Gamma-matching networks, how to design W7ITB	p. 46, May 73
Impedance bridge, low-cost RX W8YFB	p. 6, May 73
Impedance-matching baluns, open-wire W6MUR	p. 46, Nov 73
Impedance-matching systems, designing W7CSD	p. 58, Jul 73
Loads, affect of mismatched transmitter W5JJ	p. 60, Sep 69
Matching, antenna, two-band with stubs W6MUR	p. 18, Oct 73
Matching system, two-capacitor W6MUR	p. 58, Sep 73
Measuring complex impedance with swr bridge WB4KSS	p. 46, May 75

Mobile transmitter, loading W4YB	p. 46, May 72
Noise bridge, antenna WB2EGZ	p. 18, Dec 70
Noise bridge, antenna (HN) K8EEG	p. 71, May 74
Noise bridge for impedance measurements YA1GJM	p. 62, Jan 73
Added notes	p. 66, May 74; p. 60, Mar 75
Phase meter, rf VE2AYU, Korth	p. 28, Apr 73
Quadrifilar toroid (HN) W9LL	p. 52, Dec 75
Stub-switched, stub-matched antennas W2EY	p. 34, Jan 69
Swr alarm circuits W2EY	p. 73, Apr 70
Swr bridge WB2ZSH	p. 55, Oct 71
Swr bridge and power meter, integrated W6DOB	p. 40, May 70
Swr bridge readings (HN) W6FPO	p. 63, Aug 73
Swr indicator, aural, for the visually handicapped K6HTM	p. 52, May 76
Swr meter W6VSV	p. 6, Oct 70
Swr meter, improving (HN) W5NPD	p. 68, May 76
Transmatch, five-to-one W7IV	p. 54, May 74
Transmission lines, grid dipping (HN) W2OLU	p. 72, Feb 71
Transmission lines, uhf WA2VTR	p. 36, May 71
Uhf coax connectors (HN) WØLCP	p. 70, Sep 72

towers and rotators

Antenna and rotator preventive maintenance WA1ABP	p. 66, Jan 69
Antenna and tower restrictions W7IV	p. 24, Jan 76
Antenna mast, build your own tilt-over W6KRT	p. 42, Feb 70
Correction	p. 76, Sep 70
Az-el antenna mount for satellite communications W2LX	p. 34, Mar 75
Cornell-Dubilier rotators (HN) K6KA	p. 82, May 75
Ham-M modifications (HN) W2TQK	p. 72, May 76
Keeping your beam, tips for W6BLZ	p. 50, Aug 68
Pipe antenna masts, design data for W3MR	p. 52, Sep 74
Added design notes (letter)	p. 75, May 75
Rotator, AR-22, fixing a sticky WA1ABP	p. 34, Jun 71
Rotator for medium-sized beams K2BT	p. 48, May 76
Rotator, T-45, Improvement (HN) WAØVAM	p. 64, Sep 71
Stress analysis of antenna systems W2FZJ	p. 23, Oct 71
Telescoping tv masts (HN) WAØKKC	p. 57, Feb 73
Tilt-over tower base, low-cost WA1ABP	p. 86, Apr 68
Tilt-over tower uses extension ladder W5TRS	p. 71, May 75
Tower, homemade tilt-over WA3EWH	p. 28, May 71
Tower, wind-protected crank-up (HN) K6KA	p. 74, Oct 69
Towers and rotators K6KA	p. 34, May 76
Wind loading on towers and antenna structures, how to calculate K4KJ	p. 16, Aug 74
Added note	p. 56, Jul 75

transmission lines

Coax cable dehumidifier K4RJ	p. 26, Sep 73
Coax connectors, repairing broken (HN) WØHKF	p. 66, Jun 70
Coaxial cable (C&T) W1DTY	p. 50, Jun 76
Coaxial cable, checking (letter) W2OLU	p. 68, May 71
Coaxial cable connectors (HN) WA1ABP	p. 71, Mar 69
Coaxial-cable fittings, type-F K2MDO	p. 44, May 71
Coaxial cable supports (HN) W2GA	p. 56, Jun 68
Coaxial cable, what you know about W9ISB	p. 30, Sep 68
Coaxial connectors can generate rfi W1DTY	p. 48, Jun 76
Coaxial feedthrough panel (HN) W3URE	p. 70, Apr 69



There's
nothing
like it !

RADIO AMATEUR
callbook

Respected worldwide as
the only complete authority
for radio amateur
QSL and QTH information.

The U. S. Callbook has nearly
300,000 W & K listings. It lists
calls, license classes, names
and addresses plus the many
valuable back-up charts and
references you come to expect
from the Callbook.

Specialize in DX? Then you're
looking for the Foreign Callbook
with almost 235,000 calls,
names and addresses of ama-
teurs outside of the USA.

U.S. Callbook \$14.95

Foreign Callbook \$13.95

Order from your favorite elec-
tronics dealer or direct from the
publisher. All direct orders add
\$1.25 for shipping. Illinois residents
add 5% Sales Tax.

RADIO AMATEUR
callbook INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

COMPETITIVELY PRICED!

ALL PRODUCTS FULLY ASSEMBLED, TESTED AND WARRANTED.
PRICES INCLUDE ALL POSTAGE FEES WITHIN THE USA.
FOREIGN ORDERS, ADD \$3.00 TO COVER POSTAGE & HANDLING.

Arizona Residents
Add 5% Sales Tax



\$49.95
EPC-300
300 MHz Prescaler

- o Built-In 117 vac 60 Hz power supply
- o Size 3 1/2" w x 2 1/2" h x 4" L
- o BNC input, output connectors
- o Input impedance = 50 ohms
- o Output TTL. Fan out of 1
- o Sensitivity 14 mv @ 150 MHZ,
150 mv @ 300 MHZ



\$32.95
EPC-144-B
2 Meter FM Transmitter

- o 2 Channels, 144-148 MHZ
- o Power Output 2 watts typical, 1 watt
min @ 12.5 VDC
- o 50 ohm output impedance
- o Narrow band FM ± 5 KHZ
- o Rugged balanced emitter output
transistor
- o Small size 1 7/8" w x 1" h x 3 3/4" L



Input Watts	Output Watts Min. Typical
1	15 20
2	20 25
4	30 30

\$39.95
LA-144

- 30 Watt 2 Meter Power Amplifier
- o Frequency range 144-148 MHZ
 - o Maximum RF output power 30 watts
 - o Maximum RF input power 5 watts
 - o Supply voltage 13.6 VDC
 - o Small size 1 7/8" w x 5/8" h x 3 3/4" L
 - o Virtually burn-out proof balanced
emitter output transistor.
 - o Fully compatible with the EPC-144-B
 - o 50 ohm input & output impedance
 - o Sold as a fully tested & assembled
circuit board less case, connectors
and heat sink

Send Self-Addressed Stamped
Envelope For More Information

Elprocon
ELECTRONIC PROTOTYPE CONSULTANTS
1907 W. Campbell / Phoenix, Arizona 85015

COMPARING KEYS ?




Check these features :

- operates on 110 VAC or 12 VDC
no batteries to change
- not a kit, wired and tested
- your choice of dot and/or
dash memory

*m-one introductory price \$49.00


MONOLITH ELECTRONICS
box 2952 sta. A, Champaign, Ill. 61820

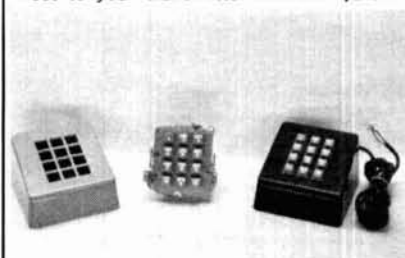12 Button touch-tone pads calibrated and
guaranteed 90 days (abuse excluded) with
diagram \$14.00
Attractive plastic mounting box with
brackets \$4.75
Complete working system ready to connect
to your transmitter \$24.95



TELEPHONE EQUIPMENT COMPANY
Post Office Box 596, Leesburg, Florida 32748
(904) 728-2730

VHF TRANSVERTERS

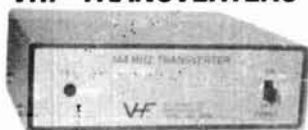

- 50, 144 & 220MHZ models
- 1 watt min. output
- Compatible with HF SSB equipt
\$129.50

VHF Signal Co.
2246 Beech St.
Laurel, DE 19956 (302) 846-2691

**MILITARY
SURPLUS WANTED**

Space buys more and pays more. High-
est prices ever on U.S. Military sur-
plus, especially on Collins equipment
or parts. We pay freight. Call collect
now for our high offer. 201 440-8787.

SPACE ELECTRONICS CO.
div. of Military Electronics Corp.
35 Ruta Court, S. Hackensack, N.J. 07606

DIPOLE ANTENNA CONNECTOR



HYE-QUE (HQ-1) dipole connector
has coax SO-239 socket molded into
glass filled plastic body to accept
coax PL-259 plug on feeding. Drip-
cap keeps coax fittings dry. Instruc-
tions included. Guaranteed. At your
dealers or \$1.95 postpaid. Com-
panion insulators, 2/\$.99.

BUDWIG MFG. Co. PO Box 97H, Ramona, CA 92065

ANTENNA SUPERMARKET, PO Box 1682, Dept. H, Largo, Fla. 33540

DIPOLE AND WIRE ANTENNA KITS, complete with HI-Q BALUN, 100' rope, copper
antenna wire and insulators.

80/40/15 parallel dipole	\$36.95	160 short, 130' length	\$36.95
40/20/15 parallel dipole	\$30.95	80 short, 63' length	\$31.95
80/40 trap dipole	\$41.95	40 short, 33' length	\$28.95
40/20 trap dipole	\$36.95	Single band models from	\$24.95

VERTICALS — complete with Universal Mounting Base, Folds
to 5' for Easy Transport, Hvy. Duty Aluminum Tubing.

20/15 trap, 13' hgt.	\$29.95	160 compact 23' hgt.	\$44.95
40/20/15 trap 22' hgt.	44.95	80 compact 20' hgt.	39.95
80/40/20 trap 30' hgt.	69.95	40 compact 15' hgt.	34.95
80/40/15 trap 20' hgt.	59.95	20/15/10 full size vertical	29.95
10 meter cov. for above add	9.95		

NEW

Apartment / Portable
apt. roof or patio,
camper, trailer, mo-
tor home. All bands
80 10, folds to 5'
easily, 13' height.
80 40-20 15-10 \$49.95

TO ORDER — Include \$1.95 shipping (\$2.95 West Coast)
24 hour shipment, 30 day guarantee.
For Info: 1st Class Stamp.



Include Interbank # and
Expiration date on Credit
Card orders.

Coaxial-line loss, measuring with reflectometer
W2VCI p. 50, May 72

Coax, Low-cost (HN)
K6BIJ p. 74, Oct 69

Coaxial transmission lines, underground
W0FCH p. 38, May 70

Impedance transformer, non-synchronous (HN)
W5TRS p. 66, Sep 75
Comments, W3DVO p. 63, May 76

Open-wire feedthrough insulator (HN)
W4RNL p. 79, May 75

Single feedline for multiple antennas
K2ISP p. 58, May 71

Solenoid rotary switches
W2EEY p. 36, Apr 68

Transmission line calculations, using your pocket calculator for
W5TRS p. 40, Nov 76

Tuner, receiver (HN)
WA7KRE p. 72, Mar 69

Tuner, wall-to-wall antenna (HN)
W2OUX p. 56, Dec 70

Uhf microstrip swr bridge
W4CGC p. 22, Dec 72

audio

Audio agc principles and practice
WA5SNZ p. 28, Jun 71

Audio amplifier and squelch circuit
W6AJF p. 36, Aug 68

Audio CW filter
W7DI p. 54, Nov 71

Audio filter, tunable, for weak-signal communications
K6HCP p. 28, Nov 75

Audio filters, aligning (HN)
W4ATE p. 72, Aug 72

Audio filters, inexpensive
W8YFB p. 24, Aug 72

Audio filter mod (HN)
K6HILL p. 60, Jan 72

Audio mixer (HN)
W6KNE p. 66, Nov 76

Audio module, a complete
K4DHC p. 18, Jun 73

Audio-oscillator module, Cordover
WB2GQY p. 44, Mar 71
Correction p. 80, Dec 71

Audio-power integrated circuits
W3FQJ p. 64, Jan 76

Audio transducer (HN)
WA1OPN p. 59, Jul 75

Binaural CW reception, synthesizer for
W6NRW p. 46, Nov 75

Compressor, dual channel
W2EEY p. 40, Jul 68

Distortion and splatter
K5LLI p. 44, Dec 70

Dynamic microphones (C&T)
W1DITY p. 46, Jun 76

Filter for CW, tunable audio
WA1JSM p. 34, Aug 70

Filter-frequency translator for cw reception, integrated audio
W2EEY p. 24, Jun 70

Filter, lowpass audio, simple
OD5CG p. 54, Jan 74

Filter, simple audio
W4NVK p. 44, Oct 70

Filter, tunable peak-notch audio
W2EEY p. 22, Mar 70

Filter, variable bandpass audio
W3AEX p. 36, Apr 70

Hang agc circuit for ssb and CW
W1ERJ p. 50, Sep 72

Headphone cords (HN)
W2OLU p. 62, Nov 75

Headphones, lightweight
K6KA p. 34, Sep 68

Impedance match, microphone (HN)
W5JJ p. 67, Sep 73

Increased flexibility for the MFJ Enterprises CW filters
K3NEZ p. 58, Dec 76

Intercom, simple (HN)
W4AYV p. 66, Jul 72

Microphone preamplifier with agc
Bryant p. 28, Nov 71

Microphone, using Shure 401A with the Drake TR-4 (HN)
G3XOM p. 68, Sep 73

Microphones, muting (HN)
W6IL p. 63, Nov 75

Notch filter, tunable RC
WA5SNZ p. 16, Sep 75

Oscillator, audio, IC
W6GXN p. 50, Feb 73

Oscillator-monitor, solid-state audio
WA1JSM p. 48, Sep 70

Phone patch
WBGRG p. 20, Jul 71

Pre-emphasis for ssb transmitters
OH2CD p. 38, Feb 72

RC active filters using op amps
W4IYB p. 54, Oct 76

Rf clipper for the Collins S-line
K6JYO p. 18, Aug 71

Rf speech processor, ssb
W2MB p. 18, Sep 73

Speaker-driver module, IC
WA2GCF p. 24, Sep 72

Speech amplifiers, curing distortion
Allen p. 42, Aug 70

Speech clipper, IC
K6HTM p. 18, Feb 73
Added notes (letter) p. 64, Oct 73

Speech clippers, rf
G6YN p. 26, Nov; p. 12, Dec 72
Added notes p. 58, Aug 73; p. 72, Sep 74

Speech clipping in single-sideband equipment
K1YZW p. 22, Feb 71

Speech clipping (letter)
W3EJD p. 72, Jul 72

Speech compressor (HN)
Novotny p. 70, Feb 76

Speech processing
W1DITY p. 60, Jun 68

Speech processing, principles of
ZL1BN p. 28, Feb 75
Added notes p. 75, May 75; p. 64, Nov 75

Speech processing technique, split audio band
W1DITY p. 30, Jun 76

Speech processor for ssb, simple
K6PHT p. 22, Apr 70

Speech processor, IC
VK9GN p. 31, Dec 71

Speech processor, logarithmic
WA3FIY p. 38, Jan 70

Squelch, audio-actuated
K4MOG p. 52, Apr 72

Synthesizer-filter, binaural
W6NRW p. 52, Nov 76

Tape head cleaners (letter)
K4MSG p. 62, May 72

Tape head cleaning (letter)
Buchanan p. 67, Oct 72

commercial equipment

Alliance rotator improvement (HN)
K6JVE p. 68, May 72

Alliance T-45 rotator improvement (HN)
WA0VAM p. 64, Sep 71

CDR AR-22 rotator, fixing a sticky
WA1ABP p. 34, Jun 71

Clegg 27B, S-meter for (HN)
WA2YUD p. 61, Nov 74

Collins KWM-2/KWM-2A modifications (HN)
W6SAI p. 80, Aug 76

Collins R390 rf transformers, repairing (HN)
WA2SUT p. 81, Aug 76

Collins receivers, 300-Hz crystal filter for
W1DITY p. 58, Sep 75

Collins S-line, improved frequency readout for the
W1GFC p. 53, Jun 76

Collins S-line power supply mod (HN)
W6IL p. 61, Jul 74

Collins S-line receivers, improved selectivity
W6FR p. 36, Jun 76

Collins S-line, reducing warm-up drift
W6VFR p. 46, Jun 75

Collins S-line, rf clipper for
K6JYO p. 18, Aug 71
Correction p. 80, Dec 71

Collins S-line spinner knob (HN)
W6VFR p. 69, Apr 72

Collins S-line transceiver mod (HN)
W6VFR p. 71, Nov 72

Collins 32S-3 audio (HN)
K6KA p. 64, Oct 71

Collins 32S-1 CW modification (HN)
W1DITY p. 82, Dec 69
Correction p. 76, Sep 70

Collins 51J PTO restoration
W6SAI p. 36, Dec 69

Collins 70K-2 PTO, correcting mechanical backlash (HN)
K9WEH p. 58, Feb 75

Collins 75A4 avc mod (letter)
W9KNI p. 63, Sep 75

Collins 75A4 hints (HN)
W6VFR p. 68, Apr 72

Collins 75A4, increased selectivity for (HN)
W1DITY p. 62, Nov 75

Collins 75A-4 modifications (HN)
W4SD p. 67, Jan 71

Collins 75A4 noise limiter
W1DITY p. 43, Apr 76

Collins 75A4 PTO, making it perform like new
W3AFM p. 24, Dec 74

Collins 75A-4 receiver, improving overload response in
W6ZO p. 42, Apr 70
Short circuit p. 76, Sep 70

Collins 75S frequency synthesizer
W6NBI p. 8, Dec 75
Short circuit p. 85, Oct 76

Collins R390A, improving the product detector
W7DI p. 12, Jul 74

Collins R390A modifications
WA2SUT p. 58, Nov 75

Comdel speech processor, increasing the versatility of (HN)
W6SAI p. 67, Mar 71

Cornell-Dubilier rotators (HN)
K6KA p. 82, May 75

Drake R-4 receiver frequency synthesizer for
W6NBI p. 6, Aug 72
Modification (letter) p. 74, Sep 74

Drake R-4C, electronic bandpass tuning in
Horner p. 58, Oct 73

Drake TR-4, using the Shure 401A microphone with (HN)
G3XOM p. 68, Sep 73

Drake W-4 directional wattmeter
W1DITY p. 86, Mar 68

Elmac chirp and drift (HN)
W5OZF p. 68, Jun 70

EX crystal and oscillator
WB2EGZ p. 60, Apr 68

Galaxy feedback (HN)
WA5TFK p. 71, Jan 70

Hallcrafters HT-37, increased sideband suppression
W3CM p. 48, Nov 69

Ham-M modification (HN)
W2TQK p. 72, May 76

Hammarlund HQ215, adding 160-meter coverage
W2GHK p. 32, Jan 72

Heath CA1, ten-minute timer from (HN)
K8HZ p. 74, Jul 68

Heath HG-10B vfo, independent keying of (HN)
K4BRR p. 67, Sep 70

Heath HM-2102 wattmeter, better balancing (HN)
VE6RF p. 56, Jan 75

Heath HM 2102 vhf wattmeter, high power calibration for (HN)
W9TKR p. 70, Feb 76

Heath HM-2102 wattmeter mods (letter)
K3VNR p. 64, Sep 75

Heath HO-10 as RTTY monitor scope (HN)
K9HVW p. 70, Sep 74

Heath HW-7 mods, keying and receiver blanking (HN)
WA5KPG p. 60, Dec 74

Heath HW-12 on MARS (HN)
K8AUH p. 63, Sep 71

Heath HW-16 keying (HN)
W7DI p. 57, Dec 73

Heath HW16, vfo operations for
WB6MZN p. 54, Mar 73
Short circuit p. 58, Dec 73

Heath HW-17A, perking up (HN)
Heath HW-17 modifications (HN)
WA5PWX p. 66, Mar 71

Heath HW-100, HW-101, grid-current monitor for
K4MFR p. 46, Feb 73

Heath HW-100 incremental tuning (HN)
K1GUU p. 67, Jun 69

Heath HW-100, the new
W1NLB p. 64, Sep 68

Heath HW-100 tuning knob, loose (HN)
VE3EPY p. 68, Jun 71

Heath HW-101, using with a separate receiver (HN)
WA1MKP p. 63, Oct 73

Heath HW-202, adding private-line
WA8AWJ p. 53, Jun 74

Heath HW-202, another look at the fm channel scanner for
K7PYS p. 68, Mar 76

Heath HW-202 lamp replacement (HN)
W5UNF p. 83, Sep 76

Heath IM-11 vtvm, convert to IC voltmeter
K6VCI p. 42, Dec 74

Heath SB-100, using an outboard receiver with (HN)
K4GMR p. 68, Feb 70

Heath SB102 modifications (HN)
W2CNO p. 58, Jun 75

Heath SB-102, rf speech processor for
W6IVI p. 38, Jun 75

Heath SB-102, receiver incremental tuning for (HN)
K1KXA p. 81, Aug 76

Heath SB-200 amplifier, modifying for the 8873 zero-bias triode
W6UOV p. 32, Jan 71

Heath SB-200 amplifier, six-meter conversion
K1RAK p. 38, Nov 71

Heath SB-300, RTTY with
W2ARZ p. 76, Jul 68

Heath SB-303, 10-MHz coverage for (HN)
W1JE p. 61, Feb 74

Heath SB-400 and SB-401, improving a/c response in (HN)
WA9FDQ p. 71, Jan 70

Heath SB-610 as RTTY monitor scope (HN)
K9HVW p. 70, Sep 74

Heath SB-650 using with other receivers
K2BYM p. 40, Jun 73

Heath SB receivers, RTTY reception with (HN)
K9HVW p. 64, Oct 71

Heath SB-series crystal control and narrow shift RTTY with (HN)
WA4VYL p. 54, Jun 73

Heath ten-minute timer K6KA	p. 75, Dec 71
Heathkit Sixer, spot switch (HN) WA6FNR	p. 84, Dec 69
Heathkit, noise limiter for (HN) W7CKH	p. 67, Mar 71
Heathkit HW202, fm channel scanner for W7BZ	p. 41, Feb 75
Icom IC-230, adding splinter channels (HN) WA10JX	p. 82, Sep 76
James Research oscillator/monitor W1D7Y	p. 91, Mar 68
James Research permaflex key W1D7Y	p. 73, Dec 68
Kenwood TS-520 CW filter modification (HN) W7ZZ	p. 21, Nov 75
Knight-kit inverter/charger review W1D7Y	p. 64, Apr 69
Knight-kit two-meter transceiver W1D7Y	p. 62, Jun 70
Mini-mitter II W6SLQ	p. 72, Dec 71
Mini-mitter II modifications (HN) K1ETU	p. 64, Apr 76
Motorola channel elements WB4NEX	p. 32, Dec 72
Motorola Dispatcher, converting to 12 volts WB6HXU	p. 26, Jul 72
Short circuit Motorola fm receiver mods (HN) VE4RE	p. 64, Mar 74
Motorola P-33 series, improving WB2AEB	p. 60, Aug 71
Motorola receivers, op-amp relay for W6GDO	p. 34, Feb 71
Motorola voice commander, improving W0DKU	p. 16, Jul 73
Motrac Receivers (letter) K5ZBA	p. 70, Oct 70
Quement circular slide rule W2DXH	p. 69, Jul 71
Regency HR transceivers, signal-peaking indicator and generator for (HN) W8HVG	p. 62, Apr 68
Regency HR-2, narrowbanding WA8TMP	p. 68, Jun 76
Regency HR-212, channel scanner for WA0SJK	p. 44, Dec 73
R-392 receiver mods (HN) KH6FOX	p. 28, Mar 75
SBE linear implifier tips (HN) WA6DCW	p. 65, Apr 76
SB301/401, Improved sidetone operation W1WLZ	p. 71, Mar 69
Signal One review W1NLB	p. 73, Oct 69
Spurious causes (HN) K6KA	p. 56, May 69
Standard 826M, more power from (HN) WB6KVF	p. 66, Jan 74
Swan television interference: an effective remedy W2OUX	p. 68, Apr 75
Swan 120, converting to two meters K6RIL	p. 46, Apr 71
Swan 250 Carrier suppression (HN) WB8LGA	p. 8, May 68
Swan 350 CW monitor (HN) K1KXA	p. 79, Oct 76
Correction (letter) W2OUX	p. 63, Jun 72
Swan 350, receiver incremental tuning (HN) K1KXA	p. 77, May 73
Swan 350 and 400, RTTY operation (HN) WB2MIC	p. 64, Jul 71
Swan 250, update your (HN) K8ZHZ	p. 67, Aug 69
Telefax transceiver conversion K0QMR	p. 84, Dec 69
Ten-Tec Argonaut, accessory package for W7BBX	p. 16, Apr 74
Ten-Tec KR-20 keyer, stabilization of (HN) W3CRG	p. 26, Apr 74
Ten-Tec RX10 communicators receiver W1NLB	p. 69, Jul 76
T150A frequency stability (HN) WB2MCP	p. 63, Jun 71
Yaesu sideband switching (HN) W2MUU	p. 70, Apr 69
Yaesu spurious signals (HN) K6KA	p. 56, Dec 73
Units affected (letter) Yaesu FT101 clarifier (letter) K1NUN	p. 69, Dec 71
	p. 67, Oct 73
	p. 55, Nov 75

construction techniques

AC line cords (letter) W6EG	p. 80, Dec 71
A dab of paint, a drop of wax (HN) VE3BUE	p. 78, Aug 68
Aluminum's new face W4BRS	p. 60, May 68
Aluminum tubing, clamping (HN) WA9HUV	p. 78, May 75
Antenna insulators, homemade (HN) W7ZC	p. 70, May 73

APC trimmer, adding shaft to (HN) W1ETT	p. 68, Jul 63
Blower-to-chassis adapter (HN) K6JYO	p. 73, Feb 71
BNC connectors, mounting (HN) W9KXJ	p. 70, Jan 70
Capacitors, oil-filled (HN) W2OLU	p. 66, Dec 72
Center insulator, dipole WA1ABP	p. 69, May 69
Circuit boards with terminal inserts (HN) W3KBM	p. 61, Nov 75
Coaxial cable connectors (HN) WA1ABP	p. 71, Mar 69
Coax connectors, repairing broken (HN) W0HKF	p. 66, Jun 70
Coax relay coils, another use (HN) K0VQY	p. 72, Aug 69
Cold galvanizing compound (HN) W5UNF	p. 70, Sep 72
Color coding parts (HN) WA7BPO	p. 58, Feb 72
Component marking (HN) W1JE	p. 66, Nov 71
Deburring holes (HN) W2DXH	p. 75, Jul 68
Drill guide (HN) W5BVF	p. 68, Oct 71
Drilling aluminum (HN) W6IL	p. 67, Sep 75
Enclosures, homebrew custom W4YUU	p. 50, Jul 74
Exploding diodes (HN) VE3FEZ	p. 57, Dec 73
Ferrite beads W5JJ	p. 48, Oct 70
Files, cleaning (HN) Walton	p. 66, Jun 74
Ferrite beads, how to use K1ORV	p. 34, Mar 73
Filter chokes, unmarked W0KMF	p. 60, Nov 68
Grommet shock mount (HN) VE3BUE	p. 77, Oct 68
Grounding (HN) W9KXJ	p. 67, Jun 69
Heat sinks, homemade (HN) WA0W0Z	p. 69, Sep 70
Homebrew art W0PEM	p. 56, Jun 69
Hot etching (HN) K8EKG	p. 66, Jan 73
Hot wire stripper (HN) W8DWT	p. 67, Nov 71
IC holders (HN) W3HUC	p. 80, Aug 76
IC lead former (HN) W5ICV	p. 67, Jan 74
Inductance, toroidal coil (HN) W3WLX	p. 26, Sep 75
Industrial cartridge fuses, using (HN) VE3BUE	p. 76, Sep 68
Magnetic fields and the 7360 (HN) W7DI	p. 66, Sep 73
Metric conversions for screw and wire sizes W1D7Y	p. 67, Sep 75
Miniature sockets (HN) Lawyer	p. 84, Dec 69
Minibox, cutting down to size (HN) W2OUX	p. 57, Mar 74
Mobile installation, putting together W0FCH	p. 36, Aug 69
Mobile mount bracket (HN) W4NJF	p. 70, Feb 70
Modular converter, 144-MHz W6UOV	p. 64, Oct 70
Neutralizing tip (HN) ZE6JP	p. 69, Dec 72
Noisy fans (HN) W8IUF	p. 70, Nov 72
Correction (letter) Nuistor heat sinks (HN) WA0KKC	p. 67, Oct 73
Parasitic suppressor (HN) WA9JMY	p. 57, Dec 73
Printed-circuit boards, cleaning (HN) W5BVF	p. 80, Apr 70
Printed-circuit boards, how to clean K2PMA	p. 66, Mar 71
Printed-circuit boards, how to make K4EEU	p. 56, Sep 76
Printed-circuit boards, low-cost W6CMQ	p. 58, Apr 73
Printed-circuit boards, low-cost W8YFB	p. 44, Aug 71
Printed-circuit boards, practical photofabrication of Hutchinson	p. 16, Jan 75
Printed-circuit labels (HN) WA4WDK	p. 6, Sep 71
Printed-circuit standards (HN) W6JVE	p. 76, Oct 70
Printed-circuit tool (HN) W2GZ	p. 58, Apr 74
Printed circuits without printing W4ZG	p. 74, May 73
Professional look, for that VE3GFN	p. 62, Nov 70
	p. 74, Mar 68

Punching aluminum panels (HN) W7DIM	p. 57, Jun 68
Rack and panel construction W7OE	p. 48, Jun 68
Rack construction, a new approach K1EUJ	p. 36, Mar 70
Rectifier terminal strip (HN) W5PKK	p. 80, Apr 70
Restoring panel lettering (HN) W8CL	p. 69, Jan 73
Screwdriver, adjustment (HN) WA0ZKGS	p. 66, Jan 71
Silver plating for the amateur W4KAE	p. 62, Dec 68
Small parts tray (HN) W2GA	p. 58, Jun 68
Solder dispenser, simple (HN) W2KID	p. 76, Sep 68
Soldering aluminum (HN) ZE6JP	p. 67, May 72
Soldering fluxes (HN) K3HNP	p. 57, Jun 68
Soldering tip (HN) Lawyer	p. 68, Feb 70
Soldering tip cleaner (HN) W3HUC	p. 79, Oct 76
Soldering tips WA4MTH	p. 15, May 76
Thumbwheel switch modification (HN) VE3DGX	p. 56, Mar 74
Tilt your rig (HN) WA4NED	p. 58, Jun 68
Toroids, plug-in (HN) K8EEG	p. 60, Jan 72
Transfer letters (HN) WA2TGL	p. 78, Oct 76
Transformers, repairing W6NIF	p. 66, Mar 69
Trimmers (HN) W5LHG	p. 76, Nov 69
Uhf coax connectors (HN) W0LCP	p. 70, Sep 72
Uhf hardware (HN) W6CMQ	p. 76, Oct 70
Underwriter's knot (HN) W1D7Y	p. 69, May 69
Vectorbord tool (HN) WA1KWJ	p. 70, Apr 72
Volume controls, noisy, temporary fix (HN) W9JUW	p. 62, Aug 74
Watercooling the 2C39 K6MYC	p. 30, Jun 69
Wiring and grounding W1EZT	p. 44, Jun 69
Workbench, electronic W1EZT	p. 50, Oct 70

features and fiction

Alarm, burglar-proof (HN) Eisenbrandt	p. 56, Dec 75
Binding 1970 issues of ham radio (HN) W1DHZ	p. 72, Feb 71
Brass pounding on wheels K6QD	p. 58, Mar 75
Dynistor, the W6GXN	p. 49, Apr 68
Catalina wireless, 1902 W6BLZ	p. 32, Apr 70
Early wireless stations W6BLZ	p. 64, Oct 68
Electronic bugging K2ZSQ	p. 70, Jun 68
Fire protection in the ham shack Darr	p. 54, Jan 71
First wireless in Alaska W6BLZ	p. 48, Apr 73
Ham Radio sweepstakes winners, 1972 W1NLB	p. 58, Jul 72
Ham Radio sweepstakes winners, 1973 W1NLB	p. 68, Jul 73
Ham Radio sweepstakes winners, 1975 W1NLB	p. 54, Jul 75
How to be DX W4NXD	p. 58, Aug 68
Nostalgia with a vengeance W6HDM	p. 28, Apr 72
Photographic illustrations WA4GNW	p. 72, Dec 69
QSL return, statistics on WB6IUH	p. 50, Dec 68
Reminiscences of old-time radio K4NW	p. 40, Apr 71
Secret society, the W4NXD	p. 82, May 68
Ten commandments for technicians Foster	p. 58, Oct 76
Use your old magazines Foster	p. 52, Jan 70
What is it? WA1ABP	p. 84, May 68
Wireless Point Loma W6BLZ	p. 54, Apr 69
1929-1941, the Golden years of amateur radio W6SAI	p. 34, Apr 76
1979 world administrative radio conference W6APW	p. 48, Feb 76

fm and repeaters

Amateur vhf fm operation p. 36, Jun 68
 W6AYZ

Antenna and control-link calculations for repeater licensing p. 58, Nov 73
 W7PUG
 Short circuit p. 59, Dec 73

Antennas, simple, for two-meter fm WA3NFW p. 30, May 73

Antenna, two-meter fm (HN) WB6KYE p. 64, May 71

Antenna, $\frac{1}{2}$ -wavelength, two-meter K6KLO p. 40, Jul 74

Antenna, $\frac{1}{2}$ wavelength two-meter, build from CB mobile whips (HN) WB4WSU p. 67, Jun 74

Audio-amplifier and squelch unit W6AJF p. 36, Aug 68

Automatically controlled access to open repeaters W8GRG p. 22, Mar 74

Autopatch system for vhf fm repeaters W8GRG p. 32, Jul 74

Base station, two-meter fm W9JTQ p. 22, Aug 73

Carrier-operated relay KØPHF, WAØUZO p. 58, Nov 72

Carrier-operated relay and call monitor VE4RE p. 22, Jun 71

Cavity filter, 144-MHz W1SNN p. 22, Dec 73

Channel scanner W2FPP p. 29, Aug 71

Channels, three from two (HN) VE7ABK p. 68, Jun 71

Charger, fet-controlled for nicad batteries WAØJYK p. 46, Aug 75

Collinear antenna for two meters, nine-element W6RJO p. 12, May 72

Collinear array for two meters, 4-element WB6KGF p. 6, May 71

Continuous tuning for fm converters (HN) W1DHz p. 54, Dec 70

Control head, customizing VE7ABK p. 28, Apr 71

Detectors, fm, survey of W6GXN p. 22, Jun 76

Deviation measurement (letter) K5ZBA p. 68, May 71

Deviation measurements W3FQJ p. 52, Feb 72

Deviation meter (HN) VE7ABK p. 58, Dec 70

Digital touch-tone encoder for vhf fm W7FBB p. 28, Apr 75

Discriminator, quartz crystal WAØJYK p. 67, Oct 75

Distortion in fm systems W5JJ p. 26, Aug 69

Encoder, combined digital and burst K8AUH p. 48, Aug 69

European vhf-fm repeaters SM4GL p. 80, Sep 76

Filter, 455-kHz for fm WAØJYK p. 22, Mar 72

Fm demodulator, TTL W3FQJ p. 66, Nov 72

Fm receiver frequency control (letter) W3AFN p. 65, Apr 71

Fm techniques and practices for vhf amateurs W6SAI p. 8, Sep 69
 Short circuit p. 79, Jun 70

Fm transmitter, solid-state two-meter W6AJF p. 14, Jul 71

Fm transmitter, Sonobaby, 2 meter WAØUZO p. 8, Oct 71
 Short Circuit p. 96, Dec 71
 Crystal deck for Sonobaby p. 26, Oct 72

Frequency meter, two-meter fm W4JAZ p. 40, Jan 71
 Short circuit p. 72, Apr 71

Frequency synthesizer, inexpensive all-channel, for two-meter fm WØOA p. 50, Aug 73
 Correction (letter) p. 65, Jun 74

Frequency-synthesizer, one-crystal for two-meter fm WØMV p. 30, Sep 73

Frequency synthesizer, for two-meter fm WB4FPK p. 34, Jul 73

Identifier, programmable repeater W6AYZ p. 18, Apr 69
 Short circuit p. 76, Jul 69

I-f system, multimode WA2IKL p. 39, Sep 71

Indicator, sensitive rf WB9DNI p. 38, Apr 73

Interface problems, fm equipment (HN) W9DPY p. 58, Jun 75

Interference, scanning receiver (HN) K2YAH p. 70, Sep 72

Logic oscillator for multi-channel crystal control W1SNN p. 46, Jun 73

Magnet mount antenna, portable WB2YYU p. 67, May 76

Mobile antenna, magnet-mount W1HC1 p. 54, Sep 75

Mobile operation with the Touch-Tone pad WØLPQ p. 58, Aug 72
 Correction p. 90, Dec 72
 Modification (letter) p. 72, Apr 73

Mobile rig, protecting from theft (C&T) W1DTY p. 42, Apr 76

Modulation standards for vhf fm W6TEE p. 16, Jun 70

Monitor receivers, two-meter fm WB5EMI p. 34, Apr 74

Motorola channel elements WB4NEX p. 32, Dec 72

Motorola fm receiver mods (HN) VE4RE p. 60, Aug 71

Motorola P-33 series, improving the WB2AEB p. 34, Feb 71

Motorola voice commander, improving WØDDU p. 70, Oct 70

Motrac Receivers (letter) K5ZBA p. 69, Jul 71

Narrow-band fm system, using ICs in W6AJF p. 30, Oct 68

Phase-locked loop, tunable, 28 and 50 MHz W1KNI p. 40, Jan 73

Phase modulation principles and techniques VE2BEN p. 28, Jul 75
 Correction p. 59, Dec 75

Power amplifier, rf 220-MHz fm K7JUE p. 6, Sep 73

Power amplifier, rf, 144 MHz Hatchett p. 6, Dec 73

Power amplifier, rf, 144-MHz fm W4CGC p. 6, Apr 73

Power amplifier, two-meter fm, 10-watt W1DTY p. 67, Jan 74

Power supply, regulated ac for mobile fm equipment WA8TMP p. 28, Jun 73

Preamplifier, two-meter WA2GCF p. 25, Mar 72

Preamplifier, two meter W8BBB p. 36, Jun 74

Private-line, adding to Heath HW-202 W8AWA p. 53, Jun 74

Push-to-talk for Styleline telephones W1DRP p. 18, Dec 71

Receiver alignment techniques, vhf fm K4IPV p. 14, Aug 75

Receiver for six and two meters, multichannel fm W1SNN p. 54, Feb 74

Receiver for two meter, fm W9SEK p. 22, Sep 70
 Short circuit p. 72, Apr 71

Receiver isolation, fm repeater (HN) W1DTY p. 54, Dec 70

Receiver, modular fm communications K8AUH p. 32, Jun 69
 Correction p. 71, Jan 70

Receiver, modular, for two-meter fm WA2GBF p. 42, Feb 72
 Added notes p. 73, Jul 72

Receiver performance, comparison of VE7ABK p. 68, Aug 72

Receiver performance of vacuum-tube vhf-fm equipment, how to improve W6GGV p. 52, Oct 76

Receiver, tunable vhf fm K8AUH p. 34, Nov 71

Receiver, vhf fm WA2GCF p. 6, Nov 72

Receiver, vhf fm WA2GCF p. 8, Nov 75

Receiver, vhf fm (letter) K8IHQ p. 76, May 73

Relay, operational-amplifier, for Motorola receivers W6GDO p. 16, Jul 73

Repeater control with simple timers W2FPP p. 46, Sep 72
 Correction p. 91, Dec 72

Repeater decoder, multi-function WA6TBC p. 24, Jan 73

Repeater installation W2FPP p. 24, Jun 73

Repeater linking, carrier-operated relay for KØPHF p. 57, Jul 76

Repeater problems VE7ABK p. 38, Mar 71

Repeater, receiving system degradation K5ZBA p. 36, May 69

Repeater transmitter, improving W6GDO p. 24, Oct 69

Repeaters, single-frequency fm W2FPP p. 40, Nov 73

Reset timer, automatic W5ZHV p. 54, Oct 74

Satellite receivers for repeaters WA4YAK p. 64, Oct 75

Scanner, two-channel, for repeater monitoring W8GRG p. 48, Oct 76

Scanner, vhf receiver K2LZG p. 22, Feb 73

Scanning receiver, improved for vhf fm WA2GCF p. 26, Nov 74

Scanning receiver modifications, vhf fm WA5WOU p. 60, Feb 74

Scanning receivers for two-meter fm K4IPV p. 28, Aug 74

Sequential encoder, mobile fm W3JJU p. 34, Sep 71

Sequential switching for Touch-Tone repeater control W8GRG p. 22, Jun 71

Single-frequency conversion, vhf/uhf W3FQJ p. 62, Apr 75

S-meter for Clegg 27B (HN) WA2YUD p. 61, Nov 74

Squelch-audio amplifier for fm receivers WB4WSU p. 68, Sep 74

Squelch circuit, another (HN) WB4WSU p. 78, Oct 76

Squelch circuits for transistor radios WB4WSU p. 36, Dec 75

Synthesized two-meter fm transceiver W1CMR, K11JZ p. 10, Jan 76
 Letter, W5GQV p. 78, Sep 76

Telephone controller, automatic for your repeater KØPHF, WAØUZO p. 44, Nov 74

Telephone controller for remote repeater operation KØPHF, WAØUZO p. 50, Jan 76

Test set for Motorola radios KØBKD p. 12, Nov 73
 Short circuit p. 58, Dec 73
 Added note (letter) p. 64, Jun 74

Time-out warning indicator for fm repeater users K3NEZ p. 62, Jun 76

Timer, simple (HN) W3CIX p. 58, Mar 73

Tone-burst generator (HN) K4COF p. 58, Mar 73

Tone-burst keyer for fm repeaters W8GRG p. 36, Jan 72

Tone encoder and secondary frequency oscillator (HN) K8AUH p. 66, Jun 69

Tone encoder, universal for vhf fm W6FUB p. 17, Jul 75
 Correction p. 58, Dec 75

Touch-tone circuit, mobile K7QWR p. 50, Mar 73

Touch-tone decoder, multi-function KØPHF, WAØUZO p. 14, Oct 73

Touch-tone decoder, three-digit W6AYZ p. 37, Dec 74
 Circuit board for p. 62, Sep 75

Touch-tone, hand-held K7YAM p. 44, Sep 75

Touch-tone handset, converting slim-line K2YAH p. 23, Jun 75

Transceiver for two-meter fm, compact W6AOI p. 36, Jan 74

Transmitter for two meters, phase-modulated W6AJF p. 18, Feb 70

Transmitter, two-meter fm W9SEK p. 6, Apr 72

Tunable receiver modification for vhf fm WB6VKY p. 40, Oct 74

Vertical antennas, truth about $\frac{1}{4}$ -wavelength KØDOK p. 48, May 74
 Added note (letter) p. 54, Jan 75

Weather monitor receiver, retune to two-meter fm (HN) W3WTO p. 56, Jan 75

Whip, 5/8-wave, 144 MHz (HN) WE3DDD p. 70, Apr 73

144-MHz digital synthesizers, readout display WB4TZE p. 47, Jul 76

144-MHz fm exciter, high performance WA2GCF p. 10, Aug 76

144-MHz vertical mobile antennas, $\frac{1}{4}$ and $\frac{1}{2}$ wavelength, test data on W2LTJ, W2CQH p. 46, May 76

144-MHz, $\frac{1}{4}$ -wavelength vertical antenna W1RHN p. 50, Mar 76

144-MHz, $\frac{1}{2}$ -wavelength, vertical antenna for mobile K4LPQ p. 42, May 76

220 MHz frequency synthesizer W6GXN p. 8, Dec 74

450-MHz preamplifier and converter WA2GCF p. 40, Jul 75

integrated circuits

Amateur uses of the MC1530 IC W2EEY p. 42, May 68

Amplifiers, broadband IC W6GXN p. 36, Jun 73

Applications, potpourri of IC W1DTY, Thorpe p. 8, May 69

Audio-power ICs W3FQJ p. 64, Jan 76

Balanced modulator, an integrated-circuit K7QWR p. 6, Sep 70

Cmos logic circuits W3FQJ p. 50, Jun 75

Counter gating sources K6KA p. 48, Nov 70

ORLANDOHAMCATION 77 ORLANDOHAMCATION 77
Presents
The SOUTHEASTERN
ARRL CONVENTION
and
The Greatest ORLANDO HAMFEST ever!!
AT ORLANDO FLORIDA'S SHERATON'S TWIN
TOWERS HOTEL & CONVENTION COMPLEX
FEBRUARY 12 & 13 1977 *
ADVANCE REGISTRATION \$3, AT DOOR \$4
SWAPFEST TABLES \$5 PER DAY
 For Hamfest information write; HAMFEST SECRETARY, GEORGIA
 DENMAN K4ZXS, 405 ENKA WAY, ORLANDO FLA. 32811.

FOR HOTEL RESERVATIONS AND INFORMATION WRITE TO:
 SHERATON TWIN TOWERS, HOTEL, 5780 MAJOR BLVD. ORLANDO
 FLORIDA 32805. Rooms single \$28, double \$36 per day.

*SWAPFEST TABLES WILL BE AVAILABLE FRIDAY FEB. 11 AT 6PM
 SWAP AREA WILL BE OPEN FRIDAY NIGHT, No additional charge for
 Friday night required.

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION
 (Required by 39 U.S.C. 3685)

1. TITLE OF PUBLICATION
HAM RADIO Magazine

2. NUMBER OF ISSUES
 Monthly

3. DATE OF THIS STATEMENT
 October 1, 1976

4. LOCATION OF HEADQUARTERS OR GENERAL BUSINESS OFFICES OF THE PUBLISHERS
 Main Street, Greenville, NH 03048

5. LOCATION OF THE HEADQUARTERS OF THE PUBLISHERS AT THE TIME OF THIS STATEMENT
 Main Street, Greenville, NH 03048

6. FULL NAME AND ADDRESS OF THE PUBLISHERS
 T. H. Tenney, Jr., Main Street, Greenville, NH 03048

7. FULL NAME AND ADDRESS OF THE EDITOR
 J. R. Fisk, Main Street, Greenville, NH 03048

8. FULL NAME AND ADDRESS OF THE BUSINESS MANAGER OR OWNER
 T. H. Tenney, Jr., Main Street, Greenville, NH 03048

9. ESTABLISHED BY
 Communications Technology, Inc.
 T. H. Tenney, Jr.

10. ESTABLISHED AT
 Main Street, Greenville, NH 03048

11. ESTABLISHED IN
 Main Street, Greenville, NH 03048

12. ESTABLISHED FOR
 Main Street, Greenville, NH 03048

13. ESTABLISHED UNDER
 Main Street, Greenville, NH 03048

14. ESTABLISHED AS
 Main Street, Greenville, NH 03048

15. ESTABLISHED AS
 Main Street, Greenville, NH 03048

16. ESTABLISHED AS
 Main Street, Greenville, NH 03048

100. ESTABLISHED AS
 Main Street, Greenville, NH 03048

ORLANDOHAMCATION 77 ORLANDOHAMCATION 77 ORLANDOHAMCATION 77

TRAGIC WASTE OF RF
 could be your fate as precious watts zig-zag round the world to shower just a little — or little or none — on that hoped for DX station. BUT WE HAVE AN ALTERNATIVE — THE JOYSTICK VFA (Variable freq. ant.), which gives low angle, omnidirectional, harmonic free radiation on all bands 160 thru 10 (+ MARS and receive on all BC & SW). Stalwarts W6TYP and G4DJY achieved notable results in contests — just to mention two of the many who have sent glowing reports of the VFA in use, often in poor QTH and/or under QRP. Receiving Only

SYSTEM 'A' \$69.90
 250W P.E.P. &/or Receiving Only

SYSTEM 'J' \$91.33
 500W P.E.P. &/or Improved Q Factor Receive

Air Mail cost included
 (each system 3 sections easily assembled to make unit 7" 6" long, Matching ATU.) Not only will you save space but you will save \$\$\$ at present low exch. rate and by buying direct UK manuf. Rush your order — Mastercharge or check, or ask for brochure.

PARTRIDGE (HR) ELECTRONICS LTD.
 BROADSTAIRS, KENT, ENGLAND
 G3CED TEL. THANET 62525 G3VFA

NEW! \$24.95
LOGIC PROBE
 from Logic Systems Inc.
Look at This!

- 2 meg input Z
- Input protection
- Automatic memory
- Use with TTL/DTL/MOS/CMOS
- Detects 16 nsec pulses
- Assembled and tested

Check or M.O.
 L.S.I., Box 7197, Univ. Sta., Provo, Utah 84602

NEW ELECTRONIC PARTS

Resistors Meters LED Displays Fuses
 Capacitors Switches Proto Boards IC sockets
 Diodes Dozy Boxes Mod U-Line Test Clips
 Trim pots Transistors Hardware And much more

SASE brings our new parts catalog.

NuData Electronics
 104 N. EMERSON ST. MOUNT PROSPECT, ILLINOIS 60056

SST T-1 RANDOM WIRE ANTENNA TUNER

All band operation (160-10 meters) with most any random length wire 200 watt output power capability ideal for portable or home operation. Tuned inductor for small size 2" x 4" 1/8" x 2 3/8". Built-in meter tune-up indicator. SO-239 coax connector. Guaranteed for 1 yr., 10 day trial. Compact — easy to use — only \$29.95 postpaid (Add Sales Tax in Calif.) (213) 376-5887

SST ELECTRONICS, P.O. BOX 1, LAWDALE, CA 90260

NEW 60/600MHZ PORTABLE COUNTER

- Large .3" 7-segment LED display
- CMOS 101 counter/pullups
- Small—ideal for field use
- Portable battery operated
- 400 mA NiCd battery & charger
- Internal crystal time base
- Inputs overload protection
- 1/2 Hz resolution on low range
- 1 meg. input-sensitivity 50 mv
- 50 ohm input-impedance 100 mv
- Size: 2 7/8" x 2 7/8" x 1 1/2"
- A 600 Mhz FREQUENCY COUNTER THAT CAN GO ANYWHERE — NOT A KIT

ONLY \$299

Dealer Inquiries Invited
 CBS ENTERPRISE P.O. BOX 1355 COOBA BEACH FLA. 32931

SYNTHESIZERS

We have the worlds largest selection of synthesizers for receivers, transmitters and transceivers. For complete details see our 1/3 page ad in the April 1976 issue of this magazine or call or write for additional information. Phone orders accepted between 9 AM and 4 PM EDT. (212) 468-2720

VANGUARD LABS
 196-23 JAMAICA AVENUE
 HOLLIS, N. Y. 11423

New! Hi Sensitivity!
500 MHz PRESCALER
 Model PS-500



- Extend your frequency counter to 500 MHz.
- Switch Selectable division ratios of 10 or 100.
- 75 mV rms sensitivity @ 450 MHz.
- Requires 5 Vdc 160 mA (available from your counter).
- Plugs directly onto your counter input conn.
- Order APS-5 AC adapter for 110v, only \$12.95.

PS-500 only \$59.95 ppd.
 send check or m.o. to

Mini Labs INDUSTRIES
 P.O. Box 26276C
 Phoenix, AZ 85068

1976 ham radio
Bigger & Better with MORE for everyone

Counter reset generator (HN)	
W3KBM	p. 68, Jan 73
C L logic circuit	
W1D7Y	p. 4, Mar 75
Digital counters (letter)	
W1GGN	p. 76, May 73
Digital ICs, part I	
W3FQJ	p. 41, Mar 72
Digital ICs, part II	
W3FQJ	p. 58, Apr 72
Correction	p. 66, Nov 72
Digital mixers	
WB81FM	p. 42, Dec 73
Digital multivibrators	
W3FQJ	p. 42, Jun 72
Digital oscillators and dividers	
W3FQJ	p. 62, Aug 72
Digital readout station accessory, part I	
K6KA	p. 6, Feb 72
Digital station accessory, part II	
K6KA	p. 50, Mar 72
Digital station accessory, part III	
K6KA	p. 36, Apr 72
Divide-by-n counters, high-speed	
W100P	p. 36, Mar 76
Electronic counter dials, IC	
K6KA	p. 44, Sep 70
Electronic keyer, cosmos IC	
WB2DFA	p. 6, Jun 74
Short circuit	p. 62, Dec 74
Emitter-coupled logic	
W3FQJ	p. 62, Sep 72
Flip-flops	
W3FQJ	p. 60, Jul 72
Flop-flip, using (HN)	
W3KBM	p. 60, Feb 72
Function generator, IC	
W1D7Y	p. 40, Aug 71
Function generator, IC	
K4DHC	p. 22, Jun 74
IC power (HN)	
W3KBM	p. 68, Apr 72
IC-regulated power supply for ICs	
W6GXN	p. 28, Mar 68
IC tester, TTL	
WA4LCO	p. 66, Aug 76
Integrated circuits, part I	
W3FQJ	p. 40, Jun 71
Integrated circuits, part II	
W3FQJ	p. 58, Jul 71
Integrated circuits, part III	
W3FQJ	p. 50, Aug 71
I L logic circuits	
W1D7Y	p. 4, Nov 75
Logic families, IC	
W6GXN	p. 26, Jan 74
Logic monitor (HN)	
WA5SAF	p. 70, Apr 72
Correction	p. 91, Dec 72
Logic test probe	
VE6RF	p. 53, Dec 73
Logic test probe (HN)	
Rossman	p. 56, Feb 73
Short circuit	p. 58, Dec 73
Low-cost linear ICs	
WA7KRE	p. 20, Oct 69
Missent ID	
K6KA	p. 25, Apr 76
Modular modules	
W9SEK	p. 63, Aug 70
Motorola MC1530 IC, amateur uses for	
W2EY	p. 42, May 68
Multi-function integrated circuits	
W3FQJ	p. 46, Oct 72
National LM373, using in ssb transceiver	
W5BAA	p. 32, Nov 73
Op amp (741) circuit design	
WA5SNZ	p. 26, Apr 76
Operational amplifiers	
WB2EGZ	p. 6, Nov 69
Phase-locked loops, IC	
W3FQJ	p. 54, Sep 71
Phase-locked loops, IC, experiments with	
W3FQJ	p. 58, Oct 71
Plessey SL600-series ICs, how to use	
G8FNT	p. 26, Feb 73
Removing ICs (HN)	
W6NIF	p. 71, Aug 70
Seven-segment readouts, multiplexed	
W5NPD	p. 37, Jul 75
Ssb detector, IC (HN)	
K4ODS	p. 67, Dec 72
Correction (letter)	p. 72, Apr 73
Ssb equipment, using TTL ICs in	
G4ADJ	p. 18, Nov 75
Surplus ICs (HN)	
W4AYV	p. 68, Jul 70
Sync generator, IC, for ATV	
W2KGI	p. 34, Jul 75
Transceiver, 9-MHz ssb, IC	
G3ZVC	p. 34, Aug 74
Circuit change (letter)	p. 62, Sep 75
U/ART, how it works	
Titus	p. 58, Feb 76
Using ICs in a nbfm system	
W6AJF	p. 30, Oct 68
Using ICs with single-polarity power supplies	
W2EY	p. 35, Sep 69

Using integrated circuits (HN)	
W9KXJ	p. 69, May 69
Voltage regulators, IC	
W7FLC	p. 22, Oct 70
Voltage-regulator ICs, adjustable	
WB9KEY	p. 36, Aug 75
Voltage-regulator ICs, three-terminal	
WB5EM1	p. 26, Dec 73
Added note (letter)	p. 73, Sep 74
Vtvm, convert to an IC voltmeter	
K6VCI	p. 42, Dec 74

keying and control

Accu-Mill, keyboard interface for the Accu-Keyer	
WN9OVY	p. 26, Sep 76
ASCII-to-Morse code translator	
Morley, Sharon	p. 41, Dec 76
Automatic beeper for station control	
WAGURN	p. 38, Sep 76
Break-in circuit, CW	
W8SYK	p. 40, Jan 72
Break-in control system, IC (HN)	
W9ZTK	p. 68, Sep 70
Bug, solid-state	
K2FV	p. 50, Jun 73
Carrier-operated relay	
KØPHF, WAØUZO	p. 58, Nov 72
Cmos keying circuits (HN)	
WB2DFA	p. 57, Jan 75
Contest keyer (HN)	
K2UBC	p. 79, Apr 70
Contest keyer, programmable	
W7BBX	p. 10, Apr 76
CW reception, enhancing through a simulated-stereo technique	
WA1MKP	p. 61, Oct 74
CW regenerator for interference-free communications	
Leward, WB2EAX	p. 54, Apr 74
CW sidetone (C&T)	
W1D7Y	p. 51, Jun 76
Differential keying circuit	
W4IYB	p. 60, Aug 76
Electronic hand keyer	
K5TCK	p. 36, Jun 71
Electronic keyer, cosmos IC	
WB2DFA	p. 6, Jun 74
Short circuit	p. 62, Dec 74
Electronic keyer, IC	
VE7BFB	p. 32, Nov 69
Electronic keyer notes (HN)	
ZL1BN	p. 74, Dec 71
Electronic keyer package, compact	
W4ATE	p. 50, Nov 73
Electronic keyer with random-access memory	
WB9FHC	p. 6, Oct 73
Corrections (letter)	p. 58, Dec 74
	p. 57, Jun 75
	p. 62, Mar 75
Increased flexibility (HN)	
Electronic keyer, 8043 IC	
W6GXN	p. 8, Apr 75
Electronic keyers, simple IC	
WA5TRS	p. 38, Mar 73
Grid-block keying, simple (HN)	
WA4DHU	p. 78, Apr 70
Improving transmitter keying	
K6KA	p. 44, Jun 76
Key and vox clicks (HN)	
K6KA	p. 74, Aug 72
Keyboard electronic keyer, the code mill	
W6CAB	p. 38, Nov 74
Keying, paddle, Siamese	
WA5KPG	p. 45, Jan 75
Keyer modification (HN)	
W9KNI	p. 80, Aug 76
Keyer mods, micro-TO	
DJ9RP	p. 68, Jul 76
Keying the Heath HG-10B vfo (HN)	
K4BRR	p. 67, Sep 70
Latch circuit, dc	
WØLPQ	p. 42, Aug 75
Correction	p. 58, Dec 75
Memo-key	
WA7SCB	p. 58, Jun 72
Memory accessory, programmable for electronic keyers	
WA9LUD	p. 24, Aug 75
Mini-paddle	
K6RIL	p. 46, Feb 69
Morse generator, keyboard	
W7CUU	p. 36, Apr 75
Morse sounder, radio controlled (HN)	
K6QEQ	p. 66, Oct 71
Oscillators, electronic keyer	
WA6JNJ	p. 44, Jun 70
Paddle, electronic keyer (HN)	
KL7EVD	p. 68, Sep 72
Paddle, homebrew keyer	
W3NK	p. 43, May 69
Push-to-talk for Styleline telephones	
W1DRP	p. 18, Dec 71
RAM keyer update	
K3NEZ	p. 60, Jan 76
Relay activator (HN)	
K6KA	p. 62, Sep 71

Relays, surplus (HN)	
W2OLU	p. 70, Jul 70
Relay, transistor replaces (HN)	
W3NK	p. 72, Jan 70
Relays, undervoltage (HN)	
W2OLU	p. 64, Mar 71
Remote keying your transmitter (HN)	
WA3HOU	p. 74, Oct 69
Reset timer, automatic	
W5ZHV	p. 54, Oct 74
Sequential switching (HN)	
W5OSF	p. 63, Oct 72
Solenoid rotary switches	
W2EY	p. 36, Apr 68
Station control center	
W7OE	p. 26, Apr 68
Step-start circuit, high-voltage (HN)	
W6VFR	p. 64, Sep 71
Suppression networks, arc (HN)	
WASEKA	p. 70, Jul 73
Time base, calibrated electronic keyer	
W1PLJ	p. 39, Aug 75
Timer, ten-minute (HN)	
DJ9RP	p. 66, Nov 76
Transistor switching for electronic keyers (HN)	
W3QBO	p. 66, Jun 74
Transmit/receive switch PIN diode	
W9KHC	p. 10, May 76
Transmitter switching, solid-state	
W2EY	p. 44, Jun 68
Typewriter-type electronic keys, further automation for	
W6PRO	p. 26, Mar 70
Vox and mox systems for ssb	
Belt	p. 24, Oct 68
Vox, IC	
W2EY	p. 50, Mar 69
Vox keying (HN)	
VE7IG	p. 83, Dec 69
Vox, versatile	
W9KIT	p. 50, Jul 71
Short circuit	p. 96, Dec 71

measurements and test equipment

Absorption measurements, using your signal generator for	
W2OUX	p. 79, Oct 76
Ac current monitor (letter)	
WB5MAP	p. 61, Mar 75
Ac power-line monitor	
W2OLU	p. 46, Aug 71
AFSK generator, crystal-controlled	
K7BVT	p. 13, Jul 72
AFSK generator, phase-locked loop	
K7ZOF	p. 27, Mar 73
Amateur frequency measurements	
K6KA	p. 53, Oct 68
A-m modulation monitor, vhf (HN)	
K7UNL	p. 67, Jul 71
Antenna gain, measuring	
K6JYO	p. 26, Jul 69
Antenna matcher	
W4SD	p. 24, Jun 71
Antenna and transmission line measurement techniques	
W4OQ	p. 36, May 74
Base step generator	
WB4YDZ	p. 44, Jul 76
Beta master, the	
K8ERV	p. 18, Aug 68
Bridge for antenna measurements, simple	
W2CTK	p. 34, Sep 70
Bridge, noise, for impedance measurements	
YA1GJM	p. 62, Jan 73
Added notes	p. 66, May 74; p. 60, Mar 75
Bridge, rf noise	
WB2EGZ	p. 18, Dec 70
Calibrating ac scales on the vtvm, icvm and fet voltmeter	
W7KQ	p. 48, Sep 76
Calibrators and counters	
K6KA	p. 41, Nov 68
Calibrator, plug-in IC	
K6KA	p. 22, Mar 69
Capacitance meter, digital	
K4DHC	p. 20, Feb 74
Capacitance meter, direct-reading	
ZL2AUE	p. 46, Apr 70
Capacitance meter, direct-reading	
W6MUR	p. 48, Aug 72
Short circuit	p. 64, Mar 74
Capacitance meter, direct-reading	
WA5SNZ	p. 32, Apr 75
Added note	p. 31, Oct 75
Capacitance meter, direct reading, for electrolytics	
W9DJZ	p. 14, Oct 71
Coaxial cable, checking (letter)	
W2OLU	p. 68, May 71
Coaxial-line loss, measuring with a reflectometer	
W2VCI	p. 50, May 72

Converter, mosfet, for receiver instrumentation WA9ZMT	p. 62, Jan 71	Harmonic generator (HN) W5GDQ	p. 76, Oct 70	Resistance standard, simple (HN) W2OLU	p. 65, Mar 71
Counter, compact frequency K4EEU	p. 16, Jul 70	I-f alignment generator 455-kHz WASSNZ	p. 50, Feb 74	Resistor decades, versatile W4ATE	p. 66, Jul 71
Short circuit	p. 72, Dec 70	I-f sweep generator K4DHC	p. 10, Sep 73	Rf current probe (HN) W6HPH	p. 76, Oct 68
Counter, digital frequency K4EEU	p. 8, Dec 68	Impedance bridge (HN) W6KZK	p. 67, Feb 70	Rf detector, sensitive WB9DNI	p. 38, Apr 73
Counter gating sources K6KA	p. 48, Nov 70	Impedance bridge, low-cost RX W8YFB	p. 6, May 73	Rf generator clip W1DTY	p. 58, Mar 68
Counter readouts, switching (HN) K6KA	p. 66, Jun 71	Impedance bridge, simple WA9QJP	p. 40, Apr 68	Rf power meter, low-level W5WGF	p. 58, Oct 72
Counter reset generator (HN) W3KBM	p. 68, Jan 73	Impedance, measuring with swr bridge WB4KSS	p. 46, May 75	Rf signal generator, solid-state VE5FP	p. 42, Jul 70
Counters: a solution to the readout problem WAØGOZ	p. 66, Jan 70	Impulse generator, pulse-snap diode Siegal, Turner	p. 29, Oct 72	RTTY monitor scope, solid-state WB2MPZ	p. 33, Oct 71
CRT intensifier for RTTY K4VFA	p. 18, Jul 71	Instrumentation and the ham VE3GFN	p. 28, Jul 68	RTTY signal generator W72TC	p. 23, Mar 71
Crystal checker W6GXN	p. 46, Feb 72	Intermodulation-distortion measurements on ssb transmitters W6VFR	p. 34, Sep 74	Short circuit	p. 96, Dec 71
Crystal test oscillator and signal generator K4EEU	p. 46, Mar 73	L, C, R bridge, universal W6AOI	p. 54, Apr 76	RTTY test generator (HN) W3EAG	p. 67, Jan 73
Crystal-controlled frequency markers (HN) WA4WDK	p. 64, Sep 71	Linearity meter for ssb amplifiers W4MB	p. 40, Jun 76	RTTY test generator (HN) W3EAG	p. 59, Mar 73
Cubical quad measurements W4YM	p. 42, Jan 69	Line-voltage monitor (HN) WA8VFK	p. 66, Jan 74	RX impedance bridge W2CTK	p. 34, Sep 70
Curve master, the K8ERV	p. 40, Mar 68	Current monitor mod (letter) WASSAF	p. 70, Apr 72	RX impedance bridge, low-cost W8YFB	p. 6, May 73
Decade standards, economical (HN) W4ATE	p. 66, Jun 71	Logic monitor (HN) Correction	p. 91, Dec 72	Safer suicide cord (HN) K6JYO	p. 64, Mar 71
Digital counters (letter) W1GGN	p. 76, May 73	Logic test probe VE6RF	p. 53, Dec 73	Sampling network, rf — the milli-tap W6QJW	p. 34, Jan 73
Digital readout station accessory, part I K6KA	p. 6, Feb 72	Logic test probe (HN) Rossman	p. 56, Feb 73	Signal generator, tone modulated for two and six meters WA8OIK	p. 54, Nov 69
Digital station accessory, part II K6KA	p. 50, Mar 72	Short circuit	p. 58, Dec 73	Signal generator, wide range W6GXN	p. 18, Dec 73
Digital station accessory, part III K6KA	p. 36, Apr 72	Makeshift test equipment (HN) W7FS	p. 77, Sep 68	Signal injection in ham receivers Allen	p. 72, May 68
Dipper without plug-in coils W6BLZ	p. 64, May 68	Meter amplifier, electronic WA9HUV	p. 38, Dec 76	Signal tracing in ham receivers Allen	p. 52, Apr 68
Dummy load and rf wattmeter, low-power W2OLU	p. 56, Apr 70	Meter interface, high-impedance Laughlin	p. 20, Jan 74	Slow-scan tv test generator K4EEU	p. 6, Jul 73
Dummy load low-power vhf WB9DNI	p. 40, Sep 73	Meters, testing unknown (HN) W1ONC	p. 66, Jan 71	S-meter readings (HN) W1DTY	p. 56, Jun 68
Dummy loads W4MB	p. 40, Mar 76	Microwave marker generator, 3cm band (HN) WA4WDL	p. 69, Jun 76	Spectrum analyzer, four channel W91A	p. 6, Oct 72
Dummy loads, experimental W8YFB	p. 36, Sep 68	Milliammeters, how to use W4PSJ	p. 48, Sep 75	Spectrum analyzers, understanding WASSNZ	p. 50, Jun 74
Dynamic transistor tester (HN) VE7ABK	p. 65, Oct 71	Mini-spotter frequency checker W7OE	p. 48, May 68	Ssb, signals, monitoring W6VFR	p. 35, Mar 72
Electrolytic capacitors, measurement of (HN) W2NA	p. 70, Feb 71	Monitoroscope, miniature WA3FIY	p. 34, Mar 69	Sweep generator, how to use Allen	p. 60, Apr 70
Fm deviation measurement (letter) K5ZBA	p. 68, May 71	Monitoroscope, RTTY W3CIX	p. 36, Aug 72	Sweep response curves for low-frequency i-f's Allen	p. 56, Mar 71
Fm deviation measurements W3FQJ	p. 52, Feb 72	Multi-box (HN) W3KBM	p. 68, Jul 69	Switch-off flasher (HN) Thomas	p. 64, Jul 71
Fm frequency meter, two-meter W4JAZ	p. 40, Jan 71	Multitester (HN) W1DTY	p. 63, May 71	Swr bridge WB2ZSH	p. 55, Oct 71
Short circuit	p. 72, Apr 71	Noise bridge, antenna (HN) K8EEG	p. 71, May 74	Swr bridge and power meter, integrated W6DOB	p. 40, May 70
Frequencies, counted (HN) K6KA	p. 62, Aug 74	Noise-figure measurements for vhf WB6NMT	p. 36, Jun 72	Swr bridge (HN) WA5TFK	p. 66, May 72
Frequency calibrator, general coverage W5UQS	p. 28, Dec 71	Noise figure, vhf, estimating WA9HUV	p. 42, Jun 75	Swr bridge readings (HN) W6FPO	p. 63, Aug 73
Frequency calibrator, how to design W3AEX	p. 54, Jul 71	Noise generator, 1296-MHz W3BSV	p. 46, Aug 73	Swr indicator, aural, for the visually handicapped K6HTM	p. 52, May 76
Frequency counter, 50 MHz, 6 digit WB2DFA	p. 18, Jan 76	Noise generators, using (HN) K2ZSQ	p. 79, Aug 68	Swr meter W6VSV	p. 6, Oct 70
Frequency measurement of received signals W4AAD	p. 38, Oct 73	Oscillator, audio W6GXN	p. 50, Feb 73	Swr meter, improving (HN) W5NPD	p. 68, May 76
Frequency meter, crystal controlled (HN) W5JSN	p. 71, Sep 69	Oscillator, frequency measuring W6IEL	p. 16, Apr 72	Swr meters, direct reading and expanded scale WA4WDK	p. 28, May 72
Frequency scaler, divide-by-ten K4EEU	p. 26, Aug 70	Added notes	p. 90, Dec 72	Correction	p. 90, Dec 72
Short circuit	p. 72, Apr 71	Oscillator, two-tone, for ssb testing W6GXN	p. 11, Apr 72	Time-domain reflectometry, experimenter's approach to WAØPIA	p. 22, May 71
Frequency scaler, divide-by-ten W6PBC	p. 41, Sep 72	Oscilloscope calibrator (HN) K4EEU	p. 69, Jul 69	Transconductance tester for fets W6NBI	p. 44, Sep 71
Correction	p. 90, Dec 72	Oscilloscope, putting it to work Allen	p. 64, Sep 69	Transformer shorts W6BLZ	p. 36, Jul 68
Added comments (letter)	p. 64, Nov 73	Oscilloscope, troubleshooting amateur gear with Allen	p. 52, Aug 69	Transistor and diode tester ZL2AMJ	p. 65, Nov 70
Pre-scaler, improvements for W6PBC	p. 30, Oct 73	Oscilloscope voltage calibrator W6PBC	p. 54, Aug 72	Transistor curve tracer WA9LCX	p. 52, Jul 73
Frequency scaler, uhf (11C90) WB9KEY	p. 50, Dec 75	Panoramic reception, simple W2EEY	p. 14, Oct 68	Short circuit	p. 63, Apr 74
Frequency scaler, 500-MHz W6URH	p. 32, Jun 75	Peak envelope power, how to measure W5JJ	p. 32, Nov 74	Transistor tester WA6NIL	p. 48, Jul 68
Frequency scalars, 1200-MHz WB9KEY	p. 38, Feb 75	Phase meter, rf VE2AYU, Korth	p. 28, Apr 73	Transistor tester for leakage and gain W4BRS	p. 68, May 68
Frequency-shift meter, RTTY VK3ZNV	p. 33, Jun 70	Power meter, rf K8EEG	p. 26, Oct 73	Transistor tester, shirt pocket WØMAY	p. 40, Jul 76
Frequency standard (HN) WA7JIK	p. 69, Sep 72	Precision capacitor W4BRS	p. 61, Mar 68	Transmitter tuning unit for the blind W9NTP	p. 60, Jun 71
Frequency standard, universal K4EEU	p. 40, Feb 74	Pre-scaler, vhf (HN) W6MGI	p. 57, Feb 73	Trapezoidal monitor scope VE3CUS	p. 22, Dec 69
Short circuit	p. 72, May 74	Prescaler, vhf, for digital frequency counters K4GOK	p. 32, Feb 76	Troubleshooting around fets Allen	p. 42, Oct 68
Frequency synthesizer, high-frequency K2BLA	p. 16, Oct 72	Probe, sensitive rf (HN) W5JJ	p. 61, Dec 74	Troubleshooting by resistance measurement Allen	p. 62, Nov 68
Function generator, IC W1DTY	p. 40, Aug 71	Receiver alignment Allen	p. 64, Jun 68	Troubleshooting transistor ham gear Allen	p. 64, Jul 68
Function generator, IC K4DHC	p. 22, Jun 74	Reflectometers K1YZW	p. 65, Dec 69	Turn-off timer for portable equipment W5OXD	p. 42, Sep 76
Gdo, new use for K2ZSQ	p. 48, Dec 68	Regenerative detectors and a wideband amplifier W8YFB	p. 61, Mar 70	Uhf tuner tester for tv sets (HN) Schuler	p. 73, Sep 69
Grid current measurement in grounded-grid amplifiers W6SAI	p. 64, Aug 68	Repairs, thinking your way through Allen	p. 58, Feb 71	Vacuum tubes, testing high-power (HN) W2OLU	p. 64, Mar 72
Grid-dip oscillator, solid-state conversion of W6AJZ	p. 20, Jun 70			Vhf pre-scaler, improvements for W6PBC	p. 30, Oct 73

Voltmeter, improved transistor, part I Maddever	p. 74, Apr 68
Voltmeter, transistor, part II Maddever	p. 60, Jul 68
Vom/vtvm, added uses for (HN) W7DI	p. 67, Jan 73
Vtvm modification W6HPH	p. 51, Feb 69
Vtvm, convert to an IC voltmeter K6VCI	p. 42, Dec 74
Wavemeter, indicating W6NIF	p. 26, Dec 70
Short circuit	p. 72, Apr 71
Weak-signal source, stable, variable-output K6JYO	p. 36, Sep 71
Weak-signal source, 144 and 432 MHz K6JC	p. 58, Mar 70
Weak-signal source, 432 and 1296 MHz K6RIL	p. 20, Sep 68
WWV receiver, simple regenerative WA5SNZ	p. 42, Apr 73
WWV-WVH, amateur applications for W3FQJ	p. 53, Jan 72
WWVB signal processor W9BTI	p. 28, Mar 76
Zener tester, low-voltage (HN) K3DPJ	p. 72, Nov 69

microprocessors, calculators computers and

Accumulator I/O versus memory I/O WB4HYJ, Rony, Titus	p. 64, Jun 76
Decision, how does a microcomputer make a WB4HYJ, Titus, Rony	p. 74, Aug 76
Device-select pulses, generating input/output WB4HYJ, Titus, Rony	p. 44, Apr 76
How microprocessors fit into scheme of computers and controllers WB4HYJ, Rony, Titus	p. 36, Jan 76
Input/output device, what is a? WB4HYJ, Rony, Titus	p. 50, Feb 76
Interfacing a digital multimeter with an 8080-based microcomputer WB4HYJ, Rony, Titus	p. 66, Sep 76
Interrupts, microcomputer WB4HYJ, Rony, Titus	p. 66, Dec 76
Introduction to microprocessors WB4HYJ, Rony, Titus	p. 32, Dec 75
Comments, WB4FAR	p. 63, May 76
Software UAR/T, interfacing a WB4HYJ, Rony, Titus	p. 60, Nov 76
Substitution of software for hardware WB4HYJ, Rony, Titus	p. 62, Jul 76
UAR/T, how it works Titus	p. 58, Feb 76
8080 microcomputer output instructions WB4HYJ, Rony, Titus	p. 54, Mar 76

miscellaneous technical

Alarm, wet basement (HN) W2EMF	p. 68, Apr 72
Amateur anemometer W6GXN	p. 52, Jun 68
Short circuit	p. 34, Aug 68
Antenna masts, design for pipe W3MR	p. 52, Sep 74
Added design notes (letter)	p. 75, May 75
Antennas and capture area K6MIO	p. 42, Nov 69
Bandpass filter design K4KJ	p. 36, Dec 73
Bandpass filters for 50 and 144 MHz, etched W5KHT	p. 6, Feb 71
Bandpass filters, single-pole W6HPH	p. 51, Sep 69
Basic electronic units W2DXH	p. 18, Oct 68
Batteries, selecting for portable equipment WBØAIK	p. 40, Aug 73
Bipolar-fet amplifiers W6HDM	p. 16, Feb 76
Comments, Worcester	p. 76, Sep 76
Broadband amplifier uses mospower fet Oxner	p. 32, Dec 76
Broadband amplifier, wide-range W6GXN	p. 40, Apr 74
Bypassing, rf, at uhf W6BBI	p. 50, Jan 72
Calculator, hand-held electronic, its function and use W4MB	p. 18, Aug 76
Calculator, hand-held electronic, solving problems with it W4MB	p. 34, Sep 76
Capacitors, oil-filled (HN) W2OLU	p. 66, Dec 72
Clock, 24-hour digital K4ALS	p. 51, Apr 70
Short circuit	p. 76, Sep 70

Coil-winding data, vhf and uhf K3SVC	p. 6, Apr 71
Communications receivers, designing for strong-signal performance Moore	p. 6, Feb 73
Computer-aided circuit analysis K1ORV	p. 30, Aug 70
Converting vacuum tube equipment to solid-state W2EY	p. 30, Aug 68
Converting wavelength to inches (HN) WA6SXC	p. 56, Jun 68
Current flow?, which way does W2DXH	p. 34, Jul 68
Digital clock, low-cost WA6DYW	p. 26, Feb 76
Digital mixer, introduction WB8IFM	p. 42, Dec 73
Digital readout system, simplified W6OIS	p. 42, Mar 74
Double-balanced mixers W1DTY	p. 48, Mar 68
Double-balanced modulator, broadband WA6NCT	p. 8, Mar 70
Earth currents (HN) W7OUI	p. 80, Apr 70
Effective radiated power (HN) VE7CB	p. 72, May 73
Electrical units: their derivation and history WB6EYV	p. 30, Aug 76
Ferrite beads W5JJ	p. 48, Oct 70
Ferrite beads, how to use K1ORV	p. 34, Mar 73
Fet biasing W3FQJ	p. 61, Nov 72
Filter preamplifiers for 50 and 144 MHz, etched W5KHT	p. 6, Feb 71
Filters, active for direct-conversion receivers W7ZOI	p. 12, Apr 74
Fire extinguishers (letter) W5PGG	p. 68, Jul 71
Fire protection Darr	p. 54, Jan 71
Fire protection (letter) K7QCM	p. 62, Aug 71
Fm techniques W6SAI	p. 8, Sep 69
Short circuit	p. 79, Jun 70
Freon danger (letter) WA5RTB	p. 63, May 72
Frequency multipliers W6GXN	p. 6, Aug 71
Frequency multipliers, transistor W6AJF	p. 49, Jun 70
Frequency synchronization for scatter-mode propagation K2OVS	p. 26, Sep 71
Frequency synthesis WASSKM	p. 42, Dec 67
Frequency synthesizer, high-frequency K2BLA	p. 16, Oct 72
Frequency synthesizers, how to design DJ2LR	p. 10, Jul 76
Short circuit	p. 85, Oct 76
Gamma-matching networks, how to design W7ITB	p. 46, May 73
Glass semiconductors W1EZT	p. 54, Jul 69
Graphical network solutions WINCK, W2CTK	p. 26, Dec 69
Gridded tubes, vhf-uhf effects W6UOV	p. 8, Jan 69
Grounding and wiring W1EZT	p. 44, Jun 69
Ground plow W1EZT	p. 64, May 70
Harmonic output, how to predict Utne	p. 34, Nov 74
Heatsink problems, how to solve WA5SNZ	p. 46, Jan 74
Hybrids and couplers, hf W2CTK	p. 57, Jul 70
Short circuit	p. 72, Dec 70
Impedance-matching systems, designing W7CSD	p. 58, Jul 73
Inductors, how to use ferrite and powdered-iron for W6GXN	p. 15, Apr 71
Correction	p. 63, May 72
Infrared communications (letter) K2OAW	p. 65, Jan 72
Injection lasers (letter) Mims	p. 64, Apr 71
Injection lasers, high power Mims	p. 28, Sep 71
Integrated circuits, part I W3FQJ	p. 40, Jun 71
Integrated circuits, part II W3FQJ	p. 58, Jul 71
Integrated circuits, part III W3FQJ	p. 50, Aug 71
Interference, hi-fi (HN) K6KA	p. 63, Mar 75
Interference, rf W1DTY	p. 12, Dec 70
Interference, rf (letter) G3LLL	p. 65, Nov 75

Interference, rf WA3NFW	p. 30, Mar 73
Interference, rf, coaxial connectors can generate W1DTY	p. 48, Jun 76
Interference, rf, its cause and cure G3LLL	p. 26, Jun 75
Intermittent voice operation of power tubes W6SAI	p. 24, Jan 71
Isotropic source and practical antennas K6FD	p. 32, May 70
Laser communications W4KAE	p. 28, Nov 70
LED experiments W4KAE	p. 6, Jun 70
Lighthouse tubes for uhf W6UOV	p. 27, Jun 69
Local-oscillator waveform effects on spurious mixer responses Robinson, Smith	p. 44, Jun 74
Lowpass filters for solid-state linear amplifiers WAØJYK	p. 38, Mar 74
Short circuit	p. 62, Dec 74
L-networks, how to design W7LR	p. 26, Feb 74
Short circuit	p. 62, Dec 74
Lunar-path nomograph WA6NCT	p. 28, Oct 70
Marine installations, amateur, on small boats W3MR	p. 44, Aug 74
Microprocessors, introduction to WB4HYJ, Rony, Titus	p. 32, Dec 75
Microwaves, getting started in Roubal	p. 53, Jun 72
Microwaves, Introduction W1CBY	p. 20, Jan 72
Mini-mobile K9UQN	p. 58, Aug 71
Mismatched transmitter loads, affect of W5JJ	p. 60, Sep 69
Mnemonics W6NIF	p. 69, Dec 69
More electronic units W1EZT	p. 56, Nov 68
Multi-function integrated circuits W3FQJ	p. 46, Oct 72
Network, the ladder W2CHO	p. 48, Dec 76
Networks, transmitter matching W6FFC	p. 6, Jan 73
Neutralizing small-signal amplifiers WA4WDK	p. 40, Sep 70
Noise figure, meaning of K6MIO	p. 26, Mar 69
Operational amplifiers WB2EGZ	p. 6, Nov 69
Phase detector, harmonic W5TRS	p. 40, Aug 74
Phase-locked loops, IC W3FQJ	p. 54, Sep 71
Phase-locked loops, IC, experiments with W3FQJ	p. 58, Oct 71
Phase-shift networks, design criteria for G3NRW	p. 34, Jun 70
Pi and pi-L networks W6SAI	p. 36, Nov 68
Pi network design W6FFC	p. 6, Sep 72
Pi network inductors (letter) W7IV	p. 78, Dec 72
Pi networks, series-tuned W2EGH	p. 42, Oct 71
Power amplifiers, high-efficiency rf WB8LQK	p. 8, Oct 74
Power dividers and hybrids W1DAX	p. 30, Aug 72
Power supplies, survey of solid-state W6GXN	p. 25, Feb 70
Power, voltage and impedance nomograph W2TQK	p. 32, Apr 71
Printed-circuit boards, photofabrication of Hutchinson	p. 6, Sep 71
Programmable calculator simplifies antenna design (HN) W3DVO	p. 70, May 74
Programmable calculators, using W3DVO	p. 40, Mar 75
Proportional temperature control for crystal ovens VE5FP	p. 44, Jan 70
Pulse-duration modulation W3FQJ	p. 65, Nov 72
Q factor, understanding W5JJ	p. 16, Dec 74
QRP operation W7OE	p. 36, Dec 68
Radiation hazard, rf W1DTY	p. 4, Sep 75
Correction	p. 59, Dec 75
Radio communications links W1EZT	p. 44, Oct 69
Radio observatory, vhf Ham	p. 44, Jul 74
Radio-frequency interference WA3NFW	p. 30, Mar 73
Radiotelegraph translator and transcriber W7CUU, K7KFA	p. 8, Nov 71
Eliminating the matrix KH6AP	p. 60, May 72

59+

five nine plus
3402 Campus
Claremont, CA 91711
[714] 621-1658

Antenna Products for the Amateur

All Prices Postpaid in U.S.A.
[outside U.S.A. add shipping —
shipping weight — 1 lb.]
California Residents
add 6% sales tax

IMPEDANCE CONVERSION TRANSFORMERS

BALUNS

- 3-30 MHz Bandwidth
- 2 KW Rating
- Recessed Connector-Eliminates shorting problems
- Exclusive no soldering antenna wire fastening system
- High efficiency toroidal construction
- ABS Plastic Case



6:1 and 9:1
\$22.95 each


1.1 and 4:1
\$16.95 each

Other ratios quoted
on request

SPECIAL INTRODUCTORY OFFER

..... at a price YOU can afford!

SCOTT COMMUNICATIONS SYSTEMS

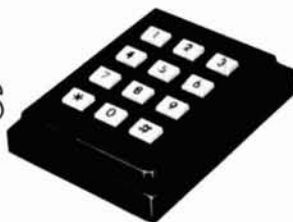

TOUCH TONE ENCODER (Shown) Complete **\$52.95**

RF ACTUATED CW MONITOR —
for the best in CW operating **\$24.95**

CRYSTAL CALIBRATOR — 100, 50, 25 kHz **\$19.95**
range extended to 10, 5, 1 kHz **\$24.95**

RTTY OPERATORS

Digital Date-Time-Message Generator, UARTS.
Quick Brown Fox Generator, many others.

MICROPROCESSOR BUFFS

CPU, Backplane, I/O Memory, Timing,
many others — boards, kits and assemblies.

VHF-FM TRANSCEIVER

TT Pad Programmable, PROM selected Channels.
Hi/Lo Power, PLL-5 kHz resolution.

Above available early '77, write for details.

Send 13¢ Stamp for latest catalog.

SCOTT COMMUNICATIONS SYSTEMS

Box 2117, Dept. H, Stamford, Ct. 06906 or
Call (203) 357-1667

Bind 'em and find 'em

HAM RADIO BINDERS . . . beautiful washable buckram binders complete with date labels. Available in two sizes, one to handle magazines through 1975 and a new large size to handle 1976 and on.

Specify size.

Order HR-BDS (Small)

Just \$5.00 each
3 for \$13.50

Order HR-BOL (Large)

\$5.95 each
3 for \$14.95

Order today from

ham radio

GREENVILLE, NH 03048

CALL TOLL FREE 800-258-5353

The easy \$25 counter kit!

An easy-to-build 50mHz (6-digit) Frequency Counter for a measly \$25! Standard easy-to-find parts, too! (Unlike other kits.) Any Radio Shack has them. Uses 7 segment LED readouts — no scarce Nixie® tubes! No tricky crystal ovens, either! Kit includes a classy cabinet with front panel, PC boards, hardware, instructions, and diagrams. A proven design! An unbeatable offer!

6-DIGIT (50 mHz Kit) FREQUENCY COUNTERS



Hufco

Write or call today!
P.O. Box 357, Dept. 56,
Provo, UT 84601 (801) 375-8566

YOUR

KENWOOD HEADQUARTERS

is

Electronic Distributors, Inc.

1960 Peck St.
Muskegon, Michigan
49441

Ramp generators W6GXN	p. 56, Dec 68	Antenna, bobtail curtain for 40 meters VE1TG	p. 58, Jul 69	Morse code, speed standards for VE2ZK	p. 58, Apr 73
Rating tubes for linear amplifier service W6UOV, W6SAI	p. 50, Mar 71	Antenna, bow tie for 80 meters W9VMQ	p. 56, May 75	Mosfet circuits W3FQJ	p. 50, Feb 75
Reactance problems, nomograph for W6NIF	p. 51, Sep 70	Antenna, converted vee for 80 and 40 W6JKR	p. 18, Dec 69	Power amplifiers, linear, basics of Belt	p.16, Apr 68
Resistor performance at high frequencies K1ORV	p. 36, Oct 71	Antenna couplers, simple W2EY	p. 32, Jan 70	Preamplifier, 21 MHz WA5SNZ	p. 20, Apr 72
Resistors, frequency sensitive (HN) W8YFB	p. 54, Dec 70	Antenna ground system installation W1EZT	p. 64, May 70	Printed-circuit boards, how to make your own K4EEU	p. 58, Apr 73
Resistors, frequency sensitive (letter) W5UHV	p. 68, Jul 71	Antenna, long wire, multiband W3FQJ	p. 28, Nov 69	Printed-circuit boards, low cost W8YFB	p. 16, Jan 75
RF amplifier, wideband WB4KSS	p. 58, Apr 75	Antenna, multiband phased vertical WA7GXO	p. 33, May 72	Q factor, understanding W5JJ	p.16, Dec 74
Rf autotransformers, wideband K4KJ	p. 10, Nov 76	Antenna systems for 40 and 80 meters K6KA	p. 55, Feb 70	Radio communications links, basics of W1EZT	p. 44, Oct 69
Rf power-detecting devices K6JYO	p. 28, Jun 70	Antenna, top-loaded 80-meter vertical VE1TG	p. 48, Jun 69	Receiver frequency calibrator W5UQS	p. 28, Dec 71
Rf power transistors, how to use WA7KRE	p. 8, Jan 70	Antenna tuning units W3FQJ	p. 58, Dec 72, p. 58, Jan 73	Receiver, novice, for 40 and 80 Thorpe	p. 66, Aug 68
Safety in the ham shack Darr, James	p. 44, Mar 69	Antenna, unidirectional for 40 meters GW3NJJ	p. 61, Jan 70	Receiver, regenerative for WWV WA5SNZ	p. 42, Apr 73
Satellite communications, first step to K1MTA	p. 52, Nov 72	Antenna, 80-meter vertical VE1TG	p. 26, May 70	Receivers, direct-conversion W3FQJ	p. 59, Nov 71
Added notes (letter) Satellite signal polarization KH6JJ	p. 73, Apr 73 p. 6, Dec 72	Antenna, 80 meters, for small lot W6AGX	p. 28, May 73	Rectifiers, improved half-wave Bailey	p. 34, Oct 73
Signal detection and communication in the presence of white noise WB6IOM	p. 16, Feb 69	Antennas, dipole KH6HDM	p. 60, Nov 75	Safety in the ham shack Darr	p. 44, Mar 69
Silver/silicone grease (HN) W6DDB	p. 63, May 71	Antennas, for apartment dwellers W2EY	p. 80, Mar 68	Semiconductors, charge flow in WB6BIH	p. 50, Apr 71
Single-tuned interstage networks, designing K6ZGQ	p. 59, Oct 68	Antennas, low elevation W3FQJ	p. 66, May 73	Semiconductor diodes, evaluating W5JJ	p. 52, Dec 71
Smith chart, how to use W1DTY	p. 16, Nov 70	Antennas, QRM reducing receiving types W3FQJ	p. 54, May 71	Single sideband, beginners guide to Belt	p. 66, Mar 68
Correction Solar activity, aspects of K3CHP	p. 76, Dec 71 p. 21, Jun 68	Antennas, simple dual-band W6SAI	p. 18, Mar 70	S-meters, circuits for K6SDX	p. 20, Mar 75
Solar energy W3FQJ	p. 54, Jul 74	Antennas, simple for 80 and 40 meters W5RUB	p. 16, Dec 72	Speaker intelligibility, improving WA5RAQ	p. 53, Aug 70
Speech clippers, rf, performance of G6XN	p. 26, Nov 72	Antennas, simple multiband W9EGQ	p. 54, Jul 68	Ssb signals, how they are generated Belt	p. 24, May 68
Square roots, finding (HN) K9DHD	p. 67, Sep 73	Audio agc principles and practice WA5SNZ	p. 28, Jun 71	Swr bridge WB2ZSH	p. 55, Oct 71
Increased accuracy (letter) Staircase generator (C&T) W1DTY	p. 55, Mar 74 p. 52, Jun 76	Audio filter, tunable WA1JSM	p. 34, Aug 70	Towers and rotators K6KA	p. 34, May 76
Standing-wave ratios, importance of W2HB	p. 26, Jul 73	Audio filters, inexpensive W8YFB	p. 24, Aug 72	Transistor power dissipation, how to determine WN9CGW	p. 56, Jun 71
Correction (letter) Stress analysis of antenna systems W2FZJ	p. 67, May 74 p. 23, Oct 71	Audio module, solid-state receiver K4DHC	p.18, Jun 73	Transistor tester, simple WA6NIL	p. 48, Jul 68
Tetrodes, external-anode W6SAI	p. 23, Jun 69	Batteries, selecting for portable equipment WBØAIK	p. 40, Aug 73	Transmitter keying, improving K6KA	p. 44, Jun 76
Thermoelectric power supplies K1AJE	p. 48, Sep 68	Battery power W3FQJ	p. 56, Aug 74, p. 57, Oct 74	Transmitter, low-power 80-meter W3FQJ	p. 50, Aug 75
Thermometer, electronic VK3ZNV	p. 30, Apr 70	Coaxial cable, what you should know about it W9ISB	p. 30, Sep 68	Transmitter, multiband low power with vfo K8EEG	p. 39, Jul 72
Three-phase motors (HN) W6HPH	p. 79, Aug 68	Current flow W1EZT	p. 34, Jul 68	Transmitter power levels WA5SNZ	p. 62, Apr 71
Thyristors, introduction to WA7KRE	p. 54, Oct 70	COSMOS integrated circuits W3FQJ	p. 50, Jun 75	Transmitter, transistor for 40 meter W6BLZ	p. 44, Jul 68
Toroidal coil inductance (HN) W3WLX	p. 26, Sep 75	CW audio filter, simple W7DI	p. 54, Nov 71	Transmitters, low-power 7-MHz W7OE	p. 3, Dec 68
Toroid coils, 88-mH (HN) WA1NJG	p. 70, Jun 76	CW audio filter, simplest W4VNK	p. 44, Oct 70	Troubleshooting, basic James	p. 54, Jan 76
Toroids, calculating inductance of WB9FHC	p. 50, Feb 72	CW monitor, simple WA9OHR	p. 65, Jan 71	Troubleshooting by voltage measurements James	p. 64, Feb 76
Toroids, plug-in (HN) K8EEG	p. 60, Jan 72	CW reception, improved through simulated stree WA1MKP	p. 53, Oct 74	Troubleshooting, resistance measurements James	p. 58, Apr 76
Transistor amplifiers, tabulated characteristics of W5JJ	p. 30, Mar 71	CW transceiver, low-power for 40 meters W7BBX	p. 16, Jul 74	Troubleshooting, thinking your way through Allen	p. 58, Feb 71
Trig functions on a pocket calculator (HN) W9ZTK	p. 60, Nov 75	Detectors, CW and ssb Belt	p. 3, Nov 68	Tuneup, off-the-air W4MB	p. 40, Mar 76
Tube shields (HN) W9KNI	p. 69, Jul 76	Detectors, regenerative W8YFB	p. 61, Mar 70	Underground coaxial transmission line, how to install WØFCH	p. 38, May 70
Tuning, Current-controlled K2ZSQ	p. 38, Jan 69	Diode detectors W6GXN	p. 28, Jan 76	Vertical antennas, improving efficiency K6FD	p. 54, Dec 74
TV sweep tubes in linear service, full-blast operation of W6SAI, W6OUV	p. 9, Apr 68	Dipoles, multiband for portable use W6SAI	p. 12, May 70	Vfo for 40 and 80 meters W3QBO	p. 36, Aug 70
Vacuum-tube amplifiers, tabulated characteristics of W5JJ	p. 30, Mar 71	Dummy load and rf wattmeter W2OLU	p. 56, Apr 70	Vfo, stable solid-state K4BGF	p. 8, Dec 71
Warning lights, increasing reliability of W3NK	p. 40, Feb 70	Electronic units, basic W1EZT	p. 18, Oct 68, p. 56, Nov 68	Wiring and grounding W1EZT	p. 44, Jun 69
White noise diodes, selecting (HN) W6DOB	p. 65, Apr 76	Feedpoint impedance characteristics of practical antennas W5JJ	p. 50, Dec 73	Workbench, electronics W1EZT	p. 50, Oct 70
Wind direction indicator, digital W6GXN	p. 14, Sep 68	Filter, tunable for audio selectivity W2EY	p. 22, Mar 70		
Wind generators W3FQJ	p. 24, Jul 76	Filters, single sideband Belt	p. 40, Aug 68		
Wind loading on towers and antenna structures, how to calculate K4KJ	p. 16, Aug 74	Fire protection in the ham shack Darr	p. 54, Jan 71		
Added note Y parameters, using in rf amplifier design WAØTCU	p. 56, Jul 75 p. 46, Jul 72	Frequency spotter, crystal controlled W5JJ	p. 36, Nov 70		
		ICs, basics of W3FQJ	p. 40, Jun 71, p. 58, Jul 71		
		ICs, digital, basics W3FQJ	p. 41, Mar 72, p. 58, Apr 72		
		ICs, digital flip-flops W3FQJ	p. 60, Jul 72		
		ICs, digital multivibrators W3FQJ	p. 42, Jun 72		
		ICs, digital, oscillators and dividers W3FQJ	p. 62, Aug 72		
		Interference, hi-fi G3LLL	p. 26, Jun 75		
		Interference, radio frequency WA3NFW	p. 30, Mar 73		
		Man-made interference, how to find W1DTY	p. 12, Dec 70		
		Meters, how to use W4PSJ	p. 48, Sep 75		

novice reading

Ac power line monitor W2OLU	p. 46, Aug 71
Amplifiers, tube and transistor, tabulated characteristics of W5JJ	p. 30, Mar 71

operating

Beam antenna headings W6FFC	p. 64, Apr 71
Code practice stations (letter) WB4LXJ	p. 75, Dec 72
Code practice — the rf way WA4NED	p. 65, Aug 68
Code practice (HN) W2OUX	p. 74, May 73
Computers and ham radio W5TOM	p. 60, Mar 69
CW monitor W2EY	p. 46, Aug 69
CW monitor and code-practice oscillator K6RIL	p. 46, Apr 68
CW monitor, simple WA9OHR	p. 65, Jan 71
CW transceiver operation with transmit-receive offset W1DAX	p. 56, Sep 70
DXCC check list, simple W2CNQ	p. 55, Jun 73

Fluorescent light, portable (HN)	
K8BYO	p. 62, Oct 73
Great-circle charts (HN)	
K6KA	p. 62, Oct 73
How to be DX	
W4NXD	p. 58, Aug 68
Identification timer (HN)	
K9UQN	p. 60, Nov 74
Magazines, use your old	
Foster	p. 52, Jan 70
Morse code, speed standards for	
VE2ZK	p. 68, Apr 73
Added note (letter)	p. 68, Jan 74
Protective material, plastic (HN)	
W6BKK	p. 58, Dec 70
QSL return, statistics on	
WB6IUH	p. 60, Dec 68
Replays, instant (HN)	
W6DNS	p. 67, Feb 70
Sideband location (HN)	
K6KA	p. 62, Aug 73
Spurious signals (HN)	
K6KA	p. 61, Nov 74
Tuning with ssb gear	
W0KD	p. 40, Oct 70
Zulu time (HN)	
K6KA	p. 58, Mar 73

oscillators

AFSK oscillator, solid-state	
WA4FGY	p. 28, Oct 68
Audio oscillator, NE566 IC	
W1EZT	p. 36, Jan 75
Blocking oscillators	
W6GXN	p. 45, Apr 69
Clock oscillator, TTL (HN)	
W9ZTK	p. 56, Dec 73
Crystal oscillator, frequency adjustment of	
W9ZTK	p. 42, Aug 72
Crystal oscillator, high stability	
W6TNS	p. 36, Oct 74
Crystal oscillator, miniature	
W6DOR	p. 68, Dec 68
Crystal oscillators	
W6GXN	p. 33, Jul 69
Crystal oscillators, stable	
DJ2LR	p. 34, Jun 75
Correction	p. 67, Sep 75
Crystal oscillators, survey of	
VK2ZTB	p. 10, Mar 76
Crystal oven, simple (HN)	
Mathieson	p. 66, Apr 76
Crystal switching (HN)	
K6LZM	p. 70, Mar 69
Crystal test oscillator and signal generator	
K4EEU	p. 46, Mar 73
Crystals, overtone (HN)	
G8ABR	p. 72, Aug 72
Goral oscillator notes (HN)	
K5QIN	p. 66, Apr 76
Hex inverter vxo circuit	
W2LTJ	p. 50, Apr 75
Local oscillator, phase locked	
VE5FP	p. 6, Mar 71
Monitoring oscillator	
W2JIO	p. 36, Dec 72
Multiple band master-frequency oscillator	
K6SDX	p. 50, Nov 75
Multivibrator, crystal-controlled	
WN2MQY	p. 65, Jul 71
Oscillator, audio, IC	
W6GXN	p. 50, Feb 73
Oscillator, electronic keyer	
WA6JNJ	p. 44, Jun 70
Oscillator, Franklin (HN)	
W5JJ	p. 61, Jan 72
Oscillator, frequency measuring	
W6JEL	p. 16, Apr 72
Added notes	p. 90, Dec 72
Oscillator, gated (HN)	
WB9KEY	p. 59, Jul 75
Oscillator-monitor, audio	
WA1JSM	p. 48, Sep 70
Oscillator, phase-locked	
VE5FP	p. 6, Mar 71
Oscillator, two-tone, for ssb testing	
W6GXN	p. 11, Apr 72
Oscillators (HN)	
W1DTY	p. 68, Nov 69
Oscillators, cure for cranky (HN)	
W8YFB	p. 55, Dec 70
Oscillators, repairing	
Allen	p. 69, Mar 70
Oscillators, resistance-capacitance	
W6GXN	p. 18, Jul 72
Oscillators, ssb	
Belt	p. 26, Jun 68
Overtone oscillator (HN)	
W5UQS	p. 77, Oct 68
Quadrature-phased local oscillator	
(letter)	
K6ZX	p. 62, Sep 75
Quartz crystals (letter)	
WB2EGZ	p. 74, Dec 72
Stable vfo (C&T)	
W1DTY	p. 51, Jun 76

TTL crystal oscillators (HN)	
W0JVA	p. 60, Aug 75
Vco, crystal-controlled	
WB6IOM	p. 58, Oct 69
Versatile audio oscillator (HN)	
W7BBX	p. 72, Jan 76
Vfo buffer amplifier (HN)	
W3QBO	p. 66, Jul 71
Vfo design, stable	
W1CER	p. 10, Jun 76
Vfo, digital readout	
WB8IFM	p. 14, Jan 73
Vfo for solid-state transmitters	
W3QBO	p. 36, Aug 70
Vfo, high stability	
W8YFB	p. 14, Mar 69
Vfo, high-stability, vhf	
OH2CD	p. 27, Jan 72
Vfo, multiband fet	
K8EEG	p. 39, Jul 72
Vfo, stable	
K4BGF	p. 8, Dec 71
Vfo, stable transistor	
W1DTY	p. 14, Jun 68
Short circuit	p. 34, Aug 68
Vfo transistors (HN)	
W1OOP	p. 74, Nov 69
Vxo design, practical	
K6BIJ	p. 22, Aug 70
455-kHz bfo, transistorized	
W6BLZ, K5GXR	p. 12, Jul 68

power supplies

Ac current monitor (letter)	
WB5MAP	p. 61, Mar 75
Ac power supply, regulated, for mobile	
fm equipment	
WA8TMP	p. 28, Jun 73
Arc suppression networks (HN)	
WA5EKA	p. 70, Jul 73
Batteries, selecting for portable equipment	
WA0AIK	p. 40, Aug 73
Battery drain, auxiliary, guard for (HN)	
W1DTY	p. 74, Oct 74
Battery power	
W3FQJ	p. 56, Aug 74
Charger, fet-controlled, for nicad batteries	
WA0JYK	p. 46, Aug 75
Converter, 12 to 6 volt (C&T)	
W1DTY	p. 42, Apr 76
Current limiting (HN)	
W0LQP	p. 70, Dec 72
Current limiting (letter)	
K5MKO	p. 66, Oct 73
Dc-dc converter, low-power	
W5MLY	p. 54, Mar 75
Dc power supply, regulated (C&T)	
W1DTY	p. 51, Jun 76
Diodes for power supplies, choosing	
W6BLZ	p. 38, Jul 68
Diode surge protection (HN)	
WA7LUJ	p. 65, Mar 72
Added note	p. 77, Aug 72
Dry-cell life	
W1DTY	p. 41, Apr 76
Dual-voltage power supply (HN)	
W1OOP	p. 71, Apr 69
Short circuit	p. 80, Aug 69
Dual-voltage power supply (HN)	
W5JJ	p. 68, Nov 71
Filament transformers, miniature	
Bailey	p. 66, Sep 74
High-power trouble shooting	
Allen	p. 52, Aug 68
IC power (HN)	
W3KBM	p. 68, Apr 72
IC regulated power supply	
W2FBW	p. 50, Nov 70
IC regulated power supply	
W9SEK	p. 51, Dec 70
IC regulated power supply for ICs	
W6GXN	p. 28, Mar 68
Short circuit	p. 80, May 68
Klystrons, reflex power for (HN)	
W6BPK	p. 71, Jul 73
Line transient protection (HN)	
W1DTY	p. 75, Jul 68
Line-voltage monitor (HN)	
W8VFK	p. 66, Jan 74
Current monitor mod (letter)	p. 61, Mar 75
Load protection, scr (HN)	
W5OZF	p. 62, Oct 72
Low-value voltage source (HN)	
WA5EKA	p. 66, Nov 71
Low-voltage supply with short-circuit protection	
WB2EGZ	p. 22, Apr 68
Low-voltage supply (HN)	
WB2EGZ	p. 57, Jun 68
Low voltage, variable bench power supply	
(weekender)	
W6NBI	p. 58, Mar 76
Meter safety (HN)	
W6VFR	p. 68, Jul 72
Mobile power supplies, troubleshooting	
Allen	p. 56, Jun 70

Mobile power supply (HN)	
WN8DJV	p. 79, Apr 70
Mobile supply, low-cost (HN)	
W4GEG	p. 69, Jul 70
Motorola Dispatcher, converting to	
12 volts	
WB6HXU	p. 26, Jul 72
Nicad battery care (HN)	
W1DHZ	p. 71, Feb 76
Operational power supply	
WA2IKL	p. 8, Apr 70
Overvoltage protection (HN)	
W1AAZ	p. 64, Apr 76
Pilot-lamp life (HN)	
W2OLU	p. 71, Jul 73
Polarity inverter, medium current	
Laughlin	p. 26, Nov 73
Power supplies for single sideband	
Belt	p. 38, Feb 69
Power-supply hum (HN)	
W8YFB	p. 64, May 71
Power supply, improved (HN)	
W4ATE	p. 72, Feb 72
Power supply, precision	
W7SK	p. 26, Jul 71
Power supply protection for your solid-state circuits	
W5JJ	p. 36, Jan 70
Precision voltage supply for phase-locked terminal unit (HN)	
WA6TLA	p. 60, Jul 74
Protection for solid-state power supplies (HN)	
W3NK	p. 66, Sep 70
Rectifier, half-wave, improved	
Bailey	p. 34, Oct 73
Regulated solid-state high-voltage power supply	
W6GXN	p. 40, Jan 75
Short circuit	p. 69, Apr 75
Regulated 5-volt supply (HN)	
W6UNF	p. 67, Jan 73
SCR-regulated power supplies	
W4GOC	p. 52, Jul 70
Selenium rectifiers, replacing	
W1DTY	p. 41, Apr 76
Servicing power supplies	
W6GXN	p. 44, Nov 76
Solar energy	
W3FQJ	p. 54, Jul 74
Solar power	
W3FQJ	p. 52, Nov 74
Step-start circuit, high-voltage (HN)	
W6VFR	p. 64, Sep 71
Storage-battery QRP power	
W3FQJ	p. 64, Oct 74
Super regulator, the MPC1000	
W3HUC	p. 52, Sep 76
Survey of solid-state power supplies	
W6GXN	p. 25, Feb 70
Short circuit	p. 76, Sep 70
Thermoelectric power supplies	
K1AJE	p. 48, Sep 68
Transformers, high-voltage, repairing	
W6NIF	p. 66 Mar 69
Transformer shorts	
W6BLZ	p. 36, Jul 68
Transformers, miniature (HN)	
W4ATE	p. 67, Jul 72
Transient eliminator (C&T)	
W1DTY	p. 52, Jun 76
Transients, reducing	
W5JJ	p. 50, Jan 73
Variable power supply for transistor work	
WA4MTH	p. 68, Mar 76
Vibrator replacement, solid-state (HN)	
K8RAY	p. 70, Aug 72
Voltage regulators, IC	
W7FLC	p. 22, Oct 70
Voltage regulator ICs, adjustable	
WB9KEY	p. 36, Aug 75
Voltage-regulator ICs, three-terminal	
WB5EMI	p. 26, Dec 73
Added note (letter)	p. 73, Sep 74
Voltage safety valve	
W2UVF	p. 78, Oct 76
Wind generators	
W3FQJ	p. 50, Jan 75
Zener diodes (HN)	
K3DPJ	p. 79, Aug 68

propagation

Artificial radio aurora, scattering characteristics of	
WB6KAP	p. 18, Nov 74
Echoes, long delay	
WB6KAP	p. 61, May 75
Ionospheric E-layer	
WB6KAP	p. 58, Aug 75
Ionospheric science, short history of	
WB6KAP	p. 58, Jun 69
Long-distance high frequency communications	
WB6KAP	p. 80, Jul 68
Maximum usable frequency, predicting	
WB6KAP	p. 70, Sep 68
Quiet sun, the	
WB6KAP	p. 76, Dec 68

Scatter-mode propagation, frequency synchronization for	
K2OVS	p. 26, Sep 71
Solar cycle 20, vhf'er's view of	
WA5IYX	p. 46, Dec 74
Sunspot numbers	
WB6KAP	p. 63, Jul 69
Sunspot numbers, smoothed	
WB6KAP	p. 72, Nov 68
Sunspots and solar activity	
WB6KAP	p. 60, Jan 69
Tropospheric-duct vhf communications	
WB6KAP	p. 68, Oct 69
6-meter sporadic-E openings, predicting	
WA9RAQ	p. 38, Oct 72
Added note (letter)	p. 69, Jan 74

Detector, superregenerative, optimizing	
Ring	p. 32, Jul 72
Detectors, fm, survey of	
W6GXN	p. 22, Jun 76
Detectors, ssb	
Belt	p. 22, Nov 68
Digital frequency display	
WB2NYK	p. 26, Sep 76
Diode detectors	
W6GXN	p. 28, Jan 76
Diversity receiving system	
W2EEY	p. 12, Dec 71
Filter alignment	
W7UC	p. 61, Aug 75
Filter, vari-Q	
W1SNN	p. 62, Sep 73
Frequency calibrator, how to design	
W3AEX	p. 54, Jul 71
Frequency calibrator, receiver	
W5UQS	p. 28, Dec 71
Frequency measurement of received signals	
W4AAD	p. 38, Oct 73
Frequency spotter, general coverage	
W5JJ	p. 36, Nov 70
Frequency standard (HN)	
WA7JIK	p. 69, Sep 72
Frequency standard, universal	
K4EEU	p. 40, Feb 74
Short circuit	p. 72, May 74
Hang agc circuit for ssb and CW	
W1ERJ	p. 50, Sep 72
Headphone cords (HN)	
W2OLU	p. 62, Nov 75
I-f cathode jack	
W6HPH	p. 28, Sep 68
I-f detector receiver module	
K6SDX	p. 34, Aug 76
I-f system, multimode	
WA2IKL	p. 39, Sep 71
Image suppression (HN)	
W6NIF	p. 68, Dec 72
Intelligibility of communications receivers, improving	
WASRAQ	p. 53, Aug 70
Interference, electric fence	
K6KA	p. 68, Jul 72
Interference, hi-fi (HN)	
K6KA	p. 63, Mar 75
Interference, rf	
W1DTY	p. 12, Dec 70
Interference, rf	
WA3NFW	p. 30, Mar 73
Interference, rf, its cause and cure	
G3LLL	p. 26, Jun 75
Local oscillator, phase-locked	
VE5FP	p. 6, Mar 71
Local-oscillator waveform effects on spurious mixer responses	
Robinson, Smith	p. 44, Jun 74
Mixer, crystal	
W2LTJ	p. 38, Nov 75
Monitor receiver modification (HN)	
W2CNQ	p. 72, Feb 76
Noise blanker	
K4DHC	p. 38, Feb 73
Noise blanker, hot-carrier diode	
W4KAE	p. 16, Oct 69
Short circuit	p. 76, Sep 70
Noise blanker, IC	
W2EEY	p. 52, May 69
Short circuit	p. 79, Jun 70
Noise figure, the real meaning of	
K6MIO	p. 26, Mar 69
Panoramic reception, simple	
W2EEY	p. 14, Oct 68
Phase-shift networks, design criteria	
G3NRW	p. 34, Jun 70
Preamplifier, wideband	
W1AAZ	p. 60, Oct 76
Product detector, hot-carrier diode	
VE3GFN	p. 12, Oct 69
Radio-direction finder	
W6JTT	p. 38, Mar 70
Radio-frequency interference	
WA3NFW	p. 30, Mar 73
Radiotelegraph translator and transcriber	
W7CUU, K7KFA	p. 8, Nov 71
Eliminating the matrix	
KH6AP	p. 60, May 72
Receiver impedance matching (HN)	
W0ZFN	p. 79, Aug 68
Receiving RTTY, automatic frequency control for	
W5NPO	p. 50, Sep 71
Reciprocating detector as fm discriminator	
W1SNN	p. 18, Mar 73
Reciprocating-detector converter	
W1SNN	p. 58, Sep 74
Resurrecting old receivers	
K4IPV	p. 52, Dec 76
Rf amplifiers for communications receivers	
Moore	p. 42, Sep 74
Rf amplifier, wideband	
WB4KSS	p. 58, Apr 75
S-meter readings (HN)	
W1DTY	p. 56, Jun 68
Selectivity, receiver (letter)	
K4ZZV	p. 68, Jan 74

Sensitivity, noise figure and dynamic range	
W1DTY	p. 8, Oct 75
S-meters, solid-state	
K6SDX	p. 20, Mar 75
Spectrum analyzer, four channel	
W9IA	p. 6, Oct 72
Squelch, audio-actuated	
K4MOG	p. 52, Apr 72
Ssb signals, monitoring	
W6VFR	p. 36, Mar 72
Superregenerative detector, optimizing	
Ring	p. 32, Jul 72
Superregenerative receiver, improved	
JA1BHG	p. 48, Dec 70
Threshold-gate/limiter for CW reception	
W2ELV	p. 46, Jan 72
Added notes (letter)	
W2ELV	p. 59, May 72
Troubleshooting the dead receiver	
K4IPV	p. 56, Jun 76
Vlf converter (HN)	
W3CPU	p. 69, Jul 76
Weak signal reception in CW receivers	
ZS6BT	p. 44, Nov 71
WWV receiver, five-frequency	
W6GXN	p. 36, Jul 76

receivers and converters general

Antenna impedance transformer for receivers (HN)	
W6NIF	p. 70, Jan 70
Antenna tuner, miniature receiver (HN)	
WA7KRE	p. 72, Mar 69
Anti-QRM methods	
W3FQJ	p. 50, May 71
Attenuation pads, receiving (letter)	
K0HNQ	p. 69, Jan 74
Audio agc amplifier	
WA5SNZ	p. 32, Dec 73
Audio agc principles and practice	
WA5SNZ	p. 28, Jun 71
Audio amplifier and squelch circuit	
W6AJF	p. 36, Aug 68
Audio filter for CW, tunable	
WA1JSM	p. 34, Aug 70
Audio filter-frequency translator for CW reception	
W2EEY	p. 24, Jun 70
Audio filter mod (HN)	
K6HIU	p. 60, Jan 72
Audio filter, simple	
W4NVK	p. 44, Oct 70
Audio filters, CW (letter)	
6Y5SR	p. 56, Jun 75
Audio filters for ssb and CW reception	
K6SDX	p. 18, Nov 76
Audio-filters, inexpensive	
W8YFB	p. 24, Aug 72
Audio filter, tunable peak-notch	
W2EEY	p. 22, Mar 70
Audio filter, variable bandpass	
W3AEX	p. 36, Apr 70
Audio module, complete	
K4DHC	p. 18, Jun 73
Batteries, how to select for portable equipment	
WA0AIK	p. 40, Aug 73
Bfo multiplexer for a multimode detector	
WA3YGJ	p. 52, Oct 75
Calibrator crystals (HN)	
K6KA	p. 66, Nov 71
Calibrator, plug-in frequency	
K6KA	p. 22, Mar 69
Calibrator, simple frequency-divider using mos ICs	
W6GXN	p. 30, Aug 69
Communications receivers, design ideas for	
Moore	p. 12, Jun 74
Communications receivers, designing for strong-signal performance	
Moore	p. 6, Feb 73
Converting a vacuum-tube receiver to solid-state	
W1OOP	p. 26, Feb 69
Counter dials, electronic	
K6KA	p. 44, Sep 70
Crystal-filter design, practical	
PY2PE1C	p. 34, Nov 76
CW filter, adding (HN)	
W2OUX	p. 66, Sep 73
CW monitor, simple	
WA9OHR	p. 65, Jan 71
CW processor for communications receivers	
W6NRW	p. 17, Oct 71
CW reception, enhancing through a simulated-stereo technique	
WA1MKP	p. 61, Oct 74
CW reception, noise reduction for	
W2ELV	p. 52, Sep 73
CW regenerator for interference-free communications	
Leward, Libenschek	p. 54, Apr 74
CW selectivity with crystal bandpassing	
W2EEY	p. 52, Jun 69
CW transceiver operation with transmit-receive offset	
W1DAX	p. 56, Sep 70
Detector, reciprocating	
W1SNN	p. 32, Mar 72
Added notes	p. 54, Mar 74; p. 76, May 75
Detector, single-signal phasing type	
WB9CYY	p. 71, Oct 76

high-frequency receivers

Bandpass filters for receiver preselectors	
W7ZOI	p. 18, Feb 75
Bandpass tuning, electronic, in the Drake R-4C	
Horner	p. 58, Oct 73
BC-603 tank receiver, updating the	
WA6IAK	p. 52, May 68
BC-1206 for 7 MHz, converted	
W4FIN	p. 30, Oct 70
Short circuit	p. 72, Apr 71
Collins 75A4 hints (HN)	
W6VFR	p. 68, Apr 72
Collins 75A-4 modifications (HN)	
W4SD	p. 67, Jan 71
Communications receiver, five band	
K6SDX	p. 6, Jun 72
Communications receiver for 80 meters, IC	
VE3ELP	p. 6, Jul 71
Communications receiver, micropower	
WB9FHC	p. 30, Jun 73
Short circuit	p. 58, Dec 73
Communications receivers, miniature design ideas for	
K4DHC	p. 18, Apr 76
Communications receiver, miniaturized	
K4DHC	p. 24, Sep 74
Communications receiver, optimum design for	
DJ2LR	p. 10, Oct 76
Communications receiver, solid-state	
I5TDJ	p. 32, Oct 75
Correction	p. 59, Dec 75
Companion receiver, all-mode	
W1SNN	p. 18, Mar 73
Converter, hf, solid-state	
VE3GFN	p. 32, Feb 72
Converter, tuned very low-frequency	
OH2KT	p. 49, Nov 74
Converter, very low frequency receiving	
W2IMB	p. 24, Nov 76
Direct-conversion receivers	
W3FQJ	p. 59, Nov 71
Direct-conversion receivers, improved selectivity	
K6BIJ	p. 32, Apr 72
Direct-conversion receivers, simple active filters for	
W7ZOI	p. 12, Apr 74
Double-conversion hf receiver with mechanical frequency readout	
Perolo	p. 26, Oct 76
ESSA weather receiver	
W6GXN	p. 36, May 68
Fet converter, bandswitching, for 40, 20, 15 and 10 (VE3GFN)	
postsript	p. 6, Jul 68
Fet converter for 10 to 40 meters, second-generation	
VE3GFN	p. 28, Jan 70
Short circuit	p. 79, Jun 70
Frequency synthesizer for the Drake R-4	
W6NBI	p. 6, Aug 72
Modification (letter)	p. 74, Sep 74
Gonset converter, solid-state modification of	
Schuler	p. 58, Sep 69
Hammarlund HQ215, adding 160-meter coverage	
W2GHK	p. 32, Jan 72
Heath SB-650 frequency display, using with other receivers	
K2BYM	p. 40, Jun 73
High dynamic range receiver input stages	
DJ2LR	p. 26, Oct 75
High-frequency DX receiver	
WB2ZVU	p. 10, Dec 76
Incremental tuning to your transceiver, adding	
VE3GFN	p. 66, Feb 71
Monitoring oscillator	
W2JIO	p. 36, Dec 72

HAM RADIO HORIZONS



The New General Interest Amateur Radio Magazine for The Beginner, The Novice, The Old-Timer Your Family & Your Friends

The Folks at Ham Radio heard you and here it is: **Ham Radio Horizons**, a down to basics monthly magazine edited by some of the most experienced and capable Amateurs in the field, experts who know how to put their experience into easy to read—easy to understand terms. Lots of color—lots of class. You're going to like **Ham Radio Horizons**.

Ham Radio Horizons is the first monthly magazine of Amateur Radio specifically for the Beginner and Novice, but in a highly skillful manner that will appeal to everyone from non-amateurs to experienced old timers.

Straight forward Theory and Construction articles will spell things out so that everyone can follow just what the author has in mind. Continuing features will highlight the **FUN** of Amateur Radio, what we're doing and where we're going.

Ham Radio Horizons is written for the Beginner, but you'll find everyone reading, learning and enjoying this exciting new magazine.

SOME FEATURE ARTICLES IN OUR INTRODUCTORY ISSUE

The Far Horizon by W9KNI...who writes on DXing, "I listen an instant before calling him—it sounds like half the world is in there. I begin to call: A7XA DE W9KNI K. I listen again. He's in there..."

Taking the Mystery Out of SSB, by W1SL. Is SSB the cure all of all Times? "Well, maybe yes, maybe no; it depends on just how perfect a cure you are looking for." W1SL fills in the background and development of SSB and tells what SSB means to you.

The Not-So-Rocky Road from CB to Ham, by W2EUQ, "Radio amateurs, traditionally and with great pride, form the backbone of non-commercial communication in the world. All that's necessary for you to begin is to have the desire; there's a huge world of communication opportunities out there just waiting for you to take part..."

30% Off

●●●●●●●●●● **Introductory Offer!** (Good til Jan. 1)

To: Ham Radio HORIZONS, Greenville, N.H. 03048		Gift Subscription for friends, wives and novices you know.	
Enclosed is my check or money order for \$7.00 (\$3.00 savings.)			
Name.....	Name.....		
Address.....	Address.....		
City.....	City.....	State.....	
	State.....	Please enclose \$7.00 per Gift Subscription.	

A HAM RADIO Publication

Multiband high-frequency converter
K6SDX p. 32, Oct 76

Outboard receiver with a transceiver
W1DTY p. 12, Sep 68

Outboard receiver with the SB-100, using an (HN)
K4GMR p. 68, Feb 70

Overload response in the Collins 75A-4 receiver, improving
W6ZO p. 42, Apr 70
Short circuit p. 76, Sep 70

Phasing-type ssb receiver
WA2JYK p. 6, Aug 73
Short circuit p. 58, Dec 73
Added note (letter) p. 63, Jun 74

Preamplifier, emitter-tuned, 21 MHz
WA5SNZ p. 20, Apr 72

Preamplifier, low-noise high-gain transistor
W2EY p. 66, Feb 69

Preselector, general-coverage (HN)
W5OZF p. 75, Oct 70

Q5er, solid-state
W5TKP p. 20, Aug 69

Receiver incremental tuning for the Swan 350 (HN)
K1KXA p. 64, Jul 71

Receiver, reciprocating detector
W1SNN p. 44, Nov 72
Correction (letter) p. 77, Dec 72

Receiver, versatile solid-state
W1PLJ p. 10, Jul 70

Receiving RTTY with Heath SB receivers (HN)
K9HVV p. 64, Oct 71

Rf amplifiers, selective
K6BIJ p. 58, Feb 72

Regenerative detectors and a wideband amplifier for experimenters
W8YFB p. 61, Mar 70

RTTY monitor receiver
K4EEU p. 27, Dec 72

RTTY receiver-demodulator for net operation
VE7BRK p. 42, Feb 73

RTTY with SB-300
W2ARZ p. 76, Jul 68

Swan 350 CW monitor (HN)
K1KXA p. 63, Jun 72

Transceiver selectivity improved (HN)
VE3BWD p. 74, Oct 70

Tuner overload, eliminating (HN)
VE3GFN p. 66, Jan 73
Attenuators for (letter) p. 69, Jan 74

Two-band novice superhet
Thorpe p. 66, Aug 68

Weather receiver, low-frequency
W6GXN p. 36, Oct 68

WWW receiver, fixed-tuned
W6GXN p. 24, Nov 69

WWW receiver, regenerative
WA5SNZ p. 42, Apr 73

WWW receiver, simple (HN)
WA3JBN p. 68, Jul 70
Short circuit p. 72, Dec 70

WWW receiver, simple (HN)
WA3JBN p. 55, Dec 70

WWW-WVVH, amateur applications for
W3FQJ p. 53, Jan 72

455-kHz bfo, transistorized
W6BLZ, K5GXR p. 12, Jul 68

160-meter receiver, simple
W6FPO p. 44, Nov 70

1.9 MHz receiver
W3TNO p. 6, Dec 69

7-MHz ssb receiver and transmitter, simple
VE3GSD p. 6, Mar 74
Short circuit p. 62, Dec 74

28-MHz superregen receiver
K2ZSQ p. 70, Nov 68

vhf receivers and converters

Converters for six and two meters, mosfet
WB2EGZ p. 41, Feb 71
Short circuit p. 96, Dec 71

Cooled preamplifier for vhf-uhf
WA0RDX p. 36, Jul 72

Fet converters for 50, 144, 220 and 432 MHz
W6AJF p. 20, Mar 68

Filter-preamplifiers for 50 and 144 MHz etched
W5KNT p. 6, Feb 71

Fm channel scanner
W2FPP p. 29, Aug 71

Fm communications receiver, modular
K8AUH p. 32, Jun 69
Correction p. 71, Jan 70

Fm receiver frequency control (letter)
W3AFN p. 65, Apr 71

Fm receiver performance, comparison of
VE7ABK p. 68, Aug 72

Fm receiver, multichannel for six and two
W1SNN p. 54, Feb 74

Fm receiver, tunable vhf
K8AUH p. 34, Nov 71

Fm receiver, uhf
WA2GCF p. 6, Nov 72

Fm repeaters, receiving system degradation in
K5ZBA p. 36, May 69

HW-17A, perking up (HN)
WBEGZ p. 70, Aug 70

Improving vhf/uhf receivers
W1JAA p. 44, Mar 76

Interdigital preamplifier and comb-line bandpass filter for vhf and uhf
W5KHT p. 6, Aug 70

Interference, scanning receiver (HN)
K2YAH p. 70, Sep 72

Monitor receivers, two-meter fm
WB5EMI p. 34, Apr 74

Overload problems with vhf converters, solving
W100P p. 53, Jan 73

Receiver alignment techniques, vhf fm
K4IPV p. 14, Aug 75

Receiver, modular two-meter fm
WA2GFB p. 42, Feb 72

Receiver, vhf fm
WA2GCF p. 8, Nov 75

Receiving converter, vhf four-band
W3TQM p. 64, Oct 76

Scanning receiver for vhf fm, improved
WA2GCF p. 26, Nov 74

Scanning receiver modifications, vhf fm (HN)
WA5WOU p. 60, Feb 74

Scanning receivers for two-meter fm
K4IPV p. 28, Aug 74

Six-meter converter, improved
K1BQT p. 50, Aug 70

Six-meter mosfet converter
WB2EGZ p. 22, Jun 68
Short circuit p. 34, Aug 68

Squelch-audio amplifier for fm receivers
WB4WSU p. 68, Sep 74

Ssb mini-tuner
K1BQT p. 16, Oct 70

Two-meter converter, 1.5 dB NF
WA6SXC p. 14, Jul 68

Two-meter mosfet converter
WB2EGZ p. 22, Aug 68
Neutralizing p. 77, Oct 68

Two-meter preamp, MM5000
W4KAE p. 49, Oct 68

Vhf converter performance, optimizing (HN)
K2FSQ p. 18, Jul 68

Vhf fm receiver (letter)
K8IHQ p. 76, May 73

Vhf receiver scanner
K2LZG p. 22, Feb 73

Vhf superregenerative receiver, low-voltage
WA5SNZ p. 22, Jul 73
Short circuit p. 64, Mar 74

28-30 MHz preamplifier for satellite reception
W1JAA p. 48, Oct 75

50-MHz preamplifier, improved
WA2GCF p. 46, Jan 73

144-MHz converter (HN)
K0VQY p. 71, Aug 70

144-MHz converter (letter)
W0LER p. 71, Oct 71

144 MHz converter, hot-carrier diode
K8CJU p. 6, Oct 69

144-MHz converter, modular
W6UOV p. 64, Oct 70

144 MHz converters, choosing fets for (HN)
K6JYO p. 70, Aug 69

144-MHz preamp, low-noise
W1DTY p. 40, Apr 76

144-MHz preamp, super (HN)
K6HCP p. 72, Oct 69

144-MHz preamplifier, improved
WA2GCF p. 25, Mar 72
Added notes p. 73, Jul 72

220-MHz mosfet converter
WB2EGZ p. 28, Jan 69
Short circuit p. 76, Jul 69

432-MHz converter, low-noise
K6JC p. 34, Oct 70

432-MHz fet converter, low noise
WA6SXC p. 18, May 68

432 MHz preamp (HN)
W1DTY p. 66, Aug 69

432 MHz preamplifier and converter
WA2GCF p. 40, Jul 75

1296-MHz converter, solid-state
VK4ZT p. 6, Nov 70

1296 MHz, double-balanced mixers for
WA6UAM p. 8, Jul 75

1296-MHz preamplifier
WA6UAM p. 42, Oct 75

1296-MHz preamplifier, low-noise
WA2VTR p. 50, Jun 71
Added note (letter) p. 65, Jan 72

2340-MHz converter, solid-state
K2JNG, WA2LTM, WA2VTR p. 16, Mar 72

2304-MHz preamplifier, solid-state
WA2VTR p. 20, Aug 72

receivers and converters, test and troubleshooting

Receiver alignment
Allen p. 64, Jun 68

Rf and i-f amplifiers, troubleshooting
Allen p. 60, Sep 70

Signal injection in ham receivers
Allen p. 72, May 68

Signal tracing in ham receivers
Allen p. 52, Apr 68

Weak-signal source, variable-output
K6JYO p. 36, Sep 71

Weak-signal source, 144 and 432 MHz
K6JC p. 58, Mar 70

Weak-signal source, 432 and 1296 MHz
K6RIL p. 20, Sep 68

RTTY

AFSK generator (HN)
F8KI p. 69, Jul 76

AFSK generator, crystal-controlled
K7BVT p. 13, Jul 72

AFSK generator, crystal-controlled
W6LLO p. 14, Dec 73
Sluggish oscillator (letter) p. 59, Dec 74

AFSK oscillators, solid-state
WA4FGY p. 28, Oct 68

Audio-frequency keyer, simple
W2LTJ p. 56, Aug 75

Audio-frequency shift keyer
KH6FMT p. 45, Sep 76

Audio-frequency shift keyer, simple (C&T)
W1DTY p. 43, Apr 76

Audio-shift keyer, continuous-phase
VE3CTP p. 10, Oct 73
Short circuit p. 64, Mar 74

Automatic frequency control for receiving RTTY
W5NPO p. 50, Sep 71
Added note (letter) p. 66, Jan 72

Autostart, digital RTTY
K4EEU p. 6, Jun 73

Autostart monitor receiver
K4EED p. 37, Dec 72

CRT intensifier for RTTY
K4VFA p. 18, Jul 71

Carriage return, adding to the automatic line-feed generator (HN)
K4EEU p. 71, Sep 74

Coherent frequency-shift keying, need for
K3WJQ p. 30, Jun 74
Added notes (letter) p. 58, Nov 74

Crystal test oscillator and signal generator
K4EEU p. 46, Mar 73

CW memory for RTTY identification
W6LLO p. 6, Jan 74

DT-500 demodulator
K9HVV, K4OAH, WB4KUR p. 24, Mar 76
Short circuit p. 85, Oct 76

DT-600 demodulator
K9HVV, K4OAH, WB4KUR p. 8, Feb 76
Letter, K5GZR p. 78, Sep 76
Short circuit p. 85, Oct 76

Electronic speed conversion for RTTY teleprinters
WA6JYJ p. 36, Dec 71
Printed circuit for p. 54, Oct 72

Frequency-shift meter, RTTY
VK3ZNV p. 53, Jun 70

Line-end indicator, IC
W2OKO p. 22, Nov 75

Line feed, automatic for RTTY
K4EEU p. 20, Jan 73

Mainline ST-5 autostart and antispace
K2YAH p. 46, Dec 72

Mainline ST-5 RTTY demodulator
W6FFC p. 14, Sep 70
Short circuit p. 72, Dec 70

Mainline ST-6 RTTY demodulator
W6FFC p. 6, Jan 71
Short circuit p. 72, Apr 71

Mainline ST-6 RTTY demodulator, more uses for (letter)
W6FFC p. 69, Jul 71

Mainline ST-6 RTTY demodulator, troubleshooting
W6FFC p. 50, Feb 71

Message generator, random access memory
RTTY p. 8, Jan 75
K4EEU p. 8, Jan 75

Message generator, RTTY
W60XP, W8KCQ p. 30, Feb 74

Monitor scope, phase-shift
W3CIX p. 36, Aug 72

Monitor scope, RTTY, Heath HO-10 and SB-610 as (HN)
K9HVV p. 70, Sep 74

Monitor scope, RTTY, solid-state
WB2MPZ p. 33, Oct 71

Performance and signal-to-noise ratio of low-frequency shift RTTY
K6SR p. 62, Dec 76

Phase-locked loop AFSK generator
K7ZOF p. 27, Mar 73

Phase-locked loop RTTY terminal unit	
W4FQM	p. 8, Jan 72
Correction	p. 60, May 72
Power supply for	p. 60, Jul 74
Optimization of the phase-locked terminal unit	p. 22, Sep 75
Update, W4AYV	p. 16, Aug 76
Precise tuning with ssb gear	
WØKD	p. 40, Oct 70
Printed circuit for RTTY speed converter	
W7POG	p. 54, Oct 72
Receiver-demodulator for RTTY net operation	
VE7BRK	p. 42, Feb 73
Ribbon re-inkers	
W6FFC	p. 30, Jun 72
RTTY converter, miniature IC	
K9MRL	p. 40, May 69
Short circuit	p. 80, Aug 69
RTTY distortion: causes and cures	
WB6IMP	p. 36, Sep 72
RTTY for the blind (letter)	
VE7BRK	p. 76, Aug 72
RTTY, introduction to	
K6JFP	p. 38, Jun 69
RTTY line-length indicator (HN)	
W2UVF	p. 62, Nov 73
RTTY reception with Heath SB receivers (HN)	
K9HWV	p. 64, Oct 71
RTTY with the SB-300	
W2ARZ	p. 76, Jul 68
Signal Generator, RTTY	
W7ZTC	p. 23, Mar 71
Short circuit	p. 96, Dec 71
Simple circuit replaces jack patch panel	
K4STE	p. 25, Apr 76
Speed control, electronic, for RTTY	
W3VF	p. 50, Aug 74
ST-5 keys polar relay (HN)	
WØLPD	p. 72, May 74
Swan 350 and 400 equipment on RTTY (HN)	
WB2MIC	p. 67, Aug 69
Synchrophase afsk oscillator	
W6FOO	p. 30, Dec 70
Synchrophase RTTY reception	
W6FOO	p. 38, Nov 70
Teleprinters, new look in	
W6JTT	p. 38, Jul 70
Terminal unit, phase-locked loop	
W4FQM	p. 8, Jan 72
Correction	p. 60, May 72
Terminal unit, phase-locked loop	
W4AYV	p. 36, Feb 75
Terminal unit, variable-shift RTTY	
W3VF	p. 16, Nov 73
Test generator, RTTY (HN)	
W3EAG	p. 67, Jan 73
Test generator, RTTY (HN)	
W3EAG	p. 59, Mar 73
Test-message generator, RTTY	
K9GSC, K9PKQ	p. 30, Nov 76
Time/date printout	
WØLZT	p. 18, Jun 76
Voltage supply, precision for phase-locked terminal unit (HN)	
WA6TLA	p. 60, Jul 74

satellites

Amateur radio in space, bibliography	
W6OLO	p. 60, Aug 68
Addenda	p. 77, Oct 68
Antenna control, automatic azimuth/elevation for satellite communications	
WA3HLT	p. 26, Jan 75
Correction	p. 58, Dec 75
Antenna, simple satellite (HN)	
WA6PXV	p. 59, Feb 75
Antennas, simple, for satellite communications	
K4GSX	p. 24, May 74
Az-el antenna mount for satellite communications	
W2LX	p. 34, Mar 75
Circularly-polarized ground-plane antenna for satellite communications	
K4GSX	p. 28, Dec 74
Communications, first step to satellite	
K1MTA	p. 52, Nov 72
Added notes (letter)	p. 73, Apr 73
Oscar antenna (C&T)	
W1DTY	p. 50, Jun 76
Oscar antenna, mobile (HN)	
W6OAL	p. 67, May 76
Oscar tracking program, HP-65 calculator (letters)	
WA3THD	p. 71, Jan 76
Oscar 7, communications techniques for	
G3ZCZ	p. 6, Apr 74
Picture transmission, recording satellite	
W6CCN	p. 6, Nov 68
Signal polarization, satellite	
KH6IJ	p. 6, Dec 72
28-30 MHz preamplifier for satellite reception	
W1JAA	p. 48, Oct 75
432-MHz OSCAR antenna (HN)	
W1JAA	p. 58, Jul 75

semiconductors

Antenna switch for meters, solid-state	
K2ZSQ	p. 48, May 69
Avalanche transistor circuits	
W4NVK	p. 22, Dec 70
Beta master, the	
K8ERV	p. 18, Aug 68
Charge flow in semiconductors	
WB6BIH	p. 50, Apr 71
Converting a vacuum-tube receiver to solid-state	
W1OOP	p. 26, Feb 69
Short circuit	p. 76, Jul 69
Converting vacuum tube equipment to solid-state	
W2EEY	p. 30, Aug 68
Curve master, the	
K8ERV	p. 40, Mar 68
Diodes, evaluating	
W5JJ	p. 52, Dec 71
Dynamic transistor tester (HN)	
VE7ABK	p. 65, Oct 71
European semiconductor numbering system (C&T)	
W1DTY	p. 42, Apr 76
Fet bias problems simplified	
WA5SNZ	p. 50, Mar 74
Fet biasing	
W3FQJ	p. 61, Nov 72
Fetrons, solid-state replacements for tubes	
W1DTY	p. 4, Aug 72
Added notes	p. 66, Oct 73; p. 62, Jun 74
Frequency multipliers	
W6GXN	p. 6, Aug 71
Frequency multipliers, transistor	
W6AJF	p. 49, Jun 70
Glass semiconductors	
W1EZT	p. 54, Jul 69
Grid-dip oscillator, solid-state conversion of	
W6AJZ	p. 20, Jun 70
Heatsink problems, how to solve transistor	
WA5SNZ	p. 46, Jan 74
Impulse generator, snap diode	
Siegal, Turner	p. 29, Oct 72
Injection lasers, high power	
Mims	p. 28, Sep 71
Injection lasers (letter)	
Mims	p. 64, Apr 71
Linear power amplifier, high power solid-state	
Chambers	p. 6, Aug 74
Linear transistor amplifier	
W3FQJ	p. 59, Sep 71
Long-tail transistor biasing	
W2DXH	p. 64, Apr 68
Microwave amplifier design, solid state	
W46UAM	p. 40, Oct 76
Mobile converter, solid-state modification of	
Schuler	p. 58, Sep 69
Mosfet circuits	
W3FQJ	p. 50, Feb 75
Mosfet transistors (HN)	
WB2EGZ	p. 72, Aug 69
Motorola fets (letter)	
W1CER	p. 64, Apr 71
Motorola MPS transistors (HN)	
W2DXH	p. 42, Apr 68
Neutralizing small-signal amplifiers	
WA4WDK	p. 40, Sep 70
Noise, zener-diode (HN)	
VE7ABK	p. 59, Jun 75
Parasitic oscillations in high-power transistor rf amplifiers	
WØKGI	p. 54, Sep 70
Pentode replacement (HN)	
W1DTY	p. 70, Feb 70
Power dissipation ratings of transistors	
WN9CGW	p. 56, Jun 71
Power fets	
W3FQJ	p. 34, Apr 71
Power transistors, paralleling (HN)	
WA5EKA	p. 62, Jan 72
Relay, transistor replaces (HN)	
W3NK	p. 72, Jan 70
Replace the unijunction transistor	
K9VXL	p. 58, Apr 68
Rf power detecting devices	
K6JYO	p. 28, Jun 70
Rf power transistors, how to use	
WA7KRE	p. 8, Jan 70
Snap diode impulse generator	
Siegal, Turner	p. 29, Oct 72
Surplus transistors, identifying	
W2FPP	p. 38, Dec 70
Thyristors, introduction to	
WA7KRE	p. 54, Oct 70
Transconductance tester for field-effect transistors	
W6NBI	p. 44, Sep 71
Transistor amplifiers, tabulated characteristics of	
W5JJ	p. 30, Mar 71
Transistor and diode tester	
ZL2AMJ	p. 65, Nov 70
Transistor breakdown voltages	
WA5EKA	p. 44, Feb 75
Transistors for vhf transmitters (HN)	
W1OOP	p. 74, Sep 69

Transistor storage (HN)	
K8ERV	p. 58, Jun 68
Transistor tester	
WA6NIL	p. 48, Jul 68
Transistor tester for leakage and gain	
W4BRS	p. 68, May 68
Transistor testing	
Allen	p. 62, Jul 70
Transistor-tube talk (HN)	
WA4NED	p. 25, Jun 68
Trapatt diodes (letter)	
WA7NLA	p. 72, Apr 72
Troubleshooting around fets	
Allen	p. 42, Oct 68
Troubleshooting transistor ham gear	
Allen	p. 64, Jul 68
Vfo transistors (HN)	
W1OOP	p. 74, Nov 69
Y parameters in rf design, using	
WAØTCU	p. 46, Jul 72
Zener diodes (HN)	
K3DPJ	p. 79, Aug 68
Zener tester, Low voltage (HN)	
K3DPJ	p. 72, Nov 69

single sideband

Balanced modulator, integrated-circuit	
K7QWR	p. 6, Sep 70
Balanced modulators, dual fet	
W3FQJ	p. 63, Oct 71
Communications receiver, phasing-type	
WAØJYK	p. 6, Aug 73
Converting a-m power amplifiers to ssb service	
WA4GNW	p. 55, Sep 68
Converting the Swan 120 to two meters	
K6RIL	p. 8, May 68
Detectors, ssb	
Belt	p. 22, Nov 68
Detector, ssb, IC (HN)	
K4ODS	p. 67, Dec 72
Correction	p. 72, Apr 73
Double-balanced mixers	
W1DTY	p. 48, Mar 68
Double-balanced modulator, broadband	
WA6NCT	p. 8, Mar 70
Electronic bias switching for linear amplifiers	
W6VFR	p. 50, Mar 75
Filters, single-sideband	
Belt	p. 40, Aug 68
Filters, ssb (HN)	
K6KA	p. 63, Nov 73
Frequency dividers for ssb	
W7BZ	p. 24, Dec 71
Frequency translation in ssb transmitters	
Belt	p. 22, Sep 68
Generating ssb signals with suppressed carriers	
Belt	p. 24, May 68
Guide to single sideband, a beginner's	
Belt	p. 66, Mar 68
Hang agc circuit for ssb and CW	
W1ERJ	p. 50, Sep 72
Intermittent voice operation of power tubes	
W6SAI	p. 24, Jan 71
Intermodulation-distortion measurements on ssb transmitters	
W6VFR	p. 34, Sep 74
Linear amplifier, five-band conduction-cooled	
W9KIT	p. 6, Jul 72
Linear amplifier, five-band kilowatt	
W4OQ	p. 14, Jan 74
Improved operation (letter)	p. 59, Dec 74
Linear amplifier, homebrew five-band	
W7IV	p. 30, Mar 70
Linear amplifier performance, improving	
W4PSJ	p. 68, Oct 71
Linear amplifier, 100-watt	
W6WR	p. 28, Dec 75
Linear, five-band hf	
W7DI	p. 6, Mar 72
Linear for 80-10 meters, high-power	
W6HHN	p. 56, Apr 71
Short circuit	p. 96, Dec 71
Linearity meter for ssb amplifiers	
W4MB	p. 40, Jun 76
Linear power amplifiers	
Belt	p. 16, Apr 68
Lines, three bands with two (HN)	
W4NJF	p. 70, Nov 69
Minituner, ssb	
K1BQT	p. 16, Oct 70
Modifying the Heath SB-200 amplifier for the new 8873 zero-bias triode	
W6UOV	p. 32, Jan 71
Oscillators, ssb	
Belt	p. 26, Jun 68
Peak envelope power, how to measure	
W5JJ	p. 32, Nov 74
Phase-shift networks, design criteria for	
G3NRW	p. 34, Jun 70
Phase-shift ssb generators	
Belt	p. 20, Jul 68

Power supplies for ssb
 Belt p. 38, Feb 69
Precise tuning with ssb gear
 WØKD p. 40, Oct 70
Pre-emphasis for ssb transmitters
 OH2CD p. 38, Feb 72
Rating tubes for linear amplifier service
 W6UOV, W6SAI p. 50, Mar 71
Rf clipper for the Collins S-line
 K6JYO p. 18, Aug 71
 Letter p. 68, Dec 71
Rf speech processor, ssb
 W2MB p. 18, Sep 73
Sideband location (HN)
 K6KA p. 62, Aug 73
Solid-state circuits for ssb
 Belt p. 18, Jan 69
Solid-state transmitting converter for 144-MHz ssb
 W6NBI p. 6, Feb 74
 Short circuit p. 62, Dec 74
Speech clipper, IC
 K6HTM p. 18, Feb 73
 Added notes (letter) p. 64, Oct 73
Speech clipper, rf, construction
 G6KN p. 12, Dec 72
Speech clippers, rf, performance of
 G6XN p. 26, Nov 72
 Added notes p. 58, Aug 73; p. 72, Sep 74
Speech clipping
 K6KA p. 24, Apr 63
Speech clipping in single-sideband equipment
 K1YZW p. 22, Feb 71
Speech processing
 W1DTY p. 60, Jun 68
Speech processing, principles of
 ZL1BN p. 28, Feb 75
 Added notes p. 75, May 75; p. 64, Nov 75
Speech processor for ssb
 K6PHT p. 22, Apr 70
Speech process, logarithmic
 WA3FIY p. 38, Jan 70
Speech processor, ssb
 VK9GN p. 31, Dec 71
Speech splatter on single sideband
 W4MB p. 28, Sep 75
Ssb exciter, 5-band
 K1UKX p. 10, Mar 68
Ssb generator, phasing-type
 W7CMJ p. 22, Apr 73
 Added comments (letter) p. 65, Nov 73
Ssb generator, 9-MHz
 W9KIT p. 6, Dec 70
Ssb transceiver, IC, for 80 meters
 VE3GSD p. 48, Apr 76
Switching and linear amplification
 W3FQJ p. 61, Oct 71
Syllabic vox system for Drake equipment
 W6RM p. 24, Aug 76
Transceiver, miniature 7-MHz
 W7BBX p. 16, Jul 74
Transceiver, single-band ssb
 W1DTY p. 8, Jun 69
Transceiver, ssb, IC
 G3ZVC p. 34, Aug 74
 Circuit change (letter) p. 62, Sep 75
Transceiver, ssb, using LM373 IC
 W5BAA p. 32, Nov 73
Transceiver, 3.5-MHz ssb
 VE6ABX p. 6, Mar 73
Transmitter alignment
 Allen p. 62, Oct 69
Transmitter and receiver for 40 meters, ssb
 VE3GSD p. 6, Mar 74
 Short circuit p. 62, Dec 74
Transmitter, phasing-type ssb
 WAØJYK p. 8, Jun 75
Transmitting mixers, 6 and 2 meters
 K2ISP p. 8, Apr 69
Transverter, 6-meter
 K8DOC, K8TVP p. 44, Dec 68
Trapezoidal monitor scope
 VE3CUS p. 22, Dec 69
TTL ICs, using in ssb equipment
 G4ADJ p. 18, Nov 75
Tuning up ssb transmitters
 Allen p. 62, Nov 69
TV sweep tubes in linear service, full-blast operation of
 W6SAI, W6UOV p. 9, Apr 68
Two-tone oscillator for ssb testing
 W6GXN p. 11, Apr 72
Vacuum tubes, using odd-ball types in linear amplifier service
 W5JJ p. 58, Sep 72
Vhf, uhf transverter, input source for (HN)
 F8MK p. 69, Sep 70
Vox and mox systems for ssb
 Belt p. 24, Oct 68
Vox, versatile
 W9KIT p. 50, Jul 71
 Short circuit p. 96, Dec 71
3-500Z in amateur service, the
 W6SAI p. 56, Mar 68
144-MHz linear, 2kW
 W6UOV, W6ZO, K6DC p. 26, Apr 70
144-MHz low-drive kilowatt linear
 W6HHN p. 26, Jul 70

144-MHz transverter, the TR-144
 K1RAK p. 24, Feb 72
432 MHz rf power amplifier
 K6JC p. 40, Apr 70
432-MHz ssb converter
 K6JC p. 48, Jan 70
 Short circuit p. 79, Jun 70
432-MHz ssb, practical approach to
 WA2FSQ p. 6, Jun 71
1296-MHz ssb transceiver
 WA6UAM p. 8, Sep 74

television

Camera and monitor, sstv
 VE3EGO, Watson p. 38, Apr 63
Color tv, slow-scan
 W4UMF, WB8DQT p. 59, Dec 69
Computer, processing, sstv pictures
 W4UMF p. 30, Jul 70
Fast-scan camera converter for sstv
 WA9UHV p. 22, Jul 74
Fast-to slow-scan conversion, tv
 W3EFG, W3YZC p. 32, Jul 71
Frequency-selective and sensitivity-controlled sstv preamp
 DK1BF p. 36, Nov 75
Slow-scan television
 WA2EMC p. 52, Dec 69
Slow-to-fast-scan television converters, an introduction
 K4TWJ p. 44, Aug 76
Sync generator, IC, for ATV
 WØKGI p. 34, Jul 75
Synch generator, sstv (letter)
 W1IA p. 73, Apr 73
Television DX
 WA9RAQ p. 30, Aug 73
Test generator, sstv
 K4EEU p. 6, Jul 73
Vestigial sideband microtransmitter for amateur television
 WA6UAM p. 20, Feb 76
50 years of television
 W1DTY, K4TWJ p. 36, Feb 76
 Letter, WA6JFP p. 77, Sep 76

transmitters and power amplifiers general

Amplitude modulation, a different approach
 WA5SNZ p. 50, Feb 70
Batteries, how to select for portable equipment
 WAØAIK p. 40, Aug 73
Blower maintenance (HN)
 W6NIF p. 71, Feb 71
Blower-to-chassis adapter (HN)
 K6JYO p. 73, Feb 71
Converting a-m power amplifiers to ssb service
 WA4GNW p. 55, Sep 68
Efficiency of linear power amplifiers, how to compare
 W5JJ p. 64, Jul 73
Electronic bias switching for linear amplifiers
 W6VFR p. 50, Mar 75
Fail-safe timer, transmitter (HN)
 K9HVV p. 72, Oct 74
Filters, ssb (HN)
 K6KA p. 63, Nov 73
Frequency multipliers
 W6GXN p. 6, Aug 71
Frequency translation in ssb Transmitters
 Belt p. 22, Sep 68
Grid-current measurement in grounded-grid amplifiers
 W6SAI p. 64, Aug 68
Intermittent voice operation of power tubes
 W6SAI p. 24, Jan 71
Key and vox clicks (HN)
 K6KA p. 74, Aug 72
Linear power amplifiers
 Belt p. 16, Apr 68
Lowpass filters for solid-state linear amplifiers
 WAØJYK p. 38, Mar 74
 Short circuit p. 62, Dec 74
Multiple tubes in parallel grounding grid (HN)
 W7CSD p. 60, Aug 71
Networks, transmitter matching
 W6FFC p. 6, Jan 73
Neutralizing tip (HN)
 ZE6JP p. 69, Dec 72
Parasitic oscillations in high-power transistor rf amplifiers
 WØKGI p. 54, Sep 70
Parasitic suppressor (HN)
 WA9JMY p. 80, Apr 70

Pi and Pi-L networks
 W6SAI p. 36, Nov 68
Pi network design aid
 W6NIF p. 62, May 74
 Correction (letter) p. 58, Dec 74
Pi-network design, high-frequency power amplifier
 W6FFC p. 6, Sep 72
Pi-network inductors (letter)
 W7IV p. 78, Dec 72
Pi networks, series tuned
 W2EGH p. 42, Oct 71
Power attenuator, all-band 10-dB
 K1CCL p. 68, Apr 70
Power fets
 W3FQJ p. 34, Apr 71
Power tube open filament pins (HN)
 W9KNI p. 69, Apr 75
Pre-emphasis for ssb transmitters
 OH2CD p. 38, Feb 72
Relay activator (HN)
 K6KA p. 62, Sep 71
Rf power amplifiers, high-efficiency
 WB8LQK p. 8, Oct 74
Rf power transistors, how to use
 WA7KRE p. 8, Jan 70
Screen clamp, solid-state
 WØLRW p. 44, Sep 68
Sstv reporting system
 WB6ZYE p. 78, Sep 76
Step-start circuit, high-voltage (HN)
 W6VFR p. 64, Sep 71
Swr alarm circuits
 W2EEY p. 73, Apr 70
Temperature alarms for high-power amplifiers
 W2EEY p. 48, Jul 70
Transmitter power levels, some observations regarding
 WA5SNZ p. 62, Apr 71
Transmitter, remote keying (HN)
 WA3HOU p. 74, Oct 69
Transmitter switching, solid-state
 W2EEY p. 44, Jun 68
Transmitter-tuning unit for the blind
 W9NTP p. 60, Jun 71
TV sweep tubes in linear service, full-blast operation of
 W6SAI, W6UOV p. 9, Apr 68
Vacuum tubes, using odd-ball types in linear amplifiers
 W5JJ p. 58, Sep 72
Vfo, digital readout
 WB8IFM p. 14, Jan 73

high-frequency transmitters

ART-13, Modifying for noiseless CW (HN)
 K5GKN p. 68, Aug 69
CW transceiver for 40 and 80 meters
 W3NNL, K3OIO p. 14, Jul 69
CW transceiver, low-power 20-meter
 W7ZOI p. 8, Nov 74
CW transmitter, half-watt
 KØVQY p. 69, Nov 69
Driver and final for 40 and 80 meters, solid-state
 W3QBO p. 20, Feb 72
Electronic bias switch for negatively-biased power amplifiers
 WA5KPG p. 27, Nov 76
Field-effect transistor transmitters
 K2BLA p. 30, Feb 71
Filters, low-pass for 10 and 15 meters
 W2EEY p. 42, Jan 72
Frequency synthesizer, high frequency
 K2BLA p. 16, Oct 72
Grounded-grid 2 kW PEP amplifier, high frequency
 W6SAI p. 6, Feb 69
Heath HW-101 transceiver, using with a separate receiver (HN)
 WA1MKP p. 63, Oct 73
Linear amplifier, five-band
 W7IV p. 30, Mar 70
Linear amplifier, five-band conduction-cooled
 W9KIT p. 6, Jul 72
Linear amplifier performance, improving
 W4PSJ p. 68, Oct 71
Linear amplifier, 100-watt
 W6WR p. 28, Dec 75
Linear, five-band hf
 W7DI p. 6, Mar 72
Linear, five-band kilowatt
 W4OQ p. 14, Jan 74
 Improved operation (letter) p. 59, Dec 74
Linear for 80-10 meters, high-power
 W6HHN p. 56, Apr 71
 Short circuit p. 96, Dec 71
Linear power amplifier, high-power solid-state
 Chambers p. 6, Aug 74
Lines, three bands with two (HN)
 W4NJF p. 70, Nov 69
Low-frequency transmitter, solid-state
 W4KAE p. 16, Nov 68

BOOKS 'n STUFF from *ham radio*

HERE'S A GREAT GIFT IDEA FOR THE DX'er!

W2AB's SECOND OP

(formerly W9IOP)

7th EDITION

Fully Computer Revised

NEW

This wonderful operating aid immediately tells the prefix, continent, DX Zone, country name, local beam heading, time differential, QSL bureau and postal information for every recognized DX country. Don't go another day without this nifty tool!

Order HR-20P

A Super Gift for only \$3.50



LOW & MEDIUM FREQUENCY SCRAPBOOK

by Ken Cornell, W2IMB

Here in informal scrapbook form is the first book to explore the enticing world of those low frequencies you've been hearing about. This book shows how you can get on the air legally without any license in the 160 kHz region with simple, effective and easily built equipment. Full information is given regarding FCC rules and regulations. This may become a new Amateur band after WARC '79 — why not get a head start today with this valuable new book?

Order HR-LF Only \$6.95

In special custom loose leaf binder

Order HR-LFB Just \$8.95

The best selling technical handbook of any type ever published.

THE RADIO AMATEUR'S HANDBOOK for 1977

ARRL STAFF



Long considered as the standard reference for the Radio Amateur the 1977 edition has again been revised with approximately 20% new material to keep up with today's rapidly expanding technology. Here is your chance to have the very latest edition just as soon as it is issued. The perfect gift idea.

The softbound edition will be shipped in time for Holiday delivery.

Softbound Order AR-HB Only \$7.50

Deluxe Hardbound Edition available Feb. 1977

Order AR-BB Only \$12.50

from RSGB

VHF-UHF MANUAL by D. Evans, G3RPE and G. Jessop, G6JP

The most important new VHF-UHF book in several years.

Previous editions of this book have been world-wide best sellers and this latest edition should be no exception. Extensively rewritten and greatly expanded, the RSGB VHF-UHF Manual covers this important field from A to Z.

You'll learn about basic techniques, receivers, transmitters, space communications, antennas, specialized test equipment and much much more. There is a major all-new section on microwaves. FM is also well covered.

If you have any interest in the world above 30 MHz you deserve to have a copy of this handsome 400 page hardcover book on your bookshelf.


Order RS-VH

Just \$12.95

VHF-UHF MANUAL



NEW

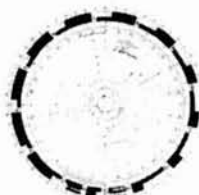

SATELLABE

A sophisticated multi-scale circular slide rule that gives the user all the data required to track and make contacts through the Amateur built OSCAR spacecraft. Using only the equatorial crossing point and time of one spacecraft orbit, the Satellabe will calculate azimuth and elevation information from the user's location for that entire orbit and predict all subsequent orbits as well. Designed by OSCAR user K2ZRO for AMSAT.

Order Satellabe

Just \$7.95

HAM RADIO, Greenville, NH 03048

Lowpass filter, high-frequency	
W20LU	p. 24, Mar 75
Short circuit	p. 59, Jun 75
Modifying the Heath SB-200 amplifier for the new 8B73 zero-bias triode	
W6UOV	p. 32, Jan 71
Phase-locked loop, 28 MHz	
W1KNI	p. 40, Jan 73
QRP fet transmitter, 80-meter	
W3FQJ	p. 50, Aug 75
Ssb exciter, 5-band	
K1UKX	p. 10, Mar 68
Ssb transceiver, miniature 7-MHz	
W7BBX	p. 16, Jul 74
Ssb transceiver using LM373 IC	
W5BAA	p. 32, Nov 73
Ssb transceiver, 9-MHz, IC	
G3ZVC	p. 34, Aug 74
Circuit change (letter)	p. 62, Sep 75
Ssb transmitter and receiver, 40 meters	
VE3GSD	p. 6, Mar 74
Short circuit	p. 62, Dec 74
Ssb transmitter, phasing type	
WA0JYK	p. 8, Jun 75
Tank circuit, inductively-tuned high-frequency	
W6SAI	p. 6, Jul 70
Transceiver, single-band ssb	
W1DTY	p. 8, Jun 69
Transceiver, 3.5-MHz ssb	
VE6ABX	p. 6, Mar 73
Transmitter, low-power	
W6NIF	p. 26, Dec 70
Transmitters, QRP	
W7OE	p. 36, Dec 68
Transmitter, universal flea-power	
K2ZSQ	p. 58, Apr 69
Transverter, high-level hf	
K4ERO	p. 68, Jul 68
Wideband linear amplifier, 4 watt	
VE5FP	p. 42, Jan 76
3-400Z, 3-500Z filament circuits, notes on	
K9WEH	p. 66, Apr 76
3-500Z in amateur service, the	
W6SAI	p. 56, Mar 68
7-MHz QRP CW transmitter	
WA4MTH	p. 26, Dec 76
14-MHz vfo transmitter, solid-state	
W3QBO	p. 6, Nov 73
28-MHz transmitter, solid-state	
K2ZSQ	p. 10, Jul 68
40-meters, transistor rig for	
W6BLZ, K5GXR	p. 44, Jul 68
160-meters, 500-watt power amplifier	
W2BP	p. 8, Aug 75

vhf and uhf transmitters

Converting the Swan 120 to two meters	
K6RIL	p. 8, May 68
Fm repeater transmitter, improving	
W6GDO	p. 24, Oct 69
Linear for 2 meters	
W4KAE	p. 47, Jan 69
Linear for 1296 MHz, high-power	
WB6IOM	p. 8, Aug 68
Phase-locked loop, 50 MHz	
W1KNI	p. 40, Jan 73
Transistors for vhf transmitters (HN)	
W1OOP	p. 74, Sep 69
Transmitter, flea power	
K2ZSQ	p. 58, Apr 69
Transmitting mixers for 6 and 2 meters	
K2ISP	p. 8, Apr 69
Transverter for 6 meters	
WA9IGU	p. 44, Jul 69
Tunnel diode phone rig, 6-meter (HN)	
K2ZSQ	p. 74, Jul 68
Vhf linear, 2kW, design data for	
W6UOV	p. 6, Mar 69
50-MHz kilowatt, inductively tuned	
K1DPP	p. 8, Sep 75
50-MHz linear amplifier	
K1RAK	p. 38, Nov 71
50-MHz linear amplifier, 2-kW	
W6UOV	p. 16, Feb 71
50-MHz linear, inductively tuned	
W6SAI	p. 6, Jul 70
50-MHz transmitter, solid-state	
WB2EGZ	p. 6, Oct 68
50-MHz transverter	
K1RAK	p. 12, Mar 71
50/144-MHz multimode transmitter	
K2ISP	p. 28, Sep 70
144-MHz fm transmitter	
W9SEK	p. 6, Apr 72
144-MHz fm transmitter, solid-state	
W6AJF	p. 14, Jul 71
144-MHz fm transmitter, Sonobaby	
WA0ZUO	p. 8, Oct 71
Short circuit	p. 96, Dec 71
Crystal deck for	p. 26, Oct 72
144-MHz low-drive kilowatt linear	
W6HHN	p. 26, Jul 70
144-MHz low-power solid-state transmitter	
K0VQY	p. 52, Mar 70
144-MHz phase-modulated transmitter	
W6AJF	p. 18, Feb 70

144-MHz power amplifier, high performance	
W6UOV	p. 22, Aug 71
144-MHz power amplifier, 10-watt solid-state	
W1DTY	p. 67, Jan 74
144-MHz rf power amplifiers, solid state	
W4CGC	p. 6, Apr 73
144-MHz transmitting converter, solid-state ssb	
W6NBI	p. 6, Feb 74
Short circuit	p. 62, Dec 74
144-MHz transceiver, a-m	
K1AOB	p. 55, Dec 71
144-MHz two-kilowatt linear	
W6UOV, W6ZO, K6DC	p. 26, Apr 70
144- and 432- stripline amplifier/tripler	
K2RIW	p. 6, Feb 70
220-MHz exciter	
WB6DJV	p. 50, Nov 71
220-MHz power amplifier	
W6UOV	p. 44, Dec 71
220-MHz, rf power amplifier for	
WB6DJV	p. 44, Jan 71
220-MHz rf power amplifier, vhf fm	
K7JUE	p. 6, Sep 73
432-MHz amplifier, 2-kW	
W6DAI, W6NLZ	p. 6, Sep 68
432-MHz exciter, solid-state	
W1OOP	p. 38, Oct 69
432-MHz rf power amplifier	
K6JC	p. 40, Apr 70
432-MHz solid-state linear amplifier	
WB6QXF	p. 30, Aug 75
432-MHz ssb converter	
K6JC	p. 48, Jan 70
Short circuit	p. 79, Jun 70
432-MHz 100-watt solid-state power amplifier	
WA7CNP	p. 36, Sep 75
1296-MHz frequency tripler	
K4SUM, W4API	p. 40, Sep 69
1296-MHz power amplifier	
W2COH, W2CCY, W2OJ, W1MU	p. 43, Mar 70
2304-MHz power amplifier	
WA9HUV	p. 8, Feb 75

transmitters and power amplifiers, test and troubleshooting

Aligning vhf transmitters	
Allen	p. 58, Sep 68
Ssb transmitter alignment	
Allen	p. 62, Oct 69
Transverter, 6-meter	
K8DOC, K8TVP	p. 44, Dec 68
Tuning up ssb transmitters	
Allen	p. 62, Nov 69

troubleshooting

Analyzing wrong dc voltages	
Allen	p. 54, Feb 69
Audio distortion, curing in speech amplifiers	
Allen	p. 42, Aug 70
Basic troubleshooting	
James	p. 54, Jan 76
Dc-dc converters, curing trouble in	
Allen	p. 56, Jun 70
Fets, troubleshooting around	
Allen	p. 42, Oct 68
High-voltage troubleshooting	
Allen	p. 52, Aug 68
Mobile power supplies, troubleshooting	
Allen	p. 56, Jun 70
Ohmmeter troubleshooting	
Allen	p. 52, Jan 69
Oscillators, repairing	
Allen	p. 69, Mar 70
Oscilloscope, putting to work	
Allen	p. 64, Sep 69
Oscilloscope, troubleshooting amateur gear with	
Allen	p. 52, Aug 69
Receiver alignment	
Allen	p. 64, Jun 68
Receiver alignment techniques, vhf fm	
K4IPV	p. 14, Aug 75
Receivers, troubleshooting the dead	
K4IPV	p. 56, Jun 76
Resistance measurement, troubleshooting by	
Allen	p. 62, Nov 68
Resistance measurement, troubleshooting by	
James	p. 58, Apr 76
Rf and if amplifiers, troubleshooting	
Allen	p. 60, Sep 70
Signal injection testing in receivers	
Allen	p. 72, May 68
Signal tracing in amateur receivers	
Allen	p. 52, Apr 68
Speech amplifiers, curing distortion	
Allen	p. 42, Aug 70
Ssb transmitter alignment	
Allen	p. 62, Oct 69
Sweep generator, how to use	
Allen	p. 60, Apr 70

Transistor amateur gear, troubleshooting	
Allen	p. 64, Jul 68
Transistor circuits, troubleshooting	
K4IPV	p. 60, Sep 76
Transistor testing	
Allen	p. 62, Jul 70
Tuning up ssb transmitters	
Allen	p. 62, Nov 69
Vhf transmitters, aligning	
Allen	p. 58, Sep 68
Voltage troubleshooting	
James	p. 64, Feb 76

vhf and microwave general

Amateur vhf fm operation	
W6AYZ	p. 36, Jun 68
Artificial radio aurora, vhf scattering characteristics	
WB6KAP	p. 18, Nov 74
A-m modulation monitor (HN)	
K7JUNL	p. 67, Jul 71
APX-6 transponder, notes on	
W6OSA	p. 32, Apr 68
Band change from six to two meters, quick	
K0YQY	p. 64, Feb 70
Bandpass filters, single-pole	
W6HPH	p. 51, Sep 69
Bandpass filters, 25 to 2500 MHz	
K6RIL	p. 46, Sep 69
Bypassing, rf, at vhf	
WB6BHI	p. 50, Jan 72
Cavity filter, 144-MHz	
W1SNN	p. 22, Dec 73
Short circuit	p. 64, Mar 74
Coaxial filter, vhf	
W6SAI	p. 36, Aug 71
Coaxial-line resonators (HN)	
WA7KRE	p. 82, Apr 70
Coil-winding data, practical vhf and uhf	
K3SVC	p. 6, Apr 71
Crystal mount, untuned	
W1DTY	p. 68, Jun 68
Effective radiated power (HN)	
VE7CB	p. 72, May 73
Frequency multipliers	
W6GXN	p. 6, Aug 71
Frequency multipliers, transistor	
W6AJF	p. 49, Jun 70
Frequency scaler, 500-MHz	
W6URH	p. 32, Jun 75
Frequency scalars, 1200-MHz	
WB9KEY	p. 38, Feb 75
Frequency synchronization for scatter-mode propagation	
K2OVS	p. 26, Sep 71
Frequency synthesizer, 220 MHz	
W6GXN	p. 8, Dec 74
Gridded tubes, vhf/uhf effects in	
W6UOV	p. 8, Jan 69
Harmonic generator (HN)	
W5GDQ	p. 76, Oct 70
Impedance bridge (HN)	
W6KZK	p. 67, Feb 70
Improving vhf/uhf receivers	
W1JAA	p. 44, Mar 76
Indicator, sensitive rf	
WB9DNI	p. 38, Apr 73
Klystron cooler, waveguide (HN)	
WA4WDL	p. 74, Oct 74
Lunar-path nomograph	
WA6NCT	p. 28, Oct 70
Microwave communications, amateur standards for	
K6HIJ	p. 54, Sep 69
Microwave frequency doubler	
WA4WDL	p. 69, Mar 76
Microwave hybrids and couplers for amateur use	
W2CTK	p. 57, Jul 70
Short circuit	p. 72, Dec 70
Microwave marker generator, 3cm band (HN)	
WA4WDL	p. 69, Jun 76
Microwaves, getting started in	
Roubal	p. 53, Jun 72
Microwaves, introduction to	
W1CBB	p. 20, Jan 72
Moonbounce to Australia	
W1DTY	p. 85, Apr 68
Noise figure, meaning of	
K6MIO	p. 26, Mar 69
Noise figure measurements, vhf	
WB6NMT	p. 36, Jun 72
Noise generators, using (HN)	
K2ZSQ	p. 79, Aug 68
Phase-locked loop, tunable 50 MHz	
W1KNI	p. 40, Jan 73
Power dividers and hybrids	
W1DAX	p. 30, Aug 72
Proportional temperature control for crystal ovens	
VE5FP	p. 44, Jan 70
Radio observatory, vhf	
Ham	p. 44, Jul 74
Reflex klystrons, pogo stick for (HN)	
W6BPK	p. 71, Jul 73

Rf power-detecting devices K6JYO	p. 28, Jun 70
Satellite communications K1TMA	p. 52, Nov 72
Added notes (letter)	p. 73, Apr 73
Satellite signal polarization KH6IJ	p. 6, Dec 72
Solar cycle 20, vhf's view of WA5IYX	p. 46, Dec 74
Tank circuits, design of vhf K7UNL	p. 56, Nov 70
Uhf dummy load, 150-watt WB6QXF	p. 30, Sep 76
Uhf hardware (HN) W6CMQ	p. 76, Oct 70
Vfo, high-stability vhf OH2CD	p. 27, Jan 72
Vhf beacons K6EDX	p. 52, Oct 69
Vhf beacons W3FQJ	p. 66, Dec 71
50-MHz bandpass filter W4EKO	p. 70, Aug 76
50-MHz frequency synthesizer W1KNI	p. 26, Mar 74
144-MHz fm frequency meter W4JAZ	p. 40, Jan 71
Short circuit	p. 72, Apr 71
144-MHz frequency synthesizer WB4FPK	p. 34, Jul 73
144-MHz frequency-synthesizer, one- crystal W2KMV	p. 30, Sep 73
220-MHz frequency synthesizer W6GXN	p. 8, Dec 74
432-MHz ssb, practical approach to WA2FSQ	p. 6, Jun 71
1296-MHz microstripline bandpass filters WA6UAM	p. 46, Dec 75
40-GHz record K7PMY	p. 70, Dec 68

vhf and microwave antennas

Circularly-polarized ground-plane antenna for satellite communications K4GSX	p. 28, Dec 74
Feed horn, cylindrical, for parabolic reflectors WA9HUV	p. 16, May 76
Feeding and matching techniques for vhf/uhf antennas W1JAA	p. 54, May 76
Ground plane, portable vhf (HN) K9DHD	p. 71, May 73
Log-periodic yagi beam antenna K6RIL, W6SAI	p. 8, Jul 69
Correction	p. 68, Feb 70
Matching techniques for vhf/uhf antennas W1JAA	p. 50, Jul 76
Microstrip swr bridge, vhf and uhf W4CGC	p. 22, Dec 72
Microwave antenna, low-cost K6HIJ	p. 52, Nov 69
Parabolic reflector antennas VK3ATN	p. 12, May 74
Parabolic reflector element spacing WA9HUV	p. 28, May 75
Parabolic reflector gain W2TQK	p. 50, Jul 75
Parabolic reflector, 16-foot homebrew WB6IOM	p. 8, Aug 69
Parabolic reflectors, finding focal length of (HN) WA4WDL	p. 57, Mar 74
Swr meter W6VSV	p. 6, Oct 70
Transmission lines, uhf WA2VTR	p. 36, May 71
Two-meter antenna, simple (HN) W6BLZ	p. 78, Aug 68
Two-meter mobile antennas W6BLZ	p. 76, May 68
Vhf antenna switching without relays (HN) K2ZSQ	p. 77, Sep 68
10 GHz dielectric antenna (HN) WA4WDL	p. 80, May 75
50-MHz antenna coupler K1RAK	p. 44, Jul 71
50-MHz collinear beam K4ERO	p. 59, Nov 69
50-MHz cubical quad, economy W6DOR	p. 50, Apr 69
50-MHz J-pole antenna K4SDY	p. 48, Aug 68
50-MHz mobile antenna (HN) W4PSJ	p. 77, Oct 70
144-MHz antenna, 1/3 wave vertical K6KLO	p. 40, Jul 74
144-MHz antenna, 5/8-wave vertical, build from CB mobile whips WB4WSU	p. 67, Jun 74
144-MHz antennas, simple WA3NFW	p. 30, May 73
144-MHz antenna switch, solid-state K2ZSQ	p. 48, May 69

144-MHz collinear antenna W6RJO	p. 12, May 72
144-MHz collinear uses PVC pipe mast (HN) K8LLZ	p. 66, May 76
144-MHz four-element collinear array WB6KGF	p. 6, May 71
144-MHz ground plane antenna, 0.7 wavelength W3WZA	p. 40, Mar 69
144-MHz moonbounce antenna K6HCP	p. 52, May 70
144-MHz whip, 5/8-wave (HN) VE3DDD	p. 70, Apr 73
432-MHz corner reflector antenna WA2FSQ	p. 24, Nov 71
432-MHz high-gain Yagi K6HCP	p. 46, Jan 76
Comments, WØPW	p. 63, May 76
432-MHz OSCAR antenna (HN) W1JAA	p. 58, Jul 75
432- and 1296-MHz quad-yagi arrays W3AED	p. 20, May 73
Short circuit	p. 58, Dec 73
440-MHz collinear antenna, four-element WA6HTP	p. 38, May 73
1296-MHz Yagi W2CQH	p. 24, May 72
1296-MHz Yagi array W3AED	p. 40, May 75

vhf and microwave receivers and converters

Audio filter, tunable, for weak-signal communications K6HCP	p. 28, Nov 75
Cooled preamplifier for vhf-uhf reception WAØRDX	p. 36, Jul 72
Fet converters for 50, 144, 220 and 432 MHz W6AJF	p. 20, Mar 68
Interdigital preamplifier and comb-line bandpass filter for vhf and uhf W6KHT	p. 6, Aug 70
Microwave amplifier design, solid state WA6UAM	p. 40, Oct 76
Noise figure, sensitivity and dynamic range W1DTY	p. 8, Oct 75
Noise figure, vhf, estimating WA9HUV	p. 42, Jun 75
Overload problems with vhf converters, solving W1OOP	p. 53, Jan 73
Receiver scanner, vhf K2LZG	p. 22, Feb 73
Receiver, superregenerative, for vhf WA5SNZ	p. 22, Jul 73
Signal detection and communication in the presence of white noise WB6IOM	p. 16, Feb 69
Signal generator for two and six meters WA8OIK	p. 54, Nov 69
Single-frequency conversion, vhf/uhf W3FQJ	p. 62, Apr 75
Vhf converter performance, optimizing (HN) K2ZSQ	p. 18, Jul 68
Weak-signal source, stable, variable output K6JYO	p. 36, Sep 71
Weak-signal source, 144 and 432 MHz K6JC	p. 58, Mar 70
Weak-signal source, 432 and 1296 MHz K6RIL	p. 20, Sep 68
28-30 MHz low-noise preamp W1JAA	p. 48, Oct 75
50-MHz deluxe mosfet converter WB2EGZ	p. 41, Feb 71
50-MHz etched-inductance bandpass filters and filter-preamplifiers W5KHT	p. 6, Feb 71
50-MHz mosfet converter WB2EGZ	p. 22, Jun 68
Short circuit	p. 34, Aug 68
50-MHz preamplifier, improved WA2GCF	p. 46, Jan 73
144-MHz converter (HN) KØVYQ	p. 71, Aug 70
144-MHz converter, 1.5 dB noise figure WA6SXC	p. 14, Jul 68
144-MHz converters, choosing fets (HN) K6JYO	p. 70, Aug 69
144-MHz deluxe mosfet converter WB2EGZ	p. 41, Feb 71
Short circuit	p. 96, Dec 71
Letter, WØLER	p. 71, Oct 71
144-MHz etched-inductance bandpass filters and filter-preamplifiers W5KHT	p. 6, Feb 71
144-MHz fm receiver W9SEK	p. 22, Sep 70
144-MHz fm receiver WA2GBF	p. 42, Feb 72
Added notes	p. 73, Jul 72
144-MHz fm receiver WA2GCF	p. 6, Nov 72
144-MHz preamplifier, improved WA2GCF	p. 25, Mar 72

144-MHz preamplifier, low noise W8BBB	p. 36, Jun 74
144-MHz preamp, low-noise W1DTY	p. 40, Apr 76
144-MHz preamp, super (HN) K6HCP	p. 72, Oct 69
144-MHz preamp, MM5000 W4KAE	p. 49, Oct 68
144-MHz transverter using power fets WB6BPI	p. 10, Sep 76
220-MHz mosfet converter WB2EGZ	p. 28, Jan 69
Short circuit	p. 76, Jul 69
432-MHz converter, low-noise K6JC	p. 34, Oct 70
432-MHz fet converter, low-noise WA6SXC	p. 18, May 68
432-MHz fet preamp (HN) W1DTY	p. 66, Aug 69
432 MHz preamplifier and converter WA2GCF	p. 40, Jul 75
432-MHz preamplifier, ultra low-noise W1JAA	p. 8, Mar 75
1296-MHz converter, solid state VK4ZT	p. 6, Nov 70
1296 MHz, double-balanced mixers for WA6UAM	p. 8, Jul 75
1296-MHz noise generator W3BSV	p. 46, Aug 73
1296-MHz preamplifier WA6UAM	p. 42, Oct 75
1296-MHz preamplifier, low-noise transistor WA2VTR	p. 50, Jun 71
Added note (letter)	p. 65, Jan 72
1296-MHz preamplifiers, microstripline WA6UAM	p. 12, Apr 75
Comments, W2DU	p. 68, Jan 76
1296-MHz ssb transceiver WA6UAM	p. 8, Sep 74
2304-MHz balanced mixer WA2ZZF	p. 58, Oct 75
2304-MHz converter, solid-state K2JNG, WA2LTM, WA2VTR	p. 16, Mar 72
2304-MHz preamplifier, solid-state WA2VTR	p. 20, Aug 72
2304-MHz preamplifiers, narrow-band solid-state WA9HUV	p. 6, Jul 74

vhf and microwave transmitters

Aligning vhf transmitters Allen	p. 58, Sep 68
Converting the Swan 120 to two meters K6RIL	p. 8, May 68
External anode tetrodes W6SAI	p. 23, Jun 69
Inductively-tuned tank circuit W6SAI	p. 6, Jul 70
Lighthouse tubes for uhf W6UOV	p. 27, Jun 69
Pi networks, series-tuned W2EGH	p. 42, Oct 71
Ssb input source for vhf, uhf transverters (HN) F8MK	p. 69, Sep 70
Transistors for vhf transmitters (HN) W1OOP	p. 74, Sep 69
Vhf linear, 2 kW, design data for W6UOV	p. 7, Mar 69
2C39, water cooling K6MYC	p. 30, Jun 69
50-MHz customized transverter K1RAK	p. 12, Mar 71
50-MHz heterodyne transmitting mixer K2ISP	p. 8, Apr 69
Correction	p. 76, Sep 70
50-MHz kilowatt, inductively-tuned K1DPP	p. 8, Sep 75
50-MHz 2 kW linear amplifier W6UOV	p. 16, Feb 71
50-MHz linear amplifier K1RAK	p. 38, Nov 71
50-MHz multimode transmitter K2ISP	p. 28, Sep 70
50-MHz transmitter, solid-state WB2EGZ	p. 6, Oct 68
50-MHz transverter K8DOC, K8TVP	p. 44, Dec 68
50-MHz transverter WA9IGU	p. 44, Jul 69
50-MHz tunnel-diode phone rig K2ZSQ	p. 74, Jul 68
144-MHz fm transceiver, compact W6AOI	p. 36, Jan 74
144-MHz fm transmitter W6AJF	p. 14, Jul 71
144-MHz fm transmitter W9SEK	p. 6, Apr 72
144-MHz fm transmitter, Sonobaby WAØUZO	p. 8, Oct 72
Crystal deck for Sonobaby	p. 26, Oct 72
144-MHz heterodyne transmitting mixers K2ISP	p. 8, Apr 69
Correction	p. 76, Sep 70

144-MHz linear	
W4KAE	p. 47, Jan 69
144-MHz linear, 2kW, design data for	
W6UOV	p. 7, Mar 69
144-MHz low-drive kilowatt linear	
W6HHN	p. 26, Jul 70
144-MHz multimode transmitter	
K2ISP	p. 28, Sep 70
144-MHz phase-modulated transmitter	
W6AJF	p. 18, Feb 70
144-MHz power amplifier, high performance	
W6UOV	p. 22, Aug 71
144-MHz power amplifiers, fm	
W4CGC	p. 6, Apr 73
144-MHz power amplifier, 10-watt solid-state (HN)	
W1DTY	p. 67, Jan 74
144-MHz power amplifier, 80-watt, solid-state	
Hatchett	p. 6, Dec 73
144-MHz transceiver, a-m	
K1AOB	p. 55, Dec 71
144-MHz transmitting converter, solid-state ssb	
W6NBI	p. 6, Feb 74
Short circuit	p. 62, Dec 74
144-MHz transverter	
K1RAK	p. 24, Feb 72
144-MHz two-kilowatt linear	
W6UOV, W6ZO, K6DC	p. 26, Apr 70
144- and 432-MHz stripline amplifier/tripler	
K2RIW	p. 6, Feb 70
220-MHz exciter	
WB6DJV	p. 50, Nov 71
220-MHz power amplifier	
W6UOV	p. 44, Dec 71
220-MHz rf power amplifier	
WB6DJV	p. 44, Jan 71
220-MHz rf power amplifier, fm	
K7JUE	p. 6, Sep 73
432-MHz amplifier, 2-kW	
W6SAI, W6NLZ	p. 6, Sep 68
432-MHz exciter, solid-state	
W1OOP	p. 38, Oct 69
432-MHz rf power amplifier	
K6JC	p. 40, Apr 70
432-MHz solid-state linear amplifier	
WB6QXF	p. 30, Aug 75
432-MHz ssb converter	
K6JC	p. 48, Jan 70
Short circuit	p. 79, Jun 70
432-MHz ssb, practical approach	
WA2FSQ	p. 6, Jun 71
432-MHz stripline tripler	
K2RIW	p. 6, Feb 70
432-MHz 100-watt solid-state power amplifier	
WA7CNP	p. 36, Sep 75
1152- to 2304-MHz power doubler	
WA9HUV	p. 40, Dec 75
1296-MHz frequency tripler	
K4SUM, W4API	p. 40, Sep 69
1296-MHz linear, high-power	
WB6IOM	p. 6, Aug 68
Short circuit	p. 54, Nov 68
1296-MHz power amplifier	
W2COH, W2CCY, W2OJ, W1IMU	p. 43, Mar 70
1296-MHz ssb transceiver	
WA6UAM	p. 8, Sep 74
2304-MHz power amplifier	
WA9HUV	p. 8, Feb 75



Whenever and wherever there's news in amateur Radio you can bet that HR REPORT is right there in the middle of it insuring that our readers are the best informed amateurs anywhere.

In just three short years HR REPORT has set an enviable record for concise, accurate reporting. Others have tried to copy us, but they were no match for the experienced steady hand that editor W9JUV and his colleagues apply to this exciting newsletter each week.

Whether it happened at the FCC or the ARRL, or if it's DX, a new product, propagation news or just a worthwhile tip, if it's news and if you should know about it then it will be in HR REPORT.

Don't put off subscribing to this exciting weekly newsletter any longer. We'll have more up to the minute news in the mail this Friday and every Friday. HR REPORT is written with you in mind — we don't want you to miss it.

ENTER MY SUBSCRIPTION TO:

- HR REPORT RENEWAL NEW
 1 YEAR \$16.00 FOREIGN \$26.00

NAME _____ CALL _____

STREET _____

CITY _____ STATE _____ ZIP _____

Send to

**ham
radio**


Greenville, NH 03048

SWAN METERS HELP YOU GET IT ALL TOGETHER


These wattmeters tell you what's going on.

With one of these in-line wattmeters you'll know if you're getting it all together all the time. Need high accuracy? High power handling? Peak

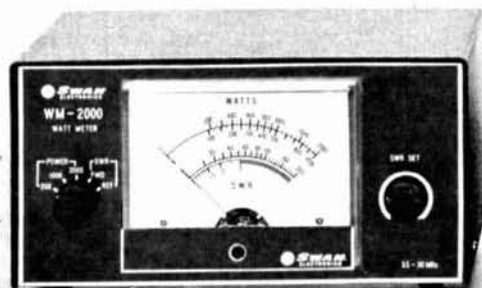power readings? For whatever purpose we've got the wattmeter for you. Use your Swan credit card. Applications at your dealer or write to us.



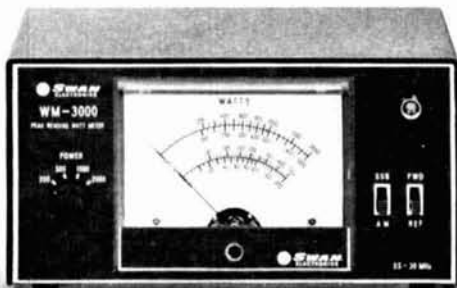WM2000 In-Line Wattmeter With Muscle. Scales to 2000 watts. New flat-response directional coupler for maximum accuracy. **\$49.95**



WM3000 Peak-reading Wattmeter. Reads RMS power, then with the flick of a switch, true peak power of your single-sideband signal. That's what counts on SSB. **\$66.95**

WM1500 High-Accuracy In-Line Wattmeter. 10% full scale accuracy on 5, 50, 500 and 1500 watt scales, 2 to 30 MHz. Forward and reflected power. Use it for trouble-shooting, too. **\$64.95**



SWAN ELECTRONICS
A subsidiary of Cubic Corporation
305 Airport Road, Oceanside, CA 92054
(714) 757-7525

(Prices FOB Oceanside, CA)

TBC

TONE ENCODER

FEATURES:

- Crystal Controlled - Digitally Synthesized Tones.
- Low Current Drain CMOS Logic.
- RFI Immune
- 16-Button Tactile Feedback Keyboard.
- Will Interface to Transceivers Using Dynamic Microphones with Only Two Wires.
- Provisions for Three Wire Interface Are Provided.
- Gold-Plated Keyboard Contacts Provided for Maximum Reliability.
- Operating Voltage Range 9-18VDC.
- Size; 2.1" x 2.1" x .250" Without Case. 2.1" x 2.1" x .312" With Case.
- 2" Square Velcro Available for Convenient Mounting - Dashboard - Sun Visor - Radio - etc.

Tone Encoder	\$34.50
Case	\$ 2.00
Velcro	\$.50

• 12-Button Tone Encoder (Case and Velcro not Available)

\$34.50

Ohio Residents Add 4.5% Sales Tax

Send Check or Money Order To:

The Barber Corporation
P. O. Box 635
Waynesville, Ohio 45068 • 513-897-2926

a NEW antenna principle

PROVEN IN EXACTING TESTS AND MANY YEARS ON THE AIR AT W₀MBH — K₀AST — KBVRM

The Little

GIANT

BEAM ANTENNA

A COMPLETELY NEW ANTENNA

Here is an ultra compact beam antenna which can be tuned to any frequency between 7.0 and 14.5 MHz. Weighing only 18 lbs. this antenna may not outperform a full sized beam but it sure will give you your share of DX and stateside contacts. Will handle 1 KW over a 100 kHz bandwidth.

- Fully weather proof
- Hi-Q, attenuates harmonics
- Mounts easily on TV masting
- Comes assembled & tested
- Figure 8 pattern

LITTLE GIANT MODEL 100X1000-40

Other models available for 10, 15 & 20 meters

KITS 10-40 \$94.50

\$149.50

Add \$3 trans.

Little Giant Antenna Labs, Box 245, Vaughnsville, Ohio 45893

Subsidiary "Apollo Products" Village-Twig Co.
419-646-3495

YOUR BEST BUY IN KITS

ANALOG-DIGI-LAB
Features 3 Regulated power Supplies. 3 Output wave forms. 8 digital level switches. 2 no bounce pulser switches. 8 LEDs with drivers. 1 AP Super strip. Easily constructed. Designed by RETS Electronic Schools.
1st time offer

\$139.00

Clock Kit (complete less case)

\$12.95

Clock Cabinet

\$6.50

or \$4.50 with purchase of clock kit.

Function Generator Kit

\$10.95

FREQUENCY COUNTER

7 Digit 0-300 MHz Freq. Counter

\$99.00

7 Digit 0-500 MHz Freq. Counter

\$139.00

8 Digit 0-30 MHz Counter with options **\$109.00**

0-300 MHz Prescaler for 8 Digit Counter **\$19.95**

0-300 MHz Prescaler with Preamp

\$29.95

0-600 MHz Prescaler for 8 Digit Counter **\$39.95**

Cabinet accessory package available for all of the above

\$24.95

Anyone of the above kits available pre-assembled for an additional \$50.00. Allow 3-4 weeks on assembled units.

HAL-TRONIX

P. O. Box 1101 • Southgate, Mich. 48195 • (313) 285-1782

Please add \$1.00 Shipping/Handling on any order under \$15.00
Send SASE for flyer. Featuring Electronic components and kits available.

DIODES				SOCKETS/PLUGS				TRANSISTORS, LEDS, etc.			
1N914	100v	10mA	.05	8-pin	pcb	.25	ww	.45	2N2222	NPN	.10
1N4004	400v	1A	.08	14-pin	pcb	.25	ww	.40	2N2907	PNP	.15
1N4005	600v	1A	.08	16-pin	pcb	.25	ww	.40	2N3906	PNP	.10
1N4007	1000v	1A	.15	18-pin	pcb	.25	ww	.75	2N3055	NPN 15A 60v	.50
1N4148	75v	10mA	.03	22-pin	pcb	.45	ww	.75	LED Green, Red, Yellow		.15
1N753A	6.2v	z	.25	24-pin	pcb	.55	ww	1.25	D.L. 747 7 seg 5/8" high		1.95
1N758A	10v	z	.25	28-pin	pcb	.35	ww	1.45	HP 276 Com-cathode .3" high		1.00
1N759A	12v	z	.25	40-pin	pcb	.50	ww	1.95	XAN72 7 seg com-anode		1.50
1N4733	5.1v	z	.25	Molex pins .01	To-3 Sockets			.25	FND 359 Red 7 seg com-cathode		1.00
1N5243	13v	z	.25	2 Amp Bridge	100-prv			1.20			
1N5244B	14v	z	.25	25 Amp Bridge	200-prv			2.50			
1N5245B	15v	z	.25								

C MOS		- T T L -									
CD4000	.25	7400	.15	7451	.25	74156	1.15	74S00	.55		
CD4001	.25	7401	.15	7453	.25	74157	.95	74S02	.55		
CD4002	.25	7402	.20	7454	.25	74161	1.25	74S03	.50		
CD4007	.35	7403	.25	7460	.25	74163	1.25	74S10	.25		
CD4009	.25	7404	.15	7470	.45	74164	.95	74S11	.45		
CD4010	.50	7405	.25	7472	.45	74165	1.50	74S20	.50		
CD4011	.25	7406	.45	7473	.35	74166	1.75	74S40	.30		
CD4012	.25	7407	.55	7474	.40	74175	.95	74S51	.45		
CD4013	.40	7408	.25	7475	.45	74176	1.25	74S64	.55		
CD4014	1.10	7409	.15	7476	.20	74180	.85	74S74	.50		
CD4015	1.10	7410	.15	7480	.65	74181	3.25	74S112	1.50		
CD4016	.45	7411	.25	7483	1.00	74182	.95	74S133	.45		
CD4017	1.10	7412	.30	7485	1.05	74190	1.75	74S151A	1.00		
CD4018	1.10	7413	.65	7486	.40	74192	1.65	74S158	.65		
CD4019	.70	7414	1.10	7489	2.75	74193	.85	74S194	1.50		
CD4020	.85	7416	.25	7490	.40	74195	.95				
CD4023	.25	7417	.50	7491	1.15	74196	1.50	74LS00	.45		
CD4024	.95	7420	.15	7492	.95	74197	1.25	74LS01	.45		
CD4025	.35	7426	.40	7493	.60	74198	2.35	74LS02	.45		
CD4026	1.95	7427	.45	7494	1.25	74367	.85	74LS04	.55		
CD4027	.75	7430	.20	7495	.85			74LS08	.45		
CD4030	.45	7432	.45	7496	.95	74H00	.25	74LS09	.45		
CD4033	1.95	7437	.45	74100	1.85	74H04	.25	74LS10	.45		
CD4040	1.35	7438	.20	74107	.45	74H22	.40	74LS11	.45		
CD4044	.95	7440	.25	74121	.40	74H52	.15	74LS20	.50		
CD4046	1.50	7441	1.15	74122	.55	74H53J	.25	74LS32	.55		
CD4049	.80	7442	.65	74123	.55	74H72	.55	74LS40	.55		
CD4050	.85	7443	.95	74125	.45	74H101	.75	74LS42	1.75		
CD4066	1.35	7444	.95	74132	1.35	74H103	.75	74LS74	.95		
CD4069	.30	7445	.95	74141	1.30	74H106	.95	74LS90	1.30		
CD4071	.35	7446	1.20	74150	1.00			74LS93	1.65		
CD4082	.45	7447	1.20	74151	.95	74L00	.35	74LS107	1.50		
75108A	.35	7448	1.20	74153	.95	74L02	.35	74LS164	1.90		
75110	.35	7450	.25	74154	.75	74L03	.45				
75491	.50					74L10	.35				
75492	.50					74L30	.45				

MEMORY, CLOCKS		LINEARS, REGULATORS, etc.							
74S188(8223)	3.00	MCT2	.95	LM311	1.35	LM340T-15	1.65	LM723	.45
8080	26.50	8038	3.95	LM320K5	1.65	LM340K-12	2.15	LM725	1.95
MM1702A	10.50	LM201AH	.75	LM320K12	1.65	LM340K-15	2.15	LM739	1.50
MM5314	3.95	LM301AH	.55	LM320T12	1.65	LM340K-24	2.15	LM741	.25
MM5316	4.95	LM308AH	1.00	LM320T15	1.65	LM373	1.95	LM747	1.10
2102-1	1.95	LM309H	.65	LM339	1.65	LM380	1.55	LM1307	1.25
2102L1	2.25	LM309K	.90	7805	1.00	LM709	.30	LM1458	.95
TMS6011	9.95	LM310	1.15	LM340T-12	1.65	LM711	.45	LM3900	.65
TR 1602A	6.95							LM75451	.65
INTEGRATED CIRCUITS UNLIMITED									
7889 Clairemont Mesa Blvd. • San Diego, CA 92111 • (714) 278-4394									
All orders shipped prepaid					No minimum				
Open accounts invited					COD orders accepted				
Discounts available at OEM Quantities									
California Residents add 6% Sales Tax									
24 Hour Phone (714) 278-4394					MasterCharge / BankAmericard				
								NE555	.50
								NE556	1.10
								NE565	1.15
								NE566	1.95
								NE567	1.35
								SN72720	.35
								SN72820	.35



Tropical Hamboree ARRL CONVENTION Miami, Fla.

**JANUARY 22-23,
1977**

Pre-Registration \$2.00

**For
Special Hotel Rates
and
Further Information**

Write:

**P.O. Box 520073, BISCAYNE ANNEX
MIAMI, FLA. 33152**

"MINI-PORTABLE" DIPOLE KIT

Mounts vertical or horizontal - Electrical 1/2 wave length
For mast, windowsill, boat, mobile home, or auto
Quick erect - Up to 500 watt PEP. Hi-Q resonators
Tuneable tip rod - 15' approximately length
40 or 20 meter band models

\$39.95

MOBILE
* \$8.95
12 ME



* **BASE**
\$6.95
12 BE



ENCLOSURES

* **Wired with clear, easily lighted W.E. pad
(ready to use) \$49.95**



16 Digit Min. Encoder
Wired w/Motorola Chip
16MPW \$39.95
16MPWE (enclosed) \$49.95

All prices PREPAID shipping Cont'l USA

KING PRODUCTS

(Dealer Inquiries Invited)

P. O. BOX A, LOMITA, CA 90717 • (213) 534-4402



GREGORY ELECTRONICS
*The FM Used
Equipment People.*



FE53:
W 9",
H 4", D 16"

150-170MHz MOBILE UNITS

GENERAL ELECTRIC T.P.L.

Transistorized Progress Line, FE53JA6,
Front Mount, 150-174 MHz, 12 volt, 35 watts,
fully solid state receive, 4 tubes in transmitter,
fully narrow band, complete with accessories,
shipping weight 50 lbs.

Regular ~~\$168~~
NEW LOW PRICE \$118.

(Schematic available on request)



GREGORY ELECTRONICS CORP

245 Rt. 46, Saddle Brook, N.J. 07662
Phone: (201) 489-9000

OLD TESTAMENT

“**T**herefore the Lord himself shall give you a sign; Behold, a virgin shall conceive, and bear a son, and shall call his name Immanuel (which means God with us).”

Isaiah 7:14 740-687 BC

But thou Bethlehem, though thou be little among the thousands of Judah, from you shall come forth one who is to be ruler in Israel, whose origin is from old, from ancient days.

Micah 5:2 740 BC

NEW TESTAMENT

“... the angel Gabriel was sent from God to a city of Galilee, to a virgin betrothed to Joseph, of the house of David; and the virgin's name was Mary... The angel said to her “Do not be afraid Mary, for you have found favor with God. And behold, you will conceive in your womb and bear a son, and you shall call his name Jesus.”

Luke 1:27-31 70-90 AD

King Herod was troubled and inquired where the Christ was to be born. They told him in Bethlehem of Judea; for so it is written by the prophet (Micah).

Mathew 2:4-5 60-70 AD

Historical evidence clearly points to Jesus as the man God, who fulfills the literal prophecies of Isaiah and Micah within 800 years. The same God who chose the Virgin Mary to bear Jesus and who chose Bethlehem for the birthplace reveals himself in holy scripture today. We thank him for the birth of Christ this Christmas, 1976.

Dentron
Radio Co., Inc.

2100 Enterprise Parkway
Twinsburg, Ohio 44087
(216)425-3173

CASH FOR 2-WAY FM RADIO
MOTOROLA, GE, RCA, ETC. EQUIPMENT
MOBILES, BASES, PORTABLES, MOBILE-
TELEPHONES, REPEATERS, REMOTE CONTROLS,
TONE EQUIPMENT, 2-WAY TEST EQUIPMENT
Operational Units Only
Commissions/Finders Fees
CAL-COM SYSTEMS, INC.
701-51A KINGS ROW, SAN JOSE, CALIF. 95112
Telephone 24 Hours 408/998-4444

SSB & CW Filters for Superior reception through QRM & QRN. Built in AC supply & AF Power Amp. SSB filters are for CB or Ham use.
DE-102A SSB filter \$51.95
DE-103A CW & SSB \$59.95
DE-104A CW filter \$49.95
Other filters & products are available.
DYNAMIC ELECTRONICS, Box 896, Hartselle, AL 35640

VHF/UHF CONVERTERS

PREAMPS
Ten meters through 432 MHz. A post card will bring our full 1976 Catalog.
JANEL laboratories
3312 S.E. VAN BUREN BLVD.
CORVALLIS, OREGON 97330
Telephone: 503-757-1134

IRON POWDER TOROIDS

CORE SIZE	MIX 2 5-30MHz u = 10	MIX 6 10-90MHz u = 8.5	MIX 12 60-200MHz u = 4	SIZE OD (in.)	PRICE USA \$
T-200	120			2.00	3.25
T-106	135			1.06	1.50
T-80	55	45		.80	.80
T-68	57	47	21	.68	.85
T-50	51	40	18	.50	.55
T-25	34	27	12	.25	.40

RF FERRITE TOROIDS

CORE SIZE	MIX Q1 u = 125	MIX Q2 u = 40	SIZE OD (in.)	PRICE USA \$
F-240	1300	400	2.40	6.00
F-125	900	300	1.25	3.00
F-87	600	190	.87	2.05
F-50	500	190	.50	1.25
F-37	400	140	.37	1.25
F-23	190	60	.23	1.10

Charts above show uH per 100 turns. Use iron powder toroids for tuned circuits. Use ferrite toroids for broadband transformers. Q1 for .1-70 MHz, Q2 for 10-150 MHz.

Ferrite beads 20-500 MHz (fit #18 wire) \$2.00 Doz. Wideband chokes 20-500 MHz (Z=850 ohms) 95¢ Ea. Specify core size and mix. Pack and ship 50¢ USA and Canada. Air parcel post delivery worldwide \$2.00; 6% tax in Calif.; Fast service; Cores shipped from stock via first class mail or air. Send for free brochure.


PALOMAR ENGINEERS
BOX 455, ESCONDIDO, CA 92025

TOUCH TONE PADS

WESTERN ELECTRIC MODEL NO. 35N1A

- COMPLETE WITH L.C. TYPE ENCODER ELECTRONICS
- DIAGRAM FURNISHED

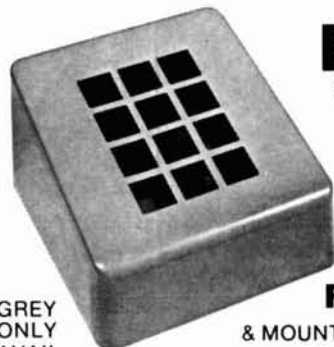Repeater • Computer • Phone • Security • Etc.



GREY ONLY AVAILABLE.

NEW
\$19.50

POSTPAID

OFFER ENDS 2-28-77

FREE CASE

& MOUNTING WITH EACH PAD

SEND \$19.50 TO:

DOLLAR VALUE ELECTRONIC SUPPLY

20748-E PLUMMER STREET, CHATSWORTH, CA 91311
California Residents Add 6% Sales Tax



Advertisers check-off

... for literature, in a hurry — we'll rush your name to the companies whose names you "check-off"

Place your check mark in the space between name and number. Ex: Ham Radio ___ 234

INDEX

Adva	265	Kenso	394
Aldelco	347	Kenwood *	
Amcomm	500	Kester Solder	492
Antenna Spec.	010	King	077
Supermarket	404	Klaus	430
Apollo	011	Lin	451
Apron	380	Little Giant	011
Atlantic *		Logic Systems	493
Atlas	198	Lyle	373
Barber	383	MFJ	082
Barry *		MHz	415
R. H. Bauman	017	Madison *	
Bird	018	Matric	084
Budwig	233	McKay Dymek	511
Bullet	328	Midland	086
Bunker Ramo	517	Mini Labs	441
Cal-Com	282	Mini Products	395
CBS	501	Monolith *	
CFP	022	M-Tech	357
Cleng	465	National Multi	396
Comm. Eng.	489	N. R. I.	397
Comm. Spec.	330	National Semi	323
Computer Room	502	New-Tronics	171
Cont. Spec.	348	Nexus	454
Cornell Dubilier	241	Northshore	296
Crecent Wire	490	NuData	455
Cush Craft	035	Optoelectronics	352
D-D	269	Orlando Hamfest *	
Data Signal	270	Palomar	093
Davis	332	Partridge	439
Dentron	259	Piezolectric	513
Digital	503	Poly Paks	096
Disc-Cap	449	Porta Pak	274
Dollar Value	406	RP	098
Drake	309	Callbook	100
Dynamic	041	Ramsey	442
Dynascan	516	Regency	102
EPA	515	Rohn	410
E. T. O. *		SST	375
Elect. Dist.	044	Sandlin	471
Electrospace	407	SAROC *	
ELPROCON	301	Scott	519
Erickson	047	Semiconductor	
59+	429	Surplus	512
Franke	289	Sherwood	435
Genave	168	Simclair	514
Gilfer	207	SOTA	506
Gray	055	Space	107
Gregory	201	Specialty Comm. Systems	318
Hal	057	Spectronics	191
Hal-Tronix	254	Spec. Int.	108
HamLine	466	Standard	109
Ham Radio	150	Swan	111
Ham Center	491	TPL	240
HR Horizons	150	Tec Kan	507
Hamtronics	246	Tel. Equip.	496
Heath	060	Timekit	482
Henry	062	Trevor	474
Hewlett-Packard	281	Ten Tec	
Hildreth	283	Hamboree *	
Hosfelt	390	VHF Eng.	121
Hufco	403	VHF Signal	497
Hy-Gain	064	Vanguard *	
Icom	065	Varian	043
Info-Tech	351	Wawasee	498
Int. Circuits	518	Webster	
Int'l Xtal	066	Comm.	423
Jade	509	Webster Radio	225
James	333	Weinschenker	122
Jan	067	Wilson	123
Janel	068	Yaesu	127
K-Enterprises	071		

*Please contact this advertiser directly.

Limit 15 inquiries per request.

December 1976

Please use before January 31, 1977

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME.....
CALL.....
STREET.....
CITY.....
STATE..... ZIP.....

R-X NOISE BRIDGE



- ✓ Learn the truth about your antenna.
- ✓ Find its resonant frequency.
- ✓ Adjust it to your operating frequency quickly and easily.

If there is one place in your station where you cannot risk uncertain results it is in your antenna.

The Palomar Engineers R-X Noise Bridge tells you if your antenna is resonant or not and, if it is not, whether it is too long or too short. All this in one measurement reading. And it works just as well with ham-band-only receivers as with general coverage equipment because it gives perfect null readings even when the antenna is not resonant. It gives resistance and reactance readings on dipoles, inverted Vees, quads, beams, multiband trap dipoles and verticals. No station is complete without this up-to-date instrument.

Why work in the dark? Your SWR meter or your resistance noise bridge tells only half the story. Get the instrument that really works, the Palomar Engineers R-X Noise Bridge. Use it to check your antennas from 1 to 100 MHz. And use it in your shack to adjust resonant frequencies of both series and parallel tuned circuits. Works better than a dip meter and costs a lot less. Send for our free brochure.

The price is \$39.95 and we deliver postpaid anywhere in U.S. and Canada. California residents add sales tax.

Italy write i2VTT, P.O. Box 37, 22063 Cantu. Elsewhere send \$42.00 (U.S.) for air parcel post delivery worldwide.

Fully guaranteed by the originator of the R-X Noise Bridge. ORDER YOURS NOW!

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CA 92025

Phone: (714) 747-3343

Advertisers Index

Adva Electronics	98
Aldelco	109
Amcomm, Inc.	95
Antenna Specialists Co.	63
Antenna Supermarket	118
Apollo Products	88
Apron	114
Atlantic Research	98
Atlas Radio	57, 114
Barber Corp.	138
Barry	81
R. H. Bauman	114
Budwig Mfg. Co.	118
Bullett	83
Cal-Com Systems, Inc.	141
CBS Enterprise	122
CFP Communications	114
Cleng Electronics	110
Communications Engineering	111
Communications Specialists	94, 143
The Computer Room	55
Continental Specialties	75
Crecent Wire & Cable, Inc.	109
Cush Craft	31
D-D Enterprises	102
Data Signal, Inc.	112
Davis Electronics	90
Dentron Radio Co.	7, 141
Digital Concepts Corp.	96
Disc-Cap	114
Dollar Value Elec. Supply	141
Drake Co., R. L.	25
Dynamic Electronics	141
Ehrhorn Technological Operations, Inc.	40
Electronic Distributors	109, 126
Electrospace	102
ELPROCON	118
Erickson Communications	104
Five Nine Plus	126
Fred Franke, Inc.	104
General Aviation	91
Gilfer Associates	108
Gray Electronics	104
Gregory Electronics	140
Hal Communications Corp.	2
Hal-Tronix	139
HamLine Electronics	110
Ham Radio	78, 126, 134, 138
Ham Radio Center	79
Ham Radio Horizons	130
Hamtronics, Inc.	112
Heath Co.	17
Henry Radio Stores	Cover II
Hosfelt Electronics	112
Hufco	84, 92, 115, 126
Hy-Gain Electronics	69
Icom	5
Info-Tech	56
Integrated Circuits Unlimited	139
International Crystal	144
Jade Company	106
James Electronics	36, 105
Jan Crystals	141
Janel Labs	141
K-Enterprises	94
Kenso Communications, Inc.	112
Trio-Kenwood Corp.	9, 71-74
Kester Solder	90
King Products	140
Klaus Radio	84
Lin Corporation	113
Little Giant Antenna	139
Logic Systems, Inc.	122
Lyle Products	110
MFJ Enterprises	1
MHz Electronics	103
Madison Electronics Supply	111
Matric	113
McKay Dymek Company	115
Midland International	99
Mini Labs Industries	122
Mini Products	112
Monolith	118
M-Tech	94
National Multiplex Corporation	65
National Radio Institute	106
New-Tronics Corporation	61
Nexus Trading Company	98
Northshore RF Technology	102
NuData Electronics	122
Optoelectronics	122
Orlando Hamfest	100, 114, 141, 142
Palomar Engineers	122
Partridge (HR) Electronics	100
Poly Paks	96
Porta Pak	108
RP Electronics	109, 118
Radio Amateur Callbook	70
Ramsey Electronics	76
Regency Electronics	80
Rohn	122
SST Electronics	92
Sandlin Electronics Engineering	8
SAROC	126
Scott Communications	110
Semiconductor Surplus	112
Sherwood Engineering	64
SOTA Industries	118
Space Electronics Corp.	88
Specialty Communications Systems	89
Spectronics	35
Spectrum International	107, 115
Standard Communications	50, 51, 108, 139
Swan Electronics	96
TPL Communications	97
Tec Kan Inc.	118
Telephone Equipment Co.	93
Ten Tec	140
Tropical Hamboree	85
VHF Engineering, Div. of Brownian	118
VHF Signal Co.	110, 122
Vanguard Labs	Cover IV
Varian, Eimac Division	45
Wawasee Electronics	108
Webster Communications	113
Webster Radio	106
Weinschenker	46, 47
Wilson Electronics	Cover III
Yaesu Electronics Corp.	

ME-3 microminiature tone encoder

Compatible with all sub-audible tone systems such as: Private Line, Channel Guard, Quiet Channel, etc.

- Powered by 6-16vdc, unregulated
- Microminiature in size to fit inside all mobile units and most portable units
- Field replaceable, plug-in, frequency determining elements
- Excellent frequency accuracy and temperature stability
- Output level adjustment potentiometer
- Low distortion sinewave output
- Available in all EIA tone frequencies, 67.0 Hz-203.5 Hz
- Complete immunity to RF
- Reverse polarity protection built-in

\$29.95 each

Wired and tested, complete with K-1 element

communications specialists

P. O. BOX 153
BREA, CALIFORNIA 92621
(714) 998-3021


K-1 FIELD REPLACEABLE,
PLUG-IN, FREQUENCY
DETERMINING ELEMENTS

\$3.00 each

for the experimenter!

INTERNATIONAL CRYSTALS & KITS

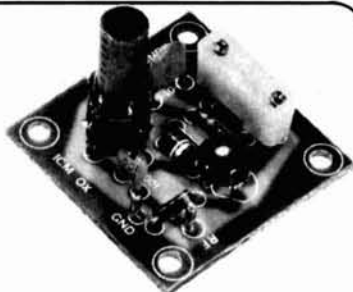OSCILLATORS • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



OX OSCILLATOR

Crystal controlled transistor type. 3 to 20 MHz, OX-Lo, Cat. No. 035100. 20 to 60 MHz, OX-Hi, Cat. No. 035101. Specify when ordering.

\$3.95 ea.



MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 30 to 170 MHz range. Harmonics of the OX or OF-1 oscillator are used for injection in the 60 to 179 MHz range. 3 to 20 MHz, Lo Kit, Cat. No. 035105. 20 to 170 MHz, Hi Kit, Cat. No. 035106. Specify when ordering.


\$4.50 ea.



PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX or OF-1 oscillator. Outputs up to 200 mw, depending on frequency and voltage. Amplifier can be amplitude modulated. 3 to 30 MHz, Cat. No. 035104. Specify when ordering.


\$4.75 ea.

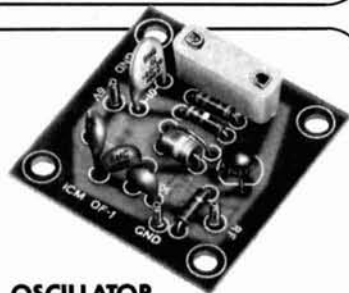

OF-1 OSCILLATOR

Resistor/capacitor circuit provides osc over a range of freq with the desired crystal. 2 to 22 MHz, OF-1 LO, Cat. No. 035108. 18 to 60 MHz, OF-1 HI, Cat. No. 035109. Specify when ordering.


\$3.25 ea.

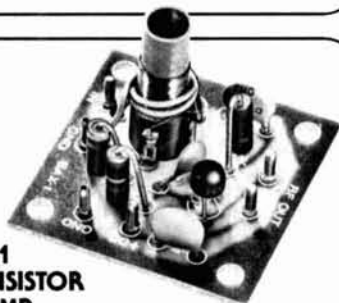

SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive the MXX-1 Mixer. Single tuned input and link output. 3 to 20 MHz, Lo Kit, Cat. No. 035102. 20 to 170 MHz, Hi Kit, Cat. No. 035103. Specify when ordering.

\$4.50 ea.

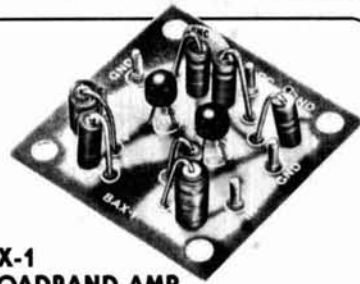

BAX-1 BROADBAND AMP

General purpose amplifier which may be used as a tuned or untuned unit in RF and audio applications. 20 Hz to 150 MHz with 6 to 30 db gain. Cat No. 035107. Specify when ordering.

\$4.75 ea.



.02% Calibration Tolerance EXPERIMENTER CRYSTALS (HC 6/U Holder)

Cat. No.	Specifications	
031080	3 to 20 MHz — for use in OX OSC Lo	\$4.95 ea.
	<i>Specify when ordering</i>	
031081	20 to 60 MHz — For use in OX OSC Hi	\$4.95 ea.
	<i>Specify when ordering</i>	
031300	3 to 20 MHz — For use in OF-1L OSC	\$4.25 ea.
	<i>Specify when ordering</i>	
031310	20 to 60 MHz — For use in OF-1H OSC	\$4.25 ea.
	<i>Specify when ordering.</i>	

Shipping and postage (inside U.S., Canada and Mexico only) will be prepaid by International. Prices quoted for U.S., Canada and Mexico orders only. Orders for shipment to other countries will be quoted on request. Address orders to:

M/S Dept., P.O. Box 32497,
Oklahoma City, Oklahoma 73132.



International Crystal Mfg. Co., Inc.

10 North Lee
Oklahoma City, Oklahoma 73102


Advanced Communications Equipment from the World's Leader in Amateur Communications



Left to right – FRG-7, Solid State Synthesized Communications Receiver • FR-101 Digital, Solid State Receiver • SP-101B, Speaker • FR-101, Digital Solid State Receiver • FL-101, 100 W Transmitter • FL-2100B, 1200 W PEP Input Linear Amplifier



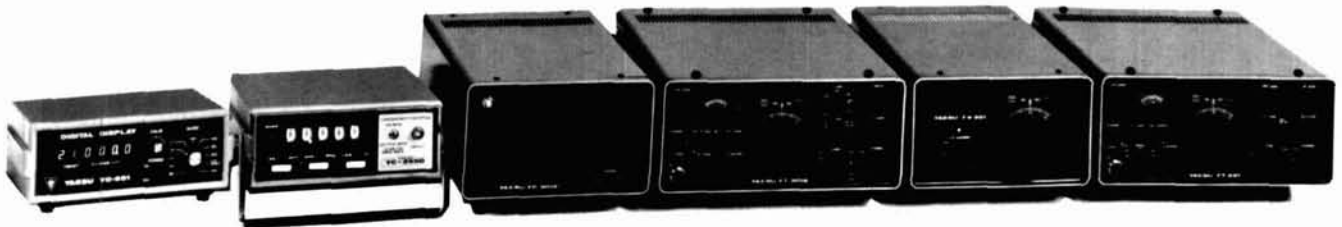Left to right – FT-620B, 6 Meter Transceiver • YP-150, Dummy Load Wattmeter • YO-100, Monitor Scope • FTV-250, 2 Meter Transverter • FTV-650, 6 Meter Transverter • FV-101B, External VFO • FT-101E 160-10 M Transceiver



Left to right – YC-601, Digital Frequency Display • YC-355D, Frequency Counter • FP-301, AC Power Supply • FT-301S Digital, All Solid State Transceiver • FV-301, External VFO • FT-221, 144-148 All Solid State All Mode Transceiver



YD-844
Dynamic Mike

Over 150 licensed radio amateurs employed at Yaesu proudly offer you the most diversified communications product line available: SSB, CW, AM, RTTY, and FM equipment - all designed for today's active amateur.



QTR-24
World Clock



YAESU *The radio.*

Yaesu Electronics Corp., 15954 Downey Ave., Paramount, CA 90723 • (213) 633-4007
Yaesu Electronics Corp., Eastern Service Ctr., 613 Redna Ter., Cincinnati, OH 45215 • (513) 772-1500

Merry
Christmas
from the
EIMAC
Division
of Varian.

The radio amateurs of EIMAC, CTC,
and other Varian Divisions wish you
a happy holiday season.

WA6ABQ	WB6GVP	W6PO
KH6ADR	WA6GXB	WB6QXF
KH6AMZ	WB6GYJ	WA1RIT
W6AVJ	WN6HBQ	W6SAI
W6AY	WA6HDD	W6SKP
WA6BAN	W6HOC	K6SRG
WB6BBS	W6IOH	W6SXA
WB6BBV	W6JFV	W6TC
WB6CEZ	WA6JQC	K6TNK
WB6CFY	W6KEV	K6TNY
K6BCM	W6KGH	WB6TOA
WA6BII	W6KHO	W6UF/7
W6CHE	W6KM	W6UMX
K6DC	WA6MUG	WB6UQU
W6DJI	WA6KOP	W2UXY
W6DOZ	WB6LAM	W6VW
K6DRN	K6LCO	W6VYH
W6EDE	WN6LEE	WA6WHC
WA6EHA	WA6LSY	W6WLD
WB6EXM	W1LTS	W6YSX
W6FBR	K6MA	WA6ZAX
WB6FFC	WA6MAC	W1ZLA
WA6FOU	W6MAG	W6ZLB
WB6FUI	EI2MC	W6ZO
WB6FUZ	WA6MLM	VK3ZSJ
WB6FVQ	W6MZ	W6ZVV
W1GKF	WA6NYB	W6ZYH
W1GKS	W6ODT	WA7MLK/6
W3GNQ	W6PHS	4X4JE

Varian, EIMAC Division,
301 Industrial Way, San Carlos,
California, 94070. (415) 592-1221.

