

HOW ROCKS MAKE YOUR RADIO GO

Elementary Electronics

MAY-JUNE 75¢

BASIC COURSE

Understanding
Transmitters &
Receivers

FIRST ELECTRONIC TRANSPLANT!

SUPERHET REGEN RECEIVER

2 tubes! • 3 bands! • 1.7 to 30 MHz coverage!



Complete plans on page 35

Unlocking the Secrets of the Mysterious MV


PRESS THE RED BUTTON

Our DALLY LIGHTER

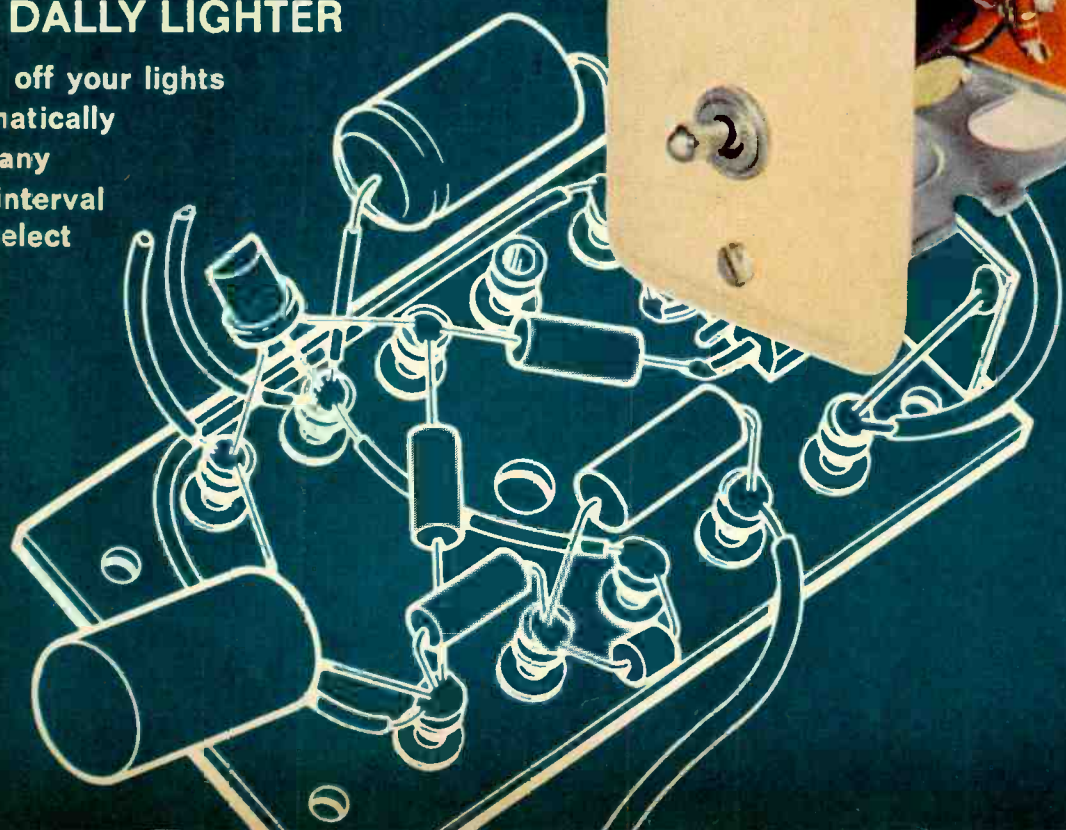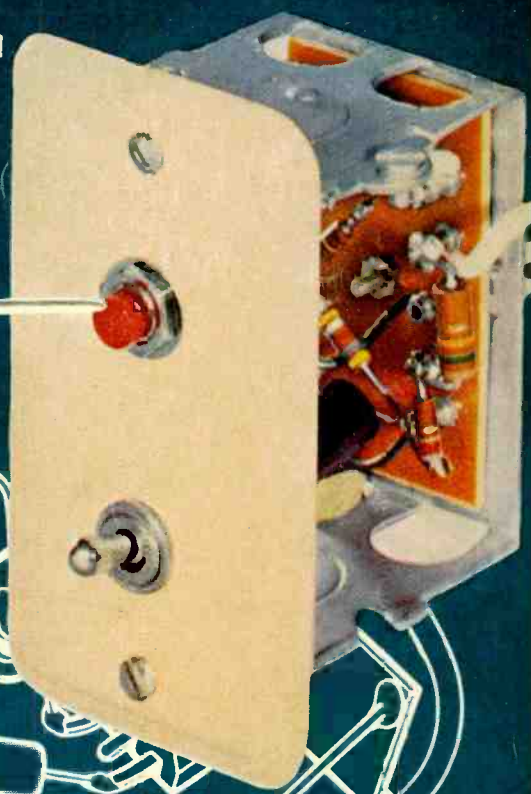Turns off your lights
automatically
after any
time interval
you select



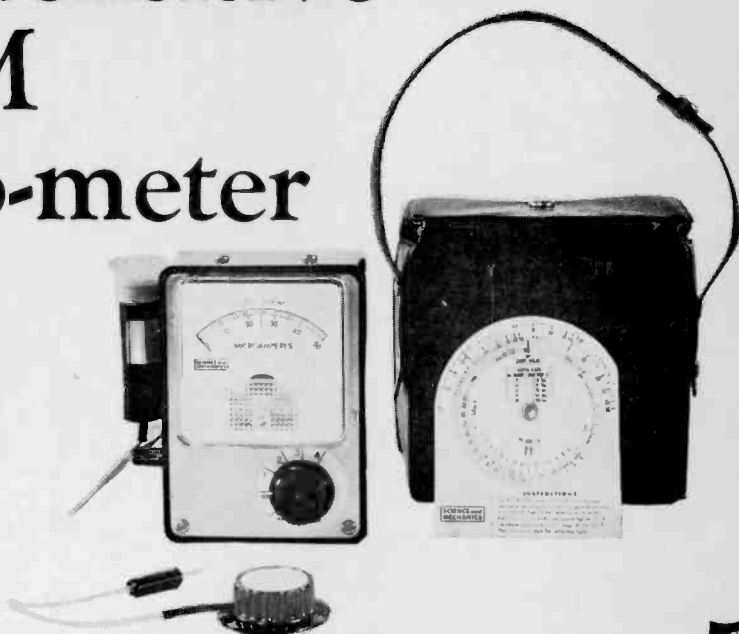The new & improved supersensitive S & M photo-meter



now better than ever!



Every photographer knows that the high quality of his photos depends on the accuracy of his equipment. Here is a precision instrument that meets the highest standards of any meter available. MODERN PHOTOGRAPHY says, "This is certainly one of the most unusual, most versatile and most sensitive exposure meters at any price today." U. S. CAMERA wrote "It is as sensitive as anything on the market. It's so adaptable—those 4 separate ranges of sensitivity have the effect of spreading the meter's scale."

Now, this S & M is better than ever! A new design feature, the use of plug and jack connections for probes, makes interchangeability of probes possible. Users of this most outstanding Light Meter can now easily find out what sensitivity values of probes are best suited for their specific applications. A new plastic cap protects the probe and permits diffused light to be read with the cap on (the probe is normally used to take readings with the cap removed). Another improvement is the battery test circuit, which indicates instantly the condition of the mercury cell that powers the unit.

This Photo Meter is utilized extensively in Photo Labs, Physics and Research Labs, Hospitals, High Schools, Universities and many industries. It is successfully used with movie or still cameras, microscopes and telescopes. For Photomicrography it is a MUST! It can even be set up for use as a densitometer.

The S & M Supersensitive Photo Meter uses the newest Clairex Corp. CL-505L Cadmium Sulfide Light Cell to

measure light levels from twilight to bright sunlight at ASA speeds of 3 to 25,000. A new $\frac{1}{8}$ " high eased type probe is now available as an accessory. The Computer gives F stops from .7 to 90; lists exposure time from 1/15,000 sec. to 8 hours; 4 range selection; EV-EVS-LV settings; weighs only 10 ounces.

*Order your S & M Supersensitive Photo Meter today.
Complete with attractive carrying case
and exposure computer.*

\$36.95 No. 102—with carrying case and Exposure Computer	\$2.00 carrying case only	Additional Exposure Computer	\$2.00
		Easel Probe	\$7.50


SCIENCE & MECHANICS—INSTRUMENTS DIVISION/229 Park Avenue South/New York, N. Y. 10003
Enclosed is \$..... Please send me the new S&M Supersensitive Photo Meter. I understand that if I am not completely satisfied, I may return the meter within 10 days for a complete refund.

- No. 102—\$36.95 with carrying case Carrying case only—\$2.00 Easel Probe \$7.50
 Additional Exposure Computer—\$2.00

Add 10% for Canadian and foreign order. New York City residents add 5% for N.Y.C. sales tax.

Name _____ (PLEASE PRINT)
Address _____
City _____ State _____ Zip Code _____

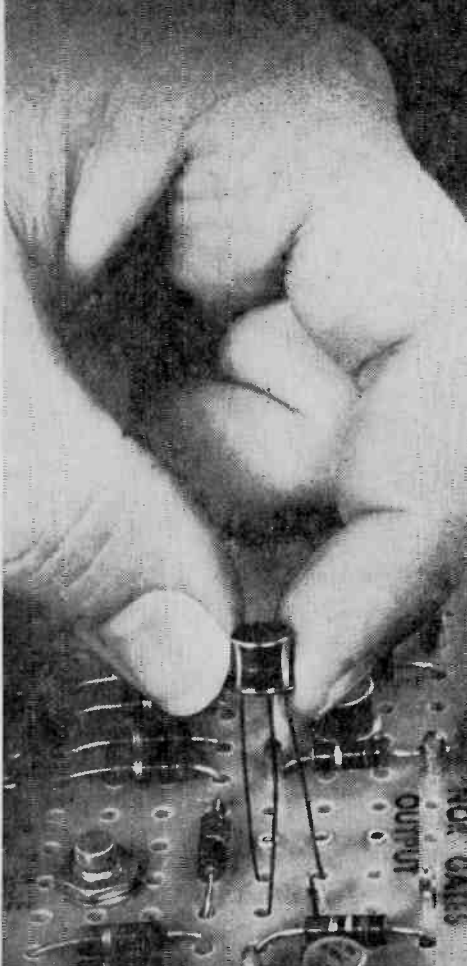Without NTS training you've only scratched the surface in electronics...



NTS digs deep into electronics. Proof? Look at the close-up at the left. It's the first transistorized digital computer-trainer ever offered by a home study school.

Fascinating to assemble, the NTS Compu-Trainer® introduces you to the exciting world of computer electronics. Its design includes advanced solid-state NOR circuitry, flip-flops, astable multivibrators and reset circuits. Plus two zener and transistorized voltage-regulated power supplies. The NTS Compu-Trainer can perform 50,000 operations per second, and is only one of many ultra-advanced kits we offer to give you incomparable, in-depth career training.

NTS... THE FIRST HOME STUDY SCHOOL TO OFFER LIVE EXPERIMENTS WITH INTEGRATED CIRCUIT KITS

With NTS Project-Method Home Training, you build a computer sub-system using the new, revolutionary integrated circuits. Each one, smaller than a dime, contains the equivalent of 15 resistors and 27 transistors.

With Project-Method, kits are carefully integrated with lesson material. All our kits are real equipment—not school-designed versions for training only. Project-Method was developed in our giant resident school... and proven effective for thousands of men like yourself. It's the practical-experience approach to learning. Gets you going in a hurry!




■ COMMUNICATIONS

This Transceiver is included in Communications courses. It's yours to build... to easily prepare for F.C.C. License exam... To become a fully-trained man in communications.



■ 25" COLOR TV

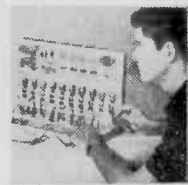Included in Color TV servicing courses. Building this advanced receiver gets you deep into color circuitry—advances you into this profitable field of servicing—the easy way. Color is the future of television, and your future, too!



■ INDUSTRIAL & COMPUTER ELECTRONICS

New ideas, new inventions, are opening whole new fields of opportunity. Electronic control systems, computers, are being applied to great numbers of manufacturing processes every day. We train you for this new field, fast! With advanced control systems devices, a new 5" oscilloscope, and the NTS Compu-Trainer. Modern, quick and easy training prepares you to enter this brand-new world like a pro.



GET THE FACTS! SEE ALL NEW KITS AND COURSES OFFERED IN THE NEW NTS COLOR CATALOG. SEND THE CARD TODAY! No obligation. No salesman will call.

Classroom Training At Los Angeles. You can take classroom training at Los Angeles. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training. Check box on coupon.

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 So. Figueroa Street Los Angeles, Calif. 90037

APPROVED FOR VETERANS



Accredited member:
National Home Study Council
National Association of
Trade and Technical Schools.





elementary Electronics

Dedicated to America's Electronics Hobbyists

- ☆
- ☆
- ☆
- ☆
- ☆

SPECIAL CONSTRUCTION PROJECTS

- 35 Build the First Electronic Transplant—*put the hearts of two great receiver circuits on one chassis*
- 57 Dally Lighter—*it lights your path and goes out after you do*

SPECIAL THEORY FEATURES

- 31 The Rocks in Your Radio—*there's more than crystals that make your rig go*
- 67 Clamp-on to Current—*there's an unique ammeter without probes that never touches the circuit it meters*
- 71 Basic Course, Part VIII—*Understanding Radio Transmitters and Receivers*
- 95 Unlocking the Secrets of the Mysterious MV—*discover how a this-or-that circuit flips the state of the art*

SWL AND DX FEATURES

- 9 DX Central Reporting
- 41 What Is Your FAC-QRP?—*just how good are you at hearing the impossible*
- 61 Return of the Radio Pirates—*kilocycle cops take to the sea and air*

AS OUR LAB SEES IT

- 65 Allied Radio Model A-2515 Communications Receiver
- 86 Unimetrics Multi-Band Portable Receiver
- 93 H. H. Scott Model LR-88 AM/FM/FM-Stereo Receiver

SOME MORE CONSTRUCTION

- 43 Soldering Iron+Know-How=Hot Receiver—*how home-brew modifications pep up a pooped receiver*
- 49 Vari-Tone Buzzer—*let your ears tell you when the circuit is completed*

ELECTRONICS IN THE NEWS

- 46 Copper's UN—*police get their ticket for radio school*
- 60 Make a Right at the Next Computer
- 90 Proof of the Pudding Is in the Testing—*consumer snoops check the products we buy*
- 101 Audible Iron Finder

ON THE LIGHT SIDE

- 30 It's the Law—*cartoon page*
- 70 A New Start for Homer Hackleby—*watch out, Fu Manchu!*

THE REGULARS

- 6 Random Noise—*editorial chit-chat*
- 11 NewScan—*misfit news that's fit to print*
- 16 Hey, Look Me Over—*the "what's new" products column*
- 22 Literature Library—*info for the asking*
- 24 En Passant—*chess column for beginners*
- 56 e/e Etymology—*words, words, words*



Cover photo
by
Leonard
Heicklen

AUTHORS IN THIS ISSUE

Len Buckwalter—K1ODH/KQA5012, John W. Collins, John P. Dixon, Herb Friedman—W2ZLF/KBI9457, Charles Getts, Charles Green—W6FFQ, Joe Gronk, Don Jensen, Jim Kyle—K5JKX, Ron Michaels, R. E. Schemel, Jack Schmidt, James Robert Squires, C. M. Stanbury II, Sol Wexton, and the ELEMENTARY ELECTRONICS' Editorial Staff.

☆
Cover
Highlights



SEE YOUR MUSIC IN DAZZLING ACTION with




**Dramatic New Breakthrough
In Audio-Visual Enjoyment**

Now you can have a thrilling psychedelic "see-in" right in your own home, club, school or business—in fact—anywhere you want to add sensational "mod" effects. Colored light beams dance and prance, whirl and swirl in perfect time with the music—each individual note creating its own unique twisting, radiating shape. Adds a spectacularly wide, new dimension to the world of music and entertainment. Combines electronics, science and art with dramatic results. Attaches in seconds to your radio, tape recorder, hi-fi, or stereo with two alligator clips. Can be used on small screens, large walls, stages and whole auditoriums. Build your own MusicVision™ with low-cost Do-It-Yourself Kit. Loads of fun! Fast! Easy! All you need is a light source. If you don't

have one, the versatile Edmund 35mm 500 Watt Projector is a terrific bargain. All kinds of other uses too—set up to accept motorized accessories. Also available in 15"x15"x27" Walnut Cabinet Model. Tube Unit, or 8" and 12" Sets which include encased 8" or 12" Motionizer, Color Wheel and set of apertures for use with your own 35mm projector. Large 12" set provides fabulous effects for commercial applications. Order by stock number listed below. Money-back guarantee. Complete information in new catalog. If you want additional details now, send 25¢ in coin for fully illustrated, 16-page Booklet No. 9096EK, "Introduction to MusicVision™".

* Patent pending.

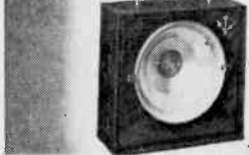- 8" DO-IT-YOURSELF KIT**—Stock No. 71,009EK \$22.50 Postpaid
- 8" SET (Motionizer, color wheel, apertures)** Stock No. 71,030EK \$45.00 Postpaid
- 12" SET (Same as above w/larger Motionizer)** Stock No. 71,032EK. \$57.50 Postpaid
- WALNUT VENEERED CABINET MODEL:** Stock No. 85,181EK \$99.50 F.O.B.
- EDMUND 500 Watt 35mm PROJECTOR**—Stock No. 71,057EK \$24.50 Postpaid



TOP-QUALITY LOW-COST STROBE

Create spectacular psychedelic lighting effects with this genuine electronic strobe. Terrific for parties, special occasions, experiments . . . perfect for homes, night clubs, dances, exhibitions. Adjusts from 1 to 10 short-duration flashes per second—not a makeshift mechanical device. Amaze friends with old-time movie effects. Best party ice-breaker ever—"freeze" the action and "unfreeze" your guests. Practical too—check action of moderate-speed machinery. Xenon lamp gives one million flashes, 6 1/4" diam. reflector. Uses REG. 110-120 volt A.C. current. Handsome solid walnut cabinet, 9 1/2" x 9 5/8" by 4". Send for Bulletin #75—describes other new unique lighting effects. Stock No. 70,989EK \$79.95 Ppd.

MEGA STROBE

Stock No. 71,041EK \$149.95 Ppd.



NEW! LOW-COST COLOR ORGAN

Accompany music with colored lighting that changes in hue and intensity. Create tremendous variety of unusual and beautiful effects. Simply plug in 3 diff. sets of colored lights and place near audio source. Notes picked up by interior "mike" determine which colored lights go on—loudness determines intensity. Surprising number of commercial, display and home uses—control lighting in pools and fountains, window and holiday decorations, great for parties. Tough, compact, unit with light intensity control. 4-9/16"x2 1/4"x4 1/4". 1 lb. 6 oz. Stock No. 1900EK \$39.95 Ppd.

4 CHANNEL DE LUXE 2,000 WATT
Stock No. 71,103EK \$195.00 Ppd.



KEEP PACE WITH THE SPACE AGE!

AMAZING BARGAINS

for Fun • Study • Profit
from
EDMUND SCIENTIFIC CO.
300 Edscorp Building
Barrington, N. J. 08007

'BRIGHT IDEAS' in UNIQUE LIGHTING
Big, new 64-page handbook packed with facts, loaded with illustrations. All latest developments, applications, equipment. 8 1/2" x 11" looseleaf paper punched to fit 3 ring binder. Stock No. 9100EK \$3.00 Ppd.




LOW-COST OVERHEAD PROJECTOR
If you've always wanted one but couldn't afford to pay \$150 here's your opportunity to get a 5"x5" model ideal for school, home and small audience use. Comes without light source—use your own 35mm projector (or buy ours). Ideal for transparencies, lantern slides, negatives, drawings, unusual lighting effects. 3 1/2 lbs. 9 1/4"x8 1/2"x5-9/16". Top-and-bottom mirrors, F/3.5, 16mm F.L. lens, double Fresnel condenser. Easy friction-focusing. Keystone adj. Portable. Stock No. 71,011EK \$29.50 Ppd.

EDMUND 500 Watt 35mm PROJECTOR
Stock No. 71,057EK \$24.50 Ppd.


WORLD'S SMALLEST BIBLE
See entire Holy Bible—all 773,746 words on 1,245 pages—reduced to piece of film 1 5/16" square. Incredible 48,400 to 1 reduction by new photochromic dye, micro-image technique that begins where microfilm leaves off. Needs 100X microscope to read. Amaze your friends! Carry in your wallet or purse. Project it on wall with scope and prism. Real conversation piece. Stock No. 41,191EK \$2.00 Ppd.

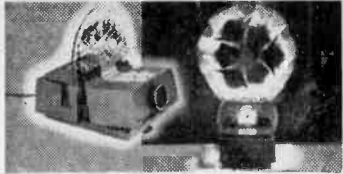50X, 150X, 300X MICROSCOPE
Stock No. 70,008EK \$16.50 Ppd.




NEW! PROJECTION KALEIDOSCOPE

At last—a low-cost unit complete with interchangeable 9" diam. liquid wheel. Projects infinite variety of brilliant color patterns which do not repeat. Specially designed wheel, 3" projection lens and Edmund Visual Special Effects Projector make it all possible. Easily operated. Large screen image at short projection distance perfect for photo backgrounds, light shows, parties, dances, etc. Front or rear projection. Incl.: 1 RPM 115V Motor, motor bracket. Instructions.
Stock No. 71,121EK . . . \$94.50 Postpaid
SOLID Multi-Colored Glass Accessory Wheel (9" Diam.)
Stock No. 71,122EK \$15.00 Ppd.

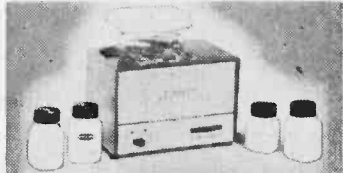

NEW LOW-COST ULTRASONIC CLEANER

Top-quality 1/2 pint unit for only \$39.95. Cleans dirt, grime completely, quickly, safely. Small delicate parts, precision electronic items, lab instruments, jewelry, coins—even dentures sparkle like new. American-made—operates on regular house current. Solid state generator w/automatic turn-off. Power regulating knob. No shocks. No radio interference. 6"x4"x4" stainless.
Stock No. 71,003EK \$39.95 Ppd.
LARGE INDUSTRIAL 1/2-GAL. SIZE
No. 85,128EK . . (Wt. 37 lbs.) \$249.95 FOB

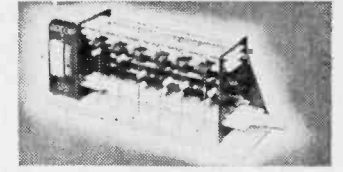

NEW MODEL DIGITAL COMPUTER

Solve problems, tell fortunes, play games with miniature version of giant electronic brains! Adds, subtracts, multiplies, shifts, complements, carries, memorizes. Colored plastic parts easily assembled. 12"x9 1/2"x4 3/4". Incl. step-by-step assembly diagrams, 32-p instruction book covering operation, computer language (binary system) programming problems and 15 experiments.
Stock No. 70,683EK \$5.98 Ppd.
BIG NEW DIGICOM II
Stock No. 70,946EK \$16.00 Ppd.

MONEY-BACK GUARANTEE
Order by Stock No.—Send Check or M.O.

GIANT FREE CATALOG

148 Pages! More than 4,000 UNUSUAL BARGAINS!

Completely new 1969 edition. New items, categories, illustrations. 148 easy-to-read pages packed with nearly 4000 unusual bargains. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes.

EDMUND SCIENTIFIC CO., 300 Edscorp Building, Barrington, N. J. 08007.
Mail coupon for FREE Catalog "EK".

Name _____
Address _____
City _____ State _____ Zip _____

elementary Electronics

May/June 1969

Vol. 8/No. 2

Dedicated to America's Electronics Hobbyists

Editor-in-Chief

JULIAN M. SIENKIEWICZ
WA2CQL, KMD4313

Managing Editor

RICHARD A. FLANAGAN
KQD2566

Art Editor

JIM MEDLER

News Editor

HELEN PARKER
KQD7967

Art Director

ANTHONY MACCARRONE

Cover Art Director

IRVING BERNSTEIN

Associate Art Director

JOHN YUSKO

Art Associate

MARGARET R. GOTTLIEB

Advertising Director

JIM CAPPELLO

Production Manager

CARL BARTEE

Production Assistant

MARILYN VARGAS

Instruments Division Manager

WILFRED M. BROWN

Chairman of the Board

B. G. DAVIS

President and Publisher

JOEL DAVIS

Vice-President and Editorial Director

HERB LEAVY, KMD4529

Vice-President and Production Director


LEONARD F. PINTO

Vice-President and Treasurer

VICTOR C. STABILE, KBP0681

ELEMENTARY ELECTRONICS is published bi-monthly by Science & Mechanics Publishing Co., a subsidiary of Davis Publications, Inc. Editorial, Business and Subscription offices: 229 Park Avenue South, New York, N.Y. 10003. One-year subscription (six issues)—\$4.00; two-year subscription (12 issues)—\$7.00; and three-year subscription (18 issues)—\$10.00. Add \$1.00 per year for postage outside the U.S.A. and Canada. Advertising offices: New York, 229 Park Avenue South, 212-OR 3-1300; Chicago, 520 N. Michigan Ave., 312-527-0330; Los Angeles: J. E. Publishers' Rep. Co., 8380 Melrose Ave., 213-653-5841; Atlanta: Pirnie & Brown, 3108 Piedmont Rd., N.E.; 404-233-6729; Long Island: Len Osten, 9 Garden Street, Great Neck, N.Y., 516-487-3305; Southwestern advertising representative: Jim Wright, 4 N. 8th St., St. Louis, 314-CH-1-1965.

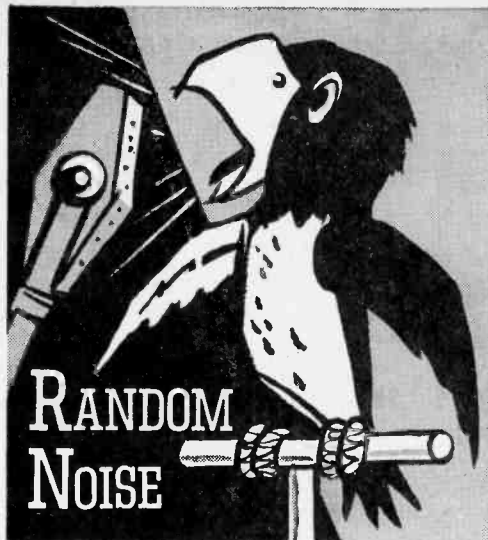Second-class postage paid at New York, New York and at additional mailing office. Copyright 1969 by Science and Mechanics Publishing Co.



BY JULIAN M. SIENKIEWICZ, Editor

There's some big news in the magazine world lately. Our sister publication is going through a name change. RADIO-TV EXPERIMENTER, the oldest small-sized electronics magazine on the stands today, will soon become SCIENCE AND ELECTRONICS. One could almost have prophesied the change because of the growing world of electronics and its application as a research tool for the sciences. Who today can investigate a new area of scientific exploration, whether it

Science and Electronics

This is what the new "logo" for Science and Electronics will look like on the newsstand. For the time being it'll share billing with the Radio-TV Experimenter logo with which everyone is familiar. Before 1969 comes to an end, Science and Electronics will get top billing.

be in space or the ghettos, without the aid of electronics? Electronic computers are used almost universally. Communications—two-way radio, video tape recorders, cable TV, electronic copying machines, etc.—have grown in step with electronics invading every field of business except possibly the post office. Even our leisure moments, vacations and hobbies have benefited by the marriage of science and electronics. So why not reflect this growth of two combined fields in a magazine title—SCIENCE AND ELECTRONICS? Watch for it on your newsstand.

Hey, Mailman! When this Editor opens his
(Continued on page 8)

You can pay \$600 and still not get professionally approved TV training.

Get it now for \$99.

Before you put out money for a home study course in TV Servicing and Repair, take a look at what's new.

National Electronic Associations did. They checked out the new TV training package being offered by ICS. Inspected the six self-teaching texts. Followed the step-by-step diagrams and instructions. Evaluated the material's practicality, its fitness for learning modern troubleshooting (including UHF and Color).

Then they approved the new course for use in their own national apprenticeship program.

They went even further and endorsed this new training as an important step for anyone working toward recognition as a Certified Electronic Technician (CET).

This is the first time a self-taught training program has been approved by NEA.

The surprising thing is that this is not a course that costs hundreds of dollars and takes several years to complete. It includes no kits or gimmicks. Requires no experience, no elaborate shop setup.

All you need is normal intelligence and a willingness to learn. Plus an old TV set to work

on and some tools and equipment (you'll find helpful what-to-buy and where-to-buy-it information in the texts).

Learning by doing, you should be able to complete your basic training in six months. You then take a final examination to win your ICS diploma and membership in the ICS TV Servicing Academy.

Actually, when you complete the first two texts, you'll be able to locate and repair 70% of common TV troubles. You can begin taking servicing jobs for money or start working in any of a number of electronic service businesses as a sought-after apprentice technician.


Which leads to the fact that this new course is far below the cost you would expect to pay for a complete training course. Comparable courses with their Color TV kits cost as much as six times more than the \$99 you'll pay for this one.

But don't stop here. Compare its up-to-dateness and thoroughness. Find out about the bonus features—a dictionary of TV terms and a portfolio of 24 late-model schematics.

Get all the facts. Free. Fast. Mail the reply card or coupon below.

ICS® Dept. M5589C
Scranton, Penna. 18515

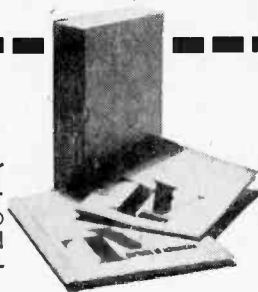Yes, I'd like all the details about your new TV Servicing/Repair basic training package. I understand there's no obligation. (Canadian residents, send coupon to Scranton, Pa. Further service handled by ICS Canadian, Ltd.)




Name _____

Street _____

City _____ State _____ Zip _____

Prices slightly higher outside U. S. and Canada.

RANDOM NOISE

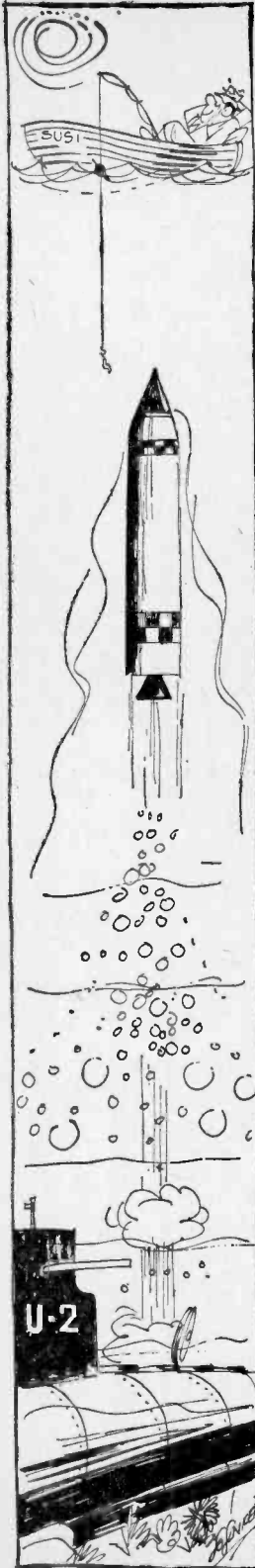

mail, he never knows what to expect. To give my readers a good example, I've decided to publish a few hot news flashes sent in by George Caisse of Levittown, Pa. I hope you'll chuckle as hard as I did.

● Chicago—Mayor Haley of this city moved quickly to day to suppress a suspected threat to the Loop. All leaders of the D'Arsonval movement were quietly arrested and held incommunicado. No other data is available.

● Washington, D. C.—The Supreme Court warned several states of appliance with fair housing and education laws, and stated that a compatible color system leading to integrated circuits was essential.

● New York—A grand jury panel which probed sensor ship made its findings public today. It held that the department distorted its function when its lightning arrester, Patrolman Audio Rourke, arrested Miss Crystal Pickup at Coney Island for wearing an arc-back bikini. When informed of this statement the policeman said, "What the helix is going on in this country?"

● Rome—The Ecumenical Council meets here to continue a dialogue on cross-modulation. A Vatican pronouncement on RC coupling is also expected momentarily. Said an observer, "They cannot be expected to sel-syn."

● Portland, Argon—Noted psychiatrist C. B. Dipole, author of the famous best-selling volume, *The Fluorescent the Place to Make Love*, attacked marriage as a dense pattern of twisted pairs reflecting a spurious response to the demands of modern-day life. He recommends the old-fashioned hayride as a tension reliever. Says Dipole, "If you're seeking an outlet chuck your hangups and tumble into the hay."

Complaint Dept. I've received a letter of protest from a reader, Ken Greenberg of Chicago, which should not go unnoticed. I would like to put Ken's complaint to you in his own words. They are: "Those little earphones that come with transistor radios are undoubtedly the most uncomfortable, ill-fitting, unsanitary, low-quality, always tangled, listening devices ever made. Surely we consumers deserve better."

Well Ken, you can bet your sweet bippy we consumers do deserve an improved product. Those uncomfortable little "plugs" that sometimes have to be hammered into our ears to stay put, are the byproduct of inexpensive transistor radio imports. Prior to World War II and immediately after, all American portable radios were designed to offer good listening pleasure for a reasonably large loudspeaker with good volume and fair fidelity. Then came the transistor radio, and the low price, and the awful earphones.


Why there was a demand for an earpiece for private listening on these cheap transistor radio products may never be truly understood. In all honesty, the best thing to do with these earphones is to toss them away when you have obtained the mini-radio and just listen to that 2½-in. loudspeaker screech away.

Back to School. A three-week summer course in Research Instrumentation will be conducted at Polytechnic Institute of Brooklyn for educators, engineers and scientists from all technical fields who need a working knowledge of electronic instrumentation as applied to problems in research. The course will be held from July 19 to August 9, 1969, on the Brooklyn campus.

The course is open to industrial and academic scientists and engineers from all disciplines. Medical research workers will find the course valuable and are also invited to apply. There are no specific prerequisites beyond a basic understanding of college physics.

The text for the course is "Electronics for Scientists" by Malmstadt, Enke and Toren. This unique volume presents both reference material and detailed experiments for laboratory work.

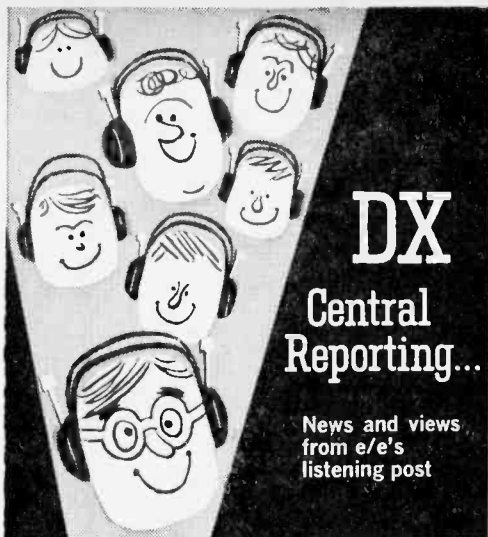Applicants should secure a place in the course at the earliest possible date. Industrial participants must file their applications by June 1. Inquiries may be directed to: Prof. Kenneth Jolls, Office of Special Programs, Polytechnic Institute of Brooklyn, 333 Jay St., Brooklyn, N.Y. 11201 (telephone: 212-643-4442 or 643-2266). ■



By DON JENSEN

● CRUCIAL TRUCIAL

With the Middle East a political tinderbox, the ears of the DX world increasingly are tuned to the shortwave voices off this turbulent region. Drawing particular attention is the sandy collection of sheikdoms known formerly as Trucial Oman.

These seven mini-states, plus neighboring Qatar and offshore Bahrein, early in 1968, joined to form the Persian Gulf Federation. Under British protection for a century and a half, the area could be up for grabs when Her Majesty's forces withdraw in 1971, unless the new federation can fill the political vacuum.


To counteract the heavy Pan-Arab propaganda barrage of Cairo Radio, Great Britain has been working hard to put the Trucial sheikdoms on the shortwave map. Since last June 25, the 100 kilowatt Qatar Broadcasting Service has been active on 9,570 kHz. (See *DX Central*, Mar.-Apr. 1969 issue.)

Its BBC-trained announcers are on the air daily from 1400 to 1730, and 0330 to 0500 GMT (Fridays until 0700). And, station director Taher Shahibi confirms that QBS sometimes extends this schedule. SWLs, who can fight their way through the interfering Chilean, Radio Portales on 9,572 kHz., have heard it around 0400 GMT.

And, last year, United Kingdom Crown Agents advertised in the London papers for a senior broadcasting engineer to supervise the installation and operation of other high-power medium and shortwave transmitters further down the Trucial Coast at Abu Dhabi. Little more is known of this project.

For the past four years, DXers have been waiting for another Persian Gulf SWer. In 1965, the Bahrein Broadcasting Service announced plans for a 10 kilowatt transmitter at the capital,

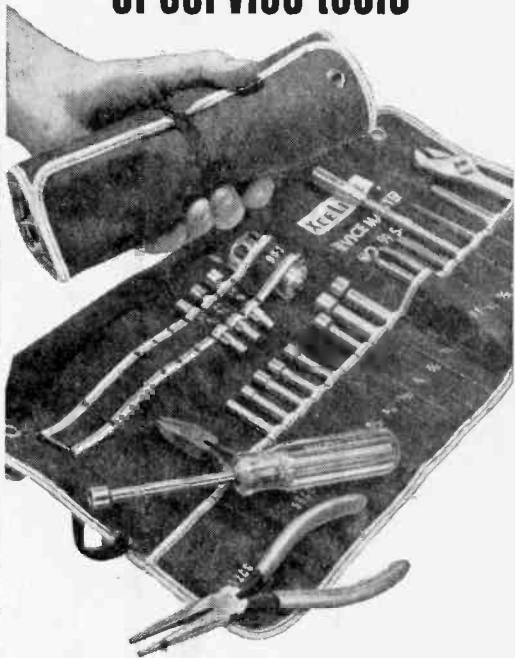SERVICE MASTER HANDIEST HANDFUL of service tools



23 essential tools at your fingertips in this lightweight (only 2¾ lbs.), compact, easy-to-carry, roll-up kit. Contains long nose plier, diagonal plier, adjustable wrench, regular and stubby plastic handles with these interchangeable blades: 9 regular and 3 stubby nutdriver, 2 slotted and 1 Phillips screwdriver, 2 reamer, 1 extension. Eyelets in plastic-coated canvas case permit wall hanging. New elastic loop secures roll, eliminates need for tying.

many optional accessories:

Junior and Tee handles... Additional nutdriver, Phillips & slotted screwdriver, and extension blade sizes... Allen hex type, Bristol multiple spline, Frearson, Scrulox, and clutch head blades... Awl/Scriber... Chuck adaptors to use blades in spiral ratchet drivers.

XCELITE

Xcelite, Inc.
80 Bank St., Orchard Park, N. Y. 14127
Send Catalog 166 containing information on
Service Master kit and accessories.

name _____
address _____
city _____ state & zip _____

DX CENTRAL

Manama. So far, no shortwave broadcasts have been reported from this island, 20 miles off Qatar's shores.

The usually reliable Foreign Broadcast Information Service, the shortwave monitoring arm of the U.S. Central Intelligence Agency, in its published logbooks, claims another station in Trucial Oman, The Voice of the Coast. Supposedly, it operates a one-kilowatt transmitter at Sharjah on 6,040 kHz.

Several months ago, an overseas shortwave bulletin stated The Voice of the Coast broadcasts daily from 1300 to 1900 GMT, with Arabic

casting Co. Over the years, FEBC has established a series of missionary stations stretching nearly half-way around the globe.

Now, an FEBC affiliate, the Far East Broadcasting Associates of Britain, has put a rare country back on the DX map with the opening of a shortwave service from the island of Mahe in the Seychelles group.

Tropical Seychelles, nearly 90 dots in the Indian Ocean, a thousand miles east of Africa, have been without shortwave since the Seychelles Broadcasting Service closed down its 40-watt transmitter three years ago.

Studio and transmitter buildings are up on Mahe and since the first of this year, tests supposedly have been conducted with a one-kilowatt transmitter on loan from the FEBC Okinawa station. A pair of powerful Marconi shortwave units were shipped from England in December and technical director John Wheatley has been shopping around for second-hand antenna towers and miscellaneous hardware.

From studios in Victoria, the Seychelles capital, programs are relayed by VHF link to the transmitter site on Mahe's coast. The first of these high-power stations should replace the test transmitter about the time you read this. The second, supposedly, is to be completed by year's end.

Though India, Pakistan and Ceylon are prime targets, U.S. listeners should have a good chance to hear FEBC-Seychelles. No frequencies have been announced, but DX Central will keep you posted.



newscasts at 1600, 1700, 1800 and 1845. And, though no American listeners have claimed reception, not long ago a well-known New Zealander reported logging it.

But, and here's a real grabber for you, DX Central, just at presstime, learned that MP4TCE, a Persian Gulf ham—and he should know—told a midwest DXer flatly, "There is no shortwave broadcast station at Sharjah on 6,040 kHz., or any other shortwave frequency!"

Until more is known of the supposed Voice of the Coast, we'll let you ponder these contradictions.

For SWLs who want to get their feet wet in Persian Gulf broadcasting, there's the new 250-kilowatt transmitter of the Kuwait Broadcasting Station, widely heard in English between 1600 and 1730 GMT, on 11,920 kHz. Though not a member of the Trucial group, prosperous, oil-rich Kuwait obviously is Britain's model for broadcasting in the fledgling federation.


● TIP TOPPER

Back in '45, with a thousand bucks and a dream, three men founded the Far East Broad-

● BANDSWEEP

660 kHz.—Medium wavers may find XERPM, Mexico City, around 0400 GMT, with mostly Spanish programming. There are occasional English announcements, though. . . . 3,225 kHz.—Brand new Latin American outlets usually are good bets for QSLs. Try the Venezuelan newcomer, Radio Occidente before 0200 GMT sign off. . . . 4,865 kHz.—Signing off with "A Portuguesa," Portugal's national anthem, at 2305 GMT, is Emisora Regional dos Acores, Ponta Delgada, on one of the mid-Atlantic Azores Islands. . . . 5,000 kHz.—The Italian standard time and frequency station, IBF, Turin, has been heard through WWV interference. This time-ticker is audible from 0645 to 0700 GMT, with code identification every five minutes and voice announcement in Italian on the hour. . . . 9,009 kHz.—Israel's Kol Yisrael has daily English language programs at 2115 GMT. It's off-beat frequency makes it easy to find. . . . 11,783 kHz.—For just plain enjoyable listening, Lorenzo Marques Radio, in Mozambique, has been a DXers' favorite for years. Try 'em at 0300 GMT sign on. . . . 15,060 kHz.—The clandestine Basque station, Radio Euzkadi heard here now until 2300. They pre-

(Continued on page 103)

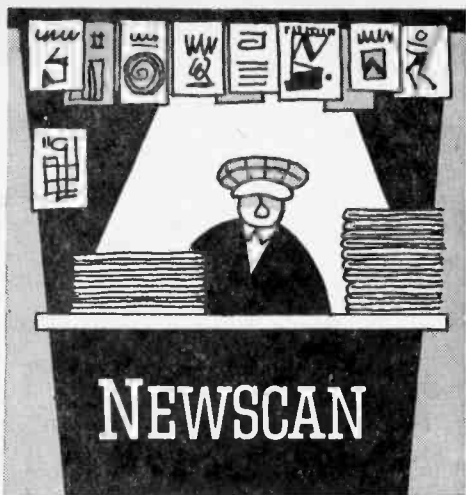

Sunshine They Have

A ship-board radar designed to sweep over the water to detect distant land is cast in a reverse role at San Jose, Calif. The landlocked radar sweeps the Santa Clara Valley and the sky above it looking for water in clouds approaching the valley. The radar is part of a sophisticated water control system operated by the Santa Clara County Flood Control and Water District.

Located some 50 miles south of San Francisco, the fertile valley is bounded on three sides by mountains ranging up to 4200 feet high. Population growth in the valley has placed



Radar detects moisture laden clouds which, when seeded with silver iodide crystals, will cause rain to fall in the Santa Clara Valley. Unseeded clouds seldom reach the height necessary for rain to form until they have passed over the valley and are many miles down wind.

*
 Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.


NAME _____
 ADDRESS _____
 CITY _____ STATE _____
 GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS

382 S. Forge Street Akron, Ohio 44308

SPECIAL INTRODUCTORY SUBSCRIPTION OFFER

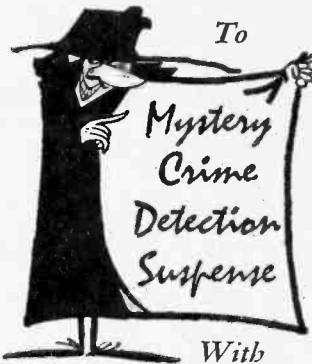

ELLERY QUEEN'S MYSTERY MAGAZINE

There's no reason for you to miss the fascinating reading of the greatest of mystery writers. You can find it in every issue of EQMM!

ELLERY QUEEN'S MYSTERY MAGAZINE 229 Park Ave. South, N.Y., N.Y. 10003 Please enter my special subscription to EQMM—12 issues for only \$3.87. <input type="checkbox"/> \$3.87 Enclosed <input type="checkbox"/> Bill me	EE-69
Name _____ <small style="text-align: center;">(please print)</small>	
Address _____	
City _____ State _____ Zip _____	

iodide injection to more effectively increase the rainfall near specific reservoirs or sections of the valley where it is wanted. It also plays an important role as a cost-lowering tool. The silver iodide is expensive and generator tenders are paid for the time they are on call.


What do valley residents think of "shower power"? Naturally, there are always some people who would prefer it with no rain, a situation that exists in the valley seven months out of the year, but the general weather pattern is so excellent that no one really begrudges the little extra rainfall. Everyone shares in the welcome bounty of water for drinking, gardening, swimming and the many other things that an ample supply of water makes possible. After all, the Santa Clara District staff can only hope to increase rainfall under certain conditions; they are not rain-makers.

For Four-Bagger Slammers

A new U. S. hardwood resource—one estimated at two billion board feet—has been uncovered by radar. And it's all because radar tubes now are being used to make baseball bats and other hardwood products. The new baseball bats are made from tanoak which is cured in a microwave kiln heated by 30,000-watt klystron radar tubes. Previous attempts at curling tanoak, which is harder than ash, required from 60 days to 18 months and gave results so unpredictable that the tree historically has been categorized as a *weed*.

The new bats, which are made in Oregon by Tanoak Industries, Inc., are cured from green fresh-cut tanoak logs in four hours by microwaves. Called "Oregon Slammers," the bats, which the manufacturer states are harder than customary ash bats yet equally resilient, will enter the market this month.

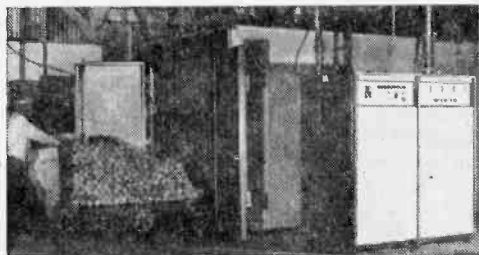The process for making the bats was developed by Varian Associates, the electronics organization noted for its invention of klystrons and production of other radar tubes and similar space age scientific hardware. Varian's Industrial Microwave Operation consists of a group of scientists devoted to harnessing the energy of



Workman (at left) at Tanoak Industries' Harbor, Oregon, mill loads the radar kiln with tanoak rough billets which will become "Oregon Slammers" baseball bats.

Live Better Electronically With

LAFAYETTE RADIO ELECTRONICS

1969 Catalog 690 **FREE!**



**Now OFF PRESS
BETTER THAN EVER
Over 500 Pages**

Stereo Hi-Fi • Citizens Band • Ham Gear • Tape Recorders • Test Equipment • TV and Radio Tubes and Parts • Cameras • Auto Accessories • Musical Instruments • Tools • Books

**Featuring Everything in Electronics for
• HOME • INDUSTRY • LABORATORY**
from the "World's Hi-Fi & Electronics Center"

LAFAYETTE Radio ELECTRONICS
Dept. 25069 P.O. Box 10
Syosset, L.I., N.Y. 11791

Send me the FREE 1969 catalog 690. 25069

Name _____

Address _____

City _____

State _____ Zip _____



Keep up to date with **SCIENCE & MECHANICS**

Science & Mechanics—the only magazine that keeps you right up to date on developments in space technology, weapons, automobiles, medicine, boats, planes, tools, new products, and exciting world events.

Keep up to date. Make sure of your home delivered copy by returning the coupon today.

SCIENCE & MECHANICS EE-69
229 Park Ave. S., N. Y., N. Y. 10003

12 issues \$4; 24 issues \$8; 36 issues \$12. (Foreign: Add \$1 a year.)


Please enter my _____ year(s) subscription.

I enclose \$ _____ Bill me. (No stamps)

Name _____ (Please Print)

Address _____

City _____ State & Zip _____

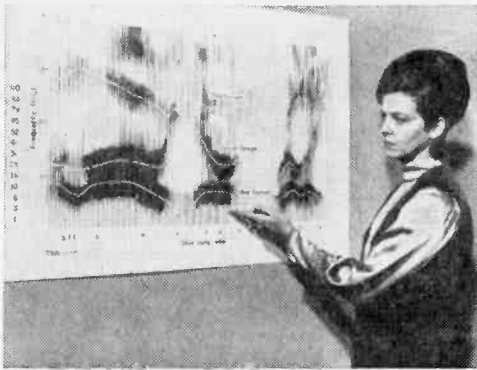

A member of the IBM Speech Synthesis Laboratory showing a sound spectrogram of the phrase "allow young Willie." The spectrogram illustrates the three lowest formants of speech, indicated by the dark, horizontal bars. The addresses for the three formants are stored by a computer and used to vary the three formant generators required for speech synthesis.

It'll be a long time before the female operator's voice at the other end of a telephone line is computerized. So dream on, lads, while our dreams may still be real.

Planning a Touchdown

Microscopic examination of thousands of lunar photographs by Raytheon Company photo-interpretation specialists will help determine the final selection of a landing spot when America's astronauts first touch down on the moon's surface. The goal is to provide a selection of can-

(Continued on page 103)



FREE

**RADIO-TV
ELECTRONICS**

69

ANNUAL CATALOG

No. 691

BURSTEIN-APPLEBEE
1100 EAST PERSHALL SERVICE, SUITE 1000, 3199 MERCIER ST., KANSAS CITY, MO. 64111

**GIANT 1969
RADIO-TV
ELECTRONICS
CATALOG**

**228 GIANT
VALUE-PACKED
PAGES**

WRITE FOR YOUR FREE COPY TODAY

BURSTEIN-APPLEBEE CO., DEPT. EE-E
3199 MERCIER ST., K. C., MO. 64111

NAME _____

ADDRESS _____


CITY _____ STATE _____ ZIP _____

Train for Electronics TECHNICIAN and Earn Your FCC License

Grantham prepares you to pass your FCC examinations by placing *primary* emphasis on electronics and *secondary* emphasis on the FCC exams. If you really understand the required subject matter, preparation for FCC exams is relatively simple. Let Grantham prepare you for success on your FCC exams and your electronics career. Length of course: three semesters. Day semesters, 16 weeks each. Evening semesters, 24 weeks each.

For complete information, write for free Bulletin.
GRANTHAM SCHOOL OF ELECTRONICS
 818—18th Street, N.W. Washington, D.C. 20006
 Telephone: (202) 298-7460


**CLASSIFIED
SECTION
ON PAGE 111**

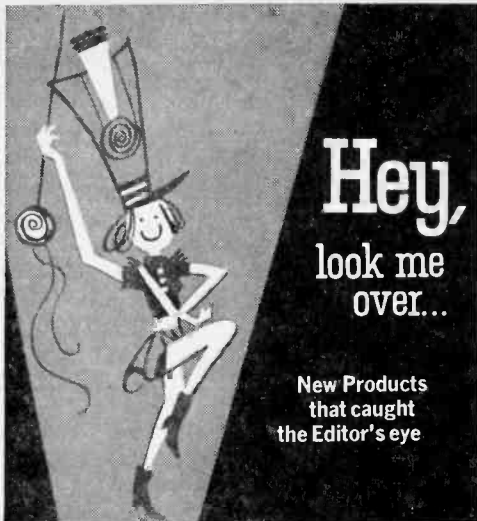

Hey, readers! ELEMENTARY ELECTRONICS is your magazine, and Hey, Look Me Over is your department. We'd like to know what you think of our new products column. Send your comments to the Editor, ELEMENTARY ELECTRONICS, 229 Park Ave. So., New York, N.Y. 10003, % Hey, Look Me Over.

Kustom Cabinets for Kit Constructors

The Bell Educational Laboratories Div. of Beltronix Systems has developed a new line of custom cabinets, aimed at all you kit builders, experimenters, and hobbyists, to be marketed under the name Flexi-Cab. Flexi-Cab consists of 6 panels and 12 vise-grip slides and can be assembled in minutes by joining the panels with the slides, a departure from conventional cabinets which require adhesives or screws or rivets. The panels are made of vinyl-clad steel and are available in a choice of walnut wood grain or black leather with a front panel of brushed brass or chrome. Flexi-Cab is packaged with a set of printed pressure sensitive labels that can be used to identify controls. For starters, they are available in these sizes: 3 x 4 x 4 in., 3 x 4 x 6 in., 3 x 6 x 9 in., and prices start at \$2.98. For

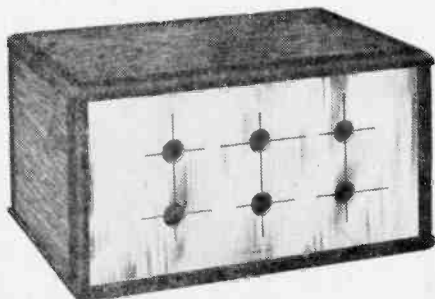

Bell Educational Labs Flexi-Cab Cabinet



further information and the name of your nearest dealer, write Bell Educational Laboratories Div., Beltronix Systems, Inc., Dept. ee, 123 Marcus Blvd., Hauppauge, N. Y. 11787.

Play To Me Only . . .

The David Clark Co. has a new stereo headset, the Clark/300, which, at \$19.00 is much more modestly priced than their previous models. But the specs are impressive: frequency range, 20 to 17,000 Hz; sensitivity, 1 milliwatt input at 1000 cycles produces 105 dB reference .0002 microbar (per earpiece, maximum power input, 1 watt per phone; nominal impedance, 8 ohms. For further information send to David Clark Co., Inc., 360 Franklin St., Worcester, Mass. 01601.



Clark/300 Stereo Headset

Treasure Hunt, Anyone?


With the TRL-1 Treasure Locator you can go looking for buried pipes, lost jewelry, coins, all types of metals, and all other such non-spiritual goodies. The circuit uses 3 FETs and 2 silicon transistors, and kit assembly is simplified with etched circuit board construction and easy-to-follow instructions. A 6-in. etched circuit coil furnished with the kit means there are no coils to wind and no test equipment needed for alignment. Glass epoxy material is used for both etched circuit boards, and construction time is said to take less than three hours. The Treasure Locator weighs only 24 oz., and is powered by any 9-volt battery. Kit comes with all parts, wire, solder, and headphone. Price is \$29.95,



Caringella Treasure Locator

and you can get a data sheet from Caringella Electronics, Inc., Box 327, Upland, Calif. 91786.

Keep 'Em Down on the Farm

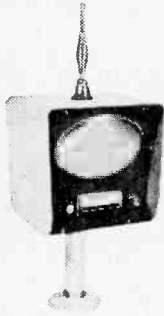


J.C. Whitney
Tractor Radio

Now farmers can hear the news, weather, livestock prices, crop prices, and music even when they're down on the lower 40. This powerful tractor radio is solid state with a 6-watt output. The heavy-gauge steel shroud is completely shockproof. There's a 5 x 7-in. speaker and a stainless steel spring base telescoping antenna, developed especially for this tractor radio. The unit can be easily installed on all tractors with 6- or 12-volt system. The price is \$51.50,

postpaid, from J. C. Whitney & Co., 1917 Archer Ave., Dept. 401, Chicago, Ill. 60616.

Solid Wave for Squares

The Heath Company announces a new solid-state sine-square wave generator, model IG-18, priced at \$67.50. Its output range is continuously variable from 1 Hz to 100 kHz, using one multiplier and two selector switches plus a vernier control. The IG-18 has 8 output voltage ranges from .003 to 10 V rms with an external load of 10 K ohms or more, and 6 output ranges from .003 to 1 V rms (-62 to +22 dB) using

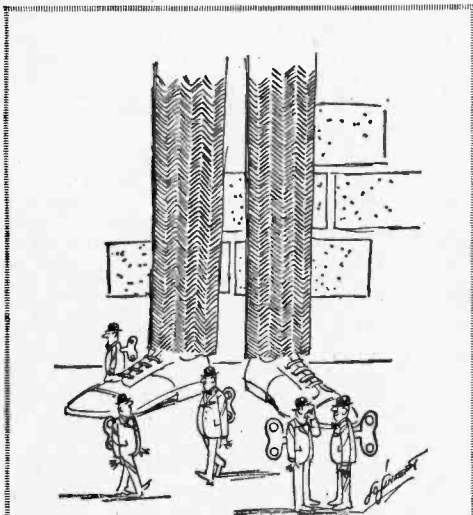

"It's on, Harry! The next sale we're all going to make a break for it!"

\$1 PEP \$ DOLLAR SALE Money Back Guarantee **\$1**

1-Amp Silicon Rectifier
Choice of Package
Bullet—Miniature—
Glass—Metal Can

- 5—800V units... \$1.00
- 4—1000V units... \$1.00
- 3—1200V units... \$1.00

5-Amp Epoxy Package

- 3—800V units... \$1.00
- 2—1000V units... \$1.00

Silicon Stud Mount
12 Amp

- 5—100V units... \$1.00
- 2—800V units... \$1.00
- 1—1000V unit... \$1.00

Silicon Stud Mount
20 Amp

- 3—100V units... \$1.00
- 1—1000V unit... \$1.00

Silicon Stud Mount
40 Amp

- 3—50V units... \$1.00
- 2—100V units... \$1.00

Silicon Stud Mount
60 Amp

- 2—50V units... \$1.00
- 1—1000V unit... \$1.00

Silicon Glass Diodes
DO-7

- 10—100V units... \$1.00

No Sales Tax
We Pay Postage

SCR

Silicon Controlled Rectifier
TO-5 Package

- 5—50V units... \$1.00
- 4—100V units... \$1.00
- 3—200V units... \$1.00
- 2—400V units... \$1.00

7-Amp SCR

- 4—50V units... \$1.00
- 3—100V units... \$1.00
- 2—200V units... \$1.00
- 1—100V unit... \$1.00

20-Amp SCR

- 2—50V units... \$1.00
- 1—300V unit... \$1.00

Gen. Purpose PNP
Germanium Transistor
Similar to 2N404

- 8 for... \$1.00

Zener Diodes, 1 Watt

- 1 Ea. 4V—6V—8V—10V
- 4 units... \$1.00

Zener Diodes, 10 Watt

- 1 Ea. 6V—8V—10V
- 3 units... \$1.00

Germanium Glass Diodes
DO-7

- Gen. Purpose
- 20 units... \$1.00
- Replaces 1N-34, 1N-60,
1N-64, 1N-295

High Voltage Stacks

- 1 Amp
- 2,000V to 20,000V
- 40¢ Per 1000 Volts
- 10,000V cost... \$4.00

PARK ELECTRONIC PRODUCTS
P. O. Box 78, N. Salem, N. H. 03073

WRITE
NOW FOR
1969
SENT FREE

**McGEE'S
CATALOG**

1001 BARGAINS IN

SPEAKERS—PARTS—TUBES—HIGH FIDELITY
COMPONENTS—RECORD CHANGERS—

Tape Recorders—Kits—Everything in Electronics
1901 McGee Street, Kansas City, Missouri 64108

TUBES! CORNELL TUBES!
FREE Send For FREE
CORNELL'S
New 1968
CATALOG
Many New Items


30¢ per tube
IN LOTS OF 100

33¢ per tube
WE SELL
PICTURE
TUBES

4219 E UNIVERSITY AVE., SAN DIEGO, CALIF. 92105

COOPERATE
WITH THE ZIP CODE PROGRAM
OF THE POST OFFICE DEPARTMENT
USE ZIP CODE NUMBERS
IN ALL ADDRESSES

HEY, LOOK ME OVER★★

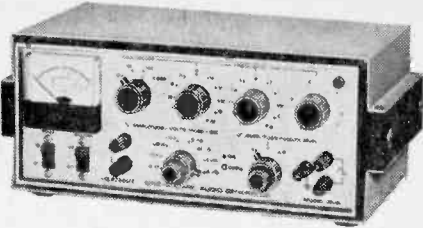


Heathkit IG-18 Sine-Square Wave Generator

the built-in 600-ohm load or an external 600-ohm load. Sine-wave output has less than 0.1% distortion from 10 Hz to 20 kHz. The square wave section has a frequency range from 5 Hz to 100 kHz at 0.1, 1 and 10 V switch-selected outputs. Unit is equipped with a dual-primary transformer for 120/240 VAC operation and a 3-wire line cord for added safety. Styled to match Heathkit's instrument line. For complete specs and how to order, write the Heath Co., Benton Harbor, Mich. 49022.

Changer Goes Mini

Lafayette's new "Mini" changer, stock No. 21-1401, is a 4-speed changer equipped with a ceramic turnover stereo cartridge and diamond stylus. Made in England, it features a low-mass tone arm, dynamically balanced 2-pole motor, and automatic shut-off after last record. You can stack and intermix up to 6 records of 10- and 12-in. size of the same speed, or manual

single play. On a walnut base, the Mini measures 14 7/8 x 5 x 10 in., weighs 6 lb. For 110-130 VAC 60 Hz, the Mini is priced at \$34.95. For more dope, write Lafayette Radio Electronics, 111 Jericho Tpk., Syosset, N. Y. 11791.

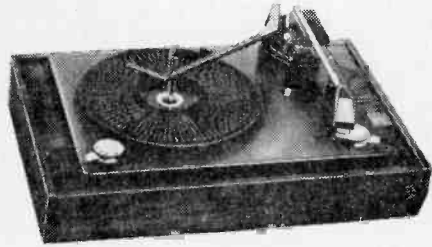

Lafayette 4-Speed Automatic "Mini" Changer

Screwdriver Gets a No-Shock Treatment


The makers of the Quick-Wedge screw-holding screwdriver, the Kedman Co., have added color-coded vinyl covering over the tubing as protection for electrical work. Dielectric strength of vinyl tubing at room temperatures averages 1100-V per mil of thickness. The vinyl cover is 20 mils thick, and will withstand 20,000 volts. There are 16 sizes being offered with color vinyl covering, and for their various prices and information on distributors, write Kedman Co., Box 267, Salt Lake City, Utah 84110.



Kedman Quick-Wedge Screw-Holding Screwdriver


Let's Hear It from the Shelf!

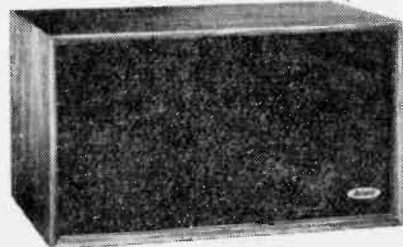Allied is very proud of their model 2370 speaker system. For one thing, the overall frequency response is 20 Hz to beyond audibility. It has a 12-in. acoustic suspension bass woofer, a compression-type midrange with diffraction horn, and a compression-type wide-dispersion horn tweeter for the treble notes. Crossover frequencies at 1000 and 5000 Hz permit each



Allied 2370 Speaker System

S&M's SUPERSENSITIVE DARKROOM METER

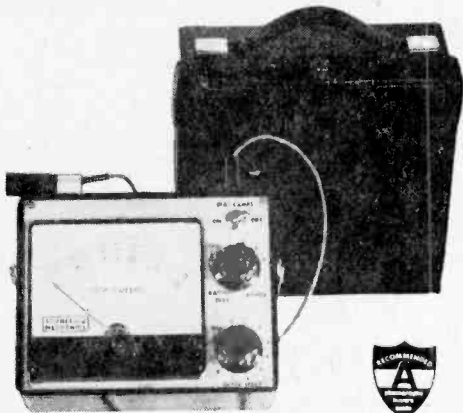

You get your money's worth when you own an S&M A-3 Supersensitive Darkroom Meter.

U.S. Camera says,
"The meter is a
marvelously sensitive
and accurate
instrument."

\$44.50 in Kit form*
\$49.50 Fully assembled*
*Carrying case included
\$4.95 extra Carrying case

This Model A-3 Meter is named the "Darkroom Meter" because it has been so widely accepted for reading enlarger easel exposures. It has earned a reputation as a precision instrument in color studio photography, copy work, portraiture, and available light photography. You can use it with movie cameras and with single lens reflex cameras. The A-3s are also used for ground glass exposure readings with microscopes, telescopes and can even be set up for use as a densitometer.


An exclusive feature of this versatile instrument is its standard plug-in probe assembly with three foot flexible cable. This probe utilizes the newest Clairex Corp. CL-505L cadmium sulfide photocell—the best grade available today—balanced for color, and the complete range of exposures from dim available light to full bright sun light. Its field of view is 43 degrees, equal to normal camera lens angles.

The meter is supplied with a 5-inch, easy-to-read computer with four-range selection and EV-EVS-LV settings to give F stops from .7 to 90 and list exposure time from 1/15,000 second to 8 hours.

The 4½-inch dial of the meter is self-illuminated with built-in battery lamps. You read on 4 sensitivity ranges, therefore the meter dial and selector switch give you an equivalent of 18 inches of total dial space for reading accuracy. The paper speed control knob is used to set sensitivity to match the various grades of printing papers. The meter sensitivity is sufficient to detect the light of a match 10 feet away.

This S&M Light Meter is supplied with a probe holding bracket for darkroom work. An accessory easel probe ⅜-inch (see photo) is recommended for use with high speed enlarging papers. The standard ¾-inch diameter probe can be used to read a ½-inch circle on the viewing glass of many SLR's. To read a smaller target through the lens of Exactas, Practicas, etc., order the ¾-inch diameter probe which has a ¼ wide photocell.

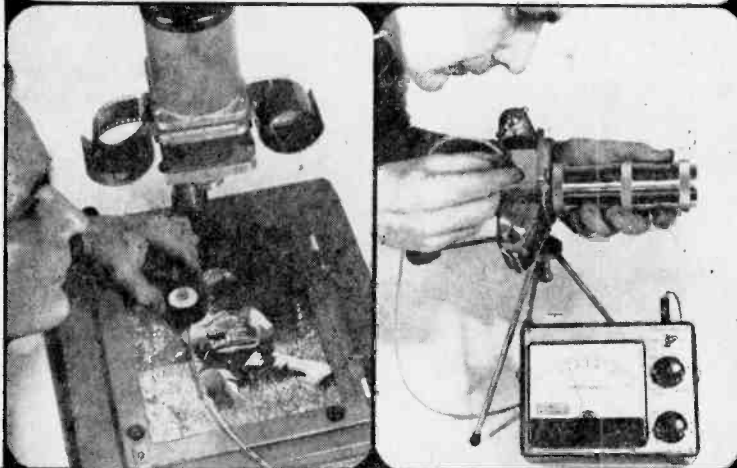Whether you buy the S&M A-3 Meter as an easy-to-assemble kit, or completely factory-assembled, you can be sure you have the advantage of owning a rugged and dependable instrument. A complete manual tells you step-by-step how to assemble the instrument, how to use it for profitable photography and how to keep it working right for years



Use the coupon below to order your meter today. Satisfaction guaranteed!

SCIENCE & MECHANICS—KIT DIVISION
229 Park Avenue South, N.Y., N.Y. 10003

EE-69

Please send the S&M, A-3 Supersensitive Darkroom Meter as I've indicated below. I understand that if I am not satisfied, I may return the meter within 10 days for a complete refund.

Add 10% for Canadian and foreign orders. N.Y.C. residents add 5% for sales tax.

_____ \$44.50—in kit form	_____ \$6.50—Easel Probe
_____ \$49.50—fully assembled	_____ \$6.50—¾-inch Miniature Probe
_____ \$ 4.95—Carrying Case	_____ Enclosed \$3.00 deposit,
_____ Check or money order enclosed,	Ship COD, plus postage & COD
ship post-paid	charges

Name (PLEASE PRINT) _____

Address _____

City _____ State _____ Zip _____

HEY, LOOK ME OVER ★★★

speaker to reproduce only those frequencies for which it is designed. There are two level controls for midrange and tweeter to permit adjustment to the personal taste of the listener. The walnut-veneered enclosure (14 x 25 x 13 in.) is Fiberglas-filled to prevent resonance. The bass speaker is matched to the size and characteristics of the enclosure. In kit form (and they even supply the oil to rub into the cabinet) you ask for the 2370K, and it's \$99.95. Factory-assembled and finished, it's \$119.95. For more info, write for a catalog from Allied Radio Corp., Dept. 20, 100 N. Western Ave., Chicago, Ill. 60680.

Stereo Over the Waves

Here is a pint-size stereo system, the *Scottie*, that the manufacturers suggest is just the thing for boat owners. Operating on AC or a 12-V battery, the *Scottie* employs FETs, so you can bring in distant stations when you're 'way out




H. H. Scott Scottie Stereo System

at sea. Scott claims their full complementary output stages provide undistorted sound at lowest listening levels. There is an optional turntable to go with the speakers-receiver system. The *Scottie* retails for \$199.95. The optional turntable is \$59.95, with cartridge and diamond stylus. Further information can be had from H. H. Scott, 111 Powder Mill Rd., Maynard, Mass. 01754.

Three-In-One Probe-ity

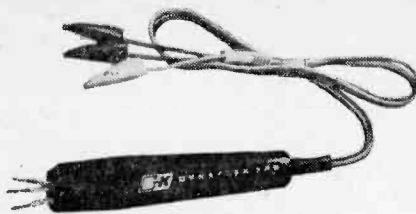The new B&K FP-3 test probe provides a way of making three termination touch-to-test contacts simultaneously using only one hand, where before it would have taken three probes and both hands. The three-point probe is called *Dyna-Flex* and is priced at \$12.95. Designed for use with in-circuit transistor testers, VTVMs, VOMs, and TVOMs, *Dyna-Flex* makes positive,



B&K Dyna-Flex FP-3 Test Probe

non-slip direct contacts to printed circuit terminations. The probe has 3 spring-loaded needle-point tips which tilt or swivel on ball joints to permit automatic adjustment to any spacing from $\frac{1}{32}$ to $\frac{3}{8}$ in. to fit the terminations of a wide variety of components. Three leads, color coded to their respective tips, terminate in insulated alligator clips for easy connection to the test instrument being used. The clips also permit making rapid component test substitutions. If you want to know more, write B&K Div. of Dynascan Corp., 1801 W. Belle Plaine Ave., Chicago, Ill. 60613.

Make With a Mallet

Here's a new construction system—a method of assembling square steel tube furniture and fixtures with the use of just a mallet. The system, called *Apton*, has three basic components: square steel tube; a tough styrene type collar; and a series of seven different joint formations. The tube can be either ordered in the desired lengths or cut to size with an ordinary hacksaw. You assemble *Apton* by sliding a collar into the end of a tube, inserting the tapered arm of joint into the collar and tube, then driving the joint solidly home with a soft-faced mallet. The tube is made in 1- and $\frac{3}{4}$ -in.-square sizes in lengths




Hobbyist designed furniture made from Dexion Square Sheet Tubes

up to 8 ft. In black matte finish, the 1-in. size is 37¢ a foot; the ¾-in. goes for 32¢ a foot. For further information write for a brochure, "Planning and Building with Apton," from Dexion, Inc., 39-27 59th St., Woodside, N.Y. 11377.

Wake Up, Musical Sleepyheads!

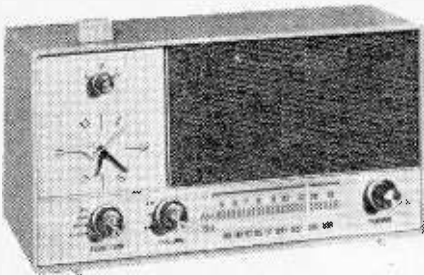The GR-58 from Heath is a solid-state AM-FM clock radio kit with a lot of cute features. For instance: a clock-controlled auxiliary AC socket on the rear panel for having hot coffee at bedside in the morning, or for turning on lights; a "snooze" button—ten minutes before the alarm goes on the radio starts, when the




Heathkit GR-58 AM-FM Clock Radio

alarm goes on you shut it off by depressing the snooze button and the radio remains on. This operation will continuously recycle until the GR-58 is reset to another position. The FM section has AFC, a built-in FM antenna, and 3-stage IF. The AM portion has a 2-stage IF, amplified AGC, and a built-in ½-in. ferrite-rod antenna. The unit comes in a blue plastic cabinet and both the AM and FM front ends are factory built and aligned. You can put together all this for the \$47.95, and for further description write to the Heath Co., Benton Harbor, Mich. 49022.

Patch Makes Dialogue

Hy-Gain has introduced a CB phone patch which will interconnect any base CB with the telephone—thus extending a CB call to any telephone in the nation. The company says having the Phone Patch on your base is equivalent to having a telephone in your car. You can talk to any local or long distance phone via your base while traveling. This could be very handy in emergencies for contacting police or other public safety units. The Hy-Gain Phone Patch (part No. 402) can easily be connected to any CB transceiver and comes with complete instructions. It sells for \$7.95; for further information write Hy-Gain Electronics Corp., Hwy 6 & Stevens Creek, Lincoln, Neb. 68501. ■

Can't find the key to electronics?

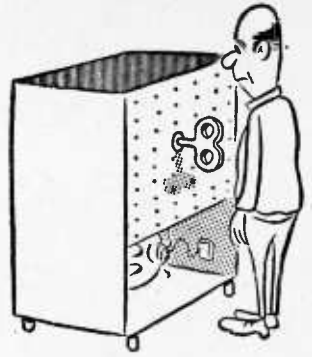

—then get your electronics cool with this introductory offer to the two leading electronics magazines! Use coupon in ad.

—Now, both of these fine magazines will be delivered to you at the special subscription rate of just \$7.00 . . . save \$2 from newsstand price.



ELEMENTARY ELECTRONICS

The magazine that serves up electronics theory in pleasant spoonfuls and reinforces the knowledge you gain with exciting and useful projects.

Radio-TV Experimenter and Science and Electronics

Dedicated to the man who wants to obtain a fuller and broader knowledge of electronics and scientific worlds.



DAVIS PUBLICATIONS, INC. EE-69
229 Park Ave. S./New York, N.Y. 10003

Yes! I want to find the key to electronics.

■ Begin my subscription to 1. RADIO-TV EXPERIMENTER and SCIENCE AND ELECTRONICS plus 2. ELEMENTARY ELECTRONICS at your low-subscription rate of \$7.00

Bill me later Check enclosed.

Name.....

Address.....

City.....State.....Zip.....

(Outside U.S.A. & Canada add \$1.50 pstge. & hndlg.)

LITERATURE



ELECTRONIC PARTS

- ★135. Get with ICs! RCA's new integrated Circuit Experimenter's Kit KD2112 is the first of its kind and should be a part of your next project. Get all the facts direct from RCA. Circle 135.
- ★140. How cheap is cheap? Well, take a gander at *Cornell Electronics'* latest catalog. It's packed with bargains like 6W4, 12AX7, 5U4, etc., tubes for only 33¢. You've got to see this one to believe it!
1. *Allied's* catalog is so widely used as a reference book, that it's regarded as a standard by people in the electronics industry. Don't you have the 1969 *Allied Radio* catalog? The surprising thing is that it's free!
- ★2. Now, get the all-new 512-page, fully illustrated *Lafayette Radio* 1969 catalog. Discover the latest in CB gear, test equipment, ham gear, tools, books, hi-fi components and gifts. Do it now!
8. Get it now! *John Meshna, Jr.'s* new 46-page catalog is jam packed with surplus buys—surplus radios, new parts, computer parts, etc.
23. No electronics bargain hunter should be caught without the 1969 copy of *Radio Shack's* catalog. Some equipment and kit offers are so low, they look like misprints. Buying is believing.
- ★5. *Edmund Scientific's* new catalog contains over 4000 products that embrace many interests and fields. It's a 148-page buyers' guide for Science Fair fans.
- ★4. *Olson's* catalog is a multi-colored newspaper that's packed with more bargains than a phone book has names. Don't believe us? Get a copy.
7. Before you build from scratch, check the *Fair Radio Sales* latest catalog for electronic gear that can be modified to your needs. *Fair* way to save cash.

★10. *Burstein-Applebee* offers a new giant catalog containing 100s of big pages crammed with savings including hundreds of bargains on hi-fi kits, power tools, tubes, and parts.

11. Now available from *EDI (Electronic Distributors, Inc.)*: a catalog containing hundreds of electronic items. *EDI* will be happy to place you on their mailing list.

106. With 70 million TV and 240 million radios somebody somewhere will need a vacuum tube replacement at the rate of one a second! Get *Universal Tube Co.'s* Troubleshooting Chart and facts on their \$1.50 flat rate per tube.

6. Bargains galore, that's what's in store! *Poly-Paks Co.* will send you their latest eight-page flyer listing the latest in available merchandise, including a giant \$1 special sale.

TOOLS

★78. *Xcelite's* Service Master roll kit puts 23 essential hand tools at your fingertips. Get Catalog 166 for complete description of kit and many optional accessories.

118. Secure coax cables, speaker wires, phone wires, etc., with *Arrow* staple gun tackers. 3 models for wires and cables from 3/8" to 1/2" dia. Get fact-full *Arrow* literature.

CB—AMATEUR RADIO— SHORTWAVE RADIO

146. It may be the first-quality catalog catering Books, rigs, what-nois—e need for your listening pc circle 146!

100. You can get increased CB range and clarity using the "Cobra-23" transceiver with speech compressor—receiver sensitivity is excellent. Catalog sheet will be mailed by *B&K Division of Dynascan Corporation*.

141. Newly-designed CB antenna catalog by *Antenna Specialists* has been sectionalized to facilitate the picking of an antenna or accessory from a handy index system. Man, *Antenna Specialists* makes the pickin' easy.

102. No never mind what brand your CB set is. *Sentry* has the crystal you need. Same goes for ham rigs. Seeing is believing, so get *Sentry's* catalog today. Circle 102.

130. Bone up on the CB with the latest *Sams* books. Titles range from "ABC's of CB Radio" to "99 Ways to Improve your CB Radio." So Circle 130 and get the facts from *Sams*.

107. Want a deluxe CB base station? Then get the specs on *Tram's* all new Titan II—it's the SSB/AM rig you've been waiting for!

96. Get your copy of *E. F. Johnson's* new booklet, "Can *Johnson* 2-

Way Radio Help Me?" Aimed for business use, the booklet is useful to everyone.

129. Boy, oh boy—if you want to read about a flock of CB winners, get your hands on *Lafayette's* new 1969 catalog. *Lafayette* has CB sets for all pocketbooks.

46. Pick up *Hallcrafters'* new four-page illustrated brochure describing *Hallcrafters'* line of monitor receivers—police, fire, ambulance, emergency, weather, business radio, all yours at the flip of a dial.

116. Pep-up your CB rig's performance with *Turner's* M+2 mobile microphone. Get complete spec sheets and data on other *Turner* mikes.

48. *Hy-Gain's* new CB antenna catalog is packed full of useful information and product data that every CBer should know. Get a copy.

111. Get the scoop on *Versa-Tronics'* *Versa-Tenna* with instant magnetic mounting. Antenna models available for CBers, hams and mobile units from 27 MHz to 1000 MHz.

45. CBers, Hams, SWLs—get your copy of *World Radio Labs'* 1969 catalog. If you're a wireless nut or experimenter, you'll take to this catalog.

101. If it's a CB product, chances are *International Crystal* has it listed in their colorful catalog. Whether kit or wired, accessory or test gear, this CB-oriented company can be relied 1 to fill the bill.

103. *Squires-Sanders* would like you to know about their CB transceivers, the "23'er" and the new "55S." Also, CB accessories that add versatility to their 5-watters.

ELECTRONIC PRODUCTS

143. Bring new life to your hobby. Exciting plans for new projects—let *Electronics Hobby Shop* give you the dope. Circle 143, now.

144. Hear today the organ with the "Sound-of-Tomorrow," the *Melo-Sonic* by *Whippity Electronics*. It's portable—take it anywhere. Send for pics and descriptive literature.

66. Try instant lettering to mark control panels and component parts. *Datak's* booklets and sample show this easy dry transfer method.

109. *Seco* offers a line of specialized and standard test equipment that's ideal for the home experimenter and pro. Get specs and prices today.

42. Here's colorful 116 page catalog containing a wide assortment of electronic kits. You'll find something for any interest, any budget. And *Heath Co.* will happily send you a copy.

128. If you can hammer a nail and miss your thumb, you can assemble *Schober* organ. To prove the point, *Schober* will send you their catalog and a 7-in. disc recording.

LIBRARY

★ Starred items indicate advertisers in this issue. Consult their ads for additional information and specifications.

9. Troubleshooting without test gear? Get with it—let Accurate Instrument clue you in on some great buys. Why do without?

145. *Alco Electronic Products* has 28 circuit ideas using their remote control relay. Get 100-and-one odd jobs done at home without calling an electrician. Get all the facts today!

44. Kit builder? Like wired products? *EICO's* 1969 catalog takes care of both breeds of buyers. 32 pages full of hi-fi, test, CB, ham, SWL, automotive and hobby kits and products—do you have a copy?

126. *Delta Products* new capacitive discharge ignition system in kit form will pep up your car. Designed to cut gas costs and reduce point and plug wear. Get *Delta's* details in full-color literature.

SCHOOLS AND EDUCATIONAL

★74. Get two free books—"How to Get a Commercial FCC License" and "How to Succeed in Electronics"—from *Cleveland Institute of Electronics*. Begin your future today!

★3. Get all the facts on Progressive Edu-Kits Home Radio Course. Build 20 radios and electronic circuits; parts, tools and instructions come with course.

142. *Radio-Television Training of America* prepares you for a career—not a job. 16 big kits help you learn as you build. 120 lessons. Get all the facts today!

114. Prepare for tomorrow by studying at home with *Technical Training International*. Get the facts today on how you can step up in your present job.

★136. *International Correspondence Schools* has a 384-page manual explaining the function, operation, and objectives of *ICS*. Get the facts on 266 courses of study currently available. Sorry, offer may expire soon.

★137. For success in communications, broadcasting and electronics get your First Class FCC license and *Grantham School of Electronics* will show you how. Interesting booklets are yours for the asking.

HI-FI/AUDIO

104. You can't hear FM stereo unless your FM antenna can pull 'em in. Learn more and discover what's available from *Finco's* 6-pages "Third Dimensional Sound."

119. *Kenwood* puts it right on the line. The all-new *Kenwood* FM-stereo receivers are described in a colorful 16-page booklet complete with easy-to-read-and-compare spec data. Get your copy today!

30. *Shure's* business is hi-fi—cartridges, tone arms, and headphone amps. Make it your business to know *Shure!*

134. Discover *PlayTape*—America's newest tape cartridge and tape players. Unit priced at under \$17 with cartridges at 45-disc prices. *PlayTape* has one of America's largest recorded libraries.

17. Mikes, speakers, amps, receivers—you name it, *Electro-Voice* makes it and makes it good. Get the straight poop from *E-V* today.

99. Get the inside info on why *Koss/Acoustech's* solid-state amplifiers are the rage of the experts. Colorful brochure answers all your questions.

26. The all new, lavishly-illustrated, full-color brochure, "At Home With Stereo" clues you in on *H.H. Scott's* 1969 stereo consoles. Discover how to pick a hi-fi console for your living room.

TAPE RECORDERS AND TAPE

123. Yours for the asking—*Elpa's* new "The Tape Recording Omnibook." 16 jam-packed pages on facts and tips you should know about before you buy a tape recorder.

31. All the facts about *Concord Electronics Corp.* tape recorders are yours for the asking in a free booklet. Portable, battery operated to four-track, fully transistorized stereos cover every recording need.

32. "Everybody's Tape Recording Handbook" is the title of a booklet that *Sarkes-Tarzan* will send you. It's 24-pages jam-packed with info for the home recording enthusiast. Includes a valuable table of recording times for various tapes.

34. "All the Best from *Sony*" is an 8-page booklet describing *Sony-Super-scope* products—tape recorders, microphones, tape and accessories. Get a copy today before you buy!

35. If you are a serious tape audiophile, you will be interested in the all new *Viking/Telex* line of quality tape recorders.

TELEVISION

★70. Need a new TV set? Then assemble a *Heath* TV kit. *Heath* has all sizes. B&W and color, portable and fixed. Why not build the next TV you watch?

127. *National Schools* will help you learn all about color TV as you assemble their 25-in. color TV kit. Just one of *National's* many exciting and rewarding courses.

ELEMENTARY ELECTRONICS

Department 669
229 Park Avenue South
New York, N.Y. 10003

Please arrange to have the literature whose numbers I have circled at right sent to me as soon as possible. I am enclosing 25¢ to cover handling. (No stamps, please.)

Indicate total number of booklets requested

	1	2	3	4	5	6	7	8	9	10
	11	17	23	26	30	31	32	34	35	42
	44	45	46	48	66	70	74	78	96	99
	100	101	102	103	104	106	107	109	111	114
	116	118	119	123	126	127	128	129	130	134
	135	136	137	140	141	142	143	144	145	146


NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____




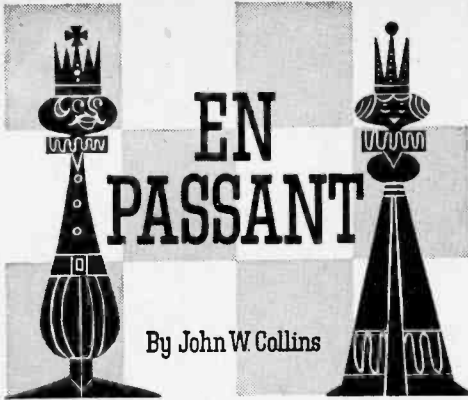

“Well begun is half done” is an old saying that particularly applies to the *opening*—the first ten or fifteen moves of a game. It is during this phase that both sides develop their pieces, get ideas, and prepare for the later phases. And it is essential to understand the concept of each debut, rather than just memorize its characteristic moves. Here are four more standard openings to add to those which have appeared before.

Four Knights' Game. The Four Knights' Game is a sound but too conservative opening. A kind of Ruy Lopez (1 P-K4, P-K4 2 N-KB3, N-QB3 3 B-N5), it counts on the first move, development, and a slight initiative. Old masters, such as Maroczy and Dr. Tarrasch, considered it a sharp weapon, but contemporary ones regard it as merely a drawing device. The Symmetrical Variation is one of its best known forms and proceeds:


- | | | | |
|---------|-------|----------|-------|
| 1 P-K4 | P-K4 | 8 B-N5 | Q-K2 |
| 2 N-KB3 | N-QB3 | 9 R-K1 | N-Q1! |
| 3 N-B3 | N-B3 | 10 P-Q4 | N-K3 |
| 4 B-N5 | B-N5 | 11 B-QB1 | R-Q1! |
| 5 O-O | O-O | 12 N-R4 | P-KN3 |
| 6 P-Q3 | BxN! | 13 P-N3 | P-Q4! |
| 7 Px8 | P-Q3 | | |

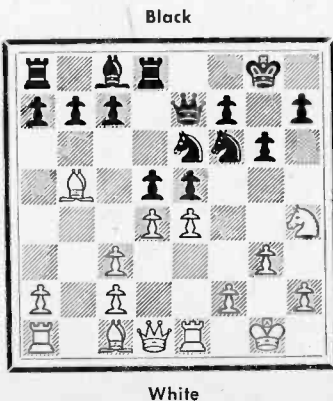

The position offers equal chances.


Reti Opening. This one is hyper-modern, subtle, and flexible, and bears the name of Richard Reti, a Czechoslovakian grandmaster who wrote and played during the first two decades of the century. It works on the center from afar and is replete with transpositional possibilities. A good defense to it is the London System, an example of which follows.

- | | | | |
|---------|-------|----------|-------|
| 1 N-KB3 | P-Q4 | 7 O-O | P-KR3 |
| 2 P-B4 | P-QB3 | 8 P-Q3 | B-B4! |
| 3 P-QN3 | N-B3 | 9 QN-Q2 | O-O |
| 4 P-N3 | B-B4! | 10 Q-B2 | Q-K2 |
| 5 B-KN2 | P-K3 | 11 P-K4! | PxKP |
| 6 B-N2 | QN-Q2 | 12 PxP | B-R2 |

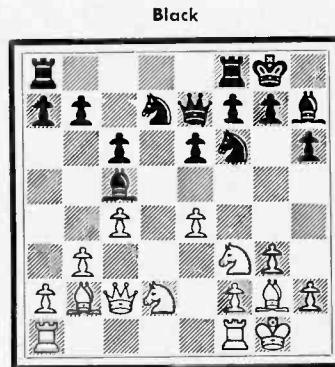

Equal chances.

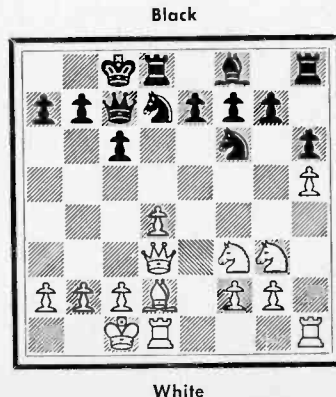Caro-Kann Defense. Safety against the rigors of 1 P-K4 is sought with the Caro-Kann Defense (1 P-QB3). Solid, if not overly dynamic, it seeks simplicity and the possibility of an early ending. World Champion Tigran Petrosian is one of its advocates and here is one of the lines he likes (see moves top of next page)—




1 P-K4	P-QB3	7 N-B3	N-Q2
2 P-Q4	P-Q4	8 P-R5	B-R2
3 N-QB3	PxP	9 B-Q3	BxB
4 NxP	B-B4	10 QxB	KN-B3
5 N-N3	B-N3	11 B-Q2	Q-B2
6 P-KR4	P-KR3	12 O-O-O	O-O-O

Equal chances.

Dutch Defense. Said to be a Dutch treat by some, this defense has nevertheless been a favorite of World Champions Alekhine, Botvinnik, and Morphy. It creates imbalance, tension, and tactics, seeks control of the K5 square, and utilizes the KB and KN files for an attack. The Stonewall Variation, hereafter given, is one of its crucial lines.

1 P-Q4	P-KB4	8 Q-B2	Q-K1
2 P-KN3	P-K3	9 B-B4	Q-R4
3 B-N2	N-KB3	10 QR-Q1	QN-Q2
4 N-KB3	B-K2	11 P-N3	K-R1
5 O-O	O-O	12 K-R1	R-KN1
6 P-B4	P-Q4	13 P-K3	P-KN4!
7 N-B3	P-B3	14 B-B7	N-K1

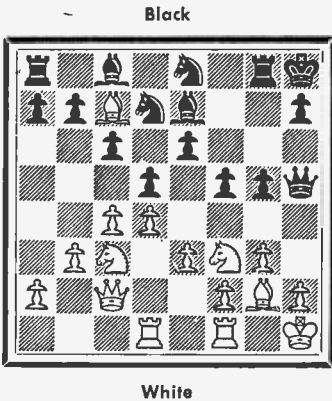

Equal chances.

Game of the Issue. Grandmaster Samuel Reshevsky, 58, of Spring Valley, N. Y., is still producing great chess. "Sammy" was born in Ozierkov, Poland, learned the game when he was four, toured Europe as a child chess prodigy at eight, and was brought here a year later. He is a five times winner of the United States Championship, winner of numerous International Tournaments, and recently competed in the Candidates' Matches for the World Championship. Reshevsky has authored "Learn Chess Fast" and "Reshevsky's Best Games of Chess" and is a regular contributor to "Chess Life."


With White in the game below against his fellow countryman Grandmaster Robert Byrne of Indianapolis, in the Interzonal Tournament at Sousse, Tunisia, 1967, Reshevsky essays his

beloved 1 P-Q4 and a favorite line against the King's Indian Defense, obtains a clear advantage by move 12, increases the pressure, and then wins by sacrificing a Bishop to secure two connected passed Pawns.

This game was cited as one of the 10 Best in Vol. 4 of the "Chess Informant," an up-to-date compilation of important parties in the world-wide arena, published by the Yugoslav Chess Federation, which contained 867 games!

1 P-Q4	N-KB3	20 R-B1	B-K3
2 P-QB4	P-KN3	21 P-B5	QPxP
3 N-QB3	B-N2	22 N-Q5!	BxN
4 P-K4	P-Q3	23 PxB	Q-K1
5 B-K2	O-O	24 PxP	P-K5
6 N-B3	P-K4!	25 Q-N3	R-N1
7 B-K3!	QN-Q2	26 P-Q6#	K-R2
8 O-O	N-N5	27 KR-Q1	R-KB1
9 B-N5	P-KB3	28 B-N5	Q-K4
10 B-Q2	P-B3	29 P-Q7	P-KR4
11 P-KR3	N-R3	30 R-Q6	P-K6
12 P-QN4!	P-KB4	31 QR-Q1	QR-Q1
13 B-N5	Q-K1	32 Q-K6!	QxQ
14 P-Q5	N-B2	33 RxQ	B-B3
15 B-B1	N-B3	34 B-R6!!	PxB
16 N-KN5!	NxN	35 P-B6	K-N2
17 BxN	P-KR3	36 P-B7	B-B2
18 BxN!	RxB	37 R-B6	R-B1
19 QPxP	QxP	38 RxB#!	Resigns

Position after 38 RxB#!

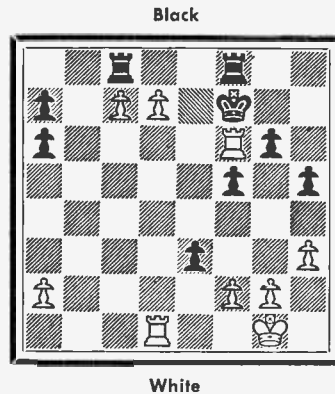

Why did Black resign? Because he must relinquish two Rooks for two Pawns and see White emerge a whole Rook ahead if he plays on. Here is the analysis:

A. If 38 . . . K-N2 39 RxR, RxR 40 P-Q8 =Q, RxQ 41 PxR=Q wins.


B. If 38 . . . KxR 39 P-Q8=Q# QRxQ (moving the King is worse) 40 PxR=Q# RxQ 41 RxR, P-K7 41 R-K8! followed by 42 RxP wins.

C. If 38 . . . KxR 39 P-Q8=Q# (not 39
(Continued on page 109)

"Performance-Plus" Kits For Home And



NEW
kit AD-27
\$169⁹⁵

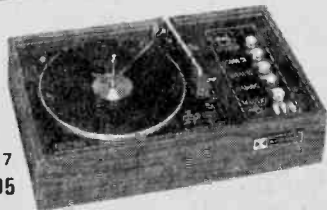


NEW
kit AD-17
\$109⁹⁵



NEW
kit TA-38
\$225⁰⁰

NEW
kit GR-58
\$47⁹⁵

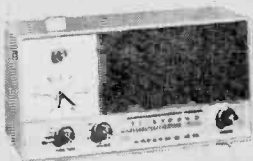

NEW
kit IG-18
\$67⁵⁰
Wired IGW-18
\$99⁵⁰

HEATHKIT AD-27 FM Stereo Compact

The new Heathkit "27" Component Compact was designed to change your mind about stereo compact performance. How? By sounding as if it were made of top quality stereo components... which in fact it is. Heath engineers took their highly rated AR-14 solid-state Stereo Receiver, modified it physically to fit the cabinet, and matched it with the precision BSR McDonald 500A Automatic Turntable. Performance? Here's the AD-27 in detail. The amplifier delivers 30 watts music power... 15 honest watts per channel — enough to drive any reasonably efficient speaker system. Response is virtually flat from 12 Hz to 60 kHz, and Harmonic & IM distortion are both less than 1% at full output. Tandem Volume, Balance, Bass & Treble controls give you full range command of all the sound. Select the FM stereo mode with a flick of the rocker-type switch and tune smoothly across the dial, thanks to inertia flywheel tuning. You'll hear stations you didn't know existed in your area, and the clarity and separation of the sound will amaze you. The adjustable phasing control insures best stereo separation at all times. And the automatic stereo indicator light tells you if the program is in stereo. AFC puts an end to drift too. The BSR Automatic Turntable has features normally found only in very expensive units, like cueing and pause control, variable anti-skating device, stylus pressure adjustment and automatic system power too. Comes complete with a famous Shure diamond stylus magnetic cartridge. The handsome walnut cabinet with sliding tambour door will look sharp in any surroundings, and the AD-27 performs as well as it looks. For the finest stereo compact you can buy, order your "27" Component Compact now. 41 lbs.

HEATHKIT AD-17 Stereo Compact

Using the component approach of the AD-27, Heath engineers took the solid-state stereo amplifier section of the AD-27, matched it with the high quality BSR-400 Automatic Turntable and put both of these fine components in a handsomely styled walnut finish cabinet. The result is the "17" — featuring 30 watts music power, 12 Hz to 60 kHz response, auxiliary & tuner inputs, less than 1% Harmonic & IM distortion, adjustable stylus pressure & anti-skate control and much more. Order your "17" now. 27 lbs.

HEATHKIT TA-38 Solid-State Bass Amplifier

The new Heathkit TA-38 is the hottest performing bass amp on the market, for quite a few reasons. First, there's all solid-state circuitry for reliability. Then there's the tremendous power — the TA-38 puts out 120 watts of EIA music power, 240 watts peak, or 100 watts continuous. Extremely low harmonic & IM distortion too. Many amps suffer from "blow-out" problems, but not the new TA-38 — *YOU CAN'T BLOW IT*... it boasts two 12" heavy duty special design speakers with giant 3 pound 6 ounce magnet assemblies mounted in a completely sealed, heavily damped ¾" pressed wood cabinet — those speakers will take every watt the amp will put out, and still not blow. Sound? The TA-38 is tailored to reproduce the full range of bass frequencies delivered by bass guitars and its sound with combo organs and other instruments is remarkable. Easy 15 hour assembly to the wildest bass amp on the market. Order one now and surprise the guys with the high-priced gear. 130 lbs.

HEATHKIT GR-58 Solid-State AM/FM Clock Radio

The easy way to get up in the morning. Choose the morning news & weather on AM or the bright sound of FM music. AFC makes FM tuning easy. The "Auto" position on the Telochron® clock turns only the radio on, or use the "Alarm" setting for both the radio and the alarm. You can even enjoy fresh coffee when you awake in the morning, thanks to the clock-controlled accessory AC socket on the back of the new GR-58. The handy "snooze" alarm feature lets you wake up gradually for ten minutes to the sound of the radio, then the alarm goes on... push the "snooze" button to silence the alarm for ten minutes more of music or news — the alarm sounds automatically every ten minutes and the "snooze" button turns it off, cycling continuously until the selector switch is moved to another position. Fast, easy circuit board construction, smart blue hi-impact plastic cabinet and top reliability make this GR-58 the clock radio for you. 8 lbs.

HEATHKIT IG-18 Solid-State Sine-Square Wave Generator

A precision source of sine or square waves at a low kit price... that's the new solid-state IG-18 from Heath. Delivers 5% accuracy thru the wide range of 1 Hz to 100 kHz. The sine wave section features less than 0.1% distortion thru the audio range, 8 output voltage ranges from 0.003 to 10V, switch-selected internal 600 ohm load or external load and metered output of both voltage & dB. The square wave section has a 50 nS rise time and three output voltage ranges from 0.1 to 10 V P-P. Both sine & square waves are available simultaneously and the frequency is switch-selected for constant repeatability and fast operation. Circuit board construction makes the new IG-18 easy to build... new Heathkit styling and engineering excellence make it easy to use. Put the new IG-18 on your bench now. 10 lbs.

Hobby... From The Leader



Now There are 4 Heathkit Color TV's...
All With 2-Year Picture Tube Warranty

NEW Deluxe "681" Color TV With Automatic Fine Tuning

The new Heathkit GR-681 is the most advanced color TV on the market. A strong claim, but easy to prove. Compare the "681" against every other TV — there isn't one available for any price that has all these features. Automatic Fine Tuning on all 83 channels... just push a button and the factory assembled solid-state circuit takes over to automatically tune the best color picture in the industry. Push another front-panel button and the VHF channel selector rotates until you reach the desired station, automatically. Built-in cable-type remote control that allows you to turn the "681" on and off and change VHF channels without moving from your chair. Or add the optional GRA-681-6 Wireless Remote Control described below. A bridge-type low voltage power supply for superior regulation; high & low AC taps are provided to insure that the picture transmitted exactly fits the "681" screen. Automatic degaussing, 2-speed transistor UHF tuner, hi-fi sound output, two VHF antenna inputs... plus the built-in self-servicing aids that are standard on all Heathkit color TV's but can't be bought on any other set for any price... plus all the features of the famous "295" below. Compare the "681" against the others... and be convinced.

GRA-295-4, Mediterranean cabinet shown..... **\$119.50**
Other cabinets from \$62.95

Deluxe "295" Color TV... Model GR-295

Big, Bold, Beautiful... and packed with features. Top quality American brand color tube with 295 sq. in. viewing area... new improved phosphors and low voltage supply with boosted B + for brighter, livelier color... automatic degaussing... exclusive Heath Magna-Shield... Automatic Color Control & Automatic Gain Control for color purity, and flutter-free pictures under all conditions... preassembled IF strip with 3 stages instead of the usual two... deluxe VHF tuner with "memory" fine tuning... three-way installation — wall, custom or any of the beautiful Heath factory assembled cabinets. Add to that the unique Heathkit self-servicing features like the built-in dot generator and full color photos in the comprehensive manual that let you set-up, converge and maintain the best color picture at all times, and can save you up to \$200 over the life of your set in service calls. For the best color picture around, order your "295" now.

GRA-295-1, Walnut cabinet shown..... **\$62.95**
Other cabinets from \$99.95

Deluxe "227" Color TV... Model GR-227

Has same high performance features and built-in servicing facilities as the GR-295, except for 227 sq. inch viewing area. The vertical swing-out chassis makes for fast, easy servicing and installation. The dynamic convergence control board can be placed so that it is easily accessible anytime you wish to "touch-up" the picture.

GRA-227-1, Walnut cabinet shown..... **\$59.95**
Mediterranean style also available at \$99.50

Deluxe "180" Color TV... Model GR-180

Same high performance features and exclusive self-servicing facilities as the GR-295 except for 180 sq. inch viewing area. Feature for feature the Heathkit "180" is your best buy in deluxe color TV viewing... tubes alone list for over \$245. For extra savings, extra beauty and convenience, add the table model cabinet and mobile cart.

GRS-180-5, table model cabinet and cart..... **\$39.95**
Other cabinets from \$24.95

Now, Wireless Remote Control For Heathkit Color TV's

Control your Heathkit Color TV from your easy chair, turn it on and off, change VHF channels, volume, color and tint, all by sonic remote control. No cables cluttering the room... the handheld transmitter is all electronic, powered by a small 9 v. battery, housed in a small, smartly styled beige plastic case. The receiver contains an integrated circuit and a meter for adjustment ease. Installation is easy even in older Heathkit color TV's thanks to circuit board wiring harness construction. For greater TV enjoyment, order yours now.

kit **GRA-681-6**, 7 lbs., for Heathkit GR-681 Color TV's..... **\$59.95**



kit **GRA-295-6**, 9 lbs., for Heathkit GR-295 & GR-25 TV's..... **\$69.95**

kit **GRA-227-6**, 9 lbs., for Heathkit GR-227 & GR-180 TV's..... **\$69.95**

kit GR-681

\$499.95

(less cabinet)

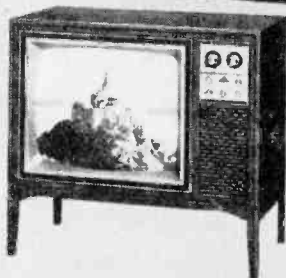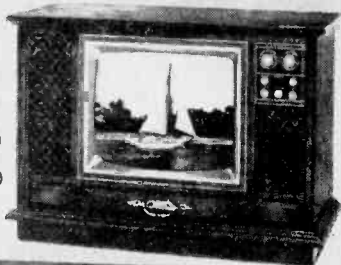

kit GR-295
now only

\$449.95

(less cabinet)

kit GR-227

now only

\$399.95

(less cabinet)



kit GR-180

now only

\$349.95

(less cabinet)



New Wireless
TV Remote Control
For GR-295, GR-227
& GR-180

\$69.95

New Wireless
TV Remote Control
For GR-681

\$59.95



NEW

FREE 1969 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 139-5
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.

Enclosed is \$....., plus shipping.

Please send model (s).....

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name.....

Address.....

City.....

State.....

Zip.....

Prices & specifications subject to change without notice.

CL-350

IT'S THE LAW

By Jack Schmidt




"Don't knock it! Our confession rate is way up since we got this rig!"




"Watch that feedback, Sarge!"



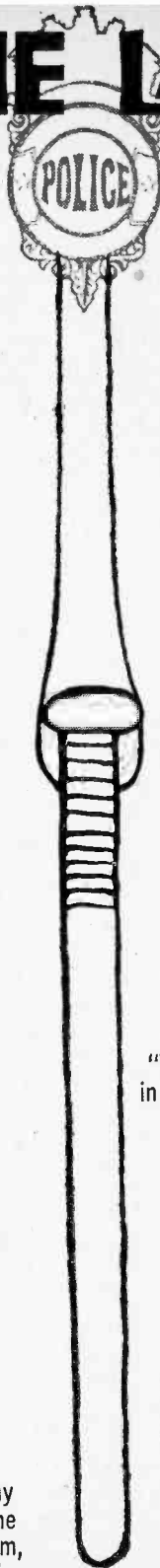"To my oldest brother, Tom, I leave my AC bench supply. To my sister, Ann, the signal generator. To my nephew, William, the 555 scope. To my aunt, Mil, . . ."



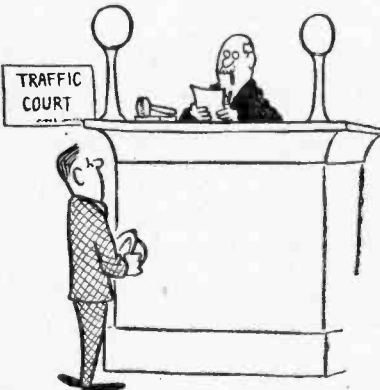"Your name better be Fred C. Corey or you'll be telling it to the judge."




"You're accused of a 73 Hz Doppler shift in a 10,525 MHz zone. How do you plead?"



"To all units—State Police have an undetectable radar on Weed Road. . ."

THE ROCKS IN YOUR RADIO

by John Dixon,
WA2FIC

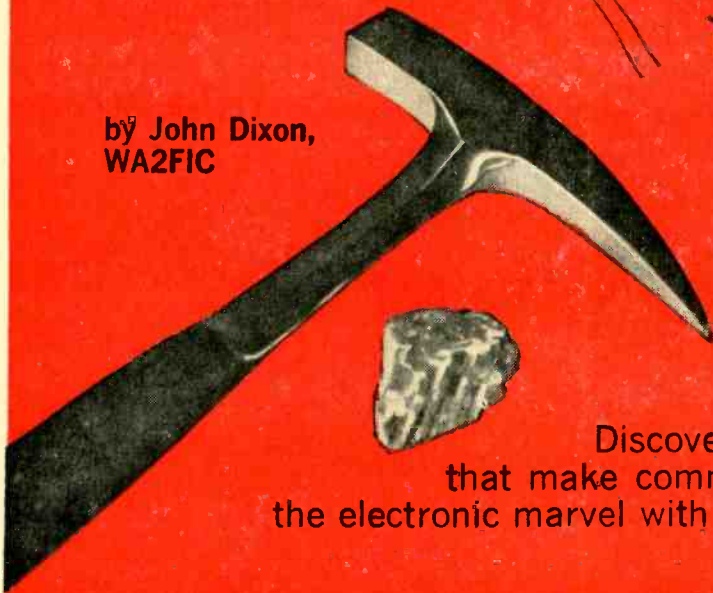

Discover the rocks
that make communications
the electronic marvel with talk power!

BELIEVE it or not, a rock is a natural enough object in a group of radio components, because almost every radio component you can bring to mind is made from one or another kind of rock. Much of the history of radio and electricity is connected with discoveries of properties of different rocks. The ancient Greeks discovered that amber, when rubbed with fur, produced static electricity. Their name for amber, *ēlektron*, is the basis for many of our words connected with electricity. Glass, which is made from sand and a rock called sandstone, was the material used for further study of static electricity. And, the early crystal radios used galena as their crystal detector. Galena is a rock, found in the central U.S. and other parts of the world, and is the chief ore of lead. But, rocks are by no means confined to the history of radio. They are part and parcel of the present state of the art, and they hold the promise of an exciting store of future improvements in all areas connected —Continued overleaf

e/e ROCKS IN RADIO

in any way with radio and electronics.

Cu. Look inside a typical radio. The first things you notice is the maze of wire—*copper* wire. The electrical industry used over 850,000 tons of this metal in 1968, and it is found in almost every component used in radio. Fortunately, the rocks from which copper is extracted are widespread.

Although much copper occurs in an almost pure state, there are a few other rocks which contain it compounded with other metals and sulfur. One of these rocks is chalcopyrite, a compound of copper, iron and sulfur, with the chemical formula CuFeS_2 . Chalcopyrite is one of the rocks known as *fools gold*, because of its appearance. This rock is mined chiefly in Quebec, Canada and much gold is found with deposits of chalcopyrite.

Al. Aluminum is another metal that is widely used in the radio industry. The chassis of the typical radio is now made of aluminum, with countless other radio parts, from washers to heat sinks made partially or totally of aluminum. And, aluminum comes from a rock, one called bauxite. The chief sources of bauxite are Jamaica and Surinam, with other deposits of importance scattered throughout the world. Bauxite is a rock that is usually light brown in color, and, like


aluminum, is surprisingly light in weight. It was first noticed near a town in France called Les Beaux, from which the rock received its name. Although it was known to contain aluminum, it was not a commercially valuable source of this metal because there was no practical way to extract the aluminum from it.

In 1886, simultaneous discoveries of a method of extracting aluminum from bauxite were made by Charles Martin Hall and Paul Heroult, and since then aluminum has been produced in quantities that were demanded. During World War II, the metal was produced in fantastic quantities to meet the war demands, and since then the demand has been very high.

Bauxite is still the chief rock which supplies aluminum, but active research to find a way to extract profitable quantities of aluminum from other rocks is now under way. This is a wise course, because the light weight, ease of working, and resistance to corrosion will keep the demand for aluminum as high as it now is.

There's More. Besides aluminum and copper, many other metals are used in radio, and each of these metals is extracted from one or more kinds of rock. Silver occurs combined in a few different kinds of rock, and is found with deposits of galena. Mercury, used in batteries and switches, occurs as an ore called cinnabar, a compound of mercury with sulfur. Nickel, cobalt, zinc, osmium are metals that are of some importance in radio. They each have a source which is a rock.

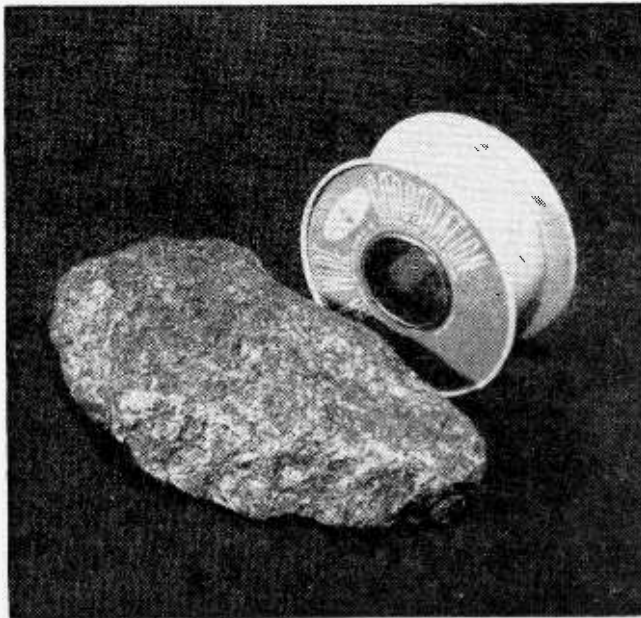Iron, and steel, are obviously important in radio. But, one of the rocks that contains iron deserves special mention, since it has historical importance in the study of magnetism. This rock is magnetite. It is iron compounded with oxygen, with a chemical formula Fe_3O_4 . Also known as lodestone, this rock was



This is a specimen of chalcopyrite, from which copper is made. Copper is used primarily as a conductor, such as copper wire. Chalcopyrite is mined in large quantities near Quebec.


Bauxite is an ore from which aluminum is extracted. The rock can be white to reddish brown in color, and like aluminum is very light.

noted in earliest times for its magnetic attraction. Discoveries in magnetism were as important to radio as were those in electricity, and lodestone can be considered the amber of magnetism.

The Brittle Stuff. Not all of the rocks in your radio are there because they are sources of metals; some of the very important components of radio are not metal at all. Glass was mentioned as being historically important, but it is just as important today. Capacitors, tubes and other often unnoticed, but undeniably important components depend on glass for their proper operation.


Glass comes from a rock known as sandstone, and from common sand. Chemically, sandstone and sand are compounds of silicon and oxygen, with a chemical formula of SiO_2 . Sandstone is mined, in the United States, in Pennsylvania and West Virginia as Oriskany sandstone, a very pure and large supply to the glass industry in the east. Other sandstones are the St. Peter, found in Illinois, Minnesota and Missouri, and a less pure variety found in New Jersey. Sand, as taken from the beaches may be used if it is of good quality. This means that it contain very little impurity in the form of other metals. These metals will discolor the glass. Though for some applications colored glass is used, most glass used in radio is colorless. The glass in a red panel light might contain some copper, and a blue lamp might contain some cobalt, but an overheated plate

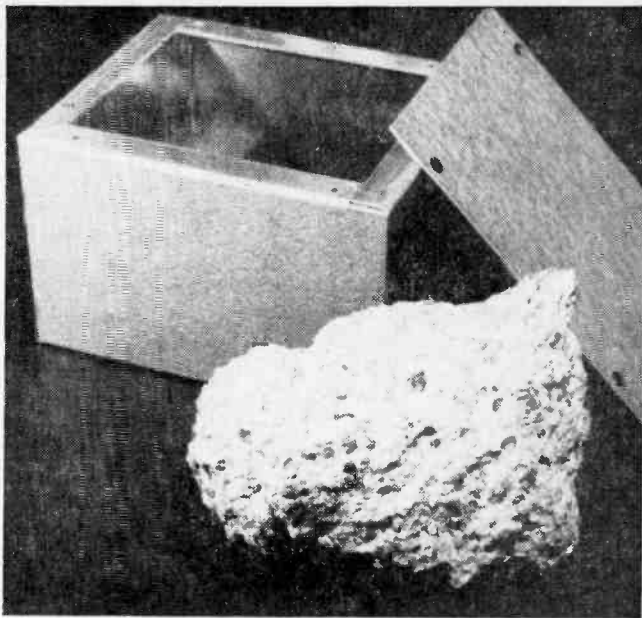These very beautiful quartz rocks are valued as piezoelectric material. The rock here is about four inches high, and can be used to make many plug-in crystals like the ones shown.



element in a vacuum tube will be seen best through clear glass.

Crystals. When you hear an amateur radio operator say he is "rockbound," you find an interesting recognition of the close relationship between rock and radios. This phrase means that the ham is operating on a frequency that is determined by a quartz crystal, as opposed to his being free to move up and down the band with a VFO. The quartz crystal is, in fact, a small slab of a rock, cut to a certain size and mounted in a

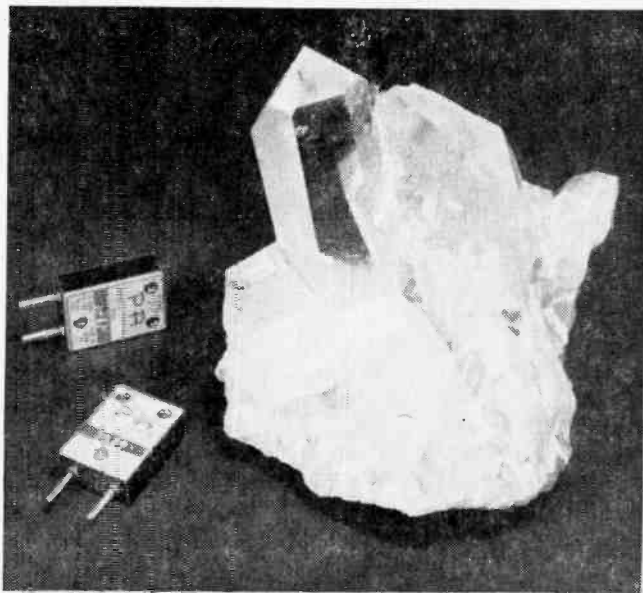

e/e ROCKS IN RADIO

holder. This rock is known as "rock" quartz, and looks like large chunks of glass.

Rock quartz is chemically identical to sand and sandstone, being a compound of silicon and oxygen, but the fact that it can occur in a single large crystal makes it valuable as a frequency control.

Mica. If you use a quartz crystal to control the frequency of an oscillator, the other components in this oscillator will be chosen to equal the stability of the crystal. One of the stables of capacitors is the mica capacitor, and this too depends on a rock. Although mica occurs in "books" that look like thin sheets of plastic stuck together, it is nonetheless a true rock. These widespread books can be quite large, even as large as several feet in each dimension. There are several varieties of mica, but one is used in the mica capacitor. This kind is called Muscovite mica, because it was used by the Russians as windowpanes in their houses and portholes in their ships.

Chemically, Muscovite mica is very complex, containing potassium, aluminum, silicon, oxygen and hydrogen. The dimensional stability and dielectric strength of this type of mica make it valuable. Other micas, used in tubes as spacers, are valuable for their ability to stand high temperatures in addition to their stability.

The Dirty Stuff. Coal is a rock you might not connect with radio. But the carbon used in resistors and the plastics used in many components are based for a large part on this widely occurring rock. Coal is also used in the manufacture of many components in radio, but is not a part of the finished product.

And One More. A class of rocks that are used to make ceramics are important


A book of mica may look like just a rock in the picture, but you can peel it apart with a fingernail. Mica finds uses as a dielectric material and wherever a stable support is needed. Mica spacers in tubes, for example, minimize changes in dimension due to heating of the cathode.

to the radio industry. These ceramics are the insulators on switches, the sockets for tubes, forms for coils and innumerable other parts. The rocks used for these ceramics are the feldspars and kaolinite. Feldspars are a variety of rocks that are very common, and are, in fact, the most abundant kind of rock. They are all aluminum silicates, but are different in that they contain other elements such as potassium, sodium and calcium. Despite the chemical differences, they are extremely difficult to tell apart with the naked eye.



Kaolinite is quite similar to the feldspars, yet it is noticeably different. It is a hydrous aluminum silicate, and is a lustrous white. The feldspars and kaolinite, when processed differently yield many types of ceramic. The most valuable ceramic in the radio industry is steatite.

The Last Roundup. This, more or less is the extent of the relationship between radio and the rocks. However, we have purposely left mention of two categories until last, for they represent the future of radio to some degree.

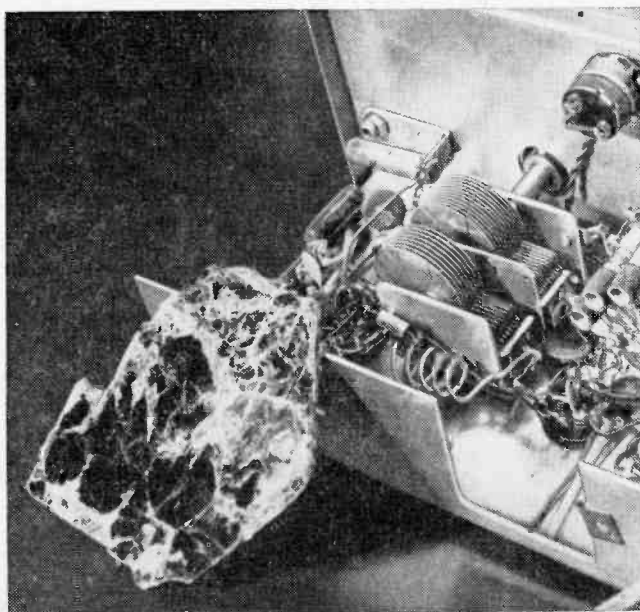Naturally, we all think of the future of radio in terms of solid state devices rather than in terms of tubes. And, these devices are also related to one or another form of rock. A little earlier, you may have connected the mention of silicon with the diode or transistor. The silicon for these devices comes from the same rocks that glass
(Continued on page 109)



**SPECIAL
SWL
CONSTRUCTION
PROJECT**

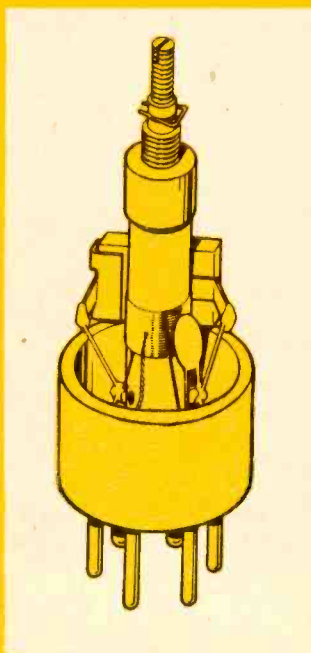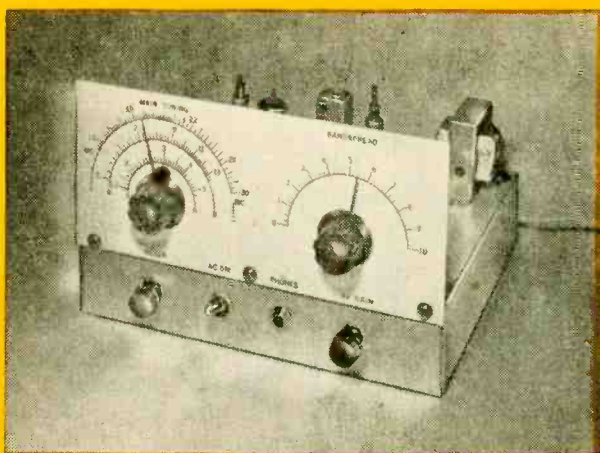

Build the first Electronic Transplant Receiver

by Charles Green, W6FFQ

The sensitivity of the regen couples with the stability of the superhet to make for a receiver that's hotter than hot!

Plenty of electronics hobbyists have experienced the fun of building and firing up their own receiver. But we'll bet a dormouse to a doughnut that you've never tackled a transplant: a superhet/regen combo. By way of explanation, this unusual circuit offers all the stability that has made the superhet the standard of the radio world, *plus* the fantastic sensitivity for which the regenerative detector is famed. This unusual combo uses two tubes in a simplified super-

e/e TRANSPLANT RECEIVER

het circuit, with pre-wound plug-in coils covering 1.7 to 30 MHz. Bandsread tuning makes easy separation of signals in crowded portions of the band; the audio circuit has plenty of gain to drive either a pair of high-impedance phones or an auxiliary amplifier.

About the Circuit. Signals from J1 are tuned by plug-in coils L1A (Band A), L1B (Band B), or L1C (Band C), and the main tuning capacitor C4A or bandsread capacitor C5A. These capacitors (associated with mixer V1A) are ganged with the oscillator circuit (V1B) capacitors C4B and C5B, which tune plug-in coils L2A, L2B, or L2C so the oscillator RF output is always 455 kHz above the incoming signal frequency. This RF output is coupled to the mixer grid via the gimmick capacitor, and the resultant 455-kHz output is fed through tuned IF transformer T1 to regenerative detector V2A. The gain of the mixer circuit is controlled by R4.

The regenerative detector circuit feedback is formed by the C9, C11, and L3, with regenerative action controlled by R7. The

detected audio signals are fed via C14 to the amplifier stage (V2B). The resulting amplified signals are connected through C16 to jack J2.


The B+ and tube filament AC supply are powered by T2, D1, and R/C filter circuit of R13-C19.

Building It. The receiver is built on a 7 x 9 x 2-in. aluminum chassis, with a 7 x 9-in. bottom plate. Best way to start construction is to tape a section of paper on the chassis and lay out the component locations as shown in our photos (see next page). For best results, follow our layout as closely as possible.


The X and Y sockets in our receiver are 6-pin sockets to fit our coil bases. Since there's nothing much critical here, you can use octal sockets and tube bases, or the 6-pin coil forms specified in the Parts List.

Drill the component mounting holes, and install the parts on the chassis. We cut 3/8-in. holes for the T2 leads and a 1/2-in. hole for the C4 and C5 leads. Install rubber grommets in these holes.

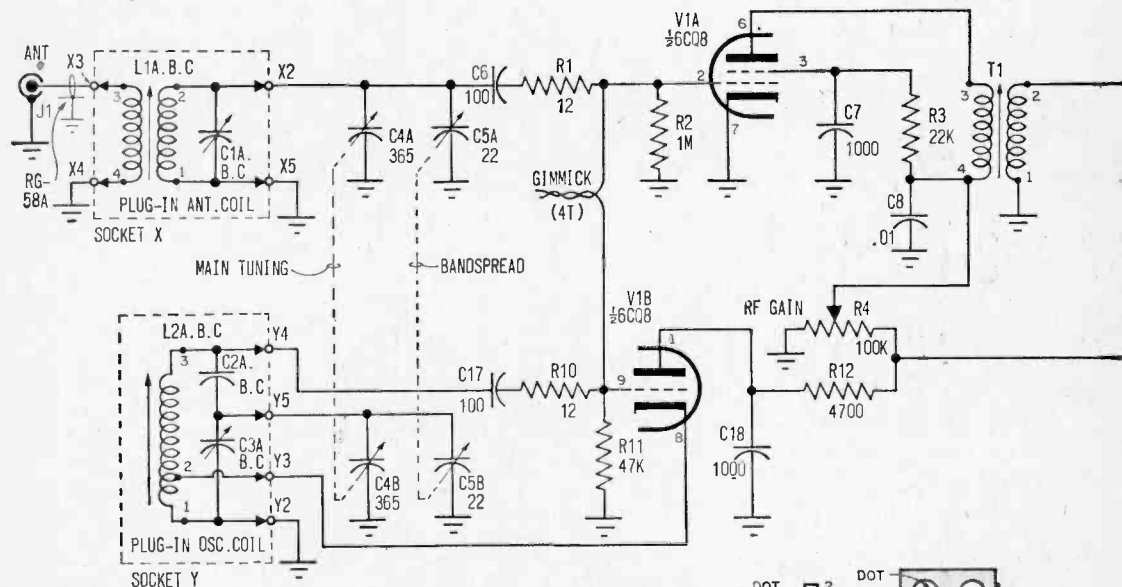Wire the receiver as shown in the schematic diagram. Use #18 solid hookup wire or bus wire for the C4 and C5 connections to the X and Y sockets, and dress these wires away from the chassis and components. Connect C6 to R1 and connect C17 to



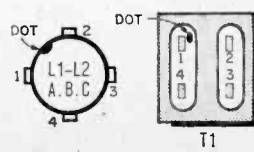Two dual-purpose tubes in unusual superhet/regen circuit account for unit's remarkable stability and sensitivity. Pot R4 controls gain of mixer V1A; pot R7 controls regeneration of detector V2A. Main tuning is done with capacitor C4A/B; bandsread tuning with C5A/B. T1 is peaked to 455 kHz.



PARTS LIST FOR THE ELECTRONIC TRANSPLANT RECEIVER


NOTE—Capacitors rated 400 VDC minimum ceramic or mica unless otherwise noted.

- C1A, C3A—2.7 to 30-pF trimmer capacitor (ARCO 461 or equiv.)
 C1B, C3B, C1C, C3C—4 to 40-pF capacitor (ARCO 422 or equiv.)
 C2A—2000-pF capacitor
 C2B—5000-pF capacitor
 C2C, C8, C14—.01- μ F capacitor
 C4A, C4B—Dual 365-pF per section (2 gang) variable capacitor (Lafayette 32 T 1102 or equiv.)
 C5A, C5B—Dual 22-pF per section (2 gang) variable capacitor (J. W. Miller 1461-2)
 C6, C17—100-pF capacitor
 C7, C15, C18, C20, C21—1000-pF capacitor
 C9—1-12-pF capacitor (ARCO 420 or equiv.)
 C10—220-pF capacitor
 C11, C12—470-pF capacitor
 C13, C16—0.1- μ F capacitor
 C19A, C19B—Dual 50- μ F, 150-V electrolytic capacitor
 C22—2- μ F, 150-V electrolytic capacitor
 D1—1N2071 silicon diode or equiv. (100 mA at 200 PIV minimum)
 J1—Phono jack, panel mounting type
 J2—Phone jack to fit earphone plug
 Gimmick capacitor—4 turns of solid #22 hookup wire, plastic covered
 L1A—Antenna coil (J. W. Miller B-5495-A)
 L1B—Antenna coil (J. W. Miller C-5495-A)
 L1C—Antenna coil (J. W. Miller D-5495-A)
 L2A—Antenna coil (J. W. Miller B-5496-C)

- L2B—Antenna coil (J. W. Miller C-5496-C)
 L2C—Antenna coil (J. W. Miller D-5496-C)
 L3—550 μ H RF choke (J. W. Miller 4649 or equiv.)

NOTE—All resistors $\frac{1}{2}$ -watt, 10% unless otherwise noted.

- R1, R10—12-ohm-resistor
 R2—1-megohm resistor
 R3—22,000-ohm resistor
 R4, R7—100,000-ohm, linear-taper potentiometer
 R5—2.2-megohm resistor
 R6, R11, R14—47,000-ohm resistor
 R8—100,000-ohm, 1-watt resistor
 R9—4.7-megohm resistor
 R12—4700-ohm resistor
 R13—1000-ohm resistor
 S1—Spst toggle or slide switch, 117 VAC, 1A min. rating
 T1—455-kHz IF transformer (J. W. Miller 12-C1)
 T2—Power transformer; sec: 125V-15 mA, 6.3V-0.6 A (Allied 54C1410 or equiv.)
 V1—6CQ8 vacuum tube
 V2—12AT7A vacuum tube
 X—Socket to fit plug-in antenna coils L1A, B, C (see text)
 Y—Socket to fit plug-in oscillator coils L2A, B, C (see text)
Misc.—Tube bases for plug-in coils L1A, B, C and L2A, B, C (6-pin tube bases used) or 6-pin plug-in coil forms (Allied 47C6697—see text), 7 x 9 x 2-in. aluminum chassis and 7 x 9-in. bottom plate, cardboard for panel, AC line cord, knobs, terminal strips, RG-58A/U coax, wire, solder, etc.

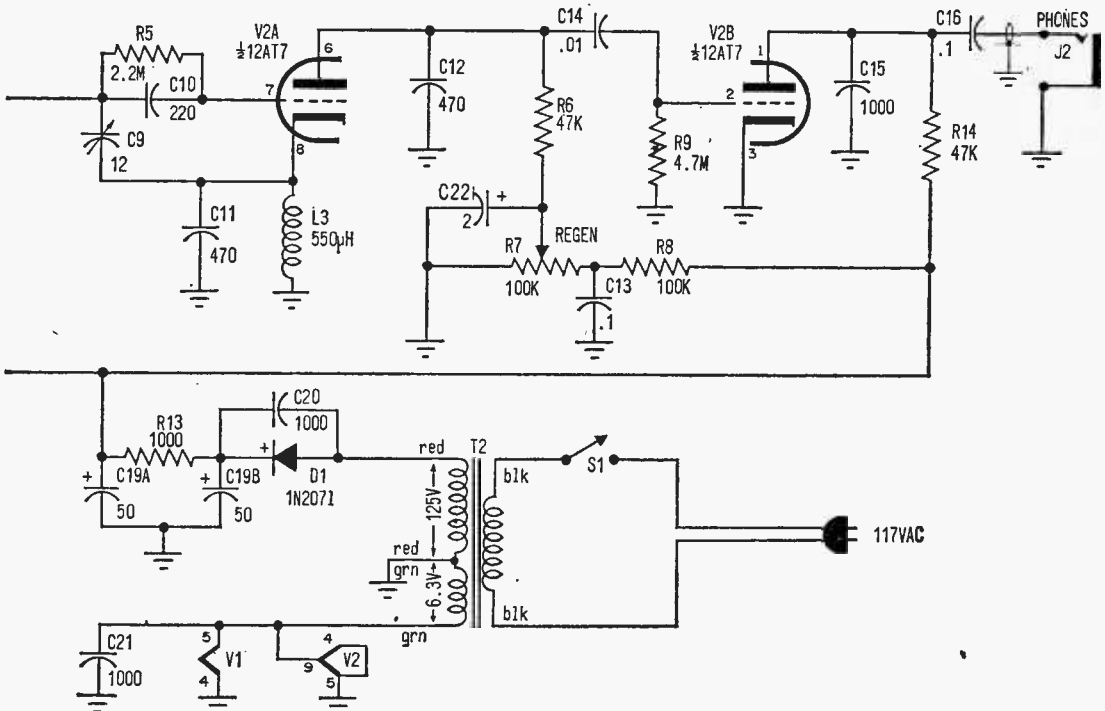

e/e TRANSPLANT RECEIVER

R10 with very short connections. Connect these assemblies with short leads between V1 and the X and Y sockets as shown in the schematic. Note that RG-58A/U coax should be used for the J1 and J2 connections.

Capacitor C9 is mounted by its lugs between V1 and T1 as shown in our photo. Keep the V1 and V2 circuit components grouped closely around their sockets with short leads. The gimmick capacitor is made by tightly twisting together two short lengths of #22 plastic covered hookup wire for four turns.


Keep the B+ and AC power leads away from the RF circuits of V1 and V2. The plug-in coils are assembled as shown in the photo and the coil table. Use lengths of bus wire to connect the coil and capacitors to their bases, or coil forms. Keep the leads

as short and rigid as possible to prevent coil movement.

Either 6-pin tube bases, octal bases or the 6-pin plug-in coil forms specified in the Parts List can be used. Make sure that you clean the base pins and socket contacts of all dirt and solder flux before soldering the coil leads in place.

We used a 4 x 9-in. section of heavy white cardboard for our dial panel. The panel is mounted on front of the chassis with sheet metal screws. Install a bottom plate on the chassis after calibration to protect against component damage or electrical shock. We used lengths of bus wire cemented in the C4 and C5 knobs for dial pointers; the wires are painted black.

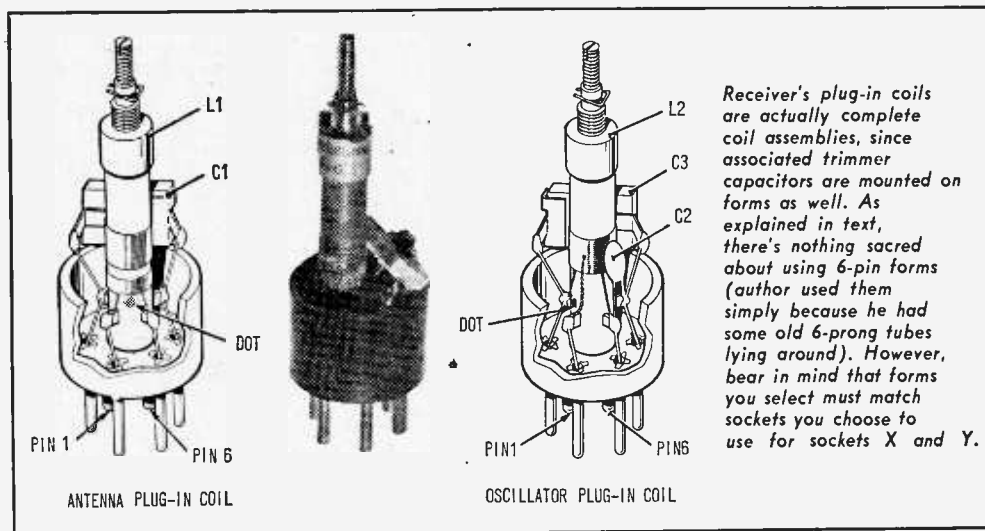Alignment and Calibration. Plug in the tubes and the band A coils (L1A-L2A) and connect the receiver to the AC line. Turn S1 on and allow the receiver to warm up for a few minutes. Connect a set of high impedance earphones (2000 ohms or high-





ANTENNA AND OSCILLATOR COIL TABLE

Band	Antenna Coil (X Socket)	Oscillator Coil (Y Socket)
A 1.7 to 5 MHz (Red)	L1A—J. W. Miller B-5495-A C1A—2.7 to 30 pF (ARCO 461)	L2A—J. W. Miller B-5496-C C2A—2000 pF C3A—2.7 to 30 pF (ARCO 461)
B 5 to 13 MHz (Green)	L1B—J. W. Miller C-5495-A C1B—4 to 40 pF (ARCO 422)	L2B—J. W. Miller C-5496-C C2B—5000 pF C3B—4 to 40 pF (ARCO 422)
C 13 to 30 MHz (Blue)	L1C—J. W. Miller D-5495-A C1C—4 to 40 pF (ARCO 422)	L2C—J. W. Miller D-5496-C C2C—.01 μ F C3C—4 to 40 pF (ARCO 422)

Some Construction Tips

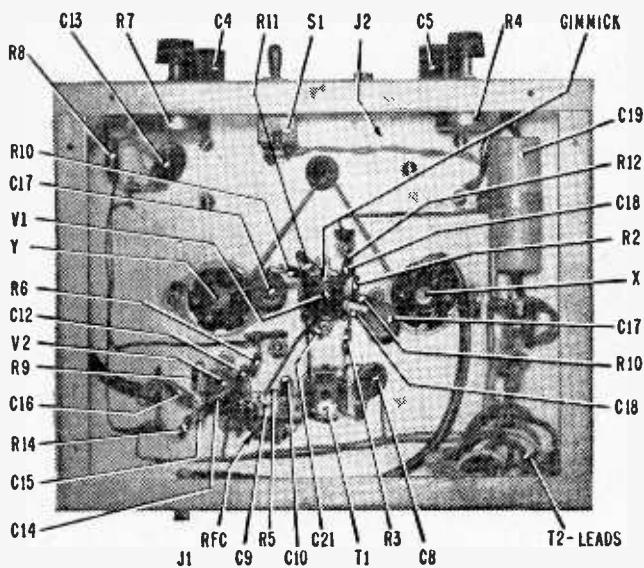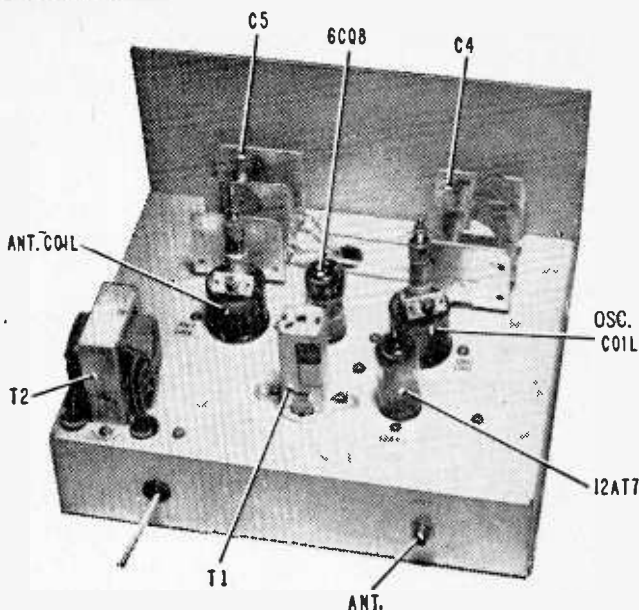Best way to undertake construction is to first purchase all parts, then mark position of major components: i.e., capacitors C4 and C5, sockets X and Y, transformers T1 and T2, and sockets for V1 and V2. After drilling holes and mounting these components, you can then proceed to wire circuit.



Removing bottom cover from Transplant Receiver reveals circuit that is relatively wide open and comparatively easy to wire. Circuit is ideally viewed as three distinct circuits on single chassis: i.e., oscillator/mixer (V1 and associated components); detector/amplifier (V2 and associated components); and power supply (T2, D1, et al).

er) to J2 and set C5 to minimum capacity.

Set R4 and R7 to midrange and connect a signal generator between pin 2 of V1 and chassis ground. Set the generator controls for a 455 kHz modulated output and adjust the T1 tuning slugs for maximum signal in the phones. Then adjust C9 so that the detector will oscillate with R7 in midrange position.

Next, connect the signal generator to J1 and adjust the generator frequency and C4

position as indicated in the alignment table. Make the adjustments as shown for each band, then calibrate the remainder of the band. We used a pencil to mark the dial lightly, then removed the dial panel and used rub-on lettering to identify the frequency points. The bandspread dial was marked from 0 to 10 as shown in the photo.

We used a small drop of model airplane paint to seal the coil and trimmer adjustments, and painted the top of each coil form

e/e TRANSPLANT RECEIVER


to identify the bands (not the coils). We painted the band A coils red, band B green, and band C blue.

Operation. Plug in the pair of coils covering the band desired. Make sure that the antenna coil is in the X socket, the oscillator coil in the Y socket. For best results, use a good ground connection and an outside antenna mounted as high as possible. Either a

T1's mounting screws, but you might prefer to install a suitable ground terminal on the rear of the chassis.

A transistorized amplifier can be plugged into J2 for speaker operation, or to give additional audio gain to dig out those weaker stations more easily. Use the main tuning capacitor (C4) to tune across the band with the handsread capacitor (C5) set a minimum capacity. When you desire to tune a particular portion of the band, set the main tuning capacitor to the high frequency end, and tune the band portion with the band-spread capacitor.

Completed Transplant Receiver has all user-operated controls neatly grouped across front panel. Once antenna and ground are connected, unit is plugged into AC outlet and pair of high-impedance phones plugged into jack J2. Switch S1 is flicked on, and, after unit warms up, R7 is advanced until rushing sound is heard in phones, then backed off slightly. RF gain control R4 acts as volume control and also prevents strong signals from overloading detector stage.

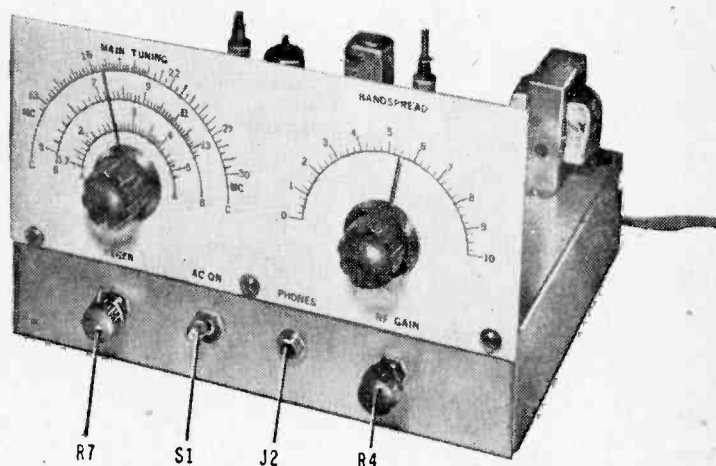


single wire or dipole type will work OK.

Speaking of a ground connection, you'll note that the schematic doesn't indicate one, since the author didn't include provision for one in his prototype. But as we've said, we found that a good ground is required for best results. We ran the ground lead to one of

The receiver is most selective with R7 set just below the point of oscillation. When R7 is advanced to cause the detector to oscillate, CW and sideband stations can be received with careful tuning. RF gain control R4 should be adjusted to prevent overloading of the detector circuit. ■

TRANSPLANT RECEIVER ALIGNMENT TABLE

Band	Signal Generator Frequency (MHz)	Setting for C4A, B	Adjust for Maximum Signal
A (Red)	1.7 5	Near maximum capacity. Near minimum capacity.	L2A and L1A. C1A and C3A. Repeat adjustments.
B (Green)	5 13	Near maximum capacity. Near minimum capacity.	L2B and L1B. C1B and C3B. Repeat adjustments.
C (Blue)	13 30	Near maximum capacity. Near minimum capacity.	L2C and L2B. C1C and C3C. Repeat adjustments.

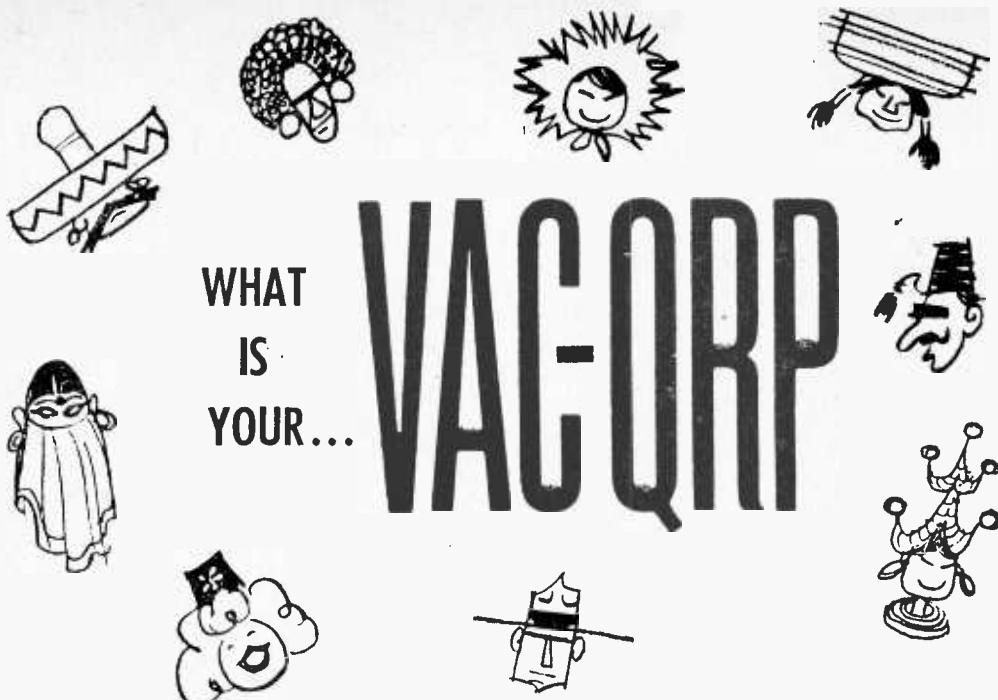

WHAT
IS
YOUR...

VAC-QRP

Now an SWL can rate his DX-Quotient in terms of low-power stations he almost didn't hear!
by Don Jensen

- How do you rate as a DXer? What's your DX-Quotient? Often these are tough questions to answer since there are few real yardsticks of ability and progress in shortwave listening.

Many listeners tally the number of different countries they've QSLed. Though useful, this popular means of evaluating DXpertise suffers from one basic flaw—it ignores the power factor.

While nearly every DXer has heard the 100,000-watt Deutsche Welle, the international Voice of Germany, how many have pulled in Munich's 10-kilowatt Bayerischer Rundfunk? Country hunters can claim Germany in their totals by verifying either, but the little domestic shortwave outlet is a better test of tuning skill.

What's the answer? "Watts is the answer," echo today's DX in-crowd, "and the fewer the better!" They measure their DX-Quotient in terms of VAC-QRP. VAC means, simply, *Verified All Continents*. QRP, a term borrowed from the hams' lexicon, signifies low power transmissions.

It's a cinch! Check your QSLs, or the *WORLD RADIO TV HANDBOOK*, the SWL's "bible," for the transmitter strengths of the low power stations you're verified. Pick the six best—one from each continent, North America (over 1000 miles distant), South

America, Europe, Asia, Africa and Oceania—and add their wattage. Divide the sum by a thousand and, *voila*, your VAC-QRP-DX-Quotient! Here's a typical example:

North America—CFCW, Montreal	Watts 500
South America—YVLK, Caracas	10,000
Europe—Deutsche Welle, Cologne	100,000
Asia—R. Ankara, Ankara	100,000
Africa—Sierra Leone R. & TV, Freetown	5,000
Oceania—R. New Zealand, Wellington	7,500
	Total 223,000
VAC-QRP = Total ÷ 1000 = 223	

As you sharpen your skills and tune more of the weaker stations, substitute them in your calculations. If you should QSL Bayerischer Rundfunk, use it, not Deutsche Welle as your European entry. Your DX-Q drops to 133. Like golf, the lower the score, the better you're doing.

How Long Can It Go? Theoretically at least, a DX-Quotient of about 0.8 is possible, considering the stations now on the air. But let's face it, it'll be a cold day in Calcutta before that ultimate is reached.

There are plenty of lower powered stations to test your abilities. For openers, check the adjoining list. And there many more where they came from. Some are tough enough to

e/e VAC-QRP

curl a veteran DXer's long wire. Others are within the realm of a persevering beginner.

Some rather remarkable records have been racked up by listeners. West coast DXer, Bill Sparks, whose listening career dates back to the 30s, has chalked up a post-war DX-Q of 26.3. Considering only his older QSLs from the days when shortwave was relatively free of interference, Sparks scores 6.0.

Another Californian, Lt. Bruce Churchill, tallies his DX-Q at 7.25, while in the mid-west, Gerry Dexter records 6.2. Chicagoan

Frank Peters, a veteran SWL, figures his at 3.85! These fellows are real pros when it comes to tuning the weak ones and their DX-Quotients reflect this skill.

How Do You Rate? You'd better peddle your crystal set if you can't break 500. If you're over 250, consider yourself a progressive novice. Hovering around the century mark? Keep up the good work. If your DX-Q is between 50 and 100, you've made the grade and if you score less than 50, you're up there with the pros. Under ten? You're a real expert.

And on that glorious someday when your DX-Quotient drops below one—*Zap! Pow! Boing!* SUPER DXER!!!

WANT TO IMPROVE YOUR DX-QUOTIENT? TRY THESE!

Continent	Station	Country	Freq. (kHz)	Power (Watts)
NORTH AMERICA	Radio CKWX	Canada	6,080	10
	Radio CFVP	Canada	6,030	100
	Radio CHNX	Canada	6,130	500
	Radio Zelaya	Nicaragua	5,950	500
	La Voz de Honduras	Honduras	5,875	1,000
SOUTH AMERICA	Radio Amazonas	Peru	6,140	25
	Radio Nickerie	Surinam	3,240	50
	Falkland Is. Bc. Sv.	Falkland Islands	3,958	500
	Radio Colosal	Colombia	4,945	1,000
	Ecos de Pasto	Colombia	6,085	1,000
	Radio El Morro	Chile	9,525	1,000
EUROPE	Radio Shkodra	Albania	8,215	200
	Pathfinders Station	Poland	7,306	350
	Radio Kozani	Greece	7,215	500
	Radio Renascenca	Portugal	6,155	3,000
	Bayerischer Rundfunk	Germany	6,085	10,000
ASIA	Radio Nha Trang	Vietnam	9,720	200
	Thai TV Radio	Thailand	7,105	1,000
	Armed Forces R-TV Sv.	Taiwan	3,990	1,000
	Philippine Bc. Sv.	Philippines	3,286	2,500
	Radio Brunei	Brunei	4,963.5	10,000
AFRICA	Tristan Radio	Tristan da Cunha	3,290	40
	Radio ZNF-4V	Lesotho	3,824	100
	Radio Clube Benguela	Angola	5,042	1,000
	Radio Cordac	Burundi	4,897	2,500
	ORTF	Comoro Islands	3,331	4,000
OCEANIA	Radio Mt. Hagen	New Guinea Territory	2,450	250
	Radio Villa	New Hebrides	3,905	500
	Radio Tarawa	Gilbert and Ellice Is.	4,912.5	2,000
	VQ02	Br. Solomon Is.	3,995	5,000
	Radio New Zealand	New Zealand	9,540	7,500

Here's how I turned an inexpensive set into a real go-getter—R. E. Schemel

Newly arrived in the U.S., I went straight to the local ham radio shop with the firm intention of buying a multiband transistor radio. My purpose: to tune in those distant shortwave broadcasts from home. I looked around the shop, but, seeing nothing in the price range that a two-month stay here would justify, I wandered over to the sales section. To my delight, there was the grooviest little communications receiver you ever saw—a Lafayette HA-226. And—wait for it!—it was going for the lower-than-low special sales price of \$13.88!

Reckoning it to be a cheap import with little or no performance, I asked for a demonstration. Truth be known, I firmly expected a stern reply that for the price did I really expect a demonstration as well? Instead, a courteous salesman connected a shielded antenna lead and pointed out that the radio was perfect, adequate for SW broadcasts, but not exactly a piece of high-class communications equipment.

I played with it for a few moments. It seemed to pull in SW broadcasts quite well except on the highest frequency range, something I put down to bad conditions. I hurriedly said I would take it before the salesman changed his mind about the price. At the checkout, the girl saw the price and shouted to the salesman with a note of astonishment in her voice, "You shouldn't have, Jack!" I beat it out of that shop so fast that I forgot to ask for the instruction book.

When I got the baby back to the motel, with a reel of wire for an antenna (and that cost me all of a dollar, compared with \$13.88 for the radio!), it worked really well on two of the shortwave bands, but not on the 12-30 MHz range. I put this down to the shielding of the motel room, and thought nothing more about it.

Zeroing the S. After a while, I noticed that the S-meter was altering its zero position from range to range, but I resisted an almighty temptation to fiddle inside. However, I did take off the covers, and found a solid type of chassis construction that augered well for future modifications. None of this printed-circuit stuff to inhibit one's enthusiasm in this little radio!

A few days later, we moved into an apartment, and by this time curiosity had got the better of me. I took off the bottom lid and saw what the trouble was. The supply for grids 2 and 4 of the 6BE6 converter was run from the same dropper resistor as the screen grid of the 6BA6 IF amplifier. As the oscillator section drew differing currents on the different wave-bands, the 6BA6 screen grid varied in voltage, and this caused the cathode current to vary.

Shorting the dropper resistor proved the point. Therefore, purloining a soldering iron and the necessary parts, I made the modification shown in Fig. 1. This cured the problem completely, and now the S-meter stayed firmly at zero on all bands.

In the interim, I had determined that this set was a real goer, defi-



W=HOT RECEIVER
VOI-WOZK + ZOR-
ROZ-
GZ-RMDROS

e/e HOT RECEIVER

nately better than the average domestic type of radio. It really pulled in stations on the three lower frequency bands, but that 12-30 MHz band remained sullenly silent. I still explained it away with bad conditions. But one fine day it clicked—stations on the 31-Meter band were strong on Range C (4.3-12 MHz), but couldn't even be heard on the bottom end of Range D (12-30 MHz)!

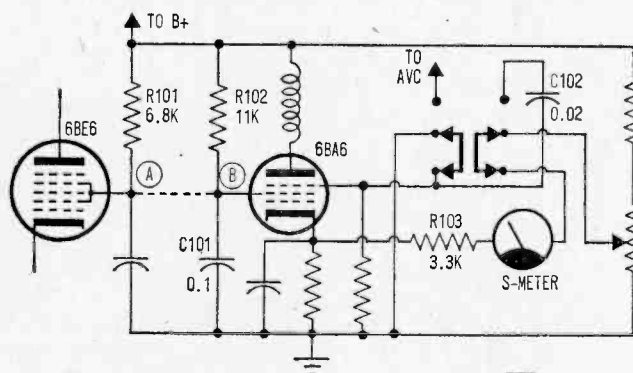



Fig. 1. Common dropper resistor for grids 2 and 4 of 6BE6 converter and screen of 6BA6 IF was first circuit shortcoming uncovered in Lafayette HA-226. Author removed jumper between points A and B, as shown, and sat back to appreciate an S-meter that no longer varied between bands.

Fig. 2. Long (4-in.) ground wire on Band D coil proved second problem with HA-226. Text tells how author handled this one.

Six for a Quarter. I checked the 6BE6 at a local drug store; it wasn't that. Something just had to be wrong with the radio. Surely not on a new one like this? Perhaps it could be a bad antenna system? Lengthening it, shortening it, using the drainpipes, nothing seemed to help. OK, I concluded triumphantly, the receiver input impedance must be wrong for these antennas; so I made a quarter-wave line (this gives a low input impedance when terminated by a high one, and vice versa) by twisting some #22 plastic-covered wire together. Presto! Here was an improvement of maybe 6 to 9 dB.

Was this it? Not really, for after a couple of days' listening I found stations could still be heard on Range C that just couldn't be found on Range D. Something just had to be wrong with that receiver! So, after studying the receiver layout, the following solution came up.

Fig. 2 shows the effective circuit of the antenna tuning on Range D. I found that the ground wire, common to both the coupling and antenna coils on Range D, ran about 4 in. before finally reaching the chassis. I figured its inductance was between 0.05 and 0.1 μ H. I also figured that the mutual inductance between the two-turn coupling coil and

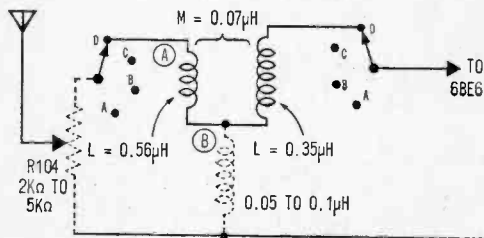

was disconnected to leave a connection for the other three antenna coils.

Grounds and Leads. For a few days I was satisfied, but then my fingers became itchy once more. That Range D could still take a lot of improvement. Everyday, the other three ranges seemed to get better, and for a 3-tube radio, we were really pulling those DX stations in. Could a good ground provide the answer? Some chrome-plated bars conveniently doing nothing in the forest near the apartment were brought into use.

Fortunately, the apartment was on terrace level, and the ground was still wet from the winter rain and snow. So with quite a lot of improvisation, under cover of darkness with an eye to objecting neighbors, those bars were driven deep. After all that there was just a small improvement, so a good ground obviously wasn't the answer. So on to the next modification!

The 6BE6 is a cathode-coupled oscillator type of frequency changer. To obtain good conversion conductance, the RF cathode-to-ground voltage should be a small fraction of the grid voltage. At low frequencies it's easy to achieve this by tapping well down the coil. However, on Band D this makes for a very small number of turns, and on this receiver the ratio of the main oscillator-to-tickler windings was about 2:5. To make matters a lot worse, the lead from the cathode of the 6BE6 to the four different oscillator coils is about 4-in. long.

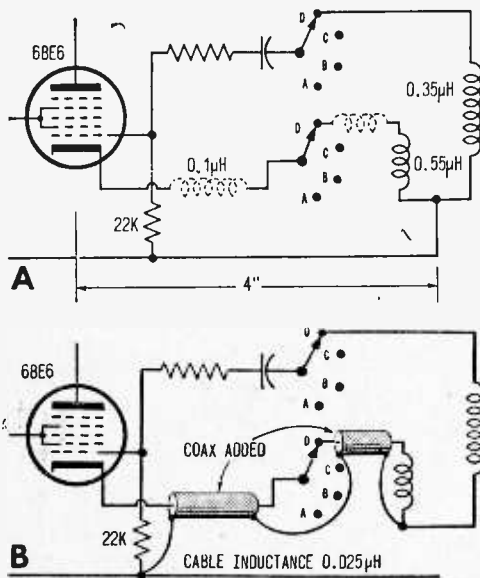


Fig. 3. Though modification detailed in Fig. 2 proved helpful, self-inductance of 6BE6 cathode lead to Band D coil was much too high for good conversion efficiency (schematic labeled A above shows effective circuit—lead, shown dotted, was calculated to have inductance of approximately 0.1 μ H). Installing length of coax (schematic B) dropped inductance to 0.025 μ H.

The self-inductance of this wire is about 0.1 μ H, and the effective circuit is shown in Fig. 3a. The effect of the lead inductance is to make the cathode voltage way above the expected value, and nearer in potential to the grid. Overall, the conversion conductance falls off rapidly as the cathode-grid potential decreases.

What was done to cure the problem is shown in Fig. 3b. I ran a 50-ohm cable, grounded only at the tube socket on the lug adjacent to pin 1, right up to the range switch and on to the tags on the Range D oscillator coil, grounding the coil only via the outer

shield of the coax. The calculated inductance of a 4-in. run of 50-ohm coax is only 0.025 μ H.

Now things really started working! But, by the latest modification, the oscillator tuning had gone astray. And on realigning it, it was noticed that the receiver worked much better when the local oscillator was tuned lower than signal frequency, rather than higher, as it was originally. I noted that on Range D the designers hadn't bothered to incorporate a padder, and figured that we might as well align with the oscillator set low.


With all these modifications, that high-frequency range was working really well. In fact, there was little difference between the top end of Range C and the bottom end of Range D.

Razor Gen. Realignment presented a small problem with no instruments available, so what I did was to screw in the oscillator coil slug until WWV was heard on 15 and 25 MHz. I checked for WWV at 14.1 and 15.9 MHz; these corresponding to the possible image frequencies. If the oscillator was set correctly, the image of WWV was found at 15.9 MHz on the dial. The process was repeated at 25 and 25.9 MHz, and this time the oscillator trimmer capacitor was altered. If you have another receiver, you could use this same procedure to set oscillator frequencies at 14.55 and 24.55 MHz.


I also checked the antenna circuit alignment, and this really was a problem—moving anything in that front end pulled the local oscillator, so using a local station was no use at all. In the end an electric razor (the AC/DC type with contacts) came to the rescue as a broad-band interference generator. There were two tuning positions for the antenna tuning slug and the trimmer capacitor, and these corresponded to the two possible tuning frequencies above and below the local oscillator. I aligned for maximum noise on the higher of the two frequencies at 13 MHz, using the coil slug (slug in the further out of the two positions) and repeated this at 26 MHz using the trimmer capacitor (set to the minimum capacity of the two positions).

Q And BFO. Well, that wasn't the end of the story. I settled in for SW broadcast listening, and realized that the stability of my little receiver wasn't bad at all—it might even be good for sideband. However, the BFO didn't work properly. In the CW mode, the 6BA6 suppressor grid is not firmly grounded, and the tube works as a dynatron oscillator.

(Continued on page 108)

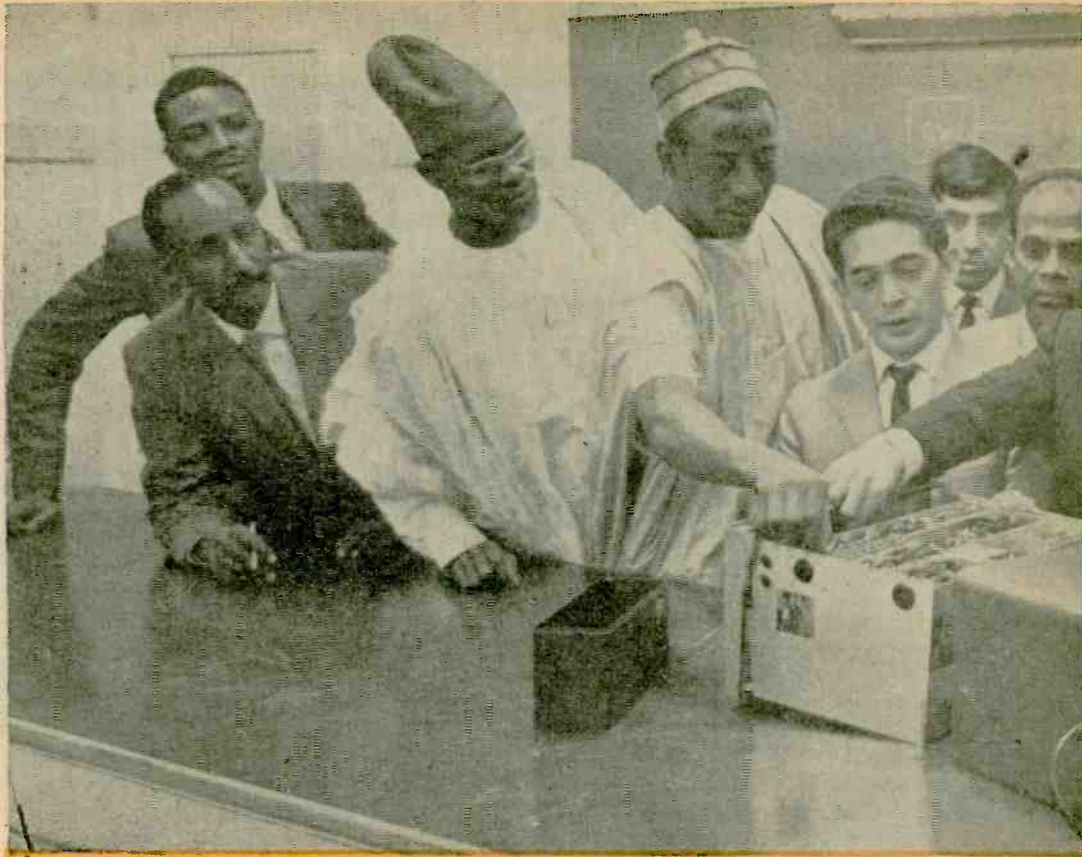

COPPER'S

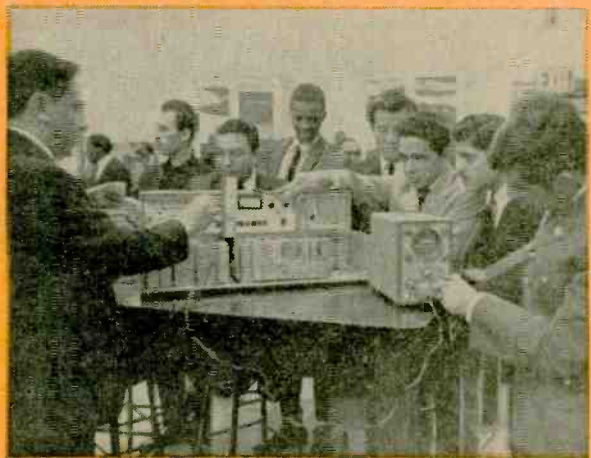

Facts and photos by Three Lions

Above, students check out a modern central communications unit. At left, test data is recorded in log book.



U.N.


Police officers from exotic lands learn to fight crime with scopes and soldering irons in a New York school.

Cops from around the world are catching up on two-way radio at New York's Telecommunications Training School. Sponsored by the U.S. State Department's Agency for International Development, the school attracts police officers from such exotic lands as Jordan, Thailand and the Republic of Chad in Africa.

About 36 foreign police communications officers are receiving specialized training at the school (about a stone's throw from the real U.N.). They represent 14 nations around the globe. Like the metropolitan areas in this country, the *(Continued overleaf)*



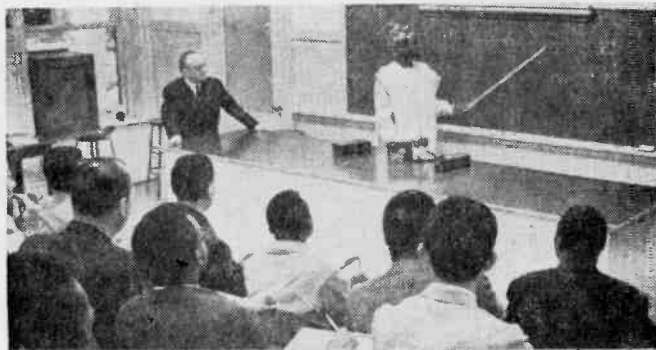Two officers from Jordan, Bani-Hani and Fayyad Bayer, work as a team repairing a transmitter.




Left, a Republic of Niger police officer, Mr. Sidi, traces through a communications transceiver block diagram, explaining what he has just learned to the rest of the class, while the instructor looks on. Below, Andre Maillard (right), director of the Telecommunications Training School, shows a Thai police officer the location of the components being discussed in theory.

smaller and newly emerging nations are also plagued with criminals of increasing sophistication and derring-do.

These countries want to fight back with one of the policeman's best friends: fast contact by mobile two-way radio.

The officers' training, as our photos show, covers basic electronics, theory of radio transmitters and receivers. They'll receive instruction in practical maintenance of equipment. Then they're given background in how to plan and operate a radio system. Since the group doesn't speak one language, lessons are given in English, French and Spanish under the coordination of the school's director, Andre M. Maillard. After the present 6-months course is over, two more officer groups will arrive, along with executives who will study telecommunications management. ■

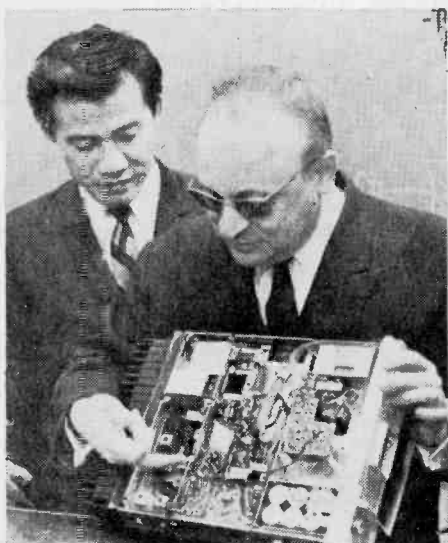

Before classes, a group of foreign law officers gather outside the school building and discuss police communications techniques practiced in their countries.



My problems started when I had to make a continuity test in a 20-wire cable. In the tried-and-true fashion, I hooked up one end of the ohmmeter to the connector end of the cable. I then began the one-in-twenty odds search for the other end of the same wire.

As I touched each of the bare wires, I had to look from the wire to the meter and then back to the wire again—I was fast developing a sore neck. Then I remembered that in the electronics industry they use a buzzer, which eliminates the need to look at a meter. Obviously, a buzzer is less expensive, too.

The buzzer I finally purchased was a temperamental gadget and never seemed to stay adjusted. I was never quite sure if it was the buzzer's fault, failing batteries, or me. Convinced that there had to be a better way, I looked around my shack for other uses that might warrant a bit more expense. I found them and the result

VARI-TONE BUZZER



By James Robert Squires

Here's an easy-to-build
electronic signal source
that lets your imagination
take over where its
frequencies leave off

was a Vari-Tone Buzzer.

Not only does this little device serve as a continuity tester, but it works as a code practice oscillator as well. Since I sometimes grow tired of the same tone, I built in different audio outputs. This multivibrator has four fixed frequencies so that when you're tired of listening to one you can shift to another. Also, each fixed output can be wired through a separate switch to indicate different things. For instance, one tone could signal "full," top speed, etc.; another would be "empty," low speed; and so on.

Multivibrator. The circuitry is designed to make your Vari-Tone signal source as versatile as possible. The multivibrator can be triggered by a number of inputs (connected through jack J1) and different battery voltages.

Frequency range is about 2.5 kHz. A fine-frequency control is also possible by simply adding an external 100,000-ohm pot between

e/e VARI-TONE BUZZER


pin 6 of J1 and the negative terminal of battery B1. Control of tone volume is then possible by varying the pot.


The unit is connected so that an external battery can be used, leaving the internal battery for emergency service. Maximum voltage should not exceed 20 V.

There are three ways to use the buzzer. The first is to connect pins 1 and 2 together


and use pins 4 and 5 as test points (a tone will be heard only if there is a short between pins 4 and 5). The second is the converse (i.e., join pins 4 and 5 and use pins 1 and 2 as test points). The third is to connect pins 4 and 5, 1 and 2, then alter the test tone by connecting one of pins 6 through 9 to pin 4.

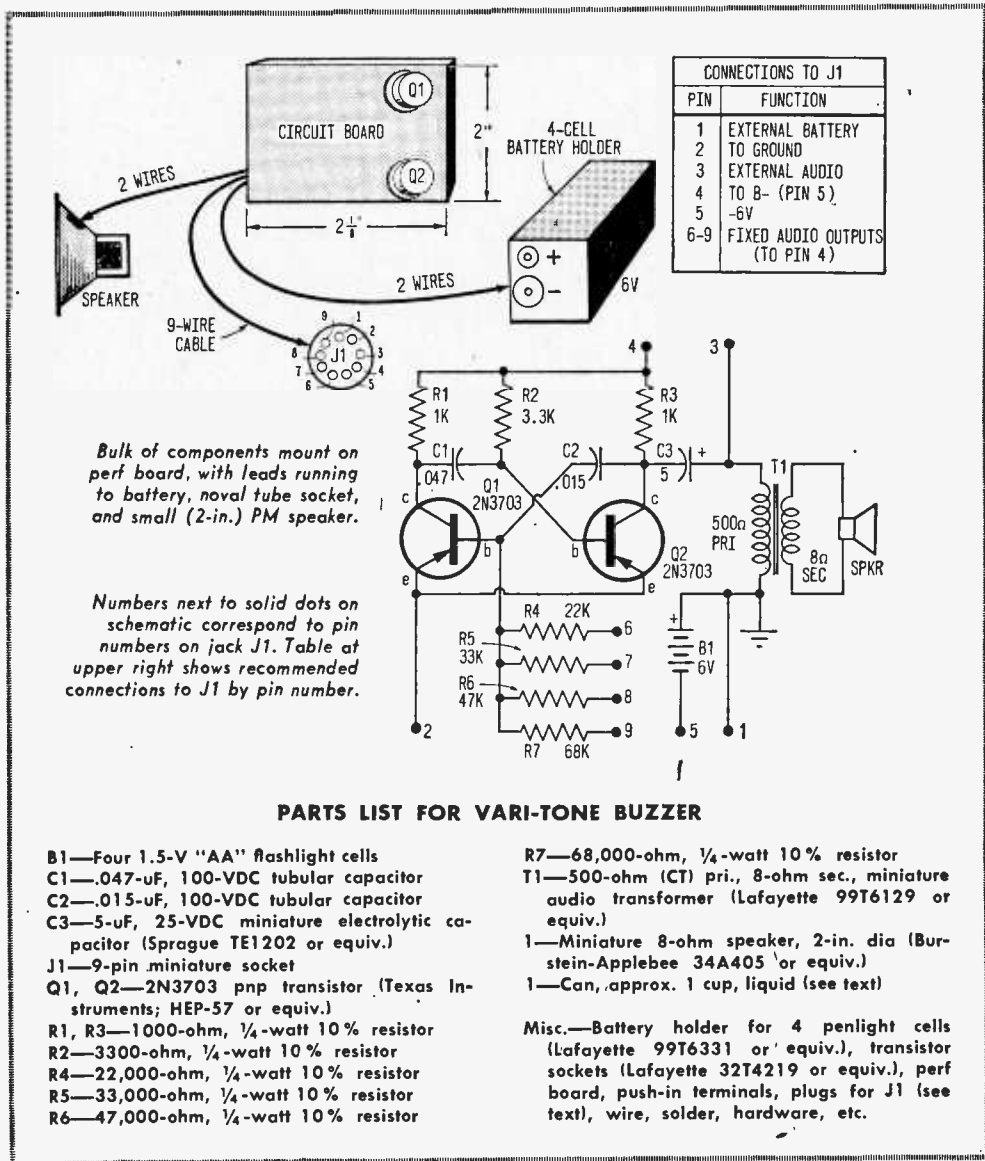Construction. A fruit can (2 $\frac{3}{8}$ in. dia x 3 $\frac{1}{4}$ in. long) was selected to house the unit because it's inexpensive and small enough to provide a compact, sturdy package. Using the speaker and the 9-pin noval socket as templates, locate them as indicated in the photos. When working with tin, either use slow drill



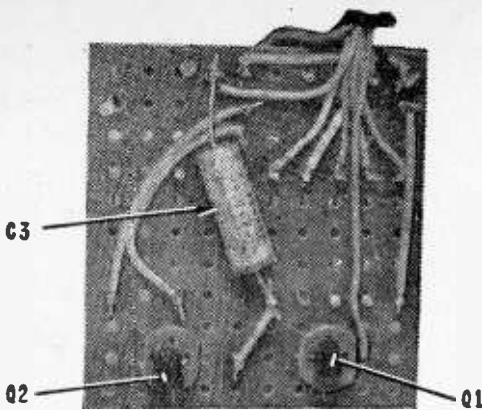

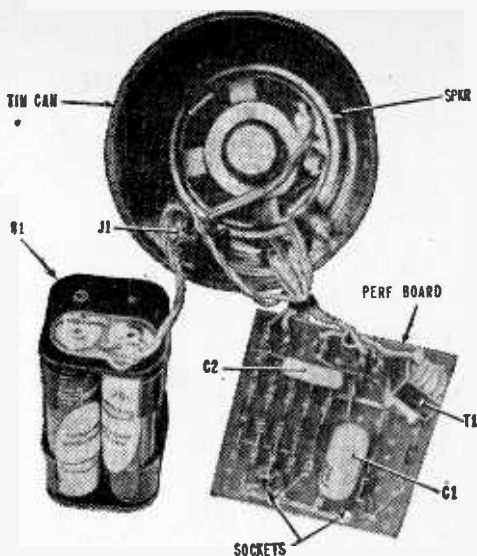Bottom view of perf board, showing placement of transistors and capacitor C3. Remaining capacitors and transformer T1 mount on other side.



Once speaker and J1 have been mounted in fruit can, assembly is mainly a matter of wiring in battery B1 and perf board. Note position of T1.

speeds or very light pressure (tin has a tendency to tear if you don't follow these precautions). Finally, drill a bunch of holes for the speaker grille at the closed end of the can.

Mount the components on a perf board using push-in terminals. Look at the photos showing both sides of the board. Output transformer T1 fits neatly into the board's


pattern when skewed at an angle. The two transistor sockets are mounted by pressing them into the board for a tight fit. I used a reamer to enlarge the holes until a tight fit was possible.

Before mounting J1 in its opening, wire all nine pins using 6-in. wires. Solder the wires close to the noval socket and feed them out through the *index slot* in the socket. The socket should be mounted so that the slot points towards the speaker. Bend the wires out the open end of the can and wire them to the circuit board. The extra length allows you to remove the perf board for servicing.

One helpful option is a plastic lid to cover the open end of the buzzer. It acts as a dust cover.

When you program the input plug for J1 the buzzer will do a task. You can use an old tube base that can be broken and wired as needed. I keep these bases around so that when the need arises for a particular function, one is readily available. Whether you require a continuity tester, code practice oscillator, or specific frequencies from a signal source, pre-wired plugs will be a great help. Naturally, you can substitute for the 9-pin arrangement if you wish.

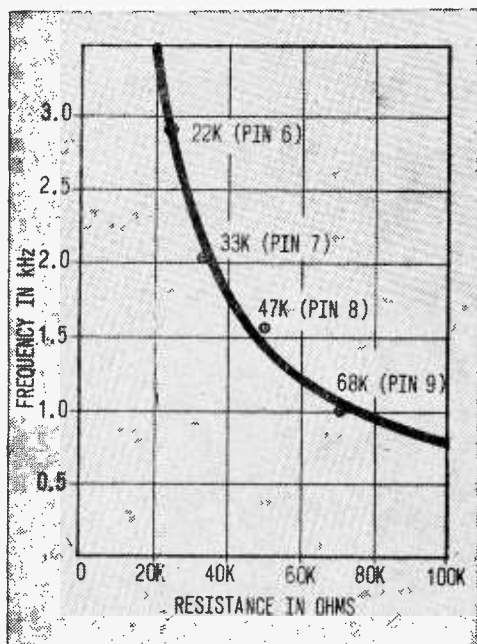Note that pin 3 on J1 enables the user to feed music into the speaker while at the same time using the buzzer. Also, pin 3 enables the buzzer's output to be used externally for testing or other purposes. ■



Output frequency of Vari-Tone Buzzer ranges from 1 to 3 kHz, depending on size of feedback resistor selected. Use of small pots rather than fixed resistors would enable frequencies to be trimmed to exact values desired with auxiliary tone source.



***Learning
electronics
at home
is faster,
easier, more
interesting with new achievement kit***

Only NRI offers you this pioneering method of "3 Dimensional" home-study training in Electronics, TV-Radio... a remarkable teaching idea unlike anything you have ever encountered. Founded more than half a century ago—in the days of wireless—NRI pioneered the "learn-by-doing" method of home-study. Today, NRI is the oldest, largest home-study Electronics school. The NRI staff of more than 150 dedicated people has made course material entertaining and easy to grasp. NRI has simplified, organized and dramatized subject matter so that any ambitious man—regardless of his education—can effectively learn the Electronics course of his choice.

**DISCOVER THE EXCITEMENT
OF NRI TRAINING**

Whatever your reason for wanting knowledge of Electronics, you'll find the NRI "3 Dimensional" method makes learning exciting, fast. You build, test, experiment, explore. Investigate NRI training plans, find out about the NRI Achievement Kit. Fill in and mail the postage-free card. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016

**GET A FASTER START IN THE
COURSE YOU CHOOSE WITH NRI'S
REMARKABLE ACHIEVEMENT KIT**

When you enroll with NRI we deliver to your door everything you need to make a significant start in the Electronics field of your choice. This remarkable, new starter kit is worth many times the small down payment required to start your training. And it is only the start... only the first example of NRI's unique ability to apply 50 years of home-study experience to the challenges of this Electronics Age. Start your training this exciting, rewarding way. No other school has anything like it. What do you get? The NRI Achievement Kit includes: your first set of easy-to-understand "bite-size" texts; a rich, vinyl desk folder to hold your training material in orderly fashion; the valuable NRI Radio-TV Electronics Dictionary; important reference texts; classroom tools like pencils, a ball-point pen, an engineer's ruler; special printed sheets for your lesson answers—even a supply of pre-addressed envelopes and your first postage stamp.



ELECTRONICS COMES ALIVE AS YOU LEARN BY DOING WITH CUSTOM TRAINING EQUIPMENT

Nothing is as effective as learning by doing. That's why NRI puts so much emphasis on equipment, and why NRI invites comparison with equipment offered by any other school, at any price. NRI pioneered and perfected the use of special training kits to aid learning at home. You get your hands on actual parts like resistors, capacitors, tubes, condensers, wire, transistors and diodes. You build, experiment, explore, discover. You start right out building your own professional vacuum tube voltmeter with which you learn to measure voltage and current. You learn how to mount and solder parts, how to read schematic diagrams. Then, you progress to other experimental equipment until you ultimately build a TV set, an actual transmitter or a functioning computer unit (depending on the course you select). It's the practical, easy way to learn at home—the priceless "third dimension" in NRI's exclusive Electronic TV-Radio training method.



SIMPLIFIED, WELL-ILLUSTRATED "BITE-SIZE" LESSON TEXTS PROGRAM YOUR TRAINING

Lesson texts are a necessary part of training, but only a part. NRI's "bite-size" texts are as simplified, direct and well-illustrated as half a century of teaching experience can make them. The amount of material in each text, the length and design, is precisely right for home-study. NRI texts are programmed with NRI training kits to make things you read come alive. As you learn, you'll experience all the excitement of original discovery. Texts and equipment vary with the course. Choose from major training programs in TV-Radio Servicing, Industrial Electronics and Complete Communications. Or select one of seven special courses to meet specific needs. Check the courses of most interest to you on the postage-free card and mail it today for your free catalog.

**Available Under
NEW
GI BILL**

If you served since
January 31, 1955, or
are in service, check GI
line in postage-free card.


custom training kits "bite-size" texts

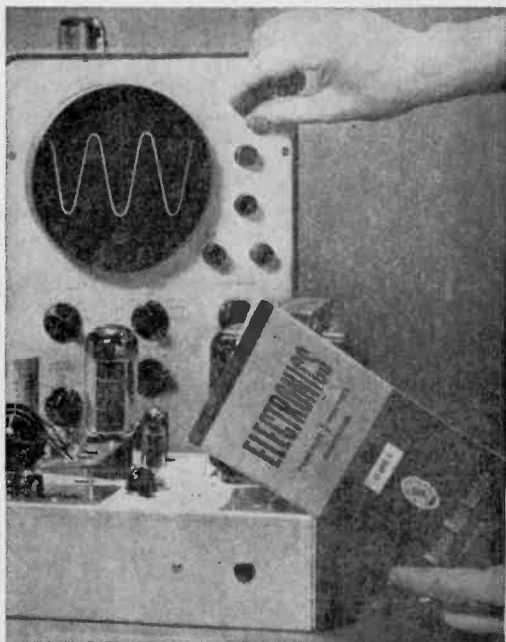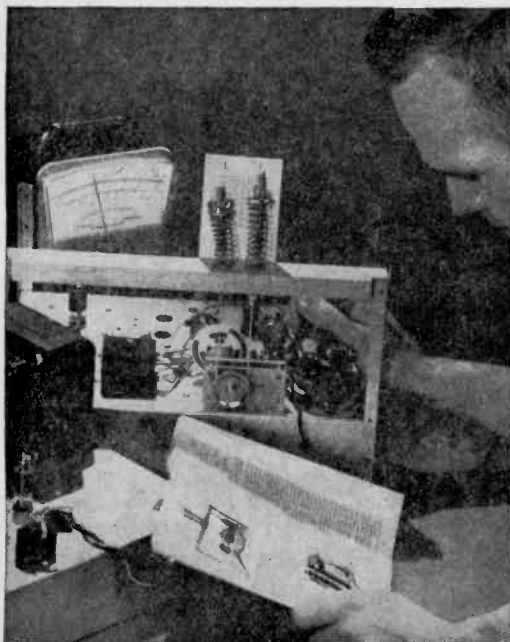



ELEMENTARY ELECTRONICS ETYMOLOGY

By Webb Garrison

 

Grid

▲ At least as early as the 13th century, Englishmen had developed a taste for the ancestor of the modern pancake. Thin cakes were baked on circular iron plates whose name was formed from Old French *gridil*—based, in turn, on an early Latin label.

A famous document known to scholars as the "South English Legendary" refers both to the *griddle* and the *gridiron*. The latter, also well known in the 13th century, was a frame of parallel metal bars used for broiling. Though the two devices bore only superficial physical resemblance, their names came from the same source. Perhaps the importance of the fact that both were used over the fire outweighed all differences in structure and mode of operation.

Not all gridirons were found in kitchens, though. Big ones were used as instruments of torture. Tradition had it that St. Lawrence was martyred by being broiled alive on a gridiron. Sometimes the devil was represented as bound to a burning gridiron with red-hot chains.

After centuries of use, the name of the metal framework was in popular speech clipped to *grid*. In this form it designated any kind of grating or arrangement of parallel bars with openings. So it was natural that makers of storage batteries should use the term to label a lead plate with heavy ridges that was a component in cells made in the late 19th century.

Inevitably, the term expanded with the electrical industry. Today there are many kinds of grids, including some that control the passage of ions or electrons through vacuum tubes. Many of them bear no resemblance to the gridiron on which St. Lawrence is said to have been roasted—but all are alike in having parallel bars or openings or both.

Live Wire

▲ By the 1890s, ordinary persons in the western world were beginning to have some personal experience with electricity. Generators, motors, and other devices were no longer seen only in experimental laboratories and exhibition halls.

Electrical equipment, with wires attached, could be found in many homes and most shops.

Inevitably, some circuits broke down. Frequently the trouble lay in transmission of current from the source of supply. When this state prevailed, it did no good to fasten a wire more securely to a motor or a light socket; the wire itself was "dead."

Because so many dead wires caused so much trouble, *live wires* entered everyday speech as a title of admiration and approval. It named not only a copper wire carrying current, but also a person who showed unusual energy and enthusiasm.

There's evidence that the term born with electricity as its midwife was used orally in its broader sense before 1900. But diligent search has revealed no printed use prior to 1909, when a writer for *The Saturday Evening Post* described a legislator as "an aggressive 'comer' of the live-wire kind."

Mica

▲ Rock-cutters were aware of it centuries earlier, but it wasn't until 1706 that any scientist made specific notes about a special kind of scale of crystal that occurs in marble and other stones. From Latin for "grain or crumb" (influenced perhaps by the verb *micare*, "to shine") the distinctive type of scale compressed in rocks was called *mica*.

Long after it received this name, the stuff remained a mere curiosity. No one had any idea as to a possible use for it. In popular speech it was often called "Cat-silver," or "glimmer."

By 1778, English chemist Peter Woulfe was telling fellow scientists that "Mica or Glimmer . . . is composed of very thin flexible flakes." He stressed importance of the fact that the substance is a crystal that cleaves very readily in one direction, and correctly concluded that there are several kinds of mica. All of them are alike in having silicate of aluminum as their basic constituent.

Mica has a high melting point, so was first used commercially to make windows in ovens of household stoves. Then it was found to be one of the best insulators known. More than a century ago a special type of "mica battery" was put on the market, but it never won general acceptance.

With the development of capacitors, commutators, and electron tubes mica came into its own. It can withstand high voltages and intense heat. A mica capacitor usually goes through an initial period in which its characteristics "drift" somewhat; then it remains remarkably stable. Even with the development of synthetic dielectric materials there is little likelihood that nature's queer crystalline "glimmer" will be displaced from its special niche in the field of electronics. ■


Outen that light, Harry, with our DALLY LIGHTER.....

Here's an AC light switch we're willing to bet is different from any you've ever seen. The reason: it sports not one, but *two* control switches. The first (the toggle switch near the bottom of the switch plate) works like any conventional light switch. Flip it up and you turn the light *on*; flip it down, and you turn the light *off*. The second (the pushbutton on top) . . . well, that's something special.

It initiates a *time delay* that turns the light *on* (just touch the button), then automatically turns it *off* again after a predetermined time. How long? That's up to you. The author's own version of the *Dally Lighter* is set for just under five minutes. But as we'll see shortly, you can select any delay time you wish from 30 seconds to 15 minutes.

In the author's house—and probably yours, too—there are several lighting control situations where the time-delay feature is worth a pound of shoe leather in saved steps. For example:

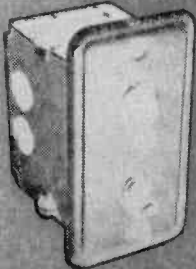- In a long corridor not equipped with two-way switches. Thanks to the *Dally Lighter*, the author can now walk from one end to the other at night without the money-wasting need of leaving the



light *on* until he walks back through.

- In a garage. Now with the *Dally Lighter*, the author has no need to walk back through the garage to reach the light switch on the rear wall when he pulls his car out at night.

- To control a front (or driveway) floodlight. The *Dally Lighter* gives a person or car plenty of time to find their way through the front yard (or down the driveway). And when they have, it turns the flood *off* automatically.

How It Works. The time delay circuit is built around a silicon controlled rectifier (Q1). This device is connected in parallel with toggle switch S2 (the conventional control switch). Whenever you touch pushbutton switch S1, the simple voltage-divider/rectifier circuit, composed of R1, R2, and D1, charges capacitor C1 to a low DC voltage (about 11 VDC). The capacitor is wired between the base and ground terminals of Q2, a Darlington amplifier connected in an emitter-follower configuration.

This circuit has a very high input impedance (several megohms) and slightly less-than-unity voltage gain. Therefore, a voltage slightly less than the voltage across C1 appears at the emitter terminal of Q2.

(Continued overleaf)

... a 1-SCR switch that turns lights off automatically after most any time interval you choose

By Ron Michaels


e/e DALLY LIGHTER

In turn, this voltage drives the gate terminal of the SCR (Q1), via current-limiting resistor R4, triggering it into a conductive state. This permits current to flow through the light bulb, causing it to light.

Since the SCR acts like a half-wave rectifier when it's *on*, only the positive-going half of each cycle of AC current can flow through the bulb. This means that the bulb lights to only about 70% of its normal brightness. Nonetheless, the loss of brightness is not important or even noticeable in most lighting situations.

The SCR will remain *on* as long as there is a sufficient driving voltage at the emitter of Q2. This, in turn, depends on the voltage across capacitor C1. The instant you release pushbutton S1, C1 starts to discharge through the base terminal of Q2. Because of the high input impedance, the time constant is very long. Therefore, several minutes will pass before the voltage across C1 drops low enough so that sufficient gate voltage is no longer applied to Q1. When it eventually does, though, the lamp goes out.

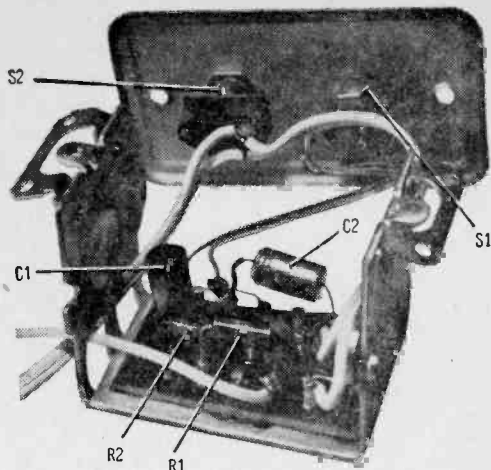Capacitor C2 acts as a filter capacitor for the simple power supply that feeds the amplifier circuit. A glance at the schematic





Dally Lighter's circuit (see schematic below) is simple enough that all components can be tucked within standard switch box. That's S1, the one with the red button, at right in photo above.

will reveal that this supply uses the same voltage-divider/rectifier pair used to charge C1.

Switch S2 functions as a normal light switch when the time delay circuit isn't activated. Flipping it *on* causes the lamp to light with normal brilliance.

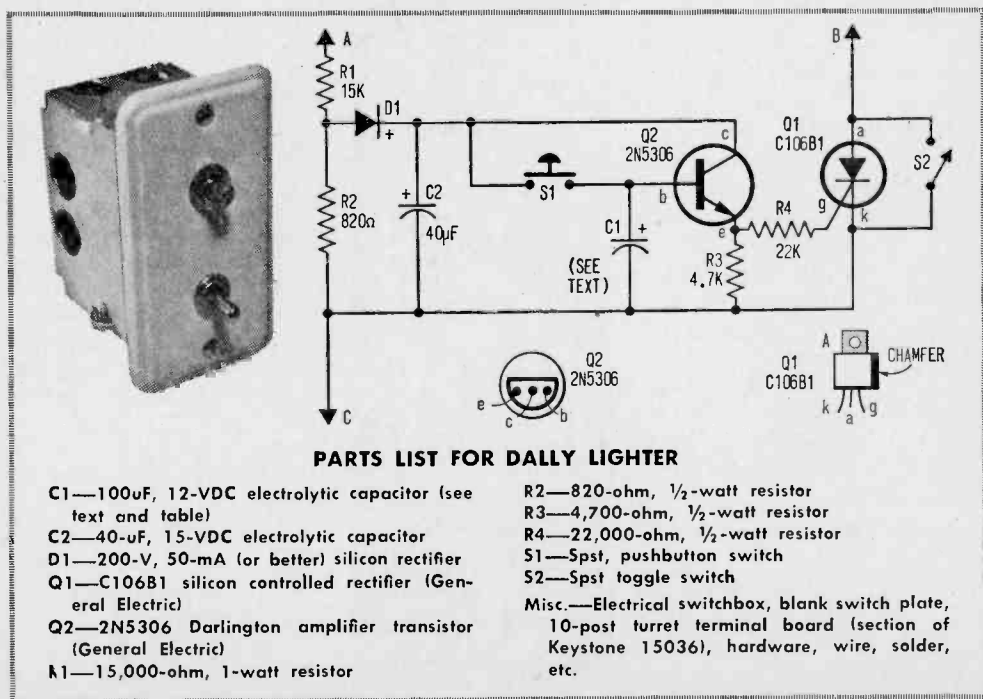Building It. For convenience and wiring safety, build the entire circuit into a stand-



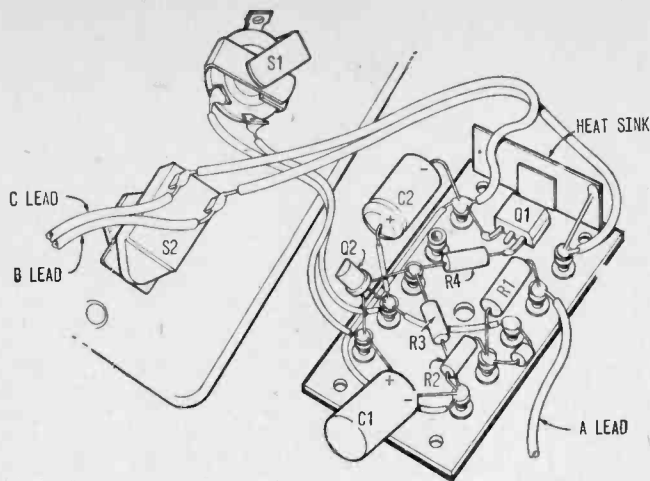

Ten-post turret terminal board holds all of Dally Lighter's components save switches S1 and S2. Physical size of time-delay capacitor C1 may prove problem if you go after extra-long time delay, though it usually can be squeezed in somehow or other.

ard-depth 2-in. switch box. Mount a single section of phenolic terminal strip (10 pins) in the base of the box as shown in our photos. Before you screw the strip in position, place several thicknesses of plastic electrical tape on the bottom of the strip so that all of the terminal ends are covered. This will prevent short circuits against the metal box.

The SCR is an inexpensive plastic-case unit. Mount it on the terminal strip with a dab of cement before you connect components to its leads. Besides being connected to the *anode* terminal, the SCR's metal tab serves as a heat sink. To improve heat dissipation, solder a 1 x 2-in. piece of copper sheet to the tab.



As with all line-voltage-operated devices, short circuits between adjacent leads are a potential hazard. Therefore, play it safe and keep all interconnecting leads as short as

possible. Also, double-check the polarities of the two electrolytic capacitors and the diode before you solder them in place (any mistakes here will ruin the components involved).


The two switches should be mounted on an undrilled switchplate of the type usually employed to cover unused switchboxes. Since these are almost always sold unpainted, be sure you paint it before you install the switches.

Installation. The complete device mounts within a wall like any other switchbox. The connection diagrams contrast the wiring of a conventional switch and this circuit.

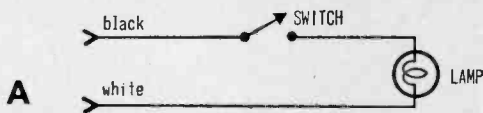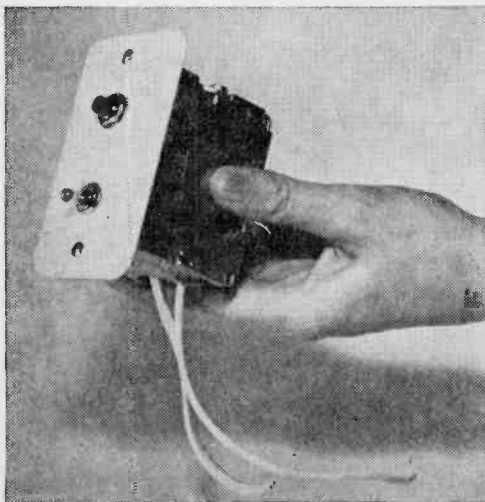For clarity, our photos show the three device connection leads protruding through the switchbox. Actually, there is sufficient room inside the box to permit you to make all interconnections with house wiring within



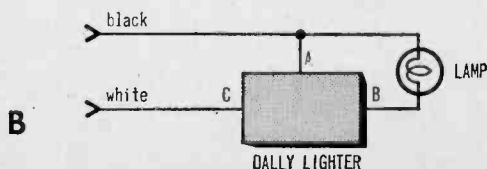Conventional lamp hookup (drawing A, above) has switch in one side of AC line to turn lamp either on or off. Since Dally Lighter contains its own switch, existing switch must be removed and Dally Lighter installed in its place. Three leads from Dally Lighter (labeled A, B, and C) should be connected as indicated in drawing B below.



e/e DALLY LIGHTER

the box proper. However, it's important that you use suitably insulated wire for all connections. Should you experience difficulty in running the BX cable into the box, attach a second box to the side of the one containing the *Dally Lighter* circuit. To do so, remove one side panel from both boxes, join the boxes together, then insert the self-tapping screw.

One thing you should keep in mind: the SCR used in this device is rated for a maximum current flow of 2A DC. This means that the *Dally Lighter* should not be connected to lamps whose current drain exceeds a maximum of 250 watts of resistive load at any time.

And now that you've built it and installed it, there's but one question remaining. Do things go smoother with the *Dally Lighter* on hand? You bet they do! (Doubting Thomases please take note and give the *Dally Lighter* a whirl for themselves!) ■

How to Select Time Delay Control Capacitor C1

With the other circuit values shown in the Parts List, a 100- μ F capacitor produces a time delay of approximately 280 seconds (about 20' seconds short of five minutes). The following table lists the capacitance values that will produce other delay times. Note that the time figures are approximate since the actual delay depends upon the gate sensitivity of the SCR. Though these devices are rated to fire when a gate current of 200- μ F is supplied, many production line SCRs are far more sensitive, and will fire with gate currents of less than 50- μ F. Thus, you should use the table as a jumping off point. If the specified value produces a longer time delay, reduce the capacitance value; to increase the delay, add capacitance.

Time	Value of C1	Time	Value of C1
30-seconds	10- μ F	3-minutes	60- μ F
1-minute	20- μ F	4-minutes	80- μ F
90-seconds	30- μ F	10-minutes	200- μ F
2-minutes	40- μ F	15-minutes	300- μ F

Note: Though larger capacitors will produce longer time delays, their larger physical size may prevent their use in this project.

Make a Right at the Next Computer


□ Ever have that sinking feeling in your stomach when, while driving on a high-speed highway, you miss your exit because you didn't see the directional sign in time? A Head-Up Display System that may eliminate those missed turns is now being tested by the Bureau of Public Roads.

The system causes a directional symbol to appear to be focused at infinity on the windshield and superimposes it on the road scene.

As the car approaches an intersection, a coded message from the computer-decoder reaches a loop antenna buried in the roadway and connected to the roadside computer.

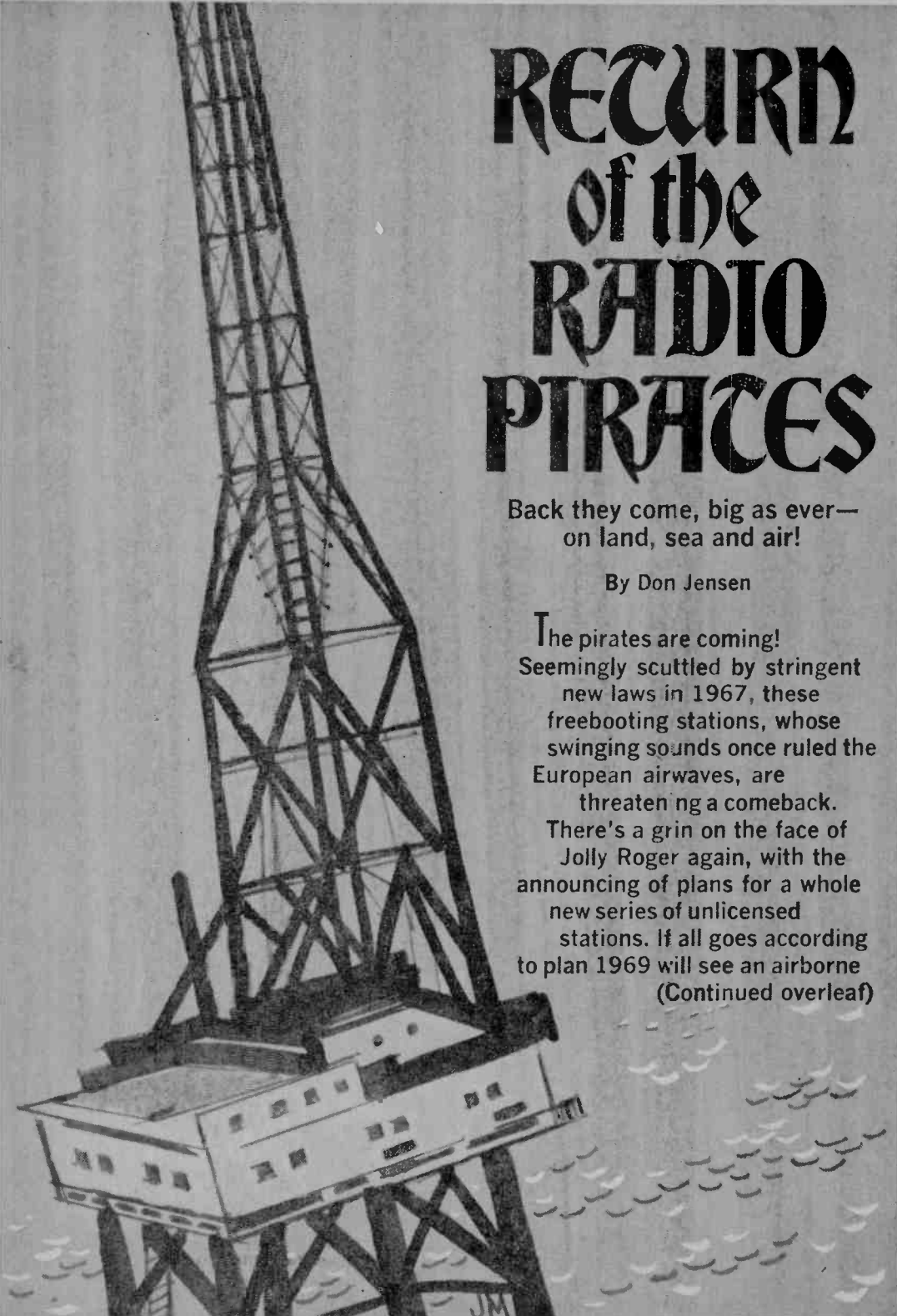That computer receives and decodes the vehicle destination code, then transmits directional instructions back to the vehicle to trigger the windshield display. At the same time, an audible beep warns the driver that instructions are about to be given. ■





RETURN of the RADIO PIRATES

Back they come, big as ever—
on land, sea and air!

By Don Jensen

The pirates are coming! Seemingly scuttled by stringent new laws in 1967, these freebooting stations, whose swinging sounds once ruled the European airwaves, are threatening a comeback. There's a grin on the face of Jolly Roger again, with the announcing of plans for a whole new series of unlicensed stations. If all goes according to plan 1969 will see an airborne
(Continued overleaf)

RADIO PIRATES

television station beaming commercial programs to the British Isles, a seagoing German outlet, and the Beatles' first venture in the field of pirate radio. And, to the dismay of European officialdom, this could be only the beginning.

Eleven Years Ago. Actually, buccancer broadcasters have bugged the hidebound state radio monopolies since 1958, when an enterprising fellow named Fogh stashed a three-kilowatt FM transmitter aboard an aging coastal vessel, sailed it beyond Danish territorial limits and began broadcasting as *Radio Mercur*.

This was followed in the early 60s by a handful of unlicensed stations off the coasts of Sweden, Belgium and the Netherlands.


The most audacious was *Radio Atlantis*, a curious dryland pirate that operated openly, thanks to a quirk of Belgian law. For over four years it was heard each Friday evening, transmitting from a TV repair shop in Stropstraat 7, in the East Flanders City of Ghent.

The gendarmes knew it was there but there was nothing they could do. Belgian law prohibits building searches after 10 p.m. At 11 o'clock, *Radio Atlantis* signed on with an hour and a half of commercials and some of the hottest jazz around.

Eight times the cops searched the building during the daylight hours; eight times they came away empty handed. Like its legendary namesake, the station's equipment vanished, only to return to the air the following Friday.

The Lion Makes a Buck. But it took the British to turn pirate radio onto the most lucrative bit of seaborne skullduggery since Sir Francis Drake. The success of the English *Radio Carolines*, which at their peak grossed \$1.4 million a year in advertising revenues, prompted a rash of imitators. Broadcasting from refitted vessels and abandoned anti-aircraft forts rising from the seabed, these stations bombarded London and other population centers with U.S.-style "Top 40" sounds.

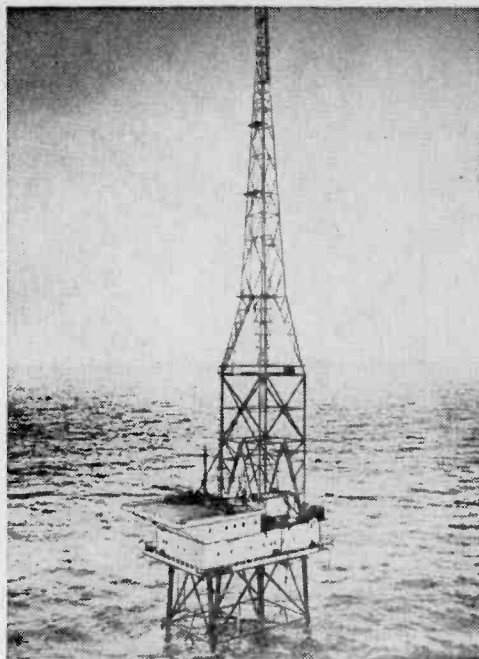They were an unstable lot, regularly changing their names, frequencies and ownership. Other stations were proposed but never got on the air, or if they did, they died after a few test broadcasts. At the peak of the craze, ten pirates, three of them on old



First pirate TV station, *Radio Noordzee*, began broadcasts to the Netherlands in 1964. Dutch authorities soon boarded tower, closed station.

ack-ack gun towers, the rest on vessels, ringed the tight little island.

Britain's young mod crowd, fed up with stodgy, old "Auntie BBC," loved 'em! Dee-jays like Spangles Muldoon, Daffy Don Allen and "Screaming" Lord David Sutch, a 22-year-old who claimed to be an honest-to-goodness blueblood, were overnight stars. But British officials were somewhat less than overjoyed by the whole business.

"No one is going to cock a snook at British law," snorted Postmaster General Edward Short, whose office was responsible for enforcing radio regulations.

But the pirate radios, operating from international waters, were beyond the reach of the law. Measures were proposed, but Parliament stalled . . . and stalled. Finally, the M.P.s got off their backbenches.

Cops and Robbers. It was June 1966, when ex-paratrooper Maj. Oliver Smedley touched off an internecine feud with a midnight raid on *Radio City*, a pirate broadcaster perched on a flak tower in the Thames Estuary. Smedley, it seemed, had "lent" a transmitter to the station's operator, Reginald Calvert, who allegedly was about to peddle the major's property to a broadcasting syndicate.



Though not widely heard in U.S. during their heyday, European pirates were picked up by some lucky DXers. These are veries owned by author.

On the theory that "possession is tenths of the law," Smedley led a bloodless invasion of the offshore tower and simply took over *Radio City*.

Outraged, Calvert confronted the ex-officer at his country estate the following day. A shotgun blast ended the angry meeting and 37-year-old Calvert lay dead. Smedley was charged with murder but a jury later acquitted him on his plea of self defense.

The following month, the postmaster general presented Parliament with a draft Marine Offenses Bill, patterned after measures adopted by the Scandinavian countries. By February, the legislators had given the bill tentative approval.

It Looked Like the End. Throughout the Continent, official opposition to the pirates grew. The Council of Europe passed a resolution denouncing the unlicensed stations. Ired because of interference to their domestic radios, Sweden, Czechoslovakia and other nations complained to the International Telecommunications Union. Italy secretly proposed sending warships to shut down the freebooters.

When the British law finally took effect, Aug. 15, 1967, most of the pirates pulled the big switch. Gone were *Radios 227, 270, 355 and 390*. Gone was *Radio London's "Big L"*


sound. With a skirl of bagpipes, *Radio Scotland* left the air. And with them, and the others of their ilk, went a collective investment of \$8.4 million.

The big moneymakers, *Radios Caroline, North and South*, stuck it out until the following February when they, too, gave up and were towed to a Dutch port.


With the exception of Holland's *Radio Veronica* and *Radio Hauraki*, off Auckland, New Zealand, halfway around the world, the pirate radios had disappeared. Only these two remained active. And *Veronica* became at least partially legit. In addition to broadcasting from its old stand off the Dutch coast, it tapes pop music shows, tagged *Radio Veronica International*, which are flown daily to the Mediterranean island of Majorca. There they are broadcast by the legitimate *Radio Popular de Mallorca* for English and Scandinavian tourists visiting the Spanish resort isle.

And *Radio Hauraki*, with the recent passage of a commercial radio law in New Zealand, is waiting hopefully for a government broadcasting license.

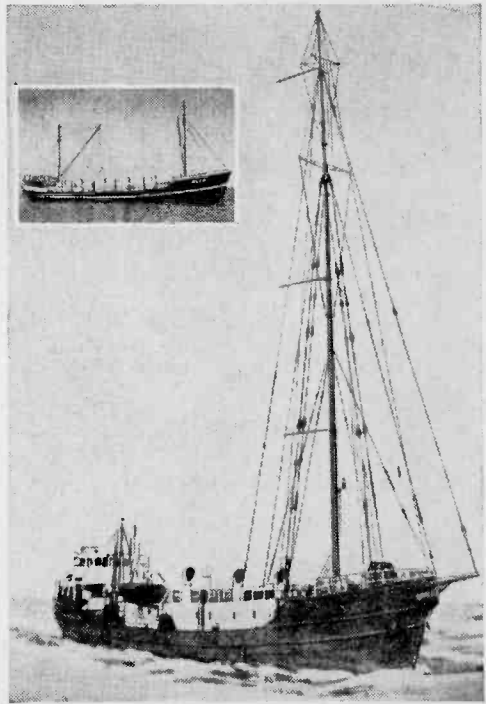We Shall Return. After the mass shutdown there was a lot of brash talk from the



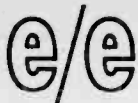In 1961, lumber-hauling motor ship (inset) was converted to pirate station and became *Radio Nord*. End came when vessel's registration was cancelled.



RADIO PIRATES

beached pirate promoters. The stations would return, they vowed. Fleet Street and the Continental press delighted in playing up these rumors.

The Swedish *Radio Syd*, it was said, would make a comeback as a combination radio station and nightclub off the West African shores of Gambia . . . Others maintained it was the Canary Islands. *Radio Scotland*, *Radio London* and the unsinkable *Carolines*, supposedly, would be back at sea shortly with fabulous new equipment.

But, in fact, the *Radio Syd* vessel, "*Cheeta II*," lay impounded in Harwich harbor, repainted and rechristened the "*Ca ne va rein*." *Radio Scotland's* floating base, the "*Comet*," was being reconverted to a lightship at Flushing. As for *Radio London*, its original own-

ers reportedly were bankrupt and its ship, "*Galaxy*," was having an unwanted six-inch ballast of barnacles scraped from its hull in Hamburg.

There were other stories too. Tales of a German syndicate about to establish a station aboard a retired American destroyer; of a U.S.-backed radio ship ready to sail from Miami for Europe; and a gaggle of would-be and sometime pirates with such unlikely names as *Albatross*, *Shamus* and *Euro-Weekend*. And, supposedly, there was a *Boss Radio* and a *Wonderful Radio Bumble*, the latter being the creation of a character named "Big Bob" in Staffordshire, England.

Many of these outlets with the wacky names were land-based mini-watters operated by teenagers, the European counterparts of the illicit, homebrew stations that plague the FCC in most of our major cities.

(Continued on page 105)

THE PIRATE CREW

Station*	Location	Frequencies**	Target Area
Radio Mercur (1958)	Aboard "Mercur"	88.0, 89.6 FM	Denmark
Radio Syd (1958-62)	Aboard "Cheeta II"	88.3 FM, etc.	Sweden
Radio Veronica (1960-69)	Aboard "Veronica"	1562, 1620	Holland
Radio Nord (1961-62)	Aboard "Bon Jour"	602	Sweden
Danmarks Comm. Radio (1961-62)	Aboard "Lucky Star"	94.0 FM	Denmark
Radio Antwerpen (1962)	Aboard "Uilenspiegel"	1492	Belgium
Radio Uilenspiegel (1962)			
Radio Atlantis (1963-67)	Ghent, Belgium (see text)	97.2 FM, 1538	Belgium
Radio Noordzee (1964)	On "REM Tower"	1399	Holland
TV Noordzee (1964)		TV Channel I	
Radio Atlanta (1964)	Aboard "Mi Amigo"	1493, 1187, etc.	England
Radio Caroline South (1964-68)			
Radio Caroline North (1964-68)	Aboard "M.V. Caroline"	1169, 1520, etc.	England
Voice of Kent (1964)	On "Red Sands Tower"	980, 1124, etc.	England
Radio Invicta (1964-65)			
Radio King (1965)		1259	
Radio 390 (1965-67)		775, etc.	
Radio Sutch (1964)	On "Shivering Sands Tower"	1034, 1529, etc.	England
Radio City (1964-67)			
Radio London (1965-67)	Aboard "Galaxy"	1137, etc.	England
Radio Essex (1965-67)	On "Ft. Knock Head Tower"	773, 1353, etc.	England
Tower Radio (1966)	On "Sunk Head Tower"	1268	England
Radio England (1966)	Aboard "Laissez Faire"	1322, etc.	England
Radio Dolfijn (1966-67)			Holland
Radio 227 (1967)			
Britain Radio (1966-67)	Aboard "Laissez Faire"	845, etc.	England
Radio 355 (1967)	(Vessel carried two xmtrs)		
Radio 270 (1966-67)	Aboard "Ocean 270"	1111	England
Radio Scotland (1966-67)	Aboard "Comet"	1257, etc.	Scotland
Radio Hauraki (1966-69)	Aboard "Tiri," "Tiri II"	1480	New Zealand

** Frequencies fluctuated greatly.

* Other proposed stations never heard, or only tested briefly.

ALLIED MODEL A-2515
5-Band, Solid-State
Communications Receiver


Using the very latest in solid-state technology the Allied Radio Model A-2515 Communications Receiver delivers a level of performance formerly available in tube-equipped receivers priced several hundred dollars higher than the A-2515's reasonably low \$99.95 price.

The A-2515 is all solid-state, and can be powered by 115 VAC or a 12 VDC power pack or battery. Frequency coverage in 5 bands is from 150 to 400 kHz and .55 to 30 MHz. AM reception is provided through a standard diode detector, with a product detector used for CW and SSB reception. The BFO is fully adjustable for CW reception, with upper and lower sideband settings indicated on the front panel for SSB reception.

Front panel controls and switches include a *Function* switch which applies power, selects the AM or AM with ANL (automatic noise limiter) modes, provides a standby position for transmitter control of the receiver, and selects the SSB-CW mode. Both *AF* and *RF Gain* controls are provided as an adjustable *BFO* control. The *Band Sel.* and *Ant. Trim* round out the front panel controls, along with the *Main Tuning* and *Bandspread*. A *Phones* jack is located on the front panel along with the S-meter.


The rear apron has terminals for the antenna and a 4 or 8-ohm speaker. A pre-punched hole (supplied covered) is located adjacent to the antenna terminals for those who would like to install a coaxial-type SO-239

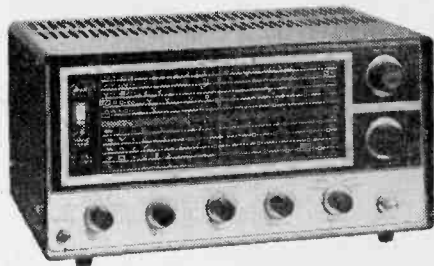The receiver is modularized, each section a complete module. Both modules, and main and bandspread capacitor, are rigidly mounted, insuring high mechanical stability for a budget receiver.



jack. The AC/DC switch and the DC power jack are also on the rear apron, as well as the S-meter zero set control and the remote control socket (supplied with matching plug).

Up-to-date Circuits. Even a quick examination of the circuit gives the user a good idea of what to expect in the way of performance. The RF amplifier is a dual gate MOSFET transistor, one gate used for the signal input and one for the AGC. The function switch automatically increases the RF amp AGC voltage in the AM mode (long time constant AGC—slow action). The mixer is similarly a dual gate MOSFET with the signal applied to one gate and the local oscillator to the other. The mixer feeds a three stage IF amplifier having its own AGC system and full mechanical filter coupling-tuning. In place of the usual IF transformers, the IF amplifier has a two section mechanical filter input, with the first two stages having single section mechanical

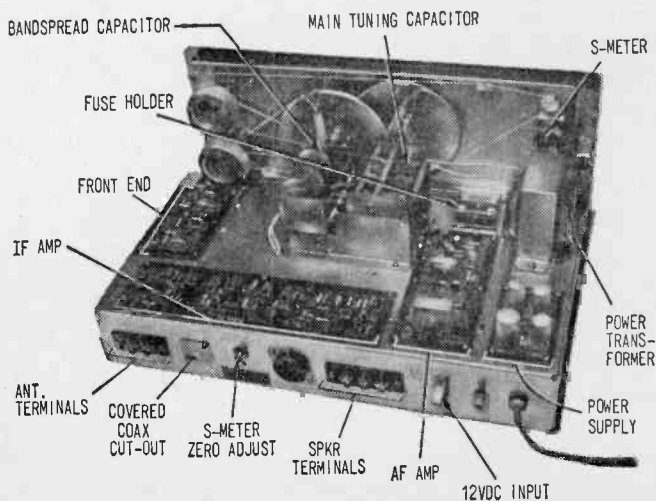

ALLIED A-2515 RECEIVER

filters for collector loads. The final IF amplifier is transformer coupled to a diode detector for AM, with the CW/SSB output stripped off before the diode. Looks like the engineers at Allied have been working overtime on this hot shot.

Performance Checkout. As far as lab measurements are concerned, the table tells most of the story. At almost all frequencies the A-2515's sensitivity for 10 dB S+N/N (signal plus noise to noise) ratio is the equal of many—if not most—receivers priced well up to \$300. The unusual reduced sensitivity of 4.0 μ V. at 11 MHz was due to sloppy alignment (not uncommon in budget receivers). In general, note that the low end sensitivity for each band was somewhat below the high end sensitivity—again, alignment. Image rejection, as shown in the chart, was notably good; even the low 15 dB image rejection on the highest band (28 MHz) compares favorably with the best single conversion receivers—better than most single conversion CB receivers.

Selectivity, the receiver's ability to reject interference from signals on adjacent frequencies, was excellent, particularly so considering the A-2515's \$99.95 price tag. At 28 MHz, where the front-end has little or no effect on total receiver selectivity, the selectivity was 77 dB at 10 kHz from the reference frequency—even better than most CB transceivers. The selectivity is rather steep, being only ± 1.5 kHz at 6dB down. While this is excellent for SW or Ham reception, when the user is trying to dig a station out from under the QRM, it makes standard "entertainment" BC listening somewhat unpleasant as the high selectivity "cuts" the BC station's sidebands, resulting in a loss of

MEASURED PERFORMANCE

Band	Frequency (MHz)	Sensitivity (μ V)	Image rejection (dB)
3	2.0	1.1	60
	4.0	1.3	38
4	5.0	1.3	50
	7.0	1.0	37
	14.0	0.9	20
5	11.0	4.0	31
	21.0	1.0	17
	28.0	0.9	15

Selectivity—77 dB at 27 MHz.
AGC Action—12 dB audio output for 90 dB RF input variation with signals over 3.2 μ V.

"highs"; but it's great for BCB DXing.


The AGC (automatic gain control) is very effective above a 3.2 μ V signal input, translating a 90 dB change in input signal into a 12 dB change in audio output. Below 3.2 μ V input there is virtually no AGC action.

Though the S-meter has the usual S-unit and above S-9 calibration, it is more like a *relative signal strength meter* as each S-unit represents a 3 dB rather than 6 dB change in input signal, and the over-S9 calibrations have no fixed signal strength relationship. S9 represents an 80 μ V signal input at the antenna terminals.

Operating performance. It is in actual operation that the A-2515's performance grabs the user's attention. The BFO and local oscillator are rock-stable, and to the top of band 4 it is possible to work through a complete 15 minute SSB contact without once correcting the tuning or the BFO. On the high band there was a very slight drift, not serious, certainly better than the average tube receiver.

The high selectivity and image rejection was immediately apparent by the lack of
(Continued on page 104)

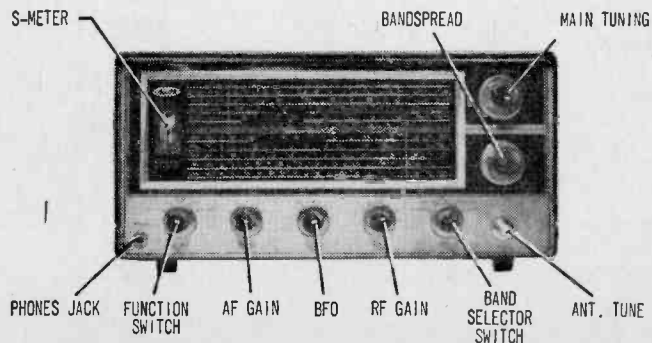With all the controls located across the bottom and side of the A-2515, a right-handed operator always get a clear view of the tuning dial and S-meter no matter what knob adjustments are made.



Unnoticed by most, a workhorse for few, the clamp-on ammeter tells you without touching!

A lot has been written about the current and voltage meters experimenters use every day. There is one useful instrument, however, that seems to go unnoticed—it's the *induction, snap-around, or clamp-on* meter which operates on the transformer principle. The clamp-on ammeter's big advantage over the usual type is that it does not require point-to-point contact with the circuit being measured. But, before we explore how it functions, let's review some basic meter theory.

When Grandpa Was a Boy.


The first practical, commercially produced meter movement was the Weston type (1888), which was a modified D'Arsonval (1881) movement. It is still one of the most widely used movements for meters of all types. Basically a galvanometer, this movement depends upon the torque exerted on a coil in a magnetic field.

The credit for such galvanometers goes back to Hans Christian Oersted and Arsene D'Arsonval. Oersted in 1819 observed that a pivoted magnet, or compass needle, deflected when placed near a wire carrying a current. In 1881, D'Arsonval applied Oersted's observation to an electromechanical arrangement which was to become known the world over as the D'Arsonval movement—grandfather of meter movements.

Meter Construction. In the moving coil or pivoted coil movement (see drawing on next page), as the modified D'Arsonval movement is commonly referred to today, Oersted's arrangement is reversed: the magnet (Oersted's compass) is stationary and the coil (the wire carrying the current) moves. The magnetic field of the horseshoe magnet, whose poles are designated N and S, is concentrated by the soft iron cylinder core (F). The coil (C) consists of turns of insulated copper wire on a rectangular frame and is connected to helix springs (H) at the top and bottom. These springs provide a restoring or counter torque when the moving coil is deflected from its normal position. The

springs also carry current to the moving coil.

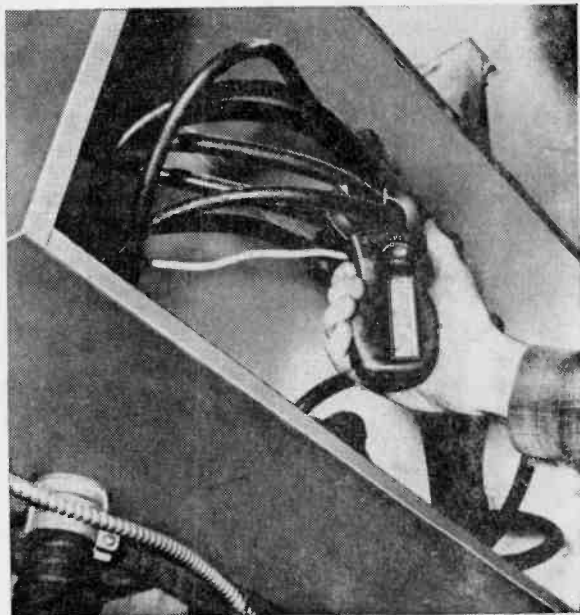When current flows through the moving coil (arrows in drawing), a magnetic field is set up around each side of the coil. Although the field will be in opposite directions on each side of the coil due to current going





Clamp-on to Current

by Sol Wexton

down one side and up the other (arrows), the interaction of this magnetic field with the magnetic field of the permanent magnet will cause force to be exerted in the same direction of rotation.

This turning moment causes the coil (C) to rotate and as it does, a counter torque is set up by the helix springs (H). The moving coil will continue to turn until it reaches a position where the torque of the springs (H) is equal and opposite to the torque of the moving coil. With no current applied

e/e CLAMP-ON METERS

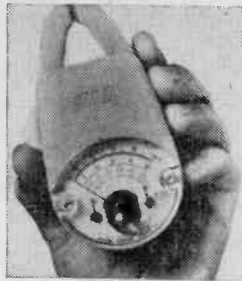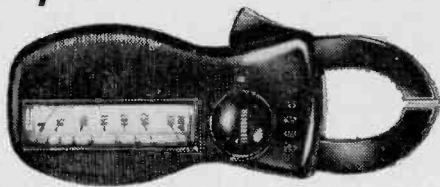

Two models of the Amprobe clamp-on testers described in this article. Unit left has rotary scale that selects correct range required. Also, meter readings stay locked so they can be taken in dark, read in light. Unit at right measures current only.


to the moving coil, the pointer (P) will automatically fall back to its zero null position.

The amount of deflection depends on the strength of the magnetic force created by the current flowing through it—the greater the current the greater the magnetic force and the farther the coil will turn. In a well-designed instrument, the deflection of the coil in angular degrees is directly proportional to the current.

The pointer (P), which is attached to the

scribed. However, its method of sampling is quite different.

Induction Theory. Twelve years after Oersted made his observation, Michael Faraday found that if current in a coil was started and stopped by closing and opening a switch, the increasing and decreasing magnetic field would induce a current in a second coil held next to it. This action is called mutual induction—the principle of a transformer. The iron core of the transformer concentrates magnetic force between the two windings—

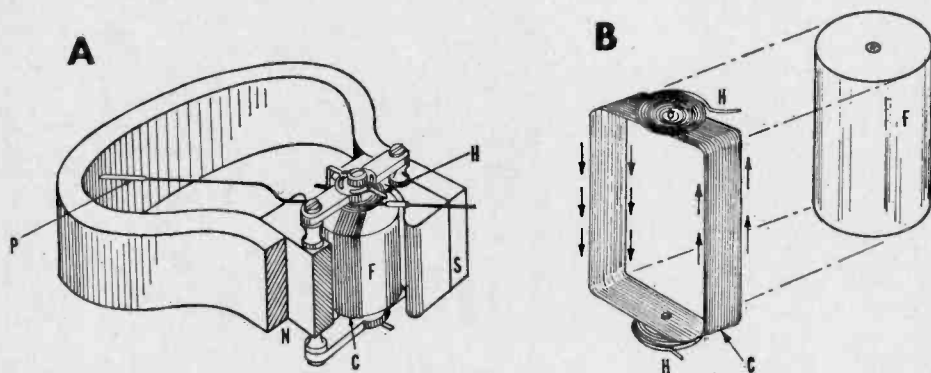


Detailed drawing of the moving-coil movement common to DC meters in use today. Cut-away diagram (A) gives complete construction details. Electrical connection to coil C (B) is made thru helix springs (H).

moving coil and moves with it, indicates on a scale (not shown) the amount of current flowing through the coil. This, fundamentally, is how the majority of meters (ammeters, ohmmeters, voltmeters, etc.) operate. The method of sampling the current and channeling it through the meter movement is also similar in most meters. It requires direct contact—through a connector or some type of test probe—with the circuit to be measured.

The induction or clamp-on meter, too, has a movement which is identical to the one de-

scribed. However, its method of sampling is quite different. Alternating current, because it is constantly reversing polarity, accomplishes the same thing as Faraday's closing and opening the switch in his direct current circuit. (See drawing above.)

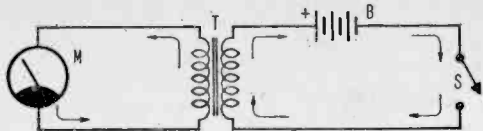
It is this principle which makes possible the induction-type ammeters shown in the photos. By encircling a single conductor with the hinged jaws of an induction pickup, it becomes, in effect, the primary winding of a transformer. The AC current flow in the conductor induces a varying magnetic field in the hinged induction pickup. The pickup



This is simple circuit Michael Faraday first used to demonstrate principles of transformer. When switch is closed current surge in battery circuit causes inductive "kick" in secondary. This kick is a current pulse that causes meter's pointer to move momentarily.

serves as the soft iron core of a transformer which, in turn, induces an AC current in the secondary coil.

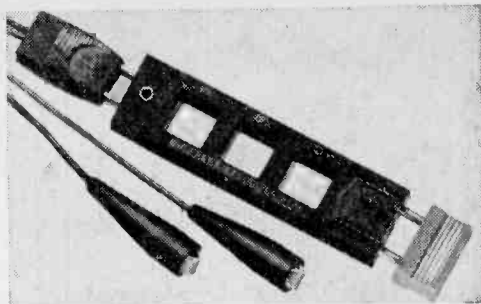
The secondary coil inside the instrument is connected to the meter movement through a series of calibrating resistors and a bridge rectifier (see schematic diagram). Rectification is required here since the meter movement is a direct current device and current being sensed by the induction method is alternating. A switch on the instrument selects appropriate circuit resistors capable of read-




Amprobe A-45L Energizer offers clamp-on meter a measuring point without breaking line cords apart.

range ammeter/voltmeter, ammeter/ohmmeter and ammeter/voltmeter/ohmmeter, all in one instrument.

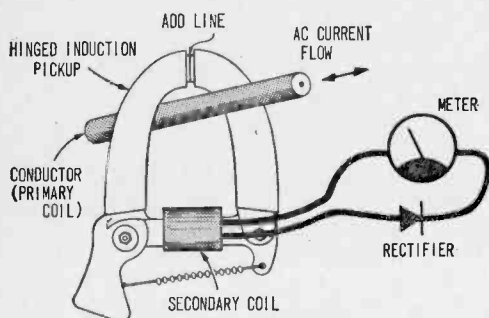Clamp-on meters which incorporate an ohmmeter usually do it through an external adapter (built into one of the test probe lines) which supplies the power and fuse for meter protection required in an ohmmeter (see photo).



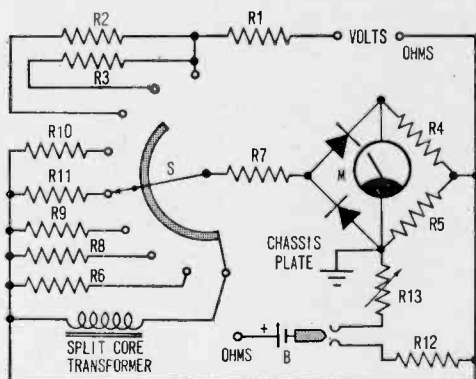This circuit is very much like that shown at top of page. Conductor is actually one turn of primary winding of transformer. Hinged induction pickup is iron core of transformer. Rectifier permits use of standard D'Arsonval meter movement offering continuous meter indications.



Schematic diagram of the Amprobe RS-3 clamp-on meter that doubles as an ohmmeter (25 ohms mid-scale) and three-range voltmeter (0-150-300-600 V.).

ing current in the circuit being measured. Thus we have a multirange AC ammeter using an induction method of sensing current.

Some Extras. This instrument, with only a few additional components, can also function as an AC voltmeter. With test lead inputs and appropriate series resistors through the range selector switch, AC voltages can be measured. The series resistors proportionately reduce voltage to a safe value for the rectifier and meter circuit.


By using the same idea an induction-type meter can also function as a single or multi-

The major advantage of the clamp-on ammeter is that it is not necessary to break into the circuit, motor or appliance to be monitored. It is only necessary to clamp the transformer jaws around one of the conductors to obtain a reading. In instances where all conductors are in a common cable or cord and the physical splitting of the cord to enable encircling one conductor is not desirable or possible, an energizer adaptor enables a reading to be made. This accessory also extends the sensitivity of the clamp-on meter 5 to 10 times for low current work. ■

a new start for HOMER HACKLEBY

Classified ads start many careers—here's one to forget!

by Charles Getts

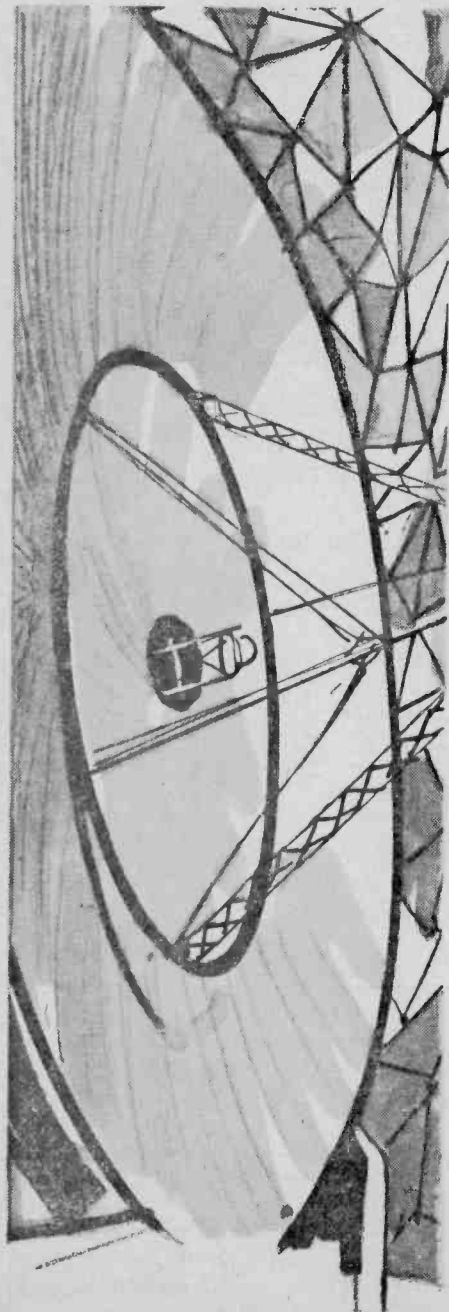

MEET EXOTIC GIRLS! Intelligent, single man with electronic background wanted as agent at once. Call Nat. Security Association KL 5-1212.

Homer Hackleby read the ad a second time, then put down the paper. Apart from the desire to follow every attractive girl he saw, he had only one minor aberration which he acquired quite recently. It was simply that, every time he looked into a mirror, he saw the image of James Bond, agent 007. As Homer was 52, bald, and rather chubby, this was quite a mental distortion.

So it is understandable that he now reached immediately for the phone and dialed the number given in the ad. After a short conversation he hung up with an excited gleam in his myopic eyes.

"Spencer, there is a possibility that I will not need your services much longer," he told the thin-faced young man pattering at a cluttered work bench in the garage. "I will probably have to close down the Hackleby Electronics Company very soon."

"Then you're not going to go ahead with the Electronic Dictatypewriter you were telling me about yesterday?", asked Spencer.

"No. Anyway, I doubt if it would sell. Most office men would prefer to have the live, flesh-and-blood secretary. Not much fun in holding a

(Continued on page 106)



EE's



BASIC COURSE IN



ELECTRICITY & ELECTRONICS*

PART VIII




RADIO TRANSMITTERS AND RECEIVERS

WHAT YOU WILL LEARN. When you have finished this part of the **ELEMENTARY ELECTRONICS Basic Course** you will have learned what the electromagnetic frequency spectrum is, what a radio transmitter is, how it develops a broadcast signal, and how radio signals are transmitted through the atmosphere. You will also learn how a broadcast signal is received, and how a radio receiver converts it into sound.

In this and the following part in the next issue you will become familiar with the

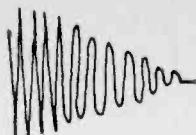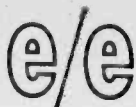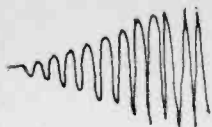* This series is based on **Basic Electricity/Electronics**, Vol. 1, published by Howard W. Sams & Co., Inc.






general principles of operation for certain equipment. As pointed out previously, an understanding of how electronic equipment works will help you put descriptions of components and circuits into proper frames of reference so their meaning is not lost.

ELECTROMAGNETIC RADIATIONS

Energy that radiates from a source is said to be an *electromagnetic wave*. *Gamma rays*, which are given off by radioactive particles such as radium, uranium, or atomic-bomb fragments, are electromagnetic waves. *Cosmic rays* from the sun travel extensive distances to the earth as electromagnetic waves. Electromagnetic waves, which include light, radiated heat, and radio signals, travel through space at the rate of 186,000 miles per second.

Electromagnetic Frequency Spectrum

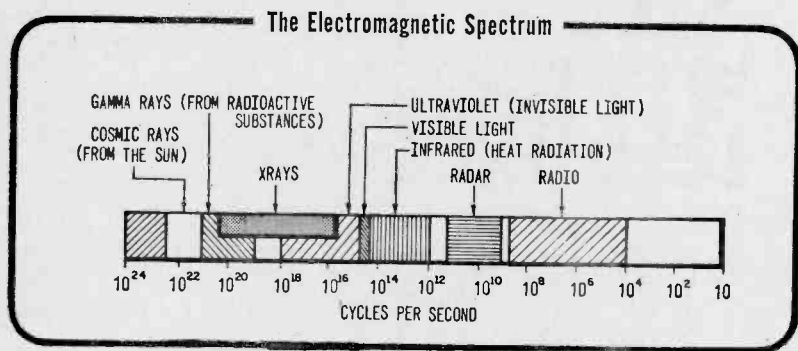Electromagnetic radiations differ from each other in terms of their frequencies (cycles per second). The frequency of one of these radiations is the number of times a single cycle repeats itself in 1 second. An *electromagnetic spectrum chart*, showing the relationship of these frequencies, is given below.




The chart shows that cosmic rays are radiated at a frequency of around 10^{22} cycles per second. (The number 10^{22} is 1 followed by 22 zeroes, or ten-thousand, million, million, million cycles per second.) At the lower end of the radio portion, radiation frequency is under 10^4 , or 10,000 cycles per sec.

Assigned Broadcast Frequencies

The Federal Communications Commission (FCC) has assigned specific groups of frequencies to different types of communications transmissions. This is shown in an expansion of the radio-frequency portion of the spectrum.

Commercial transmitters (radio and television, for example) are assigned a transmitting frequency in the appropriate part of the radio-frequency spectrum. Transmitters broadcasting in the home radio band are on 535 kHz to 1605 kHz.

The Radio Frequency Spectrum

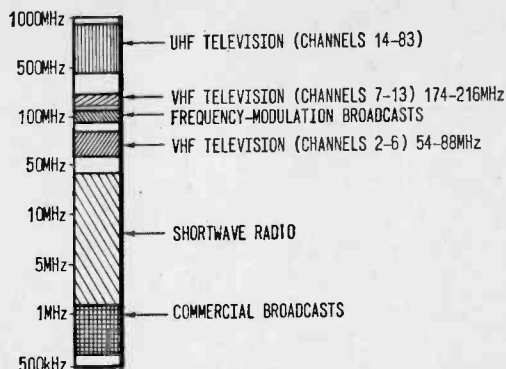




- Q1. Cosmic rays and radio waves are examples of -----.
- Q2. Sound (is, is not) electromagnetic radiation.
- Q3. Radio waves travel from the broadcast station to a receiving antenna at the rate of ----- miles per second.
- Q4. ----- is the characteristic which distinguishes one electromagnetic wave from another.
- Q5. Commercial radio transmissions are at a (higher, lower) number of cycles per second than television.
- Q6. A frequency of 1000 kilohertz would be assigned to (commercial, short-wave) radio.

Your Answers Should Be:

- A1. Cosmic rays and radio waves are examples of *electromagnetic radiations* (waves).
- A2. Sound *is not* electromagnetic radiation. Remember? It is changing air pressure.
- A3. Radio waves travel from the broadcast station to a receiving antenna at the rate of *186,000* miles per second.
- A4. *Frequency* is the characteristic which distinguishes one electromagnetic wave from another.
- A5. Commercial radio transmissions are at a *lower* number of cycles per second than television.
- A6. A frequency of 1000 kilohertz would be assigned to *commercial* radio. (1000 kilohertz is equal to 1 MHz.)

RADIO TRANSMITTERS

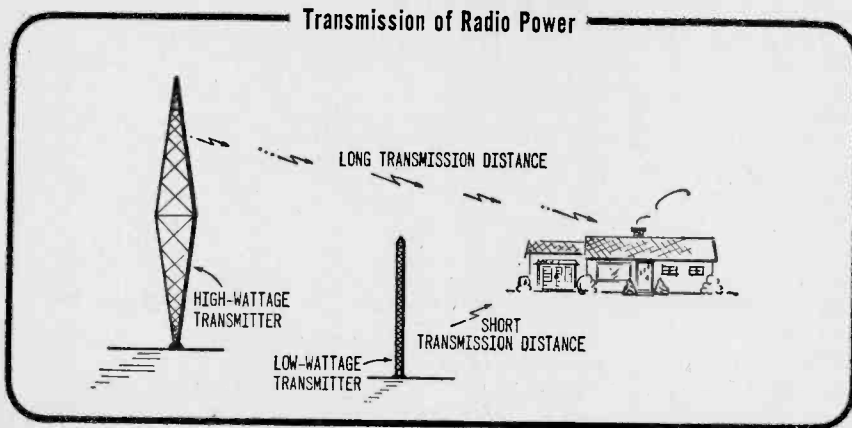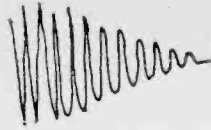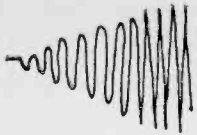The dial on your home receiver is marked off in numbers, probably from 540 to 1,600 kilohertz (or 54 to 160). By rotating the tuning dial, you select the desired station. Since each local station broadcasts at a different frequency, you are able to select the one you desire. The dial setting indicates the broadcast, or *carrier*, frequency of the station.



Transmitter Power

You have also noted that some stations come in stronger than others. The stronger stations broadcast at higher power (measured in *watts* or *kilowatts*) than the weaker. Or, if one of two stations broadcasting at equal power is stronger than the other, the stronger station is closer to your home.

The illustration seen above shows two antennas transmitting at different frequencies in the broadcast band. The one farther away is broadcasting at many kilowatts of power and is able to reach the receiver. The low-wattage transmitter, although nearer, does not have enough power to span the distance. This may explain why you cannot pick up some stations that are located in your general area.

Carrier and Audio Frequency

The frequency assigned to a broadcast station is called its *carrier frequency*. The transmitter and its antenna are designed and tuned to that specific frequency. As its name implies, the carrier frequency carries the reproduction of the sound originating in the studio. Actually, there are two frequencies that leave the transmitter, a *radio frequency* (carrier) and an *audio frequency* (sound). Audio frequencies are classified as being between 20 and 20,000 cycles per second. The frequency range of most human ears, however, is usually no higher than 15,000 cps.

- Q7.** A home radio receiver (can, cannot) be tuned to 1 megacycle.
- Q8.** 900,000 cycles per second (could, could not) be a carrier frequency of a commercial broadcast station.
- Q9.** The power of Station A is one megawatt. Station B is broadcasting at 500 kilowatts. Which station will transmit the longer distance?


- Q10.** Two broadcast stations are equally distant from your home. Assuming your receiver is good, what would be the reason you could not receive one of them?
- Q11.** A human ear (can, cannot) hear a radio frequency.
- Q12.** A frequency of 600 kilocycles is classified as a(an) (audio, radio) frequency.

Your Answers Should Be:

- A7.** A home radio receiver *can* be tuned to 1 megacycle. One megacycle (1,000 kc) is within the broadcast band.
- A8.** 900,000 cycles per second *could* be a carrier frequency of a commercial broadcast station. It is the same as 900 kc.
- A9.** *Station A.* It has twice as much power.
- A10.** *One station* is so weak in power it cannot transmit the distance.
- A11.** The human ear *cannot* hear a radio frequency.
- A12.** A frequency of 600 kc is classified as a *radio* frequency.

A Basic Transmitter



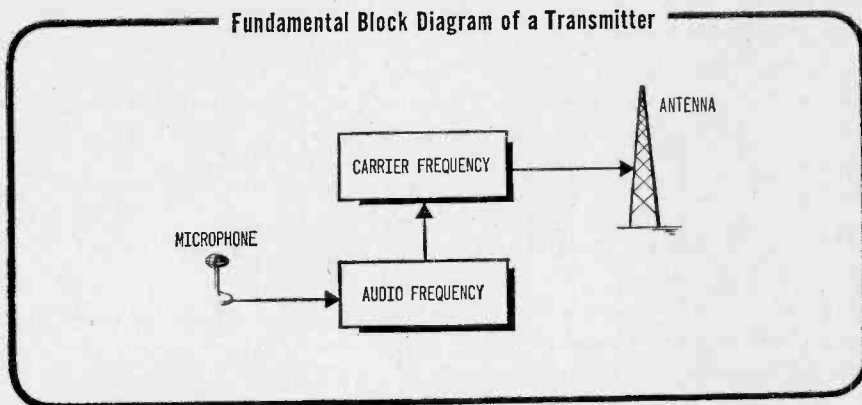
The diagram below shows a *functional block diagram* of a typical broadcast transmitter. It is called a functional block diagram because each block is representative of a general electronic function and may include several circuits.




The arrowheads between blocks show the direction of signal flow. You can probably already read what the diagram reveals.

Sound enters the *microphone* and is fed to the audio-frequency (AF) section. The sound, because it is too weak for transmission purposes, is amplified (signal amplitude is increased) and then passed to the carrier-frequency section.

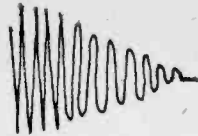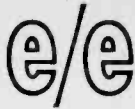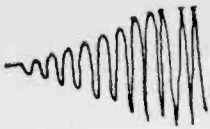Carrier Frequency. The specific radio frequency (RF) assigned to the broadcast station is developed in the carrier-frequency block. Passing through several circuits, the RF signal is boosted in power (increased in amplitude) to the rated wattage output of the transmitter. Just before the RF carrier is fed to



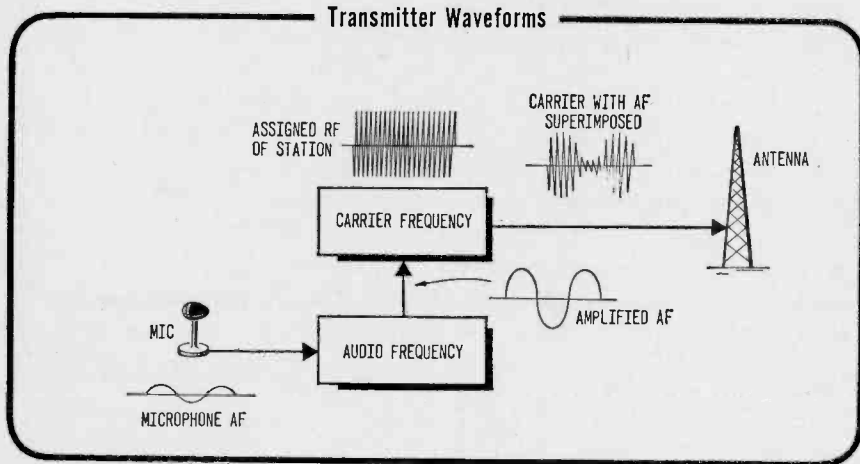the antenna, the AF signal is superimposed on it. Waveforms developed in each block are shown below.



Superimposing the Sound. The process of superimposing AF on the carrier, as shown in this particular example, is called *amplitude modulation* (AM). In amplitude modulation the audio frequency (varying at the changing rate of the original sound) is mixed with the carrier (a constant frequency) in a manner that causes that carrier *amplitude* to vary at the same rate as the audio. The carrier *frequency* remains unchanged.


- Q13. The drawing on the opposite page is called a(an) ----- diagram.
- Q14. Sound enters the AF section by way of a device called a(an) -----.
- Q15. ----- on a block diagram show the signal direction between blocks.
- Q16. Placing AF on a carrier without changing the carrier frequency is called -----.

Your Answers Should Be:

- A13. The drawing on the opposite page is called a *functional block* diagram.
- A14. Sound enters the AF section by way of a device called a *microphone*.
- A15. *Arrowheads* on a block diagram show the signal direction between blocks.
- A16. Placing AF on a carrier without changing the carrier frequency is called *amplitude modulation*.

Carrier-Frequency Circuits

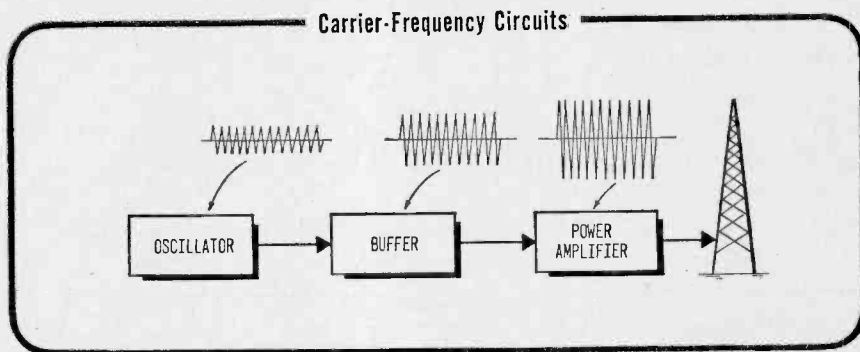A minimum number of carrier-frequency circuits are shown in the diagram below. An actual broadcast station has many more circuits to attain the frequency stability and power required of its transmitter. The additional circuits are similar to those shown, however.





The Oscillator. The purpose of the *oscillator* is to generate a stable RF signal. The resistance, inductance, and capacitance that make up its input circuit are such that they will not allow the vacuum tube in the oscillator to amplify any other signal but that of the desired frequency. The stable-frequency, low-amplitude output of the oscillator is shown above.

The Buffer. This stage (another name for circuit) is sometimes called an *intermediate power amplifier*, or *frequency multiplier*. In most transmitters it performs three functions. As a *buffer*, the stage isolates the oscillator from the effects of the other circuits. Without this isolation, stray signals may be fed back to the oscillator, causing it to operate at the wrong frequency. As an *amplifier*, the buffer increases the amplitude of the oscillator signal to a level that is between the desired transmitter output and the amplitude of the oscillator signal. In many transmitters the buffer circuit *doubles* (or even *triples*) the frequency of the oscillator output. The oscillator may not be capable of generating the station frequency by itself. In order to produce the assigned frequency, a transmitter may require several multiplier stages.

The Power Amplifier. The purpose of the *power amplifier* is to increase the amplitude of the RF signal to the power (wattage) requirements of the station. Several stages of power amplification may be required to achieve this. Normally, the audio signal from the AF circuitry is fed to the final power amplifier and used to modulate the carrier.

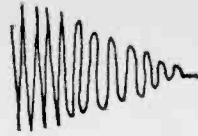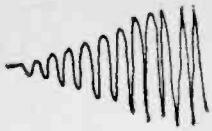- Q17. A transmitter circuit which amplifies a signal and increases its frequency is called a(an) -----.
- Q18. A(an) ----- generates a signal which has a uniform frequency.
- Q19. ----- amplifier output is measured in watts.
- Q20. AF and RF are mixed in what stage?
- Q21. The carrier arrives at the antenna with its waveform (amplitude, frequency) modulated.




Your Answers Should Be:

- A17. A transmitter circuit which amplifies a signal and increases its frequency is called a *multiplier*.
- A18. An *oscillator* generates a signal which has a uniform frequency.
- A19. *Power* amplifier output is measured in watts.
- A20. AF and RF are mixed in the *final stage of the power amplifier*.
- A21. The carrier arrives at the antenna with its waveform *amplitude* modulated.

Audio-Frequency Circuits

The Microphone. Regardless of the many different types of microphones that are available, even the best develop only a weak signal.

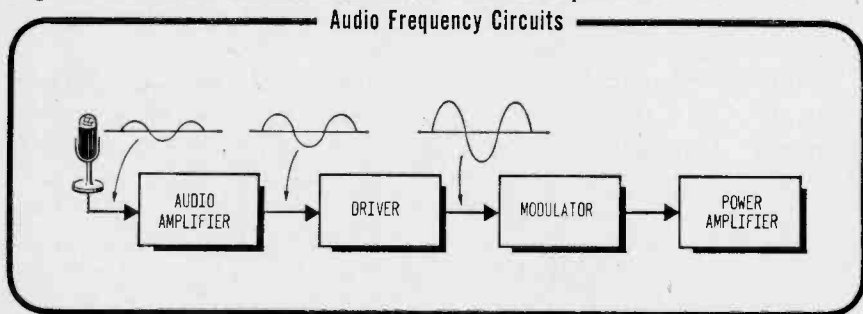The Audio Amplifier. Although a single stage of audio amplification is sometimes all that is necessary, larger transmitters may have two, three, or more stages to obtain the desired undistorted level of amplitude.



The Driver. Like most circuits, the *driver* obtains its name from its purpose. The driver amplifies the AF to the voltage level required to “drive” the tubes of the modulator. The modulator tubes require large changes in signal amplitude to operate properly.


The Modulator. The *modulator* is a power amplifier quite similar to the final circuit of the carrier-frequency block. It amplifies the audio signal to a power level suitable for modulating the carrier power in the final power amplifier. Its power output is roughly half that of the final carrier amplifier.

Antennas

If all circuits are operating properly, an AM (amplitude-modulated) carrier is fed to the antenna and transmitted into the atmosphere.

Power is fed to the antenna in the form of both current and voltage. Voltage sets up an electric field along the length of the antenna. Current, in traveling through the antenna (a conductor), sets up a corresponding magnetic field. Both fields vary at the rate of the carrier frequency and at the amplitude and frequency of its audio envelope.

Antenna Radiation



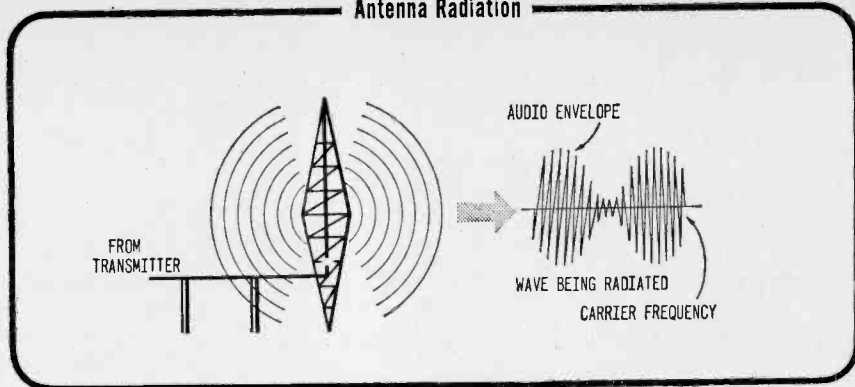


Both fields expand outward and collapse back to the antenna at the rate of the carrier frequency. The outermost waves continue through space and do not return to the antenna. This action is similar to dropping a pebble in a pool. The energy of the waves moves outward in ever-widening circles; the water, however, remains in place.

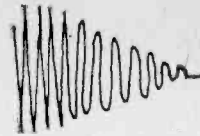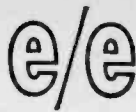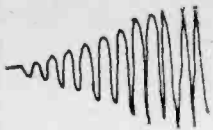- Q22. The weak output of a microphone is fed to one or more stages of ----- amplification.
- Q23. The output of even the best microphone (can, cannot) be fed directly to the modulator.
- Q24. The output of the ----- is connected to the carrier power amplifier.
- Q25. For proper modulation, the output of the modulator stage must be ----- that of the power amplifier.
- Q26. Carrier voltage develops a(an) ----- field and carrier current develops a(an) ----- field on the antenna.
- Q27. All of the energy in the antenna fields (does, does not) leave the antenna.


Your Answers Should Be:

- A22. The weak output of a microphone is fed to one or more stages of *audio* amplification.
- A23. The output of even the best microphones *cannot* be fed directly to the modulator. (Even the most powerful microphones develop a signal that is much too weak to drive the modulator.)
- A24. The output of the *modulator* is connected to the carrier power amplifier.
- A25. For proper modulation, the output of the modulator stage must be *half* that of the power amplifier.
- A26. Carrier voltage develops an *electric* field and carrier current develops a *magnetic* field on the antenna.
- A27. All of the energy in the antenna fields *does not* leave the antenna.



A RADIO RECEIVER

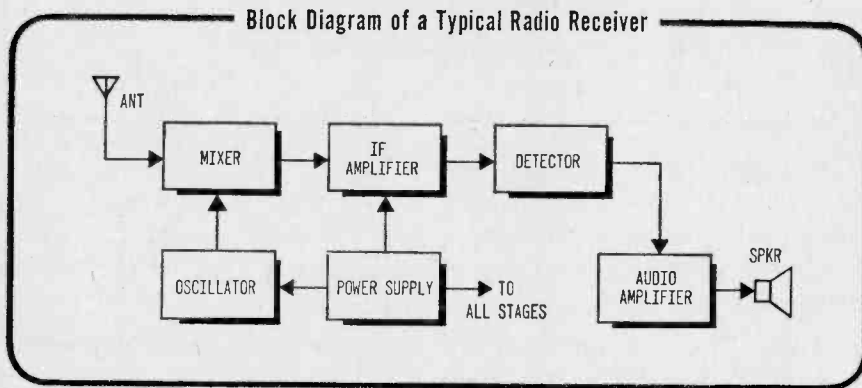
The block diagram for a radio receiver similar to the one in your home is shown below.



The purpose of the radio receiver is to convert the amplitude modulation on the carrier back to its original sound. As the carrier increases in ever-widening circles on leaving the transmitter antenna—like ripples in a pool—its energy decreases in amplitude. The increasing circumference of the circles causes power in the waveform to be distributed over an ever-increasing area. By the time the signal reaches the receiver antenna it is rather weak, usually around a few thousandths or millionths of a volt. The receiver, therefore, must amplify the received signal to a level that will operate the speaker within the hearing range of the human ear. The receiver must also extract the audio component (the *envelope*) from the carrier. The carrier brings the signal to the receiver, but has no value in the reproduction of the audio frequency in the receiver.

RECEIVER CIRCUITS

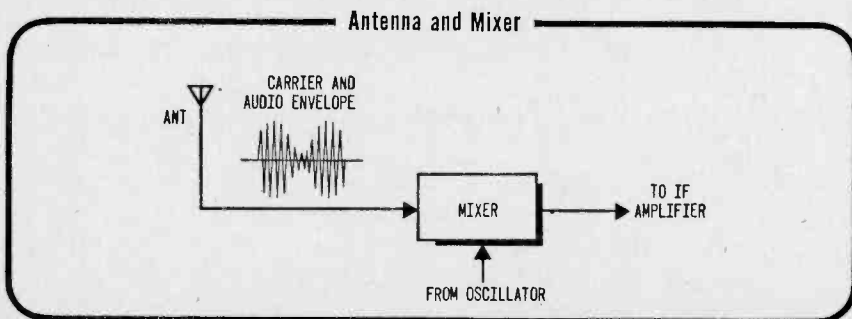The Power Supply. Each receiver has a power supply. Its purpose is to convert 115 volts AC from an electrical outlet (or to provide DC if the receiver is battery-operated) to voltages that will operate the receiver properly.



The Antenna and Mixer. Carrier frequencies from all stations within range


of a receiver appear on the antenna of the receiver. When you turn the dial of your radio to a specific station, you adjust the electronic components of the *mixer* input so that the receiver will accept a particular carrier frequency and reject all others. The received carrier enters the mixer to be amplified. Some radios have, in addition, an *RF amplifier* between the mixer and antenna.




- Q28.** What part of the received radio wave does the receiver convert back into original sound?
- Q29.** A radio wave decreases in power as the circumference of its area increases. What is the approximate amount of voltage that enters the receiver antenna?
- Q30.** The ----- converts AC to voltages required to operate the receiver circuits.
- Q31.** A single broadcast frequency appears at the input of the (antenna, mixer).

Your Answers Should Be:

- A28.** The *amplitude modulation* (or audio envelope).
- A29.** A few *thousandths* or *millionths* of a volt.
- A30.** The *power supply* converts AC to voltages required to operate the receiver circuits.
- A31.** A single broadcast frequency appears at the input of the *mixer*.


The Oscillator. The receiver oscillator is similar to its counterpart in the transmitter. Both generate a signal of constant frequency and amplitude. The purpose of the receiver oscillator is slightly different, however. It is designed to generate a frequency that is a constant number of kilocycles above the carrier frequency, regardless of the station to which the receiver is tuned. The tuning dial changes the values of the electronic components in the frequency-generating circuit of the oscillator at the same time it is adjusting the frequency-reception components of the mixer. The arrangement of adjustable components is such that the oscillator will always be tuned 456 kilocycles (or a similar frequency) above the frequency of the carrier being accepted by the mixer. The output of the oscillator is fed to the mixer, as shown in the diagram below.

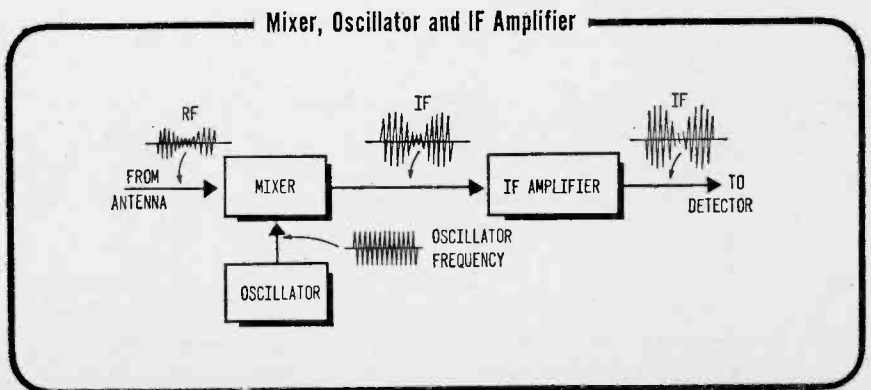

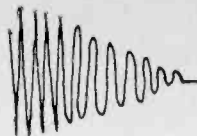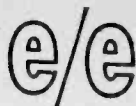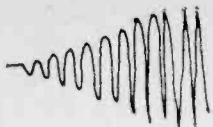


The Mixer. The carrier and oscillator frequencies combine in the mixer tube and four different frequencies appear at the output. One of these four is the *difference* between the oscillator and the carrier frequencies, and is usually 456 kilocycles. The other three are rejected by the next stage.

The IF Amplifier. The abbreviation for *intermediate frequency* is IF. In most home receivers the IF is 455 or 456 kc. Amplifying a single frequency in the IF circuit is much easier and causes less distortion than if it were necessary to tune this amplifier to each of the many station frequencies. The only purpose of this stage is to amplify the IF (which still retains the original audio frequency) and pass it on to the detector.

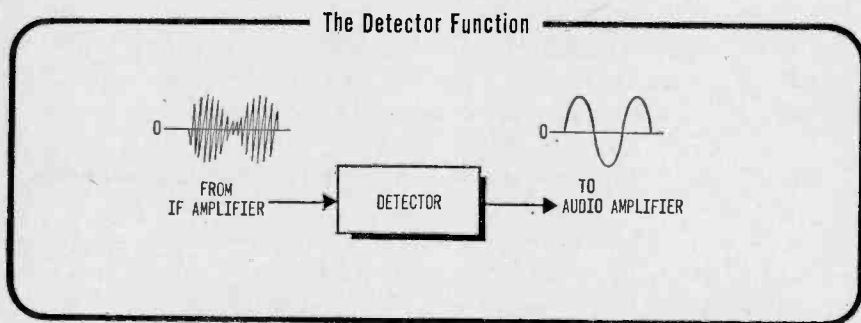

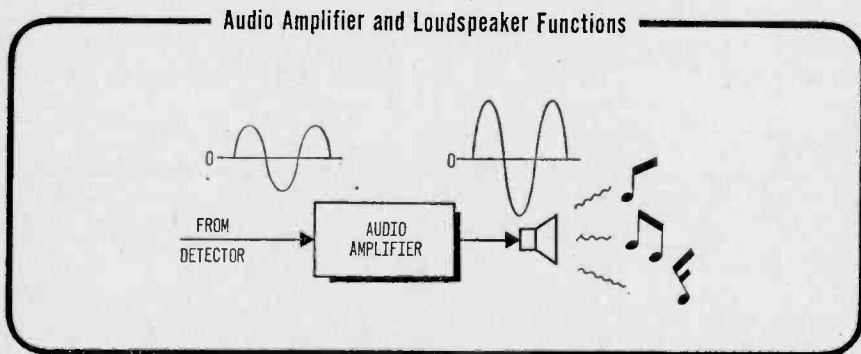The Detector. The purpose of the *detector* is to extract the audio component from the IF waveform. The audio envelope is the same (although reversed) at the top of the waveform as it is at the bottom. The detector circuit is so designed that it accepts only the audio frequency at the top and rejects the IF frequency in the waveform.



The Audio Amplifier. The final circuit in the receiver amplifies the AF fed to it by the detector. The amount of amplification can be varied by the volume-control knob on the front of the receiver. The output of the audio amplifier is applied to the speaker voice coil, causing the speaker cone to reproduce the sound that originated at the studio.


- Q32. The ----- removes the AF from the IF waveform.
- Q33. The oscillator develops a signal at a constant ----- and -----.
- Q34. The detector extracts the (audio, RF) component from the IF signal.

Your Answers Should Be:

- A32. The *detector* removes the AF from the IF waveform.
- A33. The oscillator develops a signal at a constant *amplitude* and *frequency*.
- A34. A detector extracts the *audio* component from the IF signal.

FREQUENCY MODULATION



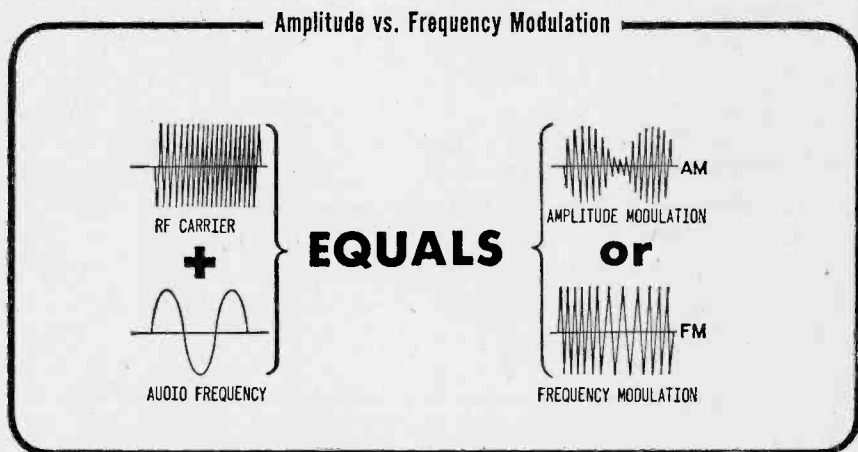
The transmitter and receiver with which you have just become familiar employs amplitude modulation (AM) to carry the audio. Another method of superimposing audio on a carrier is called *frequency modulation* (FM). Its process is quite different. The two are compared below.




Both AM and FM start out with a carrier frequency and an audio frequency (sound originating in the studio). In amplitude modulation, as you already know, the sound is superimposed on the carrier frequency (which is constant) by varying the carrier *amplitude* in conformance with the voltage and frequency of the audio.

In FM, however, the audio is mixed with the RF in such a way that the carrier *frequency* is varied in accordance with the amplitude of the sound. As the audio cycle goes positive, carrier frequency increases. When the audio cycle goes negative, carrier frequency decreases. The sum of the two changed frequencies in one audio cycle is still equal to the original carrier frequency.

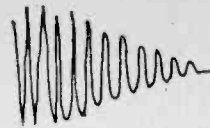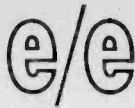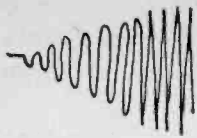One of the advantages of frequency modulation is its freedom from distortion. Noise and other forms of distorting voltages in the atmosphere or receiver are added to amplitude modulation. Since FM does not depend on a changing



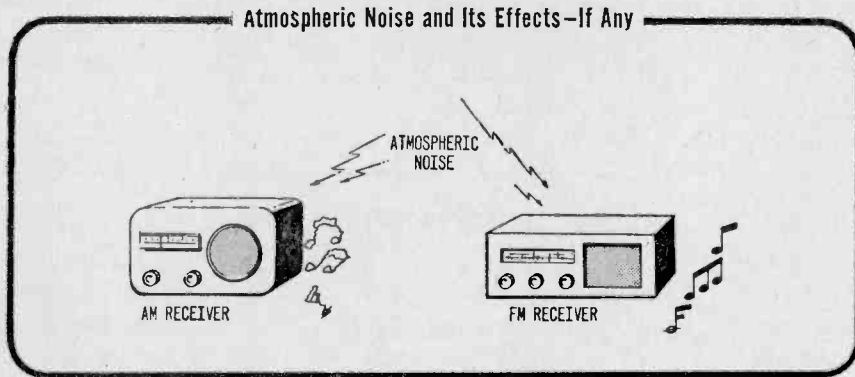amplitude to carry audio, noise has little or no effect on it. This is part of the reason for the clarity of sound that you get from an FM receiver.



- Q35.** In AM, the carrier ----- changes to match the audio.
- Q36.** In FM, the carrier ----- changes to match the audio.
- Q37.** An FM receiver is (more, less) subject to atmospheric noise than an AM receiver.

Your Answers Should Be:

- A35.** In AM, the carrier *amplitude* changes to match the audio.
- A36.** In FM, the carrier *frequency* changes to match the audio.
- A37.** An FM receiver is *less* subject to atmospheric noise than an AM receiver.

WHAT YOU HAVE LEARNED

- 1.** Radiant energy is given off by electromagnetic waves. The electromagnetic spectrum includes cosmic rays, X rays, visible and invisible light, infrared, radar, as well as radio waves.
- 2.** A radio transmitter is a device that produces electromagnetic waves in the radio portion of the spectrum. Its essential functions are the development and amplification of a carrier frequency and modulating it with an amplified audio frequency. A specific carrier frequency is assigned to each radio station. The distance that the carrier, with its superimposed audio, travels is determined by the power that is developed in the final stage of the transmitter.
- 3.** Energy in the form of voltage and current is fed from the transmitter to an antenna. This sets up electric and magnetic fields around the antenna that expand and collapse at the frequency of the carrier. Part

of the energy is in the form of electromagnetic radiations and is transmitted through the atmosphere. The farther it travels, the weaker the signal becomes.

4. All carrier signals within range are picked up by the receiver antenna. The tuning control on the front of the receiver adjusts the input of the mixer so that only the desired station carrier frequency is received. At the same time, it adjusts an oscillator to generate an IF above the carrier frequency. Carrier and oscillator frequencies are joined in the mixer and the difference between the two, the intermediate frequency, is amplified and fed to the IF amplifier. Here the signal and its audio component are further amplified. The next stage (detector) extracts the audio component and passes it to the final stage (audio amplifier). The audio is amplified and fed to the speaker, causing the cone to reproduce the sound that originated at the studio.
5. Amplitude (AM) and frequency (FM) modulation are two methods of transmitting audio on a carrier. When AM is used the amplitude of the carrier varies according to the loudness (amplitude) and frequency of the audio. In FM, the frequency of the carrier is varied instead of the amplitude. FM transmissions are less bothered by atmospheric and receiver noises.

NEXT ISSUE: PART IX

Understanding Television Transmitters and Receivers

This series is based on material appearing in Vol. 1 of the 5-volume set, BASIC ELECTRICITY/ELECTRONICS, published by Howard W. Sams & Co., inc. @ \$19.95. For information on the complete set, write the publisher at 4300 West 62nd St., Indianapolis, Ind. 46268.

DID YOU MISS ANY PART OF OUR BASIC COURSE?

Many readers have written letters requesting information on our Elementary Electronics Basic Course—what has been published and what will be published. The table below lists the parts of the Basic Course and the issues they have appeared or will appear in. If you missed any part and wish to obtain an issue of Elementary Electronics that contains it, send \$1.00 for each issue to Back Issue Dept., Elementary Electronics, 229 Park Ave. So., New York, N.Y. 10003. Be sure to tell us exactly which issue(s) you want and include your name and address.

Issue	Part	Title
Mar./Apr. 1968	I	Basic Electrical Circuits
May/June 1968	II	Understanding Resistors
July/Aug. 1968	III	Understanding Capacitors
Sept./Oct. 1968	IV	Understanding Transformers
Nov./Dec. 1968	V	Understanding Vacuum Tubes
Jan./Feb. 1969	VI	Understanding Basic Circuit Actions
Mar./Apr. 1969	VII	Understanding Transistors
May/June 1969	VIII*	Understanding Radio Transmitters & Receivers
July/Aug. 1969	IX**	Understanding TV Transmitters & Receivers

* In this issue. ** Available at newsstands on May 22, 1969.

UNIMETRICS OMNIBAND III
VHF/AM/FM
Portable AC/DC Radio



Radio entertainment is not limited to just the AM, FM and BCSW frequencies. You'll find two public service VHF bands, the low one at 30 to 50 MHz and the high at 147 to 174 MHz, provide some of the most exciting listening to be found in the radio spectrum. To name just a few: fire, police and emergency services; radio-TV news reporters calling in their stories and the continuous regional weather reports of the U.S. Weather Bureau, which are not only up to the minute but which can be a lifesaver to a boat owner.


We Took the High Road. The Unimetrics Omniband radios all designed to provide portable or fixed monitoring of the public service bands as well as the standard AM and FM broadcast frequencies. They are available in two models, one tuning AM, FM and the low-band VHF (30-50 MHz), the other tuning AM, FM and the high-band VHF (147-174 MHz). Since high-band listening is more popular, because of the regional weather reports, we chose to test the high-band model.

The Unimetrics Omniband III high-band VHF radio uses twelve transistors and is powered either by four internal C batteries or a built-in 117-VAC power supply. A switch under the battery cover selects the AC or DC mode of operation. A three-stage

IF amplifier feeding a standard diode detector is used for AM reception. While the same three IF amplifiers do double duty as the FM/VHF IF amplifiers, the VHF selector switch cuts in a fourth IF amplifier and a ratio detector for the FM and VHF reception. Since the ratio detector is in itself "inter-station noise immune" to a large degree, no squelch is provided. Under normal conditions only a faint background noise is heard between FM and VHF stations. Separate local oscillators are provided for the AM, FM and VHF bands. A built-in ferrite antenna is provided for AM reception, with a telescopic whip for FM and VHF. An antenna jack provides for connection of an external FM or VHF antenna.

The audio amplifier feeds a 3½" speaker. A supplied earphone can be plugged into the unit automatically disconnecting the speaker.

Performance. The Unimetrics Omniband III, compared to other combination VHF receivers in its price range, proved to be a "hot" performer. As an AM radio it is extremely sensitive, pulling in stations just above the noise level which could barely be heard on AM radios priced to \$50. FM performance was equally good. Since a sensitivity measurement is really valueless on a portable radio, we again compared the Omniband III's performance against competitive FM radios. The Omniband proved about as sensitive as the best of FM portable
(Continued on page 110)

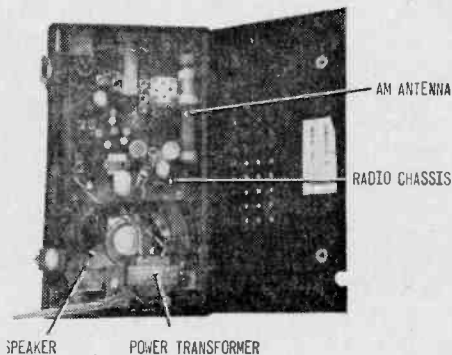

Good quality sound is delivered by the relatively large 3½" speaker. All critical tuned circuits on the chassis are secured to the chassis by a "blob" of wax. Severe jolts will not detune the set's high frequency circuits.

10 Reasons why RCA Home Training is

your best investment for a rewarding career in electronics:



Transistor experiments on programmed breadboard—using oscilloscope.

1 LEADER IN ELECTRONICS TRAINING

RCA stands for dependability, integrity and pioneering scientific advances. For over a half century, RCA Institutes, Inc., has been a leader in technical training.

2 RCA AUTOTEXT TEACHES ELECTRONICS FASTER, EASIER

Beginner or refresher — AUTOTEXT, RCA Institutes' own method of Home Training will help you learn electronics faster, easier, almost automatically.

3 THOUSANDS OF WELL PAID JOBS ARE OPEN NOW

RCA Institutes can help you qualify for a rewarding career if you have an interest in electronics. Every year, thousands of well paid electronics jobs go unfilled just because not enough men take the opportunity to train themselves for these openings.

4 WIDE CHOICE OF CAREER PROGRAMS

Select from a wide choice of courses and career programs ranging from basic Electronics Fundamentals to advanced training including Computer Programming and Electronics Drafting. Each

Career Program begins with the amazing AUTOTEXT method.

5 SPECIALIZED ADVANCED TRAINING

For those working in electronics or with previous training, RCA Institutes offers advanced courses. Start on a higher level. No wasted time on material you already know.

6 PERSONAL SUPERVISION THROUGHOUT

All during your program of home study, your training is supervised by RCA Institutes experts who become personally involved in your efforts and help you over any "rough spots" that may develop.

7 VARIETY OF KITS, YOURS TO KEEP

At no extra cost, a variety of valuable specially engineered kits come with your program—yours to keep and use on the job.

8 TRANSISTORIZED TV KIT AND VALUABLE OSCILLOSCOPE

You will receive in most career programs a valuable oscilloscope. Those enrolled in the TV Program or courses receive the all-new Transistorized TV Receiver—exclusive with RCA. Both are at no extra cost.

9 TWO CONVENIENT PAYMENT PLANS

Pay for lessons as you order them. No contract obligating you to continue the course. Or, you can take advantage of RCA's convenient monthly payment plan.

10 RCA GRADUATES GET TOP RECOGNITION

Thousands of graduates of RCA Institutes are now working for leaders in the electronics field; many others have their own profitable businesses... proof of the high quality of RCA Institutes training.

RCA INSTITUTES, INC. Dept. EAQ-59
320 West 31st St., N.Y., N.Y. 10001


Canadians: These same RCA courses are available to you in Canada. No postage. No customs. No delay. Your inquiry will be referred to our school in Canada.

All courses and programs approved for veterans under new G. I. Bill.

CLASSROOM TRAINING ALSO AVAILABLE. FREE CATALOG ON REQUEST.

ACCREDITED MEMBER National Home Study Council

Construction of Oscilloscope.

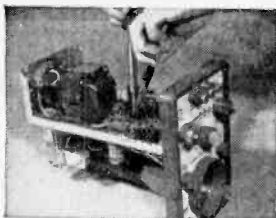

Construction of Multimeter.



RCA

If Reply Card Is Detached—Send This Coupon Today

RCA INSTITUTES, INC.

Home Study Dept. EAQ-59
320 West 31st Street
New York, N.Y. 10001

Name _____


Address _____

City _____

State _____

Zip _____

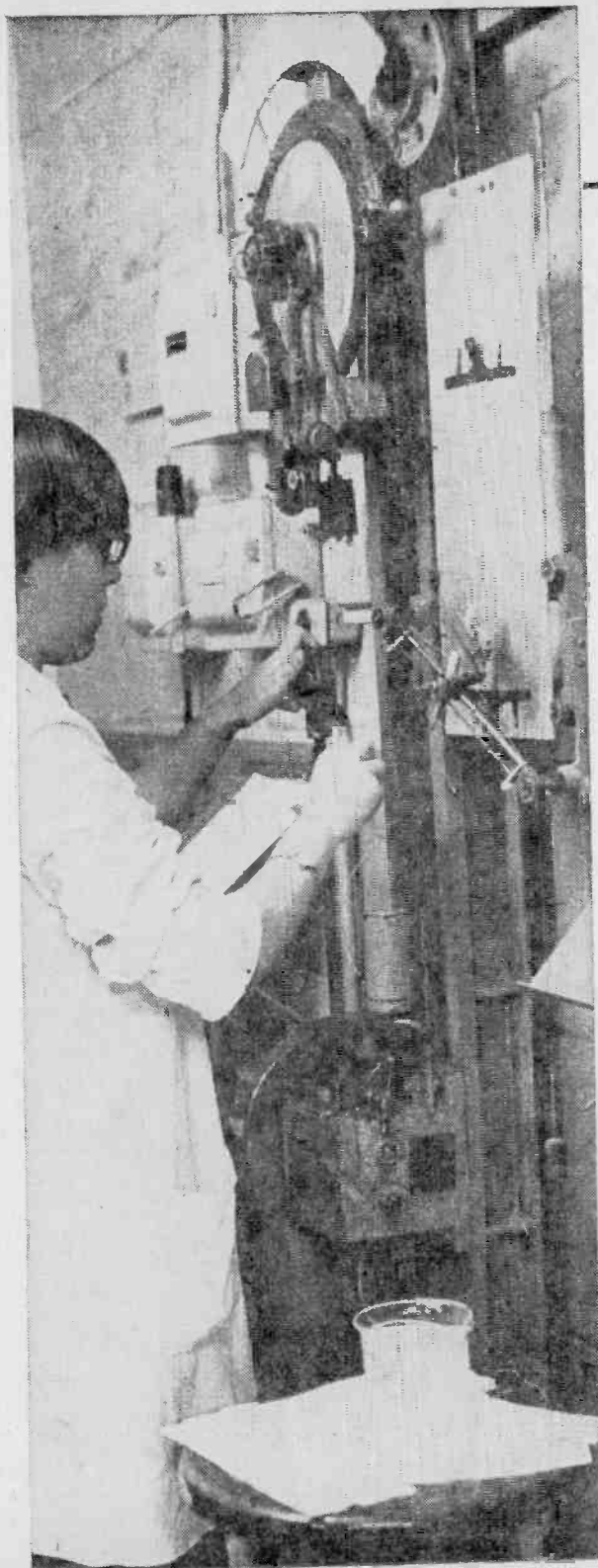Check here if interested in Classroom Training



Proof of the Pudding is in the Testing!

There's nothing particularly fishy about testing resiliency of sturdy fishing line at U.S. Testing Co. Girl winds strands around pulley, checks gauge for data.

There's a time-honored saying that a little knowledge may be dangerous. But when it comes to consumer products, a little ignorance can be cause for the panic button. If something you buy is chewed by the baby and proves toxic, he's in for trouble. If a raincoat isn't really waterproof, you may end up drenched. And if a food product said to be preserved has actually spoiled, indigestion may be the best (the least?) you can hope for.


For the sake of safeguarding consumers, therefore, the proof of the pudding is in the testing. And at the Hoboken, N.J., headquarters of the U.S. Testing Co., Inc., a team of researchers conducts no end of experiments in hopes of catching flaws in all sorts of products.

Testing takes many forms, and equipment for the tests varies greatly. One device, for example, called the FadeOmeter, subjects material to simulated sunlight. It consists of a carbon arc burning inside a glass globe that acts as a filter to correct the available spectrum. The materials being exposed are mounted in a rack revolving around the arc. Main function of the apparatus: to determine the material's resistance to color fading on exposure to sunlight.


(Continued overleaf)



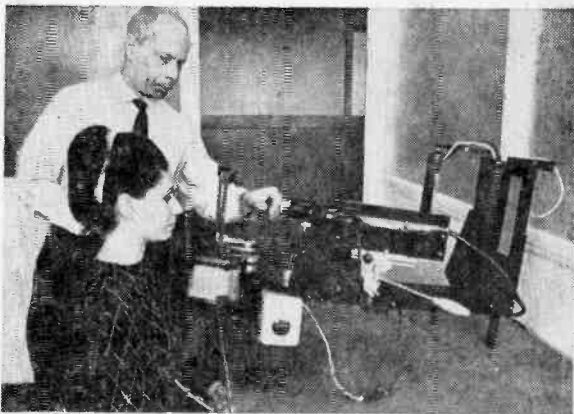FadeOmeter test at U.S. Testing Co. creates simulated sunlight to test fabrics for fading. Here, draperies reveal sunfastness.




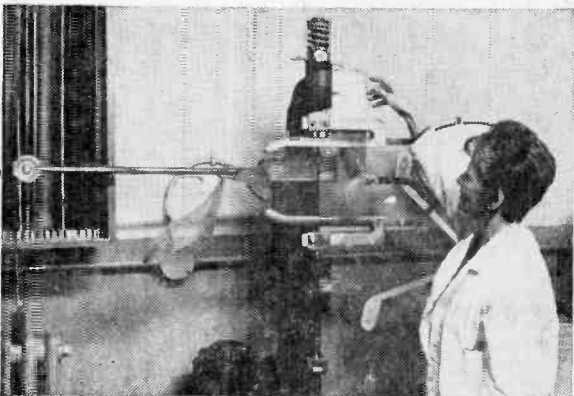Pupillometer tester records changes in diameter of subject's pupils, is used to improve teaching methods, study eye disorders.




Stretchometer tells researcher what she wants to know about elasticity of sheer nylon stockings before it goes on lady's leg.

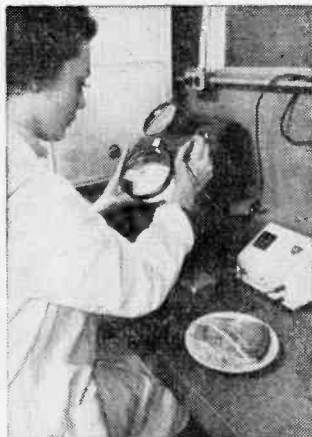Left, food preservation is important to many a supermarket. This special apparatus reveals rate of apple pie's bacterial growth. Right, lab technician heats test tubes containing variety of cultures, checks them for bacterial growth over 24-hr. period.



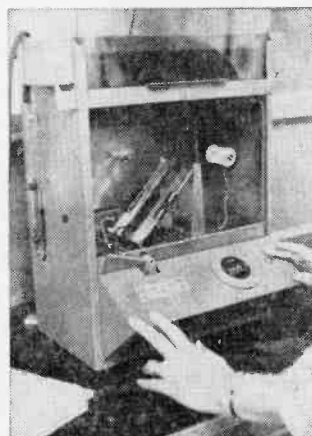Flammability tester (left) subjects wearing apparel for combustibility. Electrical micro-burner, fed by pure butane, catches up answer within one second. Right, researcher braces to use eye-movement camera. Device discloses what driver, pilots actually look at on job.




From FadeOmeter to pupillometer, the course of consumer product testing goes in one direction—progress. After all, no manufacturer can afford to rest on his old laurels while his competitors continue to improve and perfect a safer, more convenient, and superior product. Quietly working behind the scenes, the scientists at U.S. Testing help make the world a safer place to live in.

—C. Hansen ■

H.H. SCOTT MODEL LR-88

AM/FM/FM-Stereo

Solid-State Receiver Kit

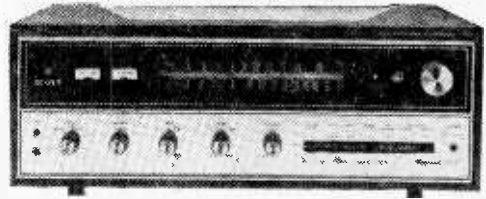

If you've had the itch to build a really top quality stereo receiver kit but have been scared off by thoughts of "acres" of PC boards, and bags and bags of parts, the Scott LR-88 FM Stereo Receiver kit is for you. Using Scott's by now familiar preassembled PC boards and color-matched pictorials, the LR-88 comes out as almost a *beginner's* kit.


Featurewise. The LR-88 is loaded! You name it and the LR-88 can do it. On the input side is AM, FM, Phono (with switch-selected *High* and *Low* level sensitivity), Mic. (with *L* and *R* mike inputs on the front panel), Extra (auxiliary), and Tape. More than enough outputs are provided. The main-liners are: front panel stereo phone jack, main stereo speakers, remote stereo speakers, mono remote with stereo main speakers (which can be used as a center channel fill), and tape recorder. As extras there are auxiliary high-level outputs which can be used to drive remote power amplifiers or additional tape recorders if you want the LR-88's tone and compensation controls to affect the tape recorder feed. A switched

and an unswitched AC outlet are provided.


Front panel controls include: *Input*, *Balance*, dual concentric *Bass*, dual concentric *Treble*, and *Loudness*. Front panel switches include: *Volume Comp.* (ensation) on-off, *Tape* monitor, stereo-mono *Mode* (for complete amplifier), *Noise Filter*, *FM Muting*, *Remote Speakers* on-off, and *Main Speakers* on-off. A switch on the back panel provides for remote speakers only and mono/stereo selection.

Extra features include both a Signal Strength and a Center Tuning meter, an FM stereo light and FM control by the amplifier mono-stereo mode switch. When the switch is set to mono both the amplifier and the FM are switched to mono operation. The FM receives stereo (automatically) only when the Mode switch is set to stereo.

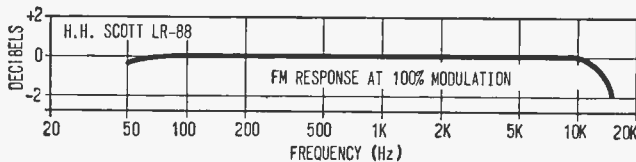Circuit design is up-to-date and has all the user-desired elements hi-fi buffs want. The front end input is FET (field-effect transistor) for prevention of strong signal overload. The IF strip is all IC (integrated circuits). Four IF stages are used for FM, with two




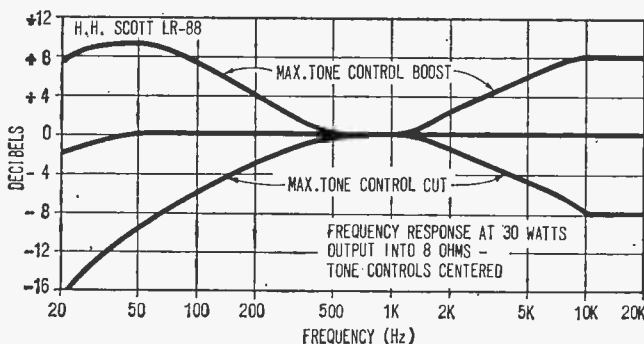Flat as a board—that's what can be said for LR-88's response at 100% modulation. ± 1 dB performance is considered excellent.



With tone controls centered, amplifier section of LR-88 can knock out solid 30 watts with less than 0.5% THD. That's great when you consider that both channels are driven simultaneously, putting maximum drain on unit's power supply. Tone controls offer modest boost and cut—enough for two equally matched speaker systems.

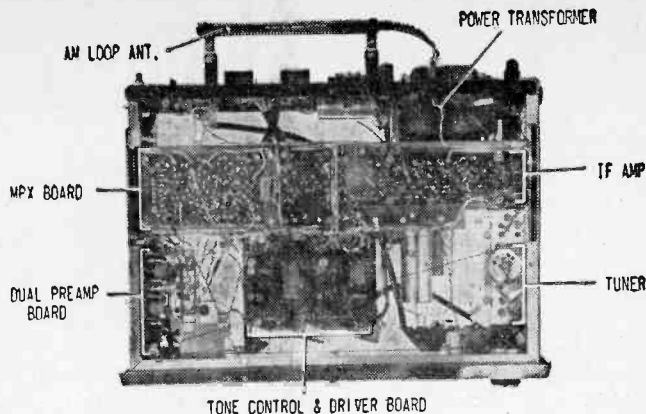Open-frame construction of LR-88 provides ultimate in heat dissipation. IF and MX boards are almost fully shielded by cross-bar, and virtually every circuit is separate module. Notice that wiring harness is far from usual "rat's nest" frequently found in kits that are not carefully engineered.



serving double purpose for AM, too! All circuits are modular—each circuit from IF amplifier to AF output to FM muting has its own individual circuit board.

The chassis itself serves as a hollow frame for the critical circuits which also provide extensive inter-circuit shielding. The arrangement also provides more ventilation than will ever be needed by solid-state circuitry. We would guess that the LR-88 will never go out of alignment or drift due to component value changes caused by heat.

Building the Kit. While the LR-88 is jam-packed with parts, most of the boring and critical wiring and assembly was done at the factory. Essentially, the kit builder assembles the frame, power supply and miscellaneous hardware. Wiring involves only the power supply, jacks and switches and PC board interconnections.

The pictorials are excellent, almost full scale and fragmented so the user always works and "reads" a small independent section at a time. All pictorial wiring is shown in exact matching colors to the actual wires. Another feature is that all wires from a harness are different; no two are alike. When similar circuit wires use identical color coding (for ease of troubleshooting) the two leads will be markedly different physically:


one will be thin; the other will be thick.

Finally the kit is supplied with a large selection of cable ties. When the wiring is tied down after completion of the kit, the LR-88 in no way looks home-brewed. In fact, it's more akin to the appearance of laboratory-grade equipment, factory-made.

Performance. As with all Scott high-fidelity equipment, the specifications are limited to the audio or broadcast range. Scott does not go in for measurements meaningful only to dogs and birds. As example, the amplifier response specification is from 20 to 20,000 Hz, and the FM response is from 50 to 15,000 Hz (the limits of the FCC FM proof-of-performance measurements for FM stations). To keep in the same spirit, our measurements were made within the range of Scott's specifications.

Our LR-88's IHF sensitivity checked out at 1.5 μ V, much better than Scott's rating of 2.5 μ V. Full noise suppression (optimum signal to noise ratio) of 65 dB was obtained with a 20 μ V input (*exactly on specs*). Mono THD at 100% modulation of the FM carrier was 0.58%, stereo THD measured 0.78% (*both extremely good*). The FM frequency response was within the ± 2 dB specification from 50 to 15,000 Hz.


(Continued on page 103)

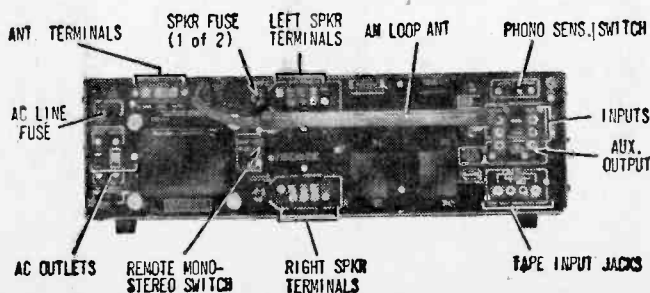

Back of LR-88 is designed to permit easy and unerring connection of (both main and remote) and auxiliary equipment. Unique remote speaker monostereo switch permits simultaneous/mono operation of remote speakers while main speakers are fed stereo programming. This feature permits remote speakers to be used as center channel fill to kill ping-pong effect.

Unlocking the Secrets of the Mysterious

MV

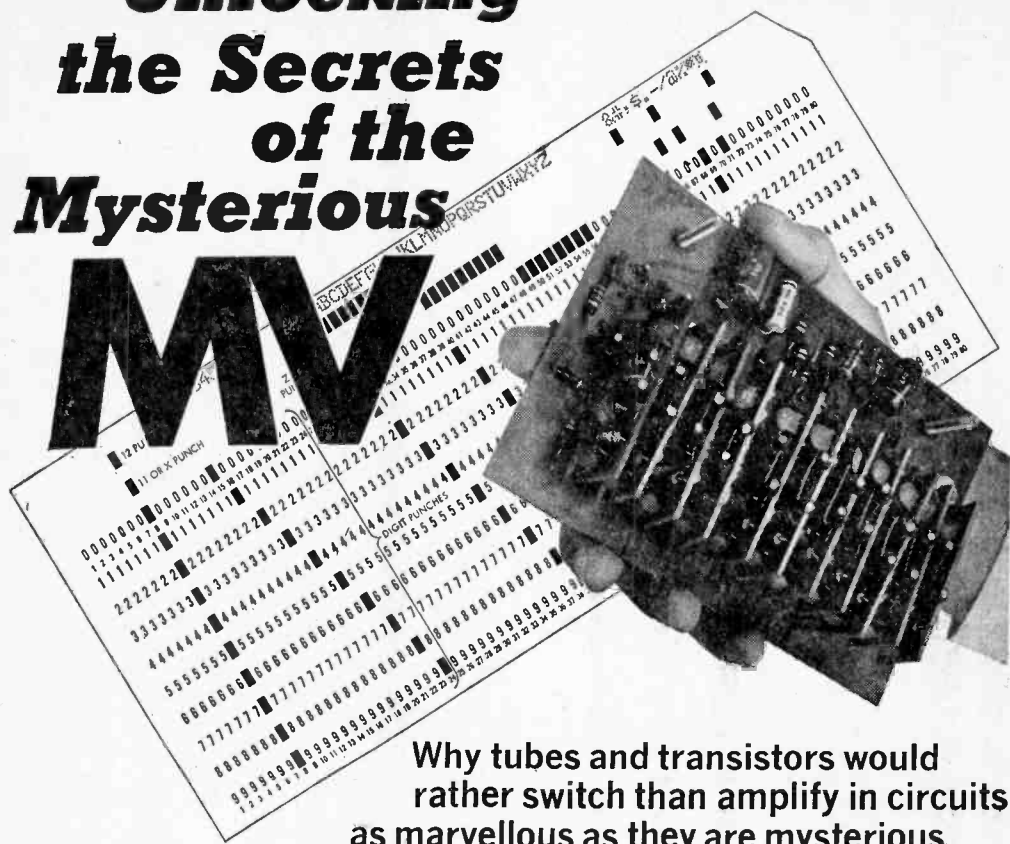

Why tubes and transistors would rather switch than amplify in circuits as marvellous as they are mysterious

By Jim Kyle, K5JKX

Televisi**o**n couldn't get along without them. Neither could radar or digital computers. Electronic organs and pianos are packed with them. The mysterious multivibrator, the man-made device that can change its mind faster than a woman, appears in nearly every major electronic device—but few electronics hobbyists really know how it works.

According to one authority, a multivibrator (MV for short) is "a relaxation type of oscillator consisting essentially of a resistance-coupled amplifier in which part of the output is fed back to the input circuit." Even if the double-talk doesn't throw you astray, there's only one thing wrong with that explanation—the MV isn't an amplifier!


In fact, other authorities acknowledge this when they admit that exact analysis of multivibrator action by use of the standard

amplifier formulas is well-high impossible.

Sound like a formidable circuit? Relax—it's actually not difficult at all, when you look at it from the right point of view. And once you understand the mysterious MV, you can undoubtedly find dozens of ways to use it in your own circuits and projects, for it's one of the most applied circuits around.

What It Isn't, and What It Is! Granted, the typical multivibrator circuit (see Fig. 1) looks for all the world like a two-stage RC amplifier with the output returned to the input. This resemblance led a whole generation of engineers astray, because when the MV first made its appearance nobody expected a vacuum tube to do anything but amplify.

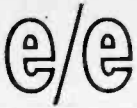But the MV isn't an amplifier at all. The tubes, transistors, or other active elements (what others are there? Stick around!)



MYSTERIOUS MV

aren't acting as amplifiers in this circuit. Instead of amplifying, they're acting as electrically-controlled switches. Relays, if you will. In fact, relays themselves can be used as active elements in a MV and the theory becomes much easier to analyze when this is done.

What makes the difference between "amplifier" and "relay" is simply the "operating point" of the tube or transistor. Fig. 2 shows a typical set of characteristic curves for a triode tube; when this tube is amplifying, the resistance values in the circuit (which control grid bias and plate voltage swing) are chosen so that in the absence of a signal, the tube operates at point "O".

When used as a switch, however, the load resistance, grid bias, and input signal levels are all changed; the tube then operates at one of two points, "P" and "Q". When the input signal is present, the tube operates at "P", and when the input is absent, the tube operates at "Q". Now mind your "P"s and "Q"s.

Other than Tubes. Transistors, incidentally, are superior to tubes in MV circuits provided that they are able to handle the voltages involved. The collector of an "off" transistor (point Q) is usually within a few tenths of a volt of the supply voltage level, and when the transistor turns "on" (point P) this voltage drops to well under 1/10 volt. With a tube, on the other hand, the "off" voltage may be appreciably lower than the supply voltage, while the "on" voltage is seldom lower than 15 to 25 volts.

At slow operating speeds, relays are superior to transistors for the same reasons; they are better switches. Relays, however, can only operate a few times each second. Transistors can operate reliably a million times a second, and tubes can go up to several million times a second if need be.

The Relay MV. If we substitute a pair of s.p.d.t. relays for the two triodes shown in Fig. 1, the circuit looks like Fig. 3—and the action of this MV becomes much easier to analyze.

Until power is applied, both relays are de-energized; this is the condition in which the circuit is drawn. When power is applied, both capacitors begin to charge. C1 charges


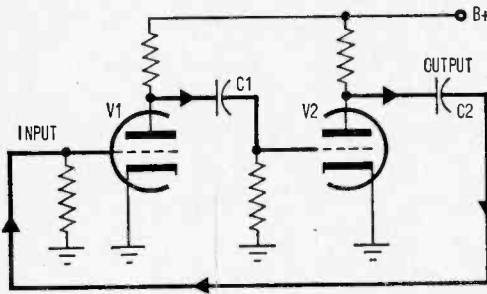


Fig. 1. Typical multivibrator circuit resembles a resistance-coupled amplifier. Circuit actually is a pair of switches which alternate from "on" to "off" and back again, timed by charging current of the two capacitors, C1 and C2. Heavy lines and arrows indicate direction of signal flow.

Fig. 2. Typical vacuum-tube triode characteristic curves. Load line connecting 250-volt point on horizontal scale and 20 mA point on vertical scale represents 12,500-ohm load resistor. Triode normally operates at O and swings short distances either side of this point with signal. When switching as in an MV circuit, however, operating points are P (on) and Q (off). Transition from P to Q or back occurs in fractions of a millisecond.

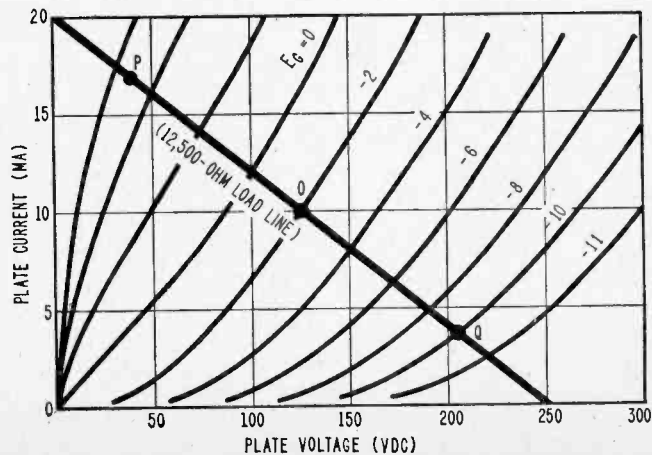

through the upper contact of K1, while C2 charges through the corresponding contact of K2. Current will flow through the coils of K1 and K2.

One of the two relays will operate at least a little bit faster than the other as the charging currents of the capacitors flow through the coils. The first relay to energize (let's assume that K1 pulls in first) interrupts the power to capacitor C1. This disconnects power from K2's coil. So long as C2 is charging, current will flow through K1, holding the relay in the energized state.

When C2 is fully charged, the charging current stops. No more current is flowing through the coil of K1, so this relay drops out or deenergizes. When K1 drops out, it re-connects C1 to the power source. C1 begins charging, which draws current through the coil of K2 and thus energizes K2. When K2 energizes, C2 is disconnected from its power source and begins to discharge through the short circuit connected across it by the bottom contact of relay K2.

When C1 completes its charging, current flow through the coil of K2 stops, which permits K2 to drop out. By this time C2 has discharged, and as soon as K2 drops out C2 begins to recharge. This action draws current through the coil of K1 and starts the cycle all over again. It will continue so long as power is applied; first one relay, then the other, will pull in.

Now Do It with Tubes. In the tube circuit, Fig. 1, the action is almost identical. When power is first applied, both capacitors begin to charge through the plate and grid resistors. This action reduces plate voltage of both tubes, and drives both grids in the negative direction. One of the two tubes, as well, will draw slightly more current than

the other; plate voltage of this tube will drop more rapidly, which drives the grid of the *other* tube more negative because of charging current through the coupling capacitors. Within a few fractions of a microsecond one tube is fully "on" and the other is fully "off." Current flow continues through the capacitor from "off" plate to "on" grid, but not through the other capacitor. This current flow makes the "off" grid less negative, tending to turn it "on." The resulting decrease in plate voltage at the "off" plate causes a reverse current flow through its capacitor which turns the "on" grid "off." This, in turn, helps the original current flow which is turning the "off" grid "on." The two processes together flip the circuit over so that the tube originally "off" turns "on," and vice versa. As soon as the transition is complete, however, both processes begin again—and continue so long as power is applied.

Thus, whether tubes, transistors, or relays are used as active elements, the MV behaves in the same manner. The secret to its action is the operation of one switch as a result of a second switch's operation, and operation of the second as a result of the first. *Any* circuit which fits this description is a MV, regardless of its active elements or its timing devices.

Types of Multivibrators. Actually, multivibrators can be (and usually are) divided into *three* distinct classes. The only type we've looked at so far is the "astable" multivibrator. It gets that name because it has *no* stable condition. No matter what point of its operating cycle it may be in at any instant, it's merely on its way to some place else. There is no stationary resting place. Other names for the astable MV are "relaxation oscillator" (although not all relaxation oscillators are MVs), "free-running MV," "synchronized divider," and "frequency divider."

The other two classes each have at least one stable state. In fact, that's the distinction between them. One, the "monostable" multivibrator, has only *one* stable state. The other, the "bistable" multivibrator, has *two* stable states.

The monostable MV is frequently called a "one-shot" multivibrator. It normally stays in its stable state. When triggered, it switches to the unstable state, and after a period of time determined by the design, switches itself back to the stable state. It thus produces a single output pulse.

The bistable multivibrator is sometimes

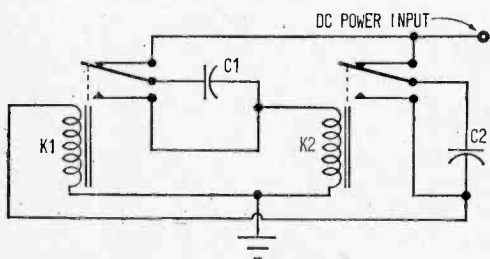


Fig. 3. This circuit is equivalent to that shown in Fig. 1; here vacuum tubes are replaced by relays as the switching devices. Leads connected from the bottom contacts of K1 and K2 to the capacitors permit the capacitors to discharge when power is removed by switching action. See text for details of circuit operation.

e/e MYSTERIOUS MV

known as an "Eccles-Jordan" multivibrator, for the persons who first developed it. The most common name in the U.S. for this circuit, however, is "flip-flop," and under this name the circuit is widely known in the computer industry.

Before we examine the means by which the three types of MVs operate, and the method for converting one type into another by a simple change of one or two components, let's work out a generalized approach so that the discussions will apply to all kinds of MVs, rather than being limited to relay versions, or vacuum-tube versions, or transistor circuits.

That Sounds Logical. We've already seen how any type of electrically-actuated switch can be used as the active element in a MV. Besides vacuum tubes, transistors, and relays, we can use SCRs or even neon glow lamps for the switches. Since the active element can be any of these devices without affecting basic operating theory (although speed, power, and many operating characteristics *will* be affected), let's choose a single symbol to represent *any* kind of active element, and use it in all discussions.

The triangle symbol shown in Fig. 4A is used in industrial electronics to represent both amplifiers and switching circuits; it is used in the computer industry to indicate "buffer" or "driver" circuits. Adding the small bubble at the point of the triangle makes it an "inverter," with an output sig-

nal always the opposite of the input. If input voltage is high, output voltage is low, and vice versa. This is the characteristic needed for our active elements, so let's use this symbol. Figs. 4B, C and D also show some typical vacuum-tube, transistor and relay circuits which may be represented by the symbol in A, and used in any of our circuits.

The MV operates in real time; most study of electronics circuits assume that time is standing still while we look at the circuit, but the whole basis of the MV is the way in which signals change as time passes. For this reason, each of our MV generalized schematics must contain a "timing diagram" which shows how signals change with time. Fig. 5 is a typical timing diagram for the charging of a capacitor.

The Astable Multivibrator. Fig. 6 shows both the generalized circuit and the timing diagram for the astable multivibrator; this is the type of multivibrator which we have examined in Figs. 1 and 3, so this description will be abbreviated.

Let's start our examination at the instant that point 1, the input to the left-hand active device, reaches its "low" point and permits the output of this device to swing high. This is shown as line 2 on the timing diagram. When point 2 swings high, a high charging current flows through the timing capacitor between points 2 and 3, but as the capacitor charges the current flow drops off to zero. This current develops a voltage across the resistor from point 3 to ground, producing the voltage level shown as line 3. So long as this voltage is above its "low" point, the output of the second device (point 4) is held low, but when point 3 reaches its "low" level, the voltage at point 4 swings high.

When point 4 swings high, the same things happen between points 4 and 1 that we have just examined between points 2 and 3. Point 2 is now held low until the voltage at point 1 again reaches its low point. When it does, one full

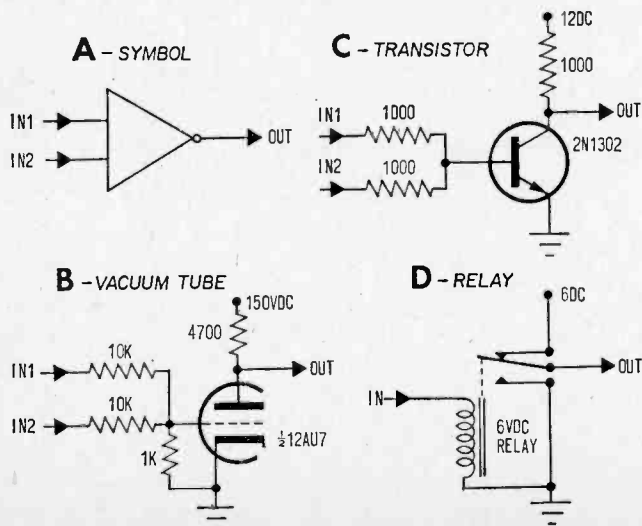


Fig. 4. Any of circuits in B, C, or D can be used to replace the generalized switching-device symbol shown in A. In the following figures only the generalized symbol is used. Be sure you understand what it signifies before you proceed from this point.

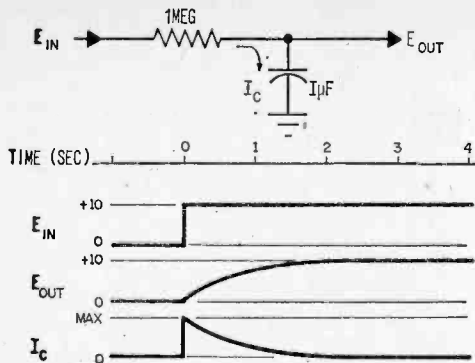


Fig. 5. Here is a typical MY timing diagram which illustrates the voltage and current relationships during the charging of a capacitor from the time voltage is first applied until the capacitor reaches nearly full charge. The timing diagrams in Fig. 6 through 12 all make use of the curves shown here, but for simplicity the true curve is replaced by a straight line.

cycle has been completed and the process begins again. It continues so long as power is applied to the circuit.

If vacuum tubes or transistors are used as the active elements, the resistors shown in the general circuit may be omitted since they already exist in the active-element detail circuit (Fig. 4).

Fig. 6 shows that the length of time during which point 4 is low depends upon the time it takes the capacitor between 2 and 3 to charge, while the length of time that point 2 is low is determined by the charge time of the capacitor between points 1 and 4. Although the timing diagram indicates that the two times are equal, they need not necessarily be the same. If a small capacitor is used at one point and a large one at the other, a "lop-sided" output can easily be obtained from this circuit.

Actual timing depends not only upon capacitor charging time, but upon the voltage levels at which the active devices switch from low to high output. The capacitor charge time itself depends upon three things: the size of the capacitor in microfarads (the larger, the slower), the charging voltage available (the higher, the faster), and the resistance between capacitor and voltage source (the plate or collector load resistance, in series with the base or grid resistor; the less resistance, the faster the charge). Exact times for any specific circuit are normally determined by experimenting; the starting values are determined by RC time constant of total resistance times voltage.

The resulting time is in seconds if resistance is in megohms and capacitance in microfarads.

The Monostable Multivibrator. The characteristic which distinguishes the monostable multivibrator is that it has *one* stable, and *one* unstable, state. The astable, on the other hand, has *two* states, both of which are *unstable*. Fig. 7 shows a generalized circuit and a timing diagram for the monostable variety.

Comparing Fig. 7 to Fig. 6 shows that the only difference between the general *astable* circuit and the general *monostable* circuit is the removal of the coupling capacitor between points 2 and 3 (Fig. 6) and replacing it by a short circuit.

The engineers describe this difference by saying that the astable circuit has only AC coupling, while the monostable has one AC coupling and one DC coupling.

The timing diagrams show how this one-component change makes a major difference in circuit operation. Let's assume that the circuit has been left alone for an indefinite time, with power applied. The lone coupling capacitor has long since been fully charged and therefore the voltage at point 2 is zero. Since point 1 is also zero, the left-hand active device has no high input. This makes its output, point 3, high. The high level at point 3 holds point 4 low. Point 4 being low has removed all voltage from the capacitor and so any charge it may have had has been drained off.

When we apply a brief pulse to point 1, the picture changes. When the pulse hits point 1, it causes point 3 to go to low level

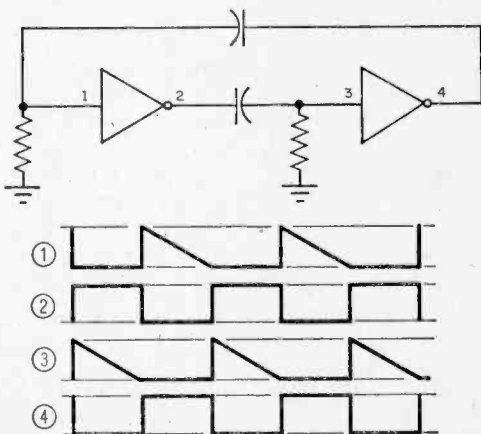


Fig. 6. Generalized schematic and timing diagrams of the astable multivibrator.

E/E MYSTERIOUS MV

—at least for the duration of the pulse. Point 3 going to low level brings point 4 to high level, and starts the capacitor charging current flowing. This charging current flows through the resistor from point 2 to ground, producing a high level at point 2 for the charging time of the capacitor. This high level at point 2 holds point 3 low, even after the original “trigger” pulse is gone, until the capacitor is fully charged.

When the capacitor reaches full charge, current flow through the resistor stops and point 2 is again low. At this time, since the trigger pulse is long gone, point 3 returns to its high level. Point 3 going high forces point 4 low, and the capacitor discharges. The resistor from point 2 to ground is not in the discharge circuit, so the capacitor discharges rapidly. As soon as the capacitor is discharged, the circuit is ready to accept another trigger. Until the next trigger arrives, however, point 4 will remain low and point 3 high.

The major characteristic of the monostable MV, then, is that it produces a single output pulse when it is triggered. The duration of this output pulse is determined by the design of the MV, and is not affected by the nature of the trigger pulse.

The Bistable Multivibrator. The bistable MV is distinguished from its cousins by having *two* stable states, compared to *one* for the monostable and *none* for the astable.

If you expect to find that the other coupling capacitor is taken out to make a bistable out of a monostable, you're ready to go to the head of the class—for that's exactly how it's done. Fig. 8 shows the general circuit and timing diagram.

With no timing capacitors, this circuit does no timing at all. It serves a different function—it is a “memory” circuit which remembers which of its two inputs was last triggered, and will hold that information so long as power is applied. Hence, its name flip-flop.

The timing diagram in Fig. 8 shows how the bistable MV remembers. Let's assume that the right-hand active element is a fraction of a microsecond faster in its operation than is the other. Then when power was applied, this element operated first and brought

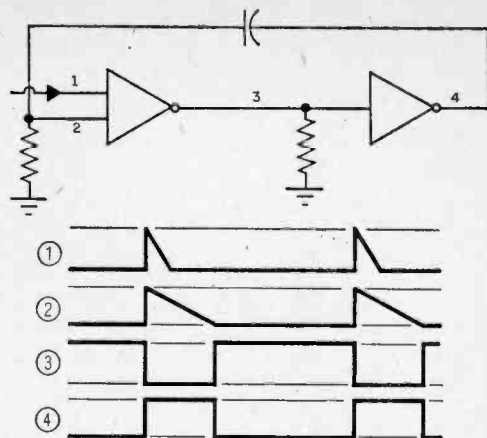


Fig. 7. Generalized schematic and timing diagrams of the monostable multivibrator. Output pulse width is determined by capacitor value.

point 4 to a low level. With points 1 and 4 both low, point 2 had to be high. Point 2 being high kept point 4 low, and this stable state was retained until a value was applied to point 1.

The pulse at point 1 brought point 2 low at least briefly, and when point 2 went low (since point 3 was also low) point 4 went high. The time scale is exaggerated in the timing diagram to emphasize this falling-domino sequence of happenings; it actually happens as fast as the active elements can operate, and with normal transistors is completely accomplished within a few hundredths of a microsecond.

Point 4 being high keeps point 2 low, and point 2 being low holds point 4 high. This

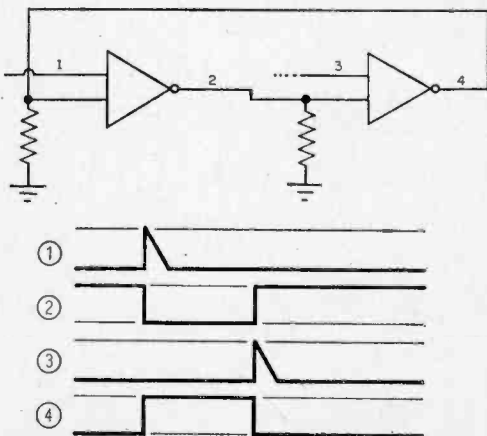


Fig. 8. Generalized schematic and timing diagrams of the bistable multivibrator. This is the basic “flip-flop” so widely used in digital equipment.

state is also stable, and will remain until a pulse comes in at point 3. Additional pulses at point 1 will have no effect.

An incoming pulse at point 3 makes point 4 go low, and by the same sequence point 2 comes high and holds point 4 low.

Points 2 and 4, therefore, "remember" which input received the last pulse. If point 2 is high, the last pulse came in at point 3; if point 4 is high, the last pulse came in at point 1.

Remember that we simply assumed that point 4 was initially low. When such a circuit is actually being used, the designer cannot make such an assumption. He must add some other circuit to send an "initializing" pulse to whichever input he wants; if he does not, he will not know whether the output indication is the result of actual inputs, or whether it is the result of one element switching before the other at the time power was turned on.

Some Multivibrator Applications. As we have seen in our examination of the different types of MVs, the circuits have many potential uses. Here are just a few to stimulate your imagination.

A monostable MV's uniform output pulse can be the heart of an accurate tachometer, by using a signal from the engine ignition to trigger the MV and simply applying the MV pulse output to an indicating meter. The faster the engine goes, the more pulses

per second will be generated, and the more the meter will deflect.

The astable MV's rectangular-wave output is rich in harmonics; if the MV operates at audio frequency, its harmonics can be heard throughout the radio spectrum. An astable MV is an excellent signal source for troubleshooting any radio receiver.

The bistable MV's memory characteristic plus a pair of reed switches can provide a "photo-finish" device for slot-car racing. As each car passes above its reed switch it will provide a pulse to the multi; the multi will then show which car crossed the line *last*.

Photo fans and others who need accurate timers can use the astable multi to generate a train of accurately timed pulses at a low frequency, and then use these pulses to charge a capacitor. This permits long time intervals to be measured by relatively small timing capacitors.

Combining the astable, monostable, and bistable multis all into a single unit can provide the enterprising ham with an electronic keyer of the "TO" type; the astable multi provides the basic speed control, two monostables (one producing a pulse three times as long as the other) produce dits and dahs, and the bistable "remembers" whether dits or dahs were last selected by the operator.

From here, you're on your own. Turn your thinking loose, and have fun with multivibrators. ■



Audible Iron Finder


When you hear the high-pitched warning, you're almost on top of your objective. Who's you? Well, you *could* be a police officer checking for weapons among persons entering a courtroom. Or you could be a highway surveyor hoping to uncover stakes buried three years ago. Or you could be a weekend treasure hunter looking for an elusive prize stashed in a steel box. In short, you're looking for an object that, in one form or another, has an iron content. And you're using a new magnetic measuring device that detects objects up to 1 ft. away.

Developed by Schonstedt Instrument Co. of Reston, Va., the GB-1A magnetic locator is a single, self-contained unit that, at 3 lb. weighs less than the search head alone on conventional detectors. Externally, it is nothing more than a headset connected to the 42-in.-long probe. The operator points or waves the probe at a likely target, and the headset tells him whether he's found anything.

The detector sells for just \$595.00. Think you can find \$596.00 worth of treasure for a cool \$1.00 profit?—*Joe Gronk* ■

Yours FREE

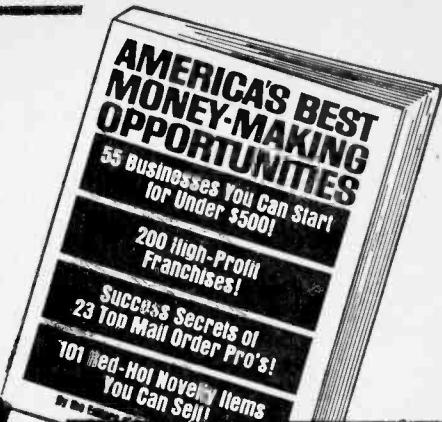this valuable guide to
MONEY-MAKING OPPORTUNITIES
with your NO RISK TRIAL
subscription to the new
INCOME OPPORTUNITIES
Newsletter



**NOT FOR SALE at any price...
 but you can get a copy FREE
 by returning the coupon below.**

HUNDREDS OF IDEAS that can mean big money for you assembled by **INCOME OPPORTUNITIES** staff in a special report can be yours **FREE** when you mail the coupon below accepting a **NO RISK** Charter subscription to the new **INCOME OPPORTUNITIES Newsletter**—the new confidential reporting service that brings you exclusive reports of new business breakthroughs **FAR IN ADVANCE** of any other source.

YOUR FREE SUCCESS GUIDE contains these powerful profit-makers:

- Success secrets of millionaire mail order professionals!
- 200 high-income, low investment opportunities!
- 55 Businesses you can start right now for under \$500 investment!
- 101 Red-hot novelty items you can sell for phenomenal commissions!

EACH MONTH this exclusive confidential newsletter reporting service will bring you exclusive advance news of opportunities in every area...always with the names and addresses of the sources so that you can take full advantage of money making opportunities and can go into action immediately long before anyone else has even heard of them.

OUR NATIONWIDE STAFF of reporters and the editors of **INCOME OPPORTUNITIES**, the world's leading magazine in this field, are in constant touch with **EXCLUSIVE** sources of inside information about unusual opportunities of increasing your income...and this information is rushed to subscribers in fast-reading newsletter format...together with special in-depth reports of information you can get nowhere else.

YOU TAKE NO RISK WHEN YOU SUBSCRIBE SINCE YOU MUST BE 100% SATISFIED

To get your **FREE** exclusive report on **AMERICA'S BEST MONEY-MAKING OPPORTUNITIES**, all you need do is mail the post card facing this ad or the coupon below to enter your **NO RISK** trial subscription to the new **INCOME OPPORTUNITIES Newsletter**. The cost is less than 5¢ a day...and a single idea you get from it can be worth many times the cost of a year's subscription.

THESE SPECIAL REPORTS are included with your subscription as an **EXTRA VALUABLE BONUS**

22 MAIL ORDER FIRMS THAT WILL PUT YOU IN BUSINESS!
 Top-notch, reputable firms...each with a profit-producing mail order program. Choose your own hours...work full- or part-time.

33 SELECT FRANCHISES FOR UNDER \$5,000!
 Choice franchises selected to return maximum profit for an investment within your means. Restaurants, automotive, stores, and many, many more!

25 HOME-BASED, SPARE-TIME MONEYMAKERS
 For anyone who would want additional income—laminating specialty mail order, secretarial services. Full details on how to get customers and how to price your product for profit!

DIRECT SELLING DIRECTORY!
 Leaders in the direct selling field—Sajadmaster, Tupperware, Stanley, and many others help put you on the path to financial independence selling nationally known products...and earning commissions of up to \$1,000 monthly!

20 FASTEST GROWING RETAIL BUSINESSES!
 Survey and report of independent businesses which are currently booming—coin-op car wash, beauty/wig salons, poolside grooming parlors...economic indicators to help you make the wisest choice for a profitable business!

AND REMEMBER...THIS SUCCESS GUIDE IS NOT FOR SALE, anywhere else, AT ANY PRICE!

TO GET YOUR FREE report on **AMERICA'S BEST MONEY-MAKING OPPORTUNITIES**, mail the coupon below to enter a **NO RISK** Charter subscription to the new **INCOME OPPORTUNITIES Newsletter**—the confidential report that brings you exclusive advance news of money-making opportunities month after month.

HUNDREDS OF EXCLUSIVE IDEAS YOU CAN USE TO MAKE MORE MONEY

THE REASON we want to send you this valuable report on **AMERICA'S BEST MONEY-MAKING OPPORTUNITIES** as a **FREE** gift with your **NO RISK** subscription to **INCOME OPPORTUNITIES Newsletter** is we know that once you become a reader you will never want to be without it.

22 MONEY-MAKING HOBBIES!
 Hobbies are not only for fun, but can be profitable as well! Here's how to turn your coin/stamp collecting, your tropical fish or even your own art and craft items into a substantial secondary source of income!

HERE'S THE EXCLUSIVE VALUABLE INFORMATION

You'll find in your **FREE** copy of **AMERICA'S BEST MONEY-MAKING OPPORTUNITIES**:

55 BUSINESSES YOU CAN START FOR UNDER \$500!

Proven profit makers which offer independence and financial security...many can be started on a part time basis...with addresses for obtaining detailed information.

200 HIGH-PROFIT FRANCHISES!

Selected franchise profit-making opportunities with initial investment of under \$5,000...covers all major areas such as: services...products...schools...sports and recreation...stores...vending machines...cosmetics...health aids and much more.

SUCCESS SECRETS OF 23 TOP MAIL ORDER PROS

The inside success stories behind the big mail order money makers...and full details you can use to get into the big mail order field.

101 RED HOT NOVELTIES FOR SALESMEN
 How to get your share of the multi-billion dollar advertising specialties industry which offers unlimited opportunities to salesman.

SEND NO MONEY NOW to get your **FREE** Money-Making Opportunities Report.

Enter my Charter **NO-RISK** subscription to the new **INCOME OPPORTUNITIES Newsletter** including 6 special reports listed above and send me **FREE** the exclusive report: **AMERICA'S BEST MONEY-MAKING OPPORTUNITIES**. The cost is \$1.50 per month payable annually or semi-annually.

Bill me Annual Basis Semi-Annual Basis

I understand I may cancel my subscription at any time and will receive a **FULL REFUND** with no questions asked for all issues still due me at that time. The cost of my subscription is **TAX DEDUCTIBLE** as a business expense.

NAME

(Please PRINT — it prevents errors)

STREET ADDRESS

CITY

STATE

ZIP CODE

CHECK HERE TO GET AN EXTRA MONTHS' SERVICE FREE.

Enclose your payment of \$18.00 now and save us bookkeeping costs and we'll add an extra month to your subscription. **SAME NO RISK GUARANTEE.** You may cancel your subscription at any time for a **FULL PROMPT REFUND** for all undelivered issues.

Mail to:
INCOME OPPORTUNITIES Newsletter
 229 Park Avenue South, New York, N.Y. 10003

EE-69

H. H. Scott LR-88 Receiver

Continued from page 94

AM performance, typical of most AM-FM receivers, is best described as good.

It should be noted that the FM and AM alignment was "as delivered by the factory" and "user trimmed" as per the instruction manual. We could not see how an instrument alignment in our lab could offer any significant improvement. Our hats are off to Scott.

By a novel adaptation to the signal strength meter, and built-in switching circuits, the LR-88 uses the signal strength meter both as a voltmeter for circuit check-out and as an alignment meter. We do not suggest any builder attempt an instrument alignment beyond the minor trimming adjustments specified for the tuning meter.

The Curves. The amplifier performance is illustrated in the charts. The amplifier frequency response is at a full 30 watts RMS sustained output—both channels driven—with the THD well below 0.5% at 20 to

20,000 Hz (*better than specs*). Midband power output for less than 0.5% THD was 30 watts into 8 ohms, 35 watts into 4 ohms, and 25 watts into 16 ohms.

As shown, the tone control range is modest, with a maximum of 9 dB boost at 40 Hz. The *Volume Comp.* switch provides primarily a bass boost (with the volume control $\frac{1}{4}$ open), which almost exactly matches the normal maximum bass boost characteristic.

The *Noise Filter* is a hi-cut design—being only 6 dB down at 7 kHz provides enough filtering to "clean up" a noisy disc or weak FM signal without destroying the music.

Summing Up. As you have most likely surmised, we are impressed by the LR-88. Though complex, the kit is well thought out and relatively trouble-free in assembly, check-out and adjustment. The instruction/assembly manual is superb. The LR-88's sound quality and conveniences are excellent.

The LR-88, with metal enclosure, is priced at \$299.95. An optional wood grain cabinet is available at \$26.95. For additional information write to H. H. Scott, Dept. D, 111 Powder Mill Rd., Maynard, Mass. 01754.

Newscon

Continued from page 15

computer-simulated landings of the Apollo Lunar Module. To date, five sites meeting both vehicle and orbital constraints have been selected and forwarded to the Apollo site selection board for final selection.


In selecting candidate landing areas, the emphasis is on making sure there is a clear approach path and terrain is free of sharp slopes and large rocks, craters, and hills that may be misinterpreted by the Lunar Module's landing radar.



Moon craters are counted and measured on a high resolution Orbiter photograph using a 10-power hand magnifier by Raytheon Company specialist in the field of photo-interpretation.

Called "footprints," the elliptically-shaped, three-by-five mile areas having topographic features suitable for a Lunar landing are then used in a series of computer-simulated landings.

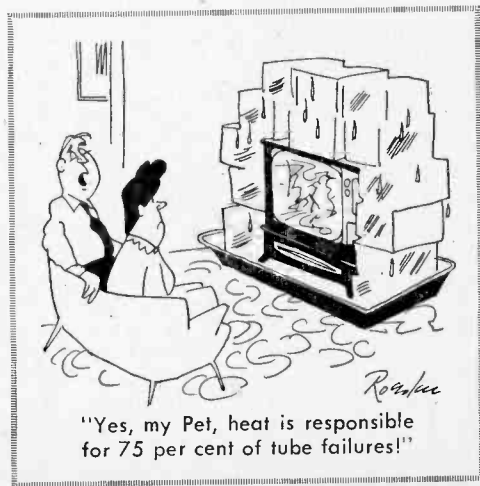Working on high and medium resolution photographs returned by Lunar Orbiters 1 and 2, the Raytheon specialists perform a variety of operations varying from the simple counting of craters to the precise measurement of the distance between points on the moon in the spatial triangulation process. You can be sure Apollo 8 photos will be studied, too!



"Yes, my Pet, heat is responsible for 75 per cent of tube failures!"

DX Central

Continued from page 10

tend to have a mobile station hidden in Spain. We'll put our money on a South American location, though. . . . 15,205 kHz.—All India Radio's General Overseas Service is noted in English on this new frequency from 1000 to 1100 GMT. (Credits: A. R. Niblack, Indiana; Frank Peters, Illinois; Del Hirst, Texas; Bill Berghammer, N. Y.; Craig Koukol, Ill.; National Radio Club; North American SW Association.)

● POSTSCRIPT FROM PRAGUE

Lately, SWLs have reported receiving verifications from Radio Prague for reception of Czech clandestine broadcasts during last August's Soviet invasion. These QSLs, understandably, are vague about the operations, usually stating simply that the broadcasts were aired from "various locations" in the country.

Some of the secret stations set up shop in apartments, factory buildings, even in the police headquarters. They used civil defense and government standby facilities, Army equipment, and transmitters belonging to the huge Tesla electronics firm at Prague-Hloubetin. Elsewhere, stations at the Ceska Lodenice shipyard and at the Ceskomoravska-Kilben-Danek machine works were used, too!

Only recently have some of the details filtered out of Prague. One of the most fascinating tales concerns clandestine Radio Czechoslovakia I.

On invasion morning, August 21, Russian infantrymen, carrying "burp" guns, burst into the downtown Radio Prague studios on Vinohradska St., and closed down the station—so they thought.

Though the Red troops guarded the building's lower floors, apparently they were unaware of a separate complex of auxiliary studios on the third floor. From these "blacked out" rooms, just over the heads of the Russians, members of the Czech broadcasting staff worked secretly. A few direct phone lines, which bypassed the monitored switchboard, kept them in contact with the rest of the nation. Messengers slipped in and out of the building through a side door, on Balbinova St. For eight hours they fed programs to the still free transmitters at Podebrady, 30 miles east of Prague, and at Velke Kostotal in Slovakia.

By the time the Ruskies got wise, the phantom broadcasters had moved on to a pair of sub-studios of the Czech broadcasting system in the eastern suburbs of Karlin and Vinohrady. The Karlin studio, used normally for recording concerts and plays, was in a big, private residence. Together with the feature program studio in Vinohrady, it escaped Russian notice.

On August 23, a tank and a jeep pulled up outside the Karlin building. But, tipped off by friendly Czech police agents, the broadcasters

had escaped again. Soviet officers checked out the studio, found it empty and drove off toward the city's center.

The new location of Radio Czechoslovakia I was the Czech Army barracks on Prague's western fringe. There, for a half day, they kept going with an Army transmitter.

Then, in one of the neatest tricks of the whole Czech crisis, they doubled back on their pursuers and re-occupied the Karlin and Vinohrady suburban studios, which the Russians carelessly had left unguarded.

And there they operated, undisturbed, until the entire underground network voluntarily shut down nearly a week later. ■


Allied SWL Receiver

Continued from page 66

SW segments. It was particularly noticeable on the Citizens Band where the receiver appeared to "split" a channel in half; if two stations were slightly off-frequency, one on the high side and one on the low side of center-channel, it was possible to tune for only one signal cleanly; the second station came through only on the sideband and at a much reduced level.

Summing up. Though priced at \$99.95, the Allied Radio Model A-2515 Communications Receiver offers performance associated with receivers in the \$200 to \$300 price range. Both for general coverage and as a Ham receiver the A-2515 delivers outstanding performance and value. Allied's A-2515 is that kind of "first receiver" that'll grab stage center in your listening slack for many years.

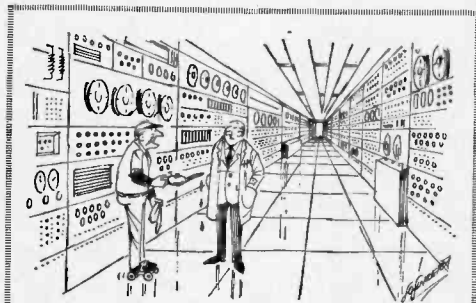An optional matching speaker is available as an accessory. For additional information write to Allied Radio, Dept. 20, 100 N. Western Ave., Chicago, Ill. 60680. ■



"Sorry, Higgins, we have to let you go.
We need somebody faster around here!"

Radio Pirates

Continued from page 64

The Comeback. Then, late last fall, there were a few solid signs of a pirate comeback. Encouraged by a favorable court ruling that clarified the status of the offshore seabed towers, ex-*Radio Essex* owner Roy Bates proclaimed his old tower the independent nation of Sealand. Prince Roy, as he dubs himself, says he intends to reestablish a commercial station there to cover the London area. To scrape up some cash, Prince Roy has even issued his own Sealand postage stamps.

And a Swiss corporation, The Concorde, announced plans to broadcast tri-lingual variety and pop music programs, complete with commercials, for Britain, France and the Low Countries from a ship moored off Belgium.

A temporary office opened recently somewhere in Brussels, says the Belgian press service, Agency Belga. There seems to be real money behind the plans for 50 kilowatt transmitters on long, short and VHF-FM wavelengths.

Also in the news are reports that Ronan O'Rahilly, the flamboyant Irish mastermind behind the *Caroline* organization, has joined forces with the Beatles' new Apple Corp. This may lend credence to stories that a transmitter purchased recently in the U.S. by Beatle Paul McCartney is to be installed on an uninhabited island, owned by John Lennon, off the west coast of Ireland.

O'Rahilly, himself, has announced plans for a pirate TV outlet, *Caroline TV*, which in mid-1969 will transmit 9 to 12 hours daily in color and black-and-white. Targeted will be "telly" viewers in Great Britain and Ireland.

The UHF station will broadcast from a pair of Super Constellation aircraft, already purchased, flying a tight pattern above the Irish Sea. Earlier, airborne television proved technically feasible in U.S. educational TV tests.

To get the *Caroline TV* project off the ground, O'Rahilly will have to skirt the tough Marine Offenses Act, which deep sixed the buccaneer radios by sawing off the plank behind them, making it a criminal offense for Britains to aid or supply the maritime broadcasters, or to advertise over their facilities.

According to the canny Irishman, the law stopped British firms from advertising on pirate radio and foreign companies weren't very interested in doing so.

The American Buck! But, says O'Rahilly, non-British firms are keen to reach a nationwide television audience. He has termed the interest by American advertisers as "fantastic."

Some sources say the semi-autonomous Isle of Man will be used for supplying and refueling the *Caroline TV* aircraft. But O'Rahilly says, "At the moment I do not want to say where our aircraft headquarters are. If the (British) government were to know, it would probably arrange a deal with the country to close us down."

Though pirate ventures are notoriously long on ballyhoo and woefully short on meeting their projected on-the-air dates, there's a fair chance that a new one, *Radio Nordsee*, will be operating by the time you read this.

Owned by Swiss and Lichtenstein businessmen, *Radio Nordsee*, not to be confused with the *Dutch Noordzee*, a tower-based radio and TV combination, circa 1964, was to begin 24-hour-a-day broadcasting in German in 1128 kHz about the first of the year. It was to transmit from the former *Radio Caroline South* vessel, "Mi Amigo," which spent the better part of last year, before the *Nordsee* project was launched, chained to a wharf at Amsterdam's Verschure shipyard. Anchored off Helgoland, its programs were to be beamed at West Germany.

The same business syndicate is trying to swing a commercially-sponsored television station in East Germany to transmit programs over the border to the West. Its prospects for success seem slim.

And so, as the pirate broadcasters prepare to run up the skull and crossbones again, Europe's governments are bracing themselves for another battle. The outcome of this struggle is anybody's guess. ■



Homer Hackleby—Ace Spy

Continued from page 70

machine on your lap, you know. Besides, my electronic knowledge is needed by National Security. I have an appointment for tomorrow morning and probably in a few days I will be relaxing in the perfumed arms of some shapely, enchanting temptress in Algiers or Nice."

The next morning he sat before the desk of J. J. Watkins, the Chief of Security for the New York office of the Association.

"Could you tell me a little of your electronic background, Mr. Hackleberry?" he asked Homer. "Some of your inventions perhaps?"

"The name is Hackleby, sir. Well, I discovered the use of most quartz crystals to provide damped oscillating circuits. I planned to use them in a vibrating, micro-electronic scalp massager to restore the hair on bald-headed men. The device could be fastened inside the hat, you see, and work anywhere—even under water. Swiss engineers stole the idea from me before I could patent it and are using it in waterproof watches."

"A dirty shame," cried Watkins. "Are you working on any electronic projects at present?"

"Yes. I have drawn up blueprints for a color X-ray tube to be used in television cameras," said Homer calmly, as his fertile mind went into high gear. "With my tube, the screen would show all of the internal organs of the performers instead of their faces . . . in full color, of course. A large percent of the viewing audience is getting sick of the same performers each year, only with a few more wrinkles in their faces. Think of the novelty of seeing the digestive juices attacking a delivery of Chop Suey inside the human stomach."

"Well, with such a broad background of electronic experience as that, you're just the man I'm looking for, Hacklebrush," said Watkins as he lit a cigar. "I have a case that is top secret and which may involve the security of our entire nation . . . maybe even of the Milky Way and our entire Galaxy! You are no doubt well informed about the nature of these new *Pulsar* radio waves?"

"Of course. They are the waves coming back from our capsules and sent by the tiny metronomic-electronic instruments fastened on

the wrists of the Astronauts to record their pulse in Space."

"I'm sorry, Hacklebutt," said Watkins as he shook his head. "You're not running in the money this time. The only word you said which was close was 'Space'." He picked up a paper from his desk. "Pulsars are radio waves coming from Space and discovered in 1967 by Cambridge University astronomers. They are now believed to be coming from beyond the Milky Way and our Galaxy. It is believed by many people that they are being sent by some other civilization."

"Oh, *those* Pulsars," said Homer quickly. "They're spelled with an 'a' while the ones I spoke of are spelled with an 'e'. Yes, I have studied them carefully and my theory is that they are being sent by ham shortwave operators from the Planet Pulsa which, ah, has its orbit on the very edge of Space . . . where it drops off into absolute nothingness, in fact. Really out in the woods, you know."

"I don't know about that but it says in this report that their energy output per square inch equals the entire output of the sun or several thousand hydrogen bombs detonating every second. That means that if some little thing went wrong in some way, they might blow us into Kingdom Come."

Homer felt a slight, cold chill pass quickly down his back.

"Our job is to locate a missing Professor Blotchet, an astronomer at the United States National Radio Observatory in Green Bank, West Virginia. He operates the trainable, dish-type radio telescope there . . . largest in the world. Has a diameter of three hundred feet, fifty feet more than the Jodrell Bank telescope in England."

"We have reason to believe Professor Blotchet had discovered a way of storing up these Pulsar things in some kind of a battery. Then he must have stumbled some new discovery for he wired me that he was coming to New York to see me. He checked into the Park View Hotel on Monday and then disappeared. I lost three of my best men since Monday and I'm down to the bottom of the barrel. That's why I'm going to send you out to find him, Hacklebum," said Watkins.

"Yes, sir! The name is Hackleby, sir," said Homer.

"What? Oh, well, it probably won't make much difference by tomorrow. Now get out and get to work."

"Yes, sir," said Homer as he rose, hat in

hand, and walked out of the office.

He went back to his garage-laboratory and dismissed Spencer. Next, he opened a false bottom in a cigar box on his desk and took out several electronic items including a hearing-aid which he inserted in one ear. The other things he put in his coat pocket.

A half-hour later he was walking down a hall in the Park View Hotel toward the Professor's room. He unlocked the door with the pass key the clerk had given him and entered the room. The professor's suit-case was at the foot of the bed and his personal toilet articles in the bath-room. By the telephone, Homer noticed a small notation pad. There was a number scrawled over it.

He picked up the phone, asked for an outside line and then dialed the number. A voice answered, "Hello, Shanghai Bar."

"This is, ah, Professor Hackleby speaking. I am trying to locate a friend of mine by the name of Blotchet, Professor Blotchet. I notice your number here in his hotel room. Is he there now?"

"No, sorry, but I've never heard of any Professor Blotchet."

"Is it most important that I find him. I am a scientist from England . . . the Jordell Bank Radio Telescope. I have discovered vital data that fits in with my friend's research, I must find him."

"Hold the line, please." There was a slight pause. "Hello, yes, your friend is here but very busy and unable to come to the phone. He asks that you come to the Shanghai Bar at once."

"Fine. I'll be there shortly," said Homer as he hung up. He dialed another number and spoke a few words, then hung up and left the room. Outside the hotel he caught a cab for the Shanghai Bar.

The Bar was on Mott street in the Chinese section downtown and after paying his driver Homer walked in and sat on a stool.

"I'm Professor Hackleby," he told the bartender. "I was told over the phone that a friend of mine is waiting here to see me."

"Oh yes," said the bland-faced Chinaman. "Your fiend be here in few minutes. Please to have drink on house. Shanghai Special!"

He mixed a drink in a tall glass and handed it to Homer. It was a slightly bluish color and a wisp of smoke rose from the top.

Homer was busy smiling at an attractive girl on the next stool and he took the drink and tossed it down with a nonchalant air.

He started to ask the girl her name when

the lights went out and a block of concrete fell on his head. He went rigid and fell back into the arms of two waiters standing behind him . . . waiting.

He opened his eyes to find himself tied to a heavy chair in a basement. Nearby, bound in another chair, sat an elderly man. There was a circular, metal cone with electrical attachment held by a bracket so that it hung down over the top of his head.

"Professor Blotchet, I presume," said Homer calmly. "I am Professor Hackleby of Jodrell Banks, England. May I inquire, sir, if you are having your hair dried?"

"This is an electronic brain-washer," replied Professor Blotchet. "That fiend will be back any minute to turn it on again. It plays a tape of TV commercials in my ears while the picture goes on the opposite wall there. No programs, you understand, only commercials for hours. I don't know how much longer I can hold out. My brain cells are deteriorating faster than butter in a frying pan."

"What did you discover about Pulsars that you wanted to tell National Security? I'm an agent with them. You'd better tell me now before you go mad, Professor, and while we're alone here."

"The Pulsar waves carry a mysterious, creative element that is unknown to mankind. This element causes an immediate cellular growth of any living organism it touches. I discovered it when I accidentally reflected a Pulsar in my laboratory and it fell upon a common fly. The insect began to swell before my eyes until it was four feet high. I managed to turn off the telescope and seize a fire-ax from the wall to cut off the monster's head just as it was preparing to attack me."

"Amazing!" cried Homer. "Think of the possibilities of it."

"Yes. You see, I also discovered a way to store Pulsars in a battery so that they may be transported about and used later."

"Where did you put the formulas for these discoveries, sir?"

"They are on a piece of paper in the Bible in my hotel room," said the Professor. "Can you imagine what would happen if those Pulsars were released over New York. They penetrate walls the same as radio waves. Think of ten million flies and cockroaches ten or fifteen feet high looking around for something to eat."

"Thank you for telling me where you hid the formulas, Professor Blotchet," said a

soft, sinister voice as a tall, thin Chinaman entered the basement and walked up to the prisoners. "After the insects have eaten the population of your country, we will breed huge birds in China to eat the insects. Then we will come over and enjoy your fine cars, swimming pools and luxurious apartments."

"But Red China does not have a radio telescope," said Homer.

"We will complete ours next week. Ten miles in diameter and built in the cone of an extinct volcano in the Kunlun Mountains. This will give us enough Pulsars to rule the world. And now, since neither of you are of further use to me, I am going to eliminate you. Have you any last request to make before leaving this life?"

"Yes," said Homer quickly. "I would like to make a will leaving my Electronic Company to my assistant. If you would release my right hand, I have a pen and paper in my pocket."

"Very well," said the man as he removed the leather strap holding Homer's wrist to the arm of the chair. "Write it quickly."

Homer drew a pen from his coat and pointed it at the man.

"I hope you are wearing a five-inch vest under that silk kimono, Fu Manchu. Do not move! This is a micro-electronic *Laser*

ray gun that will go right through your heart and across New Jersey."

The yellow face of the arch-criminal turned white in fear.

"Release Professor Blotchet," ordered Homer. "And now, Professor, if you will come and free me, I will send for assistance immediately."

When he stood up, Homer snapped on a small switch in his hearing aid. "This will give our exact location to the police who are waiting on the corner," he said with a smile to the Professor. "I gave them the wavelength just before leaving the Park View Hotel."

Within a few minutes, the police rushed into the basement and quickly rounded up the rest of the gang. Homer walked up to the tall, evil-faced leader and slipped the pen into his kimono pocket.

"Here, Fu," he said, "You might want to write a letter from where you're going. That's a pretty good ballpoint."

The man gave a snakelike hiss of rage as the police led him out. Professor Blotchet walked over to Homer and shook his hand.

"A wonderful job, sir. Then you were bluffing with that pen all of the time and it wasn't a micro Laser ray gun at all?"

"Of course not," said Homer with a smile. "I just took a chance that he had seen the same spy picture that I had, shall we go?" ■

Hot Receiver

Continued from page 45

I changed the 220-ohm suppressor-to-ground resistor to one of about 3000 ohms, and bridged the fone/CW switch by a 0.02 μ F or larger capacitor as shown in Fig. 1. This switches the S-meter zeroing potentiometer from suppressor to ground when the receiver is in the CW mode.

By rotating the potentiometer, really fine control of oscillation can be obtained, and the final IF stage can be used as either a Q multiplier or BFO. The modification doesn't interfere with normal S-meter operation when the receiver is switched back to fone. I could now receive 28 MHz hams on SSB. Not bad for such a simple receiver.

One more suggestion which could be useful: on such a simple receiver, it isn't possible to have both automatic gain control and a BFO at the same time, so strong stations

can cause blasting. Connecting the antenna to a 2000- to 5000-ohm potentiometer, as shown in Fig. 2, gives a simple gain control that doesn't alter anything in the receiver.

Having made these modifications—without any more equipment than a soldering iron—I am now the proud possessor of a rather more grown-up HA-226. ■



En Passant


Continued from page 25

PxR=Q?? RxQ 40 R-QB1, P-K7! and Black gets the better of it!) KRxQ 40 PxR=Q# RxQ 41 RxR, K-K2 42 R-Q1! PxP# (42 . . . P-K7 43 R-K1 wins) 43 KxP and the win is child's play.

Problem 18

By Guidelli

Black

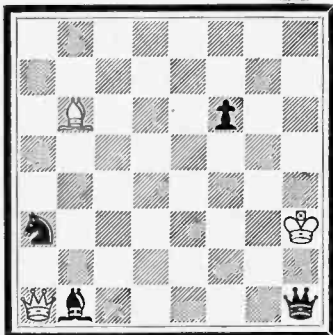

White


White to move and mate in two.
Solution in next issue.

Sometimes a mate can be far away—even in a two mover!

Solution to Problem 17: 1 P-N6.

Combination #1

Black

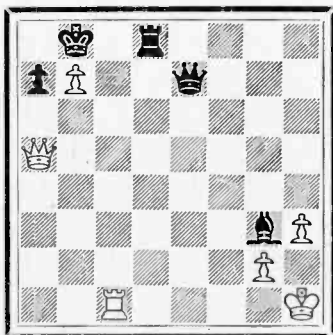

White

White to Play and Win.
Solution in next issue.

The basis of this clever combination is a Knight fork. But there are no Knights on the

board! Exactly. And that is the clue to the three move solution.

News and Views. Chess Olympiad (International Team Championship), Lugano, 1968: I. Soviet Union, 39½-12½, II. Yugoslavia, 31-21, III. Bulgaria, 30-22, IV. United States, 29½-22½. When will we ever win this prestigious event? When our government and people support chess as it is supported in most other countries!

Amsterdam Tournament, 1968 (sponsored by IBM Corporation!): L. Kavalek of Yugoslavia won it (10½ points) and David Bronstein, USSR, 10, was runner-up.

U. S. Junior Open, Cleveland, 1968: The joint winners with 7½-1½ were John Anderson of Milwaukee and Steve Stoyko of Newark. ■

Rocks in Radio

Continued from page 34

or quartz crystals come from. The rocks are processed, giving the metal, and the metal is used in the devices. And, in reality, these devices are the future of radio.

Rock centered research is active not only in the semiconductor field, but in the area of *rare earths*. These hard-to-find elements are used in the phosphor coating on the color picture tube. Right now, research is aimed at finding ways of supplying the rare earths, but applications are not being neglected. These too, are in the future of radio.

In fact, if you want a crystal ball to gaze into the future, or past, of radio, pick up any rock. That tells it all. ■

ADVERTISING INDEX

Advertiser	Page
Burstein-Applebee	15
Classified Advertising	111
Cleveland Institute of Electronics	112-113-114-3rd Cover
Cornell Electronics Co.	17
Edmund Scientific Co.	5
Grantham School of Electronics	15
Heath Co.	26-27-28-29
International Correspondence Schools	7
Lafayette Radio	13
McGee Radio Co.	17
National Radio Institute	52-53-54-55
National Technical Schools	1-2-3
Olson Electronics, Inc.	11
Park Electronic Products	17
Progressive "Edu-Kits" Inc.	4th Cover
RCA Institutes, Inc.	86-87-88-89
Xcelite, Inc.	9

Unimetrics Receiver


Continued from page 86

radios in the \$50 price class. In fact, just the short length of internal wiring from the whip to receiver is all that's needed for average reception; whip extension was only required for the weak FM stations or very distant stations.

The VHF performance proved clearly superior to most of the so-called "hand-held" VHF receivers. Because of the vernier tuning (used for all three bands) it was very easy to tune in the VHF stations *cleanly* dead on channel center. Sensitivity, while not quite up to that of a "communications receiver" in the \$70 to \$100 price range, was substantially better than the average low cost hand-held models. Selectivity was notably good, and the Omniband III was easily able to separate the fire, police and marine frequencies grouped around the 152 to 157 MHz portion of the dial.

Because of the filter network in the front end, image interference from services outside the VHF band is sharply reduced to a non-objectionable level.

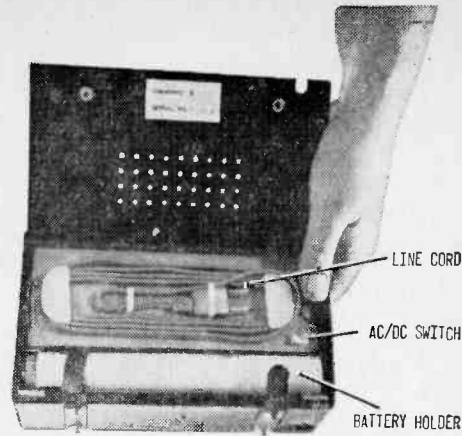Sound quality. Unlike most transistor portable radios the Omniband III's sound quality is not *shrill*—there are no overbalanced highs. This is due, in part, to the fact that there is no speaker grille. The front panel, though it appears to be an open grille, is really solid, thereby muting the highs and producing a total sound quality best described as *mellow* (at least it doesn't grate




Two snaps release the rear cover which provides access to the AC line cord, the battery holder and the AC-DC switch. Line cord holder and tie-down straps are supplied with radio.

on one's ear). Maximum sound level (before distortion becomes objectionable) is just about equal to that of a good quality solid-state table radio.

Summing Up. The Omniband III (high-band model) priced at \$39.95, including batteries and earphone, would be a good value as either an AM/FM or VHF radio. As a combination AM-FM-VHF radio it is an *excellent* buy worthy of your consideration if you're looking for a VHF totable with AM and FM coverage.

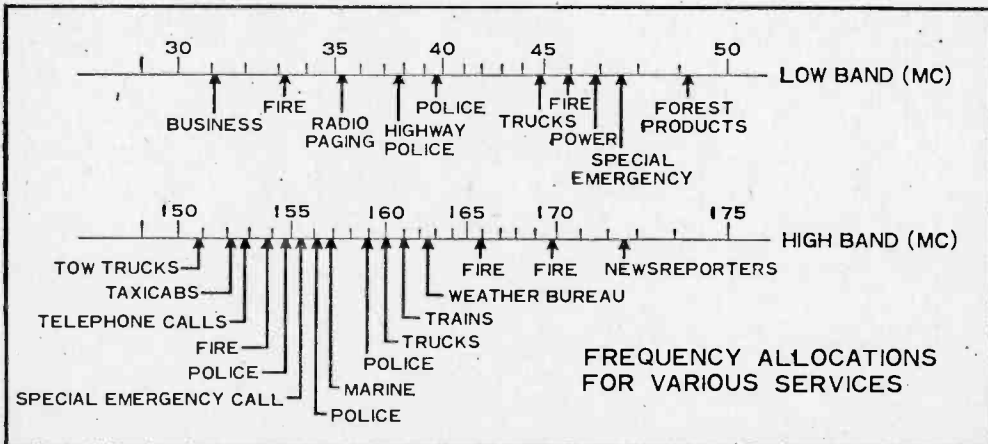For additional information on the Omniband III write to Unimetrics, Inc., Dept. TEC, 39 Werman Court, Plainview, N.Y. 11803. ■



You need a score card to spot the stations and the above diagram fills the bill. For emergency station listings, we suggest you check White's Radio Log every issue.

CLASSIFIED Market Place

FOR BIGGER PROFITS! NEW CAREER OPPORTUNITIES!
READ AND REPLY TO THESE CLASSIFIED ADS

Classified Ads 65¢ per word, each insertion, minimum 10 words, payable in advance. To be included in the next available issue of **ELEMENTARY ELECTRONICS**, copy must be in our New York Office by May 10th. Address orders to C. D. Wilson, Manager, Classified Advertising, **ELEMENTARY ELECTRONICS**, 229 Park Avenue South, New York, N. Y. 10003.

ADDITIONAL INCOME

MONEY—Sparetime Opportunity Panelists At Home Wanted By New York Researcher. Leading research firm seeking people to furnish honest opinions by mail from home. Pays cash for all opinions rendered. Clients' products supplied at no cost. For information write: Research 669, Mineola, N. Y. 11501, Dept. 633-EE.

FREE! The World's Leading Money-making Magazine. How and when to earn a Second Income, develop a Spare-time Business, get into Profitable Franchising, become a successful Agent. For your free copy—write Income Opportunities, 229 Park Ave., South, New York, 10003.

AUTHOR'S SERVICE

PUBLISH your book! Join our successful authors: publicity advertising promotion, beautiful books. All subjects invited. Send for free manuscript report and detailed booklet. Carlton Press, SMH, 84 Fifth Avenue, New York, 10011.

AUTO PARTS & ACCESSORIES

ALERT Vacationers—Avoid Speed Traps. Compact Radar Sentry Dual Band. Satisfaction Guaranteed—only \$39.95. International Supply, P.O. Box 575, Dalton, Georgia 30720.

BOOKS & PERIODICALS

SEND \$1.00. Seven Assorted. New Books. Sales, 2217 Lackland, St. Louis, Missouri 63114.

CATALOG of all Science & Mechanics Craftprints. Send 25¢ to cover postage to Craftprint Div., Science & Mechanics, 229 Park Ave., South, New York 10003.

BUSINESS OPPORTUNITIES

I MADE \$40,000.00 Year by Mailorder! Helped others make money! Start with \$10.00—Free Proof! Torrey, Box 318-T, Ypsilanti, Michigan 48197.

FREE Book "990 Successful Little-Known Businesses." Fascinating! Work home! Plymouth 311-W, Brooklyn, N. Y. 11218.

AEROSOL Fire Extinguisher \$1.98 Retail—your cost 96¢. Sample Postpaid \$1.50. G. E. Warren, 6922 East Congress, Detroit, Michigan 48207.

MAKE MONEY Operating Home Mail-Order Business. No Inventory. Write Russell Enterprises, 14803 Crossdale Avenue, Norwalk, Calif. 90650.

EARTHWORMS

BIG Money Raising Fishworms and Crickets. Free Literature. Carter Farm-O, Plains, Georgia 31780.

EDUCATION & INSTRUCTION

SAILMAKING: Step by Step. No Theory. \$4.00. Saugor, 41 Yonge Street, Richmond Hill, Ontario, Canada.

ELECTRONIC COMPONENTS

1,000 **VOLT** Power Supply Module \$14.95. 1,500 Volt Shocker Module \$5.95. Catalog 25¢. Franks Scientific Co., P.O. Box 156, Martelle, Iowa 52305.

GIFTS THAT PLEASE

NEW: Personal Telephones For Home or Office—22 styles to choose from. The most Unusual on the Market. Send today for Free Color Catalog. Fantasma-Goria, Parkland Shopping Center, Dept. EE, Cayce, South Carolina 29033.

HYPNOTISM

ADULTS Only! Hypnotize Successfully! "Instantaneous"—"One Word"—"Against Will" Methods Exposed! Complete illustrated course—including Self-Hypnosis—10" Hypnodisk—"Secret Nerve Pressure Technique." (They never know!) \$3.00. Results Absolutely Guaranteed! Fowler, Box 4390, Woodbury, N. J. 08096.

INVENTIONS WANTED

WE either sell your invention or pay cash bonus. Write for details. Universal Inventions, 298-3, Marion, Ohio 43302.

MAGNETS

MAGNETS. All types. Specials—20 disc magnets or 2 stick magnets, on 10 small bar magnets, or 8 assorted magnets, \$1.00. Maryland Magnet Company, 5412-R, Gist, Baltimore, Md. 21215.

MISCELLANEOUS

ROOT BEER, homemade instructions, \$3.00—Particulars, 10¢; Tomarch, 1114 41st, Brooklyn, N. Y. 11218.

ADULT books, magazines. Free illustrated catalogue. Clifton's, Box 1068-SM, Saugus, Calif. 91350.

WINEMAKERS—Free Catalog and Recipes: Kraus, Box 451-B, Nevada, Missouri 64772.

MONEYMAKING OPPORTUNITIES

INSTANT Money! Plastics are the wave of the future. Big profits now! At home! Spare time! Materials costing 11¢ bring \$2.58 profits immediately! Free information! Rush name on postcard to: Warner, 1513 Jarvis, Dept. CL-107-A, Chicago, Ill. 60626.

EIGHT Ways to Success. Free Details. Dixie, 2913 Colonial, Norfolk, Va. 23508.

I MADE \$1,000,000.00 in Mail Order. Simple Trick! Anyone can work it! Confidential Secrets \$1.00. Millionaire, 1901 Moonlight Drive, Denton, Texas 76201.

EARN \$200.00 Daily—Selling this Nationally Advertised Men's Helbros Wrist Watch—Factory Priced \$59.75. Rush \$18.95 for Sample. Satisfaction Guaranteed. Fantasma-Goria, Parkland Shopping Center, Dept. EE, Cayce, South Carolina 29033.

OF INTEREST TO WOMEN

HELP—Addressers, Mailers. Everything furnished, including Postage Stamps. For Application Blank—send 25¢. Mailers, Box 2706, Abilene, Texas 79604.

HONG KONG Fashions. Leroy Schmalstig, 612 Hulbert, Dayton, Ohio 45410.

PERSONAL

CANCER! You may be next! Stop Smoking! New Book reveals Medical and Psychological Method. Money Back Guarantee. \$2.00. Al J. Fields, 708 Peter, Garrett, Indiana 46738.

PRINTING, MIMEOGRAPHING & MULTIGRAPHING

1000 **LABELS**, 4 Lines \$1.00. Pocket Stamp \$1.00. Cash, Check, Stamps. Catalog 25¢. Seal, Box 505-M, Elgin, Ill. 60120.

RADIO & TELEVISION

THOUSANDS and thousands of types of electronic parts, tubes, transistors, instruments, etc. Send for Free Catalog. Arcurus Electronics Corp., EME, 502—22nd St., Union City, N. J. 07087.

POLICE—Fire—Aircraft—Marine—Amateur calls on your broadcast radio! Free catalog. Saich Company, Woodsboro EE14, Texas 78393.

"COIL WINDING" Handbook—50¢. Experimenter's catalog includes 250 exclusive items—25¢, refundable. Laboratories, 12041-G Sheridan, Garden Grove, Calif. 92640.

SEEDS, PLANTS & NURSERY STOCK

GROW Exquisite Miniature Bonsai. Pre-plant \$2.95. Helbro Nurseries, Livingston Manor, N. Y. 12758.

START YOUR OWN BUSINESS

FREE Booklet! Home-Based Businesses. Hacienda House, 900 North Howard, Glendale, California 91207.

MAKE Your Classified Ad Pay. Get "How To Write a Classified Ad That Pulls." Includes certificate worth \$2.00 towards classified ad. Send \$1.25 to C. D. Wilson, Science & Mechanics, 229 Park Avenue South, New York, N. Y. 10003.

TREASURE FINDERS—PROSPECTING EQUIPMENT

FIND Buried Treasure with the most popular transistorized metal detector in the country. Treasure Probe available as kit (\$14.88), assembled (\$18.88). With powerful built in speaker (\$24.88). Schematic, parts list, and step by step instructions \$1.00. Ten day money back guarantee. Free catalog available. Treasure Probe, EGE, P.O. Box 64, Lakewood, New Jersey 08701.

Hunting for a better job?

**Here's the
license
you need
to go after
the big ones**



A Government FCC License can help you bring home up to \$10,000, \$12,000, and more a year. Read how you can prepare for the license exam at home in your spare time—with a passing grade assured or your money back.

IF YOU'RE OUT TO BAG A BETTER JOB in Electronics, you'd better have a Government FCC License. For you'll need it to track down the choicest, best-paying jobs that this booming field has to offer.

Right now there are 80,000 new openings every year for electronics specialists—jobs paying up to \$5, \$6, even \$7 an hour... \$200, \$225, \$250, a week... \$10,000, \$12,000, and up a year! You don't need a college education to make this kind of money in Electronics, or even a high school diploma.

But you *do* need knowledge, knowledge of electronics fundamentals. And there is only one nationally accepted method of measuring this knowledge... the licensing program of the FCC (Federal Communications Commission).

Why a license is important

An FCC License is a legal requirement if you want to become a Broadcast Engineer, or get into servicing any other kind of transmitting equipment—two-way mobile radios, microwave relay links, radar, etc. And even when it's not legally required, a license proves to the world that you understand the principles involved in *any* electronic device. Thus, an FCC "ticket" can open the doors to thousands of exciting, high-paying jobs in communications, radio and broadcasting, the aerospace program, industrial automation, and many other areas.

So why doesn't everyone who wants a good job in Electronics get an FCC License and start cleaning up?

The answer: it's not that simple. The government's licensing exam is tough. In fact, an average of two out of every three men who take the FCC exam fail.

There is one way, however, of being pretty certain that you will pass the FCC exam. And that is to take one of the FCC home study courses offered by Cleveland Institute of Electronics.

CIE courses are so effective that better than 9 out of 10 CIE graduates who take the exam pass it. That's why we can back our courses with this iron-clad Warranty: Upon completing one of our FCC courses, you must be able to pass the FCC exam and get your license—or you'll get your money back!

They got their licenses and went on to better jobs

The value of CIE training has been demonstrated time and again by the achievements of our thousands of successful students and graduates.

2 NEW CIE CAREER COURSES

- 1. BROADCAST (Radio and TV) ENGINEERING...** now includes Video Systems, Monitors, FM Stereo Multiplex, Color Transmitter Operation and CATV.
- 2. ELECTRONICS ENGINEERING...** covers steady-state and transient network theory, solid state physics and circuitry, pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Ed Dulaney, Scottsbluff, Nebraska, for example, passed his 1st Class FCC License exam soon after completing his CIE training...and today is the proud owner of his own mobile radio sales and service business. "Now I manufacture my own two-way equipment," he writes, "with dealers who sell it in seven different states, and have seven full-time employees on my payroll."

Daniel J. Smithwick started his CIE training while in the service, and passed his 2nd Class exam soon after his discharge. Four months later, he reports, "I was promoted to manager of Bell Telephone at La Moure, N.D. This was a very fast promotion and a great deal of the credit goes to CIE."

Eugene Frost, Columbus, Ohio, was stuck in low-paying TV repair work before enrolling with CIE and earning his FCC License. Today, he's an inspector of major electronics systems for North American Aviation. "I'm working 8 hours a week less," says Mr. Frost, "and earning \$228 a month more."

Send for FREE book

If you'd like to succeed like these men, send for our FREE 24-page book "How To Get A Commercial FCC License." It tells you all about the FCC License... requirements for getting one... types of licenses available... how the exams are organized and what kinds of questions are asked... where and when the exams are held, and more.

With it you will also receive a second FREE book, "How To Succeed In Electronics." To get both books without cost or obligation, just mail the attached postpaid card. Or, if the card is missing, just mail the coupon below.

ENROLL UNDER NEW G.I. BILL. All CIE courses are available under the new G.I. Bill. If you served on active duty since Jan. 31, 1955, or are in service now, check box on reply card for complete details.

CIE Cleveland Institute of Electronics

1776 E.17th St., Cleveland, Ohio 44114

Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934



Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:
Your 40-page book "How to Succeed In Electronics" describing job opportunities in Electronics today, and how your courses can prepare me for them.
Your book on "How To Get A Commercial FCC License."

I am especially interested in:

<input type="checkbox"/> Electronics Technology	<input type="checkbox"/> Electronic Communications
<input type="checkbox"/> Broadcast Engineering	<input type="checkbox"/> Industrial Electronics
<input type="checkbox"/> First Class FCC License	<input type="checkbox"/> Electronics Engineering

Name _____ (PLEASE PRINT)

Address _____

City _____

State _____ Zip _____ Age _____

Check here for G.I. Bill information EL-14

DU-20 RADIO

Reg. U. S. Pat. Off.

CIRCUITS AT HOME
with the New Improved
PROGRESSIVE RADIO "EDU-KIT"®

only

\$ **20** 95



Training Electronics Technicians Since 1946

A Practical Home Radio Course

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold In 79 Countries

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of Punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background in television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with an excellent background for television, Hi-Fi and Electronics. Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with an excellent background for television, Hi-Fi and Electronics. Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with an excellent background for television, Hi-Fi and Electronics.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector Circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build twenty different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tuning, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, coils, volume controls and switches, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C. Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

Progressive "Edu-Kits" Inc., 1186 Broadway, Dept. 531DJ, Hewlett, N. Y. 11557

UNCONDITIONAL MONEY-BACK GUARANTEE

Please rush my Progressive Radio "Edu-Kit" to me, as indicated below. Check one box to indicate choice of model:

- Regular model \$26.95.
- Deluxe model \$31.95 (same as regular model except with superior parts and tools plus valuable Radio & TV Tube Checker).

Check one box to indicate manner of payment

- I enclose full payment. Ship "Edu-Kit" post paid.
- I enclose \$5 deposit. Ship "Edu-Kit" C.D.D. for balance plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name _____

Address _____

City & State _____

Zip _____

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 531DJ, Hewlett, N. Y. 11557

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE + QUIZZES
- TELEVISION BOOK + RADIO TROUBLE-SHOOTING WORK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE + FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct for your friends, and made causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I employed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get it and swing it so quickly. The Trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.