

JULY 1970 A HARCOURT BRACE JOVANOVIĆ PUBLICATION

# ELECTRONIC TECHNICIAN / DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION



XX  
FRISE  
WILLIAM W. FRISE  
7176 GALE RD.  
ATLAS MI  
48411

**Installing a  
Mobile Transceiver**

**Teklab Report on  
Emerson 26C56**

**Servicing Solid-State  
Stereo-Part II**



### **The easy outlet for MATV installers**


Channel Master variable isolation wall tapoffs offer such speed, convenience and utter accuracy of installation that you're bound to feel guilty about using them. They're so quick and easy to connect, inspect and set, you'll be amazed at how little time it takes to finish the most complex MATV system professionally!

You'll also be amazed at how they simplify inventory and end up saving you time, money and trouble.

So please, don't feel guilty about taking the easy outlet.
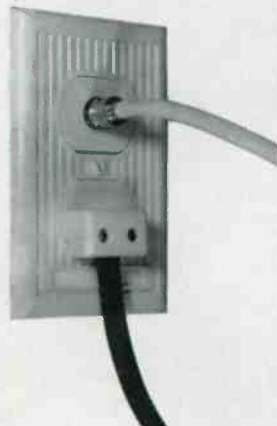
## **CHANNEL MASTER**

DIVISION OF AVNET, INC. Ellenville, New York 12428





COMPLETE MANUFACTURER'S CIRCUIT DIAGRAMS  
AND TECHNICAL INFORMATION FOR 5 NEW SETS

GROUP  
**215**

SCHEMATIC NO.

SCHEMATIC NO.


GENERAL ELECTRIC .....1307  
Color TV Chassis N-1

RCA VICTOR .....1306  
TV Chassis KCS169X Series

MAGNAVOX .....1310  
TV Chassis T949 Series



ZENITH .....1309  
Color TV Chassis  
14A9C29/14A10C29

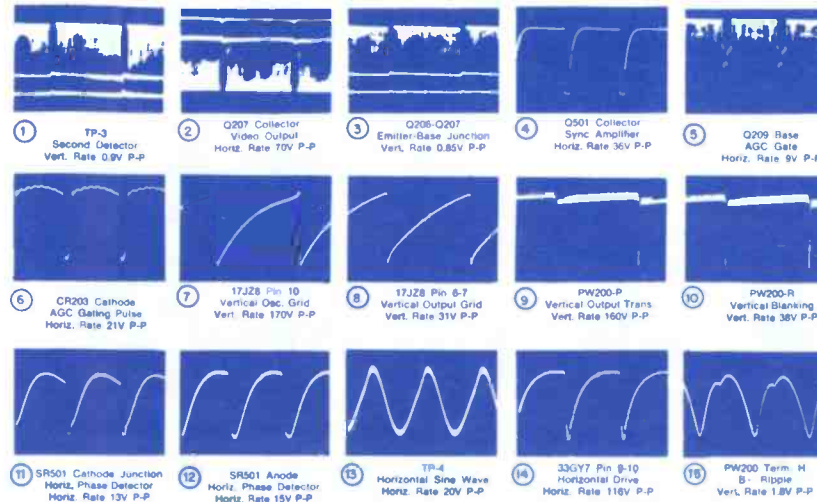RCA VICTOR .....1308  
Color TV Chassis CTC43 Series



SYMBOL	DESCRIPTION	RCA VICTOR PART NO.
C601	3 section electrolytic	125989
C601A	200µf, 175v	114314
C601B	50µf, 175v	107463
C601C	400µf, 175v	125129
F201	Fuse-50	107385
L201	RF	107385
L202	2.7µh	127043
L501	horiz hold	125120
L502	RF Choke	121229
L503	RF Choke	125123
L601	reactor-filter	122768
R101	1500Ω 15w	125122
R106	47Ω 5%, 7w, WW	124263
R210	control, contrast/bright/vol	128492
R241	control, video bias	125114
R526	control, vert lin vert size vert hold	125115
RF601	fuse-0.35Ω	125116
RT601	therm-16Ω cold	113097
T201	audio trap-band pass	113097
T202	ratio det	116115
T203	audio output	116116
T204	IF input	129708
T205	IF input	125117
T206	1st pix IF	
T208	2nd pix IF	
T501	horiz output	
T502	vert output	
Yoke	deflection	

Chassis Layout

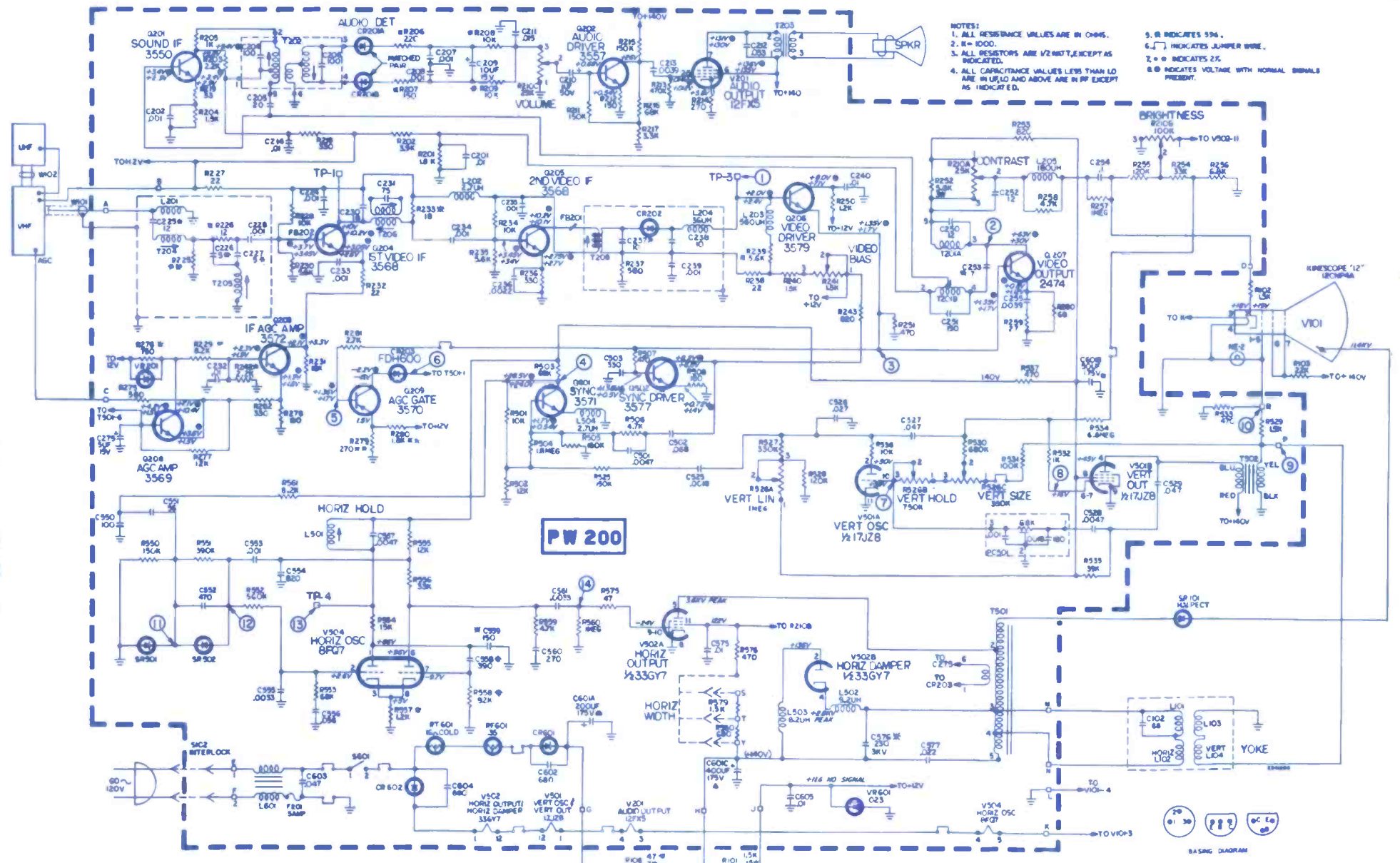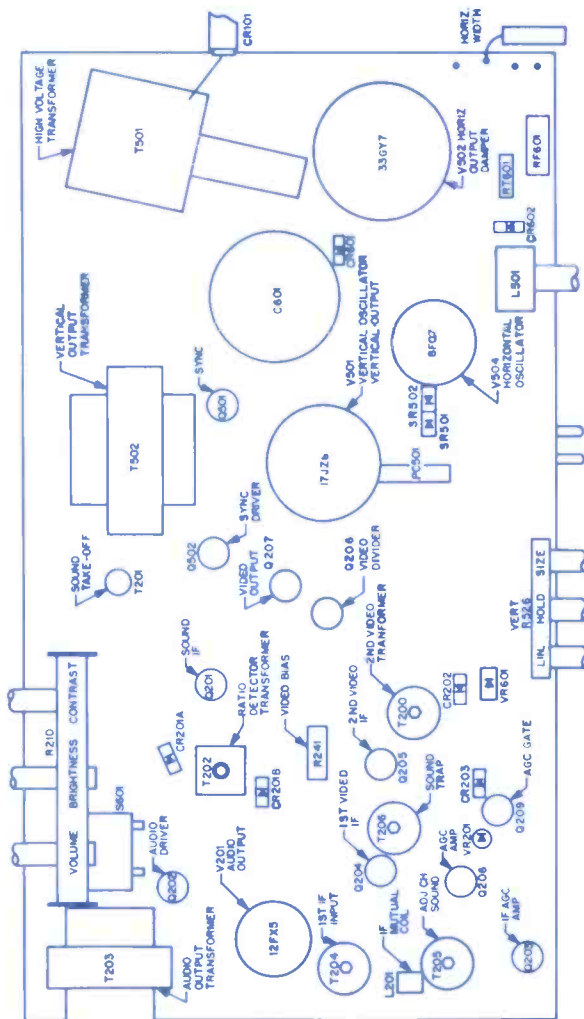


NOTES:  
1. ALL RESISTANCE VALUES ARE IN OHMS.  
2. K=1000.  
3. ALL RESISTORS ARE 1/2WATT, EXCEPT AS INDICATED.  
4. ALL CAPACITANCE VALUES LESS THAN 10 ARE IN PICO AND ABOVE ARE IN PPF EXCEPT AS INDICATED.  
5. R INDICATES 5%.  
6. J INDICATES JUMPER WIRE.  
7. Z INDICATES 2K.  
8. B INDICATES VOLTAGE WITH NORMAL SIGNALS PRESENT.



SYMBOL	DESCRIPTION	GENERAL ELECTRIC PART NO.
X501	Quartz, Crystal, 3.58MHz	EP41X1
C402A	200µf, +100% -10%, 350v electro	EP31X18
C402B	100µf, +100% -10%, 175v, electro	EP31X18
C402C	50µf, +100% -10%, 175v, electro	EP31X18
C403A	200µf, +100% -10%, 350v, electro	EP31X18
C403B	100µf, +100% -10%, 175v	EP31X18
C403C	50µf, +100% -10%, 175v electro	EP31X18
Q152	trans, NPN, silicon, AGC keyer	EP15X7
Q200	trans, NPN, silicon, Sync amp	EP15X3
Q201	trans, horiz, etc	EP15X7
Q202	trans, horiz react	EP15X9
Q203	trans, horiz osc	EP15X9
Q204	trans, horiz driver	EP15X10

Q501	trans, NPN, silicon, burst amp	EP15X5
Q502	trans, NPN, silicon, blanking driver	EP15X9
R165	control, AGC, 1K	EP49X44
R171	control, triple contrast, 500K, 20%	EP49X50
R176	contr, trip brite, 200K, 30%	EP49X50
R177	contr, 50K, brite limit adjust	EP49X52
R236	contr, HV adjust, 350K	EP49X46
R242	contr, 20M, focus adjust	EP49X51
R244	contr, triple V hold, 500K, 30%	EP49X50
R257	contr, dual, V height, 1M	EP49X45
R309	contr, on-off vol., 1M(WM25 1NBG-1)	EP49X3
R511	contr, color, 500Ω (WM253NWD-1)	EP49X54
R511	contr, color, 500Ω (WM251NBG-1)	EP49X16
R513	contr, tint, 2KΩ (WM253NWD-1)	EP49X55
R513	contr, tint, 2KΩ (WM251NBG-1)	EP49X56

R542	contr, triple, red screen, 1M	EP49X43
L151	coil, 47.25 trap	EP36X13
L152	coil, IF xformer	EP36X42
L156	coil, LC filter	EP36X51
L157	coil, 4.5MHz trap w/core	EP61X3
L159	coil, delay line	EP36X50
L201	coil, horiz, osc	EP36X55
L302	coil, quad	EP36X52
L402	coil, degaussing	EP36X62
L403	filter reactor	EP63X3
T151	xformer, 1st IF plate	EP61X9
T152	xformer, 2nd IF plate	EP61X7
T153	xformer, 3rd IF plate	EP61X8
T201	xformer, horiz output	EP77X7
T202	xformer, vert output	EP64X7


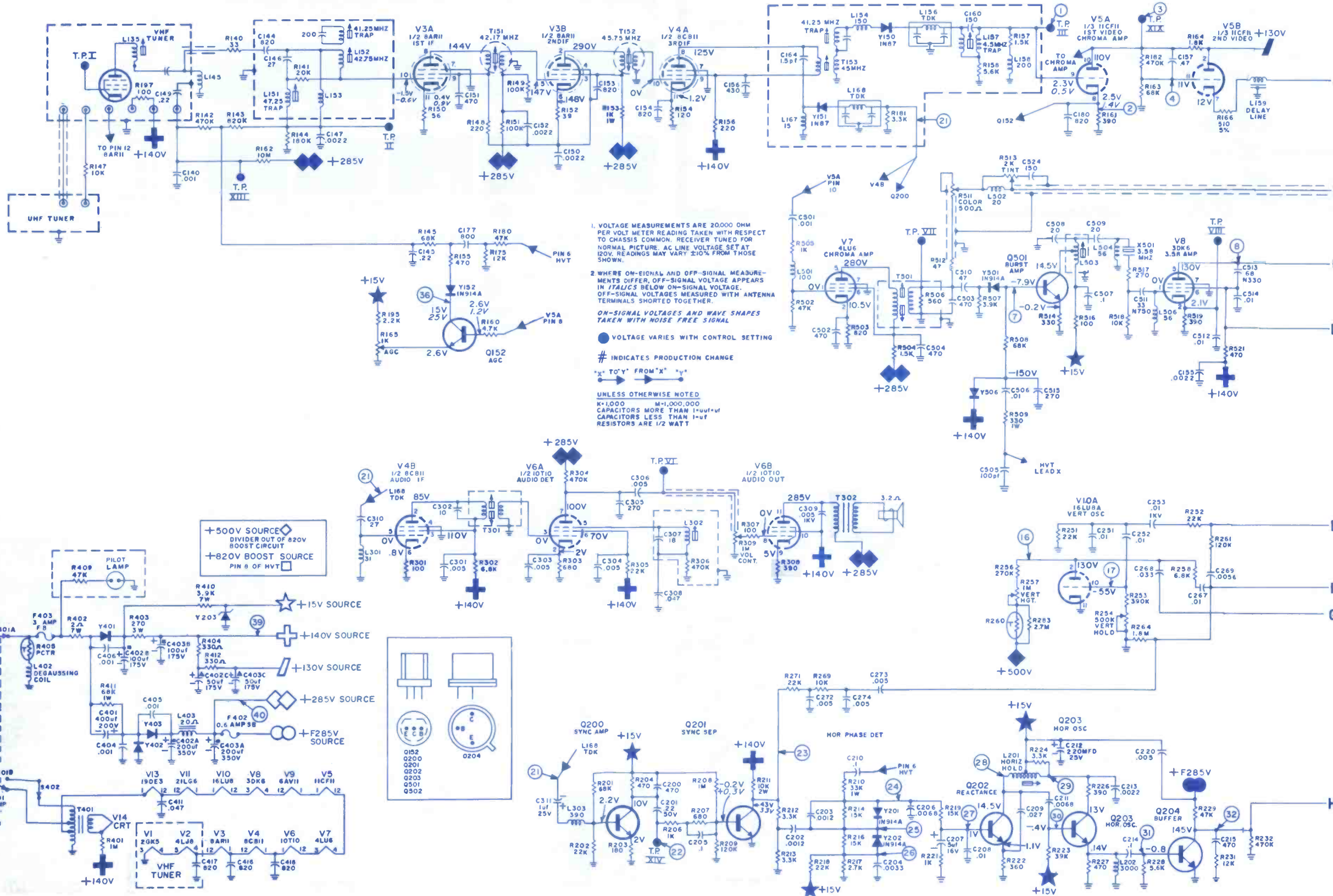




- T302-xformer, audio output.....EP64X8
- T401-xformer, filament.....EP64X9
- T501-coils, chroma bandpass.....EP36X2
- T502-xformer, chroma demod.....EP36X65
- R173-5K, ±10%, 5w, carbon film.....EP14X19
- R237-4.7K, ±10%, 7w, WW.....EP14X6
- R241-focus, voltage dropping.....EP41X2
- R243-47M, ±10%, 1.5w, 4kv.....EP14X1
- R244-varistor, 1ma, ±15% @85v.....EP13X2
- R246-varistor, 1ma, ±15% @575v.....EP13X3
- R260-therm, 500K, ±10%, @25°C.....EP14X20
- R402-2, ±5%, 7w WW.....EP14X21
- R403-270, ±10%, 3w WW.....EP14X22
- R410-3.9K, ±10%, 7w, WW.....EP14X26

- fuse, 4a slow-blo (F401).....EP10X7
- fuse, 6a slow-blo (F402).....EP10X5
- fuse, 3a fast-blow (F403).....EP10X4
- yoke, deflection.....EP76X5
- CRT socket assembly.....EP34X11

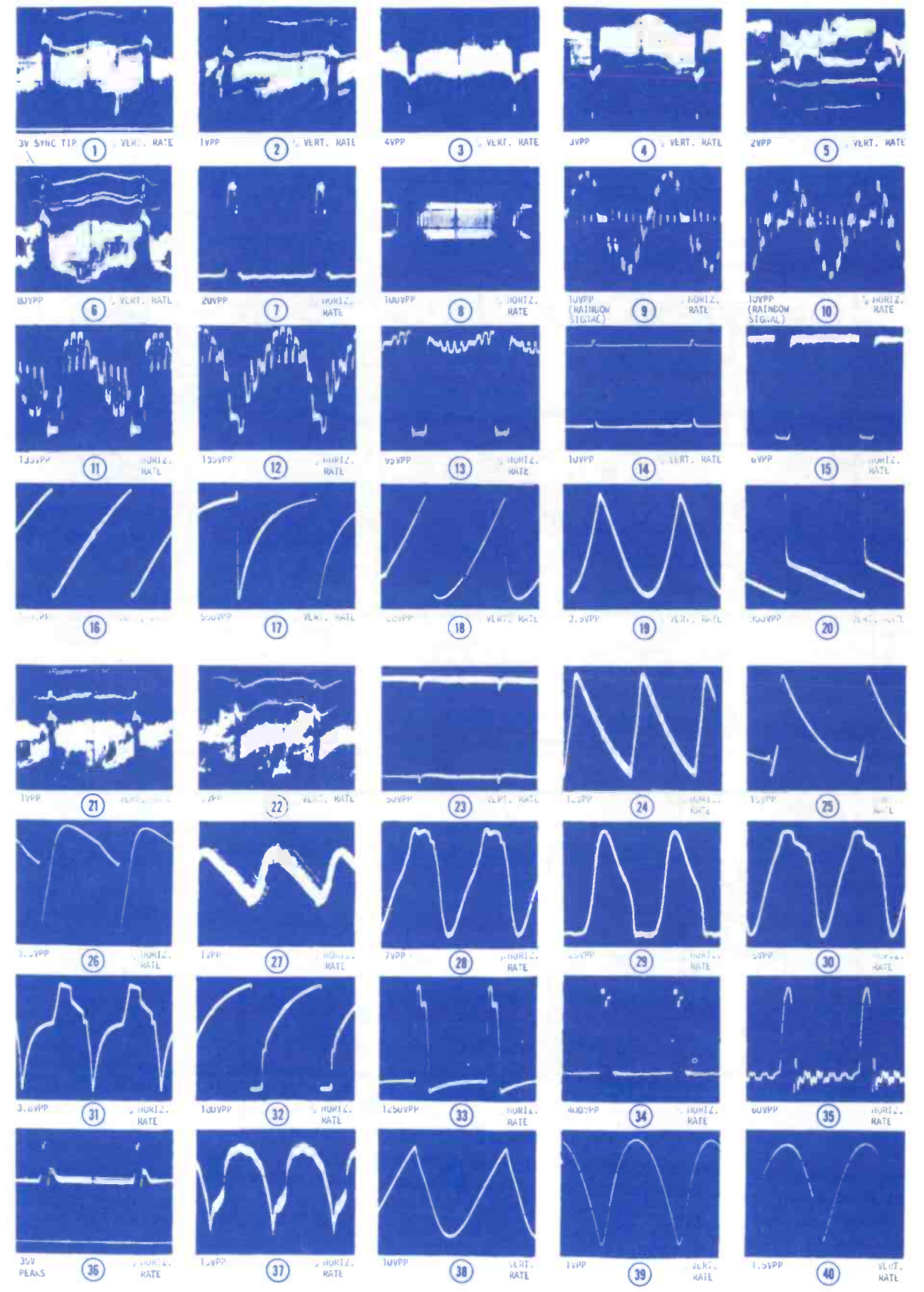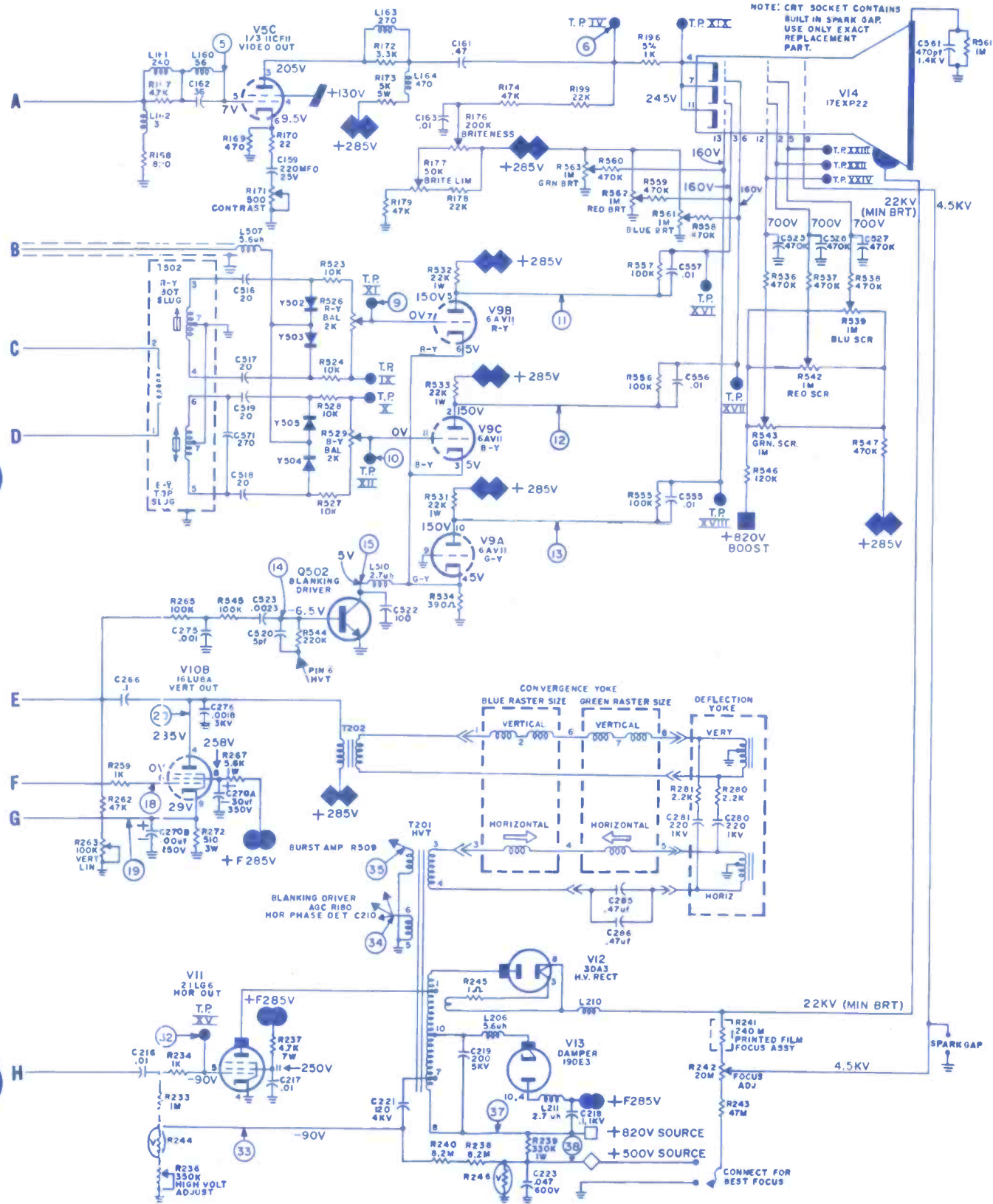**GENERAL ELECTRIC**  
Color TV Chassis N-1





JULY • 1970




6 PW500-F  
200V P-P Horiz. Rate  
Output AGC Keyer




7 TP501  
7.5V P-P Horiz. Rate  
Output Sync Amp



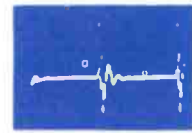8 TP501  
7.5V P-P Vert. Rate  
Output Sync Amp



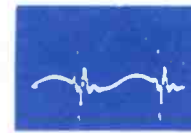
9 TP503  
300V P-P Horiz. Rate  
Center Tap L501-B



10 TP502  
45V P-P Horiz. Rate  
Cathode Horiz. Oscillator



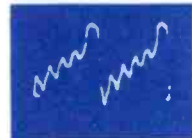11 V502-9  
90V P-P Vert. Rate  
Grid Vert. Oscillator




20 V705-9  
115V P-P Horiz. Rate  
Grid Blanker




21 CR706 Cathode  
5V P-P Horiz. Rate



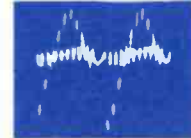
22 V706-2  
18V P-P Horiz. Rate  
Grid Video Output



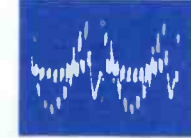
23 PW700-12  
150V P-P Horiz. Rate  
B-Y Amp Output



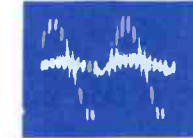
24 PW700-7  
36V P-P Horiz. Rate  
G-Y Amp Output



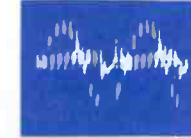
25 PW700-3  
130V P-P Horiz. Rate  
R-Y Amp Output



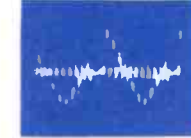
26 V701-9  
3V P-P Horiz. Rate  
Grid G-Y Amp



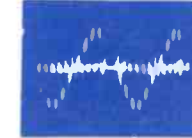
27 V702-1  
6V P-P Horiz. Rate  
Grid B-Y Amp



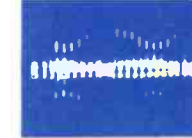
28 V704-2  
6V P-P Horiz. Rate  
Grid R-Y Amp



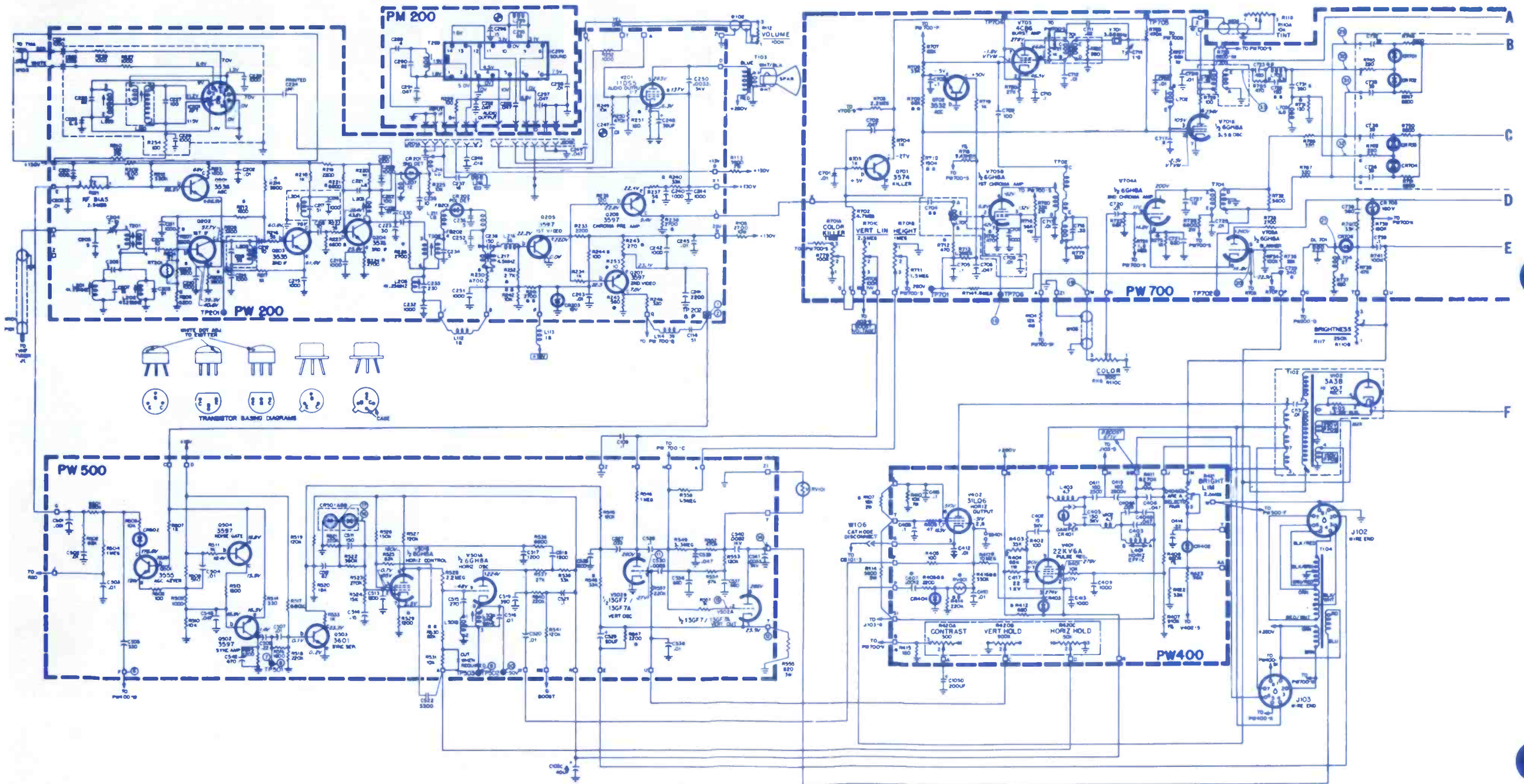29 A701-1 and 9  
9V P-P Horiz. Rate  
Chroma Input to Demod





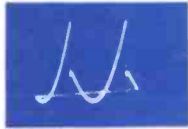

12 V502-3 (Term. T)  
14V P-P Vert. Rate  
Cathode Vert. Output




13 V502-2  
400V P-P Vert. Rate  
6nd Vert. Output



14 V502-6 (Term. L)  
1200V P-P Vert. Rate  
Vertical Output



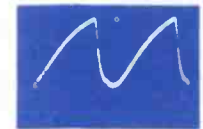15 V502-8  
400V P-P Vert. Rate  
Plate Vert. Oscillator




16 CR501-Anode  
22V P-P Horiz. Rate  
Horiz. Phase Detector




17 CR501 Cathode  
12V P-P Horiz. Rate  
Horiz. Phase Detector



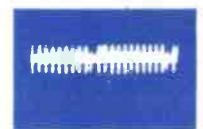18 Term. C  
2.5V P-P Vert. Rate  
Sync Input



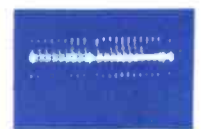19 TP706  
1V P-P Horiz. Rate  
Grid 1st Chroma Amp



20 PW700-M  
5V P-P Horiz. Rate  
Input 2nd Chroma Amp




30 A701-2  
10V P-P Horiz. Rate  
Demod Reference



31 A701-3 and 7  
8V P-P Horiz. Rate  
Chroma Input to Demod



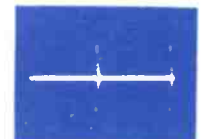
32 A701-8  
10V P-P Horiz. Rate  
Demod Reference




33 T703-E  
60V P-P Horiz. Rate  
Chroma Reference Output



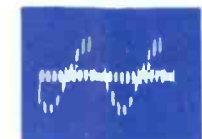
34 A701-4  
7V P-P Horiz. Rate  
Demod Output



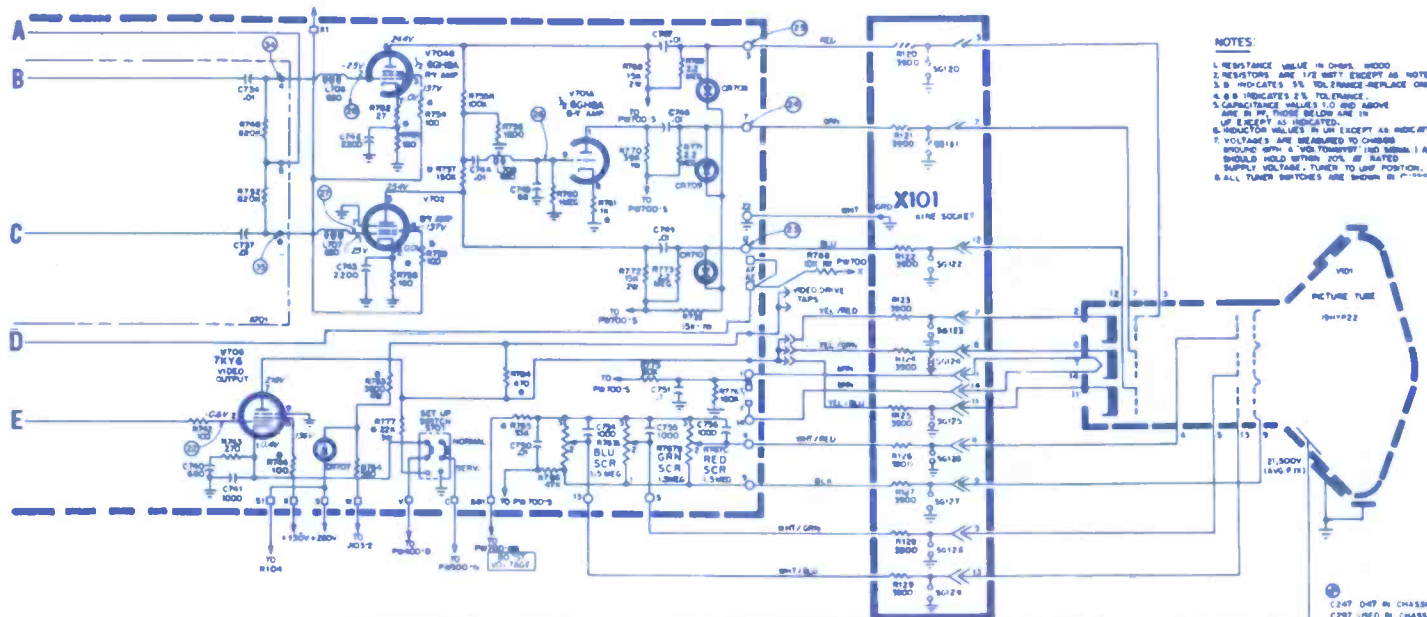
35 A701-6  
6V P-P Horiz. Rate  
Demod Output



NOTES:  
1. RESISTANCE VALUE IN OHMS, 1000  
2. RESISTORS ARE 1/2 WATT EXCEPT AS NOTED.  
3. B INDICATES 5% TOLERANCE; REPLACE ONLY WITH APPROVED PART.  
4. B INDICATES 2% TOLERANCE.  
5. CAPACITANCE VALUES 1.0 AND ABOVE  
ARE IN PF, THOSE BELOW ARE IN  
UF EXCEPT AS INDICATED.  
6. HORIZONTAL VALUES IN UF EXCEPT AS INDICATED.  
7. VOLTAGES ARE REFERRED TO CHASSIS  
GROUND UNLESS OTHERWISE INDICATED AND  
SHOULD HOLD WITHIN 20% OF STATED  
SUPPLY VOLTAGE. FLUOR TO LEFT POSITION.  
8. ALL TUNER SWITCHES ARE SHOWN IN  
CHANNEL 13 POSITION.

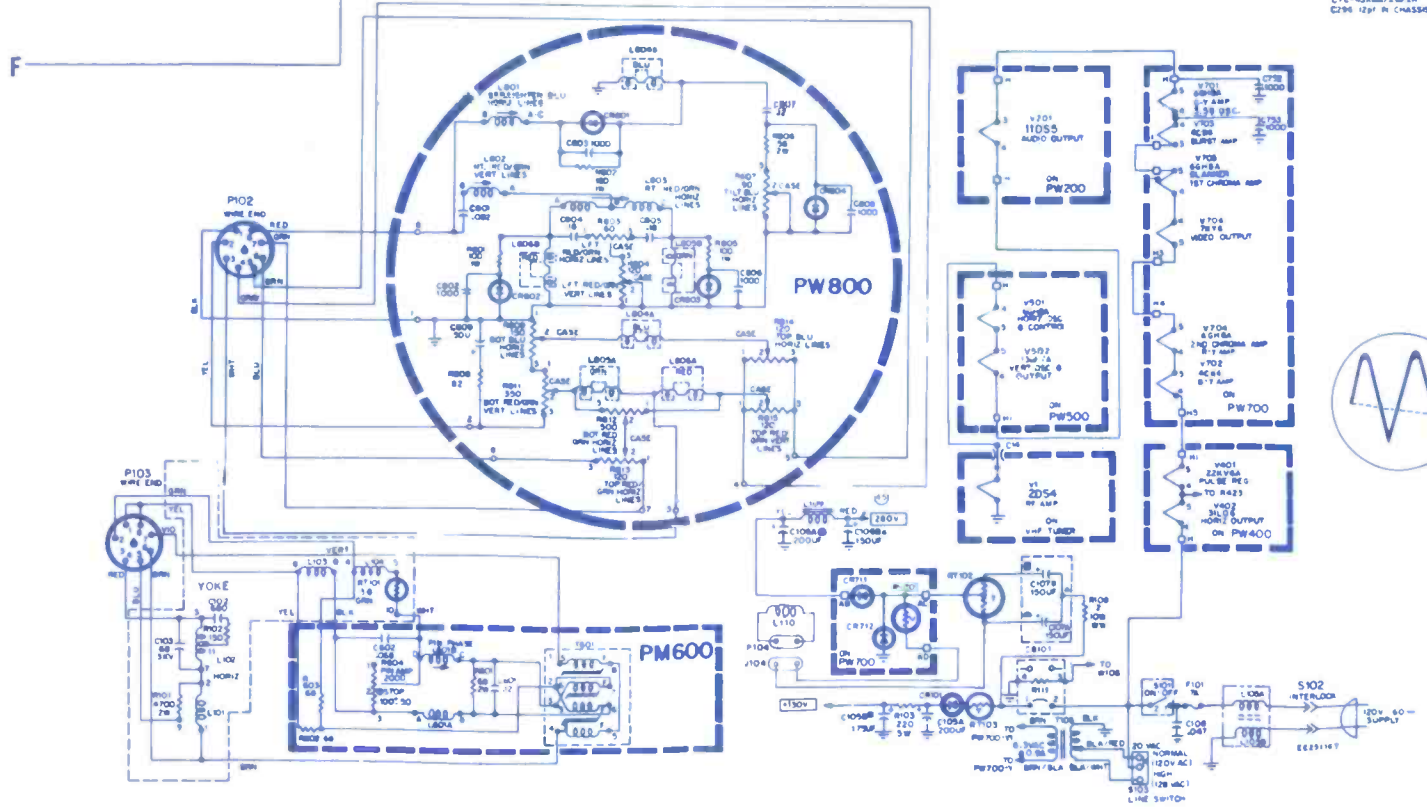

SYMBOL	DESCRIPTION	RCA VICTOR PART NO.
C105	4 section electrolytic	130821
C105A	200µf, 200v	130821
C105B	175µf, 175v	130821
C105C	40µf, 300v	130821
C105D	200µf, 10v	130821
C106	2 section electrolytic	126340
C106A	200µf, 350v	126340
C106B	150µf, 350v	126340
C107	2 section electrolytic	130769
C107A	150µf, 175v	130769
C107B	150µf, 175v	130769
CR101	breaker-circuit	130077
CR401	dampner	120818
CRM1	module-color	130058
F101	Fuse-7a	120785
IC201	circuit-integ. AFT, CTC, 43XT, XU, XR	130130
IC299	circuit-integ. CTC 43A, XT, XU	130122
IC299	circuit-integ. CTC 43A, XT, XU	130751
L105	AC line filter	126602
L299	discriminator	130121
L401	horiz eff	129453
L501	horiz	109947
L702	osc strength	121591
L709	rag mutual	115427
Q201	AGC	124753
Q202	1st pix 1F	124757
Q204	3rd pix 1F	124754
Q205	1st video	130139
Q206	chroma preamp	130139
Q207	2nd video	130139
Q501	AGC keyer	126712
Q502	sync amp	130139
Q503	sync sep	129899
Q504	noise gate	130139
Q701	killer	124755
Q702	acc	123941
R106	2700Ω 10%, 10w, film	130082
R108	2Ω 10%, 10w, WW	126360
R130	910,000Ω 5%, 1/2w, special CTC 43XR	131041
R420	control, contrast/vert hold/horiz hold	130108
R421	control, bright limiter	125076
R701	control, killer/vert height/vert lin	130107
R767	control, blue/green/red screen	126763
RT102	therm 240Ω cold	127227
RT103	therm 17Ω cold	131164
RT201	therm 4300Ω cold	124813
RV401	varistor hold down	124811
RV501	varistor 635v	130147
RV701	varistor degauss	126424
RV1101	varistor	130042
T102	horiz output	131044
T403	audio output	129822
T104	vert output	130092
T105	filament	130624
T105	filament	130090
T701	burst	130104
T703	oscillator	121559
T704	2nd chroma	130101
T1101	driver	130041
RT101	therm, temp comp, 3.8Ω	115942
	yoke deflection	131772



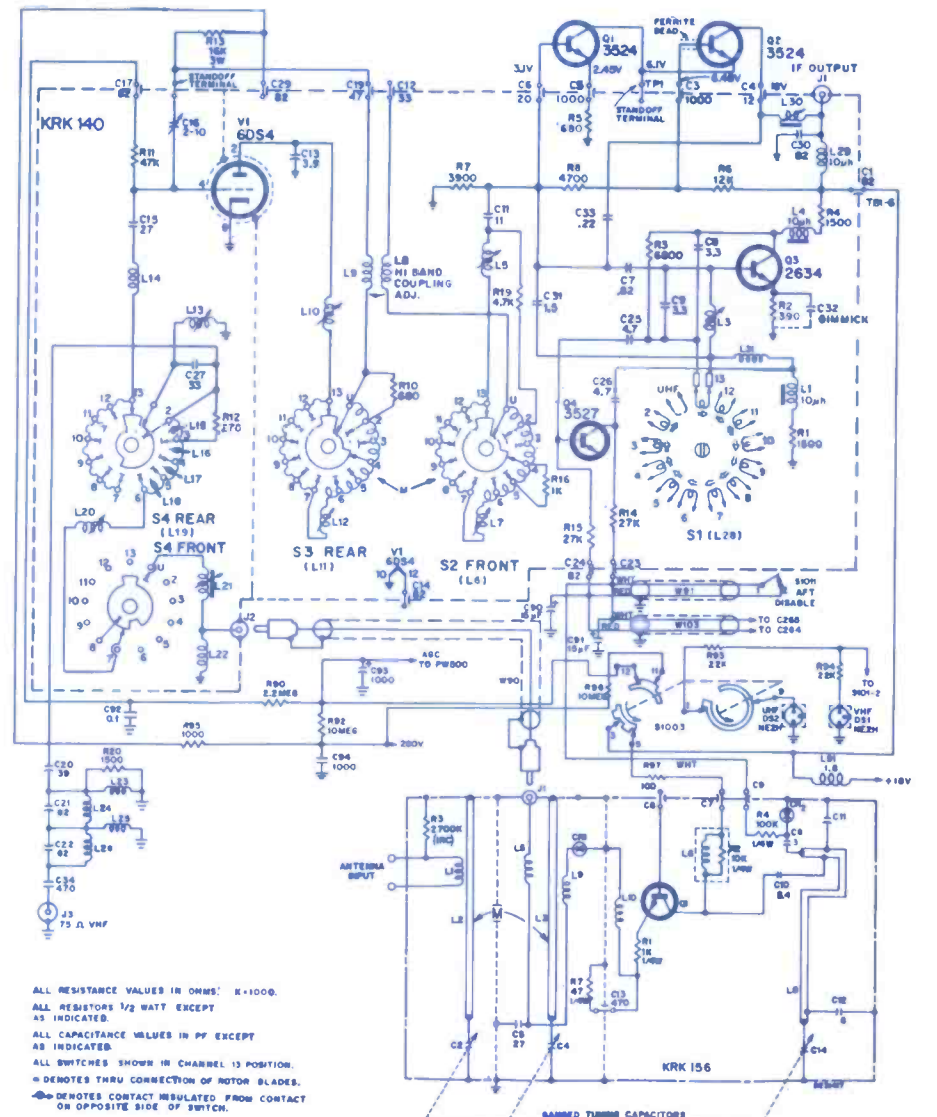


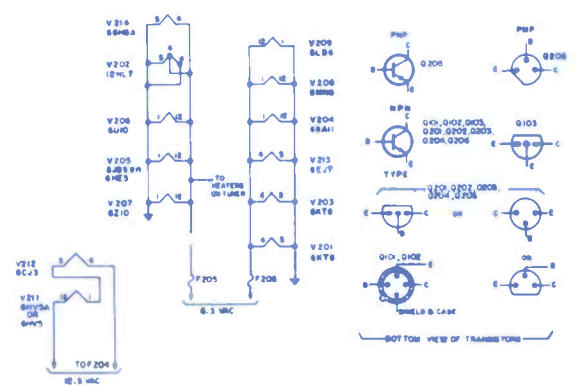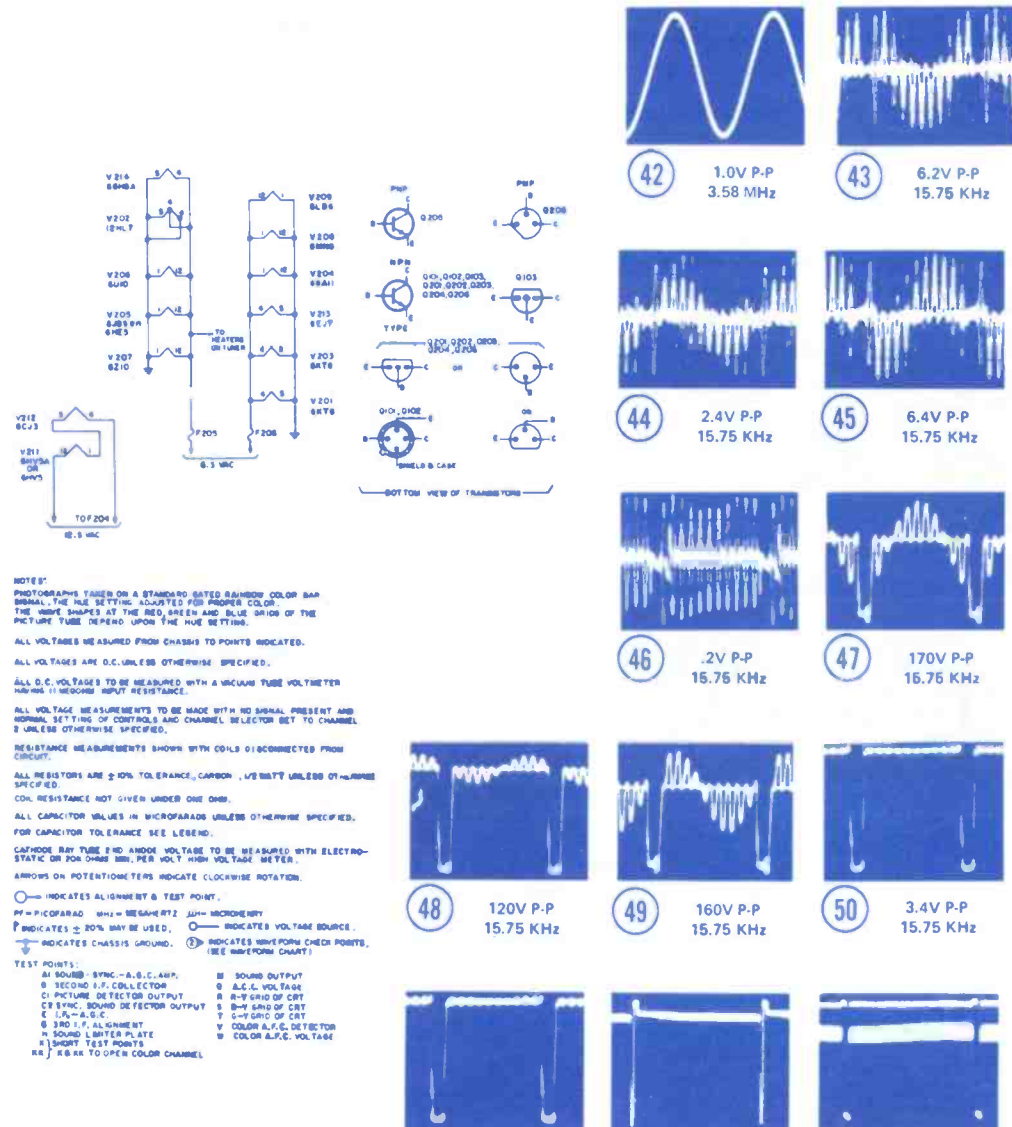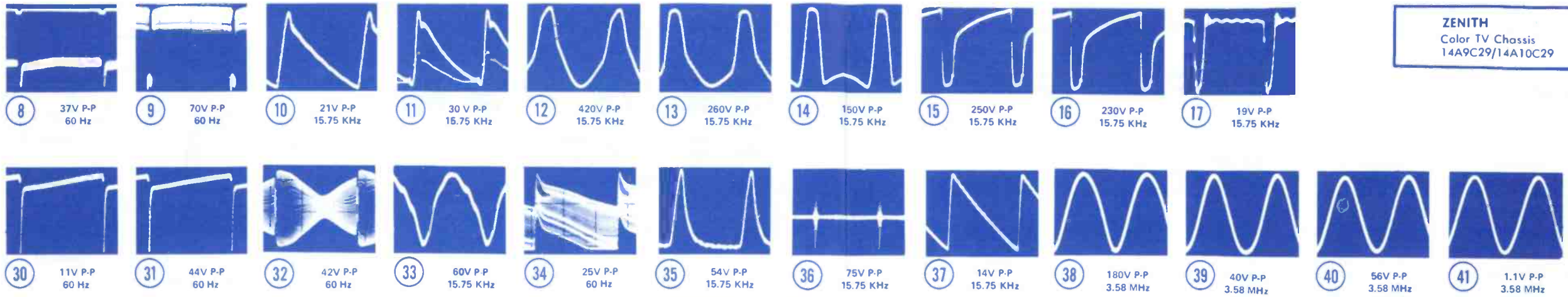ALL RESISTANCE VALUES IN OHMS; K=1000.  
ALL RESISTORS 1/2 WATT EXCEPT  
AS INDICATED.  
ALL CAPACITANCE VALUES IN PF EXCEPT  
AS INDICATED.  
ALL SWITCHES SHOWN IN CHANNEL 13 POSITION.  
⊕ DENOTES THRU CONNECTION OF ROTOR SLIDES.  
⊖ DENOTES CONTACT INSULATED FROM CONTACT  
OR OPPOSITE SIDE OF SWITCH.











NOTE:  
PHOTOGRAPHS TAKEN ON A STANDARD RATED RAINBOW COLOR BAR SIGNAL. THE HUE SETTING ADJUSTED FOR PROPER COLOR. THE WAVE SHAPES AT THE RED, GREEN AND BLUE SIDES OF THE PICTURE TUBE DEPEND UPON THE HUE SETTING.  
ALL VOLTAGES MEASURED FROM CHASSIS TO POINTS INDICATED.  
ALL VOLTAGES ARE D.C. UNLESS OTHERWISE SPECIFIED.  
ALL D.C. VOLTAGES TO BE MEASURED WITH A VACUUM TUBE VOLTMETER HAVING 11 MEGOHM INPUT RESISTANCE.  
ALL VOLTAGE MEASUREMENTS TO BE MADE WITH NO SIGNAL PRESENT AND NORMAL SETTING OF CONTROLS AND CHANNEL SELECTOR SET TO CHANNEL 3 UNLESS OTHERWISE SPECIFIED.  
RESISTANCE MEASUREMENTS SHOWN WITH COILS DISCONNECTED FROM CIRCUIT.  
ALL RESISTORS ARE ±10% TOLERANCE, CARBON, UNLESS NOTED OTHERWISE SPECIFIED.  
CON. RESISTANCE NOT GIVEN UNDER ONE OHM.  
ALL CAPACITOR VALUES IN MICROFARADS UNLESS OTHERWISE SPECIFIED. FOR CAPACITOR TOLERANCE SEE LEGEND.  
CATHODE RAY TUBE END ANODE VOLTAGE TO BE MEASURED WITH ELECTROSTATIC OR FOR OHMS ONLY, PER VOLT HIGH VOLTAGE METER.  
ARROWS ON POTENTIOMETERS INDICATE CLOCKWISE ROTATION.  
○ INDICATES ALIGNMENT & TEST POINT.  
P=PICTORIAL M=MEASURED μ=MICROHERTZ  
F INDICATES ±20% MAY BE USED. ○ INDICATES VOLTAGE SOURCE.  
— INDICATES CHASSIS GROUND. ⊕ INDICATES WAVEFORM CHECK POINTS. (SEE WAVEFORM CHART)  
TEST POINTS:  
A) SOUND SYNC-A.S.C. AMP. B) SOUND OUTPUT C) SOUND A.F. COLLECTOR D) A.C. VOLTAGE  
E) PICTURE DETECTOR OUTPUT F) R-Y GRID OF CRT G) SYNC. SOUND DETECTOR OUTPUT H) SYNC. OF CRT I) A-A.G.C. J) B-Y GRID OF CRT K) 3RD I.F. ALIGNMENT L) SOUND LATER PLATE M) SOUND A.F.C. DETECTOR N) SHORT TEST POINTS O) SHORT TEST POINTS  
R) 1/8 X 1/4 TO OPEN COLOR CHANNEL

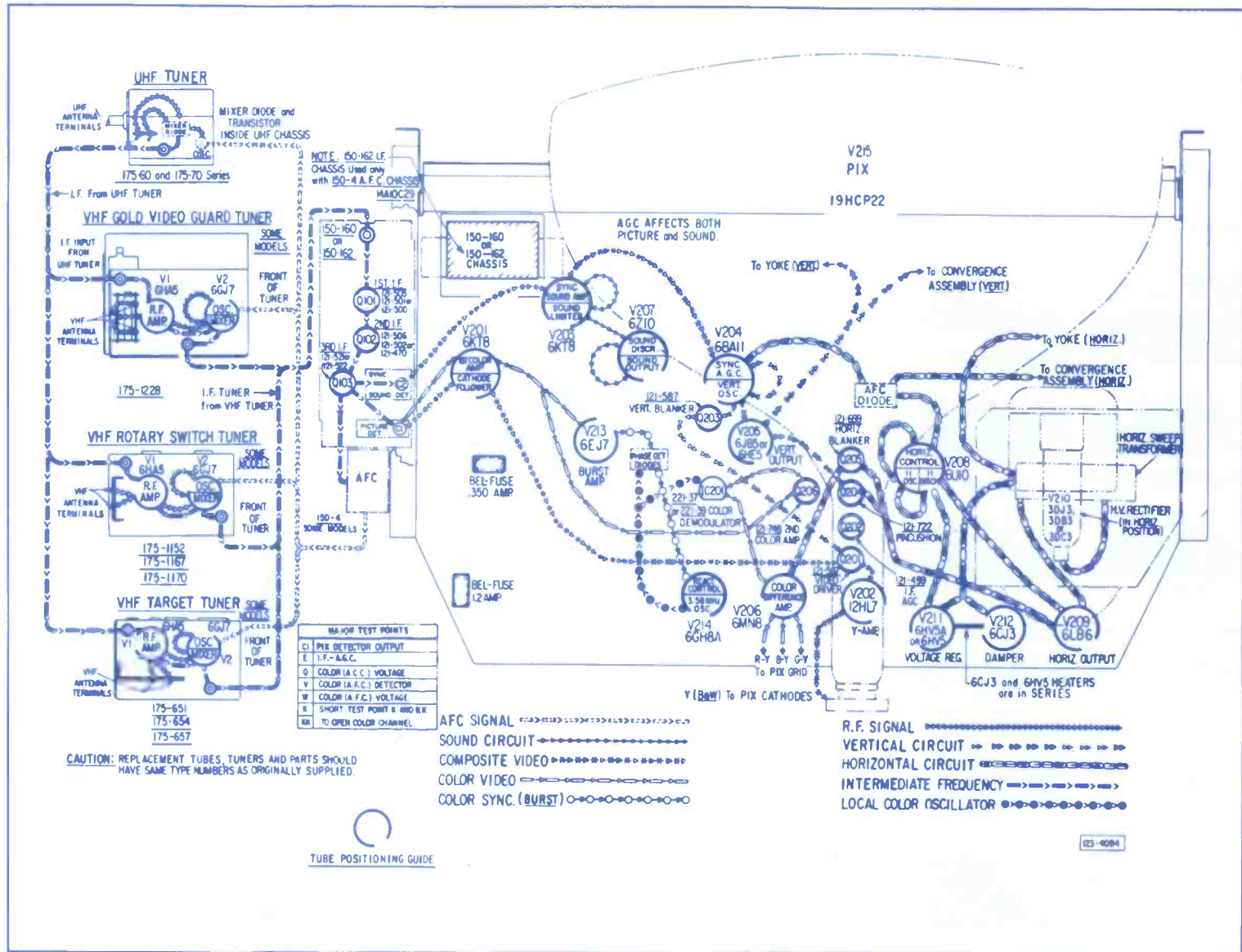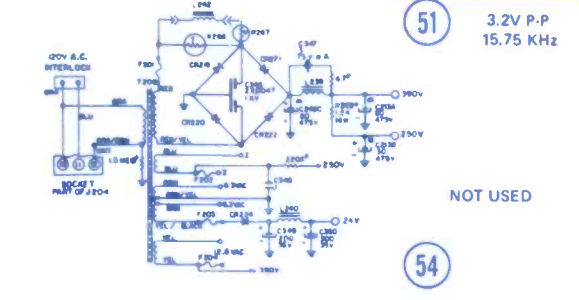

SYMBOL	DESCRIPTION	ZENITH PART NO.
C213A	4μf electrolytic cap 475v	22-5360
C213B	4μf elect cap 475v	22-5360
C213C	80μf elect cap 475v	22-5360
C213D	30μf elect cap 475v	22-5360
C249A	30μf elect cap 475v	22-5513
C249B	10μf elect cap 475v	22-5513
C249C	80μf elect cap 475v	22-5513
R204	3M bright range control	63-7101
R206	500Ω contrast control	63-6980
R214	5M green G1 control	63-6976
R215	5M blue G1 control	63-6977
R216	5M red G1 control	63-6978
R222	500Ω AGC delay control	63-8308
R227	7KΩ AGC level control	63-8235
R229	750KΩ vertical hold control	63-6979
R230	3.5M vert size	63-8443
R231	voltage dependent resistor	63-5058
R233	2KΩ vert lin control	63-6951
R235	10Ω vert centering control	63-7009
R238	250KΩ color killer control	63-8449
R245	750Ω color killer control	63-6950
R246	1M tone buzz control	63-7351
R255	voltage dependent resistor	63-7145
R257	20M focus module control	63-7658
R258	10Ω horiz centering control	63-7211
R260	3M high voltage adjust control	63-8460
R262	voltage dependent resistor	63-8161
R267	voltage dependent resistor	63-7146
R268	therm	63-7346
L202	4.5MHz coil	5-77669
L206	delay line	5-80475
L212	sound take off coil assy	5-77414
L225	intercarrier coil	5-74445
L226	quad coil	5-80480
L227	horiz osc coil	5-56877
L230	horiz efficiency coil	5-77975
L233	burst amp and phase det coil	5-80590
L236	color freq adjust coil	5-66627
L239	filter choke	95-2702
T201	vert output xformer	95-2663
T203	deflect yoke	95-2667
T204	audio output xformer	95-2660
T206	power xformer	95-2748
A201	integrator	87-4
P203	plug, yoke assembly	43-873
F201	1.2a bel-fuse	136-63
F203	.35a bel-fuse	136-75



1310

MAGNAVOX



TV Chassis  
T949 Series

ELECTRONIC TECHNICIAN/DEALER **TEKFA**X

COMPLETE MANUFACTURERS' CIRCUIT DIAGRAMS AND TECHNICAL INFORMATION FOR 5 NEW SETS





JULY • 1970

SYMBOL	DESCRIPTION	MAGNAVOX PART NO.
L101	—47.25MHz trap coil	36C011-2
L103	—peaking coil	36C011-13
L201	—quad coil	36C011-8
L401	—horiz osc coil	36C011-17
T101	—VIF xformer	36C011-3
T102	—VIF xformer	36C011-4
T103	—VIF xformer	36C011-5
T151	—sound take-off xformer	36C011-6
T201	—SIF xformer	36C011-7
T202	—audio output xformer	32C001-1
T301	—vert output xformer	36C011-18
T401	—horiz output xformer	36C011-19
T402	—deflection yoke	36C012-1
C412	—ceramic, 120pf, 10%, 5kv	25X009-1219
C504	—electrolytic, 250uf 200uf 10uf, 180v	27C020-1
R410	—1000, 10%, 2w, metal oxide	23C004-2
R154	—contrast, 20K	22C007-2
R157	—bright, 200K	22C007-3
R209	—vol. (includes switch) 1M	22C007-1
R301	—AGC, 1K	22C007-7
R354	—vert hold, 1.5M	22C007-4
R350	—vert lin, 2M	22C007-6
R360	—height, 500K	22C007-5
Z102	—VIF pac	25C027-1
Z201	—SIF pac	25C027-2
Z203	—SIF pac	25C027-3
Z301	—sync sep pac	25C027-4
Z302	—vert int pac	25C027-5
Z402	—horiz osc pac	25C027-6
Z501	—isolation pac	25C026-1
D101	—germanium diode	53C001-1
D401	—dual diode	53C008-1
D501	—silicon diode	53C005-3
M3	—UHF tuner	34C002-3
M4	—VHF tuner	34C002-2
X501	—2a fuse	18C014-1

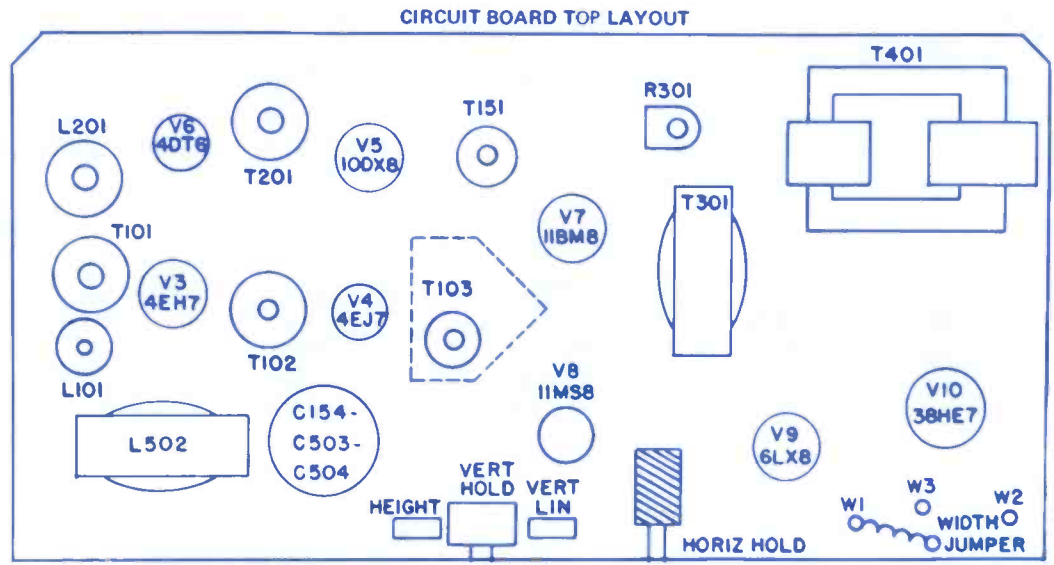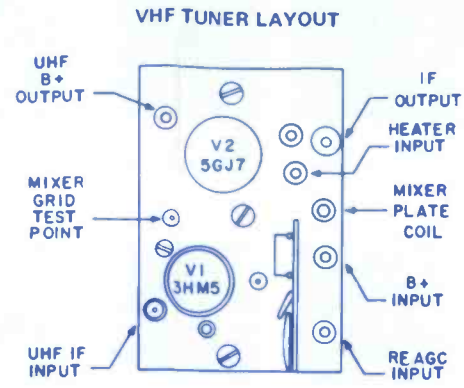


WAVEFORMS

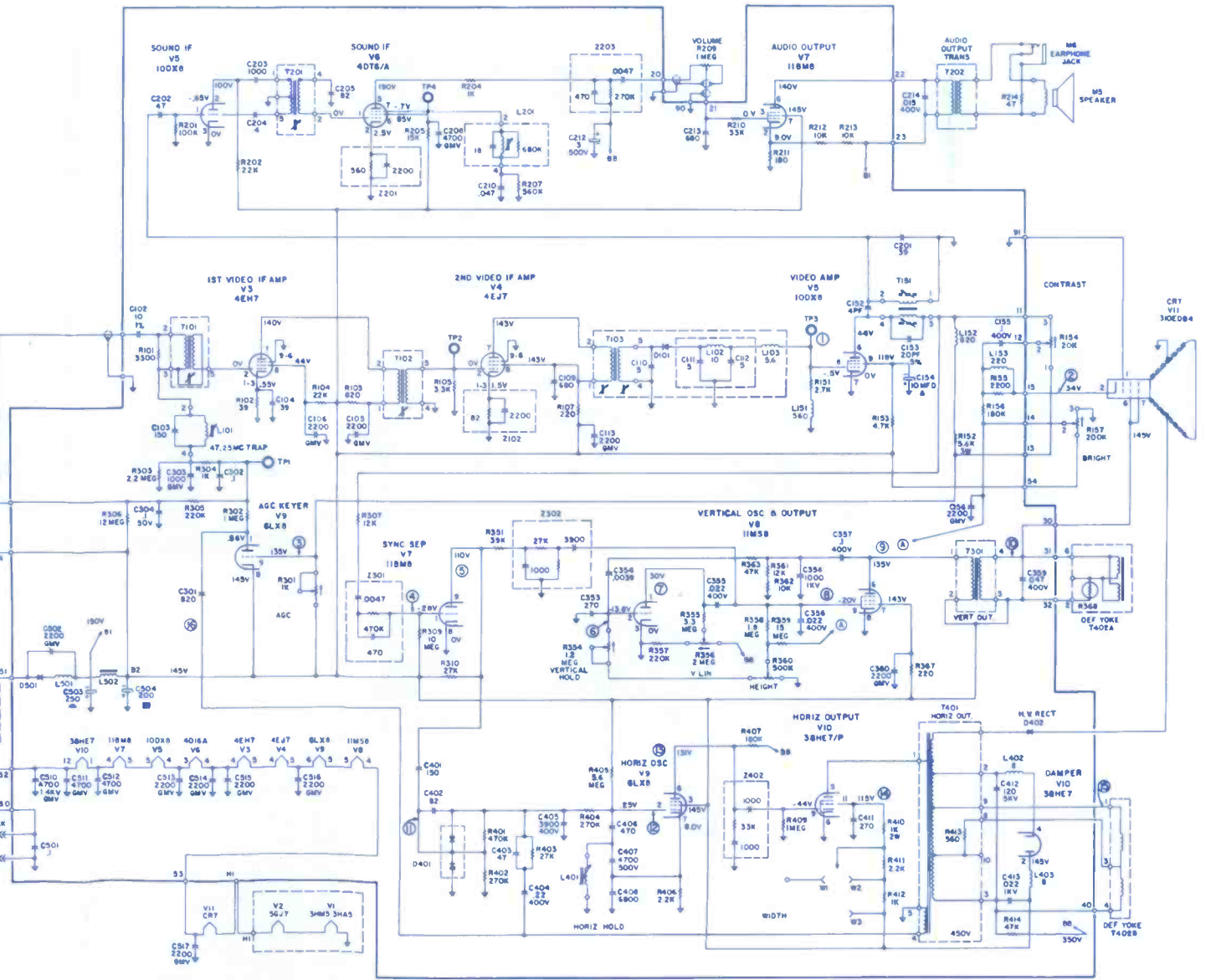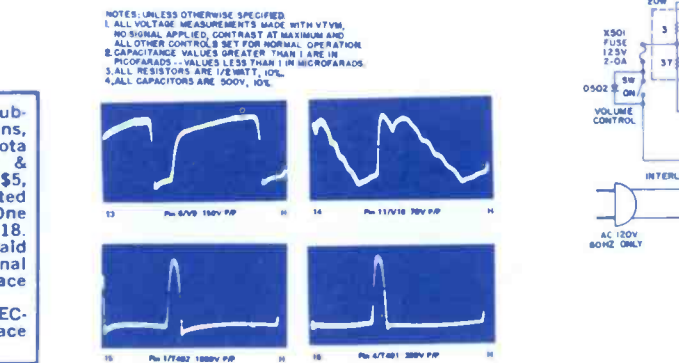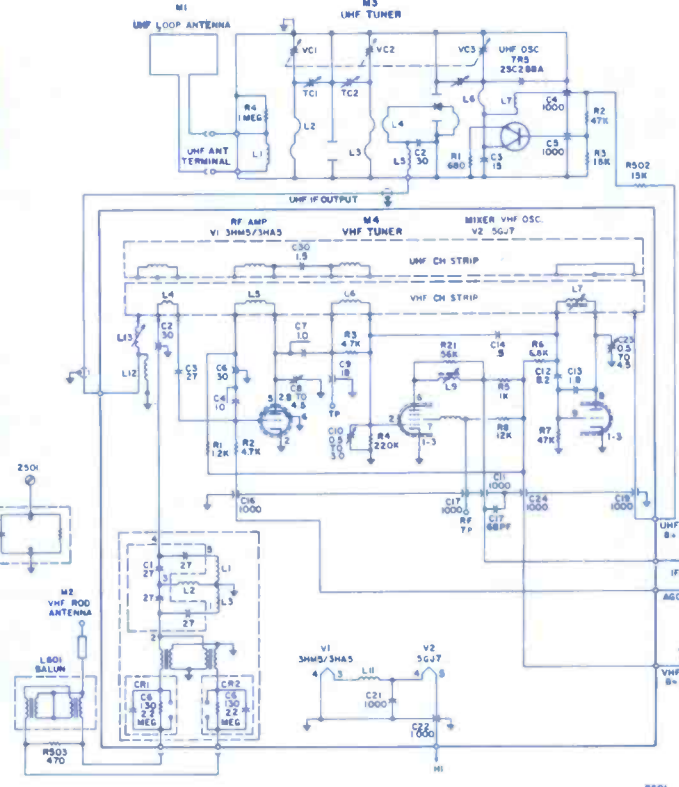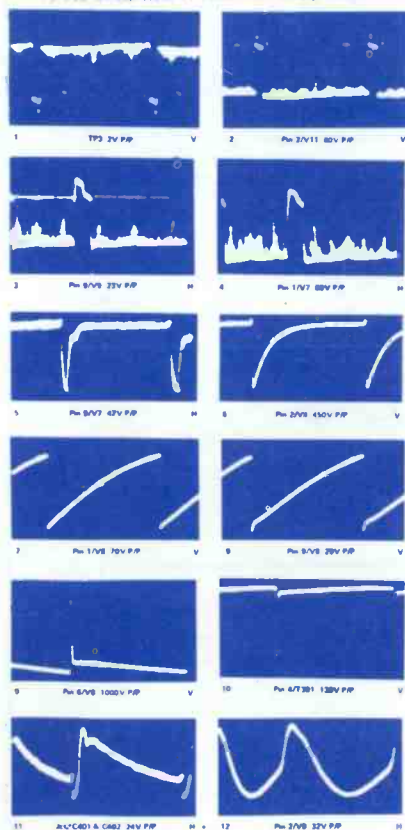Waveforms measured with signal, controls set for normal operation, and 5.5 VDC at TP1.  
V=Vertical Sweep Rate H=Horizontal Sweep Rate



ELECTRONIC TECHNICIAN/DEALER is published monthly by Harbrace Publications, Inc., Harbrace Building, Duluth, Minnesota 55802, a subsidiary of Harcourt, Brace & World, Inc. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: One year \$9, two years \$14, three years \$18. Single copies 60¢. Second class postage paid at Danville, New York and at additional mailing offices. Copyright 1970 by Harbrace Publications, Inc.  
POSTMASTER: Send Form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.



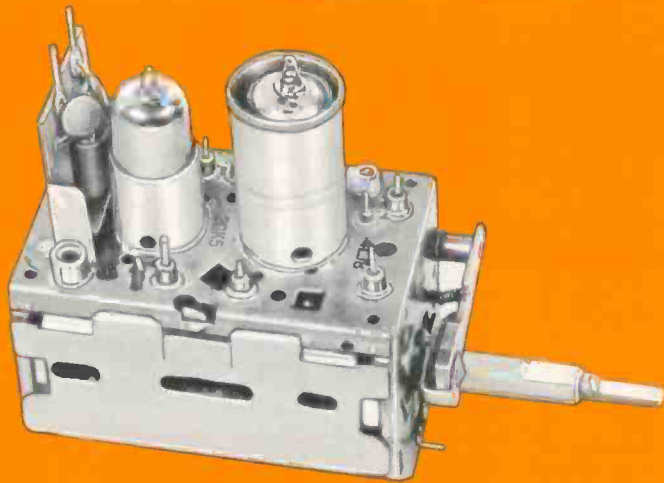

# \$9.75

## TUNER SERVICE CORPORATION

**PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.**

### TUNER REPAIR

VHF Or UHF Any Type \$9.75.  
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our four conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN, INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

### TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the same for every type of universal replacement tuner.

#### Specify heater type

Parallel 6.3V  
Series 450 mA  
Series 600 mA

All shafts have the same length of 12".

#### Characteristics are:

Memory Fine Tuning  
UHF Plug In  
Universal Mounting  
Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



## TUNER SERVICE CORPORATION

**FACTORY-SUPERVISED TUNER SERVICE**

**MIDWEST** . . . . . 817 N. PENNSYLVANIA ST., Indianapolis, Indiana . . . . . TEL: 317-632-3493  
(Home Office)  
**EAST** . . . . . 547-49 TONNELE AVE., Jersey City, New Jersey . . . . . TEL: 201-792-3730  
**SOUTH-EAST** . . . . . 938 GORDON ST., S. W., Atlanta, Georgia . . . . . TEL: 404-758-2232  
**WEST** . . . . . SARKES TARZIAN, Inc. TUNER SERVICE DIVISION  
10654 MAGNOLIA BLVD., North Hollywood, California . . . . . TEL: 213-769-2720  
. . . for more details circle 132 on Reader Service Card



# Crime does pay.

If you're an alert distributor.

Because we are introducing a new product with a suggested retail list of \$89.95 that will sound a warning when it detects an intruder, vandal or trespasser. It's the Mallory Crime Alert<sup>®</sup> ultrasonic intruder alarm.

This new Mallory product is easy to stock—no time consuming installation—no big warehouse space needed. It's bound to be a sure-fire seller because it's so beautifully simple and effective. It gives 24-hour surveillance for homes, offices, stores and plants at small cost and needs no maintenance.

In use, there are no wires, no light beams, no door and window devices . . . just the compact Crime Alert unit itself. Set up in a room or hall, it sends out continuous ultrasonic waves that can't be seen, heard, or avoided. Yet the smallest movement is detected in a split second, activating the built-in alarm and any spotlights, sirens, recorders or other devices plugged into it.

The same type of system is used in the Pentagon to guard the security of top secret areas. It's an item everybody needs today. So put in an order now.

**MALLORY**

**MALLORY DISTRIBUTOR PRODUCTS COMPANY**

a division of P. R. MALLORY & CO. INC.  
Box 1558, Indianapolis, Indiana 46208; Telephone: 317-636-5353

Batteries • Capacitors • Cassette Tapes • Controls **Crime Alert<sup>®</sup>** Resistors • Semiconductors • Sonalert<sup>®</sup> • Switches • Timers • Vibrators

ACTUAL SIZE



... for more details circle 118 on Reader Service Card



**HUGH "SCOTTY" WALLACE**

Publisher

Chicago:

(312) 467-0670

**PHILLIP DAHLEN**

Editor

Duluth:

(218) 727-8511

**JOSEPH ZAUHAR**

Managing Editor

**EMILY WILSON**

Associate Editor

**DEBBIE GOLDBERG**

Production Editor

**BOB ANDRESEN**

Graphic Design

**LILLIE PEARSON**

Circulation Fulfillment

**JOHN KESSLER**

Manager, Reader Services

**BERNICE GEISERT**

Advertising Production

#### OFFICES

757 Third Avenue

New York, N.Y. 10017

Phone: (212) 572-5000

Telex: 01-26286

43 East Ohio St.

Chicago, Ill. 60611

Phone: (312) 467-0670

Telex: 02-53549

1901 West 8th St.

Los Angeles, Calif. 90057

Phone: (213) 483-8530

Harbrace Building

Duluth, Minn. 55802

Phone: (218) 727-8511

Telex: 02-94417

#### MANAGERS

**HUGH "SCOTTY" WALLACE**

Chicago: (312) 467-0670

**DEAN GREENER**

Chicago: (312) 467-0670

**ALFRED A. MENEGUS**

New York: (212) 572-4829

**DONALD D. HOUSTON**

Los Angeles: (213) 483-8530

**ROBERT UPTON**

Tokyo, Japan

I.P.O., Box 5056

**CHARLES S. HARRISON,**

**CY JOBSON**

San Francisco:

(415) 392-6794

**HARBACE PUBLICATIONS, INC.**

**JOHN B. GELLATLY**

President

**RICHARD MOELLER**

Treasurer

**LARS FLADMARK**

Senior Vice-President

**HARRY RAMALEY**

Vice-President

**TOM GRENEY**

Vice-President

**JAMES GHERNA**

Art Director

**EDWARD CROWELL**

Director of Marketing Services

# ELECTRONIC TECHNICIAN / DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

JULY 1970 • VOLUME 91 NUMBER 7

## 43 INTRODUCING EMERSON'S MODEL 26C56 COLOR TV SET

Part I—The receiver's Automatic Fine Tuning Circuit and techniques for troubleshooting its integrated circuit.

## 46 INSTALLING A MOBILE TRANSCEIVER

Pictorial demonstration of techniques used in installing an amateur-band mobile transceiver.

## 50 SERVICING SOLID-STATE STEREO

Part II—The problem of excess audio power, some basic protective circuits and the maintenance of these circuits.

## 54 TESTLAB REPORT

Evaluating EICO's Model 379 Signal Generator and its Model 150 Signal Tracer.

22 EDITOR'S MEMO

60 DEALER SHOWCASE

24 LETTERS TO THE EDITOR

62 CATALOGS AND BULLETINS

30 TECHNICAL DIGEST

64 NEWS OF THE INDUSTRY

32 COLORFAX

66 NEW PRODUCTS

40 PUBLISHER'S MEMO

78 READER SERVICE INDEX

## COVER

Paul and Joe checking out the final adjustments on the Drake TR-4 transceiver that they installed in Paul's 1970 Chevrolet Townsman station wagon. A pictorial account of their installation procedures is given in the article beginning on page 46.

## TEKFAQ • 16 PAGES OF THE LATEST SCHEMATICS • Group 215

GENERAL ELECTRIC: Color TV Chassis N-1

MAGNAVOX: TV Chassis T949 Series

RCA VICTOR: Color TV Chassis CTC43 Series

RCA VICTOR: TV Chassis KCS169X Series

ZENITH: Color TV Chassis 14A9C29/14A10C29




A HARCOURT BRACE JOVANOVIICH PUBLICATION

Harbrace Publications, Inc.



ELECTRONIC TECHNICIAN/DEALER is published monthly by Harbrace Publications, Inc., a subsidiary of Harcourt Brace Jovanovich Publications, Inc. Corporate Offices: 757 Third Avenue, New York, New York 10017. Advertising Offices: 43 East Ohio Street, Chicago, Illinois 60611 and 757 Third Avenue, New York, New York 10017. Editorial, Accounting and Circulation Offices: Harbrace Building, Duluth, Minnesota 55802. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: one year \$9, two years \$14, three years \$18. Single copies: 75¢ in the U.S. and Canada; all other countries \$2. Second class postage paid at Dansville, New York 14437 and at additional mailing offices. Copyright 1970 by Harbrace Publications, Inc. POSTMASTER: Send form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.



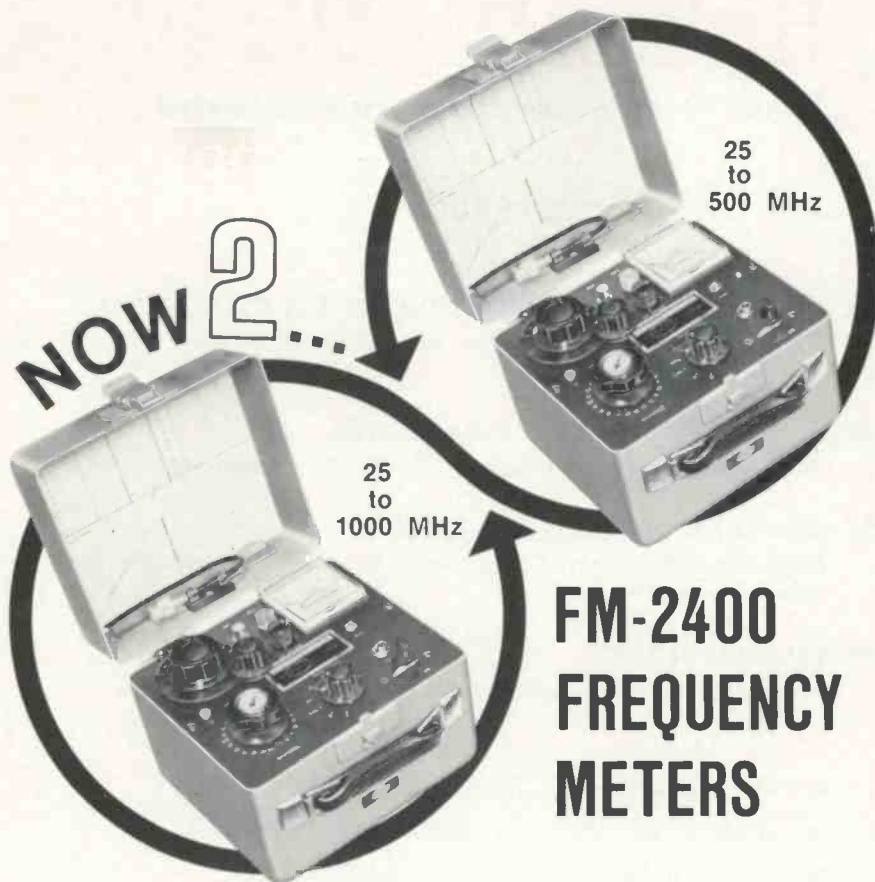

## FM-2400 FREQUENCY METERS

### FM-2400CH (New)

- Tests Predetermined Frequencies 25 to 1000 MHz
- New Extended Range Covers 950 MHz Band
- Pin Diode Attenuator

### FM-2400C

- Tests Predetermined Frequencies 25 to 500 MHz

The new FM-2400CH and the FM-2400C provide an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies. The FM-2400CH with its extended range covers 25 to 1000 MHz. The Model FM-2400C covers 25 to 500 MHz. The frequencies can be those of the radio frequency channels of operation and/or of the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability:  $\pm .0005\%$  from  $+50^{\circ}$  to  $+104^{\circ}\text{F}$

Frequency Stability: with built-in thermometer and temperature corrected charts.  $\pm .00025\%$  from  $+25^{\circ}$  to  $+125^{\circ}$  (.000125% special 450 MHz crystals available)

Both the FM-2400CH and the FM-2400C are self contained in small portable cases. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only).....	\$595.00
RF crystals (with temperature correction).....	24.00 ea.
RF crystals (less temperature correction).....	18.00 ea.
IF crystals.....	catalog price
FM-2400C (meter only).....	\$445.00
RF crystals (with temperature correction).....	24.00 ea.
RF crystals (less temperature correction).....	18.00 ea.
IF crystals.....	catalog price

Write for catalog



CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102

... for more details circle 116 on Reader Service Card

Everyone seems to have an eye on the stock market—even many of us without money to invest. And the frequent downward trends observed have been a cause of great concern.

This threat of a coming depression has also been reflected in the sudden drop in color-TV sales. At least one major manufacturer has closed down its color picture tube plant, laying off virtually all plant employees. Newspaper accounts tell of other manufacturers laying off hundreds and then thousands of employees.

Does such talk of gloom mean that we should close shop and prepare to stand in food lines, as did many well trained men during the depression of the 1930's? Quite the contrary.

Although an economic recession may result in reduced income from the sale of consumer electronics, this simply means that more people will be having their radios, TV sets and phonographs repaired rather than replaced—and for many of you, electronic maintenance is where the money is.

Instead of preparing to give up, electronic technicians should be “boning up” on their basic tube and transistor circuits so that they can handle these increased work loads with greater efficiency—resulting in even greater profits as the economy declines.

ELECTRONIC TECHNICIAN/DEALER will continue to provide you with technical articles, written to supply you with the information needed for effective servicing. This will be done with the many original articles that Joe Zauhar and I plan to write, supplemented with any service tips that you, the reader, can provide.

We are always interested in learning what you are doing. And if you feel inclined to send us details concerning some helpful or unique servicing techniques that you have developed (with sketches or photos), we are interested in publishing this material as a feature article. You need only supply us with a clear explanation of what you have been doing—stating specifically your interest in the material being used as a feature article on a free-lance basis—and we will be glad to rewrite it, as necessary, paying you for your efforts.



*Phillip Dahlen*



To the planners  
of those companies  
who will build new  
offices totalling  
\$11,500,000,000  
in 1970.



**MASTERCOM™ M100**  
World's most  
efficient intercom...  
easiest to install!

When you call in your architect, it's time to consider the Norelco Mastercom M100. This new intercom system now sets the standard for modern internal communications. It offers instant hands-free operation . . . assured privacy of conversations . . . and superb voice reproduction. Matching handset also available.

Installation is simplified, using a single 8-pair cable and noiseless all-electronic control pack, only 3.1 cubic feet *small*. The handsome rosewood stations can be easily relocated without rewiring. And the system allows for unlimited expansion.

A Norelco specialist will gladly survey your intercom needs and supply facts on costs and savings. Call him today. See the yellow pages under "Intercommunication Equipment" or mail coupon today.

**Norelco®**

PHILIPS BUSINESS SYSTEMS, INC.  
A NORTH AMERICAN PHILIPS COMPANY

100 East 42nd Street, New York, N. Y. 10017

Gentlemen:  
Please send full details on the  
Norelco Mastercom M100

Company Name \_\_\_\_\_

My Name \_\_\_\_\_

Street Address \_\_\_\_\_

City, State \_\_\_\_\_ Zip \_\_\_\_\_

ETD-770

DICTATION EQUIPMENT • MASTERCOM SYSTEMS • ELECTRONIC PRINTING CALCULATORS • OFFICE COMPUTERS

. . . for more details circle 119 on Reader Service Card




# FAST

## COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(90 Day Warranty)

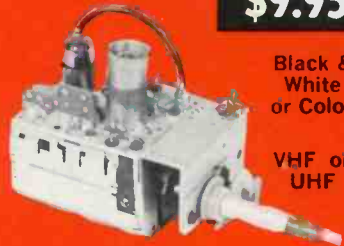(WE SHIP C.O.D.)  
YOU PAY SHIPPING  
**\$9.95**



Black &  
White  
or Color

VHF or  
UHF

### UV Combos \$16.50

Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner.

When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

All tuners must have remote control units and/or mounting brackets removed before tuner can be cleaned and repaired. Please remove these accessories before shipping, as we will not be responsible for loss or damage.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURER'S SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

## GEM CITY TUNER REPAIR SERVICE

Box 6D Dabel Station  
2631 Mardon Drive  
Dayton, Ohio 45420

## ET/D LETTERS TO THE EDITOR

### Comments on Articles


I would like to bring to your attention an error in the May 1970 issue of *ELECTRONIC TECHNICIAN/DEALER*. In the article entitled "Electronic Depth Finders" it was stated in the calibration of the dial that the time it took the pulse to reach bottom was 50 times 0.000208 or 0.0104 sec. It was then erroneously stated as 104ms. The figure should have been 10.4ms.

I would like to take this opportunity to say that I find the articles in *ELECTRONIC TECHNICIAN/DEALER* interesting and knowledgeable.

RALPH E. MACLEOD

I am writing concerning the comments of Ronald B. Lorbecki in April 1970's "Letters to the Editor." I agree with him 100%, however I feel a note of caution should be voiced.

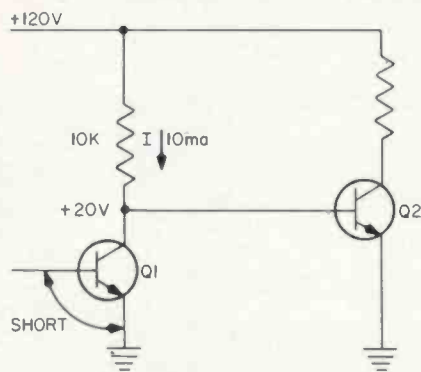In short, it is not always okay to short the base to the emitter of a transistor. I have noted a number of cases where the collector supply is dropped from a high voltage source. Removing forward bias will do two things: the collector voltage will rise, thus produc-



ing "punch through" in the transistor. If the transistor in question is directly coupled to the base of another stage, it will probably "fail" that transistor too.

I enclose a diagram to illustrate.

VICTOR CASTENS

In reading the article on selling CCTV in your March 1970 issue, I noticed that it said (page 50) to pass the Q-Tip past the head in an up-and-down motion.

I am an owner of a Sony CV-2200A, and the owner's manual and service manual say to press the tip of the cleaner lightly against the head and clean by moving the tip horizontally. I have talked to the Sony tech-

nicians in Tokyo, and they say that cleaning the rotary heads vertically can cause them to get out of alignment.

Always check the service manual to see how the heads are to be cleaned. Not all are cleaned the same way.

TERRELL E. MARKLAND

A few years ago you ran an article on garage door operators. It sounded good to us. Now we are distributor in Boca Raton for the Alliance garage door operators. We do quite a service business in all makes of control units. Anything too complicated we send back to the factory. Most of them just need new tubes and alignment, which is no problem. Transistorized ones we haven't gotten so involved in outside of open filters in the Alliance.

This is just to let you know that your articles don't go unnoticed.

GERALD VANCE ELECTRONICS

I have just read your article on servicing cassette recorders by Homer Davidson.

I would like to say that I feel it was an excellent article.

Should you ever run an article on auto-tape players, this may be of interest to you:

Most of my friends and myself, who have auto-tape players, usually leave our tapes in the car—under the seat or in the trunk. I have found that when it is cold outside the tapes will tend to bind up or play slower than normal, indicating a tight or loose pulley drive. I feel that they must be kept at a reasonable temperature.

FRANKLIN ROBINSON

I read your article "Color Service Case Histories" with great interest. Would you consider repeating it more often and perhaps cover equipment other than TV sets?

The article showed the technique of the technician's trouble shooting process, which can be added to my own store of experiences as indelibly as if I had done it myself.

Very clear shop talk like this really stays with me. Thanks a lot.

PAUL P. WATSON

I have now been a subscriber to *ELECTRONIC TECHNICIAN/DEALER* for almost two years, and I have only praise for the good work that your staff does in keeping myself and other service technicians up-to-date on electronics. I have read letters that have been quite critical of the material that you have printed. As for myself, I en-



Do you choose capacitors  
the same way  
Fran French and Lew Russell do?

Then you're sure to pick  
Sprague Twist-Lok<sup>®</sup> Capacitors when  
you need twist-prong electrolytics.

Fran French and Lew Russell keep everything humming smoothly at Delaware Valley TV Service, Philadelphia, Pa. Fran, as Gen. Mgr., and Lew, as Shop Mgr., have had a lot to do with building this 13-man organization's reputation as specialists in color TV. With 20 years' TV servicing experience apiece, Fran and Lew agree about many things. One is twist-prong electrolytics. Both prefer Sprague Twist-Lok Capacitors for reliability and availability.



Ask your Sprague distributor for a copy of Sprague's Electrolytic Capacitor Replacement Manual K-109 or write to: Sprague Products Company, 65 Marshall St., North Adams, Mass. 01247.

**P.S. You can increase your business 7½% by participating in EIA's "What else needs fixing?" program. Ask your distributor or write to us for details.**





joy reading all of the articles, even the ones slightly over my head or, I should say, slightly out of my line of work.

One of the articles I especially liked was "The CAT Game." In my opinion, an article of this nature would be helpful and of interest to any technician in the service business. I would like to see more articles of this nature.

I would like to see more articles like "Stereo Servicing with a Scope" which appeared in March and April issues.

JOHN L. DANTZLER

#### Information Needed

I have a Gray 50w power amplifier, Model AM-50, manufactured by the Gray Research and Development Co., Inc., of Manchester, Conn. I need a schematic in order to repair it.

I wrote to the manufacturer and my letter was returned, stamped removal order expired. Would you have information about whether or not this com-

pany is still in business? If so, let me have their present address; and if they are out of business, could you tell me how I could obtain a schematic for the above amplifier.

THOMAS GRAHAM

RADIO TV REPAIR SHOP  
BOX 366 TC  
BRIDGEWATER, MASSACHUSETTS 02324

I would appreciate it very much if some reader would loan me a manual for a DuMont 304-A Oscillograph, which I would photocopy and return.

I also need to copy the manual or schematic for Webcor Tape Recorder Model No. EP2711-1.

Perhaps I can return the favor.

R. L. TROTT

1690 SHARKEY STREET  
TALLAHASSEE, FLORIDA 32304

## Here's The ONLY ONE You Can Grip and Release With ONE HAND



Patented E-Z Cushion Grip Release OUTSIDE The Handle. Close Jaws With One Hand ... Release Jaws With SAME HAND.

# TOG-L-LOK

USE IT AS A PLIER... AS A WRENCH... AS A CLAMP

Here it is! The ONLY multi-purpose plier/wrench you can work with one hand. Finger-squeeze the handles to lock jaws onto the work... WITH THE SAME HAND, finger-trip the release lever to open the jaws. Simple, fast, efficient.


Only TOG-L-LOK gives you the release lever where it belongs: OUTSIDE the lower handle. Easy to get at. No chance of pinched finger. No snap-sting when you

trip the lever (it's plastic cushion-coated).


All this PLUS well-known CHANNELLOCK quality. Jaws drop forged of high grade steel. Heat treated rite-angle teeth for most efficient bite. Black oxide finish resist rust and corrosion.

Look For... Ask For TOG-L-LOK At Your Tool Supplier.

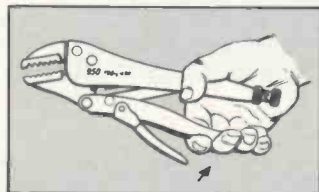Complete Catalog Information Is Yours For the Asking... Write Us.



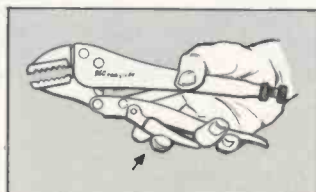Finger-tip Lock Tool Onto Work With One Hand And Then...



WITH THE SAME HAND... Finger-tip Release It.

TOOLS BY  
**CHAN-NEL-LOCK**

MEADVILLE, PA.

... for more details circle 103 on Reader Service Card

The May article about MATV cables written by Robert Sharp and Paul Miller was a really good one.

When I recently installed some shielded twin lead it occurred to me that the shield should be terminated. However, my search for this information has been fruitless. I have asked several technical people and their replies are not positive.

I should appreciate hearing from you.

E. W. BLAU

*The twin lead shield should be grounded in the same manner as the antenna mast. Ed.*

I have been an avid ELECTRONIC TECHNICIAN/DEALER reader for years, and I wish to commend you for all the service you have given me in the past through your magazine. Keep up the good work!

Recently I was given a Timex record-making and phono player Model No. 40-1. It is in very good condition. I wrote to Timex, and they were very good in answering. But they do not have parts or the disc to make recordings. Now my big question is where can I get these discs?

I hope you or your readers can help me.

ANTHONY BOCHICHO

45 ANDREWS STREET  
STATEN ISLAND, NEW YORK 10305

#### Items Free and For Sale

I have an excellent service business on a four-lane boulevard in northeast Florida's oldest city St. Augustine. Fine people, climate, business; and excellent fishing.

My shop is fully stocked with up-



# Have you tried our canned tuner?

It's not only great for color television sets, it's also great for guided missiles.

As a matter of fact, Krylon® Tuner Cleaner is made with the same solvent used in the missile industry. Plus a special lubricating oil.

Just one little spray leaves a thin, non-drying film of lubricant that conditions contact surfaces and protects them from corrosion.

And that same little spray keeps surfaces self cleaning and water repellent without ever harming any plastic surface.

Krylon Tuner Cleaner also comes with a plastic tube for controlled spraying in hard-to-reach areas.

Try it just once. You're sure to develop a taste for it.



Krylon Coatings—from the makers of Elmer's® Adhesives and Mystik® Tapes.



... for more details circle 102 on Reader Service Card



# passivated rectifier

GE-509



- Up to 1000 volts PIV
- Transient Voltage Protection
- Passive Junction
- All Diffused Structure
- High Surge Current Capacity
- Hermetically Sealed
- Dual Heat Sink Design
- Low Thermal Impedance

#### applications:

- Free-Wheeling Rectifier
- TV and Radio Power Supplies
- Time-Delay Circuits
- Communications Equipment
- Power Logic Circuits
- SCR Trigger Circuits
- ARC Suppression
- Small Portable Appliances
- Battery Chargers
- General Purpose Power Supplies
- TV Damper Diodes
- Low Level Limiters

your authorized  
GE distributor can  
fill all your  
entertainment  
semiconductor  
requirements

TUBE DEPARTMENT  
OWENSBORO, KENTUCKY

GENERAL  ELECTRIC

... for more details circle 110 on Reader Service Card

ET/D

## LETTERS TO THE EDITOR

to-date parts and instruments. The property is available as a whole: the lot (100 ft by 96 ft), the building and a large parking area. Full particulars will be given on request.

I have enjoyed your magazine for a great many years. I think it is tops in the field.

W. C. POPE

POPE'S RADIO & TV SERVICE  
312 ANASTASIA BOULEVARD  
ST. AUGUSTINE, FLORIDA 32084

I have the Sarns Photofact Albums listed by number: 46, 47, 70, 85, 87, 100, 113, 132, 171, 179, 184, 189, 199, 223, 227, 234, 237, 245, 249, 258, 277, 282, 283, 284, 286, 291, 300, 307, 322, 354. I will give them to anyone who sends a postpaid envelope, or I will provide more detailed information on what models are covered in each album.

MRS. FRED MAGNUS

7403 MAPLE AVENUE  
TAKOMA PARK, MARYLAND 20012

I would like to let you know how much I enjoy reading *ELECTRONIC TECHNICIAN/DEALER*. It is one of the best trade magazines available. Keep up the good work.

I have for sale Riders Television Manuals Volumes 1 through, and including, Volume 27, also four volumes of RCA Victor Service Data. These cover RCA radios from 1923 to 1948.

No reasonable offer for the volumes will be refused.

BILL METZ, JR.

Metz TV Sales and Service  
Box 362  
Augusta, Wisc. 54722

I want to take this opportunity to express my appreciation for the informative service articles you publish in *ELECTRONIC TECHNICIAN/DEALER*. Since I am a young technician just out of technical school and only in business for a short time, I appreciate all the experience I can pick up. Since working with an older technician is not possible, I appreciate the tips passed on in your journal.

I would like to make available to other readers the following used equipment that I have for sale: I have a B & K color analyst 850, a Hickok 191X RF generator and a Gertsch FM-3 frequency meter. If any readers are interested or would like to make

an offer on these pieces of gear, they can contact me.

R. D. ZAGRABELNY

Route 4  
Marshall, Mo.

### Overwhelming Response

Thank you for printing our request for schematics in the Readers' Aid Department.

Directly above our request was a letter headed "Overwhelming Response."

We have received a tremendous number of replies and copies of the information we requested, so our experience has been the same as that of Mr. Watkins.

Please pass on our thanks to all of those who responded. It is encouraging to realize that people in the electronics service industry are so willing to help one another. Once again, our sincere thanks to you and our fellow readers.

G. M. BOYES

### Helpful Suggestion

Two points always present in alignment instructions for TV IF stages are:

- Disable the oscillator section of the mixer-oscillator.
- Connect the high side of the signal generator to the ungrounded tube shield over mixer-oscillator tube, low side to ground.

There is no such thing anymore as a removable tube shield over the mixer-oscillator tube, so how is it possible to replace it with an ungrounded shield?

I made an insert from a width control sleeve, which is used between the yoke and the neck of some picture tubes, to insert between the present grounded tube shield and the tube. The high side of the generator can then be connected to the extended portion of this insert with a cliplead or alligator clip.

The most common way to disable the oscillator section of the mixer-oscillator tube is to cut off a tube prong of a good tube. This is expensive, and the dehorned tube should be kept for the next job using the same type of tube. Why not ground the control grid of the oscillator section or connect it to the oscillator cathode if, as in some cases, the cathode is grounded?

In lieu of all this, why doesn't the test instrument manufacturer provide for accomplishing these things with the equipment?

Perhaps if you print this the manufacturers will do something about it.




GEORGE W. THOMPSON



Precision Tuner Service  
 gives you  
**profit power**  
 ..with even  
 finer, faster,  
 Service!

WE HAD JUST REPRINTED OUR LITERATURE . . .  
 ADDING OUR THIRD NEW PLANT . . .  
 WHEN WE DID IT AGAIN . . . PRECISION TUNER SERVICE

**ADDS**

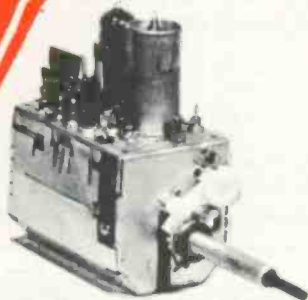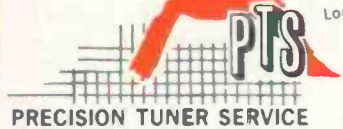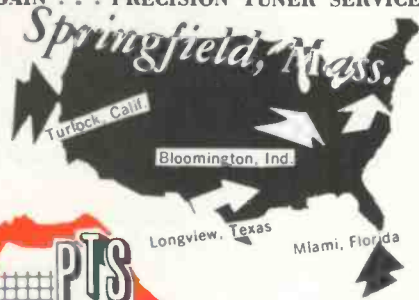

**does  
 its  
 thing**



**..again!**

YOU can offer this specialized, expert service. Quality Tuner Service is our bag, man! Experienced, conscientious PTS craftsmen with sophisticated, precision (and expensive) tools and equipment mean faster PROFIT for you with PTS 8-hour service. . . .

**For YOU:  
 MORE &  
 FASTER  
 PROFIT**

**TURNOVER**

. . . . No doubt about it! PTS mails your tuner back the SAME DAY it is received! Now less in-transit time, too!

**8 Hr.  
 Service**

. . . and  
 now with  
 even  
 shorter  
 in-transit  
 time!

VHF or  
 UHF  
**\$8.95**  
 UV Combo's  
**\$14.95**  
 Major Parts, Tubes,  
 Transistors  
 charged at Net Price

**Precision  
 Tuner Service**

FREE JOB CARDS FREE SHIPPING LABELS

**CUSTOMIZED REPLACEMENTS AVAILABLE  
 FOR \$12.95 UP (NEW OR REBUILT)**

FIRST TO OFFER 365-DAY GUARANTEE!  
 COLOR — BLACK & WHITE — TRANSISTOR TUNERS — ALL MAKES  
 GUARANTEED COLOR ALIGNMENT — NO ADDITIONAL CHARGE

For fastest service, send faulty tuner with tubes, shields and all broken parts to:

HOME OFFICE—Box 272—Bloomington, Ind. 47401	Tel. 812/824-9331
EAST—Box 334—W. Springfield, Ma. 01089	Tel. 413/734-2737
SOUTHEAST—4451 N.W. 37th Ave., Miami, Fla. 33142	Tel. 305/633-0002
SOUTHWEST—Box 7332—Longview, Tex. 75601	Tel. 214/753-4334
WEST—Box 1431—Turlock, Calif. 95380	Tel. 209/632-2928

. . . for more details circle 120 on Reader Service Card



The material used in this section is selected from information supplied through the cooperation of the respective manufacturers or their agencies.


## RCA VICTOR

Color TV Chassis CTC42XR—Remote On/Off and Channel Functions

The CTC42XR remote control system uses an integrated circuit preamplifier and transistor driver stage (PW900) to amplify ultrasonic command frequencies emanating from the CRK13 four-function remote hand unit. The amplified signals of the PW900 are applied to the primary of driver transformer T1101, located on the PW1100 remote board. The secondary voltages of this transformer drive tuned circuits that trigger the appropriate controlled functions.
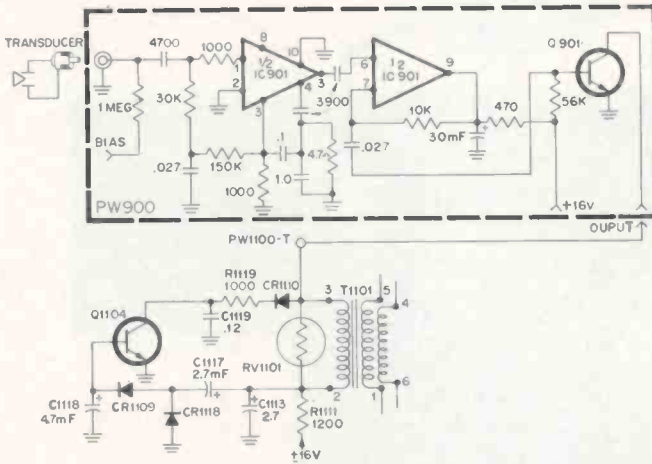
### Noise Immunity Circuit

Shown in the illustration is the noise immunity circuit, transistor Q1104, that serves to minimize the possibility of the remote circuits being triggered by extraneous noise




pulses, such as jingling coins, etc. Under normal conditions (when a valid remote signal is processed through the system) a steady dc voltage proportional to the amplitude of the ultrasonic signal will be developed across capacitor C1113. The noise immunity transistor (Q1104) is inactive at this time because it has no base current. When noise pulses occur, the voltage at C1113 will vary in relationship to the low-frequency amplitude changes of the noise. An ac signal appears at this point and is coupled through a capacitor, C1117, to be rectified by diode CR1109. The rectified ac produces a dc charge on capacitor C1118. When this noise-induced voltage exceeds approximately +0.6 to +0.7v, transistor Q1104 is biased into conduction. The load across the primary of transformer T1101, caused by the conduction of transistor Q1104 (through CR1110 and R1119), reduces the T1101 secondary voltage sufficiently to preclude erroneous remote control operation.

An additional component—voltage dependent resistor (RV101)—serves to limit the amplitude of the pulse on the collector of the driver transistor (Q901) to prevent breakdown.
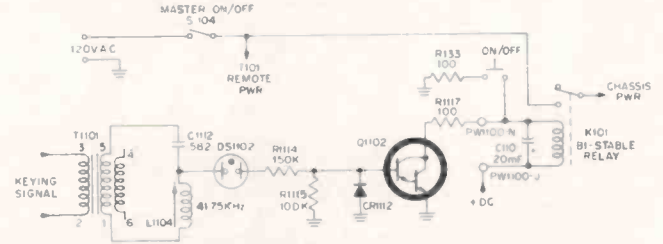
### Function Circuits Operation

The On/Off circuit responds to a 41.75kHz command


signal—as shown in the illustration. When a signal of that frequency appears across the series resonant circuit, consisting of capacitor C1113 and coil L1104, a neon bulb (DS1102) is ignited and acts as a low resistance path to



the base of a Darlington transistor, Q1102. Base current for this transistor is provided by the positive portion of the signal voltage obtained from the resonant circuit—through the conducting neon bulb and current limiting resistor, R1114 (150K). Diode CR1112 serves to conduct the negative portion of the signal voltage to ground.

The Darlington transistor is actually two transistors connected so that the individual betas of the transistors are compounded. This compounded transistor has an amplification capability (beta) of 1000 or more. A small base current at its input produces substantial collector current. The collector circuit of Q1102 controls a bi-stable relay (K101), which is powered from the -35v remote power supply that remains operative while the instrument master switch is on.

When the receiver is remotely turned ON, the Darlington transistor conducts, causing the bi-stable relay contacts to latch closed to complete the 120vac power circuit to the chassis. When the receiver is turned OFF, the bi-stable activates and latches to the OFF position. Manual ON/OFF is provided by a "push-push" switch on the front panel, which completes the ground path for the bi-stable relay by means of resistor, R133, a 100Ω resistor.

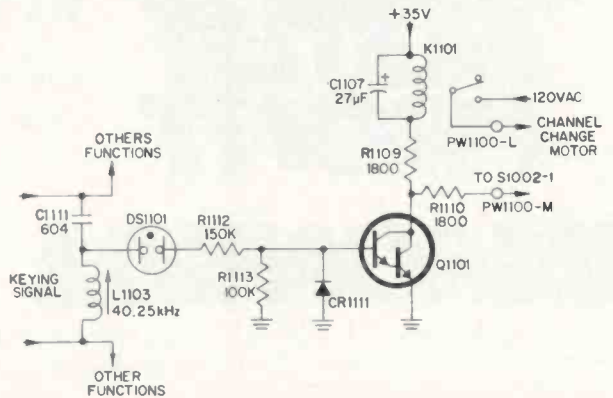

Remote Channel-Change, shown in the second illustration, is accomplished in a similar manner. The channel-change circuit responds to 40.25kHz signal. This causes Darlington transistor Q1101 to conduct, closing the contacts of the channel-change relay (K1101) to apply 120vac to the channel-change motor. Once the motor is activated by depressing the channel-change button on the remote hand unit (see illustration), the pull-in engagement of the

*continued on page 64*







# COLORFAX

by JOSEPH ZAUHAR

The material used in this section is selected from information supplied through the cooperation of the respective manufacturers or their agencies.

## GENERAL ELECTRIC

### Color TV Chassis C-1—Troubleshooting "No High Voltage" Problems

"No High Voltage" problems in C-1 chassis receivers can be easily solved if a systematic troubleshooting procedure is used and one important point is remembered.


The point to remember is that the drive signal to the horizontal output tube grid cannot be measured with a dc voltmeter. The dc grid voltage is a combination of the voltage produced by grid rectification of the drive signal, and the feedback voltage developed by the high-voltage regulation system. A fault in the horizontal output stage may result in less feedback voltage and consequently less dc voltage on the grid. Therefore, using this dc voltage as a measure of drive signal can lead to false conclusions.

The easiest troubleshooting method is to systematically isolate the horizontal output stage from its various load circuits, making use of the plugs and sockets incorporated in the receiver design. During this procedure, connect a high-voltage meter to the CRT second anode to continuously monitor the high voltage. If disconnecting a component restores the high voltage, the trouble is obviously in that component or its associated circuitry.

### Troubleshooting Procedure

- Change the tubes; V10, horizontal output; V11, damper; V13, HV rectifier.
- Disconnect the CRT socket. This checks the possibility of a shorted CRT. Leave the CRT socket disconnected while performing the following step. Otherwise, should the high voltage be restored with the yoke disconnected, the undeflected beams may permanently damage the CRT screen.
- Disconnect the yoke plug. With the yoke and CRT disconnected, the normal high voltage is 10 to 12kv. The boost voltage will remain normal at 750 to 860v. If the trouble is not in the yoke, reconnect the yoke, and CRT.
- Disconnect the convergence plug. If the problem is in the convergence assembly, all voltages will return to normal.
- Check the drive voltage to the horizontal output tube

*continued on page 38*

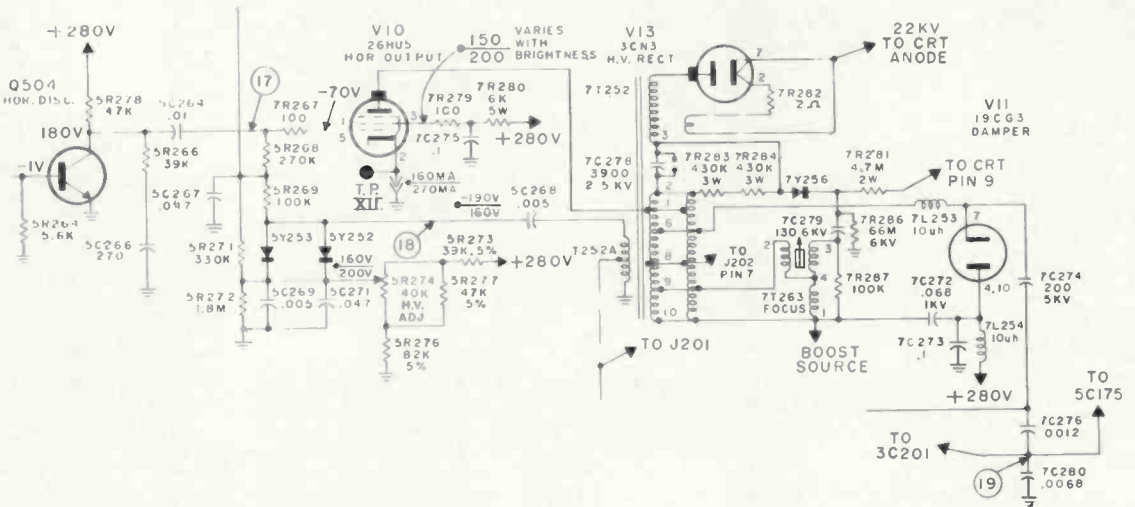

CONDITION	HORIZONTAL OUTPUT SIGNAL GRID P-P VOLTS	HORIZONTAL OUTPUT SIGNAL GRID DC VOLTS	HORIZONTAL OUTPUT SCREEN GRID DC VOLTS	B+ BOOST VOLTS	HV, CRT SECOND ANODE	FOCUS VOLTS	JUNCTION 5C268 T252A, P-P VOLTS
Normal receiver	270	-70	150 to 200	740	22kv	4kv	560
Convergence plug disconnected	280	-82	155 to 200	680	20kv	4kv	560
Yoke plug disconnected	250	-54	70 to 75	860	10 to 12kv	3kv	380
Focus coil and rectifier disconnected	270	-76	160 to 200	725	25kv	68v	580
Junction 5C268, T252A shorted to chassis	220	-44	90	625	20kv	5kv	0
5C268 open	240	-46	90	720	26kv	4.5kv	600
5C268 shorted	240	-46	90	700	26kv	4kv	600
7C280 shorted	270	-88	160 to 200	750	22kv	4kv	560
7C276 shorted	270	-74	155 to 200	700	22kv	4kv	520

# Now there is a better Color-Bar Generator for your servicing work



## THE RCA WR-502A.

New . . . solid state . . . battery or AC operated . . . portable, weighing only four pounds.

The RCA WR-502A "CHRO-BAR" color-bar generator provides *six* separate test signals: color bars, dots, cross-hatch, vertical lines, horizontal lines, and blank raster.

The sound carrier, pattern, RF output, and color subcarrier are all crystal controlled. Designed for exceptional stability with no flicker.

Included as part of the package — at no extra cost — is an AC adaptor for line operation. This unit was formerly available only as an accessory at a cost of \$9.00\*.

The new CHRO-BAR Generator WR-502A, complete with separate AC adaptor — now only \$148.50\*.

RCA Electronic Components,  
Harrison, N. J. 07029.

\* Optional Distributor resale price.



. . . for more details circle 123 on Reader Service Card



# InfoMetrics<sup>®</sup> introduces a bold new concept in information gathering

InfoMetrics is the marketing and research service of Harcourt Brace Jovanovich Publications. Originally set-up to qualify magazine subscriptions using economical wide area telephone service (WATS), InfoMetrics now is equipped to offer a wide-range of market research and information services to the business community.

As a special marketing service to our readers and advertisers, InfoMetrics is available to fulfill your research and marketing requirements *quickly* and *economically*. Each survey will be tailored to meet your needs. Whether your research needs call for a telephone survey, a mail questionnaire, or a combination of both, InfoMetrics can provide you with any type of information with professional competence. These are just some of the areas:


- |  |   |
|--|---|
| <input type="checkbox"/> product testing   | <input type="checkbox"/> media research         |
| <input type="checkbox"/> brand recognition | <input type="checkbox"/> advertising evaluation |
| <input type="checkbox"/> attitude survey   | <input type="checkbox"/> test marketing         |
| <input type="checkbox"/> buying influences | <input type="checkbox"/> inquiry qualification  |

**For more information about InfoMetrics  
and a copy of our informative  
brochure write or telephone:**
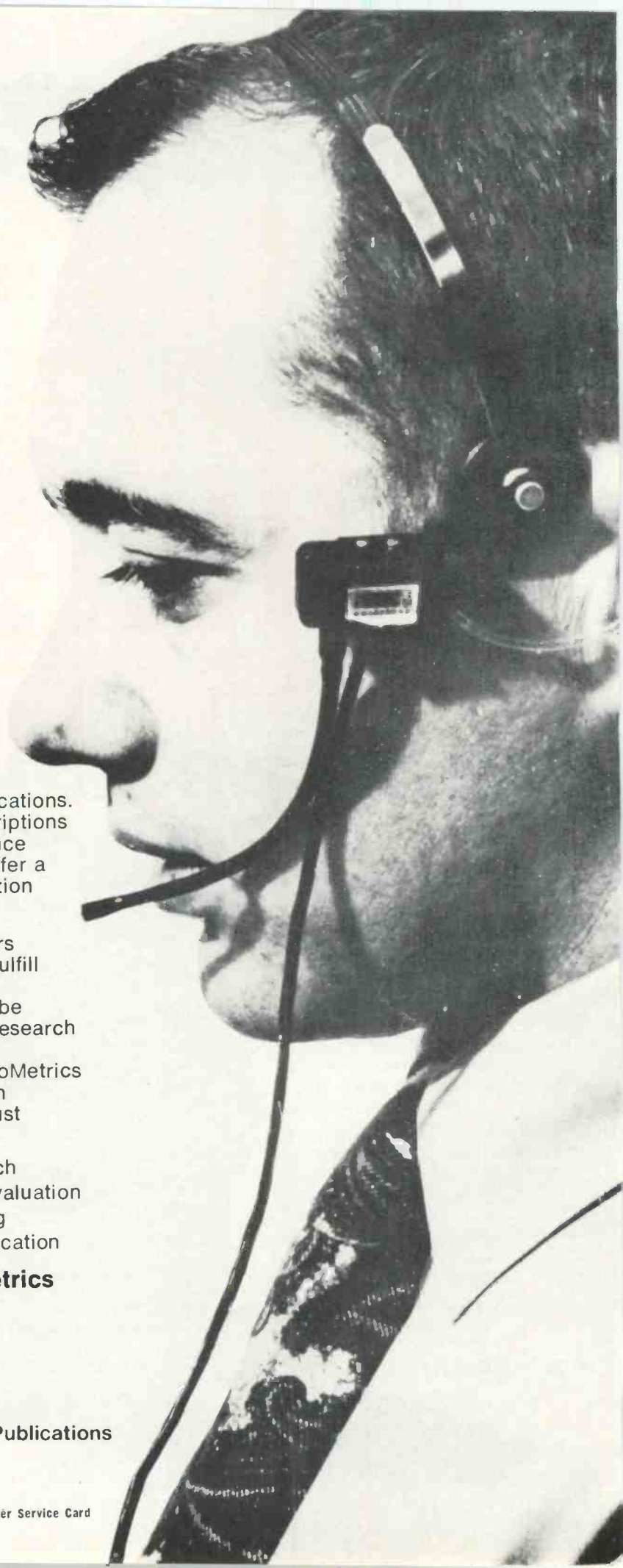
## InfoMetrics<sup>®</sup>

Bayard Nicholas - Director  
A service of Harcourt Brace Jovanovich Publications  
757 Third Avenue (212) 572-4892  
New York, N.Y. 10017

... for more details circle 134 on Reader Service Card



# You can earn more money if you get a Government FCC License

... and here's our famous **CIE Warranty** that you **will get your License** if you study with us **at home**

NOT SATISFIED with your present income? The most practical thing you can do about it is add to your Electronics know-how, pass the FCC exam and get your Government License.

The demand for licensed men is enormous. Today there are over a million licensed broadcast installations and mobile transmitters on the air, and the number is growing constantly. And according to Federal Law, no one is permitted to operate or service such equipment without a Government FCC License or without being under the direct supervision of a licensed operator.

This has resulted in a gold mine of new business for licensed service technicians. A typical mobile radio service contract pays an average of about \$100 a month. It's possible for one trained technician to maintain eight to ten such mobile systems. Some men cover as many as fifteen systems, each with perhaps a dozen units.

## Opportunities in Plants

And there are other exciting opportunities in the aerospace industry, electronics manufacturing, telephone companies, and plants operated by electronic automation. Inside indus-



**Matt Stuczynski, Senior Transmitter Operator, Radio Station WBOE:** "I give CIE credit for my First Class Commercial FCC License. Even though I had only six weeks of high school algebra, CIE's lessons made Electronics easy. I now have a good job in studio operation, transmitting, proof of performance, equipment servicing ... and am on my way up."




**Thomas E. Miller, Jr., Engineer, Indiana Bell Telephone Company:** "I completed my CIE course and passed my FCC exam while in the Navy. On my discharge, I was swamped with job offers from all over the country. My only problem was to pick the best one, and I did—engineer with Indiana Bell Telephone. CIE made the difference between just a job and a management position."

**Cleveland Institute of Electronics**
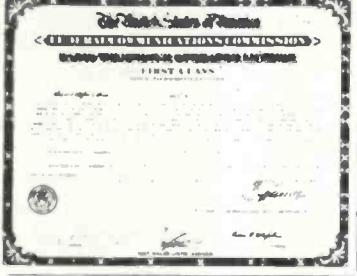
## WARRANTY

**OF SUCCESS IN OBTAINING  
A GOVERNMENT FCC LICENSE**

A Cleveland Institute of Electronics FCC License course will quickly prepare you for a Government FCC License. If you don't pass the FCC exam after completing your course, CIE will refund all your tuition. You get an FCC License...or your money back!



*Ed Miller*

trial plants like these, it's the licensed technician who is always considered first for promotion and in-plant training programs. The reason is simple. Passing the Federal Government's FCC exam and getting your License is widely accepted proof that you know the fundamentals of Electronics.

So why doesn't everybody who "tinkers" with electronic components get an FCC License and start cleaning up?

The answer: it's not that simple. The Government's licensing exam is tough. In fact, an average of two out of every three men who take the FCC exam fail.

There is one way, however, of being pretty certain that you will pass the FCC exam. That's to take one of the FCC home study courses offered by the Cleveland Institute of Electronics.

CIE courses are so effective that better than 9 out of every 10 CIE gradu-

ates who take the exam pass it. That's why we can afford to back our courses with the iron-clad Warranty shown above: you get your FCC License or your money back.

## Mail Coupon for Two Free Books

Want to know more? Send the coupon below for free copies of our school catalog, "How To Succeed In Electronics," describing opportunities in Electronics, together with our special booklet, "How To Get A Commercial FCC License." If coupon has been removed, just send your name and address to us.

## ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box in coupon for G.I. Bill information.

**CIE** Cleveland Institute of Electronics  
1776 East 17th Street, Cleveland, Ohio 44114

**Cleveland Institute of Electronics**  
1776 E. 17th St., Cleveland, Ohio 44114

Please send me without cost or obligation:

1. Your 40-page book "How To Succeed In Electronics" describing the job opportunities in Electronics today and how your courses can prepare me for them.
2. Your book "How To Get A Commercial FCC License."

Name \_\_\_\_\_ Age \_\_\_\_\_  
(Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Check here for G.I. Bill information  
Accredited Member National Home Study Council  
A Leader in Electronics Training... Since 1934

ET 57

... for more details circle 106 on Reader Service Card



continued from page 32

with a scope connected to the junction of 5C264. The P-P voltage should be 200v or more.

- Check the screen voltage of the horizontal output tube. Use a socket adaptor or measure at the terminal board adjacent to the socket. (The third terminal from the side of the receiver is the screen connection. It is accessible from the top of the chassis.) The voltage is normally 150 to 200v. It will drop to 70 to 90v if the yoke is disconnected or if the high-voltage regulation system is not operating.
- Unsolder the focus coil and the focus rectifier. If the problem is in this circuit, all voltages will return to normal, except there will be no focus voltage.


This procedure checks all the major components in the horizontal output circuit except for the high-voltage transformer. Before concluding that the transformer is defective, check the miscellaneous small components in the circuit—capacitors, resistors, choke coils, etc.

The voltages in the chart were taken at the points indicated, using a normal receiver with faults introduced as noted. It illustrates the effect that output circuit faults have upon horizontal-output-tube-screen and control-grid voltages and may be an additional aid in troubleshooting C-1 receivers.

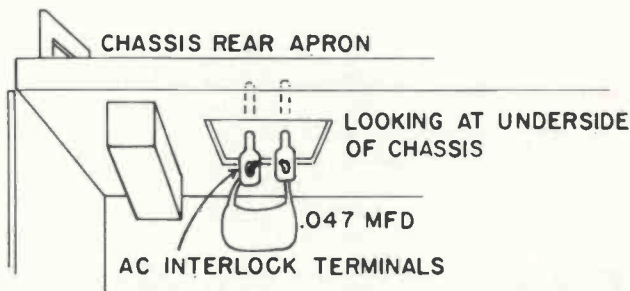**RCA SALES CORPORATION**

Color TV Series "G"—AC Line Capacitor

The color television receivers referenced have a .047μf filter capacitor connected across the ac input line. Due to its physical location (wired directly across the ac interlock terminals), the capacitor can easily be checked and/or replaced in the home using the following guidelines and il-



**WHOLESALE TO ALL**

Breadboard Kits—"RF" Kits—"PC" Kits—Perf. Phenolic Board — Copper Clad Board — Cowl Type Electronic Cabinets — Heat Sinks — Solid State Hobby Kits — Solderless Connectors — Hardware Kits — Transistor Sockets and many more items. (Products approved by the Defense Supply Agency—Federal Supply Code number furnished upon request.) Send for free catalog from:

**H.M.C. SALES, P.O. Box 276, Santa Susana, Calif. 93063**


... for more details circle 115 on Reader Service Card

lustration: (1) Remove rear cover and chassis retaining bolts; slide chassis slightly rearward to inspect capacitor across interlock terminals. (2) If the approved capacitor, identified by its white color and stamped with drawing number 90097-221 or 1442487-221 is used, secure chassis and restore receiver operation. No further action is necessary. (3) If the capacitor viewed is brown or reddish-brown in color, it should be replaced with the approved type. The RCA Stock Number of the approved capacitor is 111286. It is recommended that all service technicians carry this approved type capacitor.

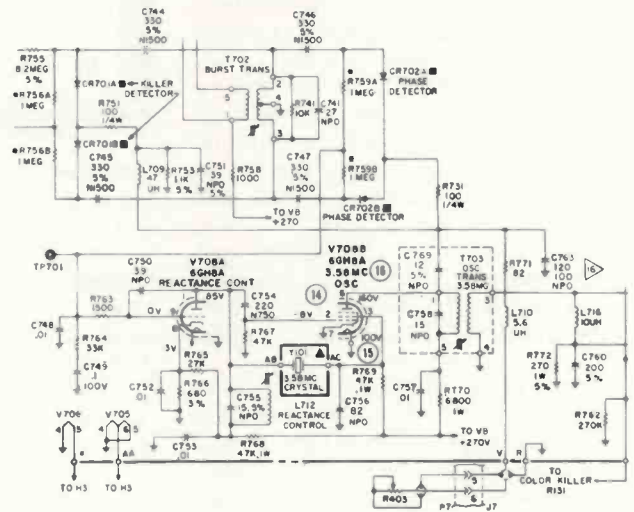**MAGNAVOX**

Color TV Chassis T931/T933/T940—Color Sync Problems

The mentioned chassis as well as earlier chassis—such as the T920, T919, T918 and T911—use a matched pair diodes in the color killer and phase detector circuits. You



are reminded to include these diodes in your troubleshooting checks whenever you are working on a color sync problem. Either the color killer detector diodes (CR701A and CR701B) or the color phase detector diodes (CR702A and CR702B) can be the cause of intermittent loss of color sync, poor color sync or in some cases even loss of color. These diodes are specified as matched pairs, meaning they have identical characteristics. If one of the diodes in these matched pairs should suffer a change in characteristics, operation of the circuit will be impaired. The usual resistance checks will not be satisfactory in determining if the suspected diode has changed characteristics. If you suspect that either the killer detector or phase detector circuits are at fault, the following check is suggested:

Connect a color-bar generator to the receiver and set it for a normal color-bar display. Remove the 3.58MHz Oscillator tube (V708) and ground the junction of R756A and R756B in the color-killer detector circuit. Using a VTVM, measure the dc voltage to ground at each outside terminal of a diode pair—for example, at the anode of diode CR701A and cathode of CR701B. The voltage at the anode should be negative, while positive at the cathode. The exact value of the voltages measured at these points will vary from set to set and also with the level of the burst signal. (Typical values might be +55v at the cathode and -55v at the anode.) The important point is the difference, if any, between the voltages measured across each of the diode pairs. Under ideal conditions there should be no difference. However, a 10 percent variation is allowable. If a voltage difference in excess of 10 percent exists across either diode pair, replace the pair with a matched pair, Part No. 170733-1.

# Now a Heathkit® Solid State **Vectorscope/Color Generator** Only \$124.95\*



## Accurately Performs All Of These Adjustments:

- Raster
- Static & Dynamic Convergence
- Purity
- Gray Scale

- 3.58 MHz Oscillator
- Reactance Coil
- Phase Detector Transformer
- Demodulator Angle Check
- Chroma Bandpass Touch-Up

Kit IO-101, 12 lbs. . . . . \$124.95\*

## Fast switch selection of standard 9 x 9 display . . . or exclusive Heath "3 x 3" display



**IO-101 SPECIFICATIONS — PATTERNS — Purity:** Produces a snow-free raster for purity adjustments. **Dots:** 9 x 9 produces a display of 110 small dots. 3 x 3 produces a display of nine dots for convergence adjustments. **Crosshatch:** 9 x 9 produces a display of 11 vertical and 10 horizontal lines. 3 x 3 produces a display of three vertical and three horizontal lines for convergence and linearity adjustments. **Horizontal Lines:** 9 x 9 produces a display of 10 horizontal lines. 3 x 3 produces a display of three horizontal lines for vertical linearity and pin-cushion adjustments. **Vertical Lines:** 9 x 9 produces 11 vertical lines. 3 x 3 produces a display of 3 vertical lines for horizontal linearity and convergence adjustments. **Color Bars:** 9 x 9 produces a display of ten standard color bars. 3 x 3 produces a display of three standard color bars. A visual-fingerprint (voltage pattern) of all ten color bars in the form of a petal pattern is displayed for color circuit servicing. **Gray Scale:** Provides a wide bar crosshatch pattern with six shades of brightness for color gun level adjustments. **OUTPUT SIGNALS — Video:** Greater than ±1 volt peak-to-peak composite signal for composite signal injection beyond the video detector. **RF:** Variable to approximately 25,000 uV output, channels 2 through 6, for composite signal injection into the TV receiver antenna input terminals. **Sync:** Greater than 3.5 volts peak-to-peak signal for servicing sync circuits without video, or sets having separate video and sync demodulator phase adjustments. **GENERAL — Power Requirements:** 105-125 or 210-250 VAC, 50/60 Hz, 20 Watts. **Cabinet Dimensions:** 6 3/4" W x 9 1/4" H x 14 1/2" D. **Net Weight:** 9 1/2 lbs.

\*The number of dots, lines, and bars indicated for a 9 x 9 display is the number displayed if the receiver under test has no overscan.

a Schlumberger company

**HEATH COMPANY, Dept. 24-7**  
Benton Harbor, Michigan 49022

Please send FREE Heathkit Catalog  
 Please send IO-101 Specification Sheet

Enclosed is \$ \_\_\_\_\_ plus shipping.  
Please send Model IO-101

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices and specifications subject to change without notice.  
 \*Mail Order Prices; F.O.B. Factory

TE-222

. . . for more details circle 114 on Reader Service Card



# publisher's memorandum from Scotty Wallace



SCOTTY WALLACE

I am happy to announce the following promotions and additions to the Editorial Staff of ELECTRONIC TECHNICIAN/DEALER. These changes are part of our program to keep our publication in the number one position in the Electronic Industry. Phillip Dahlen has moved up to Editor, with Joseph Zauhar moving to Managing Editor. We have also added the talents of Emily Wilson as Associate Editor, all of whom are based in our Duluth, Minnesota, office. I am certain all of our readers and advertisers will appreciate the following outline of their backgrounds and join me in welcoming them to their newly appointed positions.

Phil first worked in electronics as an apprentice in a Fairport, New York, TV repair shop; and his electronic background was further improved in college where he majored in Physics, graduating from HAMLIN UNIVERSITY in 1959.

After teaching a year, Phil was drafted into the Army where, with his electronics background, he was assigned an Electronic Instrument Repair MOS. While on duty he assisted in the development of electronic instruments designed for detecting biological organisms, while during his free time Phil worked in a Frederick, Maryland, TV shop.

Prior to coming to Harbrace Publications, Phil invented the Needleless Phonograph that was described a couple of years ago in this publication, and for which Phil has obtained personal U.S. and foreign patents. Designed for playing conventional stereo records with an optical system rather than a needle, he feels that it is capable of a frequency response high enough for TV-type images. By the way, he is currently looking for a manufacturer interested in a favorable licensing agreement.

Just about as soon as Phil came to this company, he began writing the "Semiconductors from A to Z" series. Reader response was so great that the series was later published in book form, which is now in its second printing.

Editorial demands at Harbrace required Phil's transfer to two other company publications for which he was editor prior to being transferred back to our publication.

After two years in Korea as an Army squad leader, Joe enrolled in the Duluth Area Institute of Technology for a two-year course in radio and television, and then an advanced course with the CLEVELAND INSTITUTE OF ELECTRONICS. His first job in electronics servicing, one of three offered, was part time while finishing his schooling. He then worked twelve years in this field prior to joining Harbrace Publications. During the past four years, Joe has served as Technical Editor of the publication, preparing a number of staff-written articles, as well as preparing the Tekfax, Colorfax, Technical Digest and the New Products listing.

Despite the fact that Joe is employed full time on our publication, there are still customers who remember the quality of his work prior to coming to Harbrace and who still "bug" him into fixing their electronic equipment. As a result of these continuing service contacts, Joe is kept well abreast of new innovations from the service viewpoint.

Emily is the newest member of our editorial staff. A 1969 graduate of the UNIVERSITY OF MINNESOTA, she has just recently come to us from American Heritage Publishing Company in New York, a subsidiary of McGraw-Hill, where she was involved in both promotion and circulation for the American Heritage Society's official publication, AMERICAN HERITAGE MAGAZINE.



PHILLIP DAHLEN



JOSEPH ZAUHAR




EMILY WILSON


*Scotty Wallace*  
ELECTRONIC TECHNICIAN/DEALER

# The hunt is on!

(Beware of the Grope.)

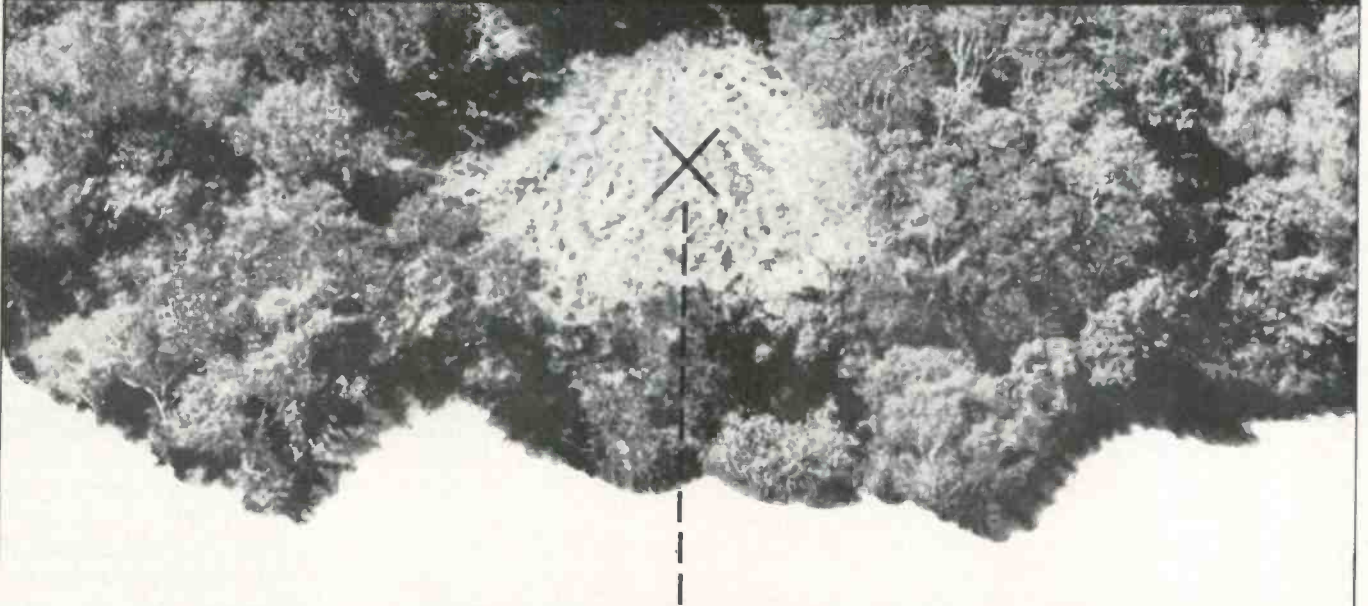

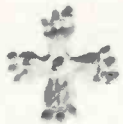How to head the hunt away from the Grope.  
Draw your prospect a map.



The Grope footprint goes in all directions, like you without the Yellow Pages.

That dratted Grope! He preys on people who don't know where to find what they're hunting for . . . turning their search for you into a jungle hunt!

So be prepared. Have your own special map in the Yellow Pages, so the only one that loses out is the Grope. It's easy, and it's the best selling map in town.

Here's your do-it-yourself speed lesson on the Yellow Pages Map Drawing course.

Call your local Yellow Pages representative today and place your Map with him!



**The Yellow Pages**

**Emergency Service  
Day or Night**

**BARRY'S HEATING & PLUMBING**

Since **BHP** 1921

**COMMERCIAL,  
INSTITUTIONAL, RESIDENTIAL,  
INSTALLATION & REPAIRS**

Complete line of:

<ul style="list-style-type: none"> <li>• Kitchens</li> <li>• Laundries</li> <li>• Sewage Systems</li> </ul>	<ul style="list-style-type: none"> <li>• Water Pumps</li> <li>• Heating Systems</li> <li>• Pipes and Drains</li> </ul>
---	--

<ul style="list-style-type: none"> <li>★ References</li> <li>★ Ample Parking</li> </ul>	<ul style="list-style-type: none"> <li>★ Estimates</li> <li>★ Delayed Payment Plans</li> </ul>
---	--

phone  
**678-0743**

**77 Locust Lane. (Between Main and  
Central, one mile from RR. Station).**

Tell people what you will do for them. How you're different.

Be under the proper headings so people can find you fast. Maybe you should be under more than one heading. Think about that!

Use your logotype to gain recognition. Give facts about your qualifications.


Tell people about your special services . . . repairs, rentals.

List the products you carry.

Tell how easy it is to deal with you . . . credit, parking, hours, delivery.

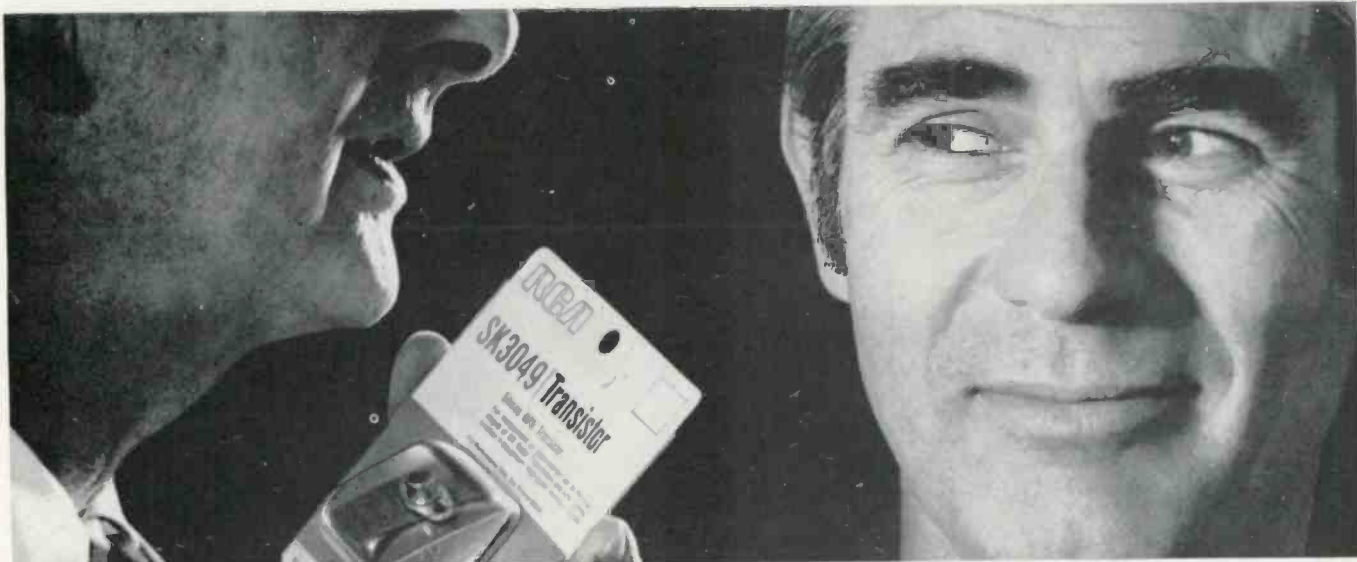Give telephone number and address, and if you're hard to locate, directions.





## The story on RCA SK devices is told in confidence

Since top quality is assured in all SK-Series Devices, they are bought and used in total *confidence*... key to the success of RCA's comprehensive replacement line.

This SK line is precisely engineered. Each device—transistor, rectifier, or integrated circuit—is manufactured and tested to tight, premium specifications. And the SK line is designed especially to fit a broad number of applications in entertainment-type electronic equipment.

No wonder RCA SK's are among the industry's top performing replacements!

This line now numbers 47 devices that can replace more than 14,000 units—foreign, domestic, even unbranded part-number types! All are backed by electrical parameters that make them comparable to—often better than—original devices.

Featuring only premium types—no cast-offs, no factory seconds, no unbranded culls, RCA SK devices cover most jobs you face—from small signal applications to TV deflection circuits to the latest in 100-watt audio amplifier outputs.

All RCA devices, after careful checking and rechecking of the types they replace, are cross-referenced in the current RCA SK Replacement Guide. It also includes:

- A new, quick-selection chart by application
- A new, technical data selection in tabular form
- A new listing of types recently added to the line



For more information on RCA SK replacements and your copy of the RCA Replacement Guide, see your local RCA Distributor.

RCA | Harrison, N.J. 07029

# RCA

## ET/D TEKLAB REPORT

Troubleshooting an Automatic Fine Tuning circuit employing an integrated circuit is easy if you understand the circuit and use the checking procedure described

# Emerson Model 26C56 Color TV-Part I


by JOSEPH ZAUHAR

■ The Emerson Model 26C56W color TV set received for this report employs a 120924 chassis, which is similar to the chassis employed in Models 26C45, 26C47 and 26C48. This chassis employs a number of previous field proven circuits, modified by the addition of a few new circuit improvements.

Taking a look at the schematic we found a number of important features incorporated. The receiver retains all of the features found in previous full powered transformer models, which include the following: Three Video IF Stages, Three Video

Amplifiers, Shunt Regulated 25kv High Voltage Supply, X and Z Color Demodulators with separate R-Y/B-Y/G-Y Amplifier and Phase Detector—Reactance tube—AFPC.

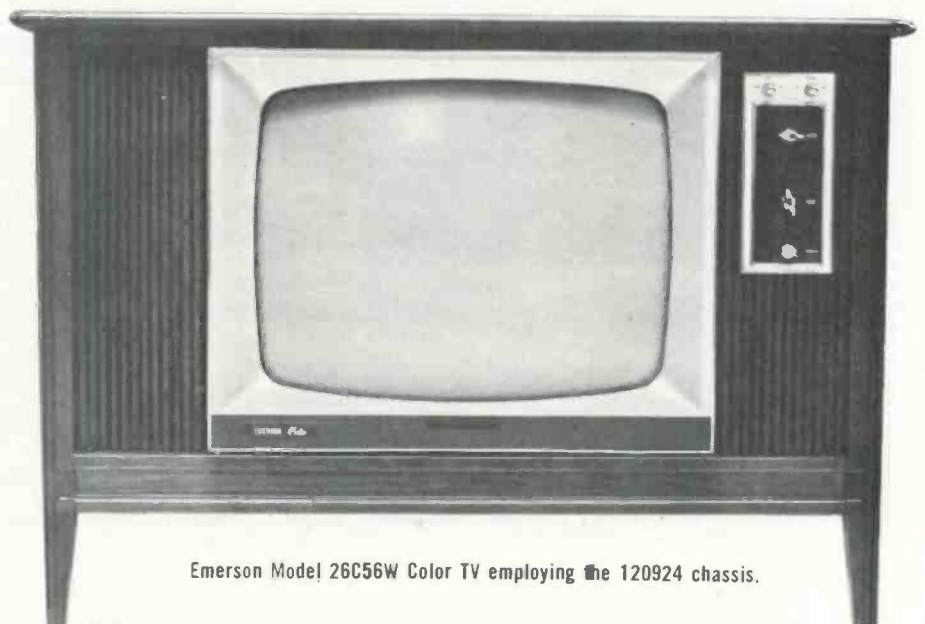A number of new circuits will be found on this chassis which include: (1) quick-on provisions, (2) improved Automatic Fine Tuning (AFT) employing integrated circuitry, (3) improved Automatic Color Control circuit with two stages of chroma amplification, (4) increased burst amplification, and (5) diode horizontal centering for cooler and more reliable HOT chas-



Emerson Model 26C56W Color TV employing the 120924 chassis.



sis operation. All of the customer controls are located on the front panel and the control shafts, except the quick-on, pull out about 1 in. for ease of adjustments.

There were a number of things that we felt could be improved to shorten the technician's service time, such as: wing type fasteners on the back cover panel, a removable panel on the bottom of the cabinet exposing the components without chassis removal, and an easier means of removing the front control panel.


The physical chassis layout is similar to the previous "U" shaped chassis, which consumes less cabinet space. The brace through the center of the chassis not only strengthens the chassis but makes a convenient carrying handle when removed.

The circuit boards are well road-mapped, making components and test points easy to locate when service or alignment is required.


The shunt-regulator tube and the high-voltage-rectifier tube are shielded by the high-voltage cage, and the cover should be kept in place when servicing an energized chassis.

The high voltage specified for this receiver is 25kv. The adjustments in the horizontal output circuits are similar to previous chassis and precautions should be taken to make sure all adjustments are properly set.

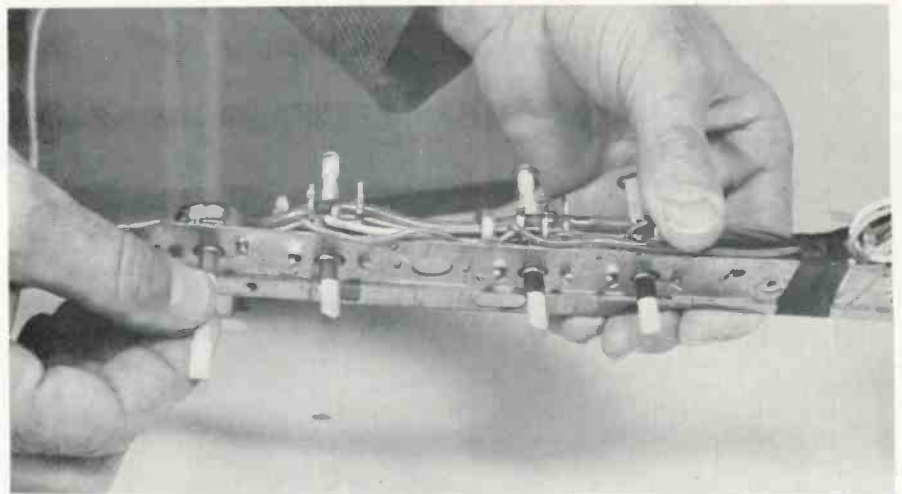Picture tube type numbers 25XP22 and 25ZP22 are employed



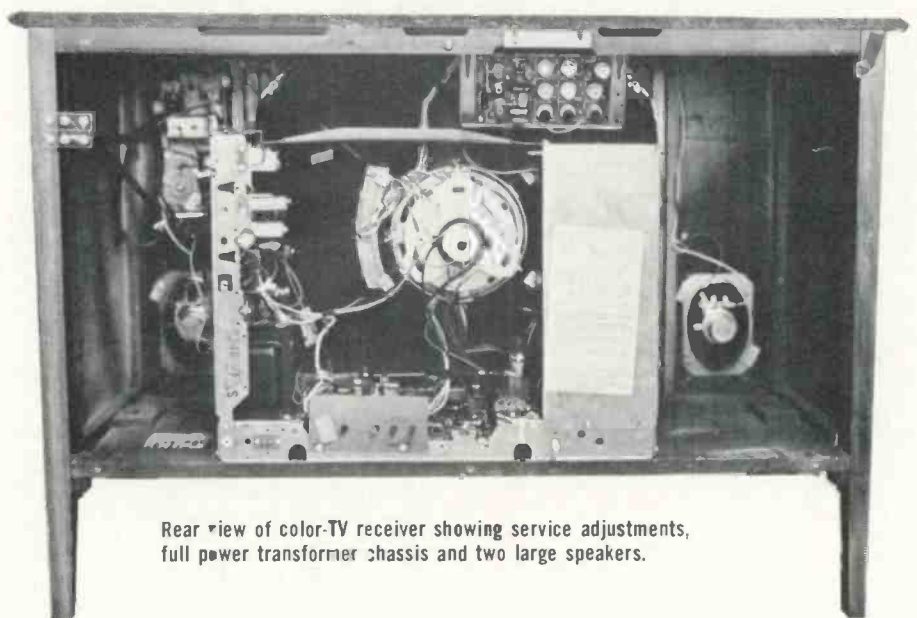All knobs, except the Quick-On, may be pulled out approximately 1 in. for ease of adjustment.



Rear view of color-TV receiver showing service adjustments, full power transformer chassis and two large speakers.

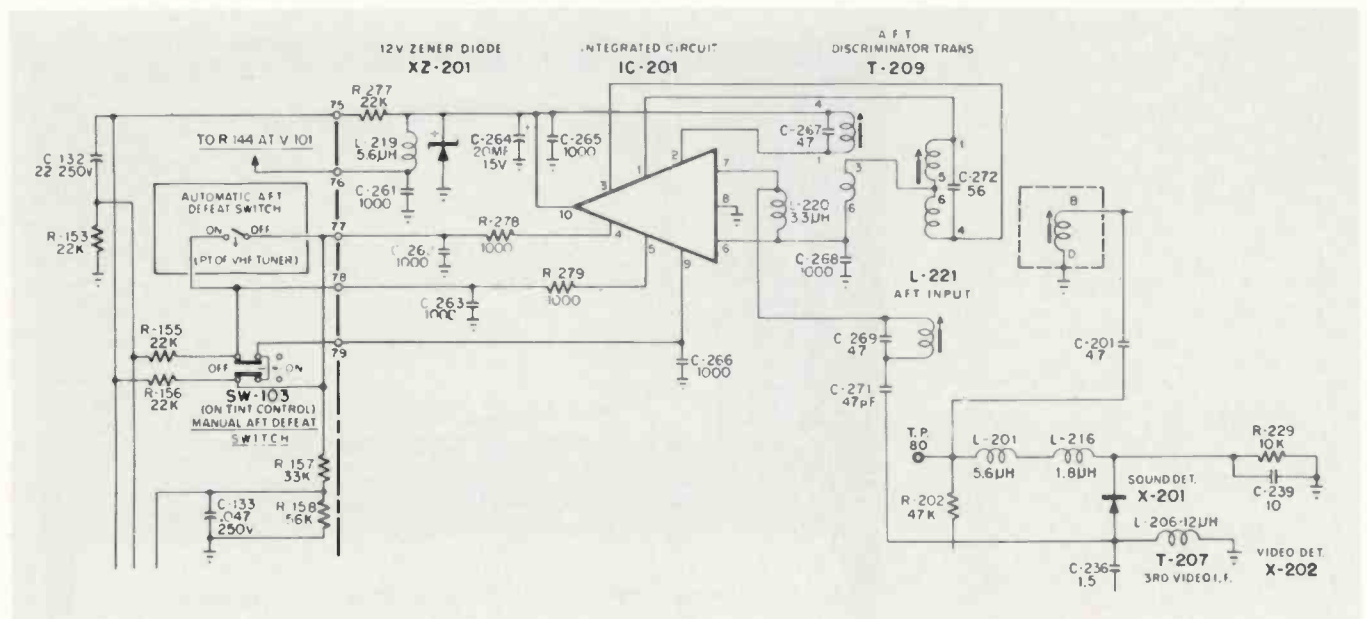


Fig. 1—Schematic of the Automatic Fine Tuning circuit employing an Integrated Circuit IC201.

in these models. These tubes are interchangeable with type number 25AP22, which was used in previous models.

Most technicians are familiar with

many of the circuits employed, which have been proven in the field for a number of years. The article is therefore limited to a review of the new circuits and modifications.

## AUTOMATIC FINE TUNING (AFT) CIRCUIT

The AFT circuit shown in Fig. 1 contains an integrated circuit, IC-201, which is located on the video and sound printed-circuit board, PC2. The dc voltage for powering IC201 is obtained from the cathode of the vertical output tube. A resistor connected to the 6JE6 horizontal-output tube supplies an additional bias voltage to terminal 76 of this printed circuit and terminal 10 of IC201—zener diode XZ-201 regulating this 12v supply.


The video IF carrier signal is obtained from the third video IF plate circuit amplifier stage. The signal passes through capacitor C236 (1.5pf) and C271 (.47pf) to a tuned input circuit consisting of capacitor C269 (47pf) and coil L221. This tuned circuit is adjusted to 41.25MHz and serves as a sound rejection trap.

The video IF carrier signal is applied to terminal seven of IC201. This IC operates in a manner similar to the previous AFT circuitry using transistors and diodes. The video IF carrier signal is then applied to a discriminator circuit, which in turn provides error control voltages. Transformer T209 is the AFT discriminator and is tuned to 45.75MHz.


The control voltages are obtained from terminals four and five of the integrated circuit. When the set is properly tuned and the video IF carrier is at 45.75 MHz, both terminals will develop 6v, which is supplied to the voltage dependent capacitor (varactor) in the VHF tuner oscillator circuit. If not tuned properly, the voltage potential of terminals four and five will change and in some instances terminal four will increase above 6v while terminal five will decrease to a voltage below 6v. This in turn will apply a voltage across the voltage independent capacitor (varactor) correcting the oscillator for proper tuning.

The circuit employs an automatic AFT defeat switch on the VHF tuner, fine tuning shaft plus a manual AFT defeat switch. When the manual switch, SW103, is placed in its off position, terminals four and five of IC201 are connected together

*continued on page 77*

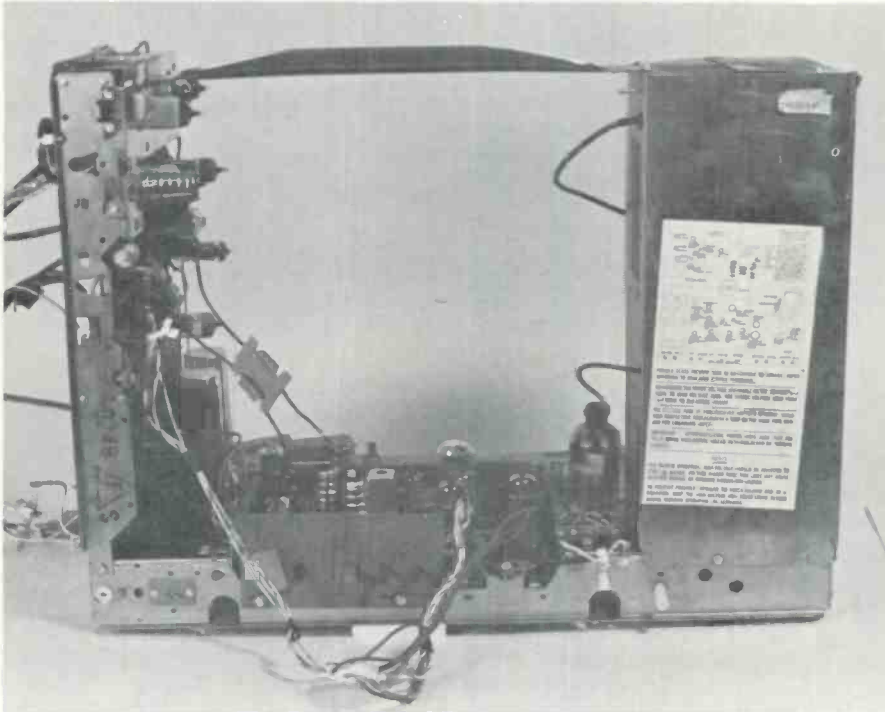

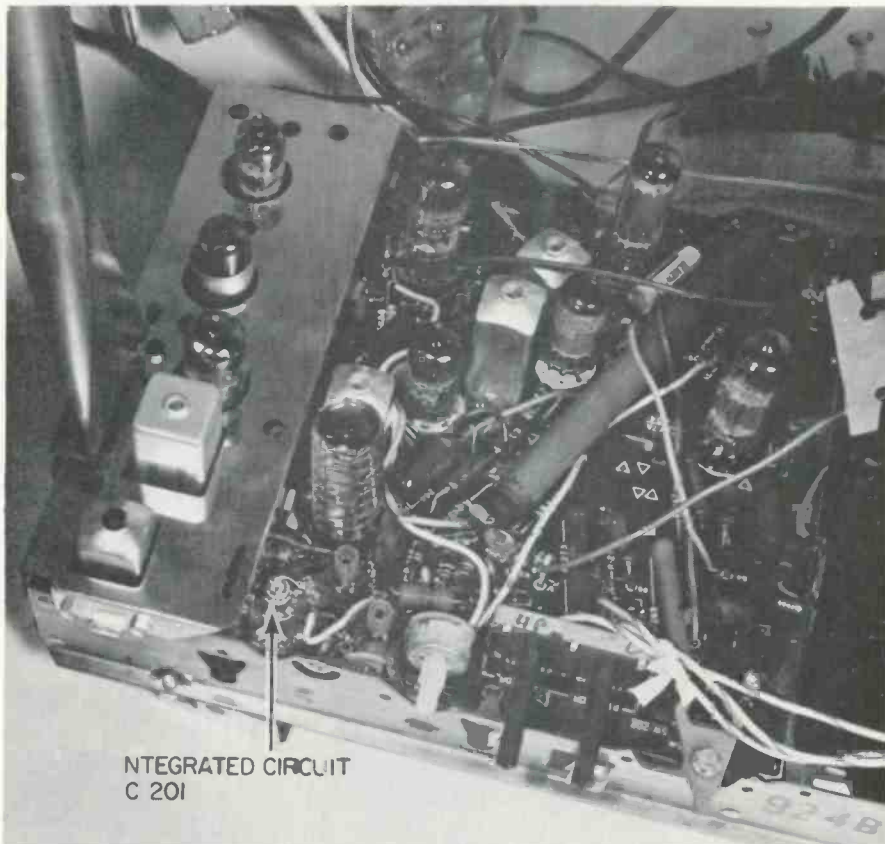The "U" shaped chassis includes a rigid brace that can be used as a carrying handle.



The Integrated Circuit IC201, with shield removed, is located on the video and sound printed board.



# Installing A Mobile Transceiver

by PHILLIP DAHLEN

With the fantastic variety of automobiles on today's market, custom fitting becomes a necessity if a really good job is to be done installing two-way communications equipment

■ There are very few alternatives available when determining the location of a mobile transceiver and its power supply. Most manufacturers require that the power supply not be located in front of the engine fire wall since it will then be exposed to excess dampness and corrosive or oily vapors. High-power requirements from the vehicle's 12v system requires positioning the power supply as near the fire wall as possible, since any excess length of power cable—leading to say the trunk—will result in an excess voltage drop through the cable, unless it is of unreasonably large gauge.

Accessibility restricts the choice of locations for mounting the transceiver chassis. The trunk of the vehicle is a fine, out of the way location for the transceiver if provision is made for its remote control operation, but then transmission is limited to predetermined frequencies. For amateur use, unless you have a chauffeur, the entire transceiver must be within easy reach of the driver.

Since every installation is different, and space does not permit a description of all possible installations, the balance of this article includes only the procedures carried out when Paul Dorweiler, the previous Editor of *ELECTRONIC TECHNICIAN/DEALER*, and Joe Zauhar, now Managing Editor, installed a Drake TR-4 mobile transceiver in Paul's 1970 Chevrolet Townsman station wagon.

The Drake TR-4 was obtained with two power supplies—one designed to operate at line voltage for stationary or bench use and the other designed for 12v mobile operation. We found that the most convenient location for the mobile supply was on the floor behind the cartridge tape recorder. Once this location had been selected, a soldering iron was used (Fig. 1) to burn holes in the carpet. These holes marked the location of the holes to be drilled into the fire wall for securing the power supply (Fig. 2) and eliminated the need for drilling through the carpet itself (the carpet may have otherwise become twisted around the drill bit, tearing or otherwise hindering drilling).

Fortunately an extra unused rubber grommet was found extending through the fire wall, permitting easy

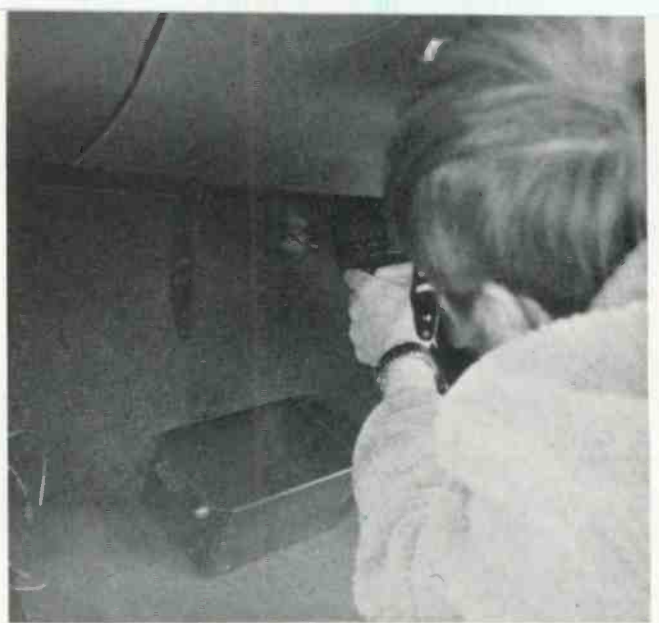


Fig. 1—Burning holes in carpeting for locating position of future power supply bolts.

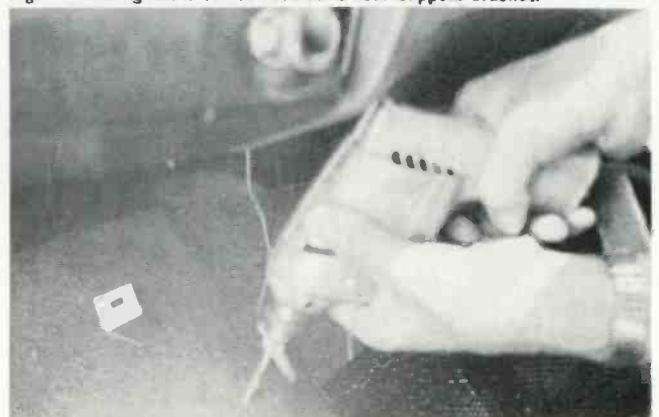


Fig. 2—Drilling holes for power supply bolts.



Fig. 3—Bolting fused power line to positive terminal of battery.

Fig. 4—Drilling holes for transceiver's rear support bracket.



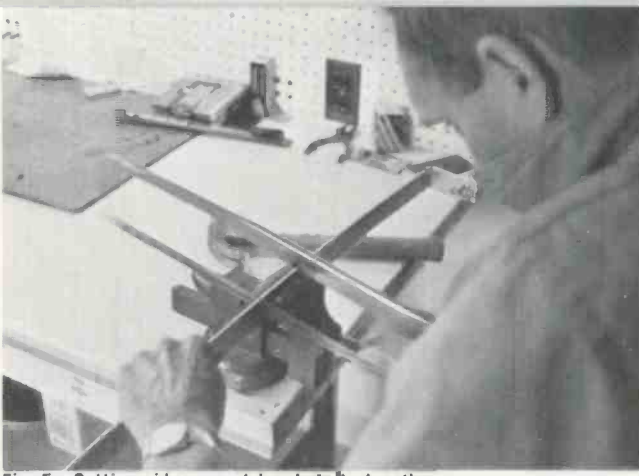


Fig. 5—Cutting side-support brackets to length.

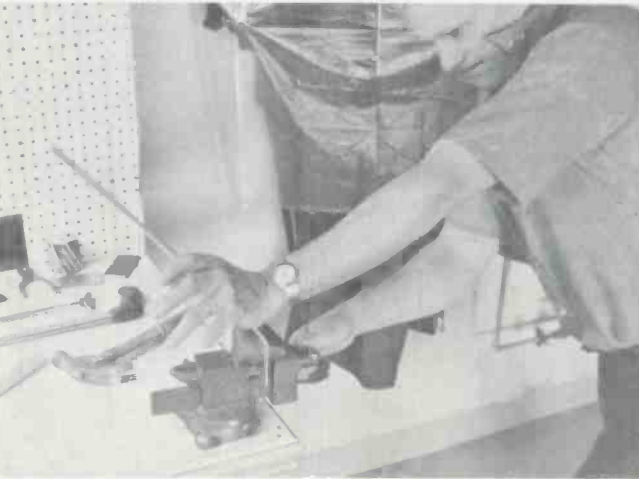


Fig. 6—Bending side-support brackets into shape.

Fig. 7—Sanding a rounded edge at the top of each side-support bracket.



passage of the power line. After bolting a fuse holder in place under the hood, the fused power line was bolted to the positive terminal of the battery (Fig. 3). (To some readers this battery may appear a little unusual without its terminals at the top. However, batteries in 1970 General Motors vehicles have bolt-on terminals on the side to eliminate the former problem of battery-acid corrosion.)

For ease of operation, the hump in the floor above the station-wagon transmission was selected as the location for mounting the transceiver. It was positioned just far enough back on the hump to permit moving the car seat fully forward.

After having determined the location for mounting the transceiver, its rear support bracket was placed in proper position on the hump, the location of its mounting holes were marked with a soldering iron, holes were drilled (Fig. 4), and the bracket was bolted into position.

Once positioned on its back supporting bracket, the front of the transceiver was lifted to a convenient elevation; and the distance between the floor and the transceiver's forward mounting holes was measured. With these dimensions, Joe was able to cut the side-supporting brackets to length (Fig. 5). He then bent the bottom portion of each bracket (Fig. 6) to match the contour of the floor.

To add an additional touch of professionalism to the installation, Joe ground rounded edges at the ends of each side support (Fig. 7), using a 7-in. rotary industrial-type sander. Mounting holes were then drilled (Fig. 8) in the side-support brackets.

The transceiver was originally equipped with rubber



Fig. 8—Drilling mounting holes in legs of side-support brackets.



## INSTALLING TRANSCEIVER . . .

feet for base station use, but since they would serve no practical function once the unit was mounted in the station wagon, they were removed to permit the attachment of an additional support to the bottom of the transceiver. (This brace had originally been supplied by the manufacturer for securing the front of the transceiver to the dash of some cars.) Paul drilled holes in the transceiver's bottom plate (Fig. 9) for mounting this bracket, after having bolted the mate to the rear support bracket onto the same plate. The additional bracket was then riveted to the plate.

When again placing the transceiver into position on the rear pair of supporting brackets, it was found that these brackets failed to adequately secure the transceiver, any forward motion pulling them apart. To solve this problem, a hole was drilled into the protruding lip of one bracket and a pin was inserted after the two brackets were again coupled together—thus assuring additional stability.

After bolting the side-support brackets to the floor of the car and securing them to the side of the transceiver (using special bolts and washers supplied by the manufacturer), the side brackets were again drilled (Fig. 10); the new holes matching those in the additional bracket beneath the transceiver.

Paul decided that since he had a rather large antenna, he would prefer to have it mounted near the back of the station wagon, on the lower right-hand side. Using a portion of the antenna mount as a template, Paul marked this location with a pen (Fig. 11), and Joe then marked them more permanently with a center punch (Fig. 12). After drilling the holes (Fig. 13), the central hole was enlarged with a file (Fig. 14) so that the central bolt could pass through freely and no arcing would occur between the bolt and ground.

Paint, tar and other material inside the spare-tire storage compartment were then sanded away (Fig. 15) so that the ground lead to the antenna bracket could be well grounded.

Probably one of the most difficult jobs in the entire installation was the task of running the coaxial cable between the transceiver and the antenna. It was not too difficult getting the cable beneath the front- and back-seat carpeting, but Joe and Paul had to practically tear the car apart (Fig. 16) in order to run the coaxial cable further back to the antenna mount. But once the cable was pulled through and secured to the antenna mount (Fig. 17), the job was nearly complete. All that remained to do was bolt the antenna to the mount (Fig. 18).

After a few minor electronic adjustments were made in the transceiver, the job was complete. And we feel that it was quite a success. Both the transceiver and power supply were very securely mounted in place, and Paul was able to DX other ham radio operators in several parts of the country. ■



Fig. 9—Drilling holes for mounting additional support brackets to base of transceiver.

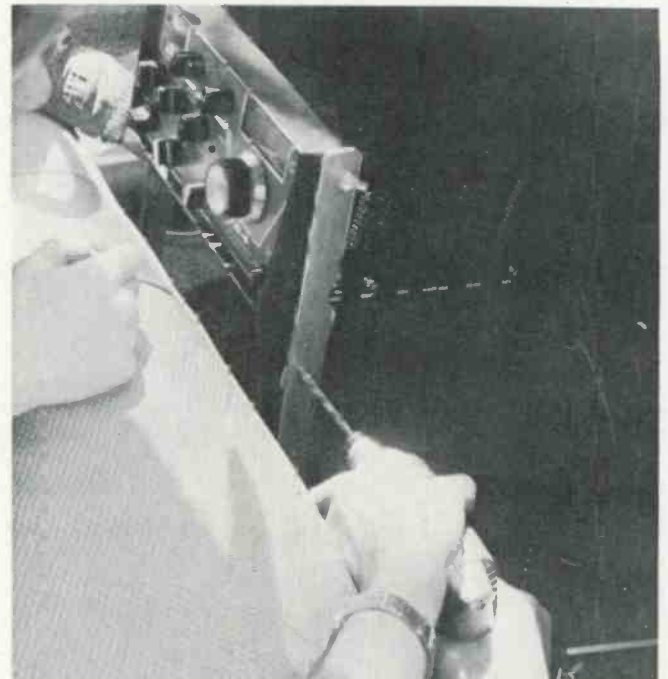


Fig. 10—Drilling side-support brackets for bolting to additional brackets secured beneath transceiver.

Fig. 11—Marking location of holes required for antenna mount.





Fig. 12—Center punching antenna-mount holes for drilling.



Fig. 13—Running antenna coaxial cable from front to rear.



Fig. 13—Drilling antenna-mount holes.

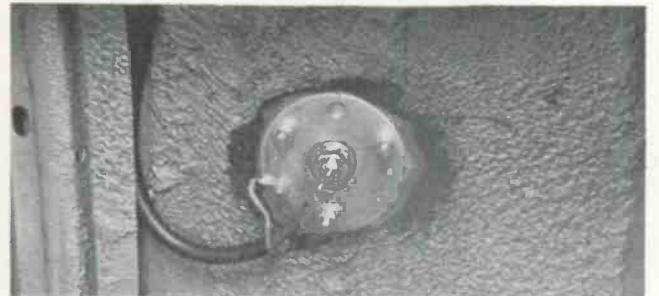


Fig. 17—Completing job with coaxial cable bolted to antenna mount.

Fig. 18—Viewing mounted antenna in position for transmission


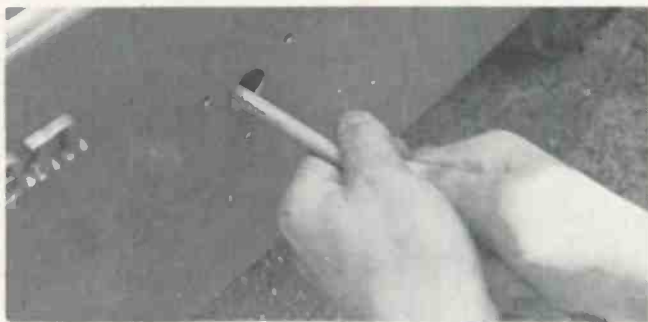


Fig. 14—Enlarging central hole for antenna mount.

Fig. 15—Grinding away protective coating for better antenna ground.

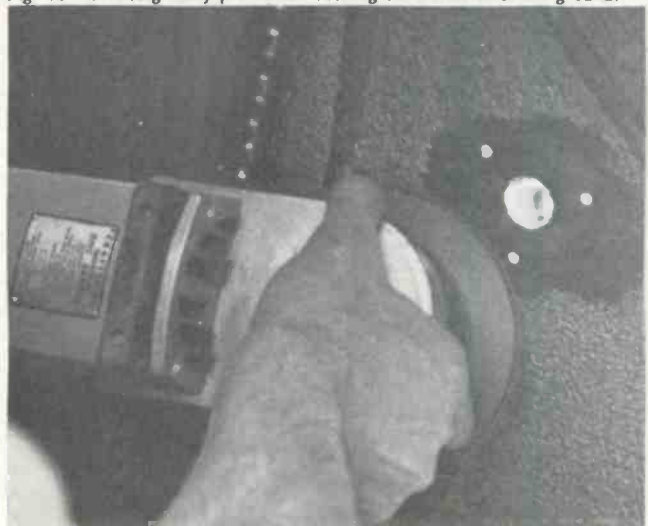



# Servicing Solid-State Stereo

by NORMAN H. CROWHURST

## Part II—Applying more basic electronics to improve servicing techniques and prevent call backs

■ Transistors are more easily damaged than tubes, generally requiring the use of more protective circuits. To understand all aspects of transistor protection, it is necessary to keep in mind the different damages to which they can be exposed.

Excess currents can destroy them. And, as mentioned in the previous article, circuits are now in rather common use for protecting transistors against these currents. Reverse voltage is another danger that has also been covered. Still another possibility is excess voltage of the normal polarity.

### EXCESS AUDIO POWER

But voltages and currents alone do not cover the entire problem. While an excessive current can "blow" a transistor junction and an excessive voltage can break it down, making sure that both current and voltage always stay within these limits does not completely ensure its safe operation. A combination of voltages and currents can result in heating, which if not properly dissipated, may cause transistor breakdown and failure. Every transistor has a maximum power dissipation rating—possibly more than one, depending on its mounting or provisions for conducting heat away.

It might seem as if excess-current protection would also guard against excess heat-producing power across the transistor. In some instances it does, but in others such circuits aggravate the problem.

When the current through the output transistor is allowed to rise, there is a greater voltage drop across the load, resulting in a lower voltage drop across the transistor and a smaller amount of power ( $W = I \times V$ ) dissipated across the transistor (such voltage, current, power relationships are shown in Fig. 6 of

the previous article). Limiting the current to less than maximum through the transistor and load also

limits the voltage developed across the output load, thus increasing the voltage across the transistor at maximum current and the power dissipated in the transistor.

This does not mean that removing the current limitation would avoid the danger, because then the transistor would blow for a different reason—excess current rather than excess power dissipation.

The important factor is the transistor voltage when the current reaches its limiting value. If the transistor is close to saturation so


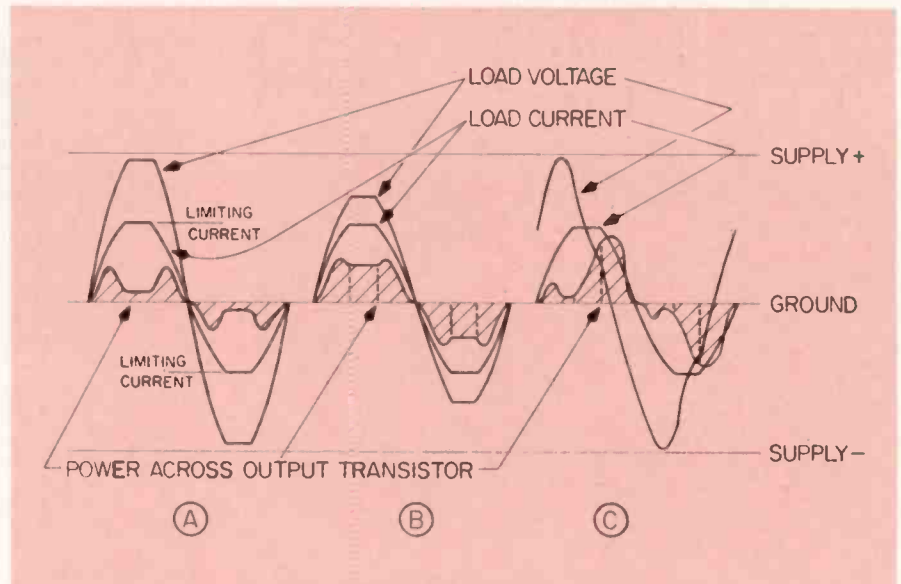


Fig. 1—Some waveforms associated with current limiting; (A) when the load is resistive and of near normal value; (B) when the load is resistive and lower than normal value; and (C) when the load is reactive but of nearly normal impedance.

Fig. 2—A basic current-limiting circuit.

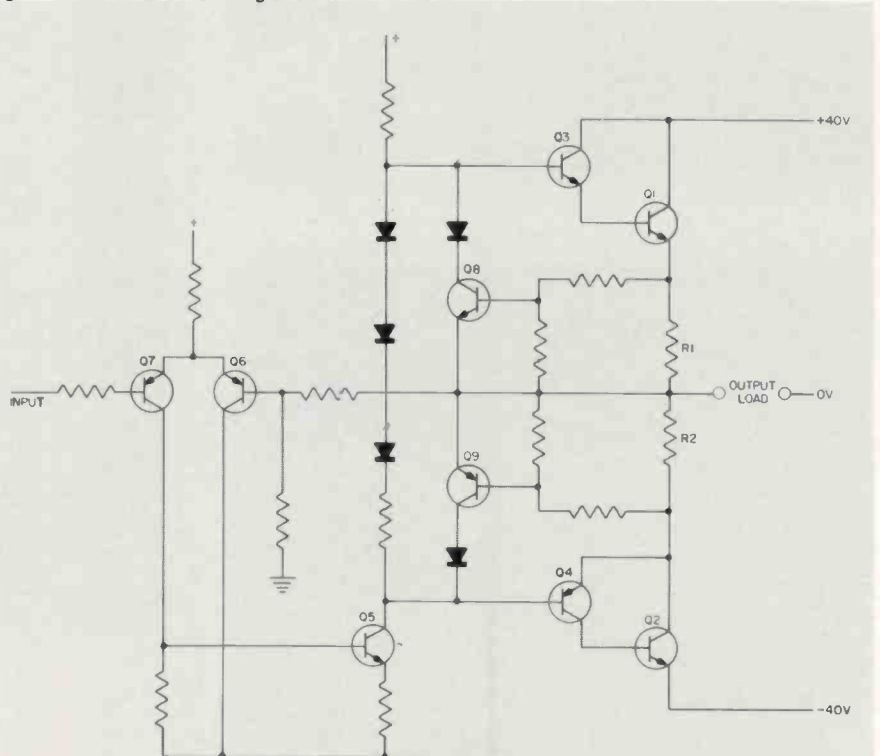

that the voltage across it is small, most of it appearing across the load, there is no power problem (Fig. 1A). But, if the voltage across the load is substantially below the maximum available when the current is limited, the rest of the voltage results in a greater power dissipation in the transistor (Fig. 1B).

Two factors can result in excess transistor voltage at maximum current: Either the load resistance is too low for the amplifier, or it is nearly the correct value but too reactive, the maximum current not

completely coinciding with the maximum load voltage (Fig. 1C).

### BASIC PROTECTIVE CIRCUITS

Fig. 2 contains basically the same schematic as that shown in Fig. 5 of the previous article. In this output section, voltages less than maximum swing are harmful to the circuit only if they coincide with the maximum current, causing current limiting to come into effect. What is needed is a device that will detect what the output voltage is when the current reaches its maximum. A circuit that

will "do something about it" if the transistor voltage exceeds a safe value during maximum current.

Fig. 3 shows an essential portion of such a circuit applied to half an output stage. When there is no current limiting, transistor Q8 and diode D1 are not conducting and they do not affect the transistor's collector voltage. But as soon as current limiting occurs, the transistor and diode both conduct, the collector voltage then being nearly equal the output voltage.

If the voltage across the output transistor (Q1) is low, it will not reach the zener voltage of diode D3, and transistor Q10 will remain in its normal non-conducting state. But, if the voltage across transistor Q1 exceeds the zener voltage of diode D3, current limiting occurs and transistor Q10 will be switched on, charging capacitor C1 through resistor R4 and causing transistor Q11 to conduct.

When conducting, transistor Q11 short circuits the positive audio input signal, restoring the output transistor to a safe condition. It takes a few moments for the voltage across capacitor C1 to discharge through resistor R5, allowing the input signal time to change from its harmful condition and the output transistor time to cool off.

Although a definite improvement over no voltage protection at all, there are two problems with this simple circuit. The most obvious is the fact that only half the output is voltage protected. If the signal waveform is asymmetrical in such a way that the upper output transistor (Q1) is not overloaded while the lower one (Q2) is, then the lower one may burn out without triggering the protective circuit.

The other problem relates to the duration of the harmful signal. A signal burst of dangerous waveform will trigger the shorting of the input signal just as it would a harmful continued waveform. In fact, the circuit has no means of telling the difference since it either triggers the shunting transistor or it does not, depending on the precise voltage waveform present during current limiting conditions.

Obviously, if the voltage chosen (by the selection of a zener voltage


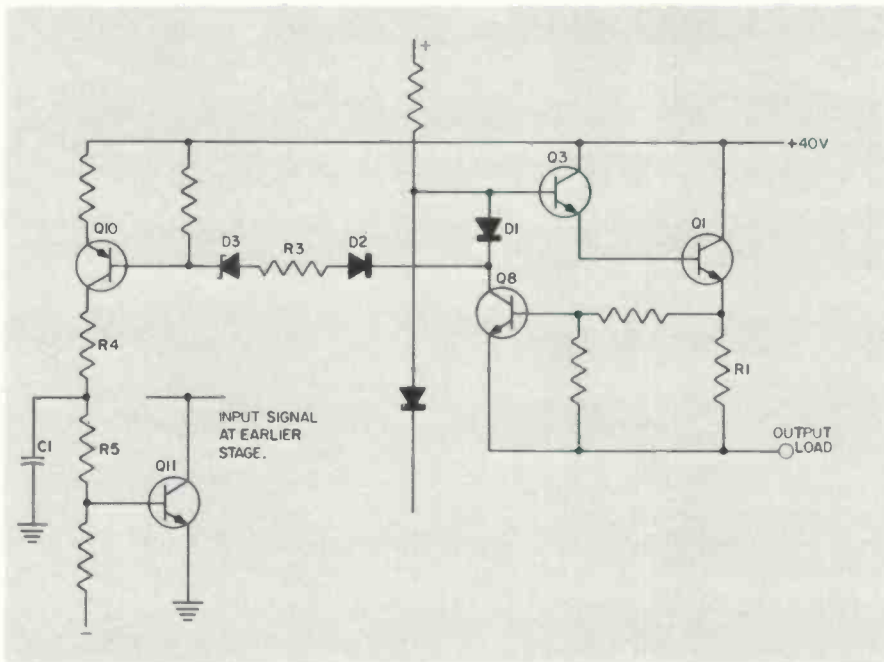


Fig. 3—Additional circuit features for providing protection against excess voltages across the output transistor when current limiting occurs.

Fig. 4—One simple addition to the circuit (capacitor C2, with appropriate changes) enables the circuit to discriminate between various degrees of excess power dissipation over different periods of time.

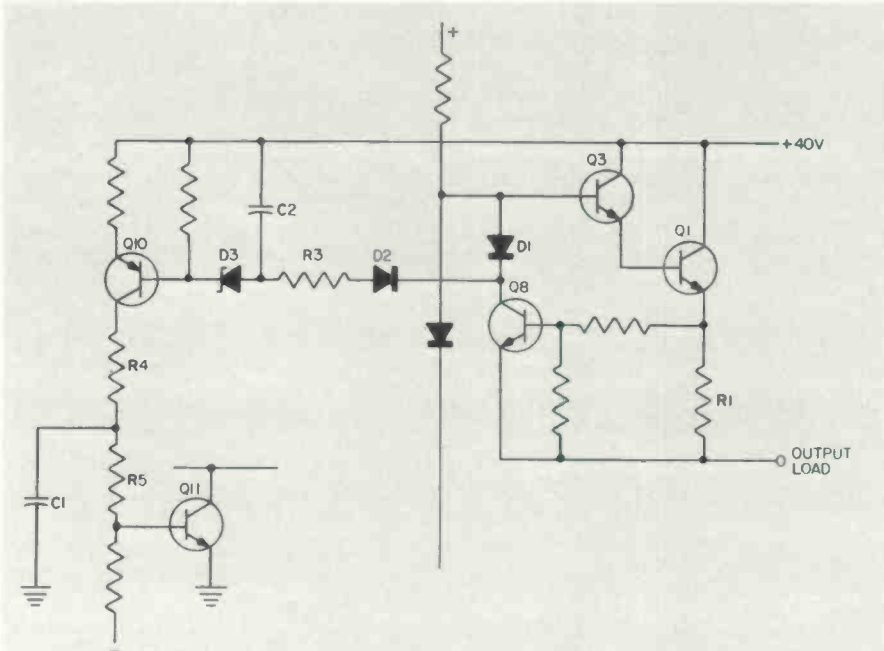



for diode D3) is such that the output transistor is protected from a power level that might require a second or more to burn it out; a signal burst of the same power level, but a shorter duration, would not endanger the transistor; though the protecting circuit would still be unnecessarily triggered.

Conversely, if the signal level chosen offered protection only under conditions that could produce almost instant burn out, a slightly lower signal level would not trigger it and, if sustained for a second or so, could destroy the transistor. Some compromise is needed that will take into consideration the duration of the excessive power dissipation, so that the protected circuit will be triggered at a lower power dissipation level for a sustained signal than it will for a more powerful, sharp audio pulse in the circuit.

This can be achieved by putting a time constant ahead of the zener diode (Fig. 4) with the use of a capacitor, C2. The series resistor (R3) must now be of a different value since it must now charge the capacitor as well as turn transistor Q10 on when the zener voltage is exceeded.

A similar circuit can be used to protect the other half of the audio output circuit. The semiconductors in this second circuit are of opposite polarity but function in the same manner as those shown in Fig. 4. Excess signal power turns transistor Q12 on (in the circuit shown in Fig. 5) in the same manner excess signal power turns transistor Q10 on (in the circuit shown in Fig. 4). When transistor Q12 is turned on (Fig. 5), its collector current turns transistor Q10 on.

One additional circuit refinement is still required for adequate protection of *both* output transistors. In Fig. 3, transistor Q11 shunts the positive audio input signal to ground to reduce the excess power applied to transistor Q1. This transistor (Q11) cannot operate at a reverse polarity to shunt a negative audio input signal to ground when excess power is applied to transistor Q2.

Fig. 6 shows a circuit that has been designed to handle this function. When excess voltages are ap-

plied to either transistor Q1 or Q2, transistor Q10 conducts current (as described with Fig. 5). As a result, a positive voltage is developed across capacitor C1, and the base of transistors Q11 and Q13 becomes forward biased. Transistor Q11 can then conduct excess positive input signals to ground as it did in Fig. 4, diode D8 preventing a damaging negative signal voltage from devel-

oping across the transistor.

As transistor Q13 conducts current, it forward biases transistor Q14, which in turn is also able to conduct current—excess negative signal voltages then being shunted through the two transistors (Q13 and Q14) to the positive supply.

## FINAL PROTECTIVE CIRCUIT

The complete circuit, shown in

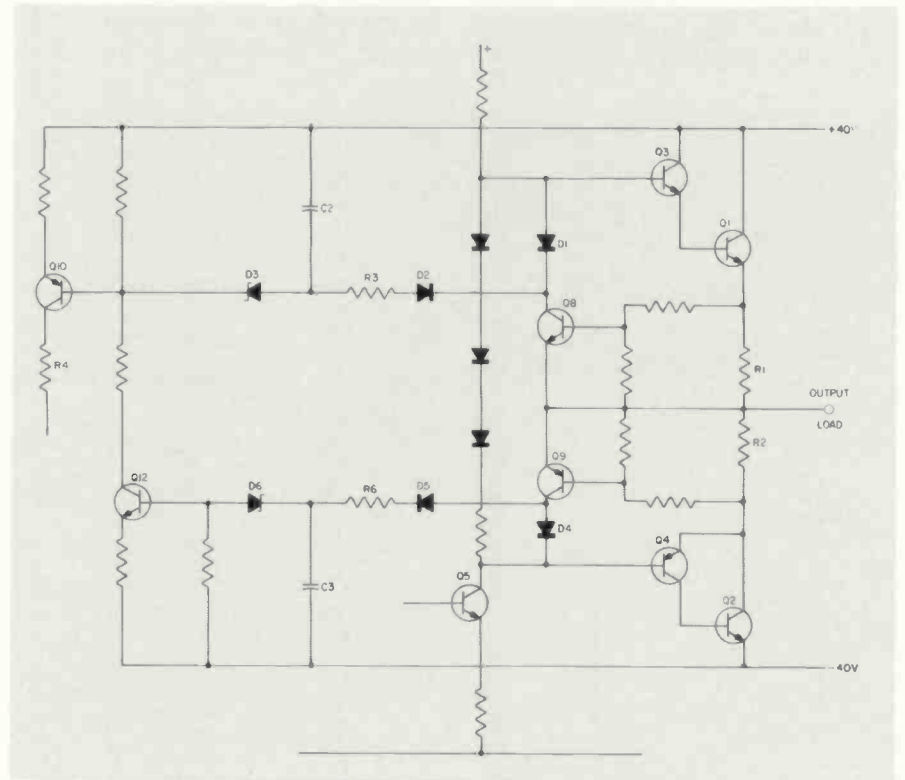


Fig. 5—Another addition to the circuit enables it to protect both output transistors equally.

Fig. 6—A two-way clamp circuit, used to provide protection for both halves of the audio output.

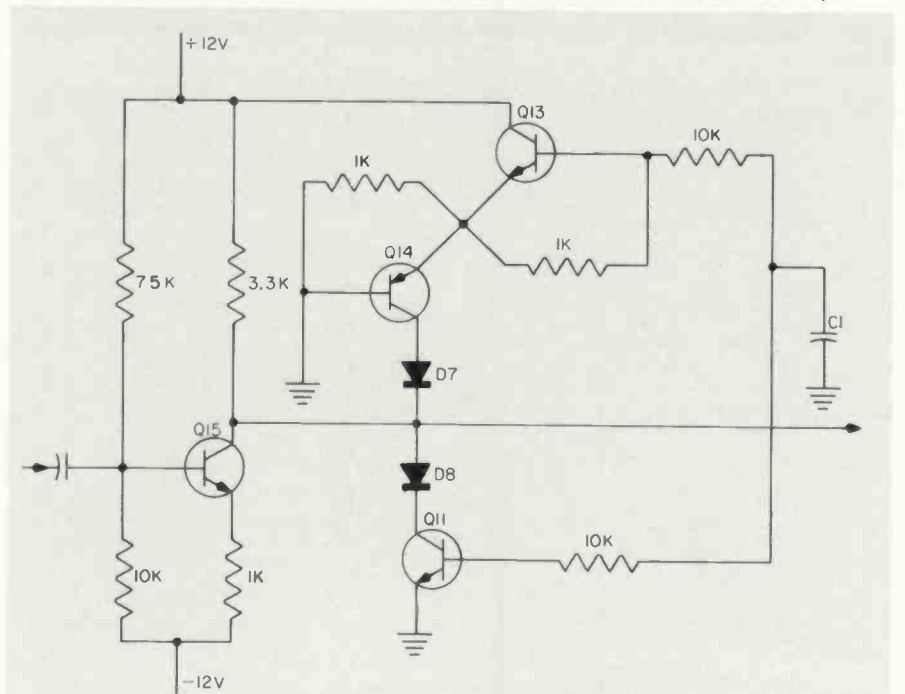


Fig. 7, illustrates the various properties of a circuit designed for output transistor protection. There, a burst of audio signal may momentarily exceed the circuit's power rating, triggering the protective circuit for but a second or two. This can occur when the audio burst is of too short a duration for capacitor C1 to become fully charged. Although this charge turned on transistors Q11, Q13 and Q14, it was relatively small and dissipated rapidly, the three transistors then ceasing to shunt the input signal.

A really serious signal overload—either short and sharp, or of lower amplitude but sustained—may trigger the protective circuit for 10 to 15 seconds, the time it takes a maximum charge across capacitor C1 to dissipate. If the signal is still dangerous when the circuit restores amplification, it will immediately trigger again. The circuit will continue to be triggered until the input signal re-

turns to normal, thus indefinitely maintaining protection.

The circuit can also protect against an increase in output transistor power dissipation resulting from reactive load (Fig. 1C). The impedance of the load might not be too low if it were merely resistive; but due to its reactance, the resulting voltage across the output transistor may become excessive. During a portion of this time the current-limiting segment of the protective circuit is functioning, and as a result the protective circuit starts to work, shunting the input signal as described previously.

### CIRCUIT MAINTENANCE


This is a typical, fairly sophisticated circuit. But as with the simpler current-protection circuit described in the previous article, an understanding of how it is designed to function is a major part of fault tracing it—any fault can then be de-

ductively analyzed.

The most obvious protective circuit failure would occur in the zener diodes. However, since the circuit is designed to keep them within their power dissipation ratings, when they exceed their zener voltages, the failure of any one of these diodes usually means that something else was wrong, which caused the diode to fail (i.e., failure may have been caused by a resistor that had changed value through overheating).

With a failure of this type, try to determine the prime cause of the failure and see that it is remedied. This is as important as replacing the component that eventually failed as a result of the problem. The same basic theory applies to all the other semiconductors in this type circuit. Whatever component has failed in this protective circuit, check to see what was the first cause of the failure. ■

Fig. 7—One version of a complete circuit, using the techniques developed in this article. Although a typical circuit, it may differ from any particular circuit being serviced.

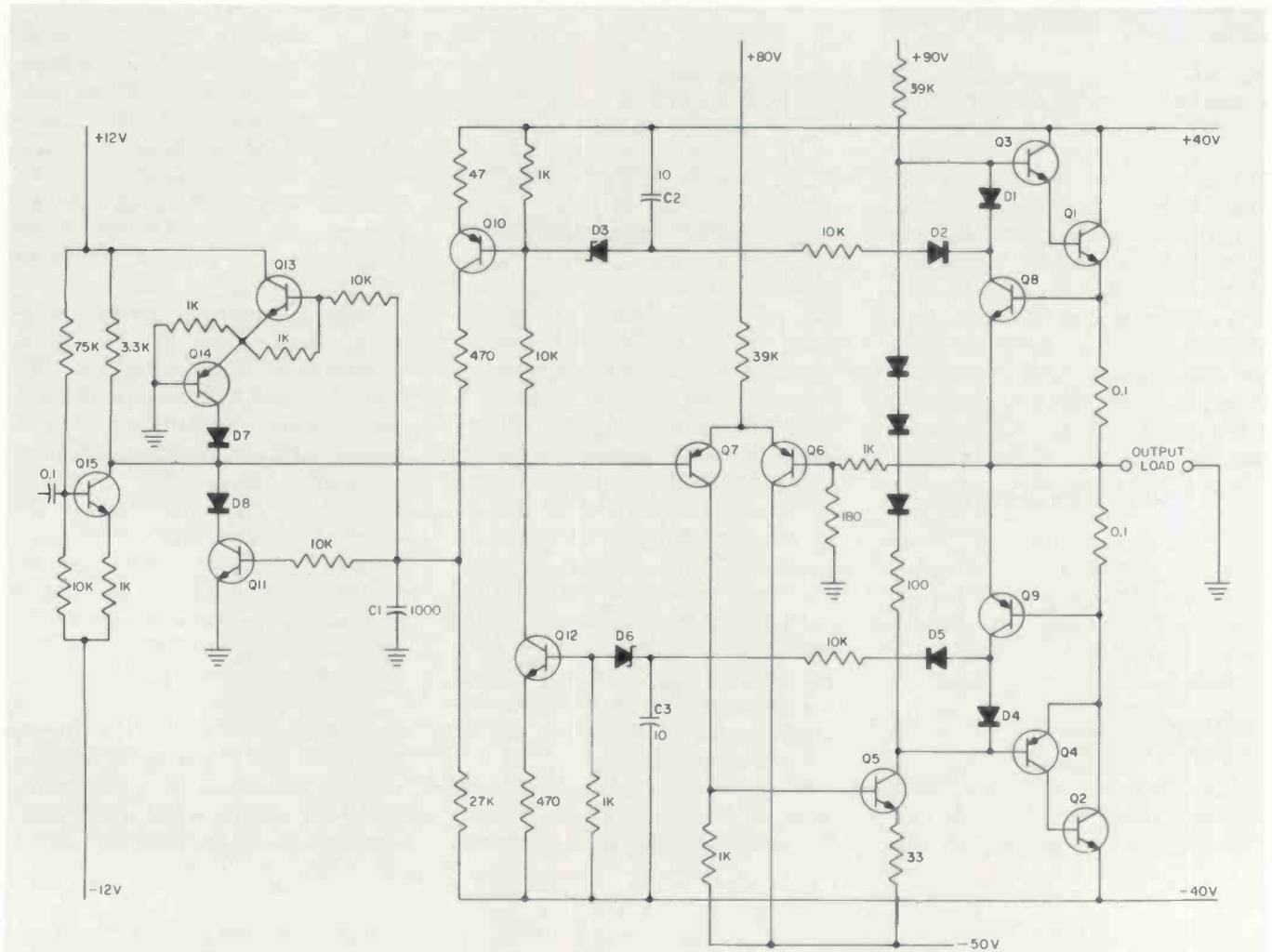



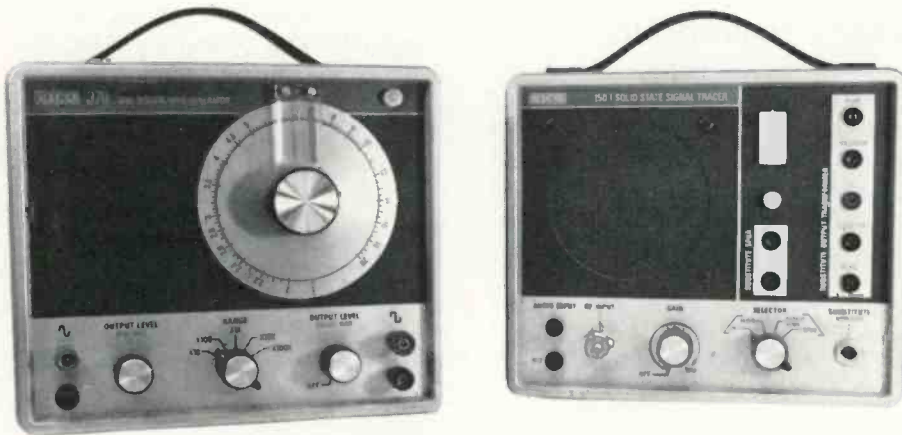
# EICO Model 379 Signal Generator and Model 150 Signal Tracer

by PHILLIP DAHLEN

Solid-state instruments designed for assisting in the maintenance of audio circuits



EICO's Model 379 signal generator (left) and Model 150 signal tracer (right). For more details circle 900 (generator) and 901 (tracer) on Reader Service Card.

■ The maintenance of audio circuits can be simplified with the use of EICO's Model 379 sine/square-wave generator and its Model 150 signal tracer. Built in matching cabinets with solid-state circuitry, these instruments are designed to inject and detect signals in all audio stages of circuits under test, and thus assist in the job of locating defective components.

## SIGNAL GENERATOR

The circuit used in EICO's Model 379 signal generator is shown in Fig. 1. Its function can be more readily understood by seeing what happens when a portion of a sine wave passes through it.

## OSCILLATOR SIGNAL AMPLIFICATION

When the gate of the field-effect transistor (Q1) becomes more positive (Fig. 2), it "pinches off" the

current flowing through the semiconductor, reducing the voltage drop across the source resistor (R4).

Since the base of transistor Q2 is connected directly to the source of FET Q1, this voltage change reduces the transistor base forward bias, and the transistor conducts less current. Being a zener diode, the voltage drop across diode D1 remains virtually unchanged as the transistor (Q2) emitter current changes—the entire change in voltage drop occurring across emitter resistor R5. In this manner, the diode permits the emitter of transistor Q2 to be biased at a different potential than the base of transistor Q3 without any resulting signal loss. Capacitor C1 shunts across the diode any small signal that might have still developed across it.

Since the base of transistor Q2 becomes less forward biased with less current flowing through resistor

R5, the voltage drop across that resistor (R5) is reduced, reducing the forward bias at the base of transistor Q3. That transistor (Q3) in turn conducts less collector-to-emitter current, resulting in a lower voltage drop across its collector and emitter resistors—the collector becoming more positive and the emitter becoming more negative.

Diodes D2 and D3 serve to provide a relatively constant voltage drop between the bases of transistors Q4 and Q5. Although the base of each transistor is biased at a different potential, the diodes maintain virtually constant voltage drops so that any change in transistor Q4 base bias voltage will result in the same amount of voltage change at the base of transistor Q5.

With the reduced voltage drop across resistor R6, as a result of transistor Q3 conducting less current, the base of transistor Q4 becomes more forward biased and there is a smaller resulting collector-to-emitter voltage drop across it (Q4). However, since transistor Q5 is an NPN rather than a PNP transistor like the others in the circuit, it (Q5) is less forward biased when its base becomes more positive; and there is a greater resulting collector-to-emitter voltage.

In the manner just described, a more positive voltage at the gate of the FET (Q1) results in a more positive voltage at the instrument's sine-wave output, while a less positive voltage at the gate will result

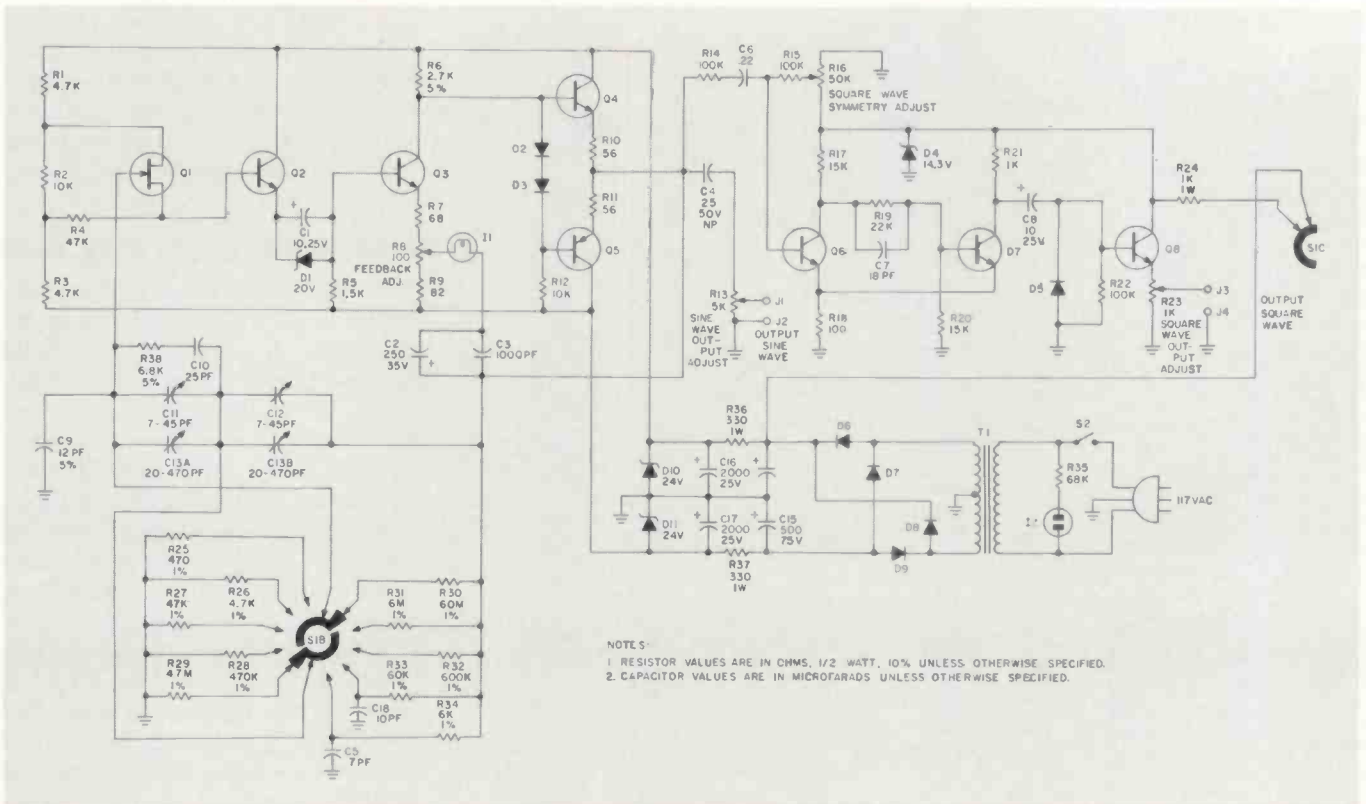


Fig. 1—Manufacturer's schematic of the EICO Model 379 signal generator.

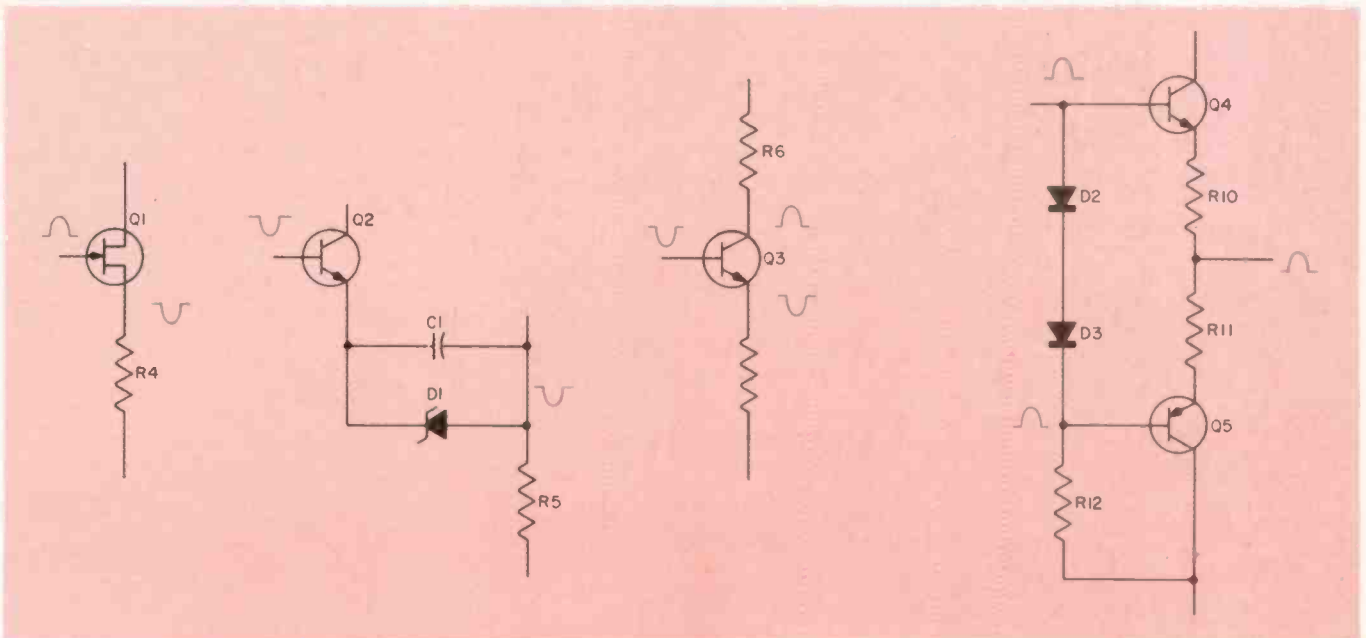


Fig. 2—Signal amplification in various stages of the oscillator circuit.

in a less positive output voltage—the change in voltage resulting in a sine-wave signal at the output.

### OSCILLATOR TUNING CIRCUIT

A bridge "T" network (Fig. 1) is connected between the output of the oscillator circuit and the gate of

FET Q1. It is composed of 1 percent precision resistors and a large two-gang tuning capacitor (C13A and C13B).

By tuning the two-gang capacitor and using series and parallel resistors to vary capacitor time constants, the "T" network (Fig. 3)

functions by changing the phase angle of all but the desired frequency signal. Sine-wave signals of the desired frequency return from the output to the FET gate, producing positive feedback and causing the circuit to oscillate at the desired frequency. Stray signals of other fre-



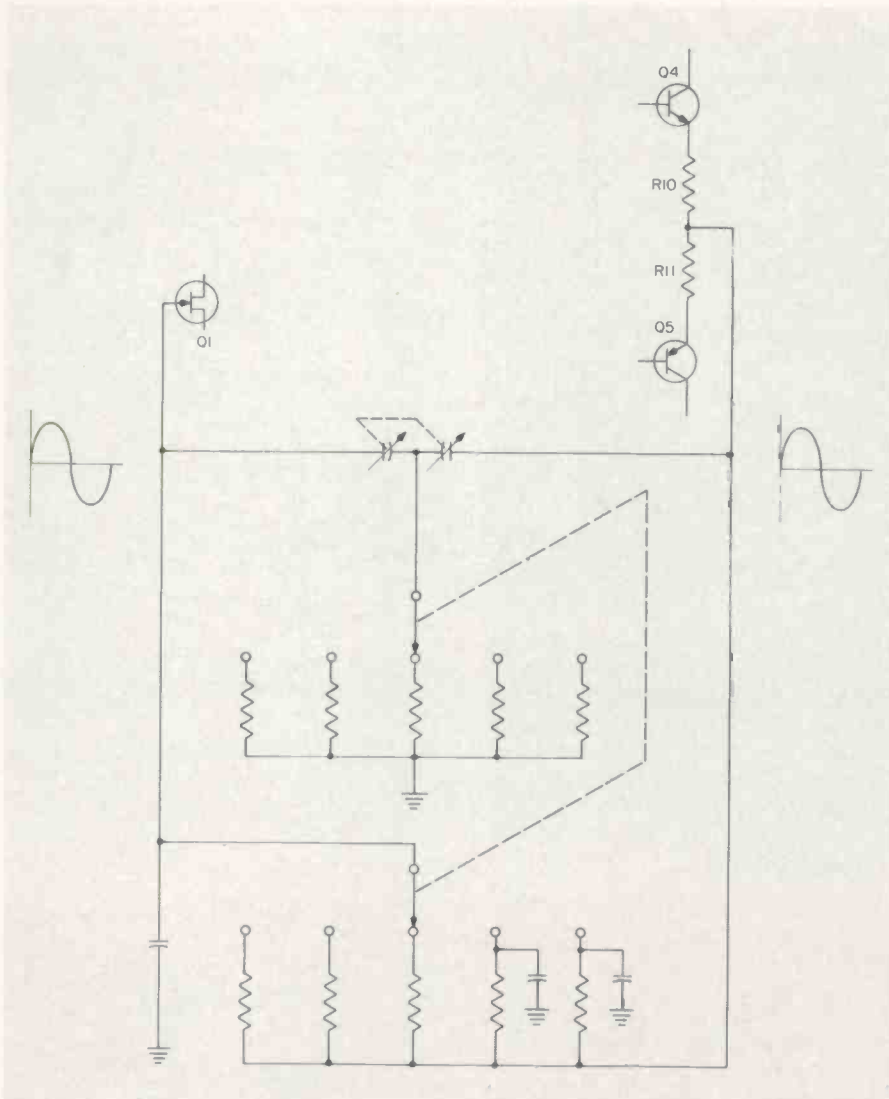


Fig. 3—Simplified diagram of the "T" network used to tune the oscillator circuit.

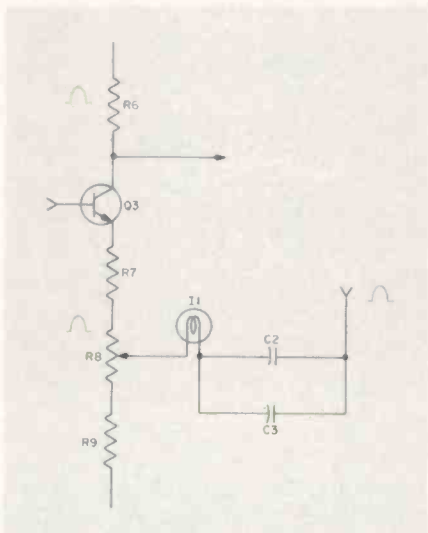


Fig. 4—Positive-feedback circuit used to increase oscillator output.

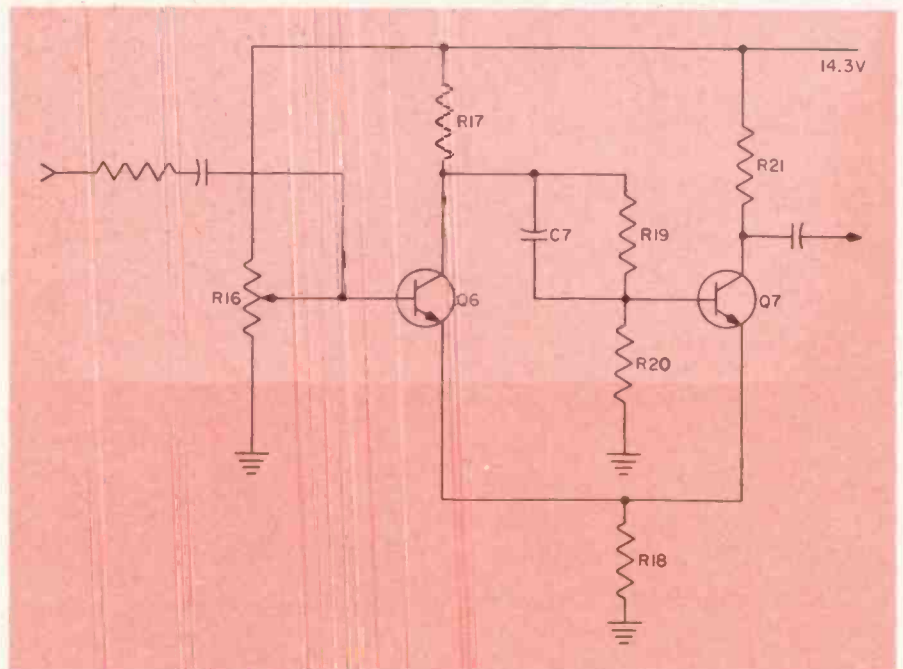


Fig. 5—Switching circuit converts sine-wave to square-wave signal.

quencies experience a phase shift in the bridge "T" network; and at these frequencies a positive signal output voltage will result in a negative signal voltage at the FET gate—the positive and negative signal voltages being cancelled out or neutralized.

### INCREASING OSCILLATOR GAIN

A second positive feedback circuit (Fig. 4) is also included in the instrument to increase the gain in the final stages of sine-wave amplification. When the positive portion of a sine wave passes from the oscillator output to the transistor Q3 emitter circuit, it makes the transistor's emitter more positive. If at the same time the voltage applied to the transistor's base remains unchanged, there will be a reduction in the base-to-emitter voltage. This positive emitter pulse thus has the effect of reducing the transistor's base forward bias, reducing the transistor's collector-to-emitter current and the resulting voltage drop across resistor R6. In this manner, the circuit functions as a common-base amplifier, with the positive feedback signal applied to the emitter circuit of transistor Q3 being amplified.

In an earlier description of the portion of the circuit containing transistor Q3 (Fig. 2), it was indicated that a negative signal voltage applied to the base of the transistor

will result in a negative signal voltage at its emitter. This negative signal emitter voltage is overridden by the positive signal-feedback emitter voltage. Thus, as feedback produces a positive signal voltage at the transistor's emitter while a negative signal voltage is applied to its base, there is an even greater reduction in the base-to-emitter voltage, even more greatly reducing the transistor's collector-to-emitter current and further increasing the positive signal voltage developed across resistor R6.

This second feedback circuit contains a 250mf capacitor (C2) for low-frequency feedback, while a smaller capacitor (1000pf, C3) conducts the higher-frequency signals that electrolectic capacitors are typically unable to handle due to the nature of their design. The negative resistance characteristics of the filament lamp (I1) protects transistor Q3 from excessive signal voltages that may develop as the band switch is turned. (Under normal operation this lamp glows dimly, glowing much more brightly as the band switch is turned. At one intermediate switching position this glow was seen to vary noticeably at a frequency of about 5Hz.)

### OSCILLATOR-FREQUENCY SWITCHING

Signals from the sine-wave output (Fig. 1) are fed to a switching circuit (Fig. 5). The positive portion of a sine-wave signal applied to the base of transistor Q6 will increase the transistor's forward bias, increasing the transistor's collector-to-emitter current and the voltage drop across resistor R17. As a result of this voltage drop, the base of transistor Q7 is less forward biased, it has less collector-to-emitter current, and there is a smaller voltage drop across resistor R21.

Since transistor Q7 provides additional amplification to the signal amplified by transistor Q6, the signal change in its emitter current is greater than the signal change in transistor Q6 emitter current. As in the sine-wave oscillator's second feed-back circuit (Fig. 4), emitter voltage changes from the higher stage of amplification (transistor Q7) will override those from the earlier stage (transistor Q6). Transistor Q6 then functions as both a common-emitter and common-base amplifier, and produces positive feedback at the input frequency, increasing circuit gain.

Sine-wave voltage changes at the base of transistor Q6 are amplified so greatly by this positive-feedback circuit that the two transistors (Q6 and Q7) will in effect act as switches, alternately turning on and off to provide a square-wave signal at the frequency of the applied sine wave.

### IMPROVING SWITCHING CHARACTERISTICS

Capacitor C7 helps improve the

circuit by shunting higher frequencies across resistor R19, peaking the frequency response of the switching circuit. Resistor R16 also helps improve the circuit by adjusting the base bias of transistor Q6 so that it will more-or-less readily conduct current as the sine-wave signal alternates between positive and negative voltages. If the base bias is too low, only the positive peaks of the applied sine wave will switch transistor Q6 on, transistor Q7 being on during a longer time interval. And if the base bias is too high, transistor Q6 will conduct until negative peaks of the applied sine-wave signal have adequately reduced the bias voltage, transistor Q6 conducting during longer time intervals than transistor Q7. For the positive and negative portions of the square wave to be of the same length (symmetrical), the bias adjustment must be such that each transistor alternately conducts current during equal time intervals.

Although most technicians use only symmetrical square waves, others also make use of non-symmetrical ones. By adjusting this control, positive square-wave pulses may be shortened so that they appear the same as positive symmetrical pulses normally produced at much higher frequencies, while the negative square-wave pulses correspond to negative symmetrical pulses normally produced at a slightly lower frequency—the complete square wave (both positive and negative pulses together) still being produced at the sine-wave frequency.

### SQUARE-WAVE OUTPUT CIRCUIT

Transistor Q8 (Fig. 6) supplies additional gain and stability by amplifying the square-wave signal,



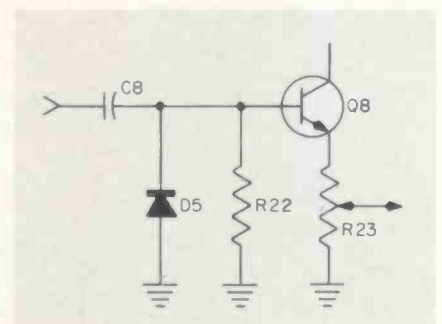



Fig. 6—Emitter-follower output circuit reduces square-wave distortion.

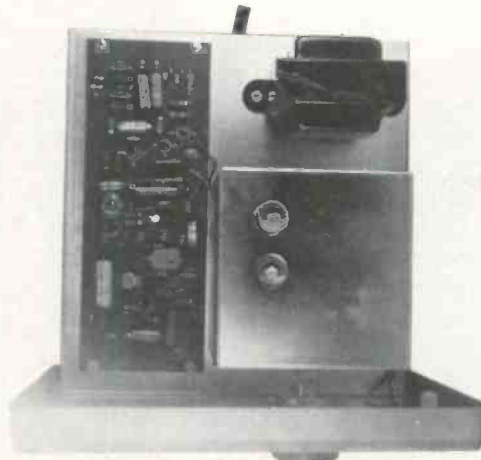

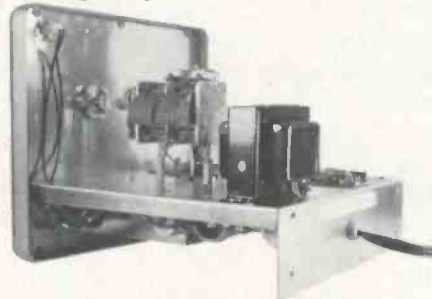Top inside view of signal generator with shield enclosing tuning circuit.



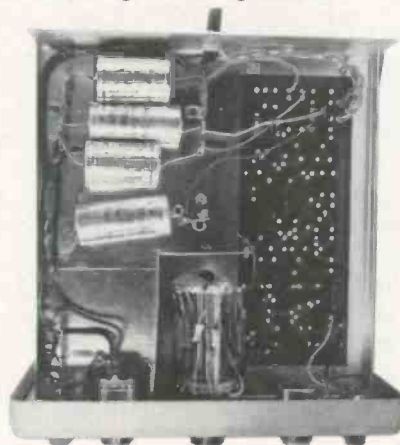Insulated two-gang capacitor used in signal-generator bridge "T" tuning network.



Bottom inside view of signal generator.



somewhat isolating the switching circuit from the output, and reducing the output impedance.

When the capacitor (C8) is positive with respect to ground, it forward biases the transistor (Q8), increasing its emitter current and the voltage drop across resistor R23. But when it is negative with respect to ground, diode D5 shorts the negative voltage to ground, thus protecting the transistor base from any damage resulting from a reverse base-bias voltage supplied by the capacitor, eliminating differentiation.

When the capacitor is negative with respect to ground, electrons (which flow from negative to positive) flow from the capacitor through the diode to the more positive ground, depleting the capacitor's supply of electrons. Then during the positive portion of the

square-wave cycle, the positive voltage at the capacitor forward biases the transistor (Q8). The capacitor is of a large enough value (10mf) to permit the flow of electrons from both the base of transistor Q8 and resistor R22, without a significant reduction in the base-bias voltage, before the square wave returns to a negative voltage—the transistor remaining switched fully on during the entire positive half cycle. Without the diode, there would not be sufficient flow of electrons out of the capacitor to maintain a sufficient positive voltage and keep the transistor fully on during the entire positive half cycle. A similar problem would occur during the negative half cycle. The "drooping" effect that would result is called differentiation.


Unlike the sine-wave output,

which is obtained through a capacitor (C4), the square-wave output is obtained directly from the emitter resistor (R23). This low-impedance signal source is not subject to the problems of differentiation just described.

## SIGNAL GENERATOR SPECIFICATIONS

The signal generator has a 20Hz to 20MHz sine-wave frequency range on five bands and simultaneously a 20Hz to 200kHz square-wave frequency range on four bands—the square-wave generator being automatically turned off on the 200 kHz to 2MHz band. The instrument reportedly has a calibrated accuracy of  $\pm 5$  percent from 20Hz to 100Hz and from 1MHz to 2MHz, with  $\pm 3$  percent accuracy between 100Hz and 1MHz. At 20kHz, square-wave

Fig. 7—Manufacturer's schematic of EICO Model 150 signal tracer.

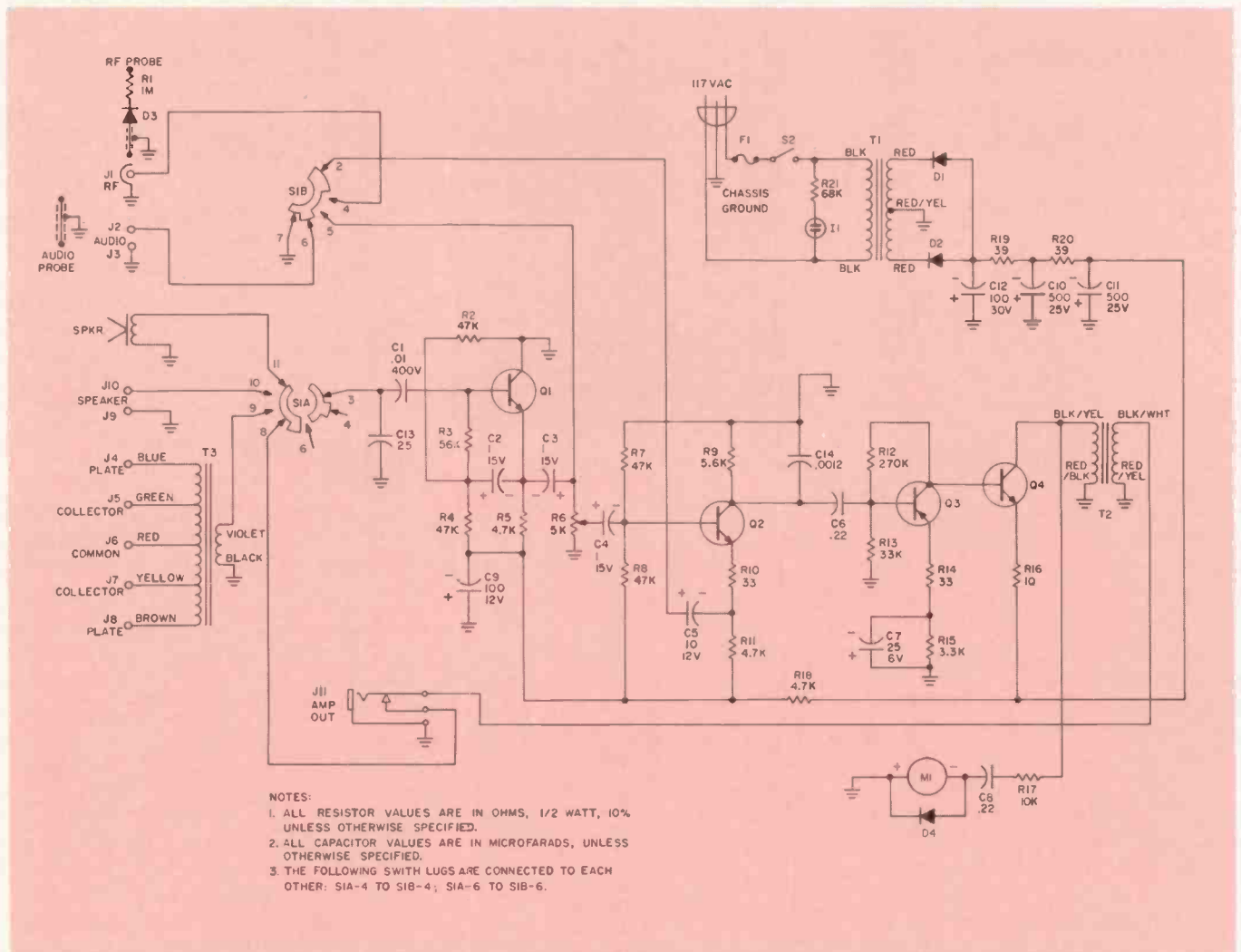

rise time is said to be less than  $0.1\mu$  sec.


## SIGNAL TRACER

The circuit used in EICO's Model 150 signal tracer more closely resembles those with which the average electronic technician is familiar (Fig. 7).

### BOOTSTRAPPED INPUT CIRCUIT

The first stage of amplification uses a "bootstrapped" circuit (Fig. 8) in which positive feedback is used to reduce the effective input impedance. When the positive portion of a signal is applied to the base of transistor Q1, it is more forward biased, conducts more collector-to-emitter current, and there is a greater voltage drop across resistor R5. This positive signal voltage across the resistor (R5) is fed through

Fig. 8—"Bootstrapped" circuit used to increase signal-tracer input impedance.

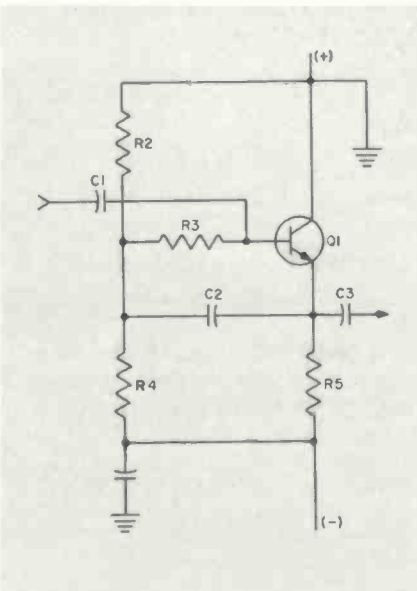

Top inside view of signal tracer.



capacitor C2 back to the base of transistor Q1, the positive-feedback signal current being reduced by resistor R3 to prevent the circuit from going into oscillation. By reducing the amount of input signal current required to provide the same output signal across capacitor C3, the circuit, in effect, reduces its input impedance.

### OTHER AUDIO CIRCUITS

Additional amplification is provided by transistor Q2, which obtains its signal through a capacitor (C4) from the volume control (R6). Any RF signals remaining after this stage of amplification are shunted to ground through capacitor C14, while other signals pass through capacitor C6 to the two following stages of amplification.

As the voltage drop across transistor Q3 varies with the signal applied its base forward bias, a change in voltage occurs at the transistor's collector and emitter. By shunting some of the emitter's signal to ground with capacitor C7, more signal voltage must develop at the transistor's collector during each change in collector-to-emitter voltage. Thus as resistor R15 reduces the dc emitter current to match the dc characteristics of the transistor to the circuit, capacitor C7 increases amplification by reducing the corresponding signal emitter current.

### CHANGING CIRCUIT FUNCTION

The signal generator contains a four-position function-selection switch. When turned to the RF position, capacitor C5 is connected to ground and the RF terminal is connected to capacitor C1. With one lead grounded, capacitor C5 functions like capacitor C7 (described

previously) to increase the amount of amplification in the circuit's second stage. After the final stage of amplification, the signal may be either taken directly from the amplifier to improve scope or other instrument sensitivity, or to drive the internal speaker when the amplifier jack is not used. The relative strength of the amplified signal is indicated by a handy meter.


Since less gain is generally required in amplifying signals applied to the audio terminal, turning the function-selection switch to the audio position disconnects capacitor C5 from ground, while connecting the audio input terminal to capacitor C1. Disconnecting the capacitor (C5) allows a signal voltage to develop across resistor R11, reducing the remaining signal voltage developed across resistor R9 and applied to the following stage of amplification. The signal is then amplified as was the audio signal applied to the RF terminal. (If greater gain is required, the audio signal may be applied to the instrument's RF terminal since the RF probe converts RF signals to audio signals before they enter the RF terminal.)

The selector switch grounds the audio input terminal and RF input terminal until they are selected—the audio input being grounded when the RF input is selected and vice versa. To eliminate any stray signals when the internal speaker is used either alone or through the substitute output-transformer circuit, the selector switch grounds not only signals present at the RF and audio input terminals but also those present at the volume control (R6), while disconnecting the amplifier from the speaker.

### SIGNAL TRACER SPECIFICATIONS

The signal tracer's audio output is rated at 400mw with a 1mw RF input or a 65mw audio input. The meter reportedly contains a  $200\mu$ a movement, and the substitute transformer included is designed to match the speaker impedance with the impedance of typical amplifier output tubes or transistors. Specifications indicate that the hum is better than 60dB below 400 mw. ■

Bottom inside view of signal tracer.

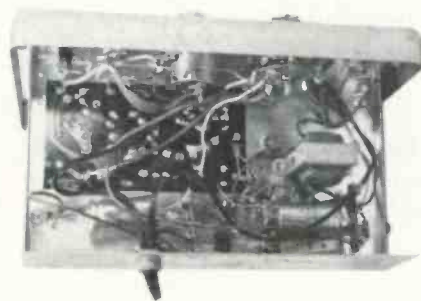



For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.

### CLOSED-CIRCUIT CAMERA 700

*Built-in automatic light compensator*

Introduced is the Model MC920 Mini-Pro Camera, a reported breakthrough in the development of surveillance cameras. Entirely of solid-state, module construction, the camera comes in an attractive gray aluminum case, approximately half the size and weight of other transistorized cameras. Featured is the automatic light compensator, which is built in directly behind the lens and responds to changing light conditions. Other features are said to include switchable RF and Video output, rear electronic focus for ultra sharp image adjustment, and thermally compensated circuitry for continuous operation. Simplicity of installation and operation are other features of the camera. The camera weighs 4 lb and measures 2 $\frac{5}{8}$  by 4 $\frac{3}{4}$  by 7 in. Net price under \$200. Javelin



### STEREO HEADPHONE 701

*Listening level from 50 to 16,000Hz*

Introduced is the Model 10R200 stereo headphone set which features extremely high sensitivity, reportedly capable of delivering over 100dB of sound with as little as 10mw input.




The frequency response of the headphone set yields a listening level from below 50Hz to beyond 16kHz. The soft, foam ear pads enhance the bass response and affords greater listening comfort. Freedom of movement is provided for the listener by a 6 $\frac{1}{2}$ -ft. cable. The standard stereo plug allows universal application to stereo amplifiers equipped with the usual headphone jacks. The price of the headphone set is \$19.95. RCA
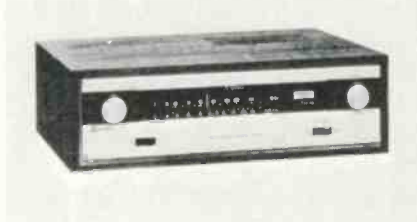
### CITIZENS BAND SCANNER 702

*Visually monitors all CB channels*

A 23 channel Citizens Band scanner has been designed to permit visual identification of all CB channels in use. This unit is designated Scanalyzer 23, Model 779. This solid-state scanner reportedly allows continuous and simultaneous visual monitoring of all 23 channels and permits the instant determination of the channels in use. It reportedly can also be used to determine the signal strengths of all 23 channels by the use of an adjustable sensitivity control, which can be used to visually indicate each channel having a signal exceeding the pre-select sensitivity level. The response time of individual channel indicators is reportedly less than 10ms. Sensitivity is




said to be better than 0.5 $\mu$ v with selectivity rated at -80dB at  $\pm$ 10kHz. Another control is designed to permit adjusting the RF sensitivity over a range of from 0.5 $\mu$ v to 100 $\mu$ v. The scanner is an all solid-state unit employing 38 semi-conductors. Price \$149.95. Commander

### RECORD/PLAYBACK DECK 703

*Pre-select the amount of tape you want to hear or record*

A Model RD8S eight-track record/playback tape deck is introduced. Incorporated in the deck is an exclusive

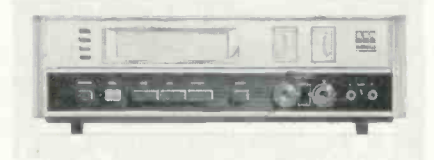operating feature that allows the user to pre-select how much of the tape he wants to hear or record. The deck will play the entire tape continuously or automatically eject the tape after the




first or fourth program. This feature overcomes the most common cause of eight-track cartridge damage. The deck is of particular interest to the customer who already owns an eight-track playback system for his car. With this deck, he can record his own tapes at home and by doing so can quickly amortize the cost of the deck by making his own tape library. The deck comes complete with a factory-installed walnut cabinet and 3 ft. patch cord. BSR

### COLOR-TV SET 704


*Table model of Early American design*

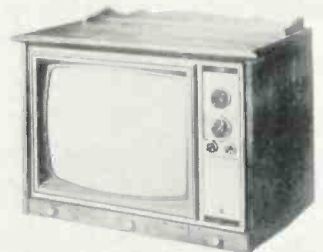Introduced is a table-model color-TV set of Early American design, complete with top gallery rail. The Colonial, Model CT-391E, has an 18 in. diagonal screen. Features include Panalock (AFT), which is designed to allow the viewer to instantly lock in the best picture electronically with a touch of a button. Another feature is



the Auto-Color, a new feature where pre-setting at the factory is said to automatically lock in color on every channel. The use of "Speed-O-Vision" eliminates a "warm-up" period by offering instant picture and sound. The set also includes dipole and bowtie antennas, separate UHF and VHF channel selectors plus a 5 by 3 in. oval speaker. Retail price \$419.95. Panasonic





**professional  
hands require  
years of training**

**professional TV  
service dealers insist on  
GE ULTRACOLOR picture tubes  
(made by professionals for professionals)**

**GENERAL  ELECTRIC**

**TUBE DEPARTMENT  
OWENSBORO, KENTUCKY 42301**





**TWO YEARS AGO  
WE PROMISED  
MIRACLES  
FROM  
BLUE STUFF**

We Promised that  
**BLUE STUFF**  
would. . . . .



**BLUE STUFF**  
A CAN FULL  
OF MIRACLES



P. O. Box 949 ■ Amarillo, Texas  
Canada: Wm. Cohen, Montreal  
Export: Empire Exporters, N.Y.C.

... for more details circle 131 on Reader Service Card

**ET/D CATALOGS & BULLETINS**

**400 Semiconductor and Components**

A condensed semiconductor and components catalog is available. This 60-page booklet, CC300, provides information on new products as well as a listing of semiconductor product lines. A 10-page section highlights recently introduced semiconductors, ranging from TTL/MSI integrated circuits through discrete optoelectronic devices. Preferred semiconductors recommended for current and new designs are easily identified in this publication. Condensed listings are given for TI's integrated circuits, silicon transistors, optoelectronic devices, germanium transistors, diodes, rectifiers, resistors, microwave components, thyristors, trigger diodes and power transistors. Electrical parameters, mechanical data, product features, application information and circuit diagrams are provided. Seven pages are devoted to case outlines of discrete devices and a military device selection is featured. Texas Instruments.

**401 Electronic Test Accessories**

A 56-page catalog of electronic test accessories is offered. The edition contains 420 items—50 of which are new this year. The general catalog contains the entire line of 3/4 and 1/2 in. spaced molded test accessories, molded patch cords, cable assemblies, test leads, connecting leads, test socket adapters, "Black Boxes" and other electronic test accessories; all designed to meet rigid industrial and military specifications. Catalog provides complete engineering information on all items, including product photographs, dimension drawings, schematics, specifications, features and operating ranges. Pomona.

**402 Electronic Hardware**

A catalog No. 2570 containing wire, cable, tubing and hardware to the electronics industry is offered. The new catalog is a distillation of the full-line catalog and contains those products most in demand by distributors. The catalog will make it easier for most customers to find what they are looking for quickly. Birnbach.

**403 Power Supplies**

Nine lines of dc power supplies are introduced in a catalog supplement now available. Described are a new LV series of high efficiency, low-ripple power modules designed to power

TTL, ECL, DTL, RTL and HTL logic. This series offers ripple as low as 10mv RMS. An LW series of dc power modules, designed to power transistor circuitry, relays, motors, lamps and solenoids, are also introduced. Other new products include an LXD-3-152 dual output tracking power supply, designed to power operational amplifiers and an integrated circuit regulated laboratory power supply with built-in tracking overvoltage protection, and an LCS-A package modular power supply that is IC regulated and available in 19 fixed voltage models to 150vdc and up to 3a, and 5 wide range models to 120vdc, up to 2a. Lambda.

**404 Instructional TV Fixed Service**

An 8-page catalog of hardware for equipping school districts and individual schools with complete Instructional Television Fixed Service (ITFS) 2500MHz micro-wave systems is issued. Available to educators and ETV system contractors on request, the new catalog covers 10w transmitters, mini-power transmitters, micro-power transmitters, repeaters, receiving systems, down converters, distribution systems, transmitting and receiving antennas, accessories and calibration equipment. Using this equipment, a school district may originate one to four instructional TV channels and transmit them to all schools within the district. JFD.

**405 Recording Tape**

Offered is a confidential distributor cost sheet which lists distributor cost and suggested resale prices for all of the company's audio tapes, cassettes and accessories. It now combines three previous pricing sheets into one easy-to-use reference. The new distributor pricing sheet also spells out terms and conditions, standard packaging, pre-paid freight, assorting privileges and cash discount. Irish Recording Tape.

**406 Clips/Insulators**

An 8-page catalog No. 350 containing electric clips and insulators for quick, temporary electrical connections is offered. Complete specifications are given for each clip and the line is fully illustrated: miniature clips, alligator clips, completely insulated alligator clips, crocodile clips, "Pee-Wee" clips, general purpose test clips, heavy-duty test and battery clips, welding ground clamps, a general ground clamp, plier-type clips for automotive battery booster cables and battery chargers and testers, complete battery booster cable sets, ignition cable assemblies, also a twin-ended test clip and a needle clip. Mueller.



# Shortstop.

Our exclusive posted-filament design stops shorts in high-voltage rectifiers.

And you know what shorts cause . . . catastrophic failure, or weakened tubes and components.

The result: unprofitable callbacks.

Our 3CU3A, 3BM2A, 3BL2A, and 3DC3 high-voltage rectifiers all use the fail-safe posted-filament design.

Put our shortstops on your team. You'll find that callbacks won't even get to first base.

Sylvania Electronic Components, Electronic Tube Division, West Third St., Emporium, Pa. 15834.

**SYLVANIA**  
GENERAL TELEPHONE & ELECTRONICS



**Jerrold Offers  
MATV Course**

The second in a series of comprehensive courses on master antenna television (MATV) presented by Jerrold Electronics Corp. was held recently at the O'Hare Concord Motel in Chicago and attended by dealers and distributors from a wide midwest regional area.

Sponsored mostly for Jerrold representatives, the three-day course, conducted by Jerrold's senior systems engineer Allen Pawlowski, included discussions on decibels, antennas, amplifiers, system layout, headends and J-Jacks.

"Through these concise and to-the-point courses we intend to build a nationwide cadre of representatives updated in the state-of-the-art and able to provide fast and quality service," reported Bert Wolf, manager of Jerrold's Distributor Sales and Educational and Communication Systems Divisions.

MATV courses are scheduled for other U.S. cities, three of which will include discussion on instructional television (ITV). A separate class on instructional television fixed service (ITFS) was held in Philadelphia, June 24-26.

Courses are scheduled for New Orleans, July 14-16; Salt Lake City, September 17-18; San Francisco, September 21-23, and Atlanta, October 27-29. A one-day summary seminar will be held in Denver on September 15.

**Precision Tuner  
Service Moves**

Precision Tuner Service announced its move to a new modern air conditioned plant at 5233 South Highway 37, Bloomington, Ind. The plant covers 4800 sq. ft, with offices for company executives, a large lounge for employees, and a huge, well planned area for receiving and shipping.

Repair positions have been laid out carefully to provide excellent lighting and generous work space for each technician. The company currently has 14 positions in operation, and plans to open 10 more positions as soon as equipment becomes available.

About half of the floor space is devoted to storage of spare tuners and parts.

**First Single Tube, Black-and-White  
TV Camera Convertible to Color**

RCA announced the television industry's first single-tube, black-and-white TV camera that can be converted to full color operation.

Basically a high-resolution monochrome camera, the new PK-430 produces color pictures when a special color-encoding optical system is added and a small package of color processing electronics is plugged in, according to Gordon W. Bricker, Manager, RCA Professional Electronic Systems.

He said the new design permits educators, industrial trainers, cable TV operators and other closed-circuit TV users to invest in black-and-white program equipment without risking camera obsolescence when they decide to switch to color. Changeover to color operation normally requires the purchase of color cameras to replace monochrome models.

The convertible camera, scheduled for deliveries begin-

ning this fall, is priced at \$5995 and the equipment needed to modify it for color operation at \$4755. Factory-built color-TV cameras range in price from approximately \$10,000 to more than \$80,000.

In the one-tube system, color information is obtained by passing light from the televised scene through two striped filters before it reaches the pickup tube. This technique also produces other essential information about picture detail, content and brightness. The information is gathered on the face of the single tube and processed electronically to produce the color picture.

When the camera is converted for color, it employs this optical system in conjunction with an electronic color processor. The latter occupies only about 10 in. of space in the standard TV equipment rack.


The basic black-and-white camera includes a 10:1 zoom and a type 8507 vidicon tube, which is said to provide a horizontal resolution of 600 lines for detailed pictures.

**Supreme Publications  
Increases Staff**

Supreme Publications of Chicago and Highland Park, Ill., announced its continued activity in supplying service manuals with releases planned for early Fall on new and separate black-and-white and color TV manuals. Almost doubling its publication staff, Supreme plans to introduce a unique production technique in manual preparation.

*continued from page 30*

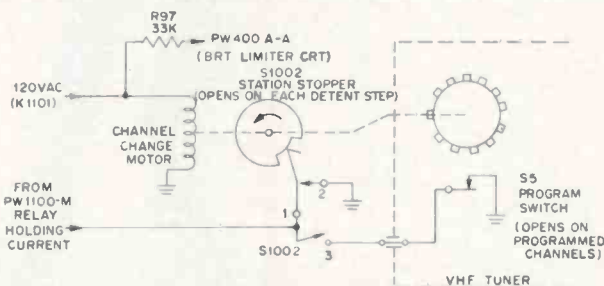armature closes contacts 1-3 on S1102 (station stopper switch), and they remain closed while the motor is activated. The rotation of the tuner shaft closes contacts 1-2 on S1102 to complete a path to ground for the channel-



change relay. This relay holding current path connects to PW1100-M and the collector of transistor Q1101 through resistor R1110 (1800Ω), furnishing sufficient current to hold relay K1101 in an activated mode. The motor will continue to run after the keying signal is removed. Just prior to every detent position of the tuner, contacts 1-2 on S1002 open so that if the next channel is programmed "in," the motor stops—since the holding current path for the channel-change relay is opened. If the next station is programmed "out," just prior to the opening of contacts 1-2 on S1002, the programming switch closes to furnish a holding current path for the channel-change relay through contacts 1-3 on S1102 and the programming switch. This action maintains the motor activated and prevents the tuner from stopping on an unwanted (unprogrammed) channel until desired channel is reached.



## Discovery in the art of performance

Find *your* sound! The Starmaker collection not only includes microphones for many different applications, but—even more important—microphones to enhance the personal techniques of professional performers as well.

You can choose characteristics like "flat" frequency response. Tapered low-frequency response. Switchable Bass Roll Off. A host of others. To make "today's" sound come alive—close up or far out.

That's the way it goes up and down the Starmaker

line (at optional list prices from \$12 to \$93). For pop, rock, and classical performers. At concerts, theatres, night clubs. In reel-to-reel and cassette home recordings. For discussion/panel, paging, P.A., CB, and ham applications... you name it.

To get specific, ask for the new Starmaker brochure 1S1056 at your RCA microphone distributor or, write: RCA Electronic Components, Commercial Engineering, Section 69G /J10, Harrison, New Jersey 07029.



And, remember, for further professional needs, RCA also produces the renowned BK and SK microphone lines.

# RCA

... for more details circle 121 on Reader Service Card




For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.
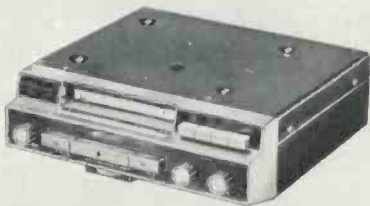
### CASSETTE RECORDER/FM 705 MULTIPLEX RADIO

*Has direct stereo  
record feature*

A Model TPR-2011 cassette stereo-recorder/FM-multiplex radio combination features mode controls, automatic volume control for recording, mono-stereo, FM multiplex, left and right balance, tape record and tape playback, fast forward and reverse—plus automatic cartridge pop-out, when the music program is completed. A mounting bracket, four-prong con-



ductor, fuse and head cleaner are reportedly standard accessories. The unit operates from a 12v system, weighs 7 lb and measures 9¼ by 9¼ by 3 in. List price is \$199.95. Aiwa

### UHF BROADBAND AMPLIFIER

*Built-in output  
UHF/VHF multiplexer*

706

The Model CUB-50 solid-state broadband UHF amplifier is used to amplify UHF-TV signals for direct "on-channel" distribution in MATV systems, eliminating the need for headend UHF-to-VHF converters. The unit reportedly features low-noise and high-output capability obtained through the exclusive use of silicon transistors. A control on the front panel reportedly permits adjusting the UHF gain over a 21dB range. The unit also has a built-in output UHF/

VHF multiplexer. This feature permits the use of the amplifier with a companion VHF amplifier, without the need for any external mixing equipment. Manufacturer's specifications: Gain—41.5dB. Bandpass—±0.7dB flatness at full gain. Gain Con-



Control Range—20.5dB to 41.5dB gain. Noise Figure—10.0dB. Maximum Input, Per Channel (gain controls at minimum gain)—37dB (70,000μv) single channel for less than 1dB gain compression; 28dB (25,000μv) for three channels. Maximum Output Per Channel (for —46dB crossmodulation products)—+59dB (0.9v) single channel and 50dB (0.3v) each channel for three channels (at threshold of perceptible interference). Output Test Jack—30dB ±2dB, minimum return loss 14dB (1.50VSWR). Output Multiplexer—VHF through loss—0.75dB. VHF return loss—23dB (1.15 VSWR). Size—8¾ in. L by 5¼ in. W by 3¾ in., universal slotted mounting. Blonder-Tongue

## EXCLUSIVE! NOBODY BUT NOBODY CAN TOP THESE FEATURES!

- PRIORITY CHANNEL SIGNAL LOCKS TO THE EXCLUSION OF ALL OTHER SIGNALS\*
- CARRIER DELAY ALLOWS OPERATOR TO HEAR THE MOBILE CALLBACKS\*
- MANUAL SELECTION ACCOMPLISHED BY SLOW SCAN TECHNIQUE\*

## SONAR-SCAN™ FM MONITOR RECEIVERS

A new standard of excellence that defies comparison. With versatility that's surpassed only by performance. It's advanced design, circuitry and unusually crisp clear sensitivity (0.5μv) are only a few of the many features for the ultimate in FM Monitor Receivers. Plus SONAR-SCAN will signal search and automatically lock a signal on any of 8 pre-programmed channels... Solid state—for rugged use over a wide temperature range... Noise free squelch... 8 crystal controlled channels... Dual purpose power supply for 117VAC or 12VDC, negative or positive ground. Once you see and hear the difference you will know why SONAR represents the standard of value that defies comparison.

FR-2514 (25-50MHz) FR-2515 (150-175MHz)  
Comes complete with AC and DC power cables,  
mounting bracket less crystals — Crystals \$5.00 ea.

\$189.95

EXCLUSIVE WITH SONAR and PATENT PENDING \*



**SONAR RADIO  
CORPORATION**  
73 Wortman Avenue  
Brooklyn, N.Y. 11207

Send information on Model FR2514/15 SONAR-SCAN.  
Dept. 896

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

### VHF MONITOR RADIO 707

*Automatically receives any  
combination of both high- and  
low-band signals*

The Hi/Lo Monitorradio Scanner is designed to automatically receive any combination of both high- and low-band signals. The radio is capable of scanning any mixture of frequencies in the 30 to 50MHz and 144 to 174 MHz ranges, through eight crystal-controlled channels. The receiver can reportedly cross-band monitor police, fire, radio telephone and marine signals in either band. The unit searches for a signal with the process detailed by read out lights for each channel. Upon detection of a high- or low-band signal, the receiver stops to monitor the entire transmission. At completion

*continued on page 72*

... for more details circle 129 on Reader Service Card

**GENERAL  ELECTRIC  
COMPANY**

OAK BROOK EXECUTIVE PLAZA, 1301 W. 22ND STREET, OAK BROOK, ILLINOIS 60521 (312) 654-2030

**ELECTRONIC  
COMPONENTS  
SALES  
OPERATION**

May 15, 1970


TO: THE INDEPENDENT ELECTRONICS DISTRIBUTION AND SERVICE INDUSTRY

Many inquiries have been received from independent distributors, service dealers and technicians as to General Electric's long-range posture with respect to the electronics service business.

As a Company, General Electric is basically a manufacturer and, therefore, is concerned primarily with the investment of capital and capabilities in technological developments in such areas as integrated circuits, nuclear power, computers, jet engines, appliances, chemicals and with the growth of many other existing businesses.

As a manufacturer, the Company has a long-term interest and obligation to assure complete customer satisfaction and is continually examining new approaches to fulfill this obligation with respect to its own products, including television sets.


ON THE OTHER HAND, GENERAL ELECTRIC IS ALSO A COMPONENTS MANUFACTURER AND, AS SUCH, WE PLACE AN EXTREMELY HIGH VALUE ON OUR RELATIONSHIPS WITH INDEPENDENT DISTRIBUTORS AND INDEPENDENT SERVICE DEALERS AND TECHNICIANS. THESE RELATIONSHIPS OF MUTUAL RESPECT AND UNDERSTANDING WERE CAREFULLY AND DILIGENTLY DEVELOPED OVER THE LAST QUARTER CENTURY BY PEOPLE WHO, WHILE REFLECTING WITH PRIDE ON THE PAST, LOOK TO A FUTURE OF CONTINUED COOPERATION, GROWTH AND PROFITABILITY. WE SEE NO REASON TO ABDICATE THESE LONG-STANDING RELATIONSHIPS. WE PLAN TO CONTINUE OUR SUPPORT OF THE INDEPENDENT DISTRIBUTION AND SERVICE CHANNELS AND WE ARE CONFIDENT THEY WILL CONTINUE TO PLAY A VITALLY IMPORTANT ROLE IN THE SERVICE INDUSTRY.

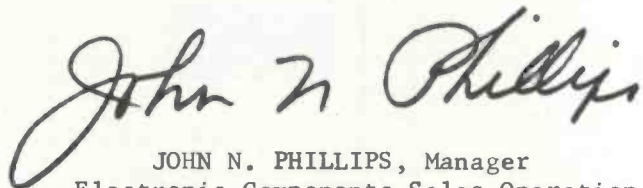  
JOHN N. PHILLIPS, Manager  
Electronic Components Sales Operation

... for more details circle 112 on Reader Service Card



## Electronic Circuit Design Handbook

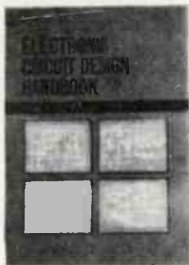

New Third Edition—A brand-new, enlarged edition of the ever popular circuit designer's "cookbook," now containing over 600 proven circuits, for all types of functions, selected from thousands on the basis of originality and practical application. Now you can have, at your fingertips, this carefully-planned reference source of tried and

tested circuits. Selected from thousands submitted by distinguished engineers, these "thought-starters" are a collection of original circuits selected on the basis of their usefulness. This detailed compilation of practical design data is the answer to the need for an organized gathering of proved circuits . . . both basic and advanced designs that can easily serve as stepping stones to almost any kind of circuit you might want to build. 384 pps., 19 big sections, over 600 illus., 8½" x 11".

List Price \$17.95

Order No. T-101

## Motorola Color TV Service Manual



This brand-new all-in-one handbook covers all models using the TS-907 through TS-924 chassis — including the all-transistor TS-915/919 chassis — all the information you need to know about setup, alignment troubleshooting, etc., slanted specifically to unique Motorola characteristics. In addition to general data, there's specific information on each chassis, detailing special features, test-point locations, individual alignment procedures, setup kinks unique to each chassis, CRT replacement instructions, troubleshooting tips and modifications, etc. Also, there's a BIG 18-page foldout section with complete schematic diagrams for ALL Motorola Color chassis. 160 pps., BIG 8½" x 11" size, plus 18-page schematic foldout section. Long-life vinyl cover.

Information on each chassis, detailing special features, test-point locations, individual alignment procedures, setup kinks unique to each chassis, CRT replacement instructions, troubleshooting tips and modifications, etc. Also, there's a BIG 18-page foldout section with complete schematic diagrams for ALL Motorola Color chassis. 160 pps., BIG 8½" x 11" size, plus 18-page schematic foldout section. Long-life vinyl cover.

List Price \$7.95

Order No. 509

## Electric Motor Test & Repair



A guide to maintenance practices for all types of small horsepower motors. While many of the larger motor repair shops find it more expedient to replace low horsepower units, re-winding of small electric motors is still a wide-spread and profitable practice. This practical guide contains a wealth of information on testing and re-

winding small motors of every type, including fan, starter, polyphase, capacitor, induction, synchronous, etc. Early chapters tell you how to set up a motor test panel, make general tests and measurements, and advise you about the tools and equipment necessary (such as an armature winder, wedge driver, cutting and gauging board, coil taper, puller plate, etc.). 160 pps., 102 illus. Comb-bound with soft cover.

List Price \$6.95

Order No. T-97

## Color TV Trouble Factbook



Here's a complete guide to color TV troubles and solutions, arranged by make and model, a low-cost, all-in-one reference handbook every TV service technician should own. The information it contains may easily save you hours of time repairing a "tough-dog" color TV. Included are details concerning repetitive troubles, field-factory

changes, new and unusual circuits and descriptions of how they work, special adjustment procedures and other such pertinent service information. The content is arranged by brand names, covering every major make of color TV receiver produced in the past several years. Models and chassis covered are arranged in alpha-numerical order. 176-pps. Hardbound.

List Price \$6.95

Order No. 519

## Audio Systems Handbook



Complete reference and guide to audio system design, encompassing home entertainment, commercial sound and studio installations. Chapter 1, covering amplifiers and amplification, explains db and impedances, level limitations, insertion gain, plus a host of other basics necessary for practical system design. The author goes to

great lengths to impart an understanding of these vital ingredients as they apply to overall operation. The same may be said of the treatment in succeeding Chapters on equalizers, mixers, filters, distribution systems, program sources, commercial systems, studios, and loudspeaker systems. 192 pps., 125 illus. Hardbound.

List Price \$7.95

Order No. 494

## 104 Easy Transistor Projects You Can Build




How would you like to have a high-gain telephone pickup, a wireless mike, an electric megaphone, a CB receiver, light dimmer, fence charger, or any one of 104 such useful devices? You can build them yourself, at very little cost, and have a lot of fun in the process. What's more, you're bound to learn a lot about transistor cir-

cuits (including FETs and SCRs). A complete schematic diagram is included for each device, along with a parts list, plus a brief description of its operation and application, and notations concerning any critical points. All of the devices have practical application in the home, on the repair bench, in the ham shack, on your car, boat, airplane, etc. 224 pps. Hardbound.

List Price \$6.95

Order No. 462

## Handbook of Semiconductor Circuits

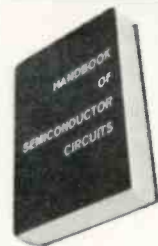

Contains 124 examples of standard transistor circuits, complete with operational data for amplifiers, oscillators, logic and switching circuits, power supplies, and various nonlinear circuits. The broad range of circuits included were selected on the basis of application and practicality. A design philosophy section is

included with each group of circuits, thereby providing a basis for understanding circuits other than those selected as examples. This is not a handbook of "preferred" circuits, but rather a collection of practical circuits which have wide application and exemplifying good engineering design. Each circuit description includes data concerning any unique design or operational data, along with schematic diagrams. Hundreds of illustrations and diagrams. 448 pps., 6" x 9", Hardbound.

List Price \$8.95

Order No. G-30

## Digital Computer Theory




Whether you are a technician or engineer who needs comprehensive knowledge of computer operation, or simply a hobbyist with a passing interest in the subject, this outstanding text is for you. In the first section you are acquainted with basic computer technology, including computer codes and language programming. The second

section presents a detailed study of modern computer logic circuits, such as AND, OR, NAND, and NOR gates. In addition, thorough explanations of basic circuit blocks are discussed—bistable, monostable, and astable multivibrators, Schmitt trigger circuits, etc. Finally, the third section covers memory, control, arithmetic, and input-output units. 320 pps. Hardbound.

List Price \$7.95

Order No. 276

## Semiconductors From A to Z

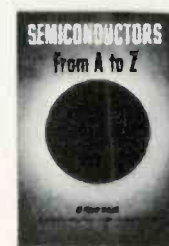

Here it is—everything you need to know about semiconductors — from basic diodes and transistors to FETs, MOS FETs, tunnel diodes, integrated circuits, varicaps, photoFETs, light-sensitive and light-emissive devices, incandescent and luminescent optic-electronic circuits, unijunction transistors, field-effect

diodes, SCR and zener diodes, etc. Explains how these various devices work and how they are used, with descriptions of all the common and unique circuits used in modern semiconductor technology. Attention is given to integrated circuit applications — variable-current and constant-current sources, unbalanced differential amplifiers, IC applications in FM and TV receivers, TV sound circuits, discriminator circuits, and cascade amplifier networks. 272 pps., over 300 illus., 26 Chapters.

List Price \$7.95

Order No. 493

# AN EXTRAORDINARY OFFER...



# An Extraordinary Offer

to introduce you to the benefits of Membership in

## ELECTRONICS BOOK CLUB

for a limited time only you can obtain

**ANY 3** OF THESE UNIQUE BOOKS . . . yours for only **99¢** each  
(Combined List Price \$34.85) Club Membership . . . with Trial

May we send you your choice of any three books on the facing page as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics.

These handsome, hardbound books are indicative of the many other fine offerings made to Members . . . important books to read and keep . . . volumes with *your* specialized interests in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, engineering—you will find that Electronics Book Club will help you.

With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your understanding of electronics, too.

### How You Profit From Club Membership

This special offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Membership in the Club offers you several advantages.

**1. Charter Bonus:** Take any three of the books shown (combined values up to \$34.85) for only 99¢ each with your Trial Membership.

**2. Guaranteed Savings:** The Club guarantees to save you 15% to 75% on all books offered.

**3. Continuing Bonus:** If you continue after this trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99, will entitle you to a valuable Book Dividend which you may choose from a special list provided members.

**4. Wide Selection:** Members are annually offered over 50 authoritative books on all phases of electronics.

**5. Prevents You From Missing New Books:** The Club's FREE monthly *News* gives you advance notice of important new books . . . books vital to your continued advancement.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours . . . that it is possible to keep up with the literature published in your areas of interest . . . and to save substantially while so doing.

### How the Club Works

Forthcoming selections are described in the FREE monthly *Club News*. Thus, you are among the first to know about, and to own if you desire, significant new books. You choose only the main or alternate selection you want (or advise if you wish no book at all) by means of a handy form and return envelope enclosed with the *News*. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway . . . without the substantial savings offered through Club Membership.

### Limited Time Offer!

Here, then, is an interesting opportunity to enroll on a trial basis . . . to prove to yourself, in a short time, the advantages of belonging to Electronics Book Club. We urge you, if this unique offer is appealing, to act promptly, for we've reserved only a limited number of books for new Members.

To start your Membership on these attractive terms, simply fill out and mail the postage-paid airmail card today. You will receive the three books of your choice for 10-day inspection. **SEND NO MONEY!** If you are not delighted, return them within 10 days

and your Trial Membership will be cancelled without cost or obligation. Electronics Book Club, Blue Ridge Summit, Pa. 17214.

### Typical Savings Offered Club Members on Recent Selections

Philco Color TV Service Manual	List Price \$7.95; Club Price \$4.95
Dictionary of Electronics	List Price \$6.95; Club Price \$5.50
CATV System Engineering	List Price \$12.95; Club Price \$7.95
Solid State Circuit Design & Operation	List Price \$9.95; Club Price \$5.95
1970 Tube/Transistor Substitution Guide	List Price \$4.95; Club Price \$2.50
How to Build a Working Digital Computer	List Price \$7.95; Club Price \$3.95
Small Appliance Repair Guide	List Price \$7.95; Club Price \$4.95
Solid State Circuit Design & Operation	List Price \$9.95; Club Price \$5.95
101 TV Troubles	List Price \$7.95; Club Price \$4.95
Zenith Color TV Service Manual	List Price \$7.95; Club Price \$4.95
Servicing Electronic Organs	List Price \$7.95; Club Price \$4.95
Digital Computer Analysis	List Price \$10.95; Club Price \$7.95
How To Test Almost Everything Electronic	List Price \$5.65; Club Price \$3.95
How to Use Your VOM, VTVM & Scope	List Price \$6.95; Club Price \$4.95
Radio Operator's Q & A Manual	List Price \$8.95; Club Price \$7.50
Tape Recording For Fun & Profit	List Price \$7.95; Club Price \$4.95
Elements of Tape Recorder Circuits	List Price \$7.95; Club Price \$3.95
Industrial Electronics Made Easy	List Price \$8.95; Club Price \$5.95
Electronic Test & Measurement Handbook	List Price \$7.95; Club Price \$4.95
Installing Hi-Fi Systems	List Price \$7.95; Club Price \$4.95
Pinpoint TV Troubles in 10 Minutes	List Price \$6.95; Club Price \$4.95
Easy Way To Service Radios	List Price \$6.95; Club Price \$3.95
Practical Color TV Servicing Techniques	List Price \$8.95; Club Price \$5.95
Mathematics for Electronics	List Price \$10.95; Club Price \$7.95
Transistor Projects	List Price \$5.95; Club Price \$2.95
Electronic Musical Instruments	List Price \$10.00; Club Price \$7.95

# SEND NO MONEY!

Simply fill in and mail postage-paid Airmail card today!



Model No. WG1

**SOLID STATE**  
**ONE GUN BOOSTER**  
FOR COLOR TV

**EXTENDS COLOR GUN LIFE**

**RESTORES RED, BLUE OR GREEN BRILLIANCE**

**EASY TO INSTALL**  
(INSTRUCTIONS ON BACK)

WORKMAN *Electronic* PRODUCTS INC.  
SARASOTA, FLORIDA

**BEFORE** WEAK SERVICE LINE

**AFTER** BOOSTED SERVICE LINE

installation of **ONE GUN BOOSTER**  
Boosts the one weak color needed for a **BALANCED** color picture.

MANUFACTURED BY **WORKMAN** *Electronic* PRODUCTS INC.  
SARASOTA, FLORIDA

... for more details circle 133 on Reader Service Card

**Save Time on PC Board Repairs!**

**MODEL 100A**

Melted solder disappears up hollow tip into tube

**The ENDECO Desoldering Iron Removes Soldered Components in seconds...without damage!** Endeco melts solder; removes last trace by vacuum. Leaves terminals and mounting holes clean. Resolders PC boards better than regular iron. One-hand operation. Temperature controlled for continuous use. Standard tip furnished, 5 other tip sizes. Pays for itself. \$20.65 net. Smaller size available. See your distributor or write:



**ENTERPRISE DEVELOPMENT CORPORATION**

5127 E. 65th · Indianapolis, Ind. 46220

... for more details circle 108 on Reader Service Card

## ET/D NEW PRODUCTS

*continued from page 66*  
of the message, the search process resumes automatically. The computer patch board matrix contains eight high- and eight low-terminal programmers in addition to eight crystal sockets. A plug-in crystal for the frequency of the user's choice is inserted and the terminal lead wire is connected to the corresponding high- or low-band terminal programmer. The pro-



cess is repeated in any high/low sequence for the remaining seven crystal positions. Front panel push buttons for each channel enable the receiver to scan all eight positions, or a choice of any combination of them. Sensitivity is rated at  $0.5\mu\text{v}$  for low-band channels and  $0.7\mu\text{v}$  for high. Specifications indicate a selectivity of 50dB @  $\pm 15\text{kHz}$  and a 5w audio output. Price is \$169. Regency

### RADIATION METER 708

*Detects both x-ray and gamma radiation*

A Model 499 VIC-CHEK Survey Meter has been designed to answer the need of TV servicemen wishing to check the amount of radiation emitted from color-TV sets. Although primarily designed for TV servicemen, the unit is also a quick and sensitive radiation survey meter. A single pushbutton switch activates the circuitry to provide almost immediate indications of the relative radiation intensity. Power is supplied by one 9v transistor-radio battery, and power is drawn only when the pushbutton is de-



pressed. The meter detects both x-ray and gamma radiation. It is said to have a range of from 0 to 1000 counts per minute, with a reported accuracy of  $\pm 20$  percent of full-scale reading. The detector, contained within the chassis, is a Geiger-Mueller counter tube with organic quench and a 10 sq. cm. aluminumized mylar radiation window. The circuits are reportedly all solid-state for lower power consumption and increased reliability. The 1 lb instrument is 3 in. wide by 5 in. high by  $2\frac{1}{2}$  in. deep. Price \$79.50. Vico-treen

### INVERTER 709

*Output Capacity of 600w*

Announced is a solid-state inverter for the operation of 117v 60Hz ac equipment from 12vdc storage battery power. This Inverter Model 12U-S6M has an output capacity of 600w continuous and 650w intermittent while maintaining frequency at 60Hz with varying load or input voltage. The inverter is reportedly well filtered and comes complete with battery cables ready for operation. Net price \$249.75. ATR.



### TV SWEEP/MARKER GENERATOR 710

*Fundamental sweep output on all VHF TV channels*

A color-TV alignment test instrument has been designed to combine features normally found in three or four separate pieces of test equipment. The TV Sweep Chanalyst, WR-514A, is said to have the combined features

of a TV sweep generator, marker generator, marker adder, and special "ChromAlign" system for color bandpass alignment. This instrument reportedly provides RF, IF and video output sweep signals for alignment of VHF tuners; IF, video and color bandpass amplifiers. When used with an



oscilloscope, the instrument reportedly provides a continuous-trace display of the bandpass characteristics of TV receiver circuits. Specifications indicate that some of the features include: Fundamental sweep output on all VHF TV channels—for sweep alignment of VHF tuners. Sweep output on all IF frequencies for stage-by-stage or overall IF alignment. Video sweep output from 50kHz to 5MHz for alignment of video amplifiers and chroma circuits. Special signal for color bandpass alignment. Built-in marker-adder function. Seven crystal-controlled IF markers for checking IF response of sound, picture and chroma carriers. FM sweep output from 88 to 108MHz for FM tuner alignment. In addition, the instrument has been redesigned to incorporate BNC connectors throughout and comes equipped with new basic output cables and snap-on alignment adapters. Price with cable accessories is \$375. RCA

## CONNECTORS

711

*Competitively priced and intermateable*

A new line of competitively priced audio connectors which are constructed of durable plastic is introduced. The connectors are durable, lightweight, and fully intermateable with all industry standard latchlock types.

The connectors are ideally suited for use in audio frequency and other low-level, high impedance circuit applications.

Known as Excellite audio connector, a new line includes straight cord plugs and wall mounting receptacles



offering both plug and socket inserts in three-, four- or five-contact configurations. Features include durable, molded ABS (acrylonitrile butadiene styrene) bodies; nickel plating throughout; convenient pushbutton lock/release; positive gripping cable clamps; unitized, removable inserts molded of high impact type six nylon; silver plated brass screw-machine contacts, with positive grounding provision when contacts engage/disengage; black neoprene rubber cable relief.

Immediate applications include public address sound systems, studio broadcast systems, recording equipment, test instruments, two-way radio communications gear, computer peripheral equipment and a host of similar high-performance uses.


Excellite cord plugs feature a single conventional, right hand, self-forming thread insert screw. For cable installation, connector disassembly requires only that the insert screw be turned counterclockwise, releasing the one-piece insert assembly.

Once the insert screw has been removed, the assembly easily slides from the connector shell.

After cable termination to solder cup contacts, the insert assembly is simply aligned with the shell and inserted. The insert screw is then replaced and tightened clockwise.

The three-pin version uses #12 contacts and is current rated at 15a; the four-pin connector uses #16 contacts at 10a; the five-pin version uses #20 contacts, rated for currents to 7.5a.

Straight cord plugs with socket contacts measure  $\frac{3}{4}$  in. diameter (socket end) by  $3 \frac{3}{16}$  in. long (tip-to-tip). Pin contact straight cord plugs are the same diameter at pin end; their length is three inches. Wall mounting receptacles with pin contacts are also  $\frac{3}{4}$  in. diameter, but are only  $\frac{7}{8}$  in. deep with a mounting plate measuring  $1 \frac{7}{16}$  in. high by  $\frac{7}{8}$  in. wide. Socket contact wall mounting receptacles are  $1 \frac{15}{16}$  in. diameter by  $1 \frac{1}{16}$  in. long, with mounting plate measuring  $1 \frac{7}{16}$  in. high by  $1 \frac{1}{16}$  in. wide. Amphenol.

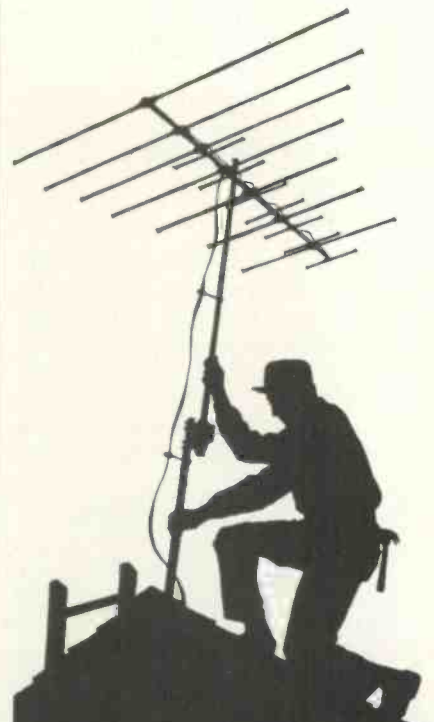

**When you're putting up an antenna, RCA supports it. With a complete line of hardware.**

Chimney, wall, and roof mounts. Mastings. Guy wires, fittings . . . and standoffs, too. Whatever your requirements . . . RCA meets them with a complete line of Antenna Installation Hardware.

Every item in the line has been given that special attention to design and quality that you've come to expect from RCA.

Ask your RCA Distributor about the RCA antenna hardware line, and about his special deal on a hardware merchandiser for profitable "do-it-yourself" sales. Sell the hardware line with built-in consumer acceptance—RCA.

Parts and Accessories,  
Deptford, N.J. 08096

**RCA**  
Antenna  
Installation Hardware

. . . for more details circle 122 on Reader Service Card



## ET/D NEW PRODUCTS

### SERVICE EXTENSIONS 712

*Cables speed  
equipment servicing*

A full line of service extensions is announced. Service extensions are designed to speed servicing of television sets, high fidelity equipment and appliances equipped with Molex interconnectors.

All service extension cables are 36 in. long, and are available in 15, 9, 6,



3, 2, 1 contact configurations.

A kit of four of the most popular cables (PA-396/PA-496) is also available.

Prices of Molex service extensions range from \$5.80 for the 15 contact to \$.50 for the 1 contact. The kit prices are \$9.95. Telematic Div. of U.X.L. Corp.

### MARINE ANTENNA 713

*Rotated 360 degrees  
from inside the boat*

A collapsible rotating all channel TV/FM RMA-1 Marine Antenna designed for use on power cruisers, houseboats, sailboats and auxiliaries is introduced.

The unit consists of an all channel, VHF-UHF-FM Color Spectrum Antenna mounted on a telescoping mast and manual motor mechanism. When in use it is telescoped up to 10ft and can be rotated by a full 360 degrees from inside the boat. When not in use the antenna telescopes down and collapses, without disassembly, into a neat package that is covered by a nylon reinforced vinyl cover.

The all weather 75Ω shielded coaxial cable transmission line system reportedly wards off any unwanted



noise or distortion from metal boat parts, operating generators or motors. Combined with a 75-300Ω set matching transformer/splitter, the antenna assures fine television reception.

The antenna is easily mounted in minutes with simple tools. Gold Corrodizing protects the antenna and all its parts from fresh water and salt water corrosion. Manufacturer's list price: \$89.95. Finney.

### SOLID-STATE DAMPER TUBE REPLACEMENT 714

*Replacing such damper  
tubes as 6AX4 and 6AU4*

The solid-state, octal based plug-in rectifier updating the set and directly replacing such damper tubes as 6AX4



and 6AU4 is introduced. The rectifier reportedly provides greater voltage at less current than conventional electron tube dampers and generates much less heat. Electrical characteristics, at 15.7kHz, include ratings of 5kv peak inverse voltage at 210ma, with a maximum peak current limit of 1300ma. Expressed with an IF of 20mv and a



### SENCORE SM152—ONLY COMPLETE SWEEP AND MARKER GENERATOR

- Sweeps all VHF channels • Sweeps all UHF channels • Sweeps chroma through IF or Direct • Sweeps FM IF and complete band of RF • Covers 20Mhz older sets and new import sets • All crystal controlled markers • Self generator base line for zero reference (as shown in all alignment instructions)

*Sure—it's a little more than others—but who else has UHF for example? And all new tuners must have UHF on them.* **\$450.00**

IN STOCK AT YOUR LOCAL  
PARTS DISTRIBUTOR.



**SENCORE**  
NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
3200 Sencore Drive, Sioux Falls, South Dakota 57100


... for more details circle 125 on Reader Service Card

recovery to an IR of  $200\mu\text{a}$ , maximum recovery time is  $4\mu\text{s}$ . Maximum ambient temperature rating is  $85^\circ\text{C}$  ( $188^\circ\text{F}$ ). The unit is designed for parallel filament circuits only. The Model XP405 rectifier sells for \$6.60. Sarkes Tarzian.
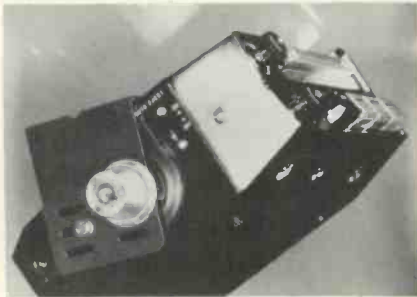
### ELECTRONIC EQUIPMENT LOCK 715

Free spinning and wrench resistant


The Model 200 Security Lock is introduced. The lock is a seven-pin tumbler cylinder lock that foils would-be thieves by securing the equipment to the desk, table or panel and cannot be removed without the owner's key. This steel device is both free spinning and wrench resistant and the owner has one of 25,000 key combinations and therefore has the "pick-resistant" quality which the authorities recommend. Priced at \$10.95. Bolen.


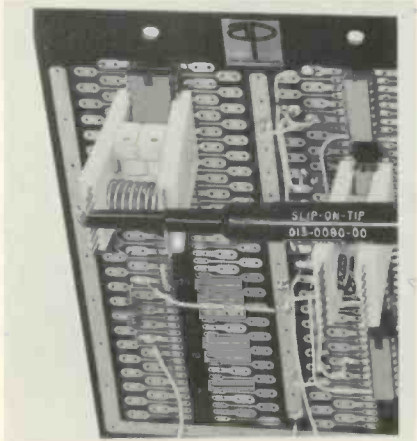
### TEST CLIP 716

Uses gold plated phosphor bronze fingers

Easy accessibility to hard-to-reach DIP pins is provided by a new IC Test Clip. The clip is ideal for field service work and for lab and production circuit checking, particularly for use with oscilloscope probes. It can also be used for easy damage-free removal of dual in-line packages. A "contact comb" assures positive short-proof positioning of the wiping-action gold plated phos-




phor bronze fingers with a helical spring to provide the correct contact tension. The new clip fits all dual in-line packages with leads on .5 and .6 in. centers. Price \$7.50 in quantities of one to nine. AP Incorporated.
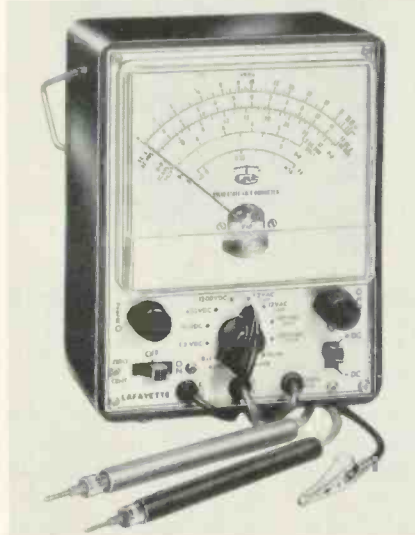
### FET VOLT-OHMMETER 717

Meter and transistors are protected against burnout

Introduced is a solid-state FET volt-ohmmeter in both kit and wired form.



## DEPENDABLE ALL-PLASTIC COLOR TUBE BRIGHTENERS



#CTB-70

Restores "New Set" performance to Color TV Sets when Color tubes become dull and lose contrast quality after one year. Increases tube brilliance by increasing the electron emission. All plastic—not paper! Reusable! Simple installation! Just plug in between the color tube and color tube socket. #CTB-70 for  $70^\circ$  button base pic tubes. #CTB-90 for  $90^\circ$  button base pic tubes. Both blister-sealed on attractive, Informative Peg-Hang Cards. For Profit Details—Write:



#CTB-90

### RMS ELECTRONICS, INC.

50 Antin Place, Bronx, N.Y. 10462  
• Tel. (212) 892-6700

... for more details circle 124 on Reader Service Card



Get in line for your all new solid state instant-on

## MIGHTY MITE VI

- Now faster than ever. Instant-on action with all solid state FET circuitry—no waiting for warm-up.
- New push-button operation speeds up every test—saves you valuable time.
- New 13th socket checks still more tubes—now over 3000 including foreign.
- New hi-style case—vinyl-clad and brushed steel. A professional instrument designed for professionals.

At your distributor now, TC-154 only \$99.50



**SENCORE**

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

... for more details circle 126 on Reader Service Card



**ET/D NEW PRODUCTS**

The FET VOM features meter and transistors which are protected against burnout. The VOM has 11M input impedance on dc and 1M impedance on ac to reduce circuit loading and a large 4½ in. 200µa meter for accurate readings. Ranges: dc and ac volts: 0-1.2, 12, 120, 1200. P-P ac volts: 0-3.33, 33, 330, 1200. Resistance: 0-1K, 100K, 10M, 1000M. DB: -24 to +56 in 4 ranges. The unit is housed in a high-impact bakelite case with handle. Size: 5¼ x 7 x 2¾ in. Complete with batteries, leads, and complete instructions. Kit stock No. 38-0115; price \$29.95. Wired stock No. 38-01164; price \$39.95. Lafayette.

**TAPE DECK 718**

*Three motors with automatic reverse*

A three-motor, reverse, custom stereo tape deck, Model 650XD, is introduced. Among the features are automatic reverse for 12.8 hours of playback or record, three-speed hysteresis

synchronous capstan motor without belt shifting, two 6-pole eddy-current reel motors, automatic shutoff, sound-on-sound, 30 to 23,000 Hz frequency response, slide-pot controls, twin VU meters, Cross Field head which records in the high frequency spectrum, and digit counter with push-button reset. The unit is designed for use with home stereo music systems, and is priced at \$399.95. Roberts.



**TUNER DEGREASER 719**

*Warmer and faster cleaning action*

Announced is the development of a degreaser for cleaning and restoring tuner contacts. The tuner spray is said




to be warmer, reducing detuning recovery time, while more powerful in its cleaning action. Called WARM TUN-O-WASH, the new tuner degreaser uses a blend of Freon 12 plus ingredients that reportedly make the spray approximately 25°F warmer than earlier sprays. Contacts and components sprayed with the tuner degreaser reportedly do not frost up and dry more rapidly. The tuner degreaser is available in 24 oz. cans for \$3.25. Chemtronics

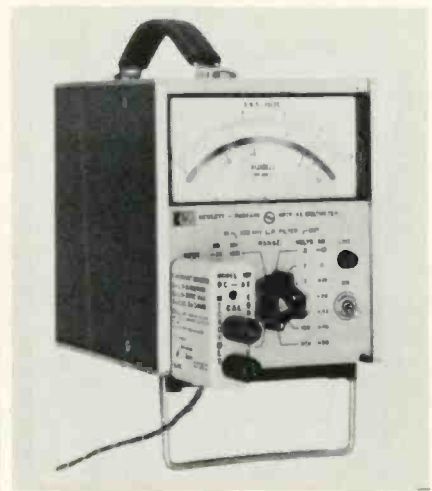**DC MICROVOLTMETER 720**

*Transforms any AC millivolt meter into a direct reading DC microvolt meter*

Introduced is a low-cost Model 100dc microvolt converter. This instrument will reportedly transform any ac millivolt meter into a direct reading dc microvolt meter with zero drift and one microvolt resolution. One percent accuracy is accomplished by the use of an ultra linear dc to ac converter. Other features are 10M input impedance and auto polarity—no ac millivolt meter modifications are required and sells for \$49.50. Electronic Applications.



**DECISION MAKER**



**The Sencore CRT Champion.** Judge and jury when it comes to color CRT analyzing. Reaches a verdict in seconds — tells you if the tube has adequate emission, and if it will track in the TV set.

**Automatic color tracking** according to industry standards with exclusive 3 Gun G2 Control.

**One-step controlled rejuvenation** with automatic RC timer. A Sencore exclusive.

Lots more, too. So fry the decision maker — the Sencore CRT Champion — at your distributor today. You'll reach the right verdict. ....CR-143 \$119.50



**SENCORE**  
NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

... for more details circle 127 on Reader Service Card

## TEKLAB REPORT . . .

*continued from page 45*

er. At the same time a 6v regulated control voltage is obtained from pin nine of IC201, which is connected to resistor R155 and R156—providing control voltage for the voltage dependent capacitor in the VHF tuner.

The UHF tuner is also provided with an AFT voltage, which is obtained from terminal four of the IC-201 through resistors R278, R157 and R158.

The circuit configuration of IC-201 is fairly complex and it is not possible to make resistance measurements to determine if the integrated circuit is defected. Any accidental shorting of the integrated-circuit pins can destroy it.

### PRODUCTION CHANGES INCORPORATED

The following production change is incorporated in this chassis:

In the AFT circuits, the lead from Pin 9 of IC201 to SW103 has been removed. The leads from Pins 77 and 78 of PC2 to the tuner have been shielded.

### TROUBLESHOOTING THE IC

Troubleshooting the integrated circuit is accomplished by checking the terminal voltages with an FET

## NOW A ONE STOP SHOPPING CENTER FOR YOUR AUTO RADIO AND 8 TRACK STEREO PARTS. AT FACTORY DISCOUNTS

WE ARE AUTHORIZED PARTS DISTRIBUTORS FOR:

DELCO	PANASONIC
BENDIX	PHILIPS
MOTOROLA	BELLE WOOD
LEAR JET	WARD
TENNA	QUICKMOUNT
METRA	DEWEKO
AUTOMATIC	AC SPEEDO
ON GUARD	KING SEELEY
CRAIG	STEWART WARNER

STEREO LOCK MOUNTS

SEND YOUR ORDERS WITH PART NUMBERS TO

**Laran Electronics, Inc.**

3768 BOSTON ROAD  
DEPT. 100 BRONX, N.Y. 10469

OR SEND MODEL, MAKE AND DESCRIPTION OF PART WANTED.

meter or VTVM. In this way, a defective unit can be quickly detected. With the AFT switch in an on position and accurately tuned, the voltages should read as follows:

Terminal	Terminal
1 +2.5v	6 +2.5v
2 +12v	7 +2.4v
3 +2.5v	8 0v
4 +6v	9 +7v
5 +6v	10 +12v

To identify the terminals of IC-201, count the terminals from the bottom of the circuit board. The lead adjacent to the tab is terminal 10, and the terminal numbers decrease in a counter-clockwise direction.

With AFT defeat switch in the off position, the voltage at VHF tuner terminal "A" will be 9v, while terminal "B" will be 3v. This is due to the voltage divider consisting of resistors R277, R155, R156 and R153, which are connected in series.

It is also important that external checks be made up to the integrated circuit. The 12vdc obtained from the Zener diode, XZ201, should be present at terminal 10 of IC201.

The video carrier signal should be present at terminal 7 and the AFT discriminator transformer should be adjusted to 45.75MHz. The discriminator transformer should be adjusted for a symmetrical "S" curve. ■

*Next month we will discuss the Automatic Color Control Circuit (ACC), Quick-On Circuit, and various adjustments related to this chassis.*

## MOVING?

Send Change of Address to:

**ELECTRONIC**  
TECHNICIAN/DEALER

Harbrace Building  
Duluth, Minn. 55802

# Check'em ALL!

TRANSISTORS  
FET'S IN OR  
OUT OF CIRCUIT



The TF17 works every time using tried and proven signal injection techniques. New, improved tests on special RF transistors and the latest high power transistors, mean that the TF17 is the only up-to-date transistor tester on the market. A new, exclusive setup book in rear compartment guides you to every test for over 12,000 transistors and FETs. The book is not needed for general service troubleshooting. Regular transistors are checked for beta gain and  $I_{cbo}$  leakage. FETs are checked for transconductance and  $I_{gss}$  leakage. Only \$109.50



**SENCORE**

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT  
426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101



# READERS SERVICE INDEX

## NEW PRODUCTS

700	Closed-Circuit Camera	60
701	Stereo Headphone	60
702	Citizens Band Scanner	60
703	Record/Playback Deck	60
704	Color-TV Set	60
705	Cassette Recorder/FM Multiplex Radio	66
706	UHF Broadband Amplifier	66
707	VHF Monitor Radio	66
708	Radiation Meter	72
709	Inverter	72
710	TV Sweep/Marker Generator	72
711	Connectors	73
712	Service Extensions	74
713	Marine Antenna	74
714	Solid-State Damper Tube Replacement	74
715	Electronic Equipment Lock	75
716	Test Clip	75
717	FET Volt-Ohmmeter	75
718	Tape Deck	76
719	Tuner Degreaser	76
720	DC Microvoltmeter	76

## CATALOGS AND BULLETINS

400	Semiconductor and Components	62
401	Electronic Test Accessories	62

402	Electronic Hardware	62
403	Power Supplies	62
404	Instructional TV Fixed Service	62
405	Recording Tape	62
406	Clips/Insulators	62

## TEST INSTRUMENTS

900	EICO Model 379 Signal Generator	54
901	EICO Model 150 Signal Tracer	54

## ADVERTISER'S INDEX

American Telephone & Telegraph Co.		41
101	Book Club—Tab Books	68-71
102	Borden Chemical Co.	27
103	Channellock, Inc.	26
104	Channel Master Corp.	2nd Cover
105	Chemtronics, Inc.	78
106	Cleveland Institute of Electronics	35-37
107	Cornell-Dubilier	3rd Cover
108	Enterprise Development Corp.	72
109	Gem City Tuner Service	24
110	General Electric Co.	28
111	General Electric Co.	61
112	General Electric Co.	67
113	Grantham School of Engineering	78
114	Heath Co., The	39
115	Houle Manufacturing Co.	38
116	International Crystal Mfg. Co.	22
117	Laran-Electronics, Inc.	77
118	Mallory Distributor Products Co.	20
119	Philips Business Systems, Inc.	23

120	Precision Tuner Service	29
121	RCA Electronic Components—Microphones	65
122	RCA Parts & Accessories	73
	RCA Picture Tubes	4th Cover
	RCA Semiconductor Distributor Products	42
123	RCA Test Equipment	33
124	RMS Electronics, Inc.	75
125	Sencore, Inc.	74
126	Sencore, Inc.	75
127	Sencore, Inc.	76
128	Sencore, Inc.	77
129	Sonar Radio Corp.	66
130	Sprague Products Company	25
	Sylvania Electric Products	31
	Sylvania Electric Products	63
131	Tech Spray	62
132	Tuner Service Corp.	19
133	Workman Electronic Products, Inc.	72
134	InfoMetrics	34

Technicians, Earn Your Associate  
**DEGREE**  
*mostly by correspondence*  
 Accredited by the Accred. Comm. of National Home Study Council. G.I. Bill Approved. Free catalog.  
 Write: Dept. T  
**Grantham School of Engineering**  
 1505 N. Western, Hollywood, Calif. 90027  
 ... for more details circle 113 on Reader Service Card

**SAVE \$478**  
**WHEN YOU BUY THIS 6-PACK!**

AVAILABLE FROM YOUR CHEMTRONICS DISTRIBUTOR



**CHEMTRONICS INC.** 1260 RALPH AVENUE  
 BROOKLYN, N. Y. 11236

... for more details circle 105 on Reader Service Card

**GET  
MORE  
FACTS**  
NO POSTAGE  
NECESSARY

Circle  
the  
Reader  
Service  
numbers  
of those  
items of  
interest  
to you.

**OK**

**FOR MORE INFORMATION fill out and mail today!**

Please send more information on items circled.

**ADVERTISED PRODUCTS**

101	102	103	104	105	106	107	108	109
110	111	112	113	114	115	116	117	118
119	120	121	122	123	124	125	126	127
128	129	130	131	132	133	134	135	136
137	138	139	140	141	142	143	144	145
146	147	148	149	150	151	152	153	154

**TEST INSTRUMENTS**

900	901	902	903	904	905	906	907	908
-----	-----	-----	-----	-----	-----	-----	-----	-----

**NEW PRODUCTS**

700	701	702	703	704	705	706	707	708
709	710	711	712	713	714	715	716	717
718	719	720	721	722	723	724	725	726
727	728	729	730	731	732	733	734	735

**CATALOGS & BULLETINS**

400	401	402	403	404	405	406	407	408
409	410	411	412	413	414	415	416	417

Note: Inquiries serviced until October 7, 1970.

(Please type or print)

7/70

Name .....

Position .....

Company .....

Street .....

City .....

State ..... Zip Code .....

Please describe your type of business.  
.....

**FOR MORE INFORMATION fill out and mail today!**

Please send more information on items circled.

**ADVERTISED PRODUCTS**

101	102	103	104	105	106	107	108	109
110	111	112	113	114	115	116	117	118
119	120	121	122	123	124	125	126	127
128	129	130	131	132	133	134	135	136
137	138	139	140	141	142	143	144	145
146	147	148	149	150	151	152	153	154

**TEST INSTRUMENTS**

900	901	902	903	904	905	906	907	908
-----	-----	-----	-----	-----	-----	-----	-----	-----

**NEW PRODUCTS**

700	701	702	703	704	705	706	707	708
709	710	711	712	713	714	715	716	717
718	719	720	721	722	723	724	725	726
727	728	729	730	731	732	733	734	735

**CATALOGS & BULLETINS**

400	401	402	403	404	405	406	407	408
409	410	411	412	413	414	415	416	417

Note: Inquiries serviced until October 7, 1970.

(Please type or print)

7/70

Name .....

Position .....


Company .....

Street .....

City .....

State ..... Zip Code .....

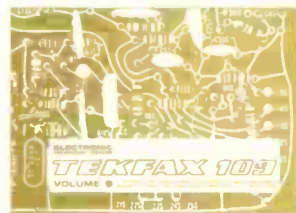Please describe your type of business.  
.....



**GET THIS FREE BONUS WITH YOUR PERSONAL SUBSCRIPTION TO ELECTRONIC TECHNICIAN/DEALER!**

Enter your subscription for a two- or three-year term and we'll send you the new TEKFAX 109 Book of Schematics—FREE!

- \$10 for 3 Years     \$8 for 2 Years     \$5 for 1 Year  
 Payment Enclosed     Bill Me Later

**PLEASE CHECK BELOW:**

1. In the TV, Radio and other consumer products fields, is your firm **PRIMARILY a:** (check most descriptive item)
- Retailer with service department
  - Service/repair firm with some retail
  - Industrial electronics service firm
  - Manufacturer
  - Other (please describe)
2. Title: (please check one)
- Owner, manager, buyer, other executive
  - Service manager
  - Service repairman or other employee

If you are renewing your subscription, check here and attach your address label. If you renew your subscription for 2 to 3 years, you are still eligible to receive the TEKFAX 109 as your free bonus.



**BUSINESS REPLY MAIL**

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY

Reader Service Department


**ELECTRONIC  
TECHNICIAN / DEALER**

HARBRACE BUILDING, DULUTH, MINNESOTA 55802

FIRST CLASS

PERMIT NO. 665

DULUTH, MINNESOTA

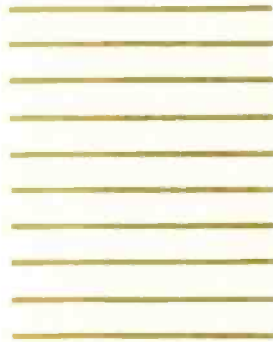

**GET  
MORE  
FACTS**

NO POSTAGE  
NECESSARY

**BUSINESS REPLY MAIL**

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY

Reader Service Department


**ELECTRONIC  
TECHNICIAN / DEALER**

HARBRACE BUILDING, DULUTH, MINNESOTA 55802

FIRST CLASS

PERMIT NO. 665

DULUTH, MINNESOTA

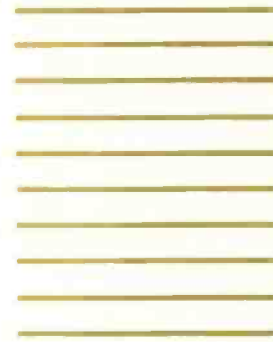

**GET  
MORE  
FACTS**

NO POSTAGE  
NECESSARY

**BUSINESS REPLY MAIL**

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY

Circulation Department


**ELECTRONIC  
TECHNICIAN / DEALER**

HARBRACE BUILDING, DULUTH, MINNESOTA 55802

FIRST CLASS

PERMIT NO. 665

DULUTH, MINNESOTA

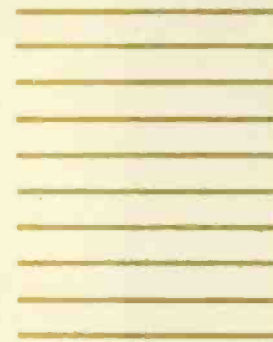

**FOR  
ONLY  
PENNIES  
PER  
MONTH—  
YOUR  
OWN  
PERSONAL  
COPIES**



## Put your parts in order.

All it takes is genius to arrive at simplicity. This new display stand is deceiving. It's more than a display stand. It's set up to operate like a store within your store for instant servicing.

Here, within this unit, is a complete stock of all the wide range twist prongs you'll need plus micas, miniature electrolytics, ceramics, wide range tubulars and dipped paper Mylar.\* The selection was based on an extensive study of all capacitors used in the replacement market. Now, with the Re-Place, you're in the capacitor

replacement business. The Re-Place only takes 2' x 5' in space and you have all your parts in order.

Interested? Write for our new catalog on The Re-Place™ capacitor line. "The Replacers" — the most complete line of replacement capacitors in the smallest possible package.





The brilliance of our new color replacement tube is matched only by the sharpness of its pictures

# RCA MATRIX



Now it's easier to sell up to the best. RCA has added brightness without sacrificing sharpness!

Here's how and why:

To produce the brightest color picture tube in RCA's history, we developed a new phosphor-dot screening process that incorporates a jet-black matrix. But we didn't stop there. We wanted a tube that could deliver sharp, vivid pictures even in strong room light. So, we added the brilliance of new phosphors and deposited each red, green and blue phosphor-dot within the black matrix. Result: brighter pictures with no loss of contrast. Thanks to the matrix technique, combined with our new high resolution gun and greatly improved phosphors, the Matrix is also the *sharpest* color picture tube in

RCA's history. Matrix owners can turn up brightness *without* "turning down" color!

Will your customers see the difference? You bet! What's more, they'll be pre-sold on the difference—every time they see the 1970 big-screen color sets people are talking about! So when they need a replacement tube, satisfy their appetite for brighter, sharper pictures. Give their sets new brilliance and more vividly detailed pictures with RCA Matrix. The Matrix Tube is 100% brighter than any previous color picture tube manufactured by RCA.

For complete details, call your RCA Distributor.

RCA Electronic Components,  
Harrison, New Jersey



The RCA 25BCP22 Matrix Tube can directly replace 25XP22, 25BAP22 and also the following types: 25ABP22, 25AFP22, 25ANP22, 25AP22, 25AP22A, 25AQP22, 25BMP22, 25CP22, 25CP22A, 25GP22, 25GP22A, 25SP22, 25WP22, 25XP22/25AP22A and 25ZP22.