

43 Different, Entertaining, Make-It-Yourself Projects

RADIO-TV Experimenter

Published by
Science and Mechanics Magazine

75c
No. 559



**WHITE'S
RADIO
LOG**




Up-to-Date with 1750 Changes
Directory of North American
AM-FM-TV STATIONS
WORLD-WIDE SHORT WAVE

Telephone
Amplifier



Clip
Radio

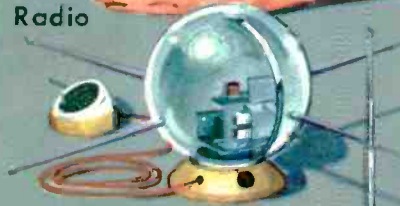

Model Beeper




Thermoscope



Bike Radio



Strobe-
Flash

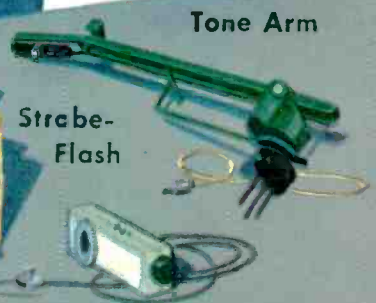

Hi-Fi
Tone Arm

Versaflex Receiver

PLUS—

- Sur-Powered Model Car
- Simple Signal Mixer
- TV Rotator Remote Control
- 15-Meter Ham Rig
- Transistor Power Supplies
- Hidden Metal Detector
- Packet Signal Tracer
- Aligning Superhets
- Low-Power DXing
- Repairing PC Boards
- Electronic Moisture Tester




Portable
Phonograph





Megaphones

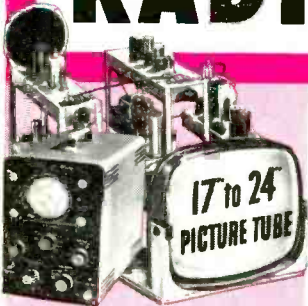HOW TO GET A GOOD PAYING JOB IN RADIO-TELEVISION



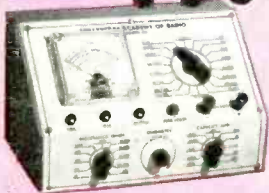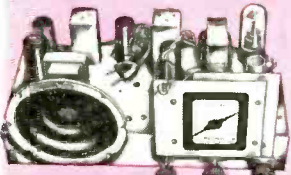Build this equipment while learning... it's yours to keep!



EARN WHILE YOU LEARN AT HOME IN SPARE TIME

I'll prove to you that I can prepare you to become a trained Radio and Television Serviceman in a few months' time... ready to step into a good paying job with a real future! Mail coupon-postcard NOW!



MASON R. WARNER, President

Only \$6 starts you On Sprayberry "Learn by Doing" Training Plan

Men by the thousands... trained Radio-Television Service Technicians... are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up-to-date home study training in Radio-Television! This offer is made because Radio-Television must have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need... to step into a fine job or your own Radio-Television Service Business—

Get Practical Experience with 25 Kits of Radio-TV Parts

In addition to modern lessons, you train with actual parts and equipment. Build the famous Sprayberry Training Television Set, Multi-Range Tester, 2-Band Radio, other Test Equipment—all yours to keep. Get latest training on Color TV, Transistors, Hi-Fi and UHF Conversions to make your training more valuable.

Radio-TV Needs You Now! Get all the facts... FREE!

Radio-Television needs you! See how and why Sprayberry Radio-Television home training offers you *more*. Three training plans to suit your exact needs. Low payment... only \$6 starts you. Backed by over 27 years of distinguished training experience. Rush special postcard—reply coupon for catalog and free sample lesson.

The Radio-Television industry is begging for trained men for interesting, profitable service work... get set now!

WRITE NAME AND ADDRESS—Cut out card and mail.

YOUR NAME _____
 ADDRESS _____
 TOWN _____ STATE _____

No Postage Stamp Necessary If Mailed in the United States

BUSINESS REPLY MAIL
 First Class Permit No. 34316, Chicago, Ill.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

Dept. 212-T 1512 Jarvis, Chicago 26, Ill.



FREE
 new 60 page catalog and actual sample lesson

This coupon needs no stamp or envelope. Just write name in upper left corner, cut out along dotted line and drop in any mail box. Pay no attention to printing on back of the card. By return mail you'll receive our big 60 page catalog and free sample lesson.

SPRAYBERRY

ACADEMY OF RADIO-TELEVISION
 Dept. 212-T
 1512 Jarvis, Chicago 26, Ill.

RADIO-TV Experimenter

VOLUME SEVEN CONTENTS

Boy's Bike Radio	23	Telephone Voice Amplifier	92
Six-Transistor Portable Superheterodyne	27	How to Wind Small Coils	95
Hi-Fi Tone Arm and Moving-Coil Pickup	30	Telethermoscope Weather Station	97
Portable Record Player	36	Pocket Signal Tracer	100
Versaflex Radio	38	Resistor Color Coding	102
Headphone-Handset Receiver	42	Power Supplies for Transistors	103
Zim Game Machine	43	One-Transistor Metal Detector	108
Combination Strobe-Flash Slave Unit	45	Line Voltage Meter	111
TV Rotator Remote Control	49	"Working-in" a Speaker	112
Two Tin-Can Megaphones	51	Talking on a Light Beam	113
Calibrated Potentiometer	53	Wave-Powered Tuner	116
DECCA—160's Last Chance?	55	Low Power DX	119
Versatile TV Stand	57	How to Insulate Tool Handles	121
Sound-Powered Interphone	60	Lab Reports on Two Vacuum-Tube Voltmeter Kits	122
Making and Testing Magnets	61	How to Repair Circuit Boards	132
Power-Line Antenna for Crystal Set	62	Solar-Powered Car	133
Reading the First Sputniks	63	Powered-Phone Intercom	137
How to Align Superhet Circuits	66	One-Tube Cigar-Box Amplifier	139
Small Fry Crystal Set	69	Low-Cost Fire Alarm Systems	141
Isotron—15 Meter Ham Transceiver	70	Finger-Clip Transistor Radio	145
Transistorized Tone Generator	79	Toys for Practicing Radio Code	148
Electronic Stethoscope	81	Electronic Moisture Tester	149
Dress It Up for Convenience	86	How to Make a VHF Antenna	152
Model Satellite Transmitter	87	Miniature Tube Guide	153
Simple Signal Mixer	90	Getting the Most from Plastic Cases	160
		WHITE'S RADIO LOG	161

Cover by Dick Locher

Curt Johnson, Handbook Editor
Herb Siegel, Assistant Editor, Handbooks
Bill Wadkins, Assistant Art Director, for Handbooks
Thomas A. Blanchard, Radio-TV Editor

Published and Copyrighted 1959 by

SCIENCE AND MECHANICS PUBLISHING COMPANY

450 East Ohio Street

Chicago 11, Illinois

The Radio-TV Experimenter contains a selection of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subjects appearing for the first time.

Science and Mechanics Handbook Annual No. 2, 1959—No. 559

Editorial Board

V. D. ANGERMAN
Editor and Publisher
DON DINWIDDIE
Managing Editor
ART YOUNGQUIST
Home Workshop Editor
P. D. URBAIN
Associate Editor
LILLIAN ANDERSEN
Associate Editor
WAYNE WILLE
Assistant Editor
RAY S. LINDENMEYER
Technical Editor
F. M. EISENZOPH
Art Director
CHUCK BACHTELL
Assistant Art Director

UPGRADE YOUR INCOME

through Grantham Training and an F.C.C. License!

What's in Your Future?

Are you *planning* your future or just drifting into it? Now is the time to get ahead in electronics—the world's fastest growing major industry. Now is the time to add technical knowledge and an F.C.C. license to your practical experience. Now is the time to prepare for higher pay—time to make your future secure.

Grantham Training Prepares You

Grantham School of Electronics specializes in quality training in communications electronics, preparing students to pass F.C.C. operator license examinations. This training is available either by correspondence or in resident classes.

The Grantham Communications Course does not include actual work with practical kits or other equipment. That is, for example, it does not teach you how to solder or how to remove a TV chassis from the cabinet, etc. It is not a repair course but, instead, is bona fide technical training which teaches you to understand electronic theory—which teaches you the "why" of electronics.

If you are a beginner in this field, the Grantham course will give you the kind of detailed training in radio-electronics theory and operating practices that will enable you to obtain your first class F.C.C. license quickly. Then, this license plus your knowledge of theory will qualify you for certain types of employment, and you can improve your practical ability while on the job earning a salary.

If you already have practical experience in radio-electronics, the Grantham course can add a knowledge of theory and an F.C.C. license to that practical experience. This should qualify you for higher pay and greater job security.

Train by Correspondence or in Resident Classes

RESIDENT CLASSES—The Grantham Communications Electronics Course is offered in both DAY and EVENING classes in Washington, Hollywood, and Seattle. The DAY course meets five days a week, from 9 a.m. until 1 p.m., and prepares you for a first class F.C.C. license in 12 weeks. The EVENING course meets two nights a week, from 6:30 p.m. until 10:30 p.m., and prepares you for a first class F.C.C. license in 30 weeks. All courses "begin at the beginning"—NO previous electronics training required or assumed.

CORRESPONDENCE TRAINING—The Grantham Communications Electronics Course is offered by correspondence from all Divisions of the School—Washington, Hollywood, and Seattle. The course has two major objectives—(1) to *teach* you a great deal of electronics, and (2) to prepare you to pass all F.C.C. examinations required for a first class license.

This course can prepare you *quickly* to pass F.C.C. examinations because it presents the necessary principles of electronics in a simple "easy-to-grasp" manner. Each new idea is tied in with familiar ideas. Each new principle is presented first in simple, everyday language. Then after you understand the "what and why" of a certain principle, you are taught the technical language associated with that principle. You learn more electronics in less time, because we make the subject easy and interesting.

Which License for Which Job?

The THIRD CLASS radiotelephone license is of value primarily in that it qualifies you to take the *second class*

examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

THE FIRST CLASS radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

Here's Proof . . .

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Walter Mengel, Jr., 423 James St., Crystal Lake, Ill. . . .	1st	8
Serge G. Miller, 1315 W. 15th St., San Pedro, Calif. . . .	1st	12
John A. Hayes, 1519 Madison Ave., Memphis, Tenn. . . .	1st	14
Robert A. Morgan, 25 Barrow St., New York, N.Y. . . .	1st	9
Hal Moon, Cook Hotel, 1334 Central, Kansas City, Mo. . . .	2nd	5
W. R. Smith, 1335 E. 8th St., Long Beach, Calif. . . .	1st	12
Erskin D. Davis, 4220 Clay St., NW, Washington, D.C. . . .	1st	12
John R. Bahrs, 72 Hazelton St., Ridgefield Park, N. J. . . .	1st	12
Earl A. Stewart, 3918 Modesto Dr., San Bernardino, Calif. . . .	1st	14
Robert H. Moore, 807 Grace St., Baldwin, L.I., N.Y. . . .	1st	12
Otis A. Towns, 3638 Bates St., St. Louis, Mo. . . .	1st	12

THREE COMPLETE SCHOOLS: To better serve our many students throughout the entire country, Grantham School of Electronics maintains three complete schools—one in Washington, D.C., one in Hollywood, Calif., and one in Seattle, Wash. All schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.

MAIL COUPON FOR FREE BOOKLET: Our free booklet, *Careers in Electronics*, gives details of how you can prepare quickly for your F.C.C. license. For your free copy of this booklet, clip the coupon below and mail it to the Grantham School nearest you.

GRANTHAM SCHOOL OF ELECTRONICS

821-19th Street, N.W.
Washington 6, D. C.
(Phone: ST 3-3614)

408 Marion Street
Seattle 4, Wash.
(Phone: MA 2-7227)

1505 N. Western Ave.
Hollywood 27, Calif.
(Phone: HO 7-7727)

(Mail in envelope or paste on postal card)

TO: **GRANTHAM SCHOOL OF ELECTRONICS**

821-19th, NW
Washington

408 Marion
Seattle

1505 N. Western
Hollywood

Please mail me your free booklet telling how Grantham training can prepare me quickly for my commercial F.C.C. license. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes E-9C


These men are getting practical training in **ELECTRONICS**

ELECTRICITY

ELECTRONICS

ON REAL

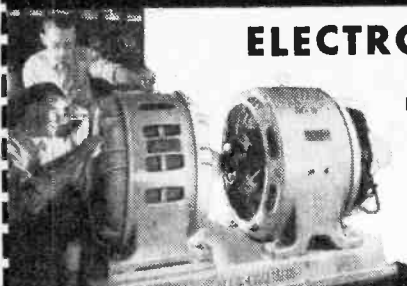Motors—Generators
—Switchboards—
Controls—Modern
Appliances—
Automatic
Electronic
Control Units



TELEVISION

RADIO ELECTRONICS

ON REAL

TV Receivers—
Black and White
and Color
AM-FM and
Auto Radios
Transistors
Printed Circuits
Test Equipment



Train in NEW Shop-Labs of COYNE

in Chicago—prepare for today's TOP OPPORTUNITY FIELD. Train on real full-size equipment at COYNE where thousands of successful men have trained for over 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. Employment Service to Graduates.

START NOW—PAY LATER—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK**—"Guide to Careers" which describes your training in **ELECTRICITY-ELECTRONICS** and **TELEVISION-RADIO ELECTRONICS**—no obligation; **NO SALESMAN WILL CALL.**

Coyne Electrical School, 1501 W. Congress Parkway
Chartered Not For Profit • Chicago 7, Dept. 39-23A

MAIL COUPON OR WRITE TO ADDRESS BELOW

COYNE ELECTRICAL SCHOOL
Dept. 39-23A—New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.
Send **BIG FREE** book and details of all the training you offer.

Name _____
Address _____
City _____ State _____



**COYNE offers
LOW COST**

TELEVISION RADIO-COLOR TV

Training in
Spare Time **AT HOME**

The future is **YOURS** in **TELEVISION!**
A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—**no costly "put together kits."** Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including **Radio, UHF and Color TV.** No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—**make money early in course.** Free Lifetime Employment Service to Graduates.


COYNE ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION
NOT FOR PROFIT

1501 W. Congress Parkway • Chicago 7, Dept. 39-H23



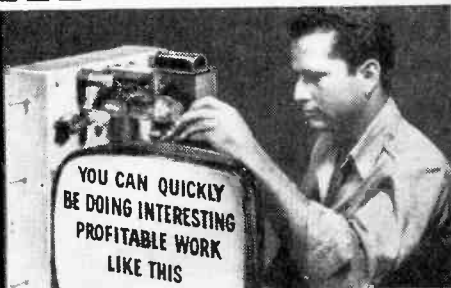B. W. COOKE, Jr., President
Coyne—the Institution behind this training... the largest, oldest, best equipped residential school of its kind. Founded 1899.



Send Coupon or write to address below
for **Free Book**

and full details,
including easy
Payment Plan.
**No obligation, no
salesman will call.**



COYNE Television Home Training Division

Dept. 39-H23, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____
Address _____
City _____ State _____

"Visible File" for Records


• This 3-panel wrought iron folding screen has 15 compartments, each holding up to seven 12-in. LP albums. Each assembled panel measures 6 ft. high, 12½ in. wide and 2½ in. thick, interlocks with adjoining panel and adjusts to de-

sired screen position. Mitred compartment corners make records easily accessible from any angle of screen, front or back. Priced at \$29.95 plus express charge on delivery, the screen is available from Leslie Creations, Dept. 178, Lafayette Hill, Penna.



Tape Recording Timer

• Timing any type of recording tape is easy with a new timer. Available as a ruler (50¢) with any 7-in. tape reel or as a 7-in. reel (\$1.75), the timer also carries a conversion table that shows how much recording time is left on the reel. By using a timer on each reel you can see at a glance both how much recording time is left and how much you have recorded. Manufactured by General Transcription of America, Dept. HMG, 1830 S.W. Fourth St., Miami 35, Fla.

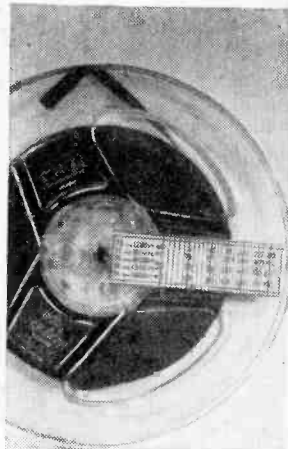

NO INSTALLATION! MOST MODELS JUST PLUG INTO CIGARETTE LIGHTER RECEPTACLE!

ATR


INVERTERS
for changing storage battery current to A.C. Household Electricity Anywhere . . . in Car, Boat, or Plane!

Electronic Tube PROTECTOR

protects ALL Electronic Tubes in TV or Hi-Fi, Amplifiers, and other Electronic Equipment. Will double or triple tube life including TV Picture Tube.

ATR

ATR SHAV-PAKS

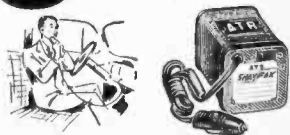

Keep Clean-Shaved! Plugs into Cigarette Lighter Receptacle. Keep in Glove Compartment. Operates Standard A.C. • **ELECTRIC SHAVERS** • Small Timing Device . . . in Cars, Buses, Trucks, Boats, or Planes.

MODELS
6-SPB (6 volts) 15 watts. Shipping weight 2½ lbs. **DEALER NET PRICE \$6.63**
List Price . . . \$9.95
12-SPB (12 volts) 15 watts. Shipping weight 2½ lbs. **DEALER NET PRICE \$6.63**
List Price . . . \$9.95

ATR Universal INVERTERS*



Operates Standard A.C.

• **TAPE RECORDERS** • **TV sets**
• Dictating Machines • Radios
• Public Address Systems
• Electric Shavers
• Record Players • Food Mixers
• and Emergency Lighting
MODELS
6U-RHG (6 volts) 125 to 150 watts. Shipping weight 27 lbs. **DEALER NET PRICE \$59.97**
List Price . . . \$89.95
12U-RHG (12 volts) 150 to 175 watts. Shipping weight 27 lbs. **DEALER NET PRICE \$59.97**
List Price . . . \$89.95

ATR Plug-in Type Portable INVERTERS*



Operates Standard A.C.
• **DICTATING MACHINES**
• Small Radios
• Record Players
• Electric Shavers
• Heating Pads, etc.
MODELS
6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. **DEALER NET PRICE \$30.00**
List Price . . . \$45.00
12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. **DEALER NET PRICE \$28.33**
List Price . . . \$42.50

***ADDITIONAL MODELS AVAILABLE**

ATR Plug-in Type Portable MIGHTY MIDGET INVERTERS*



Operates Standard A.C.
• **SMALL DICTATING MACHINES**
• Small Record Players
• Electric Shavers, etc.
MODELS
6-DME (6 volts) 30 to 40 watts. Shipping weight 5 lbs. **DEALER NET PRICE \$13.30**
List Price . . . \$19.95
12-DME (12 volts) 40 to 50 watts. Shipping weight 5 lbs. **DEALER NET PRICE \$13.30**
List Price . . . \$19.95

ATR Electronic Tube PROTECTORS

WILL DOUBLE OR TRIPLE THE LIFE OF ALL TYPES OF ELECTRONIC TUBES, INCLUDING TV PICTURE TUBE.
Model 250 (Wall Model) 115 volts A.C. Shipping weight 1 lb.
DEALER NET PRICE . . . \$3.30
List Price . . . \$4.95



See your jobber or write factory today!

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.

ATR

Now! Work Over
300 PRACTICAL
PROJECTS with these
PARTS AT HOME!

to help You learn
ELECTRONICS
RADIO-TELEVISION-RADAR

NOW . . . at home in your spare time you can get the very kind of training and subsequent Employment Service you need to get started toward real earnings in one of today's brightest opportunity fields—TELEVISION-RADIO-ELECTRONICS. Now that Electronics is entering so many new fields, here is a chance of a lifetime to prepare to cash in on its remarkable growth.

DeVry Tech's amazingly practical home method enables you to set up your own HOME LABORATORY. You spend minimum time to get maximum knowledge from over 302 practical projects, using the same type of basic equipment used in our modern Chicago and Toronto Training Centers!

DeVry Tech Provides EVERYTHING YOU NEED . . .

— to help you master TV-ELECTRONICS. In addition to the home laboratory and easy-to-read lessons, you even use HOME MOVIES—an exclusive DeVry Tech advantage. You watch hidden actions . . . see electrons on the march. Mavies help you to learn faster . . . easier . . . better.

LABORATORY TRAINING

Full time day and evening training programs in our modern Chicago and Toronto Laboratories are also available. MAIL COUPON TODAY for facts.



BUILD and KEEP Valuable TEST EQUIPMENT

As part of your training, you build and keep a fine Jewel-Bearing Vacuum Tube VOLTMETER and a 5-inch COLOR OSCILLOSCOPE—both high quality, needed test instruments.

EFFECTIVE EMPLOYMENT SERVICE


Get the same Employment Service that has helped so many DeVry Tech graduates get started in this fast-growing field.

"One of North America's Foremost Electronics Training Centers"

Accredited Member
of National Home
Study Council



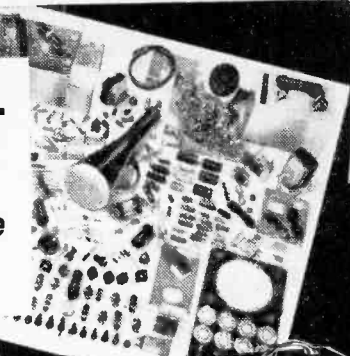DeVRY TECH INSTITUTE
Formerly DeForest's Training, Inc.
CHICAGO 41, ILLINOIS



EARN WHILE YOU LEARN

DeVry Tech's practical training helps you toward spare time income servicing Radio and Television sets.

✓ CHECK
These Exciting Job Opportunities:

- TV-Radio Broadcast Technician
- Color Television Specialist
- Radar Operator
- Laboratory Technician
- Airline Radio Man
- Computer Specialist
- Quality Control Manager
- Your Own Sales & Service Shop
- . . . PLUS MANY OTHERS

MAIL COUPON TODAY!

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. TVX-3-P

Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____
Street _____ Apt. _____
City _____ Zone _____ State _____
2045 Canadian residents address DeVry Tech of Canada, Ltd.
626 Roselawn Ave., Toronto 12, Ontario



NOW... POWER YOUR ELECTRONIC DEVICES WITH International Rectifier Corporation LOW COST SUN BATTERIES



this easy-to-understand book shows you how!

84 pages crammed with illustrations, plans, wire diagrams. Book fully explains basic theory and applications. Dozens of exciting projects thoroughly yet simply described. It's a "must".

only \$1.50

FAMOUS B2M SUN BATTERY

only \$1.50



Most widely used sun battery. Build your own light-powered radios, motors, sun relays, oscillators or light meters.

**BUY SUN BATTERIES,
BOOK AND COMPONENTS AT
YOUR ELECTRONIC
PARTS DISTRIBUTOR.**


If not available in your area, send check or money order (no C. O. D.'s, please) to:
**DISTRIBUTOR SALES DIVISION
INTERNATIONAL RECTIFIER
CORPORATION
EL SEGUNDO, CALIFORNIA**

International Rectifier Corporation

DISTRIBUTOR SALES DIVISION EL SEGUNDO, CALIFORNIA


Demonstrator Teaches Voltmeter Use

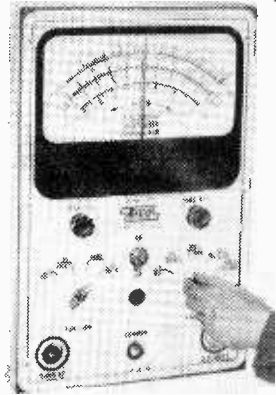• Teaching students the operation of a vacuum tube voltmeter is eased when the VTVM *Dynamic Demonstrator* is used. Simulating the Eico #221 VTVM in all its functions and ranges, the 13-in. meter scale makes classroom viewing possible. The demonstrator, measuring 14 $\frac{1}{4}$ by 23 by 3 $\frac{1}{2}$ -in., can be placed



atop a desk or wall mounted. Priced at \$10, the unit is available to teachers of physics and electronics from the Electronic Instrument Co., Inc., Dept. FME, 33-00 Northern Blvd., Long Island City 1, New York.

6 Volts from a 12-Volt Battery

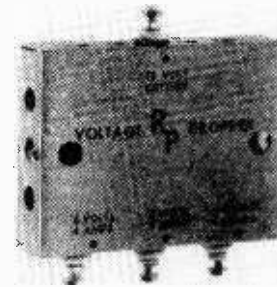


• Those shelf-bound 6-volt accessories can now go back in service with your 12-volt battery if you use the new 612 voltage dropper. Easy to install, the 4 $\frac{1}{8}$ by 3 $\frac{1}{8}$ by 1-in. unit supplies the necessary 6-volt power for radios,

trailers and what have you. The unit has nickel-chrome resistance elements terminating at four ceramic terminals.


To use the 612 dropper, connect the hot battery terminal to the voltage dropper terminal marked "12 Volt Battery," then connect those 6-volt accessories to the terminals marked with the ratings of 4 amps, 6 amps and 8 amps. The 612 comes complete with the necessary hardware and instructions, costs \$4.95 from the manufacturer, Rue Products, Dept. SM, 1628 Venice Blvd., Venice, Calif.

Tape Clips for Recording Fans

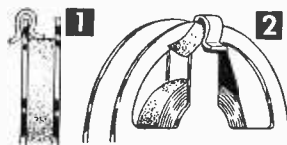

• Keeping recording tape on the reel is the job of Robins *Tape Clips*, TC-12. When reel is full, one edge of the clip holds the

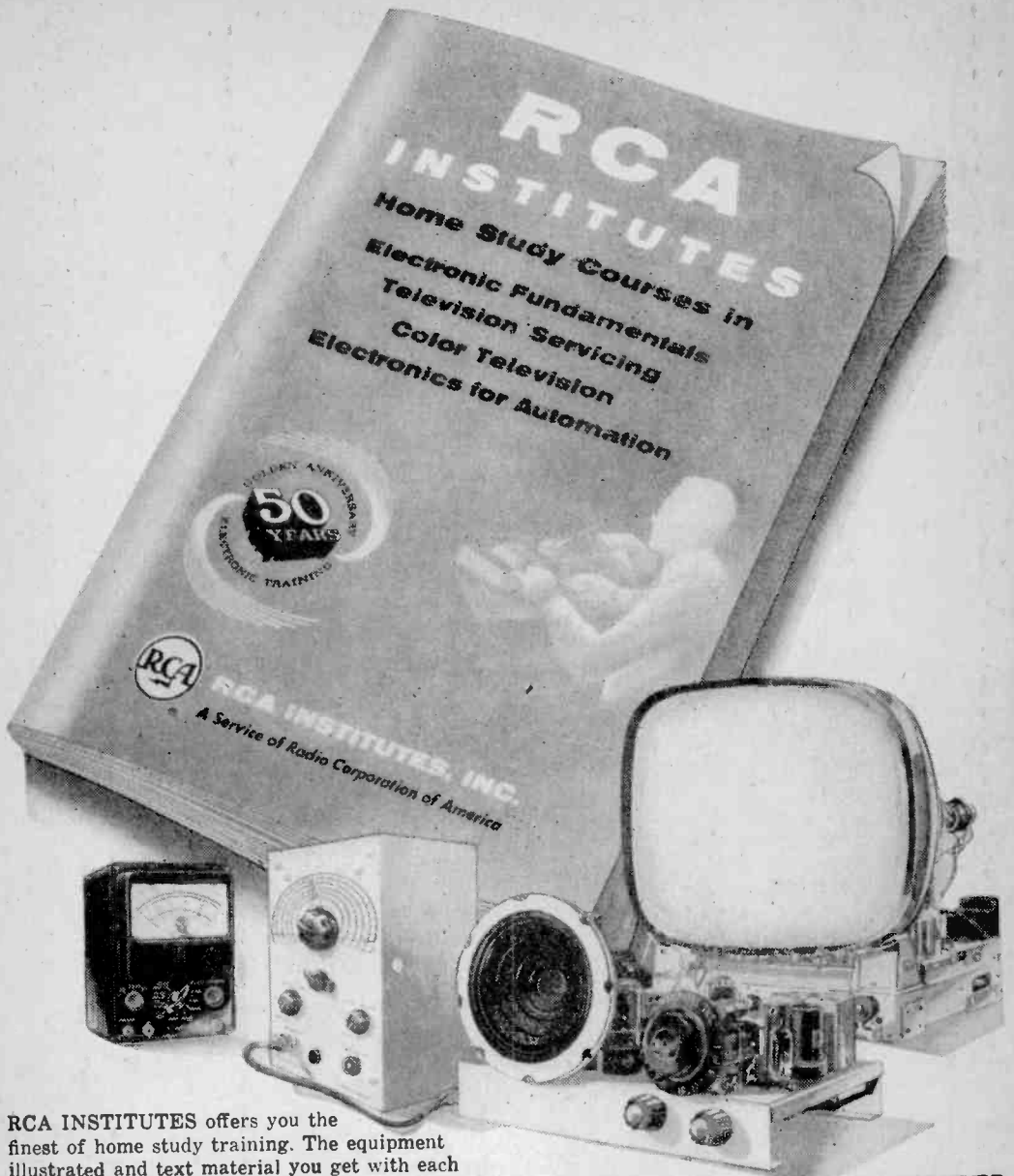tape (1); when reel is partly empty, plastic clip holds end of tape to reel (2). Available at hi-fi dealers for 35¢ a dozen, the recording tape clips are made by Robins Ind. 36-27 Prince St., Flushing 54, N. Y.



RCA INSTITUTES offers you the finest of home study training. The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.

**Send for this
FREE Book Now** ▶

RESIDENT SCHOOL offers Technical Institute and Vocational School Courses in Electronics. Day and Evening classes. Resident School Catalog sent free on request.

RCA INSTITUTES Inc. Home Study School, RTVE - 33
 A Service of Radio Corporation of America
 350 West Fourth Street, New York 14, N. Y.
 Without obligation, send me **FREE** complete CATALOG on Home Study Courses. No salesman will call.

Name.....
 please print

Address.....

City..... Zone..... State.....

Korean Vets! Enter discharge date.....

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:
 RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec
 To save time, paste coupon on postcard.

Abraham Marcus, co-author of famous best-seller
"Elements of Radio" makes amazing offer!



TRY MY TV and RADIO COURSE FREE REPAIR FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books get right to the point the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls. **DON'T WAIT!** You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.

MAIL THIS COUPON


Prentice-Hall, Inc., Dept. 5747-B1
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.60, plus a few cents postage. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.60 a month for two months.

Name
Address
City Zone State

Combination Radio-Intercom

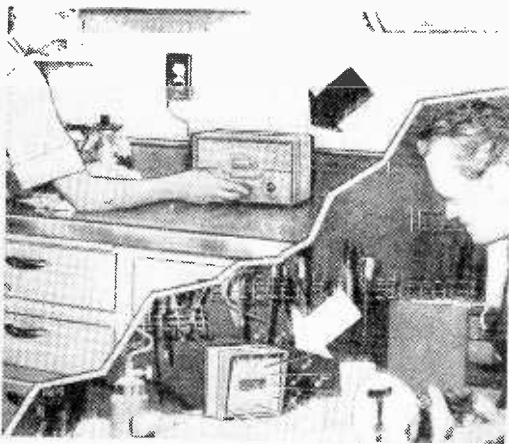• With the *Aristocom*, you can enjoy either a radio program or a two-way conversation with someone in another area of the house. Costing \$33.95, the *Aristocom* consists of a 5-tube ac-dc superhet receiver with self-contained speaker.



The wooden case measures 9¾ by 6 by 5½ in., is covered with a washable whipcord fabric in a choice of blue and grey or coral and grey combination. A switch, shown in the photo between the usual volume control and radio tuning knobs,

WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned radio-frequency tuner—AC-DC superheterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and re-adjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments, such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.




provides either radio programs to the external speaker or intercommunication.

Finished in matching colors and fabric, the external speaker measures 6¼ by 6 by 4¼ in. deep at the top, tapering to 3½ in. at the bottom. Its 50 feet of wire must be plugged into the socket in the rear of the radio. Additional speakers up to a total of four can be added to the set by purchasing a multiple speaker selector (\$6.75) and additional external speakers (\$6.75). Sets are available through radio stores or the manufacturer, *Aristocom Corp.*, Dept. RB, 5720 W. Armitage Ave., Chicago 39, Illinois.

Strobe for Tape Recorders

• A new stroboscope clocks tape recorder speeds of 3¾, 7½, and 15-inches per second. As usual with strobes, the viewing must be done with 60 cycle alternating current, a fluorescent light providing easiest reading. Costing

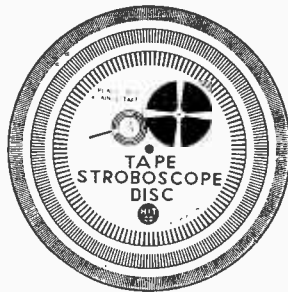\$4.95, the strobe will be sold by tape recorder dealers, according to the manufacturer, the H. & T. Company, Dept. DH, P.O. Box 6041, Montgomery 6, Alabama.



BUILD 16 RADIO

CIRCUITS AT HOME

with the New Deluxe

PROGRESSIVE RADIO "EDU-KIT"

A Practical Home Radio Course

Now Includes

- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ School Inquiries Invited
- ★ Sold in 79 Countries

ONLY
\$ **79.95**



Reg. U.S. Pat. Off.

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rack-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and service. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material. You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur License and build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television, Hi-Fi and Electronics. Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first success you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional soldering iron, and a self-powered Dynamic Radio and Electronics Professional Troubleshooting Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, Tester. In addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tester and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions. Everything is yours to keep.

Unconditional Money-Back Guarantee

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand, the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charges which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stalatis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$200 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Hunt L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with your Kit is really swell, and finds the trouble, if there is any to be found."

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name

Address

PROGRESSIVE "EDU-KITS" INC.

Progressive Building, Dept. 504NN, 1184-86 Broadway, Hewlett, N. Y.

BUILD THE BEST!


build quality money-saving
knight-kits

A PRODUCT OF ALLIED RADIO

see them all in
**ALLIED'S 1959
ELECTRONIC SUPPLY CATALOG**

free

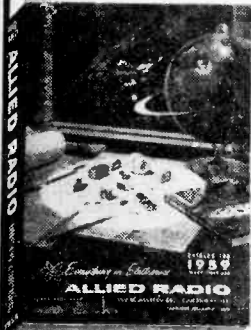**BUILD YOUR OWN!
IT'S EASY—IT'S FUN—
SAVE UP TO 50%**



452
value-packed
pages



HAM KITS



HOBBY
KITS



INSTRUMENT
KITS



HI-FI
KITS

SAVE on Everything in Electronics



WORLD'S LARGEST STOCKS: Everything for Experimenters, Builders, Amateurs, Servicemen, Engineers, Hi-Fi enthusiasts. Get more for your money in Hi-Fi systems and components, including latest Stereo; save on build-your-own KNIGHT-KITS; recorders and tape; Amateur station equipment; TV tubes, antennas, accessories; test instruments; industrial electronic equipment—plus the world's largest stocks of parts, tubes, transistors, tools and books. Send today for your **FREE 1959 ALLIED Catalog!**

EASY TERMS AVAILABLE

our 38th year

ALLIED RADIO

Everything in Electronics at Lowest Prices

send for
FREE
Catalog

ALLIED RADIO CORP., Dept. 64-C9
100 N. Western Ave., Chicago 80, Ill.

Rush **FREE** 1959 ALLIED 452-Page Catalog.


Name _____

Address _____

City _____ Zone _____ State _____

Multiple TV Sets on One Antenna

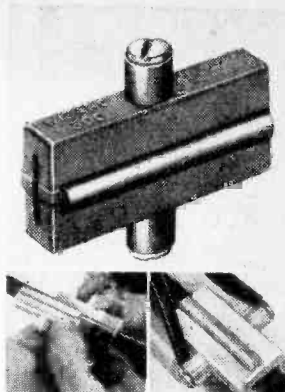• The Wizard 300 TV-FM set coupler is said to operate 20 sets from one antenna without amplification in normal signal areas. Permanent outlets may be installed throughout the building so sets may be moved from room to room or as many sets as outlets operated simultaneously. Neither strength nor quality of the signal is affected by other sets in operation.



The Wizard slides onto the antenna line and requires no splicing. The device picks up signals from the antenna line in much the same manner that the antenna picks up the signal from the transmission tower. By the use of electromagnetic coupling, insertion loss is greatly reduced, making it possible to operate the several sets from one antenna. The Wizard 300 is for 300 ohm flat line and lists for \$1.95; the 450 is for any open line where the conductors are spaced 1 in. or more and lists for \$3.30 a pair. They are made by the Charles Engineering, Inc., Dept. KJ, 6053 Melrose Ave., Los Angeles 38, Calif.

Pint-Sized Electric Organ




• This 18-lb. electric chord organ has a 3-octave range, with 37 keys and 12 chord control buttons. The left hand of the "musician" produces the full chords with a delicate 1-finger touch while the right hand seeks out the melody. Though built on the same principle as standard organs, this tiny mite can be mastered in a few minutes by following the instructions in the music book that comes with the organ.

Available in walnut or blond mahogany, the organ sells for \$129.95. A Deluxe model, at \$159.95, is equipped with microphonic pick-up and phono-jack for amplification through TV speakers and phonographs or through PA systems. Additional music books containing 25 songs each are available at \$1.50 a book. Organs are manufactured by the Magnus Organ Corp., Dept. RDI, Livingston, New Jersey.

Get into

TELEVISION RADIO-ELECTRONICS

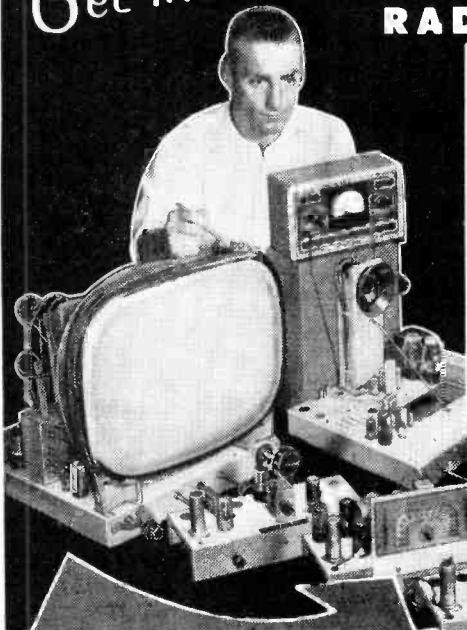

LEARN ALL 8 PHASES BY SHOP METHOD

1. Television ... including Color TV
2. Radio ... AM, FM
3. Industrial Electronics
4. Communications

OF THE INDUSTRY HOME TRAINING

5. Sound Recording & Hi-Fidelity
6. Automation
7. FCC License Preparation
8. Radar & Micro Waves

Let National Schools of Los Angeles, a Practical Resident Technical School for over 50 years, train you at home by Shop-Method for an limited opportunities in All phases of TV, Electronics, Radio.

You got 19 big kits of equipment!

GOOD JOBS ... MORE MONEY SECURITY ... ALL CAN BE YOURS

YOU are needed in the great modern Television-Electronics industry. Trained technicians are in growing demand, at excellent pay, in sales and service, manufacturing, broadcasting, telecasting, communications, research, and many other important branches of the field. National Schools Master Shop-Method Training, with newly added lessons and equipment prepares you in your spare time right in your own home for these fascinating opportunities. **OUR OUTSTANDING METHOD IS PROVED BY THE SUCCESS OF GRADUATES ALL OVER THE WORLD!**

YOUR TRAINING IS ALL INCLUSIVE

We prepare you for a long list of job opportunities. Thousands of TV and Radio receivers are being sold every day—more than ever before. And, now, Color TV is here. Applications of Electronics in industry—**AUTOMATION**—are growing in tremendous strides. The whole field is alive—opening up new, important jobs rapidly. National Schools complete training program qualifies you in all phases of the industry.

YOU EARN WHILE YOU LEARN

Many students pay for their entire training—and more—with spare time earning. We'll show you how you can, too! Early in your course you receive material that shows you how to earn extra money servicing TV and Radio receivers, appliances, etc., for friends and acquaintances.

YOU GET EVERYTHING YOU NEED

Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects—all the valuable equipment shown above—many other materials and services—consultation privilege with our qualified staff, and Graduate Employment Service. **EVERYTHING YOU NEED** for outstanding success in Electronics.

INDUSTRY NEEDS YOU. NATIONAL SCHOOLS WILL TRAIN YOU. SEND FOR FACTS TODAY NO OBLIGATION.

YOU LEARN BY SHOP METHOD ... you do servicing, circuit analysis, and do over 100 down-to-earth experiments. You build a Superhet Receiver and a modern TV Receiver, from the ground up, including a new, big screen picture tube. You also receive a professional, factory-made MULTITESTER. All of this standard equipment is yours to keep ... at just one low tuition.

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest electronic equipment - professionally installed - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - and part time job while you learn. Check box in coupon for full information.

Approved for GI Training 

NATIONAL SCHOOLS
LOS ANGELES 37, CALIF.

FREE! VALUABLE BOOK & SAMPLE LESSON - Just Send Coupon!



NATIONAL SCHOOLS
TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE - MAIL NOW TO
NATIONAL SCHOOLS, DEPT. RKK-39
4000 S. FIGUEROA ST.
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

Check if interested ONLY in Resident School training at Los Angeles. VETERANS: Give date of Discharge _____

Amazing New Handbook
Takes The "Headache"
Out of TV Trouble Shooting

Pin Point
TV TROUBLES
IN
10 MINUTES

SAVES TIME . . .
ELIMINATES GUESSWORK!

Now, a simple, practical way to accurately spot the cause of trouble in any TV set, FAST! Quick, easy-to-understand tests tell you in which of 5 TV set sections to find the cause of trouble. Fool-proof Check Charts help you locate the exact trouble spot at once, from as many as 700 possibilities. Book fits easily into your tool kit for handy on-the-job use. Over 300 spiral bound fast reference pages with 50 time-saving Check Charts; dozens of easy-to-understand diagrams and tests; explanations of circuits and designs. The hours and aggravation this amazing handbook can save you on a single servicing job more than pay its low price!

USE IT ON 7 DAYS FREE TRIAL!

Send no money, just the coupon. We'll rush your copy on FREE TRIAL. After 7 days, send only \$3.95 plus postage or return the book and owe nothing. Act NOW!

MAIL COUPON NOW!

Educational Book Publishing Div.

COYNE ELECTRICAL SCHOOL, Dept. 39-RT
1501 W. Congress Pkwy., Chicago 7, Ill.

Rush TV handbook for 7 days FREE TRIAL per offer.

Name Age

Address

City Zone State

Check here if \$3.95 enclosed. We pay postage. 7-day money-back guarantee.

186 Do It Yourself Plans

ILLUSTRATED CATALOG 10¢

NOW YOU CAN get simple, easy-to-understand plans for building boats, electrical equipment, models of gas and steam engines, famous firearms, antique automobiles, toys, games, cabin trailers, many other projects. In all, 186 useful things you can build. It's easy! It's fun! And you can save money! Do it Yourself! Send 10¢ now. Science and Mechanics Magazine, 5593 Dunham Bldg., Chicago 11, Ill.

TRAIN FOR

ELECTRONICS

RADIO-TV



AMERICA'S BIGGEST LITTLE SCHOOL
Midwest's First & Foremost

Our 25th Year Exclusively Electronics!

10-MONTH RESIDENT SHORT-COURSE

Special 10 in 1 training embraces Electronics; Radio, TV & Color TV Servicing; Communications; Radar; Microwave; Synchronos, Servomechanisms & Industrial Electronics. Prepare for F.C.C. License. Wide job opportunities & placement. Small school with big reputation. Personalized training; competent instructors. Vet. Approved.

UNIVERSAL TV-ELECTRONICS SCHOOL

318AA East 10th St. Kansas City 6, Mo.


Name Age

Address

City State

Veterans give discharge date

Timing Devices for Races

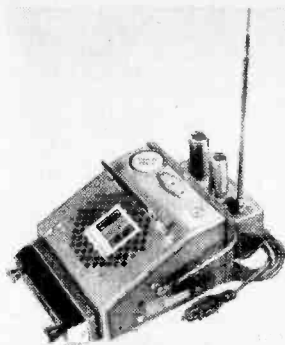

Rally-Verter shown attached to rear of car radio.



- Two new devices are being marketed for use in accurate timing from cars. The Rally-Verter (\$29.50) a compact short-wave converter, equips any car radio to receive 5000 kc time signals from radio station WWV (National Bureau of Standards) and 7335 kc signals from CHU

(Dominion Observatory near Ottawa, Canada).

The Checkpointer (\$69.50) is a portable receiver with attached converter for use at checkpoints or by contestants. It comes equipped with carrying handle, detachable telescoping antenna and cord with plug fitting any cigarette lighter receptacle. On both models one switch changes reception from broadcast to time signals. Devices are made by CGS Laboratories, Inc., Dept. JGB, Ridgefield, Conn.

Teletac for Handicapped

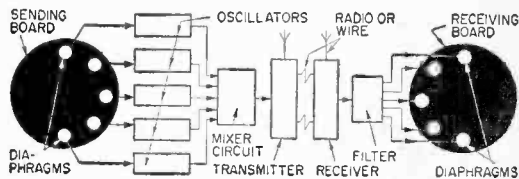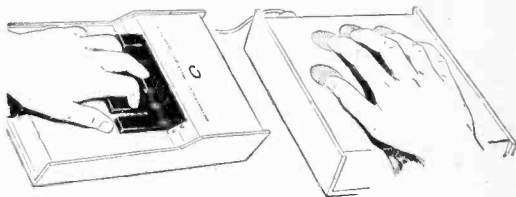- The deaf, blind-deaf and deaf-dumb will be able to "talk" and "hear" easily and quickly via an electronic touch system (Teletac) developed by Prof. Joseph Hirsch (see illustrations above) of Los Angeles State College. The sender spells out his words on the five keys of the transmit-



ter, using different combinations of keys and frequencies and varying the intensity and duration of vibrations picked up by listener on his fingertips which are resting on the diaphragms of the receiver. The device can be operated by remote radio control over any distance. Teletac is made on order by The Cardinal Instrumentation Corp., Dept. SM, 4201 Redwood Ave., Venice, Calif., for prices ranging from \$100 to \$300.

LOW COST introduction to the wonderful world of science!

The **AMERICAN BASIC SCIENCE CLUB** offers this

EXCITING HOME SCIENCE LABORATORY
Fascinating Experiments With



COMPLETE LABORATORY COMES IN 8 KITS . . . ONE A MONTH
SUPPLIES ALL THE EQUIPMENT FOR ALL THE FOLLOWING:

ELECTRICAL EXPERIMENTS

Educational fun with Electro-Magnets, Transformer, Galvanometer, Rheostat, Relay, Voltmeter, Wheatstone Bridge, and other electric equipment.

RADIO RECEIVER

A sensitive three tube regenerative radio—transformer powered. Can be plugged into regular 110 a/c home circuit. Complete with head set.

SPECTROSCOPE

Fascinating optical instrument used to identify and analyze substances by observing the spectrum of their flame. Spectrum charts included.

PHOTOELECTRIC EYE

Photoelectric Tube, Exciter lamp— and Electronic Relay. Everything you need to control motors, bells, alarms, and do other light beam experiments.

MICROPHONE

A sensitive carbon microphone that greatly amplifies unsuspected noises. Also adaptable for use with your radio transmitter.

ELECTRONIC EXPERIMENTS

Explore functions of vacuum tubes and other electronic components. Build an Electronic Switch—Amplifier, and other experimental circuits.

CODE PRACTICE SET

Signal Oscillator, Key and Flasher . . . the complete outfit to learn to receive and transmit the Morse Code . . . the first step to a Ham License.

STROBE LIGHT

A variable pulse neon light. "Freezes" motion of rapidly vibrating or rotating objects for close study and checking frequencies, RPM.

BROADCAST TRANSMITTER

Sends clear transmissions of both code and voice to nearby radios. Can be used with your microphone, record player, or code oscillator.

RADIO SERVICE EQUIPMENT

All the parts to build your own Radio Signal Tracer and a Probe Light Continuity Tester. Both pieces invaluable in radio servicing.

HEAT EXPERIMENTS

Laboratory studies of heat and its effect on solids, liquids and gases. Provides two Thermometers, Thermocouple, and Alcohol Burner.

TELESCOPE

A mounted astronomical telescope. High quality ground lens enables you to examine details of the Moon's surface and distant objects.

SOUND EXPERIMENTS

Laboratory demonstration of sound waves, resonance and pitch. Equipment includes Loud Speaker, Resonance tube and Sonometer.

SLIDE PROJECTOR

Takes 16mm and 35mm slides, sharp focusing, connect on cooled. G.E. Projection Lamp included. Also adaptable as a Projection Microscope.

MICROSCOPE

High and low power, precision-ground optical lens, self-illuminated. Adaptable for photomicrography in connection with photo lab.

PHOTOGRAPHY LAB

Complete dark room equipment: Printer—Enlarger—Electronic Timer—Safe Light—Developing Trays and supply of paper and chemicals.

LIGHT EXPERIMENTS

A group of interesting experiments with Optical Lenses, Prism, Photo-meter, Polarized Light, Ultra Violet "Black" Light and invisible infra Red.

WEATHER STATION

Aneroid Barometer—Humidistat—Sling Psychrometer—Anemometer Rain Gauge—Cloud Charts—Record Charts—Weather Map.

SPINTHARISCOPE

Gives you a blown up ringside view of the brilliant explosions of disintegrating radium atoms ejecting alpha particles at 11,000 miles per second.

ATOMIC RADIATION EXPM.

Check radioactivity of ores and do radiation experiments with sensitive Electroscope. Sample of Uranium and other radioactive ore.

ATOMIC CLOUD CHAMBER

The famous vapor chamber in which you see various types of illuminated paths made by sub-atomic particles bombarding us from outer space.



Analyzing Glowing Gases with the **SPECTROSCOPE**

Trouble Shooting with the **SIGNAL TRACER**

PHOTOMICROGRAPH of a Fly's Wing made with Microscope and Photo Lab (Actual Size 5" diameter)

These Kits are a Real Science Course Developed with World Famous

SOUTHWEST RESEARCH INSTITUTE

to bring the fascination of Science to the American Home

The set of eight Instruction Manuals is expertly written, clearly illustrated—easy to understand—exciting and interesting.

WITHOUT PREVIOUS EXPERIENCE

You can complete every project and acquire a valuable science background.

THESE KITS ARE NOT TOYS!

They consist of standard parts by: SYLVANIA, MALLORY, G. E., PYRAMID, STACKPOLE, TRIM AND OTHER RELIABLE MANUFACTURERS. Retail value of parts alone is over **FIFTY DOLLARS**

MEMBERS ARE ENTHUSIASTIC!

I wish I could provide each of my Physics students with all of your enjoyable kits. You are doing a wonderful job.

Allen T. Ayers
Physics Dept.
Jamestown High School
Jamestown, New York

Please accept my congratulations on the thoughtful study that must have gone into the planning of your Science Series.
W. B. Axtell, President
West Virginia Institute of Technology
Montgomery, W. Virginia

FREE! These 6 Auxiliary Textbooks

SAFE!

Circuits are low voltage supplied by isolation transformer that comes with first kit.



ALL THE EQUIPMENT FOR ALL THE ABOVE—only \$29.60

SEND **\$200** WITH ONLY COUPON PAY **\$345** FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 8 MONTHS)

FREE SOLDERING IRON with second Kit

Your Satisfaction or Your Money Back... AND you may cancel at any time without obligation.

These "no risk" assurances because we know you will be...

SURPRISED! AMAZED! DELIGHTED!

MAIL COUPON TODAY

AMERICAN BASIC SCIENCE CLUB, Inc., Box 524, San Antonio, Texas
Start sending me A.B.S.C.'s "Home Science Lab" in eight kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose plan checked.)
() I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
() I enclose \$29.60 as payment in full, POSTAGE PAID, for all eight kits. I may cancel at any time and get full refund on unshipped kits.

NAME _____
STREET _____
CITY _____ STATE _____

AMERICAN BASIC SCIENCE CLUB, Inc. San Antonio, Texas

OPTICAL BARGAINS

ERECT IMAGE LOW POWER MICROSCOPE



5X, 10X, 20X
\$80.00 Value — Only \$19.95
 Extremely sturdy with rack and pinion focusing, color corrected optics, turnable microscope body for inclined viewing, three different powers, long working distance under objectives, sufficient eye relief for easy viewing. Made from war surplus optical instrument so that you actually get \$80.00 of value. Weighs 4 lbs., 13" high. 10-DAY FREE TRIAL! Accessory objectives available for powers of 15X, 30X, 40X.

Stock No. 70,172-HP \$19.95 Postpaid



INFRARED SNIPERSCOPE TELESCOPE & PARTS

See in the dark—without being observed. War Surplus Sniperscope M-2. Contains the famous IP25-A Image Tube. Govt. cost about \$1200. Instrument complete, ready to use. Includes Power Pack, infrared light source. Will operate from 6V auto battery. Battery or transformer available.

Stock No. 85,053-HP \$150.00 f.o.b.
 Save still more money! Build your own Sniperscope! We will furnish instructions—parts, including: Power Packs, IP25A image tubes, light units, filters, etc. For details—request FREE Catalog "HP."

CLOSE MECHANICAL DRAWING SET

Regular Price \$18.00
 Our Price Only \$6.00 Postpaid.

American mfr. couldn't compete with foreign imports—thus you get a terrific bargain, even far below import prices. 10 handsome pieces in velvet-lined case. Nickel plated brass—

precision American-made. We guarantee you'll be satisfied or money refunded.

Stock No. 50,200-HP \$6.00 Postpaid

Quantity Price: 5 Sets for \$5.50 each Postpaid
 10 Sets for \$5.00 each Postpaid

WRITE FOR FREE CATALOG "HP"!

Complete Line of Astronomical Telescope Parts and Assembled Telescopes. Also large selection of lenses, prisms, war surplus optical instruments, parts and accessories. Telescopes, microscopes, Hand Spectroscopes, Sniperscopes, binoculars, etc. Request Catalog "HP"!

ORDER BY STOCK NUMBER, SEND CHECK OR MONEY ORDER. SATISFACTION GUARANTEED!
EDMUND SCIENTIFIC CO., BARRINGTON, N. J.

HI-FI ACCESSORIES

CROSSOVER NETWORK

WITH TREBLE CONTROL

ON GOLD EMBOSSED SOLID BRASS MOUNTING PLATE—Model CN-6

1500 cycle Crossover Frequency. 6db/octave attenuation outside of pass bands. 9db variation in treble response. Constant impedance full network (LCR) type. Negligible insertion loss in pass bands. Operates with both 8 and 16 ohm speakers. Mounts on speaker enclosure with gold embossed brass plate. All brass hardware and instructions supplied. Packed in attractive box with see-thru cover.



Pack- NET
 \$8.97

L-PAD WITH PHONE AND SPEAKER JACKS

Simplifies addition of phones and speaker to Hi-Fi system



Constant impedance devices for addition of phones and/or speaker to existing Hi-Fi system. Quality engineered L pad for smooth control of audio level. Ideal for monitoring Hi-Fi, P. A. and inter-com equipment. Completely wired—amplifier output leads are attached to two screw terminals. May be installed in multiple units for classroom or auditorium listening. Brass gold embossed plate mounts in standard wall box or on panel of Hi-Fi set. Brass hardware supplied. Packed in attractive box with see-thru cover.

Model JL-8 8 ohms NET
 Model JL-16 16 ohms \$7.77

Vidair

ELECTRONICS MANUFACTURING CORP.
 BALDWIN • NEW YORK

Camouflaged Mike for Candid Recording




• With the appearance and wearability of a wristwatch, this crystal microphone is ideal for investigative work by detection agencies and for "candid" recording. Case is chrome plated with gold-finish numerals and

hands. The strap is made of tan leather.

The thin flexible cable is 6½ ft. long, may be run up the coat sleeve to a concealed poche-type portable tape recorder or any high impedance tape recorder or amplifier mike pickup. Mike sensitivity is quite high and tiny perforations around the back of the watch case permit omnidirectional sound pickup. Known as the PA-47 Wrist-Watch crystal microphone, the unit is sold for \$5.95 by Lafayette Radio, Dept. RWT, 165-08 Liberty Ave., Jamaica 33, N. Y.

Shut-Off for Hi-Fi's

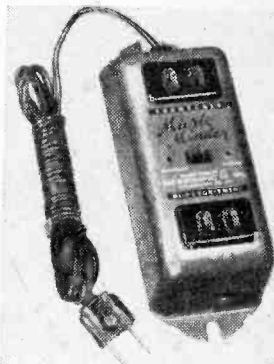• Featuring automatic shut-off for the phono after the last record is played, the *Music Minder* switch makes it possible for you to lapse into the arms of Morpheus with nary a care. Should you not need the automatic feature, set the switch to the "manual" position.



Housed in a drawn steel case with brown hammertone finish, the *Music Minder* lists at \$11.95, according to the manufacturer, the CBC Electronics Co., Inc., Dept. GA, 2601 N. Howard St., Philadelphia.


Monophonic or Monaural?

• Monophonic is the word to use when discussing high-fidelity sound, not monaural, according to a spokesman of the Institute of High Fidelity Manufacturers. While conventional high-fidelity recording does engrave the sound on both walls of the record groove, the result when reproduced is heard by both ears and is thus single-sound (monophonic), not "one-eared" (monaural). Also, the temptation to equate stereo with binaural should be suppressed, according to this spokesman. The correct term is stereophonic ("solid sound").

SUPERIOR'S NEW MODEL 82A

A truly do-it-yourself type TUBE TESTER

TEST ANY TUBE IN 10 SECONDS FLAT!

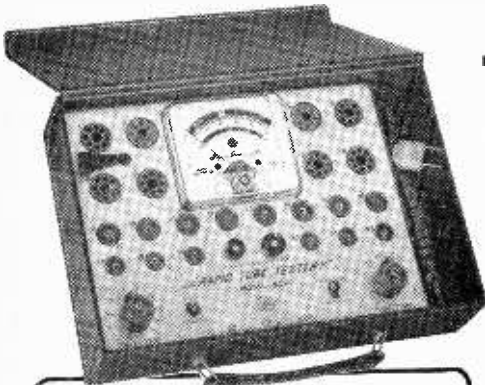

Model 82A — TUBE TESTER . . . Total Price \$36.50 — Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

- ① Turn the filament selector switch to position specified.
- ② Insert tube into a numbered socket as designated on our chart (over 600 types included).
- ③ Press down the quality button—

THAT'S ALL!

Read emission quality direct on "BAD-GOOD" meter scale.

Specifications

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. **\$36⁵⁰**
Only
(Picture Tube Adapter available for \$5.50 additional)

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more—and as proof, we offer to ship it on our examine before you buy policy.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch—THAT'S ALL! Read quality on meter. Inter-element leakage if any indicates automatically.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try it for 10 days before you buy. If completely satisfied then send \$6.50 and pay balance at rate of \$6.00 per month for 5 months.—No Interest or Finance Charges Added. If not completely satisfied return to us, no explanation necessary.

MOSS ELECTRONIC, INC.
Dept. D-567 3849 Tenth Ave., New York 34, N. Y.

Please rush one Model 82A. If satisfactory I agree to pay \$6.50 within 10 days and balance at rate of \$6.00 per month. If not satisfactory, I may return for cancellation of account.

Include Picture Tube Adapter at \$5.50.

Name.....


Address.....

City.....Zone.....State.....

All prices net. F.O.B., N.Y.C.

How To Stumble Upon A Fortune in GEMS

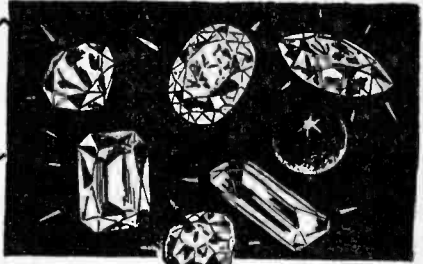All over the U.S.—Diamonds, Pearls, Amethysts, Opals, Garnets, Jade, Rubies, Topaz, Sapphires, Turquoise, Zircons, and other Precious and Semi-Precious Stones are Waiting to be Picked Up!...



Here is Exactly HOW and WHERE to Find Them...

Next time you trip on a rock—examine it carefully. You may have "walked into" a real fortune—unexpectedly. In a single year, over half a MILLION dollars worth of stones were found by week-end gem hunters. A youth pitching horse-shoes in an open lot picked up a stone and kept it in his pocket for 15 years before he discovered it was the largest alluvial diamond ever found in the U.S.A. ... 84.46 carats in weight. Two salesmen went gem-hunting on vacation and found a small pocket of "Tourmaline," a semi-precious, crystal gemstone, worth \$13,500.

IF YOU FOUND THIS IN YOUR BACKYARD



(as Wm. P. Jones of West Va. did) Would YOU know it was a 34.46 Carat Diamond? (see story at left)

the U.S.! Brand-new book, "Gem Hunter's Guide" tells all you need to know. Exactly where to find scores of precious and semi-precious gems. Where to find rich PEARL-bearing mussels. Complete town-by-town and county-by-county index helps you plan week-end and one-day gem hunting. How to recognize each variety.

53 Gem Stones Shown in Natural Color

These full-size photos make it easy to identify gem discoveries as they occur in nature. Simple tests you can give the rocks you find, plus 800 locations where gem materials

have been found all over U.S.A. and a special chapter on how to identify quickly 75 different and valuable gemstone varieties. Contains almost 200 pages packed with interesting illustrations, photos, maps, etc.

SEND NO MONEY!

Examine FREE for 5 Days

SEND NO MONEY. Just fill out and mail the coupon below. We will send the "Gem Hunter's Guide" for you to examine *Free* for 5 days entirely at our own risk and expense. If you decide to buy the book, it may be the richest investment you ever made. In a single day, it may pay you back many thousands of times its small cost. So rush coupon NOW for 5 days' FREE examination in your own home.

Science & Mechanics Magazine

450 East Ohio Street, Chicago 11, Illinois

Do You Know that

- Big, valuable, perfect Pearls have been found in many sections of the U.S.?
- 48,000 Diamonds have been found in Arkansas alone?
- A Diamond weighing over 20 carats was found in Va.?
- A vast region surrounding the Great Lakes holds the greatest store of Diamonds yet to be found in the U.S.?
- Gem sapphires are found in Colorado, Idaho, Montana, and North Carolina?
- For every diamond already found in this country, there are thousands more yet to be found?
- A cowboy found an Opal worth \$250,000.00?
- Mid-west streams have produced as much as half a million dollars worth of pearls in a single year
- 10-pound Turquoise nugget, believed largest ever found, discovered recently in one of our western states?
- Valuable Gems are discovered in all parts of the U.S.—even in New York City area?

Are You "Passing Up" Real GEMS Near Your Home?

Valuable gems are all around us—half hidden by surface dirt and other rock. Perhaps in an abandoned quarry near your home, a river bottom, a rocky hillside, a beach, or an old cave. If you know WHERE to look and how to RECOGNIZE the more precious stones—you can enjoy an educational hobby that can pay off BIG. Now you can enjoy and profit by gem-hunting—no matter where you live in



tells you:

MANY WAYS to test rocks to see how valuable they are: the color tests, hardness and specific gravity tests
HOW to plan a week-end gem-hunting trip
LOCATIONS where gem materials are found in EACH State—complete town and county index; with 81 detailed road maps giving gem-material locations
WHERE rubies are found in Georgia, Idaho, New Jersey and No. Carolina
How to make the drab rocks glisten like

magic with "black light"
HOW TO IDENTIFY over 75 different gem materials by hardness, composition, color, luster, cleavage, associated rocks, etc.
METHODS for classifying the gems by families.

WHERE big diamonds, pearls and rubies have been found in the U.S.

A SIMPLE PLAN for finding and harvesting pearl-bearing mussels.
THAT GEM QUALITY emeralds may be found in Maine, Massachusetts, New Mexico, Nevada, and North Carolina.

... ALSO special full-color portfolio shows 53 gem materials in their natural state.

Science & Mechanics Magazine, Dept. 5594 450 EAST OHIO STREET, CHICAGO 11, ILL.

Please send me—for 5 days' FREE EXAMINATION—a copy of the "Gem Hunter's Guide" packed with pictures, maps, charts, expert advice telling where gems may be found. Unless completely satisfied with the book at the end of 5 days' examination, I may return it and owe nothing. Otherwise, I will keep it and send you only \$3.95, plus 50c to cover postage and handling charges.

Name _____

Address _____

City, Zone & State _____

SAVE 50c POSTAGE AND HANDLING CHARGES by enclosing only \$3.95 WITH this coupon. Then WE will prepay ALL delivery charges. Return book within 5 days for full refund if not delighted.

New Symtronic Method

NOW! EARN MONEY IN TV SERVICING WITHIN ONE SHORT WEEK!

Make \$5 to \$10 Per Call IMMEDIATELY!

Here is the announcement our Engineering Staff has waited 5 years to make! Here is the final "break-through" in the television industry's giant efforts to perfect a simplified TV servicing system that eliminates the need for expensive training and long study! If you've thought about learning TV Service and Repair . . . if you've awaited any opportunity to have a prosperous, secure business of your own, then this is possibly the most important bulletin you'll ever read!

WHAT IS THE AMAZING NEW SYMTRONIC TRAINING METHOD?

Symtronic is a dynamic new concept based on the known fact that only a certain number of things can go wrong with any given set. For the first time these troubles, and their causes, have been isolated into three main groups. Through a comprehensive, but easily understood crossindexing system it's now possible to pin-point the trouble in one of the 3 groups in a matter of seconds! What previously required long schooling is now available to you immediately through the amazing Symtronic System. Our Free Sample Lesson shows how the Symtronic Method will work on your own set, or a friend's. Write for it today!

SYMTRONIC CUTS STUDY TIME . . . SAVES TREMENDOUS EXPENSE!

You want to get started servicing TV sets, not building them! So, why spend long months studying under old fashioned, outdated methods . . . learning things you'll never use? Why buy lots of equipment to practice with when you don't need it? With the Symtronic System the COMPLICATED TECHNICAL THEORY IS ALREADY TAKEN CARE OF BY OUR OWN SCIENTISTS! There is nothing more you need in this line. What we give you is practical, down-to-earth know-how based on our many years of solid, scientific experience! Our revolutionary Symtronic methods let you compete immediately with servicemen who have had years of experience!

FIELD-TESTING PROVES EFFICIENCY OF SYMTRONIC METHOD!

Our exclusive new training technique does not deal with "gimmicks" or "gadgets." It was perfected over a five-year period by two of the most respected electronic scientists in the TV field, in cooperation with every major TV manufacturer in the United States! Even TV Servicemen trained by the old costly, time-consuming methods were amazed by our Symtronic training technique. Typical of the general reaction was the comment of Mr. D. B. K., owner of a TV Repair Shop in Reseda, Calif. As he put it, " . . . I only wish your training

was available when I went into TV Servicing. Would have started making money a lot sooner . . . Would have saved me hundreds of dollars . . . believe your Symtronic method will revolutionize TV Repair schooling." Furthermore, this dynamic new method was first field-tested among 3000 men and women. Results proved conclusively that anyone of average intelligence could learn to diagnose and service virtually any given malfunctioning set under our system almost immediately! Fantastic? Perhaps, but remember, nearly all significant improvements are based upon simplification. This theory finds its broadest expression in our Symtronic training methods!

SYMTRONIC PUTS YOU IN YOUR OWN BUSINESS NOW!

Imagine—with our amazing training method you know everything needed to handle any make of TV set, within one short week! And, without buying any expensive tools or equipment, you learn at home—spare time. A few evenings of fascinating reading is all it takes. This is fact . . . not fiction. In just 7 days or less you will have sufficient knowledge and ability, and confidence in yourself, to make from \$5 to \$10 per service call—earn \$150 a week, working out of your home! Here, unquestionably, is your chance of a lifetime to get into the booming TV business . . . to enjoy the freedom and security that comes with a successful business of your own!

COMPLETE SYMTRONIC BUSINESS PLAN PROVIDES "BLUEPRINT TO SUCCESS"

To make our training program the most practical available, we also offer a complete Business Plan developed by leading advertising and business consultants. Step-by-step, you learn how to get business, how to operate from your home, how to charge, how to keep records, etc.—a complete "Blueprint to Success" that explains fully how to start, conduct, and expand your own TV Service Business. In short, we not only offer the most streamlined, effective TV training available, but a tested and proven Business Plan that eliminates all guesswork. Here, surely, is a "Business Package" that may easily bring you all the good things you desire . . . a practical education with a lifetime of value!



CASH IN ON THIS BIG PROFIT, BIG FUTURE INDUSTRY!

TV servicing is a multi-million dollar industry and it's growing like wildfire! To keep pace, thousands of qualified Servicemen are urgently needed each year. The pay is big and there's no limit to your future success. Television is here to stay! In this field, too, you get paid for what you accomplish, not how long you work. \$5 to \$10 per call is the usual service charge . . . even though the job may take only a few minutes! Add to this the almost 100% profit on tubes and parts and you can easily see how Symtronic can put you into the big money practically overnight!

APPLY THE SYMTRONIC METHOD TO YOUR OWN SET, OR THAT OF A FRIEND'S—prove to yourself that our amazing Symtronic method is all we say. What better proof exists! Send us your name and address today, and we'll rush you a free sample lesson along with complete information on our Symtronic training technique. Read this lesson carefully . . . apply it to your own set or a friend's, and you'll convince yourself that the Symtronic method can bring you a successful TV Servicing Business within one short week! Clip and mail coupon today—supply of free lessons is limited!

FREE!

SAMPLE LESSON PROVES SYMTRONIC METHOD WORKS!



RUSH COUPON TODAY

and you will ALSO receive free details on how you can obtain a complete "Business in a Package" (that will virtually put you in the TV Repair business with a total investment of five dollars). Wholesale Catalog of TV parts and equipment; Franchise opportunities, etc., etc., all sent free—

RUSH COUPON TODAY!

MAIL TODAY FOR FREE LESSON

TV Servicing Systems
 Dept. C-872, 1038 So. LaBrea Ave.
 Los Angeles 19, California
 Please rush proof that your Symtronic TV Training Method is all you say. Send Free Lesson and complete details, without obligation. (No salesman will call.)

Name


Address

City..... Zone..... State.....

How To Make Toys

Worth from \$2 to \$50

from Scrap Materials

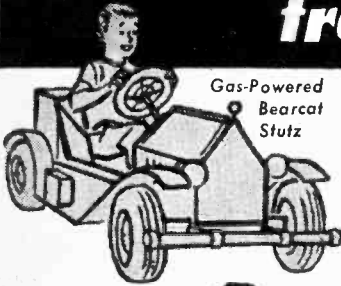

Gas-Powered
Bearcat
Stutz



Steam
Shovel



Toy-Size
Baking Range

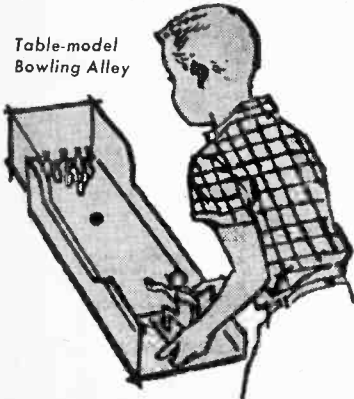


Table-model
Bowling Alley

Those pieces of scrap lumber—that discarded electric motor—or any one of the scores of “useless” parts or materials in your basement or garage—can be converted easily into exciting toys that will thrill any child. So don’t “clean house” for you can build toys for youngsters that would sell from \$2.00 to \$50.00 in the stores from all sorts of discarded things. Thousands of home workshop enthusiasts are doing this. You can too!

IT'S EASY! IT'S FUN! SAVE MONEY, TOO!

Our new 192-page handbook, **TOYS AND GAMES YOU CAN MAKE**, gives plans and instructions for making 78 action toys, thrilling games and fascinating playthings. You can make toys for Christmas gifts, birthday parties and many other occasions.

Best of all, only ordinary hand tools are needed to make most of these projects. And you don't need to be a “pro” either, for our simple, easy-to-follow plans show you exactly H-O-W to proceed. The detailed drawings, photographs, materials lists and step-by-step instructions make it easy as A-B-C.

Something for Every Child

This giant collection of toys range from pull toys for tiny tots to a suitcase-size power-cycle for the older lads. With the plans in this Handbook, you will be the real “Santa Claus” of the family. And what fun you will have making toys, plus the cash savings that go with making them.

ORDER YOUR COPY—NOW!

Ordinarily, a book like this would sell for \$3.00 or more but as long as our DeLuxe First Edition lasts, we will send you a copy for only \$1.95. But remember, the quantity is limited, so **ACT NOW**. Just attach your check or money order to the handy coupon and mail—NOW. We guarantee complete satisfaction or your money refunded.

Here's WHAT You Can Make

- Animal pull toys
- Baseball game
- Fold-up pool table
- Tricycle tractor
- Kiddy-plane
- Walking doll
- Snark missile
- Pogo stick
- Toy crossbow
- Merry-go-round
- Punching bag
- Croquet set
- Motor boat
- Steam shovel
- Backyard monorail
- Electric dart game
- Sand hoist
- Foldout sandbox
- Express wagon
- Helicopter
- Pop-up pull toy
- Doll's high chair
- Roller-skate scooter
- Portable see-saw
- Stutz Bearcat
- plus 53 more exciting toys

SCIENCE & MECHANICS MAGAZINE, Dept. 5596
450 East Ohio Street, Chicago 11, Illinois

MAIL COUPON NOW!

Enclosed is \$1.95 for which send me, all charges prepaid, a copy of the DeLuxe Edition of your new 192-page handbook, “Toys and Games You Can Make.” If I am not completely satisfied, I may return the handbook within 5 days for full refund. I take no risk.

NAME

ADDRESS

CITY, ZONE AND STATE

PEE WEE BATTERYLESS "LIFETIME" RADIO
TUBELESS



GUARANTEED—FOR YOUR LIFE! FOR AS LONG AS YOU OWN IT! NO TUBES, BATTERIES, TRANSISTORS OR ELECTRICAL PLUG-INS NEEDED! Will never run down or burn out! SMALLER THAN A PACK OF CIGARETTES! RECEIVES LOCAL RADIO STATIONS ANYTIME—ANYWHERE YOU GO! Easy thumb tuner. NO DANGLING

EARPHONES. HAS BUILT-IN SPEAKER PHONE! Black gold plastic cabinet, semi-conductor wave detector. NOT IMPORTED. MADE AND GUARANTEED BY AMERICANS—You can always get service.

SEND ONLY \$2.00 (bill, ck, mo) and pay postman \$4.99 COD postage on arrival or send \$6.99 for postpaid delivery. SENT COMPLETE READY TO LISTEN WITH LIFE GUARANTEE—NOTHING EXTRA TO BUY EVER! FREE LONG DISTANCE ANTENNA if you order now. Available only from:

MIDWAY COMPANY Dept. WRE-2 KEARNEY, NEBR.

CODE-RECEIVING SPEED



LEARN CODE the fast, easy way. Get maximum speed and efficiency to qualify as an operator in the quickest, easiest way. Picture yourself at your own transmitter, sending out radio code, messages that will be received around the globe. For 47 years the CANDLER system has trained beginners for all telegraphing requirements, operator licenses, highest ratings, and FCC specifications, both amateur and commercial.

4 CANDLER COURSES AVAILABLE:—Beginning Code Course; Amateur Code Course; Simplified Code Course; Type It Right Course. Send for Free details today.

CANDLER SYSTEM
P. O. Box 9226 Dept. 109 Denver 20, Colo.

ALL BAND TRAP ANTENNA!



Best for All-Band Receivers Low S.W. R. 80-40-20-15-10 5" x 1" — 3-ounce Molded Traps No metal or losses in field


For ALL Amateur Transmitters. Guaranteed for 300-watts For Pi-Net or Link-direct feed Light — Neat — Weatherproof

Complete as shown with 87 ft.—72 ohm feedline—102 ft. copper-weld. Eliminates inefficient multiple antennas. Gets beam results on 20-15-10. No tuners, loading troubles or hay-wire house appearance. Excellent for shortwave listeners. Looks good, works good and lasts. For novice and all class amateurs. 80-40 20-15-10 meters. Complete, assembled.....\$12.95
40-20-15-10-50 Ft. Antenna, assembled.....\$11.95
20-15-10 meter Dual Trap, 30 ft. Antenna, assembled...\$18.95

SEND ONLY \$3.00 (cash, ck., mo) and pay postman balance COD plus postage on arrival, or send full price for postpaid delivery. Available only from:

WESTERN RADIO • Dept. ARE-2 • Kearney, Nebraska

\$6.95
Ppd.


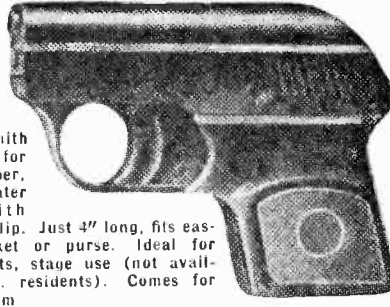


The skilled hand of the German gunsmith is responsible for this .22 caliber, 6-shot repeater automatic with self-ejecting clip. Just 4" long, fits easily into pocket or purse. Ideal for sporting events, stage use (not available to Calif. residents). Comes for \$6.95 ppd. from

BEST VALUES

Dept. G-467 403 Market, Newark, New Jersey

**Interesting, Pictorial
FREE
BOOKLET**

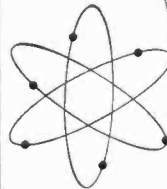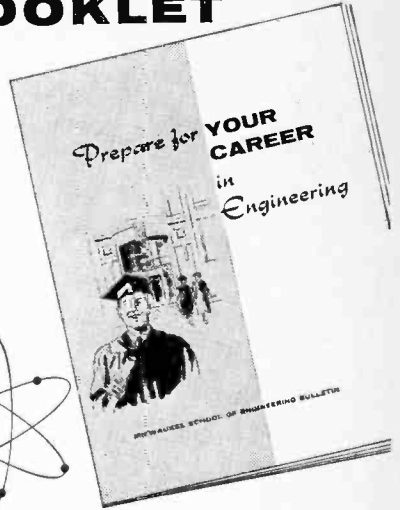

to help you decide on
your career in
**ELECTRONICS
RADIO-TV
COMPUTERS
ELECTRICAL
ENGINEERING**

Here is a graphic story about preparing for your career as an engineer or engineering technician in electronics, radio, television, computers, etc. Booklet tells about:

- Wide variety of job opportunities
- Courses offered, degrees you can earn
- Pictures of the Milwaukee School of Engineering and its facilities
- Recreation and fraternities
- Scholarships; part-time work

Milwaukee School of Engineering
— dedicated to serving young men and industry

SEND COUPON TODAY!

Milwaukee School of Engineering
Dept. RTX 59, 1025 N. Milwaukee St., Milwaukee, Wis.

Please send me free new booklet "Prepare for Your Career in Engineering"
I'm interested in Radio-TV Electronics
 Computers Electrical Engineering

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I am I am not eligible for veterans educational benefits. (discharge date)

**SCIENCE and
MECHANICS'
DO-IT-YOURSELF
LIBRARY**

Boat Builder's Handbook
Build It Yourself
Car Owner's Handbook
Craftsman's Handbook
Craftwork
Do-It-Yourself Handbook
Home Electrical Handbook
Home Owner's Handbook
Home Workshop Handbook
1001 How-to Ideas
**How to Start a
Successful Small Business**
Income Opportunities
Model Craft Handbook
Photo Craftsman
Repairing Home Appliances
Science Experimenter
Sportsman's Handbook
**Toys and Games
You Can Make**

Copyright 1959 by
SCIENCE AND MECHANICS
 Publishing Company
 450 East Ohio Street
 Chicago 11, Illinois

Boy's Bike Radio

By HOMER L. DAVIDSON

HERE is a small radio that will make the bike-riding contingent in your family very happy. Bracket-mounted to the bicycle, the homemade plastic case has the set's speaker mounted upward so that music or voice travels up to the rider for clear, loudspeaker-volume listening pleasure.

The small size of the set is due to the use of printed circuit boards, two of them, an RF-IF section and an audio section (See Figs. 2, 3, and 4).


A small ferrite antenna coil picks up the RF broadcast signal; this signal is tuned by C1. A small pull-up antenna, added to the circuit for greater signal strength, provides enough signal strength so that the receiver does not have to be turned in the direction of the signal for adequate volume. One section of a discarded rab-





Have radio, will travel with this compact superhet receiver. Stripes were painted on plastic case by masking with tape and using paint from spray cans obtainable at hardware and 5- and 10-cent stores.



bit-ear TV antenna can be used for the pull-up antenna.

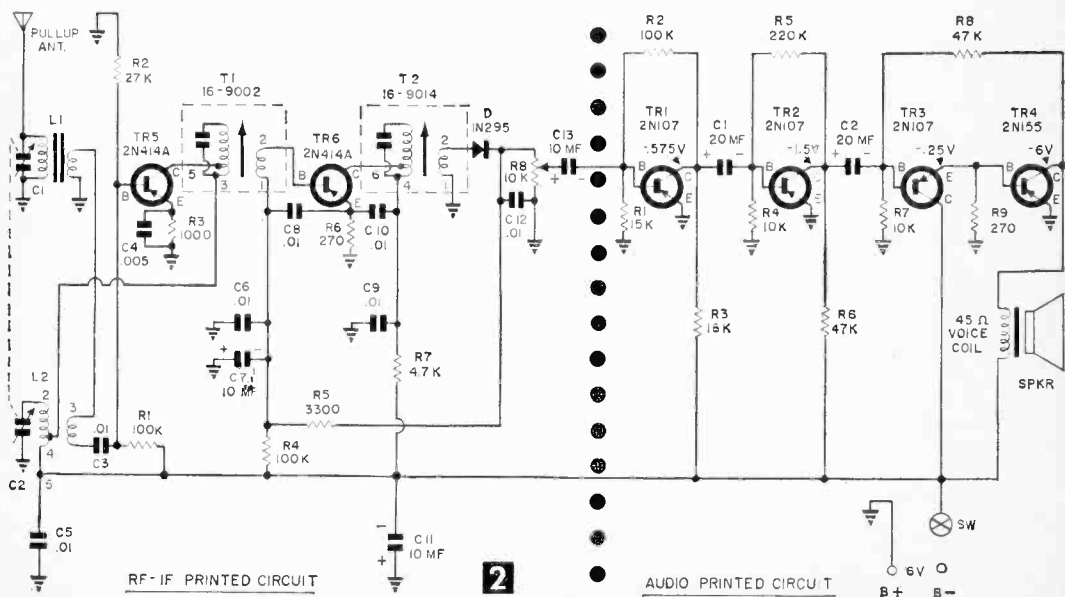The incoming RF signal is fed through one side of the oscillator coil to the base connection of TR5. The difference in frequency between the incoming signal and the oscillator frequency results in the intermediate frequency of 455 kilocycles.



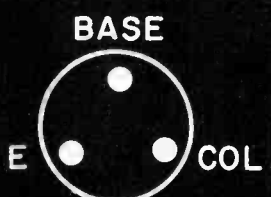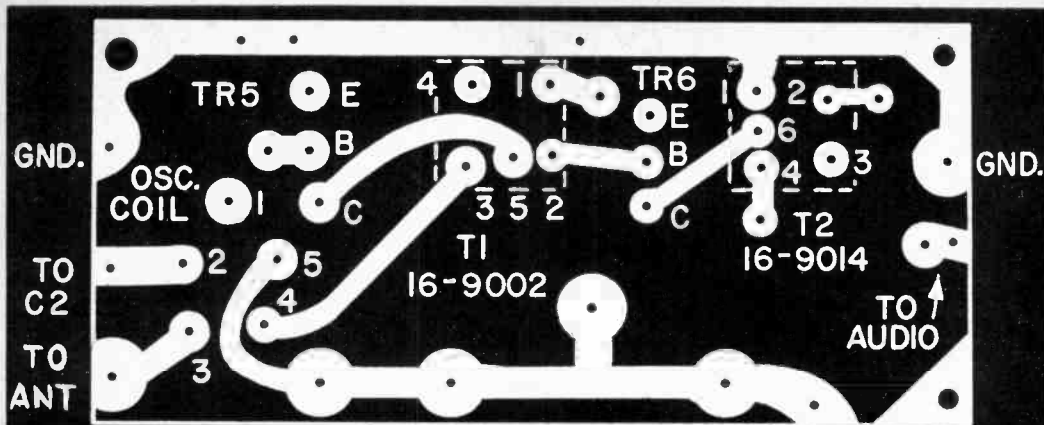


2N414A
TRANS. BASE
HOOKUP

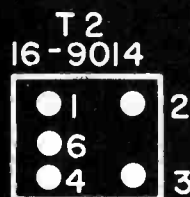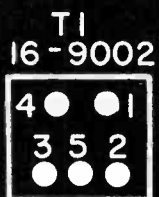

BOTTOM VIEW
OF IF TRANSFORMERS
455 K.C.

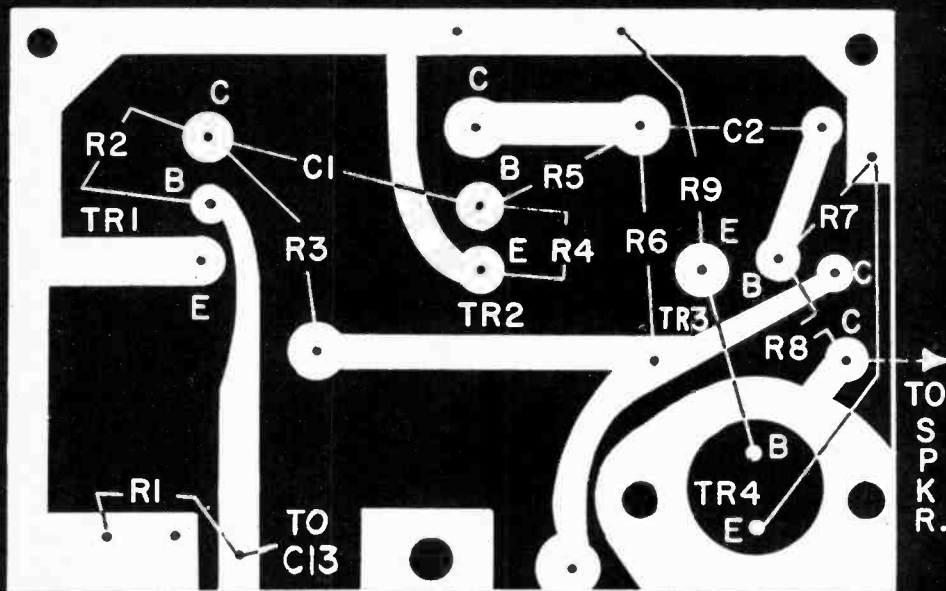3 RF-IF PRINTED CIRCUIT (ACTUAL SIZE)
(WHITED AREAS COPPER PRINTED CIRCUIT)



COMPONENTS MOUNTED ON OPPOSITE SIDE SHOWN

4 AUDIO PRINTED CIRCUIT. (ACTUAL SIZE)

The two IF frequency stages, T1 and T2, amplify the signal, after which crystal diode D1 rectifies it to audio frequency. Volume control R8 controls the volume of the AF signal before it is delivered to the audio circuit. The RF-IF printed circuit is shown actual size in Fig. 3; the audio circuit in Fig. 4. These circuits can be traced with carbon paper directly upon the copper side of the PC board. First, wash the copper side of the board with soap and water so that no grease or residue will prevent the paint or tape resist from adhering to its surface.

After the circuit has been traced on the copper side, fill in the shaded areas with resist and let dry about three hours (or less if board is placed under a lamp or in an oven). Pour enough etchant solution into a small tray so that board will be covered, then place the board in the tray and agitate the tray to hasten etching. If the solution appears to darken, the paint resist is mixing with it and no harm is done. Keep agitating the tray for 20 to 30 minutes and then wash the etched board in running water. Pour the remaining etchant solution back into the bottle; it can be used again.

Now clean the etched plate with carbon tet



or contact cleaner, wipe off all remaining paint resist and wash board again in soap and water. Wipe both surfaces dry and check to see that no connections are made between close copper terminals.

Next, take soldering paste and smear it lightly over the copper circuit. Then, with a soldering iron and rosin-core solder, tin the copper sides. When this is done, drill the small holes. A bit is included in technique-kit which comes with the boards (see Materials List) for drilling the small component mounting holes, a 1/4-in. bit is used to drill the larger holes.

Now mount circuit components (see Figs. 2, 3, 4 and 5). Make transistor soldering connections next to last. I used small dia. spaghetti insulation over the transistor tinned leads and soldered them directly in place. With wiring completed, secure transistors with rubber bands.

Mount the variable resistor and switch last. The small prongs from the volume control can be soldered directly to the printed circuit. You can test the unit by simply hooking a phonograph directly into the input of the small amplifier.

5 PICTORIAL

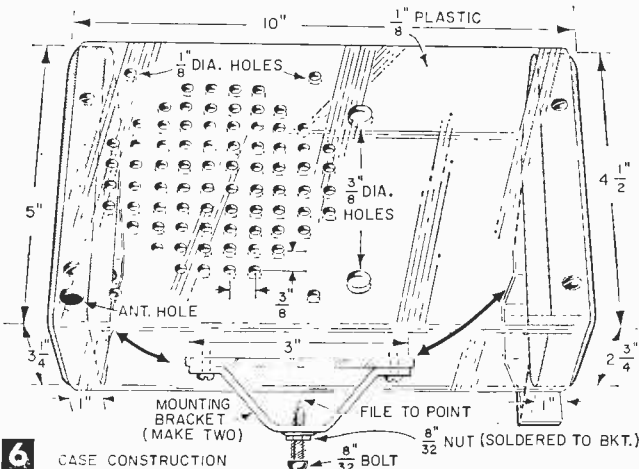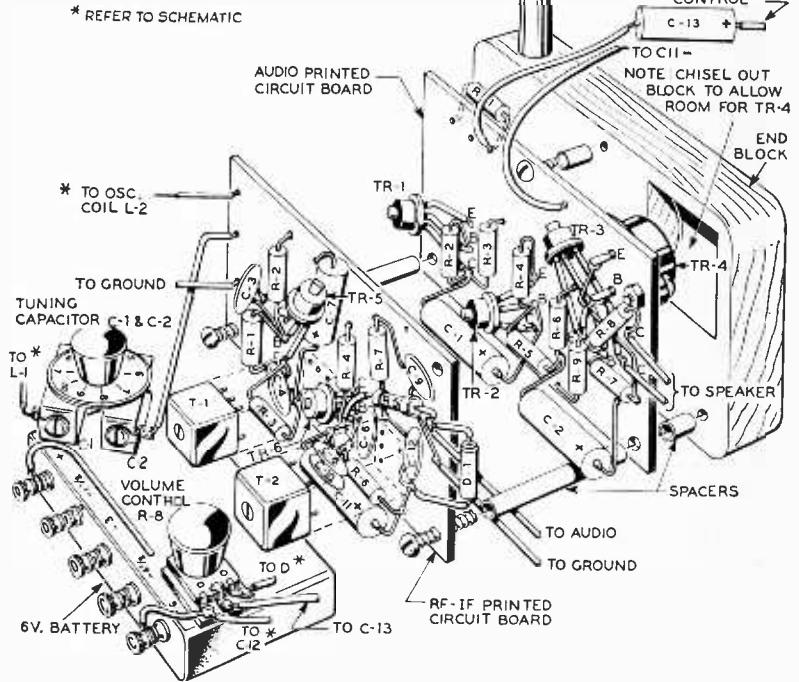

6 CASE CONSTRUCTION

MATERIALS LIST—BIKE RADIO
RF & IF SECTION

Desig.	Description	Desig.	Description
L1	antenna coil (Lafayette MS264)	R2	100,000 ohms, 1/4-watt carbon resistor
L2	oscillator coil (Lafayette MS265)	R3	18,000 ohms, 1/4-watt carbon resistor
C1 & C2	RF & OSC Capacitor (Lafayette MS261)	R4	10,000 ohms, 1/4-watt carbon resistor
C3, C5, C6, C8, C9, C10, C12	.01 mfd miniature capacitors	R5	220,000 ohms, 1/4-watt carbon resistor
C4	.005 miniature capacitor	R6	47,000 ohms, 1/4-watt carbon resistor
C7, C11, C13	10 mfd 25 v electrolytic capacitor	R7	10,000 ohms, 1/4-watt carbon resistor
R1 & R4	100K, 1/8-watt fixed resistor	R8	47,000 ohms, 1/4-watt carbon resistor
R2	27K, 1/8-watt fixed resistor	R9	270 ohms, 1/4-watt carbon resistor
R3	1000 ohms, 1/8-watt fixed resistor	C1 & C2	20 mfd 50 v electrolytic capacitors
R5	3300 ohms, 1/8-watt fixed resistor	TR1, TR2, TR3	2N107 GE transistors
R6	270 ohms, 1/8-watt fixed resistor	TR4	power CBS transistor 2N255
R7	4.7K, 1/8-watt fixed resistor	SPK	4" PM, 45-ohm voice coil operadio type
R8	10,000 ohms, 1/8-watt fixed resistor	PC Board	3 x 4 1/2" (see text)
TR5, TR6	2N414A Raytheon transistors	6 v battery	Eveready No. 409 or Eveready No. 773
T1	16-9002 455 IF transformer (Meisner)	PRINTED CIRCUITS	
T2	16-9014 455 IF transformer (Meisner)	Kit Number 5003P	
D-1	1N295 fixed diode (Raytheon)	(This kit has enough material to make up several experiments or projects). OR	
	AUDIO SECTION	1	PE-5 liquid etchant (pt.)
R1	15,000 ohms, 1/4-watt carbon resistor	1	PRL liquid resist (oz.)
All materials available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.		1	PCDXXX copper laminated board
		1	PCBXXX copper laminated board

Physical construction. The cabinet of the bike radio is constructed from 1/8-in. clear plastic. It is designed to fit between the two bike braces that go from the seat to the handle-bar assembly. Greater protection for it is found here and, also, the pull-out antenna will not be readily bumped. The cabinet measures 10 in. long and 5 in. wide at one end, tapering to 4 1/2 in. at the other. The top of the cabinet is 3 1/4 in. deep at one end, tapering down to 2 3/4 in. at the other (see Fig. 6) to fit between the two braces.

First, make the two end blocks of 1-in. pine, rounding off all corners. Then cut a scrap width to a length so that when it is placed between the two ends and nailed, the overall length of this assembly is exactly 9 1/2 in. This serves as a form for the plastic case.

Take a piece of pliable cardboard and wind around this form. Cut the cardboard to fit at both ends and to overlap at the center line about 1/2 in. Unwind it and use as a pattern to cut the plastic form by laying the plastic sheet under it and drawing around it with a pencil. Cut the plastic with a jigsaw, exercising extreme care so that it will not crack and split.

Now mold the plastic around the wooden blocks, form assembly by placing the sheet in an oven set to 400°F for a few minutes until it is pliable enough to go around these two blocks. Use gloves when bending it around. Before the plastic cools enough to take shape it has a tendency to roll off the form. To prevent this, tie a shoe lace at each end, and cinch them up as tightly as possible.

If the plastic should set before the bending is completed, simply put it back in the oven until it is workable again. Glue the case together at the bottom with chemical solution purchased with the polystyrene plastic material.

Now drill holes in the plastic for the speaker, tuning capacitor, volume control and to hold the wooden end blocks (see Fig. 6) and bolt the printed circuit boards together with long bolts and metal spacers made from discarded alumi-

num TV antenna rods. The audio printed board is screwed to the top wooden block end, the antenna is mounted and the lead-in soldered to it. Solder all extension wires (volume control, tuning capacitor and battery connections), insert battery and your bike radio receiver is ready to be fired up.

Use a signal generator to peak the RF and IF

stages, or have a radio-TV serviceman do this. (See also "How to Align Superhet Circuits," page 66 of this handbook.) The IF stages can be peaked to the correct frequency by hooking the signal generator to pin 2 of the oscillator transformer. Short out C2 with clips and set the frequency to 455 Kc; the IF stages are now peaked to the correct frequency. The signal is next applied to the antenna circuit which is tuned to around 1400 kilocycles, the variable capacitor to be adjusted until the frequency appears. Adjust the oscillator core for maximum signal volume. The variable capacitor should be rocked back and forth here until the greatest signal volume is obtained. Then repeat the previous stages of peaking. Stations should be heard over the entire broadcast band.

When tuning and testing has been completed, mount the top end, with speaker, inside the case (solder small nuts to the speaker frame so they will not be hard to hold inside the case). Cut a slot in the plastic for the pullout antenna, mount it, and then the battery, fastening it by a strap to the bottom end block. To help the tuning capacitor hold on station when in use, place a rubber grommet over its shaft and press the knob down tightly against it and case. Place small homemade brackets (see Fig. 6) underneath the cabinet and screw setscrews into the wooden blocks and your receiver is mounted.

Grommet Pulls Radio's Pilot Light




• It's no problem at all to remove a blown pilot light from its socket if you slip a rubber grommet over the bulb's slick glass envelope (see photo.) The snug-fitting grommet will grip the envelope's surface and provide an easy-to-turn "knob".

Six-Transistor Portable Superheterodyne

Small enough to fit into a cigar box, this set still has a much larger speaker than would be found in most commercial transistor radios

By THOMAS A. BLANCHARD

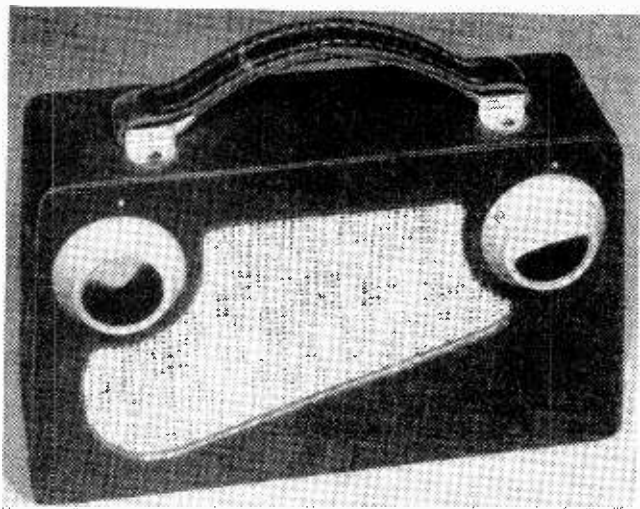

Completed set chassis mounts in this modern cabinet with woven gill-straw grille. Plastic control knobs are push-on type. Chassis mounts vertically. Set may be powered by eight penlite cells wired in series as well as by a #266 pack.


dio output. Power is provided by a #266 Eveready 9 v battery (which has up to 250 hours intermittent life).


The chassis follows the flat-plate design now employed by many TV sets. Four 1/2 x 1/2 x 1 in. wood blocks glued inside the cabinet allow the chassis to be screwed rigidly in place in a vertical position. The flat plate greatly simplifies wiring since in most instances the component leads themselves are long enough for connections. However, since these leads are bare, plastic insulating sleeving (radio spaghetti) should be used on all wires except those terminating on chassis ground lugs. Both local and mail-order parts houses can furnish a complete set of parts including cabinet and punched chassis for a fraction of the cost of the individual items (see Materials List).

The chassis plate measures 5 x 8 1/2 in. and may be of #14 steel or aluminum. The tapered cabinet sides require that the upper corners of the plate be trimmed. (With a rectangular carrying case, trimming wouldn't be necessary.) Make a rectangular opening 1 7/8 x 2 3/8 in. in the lower center of the plate to allow room for the battery (see Fig. 3). A unique method for reducing the bulk of the set's 4-in. PM speaker is the rectangular opening through which the magnet projects. This hole is located 3/8 in. above the battery cut-out, and measures 1 1/4 x 1 3/4 in. The speaker is supported by three screws (1/4 x 6-32) on 1/4 x 1 in. metal spacers.

Cut openings for the IF transformers 1/2-in. square and mount each transformer firmly grounded to the chassis by means of the end-can mounting lugs. Holes for the transistor sockets measure 1/8 x 11/32 in. Sockets are inserted in the opening and secured with a locking ring which snaps in place.

COMMERCIAL transistor sets have pared down dimensions to the very minimum through use of printed-wiring chassis boards. Here, however, is a small six-transistor superhet which employs only standard components—no printed circuits—and is still small enough to fit into a cigar box or small modern cabinet (see photo above for kit cabinet). Its circuit (see Fig. 2) employs a two-gang variable capacitor for tuning the transistor converter circuit, there are two 455 kc IF stages, a germanium diode detector, audio driver, and push-pull au-

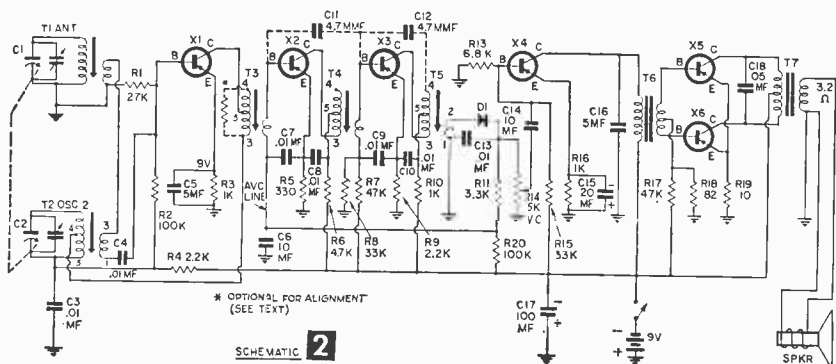

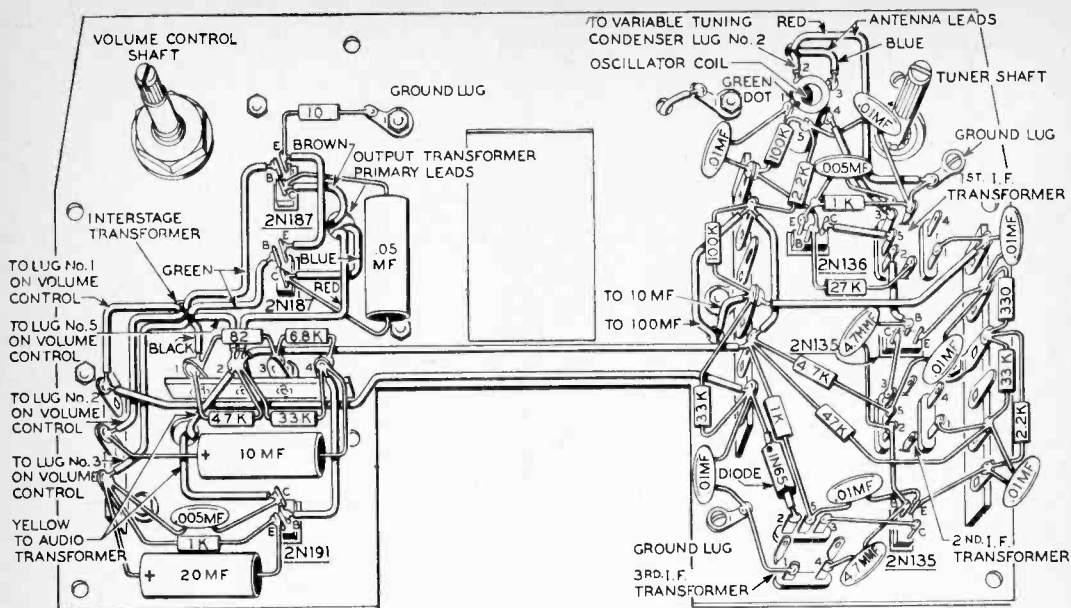

3 PICTORIAL

As soon as all stationary parts (coils, transformers, tuner, volume control, speaker and tie-strips) have been mounted to the chassis, begin wiring. Except for the speaker and ferrite loop antenna, all parts are mounted with $\frac{1}{4}$ in. 6-32 machine screws and nuts. The antenna coil is mounted on 1-in. spacers or standoffs with the rod secured by fiber clamps placed under the standoff screwheads.

Complete all connections made with solid leads first, leaving the installation of resistors and capacitors until last. Make leads as short and direct as possible (see Pictorial, Fig. 3), keeping wires close to the chassis. The small 4.7 mmf. ceramic coupling capacitors connected to the interstage IF (2nd) and output IF (3rd) stages should be placed as close to chassis as possible. Positions of other capacitors is not critical so long as it approximates that shown in Fig. 3.

Because of the minute size of the IF transformer and transistor socket lugs, bulky soldering irons or guns do not lend themselves to neat construction. Use one of the inexpensive pencil-type soldering irons when working with transistor circuits. Good solder is very important, too. The best available to the experimenter is Kester's "Resin-5."


Having ascertained that all wiring is correct, insert transistors into their sockets. Next, connect the battery—but first apply a strip of tape along the right-hand edge of the chassis opening so that battery connectors do not short circuit.

Of course the receiver should be properly aligned. Alignment instructions for transistor superheterodyne receivers will be found in the article "How to Align Superhet Receivers," page

MATERIALS LIST—PORTABLE SUPERHET

No. Req.	Description
1	T-1—ferrite rod ant. Coil: $3\frac{1}{8}$ " dia. x $5\frac{1}{8}$ " long
1	T-2—5-wire transistor oscillator coil
2	T-3, T-4—1st (input) & 2nd (interstage) IF transformers (Automatic #BS725G)
1	T-5—3rd (output) IF trans. (Automatic #BS726G)
1	T-6—audio driver trans. (Stancor #A-4292, etc.)
1	T-7—audio push-pull output trans. (Stancor #A3856, etc.)
1	X-1—GE 2N136 transistor (converter)
2	X-2, X-3—GE 2N135 transistors (1st & 2nd, IF)
1	X-4—GE 2N191 transistor (audio driver)
2	X-5, X-6—GE 2N187 transistors (audio output)
1	D-1—germanium diode detector; 1N64 or 1N48
6	transistor sockets
1	chassis plate, aluminum 5 x $8\frac{1}{2}$ ", #14 gage
misc.	hardware & tie strips as indicated in Pictorial, Figs. 3 and 4
Resistors	
1	R-1—27K, $\frac{1}{2}$ watt composition resistor
2	R-2, R-20—100K $\frac{1}{2}$ watt composition resistor
3	R-3, R-10, R-16—1K, $\frac{1}{2}$ watt composition resistor
2	R-4, R-9—2.2K, $\frac{1}{2}$ watt composition resistor
1	R-5—330 ohms, $\frac{1}{2}$ watt composition resistor
2	R-6, R-17—4.7K, $\frac{1}{2}$ watt composition resistor
1	R-7—47K, $\frac{1}{2}$ watt composition resistor
2	R-8, R-15—33K, $\frac{1}{2}$ watt composition resistor
1	R-11—3.3K, $\frac{1}{2}$ watt composition resistor
1	R-13—6.8K, $\frac{1}{2}$ watt composition resistor
1	R-14—5K ohm volume control with switch
1	R-18—82 ohm composition $\frac{1}{2}$ -watt resistor
1	R-19—10 ohm composition $\frac{1}{2}$ -watt resistor
Capacitors	
1	C-1, C-2—2-gang Variable Tuning Capacitor (11-235 mmf. Ant. Section, Osc. Section 11-111 mmf.)
7	C-3, 4, 7, 8, 9, 10 & 13—.01 mfd. ceramic disc capacitors
2	C-5, C-16—.005 mfd. ceramic disc capacitors
2	C-6, C-14—10 mfd., 25v. electrolytic capacitors
2	C-11, C-12—4.7 mmf. ceramic disc capacitors
1	C-15—20 mfd., 25v. electrolytic capacitors
1	C-17—100 mfd., 25v. electrolytic capacitors
1	C-18—.05 mfd. paper tubular capacitor
1	4-in. PM Speaker with 3.2 ohm voice coil and V magnet

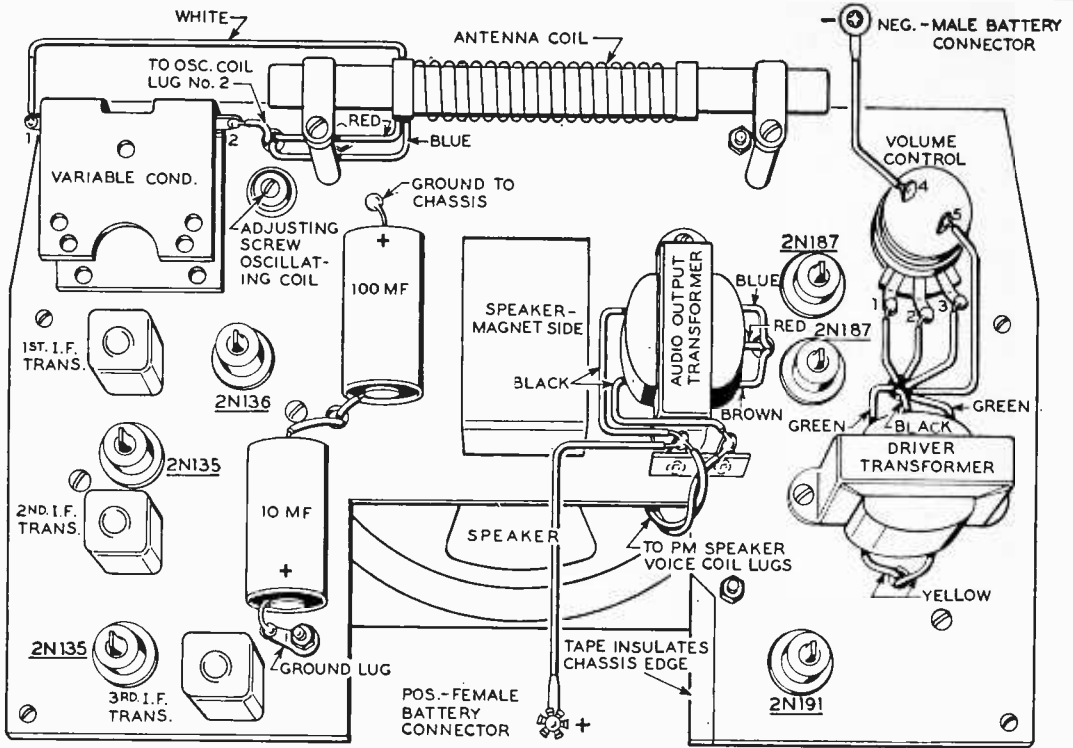This set, known as the Arkay Model TR-6 is available in kit form coast to coast from radio supply houses for \$33.95. Or write Radio Kits, Inc., 120 Cedar St., New York 6, N. Y., for literature and name of nearest dealer.



4 PICTORIAL


66 of this handbook. However, a quick check to determine that the wiring is correct can be made as follows: Wind two turns of insulated wire around the lead end of the ferrite antenna coil and attach the other bared end to a metal object such as the finger stop of a telephone. Turn on the set to full volume and rotate the tuner until a station is heard.

The oscillator which mounts in a rubber grommet on the chassis, contains an adjustable tuning screw or slug. Turn this screw with a plastic blade screwdriver. (A suitable tool for this purpose can be made by filing the end of a plastic crochet needle.) A point will be found where the signal becomes strong. A second adjustment can be made by turning the trimmer screw of the Osc. section of the tuner.

A transistor set does not have the sensitivity

or tone quality of a vacuum-tube receiver; a 4-tube battery superhet will outperform any 6- or 7-transistor superhet—but, a transistor radio's low operating cost, and unusual freedom from operating breakdowns offset its shortcomings. And to further offset its shortcomings, a flexible lead can be tucked inside the set for providing coupling between the antenna rod and an external antenna as afforded by any metal object. In addition, when only the loop is used, mounting it as far away from the chassis as possible will improve reception. In commercial sets, the antenna coil is frequently enclosed in the plastic carrying handle. This set could be so modified if the builder desired, by replacing the leather grip with a length of plastic tubing mounted on plastic standoffs. The loop would be protected and concealed by the tubing.

Crystal Holder Is Handy Connector

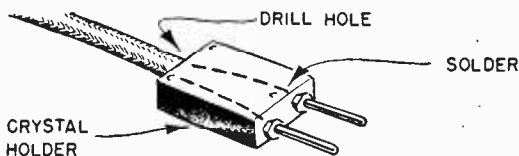


seemingly outlived its usefulness, use it in conjunction with a suitable crystal socket to make a handy two-conductor connector. Simply drill holes through the top of the holder to receive wire leads, and solder the wire ends to the holder prongs inside as shown in the diagram.—J.A.C.

• After a crystal holder of the type used in a radio transmitter or communications receiver has

• Place TV tubes in hard rubber basins, available at surplus stores, for safe keeping while trying another tube or handling other repairs on the set. The hard rubber is less likely to damage the tube than metal containers.—H. LEEPER.

Hi-Fi Tone Arm and Moving-Coil Pickup

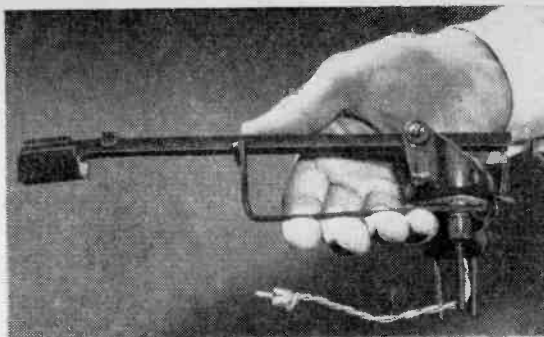

With the investment of a few hours' time and a modest outlay in parts and material, the advanced hobbyist can experience the thrill of constructing his own high-quality moving-coil pickup and tone arm.

By JOHN E. TURNER

Unquestionably, best performance is realized if the arm described in this article is used with the pickup accompanying it.

Construction. In addition to basic hand tools (hacksaw, file, needlenose pliers, diagonal cutters, tin snips, soldering gun), you'll also need the following (to complete the rather delicate construction of the stylus-moving coil subassembly): a pair of small pointed forceps, two or three small sewing needles, and a lens with a magnification of about 5 diameters, preferably mounted on a stand so that hands will be free.

The majority of the materials and parts, used in this project (see Materials List), are obtainable at the local hardware store and from radio-supply houses at relatively low cost. The matching transformer, however, which must necessarily be of high quality to insure good reproduction, entails somewhat greater expense. Likewise, a diamond tip is rather costly, but when one considers its advantages over all other phono points, it represents a modest investment.

The Pickup. Begin construction by drilling out the rivet in the magnetic door latch assembly (see Materials List) and removing the magnet and two pole pieces. From one of the steel pole pieces cut out a $\frac{1}{8} \times \frac{3}{16}$ in. block. This will be the flux block, and it may have to be filed down later to provide adequate clearance for the moving coil. Then, from the same material, cut two pole pieces measuring approximately $\frac{3}{32} \times \frac{3}{8}$ in. Be sure to file all edges of the block and pole pieces to remove burrs.

Now, remove both ends from a cleaned tin can, slit it longitudinally, and cut off the upper and lower seams. Then flatten the can, and lay out and cut out the base plate of the moving coil-stylus subassembly (see Fig. 1). If a Heppner magnetic latch is used, make the base plate $\frac{3}{4} \times 1$ in. to fit the magnet (Fig. 2). Any cur-



You get all music from your records that you pay for when you build this hi-fi tone arm and pickup. Inset shows assembly of arm lift.

IN PRINCIPLE, phonograph arms and pickups are comparatively simple devices, and the hi-fi enthusiast who possesses a reasonable amount of mechanical skill—and patience—can construct the integrated unit described in this article without trouble, and with the satisfaction of having made an arm and pickup whose performance, by listening tests, compares favorably with better-quality, expensive commercial counterparts.

The pickup can be installed in the arms of most commercial record changers, but experience has shown that results may then not be entirely satisfactory because of the high compliance and sensitivity of the stylus-coil mechanism. Specifically, the pressure of the pawl which activates the change cycle on many types of changers will cause considerable distortion when records with eccentric center holes are played.

vature remaining in the tin plate after flattening can be eliminated by squeezing the base plate between the jaws of a pair of needlenose pliers.

The bearing-block clips, coil-support-block clips, and lead-support-block clips (see Fig. 1) are cut from a strip of tin plate $\frac{3}{32}$ in. wide. They are formed with a pair of needlenose pliers and cut to length with a pair of diagonal cutters. Because of some variation in the thickness of the rubber bands used for the block assemblies, clip openings will have to be determined from the specifications of the materials on hand, but they will be roughly $\frac{1}{16}$ in. The bearing block clips must be about $\frac{7}{64}$ in. high and their top edges will be flush with the cover assembly when the unit is completely assembled. Again, it may be necessary to make small adjustments in dimensions by filing. Make the lead-support block clips and coil-support block clips about $\frac{1}{32}$ in. shorter, since they must fit below the dust cover.

Scribe a center line on one surface of the base plate to facilitate positioning of the clips (Fig. 1) and tentatively position components with a dab of airplane glue. When every component is properly aligned, solder the flux block *first* since it will require the most heat. Then solder all the clips in place, the bearing block front clip flush with the edge of the base plate, the second clip about $\frac{5}{64}$ in. behind it. Leave about $\frac{1}{32}$ in. between the rear bearing block clip and the coil-support block clip. If the last clip is located flush with the rear edge of the base plate there will be about $\frac{3}{16}$ in. space for connecting the leads.

Now, place the base-plate assembly on the edge of the magnet and fit the pole pieces as shown in Fig. 2. They must be directly opposite the flux block with their top edges flush with the surface of the block. When they

have been accurately located, secure them with airplane cement. (Since all the components of this pickup are very small, airplane glue must be applied sparingly; this can be best accomplished with a fine sewing needle.)

Unbraid a short length of 12-strand picture wire, stretch a single strand with needlenose pliers, and cut off a piece about 1 in. long. Although the finished shaft is only $\frac{1}{32}$ in. long, it will be easier to mount the jewel if it is not trimmed to length and formed until later. See Fig. 3 for details on removing the jewel tip. The metal plate in Fig. 3 can also be made from tin plate. A $\frac{1}{16}$ -in. hole drilled in it (a little smaller if number drills are available) permits the jewel to pass into the balsa block as it is forced out

the shank with the tip of a fine sewing needle. Usually it will be necessary to scrape away the cement securing the tip to the shank. A GE 1-Mil Diamond (4G-01D) is suggested, since it is reasonably priced, available from most electronics supply houses and comparatively easy to remove from its mounting.


After the jewel tip has been separated from its shank, carefully remove it from the balsa block with the moistened tip of a sewing needle. Do not attempt to pick it up with a pair of forceps unless you are very adept with this instrument. A squeeze at the wrong moment may cause it to fly out of your grasp and it is exceedingly difficult to find in a 9 x 12-ft. room. Lay the shaft on the balsa block and apply a small drop of airplane cement at a point midway between its ends, carefully pick up the jewel (with the needle) and push it into the drop of cement. This operation will take a little practice—and a steady hand, since the quantity of cement is small and it will dry rather fast. After the jewel has been positioned, and before the cement has hardened too much, carefully align the tip perpendicular to the shaft and then do not handle it again until the bond is secure.


At intervals of 15 minutes, or so, apply airplane cement very sparingly to the joint between the jewel and the shaft.

Two, or at the most three, additional applications of cement should be sufficient to insure a good joint. After the cement has thoroughly hardened, inspect the shaft assembly to see if the jewel is oriented perpendicular to the shaft. A misalignment of 3° or 4° will not be too serious, but if it is out of line more than this, dissolve the cement with nail polish remover and do the job over again.

When inspection indicates that the shaft assembly is satisfactory, cut one end of the shaft about $\frac{5}{64}$ in. from the jewel and the other end $\frac{1}{32}$ in. from the stylus. Bend $\frac{3}{64}$ in. of this longer end downward as shown in Fig. 3 and the shaft-jewel assembly is ready for mounting.

Wind the moving coil on a balsa wood block cut to the dimensions indicated in Fig. 4. Pass a mandrel of common stove wire through the block and cement it on both sides. Wrap a layer of kitchen aluminum foil around the block before starting the coil of wire, then wind roughly an inch of No. 40 magnet wire around the left side of the mandrel to form one lead of the coil. Wind the coil itself in two layers with a total of 21 turns. It is not essential that the coil be

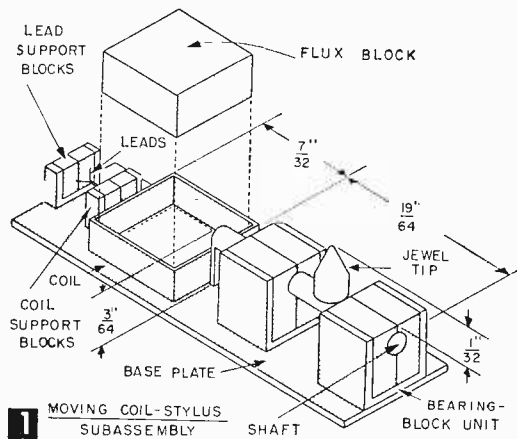

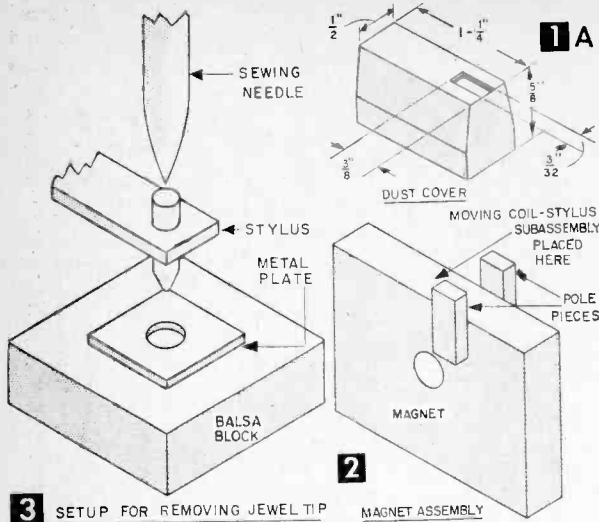

mount the coil by first slipping the leads between the coil-support blocks. If the coil does not at first fit perfectly within the air gap, even though it may be large enough, re-form it with a couple of sewing needles; it is quite soft, and adjusting its shape is not difficult. When it has been determined that the coil fits properly cut a few shims from a 3x5 file card and fit them around it to keep it perfectly centered during cementing. Cement the front end of the coil (opposite the leads) to the shaft (Fig. 1), and while the cement is drying, squeeze together the coil-support block clips and trim off the excess rubber. As soon as the cement has hardened, remove the shims and test the movement of the stylus-coil assembly by deflecting the jewel with the tip of a needle. The coil should swing freely through a reason-

able arc with a very light touch of the needle. If it does not, reshape it until it does. Although the attraction of the magnet appears to hold the moving coil-stylus subassembly quite securely, it is best to apply a little cement to both surfaces before mounting the base plate permanently to the magnet.

as perfect as shown in Fig. 4, but it should be as thin as possible to facilitate alignment of the coil within the air gaps. When 21 turns have been wound around the form, twist the free end of the wire around the right side of the mandrel and paint the coil with airplane dope, using a fine sewing needle for this job. When the dope has dried, remove the coil from the block by slipping off the layer of aluminum foil. When the coil has been freed from the block, peel the foil from the inside of the coil and strip off any excess dope that may be hanging from the edge of the coil. Finally, dip the coil directly in the dope and blot the excess with a piece of facial tissue. As soon as the coil is dry, mount it (Fig. 1).

The dust cover (Fig. 1A) is also made of tin plate and is of two-piece construction. The sides and bottom are made from a single strip, 1 1/4 in. wide, and formed as shown. The width of the bottom will vary depending on the magnet used, but will be about 3/8 in. Lining the inside of the cover with a thin blotting paper will decrease resonance. Solder the end piece to the sides and bottom from the inside. With a small file, remove any solder that oozes through.

Make the bearing blocks and support blocks from a rubber band, making them oversize to begin with and then trimming them flush with the top of the clips after the shaft and leads have been inserted. (Spread the clips slightly before insertion of these parts, re-applying pressure afterwards by compressing them with a pair of forceps.) Insert the shaft assembly by spreading apart the portion of the rubber block extending above the clip and then pushing the shaft down to a point just below the top edge of the clip. Swing the shaft around so that the stylus is perpendicular to the base plate, then squeeze the clips with a pair of forceps just enough so that the shaft will not slip out of the blocks. Finally, trim off the blocks with a razor blade. Remember, the compliance of the stylus-coil mechanism is a function of the block pressure.

Now place the base-plate assembly on the magnet and inspect the air gap between the pole pieces and the flux block. It should be between 3/14 in. and 1/16 in. If the coil is a little thicker than it should ideally be, enlarge the gap by filing down the sides of the block. Be sure to clean away any filings so they will not plug the air gap. When the gap has been adjusted,

Paint the dust cover and attach transformer leads, and the moving-coil pickup is completed.

Building the Tone Arm. Cut a piece of Reynolds "Do-It-Yourself" aluminum channel 10 1/4 in. long and make a notch in one end (see Fig. 5). If the magnet from a Heppner Power Latch is used, this notch should be 1/4 in. wide by 1 1/4 in. long. If a magnet of a different size is used, the notch should be layed out to provide approximately 1/16 in. clearance between the channel and the pickup assembly. Drill two 3/32-in. holes 8 7/32 in. from the notched end of the channel and at a point about 3/16 in. from the opposite end drill a 7/64-in. hole. Then, 1 3/4 in. from the notched end lay out and remove a 16° sector and bend the channel as shown in Fig. 5. Finally, drill two 7/64-in. holes on either side of the cut. (The attachment of the arm lift will stabilize the joint.)

Lay out, cut out, and form the arm lift from a piece of aluminum or copper sheet. Dimensions for it are not critical, except that it should extend out over the channel far enough to permit easy handling of the arm. Secure it to the channel with two 3-48 screws. Next, cement

two 1/8-in. ball bearings into the pair of holes previously drilled in the sides of the arm. In the event that the ball bearings available are larger or smaller than the size suggested, simply alter the size of the holes drilled for the vertical pivots to allow the bearings to be recessed to about 1/3 of their diameter.

Make the counterbalance spring adjusting stud from a 3-48 x 3/4 in. machine screw by cutting off the head. Flatten the cut end of the screw and drill a hole with a No. 67 drill. One end of the counterbalance spring will be attached here.

Remove the wheel from a Colson, double ball-bearing, plate-type caster. From a length of 1/8-in. bronze welding rod cut a piece 1/4 in. long and drill a No. 67 hole close to one end. Then solder this pin to the body of the caster at the rear as shown in Fig. 5. The other end of the counterbalance spring anchors here. Using a 1/8-in. drill, carefully dimple the ends of two 6-32 machine screws and then insert them in the axle holes of the caster body using a flat washer and nut on either side. The over-size holes provide for alignment of the arm. Turn in the pair of screws so that the arm is held securely, but at the same time pivots freely on its vertical axis. Form the arm rest from two pieces of 1/8-in. bronze rod. Make the rest high enough to support the arm approximately parallel to the motor board and solder it to the base plate of the caster.

The counterbalance spring must be fairly soft to provide the arm with the correct degree of vertical sensitivity. A soft tension spring of 1 5/16 in. dia. and cut to a length of about 1/2 in. will provide the proper action and degree of adjustment. Twist a hex nut down on the counterbalance spring stud, insert the stud in the arm, and fit a second nut on top.

Hook the spring into the holes provided in the bottom stud and adjusting stud. Do not bother to adjust the spring tension until assembly has been completed.


The pickup is isolated from the aluminum channel with a cork insulator. Although the insulator is 1/4 in. thick, it can be made from two layers of 1/8-in. cork sheet available at most auto supply stores. First cut the pieces to fit the inside of the channel and then cut the slot just wide enough to hold the pickup snugly. Glue the two layers together and then glue them to the inside of the channel with airplane cement.

Final Assembly. Slide the pickup assembly into the cork insulator and position the upper edge of the magnet 1/8 in. above the insulator. Turn the arm over and secure the pickup with 4 drops of airplane cement. Cut two 15-in. lengths of Litz Wire (5x44), and twist them together. Strip and tin one end of the twisted leads and slip them between the lead support blocks. Squeeze the clips together and trim off

the excess rubber band with a razor blade. Splice the Litz-wire leads and coil leads together and carefully solder the joints. From a spool of plastic electrician's tape, cut off six pieces 3/16 x 1/2 in. Use these strips to hold the lead in place along the inside of the channel. Allow the twisted leads to drop down from the arm at a point about 1/4 in. in front of the counterbalance spring assembly.

Carefully stretch the lead down and cut it 1 in. below the base plate of the caster. Now strip and tin this end and check the lead, soldered connections and coil for continuity. If the circuit is correct, slip on the dust cover and make preliminary adjustment of the counterbalance spring tension. Tighten the spring until the stylus pressure is approximately 2 grams. This unit is exceedingly sensitive and it may be possible to decrease the stylus pressure a little more after the arm has been mounted on the motor board.


A high-fidelity output transformer is used to match the low internal resistance of the moving coil to the input of the first preamplifier tube grid. Twist the leads of the primary and attach a phono jack. The primary side should be attached to the preamplifier input with a well-shielded cable, such as RG-59U. With an ohmmeter (or using the manufacturer's color code) select the pair of secondary with the lowest impedance, twist them together and install a second phono jack. The remaining leads will not be used and may be clipped off. The remainder of the lead between the arm and the matching transformer is made from stranded hookup wire, but is not prepared until the exact

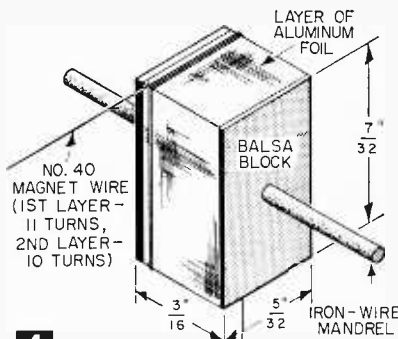

4 SET-UP FOR WINDING MOVING COIL

MATERIALS LIST—TONE ARM AND PICKUP

No. Req.	Description
1	caster (Colson, double ball bearing, plate type, w/2" wheel, Elyria, Ohio)
2	ball bearings (approx. 1/8")
1	lgth 1/2" x 1/4" aluminum channel (Reynolds "Do-It-Yourself")
1	tin can
1	soft spring (1/2 x 1 5/16")
1	bronze welding rod (1/8")
1	high-fidelity audio output transformer (Stancor A-8072, or equivalent)
1	1-mil stylus (GE 4G-01D)
1	No. 19 rubber band
1	magnetic power latch (Heppner Sales Company, Round Lake, Ill.)
	6-32 machine screws and nuts; 3-48 machine screws and nuts; 3/16" stove bolts and nuts; 3/16" flat washers; sheet cork (1/8" or 1/4"); No. 40 magnet wire; Litz wire (5 x 44); 12-strand picture wire; airplane cement; dampening jelly (silicone base type, or Black & Decker Lubricant, Cat. No. U-2194); plastic electricians tape; stranded hookup wire; enamel (for finishing); airplane dope (any color); rosin core solder.

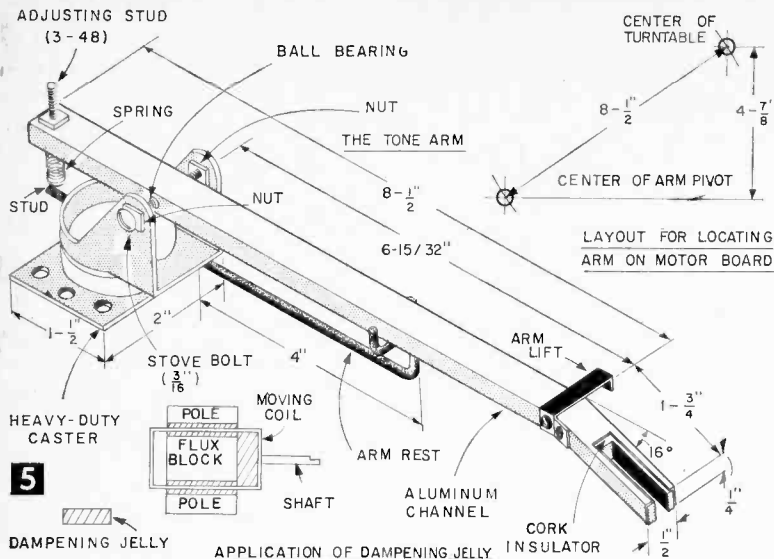

pearance, dictate placing the transformer at a reasonable distance from the pickup. In our high-fidelity installation, the matching transformer is located on the bottom shelf of the cabinet, concealed behind a row of records. Signal loss is negligible if the transformer is placed as much as three feet away, so this allows considerable flexibility in the arrangement of individual units.

After a suitable location for the matching transformer has been determined, make a pair of twisted leads from braided hook-up wire of sufficient length to reach

location for the matching transformer has been selected.

Mounting and Adjustment. The layout for locating the arm is shown in Fig. 5A. Although the caster plate is stamped with six holes, only three stove bolts are required to mount the unit securely to the motor board. Three-sixteenths in. bolts fit the plate nicely; their length will be dependent on the thickness of the motor board and the height to which the caster base will have to be shimmed up. Vertical and leveling adjustment are provided for by a combination of $\frac{3}{16}$ -in. flat washers and a $\frac{1}{8}$ -in. cork shim. Enough flat washers should be slipped over the portion of the stove bolts between the plate and the motor board to raise the arm high enough so that the jewel tip will ride perpendicular to the record surface. Level the arm by tightening the mounting bolts and compressing the cork shim.

Locate the arm and drill the mounting bolt holes in the motor board, but do not actually mount the unit until it has been given a preliminary test. Also bore a $\frac{3}{8}$ -in. hole in the motor board directly under the center of the arm pivot; the arm lead will pass through this opening. Next, cut two 5-in. lengths of stranded hookup wire, strip and tin both ends, and twist them together. Solder a phono plug to one end and push the other up through the center of the cork shim. Pull the wire through the shim about $\frac{1}{2}$ in. and bend at a right angle. This will prevent the lead from pulling out and will protect the Litz-wire lead from any strain. Solder the Litz-wire lead to the short section of hook-up wire and check continuity with an ohmmeter.

To minimize resistance losses, locate the matching transformer as close as possible to the source (the moving coil). Other considerations, such as isolation from magnetic fields and ap-

pearance, dictate placing the transformer at a reasonable distance from the pickup. In our high-fidelity installation, the matching transformer is located on the bottom shelf of the cabinet, concealed behind a row of records. Signal loss is negligible if the transformer is placed as much as three feet away, so this allows considerable flexibility in the arrangement of individual units.

After a suitable location for the matching transformer has been determined, make a pair of twisted leads from braided hook-up wire of sufficient length to reach from the transformer to the under side of the motor board. Splice one end of the lead to the secondary of the transformer and secure a phono plug to the other. Then, attach the primary of the transformer to the preamplifier with shielded cable.

A light silicone-base jelly is the most satisfactory dampening agent, but, unfortunately, this material is rather difficult to obtain through ordinary sources of supply. Two alternatives are available: 1) salvage the jelly from a discarded pickup; 2) use a substitute material. Black and Decker lubricant (Catalog No. U-2194) works satisfactorily, but it does evaporate slowly and must be reapplied from time to time.

Turn the arm over and remove the dust cover. Using a fine sewing needle apply the jelly sparingly to the areas indicated in Fig. 5B. Now connect the arm to the lead from the transformer and turn on the amplifier. After it has warmed up, make a preliminary test of the pickup by carefully running a finger across the stylus. If the quantity of dampening jelly applied is optimum, a rather deep rumble will be heard from the speaker. If the sound is highly resonant, more jelly will have to be added. If gain is poor, chances are that too much jelly has been applied. Use the sewing needle to remove excess jelly a little at a time and make the finger test frequently.

Playing a disc, of course, is the real test. In general, too little dampening jelly will cause resonance and permit excessive needle talk; too much will attenuate the highs and reduce gain. When preliminary tests indicate that the pickup is functioning correctly, replace the dust cover and bolt the arm to the motor board. Check to see if the arm is level by rotating it about 30° away from the turntable. If the arm remains in position, it is level; if it swings toward the turntable, tighten the bolt on the left; if it turns

away from the turntable, screw down the bolts on the right. Check the stylus pressure with a gauge and adjust to about two grams pressure. A coat or two of enamel to suit your own taste completes the unit.

Operation of the Unit. The design of a moving-coil pickup is simplicity itself. The modulations of the record grooves cause the stylus to swing laterally. This motion is imparted to the coil through the shaft, to which the jewel is cemented. The rubber blocks function both as a fulcrum and a restoring mechanism. The actual force in dynes required to deflect the stylus was not measured by the author, but compliance is high as indicated by the excellent low-frequency response of the pickup. It should be noted that the rubber blocks also provide sufficient vertical compliance to overcome much of the "pinch" effect.

The moving coil generates a feeble current and because the internal resistance of the source is so low a reversed audio output transformer must be used to match the coil to the high resistance of the preamplifier input. To prevent the loss of high- and low-audio frequencies, a good quality high-fidelity output transformer is essential for this application. If you can obtain an input transformer used with some commercial low-level pickups, so much the better, as some savings can be realized.

Tests indicate that this pickup will track satisfactorily with a stylus pressure of 2 grams. This low tracking force will significantly increase the life of records. Best undistorted output appears to be obtained when the unit feeds into 22,000 ohm load.

The placement of the matching transformer



and lead dress are critical as this type of pickup is quite sensitive to external sources of hum. The transformer may be located either above or below the motor board but must be far enough away to isolate it from the magnetic field of the phono motor. Hum pickup is further minimized by twisting together all leads. Repositioning the transformer and making slight changes in lead dress may make considerable difference where hum is a problem.

That portion of the lead between the pickup and tone-arm base must be very flexible so that there is no interference with the radial movement of the arm. Because the tracking pressure is so low, the arm does not readily overcome even slight lateral stresses—such as may be caused by the flexing of the leads—without inducing distortion. Litz wire was selected because it is very soft and therefore ideal for this purpose.

The mechanics of the tone arm are virtually self-evident. The two primary design considerations are: 1) freedom of movement; and 2) proper tracking. Smooth horizontal and vertical action is obtained by the use of ball-bearing suspension. Perfect tracking is more difficult to come by and precise setups can involve considerable mathematical computation of a high order. Theoretically, the arm should be tangential to the record groove at all times. Obviously, this is impossible since the arm swings radially from a fixed point on the motor board. The best that can be done is to mount the arm in a more or less compromise position. In addition, it has been determined that a slight overhand (over the center of the record) will significantly reduce tracking error.

Syringe Is Handy Service Tool

• A veterinarian's syringe or doctor's hypodermic needle makes an ideal service tool for injecting cleaning fluid into the noisy control of a radio or TV set, since its tiny needle point can reach into the smallest opening with ease and, thus, there's no need to take the control apart. Filled with grease, a hypo needle or syringe makes a handy miniature "grease-gun," too. If your local veterinarian or druggist can't supply you with one of the syringes, perhaps you can obtain one from your dentist or doctor.—JOHN A. COMSTOCK.

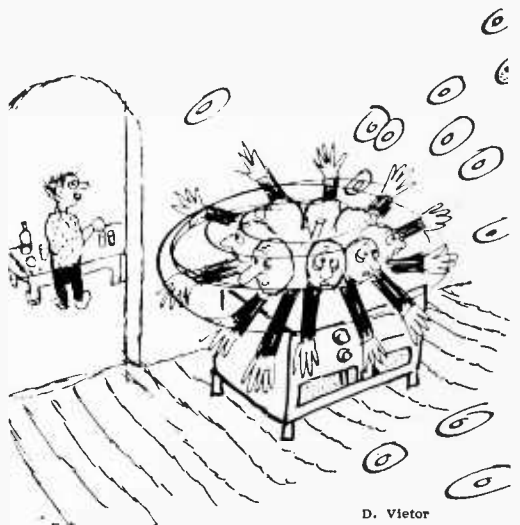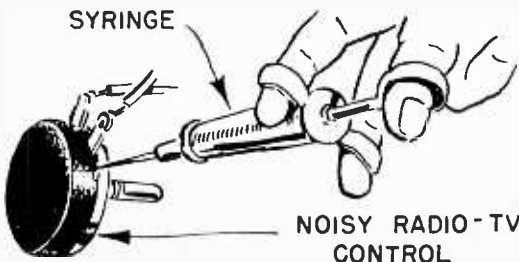

"Put on a record, Joe—but let me warn you—our new five-way player is a little tricky to handle—"

A Really Portable Portable Phonograph


By HOMER L. DAVIDSON



ANYTIME you find yourself far from an ac outlet, this little portable phonograph will solve your music problems. Small, thin, light and rugged, it operates on battery power (two of them, wired in parallel for harder and longer service). The small transistorized amplifier is constructed upon a flat, printed circuit board.

Begin construction by taking the printed circuit diagram (Fig. 2) and tracing it directly upon the copper side of the printed circuit board (see Materials List). Use carbon paper. Then apply resist tape to the lines, pressing it snugly to the copper side with a knife. Draw in the small dot circles with liquid resist or use resist tape circles for them.


When the circuit has been completely laid out on the board, pour enough liquid etchant into a flat dish or tray to completely cover the board when it is immersed. Agitate the etching solution by rocking it back and forth to quicken the etching process. It will take approximately 45 minutes to completely etch the board. When etching has been completed, wash the board off with tap water and wash the tray. (Pour the solution back into its container; it can be used

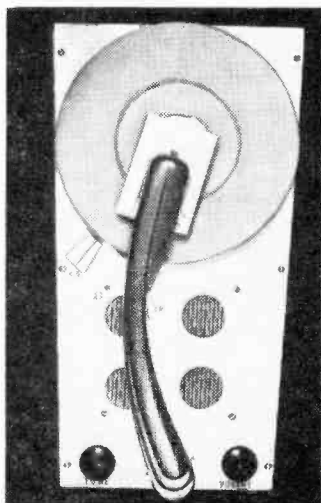

Pick it up and walk right out of the house with it, you'll still hear music with this portable phonograph that's really portable. Inset shows arm resting on keeper block.

again.) Remove tape and resist with a penknife or other sharp blade and drill through circles with a small bit ($\frac{1}{32}$ in. for resistor and capacitor leads, $\frac{3}{32}$ in. for others).

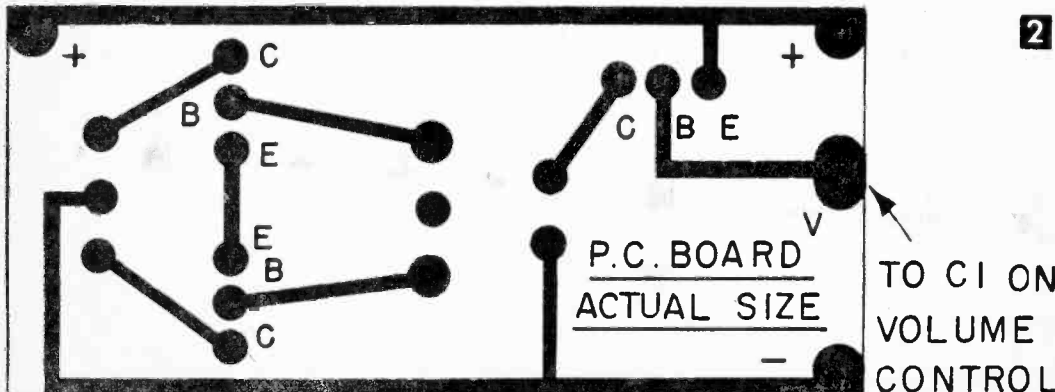
The amplifier has two matched transistors in its output circuit, one transistor as a driver. A 500K-potentiometer (R1) is used in the input circuit as a tone control and to cut down needle




scratch on worn or dirty records (see Fig. 3). A volume control (R2) varies the output from the crystal cartridge to the base circuit of the first transistor. A push-pull interstage transformer couples the driver to the input of the two matched output transistors. The first transistor can be any transistor of audio quality (such as the CK722 or 2N107). A pair of matched transistors drives the small 4-in. PM speaker for plenty of volume, and the amplifier itself pulls only about 5 ma of current under normal operating conditions.

Mount all components except the transistors and solder them into place; mount the transistors last (see Fig. 4). Test board and install in cabinet when that unit is completed (see Fig. 5). Be sure when wiring in the phono motor that it runs clockwise. If it doesn't, reverse the connections at the motor.


Cabinet. The top panel mounting board is made from Masonite (see Materials List) finished with two coats of enamel. Cut and drill all holes before painting (see Figs. 5 and 6). Plastic grille cloth covers the speaker opening and due to its supporting strength no hardware cloth or screen is needed behind it. The small phonograph is mounted on the top panel. The cabinet is narrower at one end than the other, making it appear much thinner and more compact. After pieces have been nailed and glued together, apply two finish coats of paint, your choice of color. If you spray-paint and use sand-blasted plywood, apply a coat of red. Since the red paint hits only the high spots on the sand-blasted plywood, the aluminum paint lies deep in the grooves, giving a leathery looking finish.

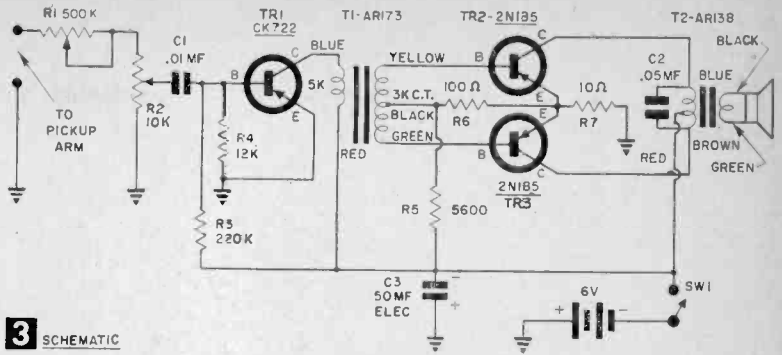

3 SCHEMATIC

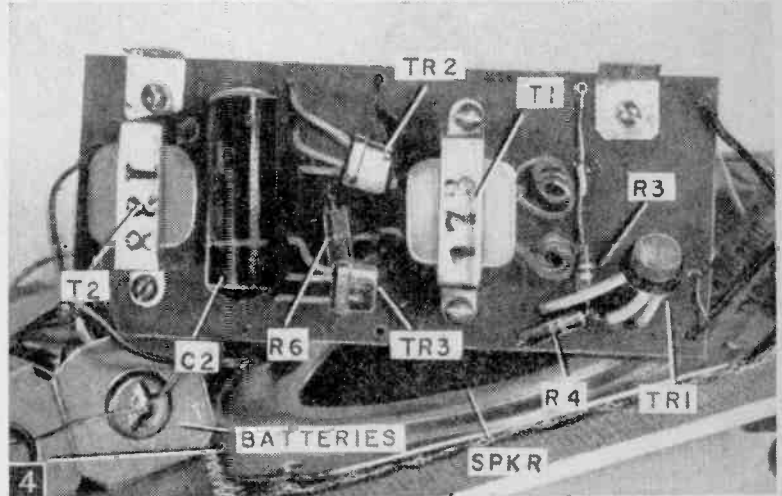

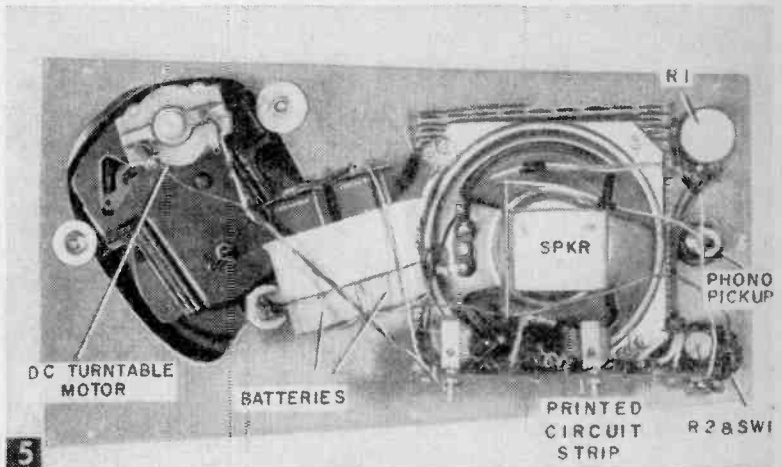Top side of printed-circuit board assembly, components in place.



Bottom view of completed assembly.


Finally, shape a small block of wood for the arm keeper as shown in Fig. 6. The pickup arm lies in the groove of this block, the top lid fastens down on it. Glue a piece of sponge rubber in the top of the lid so that the arm will rest firmly when the unit is carried. A small hole the size of the phono turntable rod support will

MATERIALS LIST—PORTABLE PHONOGRAPH


Desig.	Description
R1	500K potentiometer
R2	10K potentiometer with switch
R3	220K fixed resistor
R4	12K fixed resistor
R5	5600-ohm fixed resistor
R6	100-ohm fixed resistor
R7	10-ohm fixed resistor
C1	.01 capacitor, paper, 200v
C2	.05 capacitor, paper, 200v
C3	50 mfd. electrolytic capacitor, 25v
T1	Interstage transformer 5000-ohm primary, 2000-ohm secondary; Argonne AR173
T2	Output transformer, 1000-ohm impedance, 3.2-ohm secondary; Argonne AR138
TR1	CK722 (see text)
TR2, TR3	2N185 (Texas Instrument)
	Pickup arm (Lafayette PK-89)
	Turntable motor 6 volt 16, 33 $\frac{1}{3}$, 45 RPM (Lafayette ML-9)
	2 Batteries (Eveready 724 or equivalent)

Printed Circuit Materials

No. Req.	Description
1 pt	PE-5 liquid etchant
1	2 x 4 $\frac{1}{2}$ " XXXP copper laminated board
1	PRLT ball point pen
1	roll tape resist
	All material available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

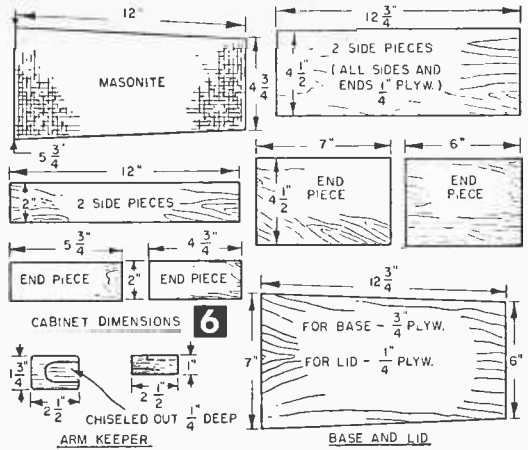

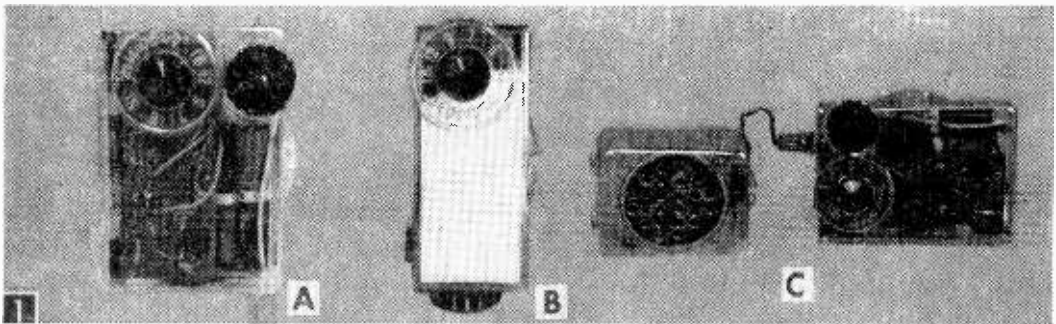prevent the keeper from side travel. Two small clip-on hinges, like those on a suitcase, hold the lid to the bottom of the cabinet. These can be purchased at the local hardware store.



Economy Versaflex (A), Tiny Model (B) and Loudspeaker Model (C), three options by which to make the versatile Versaflex.

The Versaflex

Take your choice of battery economy model, extra tiny model, or loudspeaker drive economy model, this is still a sensitive reflex receiver


By FORREST H. FRANTZ, SR.

WANT a small radio, say 1 x 1 $\frac{3}{16}$ x 2 $\frac{7}{8}$ inches? Or can you tolerate a radio as large as 1 x 2 x 2 $\frac{7}{8}$ inches? Okay, either way, try the *Versaflex*. This little two-transistor receiver will pick up stations without an external antenna lead of any kind within 10 miles of a station. You can build it for roughly \$10, including batteries and headphone, and with a slight change in the Economy Model—which uses ordinary penlite cells—you can drive a loudspeaker on local radio stations.


How It Works. The *Versaflex* is a reflex receiver. That is, one of its transistors (T1 in Fig. 2) does double duty as an RF and AF amplifier.

The feedback arrangement through gimmick capacitor C2 (see Materials List) makes the set operate reasonably close to the oscillation level, and it also contributes to increased sensitivity. Other features which contribute to the sensitivity of the *Versaflex* are transformer coupling to the output transistor stage (T2), the use of entertainment- rather than experimenter-grade transistors, a high-Q antenna coil (L1), and a reasonably high battery voltage.

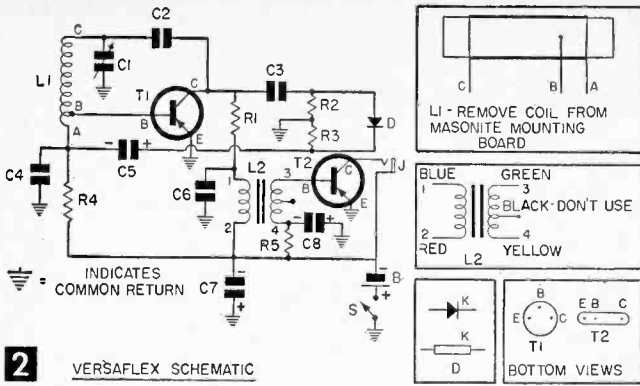The antenna coil (L1), which is matched to transistor T1, picks up the incoming RF signal; L1-C1 form the tuning combination. Transistor T1 amplifies the RF signal and feeds it through



2 VERSAFLEX SCHEMATIC

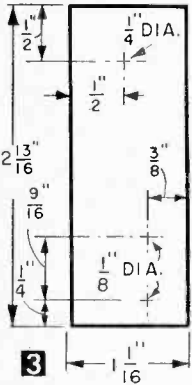

3 PERFORATED BAKELITE CHASSIS BOARD (FRONT VIEW)

capacitor C3 to diode D. Capacitor C3 blocks the collector operating voltage of T1 from diode D, which rectifies the signal and feeds the audio portion through C5 to the junction of R4, C4 and L1; C4 provides an RF return to ground. The signal at this junction is therefore pure audio, and it flows through L1 to the base of T1 without disturbing the RF amplifier operation of T1. Amplified, it appears across R1 and the primary of L2. Since the primary impedance of L2 is about 10 times the resistance of R1, most of the audio signal


is transferred to the secondary of L2. T2 amplifies this signal and it is transferred to the output jack.

The power consumption of the Versaflex is very small. Your set will draw between one and three milliamperes. The power consumption is therefore between 6 and 18 milliwatts when you're using a 6-volt battery.

Construction. The Versaflex circuit is the same for all three options: (1) Economy Model; (2) Tiny Model; (3) Loudspeaker Model. The parts values are the same for all three options with these exceptions: Options 1 and 3 use penlite cells, option 2

uses a miniature transistor battery; the value of R5 is 330K in options 1 and 2, but R5 is 220K for option 3. This increases the power consumption of the set slightly for loudspeaker operation.

Begin construction by cutting and drilling the chassis board as shown in Fig. 3. Cut off the black lead on transformer L2; cut the other leads to a length of 1½ in. and strip the ends. (Be careful not to pull the leads out when you do this.) Mount tuning capacitor C1 and transformer L2 on the chassis board, bending the mounting lugs of L2 on the bottom side of the chassis board. Next, mount transistor T1 by soldering the emitter lead to the ground lug on C1. This lead must be very short and T1 must be placed close to the frame of C1. You'll have to be very careful not to get the transistor too hot. As a precaution, grasp the emitter lead with a pair of needle-nose pliers between the body of the transistor and the lug of C1 while soldering.

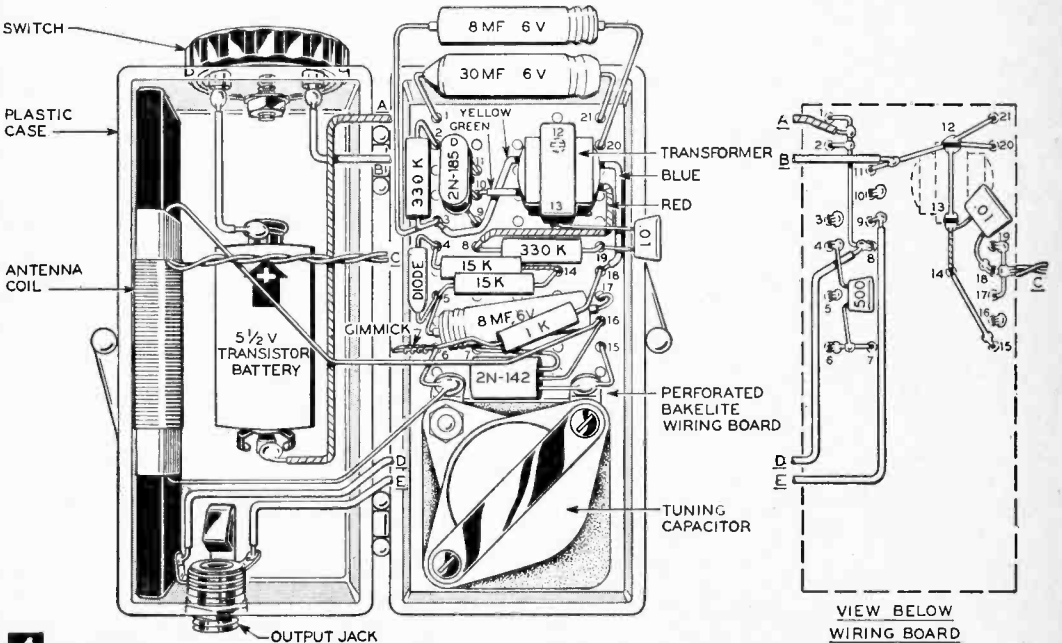


4 PICTORIAL

Next, mount C7, R5, R4, R3, R2, D, C5, R1, C8, and T2 in the order listed. The parts are mounted by pushing the pigtail leads through the perforations in the chassis board. Be sure to get all capacitors and resistors as close to the board as possible or you may have trouble getting them all in the set or in closing the case of the completed radio. The connections are made by soldering leads together on the bottom (front) of the chassis board and clipping them close to the board. Again, be careful not to damage the transistors while you're soldering. When you've finished making these connections, recheck to be sure that you haven't made any wiring mistakes. Check capacitor and diode polarities; be sure your connections to the transistors are correct. If you have any shorts between leads that shouldn't be connected, bend leads till they don't touch.

Mount and connect C3, C4, and C6. Make gimmick capacitor C2 by loosely twisting two 2-in. pieces of #28 insulated (enameled or cloth-covered) wire together. Use one set of ends to connect into the circuit; be sure the other set of ends do not touch. Leave the gimmick sticking out where you can get to it to adjust it according to instructions which will be given later. Connect 3½-in. long leads for the switch, battery, and phone jack. You can cut these to length when you put the set in the case. Figure 4 shows front and back of the wired chassis board with the switch, battery and phone jack leads.

Next, make pilot holes in the plastic case with a heated ice pick. Ream the holes to size with a taper reamer. The hole layout for the radio case of option 1 and 3 is shown in Fig. 5A. The case for option 2 is shown in Fig. 5B. The speaker case for option 3 is shown in Fig. 5C.

Now cut off the two middle lugs on switch S. Two of the switch's three On positions are not used. Mount the switch and the phone jack J in the case. Place the assembled chassis board, antenna coil L, and battery B in the case. Cut leads to switch, battery, and jack to length. Push L1 leads out of the way and close the case. If it won't close, it may be necessary to slightly gouge out the inside of the case with a hot soldering iron. I was a little reckless with space on the original model. Although the Economy Model (option 1) fitted nicely, I had to gouge out the inside of the case for the Tiny

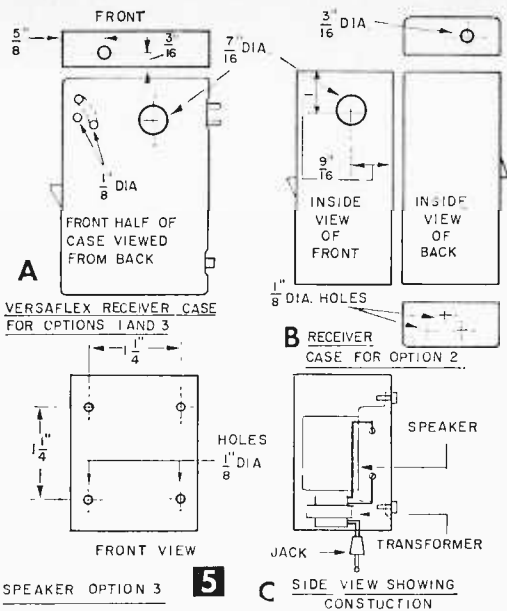

Model. If you have to resort to this, cut out a piece of a filing card and fasten it to the front of case with Carter's rubber cement as I did to improve the set's appearance. The edge of the card serves as a tuning index.

When you're sure everything fits, connect the battery, switch, phone jack, and antenna coil to the batteries. Dress the antenna coil leads so they won't be damaged or shorted to other components when the case is closed. Be careful not to get your soldering iron against the plastic case while you're doing this final soldering. Insulate battery connections with transparent tape. Fasten the dial to the tuning capacitor with the knurled screw, and you're

ready to try out your Versaflex.

Final Tune-Up. Turn the set on and tune C1 till you get a station or a squeal. If you can get either of these results, you're in business. If you get a squeal, untwist part of the gimmick C2 till the squeal just disappears. Remove your hand from the gimmick to check for absence of the squeal. When the squeal no longer exists at this point, try the rest of the tuning dial. If you don't hear any squeals, close the case and enjoy the set. To control volume, rotate the set away



"It hasn't uttered a sound for three days—and neither has he."

D. Vietor

MATERIALS LIST—VERSAFLEX

Desig.	Description
R1	1K. 1/2 watt, 10%
R2, R3	15K. 1/2 watt, 10%
R4, R5	330K. 1/2 watt, 10%
C1	365 mmfd tuning capacitor & knob (Lafayette MS-445)
C3	500 mmfd, 75 v. capacitor (Lafayette C-608)
C4, C6	.01 mfd, 75 v capacitor (Lafayette C-612)
C5, C8	8 mfd, 6 v electrolytic capacitor (Lafayette P6-8)
C7	30 mfd, 6 v electrolytic capacitor (Lafayette CF-104)
C2	Gimmick—2 pieces of insulated #28 wire about 1' long twisted together
L1	antenna coil (Miller 2004)
L2	subminiature driver transformer 10K to 2K (Lafayette TR 98)
T1	RF-1st audio transistor (RCA 2N412)
T2	audio output transistor (Texas Instruments 2N185)
D	diode detector (Raytheon 1N66)
J	output jack and earphone (Lafayette MS-368)
S	Switch (Lafayette SP-88)
	Perforated Bakelite Board (Lafayette MS-304)
Option 1, Economy Model	
B	4 penlite cells connected in series (RCA VS0-74, Burgess #7, or Eveready 912)
I	plastic case (Lafayette MS-158)
Option 2, Tiny Model	
B	5.5 volt Battery (RCA VS310)
I	plastic case (Lafayette MS-157)
Option 3, Loudspeaker Model	
SK, L3	loudspeaker and output transformer (Lafayette SK-62)
I	plastic loudspeaker case (Lafayette MS-156)
	All components for the Versaflex are available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, New York

from the direction of maximum pick-up or detune C1 slightly.

If the set doesn't squeal initially, but picks up stations, twist gimmick C2 tighter. This will increase the sensitivity since the RF feedback capacity of transistor T1 is being increased. When you hit the squeal point, you'll have to decrease the gimmick capacity slightly to eliminate it.

If you don't pick up a station when you turn the set on, move the phone plug in and out of the jack. You should hear clicks when you do this. The absence of clicks may mean a dead battery or a bad connection.

The antenna axis must be horizontal for best pick-up, the set is very directional. Assuming you're OK on this score, hold a metal object such as a screwdriver or pen knife in contact with your fingers and touch the junction of C4, R4, C5, and L1 with the tip. If you hear a hum, the entire audio portion of the radio is okay. Look for trouble in the L1-C1 combination or in the connection of C6. A transistor with low frequency cut-off could also be the cause. On the other hand, if you don't hear a hum, look for trouble in the audio amplifier portion of the set. This includes both transistors.

You'll usually find that any difficulties you may have are due to errors in wiring, short circuits, or poor connections.

If you're some distance from radio stations, you can make the Versaflex pick up stations for you by connecting a 2- or 3-foot lead to the side of the tuning capacitor which isn't grounded. But till you're very sure you need this assist,

don't add it. I've picked up stations about 15 miles away without resorting to it.


Because the Versaflex is small, it would make an ideal wrist watch radio. A wrist watch band may be attached to the Tiny Model case (option 2) by passing the band through slits provided in the side of the case near the back. The slits can be made with a heated ice pick. Use a cloth band. There is no noticeable decrease in Versaflex sensitivity when the receiver is held near the body. The sensitivity, of course, decreases if the antenna is tilted out of the horizontal plane. Since the receiver has a phone jack, the cord may be left connected and tucked inside your coat sleeve with the headphone in your inside coat pocket when it's not in use. Or the headphone and cord may be carried in your pocket when the receiver isn't in use and plugged in with the cord passing outside your clothes for use.

Either the Tiny or the Economy Versaflex will fit nicely into milady's purse. The Versaflex could be built into a case which doubles as a compact or coin purse. There's plenty of room for originality here.

The Loudspeaker Model (option 3) can be built with speaker and receiver in a single case. Provide any of the Versaflex options with a clip to fasten on the handle bars, and you've got a bicycle radio. Does anyone wonder why I named this set the "Versaflex"?

Aluminum Windows Serve as Antennas

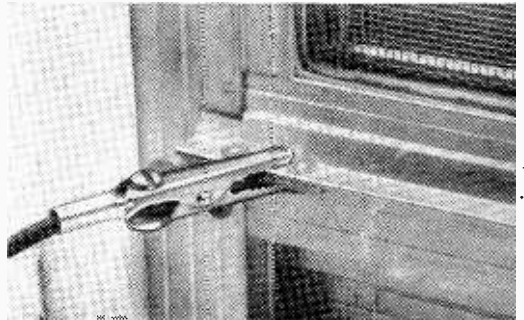• An aluminum combination window makes a good antenna for boosting the range of broadcast receivers, table-top radios and short-wave receivers, since the metal covers a fairly large area. Just clip a length of wire to the aluminum frame (see photo) and connect the other end to the antenna terminal on the radio, using alligator clips. If you prefer a permanent connec-



tion, fasten the end of the wire lead under one of the screwheads on the window frame. If your radio is an ac-dc table model, or any other type which works off the power lines but uses no power transformer or isolation transformer, connect a .01 mfd 600-volt fixed capacitor between the antenna terminal and the aluminum window frame to isolate the frame from the radio and prevent shocks.—ARTHUR TRAUFFER.



1 A handful of circuit components, but an earful of fun, this handset receiver can be constructed in one hour.

A ONE-EVENING project, this headphone-handset (Fig. 1) employs only a handful of parts, but obtains surprising results in pulling in local stations. A modified, high-gain antenna coil is used as the tuning circuit, the modification consisting of 35 turns of No. 28 enameled wire wound and taped in place over the coil's original winding.

The antenna coil (and thus the receiver itself) is tuned by varying the inductance of the high-gain coil by moving its ferrite slug up and down within it. A 400 mmf padder capacitor is adjusted to separate strong local stations.



The broadcast signal is then rectified by an 1N64 crystal (see the schematic, Fig. 2), coupled through a 25 mfd electrolytic capacitor to the base of a CK722 transistor (the base resistor is 220,000 ohms), and then fed directly from the transistor's collector to the winding of the earphone.

Headphone- Handset Receiver


By HOMER L. DAVIDSON

To construct, first cut a piece of Masonite (or plywood) to the same circle size as the phone. Cut it with an extended piece (see Fig. 3) for a handle and drill three small holes into the back of the phone and the Masonite, securing the phone in place with two $\frac{3}{32}$ bolts and nuts (see Fig. 4), and fastening the tuning coil's mounting strap in place with one of these mounting bolts (see Fig. 3). The 15-v cell that provides power for this unit is strapped in place on the handle by means of a scrap piece of light-weight metal bolted through the Masonite.

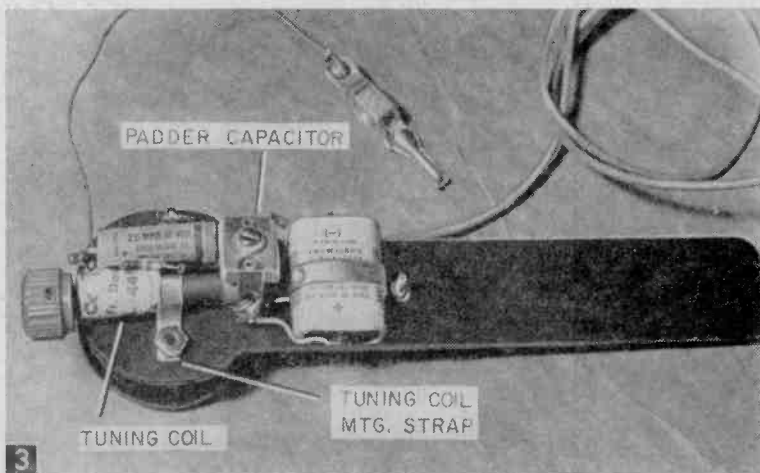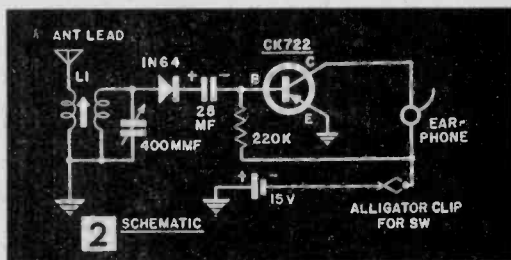Mount the transistor inside the earphone, and solder leads directly into the circuit, keeping them as short as possible. Mount the 400



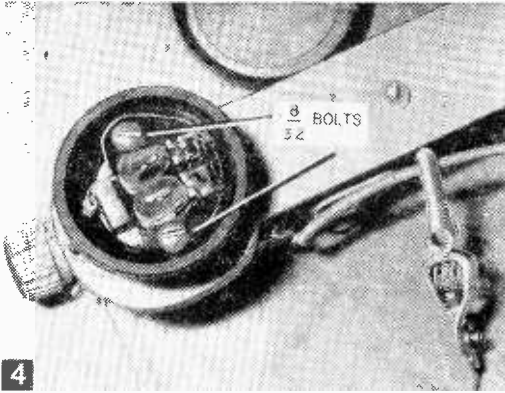3 Pictorial view of handset circuit, inside of phone.




Pictorial view of handset circuit, outside.

MATERIALS LIST—HEADPHONE-HANDSET RECEIVER	
No. Req'd.	Description
1	ferrite antenna coil (L1; see text for modification)
1	400 mmf capacitor, padder type
1	25 mfd. 50v capacitor
1	1N64 fixed crystal
1	220,000 ohm. 1/2-watt resistor
1	15 v Burgess hearing aid battery
1	CK722 Raytheon transistor
1	single unit earphone (from scrap box)
1	miniature alligator clip


mmf padder capacitor on the antenna coil lugs as shown in Fig. 3. Be sure to observe polarity on the small hearing aid battery when connecting it into the circuit or you may damage the transistor. To turn the receiver On, simply clip the alligator clip to the minus side of the battery.

Machine to Play ZIM

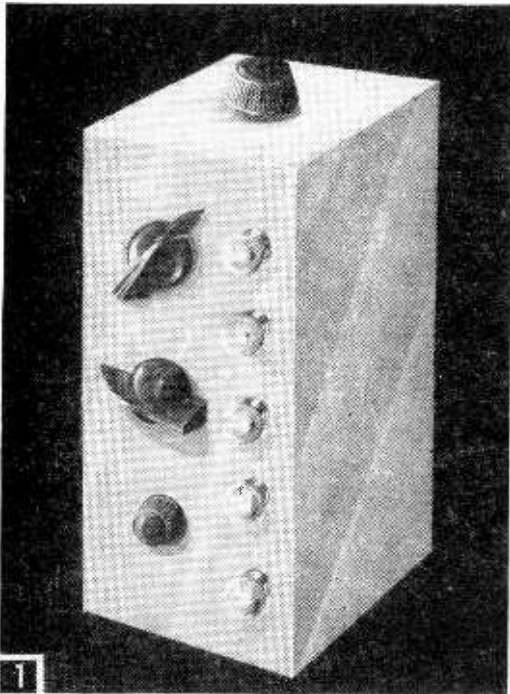

indicating its move by the use of bulbs. For example, if bulb No. 1 lights, the machine has taken one stick; bulb two, two sticks, etc.

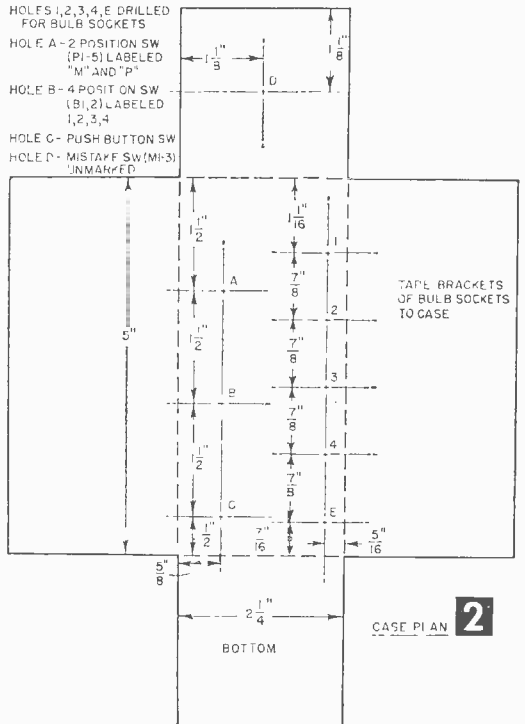Operation. When you want to start the game:
1) Turn the two-position switch to the "P"



THIS *Zim* machine is a new version of an old game. In the original game, two players alternately took one to four sticks from a pile of 21 sticks. The player who forced his opponent to take the last stick won the game. The *Zim* machine takes the place of one of the players,

CASE PLAN **2**

(person), or second position. 2) Turn the four-position switch to the position indicating the number of sticks (1-4) you take from the pile of 21 sticks. 3) Press the push-button switch. 4) A bulb will light indicating the number of sticks the machine wishes to take (take these sticks from the pile). 5) Continue steps 2, 3, and 4 to the end of the game.

When you want the machine to start the game: 1) Take the four sticks of the machine's first move from the pile. 2) Turn the two-position switch to the "M" (machine), or first position. 3) Follow steps 2, 3, 4, and 5 of preceding instructions.


If the *extra bulb* lights, the two-position switch should be in the "M" position and kept there until the bulb goes off. Turn it to the "P" position the turn *after* the bulb goes off.

So that you may win once in a while, the machine has a Mistake Switch built into it with an unmarked knob. Every so often this knob should be turned to change the mistake the machine

will make as a reply to a certain move. However, any errors made by the machine will be corrected unless you immediately take advantage of them. The elimination of the Mistake Switch makes the machine impossible to beat when *you* start the game. (To eliminate the switch, connect position two of P2 directly to bulb four, position two of P3 directly to bulb three, and position two of P4 directly to bulb two.)

Construction. Begin by drilling holes in the front section (containing the two ends and the front) of the chassis (see Fig. 2). Then remove the adjustable stop on the Mistake Switch (6 pos., 3 poles per pos.), and install all switches. Cut brackets on sockets even with the sockets themselves. Next, wire the circuit, leaving ample lengths of wire connected to the bulb sockets. Then, placing them under their respective openings, tape or solder brackets to the rear half of the chassis as indicated in Fig. 2. If you use tape, apply tape to the complete group of sockets as well as to each individually.—B. DICKMAN.

3 SCHEMATIC

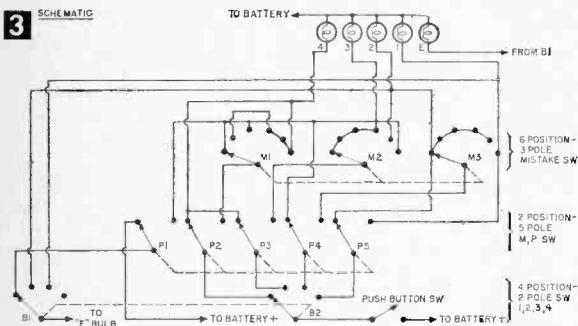


MATERIALS LIST — ZIM MACHINE

No. Req.	Description
5	miniature screw pilot light sockets with socket arms (Allied 34 B 257)
5	miniature screw lamps—GE222 (Allied 52 E 330)
1	chassis—2 1/4 x 2 1/4 x 5" (Allied 80 P 346)
1	miniature push-button switch (Allied 34 B 944)
1	non-shorting, 6 pos., 3 pole switch (Allied 34 B 360)
1	non-shorting, 2 pos., 5 pole switch (miniature) (Allied 34 B 928)
1	non-shorting, 4 pos., 3 pole (one not needed) switch (Allied 34 B 355)
1	1 1/2-v. 935C dry cell
	wire, solder, unmarked knob, dial plate

Shock-Absorbing Adapter for Mike

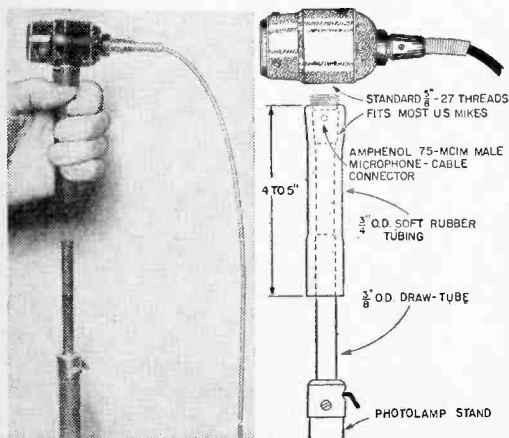
• This simple adapter and stand helps to cushion the microphone from bumps and vibrations that could ruin a perfect transmission or recording or damage the mike, yet total cost of project is



male mike-cable connector and press connector into one end of a length of 3/4 in. soft rubber tubing, allowing only the threads of the connector to protrude from the end of the tubing. Force the other end of the tube onto the top draw-tube of a standard folding and telescoping photolamp stand, distance depending on the weight of the microphone and the amount of cushioning desired. When you want to hold the mike in your hand, simply pull the rubber tube off the photolamp draw-tube and use it as a handle.—ARTHUR TRAUFFER.

Alligator Clip Receives Phone Tip

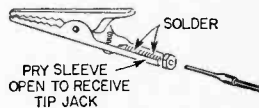• When you need to connect a cord tip to an alligator clip in order to make a special connection, convert the clip to take tip rather than purchase a more expensive clip with tip jack attached. Simply pry open the sleeve of the alligator clip, insert a metal tip jack, pinch the sleeve tightly around the jack with a pair of pliers and solder securely.—A. TRAUFFER.



less than the usual microphone stand. To install adapter, remove the cord-protecting spring in a

Combination Strobe-Flash Slave Unit

Flash or strobe, you can use two lighting units synchronized with your camera's shutter with this "slave" as the second unit


By W. F. GEPHART

ONLY recently have electronic flash slave units appeared on the market, but due to synchronization difficulties, most of these units cannot be used with flash bulbs when the occasion requires, such as when the coverage exceeds the capacity of the strobe light. And, either for balanced lighting or increased lighting values, there are any number of times when you'll want to use two synchronized units.

The unit shown in Fig. 1 can be used as a flash or strobe "slave" unit or simply as an extension unit, using interconnecting wires. (In some cases, it is not feasible to have a line-of-sight light path between the camera and the unit, and extension wiring is required.) The unit's versatility also includes ac operation or self-contained battery operation.

Figure 1 shows a panel view of the unit, the schematic in Fig. 2 shows that the unit consists of two basic circuits: 1) the strobelight circuit; and 2) the photocell triggering circuit. Interconnecting switches control the unit's function and its power source.


The strobelight circuit is a low-voltage, high-capacity type which reduces insulation and shock hazard problems. To reduce costs, the same voltage multiplier circuit is used on both ac and dc and, when using dc, an ordinary filament transformer is used instead of the more expensive vibrator transformer. When S2 is at "AC" and S1 is "On," line voltage is fed to the multiplier circuit, consisting of three selenium rectifiers and two capacitors which provides about 450 v to charge

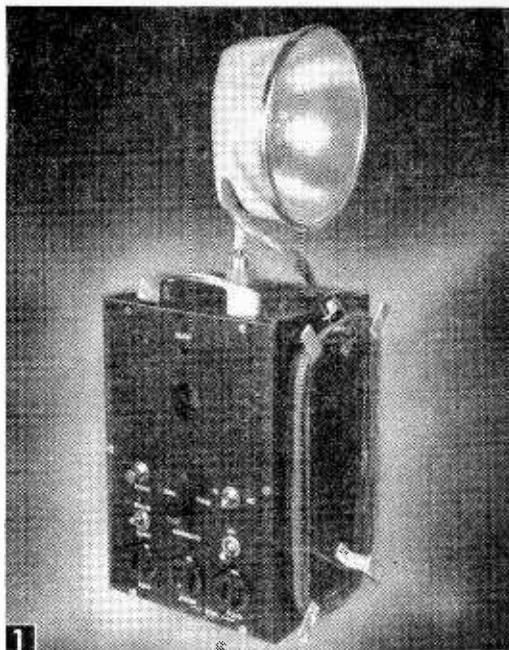


View of completed strobe-flash slave unit. Cord on brackets on unit is used only when light from camera unit cannot reach unit's cell.

main capacitors C4 and C5, providing slightly in excess of 100 watt-seconds light output.

When S2 is on "DC" and S1 is "On," the battery voltage is converted to ac in the vibrator (VIB, Fig. 2) and fed into the secondary of filament transformer T1. The voltage appearing in the primary of the transformer (which is used as a secondary) is approximately the same as normal line voltage and is fed into the same voltage multiplier circuit (through S2), again providing approximately 450 v. Exact voltage will depend on battery condition. With fresh batteries, light output will almost equal 100 watt-seconds, but

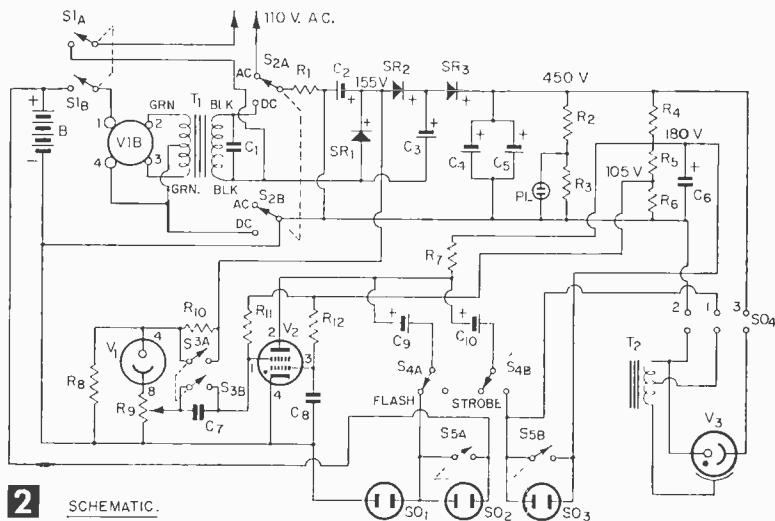

SCHEMATIC.

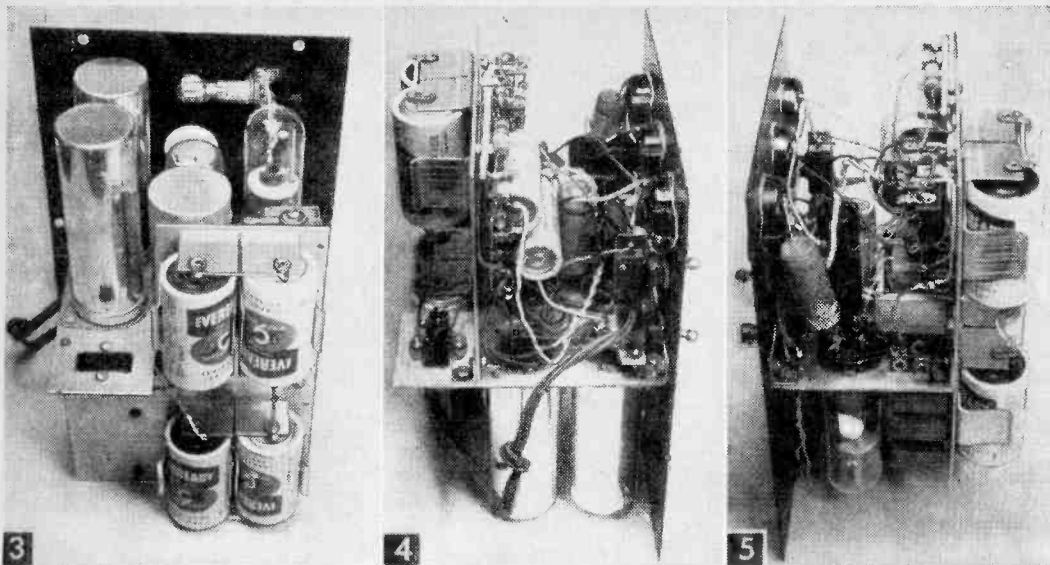

3 Back view of unit out of case (left) showing battery mounting; under-chassis view, showing three rectifiers stacked (at lower-center); and under-chassis view (right) show need for sub-assembly wiring.

will drop to about 80 watt-seconds as the batteries weaken.

Two voltage dividers are used to provide control and indicator voltages. The first of these, R2 and R3, provides approximately 90 v to fire the neon pilot light when the main capacitors are fully charged. Due to variations in neon bulbs, the value of R3 may have to be adjusted in assembling the unit. It should be set at a value that causes the neon bulb to light when the charging voltage reaches about 425 v.

The second voltage divider (R4, R5, and R6) provides ignition voltage for the flash tube (V3) and biasing voltage for the trigger tube (V2). These voltages are quite critical, and the values of these resistors may have to be changed slightly to provide the voltages shown in Fig. 2.


The "slave" circuit consists of a photocell (V1) and a strobotron trigger tube (V2). The trigger tube, a 1D21/SN4, is a grid-controlled gas tube capable of very high peak currents. Like most such tubes, it acts as a relay; the resistance between plate and cathode is almost infinite until "firing," upon which the resistance drops to nearly zero. Firing, or ionization, is controlled by the grids; de-ionization is controlled by the plate voltage. In this circuit, the grid voltages are established just below the ionization point by fixed dc bias (through R11 and R12), and a slight

additional voltage from the photocell (when light strikes it) causes the tube to ionize, short-circuiting C9 (or C10) through ignition coil T2. The discharge of the capacitor through the coil fires the flash tube, the whole operation occurring within a few *microseconds* of the time that light strikes the photocell.

As soon as the plate capacitor (C9 or C10) is discharged, the trigger tube de-ionizes since charging current for the capacitors, flowing through R7 causes the plate voltage of the trigger tube to fall below its ionization point. If the output of the photocell maintained sufficient voltage on the grid of the trigger tube, however, the latter would fire again as soon as the plate capacitor was

re-charged. To prevent this, the output of the photocell is normally connected to the grid through a capacitor. Thus, the grid voltage of the trigger tube is not increased unless there is a sudden pulse of voltage such as would be created by a flash, or rapid increase of light. Use of this feature avoids the necessity of any sensitivity adjustment of the unit in usage.

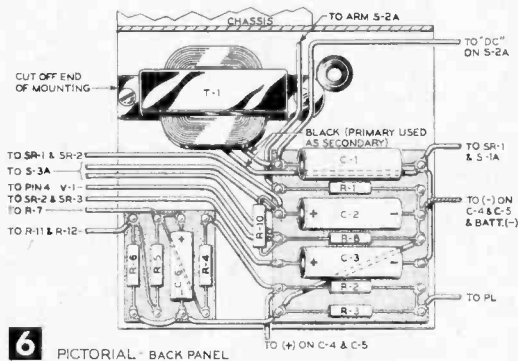In some cases, "pulse" of light operation can be a handicap. In a brightly-lighted room, for instance, movement between the main light source and the cell might trigger the unit. In such cases, closing S3 provides for operation on a "light intensity increase" basis, with adjust-




6 PICTORIAL - BACK PANEL

tion of light from the unit may vary. Convenience in handling is provided by a handle on top and aluminum angles for the ac cord.

Figure 3 shows a top view of the unit. The batteries are accessible from the back of the case for replacement. Only about 40 or 50 flashes can be secured from a set of "D" cells, and the unit should be used on ac whenever possible. If it is to be used on battery, the main capacitors should be charged initially on ac, particularly if the unit has been standing for some time.

Figures 4 and 5 show construction details. To get all components into the cabinet, it is necessary to use dual-panel construction, which requires pre-wiring before assembly. In practice, parts are mounted on the front panel and chassis, and these units are fastened together and wired, leaving long leads going to other components which will be mounted on the back panel. Then parts are mounted on the back panel, as shown in Fig. 6, and wired as shown. Capacitors and resistors can be mounted on mounting boards or with terminal strips. The back panel is then attached to the chassis and wiring completed.

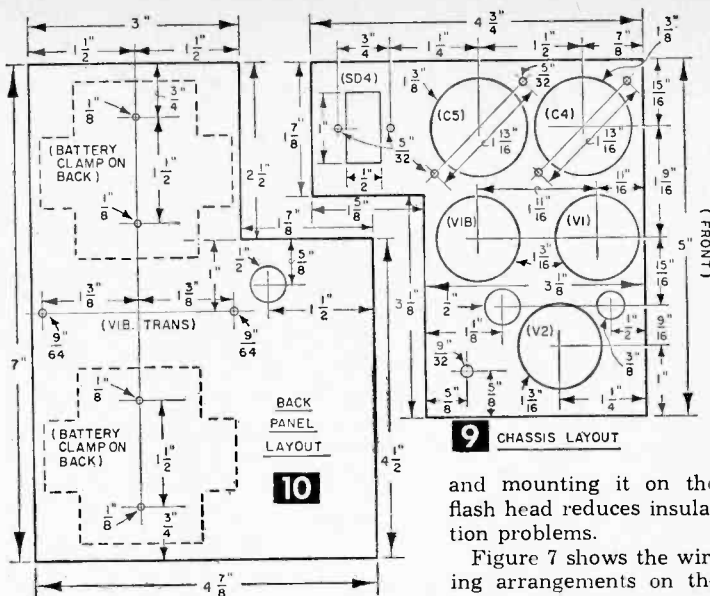Notice that the ignition coil is mounted on the flash head. Extremely high voltages (several thousand) are present in the output of this coil,




and mounting it on the flash head reduces insulation problems.

Figure 7 shows the wiring arrangements on the front panel and chassis.

Miniaturized components should be used, if available to meet specifications, to permit adequate wiring space. Figures 8, 9 and 10 show the layouts of the panels and chassis. The chassis layout shows space for two main capacitors as salvaged from a commercial strobe unit. If a single unit is used (as the alternate mentioned in the Materials List), it can be mounted in the center of the space shown for the two units. Both the chassis and rear panel are made of scrap aluminum and fastened to each other and to the front panel with small sections of aluminum angle.

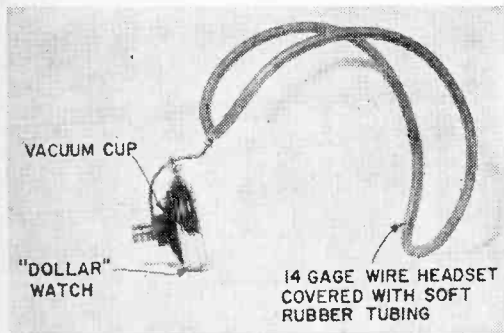Ticking Headset for Split-Second Photo Timing





• There's no need to keep your eye on a timer while you are busy at the printer, enlarger, or camera with a ticking headset. Timing is more accurate, because most watches tick four times per second and you simply count the ticks for split-second timing. Also, the inexpensive pocket watch used saves the cost of a special photo timing clock.

Bend a double headband from 14-gage solid copper wire, or from a wire coat hanger. Slip soft rubber tubing over the wire before you twist the wires together. Form an eye in the free end of the wire and fasten under the thumb-nut of a 1¼ in. diameter vacuum cup which has a screw molded into the rubber. When wetted, the vacuum cup will stick securely to the smooth back of a pocket watch. However, as an added precaution, slip the headband wire through the loop on the winding stem of the watch before sticking the cup to the back of the watch, as shown in photo.

If you use a wrist watch instead of a pocket watch, you can dispense with the vacuum cup. Just staple a small block of wood to the headband so that the wrist watch can be strapped to the block.

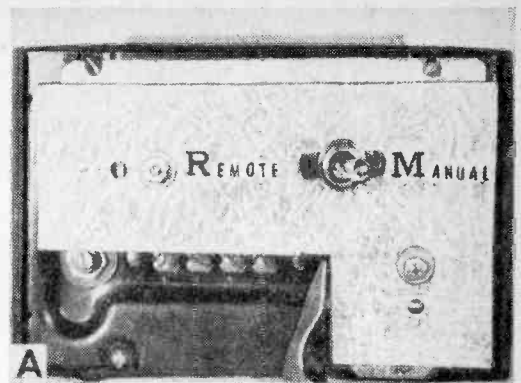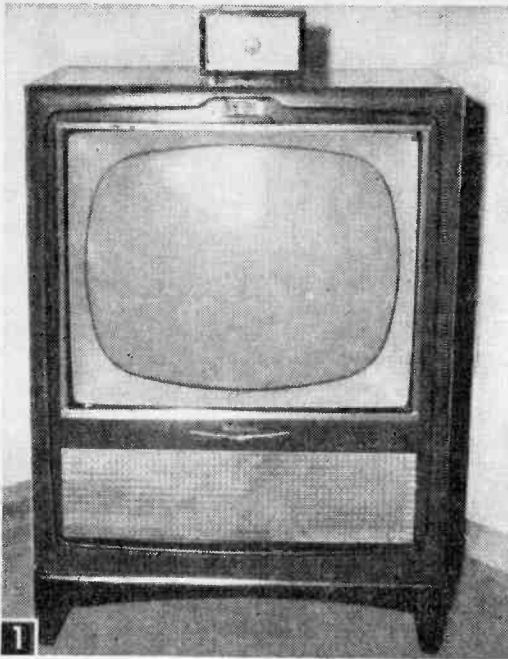Some wrist watches tick faster than pocket watches, so count the number of ticks in a five-second period to determine how many ticks there are in one second.—ARTHUR TRAUFFER.



ROTATOR Remote Control

By HOMER L. DAVIDSON

Just about all you do to control your TV antenna rotator from your armchair is to look at it—and flick a switch after having set the switch on the remote unit (see A, above right) to Remote.


SINCE the TV receiver has become remotely controlled, the owner usually likes to remain in his easy chair and control everything from there. But nothing has been done about the lonely rotator control box that sets on top of the set. Sometimes when the television receiver is moved to another location, the rotator control box remains behind. Then, when a desired distant station is in a different direction you still have to get up and operate the rotator control box. So here's the solution to that problem: a rotator remote control.

Generally, the indicator on the rotator control

box gives a direction of rotation, but does not pin-point it. The operator watches the picture on the screen for indication that he is approaching the direction of the station or passing it. With this in mind, the remote rotator control operator simply pushes the switch to right or left and watches the picture on the screen. The small remote box that he uses is nothing more than a single-pole, three-position rotary switch. A standard 4-conductor rotator cable is used to hook the remote box to the relays on the back of the rotator control box.

Any manually operated rotator, regardless of make, can be wired as described in this article; connections shown in the Figures are those made to an Alliance T-12 control. The chassis will vary in size and dimensions depending upon what manual rotator you have.

Pick up a small sheet of Reynolds aluminum at your local hardware store to form the chassis for the control unit and drill two 1/4-in. holes in it (see Fig. 2) and a 7/8-in. hole to mount the toggle switch. After the chassis has been cut and drilled, bend it to house the small relays. Then drill the chassis mounting holes. I bent my unit so that the mounting holes and screws for the rotator unit's plastic case attachment could also be employed to fasten the small

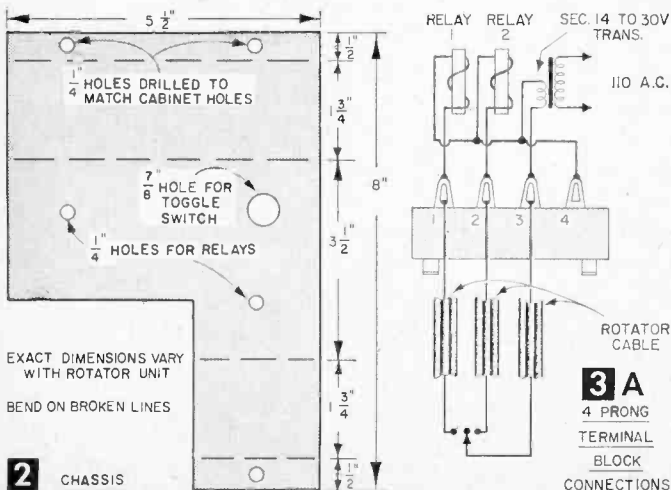

MATERIALS LIST—ROTATOR REMOTE CONTROL

No. Req'd	Description
1	single-pole, 3-position rotary switch (No. 12B579)*
20'	4-conductor antenna rotator cable (No. 2B20, Belden type 8464)
2	Potter and Brumfield K111AY DPDT relays (No. 19A1424)
1	SPST toggle switch (No. 12A403)
1	Jones solder type terminal strip (No. 12A1584)
1 pc	6 x 8" aluminum $\frac{1}{16}$ " thickness, or to suit antenna rotator unit

* (all catalog numbers are those of Burstein-Applebee Co., Dept. SM-8, 1012-14 McGee St., Kansas City 6, Mo. The antenna rotator adapted in this article is the Alliance Tenna-Rotor T-12, No. 4W172)


chassis of the remote unit to the control box.

After the two relays and the toggle switch have been mounted, solder a lead to one side of each coil of the relays and run this directly to the terminal block (see Fig. 3A and 4). Tie the remaining two leads of the coil connections together and tie to one of the remaining outside lugs on the 4-lug terminal block (see Fig. 3A). Next, solder the first three terminal lugs to the flat rotator wire.


The small toggle switch actually switches the ac current into the primary circuit of the rotator transformer. These two wires are soldered in parallel with the strip switch of the original control box. The relay point-contact connections are soldered across (in parallel) with the strip switch that, when pressed down, activates the direction of the small rotator motor (see Fig. 3B). It is best to just parallel these wires and when hooking them to the remote control switch they can be switched so that the rotator turns in the right or left direction.

In most rotators when the switch is turned right or left, the 110-v ac is applied to the transformer and the rotator motor connections are wired so the motor will go to right or left when so pressed. With this remote control, you simply turn the switch to Remote (see Fig. 1A), then remain seated the rest of the evening. When through using the remote control, switch the unit back to Manual.

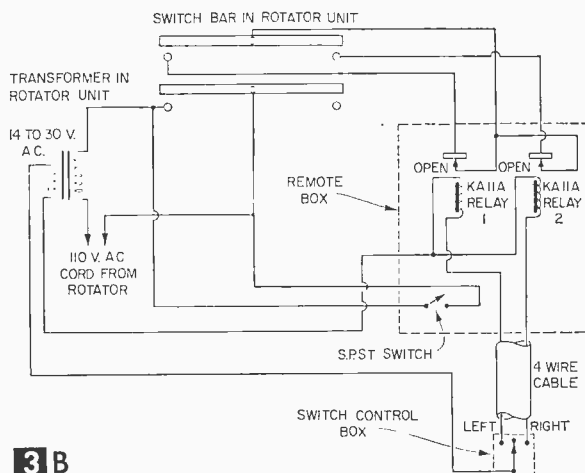After the wiring has been completed, the unit is ready to be checked out. Do not screw the



3 B

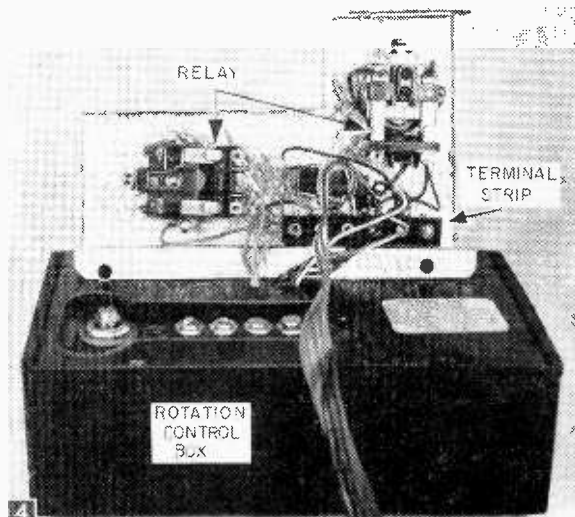

chassis to the rotator control box until the unit has been completely tested. First check over the wiring, then throw the toggle switch to the Remote position. Press the remote control switch to the "right" position. The needle on the control box should move in this direction. If not, simply reverse the two wires in the control box. Now try the unit to the "left" position. (The relays used are very quiet and do not chatter when in operation.) Finally, turn the rotator a complete rotation in both directions.

This Makes Used Volume Controls as Good as New

When a radio set needs a new volume control and it cannot be obtained, the old one can be made to give service as well and as long as a new one. All that is needed is to apply a thin coating of carbon in liquid form and allow it to dry thoroughly, after which one drop of some good machine oil is put on the control and the control rotated for a short time until the oil has been distributed in the form of a thin film over

the carbon coat. A drop of oil will also give longer life to new controls.—HAROLD H. PEER

• According to a recent survey taken of U. S. married couples, TV viewing has virtually eliminated family quarrels. Reason: 50% of those surveyed stated they no longer spoke to their wives in the evening; the other 50% no longer spoke to their husbands.

Two Tin-Can Megaphones



"Calling all cars, calling all cars, go to Vine and Cherry and pick up two young men riding on a bicycle." This could be the voice of any youngster, perhaps one of your children, using these small megaphones



Experimental jobs, the two tin-can megaphones for which plans are given in this article will afford children a lot of fun.

By
HOMER L. DAVIDSON



THESE experimenter's projects, from which surprising results have been obtained, can be used as megaphones or as portable microphones. Voice clarity is quite good and volume is good enough for the purpose intended.

The first megaphone (Fig. 2) uses only four major components: a small homemade mike, a 2N255 power transistor, $4\frac{1}{2}$ v batteries, and a surplus, powered phone. The microphone requires the most work, but by building it yourself, you'll save roughly the \$5 a commercial button would cost. First, secure a small, thin, metal container such as those used for transparent tape. The spool on which the tape was rolled will serve as the heart of the microphone. Glue it to the bottom of the metal container and fill the core of the spool with corrugated cardboard spacers. Place a metal washer over this assembly and drill a small hole through the center of the metal container. Solder a length of flexible wire to the washer and push it through this hole. Glue washer and cardboard spacer in place,


leaving about $\frac{3}{16}$ in. space at the top of the spool. Solder another short length of flexible wire to the container. (Be sure to scrape off paint so a good contact can be made.)

Now remove the core from a small discarded flashlight battery and crush the carbon into very small particles. Scoop these up and place them in the depression above the washer in the tape container (see Fig. 1). Do not pack them tightly, but fill the space. Place a piece of tin foil over the assembly, put lid in place, and test the unit. Some granules may have to be removed for best results.

Mount the transistor and powered phone on the fiber board as detailed in Fig. 3. Remove the bolt that holds the powered phone together and substitute a larger one that will clear the small wood block, fiber board, and powered phone. (The small wood block prevents the transistor from shorting against the metal container.) Mount a 9-prong wafer tube socket on the other side of the power transistor to plug the power transistor into, and insert the three penlite batteries

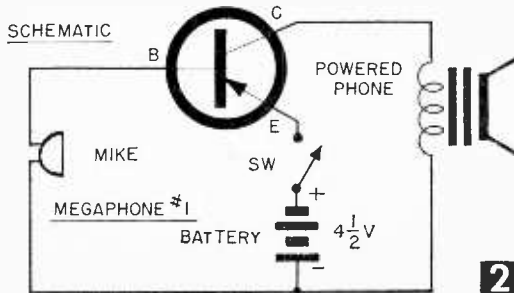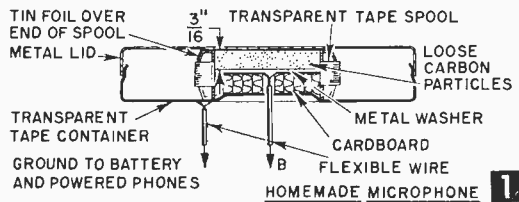

2

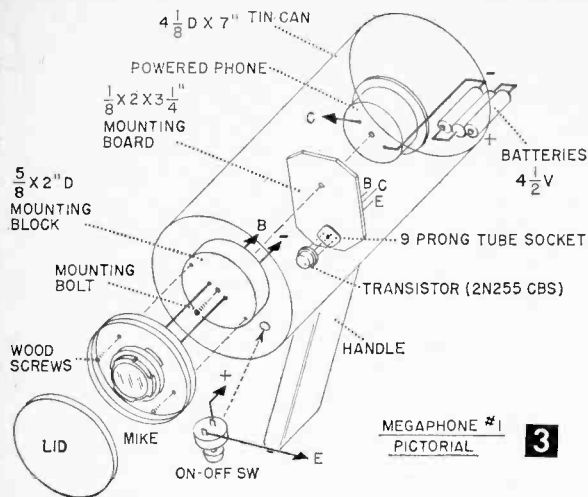MEGAPHONE #1
PICTORIAL

3


MATERIALS LIST—TIN-CAN MEGAPHONES

Megaphone No. 1	Description
Microphone Sneaker	homemade (see text and Fig. 1)
Transistor	powered phone (surplus)
Battery	2N255 CBS power transistor
Switch	3 penlite cells & holder
	SPST rotary

Megaphone No. 2	Description
P1 & P2	powered phones (surplus)
C1	.01 mfd paper capacitor, 200 v
R1	10K fixed resistor, 1/4 watt
R2	220K fixed resistor, 1/4 watt
T1	Argonne AR173 interstage transformer
TR1	2N107 GE transistor
TR2	2N255 CBS power transistor
Battery	6-v Eveready
Switch	Rotary SPST switch

bolts that hold the plastic cases to the power phones and substitute larger ones. Countersink bolt heads so that other components mount flat against the pine board. A small rotary switch taken from a volume control turns the unit Off and On. If feedback occurs on this model, reduce the value of R1 until the howl disappears.

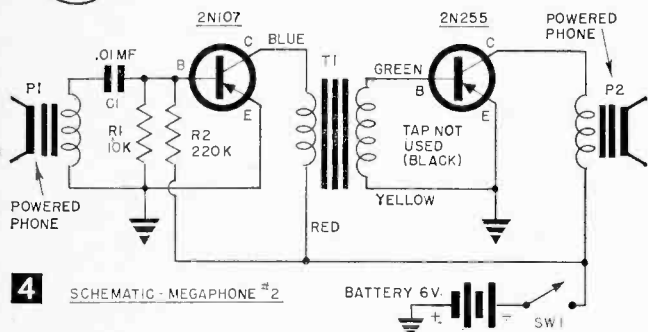On both megaphone mikes you must talk directly into the microphone. If the carbon granules of the homemade mike (Megaphone No. One) pack, hold the unit down and talk into it or give the case a tap to jar them loose again.




4 SCHEMATIC—MEGAPHONE #2

into standard holders mounted near the end of the large, juice-type tin can (4 1/8-in. dia., 7 in. long) so that they are easily accessible.

Megaphone No. Two.

This megaphone has more volume and slightly greater voice clarity than the first. A second transistor is used for amplification and a surplus, powered phone is employed as the mike. This mike is capacity coupled to the base circuit of TR1 (see Fig. 4). An interstage coupling transformer couples the two transistors together, the output signal is fed directly from the power output transformer into the surplus phone. No output transformer is needed. This megaphone is also mounted inside a large size juice can.

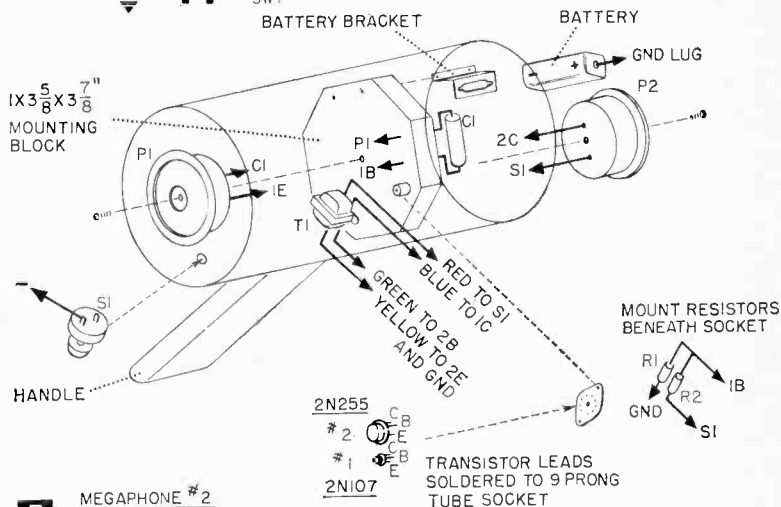First mount all components on a piece of white pine (see Fig. 5). Mount the power transistor and one surplus phone on one side of the pine board, the other phone and the small battery on the other side. Remove the small



5 MEGAPHONE #2


Hot Tip for Soldered Joints

- When soldering wires and cables in a radio receiver, immediately after the iron is removed from the soldered joint, paint the joint with lacquer-thinner, using a small brush. The rosin flux will evaporate immediately, leaving a clean joint and cold-soldered joints will show up immediately, preventing future trouble.

Calibrated Potentiometer

Precisely calibrated, an 82¢ pot is worth
10 times its purchase price

By FORREST H. FRANTZ, SR.

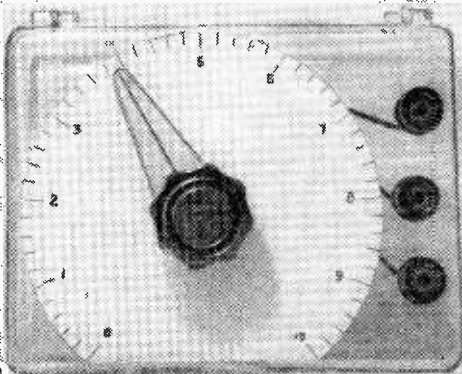

1 This precise calibrated potentiometer has many practical and time-saving applications. It can be built for less than \$2.

THOUGH inexpensive, simple, and versatile, this calibrated potentiometer can be used to do precise measuring jobs, as a calibrated voltage divider, as a Wheatstone bridge element, as a precise circuit control, as part of a reactance measurement circuit, as a circuit substitution element, and in numerous other applications.


The potentiometer adapted is a Clarostat type 58C1. It has an electrical rotation of 280° and a mechanical rotation of approximately 300° due to the metal wire retainers at the ends. Type 58C1 was chosen because it has an independent linearity of plus or minus 1%. Since most potentiometer applications involve a voltage divider scheme, 1% is usually the maximum overall error. The total (end-to-end) resistance, however, is only within plus or minus 5% of the stated value.

If you're going to use your calibrated potentiometer in rheostat fashion as a variable resistor, measure its total resistance with a Wheatstone bridge and record this value on the dial scale (Fig. 2). The actual resistance for any setting of the dial—when the zero and center terminals of the potentiometer are used—will then be the dial setting times the total resistance divided by 10. If you don't have access to a Wheatstone bridge (your parts distributor, the local high school, or your phone or power company in smaller communities may have them), you can determine the total potentiometer resistance by comparison with reasonably accurate resistances on the ohm scale of a vacuum tube voltmeter.



Begin construction by mounting the potentiometer in any box you have available with a front panel $3\frac{3}{4} \times 5$ in. or larger. I used a plastic box (see Materials List). The potentiometer mounting hole is $\frac{3}{8}$ in. Copy, cut out and paste down the scale given in Fig. 2 or the case. Use Carter's Rubber Cement and be sure to force out all air pockets between the scale and box. Also be sure to align the scale center hole and the potentiometer mounting hole on the panel accurately.

Now place the potentiometer shaft in a vise (to avoid damaging the control), saw the shaft to a length of $\frac{1}{2}$ in. and mount potentiometer and binding posts on the panel. The wiring is simply a connection from each potentiometer terminal to a binding post (see Fig. 1).

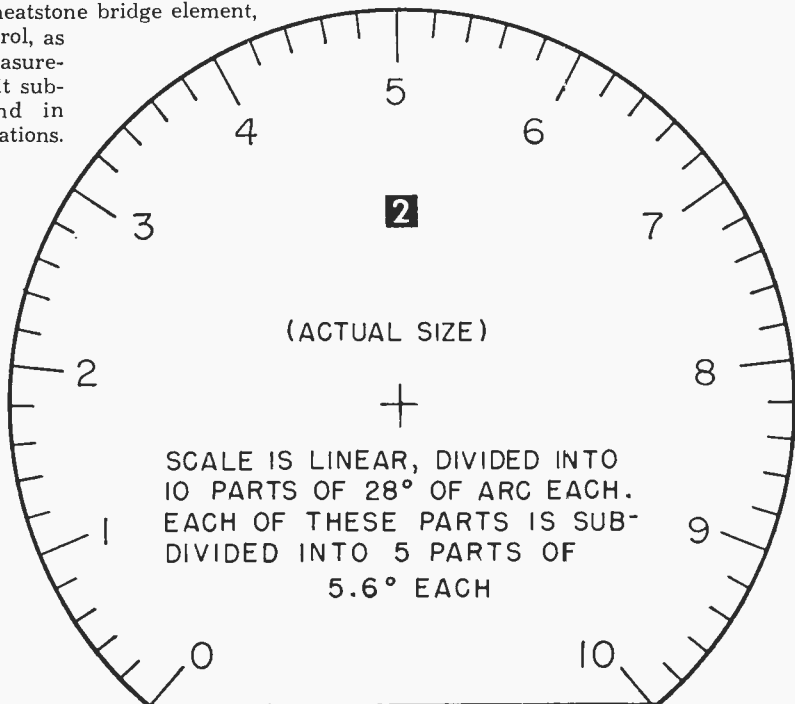Make the hairline on the plastic piece used as a pointer by scratching a straight line through the knob center line with an ice pick or other



4 WHEATSTONE BRIDGE CIRCUIT

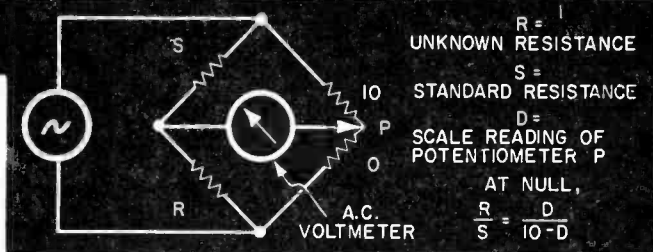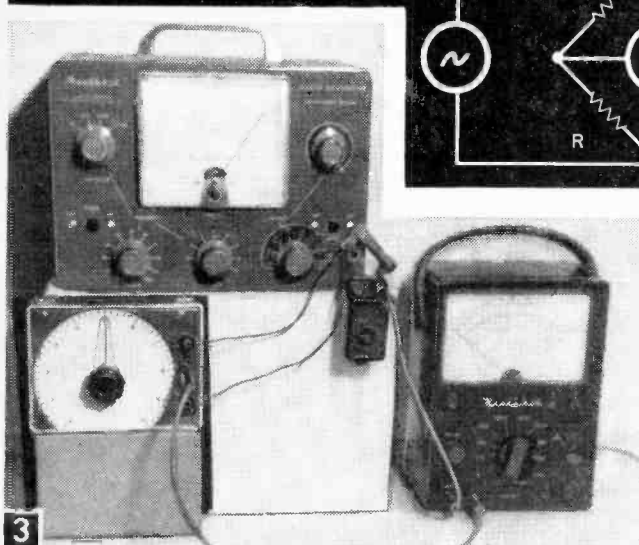

The calibrated potentiometer can be used as a Wheatstone bridge element for precise resistance measurements (see Fig. 4).

This formula for a null on the voltmeter reading holds true for readings where S is the standard resistance and D is the potentiometer (P) dial reading. Greatest accuracy is realized when R is nearly equal to S . You can get a rough idea of the value of R with your ohmmeter. If you have several calibrated potentiometers and if you know the total resistances accurately, you can readily use one of these to obtain the desired value of S . This should immediately suggest the alternate scheme of setting potentiometer P at 5 and adjusting S for null. Then R equals S . I've shown an audio signal generator as an energy source for the bridge because this is the handiest source if you have one. A battery may just as well be used with the meter switched to a dc current scale.


sharp instrument and filling the scratch with India ink. Attach this pointer to the knob with Duco cement, being careful to align the hairline accurately with the knob's center hole.

Place the knob-pointer assembly on the potentiometer shaft and fasten it so that it overrides the 0 and 10 marks by equal amounts. The knob set screw may have to be loosened and the knob reset several times before this is realized. It is, however, the only calibration required.


You'll find it convenient to build several calibrated potentiometers. Suggested values are 10, 100, 1K (1000), 10K, and 50K ohms. (The 50K pot will cost you \$1.44; the rest, 82¢ each.) They will extend the utility of all of your other in-

struments considerably. Figure 3 and 4, for example, show the potentiometer in a Wheatstone bridge circuit for measuring resistance accurately. The unknown resistance R is found with this formula for the null (zero) condition on the voltmeter:

$$\frac{R}{S} = \frac{D}{10-D}$$

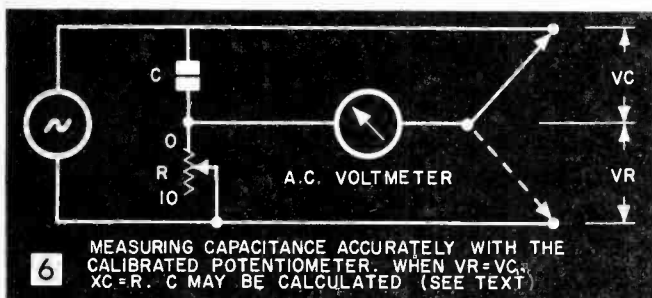


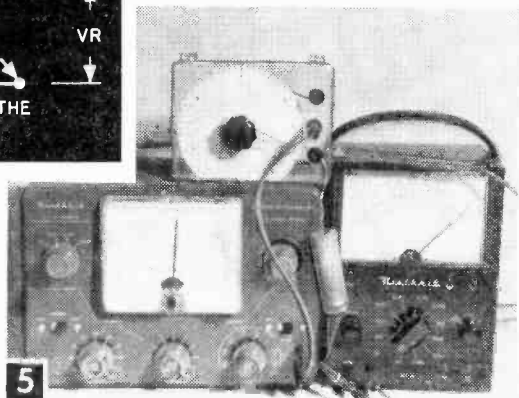The calibrated potentiometer, a source of ac voltage, and a multimeter are used to measure capacity.



struments considerably. Figures 3 and 4, for example, show the potentiometer in a Wheatstone bridge circuit for measuring resistance accurately. The unknown resistance R is found with this formula for the null (zero) condition on the voltmeter:

5

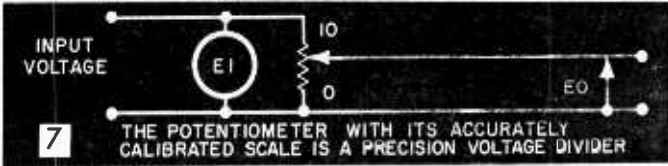

MATERIALS LIST—CALIBRATED POTENTIOMETER

No.	Req'd	Description
1	potentiometer	(Clarostat type 58C1—specify resistance value desired)
1	plastic box	(Lafayette MS-162)
3	binding posts	(1CA 623)
1	knob	(1CA 244 or equivalent)

sured capacitance may be in error by about 10%, although with an accurately calibrated signal generator and a high-impedance, ungrounded meter you can realize more precise results.

The most accurate method is to use a 25- or 30-v filament transformer for your signal source. Adjust R for equal voltage drops across R and C as before. Then C can be calculated from

$$X_c = \frac{1}{2\pi fC}$$

since resistance $R=X_c$ for this condition. Therefore C in farads equals $1/377R$ where R is the resistance and the ac line frequency is 60 cycles.

Another use for the calibrated potentiometer is as a precise voltage divider. The circuit is shown in Fig. 7. The output voltage E_o in terms of the input voltage E_i is $E_o=(D/10)E_i$ where D signifies the dial reading. This arrangement is equally satisfactory with ac or dc.

There are two points to remember in connection with the voltage divider application:

- 1) The formula given will hold to within ap-

proximately 1% if the load resistance connected across the output terminals is 20 or more times greater than the total resistance of the potentiometer used. If the load is resistance and is only 10 times the total potentiometer resistance, the error becomes approximately 2% if the potentiometer is set between 6 and 7 (where maximum loading error occurs). If the load-to-total-potentiometer-resistance ratio decreases further, the accuracy of the formula also decreases.


- 2) The 58C1 potentiometers are rated at three watts dissipation. Be careful not to exceed this. You may not burn out the potentiometer if you do, but it may damage the unit sufficiently to corrupt the accuracy of your calibrated potentiometer. The maximum voltage that can be applied across the potentiometer total resistance without exceeding the three-watt limit is $1.7\sqrt{R}$ where R is the total potentiometer resistance. This assumes a negligible load (20 times R).

DECCA

160's Last Chance?

By C. M. STANBURY II

THERE was a time when the radio amateur and the SWL who tuned the amateur bands, could take advantage of every DX challenge, medium wave, short wave and VHF (such as it was before World War II). But during WW2 all amateur radio operations were suspended and when they were resumed, MW operators were forced to share 160 meters with a new, noisy and fast growing radio service, LORAN. From that day until this, the band has steadily declined. It almost reached rock bottom when, about six months ago, the frequencies assigned for amateur use were cut from 100 kc to only 50 kc—because of another LORAN chain. It is fortunate coincidence that at that same time

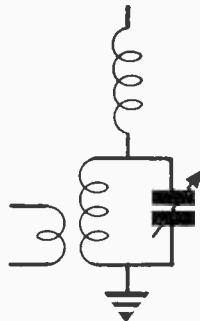

a new radio-navigation system was being introduced in North America: DECCA. This is a widely used system in Europe and has kept the ear-splitting LORAN buzz off 160 in that part of the world. It could do the same over here. A chain is already in operation along Canada's East coast.

Fourteen Years of Neglect.

Although Decca was invented by two Americans, it was developed in England and up until now has never been used

here. The system literally had a baptism of fire. It was first used on June 6, 1944, D-day, and was instrumental in the success of the Allied invasion of Europe, guiding the vast invasion armada through the few channels swept clear of enemy mines.

The first permanent chain was put into operation in 1946. And it is at this point that we can start raising our eyebrows. The U.S. Navy publishes a complete listing of radio navigational aids. The last edition was published in 1955, eight supplements have been issued since to keep it up-to-date. The publication contains all LORAN stations. It even goes so far as to list stations of a European system called CONSOL. (From the standpoint of accuracy, CONSOL is

inferior to both LORAN and DECCA.) But for the U.S. Navy, if we are to judge from this publication, DECCA does *not* exist.


Decca vs. Loran. Each DECCA system consists of four stations, a "master" and three "slave" stations designated red, green and purple. By measuring the phase difference between the master and any two slave stations, a navigation fix is obtained and position automatically plotted on a gridded chart. Its operation sounds simple and it is, much simpler than that of LORAN.

For navigational purposes, DECCA is as good, if not better than LORAN. While LORAN may have an edge in range, the accuracy of DECCA is unbeatable—it is measured in yards! DECCA is so far advanced as a medium-range aid that LORAN is not considered as competition.

From the point of view of the amateur or DX listener, DECCA is ahead all the way. First it does not now use the 160-meter band, operating instead between 70 and 130 kc. Second, each LORAN chain has a band width of 100 kc, while DECCA stations use unmodulated carriers. Thus, if these stations were to use 160 meters, which is unlikely, the interference would still be less.

The Future. There is, of course, no assurance that DECCA will ever replace LORAN in the U.S. This is true despite the fact that an experimental chain has been set up at New York, because millions of dollars have been spent on LORAN transmitting and receiving equipment. On the other hand, DECCA is somewhat cheaper and it is conceivable that a gradual changeover would save money for everybody concerned over the long run. This possibility becomes a probability when you realize that LORAN costs are going to increase for the user. Much of the present receiving equipment is war surplus and, when it wears out, replacements will be new, full-price sets.

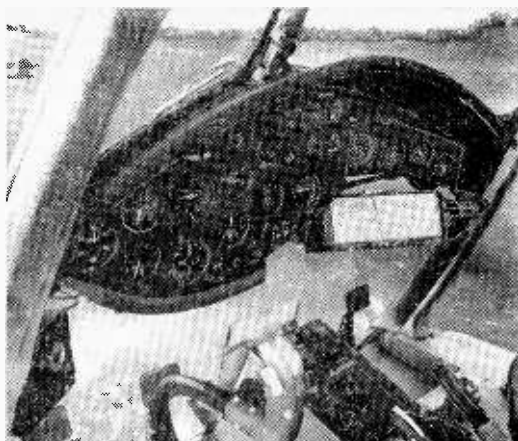Then there is the distance edge held by LORAN. Balancing this off is DECTRA, a new long range




Decca Navigator and Flight Log installed in a Bristol 171 helicopter of British European Airways. The map moves vertically on rollers, in scale with plane's forward speed. Lateral movements are traced electronically by a pen that gives the plane's second-by-second position with faultless precision.

version of DECCA. This system is being used experimentally by Pan American and a number of other airlines on their North Atlantic flights. Should DECTRA work out, and the odds are good that it will, there is little doubt that the DECCA systems will *eventually* replace the present aeronautical systems. The public will only stand for so many Grand Canyon disasters before it demands—and gets—action. From there it is only a short step to the complete deletion of LORAN.

But the biggest question mark of all is the amateur himself. At the moment his interest in the band is almost nil. In order to hold any amateur band it must be used. If this indifference continues, the amateur will not only fail to regain what he has lost on 160, he will undoubtedly lose what he has left on Medium Wave.


THE DECCA BAND IN NORTH AMERICA

K C	Exact Frequency	Chain	Station	Location
70	70.384	Newfoundland East	Purple Slave	Comfort Cove
	70.98	Newfoundland West	Purple Slave	St. Lawrence
	71.142	Nova Scotia	Purple Slave	Ecum Secum
	71.4375	Quebec	Purple Slave	St. Felix-de-Valois
80	84.461	Newfoundland East	Master	Port Blandford
	85.18	Newfoundland West	Master	Ramea Island
	85.370	Nova Scotia	Master	Chester Basin
	85.725	Quebec	Master	St. Raymond
110	112.615	Newfoundland East	Red Slave	Shore Cove
	113.57	Newfoundland West	Red Slave	Cape Ray
	113.827	Nova Scotia	Red Slave	Alma
	114.3	Quebec	Red Slave	Lac Bouchette
	117.1575	Quebec	Purple Slave(extra/ /ID frequency)	St. Felix-de-Valois
120	126.691	Newfoundland East	Green Slave	St. Lawrence
	128.055	Nova Scotia	Green Slave	Jordan Bay
	128.5875	Quebec	Green Slave	St. Camille

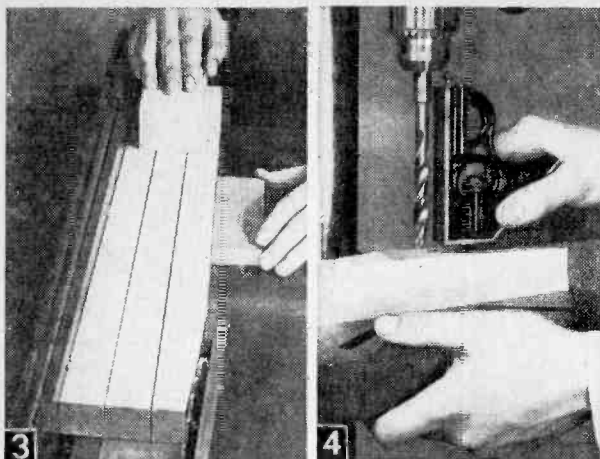


Left, when cutting the short tapers, the narrow parts of the legs face towards the operator. Note push block used to advance all three legs forward simultaneously.

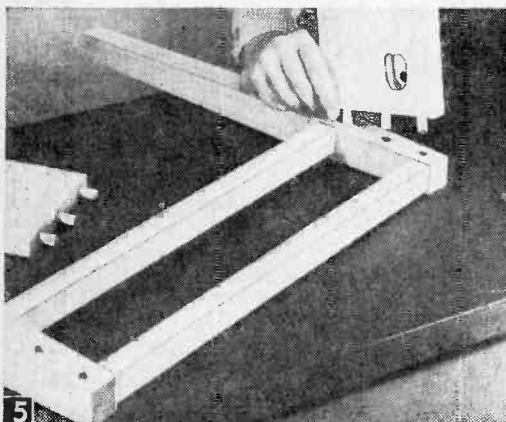Right, dowel holes in the legs should be bored at true right angles to the face side of the short tapers, using a spur bit for making the holes.



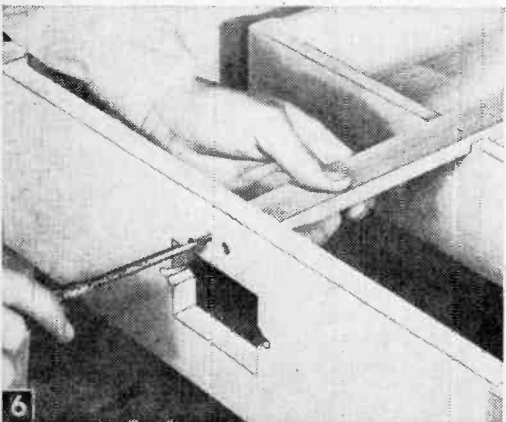Assembling right rail to front leg unit. Note mortise and thru-hole for mounting lamp control switch.



Drawer guide is attached with screws to the rear and top front drawer rail. Note notch cut in the drawer back for the guide.

dimensions are reached on the lower end of the legs. The short tapers (at the upper end of the legs) are made on two adjacent sides only, which in this instance are best cut on a circular saw (Fig. 3). Position your fence $4\frac{1}{2}$ in. from an inside tooth and sandwich two of the previously tapered legs between the fence and the leg to be short-tapered. After this taper is cut, turn the leg over to make a similar taper on an adjacent side. Then repeat the process with the other three legs.

Next, form the sides, back and drawer rails, and then cut a rectangular opening in the back rail for an outlet box, and an inside mortise in the right rail towards the front for insertion of the light-control switch (Fig. 2). Dowel holes are bored in the rails first and then spotted (preferably with dowel centers) on the short tapered sections of the legs. If these matching holes in the legs are made on a drill press, tilt the table slightly to the left, to square up the tapered surface with the bit (Fig. 4). To assemble these parts, first join the drawer rails and front legs together with dowels and a liquid hide glue to form a unit, then join the rear legs to the back rail. Then dowel and glue these two

MATERIALS LIST—TELEVISION STAND

No. Pcs.	Description	T	W	L
		(in inches)		
4	Legs	$1\frac{5}{8}$	$1\frac{5}{8}$	19
2	Drawer rails	$\frac{3}{4}$	$1\frac{1}{8}$	$17\frac{1}{2}$
2	Fillers	$\frac{3}{4}$	$1\frac{1}{8}$	$3\frac{1}{2}$
2	Side rails	$\frac{3}{4}$	5	18
1	Rear rail	$\frac{3}{4}$	5	$17\frac{1}{2}$
1	Drawer front	$\frac{3}{4}$	$4\frac{1}{4}$	$16\frac{3}{4}$
2	Drawer sides	$\frac{1}{2}$	$3\frac{1}{2}$	17
1	Drawer back	$\frac{1}{2}$	$3\frac{1}{2}$	$15\frac{1}{4}$
1	Drawer bottom (plywood)	$\frac{1}{4}$	$15\frac{1}{2}$	$16\frac{1}{2}$
2	Drawer slides	$\frac{3}{4}$	$1\frac{1}{4}$	$18\frac{1}{4}$
1	Drawer guide	$\frac{1}{2}$	$1\frac{1}{2}$	$18\frac{3}{4}$
1	Sub top (plywood)	$\frac{3}{4}$	20	$20\frac{1}{2}$
1	Swivel top (plywood)	$\frac{3}{4}$	22	$22\frac{1}{2}$
1	Roller plate (Presdwood)	$\frac{1}{8}$	$12\frac{1}{8}$	$12\frac{1}{8}$

MISCELLANEOUS ITEMS

4	Sash rollers (see drawing)			
1	Carriage bolt			
2	Lock nuts and 1 washer	$\frac{5}{16}$ dia.		$2\frac{1}{2}$
8	Dowels (for drawer rails)	$\frac{5}{16}$ dia.		$1\frac{1}{2}$
18	Dowels (for side and back rails)	$\frac{3}{8}$ dia.		$1\frac{3}{4}$
12	Dowels (for drawer assembly)	$\frac{1}{4}$ dia.		1
2	Drawer pulls			
4	Casters (swivel type)			
12	Misc. flathead screws (see drawing)			

ELECTRICAL PARTS


1	Outlet box
2	Outlet box connectors
2	Convenience outlets
1	Convenience outlet plate (duplex)
1	12 ft. Appliance cord (14 gage)
1	Appliance plug (male)
1	Socket (keyless)
1	Tubular half shade
1	Mounting bracket (metal) see drawing
1	Tubular lamp (40 watt, T 10)
1	Rotary switch

Note: Dimensions given are finished sizes. Parts are cut from solid stock unless otherwise specified.


units to the side rails (Fig. 5). Anchor the fillers in the drawer opening to the front legs with nails.

For the drawer, make the necessary rabbeting cuts for the corners, grooves for the bottom, and then fashion the lip on the drawer front (Fig. 2). Then assemble the parts by first joining the front and back to one of the sides, and then inserting the bottom in the grooves and adding the remaining side. Next, fit the runners and install the guide as in Fig. 6.


Fig. 2C shows the type of sash roller on which the revolving top rides. These rollers are installed in mortises cut in the sub top (Fig. 7), and the sub top is screwed to the legs. Next in order is the revolving top to which the roller plate (Fig. 8) is attached with brads. You mount this top on the sub top with a carriage bolt inserted through the pivot holes of these two members (Fig. 2C). Remember to oil the rollers and apply a thin coating of lubricating grease to the roller plate before using. When installing the casters, make certain the stem holes in the legs are bored on a true vertical (see front view in Fig. 2) or on a 3° angle from the leg center line. Boring them parallel with the center line interferes with the swiveling action of the casters. You can do this boring most easily after you have assembled the

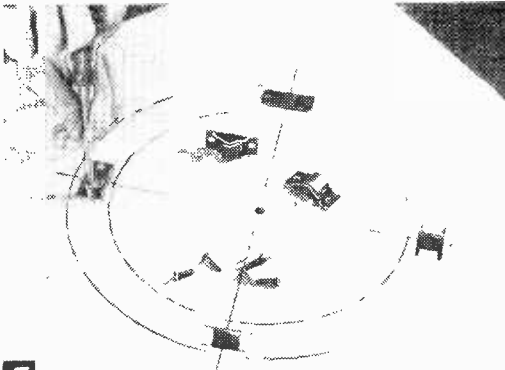

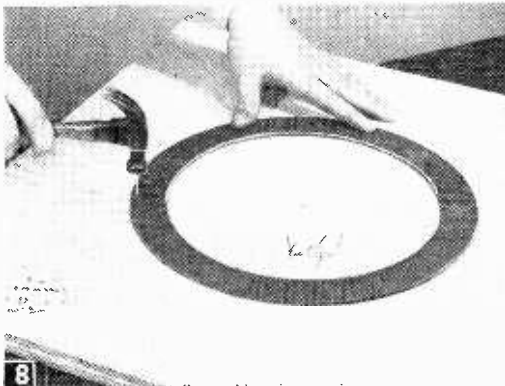
7 Attaching sash rollers diagonally to the sub top.



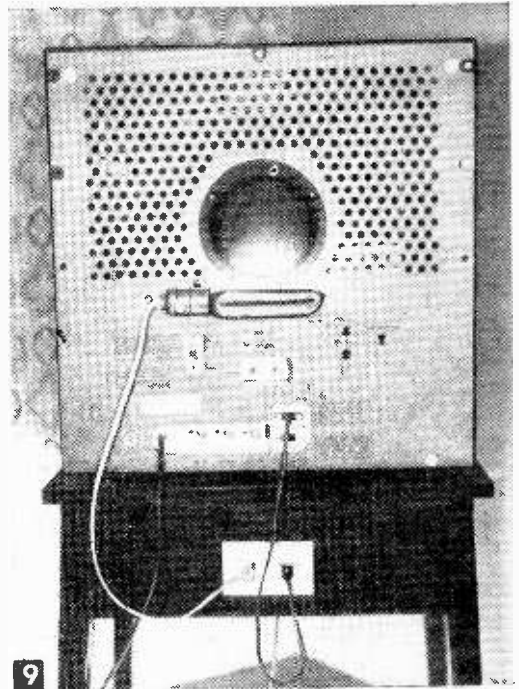8 When bradding roller plate to the revolving top make certain it is positioned to coincide with the scribed circles shown in Fig. 7.




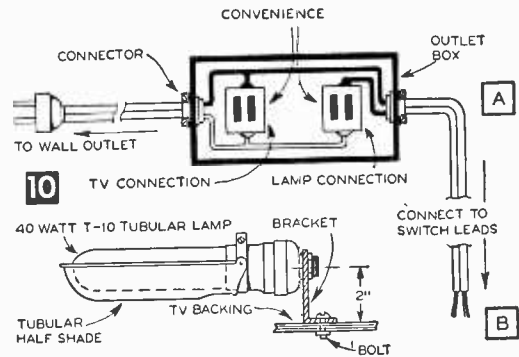9 Keep wires connecting the lamp and TV set to the receptacles fairly short if you can. With this wiring hook-up it is necessary that only one cord be connected to a wall outlet.



parts (minus the revolving top), if it is done on a drill press with the table set at the level position.

After sanding and finishing the wood, you can install the electrical units. The wiring hook-up (Fig. 10A) permits the television set to be operated as usual with its *On-Off* switch, while the lamp is controlled by a small rotary switch. To minimize eye strain, have the reflected light from the wall match the incident brightness of the picture screen. You can do this by using a 40 watt lamp and half shade (see Fig. 10B) for light walls, 60 watt for medium tones and 75 watt for dark-colored walls. A larger shade or reflector can be substituted for the half shade shown in Fig. 9 to fit the higher wattage lamps.

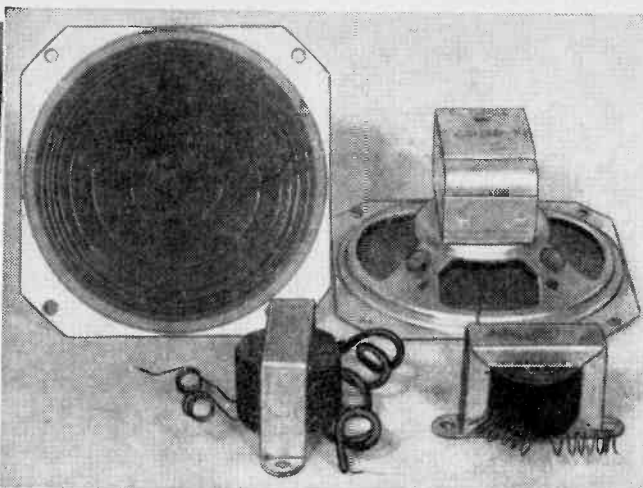

Sound-Powered INTERPHONE


THIS simple interphone system requires no electrical source of any kind to operate. The voice itself generates the necessary power to operate the two-way communicating system. Operation of the interphone is based on the fact that any moving coil, placed in a magnetic field, generates a small voltage which varies with the vibration or movement of the copper coil. A PM type radio loudspeaker is just such a moving coil device. And while intended to reproduce sound impulses, it will, by the same token, transmit them. Of course, the volume of this system is not to be compared with an interphone outfit operating through several stages of amplification and it is not advised for use in a factory or other noisy location. But it serves well otherwise.

The only materials needed for construction are a pair of 4 in. PM speakers, a suitable length of lamp cord or two conductor bell wire, and two voice coil to 500 ohm line speaker transformers. However, before even buying the line transformers, try the speakers connected *direct* to the line. You may not need the transformers. Since this system depends upon speakers with strong magnetic fields, use a pair of PM units with the largest size magnets you can buy. Standard PM speakers are available with a choice of magnet power ranging

Left, cigar box with 4½ in. hole cut in bottom, then covered with leatherette, makes neat cabinet. Above, pair of 4 in. PM speakers and two line transformers make up this interphone.

from 0.68 to 1.47 ounces or more. The heavier the speaker magnet, the more volume you can expect from this interphone. Buy the *best!*

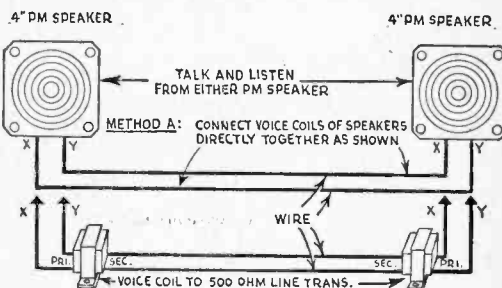Each speaker is mounted in a small cabinet which may be a metal speaker box such as those sold by radio supply houses. Or this box can be home made (see photo). A pair of terminals at the bottom allow for easy connection to the line.—T. A. BLANCHARD.




METHOD B: INSTALL LINE TRANSFORMERS BETWEEN SPEAKERS

MATERIALS LIST SOUND-POWERED INTERPHONE

- 2 PM Radio Loudspeakers, 4 in. dia. Quam type 4A15, with 1.47 oz., #5 Alnico, 3-4 ohm voice coil
- 2 Line Transformers; Thordarson type 22S80 universal line-to-voice coil. 500 ohm primary and 3.2 to 4 ohm secondary connections
- 2 Commercial or homemade speaker cabinets
- 4 Terminal clips, or binding posts
- 8 Speaker mtg. screws (6-32 x ½ in.)
- 1 Suitable length of transmission line (#18POS) lamp cord)

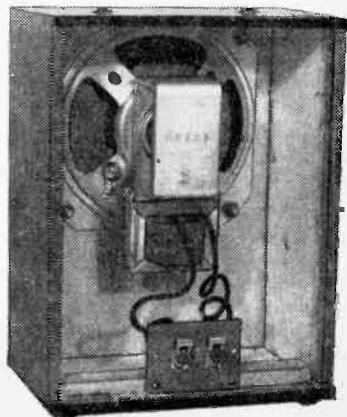Note in rear view (right) that cabinet contains nothing but speaker, transformer, and line terminals or clips.




The Making and Testing of Magnets

WHILE a simple magnet can be made by stroking a permanent magnet along a piece of hardened steel (as is demonstrated whenever someone makes a simple magnetic compass), stronger magnets are made by other methods. One often used method is to provide a coil into which the piece of hardened steel to be magnetized is placed. Then a source of d-c current is applied to the coil. The magnetic field surrounding the coil induces a strong magnetism in the piece, with a North pole at one end and a South pole at the other. Soft iron or steel will retain but very little permanent magnetism so hardened steel must be used.

To demonstrate this, make a paper cylinder by wrapping a piece of heavy paper about 2 in. wide over a 1/2-in. hardwood dowel, making about four or more turns around the dowel (Fig. 1A), and then fasten the edge down with transparent tape. Over this tube (with the dowel in place to keep it in shape), wind 200 turns of #24 enameled magnet wire, carrying it back and forth across the tube to make a uniform winding. Then remove the dowel after you have secured the end of the wire with some tape.

We now have a coil that will magnetize small hardened steel pieces or tools which will fit in the tube diameter. The source of power can be four dry cells connected in series to get 6 volts. Clean the ends of the wire down to the copper with fine sandpaper or by scraping. Then connect a wire from one side of the battery to one end of the coil. Provide a wire from the other side of the battery to go to the other end of the coil

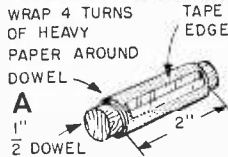


1


as a momentary contact switch. For a test piece, use a tap or a twist drill, which are always hardened steel. Place the tap in the coil and make two or three short contacts from the battery to the coil. Now remove the tap and you will find it so strongly magnetized it will pick up a screwdriver blade or other small tool from the bench as illustrated in Fig. 2. If you hold each end of the magnetized piece near a pocket compass, (Fig. 2A), you will find that one end is North and the other South.

Now suppose that you want to demagnetize this tool, which you would want to do before using it again for tapping threads. Connect a 6.3 volt filament transformer to the line with clip leads and from its secondary, connect two leads to go to the coil. Place the magnetized piece within the coil and, during a few seconds, make two or three short applications of this a-c power. Then, while the coil is still connected to the transformer, slowly withdraw the tool (Fig. 3). A test will show that the magnetism is gone. The alternating current by its constant and rapid reversals tends to knock out magnetism. This is the principle used with demagnetizers.

Alternating current can also be used for magnetizing, but not so satisfactorily as d-c from a battery or other power supply. To prove this, place the tap back in the coil and then make two or more short applications of power from the transformer to the coil. Then, with the power off, remove the piece. Unless you happened to interrupt the current at the zero point of its a-c cycle, some magnetism will be induced in the piece. If the point of cutoff happened to be at the maximum point or peak of the cycle, the induced magnetism will probably be as strong as that from the battery power.

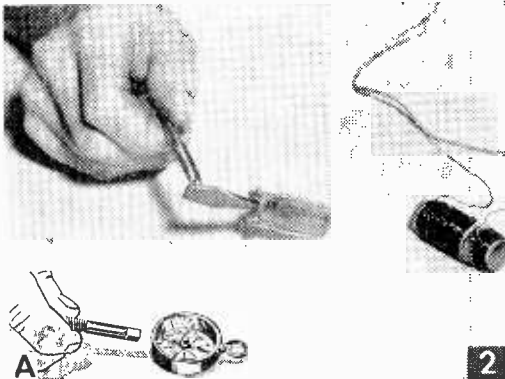Demonstrating a Solenoid. The principles of a solenoid can be demonstrated with this same coil. Solenoids are used in many types of control equipment for operating valves, plungers and



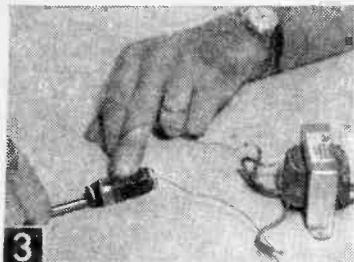

others too numerous to mention. When a source of either a-c or d-c is applied to a coil such as we have made, the tendency is to cause a piece of iron or steel to be suddenly drawn into the coil, until it is magnetically centered. Try connecting the battery to the coil with one lead open for a switch and place a short piece of iron, such as that cut off from a 1/4-in. bolt, so it just enters one end of the coil. Tape coil to the bench so that maximum pull can be observed.





Now you can make the battery contact (Fig. 4) and the piece will snap in to a point beyond the other end and then will come to rest centered in the coil.

This shows the principles of a d-c solenoid. Parts to be operated, like opening or closing a valve, are connected to the plunger and can thus be operated by

remote control. Alternating current can also be used for a solenoid as you can demonstrate by connecting the filament transformer to the coil and repeating the experiment. However, a-c solenoids usually employ laminated cores if they are to be used to any extent. This is because the a-c develops eddy currents in the core and this causes excessive heating. Laminating breaks up these eddy currents which results in the core running cooler.—H.P.S.

Power-Line Antenna for Crystal Set

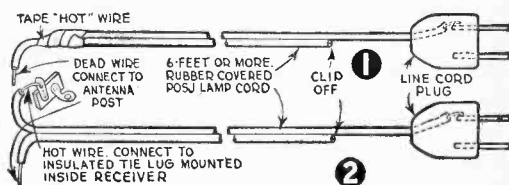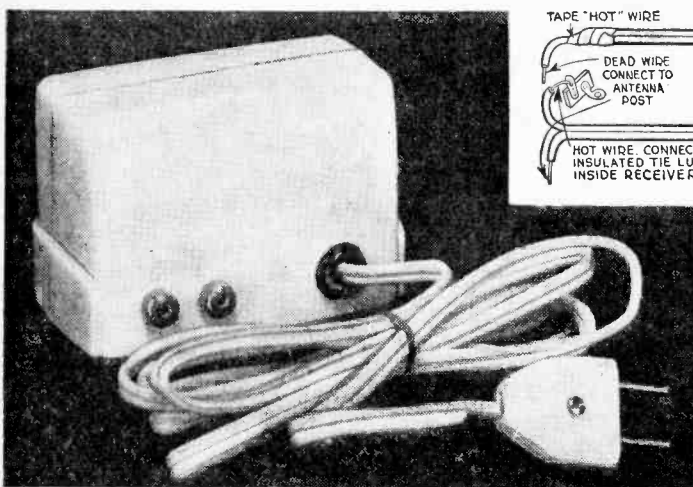

lines but ac current is blocked and cannot enter the receiver. Clip off the dead wire so it cannot enter plug, and thoroughly cover live wire on receiver end with tape.

An alternate method is to connect the hot wire to an insulated tie lug mounted inside receiver (Fig. 2). This makes an efficient antenna for crystal sets and allows the set to be used in any room of the house

HERE'S a simple and efficient power-line antenna for use with a crystal set that will bring in stations from near and far and requires no conventional blocking capacitor. It does away with the antenna nuisance, allows the set to be used in any room of the house, and makes it look like a real midget ac table model but draws no current.

A 6 ft. length of POSJ lamp cord and a plug are all you need. Connect one side of lamp cord to one prong of plug (Fig. 1), but allow other side of cord to remain free. Thus the dead wire is capacitively coupled to the "hot" wire and no conventional capacitor is needed. When the dead wire is connected to the antenna post on a receiver, it picks up r.f. energy from the power-

lines simply by "plugging in." This antenna will work on other sets but the noise picked up from the power-lines will be annoying. The longer the cord, the greater the amount of r.f. picked up from the power-lines. On the crystal set, a 6 ft. length of cord brings in local stations with good volume without a ground connection. When using a bed spring as a counterpoise in addition to the 6 ft. line cord, local stations have worked a magnetic speaker and distant stations have been received in the earphones after the local transmitters have signed off for the night. For the best results, reverse the line cord plug in the wall socket for maximum signal pick-up. In some cases this results in a decided change in volume.—ARTHUR TRAUFFER.



Electronics consultant Tannenbaum working with the set-up he used to monitor signals from both of the first two Russian Sputnik satellites. Fig. 5 lists the instruments used.

Reading the First Sputniks

An Historical Report

By JEROME TANNENBAUM
Electronics Consultant

as told to DON DINWIDDIE

I HAD BEEN at the lab for more than an hour, the Hammarlund Super-Pro tuned carefully to 20.005 megacycles.

Earlier in the evening, Moscow radio had announced that the first man-made earth satellite had been successfully launched. Many remained skeptical. It was not until 11 pm (C.D.T.) that the Chicago papers published the frequencies on which the first Sputnik was transmitting.

Of course, I had returned to the lab immediately and warmed up my equipment.

During that hour of waiting, only the usual crackling of cosmic, atmospheric and man-made line noises came from the speaker, slight


overtones above the slam of a distant door and the occasional creaking noises one hears in a silent office building at night. I was tempted to go home.

But then, at exactly 12:03, Saturday, Oct. 5, 1957, it was there—something was coming through.


I dove across the lab, turned all gains up full and there it was, sounding clearly—the now familiar da-da-da-da sound from outer space.

The signal stayed in that time for 13 minutes, driving the "S" (signal strength) meter on the receiver up to S9, indicating extremely strong signals. I carefully logged the exact starting and ending times of the reception and other observations. In this brief 13-minute period, Sputnik I had traveled about 2,200 miles.

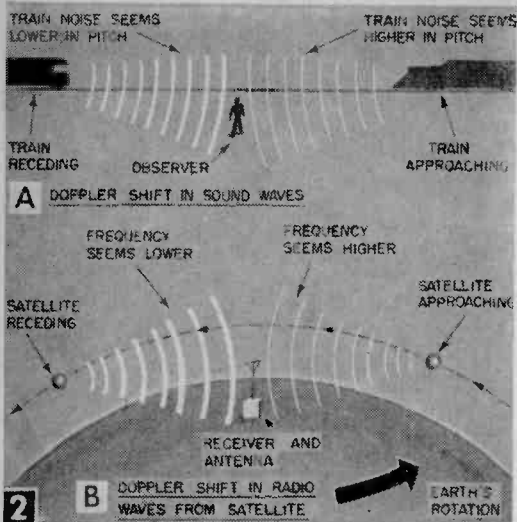Again, at 1:45 am, it came 'round again. This time it was in for only 5 minutes and its received strength was only S7 (moderately strong signals). In the next three days, Sputnik I was logged in my lab 24 times. Its strength varied from S3 to S9 and the duration of the observations varied from those as short as 1½ minutes



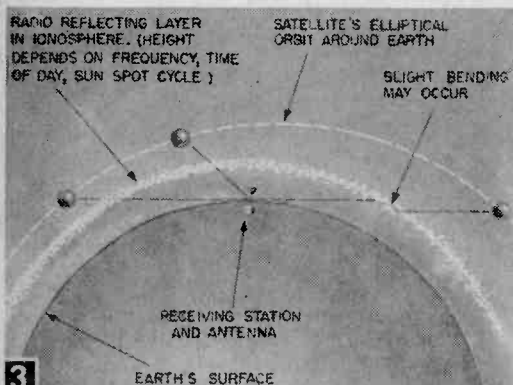Doppler shift occurs when a source of radiation is in motion with respect to an observer. It shows up as a shift in frequency.



3 Line-of-Sight Reception. Satellite is near or above the horizon of receiving antenna. Signals come in sharply and go out sharply and are much stronger when in. No echoes or fading.

to one which was 45 minutes long.

What Sputnik I Sounded Like. For the first four days the keying of the transmitter in Sputnik I was fairly consistent. When the satellite radio was in, you could hear a succession of long dots giving a da-da-da-da sound. Each dot was about one-third of a second long and the intervals between dots was about one-third of a second. There were also small but distinct frequency changes, detected as small shifts in the tone of the audio signal.

After the first few days, the keying motor or keying relay in Sputnik I failed. From then on, its signals were received as a continuous tone, no dots but still with the frequency shifts mentioned above. After Sputnik I had been up for three weeks, its radio transmissions failed completely.

Sputnik II Signals Similar. In the wee hours of Sunday morning, November 4, a local reporter called to say that Sputnik II had been launched.


Fifteen minutes later, we were at our lab, eagerly listening. At 5:08 am. C.S.T., Sputnik II announced itself on 20.005 megacycles. Here were the same da-da-da-da sounds, very similar to Sputnik I. By 9 am of that exciting morning, it had been heard distinctly four times.

Sputnik II's signals on 20 mc started as a keyed signal. There seemed to be times, however, when the transmitter gave out a continuous tone. There were other times when the signal shut off for long periods, perhaps to conserve battery life. Or Sputnik II, as it passed Russia, may have received a signal from the ground instructing the satellite to play its tape recorded information on the physical condition of the dog, Laika, within it, and the readings of other instruments.

The Sputnik II's 40-megacycle signals seemed to be more consistent, being heard only as a continuous tone without any keying.

Doppler Shift. A clear Doppler shift was also heard at various times on both Sputniks' signals. Doppler shift occurs when either a source of radiation or an observer is moving with respect to the other (Fig. 2). For example, if you are standing still by a railroad track, as a train moves toward you the noise it radiates will seem to become higher in pitch; as the train moves away from you the sound will seem to become lower in pitch, even though the train is moving at constant speed and emitting a constant noise. This happens because the speed of the train, as it approaches the hearer, imparts additional "compression" between successive sound waves, giving the effect of raising the frequency. The opposite effect obtains when a train is moving away.

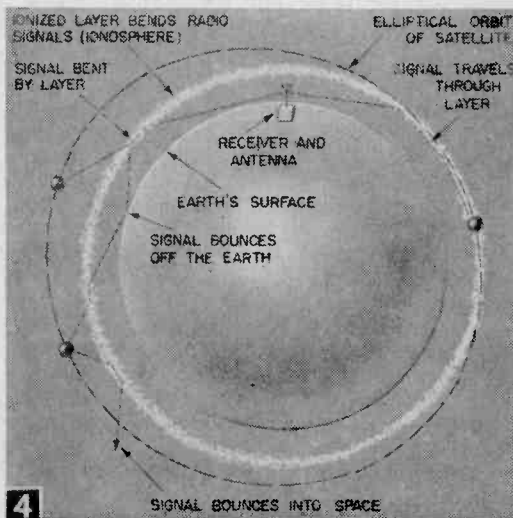Doppler shift on light waves is used in astronomy to measure whether distant stars are moving nearer or farther away from our Solar System. It has rarely been observed on radio waves.




Sky-Wave Reception. Satellite is below the horizon. Signals are bent by ionized layer in upper atmosphere. Signals are weaker, have echoes, fading and flutter. Transmitter may be great distance away.

A Sputnik's speed of about 5 miles per second (*mps*) is a measurable part of the speed of radio waves, 186,000 *mps*. Doppler shift was heard as a higher average frequency as the satellite approached and a lower average frequency as it moved away from the antenna. The maximum shift observed here due to this effect, was about 800 cycles per second.

Radio Propagation. Not only were these satellites describing their positions, orbits and speeds, their radio transmissions were a mine of information on radio conditions. An earth satellite presents an extraordinary vantage point. If it is more than about 150 miles up, it is actually on the outside of the layers in the upper atmosphere which usually reflect and bend radio signals from the earth's surface. Radio propagation, the manner in which radio waves travel through the atmosphere, is normally studied by earth-bound transmitters and receivers. Here we had a speeding probe, high above the radio reflecting layers, whose position could be accurately plotted.

On the 20 megacycle signals from both Sputniks, two types of propagation could be clearly observed. The first, called *Line-of-sight* reception, occurs when the transmitter is above the horizon at the receiving antenna (Fig. 3). *Line-of-sight* reception appeared on about a 97-minute schedule for Sputnik I and a 104-minute schedule for Sputnik II. The transmissions on these schedules were strongest and came in and went out with some sharpness.

The second type of reception, called *Sky Wave*, is described in Fig. 4. *Sky-wave* reception occurs when the transmitter is well below the horizon and its waves are bent by the radio refracting layers of the upper atmosphere. This type of reception was very much weaker and marked by echos, fading and flutter, and came in at irregular times. It was common on 20 *mc* signals, rarer on 40 *mc* signals. The result of checking these sky-wave observations against the known positions of the satellites should soon provide us with new information on the properties of the radio mirrors in the atmosphere.

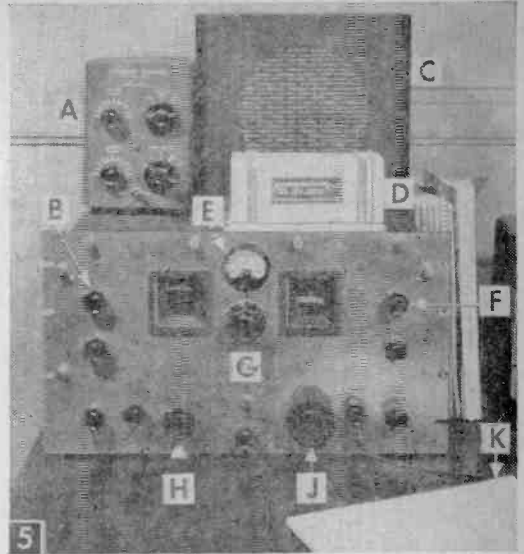

(A) Frequency standard checked against WWV; (B) selectivity control set fairly sharp but not too sharp; (C) speaker; (D) 24-hour clock set to GMT; (E) "S" meter; (F) beat oscillator turned on; (G) Hammarlund SP 300 communications receiver; (H) main tuning; (J) fine tuning or band spread; (K) log.

Close-up of the equipment the author used to monitor signals from the Russian satellites.

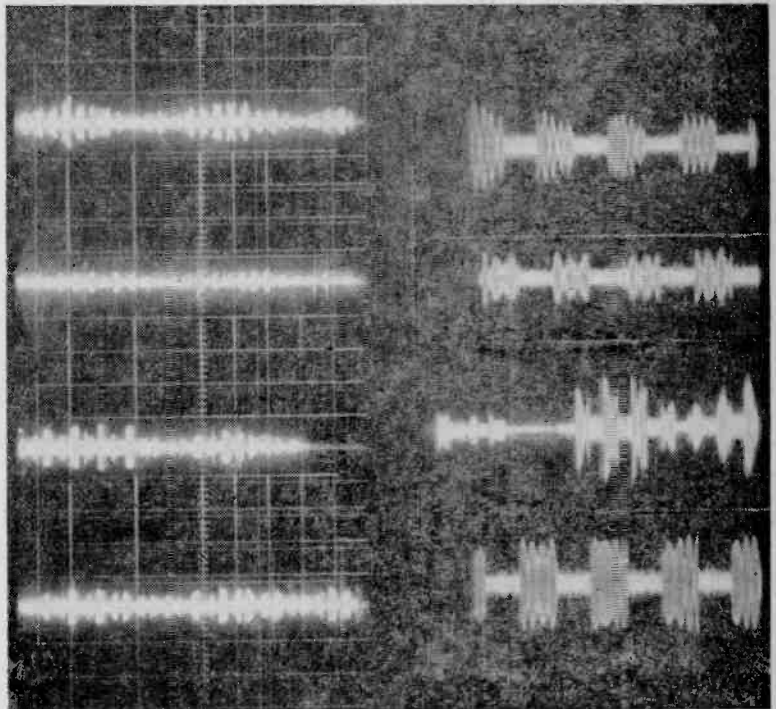


Photo courtesy Sky and Telescope magazine.

These photos of the screen of an oscilloscope fed by a short-wave receiver, show 20,005 megacycle pulses from the Russian satellite. They were made during the night of Oct. 5, 1957, one day after the satellite launching. Different pulse patterns may indicate actual telemetering or the effects of atmospheric interference. Photos were made by Robert Slavin and G. R. Miczalka, Geophysics Research Directorate, Air Force Cambridge Research Center, Bedford, Mass.

How to Align Superhet Circuits



Signal Generator output cable connects to radio antenna and ground. A plastic blade screwdriver is only tool needed.

Because of the precise fixed-tuning required by transistor and tube-type frequency conversion circuits, a signal generator is a vital tool. Here's how you can understand and use these now reasonably priced instruments

By THOMAS A. BLANCHARD

IN MANY tube and transistor radio projects described in past issues of the *Radio-TV Experimenter*, the reader has been advised to have superheterodyne sets, after completion, aligned by a local service organization to insure proper reception. The essential instrument for superhet alignment is a signal generator, and in the past such generators have been quite expensive—even when capable of tuning only the broadcast band. Recently, however, modern manufacturing methods have made possible reasonably priced signal generators that tune from a low 120 kc to an ultra-high 260 mc so that anything from a communications receiver with a 132 kc intermediate frequency to ultra-high TV or mobile equipment can be aligned as conveniently as a regular broadcast radio with a standard 455 kc IF.


The signal generator is, in effect, a min-


Adjustment points on typical small superhet radio. Foreground shows three types of IF transformers, at far right is a typical local oscillator coil. Screwdrivers are made of plastic crochet needles.

ature broadcasting station with a band selector switch to cut in the oscillator coil that will cover the desired frequency range. The oscillator is tuned with a dial calibrated in kilocycles and megacycles in six frequency bands. In addition, a 190° Log in 1° increments is included for quick reference to a precise adjustment of a dial reading.

Tuned-radio-frequency type circuits require separate variable tuning for each stage of amplification, are deficient on gain, sensitivity, selectivity, and require more components than a superhet of equal efficiency. A typical modern three-tube table superhet (plus rectifier) greatly excels in performance a five-tube (plus rectifier) TRF set. It follows that it is cheaper to align a frequency conversion (superhet) circuit, than to build the TRF set.

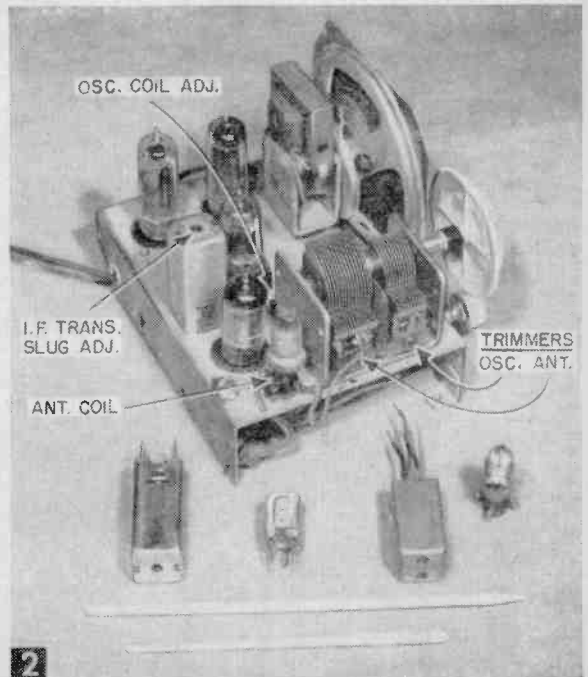Successful operation of a superheterodyne tube or transistor circuit requires that the set builder feed certain specific signals into the receiver so that its IF transformers can be tuned to 455 kc for the conventional broadcast band set, or to whatever frequency the maker of the FM, TV or communications receiver has designated. Television set IF's may be as low as 4.5 mc and as high as 47.25 mc.



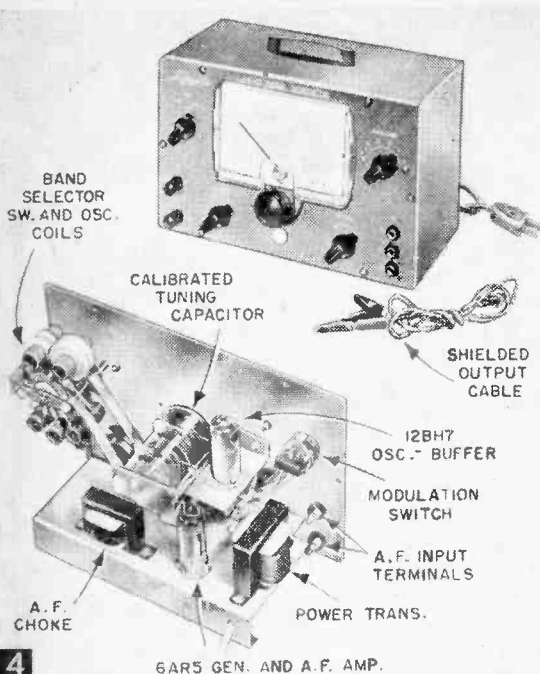

4

6AR5 GEN. AND A.F. AMP.

External and internal details of the Lafayette LSG-10 Signal Generator. Unit weighs 6 lbs.

of world-wide shortwave stations and their frequencies. Except for costly sets, however, the calibrations on the tuning dial of a receiver are not very accurate. (And of course, those of you with homemade receivers seldom have any choice but to "fish" for stations.) With the signal generator, however, you simply set the band switch to the proper range, turn the calibrated dial to the frequency of the foreign station and attach the generator's output cable to the set's antenna and ground. Then tune the set until the signal generator's 400-cycle tone is heard and you are tuned to the desired frequency. After making a note of the dial position for future reference, disconnect the generator from set.

Construction of a signal generator from "scratch" or kit is not usually practical for several reasons. The homemade instrument poses the problem of obtaining the proper set of oscillator coils, suitable chassis, cabinet and calibrated dial. Now, while these items would be in-

cluded with a kit, its calibration after assembly would still be in doubt and a heterodyne frequency meter would be needed to check out its accuracy.

Since every experimenter is interested to know "what makes it tick," Lafayette Radio of Jamaica, N. Y., authorized our use of their Model LSG-10 Signal Generator specifications. This instrument (Fig. 4) is extremely light and compact, measuring only $4\frac{3}{8} \times 6 \times 10$ in. Its circuit (see Fig. 3) is divided into two sections. The radio frequency end employs a miniature 12BH7 twin-triode tube which functions as a combined RF oscillator and buffer. One triode section serves as a Colpitts oscillator, the other as the buffer stage. The RF Fine control, plus both a high- and low-output jack provide continuously variable attenuation of the output voltage. The audio section of the generator employs a miniature 6AR5 power-pentode tube. By means of a selector switch, the tube performs two functions. The switch in the first position couples the 6AR5 to a built-in 400-cycle tone generator which provides the ideal "beep" for accurate set calibration.

Turning the modulation switch hooks the 6AR5 up as an audio amplifier to feed into the Colpitts oscillator. It is now possible to attach any AF device (such as a radio tuner, phono crystal pickup, etc.) to the left-hand terminals on the panel so that the signal generator works much like the popular, wireless record player devices.


Although the LSG-10 sells for only \$22.50, its direct scale readings over all ranges from 120 kc to 260 mc are accurate within 2%. Even greater accuracy (though seldom needed in radio work) can be obtained by using the seventh Log scale calibrated accordingly.

While neither space nor necessity allows it here, the experimenter will find it to his advantage to familiarize himself with the theory and operation of superheterodyne circuits. Two excellent textbooks are available at public libraries: *Radio Physics* by Alfred A. Ghirardi, E.E. (Radio-Technical Publishing Co., 45 Astor Plaza, N.Y.C.) and *Radiotron Handbook* by F. Langford Smith, B.Sc., B.E. (RCA Commercial Engineering Div., Harrison, N. J.).

Burn Off Stubborn Insulation

• Ever experience difficulty skinning the insulation from electric wires and cables? Some types of wire insulation are very difficult to remove (for example, the inside cotton threads found in most ordinary rubber-covered lamp cords). When the wire strands are twisted together, the threads tend to get in the way by twisting up among the wire strands. An easy way to remove such stubborn insulation is to burn it away. Sim-

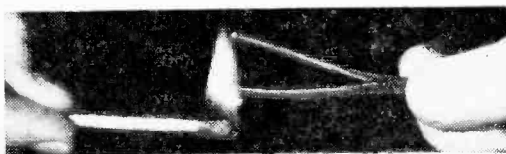
ply hold the frayed ends of the cord in the flame of a lighter or match, and then scrape away the charred insulation with a jack-knife.—JOHN A. COMSTOCK.



Small Fry Crystal Set



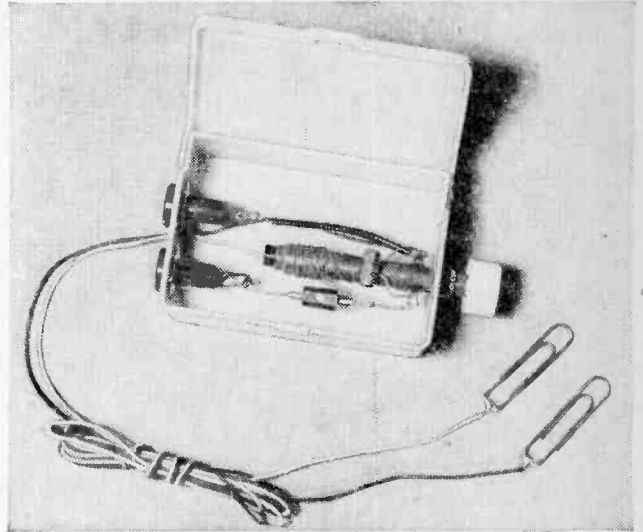
Single Alnico 2000-ohm phone may do but double headphone set of regular magnetic type gives better volume.




Although the case is tiny, there is no cramping of parts in it.

THIS extremely simple, yet highly selective, crystal set would delight any youngster (not to mention those of us oldsters who still are amazed by these tubeless, powerless receivers).

This set is housed in a $1\frac{1}{4} \times 2 \times 3\frac{3}{8}$ -in. plastic pin or jewel box. Two $\frac{3}{8}$ -in. holes are reamed in one end of the box with a rat-tail file and plastic phone jacks inserted. Just below these holes is a $\frac{1}{8}$ -in. hole through which the antenna and ground leads pass. These flexible insulated wires have "frictioned" paper clips soldered to the ends for connecting set to antenna. The finger stop on a dial phone is an ideal antenna. Ground is not needed except

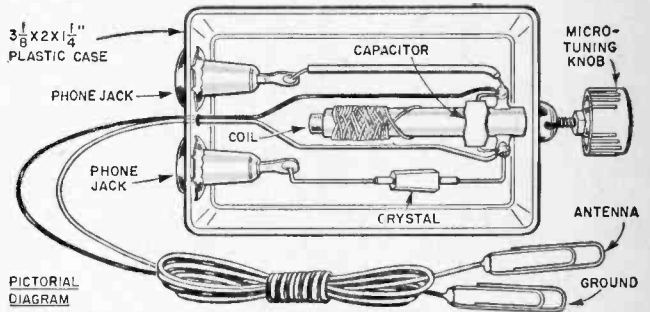

PICTORIAL DIAGRAM

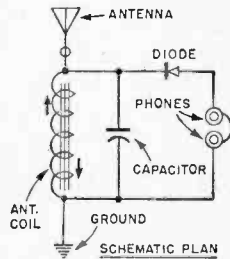

SCHEMATIC PLAN

in outlying areas.

Ream a $\frac{3}{16}$ -in. hole in the opposite end of the plastic box and, into this hole, snap a micro-tuning type ferrite antenna coil. Then attach a 4-40 threaded plastic knob to the coil screw, providing precision tuning that will not drift once set to a particular station. As most U.S. and Canadian stations are located below 1200 kc, a 150-mmf ceramic capacitor is connected across the coil lugs to tune from 1600 to 1200 kc. In large city areas where the powerful stations (with some exceptions) are between 1200 and 550 kc, use a 250-mmf ceramic capacitor. But with no capacitor, the set will often pick up amateur, police and fire signals. The detector employed in this rugged pocket set is a germanium type IN81.

Good reception and volume depend upon sensitive headphones, so use conventional magnetic or Alnico double headphones with a resistance of 2000 ohms or more for best results.—T. A. BLANCHARD.

MATERIALS LIST—SMALL FRY CRYSTAL SET

- 1 plastic box. Original measured $1\frac{1}{4} \times 2 \times 3\frac{3}{8}$ in.
- 1 IN81 germanium type crystal detector
- 1 150-mmf (or 250-mmf—see text) ceramic capacitor
- 1 micro-tuning type ferrite antenna coil
- 1 4-40 threaded plastic knob
- 1 magnetic or Alnico single or double headphones, 2,000 ohms or higher

Flexible insulated antenna and ground lead wires, and two paper clips

Note: Complete kit for building this set, including plastic case, coil, knob, germanium detector, 2 ceramic capacitors, jacks, hookup wire and clips (but not headphones) may be obtained from Electro-Mite, P. O. Box 636, Springdale, Conn., for \$2.98 postpaid. Double set headphones are available at \$2.25 postpaid.



If you have outgrown your present station, but carry a thin wallet, this low-power, amateur radiotelegraph station is for you. Designed to perform, it has unprecedented advantages for long-range communication.

The Isotron

Operating in the 21-megacycle—Fifteen-Meter—band, this effective and different low-power, amateur station has world-wide range

By C. F. ROCKEY, W9SCH/W9EDC

NO EXPENSIVE, special tubes or components are required to build this transceiver, and its total cost is less than that of a medium-priced communication receiver alone. Yet in less than two weeks of operation with it, I contacted all parts of the U.S.A. (from Chicago), as well as many locations in Europe, using only a simple dipole antenna.


In both transmitter and receiver, this unit employs controlled positive feedback and the superheterodyne principle. Its name, "Isotron," arises from the fact that *transmission and reception occur on the same frequency* and are controlled by the same tuning dial. This feature greatly increases the chance of being heard, since after a CQ call amateurs customarily listen for answers on their own frequency first. Not only this,


but the operator is automatically prevented from off-frequency operation, since the transmitting frequency can be checked in the "Receive" position provided the receiver is properly calibrated.

Operation. A variable frequency oscillator (see Fig. 2) is tuned to, let us say, 12.5 megacycles. Its signal is fed into a power mixer, along with the output of a crystal controlled oscillator on 8.5 megacycles. The power mixer adds and amplifies these two signals electronically to produce a signal of 21 megacycles (in the amateur band). This 21-megacycle signal is amplified further in the driver, and finally by the power amplifier, which feeds the antenna.


When receiving, the crystal oscillator is normally inoperative, but the VFO feeds its 12.5 megacycle signal into the first detector, which is also receiving the incoming signal on 21 megacycles. These are electronically subtracted, producing an output signal of 8.5 megacycles. The regenerative second detector then produces an audible signal which after amplification, is fed into the headphones.

As long as the second detector is tuned exactly to the crystal frequency of 8.5 megacycles, transmission and reception frequencies are identical, and remain so across the whole band. To definitely establish that this is the case, you simply press the push button while the Send-Receiver switch is in its receiving position. This will feed a small voltage to the crystal oscillator, causing it to produce enough signal to reach the second detector. Transmission and reception frequencies may then be synchronized.

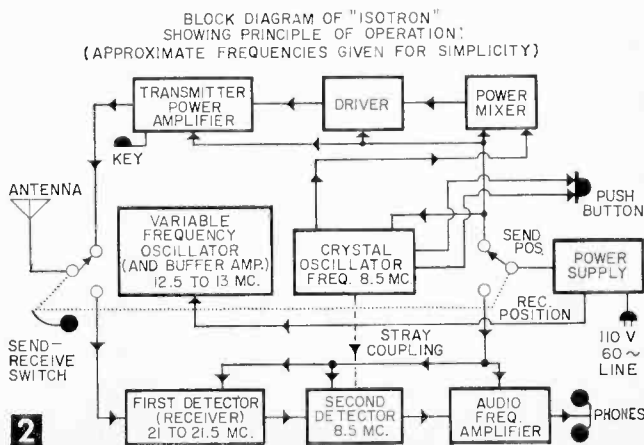

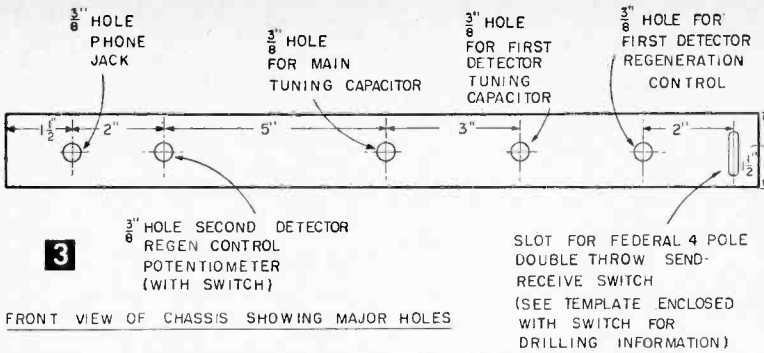

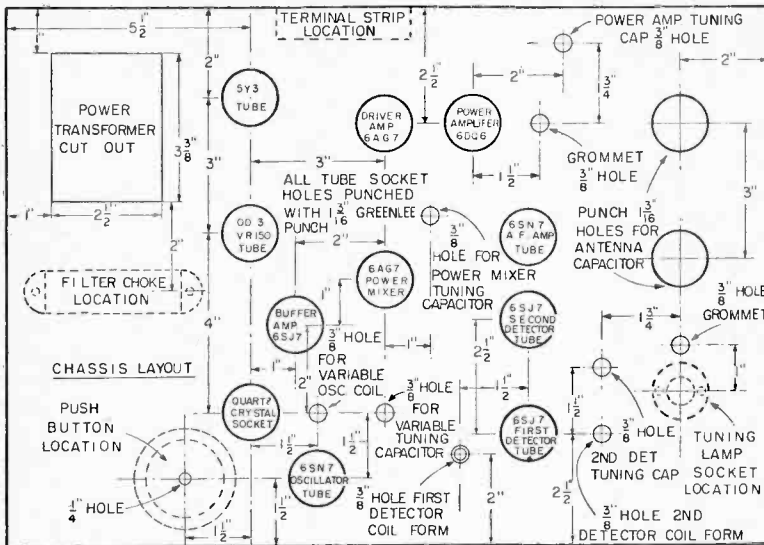FRONT VIEW OF CHASSIS SHOWING MAJOR HOLES



Entirely free from hand-capacity and "crankiness," the receiver produces a stable signal which will remain tuned-in for hours. In fact it outperforms a number of commercially-built receivers in this respect, and will hold a critical single-sideband signal—a real test of stability. The sensitivity is more than adequate; European and African stations have been regularly audible several feet from the headphones both on code and radiophone.

The transmitter produces sufficient output to provide regular communication with foreign stations (Europe and Africa) when a good antenna is used. Signal output is "clean" and meets Federal regulations for the general-class license in every respect. A *general*, or higher-class, amateur license is required before this station may be legally used in the U.S.A. The Novice or Technician class license is not adequate.

Construction. Begin by cutting out the power transformer hole in the rear left-hand corner of the chassis (Fig. 3) using either a "nibbling tool," or by drilling a number of 1/8-in. holes around the outline. Then punch out all the socket holes shown in Fig. 3, using a 1 1/16-in. socket punch. Next, drill holes for mounting tuning controls.

Now mount sockets, using 6-32 machine screws

and nuts. Fasten insulated tie-lugs under appropriate socket-mounting nuts as shown in Fig. 5. When all sockets have been mounted, screwfasten the terminal strip at the rear of the chassis and drill the wire-through holes for it, being careful to remove burrs on these holes lest they damage the insulation of the wiring.

Mount the filter choke on the top of the chassis, using 6-32 screws and nuts, and drill a 1/4-in. hole between it and the power transformer through which to pass its leads, and mount the power transformer. Then mount the *second detector* regeneration control potentiometer, (the pot with the switch) and begin wiring.


Wire the power-supply first (see Fig. 6), beginning with the 120-v primary circuit. When this is completed, connect the leads from the transformer to the 5Y3 rectifier socket, and proceed with the filter circuit.

The 20 mfd filter capacitors are suspended by their leads from suitably-placed insulated tie lugs—use the unused lugs on the OD3 regulator tube socket for mounting the 6000-ohm voltage-dropping, wire-wound resistor. (Do not use pins 3 or 7.)

Connect a line-cord to the line terminals on the terminal strip and turn on the switch. The filaments of the 5Y3G tube should glow, and so should the OD-3 voltage regulator tube. A dc voltmeter connected across the output of the second filter capacitor should indicate about 350 v, give or take 30, and the voltage across the OD-3 tube should be approximately 150.

When the power supply is operating correctly, disconnect power cord and then connect B+ to the proper point on the Send-Receive switch as shown in Fig. 6.

Transmitter. When building this project, it is more convenient to complete the transmitter before the receiver (to make sure the oscillator frequency relationships are correct). The receiver is then completed and "tracked along" with the transmitter. Therefore, when the power supply is completed, begin wiring the variable frequency oscillator. First, carefully remove one of the rotor plates from the rear of the 15 mmf Bud MC1850

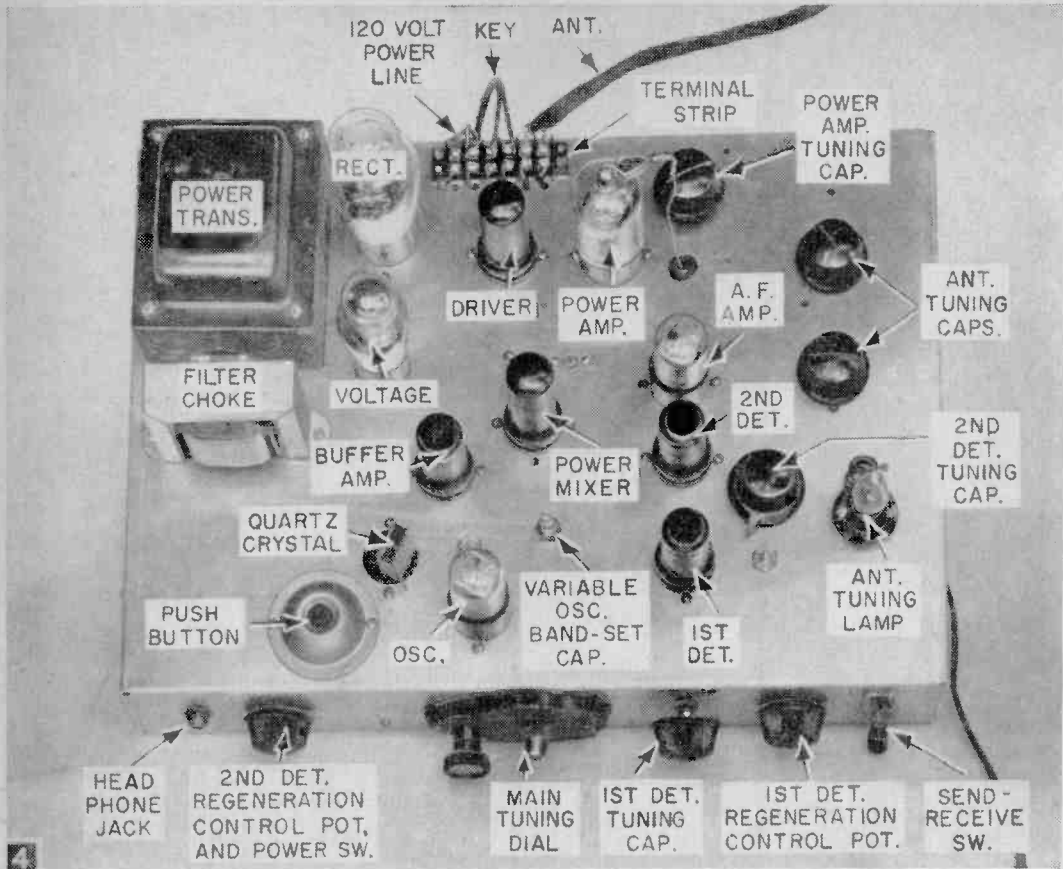

Top-chassis view of completed set.

variable capacitor. This will enable this capacitor to provide much better band spread than would otherwise be the case. When the capacitor has been altered, check that the plates do not rub as the capacitor is rotated. Then mount it, along with the vernier tuning dial, on front-center of the chassis.

Next, wind the VFO coil (see Fig. 10). (Hold the turns in place with coil dope.) Mount it and the 100 mmf "band-set" capacitor and begin the wiring as detailed in Fig. 7.

One side of the heater of all tubes used except the 5Y3 is pin No. 7. Run a wire between all No. 7 pins and connect it to one side of the 6.3 v heater winding of the power transformer. The other side of each heater (and the transformer winding) is grounded. Bypass heater pins No. 7 to ground with .005 mfd capacitors on the oscillator's 6SN7, 6AG7 and 6SJ7 tubes and on the transmitter's 6DQ6 and 6AG7 (see schematic Figs. 7 and 8).

Arrange RF leads of the VFO so that they do not flop around and spoil the oscillator's stability, and when wiring is completed, insert the 6SN7 tube and test this circuit for oscillation by holding a grid-dip-meter coil (your own, or borrowed) near the oscillator coil. A definite indi-

cation of oscillation should be obtained. If not, wiring or the tube is defective.


VFO range depends upon the frequency of the quartz crystal you have purchased. If your crystal has a frequency of 8450 kilocycles, as recommended, the band-set capacitor should be adjusted (by use of the grid-dip meter) so that the frequency range of 12.55 to 12.85 megacycles, at least, will be included within the range covered by the main tuning dial. (A somewhat wider tuning range may exist; it is not harmful.) To improve the frequency stability of the oscillator, adjust the slug within the coil so that at least one-half of the capacitance of the band-set capacitor is used; that is, the plates should be enmeshed halfway or further.

In the event a crystal frequency *different* from that recommended is used—there is nothing sacred about the particular frequency recommended, any from 8 to 9 megacycles will do—you can find the VFO tuning range by the following formula:

$$\text{Low-Frequency} = 21000 - (\text{crystal freq. in kc})$$

$$\text{High-Frequency} = 21300 - (\text{crystal freq. in kc})$$

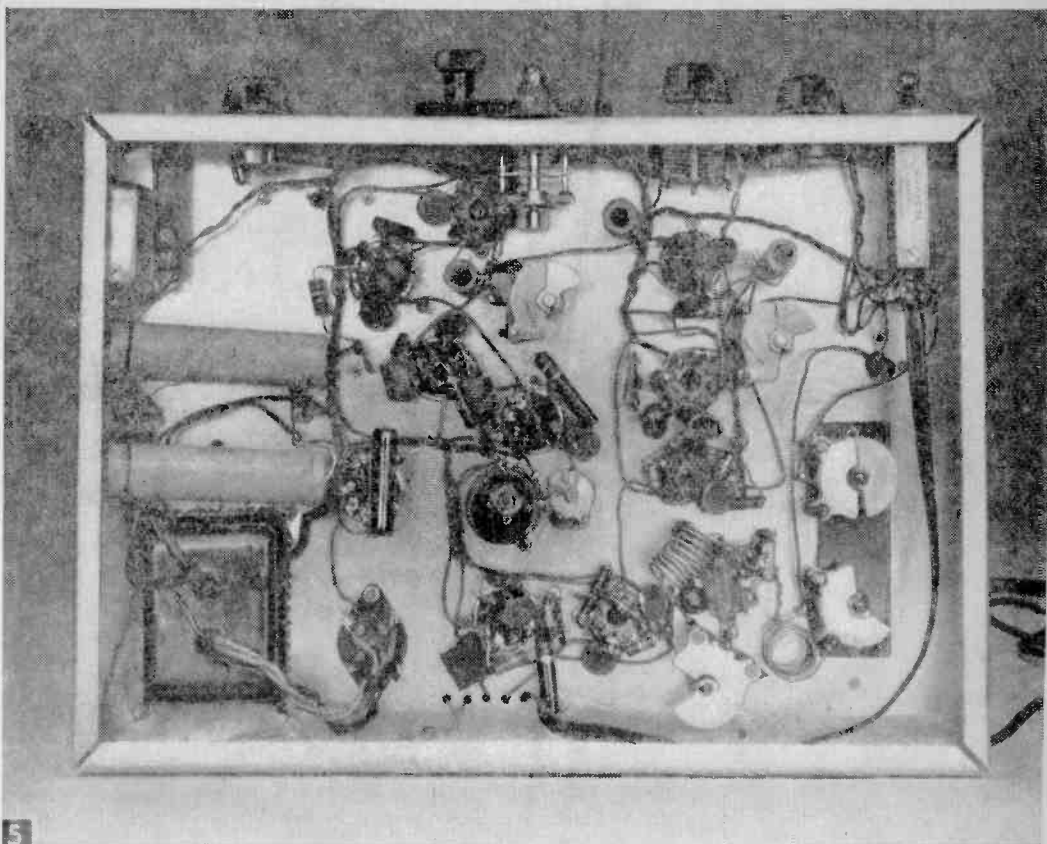This tuning range will cover the radiotelegraph portion of the 21-megacycle amateur band plus a little to spare.



With the VFO completed, wire the crystal oscillator using the other half of the 6SN7 used for the VFO (see Fig. 7). This is a simple Pierce circuit, one of the most vigorous and reliable of oscillators. Test it by holding a neon bulb (glass portion) near the RF choke (set On, of course). The bulb should glow. Remember, when testing, that the Send-Receive switch must be in the Send position so that the crystal oscillator will receive B+ from the power supply.

With the two oscillators operating properly, wire the buffer amplifier (Fig. 7). Be sure to ground pin Nos. 1 and 2 of the buffer amplifier tube socket to complete the heater circuit and ground the metal shield. To test, allow tubes to warm, throw S-R switch to Send position, and look for output within the VFO frequency range by holding the grid-dip meter against the RF choke in the buffer amplifier plate circuit. A small, but definite indication proves the circuit is functioning as it should.


Wind the power mixer coil as indicated in Fig. 10. Mount it on chassis with a machine screw and nut, then mount the APC-50 variable capacitor which tunes the output of the power mixer.

The Isotron's transmitter's power mixer differs from ordinary RF amplifiers only in that its screen grid circuit is *not* bypassed to ground in the customary manner. Instead, the output of

the crystal oscillator is fed into the screen, "screen modulating" it at the crystal frequency, as it were. The signal of the VFO, amplified by the buffer amplifier, is fed into the control-grid of the power mixer.

With wiring completed and checked, insert tubes and apply power. Tune the grid-dip meter to 21 megacycles, and with the S-R switch in Send position, tune the power mixer tuning capacitor for maximum output at this frequency. A neon bulb held against the coil should give a bright pink glow, and a check with the grid-dip meter should indicate output *only* in the vicinity of 21 megacycles. If output is also at the VFO frequency, this is due to mistuning. Proper adjustment of the mixer tuning capacitor will eliminate the condition.

The transmitter driver circuit (see Fig. 8), is known as a "cathode-follower." Similar circuits are widely used in TV and radar. The output is taken from the cathode of the tube instead of the plate which gives a low output impedance for driving the power amplifier. The "2-meter" RF choke in series with the cathode resistor serves as a peaking-coil, increasing the 21-megacycle output. With wiring of the driver stage completed, apply power, and holding a 2-watt neon lamp by the glass envelope (careful!) touch its tip to pin No. 8. If this stage is operating prop-

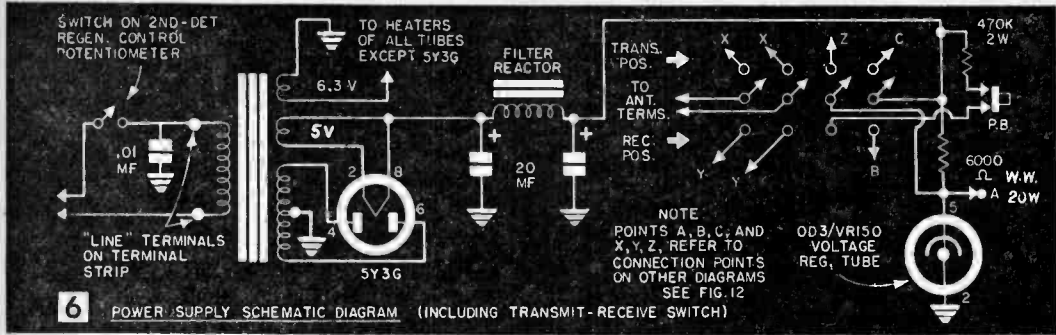

6 POWER SUPPLY SCHEMATIC DIAGRAM (INCLUDING TRANSMIT-RECEIVE SWITCH)


erly, the neon lamp should glow. Try touching up the power mixer tuning for maximum glow at this point. If no glow is observed, check tube and wiring—and make sure S.R. switch is in Send position.

Wiring of the power amplifier finishes the transmitter section. The circuit of this amplifier is standard (see Fig. 8) and practically identical to that used in most modern low-power transmitters. Mount the tuning capacitor, then the .004 mfd mica capacitor, the latter with one lug grounded by screwing it tightly to the chassis with a 6-32 machine screw and nut.


The 47-ohm resistors in series with control-grid and screen-grid effectively suppress those parasitic oscillations which cause instability and interference to neighboring TV receivers. These are connected from the screen and grid terminals to the adjacent unused lugs on the tube socket and are thus firmly anchored in place.

Connect the telegraph key in series with the cathode of the power amplifier, running one lead from the cathode terminal (pin No. 8) to one of the key terminals on the terminal strip. Ground the other key terminal at a convenient point. Drill a hole near the tuning capacitor and insert a rubber grommet to pass the plate lead which connects to the cap on the top of the 6DQ6 tube.

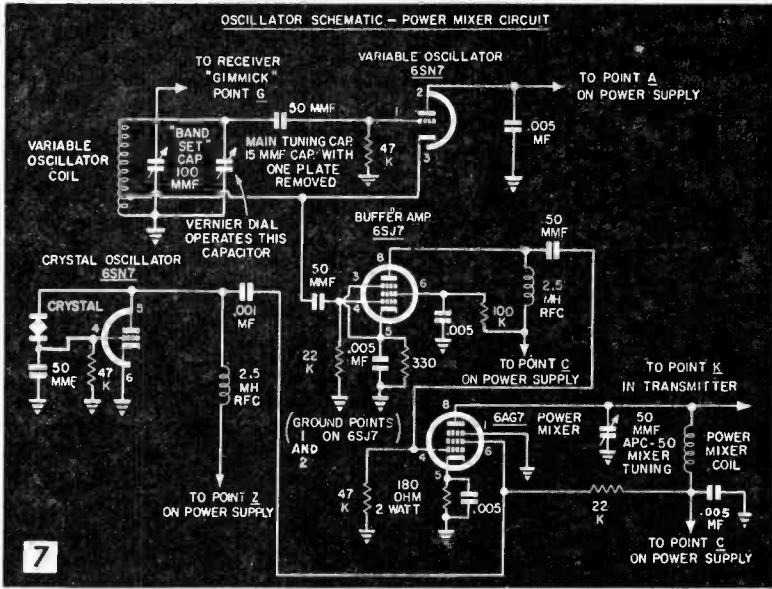The remainder of the wiring is straightforward. Wind the power amplifier coil of No. 14



7

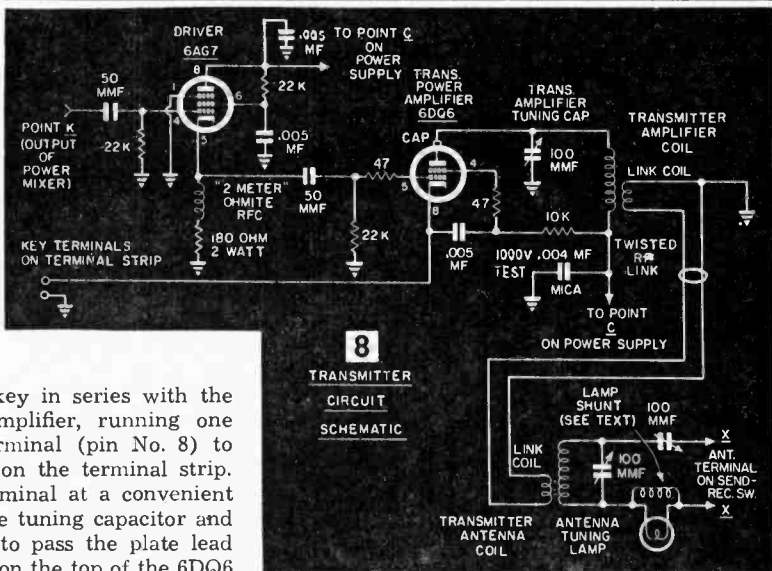

8

tinned copper wire (see Fig. 10) and connect it by short leads to the stator of the tuning capacitor and to the ungrounded end of the .004 mfd

key to its terminals with a length of lamp cord, and connect a 15-watt, 120-v lamp across the antenna terminals with leads as short as convenient. Apply power and throw S-R switch to Send position. When the key is pressed upon adjustment of the antenna tuning capacitors and slight touching up of the power amplifier tuning capacitor, the 15-watt lamp should light nearly as brightly as when screwed into a regular lamp socket on the power line. A slight retouching of the power mixer tuning should provide rated output of about 15 watts.


The final test is to listen to the signal quality on a good communications receiver tuned to the 21-megacycle band. The note should be absolutely clean and free of ripple. Keying should be clean—the slight “key-up” signal is direct radiation from the power mixer and will be inaudible under normal operating conditions.

Any transmitter, even when commercially-built, may cause interference to a poorly designed or improperly installed TV receiver. However, reasonable precautions have been taken to avoid such interference with the Isotron, and no more interference should be caused by it than by any other similar transmitter on the same frequency.


Receiver. Remove all tubes from the partially completed set and begin construction of the receiver by mounting the phone jack, the first-detector regeneration control potentiometer, and the first-detector tuning capacitor on the front of the chassis (see Figs. 3, 4 and 5). Then mount the 1 mfd “bathtub” capacitor adjacent to the second-detector regeneration control.

By wiring the receiver (see Fig. 9) from the headphone jack and working forward it will be possible to test each stage as it is completed. The 6SN7 vacuum tube is used as a two-stage audio amplifier of the simplest type. Wire its second stage first, and when it is completed, insert the rectifier and voltage regulator tubes in the power supply circuit, insert the AF amplifier 6SN7, throw the S-R switch to Receive and plug the phones into their jack. Now touch pin No. 4 of the 6SN7 with a screwdriver. A noticeable click and buzz should be heard in the phones. Next, wire and check the first stage similarly by touching the screwdriver to pin No. 1. A much louder buzz should be heard in the phones with this stage in operation.

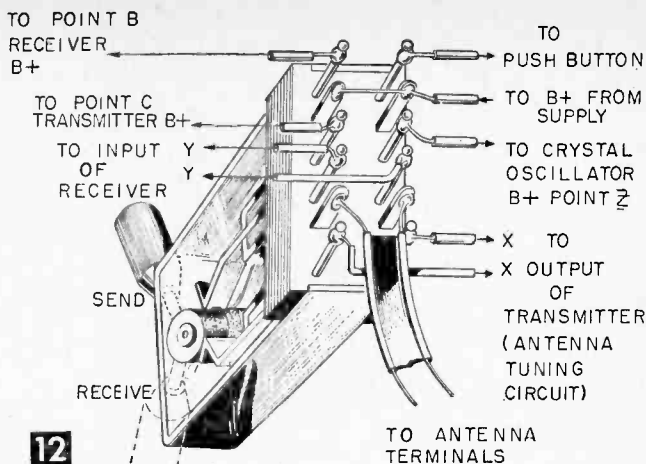Now mount the parts for the second-detector coil on a National XR-50 coil form (see Fig. 10). With coil and second-detector tuning capacitor (100 mmf) mounted, wire the second-detector stage. Keep RF leads short and direct. Note that the second detector (and the VFO) receives its B+ from the VR tube. This insures smoothness and stability in the receiver's operation.



12

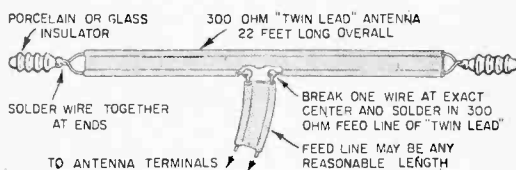

RULES FOR ERECTING ANTENNA


- (1) KEEP IT HORIZONTAL
- (2) KEEP IT BROADSIDE TO THE DIRECTIONS YOU WISH MOST TO WORK
- (3) ERECT IT AS HIGH ABOVE GROUND AS POSSIBLE.

13


With second-detector wiring completed, insert tubes, apply power (S-R switch in Receive position) and plug in phones. Slowly advance the second-detector regeneration control. An increase in noise level and a barely noticeable “plunk” indicates proper oscillation of the second detector. To further test the second detector, bring one end of an outside antenna near the coil and adjust the regeneration control just beyond the oscillation (“plunk”) point. If you live in a reasonably good reception location, rotating the second-detector tuning capacitor should produce a myriad of code and radioteletype signals, especially after dark. This is positive evidence of proper second-detector action. Improper operation usually means improper oscillation which, if wiring and tube are good, is traceable to the coil, which *must* be connected as shown in Fig. 9.

When the second detector is working correctly, wire in the push-button circuit (see Fig. 6) if you have not wired this earlier. Then, with the second detector oscillating, press the push button and rotate the second-detector tuning capacitor until the crystal oscillator signal is at zero beat. The second detector is now on the right frequency. For stability of operation, adjust the slug in the second-detector coil to make this signal come in with the capacitor plates more than half enmeshed.

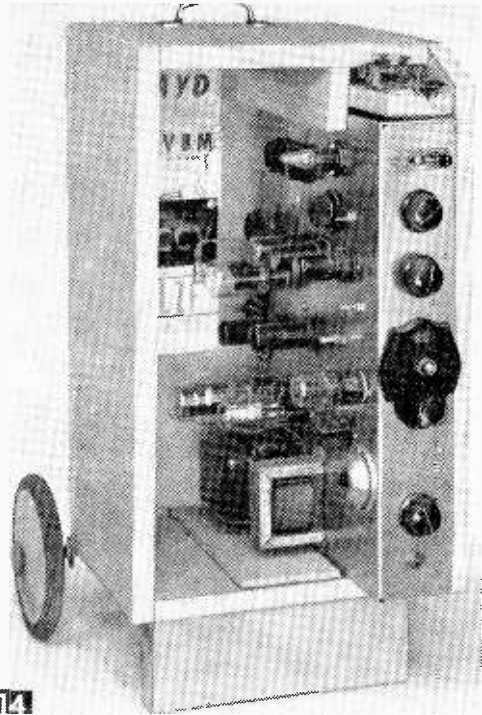If, with the push button depressed, you do not hear the crystal oscillator signal (it should be loud), check the contacts in the button and



The completed unit.

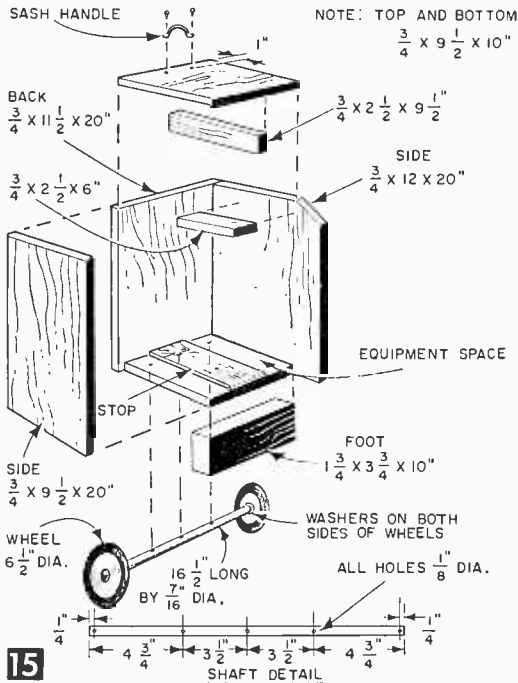

15

the 470K resistor. Finish by installing the first detector. (The first-detector coil is wound in accordance with Fig. 10.) The first-detector circuit is quite similar to that of the second detector (except for the grid-bias method used), so it

should present few difficulties.

Couple the antenna to the first-detector coil by winding two turns of hook-up wire around the ground end. The leads to this coil are twisted and run to the proper point of the Send-Receive switch (see Figs. 6, 9 and 12).

With all wiring now completed, insert all tubes, apply power, plug in phones, and switch S-R switch to Receive position. With the second detector in smooth oscillation (just above the "plunk" point), press the push button and reset the second detector to zero-beat with the crystal oscillator. Then connect an antenna (see Fig. 13) to the antenna terminals and advance the first-detector regeneration control about a third of the way above the Off position. Then rotate the first-detector tuning capacitor (front of chassis) slowly. At one point, signal strength of "sounds from the depths" should markedly increase. If it does not, take the grid-dip meter and check to make sure that the first-detector tuned-circuit will tune to 21 megacycles. Then advance the first-detector regeneration control a bit more and tune the first detector through its range again. If there is no increase in noise (or possibly a signal or two) check wiring and tube. Or perhaps the variable oscillator band-set capacitor has been disturbed. Better check the VFO frequency range again just to make sure.

When the first-detector tuning "peaks-up" as described you should be able to hear a number of 21-megacycle amateur signals, but practice is necessary before truly effective long-range reception is experienced. For instance, you should always keep the first-detector tuning capacitor peaked up for maximum strength. Secondly, the first-detector regeneration control must always be kept *below* the oscillation point. (In contrast to the *second detector*, which always oscillates when receiving code signals.) If the first detector oscillates it obscures the signals and, also, may radiate a disturbing signal to other receivers. If this control is kept just below oscillation, maximum sensitivity is achieved and no disturbance is possible. (The first-detector control also serves as a gain control; back it off to prevent overloading on very strong signals.)

With the receiver operating properly, connect the telegraph key, and throw the Send-Receive switch to Send. Press the key and adjust the antenna tuning capacitors until a 6-v, brown-bead pilot light in the miniature cleat socket (antenna tuning lamp) lights at maximum brilliancy. A retouching of the power amplifier tuning may help here. As a check, when properly tuned and loaded, substitute a milliammeter for the key (connected to key terminals). It should read between 60 and 90 milliamperes. Just to make sure, check output at antenna terminals with a grid-dip meter. There should be output on the 21-Mc. band only, to avoid unpleasantness from the FCC.

With your transmitter thus tuned up, find a station calling CQ and when he stands by, call

MATERIALS LIST—ISOTRON

No. Req.	Description	No. Req.	Description
1	aluminum chassis 3 x 12 x 17"	2	47 ohm, 1-watt composition resistor
11	Amphenol 8-prong tube sockets (MIP)	1	330 ohm, 1-watt composition resistor
1	6-terminal barrier terminal strip, small-size Jones	2	2½ millihenry R.F. chokes (National R-100)
7	plastic knobs for ¼" shafts	1	"2-meter" R.F. choke (Ohmite)
1	push button (obtain from hardware store)	18	.005 mfd, disc-type, ceramic capacitors
1	miniature type, cleat-lamp socket, screw-base	2	.001 mfd, disc-type, ceramic capacitors
1	Vernier tuning dial (National type BM, etc.); heirloom type shown in Fig. 1 used for sentimental reasons	6	50 mmf, disc-type, ceramic capacitors
1	4-pole, double-throw, anti-capacity switch, Federal Telephone	1	10 mmf, disc-type, ceramic capacitors
1	single circuit phone jack	1	.004 mfd, 1000-v. test, mica capacitor (Sangamo)
1	spring clip Mueller midget	1 pc	laminated plastic, ¼ x 1½ x 4½"
1	James Knights type H73 quartz transmitting crystal, frequency of 8450 kc	2	rubber grommets for ⅜" hole
1	power transformer, Chicago-Standard, Stancor No. PM 8411	1	piece 300-ohm, "twin lead" 18" long
1	filter reactor, Chicago-Standard, Stancor type C-1001	1	line cord and plug
2	100 K linear taper potentiometers, 1 with switch (Mailory)	1	gross nickel plated steel machine screws, 6-32. These should be ½" long
5	100 mmf variable capacitors, Bud No. MC1875	1	gross nickel plated steel hex nuts for above
1	15 mmf variable capacitor, Bud type MC 1850 (see text for modification)	1	5Y3G vacuum tube
1	50 mmf variable capacitor, Hammarlund type APC 50 (Power Mixer tuning)	1	OD3/VR150 vacuum tube
1	50 mmf variable capacitor Cardwell type PL 6004 (First Detector tuning)	3	6SJ7, metal vacuum tube
3	National XR-50, slug-tuned coil forms	2	6AG7 vacuum tube
1	I.C.A. coil form, No. 1108 B, 1¼" dia.	2	6SN7GTB (or 6SN7GTA) vacuum tube
2	electrolytic filter capacitors, 20 mfd, 600 w. v. Sprague type TVA-1966	1	6DQ6 vacuum tube
1	.01 mfd, 400 w. v. paper capacitor	1	telegraph key
1	1 mfd paper "bath tub" capacitor, Aerovox, type P30ZN, or tubular	1	pair magnetic head phones, 2000 ohms or higher
1	6000-ohm, 20-watt, wire-wound resistor (Ohmite)	1	phone plug
1	470,000 ohm, 2 watt composition resistor		hook-up wire, rosin core solder, insulated tie lugs No. 24 dcc magnet wire, 6-volt "brown bead" pilot lamp screw base, type No. 40 2-watt neon lamp, 20 feet of No. 14 tinned wire, one 15-watt 120 volt lamp for testing purposes, one bottle of coil dope, or polystyrene cement. A grid-dip meter must be used in adjusting this unit. A 0-150 ma dc milliammeter is also convenient.
2	180 ohm, 2 watt composition resistor	Cabinet parts required:	
4	100,000 ohm, 1 watt composition resistor	1	small sash handle
6	47,000, 1-watt composition resistor	2	velocipede wheels 6½" dia. including tire (obtain from toy or bicycle shop)
5	22,000, 1-watt composition resistor	16½ in.	⅞" steel rod
1	2.2 Megohm, 1-watt composition resistor	4	washers ⅞" hole dia.
3	2200, 1-watt composition resistor	30½	linear inches of white pine 9½" wide by ¾" thick
1	10,000, 1-watt composition resistor	1 pc	20½ x 12 x ¾" white pine
		1 pc	1¾ x 3¾ x 10" white pine

him. The odds are good that he'll "come back," no matter how far away he is. Good hunting!

Building the Cabinet. First saw three pieces 3¼ x 9½ x 10 in. for the top, bottom and shelf, and two ¾ x 9½ x 20½-in. pieces for the sides. Sand off the saw marks, glue meeting edges and assemble, nailing through the sides into the ends and shelf with 2-in. long finishing nails. Then cut a ¾ x 11¾ x 20½-in. piece for the back and glue and nail it in place. A 10-in. long piece of "two by four" (actually 1⅝ by 3⅝ in.) is nailed in place for the foot.

Set all nail heads with a nail-set, and fill these holes and any other fissures with wood putty.


While the wood putty is drying, cut and drill the ⅞ in. dia., 16½-in. long shaft for the wheels, as shown in Fig. 15. The end holes are for screws to hold on the wheels, while the three-center holes are for nails to fasten the shaft to the bottom of the cabinet. This shaft should be nail-fastened to the bottom, parallel to the back of the cabinet and ½ in. from back edge of bottom piece. Finish the cabinet with paint or walnut or

mahogany stain, followed by two coats of spar varnish. When the finish is dry, put on the wheels, with a washer in front and back of each. Fasten each wheel in place with a 6-32 machine screw passed through the end holes and secure with a nut. Then screw the sash handle to the top center of the cabinet one inch from the back.

Screw the telegraph key to brace piece and with the knob near the front edge, "skin-back" 18 in. of POSJ line cord, and clamp under the terminals of the key. Then pass the other end through the ¼-in. hole in the chassis.

Pass the line cord, and about 5 ft. of insulated wire (for receiver antenna) through one of the lower holes in the back of the cabinet. Now connect the line cord, the telegraph key leads, and the receiving antenna lead each to the proper terminal on the 6-terminal Jones strip on the chassis.

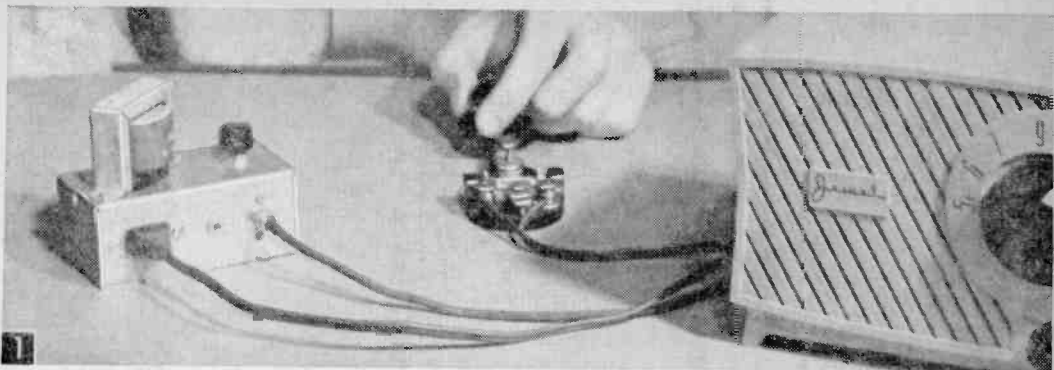
Slide the set into the cabinet as shown in Fig. 14. When ready to operate, wheel the unit beside your favorite chair, connect the antenna, plug in the power cord, and you're on the air.



Three-octave tone generator can be plugged into the phono record jack of any radio for loudspeaker code-practice or musical effects.

Transistorized Tone Generator

By THOMAS A. BLANCHARD

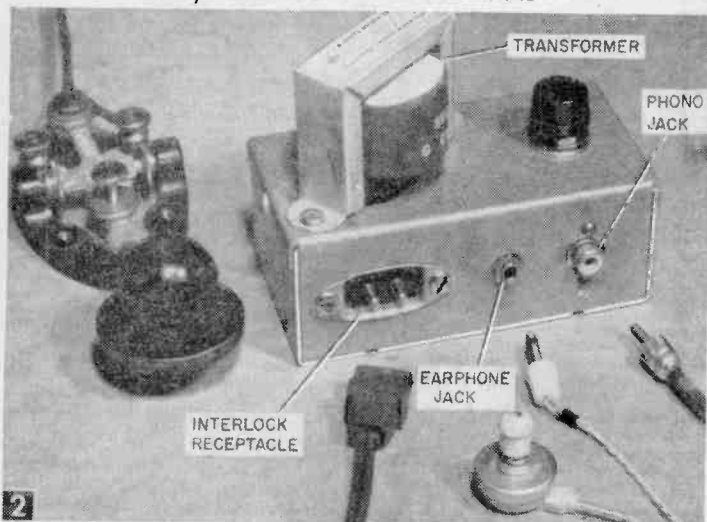

Complete tone generator is housed in a $1\frac{1}{2} \times 2 \times 4$ -in. radio utility type box. Key plugs into interlock receptacle. Center jack is for earphone use. Jack at right allows for connection to radio, TV or hi-fi amplifier.

THIS unit not only provides a springboard for interesting experiments with electronic music, but also may be used as a code practice oscillator by radio amateurs (Fig. 1).

The circuit is a transistorized version of the Hartley vacuum tube oscillator. The oscillator is the tapped secondary winding of an audio driver transformer. The transformer's primary provides inductive coupling to either a magnetic earphone or to the phono jacks of your radio or TV set for loudspeaker operation. Or connection can be made to the high impedance input jack of any amplifier. The tone generator is a completely self-contained unit requiring an inexpensive P-N-P type A.F. transistor. A single $1\frac{1}{2}$ -volt penlite battery is the sole source of power.

Mount the transformer on top of the $1\frac{1}{2} \times 2 \times 4$ in. aluminum box with a clearance hole beneath to allow for passage of primary and secondary leads (Fig. 4). Drill a hole for mounting the 500K ($\frac{1}{2}$ meg.) potentiometer, also located on the top of the box. On the front apron of the box, provide mounting holes for earphone jack, phono jack, and a male interlock receptacle to which the code practice key is connected. A jack such as used for the earphone connection may be substituted for the interlock receptacle if more convenient.

When mounting the jacks to the metal chassis, be sure that the outer shell lug of the phono jack is to the grounded side of the circuit. The same applies when connecting the earphone jack; otherwise, the unit will be inoperative due to a shorting of the output circuit.


Use a 3-lug tie strip (with or without isolated mounting eyelet) to secure the transistor (Fig. 4). This is more practical than trying to work with a flea-size transistor socket. When soldering in transistor leads, wrap a small wad of wet cleansing tissue around the leads to form a "heat sink" so that heat is not carried into the transistor to damage or destroy its delicate internal characteristics.

Because the penlite cell normally lasts for several weeks, solder it directly into the circuit and secure with a metal clamp cut from a strip of copper, aluminum or tinplate. A power switch is not required since the circuit only draws current when the key is closed.

For group code instruction, fit a length of single conductor shielded phono cable at both ends with a pin plug. Connect inner wire to plug pins and outer braided wire to plug shells. Attach cable to the radio and tone generator jacks and you are ready to roll.

In order to couple the comparatively low impedance winding of the driver transformer to the high impedance phono jack of radio or TV set, a 100K resistor is connected in series with the "hot" output lead (Fig. 3). If the completed unit operates erratically reverse the red and blue transformer leads at the earphone jack connection.


Musical Effects. Note in Fig. 3 that feedback to the B (base) of transistor is through the .02 mfd capacitor when a negative voltage is applied to the base point. When the maximum resistance of 547,000 ohms allows a minimum of power to reach the transistor base, the rate of oscillation will be slowed down, creating low musical tones. As the 500K linear potentiometer is rotated toward minimum, more voltage reaches the transistor base and frequency of oscillations generated increases, thus producing higher tones. Rotating the potentiometer from minimum to maximum will produce *three* octaves of tones, includ-

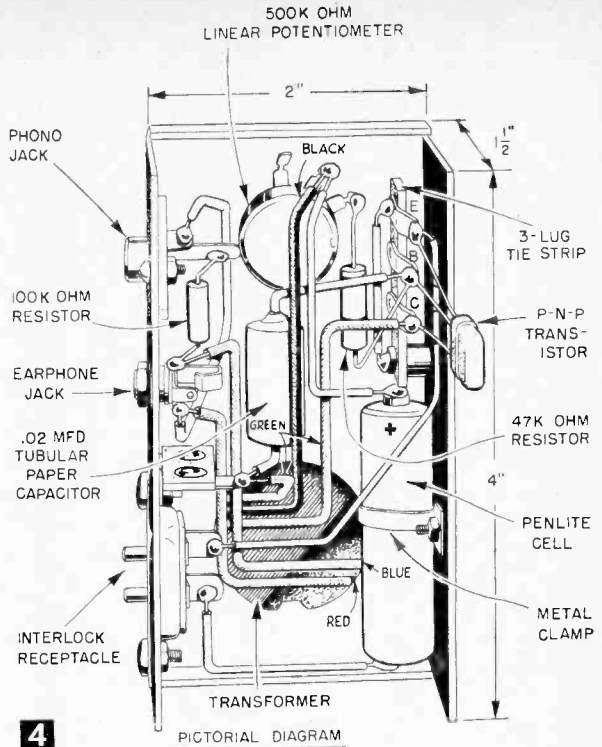

4

MATERIALS LIST—TONE GENERATOR

- | No. Req. | Description |
|----------|---|
| 1 | aluminum radio utility box. 1 1/2 x 2 x 4" (LMB, etc.) |
| 1 | P-N-P A.F. transistor (2N107, 2N34, CK-722 etc.) |
| 1 | audio interstage driver transformer; single 10K ohm plate to push-pull grids. Ratio: 2 1/2 to 1. (Stanco A-4292 or Triad A-81X) |
| 1 | 100K (100,000) ohm 1/2-watt composition resistor |
| 1 | 47K (47,000) ohm 1/2-watt composition resistor |
| 1 | 500K (500,000) potentiometer with linear taper (Mallory, IRC, etc.) |
| 1 | .02 mfd tubular paper capacitor (any voltage rating) |
| 1 | 3-lug tie strip |
| 1 | midjet phone jack and plug set (Lafayette) |
| 1 | RCA type phono jack and 2 matching plugs |
| 1 | interlock receptacle and cord |
| 1 | length single conductor shielded phono cable |
| 1 | penlite battery, 1 1/2v. |
- standard or miniature earphones may be employed, but they must be magnetic type with d-c resistance of 1500 ohms or higher.

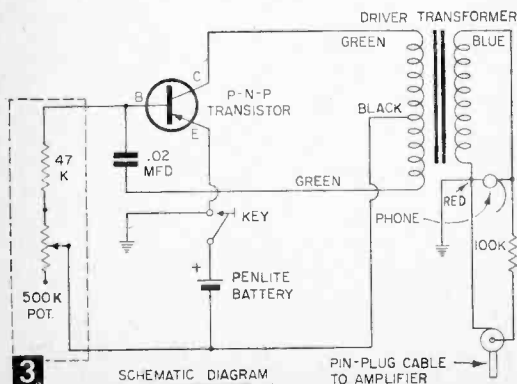

3

SCHEMATIC DIAGRAM

PIN-PLUG CABLE TO AMPLIFIER

ing, of course, not just the major, but sharp and flat tones as well.

Because a point would be reached in the high frequency ranges where too much voltage applied to the base would result in a breakdown of oscillations, you add a 47K resistor in series with the 500K potentiometer to prevent this from happening. However, should your clear high-pitched tones break down with the potentiometer in minimum resistance position, replace the 47K resistor with the next higher value that is available, which would be 51K.

To either raise or lower the three octaves covered by the tone generator, it is only necessary to use another size coupling capacitor in the feedback circuit. A .005 or .01 mfd will produce higher pitched tones, while .03 to .05 mfd will yield bass to sub-bass tones. For example, with .05 mfd in this circuit we obtained tones identical to the 13 pedalboard tones on a genuine electronic organ. Using the normal .02 mfd value, we closely duplicated genuine organ tones with violin tablet on upper manual engaged.

To convert this tone generator into a simple musical instrument, refer to the *Uke-Atron* project (see p. 77, of *Radio-TV Experimenter*, Vol. 3, published by SCIENCE AND MECHANICS, price 50¢). The "playing device" employed in *Uke-Atron* (Figs. 3, 6 and 7 of that article) may be used with this transistorized tone generator simply by adding a push switch in series with the 47K resistor and 500K potentiometer and replacing the key receptacle with a toggle or slide switch to turn on or off battery power.



Your own heart beat—or that of another human, or animal, can be heard loud and clear with this electronic stethoscope. (A dog's heart beat, when compared to that of a normal human, is usually very irregular.)



Building an Electronic Stethoscope

By HAROLD P. STRAND

HAVE you ever wondered what your heart beat sounds like to a physician as he puts his stethoscope to your chest? Build this unit and you can find out. With it, heart beats are picked up with a special microphone (which you build yourself) and amplified by a three-stage battery-powered amplifier. No layman, of course, should attempt to diagnose a heart condition with this—or any other—instrument, but if you are a physician (or veterinarian), you'll find this instrument useful in your practice; and if you're not, you'll find it simple and inexpensive to build, and a lot of fun to use as either a conversation piece or for more practical applications.

Sounds picked up by the stethoscope are much louder with a thin person than one with much fat on the chest since fat acts as a sound insulator. The volume control should be set at about 7 or 8 when first placing the pickup on the chest. If you want more volume, increase the setting. Moving the pickup around to various positions with the volume turned fully on, however, will give you a lot of noise, due to the sensitivity of the mike and the gain of the amplifier. The unit's tone control gives some control over the frequencies heard, suppressing the high frequencies and accentuating the lows. Most heart sounds fall within a range from about 40 to 600 cps, so that we are principally concerned with the low frequencies. The lowest frequency position of the pointer knob is fully counterclockwise.


Two phone jacks located in the top panel of the unit accommodate either the standard large phone plug or the miniature type. Batteries used are one 67½ v. B battery and a flashlight D cell for the A battery.



A simple general test for sensitivity can be given the equipment by plugging the mike into

the input jack of the amplifier and turning up the volume control. Very light taps on the diaphragm should produce loud sounds in the ear phones. If the mike is laid face down on a table top, tapping the table anywhere on its surface should produce clear audible sounds. If these tests prove satisfactory, try it on your own chest in the general mitral area. The heart beat should come through with good volume as the control is advanced.

Construction. Start with the amplifier, using a piece of ¼-in. thick Bakelite for the top panel. This fits in a recess in the Bakelite instrument case. Cut it carefully to size and drill four corner holes for the 4-40 attachment screws, lining these holes up with those in the case corners. Then drill the other holes detailed in Fig. 2.

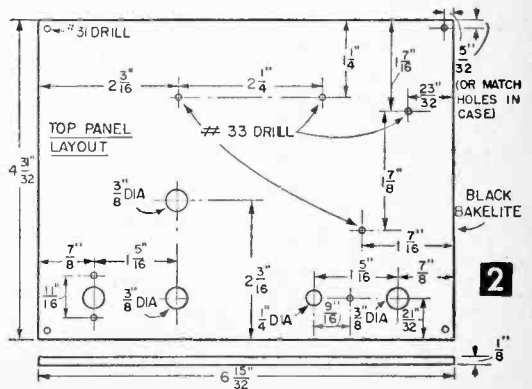
The chassis is L-shaped and bent from .065-in. aluminum. It is fastened to the top panel by the screws used at the phono jack, the locking nut on the volume control and a screw and nut placed between the two output jacks (see Fig.



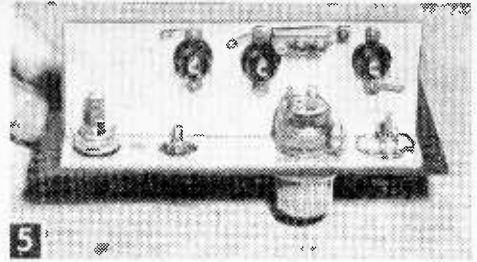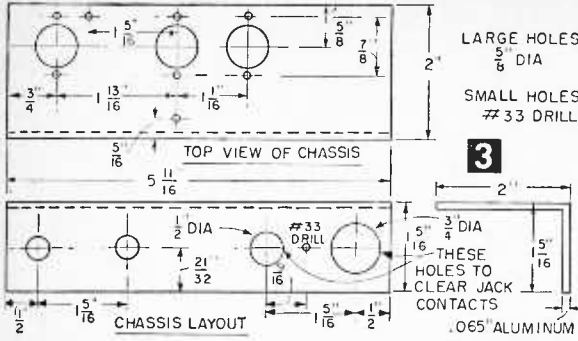

All underside parts have been secured in place in this view, ready for wiring. Note the clearance between the output jacks and the chassis by providing large holes.

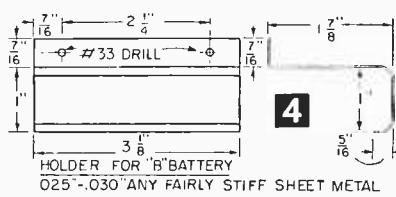3). The holder for the A battery is a standard, commercially available holder. A clip sheet metal holder for the B battery to hold it over the tubes and just below the edge of the panel. This holder can be made from any fairly stiff sheet metal.





When drilling the large chassis holes, use a counterbore or a twist drill specially sharpened for sheet metal or plastic to avoid tearing the metal. Assemble the sockets in their holes, using 4-40 screws and nuts, as well as the other chassis parts and attach the chassis to the panel (see Fig. 5).

Wire with #24 plastic insulated stranded hook-up wire (see Figs. 6 and 7). The B and A bat-

teries, their holders, and also the terminal piece for the B battery are shown in the process of assembly in Fig. 8. Connect the red lead of the B battery terminal piece to the plus (+) side of the circuit. At the A battery holder, mark one terminal (that with the lead going to the plus side of the filament circuit, see schematic Fig. 6) with a plus sign on a piece of white tape placed on the holder under this terminal to assure that the cell will be correctly installed later.

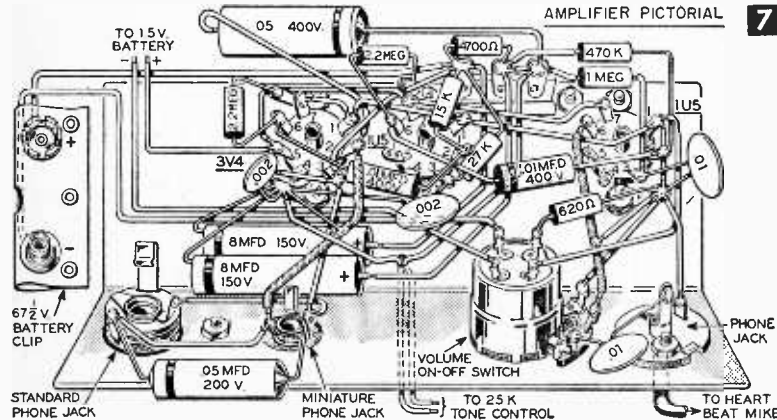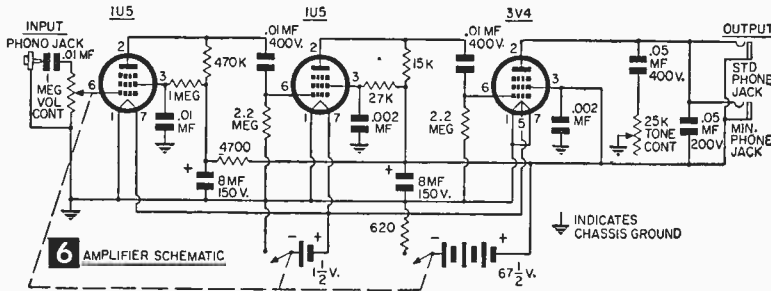A short piece of shielded wire is used at the input jack to the volume control, another piece between the volume control and pin #6 of the first 1U5 tube and also a piece between pin #2 of the 3V4 tube and the output jack (see Fig. 9)



to curtail hum. Ground the braid of this cable to the chassis with short soldered wires. Keep the strands of shielding away from the terminal connections. After placing the tubes in their sockets and installing the batteries (Fig. 10) check the amplifier by plugging in the ear phones and turning on the switch, advancing the volume control fully clockwise. A hum should be heard and if you touch the inner end of the phono jack with a finger you should get a loud click. Plug a crystal microphone into the input jack and have someone talk into the mike; voice should be heard loud and clear in the phones. Lack of sound indicates an error somewhere which must be checked and located.

ELECTRONIC STETHOSCOPE—MATERIALS LIST
AMPLIFIER

- 1 2¼ x 5¼ x 6¾" Bakelite instrument case (MS-218)
 - 1 1 meg. volume control, ½ watt linear taper, with D.P.S.T. attached switch
 - 3 7 pin Bakelite miniature sockets
 - 1 battery holder for one size D Burgess or 2LP Ray-O-Vac flashlight cell
 - 1 flashlight cell of either make as above
 - 1 67½ v. B battery Burgess P 45 M or equivalent
 - 2 1U5 tubes
 - 1 3V4 tube
 - 1 telephone jack, single circuit standard size
 - 1 telephone plug standard size
 - 1 miniature jack MS-282
 - 1 miniature plug MS-281
 - 1 phono jack RCA type
 - 1 phono plug RCA type
 - 1 dial knob type HRS National 0-10 HRS-3
 - 1 miniature knob with pointer for ¼" shaft
 - 1 25,000 ohm volume control linear taper (for tone control) ½ watt
 - 2 8 mfd. 150 volt electrolytic capacitors Sprague TVA-1405
 - 2 .05 400 volt paper capacitors
 - 2 .01 400 volt paper capacitors
 - 2 .01 disc ceramic capacitors
 - 2 .002 disc ceramic capacitors
 - 2 2.2 meg., ½ watt resistors
 - 1 620 ohm, ½ watt resistor
 - 1 4700 ohm, ½ watt resistor
 - 1 470,000 ohm, ½ watt resistor
 - 1 1 meg., ½ watt resistor
 - 1 27,000 ohm, ½ watt resistor
 - 1 15,000 ohm, ½ watt resistor
 - 1 3-terminal terminal strip Cinch-Jones #2003
 - 6' shielded cable small diameter size
 - 1 terminal pc. with snap connectors for Burgess P 45 M battery with red-yellow leads attached
- Approx. 5' #24 plastic covered stranded hook-up wire and about 10" of small spaghetti tubing
- 1 set of white alphabet decals Walsco #2115
 - 1 Cannon double headset, 3000 ohms AM-15-3

The above materials can be supplied by Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y., or in New England from their branch, 110 Federal Street, Boston, Mass.


Misc. materials

- 1 pc. black paper base Bakelite ⅛ x 5 x 6½" (case panel) Forest Products Co., 131 Portland Street, Cambridge, Mass.
- 1 pc. aluminum about .065 x 3¾ x 5⅛" (metal working shops)
- 1 pc. sheet metal (soft steel, brass or semi-hard aluminum) about .025"-.030" x 3⅛" x 3¾" (B battery holder)


If sound is distorted and undesirable noises are evident, wrong values of resistors or capacitors, or an unsoldered connection may be the trouble. If other remedies fail, test the tubes. If the volume control gives the loudest volume when the dial is on 1 rather than on 10, connections are reversed at the two outside terminals. Trouble in an amplifier can also be due to a resistor or capacitor which is defective; a substitution test may be required in order to find the faulty component. Also make sure that the electrolytic filter capacitors are connected so that the ends marked plus go to their correct locations on the terminal strip, the negative sides to chassis ground.

The completed unit with the head set and microphone plugged in is shown in Fig. 11. Lettering has been added from one of the decal sets sold by most electronic supply stores.

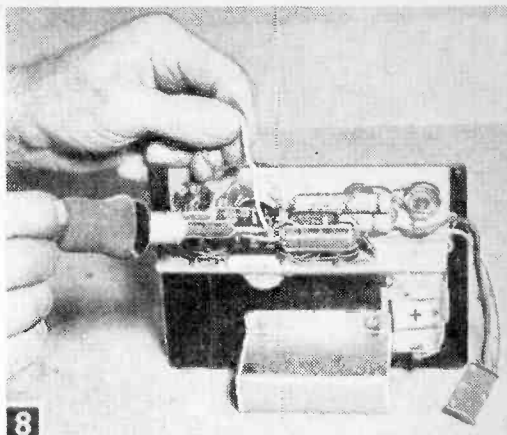The Microphone. Basically, the pickup unit consists of an Argonne MS-108 crystal cartridge. An aluminum diaphragm with a sanitary rubber



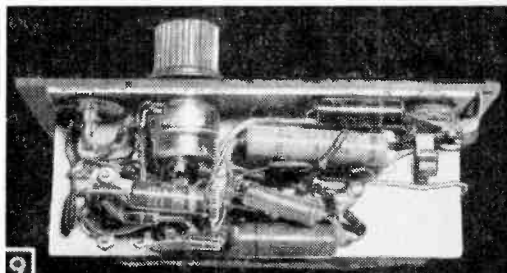8 The wiring is comparatively simple, though it must be compact to allow the chassis to fit in the Bakelite case. Use a soldering pencil on connections requiring low heat and a 60-watt iron where greater heat is needed, as on terminals having multiple leads.




9 A close-up of the completely wired chassis. Leads over edge at right go to batteries.




10 Tubes and batteries have been positioned and the snap-on terminals at the B battery are being pressed on. A piece of adhesive tape should be placed between the lower terminal of the A battery and the chassis so that this terminal will not short to the chassis. Note the tone control located between the two widest spaced tubes. Be sure that the 3V4 tube is next to the A battery or is in the output jack circuit.

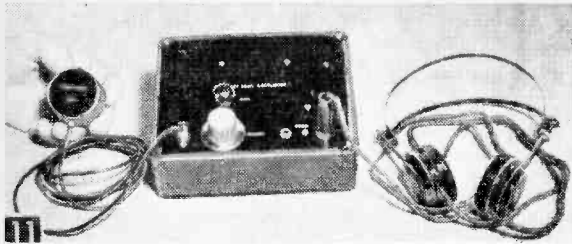
covering and a method of transmitting sounds from this diaphragm to the crystal element are needed, the latter consisting of an element made of Rochelle Salt in the form of a crystal which



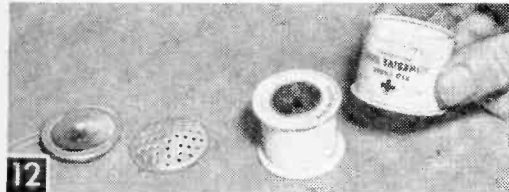
The complete unit, with a 3000-ohm headset plugged in. The back of the special pickup is at left.



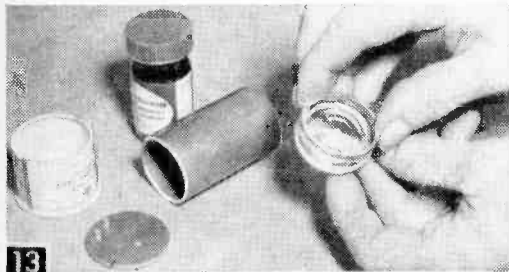The basic part of the pickup unit is a crystal microphone cartridge (at left, cover removed). A conical aluminum foil diaphragm is used; the outer section of an adhesive tape roll houses the pickup.



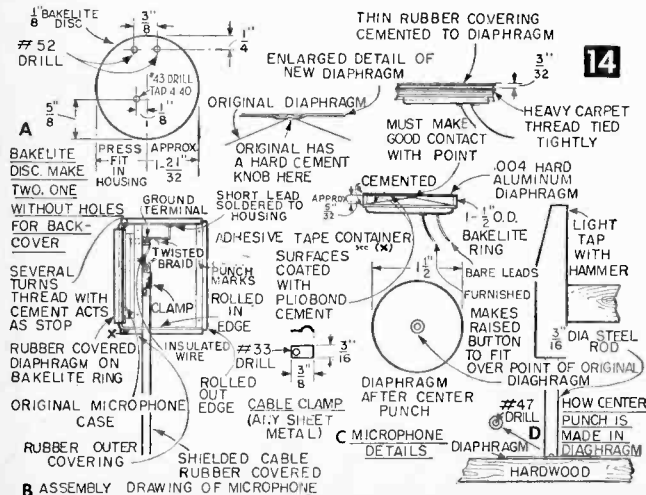Cut a ring from a piece of $1\frac{1}{2}$ in. Bakelite tubing and cement it to the edge of the diaphragm to give elevation so that a second diaphragm can be fixed in position and make light contact with the point of the first. A Bakelite disc is also shown. It has "flea" terminals and will be pressed in the housing to hold the microphone in place.



has the property of developing a small amount of electrical current if it is bent or distorted in any manner. This element, together with an actuating bar and thin aluminum foil diaphragm is supplied with the original microphone cartridge. Figure 12 shows the cartridge with its perforated cover removed and also the piece used for the outer casing for the new unit, the outer cylinder from a Johnson & Johnson 1-in. $2\frac{1}{2}$ yard long adhesive tape roll. This piece has one rolled-in edge.

Cut a ring (use a lathe) about $\frac{5}{32}$ -in. thick, $1\frac{1}{2}$ in. O.D. with a $\frac{1}{16}$ -in. wall thickness from a piece of Bakelite tubing and cement this piece to the edge of the original diaphragm base (see Fig. 13) to provide elevation so that a second diaphragm can be mounted in light contact with the apex of the cone. Some regulation of the height of this ring (which is critical) is afforded by the amount of depth put in the center depres-

MICROPHONE UNIT

- 1 Argonne miniature crystal microphone cartridge MS 108 (Lafayette Radio)
- 1 Johnson & Johnson roll of adhesive tape 1" wide, $2\frac{1}{2}$ yard size (for use of outer section of container only)
- 1 aluminum baking pan enclosed with package of Betty Crocker Answer Cake Mix. Can use other .004" hard aluminum sheet about 2" x 2" cut to $1\frac{1}{2}$ " dia. disc
- 2 pcs. $\frac{1}{8}$ " paper-base Bakelite about 2" x 2". Cut to make discs to fit in housing. Forest Products Co., or piece of scrap radio panel
- 1 pc. latex rubber sheeting about .016" thick x 2" x 2". Cut to make covering for diaphragm. A piece of Davol rubber leg bandage is type material wanted, or can use rubber sheeting of similar grade
- 2 flea terminal clips (Lafayette Cat. #MS 263, pkg. 12)
- 1 pc. of old inner tube about $1\frac{1}{2}$ " x $1\frac{1}{2}$ ". Cut to make piece for back of microphone case
- 1 pc. of old inner tube about 6" x $1\frac{1}{16}$ ". Cut to make outer covering
- 1 pc. microphone cable with rubber outer covering S-51 or Belden 8411. (Lafayette Radio) Length to suit or about 4-5 feet
- 1 pc. of sheet metal, soft steel or brass, about .016" x $1\frac{1}{2}$ " x $3/16$ ". Bend to make cable clamp
- 1 pc. Bakelite tubing $1\frac{1}{2}$ " O.D. with $\frac{1}{16}$ " wall and about 2" long. Cut off ring in lathe to make piece shown in drawing. (Forest Prod. Co.)
- 1 2 oz. bottle of General Cement Pliobond. (Lafayette Radio)
- Misc.—heavy carpet thread

sion (see Fig. 14 details). The ring height can be tested after cementing in place by laying a steel scale on the edge. The scale should come in contact with the hard cement found at the point of the original diaphragm.

Next, fit the back surface of the microphone with a piece of rubber cut from an old inner tube and cement it in place. Cut a notch out of the rubber to clear the terminals (Fig. 15). Either contact or Pliobond cement can be used, Pliobond is somewhat easier to apply since it is thinner. For most joining of materials, apply a coat to each surface and after this has dried a few seconds, press them together.

Cut the new diaphragm from the bottom of an aluminum baking pan,

the type that is supplied with a popular cake mix. This is about .004" thick and is semi-hard; it makes a thin but substantial diaphragm. The disc should be of the same diameter as the outside of the ring to which it will be attached. Figure 14D shows the tool made from a piece of $\frac{3}{16}$ in. dia. steel rod with a shallow hole drilled in one end with a #47 drill used to make a ring depression with a raised center to fit over the point of the other diaphragm. The depth of the depression can be adjusted by trial so that light but firm contact with the other diaphragm is made. The diaphragm surface should be otherwise flat and smooth.


Apply a coating of Pliobond to the underside of the disc, holding the piece with the point of a pencil and apply two light coats in a careful manner to the original diaphragm (to minimize airborne sounds). Apply cement to the top edge of the ring and then center the disc and press it down. The cement should be quite thin.

Now apply a thin rubber covering over the diaphragm. Apply cement to diaphragm and also to one surface of the rubber. Stretch the rubber a bit in the hands, press it down and then wrap several turns of heavy thread around the edge of the ring about $\frac{3}{32}$ in. down from the top (see Fig. 16). Tie tightly. The rubber I used was from an all-rubber latex leg bandage.



The assembled unit is now pressed in the adhesive tape container until the end projects just beyond the rolled-in edge. It should come to a stop against the thread turns.

The next step is to cut a disc of $\frac{1}{8}$ in. Bakelite for a light press fit in the housing. Drill two holes for the tiny flea clips, using a #52 drill (see Fig. 14A). Press the clips in carefully and then cut off the projecting ends. Drill and tap a hole in the disc for a 4-40 screw used for a cable clamp. Apply some cement to the rubber backing on the microphone case and also to the inside surface of the disc and then push the bare leads through the clips and press the disc in place tightly to the microphone. Feed the leads through the clips carefully so that there will be no slack loops inside.

From measurements of

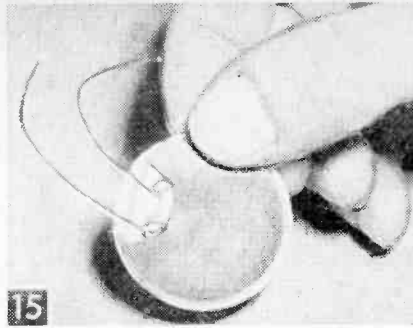

Cement a piece of rubber cut from an old inner tube to the back of the microphone, with a notch cut out to clear terminals. Upper non-insulated terminal connects to the shielded braid of the microphone cable and the inside of the housing to ground it (left). Apply a thin latex rubber covering over the diaphragm with cement, pulling the material tight and smooth and tie several turns of heavy thread around the edge, about $\frac{3}{32}$ in. down from the edge (right).

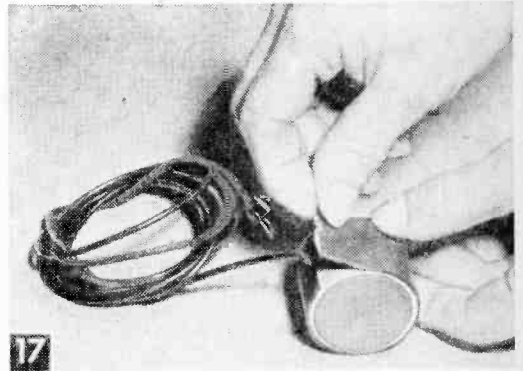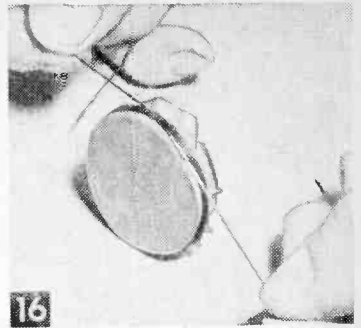

Apply a covering of rubber (with cement) to the outside of the pickup housing to dress it up and also to provide a sound-insulating grip surface.

the disc position, scribe a pencil line around the housing on the exact center of the disc thickness and then use a sharp prick punch to make a series of light indentations on the line to fix the disc permanently in place.

The center insulated wire of the shielded cable is soldered to the terminal through which the lead from the insulated microphone terminal projects, together with the microphone lead that has been cut off at the end of this terminal. Form

the metallic braid into a cable and solder it to the other terminal with the grounded microphone lead. Connect a short jumper from the grounded terminal to the housing at a soldered spot where the paint has been scraped off. A phono plug is connected to the other end of the cable. Solder the trimmed end of the insulated conductor to the end of the plug, a section of the shielded braid, to the base. The housing open end is enclosed by making a second Bakelite disc which is pressed in flush and held with prick punch spots around the housing on a center line of the disc. Cover the outside surface with a strip of rubber cut from an old inner tube (see Fig. 17).


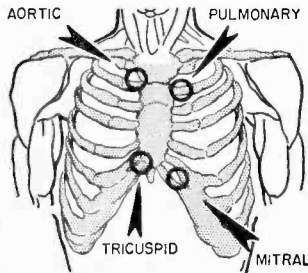


DIAGRAM SHOWING GENERAL AREAS OF THE HEART VALVES WHERE A STETHOSCOPE IS GENERALLY USED

Dress It Up, For Convenience

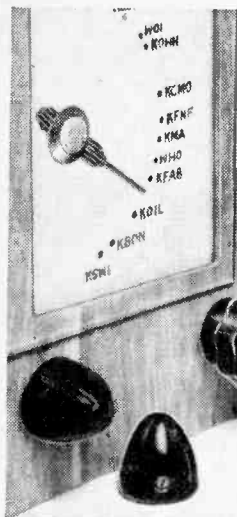


Replace the original dial plate with one that is custom call-lettered, and the original tuning knob with a spinner-type, and you've dressed up your radio as well as greatly adding to its convenience.


IF YOUR radio is not equipped with automatic tuning levers or pushbuttons, you'll appreciate the time-saving convenience of having the call letters of your favorite stations lettered on the dial plate so that you can tune to them quickly and accurately. (As radio servicemen and experimenters have discovered—to their profit—many people want and appreciate this added convenience.)

The radio's original dial plate is in no way faded or spoiled. Instead, a duplicate dial plate is cut from Bristol board (a heavyweight drawing paper) and either replaces or is placed over the original plate, depending on the design of the radio. Thus, if you move to another part of the country where there are different stations with different call letters, you can make a different plate, or you can replace the original plate if you want to sell or trade-in the radio.


Figure 1 shows the chassis of a table radio (cabinet removed) with a slide-rule type dial. By pulling out the four snap-in trimounts, the original dial plate was removed and then replaced with a strip of Bristol board the same size. The call letters of the most-listened-to stations were

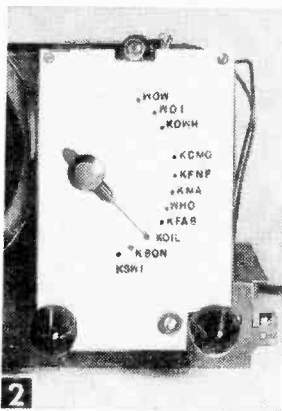

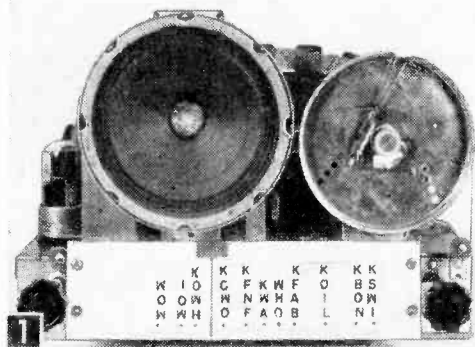2 Rotary-pointer type dial plate replacement.



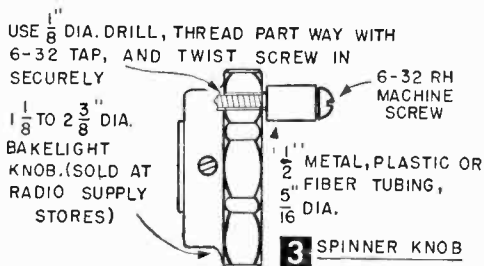1 Slide-rule type dial plate replacement.



then lettered onto the new dial plate with pen and India ink. Figure 2 shows the chassis of a table radio (cabinet removed) with a rotary-pointer type dial. An exact duplicate of the original dial plate was cut and punched from Bristol board and the desired station calls were lettered on it. (When working on an ac-dc chassis out of its cabinet, remember that it is likely to be "hot," so keep the radio disconnected when you are not actually tuning in stations for the purpose of spotting and lettering the stations on the new dial plate.)

Methods of fastening will, of course, depend upon the design of the radio. You can use small machine screws, thumb-tacks, Scotch tape, or even glue, providing you apply it where it will not show if you should ever remount the original plate. On sets where a dial lamp is mounted behind and glows through the dial plate, your new plate can be made from artist's tracing cloth, celluloid, thin plastic, or any other transparent or semi-transparent material that will take India ink. (Clear plastic can be given a dull finish on one side so that it will take India ink, if you rub one side briskly with a damp cloth and a little scouring powder.)

The perfect complement to a lettered dial plate is a spinner knob enabling you to "crank in" your favorite stations in a hurry. Figure 3 gives construction details of such a knob. The larger its diameter, the smoother and easier will be the spinning action. It should, of course, be used only with a drum-and-cord type of dial arrangement (the type most commonly used), since no advantage would be gained by installing it on sets without such a vernier arrangement, that is, sets in which the tuning knob is fastened directly to the capacitor shaft.—A. T.


Model Satellite Transmits Voice and Signals

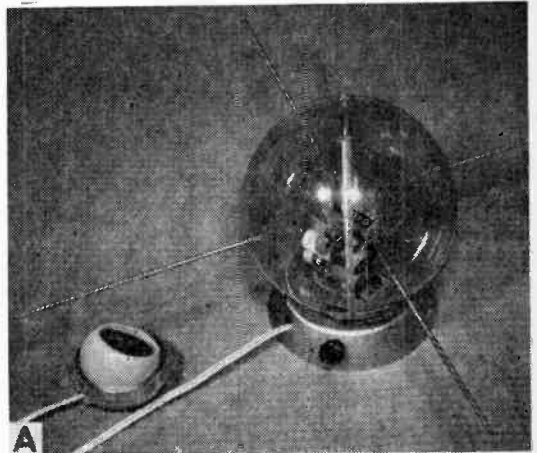By THOMAS A. BLANCHARD

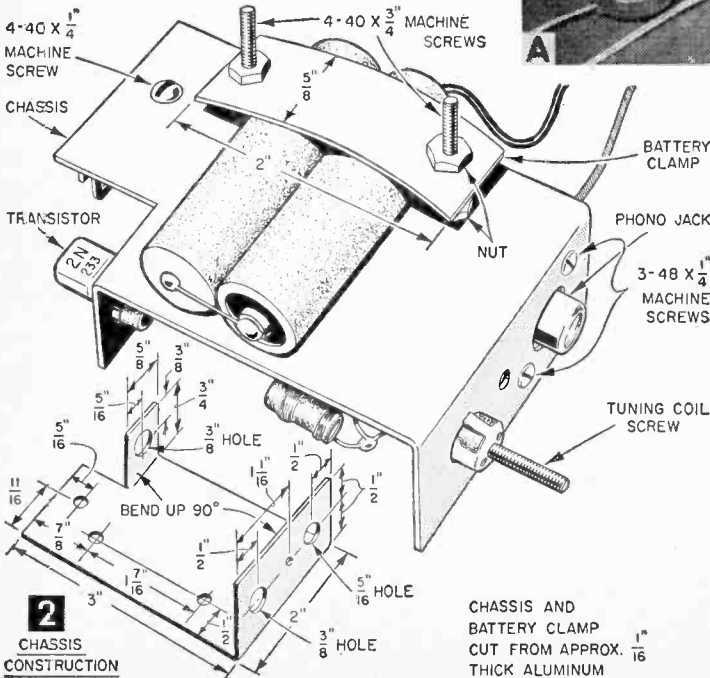


Fig. 1. The talking, beeping satellite is a small boy's delight. Transmitter is housed in a 6-in. plastic globe which mounts on a twist-lock base. Antenna elements are really aluminum knitting needles.

Fig. 1A. Closeup of model satellite and mike.




WHAT with all the talk about space travel and satellites, here is a simple electronic project (Fig. 1) that will broadcast both voice and simulated "beeps" out of any radio located within its broadcast range (100 to 200 ft.). Even more appealing is the fact that the "satellite's" transmitter is powered with just two penlite cells feeding a 1-transistor R.F. oscillator.




The oscillator is a transistorized version of the Colpitts circuit which is voice-modulated by inserting the high impedance winding of a miniature audio output or driver transformer in series with the hot side of the slug-tuned oscillator coil. The low impedance winding of the transformer is connected to a carbon telephone of mobile phone mike which is excited by the same penlite cells used to power the transmitter.

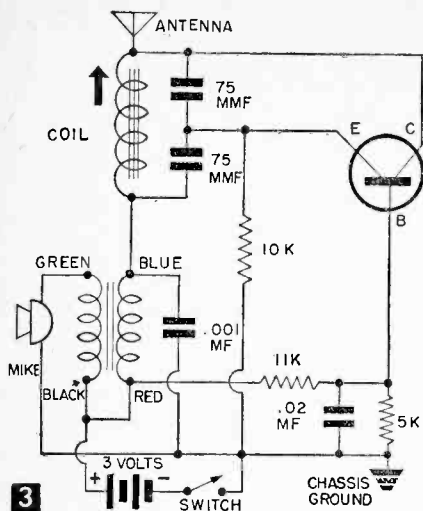Because the voltage output of the humble carbon mike exceeds by a hundredfold crystal, magnetic or other microphones, there can be no substitution. Carbon mikes are less expensive than the unsuitable types, and there are many military surplus carbon mikes still listed at giveaway



prices in various electronic parts catalogs.

The circuitry is so simple that little explanation is needed so long as the wiring details in Figs. 3 and 4 are carefully followed. The chassis is a 2 x 4-in. piece of light aluminum or other metal, with a 90° bend to serve as a mounting apron and holes for components drilled as shown in Fig. 2. When attached to the chassis with a 4-40 x 1/4-in. machine screw, the center lug of the 3-lug tie strip is self-grounding (Figs. 2 and 5).

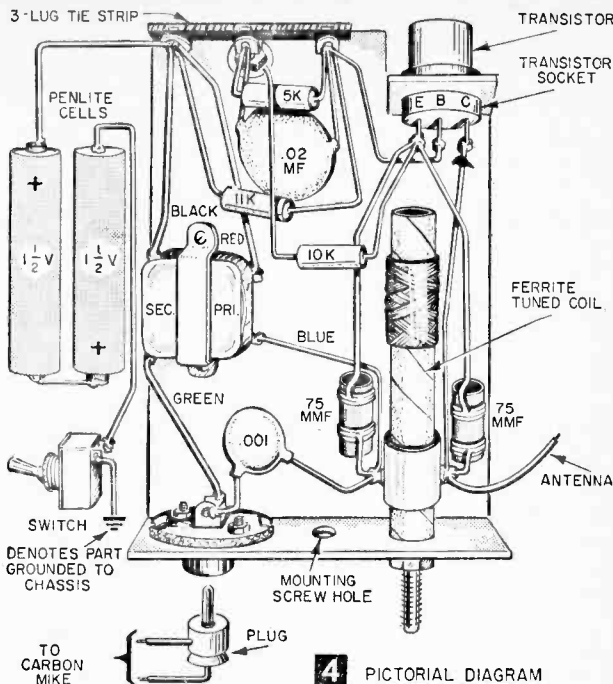

4 PICTORIAL DIAGRAM

MATERIALS LIST—MODEL SATELLITE BEEPER

No. Req.	Description
1 pc	2 x 4" aluminum or other light metal approx. 1/16" thick (chassis)
1 pc	5/8 x 2" aluminum or other light metal approx. 1/16" thick (battery clamp)
2	1 1/2-volt penlite cells
2	3-48 x 1/4" fh machine screws for mtg. phono jack w/nuts
2	4-40 x 3/4" rh machine screws for mtg. transformer w/4 nuts
2	4-40 x 1/4" rh machine screws for mtg. chassis and tie strip
1	3-lug tie strip
1	RCA phono jack and plug
1	ferrite slug-tuned antenna coil
1	round transistor socket
1	rotary or toggle SPST switch
1	Argonne #AR-116 or #AR-153 miniature transformer (Argonne Corp., Dept. SM, 165-11 South Rd., Jamaica 33, L. I., N. Y.)
1	R.F. Type transistor NPN Type 2N233 (Sylvania) or 2N170 (GE) PNP can be substituted by reversing battery connections, but it must be R.F. type. A.F. transistors will NOT work.
2	75 mmf. disc or tubular ceramic capacitors
1	.001 mf. ceramic disc capacitor
1	.02 mf. ceramic disc capacitor
1	5K, 1/2-watt composition resistor (or 4.7K or 5.1K ohm alternates)
1	10K 1/2-watt composition resistor
1	11K 1/2-watt composition resistor
1	plastic sphere, 6 in. or smaller (such as bank made by Playwell Products, Inc., New York, N. Y.)
4	7" Silvalume knitting needles (#182 Susan Bates Brand) Available in sets of 4 at variety or knitting supply stores or from C. J. Bates & Son Co., Dept. SM, 18 Liberty St., Chester, Conn.
1	mobile carbon mike with push-button (military model available from Concord Radio Corp., 45-SM Warren St., New York 7, N. Y. Stock No. MOB-MIK-C6, \$1.69. Minimum mail order \$5).

The phono jack also self-grounds when attached to chassis with 3-48 x 1/4-in. screws and nuts. The ground lug on the jack is used as a tie point for the grounded side of the .001 mf ceramic capacitor. All other grounded components are connected to the center lug of the tie strip, including the 10K resistor from emitter lug of transistor socket. When wiring the transistor socket note that lug C is twice the distance from B that B is from E (Fig. 4).

The oscillator coil is a conventional ferrite "loop" which is snap-mounted to chassis. The transformer is mounted to the chassis with a pair of 4-40 x 3/4-in. screws and nuts, which also secure the 5/8 x 2-in. strip of aluminum which clamps the two penlite cells in place (Fig. 2).

The 6-in. dia. plastic sphere which serves as our satellite (Fig. 1) is a modified toy bank sold in many toy, drug and stationery stores. Actually a smaller sphere can be used, or a plastic fish bowl, ball, planter or other such gadget.

Our clear plastic sphere mounts on a twist-lock base in which clearance holes for tuning coil and phono jack are drilled (Fig. 1). Mount completed chassis to base with one 4-40 x 1/4-in. machine screw inserted in chassis between jack and coil (Fig. 5). Drill a clearance hole in side of base so that the phono plug fitted on mike cord can be plugged into the jack. The battery switch may be either a single pole toggle or rotary type, installed in the base as in Figs. 1 and 1A. A single lead from battery connects to one switch lug (Fig. 4). Remaining switch lug is connected with a short lead to the chassis mounting screw.

The antenna elements are #3 double-pointed

anodized aluminum knitting needles, 7 in. long. Thread one end of each needle with a 6-32 die a distance of $\frac{3}{8}$ -in., while needle is clamped in a smooth-jaw vise. Drill four equidistant holes in the sphere and secure antenna elements with 6-32 nuts front and back (Fig. 1A). The antenna lead can be connected to the elements, or they may be used for appearance only, with a 3-ft. length of dangling wire serving as antenna.


For the keen observer who notes that our mock satellite has only four antenna elements, let us note that if a perfectly round plastic ball can be obtained, two more elements (one at top and one at bottom) may be added, or just one (at top) may be added. However, while many satellites have been pictured with six antenna elements, models exhibited by one of the best-known electronic firms have four elements, just as in our project.

To test your transmitter, turn on any radio set and set the dial to a silent spot near 1600KC. While the transmitter will tune all the BC band, the range is greater at the high end. Switch on the satellite and rotate the slug screw of the transmitter's tank coil until a high-pitched feedback whistle is heard through the radio. Place the mike near the set's speaker to insure picking up this tone.

With coil screw turned back out of the coil your transmitter will be tuned toward the 1600KC end of the dial; with screw turned in the signal will be toward 550KC on radio dial. Experiment until the fundamental frequency is found, as various points on the dial will yield harmonic signals which are weaker than when set and transmitter are tuned to the true frequency.

Using a surplus military mike with a push-button and pointing the mike toward the radio speaker will generate a feedback each time the mike circuit is closed, thus stimulating a beep each time the button is depressed. As with all mikes in direct range of a vibrating reproducer, for speech you must face mike away from the radio speaker or retire to another room to prevent feedback. Anyone who has previously experimented with microphones and amplifiers is well aware of this problem. You probably have heard it happen on TV shows originating from theater studios, where a misplaced mike or too much gain sets up oscillations between the stage mikes and the PA system by which the audience hears the performers.

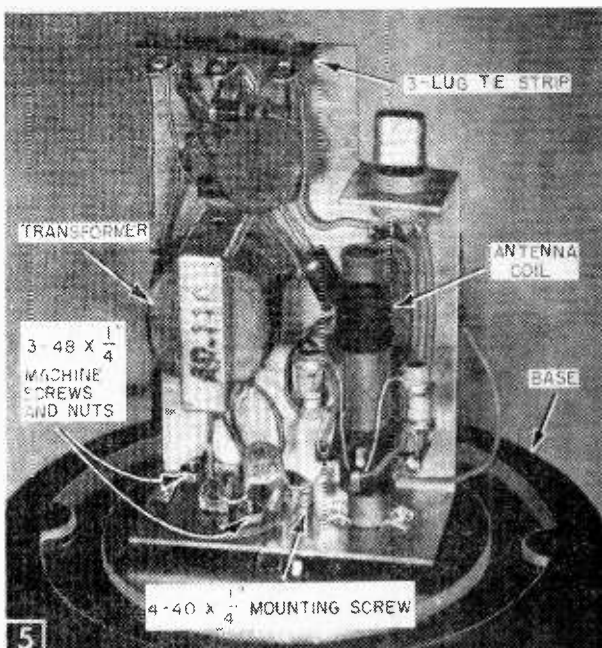A concluding note about the microphone transformer. Transformers made specifically for this purpose are not as tiny as the audio substitute used. After completion of the transmitter, which was fitted with an Argonne #AR-116 output transformer, we discovered another unit, the Argonne #AR-153 driver transformer which




Chassis mounts to base by means of a single screw located between coil and jack. While model shows transistor socket mounted on a bent tab, this extra operation is unnecessary.

might make a better impedance match than the #AR-116. The #AR-153 has a center-tapped primary winding. The center lead is simply ignored.

Note that the use to which we have put this type transformer makes the transformer hookup the reverse of its intended purpose. Thus the winding the manufacturer calls the primary (higher impedance) is actually hooked up in our circuit as the secondary winding. Color-coded transformer leads are indicated as they apply to this project so data supplied with transformers is disregarded in this instance.

Steam Iron Holds Phone Tips


- When soldering wires to phone tip plugs, borrow your wife's steam iron to hold the plug while your hands are busy with wire and soldering iron. Just rest the iron bottom-side up or clamp it in a vise, and put the plugs in the steam vents in the soleplate. Since most irons have a minimum of six vent holes, it's possible to do at least six plugs at a time. When plugs are half-filled with solder, insert the ends of the wires, pull the line plug out of the iron and let it cool slowly. Or, if you prefer, lift each individual plug out with a pair of pliers while holding the wire in place.—JOHN A. COMSTOCK.

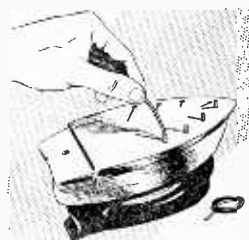

Since most irons have a minimum of six vent holes, it's possible to do at least six plugs at a time. When plugs are half-filled with solder, insert the ends of the wires, pull the line plug out of the iron and let it cool slowly. Or, if you prefer, lift each individual plug out with a pair of pliers while holding the wire in place.—JOHN A. COMSTOCK.

Your Amplifier Has More Inputs With This Simple Signal Mixer

By FORREST H. FRANTZ, Sr.

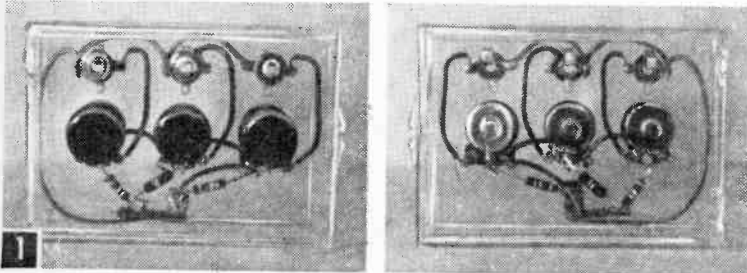

Front and back views of simple signal mixer which enables you to use a single input amplifier for several different input signals simultaneously.

THIS three-channel mixer will enable you to feed signals from a radio tuner, a microphone, and a phonograph pick-up into a single input amplifier, will give you individual volume control for each of the inputs, and enable you to talk or sing through the microphone input with music entering through the phonograph or radio input.

Signal mixer circuits vary considerably in configuration and complexity. Some mixer circuits use tubes or transistors; simpler mixer circuits use only resistors and volume controls. The circuit of this ultra-simple mixer is shown in Fig. 2. It uses three volume controls and three resistors, plus the input impedance of the amplifier to accomplish mixing. It can be built to work with a low-impedance input amplifier (such as a transistor amplifier), or to function with a high-impedance input amplifier (such as a vacuum-tube amplifier). The only difference between the two units is in the resistance values of the volume controls and the resistors used.

For a transistor-amplifier signal mixer the resistance of the volume controls should be 25K (25,000) ohms and the resistors, 10K. For a vacuum-tube amplifier mixer, the volume control should be 250K and the resistors, 270K. (This assumes that the matching to the three input devices is not too critical; in general, this is true.)

Construct the mixer in a plastic case, using miniature volume con-

trols and input jacks. (There is, however, enough room in the case to use the conventional size volume controls and jacks if you wish.) The hole layout for the front of the plastic case is shown in Fig. 3. Make holes by punching small pilot holes with a heated ice pick and reaming them to size with a taper reamer and provide a hole in the back of the case for the mixer output lead. Cut volume control shafts to a length of $\frac{5}{16}$ in.

Solder leads to the input jacks before you mount them. If you don't, you may damage the plastic case by melting some of


it. Mount jacks, volume controls, and the insulated tie-down terminal, complete the wiring and fasten an output lead with a connector or plug that fits your amplifier input.

Input jacks and matching plugs are available as an inexpensive combination (the combination is called out on the Materials List). Equip the output leads from the three signal sources you'll be using as mixer inputs with these miniature plugs. The "ground" leads connect to the body of the plugs, the other leads connect to the tips.


The mixer may have to be shielded to prevent ac hum pick-up if it's built for use with a vacuum-tube amplifier. Do this by lining the inside with aluminum foil before mounting components. The shield connection to mixer ground can be made through the volume control mountings by connecting a lead from any or all of the volume control cases to the mixer ground terminal.

There's a small signal loss in the mixer since it is made up entirely of resistive components. The loss is very small and for usual input levels and amplifier gains is of no consequence.

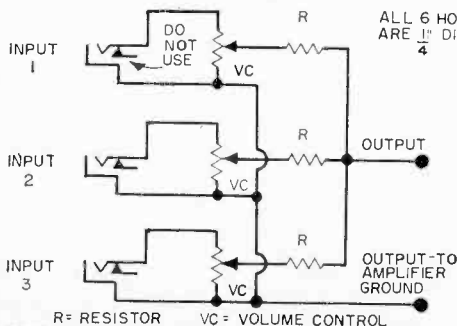The inputs to the mixer should be free of di-



2 SCHEMATIC

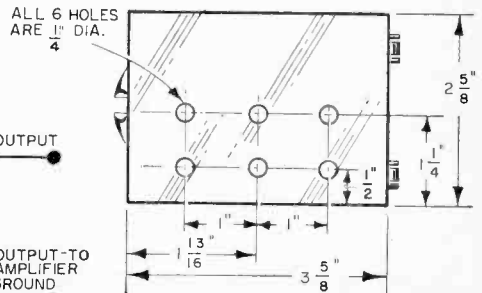

3 HOLE LAYOUT FOR PLASTIC CASE FRONT

rect current. If any of the inputs contain dc components, insert .1 mfd, 600v capacitors in

series with input leads to isolate the volume controls.

MATERIALS LIST—SIMPLE SIGNAL MIXER

No. Req'd.	Description	No. Req'd.	Description
1	1 x 2 $\frac{5}{8}$ x 3 $\frac{5}{8}$ " plastic case (Lafayette MS-159)	3	$\frac{1}{2}$ watt carbon resistors (use 10K with transistor amplifier, 270K with vacuum-tube amplifier)
3	miniature phone jack & plug sets (Lafayette MS-370)	3	miniature volume controls (use Lafayette VC-24 25K with transistor amplifier, or Lafayette VC-37 250K with tube amplifier)
3	miniature knobs (Lafayette MS-185)		
1	insulated tie-down terminal		

RADIO-TV CROSSFIGURE PUZZLE

By JOHN A. COMSTOCK

Ever work a crossfigure puzzle? This one deals with figures often encountered in radio-television and electronics. You'll find many of them already familiar to you; others you may have to figure out using simple arithmetic. In any event, this puzzle will supply an enjoyable 30 minutes or more of juggling numbers fun. And it's educational, too!


CLUES

ACROSS

- 1) Upper frequency limit of standard AM broadcast band.
- 2) Value of resistor color-coded orange, brown, brown.
- 4) The tip radius of a microgroove phono needle (decimal).
- 6) FM superhet I.F.
- 7) Current flow in a circuit when resistance is 10 ohms, voltage 200 volts.
- 8) Total scanning lines in one television frame.
- 10) Voltage dropped when 1 ampere flows through 45 ohms of resistance.
- 12) Six microhenries inductance expressed in henries.
- 14) Heater voltage of 50B5 vacuum tube.
- 16) Number of electrical degrees in one-quarter cycle of an ac signal.
- 17) Ripple frequency of a half-wave, two-phase rectifier.
- 18) Impedance of ribbon television twin-lead.
- 20) The diameter of a large hi-fi speaker.
- 21) Lower frequency limit of standard FM broadcast band.
- 22) 1.34 horsepower expressed in watts.
- 23) Impedance of a circuit when applied voltage is 40 volts, current flow 1 ampere.
- 25) Number in radiotelegraph code: two-dits, three-dahs, five-dits, five-dahs.
- 26) Power expended in a circuit which draws 2 amperes at 40 volts.
- 27) Mid-frequency of television channel 11. (Upper and lower limits are 198 and 204-megacycles respectively.)
- 28) Frequency of 4 kilocycles converted to megacycles.
- 31) In milliamperes, the current leaving a circuit when input current is 10 milliamperes.
- 33) Wavelength of a 1,000-kilocycle signal.
- 34) Width of a commercial FM broadcast channel.
- 35) Number of electrical degrees of current-voltage signal displacement through a capacitor.
- 38) Year Edison announced invention of the phonograph.
- 39) Year regular broadcasts began in the United States (KDKA).

DOWN

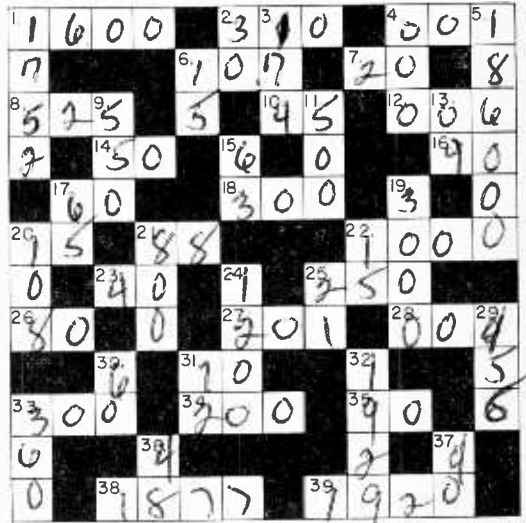- 1) Year Benjamin Franklin flew a kite and discovered certain electrical phenomenon.
- 2) The frequencies in the VHF band extend from — megacycles to 300 megacycles.
- 3) The lower frequency limit of TV channel 7.



- 4) Number of zeros represented by orange in resistor color code.
- 5) Velocity of radio waves in free space in thousands of miles per second.
- 6) Total resistance of three 5-ohm resistors connected in series.
- 9) Lower limit of AM broadcast band.
- 11) $\frac{1}{2}$ -kilowatt in watts.
- 13) Frequency of 90 cycles per second expressed in kilocycles.
- 15) Mid-frequency of television channel 3. (Lower channel limit, 60 megacycles.)
- 17) UHF television channel between 64 and 66.
- 19) Three kilocycles converted to cycles.
- 20) Upper frequency limit of standard FM broadcast band.
- 21) Second harmonic of 400 kilocycles.
- 24) Number of watt-hours consumed by a 60-watt transmitter operated for 20 hours.
- 25) Popular size television larger than 17 inches.
- 29) AM superhet I.F.
- 30) Television vertical scanning frequency.
- 31) Popular size speaker slightly smaller than 15 inches.
- 32) Year screen-grid tubes were developed.
- 33) Number of electrical degrees plate current flows in a class A amplifier.
- 36) Total voltage of 32.1 $\frac{1}{2}$ -volt cells series connected.
- 37) Total number of watts capable of being dissipated by two 50-ohm, 20-watt resistors, series connected.

For answers, see page 144.

Want an Extra "Hand" for those long conversations?

Try this Telephone Amplifier

With a telephone on this amplifier, you not only hear what the person on the other end says, but can talk back by speaking directly into the front opening

By HAROLD P. STRAND

something like the head set in a bowl to amplify the sound so others could hear it as in the old days of crystal radios, except in this case, it works in reverse. Sound waves entering the cavity are reflected from its smooth surface into the transmitter and talking close and directly into the cavity in a normal voice, will give very comparable transmission to the other party. Sitting as far as 3 feet away and raising the voice a little, still permits conversation. From a distance of about six to eight feet you can still converse, but in a louder voice.

A small 2-stage amplifier builds up energy from the inductance pick-up coil to loud speaker volume. The




Anyone who has to write while listening to the telephone needs this amplifier, but it makes all long telephone talks easier.

THERE'S no longer any need for holding a telephone during long conversations, when the other party takes off to look up records or when you need both hands for writing while listening. With this amplifier, phoning becomes easy and pleasant. Here's how it works. To start the amplifier, just place the receiver into the pick-up element and let it rest in the cradle (Figs. 1 and 2). An automatic switch operated from the weight of the telephone turns on the battery operated circuit. The other party's voice comes out the speaker at the right-hand side of the cabinet. To talk back, you simply speak into the cabinet opening around the transmitter. A volume control on the left-hand side allows you to adjust speaker volume, a big aid for persons slightly deaf.

The recess under transmitter works



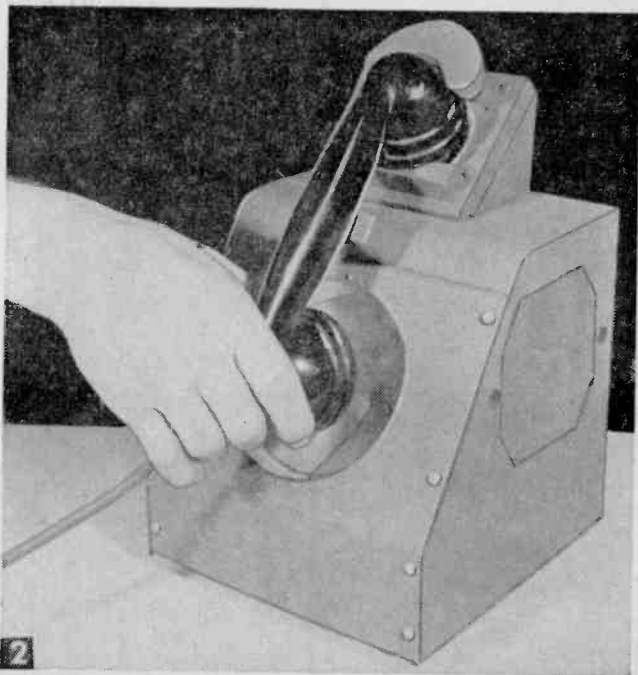
To put hand set in position, slip receiver into pick-up unit and let handle rest on cradle. Plunger in the rest automatically switches on amplifier.



MATERIALS LIST—TELEPHONE AMPLIFIER (Electronic)

- | | |
|---|---|
| <p>1 metal cabinet, sloping front, 8 x 8 x 8", Insuline Corp. 3990
 1 5" P.M. speaker, 1.47 oz. magnet or larger
 1 output transformer, 8000 ohms to 4 or 3.5 ohms
 1 volume control knob with 0-10 attached dial, National type HRS
 1 telephone pick-up unit, Permoflux Corp., model M-53 (or M-55 for newer 500 series handsets). Available from Radio Shack, 167 Washington St., Boston
 1 terminal strip, 6 terminals, Jones 6-140
 2 miniature 7-pin sockets, Amphenol 147-500
 3 rubber grommets for 1/4" hole
 1 phono jack, RCA type. 1 phono plug, RCA type
 1 volume control, 1/2 meg., Mallory Midgetrol U-48. #1 taper.
 2 chassis terminal strips, Jones lug type. 2 terminal
 1 1SS miniature 7-pin tube. 1 3S4 miniature 7-pin tube
 Resistors—1/2 watt carbon
 1 .47 meg. 1 1 meg. 1 2.2 meg. 1 680 ohm.
 Condensers—Aerovox disc type—
 2 .005
 2 snap terminals to fit 90 volt portable B battery
 1 terminal plug to fit 1/2 volt portable A battery
 1 Burgess A battery 1 1/2 volt, type 4 F
 1 Burgess B battery 90 volts, type N 60</p> | <p>Misc. Materials
 1 sheet aluminum about .050 x 3 3/4 x 9", chassis
 1 sheet aluminum about .035 x 3 1/2 x 9 1/2", pick-up bracket
 1 sheet aluminum about .025 x 6 1/2 x 6 1/2", cone
 1 birch plywood, 3 3/8 x 4", pick-up base
 1 birch or maple 1/2 x 3/4 x 3", receiver rest
 1 birch or maple 3/8 x 1 1/2 x 2", cut out for hand set rest
 1 birch or maple about 3/4 x 5 3/4 x 5 3/4", cone ring
 1 Sheet felt 1/8" thick as required to cover outside of cone
 4 rubber knobs or feet with 10-32 machine screw studs, bottom of cabinet
 1 3/16" Masonite hard board about 5 1/2 x 5 3/4", speaker baffle
 1 grille cloth 5 1/2 x 5 3/4"
 1 brass rod 1 3/4 long, 1/8" dia., switch plunger
 1 brass tubing 1/8 I.D. 1/4 O.D. x 1 3/16", plunger bushing
 4 phosphor bronze .014 x 3/16 x 3", switch springs
 4 silver alloy contacts
 1 Bakelite, canvas base, 1/8 x 7/16 x 1", switch spring spacer bar
 1 Bakelite, paper base, 3/8 x 3/4 x 1 1/2", switch support block
 2 pipe spacers, 1/8 I.D. x 1/4 O.D. x 7/16" long, switch spacers
 1 perforated sheet steel, 2 1/4 x 7 3/4", cover for back opening
 Misc. screws, nuts, hook-up wire, paint etc.</p> |
|---|---|

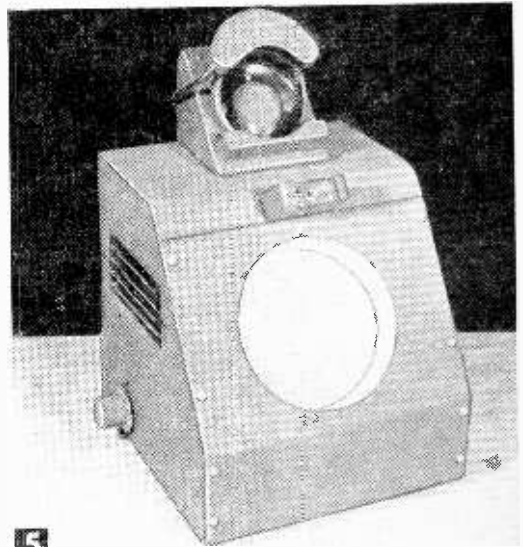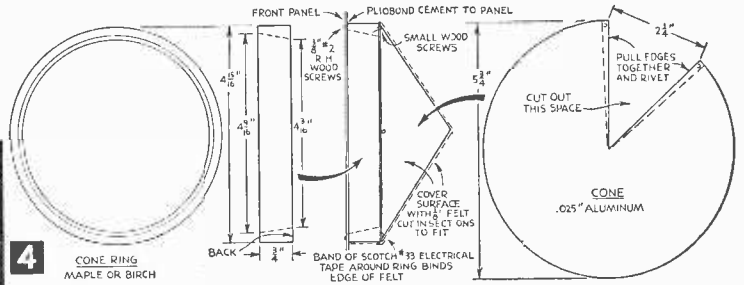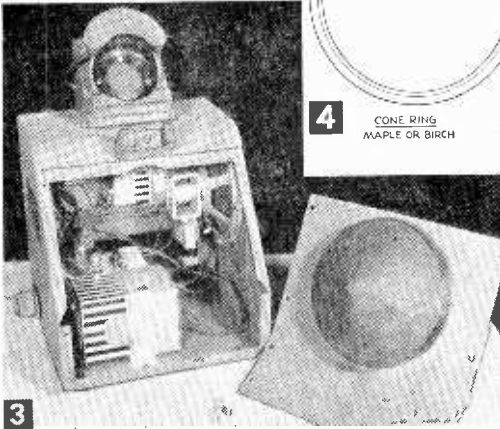Parts behind front panel. Note 1/8-in. felt backing on cone. Metal straps hold A and B batteries in place.




Cone under transmitter is open here, but may be covered with metal grill. Volume control is at left side and louvers help ventilate amplifier.

pick-up coil is made especially for picking up telephone conversation without any connections or alteration to the telephone system. It forms the most expensive component of the unit, selling for about \$15.00 at electronic supply stores, but since it is a key part, get a good one.

The unit is built around a gray-ripple finish stock cabinet, but an opening needs to be cut in front (Fig. 3). Cut the aluminum cone from .025-in. sheet stock (Fig. 4), and bend up to a cone with a rivet at the edge. Turn the wood ring from maple or other hardwood and mount between the cabinet panel and cone as shown in Fig. 4. The Permoflux pick-up unit must be trimmed around its front edge to allow the hand set to be slipped in and out easily (Fig. 6). Bend up the .035-in. sheet aluminum bracket that supports the birch plywood to which the pick-up unit is screwed (Fig. 6B). The Permoflux unit should be fitted to the receiver you plan to use it with. The receiver should be pressed into po-

sition and come to a stop against the hardwood block at the bottom. The hand set should slip in and out easily, yet be firmly held in position.

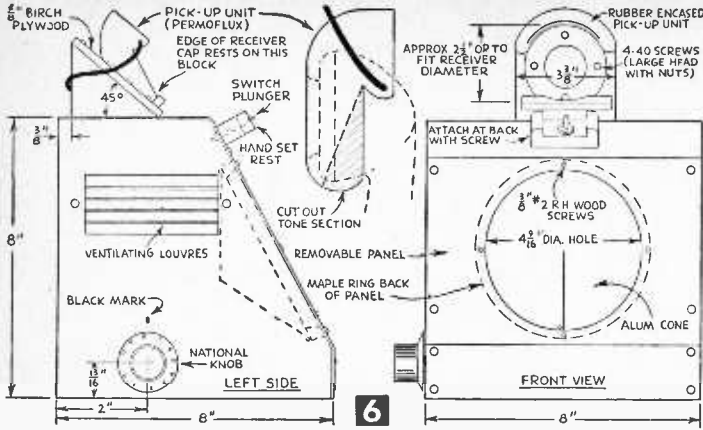Build up the leaf-spring switch that automatically switches on the set as shown in Fig. 6A. Silver alloy contacts were borrowed from the spring pack of an old telephone relay and






soldered to the ends of the springs. A piece of 1/8-in. *Bakelite* is riveted to the two top springs as a spacer bar. The brass switch plunger passes through a brass bushing in the maple block and rests against this insulated spacer.


The back surface of the aluminum cone is covered with 1/8-in. felt to deaden reflected sound and add to the accoustical value of the cone. The speaker can be seen mounted to its *Masonite* baffle, with the output transformer secured to the speaker frame. The amplifier has been placed to the left rear, where the volume control shaft can project through a hole in the side of the cabinet. The A battery is fixed in a front position with a strap and two bolts, and the B battery is secured to the upper right hand back section with a similar strap. Flexible #22 insulated wire is used for all connections, with standard attachment clips to the B battery and a plug to fit the portable A battery. These snaps make it easy to replace batteries as needed.

Bend up the chassis from the flat pattern shown in Fig. 8. Layout the holes and set the tube sockets for the two tubes.

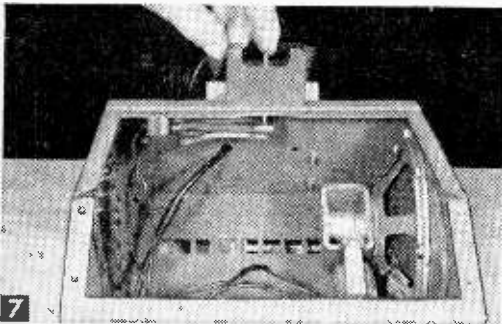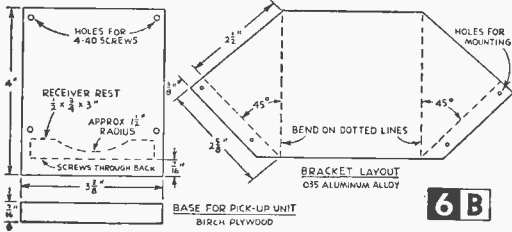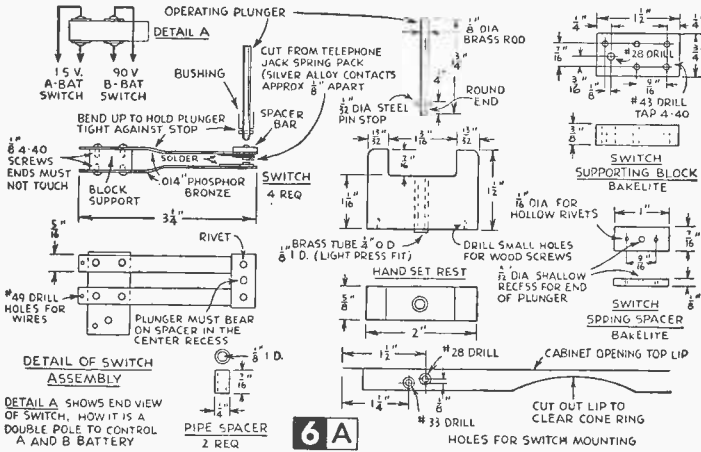Wire up the circuit according to the schematic diagram of Fig. 10. Mount the speaker behind the side hole in the cabinet and cover with grille cloth cemented over the opening. The volume control fits into a hole drilled in the left side (as shown in Figs. 5 and 6).





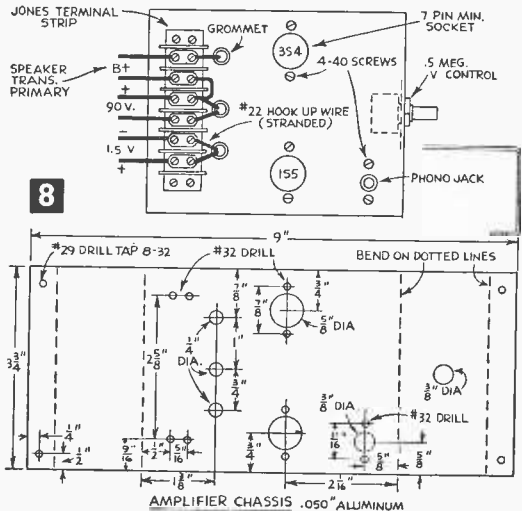Switch plunger and leaf spring. Note how speaker is mounted to Masonite panel at right side. Heavy wire at left is shielded wire from Permoflux pick-up.



8

AMPLIFIER CHASSIS .050" ALUMINUM

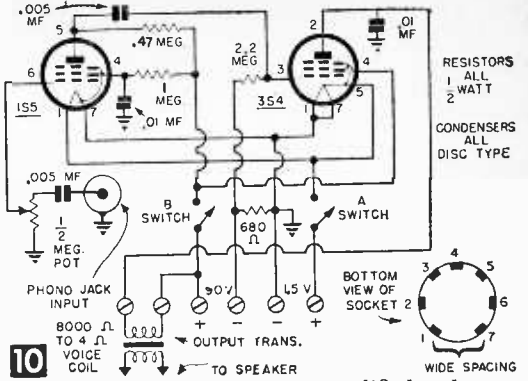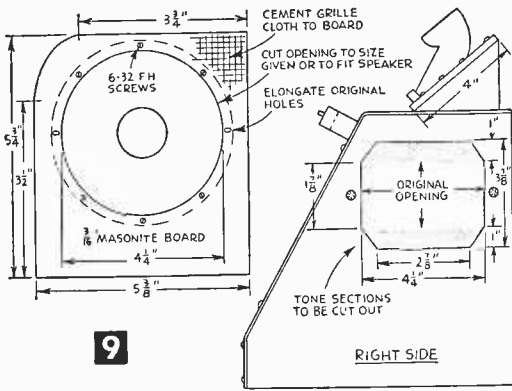

When using the amplifier, answer the telephone in the usual way to establish contact before placing the hand set in position. Then speak normally into the cone opening. The person's

voice from the phone will be amplified and come through the side speaker. Adjust the volume carefully, as the cone will pick up an annoying feedback squeal if the speaker volume is adjusted for too loud a volume.

Plug-in type radio coils are handled with a simple jig which makes a once difficult winding operation quick and easy.



Winding Small Coils

You can "roll your own" coil windings using simple shop tools and following these instructions


was 29/16-in. on the original model, but the exact size of wire spool may vary among manufacturers. Check the brand of spool wire offered by your favorite radio parts supplier, and space the vertical supports accordingly.

To prevent the spooled magnet wire from getting out of hand while winding a coil, use a simple brake to maintain spool tension as the wire is being removed. This brake is merely a strip of spring brass with a fiber or smooth wooden strip cemented on the end with *Pliobond* or other all-purpose cement. The fiber piece acts as a brake shoe over the entire wire area (Fig. 3). After mounting the brake with two small screws, bend the brass strip inward to provide sufficient pressure against the spool of wire. An ordinary hand or breast drill gripped in the vise jaws drives the coil winder. Fit the drill chuck with one of several jigs which hold the coil form during the winding operation.

WHEN electronic, radio or TV projects call for home-wound coils, you're likely to find yourself in a jungle of snarled magnet wire unless you use some system. A simple coil-winding set-up (Fig. 1) allows you to wind practically any type of coil either on an insulated cylinder or a plug-in coil form. The winding apparatus consists of a vise, hand or breast drill and a home-made spool holder for unreeling the magnet wire as it is wound onto the coil form. The spool holder (Fig. 2) is made from 1/2-in. pine. Drill 1/4-in. holes for the spool supports and use a 20d (4 in.) building nail for the spool of magnet wire to rotate on. Spacing of supports


For winding coils on paper, plastic, or Bakelite tubing, two wooden cones lock the coil form on a threaded shaft made from a 6 or 8-in. eyebolt with 14-24 or 1/4-20 threads. The eye is sawed off, and the bolt inserted in the drill chuck. To mount a tubular coil form, run a nut up on the bolt, followed by one wooden cone. Slip the coil form over the bolt, and follow with the second cone. The coil form is secured by drawing up the wingnut. The wooden cones (Fig. 4) automatically center coil forms from 1/2 to 1 1/8 in. diameter.

Fig. 5 shows how to make a handy jig for wind-

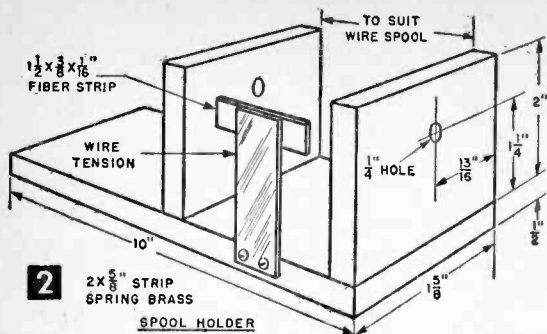

2 2X 1/2" STRIP SPRING BRASS
SPOOL HOLDER

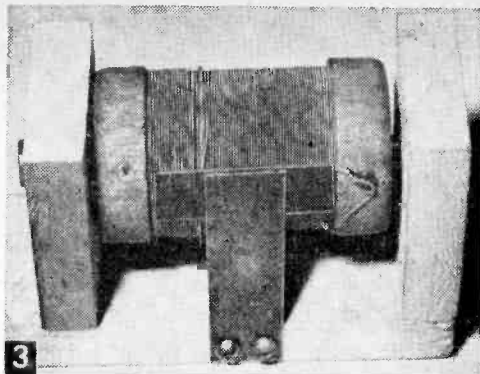
Spring brass leaf and fiber bar keep spooled magnet wire under tension, to simplify winding.




3

ing plug-in type coils. These coils, frequently used in shortwave receivers, are wound on 4, 5, or octal type bases salvaged from discarded tubes, or on plug-in type coil forms sold by many radio parts suppliers. Ordinarily, such coils are difficult to wind. Secure the jig shaft in the drill chuck and plug in the coil form, and winding the coil is quite simple.

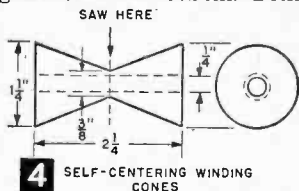
Small plastic bobbins included with motor kits, or bobbins used for winding radio RF chokes, etc. may be wound by whittling a plug of soft wood to fit inside the rectangular or round bobbin. Drill a hole through the center of the plug and use a bolt, washers and nut to make the assembly rigid. The bolt is then inserted in the drill chuck and bobbin wound with the desired number of turns.



4 SELF-CENTERING WINDING CONES

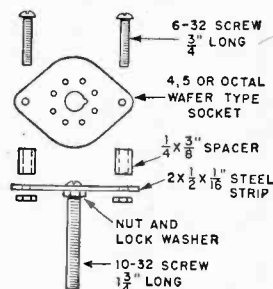

5 WINDING JIG FOR PLUG-IN COILS

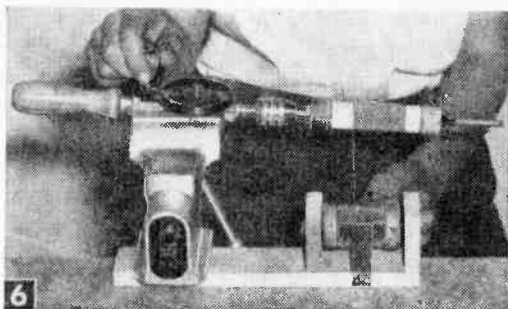

Winding coil on a tubular coil form.

The bottle will cause the wire to come off the hank in spiral fashion as you proceed to wind the electrical coil in question. Of course, the hank could be transferred to an empty wire spool but this additional operation isn't necessary if you exercise a little care.

While coil forms may be purchased in a variety of sizes, the experimenter will find many everyday household items that make ideal coil forms. Plastic pill vials, toothbrush containers, plastic sip straws, cardboard tubing from discarded flashlight cells, roll tissue or wax paper, cosmetic containers—all may be used as coil forms.

Winding Coils from Hank Wire

Figs. 1 and 6 show how wire is guided onto coil form with the thumb and index fingers holding it taut. Wire, in various gages and insulations called for in radio projects, is sold only on spools. However, construction kits may include coil wire in hank form. Motors, electromagnets, etc. may be wound from the hank, by placing the hank over a milk or beverage bottle on the floor directly under your coil winding set-up.



"Electronics experimenting is a hobby of mine."

Telethermoscope for amateur weather stations

Here's a very accurate, remote indicating electrical thermometer for indoor readings of outdoor temperature

By CHARLES A. LAIRD



Telethermoscope indicator located inside house gives accurate reading of outdoor temperature. Three-wire cable shown in insert A connects temperature-sensing bulb, which is located outside, to box housing indicator meters.

BUILT of standard electrical parts readily available, this special type of thermometer is commonly used in science and industry, and many Weather Bureau stations.

Its operation is based on the principle that


the electrical resistance of most metals increases as their temperature increases. For example, if we make up a coil of copper wire of predetermined wire size and length and insert it in a protective tube or "bulb" for use as the temperature-sensing device, and connect this coil to a simple, calibrated resistance bridge to determine the coil's electrical resistance, we have a very accurate method for determining the temperature. The advantage of this type of thermometer is that the coil or sensing device may be placed at a point remote from the indicating meter (Fig. 1).

Start construction by making the coil first. Cut off a length of #38 enameled copper wire exactly 15.16 ft. (15 ft. $1\frac{13}{16}$ in.) long plus $\frac{1}{2}$ in. for soldering leads to the ends. Wire tables in physics books show that the electrical resistance of a 15.16 ft. length of #38 copper wire is equal to 10 ohms at 68° F. Actually if a small error is made in measuring the length of wire, it's not too important because we can compensate for this in final calibration of the instrument.


Wind the wire, skein fashion, on a 2-in. length of cardboard as in Fig. 2A. To one end of the wire, solder an 8-in. length of #20 insulated flexible radio hookup wire and to the other end, two lengths of the #20 wire. Use rosin-core solder sparingly. Then cover the splices with short lengths of plastic electrical tape to make certain there will be no short between splices.

MATERIALS LIST—TELETHERMOSCOPE

No. Req.	Size and description
1	6 x 4 x 3" metal chassis box to house instrument components
1	0-100 microammeter (Calrad, type MO-38, $\frac{1}{2}$ " sq meter, available from Columbia Electronic Sales, 2251-53 W. Washington Bldg., Los Angeles 18, Calif.) for balance meter (cost, \$5.50).
1	10-ohm wire wound control Clarostat, series A10 for adjusting rheostat
1	4-ohm wire wound control Clarostat, series A10 for temperature rheostat
1	3-prong socket, Cinch-Jones S-303-AB for cable connection
1	3-prong plug, Cinch-Jones P-303-CCT
1	push button switch, Switchcraft 95L
1	$2\frac{3}{4}$ " radio dial and pointer
2	10-ohm wire wound resistors, Ohmite, 10 watt
2	D-size flashlight battery cells
1	$\frac{1}{4}$ " I.D. x 3" long copper tubing for bulb housing 10'
1	Belden No. 8443 3-wire cable (any length may be used as explained in text)
	18 ga. x 1" x 12" aluminum strip for mounting batteries and 10-ohm rheostat
	small terminal strip
16 ft	#38 enameled copper wire
	small disk cut from plastic
4	4-40 x $\frac{1}{2}$ " rd. machine screws
6	6-32 x $\frac{1}{2}$ " rd. machine screws
2 ft	#18 hookup wire
	drawing paper

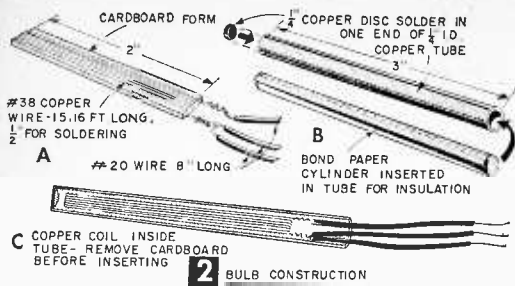

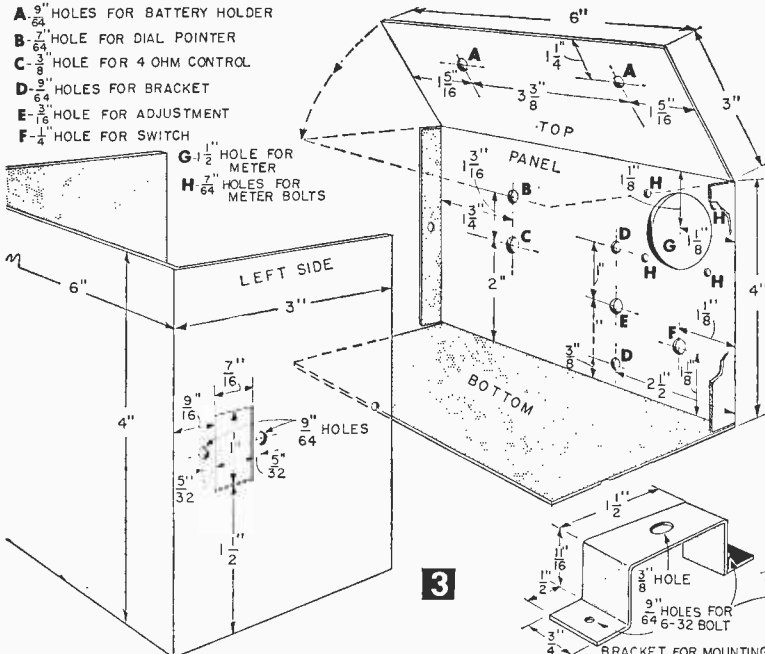
- A $\frac{9}{64}$ " HOLES FOR BATTERY HOLDER
- B $\frac{7}{64}$ " HOLE FOR DIAL POINTER
- C $\frac{3}{8}$ " HOLE FOR 4 OHM CONTROL
- D $\frac{9}{64}$ " HOLES FOR BRACKET
- E $\frac{3}{16}$ " HOLE FOR ADJUSTMENT
- F $\frac{1}{4}$ " HOLE FOR SWITCH
- G $\frac{1}{2}$ " HOLE FOR METER
- H $\frac{7}{64}$ " HOLES FOR METER BOLTS



for initial (and possibly future) adjustment only, mount it on the metal bracket detailed in Figs. 3 and 6 so its shaft will not extend through the chassis box. Then drill a hole through the box in line with the shaft so a screwdriver may be used for initial adjusting. The 4-ohm rheostat (A1 in Fig. 6) is mounted so its shaft extends through the box and is controlled by a standard radio dial. Fasten the two D-size batteries to the box side as in Fig. 7 with the metal strap detailed in Fig. 3. Use

a small terminal strip to support one of the 10-ohm resistors.

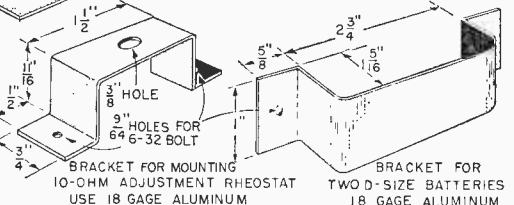A Wheatstone bridge circuit (Fig. 4) offers an accurate method for measuring resistance. If we let resistor X represent our temperature bulb, then the formula, $X = AC/B$, applies. If the four resistances are equal, the meter M will show no current. If resistor X increases in value, the meter will show current. We can bring the meter current back to zero by increasing the value of A by a



To make the protective tube or bulb, cut off a 3-in. length of $\frac{1}{4}$ -in. I.D. copper tubing and close one end by pinching and soldering or by soldering on a $\frac{1}{4}$ -in. disc of copper (Fig. 2B). Insert a cylinder of bond paper in the tube for insulation. Now, carefully remove the coil from the cardboard strip and insert it in the tube (Fig. 2C). Give the coil a slight twist to make it easier to insert. Complete the bulb by filling it with melted sealing wax.

Next, lay out and drill the mounting holes in the box (Fig. 3) and make the various brackets for the parts (see Materials List for parts).


Any microammeter may be used for the bridge balance meter. We used a 0 to 100 miniature-type, microammeter and adjusted it to read as a center zero meter by turning the two hairsprings at the front and back of the meter pivot. This is quite a delicate operation and care should be used. Unless you've had some experience with meters, it's best to use a meter with its zero already in the center of the scale. The purpose of this meter is to indicate a null, or zero, current condition.

Since the 10-ohm rheostat (A2 in Fig. 6) is

corresponding amount. This is the principle used in our telethermoscope.

The resistor X in the circuit we are using (Fig. 5) is our coil of copper wire. The resistance A is variable and has a dial calibrated in degrees. Actually, two rheostats are used in leg A of our bridge. A2 is for setting purposes, and A1 has a dial calibrated in degrees F. for direct reading of the bulb temperature. By using three leads between the bulb and the bridge, length of the leads and lead temperature will not affect accuracy of the instrument. The two outside wires (1 and 3 in Fig. 5) go to opposite sides of the bridge, so length and temperature effects will compensate. The center wire (2) goes to the meter and its length and temperature will have no effect on accuracy. A pictorial view of actual hookup is shown in Fig. 6. Use #18 plastic insulated hookup wire and solder all connections.

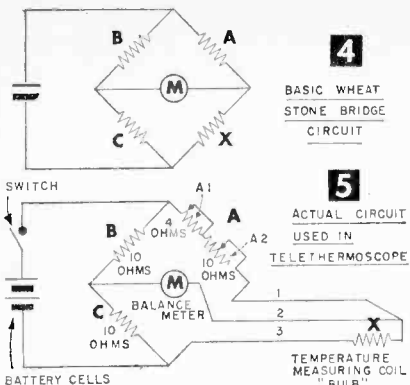The dial for the 4-ohm rheostat to be calibrated in terms of temperature is a standard radio dial. Remove the knob from the metal part of the dial (it is held with three screws) and cut




a disk from heavy drawing paper, using the metal part as a template. Then mount the paper between the dial knob and the plate. This paper disk will be calibrated in terms of temperature. A disk of transparent plastic can be mounted over the paper to protect it.

Calibration is not difficult. Use an accurate mercury or alcohol thermometer. Put the bulb and the thermometer in water, warmed (or cooled) to various temperatures, and mark the dial at corresponding points. Stir the water vigorously to assure accuracy. Allow about 1/2 hour for the bulb temperature to come to equilibrium. Adjust the dial so that the balance meter shows no current. Then mark the dial at that spot. The bulb will vary nearly 4 ohms, covering temperatures between minus 50 and plus 130° F. This will put mid-point on the dial at 40 degrees.


Cool the water in your calibrating bath with ice cubes until it shows 40° F. on your calibrating thermometer. Then adjust the 10-ohm rheostat so that your 40-degree mark will be in the center of the dial. After this, use other calibrating temperatures. One good check point is the 32° F. temperature. Put the bulb in a container of finely crushed ice and leave until no further change takes place. This will be an important check point on your dial.

The scale will be linear, so when you have found eight or ten check points, you should be able to lay out the entire scale. The more check points you use, the greater the accuracy. Use black drawing ink for dial markings and figures. The dial in Fig. 1 has a mark for each two degrees.

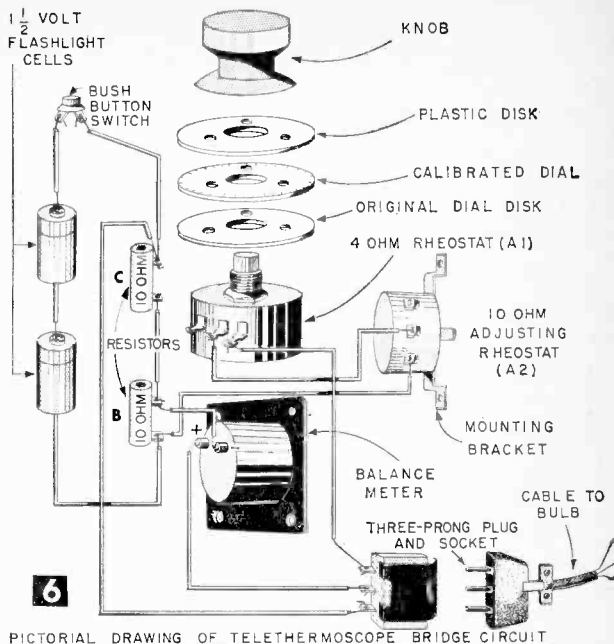To get a temperature reading with your telethermoscope, merely press the switch button and adjust the dial until the meter shows zero. The temperature is then read off the dial. Accuracy of the telethermoscope may be checked occasionally by comparing with a standard



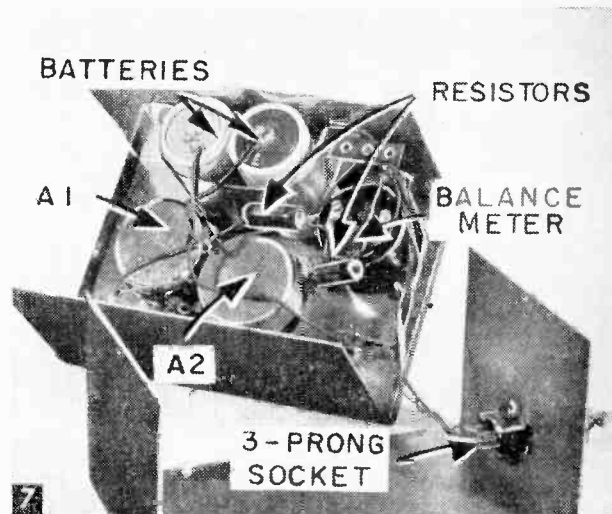PICTORIAL DRAWING OF TELETHERMOSCOPE BRIDGE CIRCUIT




Inside view of indicator box showing placement of components.

thermometer. Adjust for correct reading by turning the rheostat, A 2, with a screwdriver. The bulb resistance may tend to drift a slight amount over a long period. The instrument shown here has retained its accuracy for about six months.

The bulb should be exposed on the north side of a building if possible. The indicator (or "bridge") box may be located anywhere in the house—set it on a table or mount it on the wall. Standard Weather Bureau telethermoscopes have their bulbs exposed in a thoroughly ventilated instrument shelter with louvered sides.


Pocket Signal Tracer

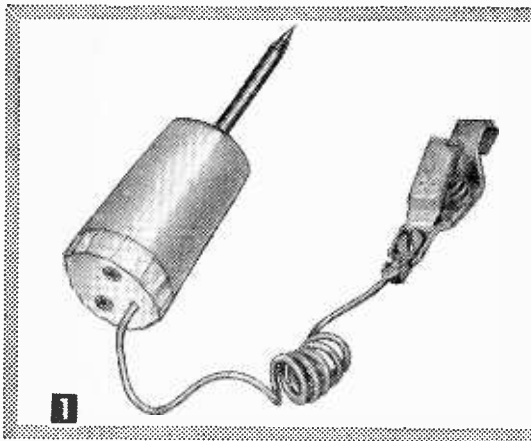You can build this simple crystal diode testing probe for locating circuit breakdowns in radio sets




Tracking down the trouble in a radio set by following the signal through the grid and plate of each tube socket. Signal tracer built in a 1x2 in. plastic salt shaker. Alligator clip attaches to the ground or B- circuit of set being checked.

WHEN the simple tests for troubles in a radio set fail, you'll welcome this pocket-size trouble-shooting signal tracer for making a stage-by-stage test to locate the radio's dead section. Operating without any external battery or line voltage, the tracer functions like a crystal radio and is built around a germanium diode. Its small size (this one was built in a salt shaker from a variety store) makes it easy to use. You can also build it into plastic packages for shaving sticks, solid skin lotions or other pharmaceuticals.

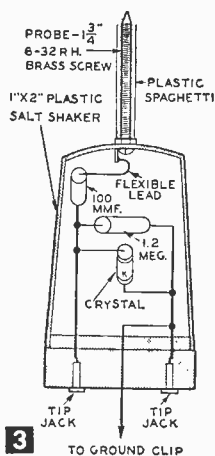

MATERIALS LIST—POCKET SIGNAL TRACER

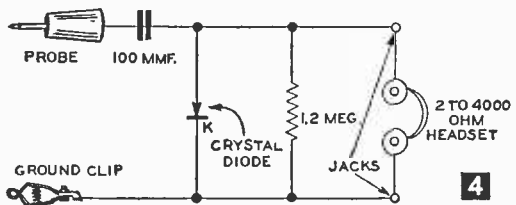- 1 Small plastic container (salt shaker, etc.)
- 1 Germanium crystal diode (1N34, 1N34A, 1N60, etc.)
- 2 Metal phone tip jacks (ICA)
- 1 Small battery clip
- 1 100 mmf. mica or ceramic capacitor
- 1 1.2-megohm, 1/2-watt resistor
- 1 1 1/2 x 6-32 RH brass screw and nut, soldering lug, short length radio spaghetti, and 2 ft. flexible hook-up wire.



The signal tracer is wired as shown in the pictorial plan (Fig. 3) or schematic diagram (Fig. 4). Drill three holes in the base or cap of the plastic container; two 1/4 in. holes for the phone jacks, and a 1/8 in. hole for the flexible lead to ground (B-) clip. Drill a single hole in the plastic shaker top for mounting the probe.

The probe is an ordinary brass machine screw with a round head (1 1/2 in. long; size 6-32) with the end ground to a point. A short length of flexible insulated wire is secured to a soldering lug. Slip the lug over the screw and mount in

the plastic housing with a 6-32 hex nut. Complete the probe by forcing a 1 1/2 in. length of radio spaghetti over the threads, leaving just the sharp screw tip exposed (Fig. 5).

The pigtail leads furnished with the three components are long enough and rigid to allow direct soldering without use of hook-up wire except for the short flexible probe connection and about 16 in. of flexible lead for the ground clip.

Here's how to use the tracer for tracking down radio set failures when you have completed wiring it. Starting at the radio set's antenna, it will

pick up the initial radio frequency (R.F.) signal transmitted from a radio station. From that starting point, you can follow the signal through the intermediate frequency (I.F.), detector and audio stages.


At any point between antenna and final audio output, the circuit breakdown will be indicated when the signal is no longer heard through the headphones attached to the signal tracer. The

defective tube, resistor or capacitor will show up between the last good stage, and the adjacent stage where no signal is heard.


Fig. 6 shows a schematic diagram of a 5-tube superheterodyne table set employing miniature tubes. Other, older table-model sets will have the same type circuit, but employing the older and larger GT octal-base tubes. Except for tube base numbering and positions, signal tracing in either of these popular type sets (and basically in all others) is the same.

With 2000- or 4000-ohm headphones inserted in signal tracer jacks, attach the ground clip to the radio set's B- circuit. The black wire terminal of the cardboard electrolytic capacitor or the can lug of the metal jacketed electrolytic capacitors are connection points for the B- circuit. On sets wired with the chassis "hot," the clip may be attached directly to chassis (Fig. 1).

To locate the defective sec-

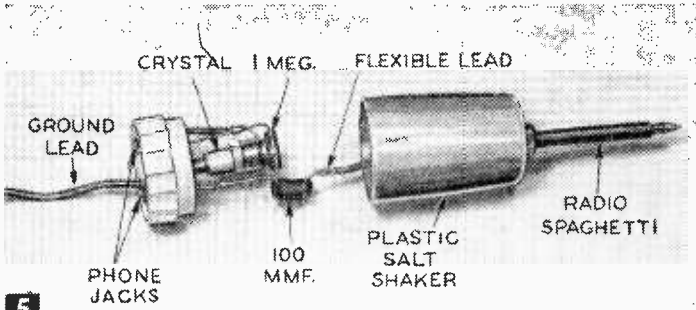

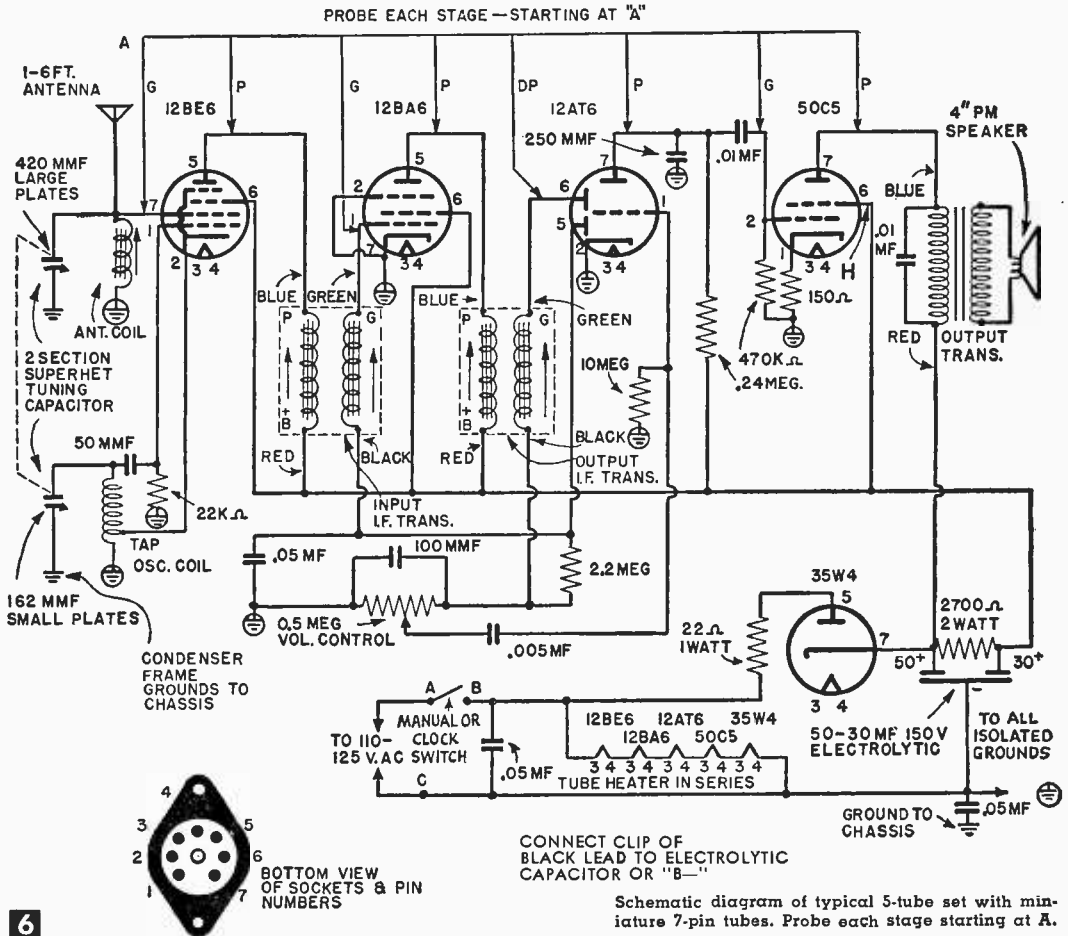5 Exploded view of actual components as built into plastic salt shaker. Flexible lead connects between probe and 100-mmf. coupling capacitor.



tion of the receiver, first find out if the trouble is not simply a *blown* tube. On popular *ac-dc* sets, one blown tube extinguishes all tubes. If the tubes light up, tune the set so the dial is on the frequency of a nearby station which came in with the most powerful signal when the set was working. Then, starting with the first R.F. or converter tube if there is no R.F. tube in the circuit, touch the tracer probe to the grid lug of the tube socket. Continue on to the plate of the same tube. Follow through—grid and plate, grid and plate of each tube in set. Assuming tubes are warm and show a visible glow, you will eventually reach a spot where you won't hear a signal.

Suppose you pick up the signal on the *grid* pin of the 12BA6 (or 12SK7GT on a set with *GT* tubes), but nothing when probe is placed on the *plate* lug of same tube socket. The trouble could be due to any of the following: defective tube; open or cold solder joint at cathode, or screen grid, lack of B+ voltage to this tube due to broken lead elsewhere in wiring, open primary winding in I.F. transformer, or defective tube socket.

The signal tracer will not single out the exact component causing set failure. It will, however, localize the source of trouble to a component or connection at the tube where no signal can be picked up off the *grid* or *plate* lug. If, for example, the probe receives a signal off the *plate* lug of the 12AT6 (or 12SQ7GT) detector, but nothing comes through when probe is moved over to *grid* of the 50C5 (or 50L6GT) output tube, look for an open .01 or .02 *mfd.* coupling capacitor.

At the point where the signal is lost, bad capacitors, resistors, open circuits or combinations of these components will prove to be the culprit. Defective resistors are often apparent on sight by their charred appearance. Bad capacitors are frequently identified by wax leakage on chassis. "Cold" soldered joints are also identified in many instances on sight. If wiggling the suspicious wires restores speaker operation, resolder leads.

Defective components do not necessarily exhibit any outward signs of failure. If loose wires are not the cause of failure, replace the resistors or capacitors in the immediate vicinity of breakdown with components known to be good.

This pocket signal tracer may be used with all types of sets. An inexpensive radio tube basing manual will provide identification of the grid (or diode) and plate socket lugs of sets other than that shown here.



D. Vietor

How to Read Color Code on Resistors

All carbon resistors are produced and color-coded under standards set by the RETMA. Under these standards the user is assured of a wide range of values and of a universal color-coding system that permits easy identification of any carbon resistor. To determine the value of a resistor, hold it with the colored bands reading from the left end, as illustrated, and refer to the chart.



BAND A		BAND B		BAND C		BAND D	
Color	Value	Color	Value	Color	Decimal Multiplier	Color	Tolerance
Black	0	Black	0	Black	X 1	None	± 20%
Brown	1	Brown	1	Brown	X 10	Silver	± 10%
Red	2	Red	2	Red	X 100	Gold	± 5%
Orange	3	Orange	3	Orange	X 1,000		
Yellow	4	Yellow	4	Yellow	X 10,000		
Green	5	Green	5	Green	X 100,000		
Blue	6	Blue	6	Blue	X 1 Million		
Violet	7	Violet	7	Violet	X 10 Million		
Grey	8	Grey	8	Gold	÷ 10		
White	9	White	9	Silver	÷ 100		

The first band (A) shows the first figure of the resistor value, the second band (B) shows the second figure, the third band (C) indicates the number of zeros to add. The fourth band (D), which is not included on all resistors, merely indicates tolerance: silver for ± (plus or minus) 10%, gold for ± 5%. If the (D) band is omitted, the tolerance is ± 20%.

Here is an example: Band A yellow, band B violet, band C yellow, band D silver = (4) (7) (X10,000) (±10%) or 470,000 ohms, ± 10% tolerance.

RETMA
COLOR
CODE
STANDARD



RESISTORS

Note: Molded tubular paper capacitors have same color coding.

Power Supplies for Transistors

By W. F. GEPHART

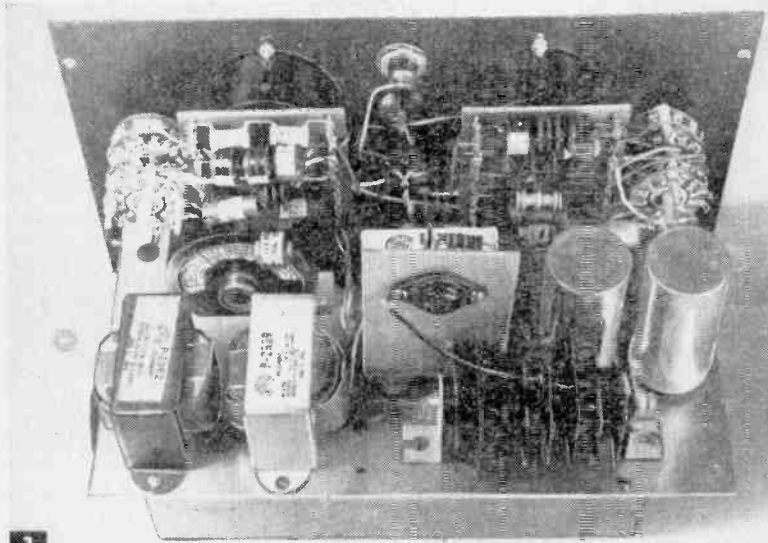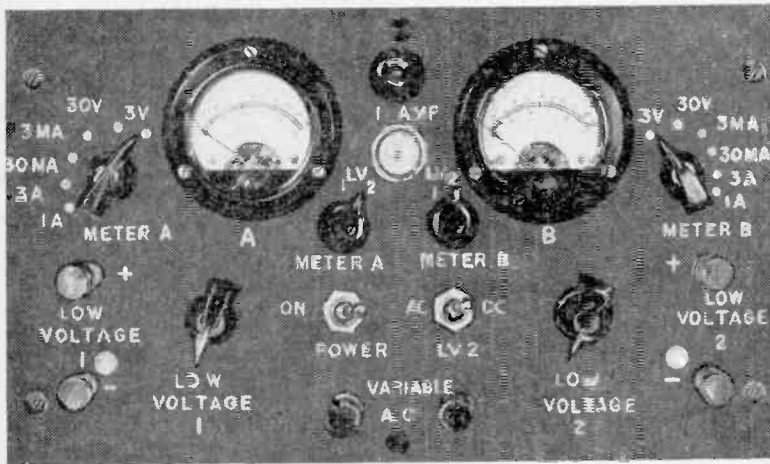To eliminate the expense (and bother) of using batteries when you are experimenting with transistors, build this ac-supplied variable power supply



1

Front and back panel views of dual power supply schematicized in Figs. 6 and 7. Note in back panel view the meter resistor mounting and the "heat sink" mounting of power transistor (center of photo).

(1:200 ratio) will do. A versatile transistor power supply, however, need only furnish between 1.5 and 30 v (1:20 ratio)—but with currents up to nearly 1 amp (1:1000 ratio), and with an extremely low ripple in order to simulate battery operation. Due to the wider variations required, the high currents involved in power transistors, and the need for good filtering, then, several problems arise.

Figure 4A shows a simple power supply for transistor equipment. While it is fairly suitable for powering low-powered devices, it is not satisfactory for bench or experimental work. Even if R_3 were made variable, the voltage output would still be dependent upon the current being drawn, which causes a voltage drop across R_1 and R_2 . This type supply is also unsatisfactory because one side of the line voltage is connected to the output.

Figure 4B shows a simple bench-type supply. The danger of contact with line voltage is eliminated in this unit by using a transformer, and the lower resistance within the circuit permits greater control of the output voltage with variable resistor R_2 . Using a choke (L) instead of a resistance (as in

THE design of a variable power supply for conventional (pre-transistor) radio work is relatively simple: Usually, a voltage range of 50-500 v (1:10 ratio) and a current range to 200 ma

4A) provides better filtering, but again presents the problem of a varying voltage drop as the current drawn varies. Furthermore, the amount of current that can be drawn is limited by the


choke. While chokes capable of handling up to 300 or 400 *ma* are readily available, chokes capable of handling higher currents are bulky, heavy and quite expensive. Also, to minimize bleeder current (and thus minimize voltage drop across the choke with no load), the resistance R_2 has to be relatively high, yet must be capable of handling full load current, thus presenting problems at high currents. With a value of 2500 ohms, for example, and a full load current of 750 *ma*, R_2 would have to be rated in excess of 1000 watts. This type of bench variable voltage supply can be used, however, up to about 50 *ma* if the components are chosen properly.

Figure 4C shows the circuit to be used for a high-current, well-filtered variable supply. The output is isolated from the line by transformer T_2 and variation in voltage is secured by varying the primary voltage of T_2 with an auto-transformer (T_1). This permits variation on the high-voltage, low-current side, enabling the use of a small auto-transformer. The current-limiting problem introduced by the choke is eliminated by using a power transistor (or two), providing excellent filtering with a small, but relatively constant voltage drop.

Transistors, like pentode tubes, "saturate" beyond certain bias points. That is, beyond these points, variation in input signal will have no effect on the output. If a transistor is biased beyond a certain point, ripple variations included in the *dc* input will not be included in the *dc* output. The same could be done with an ordinary pentode tube, except that ordinary pentodes are not capable of handling the high currents involved. The bias on the transistor is furnished through the resistor-capacitor network of R_1 , C_2 and R_2 which provides sufficient filtering for bias purposes. The output current flows through the collector-emitter circuit, and with final filter capacitor C_3 , ripple is less than .01%, equal to battery supply for virtually any application.



As pointed out, the transistor-filter circuit is only required when current requirements are fairly high, and the circuit in Figure 4B is satisfactory for most low-current applications. If very pure *dc* is required, the filter section of Fig. 4C (consisting of C_1 , C_2 , C_3 , R_1 , R_2 , and V) can be used with the circuit of Fig. 4B, substituting it for the choke-capacitor filter (L , C_1 and C_2), and still use an output resistance for voltage variation. Filtering action is even better, since the transistor bias is constant in this case.

In designing a bench supply, voltage requirements, as well as current requirements, should be considered. Even some low-current circuits use a fairly high ($22\frac{1}{2}$ to 30) voltage. Several of the components will involve a voltage drop, and allowance for this should be made when planning the output voltage. In low-current supplies (50 *ma* or less) germanium diodes make excellent rectifiers and have less voltage drop than selenium units. When using chokes, select a happy medium between inductance and resistance, to minimize voltage drop.

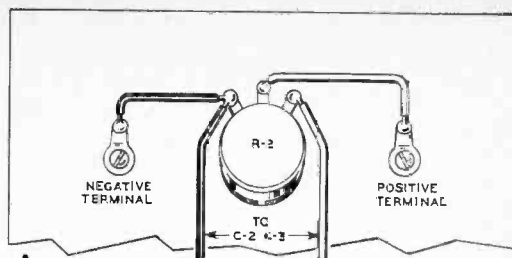

A PICTORIAL

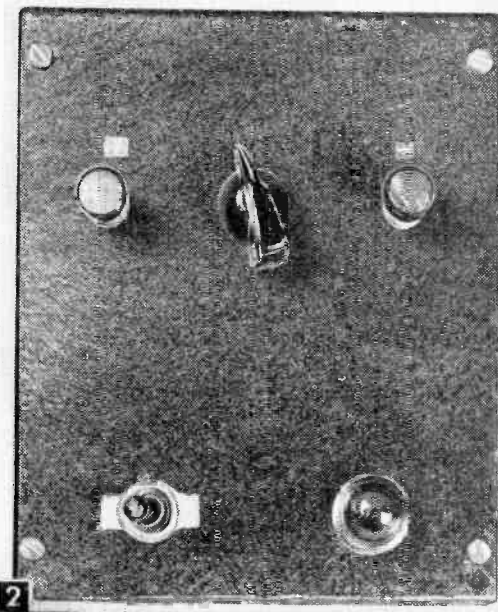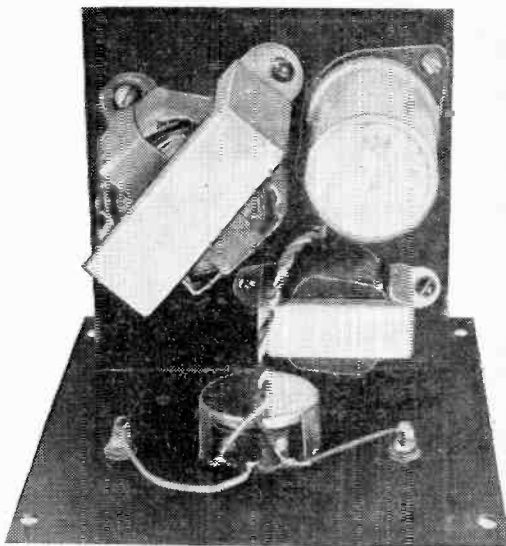Front and back panel views of power supply schematized in Fig. 4B, is shown above and below. Under-chassis wiring is shown in Fig. 3.



identical with that in Fig. 4B, and one circuit similar to that in Fig. 4C, and has built-in meters and switching circuits. The twin meters can measure voltage or current for either supply, or can be switched so that the meters measure voltage and current of either supply, keeping both circuits isolated from each other.

The schematic for this dual supply is shown in Fig. 6. Meter jacks, instead of meters and related switches, are shown, since the elimination of meters, shunts and switches greatly reduces the cost of the unit. If it is desired to build the complete unit on a "progressive" basis, holes for the meters and switches should be drilled in the panel at the time of construction, the switch holes plugged with hole plugs, and the meter jacks mounted in plastic or Bakelite plates mounted in the meter holes. (In any event, the jacks must be insulated from the chassis.) Then later, if it is desired to add the meter circuits, it can be done without drilling into a panel on which components are mounted and wiring completed.



In Fig. 6, a second transistor (V_x) is shown in dotted lines, parallel with V_1 . This is required only if the desired output current is to exceed 700 ma and if used, should be mounted on a "heat sink" (as is V_1). This "heat sink" (which is common to the collector) should be insulated from the chassis, to keep the chassis and cabinet isolated. Also, if V_x is used, the value of R_3 should be reduced to approximately half of the value given in the Materials List.

In the high-current supply, an auto-transformer, two filament transformers, and a germanium rectifier provide the dc voltage. While a high-current selenium rectifier would be somewhat cheaper, the voltage drop would require another filament transformer, and stability would not be as good at low voltages and current.

The high-current supply, using the parts specified, furnishes in excess of 30 v (transistor limit) with no load, and slightly over 19 v at 700 ma (full load). If current in excess of 700 ma is desired, the larger rectifier mentioned in the Materials List, as well as the second transistor V_x , should be used. Under those conditions, loads to about 1.1 amperes would be permissible.

In Fig. 6, S_2 switches the transformer output to a set of binding posts, since it was felt that there would sometimes be a need

for variable ac between 0 and 50 v. Fig. 7 shows the dual meter circuits used. The input leads of these circuits are connected to points "A", "B", "C" & "D" in Fig. 6, and the jacks cut out at the points marked "X". The values of the shunt resistors used are not furnished, since they will depend on the meters used. In the unit shown, the meters were surplus 0-500 microammeters, although 0-1 ma meters would do just as well.

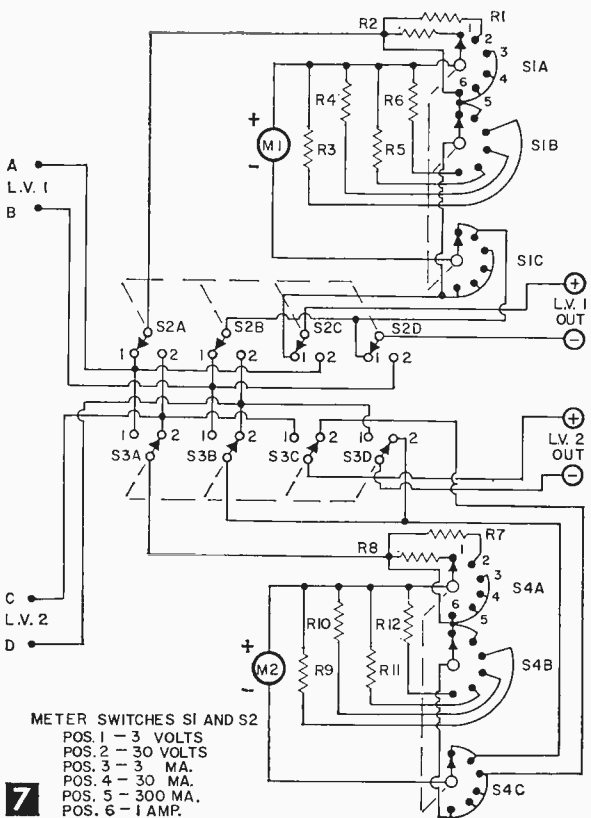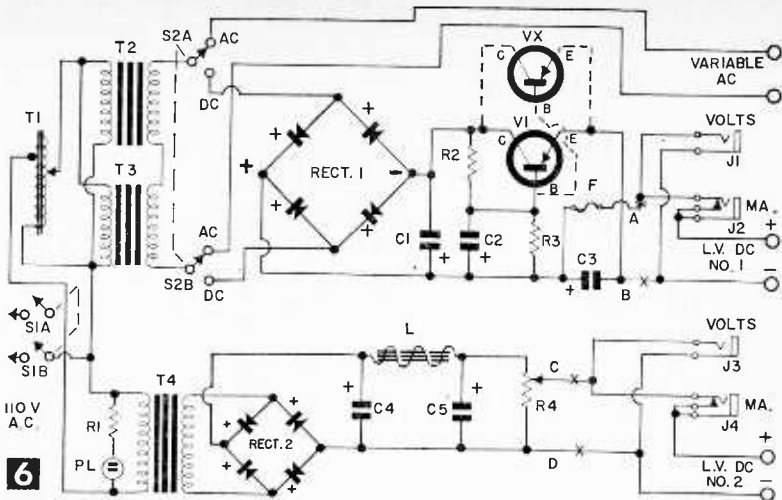

METER SWITCHES S1 AND S2
 POS. 1 - 3 VOLTS
 POS. 2 - 30 VOLTS
 POS. 3 - 3 MA.
 POS. 4 - 30 MA.
 POS. 5 - 300 MA.
 POS. 6 - 1 AMP.

MATERIALS LIST—TRANSISTOR POWER SUPPLIES

Shown in Figures 2, 3, 4B, and 5

- R1 56,000 ohms, 1/2 watt*
- R2 10,000 ohm potentiometer
- C1, C2 100-100 mf. 50 volt (Cornell-Dublier B0085 or Mallory WP202.5)
- T 25 volt filament transformer (Merit P-2962)
- L 4.5 hy, 50 ma., 200 ohm choke (Merit C-2977)
- Rect. Four 1N48 diodes, bridge-connected
- PL NE-51 neon bulb
- Small cabinet with chassis (Bud C-1796), pilot light holder, binding posts, knob, miscellaneous hardware

Components shown in Figs. 1 and 6

- R1 56,000 ohm, 1/2 watt*
 - R2 470 ohms, 1 watt
 - R3 1200 ohms, 1 watt
 - R4 10,000 ohm potentiometer
 - C1 500 mf. 50 volt (Cornell-Dublier 5005)
 - C2 250 mf. 50 volt (Cornell-Dublier 2505, Sprague TVA-1312, Mallory TC-50025)
 - C3 50 mf. 50 volt
 - T1 Auto-transformer, 0-130 volts @ 1.25 amp. (Superior Type 10, Standard Electric 100BU)
 - T2, T4 25 volt filament transformer (Merit P-2962)
 - T3 12.6 volt filament transformer (Merit P-2959)
 - L 4.5 hy, 50 ma., 200 ohm choke (Merit C-2977)
 - Rect. 1 70 volt, .7 amp. Germanium Bridge (General Electric 4AJ211AB1AC1) Note: If higher current desired, use 70 VAC 1.4 amp. (General Electric 4AJ211AB1AC2)
 - Rect. 2 Four 1N48 diodes, bridge-connected
 - S1 DPST toggle
 - S2 DPDT toggle
 - PL NE-51 neon bulb
 - J1, J3 Open circuit jacks
 - J2, J4 Closed circuit jacks
 - Cabinet (Bud CC-1092), aluminum for chassis, binding posts, knobs, miscellaneous hardware
- * Not required if included in pilot light holder such as Dialco series 952208 or 95408X.

Components shown in Fig. 7

- R1 through R12 See text
- M1, M2 See text
- S1, S4 3 pole, 6 pos. rotary switch (Centralab 1421, Mallory 1335L) Note: Mallory 3236J can be used if 20° spacing is acceptable
- S2, S3 4 pole, 2 position rotary switch (Mallory 3242J)

The most accurate means of determining shunt and dropping resistor values is to use an accurate resistance decade, a variable voltage source, and an accurate voltmeter and milliammeter. In this method, voltage-dropping resistances are selected by taking a known voltage, feeding it into the proposed meter through the decade, and adjusting the decade for the desired reading. Current shunts are determined in a similar manner, by establishing a known current through a load, placing the proposed meter in the circuit (with the decade connected across its terminals), and adjusting the decade for the desired reading.

If equipment is not available, required resistances can be determined by calculations, using the following formulas:

For voltage series resistance:

$$R_s = \frac{E_r}{I_m} - R_m$$

- R_s —Series resistance required (ohms)
- E_r —Desired full-scale range (volts)
- I_m —Full scale range of meter (amperes)
- R_m —Internal resistance of meter (ohms)

For current shunt resistances:

$$R_s = \frac{I_m R_m}{I_r - I_m}$$


- R_s —Shunt resistance required (ohms)
- I_m —Full scale range of meter (amperes)
- R_m —Internal resistance of meter (ohms)
- I_r —Desired full scale range (amperes)

In the latter formula, at high current values, I_m may be disregarded in the formula as being insignificant.

The meter ranges on the low-current supply (No. 2) need not have as high current ranges as the No. 1 meter. The meter selector switches (S_2 and S_3 in Fig. 7) permit voltage reading from either output, but current readings only on the associated circuit. For example, with both S_2 and S_3 on Position 1, meter M_1 will read either the voltage or current of output 1, and meter M_2 will only read voltage of output 1.

In the unit shown in Fig. 1, the meter resistors were mounted on terminal boards fastened to the meter terminals, saving space and wiring. (A few of the components pictured in Fig. 1 are not exactly those specified in the Materials List.)

Emergency Lite

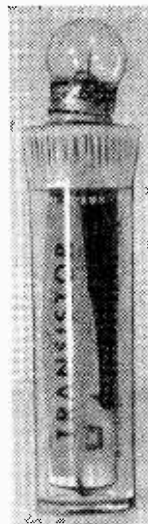


AN investment of about a quarter and five minutes of your time converts a small plastic bottle into a pocket-size emergency light. The bottle doesn't cost you a cent. If you're a transistor experimenter, you can use one of the bottles in which General Electric transistors are packaged (this same kind of bottle is frequently used by pharmacists as a pill box). In addition to the bottle you need only a flashlight bulb and a small pen-lite battery.


To make the emergency lite, ream a hole in the bottle top just large enough to allow the bulb to be screwed into it. Solder a piece of thin insulated wire to the shell of the bulb. I used #28, silk-covered magnet wire. Solder

the other end of the wire to the center terminal of the battery. Insert the battery and bottle top, with bulb, into the bottle with the center battery terminal down.

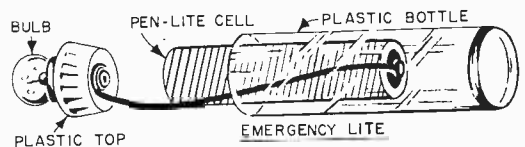To turn the light On, push the bottle top on tight. To turn it Off, loosen the top slightly.—FORREST H. FRANTZ.



One-Transistor

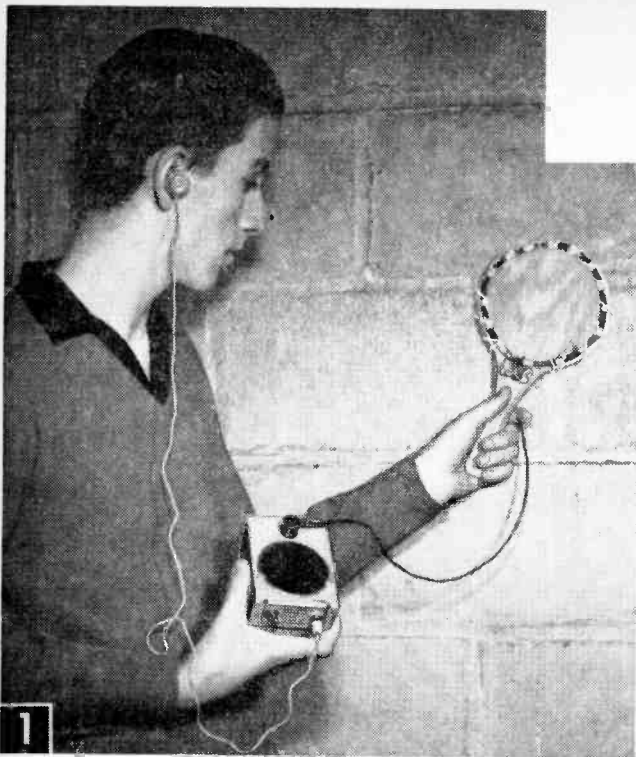

Our transistorized metal detector can be held in the hand or easily fitted with a clip for attaching to your belt. Probe coil passed over wall signals when hidden metal object is present.

Track down hard-to-find metal objects under walls, floors and paving with this pocket-size low frequency detector

By THOMAS A. BLANCHARD

WHILE you may never locate buried treasure with this little metal detector, unless the walls of your house contain a cache left behind by a former occupant, you are certain to use it often to track down buried "headaches." By running the detector's search coil over plaster, stone, brick or wood walls, ceilings or floors (Fig. 1), such concealed objects as water, steam and gas pipes can readily be traced. This applies equally well in the case of electrical conduit, BX cable, lath nails in 2x4 studs where wood lath and plaster were used, steel lath and braces. Outdoors, the detector will find manhole covers, water and gas shut-off valves that have been covered over by earth up to a 12-in. depth, cement or asphalt.


This transistorized metal detector is similar in operation to our vacuum-tube gadget (see p. 116, *Home Electrical Handbook*, Vol. 3, published by SCIENCE AND MECHANICS, price 50¢). However, there are several distinct advantages over the other type: our new unit is considerably smaller,

much more stable, requires fewer components, and uses just one small, long-life transistor battery.


The transistorized Hartley oscillator consists of a 74-turn loop, 5¼ in. in dia. and tapped at the 30th turn. Direct-coupled to the collector end of the oscillator coil is a 96-turn loop which, in conjunction with a crystal earphone shunted with a 1N34A germanium diode, serves as the detector circuit. A miniature 365 mmf. variable capacitor tunes the circuit in the more stable long wave frequencies of 150 to approximately 455KC.

The metal detector can be assembled in any radio utility box measuring 2¼x3x4 in. or more. If you use a government surplus Signal Corps BC-366 Jack Box (Figs. 1, 4 and 5), remove all its original components so just the aluminum die cast box is left. Fit phone jack, toggle switch and variable capacitor into ¾-in. holes already in the box (Fig. 4). Enlarge a fourth ¾-in. hole to ⅝ in. and fit with a 5-pin miniature cable socket to which the search coil can be attached or detached from at will.

On a 2½x2¾-in. piece of perforated phenolic plastic mount three "flea clips" for securing the transistor, along with diode, r.f. choke, capacitors and resistors (for wiring details see Figs. 2 and 3). Thread the pig-tail leads through the perforations in the plastic panel to provide a rigid components assembly. Mount with 6-32 machine screws through three built-in studs (Figs. 4 and 5). If you use a regular utility box, however, one multi-lug tie strip will be sufficient for securing the small components.

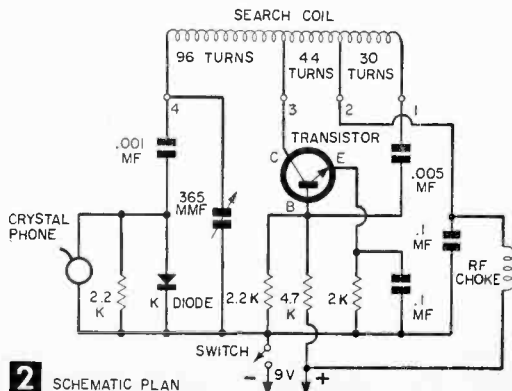

6 PROBE CONSTRUCTION

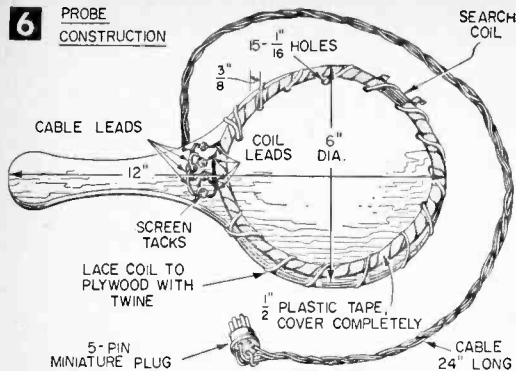

Note that we have used a cheap midget crystal earphone with the metal detector rather than the magnetic headphones specified for the majority of transistor circuits. The crystal phone is non-inductive and will not adversely influence the function of the search coil. You may be able to use a high resistance magnetic earphone by disconnecting the 2.2K resistor shunted across the phone jack. However, a crystal earphone can be purchased for about \$1, so experimentation with a magnetic phone is unnecessary.

When connecting the phone jack, carefully observe soldering lugs. One lug is riveted to the threaded mounting sleeve and is the grounded connection. The remaining lug connects to insulated plug tip contact to which .001 mfd. capacitor connects (Fig. 3). Reversing jack connections will create a short-circuit across phone, making detector inoperative.

Using the Detector. With search coil connected and switch on, a series of oscillator tones will be heard as the variable capacitor knob is rotated.

MATERIAL LIST—1-TRANSISTOR METAL DETECTOR

No. Req.	Description
1	Signal Corps BC-366 "Jack Box" or radio utility box
1	2 1/4 x 3 x 4" or larger
1	1/6 x 2 1/2 x 2 3/4" perforated plastic plate for BC-366 box
1	standard or miniature phone jack
1	5-pin miniature plug (Amphenol 71-5S)
1	5-pin miniature socket (Amphenol 78-5SS)
1	365 mmf. miniature variable capacitor (Lafayette MS-215)
1	bar knob for above
1	transistor socket or 3 "flea clips"
1	S.P.S.T. toggle switch
1	1/4 lb. spool #28 d.c.c. magnet wire (2 1/2 oz. or 255 ft. used for search coil)
1	RCA #VS300 9v. transistor battery or equiv.
1 pr	battery snap connectors
1	2.5 or 5 millihenries R.F. choke (Nat'l R-100)
1	general purpose germanium diode (1N34A)
1	N-P-N R.F. transistor (Sylvania 2N233, GE 2N170 etc.)
RESISTORS (all 1/2 watt)	
2	2.2K (2200) ohm
1	2K (2000) ohm
1	4.7K (4700) ohm
CAPACITORS	
2	0.1 mfd. paper tubular
1	.005 mfd. paper tubular
1	.001 mfd. paper tubular

Misc: Hookup wire, hardware as required; miniature crystal earphone (Lafayette MS-111); dial optional


A high-pitched tone will be heard with knob at zero; as you advance the control the tones will become lower and finally break off.

For silent operation, set the dial to the point where low tones cease. Now move the probe toward a metal object and suddenly you will hear a "cry-baby" tone similar to that produced when a phone number is incorrectly dialed. When the probe is moved away the tone will stop.

Several points will be found in rotating the tuning knob where especially high, crisp whistles are heard. In this case, as the probe approaches a concealed metal object the pitch of the steady tone will change abruptly. While you may find the steady tone a more sensitive detection method, it may prove uncomfortable to your ear.

Safe Soldering of Transistor Leads to Heavy Contacts

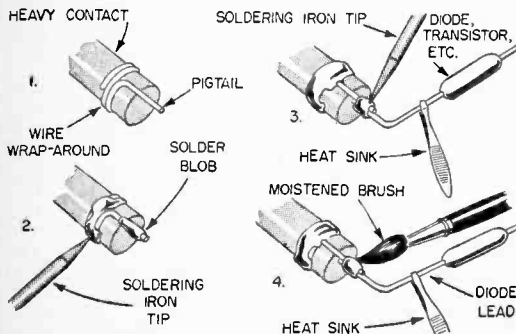• A transistor lead can be soldered to a relatively massive terminal post or lug without damage to the diode or transistor. To do this, wrap a small diameter hookup wire around the post or lug as in Fig. 1, leaving a pigtail for soldering to the lead from the diode. Solder the



wrap-around (see Fig. 2), leaving a small drop or blob of solder hanging down from the pigtail.

Apply the tip of the soldering iron to the top

of the pigtail (Fig. 3), and reheat just enough to melt the solder. Bring the diode or transistor lead, which has been inspected and tinned if corroded, to it rapidly just as the solder melts, using a heat sink (such as pliers, hemostat or tweezers). Move the iron tip to rapidly flow the solder blob onto the transistor or diode terminal or lead.

Now apply a previously moistened brush to the pigtail and lead (Fig. 4), moving it back and forth. Water will rapidly cool the lead. Re-moisten the brush and apply it to the pliers or other heat sink. Allow some moisture on the diode lead as well as the large terminal.

Phono Turntable Repair


• Poor reproduction from a phonograph having the rim-drive type turntable mechanism is usually caused by slippage of the rubber-tired drive wheel. To renew the grip of the rubber tire, sand it lightly with sandpaper. A non-slip dial compound (such as General Cement's *Non-Slip*, 2 oz. approx. 38¢) applied to the wheel will also cure slippage.—JOHN A. COMSTOCK.

Is your TV set giving sub-par performance?

HOW can you tell if the line voltage of your house current is lower than it should be? Very simply, merely plug the instrument described in this article into any wall outlet and get an immediate reading of the voltage. You will have good reason to suspect low voltage, if your electric lights are not delivering their full candlepower brilliancy; if your electrical appliances are not working at peak efficiency or, which is more noticeable, you get a reduced coverage on the screen of your television set.

There are two possible reasons for low voltage. If the low voltage symptoms are noticeable only during the evening hours when the current drain in the surrounding neighborhood is greatest, it usually indicates that the trou-


Build a Meter to Check on Line Voltage

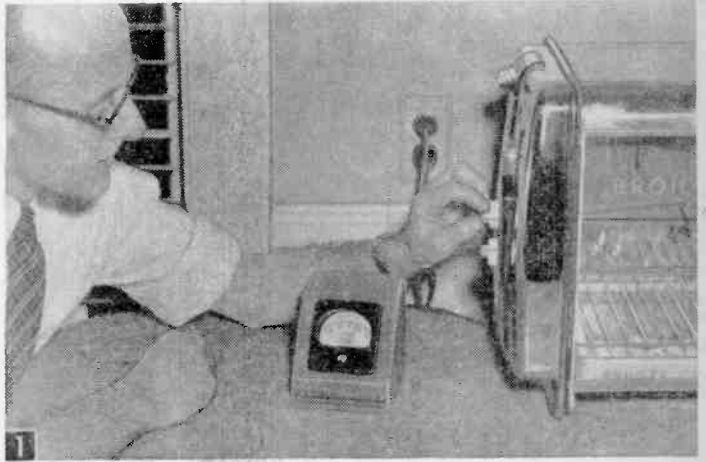


Using the voltmeter to check the drop in voltage in a circuit to which a 1320 watt broiler has been connected.



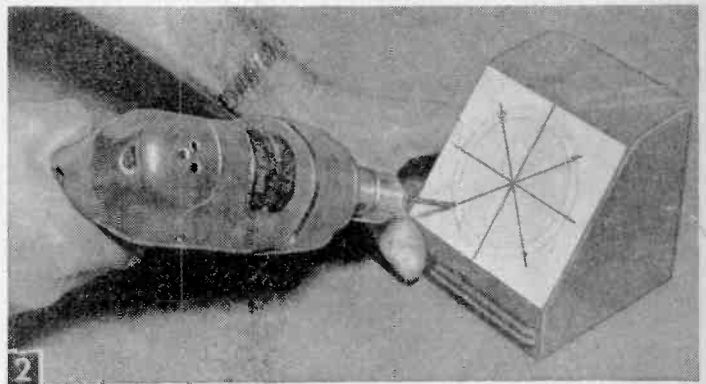The open space in the back of the case is convenient for storing the cord when not in use.




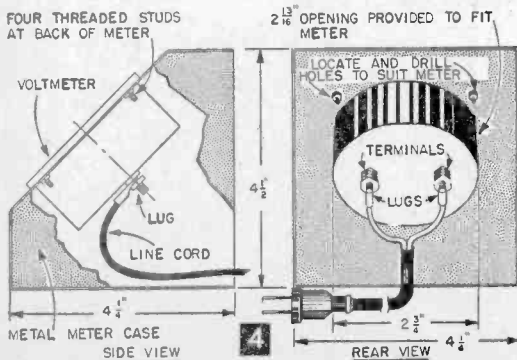Drilling meter-mounting holes located with the aid of a cardboard template taped to face of case.



ble is in the lines or pole transformer outside of your home which, of course, is beyond your control. When this is discovered, notify your power company and their representatives will investigate, and rectify the trouble. Most power companies try to keep their voltage as near 120 volts as possible. However, the voltage will vary somewhat depending upon the distance your home is from the pole distribution transformer, the type of customer load and the number of customers served from an individual transformer.

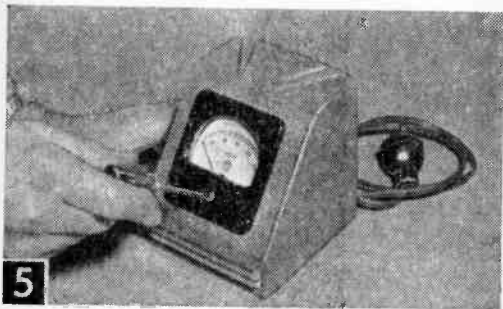The other reason for low voltage is due to inadequate house wiring, for which the home owner is responsible. This is voltage drop developed on branch circuits when appliances are plugged in.



Using a small screwdriver to adjust the pointer to the zero position.

MATERIALS LIST

- 1 A.C. 0-150 panel type, rectangular voltmeter. Simpson model 57, Triplett model 337-S or other make. 3" size. (Lafayette or Allied Radio)
- 1 sloping panel meter case with 2 3/16 in. opening. ICA # 3996. (Lafayette or Allied Radio)
- 3 ft plastic or rubber parallel lamp cord
- 1 rubber attachment plug cap
- 2 solder type terminal lugs with 1/4" ring opening
- 4 nuts and washers to fit meter mounting screws (Lafayette Radio, 165-08 Liberty Avenue, Jamaica, N. Y. Allied Radio, 110 N. Western Avenue, Chicago 80, Ill.)


For example, a test was made using a 1320 watt broiler in a house wired about 25 years ago with #14 wire circuits having both lights and appliance wall receptacle outlets on the same circuit. The meter (Fig. 1) was first plugged in and the line voltage found to be 120. The broiler was then plugged into the same circuit and the meter registered a drop to 109 volts. When the test was repeated with the light on, a noticeable drop in light value was seen. Today the National Elec-

trical Code demands that separate circuits without light outlets and wired with #12 wire, fused at 20 amperes be provided in rooms where heavy-duty appliances are normally used. When the same test was conducted on a properly wired appliance circuit, the voltage drop was only 3 volts or a drop from 120 to 117 which is normal.


To build this voltage tester, first obtain the parts given in the materials list. Then lay out and drill the holes to clear the four attachment screws located at the back of the instrument (Fig. 4), by taking center-to-center measurements of the screw spacing. Lay out this information and a circle the size of the meter on a piece of thin cardboard and attach it to the case with Scotch tape (Fig. 2). Be sure to center the circle with the opening in the case. The drill should be of a size to provide a little extra clearance for the screws so that the meter can be centered with respect to the opening.

Solder two terminal lugs to a 3 ft. length of cord equipped with a plug cap at one end and connect the lugs to the meter terminal posts. The cord and plug can be coiled up neatly in the meter case through the open back as in Fig. 3 when not in use. Adjust the pointer on the meter to zero by turning the screw as in Fig. 5 and your meter is then ready for use. If at any time the pointer is found off the zero mark simply re-adjust it.

This tester was designed for use on all ordinary circuits with a voltage not over 150 or the standard 115-120 lighting and appliance circuits. It should never be connected where the voltage exceeds this maximum value or the meter will immediately be ruined. Such outlets do exist in some homes, such as 240 volt supply for air conditioners and similar heavy duty equipment. If it were necessary to make tests at these outlets, a unit would have to be constructed which contained a meter with a 0-300 volt scale.— HAROLD P. STRAND.

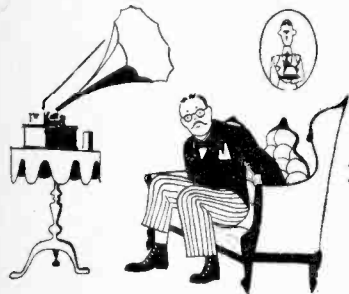

"Working-in" a Speaker

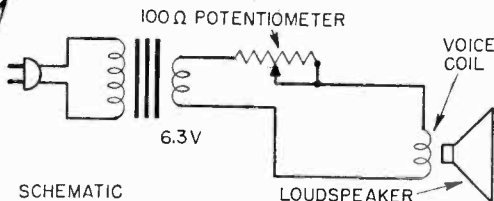


TO IMPROVE the bass response of an otherwise good loudspeaker, try softening up the edge suspension to permit greater and easier cone vibration. To do this, connect the voice coil in series with a 6.3 volt filament winding, using a current-limiting rheostat, as shown in the diagram. Any 6.3 volt filament winding will do, either as available in any convenient piece of radio apparatus, or using a separate filament

transformer (as shown).

Place the speaker where a rather loud 60-cycle (50-cycle in Canada) buzz will not irritate you, and apply power, using

the entire 100 ohms in series at first. Then gradually reduce the series resistor until the cone is vigorously vibrating at its maximum safe amplitude. (Use judgment here as it is possible to rip the cone out entirely). Allow it to vibrate thus for five or six hours.

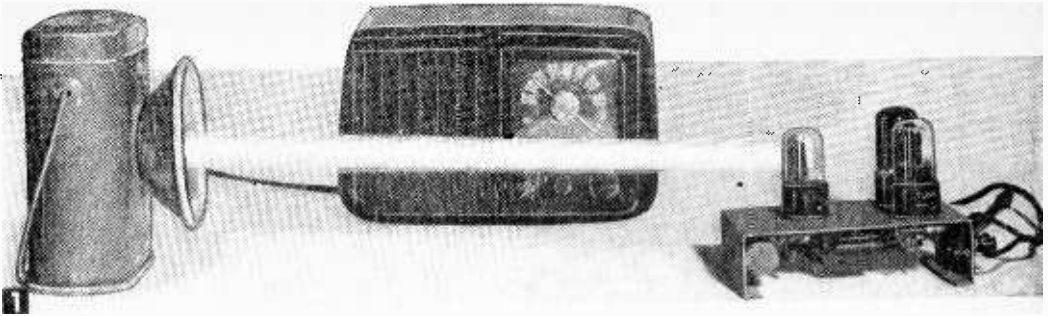Now reconnect the speaker to your hi-fi amplifier. The improvement in bass reproduction will amaze you.—C. F. ROCKEY




Program from radio is converted to light beam and sent via Delta lantern to photo-electric receiver at right. Proper spotlight or light source will transmit close to 1/4-mile. Beam is painted in here to clearly indicate action.

Talking on a Light Beam

AMAZING as the feat of talking over a light beam may seem, the idea is not new. For some 25 years movie sound reproduction in your local theater has been accomplished with a phototube and light beam. Running along the edge of the film is a narrow "sound track." The track contains little zig-zag streaks of varying lengths, or a ribbon-like strip varying from opaque to nearly transparent. As the sound track passes between light beam (exciter lamp) and phototube, the light striking the phototube literally "flutters." This "flutter" is the modulating medium—whereby a flickering light stream is converted into voice or music!


Radio experimenters can now build this simple transmitter, which broadcasts over a light beam through an ordinary radio receiver

By THOMAS A. BLANCHARD

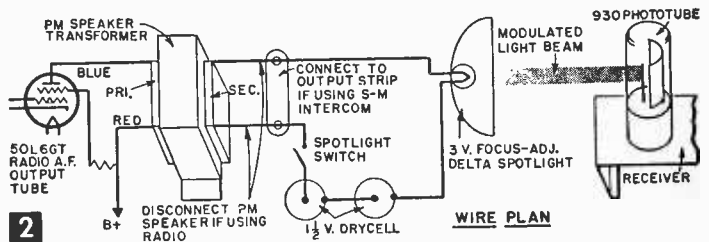

This is the same idea employed in this radio experimenter's model. However, modulation is accomplished entirely by electrical principles whereas movies are mechanically modulated, as by film. You'll find this light beam transmitter easy to construct, since a small table radio may be incorporated in its design (Fig. 1). In order to convert the sound that usually comes out the speaker to a modulated light beam, you need only disconnect the speaker and install a concentrated spotlight in series with the set's output transformer (Fig. 2).

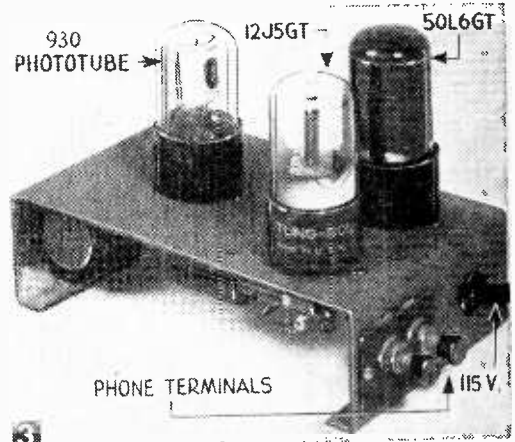The two uncovered copper wires from the output transformer are disconnected from the PM speaker cone. Solder two extension leads to these wires so that the secondary of the radio transformer may be wired in series with a battery operated light source (an ac light source will not



Light beam receiver is assembled on simple two-fold metal chassis for easy wiring.


work). With spotlight switch closed, and radio tuned to a station, the bulb will flicker madly. Now when this beam is aimed on the phototube in the light beam receiver, you will hear the program from the radio set—via light beam!

The ac impulse from the output transformer adds to or subtracts from the 3-volt battery voltage, which causes the bulb's light output to vary at the same frequency as the applied signal (or, in other words, the impulse bucks the reactance effect of the secondary winding, causing light modulation). The radio output transformer operates like an ultra-high-speed rheostat in the spotlight circuit, causing the light intensity to vary faster than the eye can see these changes. To transmit your voice over the radio, attach a mike and preamplifier into the radio phono connection. Better yet, you can use a home broadcaster mike (modulated oscillator type) available from radio supply houses.

You may find that you need to modify the secondary winding of the output transformer. For example, if the light intensity is too bright with no noticeable "flutter," more turns of #26 magnet wire should be added. On the other hand, if spotlight is too dim, remove some of the turns from secondary winding.

Rather than mutilate the set's transformer (which is often clamped to the PM speaker frame) it is best to buy a separate transformer (they cost little) for the 50L6-tube. To add or subtract secondary turns, simply remove the mounting strap, lifting the "E" lamination out of the core. You'll find the secondary winding directly under the outer paper insulation. If this insulation is carefully cut with razor blade, it may be replaced with a strip of Scotch tape after alterations.

The range of this light beam transmitter depends on the light source's efficiency. By employing optics rather than parabolic metal reflectors alone, you can improve both the range and concentration. For long-range use, the receiver will respond better if an optical condensing lens is placed in front of the phototube (a Boy Scout's "burning" lens is excellent for this purpose). Position and focus the lens so the con-

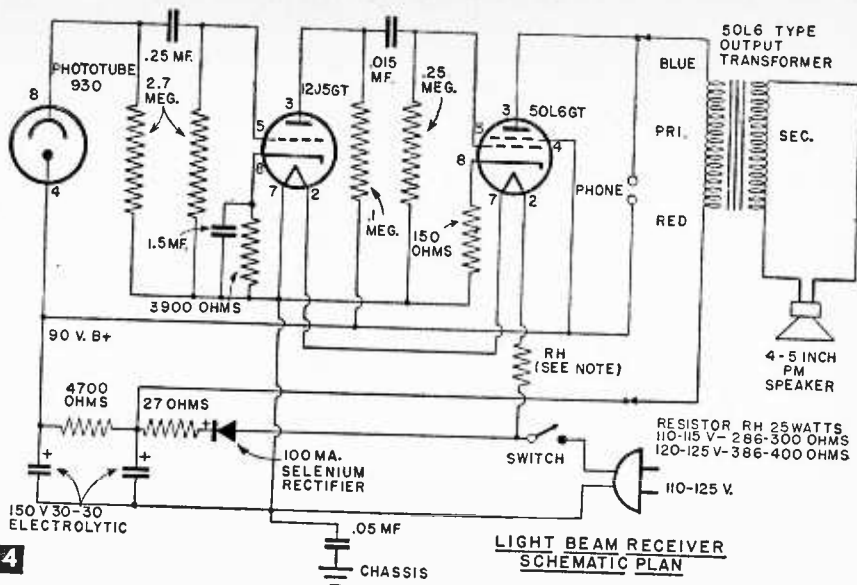

LIGHT BEAM RECEIVER
SCHEMATIC PLAN

MATERIALS LIST—LIGHT BEAM RECEIVER

- 1 pc. #14 or 14 gage aluminum or c.r. steel, 3½" x 9"
- 1 type 930 RCA phototube
- 1 type 12J5GT RCA triode tube
- 1 type 50L6GT RCA pentode tube
- 1 4-5" PM speaker and output transformer (optional)
- 1 Delta spotlight (3 or 1½ v. model)
- 1 100 ma. selenium rectifier
- 1 pair phone terminals
- 3 octal tube sockets
- 1 length fixture cord, plug and switch

RESISTORS

- 2 2.7 megohm, ½ watt
- 1 0.1 megohm, ½ watt
- 1 0.25 or 0.27 megohm, ½ watt
- 1 4700 ohm, 1 watt
- 1 27 ohm, 1 watt
- 1 3900 ohm, 1 watt
- 1 150 ohm, 1 watt
- 1 25 watt wire-wound resistor 300 to 400 ohms (see text)

CAPACITORS

- 1 30-30 or 40-40 mfd., 150 v.v. electrolytic
- 1 1.5 (or 2) mfd., 200 w.v. paper capacitor
- 1 .25 mfd., 200 w.v. paper capacitor
- 1 .05 mfd., 200 w.v. paper capacitor
- 1 .015 (or .02) mfd., 200 w.v. paper capacitor
- Miscellaneous hardware as needed

centrated light from distant electric lantern is concentrated in the center of phototube's cathode and anode elements. You can enclose the phototube amplifier in wood or metal box to keep out stray light.

Building the Light Beam Receiver

The light beam receiver (Figs. 3 through 6) uses only standard radio components and its circuit (Figs. 4 and 6) follows the same basic design used for movie sound reproducers, except that it uses tubes designed for operating on low plate voltages. Thus the receiver needs no power transformers of any kind.

As shown in Fig. 6 the receiver chassis is just 9 in. long x 3½ in. wide aluminum or steel. Each end is bent up 1½ in. to form the amplifier foundation. Ample room is available so that socket and mounting holes need not follow any precise

WAVE-POWERED TUNER


It's surprising how much hi-fi performance you can obtain from a very fine 1924 crystal circuit, updated with modern hi-Q components and semi-conductors

By THOMAS BLANCHARD


THIS tiny wave-powered fidelity tuner is a streamlined version of an antique 1924 receiver, which sold for \$75 when a dollar was worth a dollar. The original set was housed in a 7 x 7 x 18-in. walnut cabinet with a hard rubber panel and a pair of 4-in. tuning dials. It had a hand-adjusted catswhisker and galena crystal detector.

Whereas the antique set employed two separate tuning capacitors with coils wound on forms the size of oatmeal boxes, this modern receiver-tuner (Fig. 1) employs miniature hi-Q coils, with ferrite slugs, and a 2-gang tuner which was unknown in 1924. One section of the tuning capacitor serves to tune the input ferrite antenna coil which receives the radio signal from the ether. This is known as a *wave trap*.

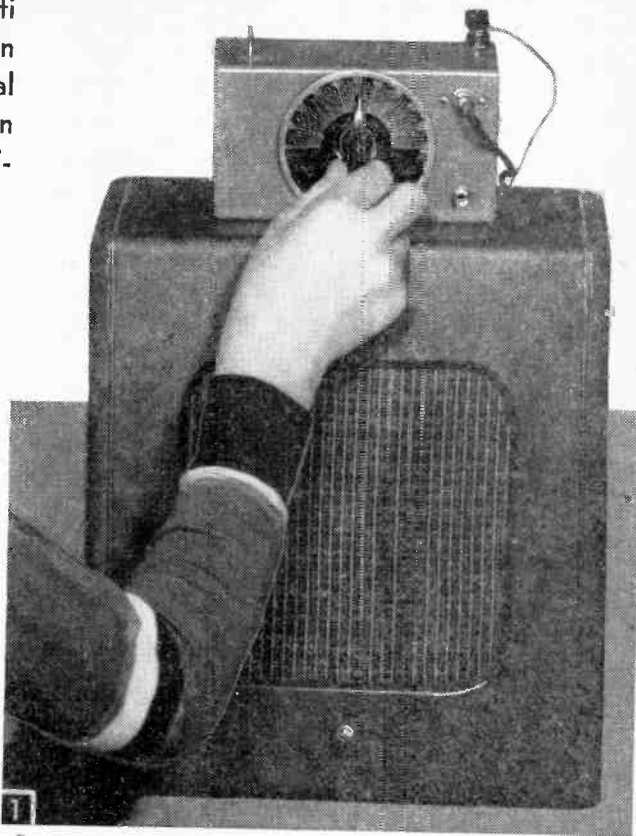Because receivers which employ simple semiconductor detectors are not very selective, the wave trap serves to pre-tune the incoming signal before it reaches the R. F. coil and its tuning



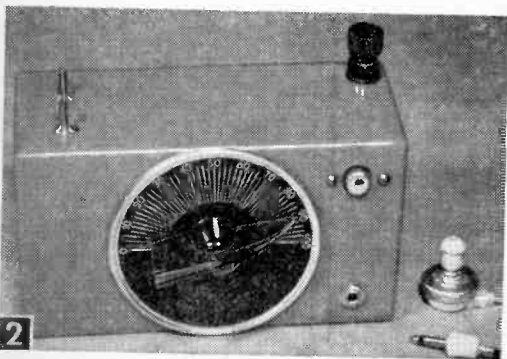Connected to any amplifier, the wave-powered tuner provides bell-clear reception free of static and power line noise.



This modern version of a 1924 crystal radio is an excellent hi-fi receptor. Lower jack provides for ear-phone reception, while phono jack allows connection to any record amplifier.

capacitor. Thus, two tuned circuits not only provide good selectivity, but provide a stronger signal than an ordinary wave-powered circuit.


Most of you already know, of course, that the crystal diode detector makes the finest hi-fi tuner, and is 95 to 100% static-free. It is especially useful in areas where regular sets pick up power line interference. The circuit shown here provides for the use of a miniature earphone, for personal listening, as well as an output jack so that the signal can be fed into the crystal pickup phono jack of your radio or to your hi-fi record amplifier.

We built this tuner-receiver in a 2¼ x 27/8 x 5½-in. plastic box. But any larger non-metallic container will serve equally well. If you are electronics-minded, you'll also find that you don't have to follow the Fig. 5 parts layout slavishly, as long as you make the correct connects, your tuner will perform properly.

Since various mounting holes are provided on the frame of the 2-gang 350- or 370 mmf tuner, it was possible to mount the ferrite antenna coils

MATERIALS LIST—RECEIVER-TUNER

- 1 plastic or wood box or cabinet large enough to hold components
- 1 2-gang variable capacitor, 350 or 370 mmf
- 1 bar knob and dial plate
- 1 miniature phone jack
- 1 phono jack
- 1 length single conductor shielded phono cable
- 2 phono plugs
- 2 ferrite slug-tuned antenna coils (Miller, Variloop, Loopstick, etc.).
- 1 germanium general purpose diode detector
- 2 .002 or .0022 mfd paper or ceramic capacitors
- 1 39,000 to 50,000 ohm 1/2-watt resistor "R" (see text)
- 1 binding post

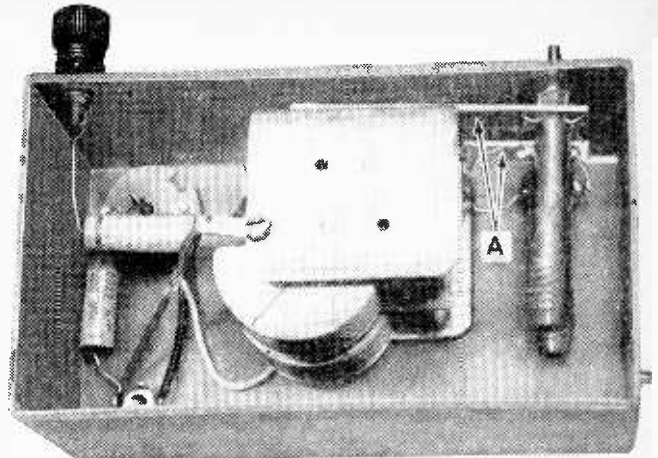

3 Arrangement of components in small plastic box. Coil mounting straps (A) have been secured to frame of 2-gang tuning capacitor.


to the capacitor frame using the metal mounting strap supplied by most coil manufacturers. Coils and tuner in this way become a single, easily handled unit requiring a minimum of wiring.

With the small plastic cabinet we used, space did not allow clearance of the ferrite slug adjustment screws. So a pair of 3/8-in. dia. holes was made with a burring reamer in the top of the box. If you use a larger cabinet, screws need not protrude. But in order to permit proper set alignment, after wiring has been completed, these screws must be accessible.


The "heart" of our tuner-receiver is the semiconductor detector. Any inexpensive general purpose type germanium diode will work here, as a crystal detector. However, some units are "hotter" than others even though of the same type number and make. If you have several diodes on hand, try each one in the circuit. Pick the one that provides the strongest signal.

The tuner output is connected directly to a miniature earphone jack, then through a .002 mfd capacitor to a phono pickup jack. A length of single conductor shielded cord is fitted with pin plugs on each end. One plug connects to the tuner and the other to the input jack of any amplifier. If the amplifier is a simple ac-dc type, and the signal comes through distorted, reverse the line cord plug in the outlet to establish proper polarity.

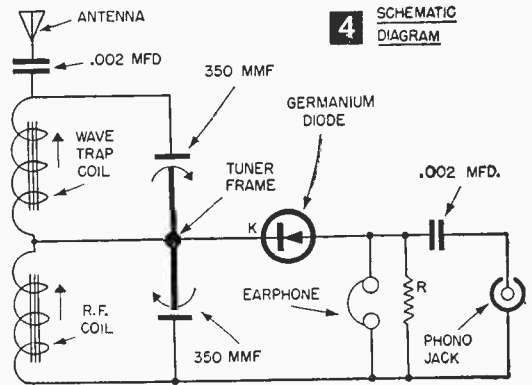Load resistance "R" is a 1/2-watt unit with a value of 39,000 to 50,000 ohms. In fact, varying this value by means of a small 100,000 ohm potentiometer provides an interesting "loudness" control. However, the employment of the resistance "R" across the output is mostly theoret-



4 SCHEMATIC DIAGRAM

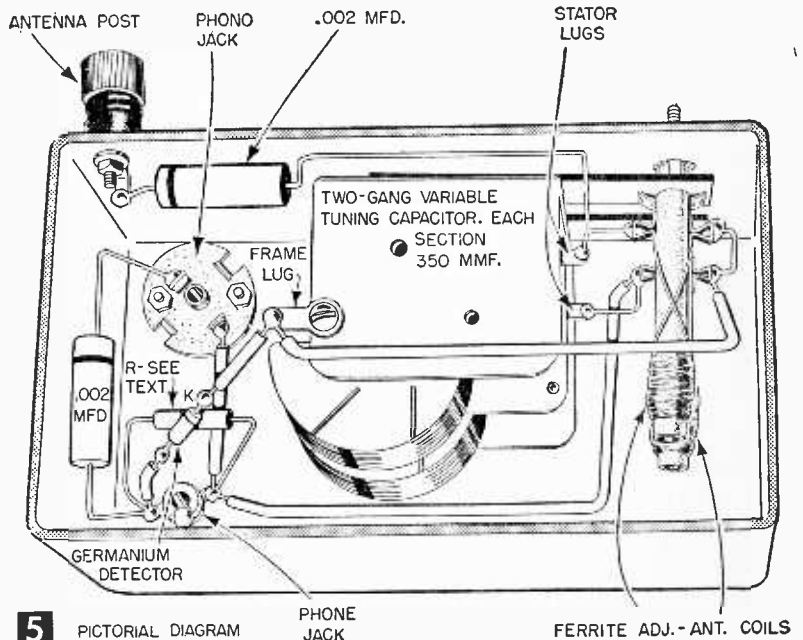

5 PICTORIAL DIAGRAM



6 Coil slug screws extend above cabinet allowing for easy alignment. Here tuner is used with miniature earphone as a personal set.

is used with an amplifier, the power line supplies necessary grounding through the shielded cable coupling.

As a safety measure, the antenna is coupled to the set through a .002 mfd capacitor. With a phono amplifier, the tuner provides excellent reception of nearby stations with a piece of wire as short as 3 feet. A length of wire fitted with a small battery clip may be attached to various metallic objects around the home if a stronger signal is desired. Or make a conventional outdoor antenna connection if you're trying to pull in distant stations.

How to Align Tuner. The slug screws on the ferrite antenna coils must be properly adjusted to insure the set's tuning the entire broadcast band, and providing maximum trap efficiency. Start by tuning to a station near 1600 kc where plates of tuner will be almost fully open. Turn the R. F. coil's slug screw until signal is strongest. Next, without changing dial setting, turn trap coil slug until signal reaches its final peak.

Now rotate the tuning dial to another station near 550 kc (plates meshed). The tuner will cover the entire broadcast band when the R. F. slug has been correctly adjusted. The ideal way to "peak" the set is to tune to a very weak station once the R. F. range is satisfactory. Now slowly turn the trap coil slug until the weak signal is loudest. Your tuner will now track with maximum selectivity from 1600 through 550 kc.

ical. You will need to add it only if the signal when fed through an amplifier is distorted. It is not needed when the earphone is used with the set.


Except when used with an earphone, a ground connection is not necessary. Indeed, little increase in signal was noted with a ground; therefore none has been employed. When the tuner



"I installed a new voltage regulator. The wife said I was nuts but I figure what the heck—"

Low Power DX

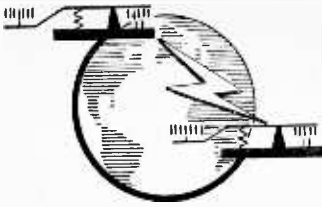Follow these eight simple principles, and get in on this most exciting of electronic sports



By C. F. ROCKEY, W9SCH/W9EDC


DO you like to stand beside a stream and try to out-think the wily trout? Or perhaps you enjoy matching wits with a deer. If you do, then you're a natural for the electronic equivalent of these sports—*low power DX*.

Many new hams gain the impression that expensive equipment, a rural hilltop location, and the luck of a veteran gambler are necessary to make foreign contacts. This is categorically untrue. Many long distance contacts are made every

Fourth, plan to spend plenty of time and work on your antenna system. Of all the technical factors involved in long-distance communication everyone agrees that the antenna system is far and away the *most important*. If you are rich, or can otherwise arrange it, a rotary directive array, otherwise called a "rotary beam" is probably the best available DX antenna. Descriptions, prices, and specifications for *good* beam antennas can be found in any amateur jobber's catalog, but unless you plan to spend upwards of \$150 on such a beam (with rotator and accessories, of course), better not try this approach. Many a home-built or flimsy beam antenna ends up in the neighbor's elms during the first thundergust.

Suppose you do not have \$150 to spend. Must you then concede defeat? Never! Experience proves that a plain piece of copper wire, fed with a few watts of high-frequency power, will produce a signal anywhere on this planet—if the wire is in the *right place*.

What is the "right" place? Books on electromagnetic theory develop neat formulas for the radiation distribution of theoretical antennas in free space and over an infinitely-conductive plane surface. These are elegant, but your backyard and mine are made of dirt, and dirt is not infinitely-conductive. Furthermore our "free space" is filled with gutter pipes, 'phone wires and power lines. The wonderful formulas are therefore useless to us. (The writer wore out a good slide rule and chased many an electromagnetic vector down a rathole before he learned this for himself.) What, then, shall we do? Here's *one* answer:

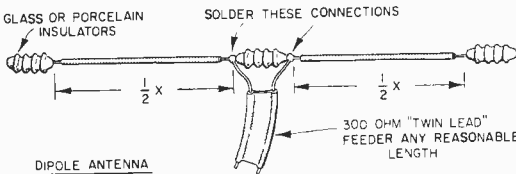

DIPLOLE ANTENNA

MATERIAL: ANY COPPER WIRE HEAVIER THAN NO. 18, B AND S GAGE. MAY BE INSULATED IF DESIRED

TOTAL LENGTH FOR VARIOUS DX BANDS:

BAND	TOTAL LENGTH, FT
28 MC	16
21 MC	22
14 MC	33


1 A

day with simple equipment, from urban residential locations just like yours.

How, then, does one start? First, we'll assume that you are a *licensed* amateur operator, or soon will become one, and that you are in a position to set up a simple station. All right, *first*, get your *General* class license as soon as possible. The restrictions imposed upon Novice-class operators are so confining as to discourage DX operation. (Although some Novices *do* make foreign contacts.) Learn your code and theory and take that test next week.

Second, plan your equipment to operate on one of the *DX bands*, 14 or 21 megacycles. While the 28-megacycle band is also good for long range contacts, the powerful 'phone stations all but monopolize it. So, as of now, it is not recommended.

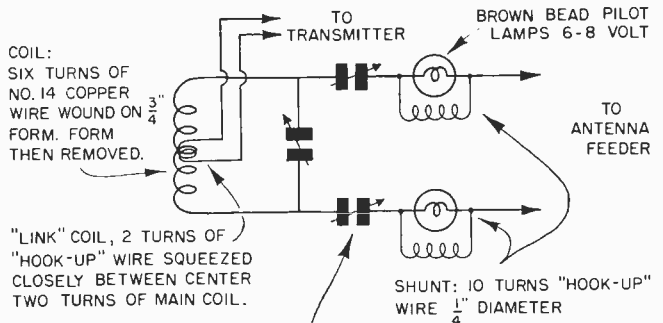Third, plan to do most of your serious long-distance work on radiotelegraph (CW). Reputable calculations indicate that about 50 times more power is required to produce a radiophone signal than is needed to produce a CW signal of the same magnitude.



ALL CAPACITORS: ANY WELL-INSULATED VARIABLE CAPACITORS HAVING AT LEAST 250 MMF MAXIMUM CAPACITANCE. (BUD: MC 1860)


ANTENNA TUNER

(IN EVENT NONE IS PROVIDED IN TRANSMITTER. TUNES ANTENNA AND REDUCES TV INTERFERENCE.)


1 B

Make yourself a half-wave dipole antenna (see Fig. 1) for the band you're interested in. It will be 22 ft. long, overall, for 21 megacycles and 33 ft. long for 14 megacycles. (Forget the odd inches; they don't matter.) Feed it as you prefer. The writer likes a tuned transmission line at the center. (With tuned feeders, the 33-footer can be used on the 21 mc. and 28 mc. bands also.)

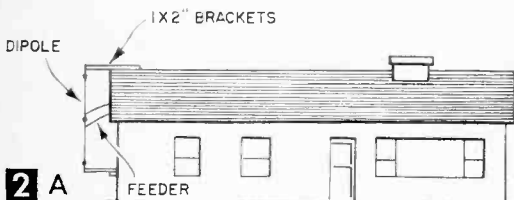When you have your antenna, try hanging it in various available positions about your real



estate (see Fig. 2). If it doesn't quite fit somewhere, you may bend it, with discretion, but do not double it back upon itself. *Somewhere on your property* is a place where such an antenna will work. Try the highest and clearest spot first and call a few foreign stations. If you do not raise them after several days of trying, move your dipole somewhere else, and try again. (Did you catch a rainbow trout in the first stream you tried?) Unscientific? Yes, but it's the only answer. When you find the right spot, then you

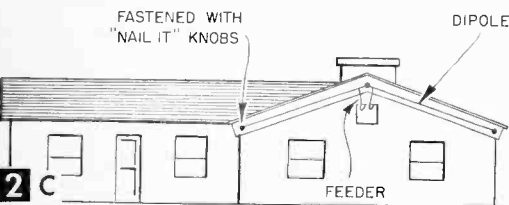

may speculate as to the whys and wherefores.


Fifth, provide yourself with a good receiver. The attributes of a good receiver are: 1) *reliability*—freedom from bad connections and hand capacity; 2) *stability*—ability to tune in and hold a signal despite reasonable mechanical shock, and over a reasonable period of time; 3) *sensitivity*—the ability to bring weak signals up to an audible level. A good practical test (on 14, 21, and 28 mc. bands) is to alternately connect and disconnect the antenna. If the noise level does not markedly increase when the antenna is connected, your receiver will hardly do well on weak foreign signals; 4) *quietness and convenience*—Your receiver should produce no sound except a smooth, quiet, hiss when the antenna is disconnected. If it hums, crackles, grunts or makes similar noises,

To operate any radio transmitter without a license in the U.S.A. is punishable by a maximum fine of \$10,000 and/or two years in prison.

it needs internal attention. Also it should have a non-slip, smooth-acting, tuning mechanism if you are to tune in the weak ones on the nose.


A receiver need not be expensive; indeed, a properly built two-tube will qualify easily on all four counts. On the other hand, many a chrome-trimmed cabinet full of tubes shows up most miserably. It's not how loud the signals are, but how well the *weak* ones come through that counts. Of course, the features of a truly fine receiver are well worth the cost, if you can afford it. Oh, yes, for best results, use your transmitting antenna for receiving also.

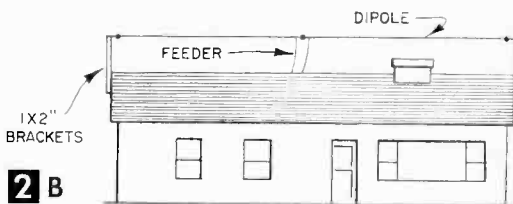Sixth, use a good variable frequency oscillator, often called a V.F.O., with your transmitter. Most



foreign operators do not tune more than a few kilocycles from their own frequency, when listening for answers to their CQ calls. If you're "rock bound," with a crystal-controlled transmitter, you have to wait for a station near your crystal frequency before you stand much of a chance for contact. Of course, you can buy a "raft" of crystals, but this becomes too expensive for most amateurs. Good V.F.O.'s may be built from kits or, if you have ingenuity plus a "junk-box," you can often build a better one by yourself from scratch. See the specialized amateur handbooks for circuits and suggestions.

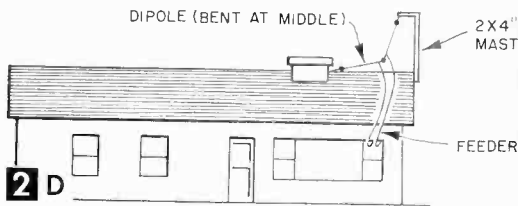Seventh, adjust your transmitter to produce a *steady, clean, reliable* signal. If one or more tubes overheat, bad connections exist, or you have to "give it a kick" to make it work, you'll miss many



good DX chances and you *may* get into trouble with the F.C.C.


The power is inconsequential; both experience and mathematics prove that a one-watt transmitter may have world-wide range. Indeed, the lower the power the greater the challenge to the true ham sportsman. You can get all the fish you want in any lake with a stick of dynamite. Similarly, you can contact all continents in one afternoon with a 1000-watt, "store bought" transmitter but this is "commercial radio," not sport. The writer recommends an input power ranging from

30 to 100 watts as being adequate and sporting.

Eighth (and last), operate intelligently:

- a) *Never* call "CQ DX." Instead answer the for-
eigner's CQ for best results. Listen *first*, then
call.
- b) Look for DX at the proper time. You must be
on hand when the ionosphere is right, if you
want results.

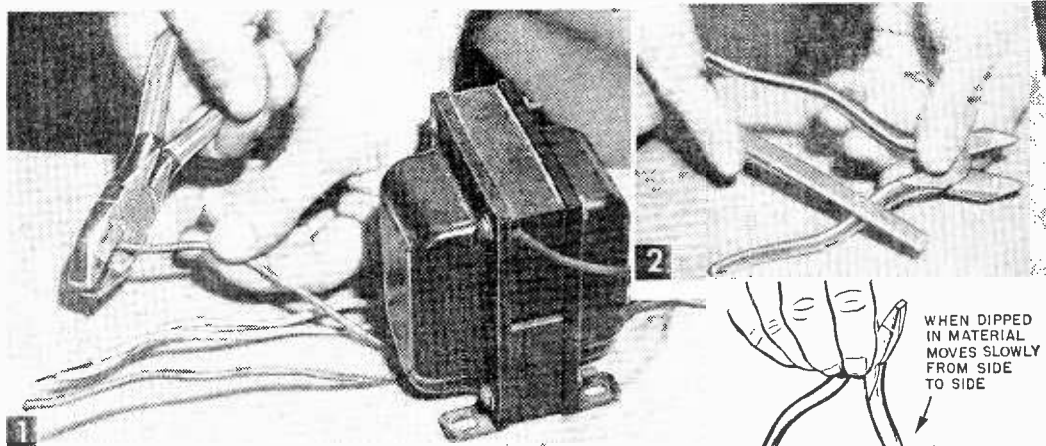- c) Be a gentleman. Other hams judge your coun-
try by the way its hams behave on the air.
Know and obey the regulations at all times,
both in spirit and letter, be brief, but polite.
- d) Don't give up! Try another day, a different
antenna arrangement, a different operating
approach. Others make foreign contacts; so
can you. Get your hook in, the fishin's fine!



There is little chance of receiving a shock through these insulated plier handles. The glass-smooth coating has high dielectric strength and will stand the usual hard usage. It is chemically inert and resists acids, alkalis and petroleum products.

Insulating Your Tool Handles

IN the interests of safety, electrical work-
ers and experimenters should always use
pliers, screwdrivers and other tools with
well-insulated handles to avoid the possi-
bility of shock when working on live wires
and equipment (Fig. 1). You can easily
insulate your tool handles by dipping them
in an insulating material such as *Rub-R-Ize*
(made by Rubber Magic, Inc., Dept. M,
4312 Third Ave., Brooklyn 32, N. Y.) or
Insl-X E-33 (made by The Insl-X Co., Inc.,
Dept. SM, Water Street and Broadway, Os-
sining, New York).

First file or grind off any sharp edges
and rough spots on the part of the tool to
be coated (Fig. 2). Then thoroughly clean
the surface with a clean cloth and a grease
solvent like carbon tetrachloride. Careful of the
fumes! Dip the tool handle into the material to
the desired depth moving it from side to side
to avoid forming air bubbles. Then remove it very
slowly (Fig. 3). The large drop which forms on
the end as it drains can be wiped off with your
finger or a small piece of wood.

Hang the tool up to dry for one hour on a
suitable support (Fig. 4), then apply the remain-
ing coats in the same manner. Three dips should
make the tool safe to use on voltages up to 230
volts. For higher voltages, apply more coats.
Always allow an hour between coats, and 24

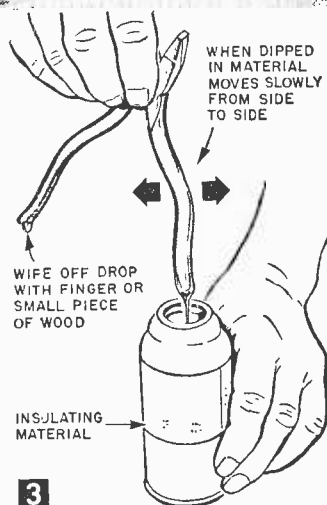
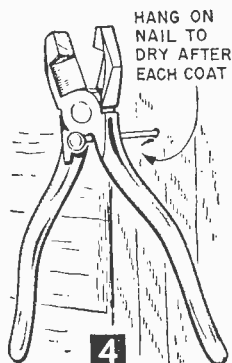


Fig. 2. Sharp edges will take only a thin coating, so use a file to round all edges.

Fig. 3. Dip plier handles into the material one at a time, move handle slowly from side to side to avoid air bubbles and then slowly withdraw.

Fig. 4. Hang the pliers on a convenient nail for drying after each coat.

hours' drying time after the last coat. When the material is dry, remove excess with a sharp knife.

For coating fixed objects or those too large to be dipped, the material can be applied with a brush. It then can be used for coating panelboards, coating terminals after making connections and also metal parts adjacent to wires that might require insulation. Wires formed into small cables can be held in place effectively by this material and thus avoid the possibility of fractured insulation. You can also use it to coat nuts and bolts so that they will remain tight permanently.—H P. STRAND.

Lab Reports and Construction Hints

Anyone constructing or repairing electronic equipment as a hobby, or professionally, *must* have a means of checking the equipment. There are many different types of electronic test equipment depending upon the application, but there is a basic piece of equipment that is a must on any test bench—a voltmeter for measuring ac and dc voltages combined with an ohmmeter for checking circuit continuity and values of resistance.

This basic piece of test equipment can be in the form of a multimeter or it can be a vacuum-tube voltmeter. If a multimeter (VOM), it must have a dc sensitivity of at least 20,000 ohms per volt to keep circuit loading at a minimum and an ac sensitivity of at least 5,000 ohms per volt. These minimum sensitivity limits are necessary to keep circuit loading low, but even with them there will be many situations where loading is excessive and readings obtained by a VOM are meaningless or there is no reading at all. And though the VOM does offer the advantages of being entirely self-contained and of requiring no external power source (and also, usually, of having several ranges for making dc current measurements), such a meter—even in kit form—will cost at least \$30. Thus, the widespread use of the vacuum-tube voltmeter (VTVM).

Instrument accuracy of no better than $\pm 10\%$,



Front panel views of the completed Knight-Kit 83Y125 VTVM kit (left) and Heathkit V-7A VTVM kit (opposite page).

**Heathkit
Model
V-7A VTVM**

sometimes $\pm 15\%$, is usually sufficient when repairing amplifiers, radios, and television sets. Absolute or true voltage values are not as important in such applications as knowing whether a certain voltage

HEATHKIT

All of the parts supplied in the Heathkit (see Fig. 2) were well packaged, the kit was complete in all important details (though solder was not supplied), and a detailed instruction manual was included.

Parts supplied were all of good quality, and though the circuit board wiring appeared tarnished, it soldered readily during the construction. (At one point, for the job, instructions specify a 25 to 50-watt soldering iron, and at another point a 60- or 100-watt iron or soldering gun is specified. Never, however, use larger than a 50-watt iron when making connections to the circuit board assembly.)

Switches had a ball-type detent which gave them a smooth easily operated action. The meter scales on the V-7A could be made more legible if the markings were made slightly heavier and given alternate pairs of scales in red and black, opposite ends of the ohmmeter scales are hidden by the case and it is necessary to read the meter from one side or the other at these extremes.

The V-7A VTVM has a clever dial lamp arrangement in the top edge of the clear plastic meter case, but the red dial lamp has low brilliance and you have to look closely to determine whether the instrument is Off or On.

The **range switch** is, in some respects, the heart of the instrument. Careful workmanship on it will insure maximum instrument reliability. It is the most difficult part of the instrument to assemble, but the "jig" shown in Fig. 3 greatly simplifies the job.

Take a scrap piece of $\frac{3}{4}$ -in. plywood and cut it to roughly $4\frac{1}{4} \times 8\frac{1}{4}$ in. with a $\frac{1}{4}$ -in. hole drilled at an approximate angle of 60° through its center. Mount the precision resistors with a minimum amount of bending and pulling of their leads, wrapping the leads around the switch terminals so that leads are not under tension when mounting is completed. Position resistors so they do not touch each other or any part of the range switch or the shaft through the center of the switch. Rotate the shaft to be sure of clearance in all positions. It is also wise to position the resistors so the values can be easily read.

Don't race with the clock when constructing your VTVM kit—to do so may result in a wiring

on Two Vacuum-Tube Voltmeter Kits

Knight-Kit Model 83Y125 VTVM

By
MILO A.
ADLER



has increased or decreased as a result of an adjustment or a parts replacement. Being able to measure voltages without upsetting an electronic circuit is also far more important than knowing exact voltage.

The ideal instrument to provide these desirable features, then, is a vacuum-tube voltmeter (VTVM). Most vacuum-tube voltmeters do not have *dc* current ranges, but this is not a serious shortcoming since *dc* current readings are not commonly taken or used when testing or repairing electronic equipment of the type commonly found in the home.

The most economical method by which to obtain a VTVM is to purchase it in kit form and construct it yourself. Kits are available at a price far below the aggregate cost of individual components and they have a "professional" appearance when completed. Moreover, they are lower in cost than a 20,000-ohms-per-volt VOM kit.

Questions such as "Which kit shall I buy?" "Is the completed kit unit any good?" and "Will the kit be too hard for me to build?" obviously enter the mind of every prospective VTVM kit buyer.

To answer these questions, a Heathkit Model V-7A vacuum-tube voltmeter kit and a Knight-Kit Model 83Y125 vacuum-tube voltmeter kit were obtained and assembled according to

the instructions supplied with them. The completed units were then subjected to rigorous tests with precision laboratory test equipment. Here are the results obtained, along with some construction tips.

error which could ruin a valuable circuit component and take many hours of tedious circuit tracing to find. The instrument will work the first time you turn it on—provided, you start at the front of the instruction manual accompanying the kit and follow its instructions to the letter. *Don't* skip the introduction, some very important information is given in this portion of the manual.

The 1% precision resistors supplied in the Heathkit were covered with impregnated paper tubing for protection. These resistors are manufactured by placing a thin conductive film on the outer surface of a glass or ceramic core. This film is then cut in a spiral pattern until the desired resistance is obtained. Since such a film is easily damaged by scratching, some sort of protective covering is required. Precision resistors of the highest quality are protected with a thick coating of insulating varnish or equivalent plastic material. This type of coating is unaffected by moisture. A paper covering provides the necessary protection, but it is not impervious to moisture.

As a test, four of the paper-covered resistors from the kit were placed in a humidity chamber along with "coated" resistors of the same ratings.

Humidity was maintained between 85% and 90% at all times, temperature was raised from 68°F to 104°F over a two-hour period, held constant at 104°F for six hours, then allowed to drop to 68°F. This temperature fluctuation was automatically repeated twice every day for three days. Resistance values were measured before the test was started, at the end of each day, and again after the resistors had been out of the humidity chamber for three days.

A 900,000-ohm, 1-watt, paper-covered resistor changed in value by more than 33%. A 900,000-ohm, ½-watt, paper-covered resistor changed in value 52%. A 90,000-ohm, ½-watt, paper-covered resistor changed 3.22%, and the remaining paper-covered, 9,000-ohm resistor changed only 1.3%. The four coated resistors changed less than 0.5% each. All resistors (paper-covered included) were within 1% of their marked values after the three-day drying out period.

This was a severe test—a most severe test, perhaps unduly so—but it does show that the high-value paper-covered resistors can change radically in resistance under high humidity and temperature conditions. And such radical changes can affect instrument calibration and accuracy.



2 Components supplied by the manufacturer of the Heathkit V-7A kit.

Two solutions to this problem are open to the V-7A kit builder. One would be to purchase a replacement set of "coated" 1% precision resistors and substitute them for those supplied with the kit. (To do this, however, voids the kit's guarantee.) The other solution would be to carefully slide the paper tubing on each precision resistor so that the tube is still around each resistor but does not touch both ends. It will still protect the resistor from physical damage, but cannot cause a change in resistance. Do this before final calibration and installation in the cabinet.

Circuit Board. Check tube socket position on the circuit board carefully before bending the lugs down and soldering to the foil pattern. Socket lugs are longer than they need be and there is some danger of a short circuit at the outer end of some of them. This danger can be eliminated by bending the outer end of the lugs upward from the circuit board or by cutting off the surplus length.

When preparing the eight-wire, color-coded cable, be sure not to cut the wires too short (save the wires that are cut off to use when wiring the balance of the voltmeter). Hook-up wire of only one color is supplied in the kit. By using wires of several different colors, you will simplify any possible trouble shooting and will also be aided in checking the wiring in your completed unit.

After all parts have been mounted on the circuit board (as shown in Figure 4) clean off the foil side of the board to remove all traces of the rosin soldering flux. Do this by wiping off the board with a cloth dipped in acetone or alcohol. Don't use an excessive amount of acetone, however, or the printing on the opposite side of the board will be removed by it.


After the foil side of the board has been

cleaned thoroughly, cover the entire side of the board with an insulating varnish or equivalent plastic coating to protect and preserve the circuit-board wiring. Pressurized spray-cans that provide a crystal clear acrylic insulating coating can be obtained from radio parts distributors at a nominal price. Do not spray the switches, since contacts within them would be coated and erratic switch action would result.

The phosphor bronze battery holder spring is somewhat difficult to mount and you will have to make several attempts before succeeding. (This portion of the VTVM assembly could have been simplified if the spring supplied had a slightly different shape to provide room for the mounting nut and lockwasher.) The battery is also somewhat difficult to install. However, the battery is firmly held in place and the battery contacts are tight, both desirable features.

The battery should not be installed in the VTVM or used in any manner until the final dc calibration is complete. Calibration accuracy for the dc ranges depends upon the terminal voltage of the battery. If the battery has been previously used, or has been accidentally shorted for just a moment, the terminal voltage could permanently drop.

Final assembly of the instrument can be accomplished without forcing any of the components. The meter and the circuit board are both rugged, but unnecessary force could permanently damage either or both. Tighten the four meter mounting screws just enough to hold the meter without coming loose under normal operating conditions. Over-tightening them could result in a cracked or broken meter case. The inside of the completed VTVM should look like Fig. 6.

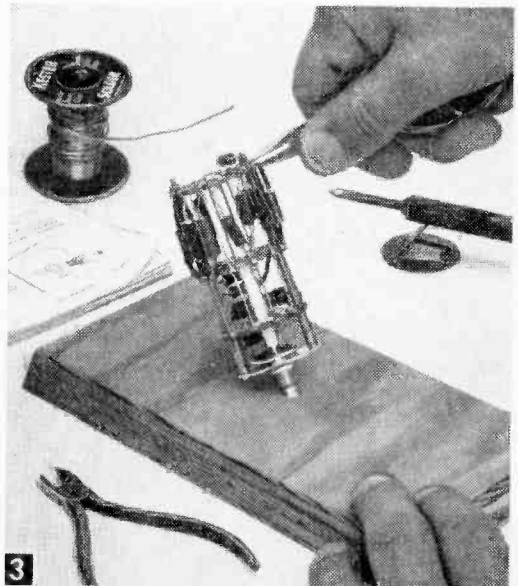

3 Installing last resistor on Range Switch. Switch is held secure for mounting of resistors by wooden jig.

Calibration. Provide a support that will hold the panel upright in the normal operating position. Make this support out of wood so that the panel is insulated, if on a metal surface, and use an insulated screwdriver.

Do not touch the metal panel when calibrating the ac ranges.

When setting the meter movement to mechanical zero, rotate the adjusting screw clockwise until the meter pointer is moving down-scale toward zero, stopping when you reach zero. If you go beyond, keep rotating the screw clockwise and again approach zero from the high side of the scale. This is the correct way to adjust to zero any meter movement of this type.

When the instrument is operating you should be able to set the meter to zero with the ZERO ADJ. control set to the approximate center of the control adjustment range. If this adjustment can be obtained only with the control at or near one end, the two triode sections of the 12AU7 are probably unbalanced. The tube is not defective and the VTVM can be calibrated and used with good results, but if you have a selection of 12AU7 tubes, pick one that will permit setting the meter to center scale with the Selector Switch in either the D.C.- or the D.C.+ position. This will make the VTVM slightly easier to use and there is also less chance of the tube drifting out of the adjustment range of the ZERO ADJ. control.

Make a rough initial calibration, install the VTVM cabinet, reconnect power, and leave the instrument on for at least 100 continuous hours.


This may seem like a long time, but using two different sets of tubes there was noticeable drifting of characteristics in the test model until the tubes had aged for at least four days and nights.

When making the final calibration, the VTVM should be thoroughly warmed up and—if at all possible—a second voltmeter with accurate or known calibration should be used as a reference, especially when calibrating the ac ranges. Your VTVM should then be adjusted to give the correct reading as determined by the reference voltmeter when connected to the same voltage source. If possible, check several scales and adjust the meter for a compromise calibration that gives the best accuracy on all ranges checked. Do not include the 1.5- and 5-volt ac ranges as they may have some inaccuracies that cannot be avoided. (This will be explained later.)

If a reference voltmeter is not available, use the calibration procedure given in the instruction manual. This procedure is accurate for the dc ranges since battery voltage will probably be

within 1% of 1.55 v. Accuracy of the ac calibration will depend upon how close the line voltage is to 117 v at the time you calibrate your unit. The line voltage could very easily be 5% to 10% from 117 v, which would automatically introduce a corresponding error in your calibration.

The three wires supplied for the voltmeter test leads are only 3 ft. long. This makes it necessary to have the meter very close to the points to which it is connected. Cables that are at least 4 ft. long will make the V-7A much easier to use.

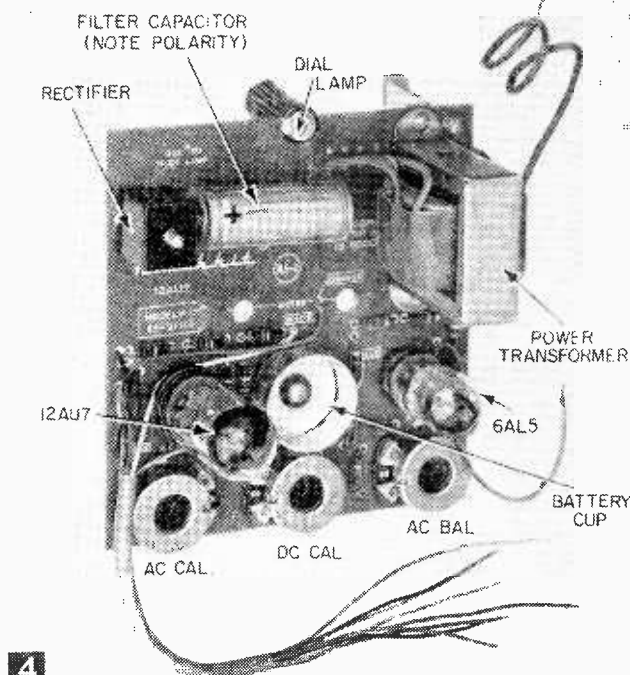

Completed V-7A circuit board ready for final assembly.

The special "test prod wire" for the COMMON and the A.C. OHMS leads, as well as the shielded type RG-58U cable for the D.C. lead, is relatively inexpensive and can be obtained from any radio parts distributor. If you make up a new set of longer cables, check the dc calibration of the VTVM with the new cable. Heat from soldering the 1-megohm resistor in the dc probe may cause the resistor to change value, affecting calibration.

Check-out. The completed V-7A VTVM model was calibrated exactly according to the instruction manual directions. Instrument accuracy was then checked by means of laboratory equipment having a dc accuracy within 0.1% and an ac accuracy within 0.25%.

The dc readings were all low, with none any lower than 2% with respect to full scale. This means that the dc portion of the unit can be recalibrated to provide a between-scale accuracy of $\pm 0.8\%$ of full scale. A tracking error of $\pm 1\%$ of full scale was found between equally spaced readings taken from one end of a scale to the other. This means that the over-all dc


accuracy of the V-7A model was $\pm 1.8\%$ with respect to full scale. Your VTVM may not be as accurate as this, it may be more accurate.

Error between the D.C.— and D.C.+ positions of the function selector switch was negligible.

Line voltage was increased to 125 v and decreased to 105 v. The ZERO ADJ. control was readjusted each time line voltage was changed. Maximum error introduced by this extreme test was only approximately $\pm 3\%$. There are no published specifications for this test, but the results obtained were far better than expected. Rarely do line voltages vary this much in any given location and it is therefore permissible to neglect any possible error due to line voltage fluctuations when using the V-7A VTVM.

The V-7A VTVM model passed the dc accuracy test easily, since published specifications are $\pm 3\%$ of full scale and $\pm 1.8\%$ was obtained ($\pm 5\%$ and up to $\pm 10\%$ is usually considered good for all except special-type, laboratory meters).

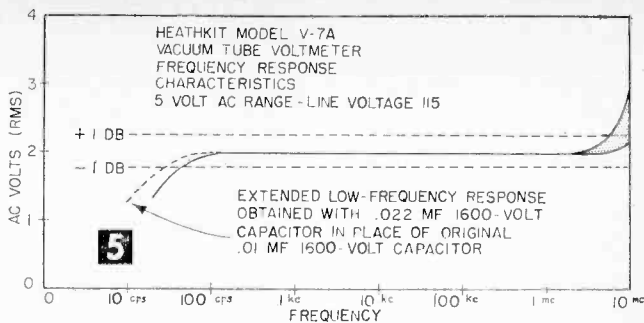Accuracy of ac calibration was then checked at a frequency of 400 cps and was found to be within $\pm 6.3\%$ of full scale on the upper five ranges. Good accuracy cannot be expected on the 1.5 v ac range (as will be explained later). The instruction manual contains the kit manu-



reasonable limits, but not quite meeting specifications for ac accuracy of $\pm 5.0\%$ of full scale. The ac line voltage was very close to 117 v when the V-7A VTVM model was calibrated.

Frequency response of the 5 v ac range was then checked; results obtained are shown in the graph of Fig. 5. The equipment used to make the frequency response measurements has an accuracy of better than $\pm 1\%$.


High-frequency response varied depending upon the position of the test leads, but usually fell within the shaded area at the upper end of the graph, Fig. 5. The frequency response obtained was much better than expected and was within ± 1 db from approximately 45 cps to 5.5 mc.

In most cases, voltmeters of this type are seldom used at frequencies above approximately

20 kc which means that the high frequency response of the model was excellent. The approximate error of 6% at power line frequencies seemed excessive, but it was very easily reduced to a satisfactory level by replacing the 0.01 mfd, 1600-v capacitor between Selector Switch terminal S12 and Range Switch terminal R6 with a 0.022 mfd, 1600-v capacitor. Frequency response was lowered by almost an octave and the error at 60 cps was reduced to approximately 2.5%. The improved low-frequency response is shown by the dotted line on the low frequency end of the response curve in Fig. 5.

Anyone building the V7A kit should make this parts substitution during assembly. (Unfortunately, the Heath Co. informs us that to do so will void the guarantee; you'll have to decide whether it's worth it to you or not. There is room for a Sprague "Black Beauty" 0.022 mfd, 1600-v capacitor in place of the original .01 mfd, 1600-v capacitor.)

The ohmmeter ranges were checked and the

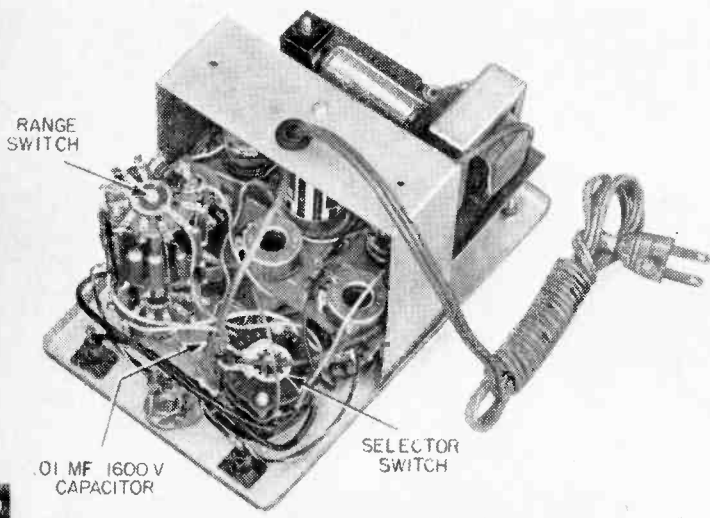

Completed V-7A VTVM ready for installation in unit's cabinet.

facturer's explanation for the error on the 1.5 volt ac scale and states that the error may be as high as $\pm 15\%$ of full scale. The error between the upper five ac ranges was not more than $\pm 3.3\%$ with respect to full scale. There was, however, an additional $\pm 3\%$ tracking error with respect to full scale, resulting in the over-all accuracy of $\pm 6.3\%$ of full scale, still well within

results obtained were:

CORRECT VALUE IN OHMS	V-7A INDICATION	ERROR IN OHMS	ERROR PERCENT
10	9.3	0.7	-7%
100	93	7	-7%
1,000	920	80	-8%
10,000	9,400	600	-6%
100,000	94,000	6,000	-6%
1,000,000	950,000	50,000	-5%
10,000,000	9,600,000	400,000	-4%

Students of mathematics and of electronics may be confused by two statements that appear in the instruction manual supplied with the kit. One statement is in the form of a chart which shows adjacent voltage ranges as being 10 decibels apart. If you wish to neglect a 0.5 db error this statement is correct. Two scales of any voltmeter are 10 db apart when the ratio between the two readings obtained with the meter needle in any position is 3.16 or 0.316 to 1. Under these conditions, 9.5 on the 15 v scale or 95 on the 150-v scale will be opposite 30 on the 50-v scale.

The scales in the V-7A voltmeter, however, are arranged so that 9 on the 15-v scale is opposite 30 on the 50-v scale. This is a ratio of 3.33 or 0.3, which can be expressed as 10.5 db. When going from the 50-v scale to the 150-v scale, 30 will be opposite 90 which is a ratio of 3.0 or 0.33. This ratio can be expressed as 9.5 db. Alternate scales are 20 db apart (as stated in the instruction manual). A corrected chart to take the place of the one in the manual would be:

VOLTAGE SCALE	DECIBEL SCALE	DIFFERENCE
0-1.5 VOLTS	READ DB DIRECTLY	10.5 DB
0-5 VOLTS	ADD 10.5 DB TO READING	9.5 DB
0-15 VOLTS	ADD 20.0 DB TO READING	10.5 DB
0-50 VOLTS	ADD 30.5 DB TO READING	9.5 DB
0-150 VOLTS	ADD 40.0 DB TO READING	10.5 DB
0-500 VOLTS	ADD 50.5 DB TO READING	9.5 DB
0-1500 VOLTS	ADD 60.0 DB TO READING	

The second questionable statement is in the circuit description where the 6AL5 is said to act as a full-wave rectifier for ac voltage measurements. The 6AL5 is actually connected in a half-wave, voltage-doubler circuit. Such a voltage-double circuit is used to obtain high sensi-


tivity in order to provide a 1.5 v range for ac voltage measurements.

In order for the voltmeter to be accurate on all ac ranges, the dc output from the 6AL5 rectifier must be directly proportional to the ac input voltage. This linearity is possible with diode rectifiers only when the input voltage has an amplitude of at least 1 to 1.5 v. When the ac input signal is less than approximately 1.5 v, a diode rectifier acts like a "square law detector" with output proportional to the square of the input signal amplitude. The voltage doubler circuit only amplifies this error. Because of this, the 1.5 v ac range of the V-7A VTVM cannot be expected to be accurate. In fact, this error will also be noted on the low end of the 5-v range. This is not faulty design, even though errors as high as 20% with respect to the actual voltage may be present in the 1.5 v range of a particular V-7A model. The circuit provides optimum performance at a low price, combined with construction simplicity. Many commercially built VTVM's costing several times the price of the V-7A have the same error on their 1.5- and 5-v ac scales. The 1.5-v ac range is still extremely useful for making relative measurements. Exact values are usually not necessary on these scales.

The V-7A VTVM can be used in any convenient location. Just remember that the common black test lead is connected to the aluminum cabinet. If you connect this lead to the hot side of the power line (as in an ac-dc receiver) and the cabinet is grounded—something has to give. The rubber feet on the cabinet are not adequate to give good insulation. In doubtful locations, sit the VTVM on a piece of dry wood, a piece of flat plastic, or a magazine.

Anyone with the ability to read and understand simple, well-written instructions can complete the Heathkit V-7A vacuum-tube voltmeter kit. The instructions are complete, without error, and are easy to follow. Some soldering experience and knowledge of the resistor color code will be helpful, as will enough previous electronic experience to be able to identify electronic components since all small parts are mixed together in one bag when received.

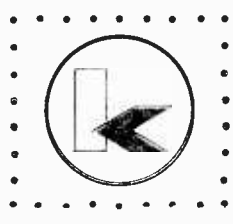The completed instrument will be rugged and dependable and more than adequate for servicing "home-type" electronic equipment. You can say "I made it" with justifiable pride, and you can use it with confidence.



All parts supplied in Allied Radio's 83Y125 kit are shown in Fig. 7. The completed Knight-Kit VTVM (see page 123) was assembled from these components with a few simple tools, a soldering iron, and a few

hours of spare time in only a few evenings. Instructions supplied with the kit are extremely complete and can be followed by even the greenest beginner. The resistors in the kit are supplied mounted on cards with their corresponding circuit designations, eliminating the need for using the color code to identify resistors, and thus greatly reducing the possibility of a wiring error resulting from the selection of a wrong part. The



7 Components furnished with the Knight-Kit 83Y125 VTVM kit. Note card-mounted resistors.

83Y125 kit is supplied with hook-up wires of different colors, cut to length. More than enough solder to complete the kit is furnished and enough cable is provided to make the test leads a full 4 ft. long.

All components furnished were of good quality; circuit-board wiring had a bright copper color and soldered easily. The circuit board was made of a translucent material, permitting viewing of the wiring or the component mounting position from either side of the board. An inspection lamp held on the opposite side of the board will show the wiring and components in silhouette, greatly simplifying possible troubleshooting. Most commercially built equipment has translucent circuit boards for this reason.


When you first unpack your VTVM kit, put the 1.5 v. battery aside and leave it there until final calibration has been completed. The battery terminal voltage may change if the battery is used in the ohmmeter circuit or accidentally shorted, even if only momentarily. Calibration accuracy of the dc voltage ranges is based on the assumption that the terminal voltage of this battery is 1.55 v. Any newly purchased, unused battery of the same type should have this terminal voltage.

The two switches supplied in the 83Y125 VTVM kit were more than adequate from an electrical viewpoint, but were stiff to turn. This can be attributed to the fact that the switches did not have a ball-type detent. Sparse lubrication with a light grease (even petroleum jelly) will keep friction at a minimum, however, and the stiffness will disappear somewhat in time.

All but one of the precision resistors supplied with this Knight-Kit had a varnish or plastic coating and were therefore not only protected from physical damage but made impervious to moisture, also. One resistor had only impregnated-paper protection. Tests made on precision resistors with impregnated paper protection (see Heathkit test results) showed that resistance values could change under high humidity and temperature conditions. You can eliminate such possible sources of inaccuracy by purchasing "coated" type 1% resistors as replacements, or you can partially slide the cardboard off the resistor. Slide the tube just far enough to clear the metal cap on one end of the resistor.

Pin jacks of the type supplied in the 83Y125 kit will, in time, lose their gripping power and the test leads will pull out of the jack under normal use. This can be somewhat prevented by using banana jacks. Also, the fiber washers used to insulate the pin jacks do not look like they would be capable of withstanding 1500 v under high humidity conditions (it is only fair to add, however, that the manufacturer states that they have never had a breakdown of these jacks). One way of eliminating the tip jacks would be to solder the test leads directly into the instrument. Put grommets in the panel holes and connect the test leads inside the panel. If you use the pin jacks as supplied, however, follow the installation instructions carefully to avoid the possibility of a short circuit.

The 83Y125 VTVM has a regular jeweled dial lamp that gives a positive indication when the VTVM is turned on, and meter scales have been planned for maximum visibility. Optical confusion is avoided by having alternate pairs of scales in black and red. The dial markings on the meter face are all clearly visible from the front of the instrument without any portion of the scales being hidden by the meter case. In addition, the lines and figures are dark enough and wide enough to be legible from several feet away, yet they are not so wide that they prevent accurate readings.

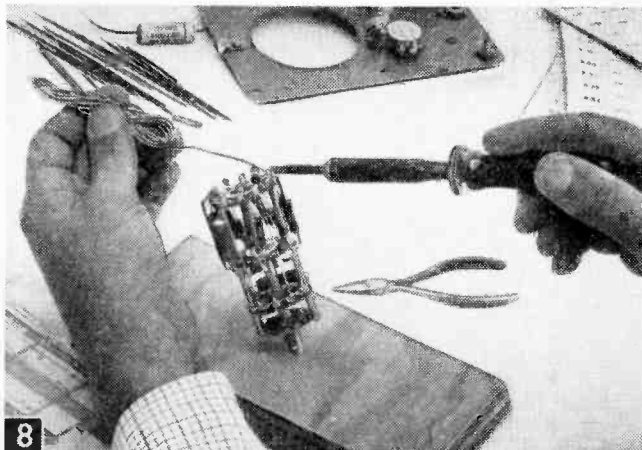

8 Wiring in last resistor on Range Switch with aid of scrap plywood jig.

Assembly instructions have been prepared with the beginner in mind.

The steps are presented in sequence designed to eliminate as many of the possible construction errors as possible.

In the instructions, you are instructed to insert the tubes in the sockets during construction of the circuit board. This apparently is done to prevent the beginner from accidentally filling the socket full of solder which would prevent insertion of the tube at a later time. The possibility of damaging the tubes, however, makes this procedure seem unwise. If you apply heat and solder only at the joint between the socket terminal and the circuit board wiring you cannot run solder into the socket.

Assembly of the Range Switch is somewhat of a construction headache—three hands are needed. In an attempt to help the builder, the instruction manual says to mount the switch on the front panel for wiring. There is considerable danger of scratching the front panel if you do this. Also, the switch is not held at a convenient angle.

Instead of using the panel, drill a $\frac{1}{4}$ -in. hole at an angle of approximately 60° through the center of a $\frac{3}{4} \times 5 \times 9$ -in. thick piece of scrap wood and insert the shaft of the switch into the hole for support. The switch can then be easily worked on as shown in Fig. 8. The soldering iron shown in Fig. 8 is a Drake, 35-watt, "Pee Wee" Model 360, and is ideal for wiring the entire VTVM. The tip temperature can be controlled by sliding the tip in or out of the iron.

Mount the resistors on the Range Switch without excessive bending and pulling on the leads. The leads must not be under tension after the resistor is mounted. Position the resistors so they do not touch each other or any part of the Range Switch or the shaft through the center of the switch. Rotate the shaft to be sure of clearance in all positions. Position the resistors so the values can be easily read.


When preparing the nine-wire color coded cable be sure not to cut the wires too short—a little long is far better than too short.

After all parts have been mounted on the circuit board as shown in Fig. 9, clean off the foil side of the board to remove all traces of soldering flux by wiping it off with a clean cloth dipped lightly in acetone or alcohol. The two tubes and the battery are shown in place in Fig. 9 but you are urged not to install these parts until later.

Covering the foil side of the board with an insulating varnish or equivalent plastic coating will increase instrument dependability and life. Pressurized spray-cans are available through radio parts distributors.

As instructed in the manual, when mounting the circuit board, cut one spacer to a length of $1\frac{1}{4}$ in. and leave the other three their original

length of $1\frac{3}{8}$ in. Use the shortened spacer over the meter mounting screw on which the line cord cable clamp is mounted (see Fig. 10), thus preventing unnecessary strain on the circuit board, and also making an electrical contact between the front panel and the circuit board wiring. If you have sprayed your circuit board with an insulated coating be sure to remove enough of the coating to insure a good contact for the shortened spacer. An ink eraser will remove the coating without damaging the foil on the circuit board.

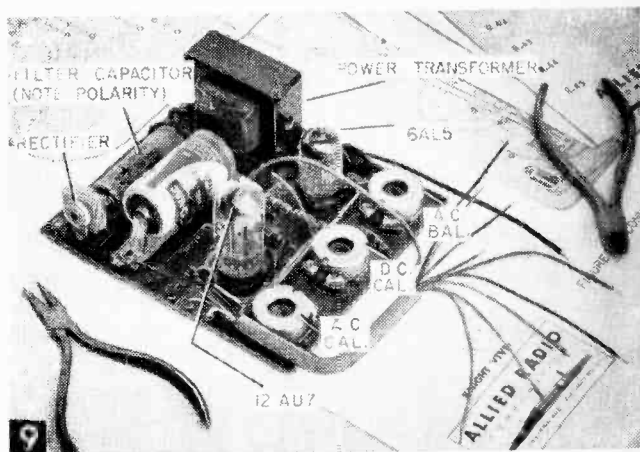

Completed circuit board ready for mounting.

The instructions with the kit say to coat the foil pattern with solder in the contact area of the shortened spacer.

You can crack or break your meter case by overtightening the four mounting nuts for the meter. Tighten the nuts just enough to hold the meter firmly in place.

To calibrate the instrument, first provide a support that will hold the panel upright in the normal operating position. Make the support out of dry wood so that the panel is insulated if on a metal surface and use an insulated screwdriver. Do not touch the metal panel when calibrating the ac ranges.

Set the meter movement to zero by rotating the adjusting screw clockwise until the meter pointer is moving downscale toward zero and stop when you reach zero. If you overshoot, keep rotating clockwise and again approach the zero from the high side of the scale and stop on zero without overshoot.

When the instrument is operating you should be able to set the meter to zero with the ZERO ADJ. control set to the approximate center of the control adjustment range. If this setting can be obtained only with the control at or near one end, the two triode sections of the 12AU7 are probably unbalanced. The tube is *not* defective and the meter can be calibrated and used with good results. If you have a selection of 12AU7 tubes, pick one that will permit setting the meter to center scale with the Selector Switch in either the D.C.— or the D.C.+ position.

Make a rough initial calibration, install instrument in cabinet, reconnect power, and turn the VTVM on for at least 100 continuous hours to stabilize tube characteristics. (If and when you replace tubes, do this also. All new tubes should be "aged" thus whenever used in such applications.)

When making the final calibration, the instrument should be thoroughly warmed up and—if at all possible—a second voltmeter with a known or accurate calibration should be used as a reference. Your VTVM should then be adjusted to give the correct reading as determined by the reference voltmeter when connected to the same voltage source. If possible, check several scales and adjust the meter for a compromise calibration that gives the best accuracy on all the ranges checked. You should not include the 1.5- and 5-*v ac* ranges as they may have some inaccuracies that cannot be avoided.

If a reference voltmeter is not available, use the calibration procedure given in the instruction manual. The procedure in the manual is accurate for the *dc* ranges since the battery voltage will probably be within 1% of 1.55 volts. The accuracy of the *ac* calibration will depend upon how close the line voltage is to 117 *v* at the time you calibrate your VTVM. This voltage could very easily be $\pm 5\%$ or $\pm 10\%$ from 117 *v* at the time, automatically introducing a corresponding error in your voltmeter *ac* calibration.


Do not attempt calibration of the 83Y125 VTVM kit *ac* voltage ranges by measuring the secondary voltage of the power transformer in the manner described in the manual as this may introduce additional calibration error. The transformer in the model tested 6 *v* when the line voltage was set exactly to 117 *v*. This represents an error of 2% with respect to full scale, or nearly 5% below 6.3 volts.

The completed 83Y125 VTVM kit was calibrated by following the instruction manual, with the exception that the *ac* ranges were calibrated by measuring the power line voltage which was assumed to be 117 volts. Instrument accuracy was then checked by means of laboratory equipment having a *dc* accuracy within 0.1% and an *ac* accuracy within 0.25%.

The *dc* readings were all high, but none were any higher than 1% with respect to full scale. This means that the *dc* portion of the VTVM can be recalibrated to provide a between-scale accuracy of $\pm 0.5\%$ of full scale. However, a tracking error of 1% with respect to full scale was found between equally spaced readings taken from one end of a scale to the other. This means that the maximum over-all *dc* accuracy of the test model was $\pm 1.5\%$ with respect to full scale. Error be-

tween the D.C.— and the D.C.+ positions of the function Selector Switch was found to be negligible.

Line voltage was increased to 125 *v* and decreased to 105 *v*. The ZERO ADJ. control was readjusted after each change and the VTVM became stable as indicated by a steady position of the meter pointer. The maximum error introduced by this extreme test was only approximately $\pm 2\%$. No published specifications for this test exist, but results obtained were far better than expected—and since line voltages rarely

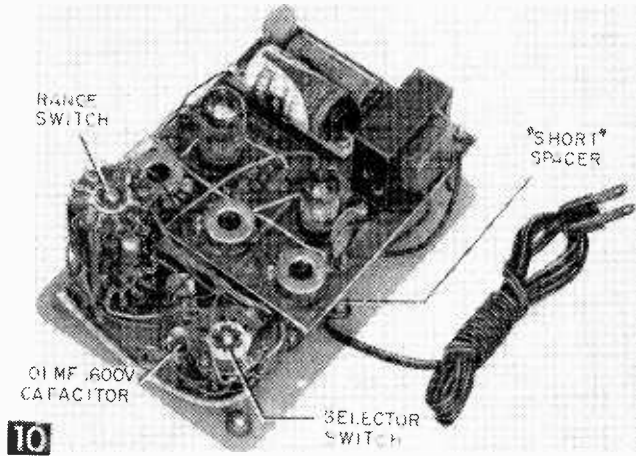

10 Completed 83Y125 VTVM ready for cabinet installation. Unit is compact, yet all components—except dial lamp—are accessible.

vary this much, it is permissible to neglect any error due to line voltage fluctuations when using your Knight-Kit 83Y125 VTVM. The 83Y125 VTVM model easily passed the *dc* accuracy test since published specifications are $\pm 3\%$ of full scale and an over-all accuracy of $\pm 1.5\%$ was obtained by test.

The accuracy of the *ac* calibration was checked at a frequency of 400 cps and was found to be $\pm 5.5\%$ of full scale on the upper five ranges. The error between any two of the upper five *ac* ranges was not more than $\pm 2.5\%$ with respect to full scale. There was also a $\pm 3\%$ tracking error with respect to full scale, resulting in an over-all *ac* accuracy of $\pm 5.5\%$, but this is still, more than adequate.

Results obtained when the frequency response of the 5-volt *ac* range was checked are shown in the graph of Fig. 11. High-frequency response varied, depending upon the position of the test leads, but usually fell within the shaded area at the upper end of the graph. The response obtained was much wider than expected and was within ± 1 db from approximately 40 cps to 4 mc.

In most applications, voltmeters of this type are seldom used at frequencies above approximately 20 kc which means that the high frequency response is much higher than necessary. Though the approximate error of 6% at the power line frequency of 60 cps seems excessive,

it can be very easily reduced by replacing the .01 mfd, 1600-v capacitor between terminal 9 of the Selector Switch and terminal 6 of the Range Switch with a .022 mfd, 1600-v capacitor. With this change, frequency response was lowered by nearly an octave and the error at 60 cps was reduced to approximately 2%. This is shown by the dotted line on the low frequency end of the response curve in Fig. 11. You are urged to make this parts substitution during construction. There is room for a Sprague "Black Beauty" 0.022 mfd, 1600-v capacitor in place of the capacitor supplied with the kit.

Ohmmeter ranges were checked with these results:


CORRECT VALUE IN OHMS	83Y125 INDICATION	ERROR IN OHMS	ERROR PERCENT
10	10.1	0.1	-1.0%
100	101	1	-1.0%
1,000	1,005	5	-0.5%
10,000	10,000	0.0	NONE
100,000	101,000	1,000	-1.0%
1,000,000	1,010,000	10,000	-1.0%
10,000,000	10,200,000	200,000	-2.0%

As with the Heathkit, two statements appearing in the instruction manual may confuse students of mathematics and electronics. One statement is in the form of a chart showing adjacent voltage ranges as being 10 db apart. This chart is correct only if you wish to neglect a .5 db error. Two scales of any voltmeter are 10 db apart when the ratio between the two readings obtained with the meter needle in any position is 3.16 or 0.316 to 1. Under these conditions, 9.5 on the 15-v scale or 95 on the 150-v scale will be opposite 30 on the 50-v scale.

The scales in the 83Y125 VTVM are arranged so that 9 on the 15-v scale is opposite 30 on the 50-v scale. This is a ratio of 3.33 or 0.30, which can be expressed as 9.5 db. Alternate scales are 20 db apart as stated in the instruction manual. A corrected chart to take place of the one in the manual is:

VOLTAGE SCALE	DECIBEL SCALE	DIFFERENCE
0-1.5 VOLTS	READ DB DIRECTLY	10.5 DB
0-5 VOLTS	ADD 10.5 DB TO READING	9.5 DB
0-15 VOLTS	ADD 20.0 DB TO READING	10.5 DB
0-50 VOLTS	ADD 30.5 DB TO READING	9.5 DB
0-150 VOLTS	ADD 40.0 DB TO READING	10.5 DB
0-500 VOLTS	ADD 50.5 DB TO READING	9.5 DB
0-1500 VOLTS	ADD 60.0 DB TO READING	

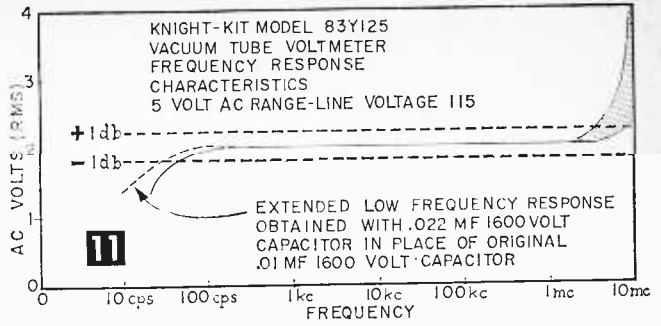The second confusing statement is in the circuit description where the 6AL5 tube is said to act as a full-wave rectifier for ac voltage measurements. For a discussion of this, see the Heath-




kit test report discussion of a similar statement in Heathkit's instruction manual.

The Knight-Kit 83Y125 VTVM can be used in any convenient location. Just remember that the common black test lead is connected to the steel cabinet. If you connect this lead to the hot side of the power line as in an ac-dc receiver and the VTVM cabinet is grounded—poof! there goes a fuse. Sit the VTVM on an insulated surface (a dry piece of wood or a 1/4-in. piece of plastic or even a copy of the *Radio-TV Experimenter*) when making connections to the power line for voltage measurement purposes. Be sure the ac power is disconnected from the device to which you connect your VTVM leads when you make the actual connections. Do not touch the VTVM cabinet or the common test lead after connecting the device under test to the power line. Remember—if in doubt, insulate.

The Knight-Kit 83Y125 VTVM has a 2.2-ohm resistor in series with the parallel connected tube heaters. This resistor adds to instrument stability, reliability, and accuracy. Tube life is extended by the reduced heater voltage, tube performance will be more consistent over a longer period of time because of it, and the VTVM remains in calibration longer.


Any serious beginner with the ability to read the extremely simple instructions can complete the 83Y125 kit. It is complete in every detail, including detailed, illustrated instructions on how to solder. Absolutely nothing extra is required other than tools. The completed instrument will be more than adequate for servicing electronic equipment found in the average home and the instrument is rugged.

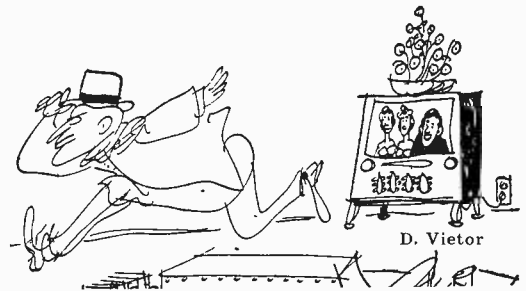

... and, while they last, these two beautiful mnphrph are included with every box of Trucut blades!"

Repairing Circuit Boards

By MILO A. ADLER

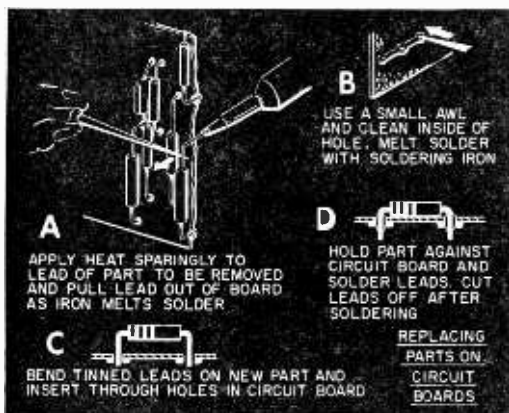

MANY home receivers for AM, FM, and TV, as well as numerous electronic construction kits utilize a circuit board for much of their wiring. The circuit board is a sheet of insulating material on which parts are mounted and connected by means of wires that are nothing but thin copper foil bonded to the circuit board. The bond between the etched wires and the circuit board will last indefinitely under normal use. But excessive heat or pressure can break the bond, and occasionally a circuit component will fail and cause a short circuit which can then burn out the copper coil wiring.

There is no mystery about the repair of these circuit boards. Repair is simple.

First, the soldering iron used should be no larger than 50 watts and all soldering operations should be performed as quickly as possible. Rosin flux can be used but such flux should be completely removed following the soldering operation. Use a cloth (or a short stiff brush with fiber or hair bristles) moistened with acetone or alcohol to wipe the flux off of the board.

Second, when mounting components, bend their leads so that they slide easily through the mounting holes. Press components firmly against the circuit board before soldering on the reverse side. Apply the soldering iron to the lead of the part, rather than to the etched wiring itself. Tin component leads before mounting to reduce the possibility of damage from heat as the joint is made. Cut off excess lead length after soldering.

Third, cover all newly soldered connections on the circuit board with a good insulating varnish or equivalent preparation. Pressurized cans containing acrylic spray-on plastic insulation are available from radio parts distributors and are ideal for this purpose. Do not, however, allow this insulation to enter controls or get on switch contacts.

A broken or burned-out section of a foil-type wire can be repaired or replaced by soldering a length of copper wire *over* the damaged section. Overlap the wire onto the undamaged portion of the foil for about $\frac{1}{2}$ in. if possible. Use pre-tinned wire with a dia. less than the width of the foil wire. A short section of wire from a capacitor or resistor lead is ideal for use for this method of repair.

Sometimes, the foil wires of a circuit board will partially raise up off the board. Cement such wires in place with a quick-drying acetate base cement such as *Duco* which has good insulating qualities when dry.


Components are usually soldered to small round tabs on the foil side of the board. Should one of these tabs become loose or broken, repair it immediately. Hold component on opposite side of board, apply soldering iron to melt solder, and press and hold the tab against board with any convenient tool until the solder sets (after removal of soldering iron). A tab can be replaced by forming a small loop in the end of a short, bare wire and then soldering the loop to the foil wires in place of the missing tab.

Components can be replaced by simply unsoldering and discarding the defective component (apply heat sparingly to lead and pull from board as iron melts solder), cleaning the mounting holes, and soldering in the replacement. Clean out holes by melting the solder and thrusting a small awl through the hole while the solder is still melted.

Tube sockets can be replaced by prying the socket up by each socket pin in succession and momentarily melting the solder on the reverse side of the board. You will have to go around the socket several times before the socket is free of the board. (Some sockets are mounted in such a manner, however, that each terminal can be loosened from the circuit board in only one operation.) Clean socket mounting holes with an awl, insert new socket, press firmly in place, and solder.

REPAIR REMINDERS

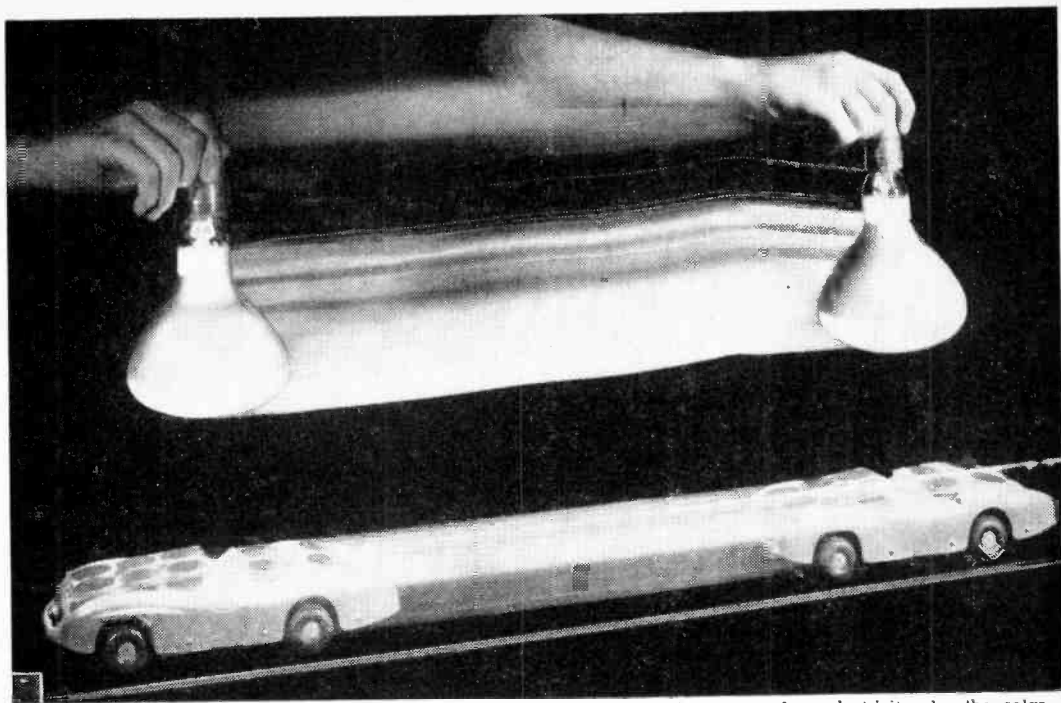- DO NOT** push or pull on attaching wires in a way that will raise the foil wiring from the board.
- DO NOT** use a soldering iron larger than 50 watts.
- DO** clean holes to receive wire leads without force.
- DO** pre-tin wire leads so connections can be soldered quickly.
- DO** clean off rosin flux residue after soldering.
- DO NOT** use any type of paste or acid soldering flux.




Light from 300-watt, reflector-type bulb used as a substitute for sun, is converted to electricity—by the solar cells on top of the car and used to drive electric motor to propel the car.

Solar Powered Car

New low-cost, silicon cell sun batteries supply all the current needed to power this electric-motor driven toy car

By HAROLD P. STRAND

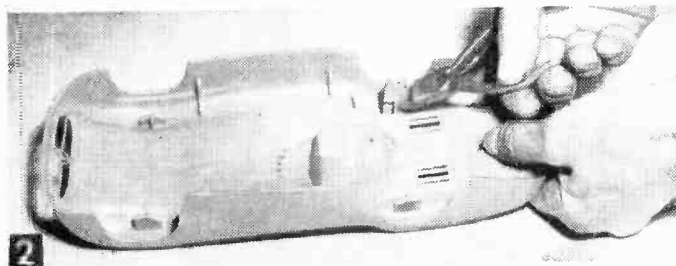

Clip off original axle supports with a diagonal cutting pliers.

WHEN one considers the rapid advancement of scientific discoveries and developments in recent years it is not too difficult to imagine this little solar powered car as the vanguard of the future full-size car.

When sunlight, or light from a 300-watt electric-light bulb, strikes the silicon solar cells mounted on top of the toy car (Fig. 1), 11-13% of the light received is converted into electricity

which powers a tiny electric motor. The motor drives the rear wheels through a gear train made of discarded clock gears. Theoretically this little car should operate indefinitely without replacing or recharging any batteries. All that's required is the free energy from the sun.

Solar Battery. After purchasing the parts called for in the Materials List, prepare the toy car for the installation of the solar cells by removing the wheels and axles and cutting off the plastic axle supports as in Fig. 2. Set the car body aside for the present and start soldering wire leads to the solar cells. On the 1-A cells, a silvered ring will be found around the underside edge of the cells and a silvered circle at the center. The ring is the positive or plus side and the center circle the negative pole of the cell. Use

twenty 4-5-in. lengths of #28 gage Alpha red and black plastic covered wire for the leads. Bare the ends $\frac{1}{8}$ in. and tin with solder. Then solder the red leads to the ring and the black leads to the center circle of the cells as in Fig. 3A. If the 2-A cells are used, solder the black lead to the back of the cell and the red lead to the silver ring on the front of the cell as in Fig. 3B. Since the cells are sensitive to heat,



each group. Connect these two reds together and splice on a red lead to go to the motor. Do the same with the two black leads.

Now, before permanently connecting these


leads to the motor, make a test for motor rotation (Fig. 10). With bright sunshine or a 300-watt bulb shining on the solar cells, temporarily connect the leads to the motor and check to see if

the rear wheels are turning in a forward direction. If not, simply reverse the leads. Then solder the connections and insulate all of the connections by slipping short lengths of spaghetti over them as in Fig. 11. Finally, assemble the chassis to the plastic car body with 4-40 screws through the 6 chassis brackets to complete the project.

This little car should be operated on a smooth and level surface to reduce starting resistance to a minimum. All d-c motors require an excessive amount of current at the initial start because the armature is at rest and its resistance so low as to be practically a short circuit for the battery. With a solar battery, this results in a severe voltage drop at the starting period and with no reserve energy as you might have with a dry cell, car starting is handicapped to begin with and cannot overcome obstacles under the wheels. Once the car has started, however, the back e.m.f. developed in the armature results in a drop in the current requirements and the car runs along very well.

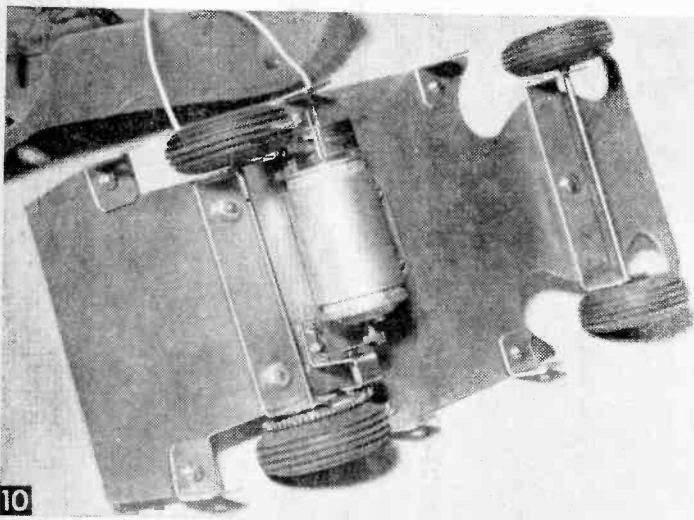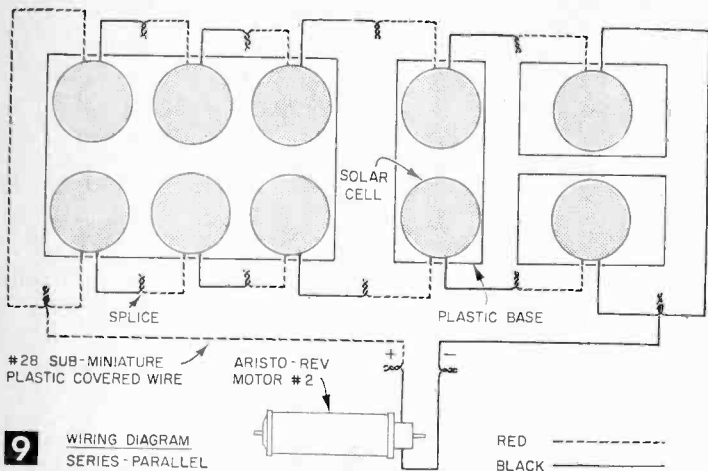

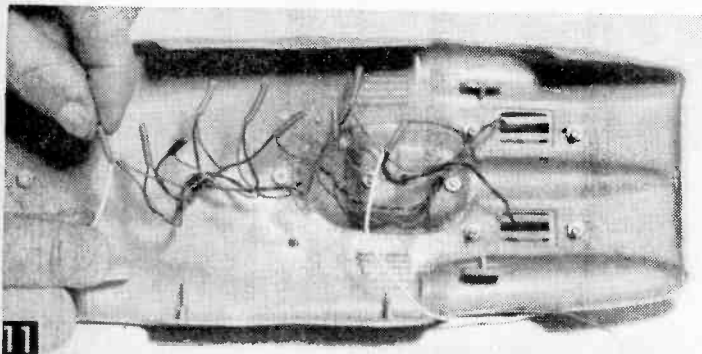Underside view of completed chassis. Test rotation of motor before assembling chassis to body.



Insulate soldered lead splices with short lengths of spaghetti tubing which must be forced over wires.

Extending Radio Battery Life

MANY portable battery-operated receivers tend to cease operation long before the batteries have terminated their useful life. This is usually due to the set's oscillator shutting off because of reduced voltages on the tube elements. By increasing the signal feed-back voltage however, the oscillator will continue operation even on reduced voltages. A few extra turns of wire added to the "tickler" winding of the oscillator coil will boost the feed-back enough to insure a longer battery life, and considerable saving in replacement dollars.

—JOHN A. COMSTOCK.


Powered-Phone Intercom

By HOMER L. DAVIDSON

HERE is a small intercom unit that is easily constructed with cabinet material taken from the scrap pile. It uses only two small transistors, two miniature transformers, two powered phones and a few capacitors and resistors. A DPDT push-type switch will switch either of the powered phones into operation when calling or listening.

The circuit is very simple. A powered phone is switched through coupling capacitor C1 to the base connection of TR1 (see Fig. 2). Transistors TR1 and TR2 can be either CK722 Raytheon or 2N107 General Electric. The emitter connection of TR1 is grounded. R1 is a 470,000-ohm, 1/2 watt, base return resistor; a miniature coupling transformer, T1, couples TR1 and TR2—a second 10 mfd electrolytic capacitor is in series with this transformer to the base of TR2. T2 is a step-down transformer matching the impedance of the powered phone units. A small rotary SPST switch turns the intercom Off and On, the 15-v. battery is a Burgess transistor miniature battery.



The mounting chassis is a 1/4 x 2 x 2 1/2-in. strip of plastic. Circuit components are mounted on one side, all of the wiring is done on the other side. Drill small holes through the plastic so that all wire leads from the components can be pulled through and soldered on the opposite side. Solder transistors directly to their common components after soldering components together, thus eliminating extra heating of the connection and presenting damage to the transistors. (Another method is to hold a long nose pliers at the point of connection so that excess heat will be distributed to the metal pliers.) Complete all of the wiring on the plastic chassis and then solder con-

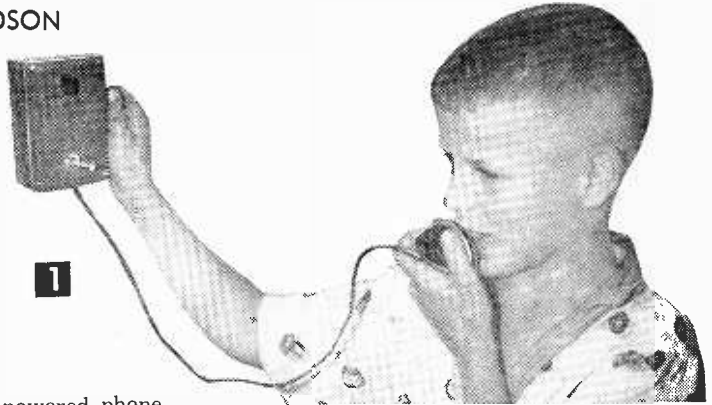

Small, rugged and inexpensive, this powered-phone intercom can be set up at any location, to any location in the house.


necting wires to the DPDT switch. Two small bolts hold the chassis securely to the rear panel; the remote phone, P2, is simply hung from a nail or screw by placing a stiff piece of wire into two small holes drilled into each side of it. P1 is suspended from the front of the intercom chassis with the same wire.

To test the unit, turn the SPST switch On. If P2 is placed within a few feet of P1, a feedback whistle should be heard. Now take the remote P2 outside or away from the master phone unit and talk into it. Talking can be heard 10 or 12 ft. from either phone unit. Each power-phone is used as a microphone to talk into and a speaker to listen to. You can hold either in the palm of your hand, speak, and easily be heard. There is no need for a volume control since volume is adequate up to 100 ft. of remote

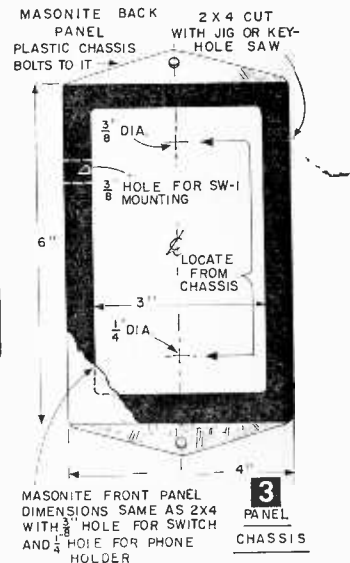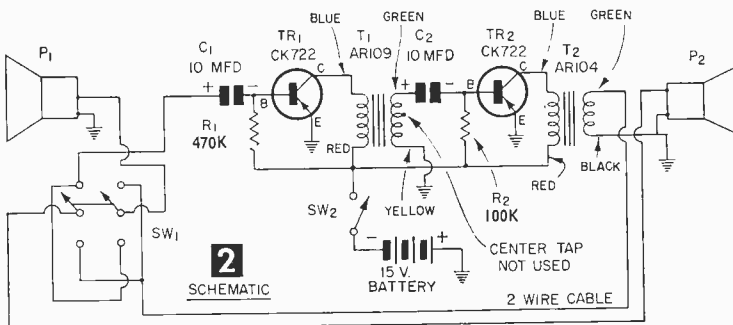

MATERIALS LIST—POWERED PHONE INTERCOM	
Design.	Description
P1 & P2	powered phones (see text)
C1 & C2	10 mfd, 15-v electrolytic capacitor
R1	470,000-ohm, 1/2-watt resistor
R2	100,000-ohm, 1/2-watt resistor
TR1 & TR2	CK722 (see text)
T1	AR109 (Argonne or equivalent)
T2	AR104 (Argonne or equivalent)
SW1	DPST push-to-talk switch
SW2	rotary On-Off switch
BaH	15 v Burgess battery

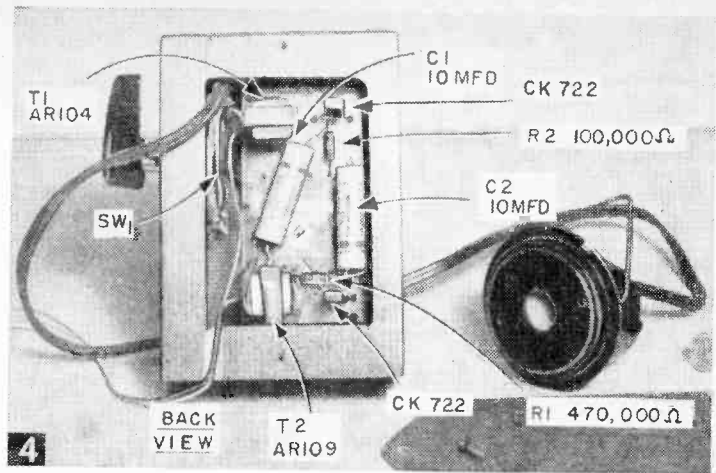All parts available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.




View of rear of unit (back panel removed) showing component placement on inner plastic panel.


cable used. You can use this small powered-phone intercom anywhere in the house.

Improved Test Clips

• Two test clips screwed together back-to-back work better for fast temporary connections than one ordinary clip. To fasten the clips together, clip off the wire support tips at the back of the clips, remove the screws and use just one common screw to fasten both clips together. Used in pairs, clips at one end connect to components and clips at other end connect to terminals or wires. By connecting wires to center screws and placing various components in the jaws of each clip, parts can be connected in parallel, increasing or reducing values to meet existing requirements.

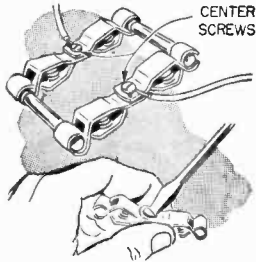


Socket Is Hot Iron Rest

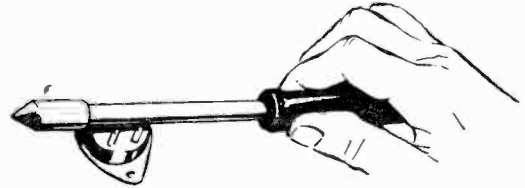

• If you've ever lost or misplaced the stand that came with your soldering iron when it was first purchased, you soon come to realize how handy the little gadget was, and wish that you could purchase another to take its place. Don't try, because you can't—that is, not without buying another soldering iron. But you can obtain a useful substitute from an old junked radio, or for about 12c from a radio parts supply store—a molded tube socket like that shown in drawing. The Bakelite base of such a socket makes an ideal heat insulator and if you obtain a four-pronged base, it's practically impossible for the iron to roll off the prongs and burn the bench top.—J.A.C.

Current Reveals Twin-Lead Break


• Often, broken wires in weathered television twin-lead are undetectable visually since they part *inside* the tough plastic insulation. Rather than discard such a line as unusable, try the hookup shown in the diagram, connecting one end of the lead-in to a bulb socket containing a 60-watt light bulb, the opposite end to a line plug. Now, plug the hookup momentarily into a convenient wall outlet. More often than not, current will bridge the gap between the broken wires and the heat produced will melt the insulation at the location of the break. Once the break is found, splice the lead-in in the usual way and the line will be serviceable once again.

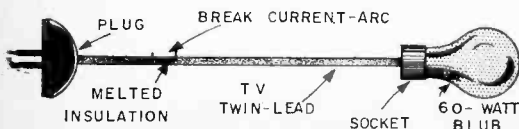

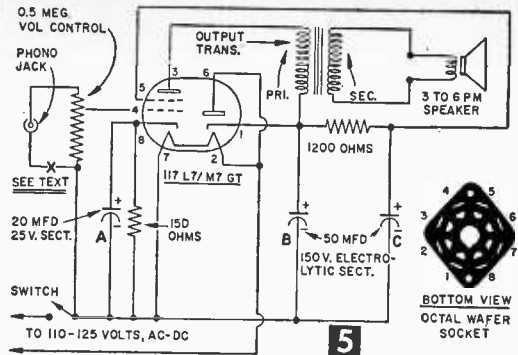D. Vietor

MATERIALS LIST—1-TUBE AMPLIFIER

- 1 pc. #16 gage aluminum (for chassis) $4\frac{1}{8} \times 4\frac{3}{4}$ "
 1 octal wafer socket; $1\frac{1}{16}$ mtg. centers
 1 C-D electrolytic capacitor, triple section (50-50 mfd., 150 v., 20 mfd., 25 v.) Type U.P., #5515C. Note: Constructor may substitute 20-20-20; 30-30-20, etc.
 1 0.5 megohm volume control with switch
 1 150 ohm, $\frac{1}{2}$ watt resistor
 1 1200 ohm, 1 watt resistor
 1 phono jack (ICA, RCA) 1 4-in. PM speaker
 1 output transformer (2500 ohm pri., 3-5 ohm sec.)
 1 117L7/M7GT tube 1 6-ft. line cord & plug
 Miscellaneous hardware, hook-up wire, rubber grommets
 Suitable pickup cartridges for use with this unit are: Astatic L-72A, L-82A, L-12, L-12U, 15L3-AG and 16L3; or Shure W42N, W56A, or W56N.



To minimize wiring, the amplifier chassis forms the negative side of the circuit as a ground. While this arrangement leaves the chassis "hot", it is quite safe from shock when mounted in a wood or other non-metallic housing. Shock that might result from handling metal pick-up arm on a record player can be prevented by inserting a .05-mfd 200-volt paper capacitor at (X) in Fig. 5 and mounting the phono jack on a Bakelite disc. However, most modern pick-up arms are plastic. The only chance for a shock from touching chassis is when you're standing on a damp concrete floor or touching some grounded object.

The completed amplifier was so small there was no commercial stock cabinet that would fit. I made the cabinet shown in Fig. 1 from a cigar box. Remove all the printing or decorative paper with a sanding disc mounted in a portable electric drill. Cut out the $3\frac{5}{8}$ -in. hole for speaker with a fly-cutter, coping or keyhole saw. After


a fine sanding, apply two coats of white shellac, sanding after each coat is dry with 6/0 garnet paper. Apply paste wax and polish. Cement a disc of cloth to the back side of the speaker hole.

The cigar box cabinet takes a 4-in. PM speaker, but any size up to 12 in. may be used in a suitable baffled box with greater volume and improved tone quality. Since the amplifier is a complete unit, the speaker may be mounted separately from the amplifier. The output transformer for the speaker may be mounted directly on the speaker (brackets are usually provided).

You can mount the amplifier in the cigar box cabinet with the threaded $\frac{3}{8}$ -in. bushing of the 0.5 megohm volume control. Bring out the two flexible leads from socket lugs #3 and #1 for connecting to the primary of the speaker transformer. Use rubber grommets on these two flexible leads and on the power line into the back of the chassis.


Antenna for Small Radio

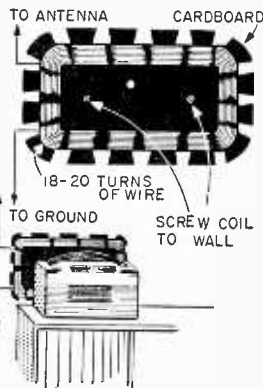• If your miniature battery radio proves almost useless in your mountain cabin, try this simple method of increasing its range, which will also work equally well on ac-dc sets. If you are unable to obtain a loop antenna coil from a junked radio or a radio supply house, cut a piece of cardboard to shape shown in sketch. In basket weave fashion, wind



on this form 18 or 20 turns of cotton-covered copper wire or bell wire. To one end of the coil connect an antenna wire 30 to 50 ft. long and at least 10 ft. from the ground. Connect the other end to a water pipe or a metal rod driven into damp ground. No connections are necessary to the set itself; simply screw the coil to the wall over a bookcase, table or shelf and place the radio close to it.—FRED W. MOOREHEAD.

Tape Recorder Kink

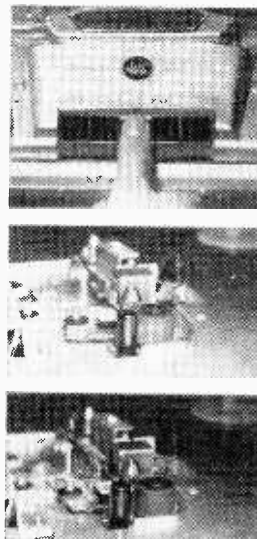


• If your tape recorder has a roller-release pushbutton marked "Stop" (as shown being depressed in top photo), it's a wise idea always to leave this button depressed when the recorder is standing idle. If you don't, the roller will develop a "bump" or depression in its surface from being tightly pressed against the round capstan (center photo). Such an irregularity in the roller's surface may cause undesirable flutter, wow, or thumping.

When the stop button is depressed, the roller and capstan separate as shown in bottom photo.—JOHN A. COMSTOCK.

Low-Cost Fire Alarm Systems

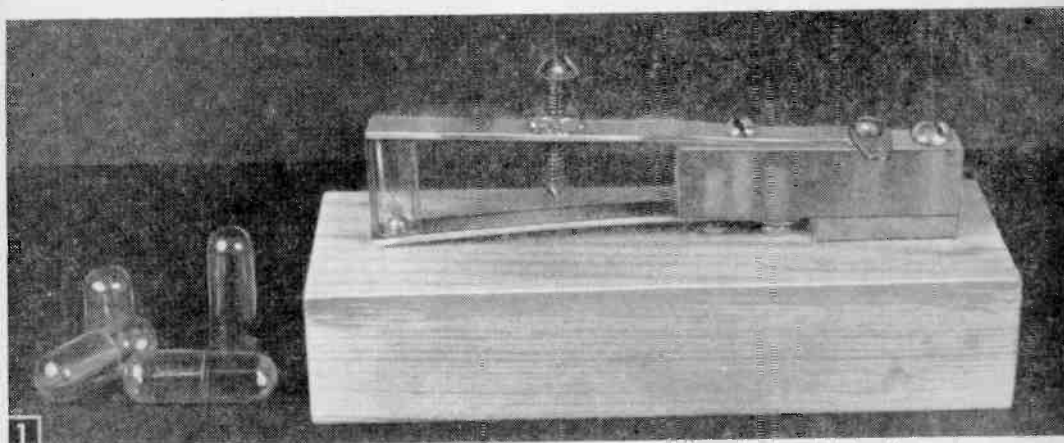These simple systems sound their alarms when a fire first starts, thus providing an opportunity to limit damage and even to save lives




Sensor unit with capsule section in place, extra capsules at left, cover removed.

By W. F. GEPHART

WITH the exception of explosions, most damaging fires start small—and aren't discovered until they have gotten a good start. If they could be discovered when they first start, they could be extinguished easily. These systems will discover them early.

Their "heart" is a simple, home-made fire "sensor" (see Figs. 1 and 2). The control element in this sensor is an ordinary pharmaceutical capsule, which melts as heat increases and by doing so closes the electrical circuit which sounds the alarm. By using different sizes and thicknesses of capsule sections, and by adjusting the tension screw on the sensor, the closing temperature can be varied between 100° up to over 250° F.

Construction details of the sensor unit are shown in Fig. 2. Basically, it consists of two strips of spring brass (#20 or #22 gauge), insulated from each other by a plastic block, and spread apart by a section of capsule. An adjustable contact is provided and—as the capsule collapses under heat—the spring brass strips move together until contact is made and the circuit closes. The bottom brass strip is held to the plastic block by two 4-36 machine screws threaded into the block, one of which has a solder lug under it for connection. The back 4-36 machine screw on the top strip goes through the plastic block and shim and wooden base to help fasten the assembly to the base; the top strip is kept in line with the bottom strip by a tension screw threaded into the plastic block.

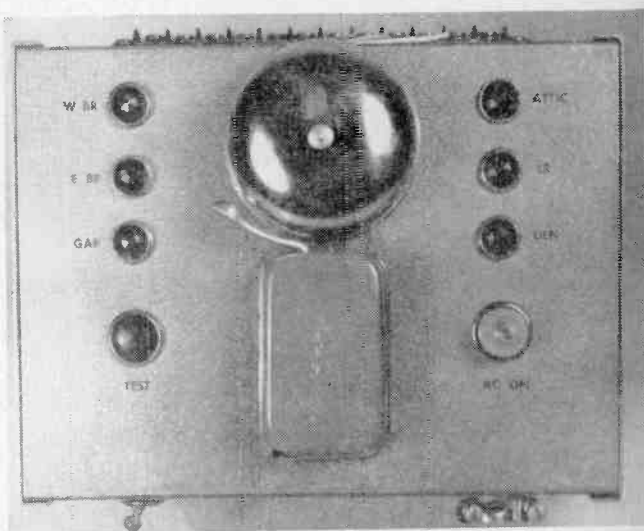


Front panel of indicating unit. Note Romax cable clamp lower right for power entry, SW1 lower left.

Bend the top brass strip slightly (see Fig. 2), so that as the tension screw is tightened, the outer end of the strip will move down. Since the two strips are held apart by a capsule section, tightening the tension screw will cause the capsule to collapse more rapidly as heat increases.

Between the end of the upper strip and the plastic block, mount a contact screw in a nut soldered to the top of the strip. To insure good contact, grind the end of the screw to a point and, to maintain adjustment, "burr" the screw's threads so it is hard to turn.

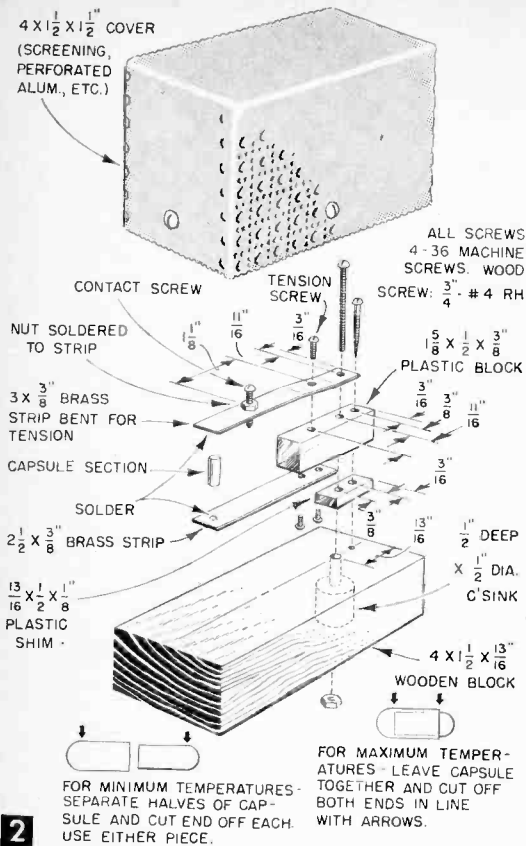A "glob" of solder at the end of each strip prevents the capsule section from slipping. To make



one for 69c) and put it in the can beside the sensor, making sure the bulb of the thermometer does not touch the side of the can and that it is as near the capsule section as possible. Lay the can on its side and play a blow torch along it. Watch the air temperature as registered on the thermometer and set the sensor to the desired alarm temperature by adjusting the tension screw and contact distance so that the capsule melts at the desired temperature, ringing the alarm or lighting the bulb. If several tests have to be made, be sure to cool the brass strips with a damp cloth between tests. Since capsules are consistent in size and thickness, changing capsules will not affect the accuracy of adjustments.

If sensors are to be placed in bedrooms, living rooms, etc., appearance becomes important, and a cover should be made. Some sort of a cover (at least screen wire) should be provided in all cases to prevent mice from eating the gelatin capsule.

A perforated aluminum or extruded metal cover makes a neat and nice appearance. For dimensions, see Fig. 2. Whatever is used should provide a free flow of air through the unit and should be painted, if possible, to minimize heat reflection. For the same reason, the wood block and inside of the cover should be painted black to absorb heat.

Alarm Unit. There are several types of alarm circuits that can be used. Figure 3A shows the simplest circuit, all sensors wired in parallel, in series with a bell. This provides an alarm, but gives no indication which sensor has closed.



Figure 3B shows an "indicating" alarm. A pilot light indicates which sensor has closed when an alarm sounds; the bell does not necessarily have to be at the pilot-light box location. This type of circuit is particularly useful when some of the sensor locations are widely separated, as would

"globs," drip hot solder on a piece of glass, hardwood or other smooth, non-metallic surface, then tin ends of the brass strips and carefully lay globs in place. Cautiously heat opposite sides of strips until bottom of globs just *begin* to melt and they will stick in place without flattening out.

Pharmaceutical capsules come in several sizes and can be purchased at any drug store. The smallest size have the thinnest walls (and therefore collapse most rapidly under heat) and should only be used when the alarm is to sound at relatively low temperatures. The largest size, particularly when used double thickness, withstands very high temperatures when only light tension is used. A single section large capsule, with moderate tension and 1/16-in. contact clearance, will close the circuit at approximately 150°.

Make a sensor for each location to be guarded. The temperature set for may vary for different locations. In a basement, for example, it should be set for a low temperature (around 100°) since normal room temperatures do not get very high, while in an attic it should be set high, since summer room temperatures sometimes exceed 110°.

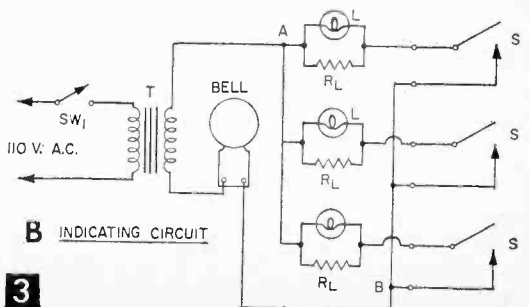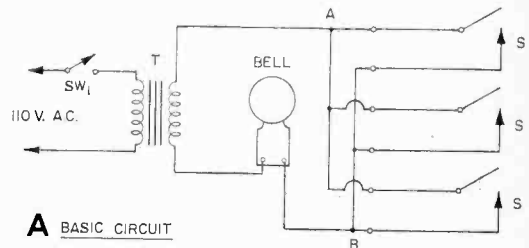
To set the sensors, connect them to the alarm unit (whose construction will be covered later) or to flashlight batteries and a bulb, and put the sensor in a large fruit juice can. Borrow your wife's candy or deep-frying thermometer (or buy



be the case with out-buildings on a farm, separate garages, etc.

Many fires, however, are started by defective electrical wiring which kindles a fire, and then blows the fuses, rendering the alarm units shown in Fig. 3 valueless, since power would be gone by the time the fire got hot enough to close the sensor switch. Figure 4 shows a complete alarm unit which provides for automatic power switch to battery in case of power failure.

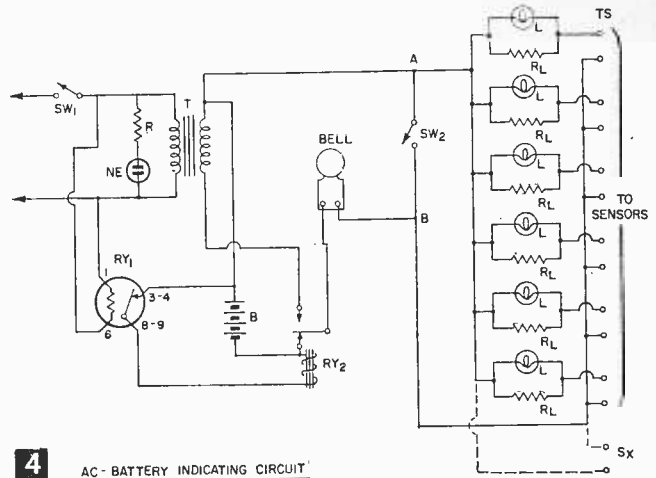A fast-acting, normally closed thermal relay (Ry1) is across the power line, and is held in the "open" position by line voltage. In this position, Ry2 is not energized and voltage from the transformer secondary operates the system. If the power fails,



4 AC-BATTERY INDICATING CIRCUIT

Ry1 closes (after a few seconds), energizing Ry2, which connects the battery to the alarm system. When power is restored, Ry1 opens, de-energizing Ry2, and re-connecting the system to the transformer voltage.

This circuit has two other features that could be added to either of the two circuits shown in Fig. 3. One is a neon lamp across the primary of the transformer to indicate the presence of line voltage, the other is a test button (SW2) for testing the alarm unit by momentarily shorting the sensor circuits. The test feature can be added to the other circuits by connecting the push buttons to points "A" and "B" (Fig. 3), the neon lamp feature can be added by wiring across the primary of the transformer.

In the indicating circuit shown in Fig. 4, Ry1 is a continuous-duty relay and it, together with the neon bulb and transformer, consumes less than 3 watts. Operating expenses are therefore only a few cents a month. The sensitive plate-circuit relay (Ry2) in the battery circuit was used instead of an ordinary 6-v dc relay because of its low power consumption. It draws only a few ma, so battery operation is possible for many hours, even on the small flashlight batteries used. A cheaper, ordinary 6-v relay can be used if larger batteries are provided.

While the Materials List specifies either a 6.3-v filament transformer or a bell transformer, and specifies four flashlight batteries, use the bell transformer (with its higher output voltage) and add two additional flashlight batteries (to provide 9 v) if there are any long leads to sensors. Lamps and resistances would not have to be changed if higher battery

Back panel view of indicating unit schematized in Fig. 4. Note "tube" relay (center), Jones terminal strip at top for sensor lead connections.

MATERIALS LIST—FIRE ALARMS

The following materials are required for all diagrams:

- SW1 SPST toggle switch
- T Bell transformer, or 6.3 volt @ 1 amp. filament transformer (see text)
- Bell 2 1/2" or 3 1/2" doorbell
- S Sensor units; one per location (see text)


The following additional materials are required for the units in Fig. 3B:

- L 2.0 volt @ .06 amp. pilot light (GE #48 or #49)
- RL 3,3 ohm 2 watt (with filament trans.) or 2.2 ohm 2 watt (with bell trans.)
- Pilot light holders

Further additional materials required for the unit shown in Fig. 4 are:

- NE Neon bulb (NE-51)
- R 56,000 ohm 1/2 watt (if not included in NE holder)
- Ry1 Thermostatic Delay relay, 115 volt, 2 second delay, normally closed (Amperite 115C2 or 115C2T)
- Ry2 SPDT relay with coil sensitivity of 12 milliwatts or less (Sigma 5F-2500-S/SIL, Advance S0/1C/6500D, or any relay that will close on the current that 6 volts will send through its coil)
- B 6 volt battery (Four flashlight batteries—see text)
- SW2 SPST push button

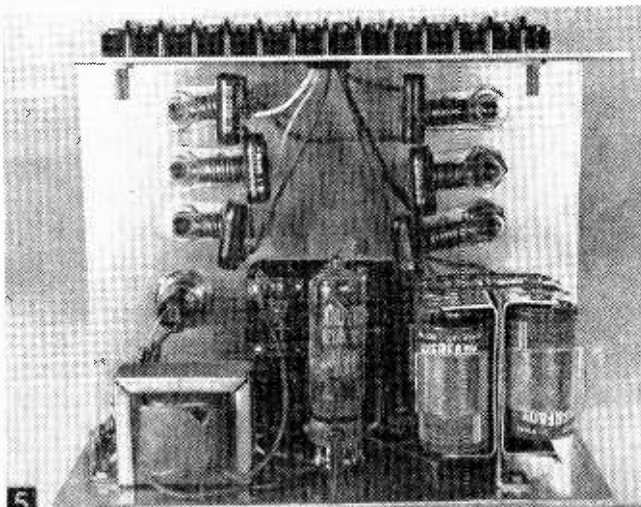Socket for Ry1 (Octal for 115C2, 9-pin min. for 115C2T)
 Optional: Battery clamps, terminal strip (Jones 140 series), screening, perforated aluminum (Reynolds), or extruded metal for sensor covers



5

voltage is used, but resistances used will vary with the transformer used (see Materials List).

With either indicating circuit, it is unnecessary to have a pilot light with the sensor covering the room in which the pilot light box is located. If the alarm sounds and you go to the pilot-light box room to check location, you don't need a light to tell you the room is on fire. (Connect the sensor as shown by the "Sx" dotted connections).

Figure 5 is a photo of the alarm unit shown in Fig. 4. Since needs will vary depending upon how many sensors your home is equipped with, layout dimensions are not given. I mounted bell and batteries with the light indicators, although either or both could have been located elsewhere. In any case where line voltage is present, enclose components in a metal box to meet Underwriter's and local electrical codes.

Some of the parts shown in Fig. 5 were used because they were on hand or were less expensive than standard items. Jeweled pilot light holders need not be used (but were on hand);

the lamp resistors were surplus items, as was the transformer, which actually gives about 7 v, not 6.3.

In setting up a system, the location of a sensor within a room or area should be on (or near) the ceiling, as near the center of the area as possible. Placing the sensor above (or in air-flow line with) a heating vent, radiator, stove, etc., may require too high an alarm temperature, and placing it too near a window may mean that it won't close (if cooled by air from the window) until the fire has gotten a good start. Keep in mind that the sensor operates due to heat. It should be located where it is unnatural for heat to build up, where only a fire can actuate it.

Once installed, the system should be tested at regular intervals. Each sensor capsule should be "burnt out" with a match to make sure the alarm sounds. If a test button is provided, the unit itself should be tested on ac, and (if battery is provided) on battery, by turning power switch SW1 to Off.

Capacitor Pops TV Pix Tube Short

• There's no need to discard a TV set's picture tube just because there's an internal short circuit between some of the inner elements. More often than not, the short is caused by conductive "dandruff" that has flaked off from one or more of the elements and can be removed easily with a charged electrolytic filter capacitor connected to the outer base pins.

Select a healthy capacitor with a high value of capacitance and a high voltage rating. (about 50 microfarads at 250 volts), and connect it momentarily to a dc source not exceeding the capacitor's voltage rating. (Be sure to observe polarity—plus to positive, minus to negative). Now connect the charged capacitor to the two element pins that are shorted internally. The current from the capacitor will flow through the internal short and burn it out with a loud pop and flash from the inside neck of the tube.—J.A.C.



It will only take me a minute to vacuum, dear!

Treating TV Tubes Like Eggs



• When transporting TV tubes to your local testing station, place them in an egg carton for carrying without danger of breakage. Attach a small piece of adhesive tape to each tube so that you can jot down its condition after checking.

Answer to Crossfigure, Page 91

1	6	0	0		2	3	1	0		4	0	0	5	1
7					6	1	0	7		7	2	0		8
8	5	2	9	5		5		10	4	11	5		12	13
2			14	5	0		15	6		0			16	9
			17	6	0			18	3	0	0		19	3
20	1	5				21	8	8				22	1	0
0			23	4	0			24	1		25	2	5	0
26	8	0		0				27	2	0	1		28	0
			30	6			31	1	0			32	1	
33	3	0	0				34	2	0	0		35	9	0
6				36	4							2		37
0			38	1	8	7	7			39	1	9	2	0

Finger-Clip Transistor Radio Is It the World's Smallest?

SO SMALL is this radio, it fits easily on a ring clip on the finger. Granted it makes a large ring, but as a radio, it might qualify as the world's smallest transistor set. Complete with built-in power supply, it measures a mere 1 1/8 in. square and 5/8 in. high. And, to make it even more interesting, it will operate on a simple, homemade "dry charge" battery using 1/10th cent worth of material, or it may be powered with a mercury cell scarcely larger than an aspirin tablet. Or the builder may, if he wishes, operate the set with a silicon solar cell.

All components used in building the ring radio are standard, with only the ferrite slug-tuned antenna coil modified, and the excess coil form cut off to fit the available space. Components are neatly and securely mounted to a 1 x 1-in. plastic chassis board, except, of course, the miniature magnetic hearing aid earphone. This makes for a neat wiring job, and the set can be removed from the tiny plastic box simply by removing the 1/4 in. long, 3/48 flathead screw and nut, which hold chassis, ring band and case together.

For the case, use a small plastic trinket box, such as is used to package fishing tackle, sewing notions, phono needles, etc. For the chassis, use 1/32-in. fiber or Bakelite (but not acetate, which would melt when making soldered connections). Draw a line from corner to corner of chassis to locate the center hole which is drilled to clear the 3/48 screw.

The coil in its original form is wound on a paper-base Bakelite form 2 in. long and 1/4 in. diameter. First unscrew the core from the coil, then unsolder the coil leads terminated on the lugs. With a safety razor blade, cut off the excess portion of the coil form so that the remaining coil form is just 3/4 in. long.


Because the coil form is brittle, use a gentle sawing motion. Once the razor's edge passes through the Bakelite, slide the ferrite core into the form, to provide an inner support while you





1 Transistorized ring radio tunes entire broadcast band. Set is housed in tiny 5/8 x 1 1/8 x 1 1/8 in. plastic case, has removable chassis.


sever the rest of the plastic tubing.

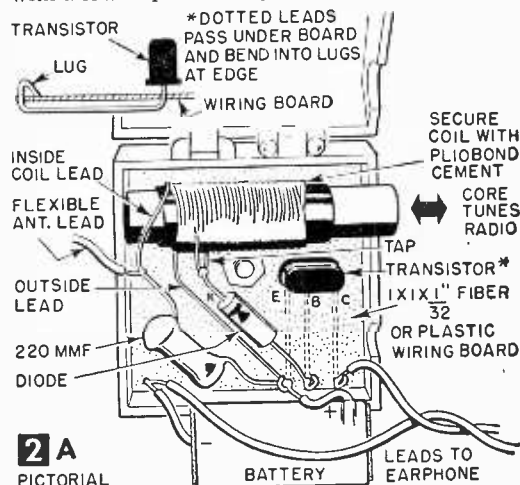To get an efficient match between the tuned circuit and diode detector, the coil is provided with a low impedance tap. To make the tap, care-




2 A PICTORIAL

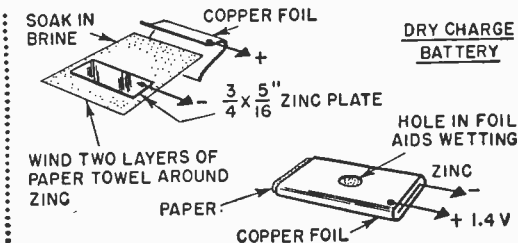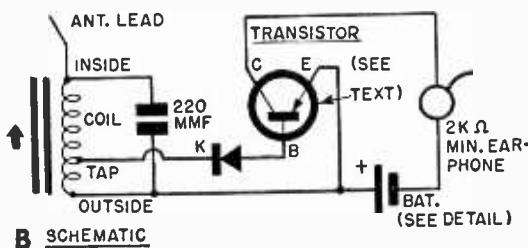

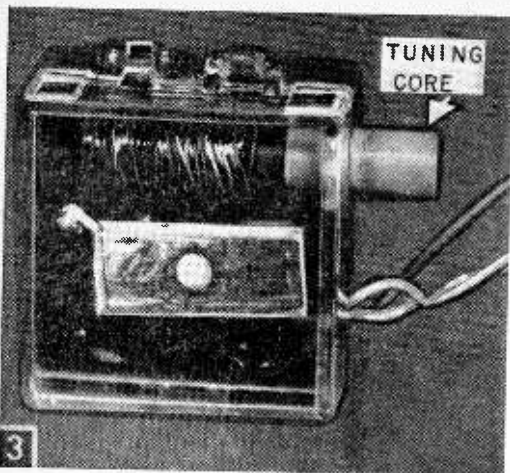

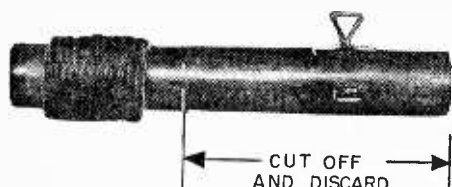Set is sharply tuned by sliding core in and out of coil.



To fit case, Standard antenna 'loop' coil-form is cut off at point shown.

fully unwind 21 inches of wire from the outside end of the coil. Gently remove about $\frac{1}{2}$ in. of the cotton insulation, bend the wire like a hair-pin and twist the bare section together for the tap point. Now rewind the wire back into the space it formerly occupied. Of course, you can't duplicate the progressive lattice effect of a machine winding nor is it necessary. Merely "scramble-wind" as neatly as you can and secure the wire about an inch from the end with a few drops of Duco cement.

Drop the chassis board into the plastic case, after first roughing the area where the coil will be located with sandpaper. Now apply a generous dab of Pliobond cement to the coil board and directly on the coil wire. Allow the cement to air dry for a minute or so; then press coil onto board while it is still in the box. This insures the coil not being too close to the edge of the wiring board, which would prevent the finished set from fitting into the case.

Once the cement has set, the radio is ready for wiring. Spacing for the three transistor leads is best determined with the transistor in hand. Pierce the three holes with a push-pin (one of those glass- or plastic-tipped tacks with a needle sharp point). Next drop in the transistor, and, holding it firmly against the wiring board, use flat- or needle-nose pliers to bend the leads flat on the underside and then up and around the front edge of the board, so that they form hook-like lugs (Fig. 2A).

In order to provide a solid termination for the antenna, capacitor and coil leads, as well as the battery minus and earphone cord, simple tie-pins are made by pushing small flathead brads (cigar box nails) through the underside of the wiring board and securing them with a drop of solder. Clip off excess length of brads with diagonal wire-cutting pliers.

The diode detector may be any miniature germanium general purpose type and the transistor can be any P-N-P a.f. type (such as the 2N107, 2N34, CK-722, etc.). When soldering in these semi-conductor devices, always use a "heat sink" so that excess soldering iron heat is not carried up the lead and into the diode or transistor. A wad of damp cleansing tissue squeezed around the leads while soldering in place will prevent internal thermal damage.

The polarity of the diode connection to coil tap shown in Figs. 1 and 2 applies to this radio when you operate it with the homemade cell or the mercury battery. If a silicon solar cell is used, reverse the diode so the K or banded end terminates on transistor B (base) lug.

The ring band is merely a strip of copper or aluminum $\frac{3}{8}$ in. wide and long enough to fit around the user's finger. Drill and countersink a hole in the center of the metal strip so that the $\frac{3}{48} \times \frac{1}{4}$ -in. machine screw fits flush. Also drill a hole through the bottom of the plastic case, using the center hole in the chassis board as a guide. For the $\frac{1}{4}$ -in. hole in the side of the plastic case which lines up with the tuning coil, first locate the hole's position with chassis board fastened in place. Since this $\frac{1}{4}$ -in. hole will be cut, half in the box lid and half in the base, hold cover securely while drilling. Finally, file a notch in the edge of the box large enough for the phone cord and antenna lead to pass through.

The radio is tuned by sliding the ferrite core in and out of the coil. If core slides too freely, stick a narrow strip of Scotch tape along its length. The antenna lead when clipped to various metal objects, such as a dial phone clip, will pick up stations with surprising volume.


Homemade Battery Power. If you want to power your ring radio with the tiny "dry charge" battery (Fig. 2B) you'll need just a few scraps of copper foil, zinc salvaged from a dead flashlight battery, and a piece of paper hand towel.

Break open the flashlight battery, remove the compound inside and cut up the zinc can into $\frac{3}{4} \times \frac{3}{16}$ -in. strips. If much of the battery case has been eaten away, use only the zinc in good condition and clean it up with steel wool. Solder a length of light flexible hookup wire to the corner or end of the zinc plate.

Next dissolve about 1 teaspoonful table salt in half a glass of water. Dip the paper into the salt solution, then hang paper up and allow it to drip dry. Meanwhile cut strips of copper foil (sold by hobby shops, etc.) $\frac{3}{4}$ in. wide and about 1 in. long. When the salt treated paper has dried, cut it into strips about $1\frac{1}{16}$ wide or just

a trifle wider than the copper and zinc plates or electrodes. Wind two layers of paper towel over the zinc plate. Finally wrap a layer of copper foil over the paper and secure the end with a drop of solder to which a second flexible lead has been attached.

Any number of cells can be made up at one time and stored in a dry place until needed. Wired into the radio circuit, the set will come to life when a drop of water is applied to the exposed paper at each end of the cell. One charge will operate the radio continuously for about 4 hours, then volume will taper off. However, after allowing the set to rest awhile with earphone disconnected, it will recharge again when moisture is ap-

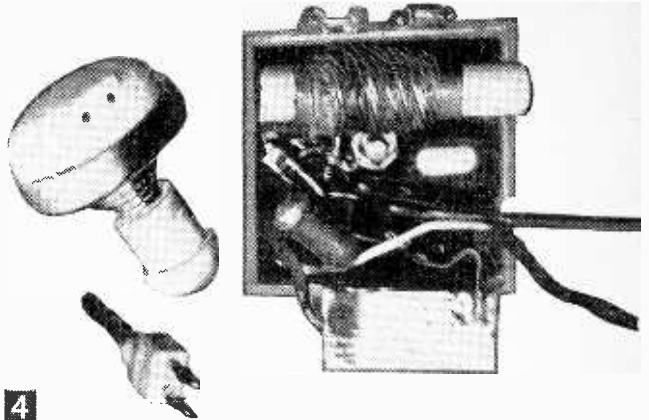

4 "Dry Charge" cell folds back for removing chassis plate screw. To disconnect battery power, disengage the cord from the miniature earphone.

MATERIALS LIST—RING RADIO

- 1 plastic trinket box, size 1 1/8" sq x 5/8" deep o.d.
- 1 pc 1/32" plastic 1" sq
- 1 General purpose germanium diode
- 1 P-N-P transistor a.f. type (2N107, 2N34, CK722, etc)
- 1 Ferrite slug-tuned antenna 'loop' coil
- 1 220 mmf ceramic capacitor
- 1 strip 3/8" wide aluminum or copper
- 1 3/48 x 1/2" fh machine screw and nut

misc. zinc scraps, copper foil, light hookup wire.

Readers may obtain all parts listed above for building the ring radio by sending \$3.49 to: Electro-Mite, Springdale 636, Conn.


NOTE: Few radio supply houses stock the #520 Mercury Cell. It is readily available throughout U. S., Canada, Alaska, T.H.I., and P. R. from any Zenith Hearing Aid dealer. See yellow pages of phone book under "Hearing Aids."

If you desire solar power, four 58C silicon solar cells are needed, available from Hoffman Electronics Corp., Semi-Conductor Div., 930 Pitnar Ave., Evanston, Ill. Cost is about 80¢ each.

plied. In tests we have discharged one battery numerous times over a period of a month and each time it came back.

This condition will not last indefinitely, however, and a new cell will be required due to minute hydrogen action on the copper foil known as polarization. A Voltaic cell variation such as this little "dry charge" unit delivers about 1.44 volts. Because its output is but a few milliwatts it cannot be measured with ordinary instruments, but current is ample for the minute needs of a transistor.

Unique Mercury Cell. If you wish to power your set with a more stable voltage source, the unique 1.34 volt #520 mercury cell employed in eyeglass hearing aids may be used. Unlike carbon/zinc and other batteries, the mercury cell delivers a steady 1.34 volts up to the moment it becomes exhausted. Moreover, these cells, which are about aspirin tablet size, will never swell up, corrode and leak electrolyte into the radio as happens with carbon/zinc cells. Because it is encased in a nickel jacket, leads cannot be soldered to the mercury cell. But two small clips can be fashioned from brass and the cell mounted

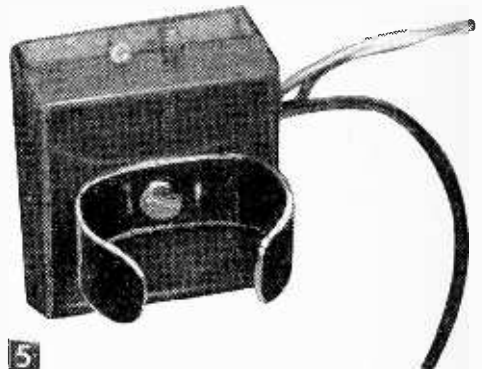

5 Strip of 3/8" aluminum or copper forms expansion ring band. A single 4/48 x 1/4-in. flathead screw and nut joins chassis, case, ring band into a secure unit.

in the lid of the plastic case for easy replacement.

For Solar-power Fans, the ring radio can be powered with a tiny silicon battery consisting of 4 horizontally stacked cells having a total length of 5/8 in. long and 3/32 in. wide. Each tiny cell has a peak output of 0.4 volt at 2 ma. Thus a unit of 4 cells, costing about \$3.20, delivers 1.6 volts which is more than ample for the ring radio.

Toys and Games You Can Make

● If the high cost of giving is getting you down, get a copy of *Toys and Games You Can Make*, a book containing detailed plans and building instructions for over 80 different toys, games and playthings. Ideal for gifts to children—children from two to twenty—the construction projects in this book will save you money while you enjoy yourself making them. *Toys and Games You Can Make* (No. 556) is available in a deluxe, rugged, special hardbound edition for your shop reference library from Dept. 5591, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois. The price is \$1.95.


Toys for Practicing Radio Code

HERE are two electric toys, sold by mail-order houses and toy stores, that with no modification whatsoever can be used for code practice. Figure 1 shows a toy electric shaver called a "Fuzz Buzz" (manufactured by the Electric Game Co., Holyoke, Mass.), Fig. 2 shows its inner workings—a buzzer, battery, and switch, just what the doctor ordered for a code practice set which can be carried around in the pocket! Fasten a paper cut-out of the radio code to the outside of the toy's case with transparent tape; to practice the code, simply press on the push-switch to make your dots and dashes.

Figures 3 and 4 show an electric game called "Electric Jack Straws" (also manufactured by the Electric Game Co.). This toy contains a buzzer, flashlight battery, and flashlight bulb. The object of the game played with it is to insert the tweezers through the holes in the metal lid, and to pull out the straws without setting off the buzzer and lighting the lamp. You can practice the code with it by tapping the tweezers on the metal lid—the buzzer sounds and the lamp lights each time you touch tweezers to lid. Figure 4 shows how to connect a transmitting key, if desired. Simply fasten the tweezers in one binding post of the key, and run a wire from the other binding post on the key to the metal lid (using an alligator clip, as shown). This gives a child a dandy "buzzer and blinker" code practice set.—ART TRAUFFER




1

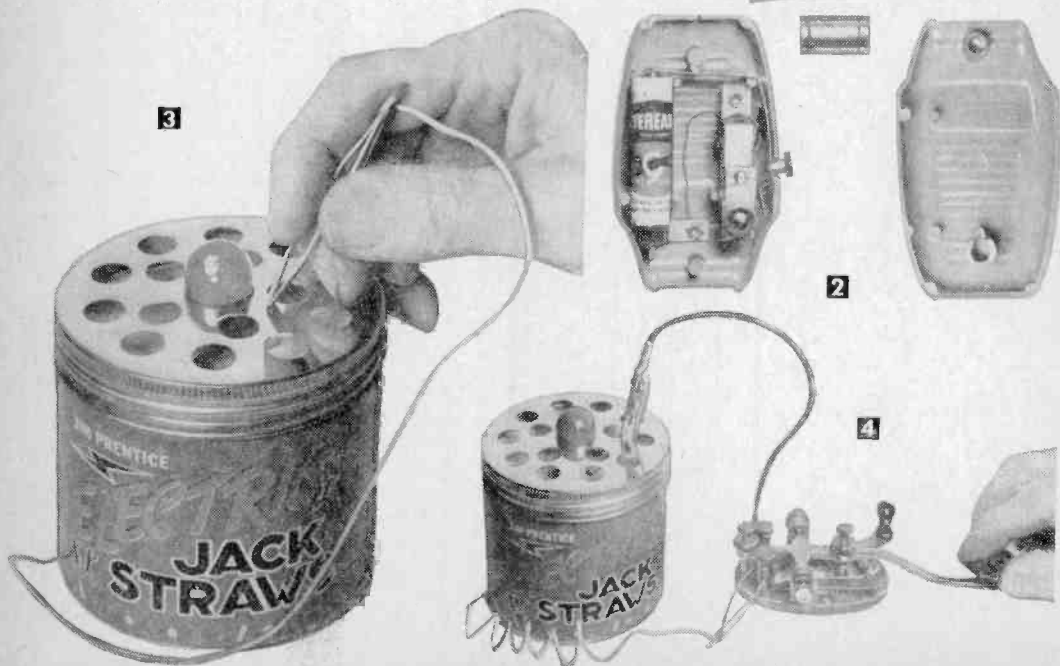

3

2

4

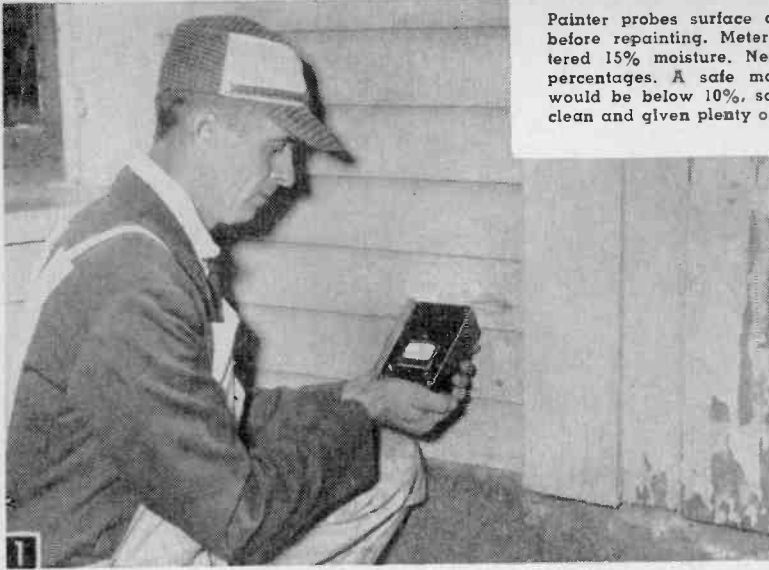

Painter probes surface of house with moisture tester before repainting. Meter showed this test spot registered 15% moisture. Nearby areas registered higher percentages. A safe moisture content for repainting would be below 10%, so this area should be scraped clean and given plenty of time to dry before repainting.

tent is shown on a milliammeter in the plate circuit.

Before using for the first time, the tester is calibrated by pressing the points into a piece of wood that has been thoroughly saturated in water (Fig. 2). You then adjust the rheostat so the meter reads full scale or 1. This represents 100% saturation. Tests in surfaces with less moisture will then be in percentage of full scale or saturation, giving you a fairly accurate picture of the percent of moisture present (Fig. 1).

For the most accurate results, the wood used for calibrating should be of the same kind as that

on the house surface you plan to test (usually pine or spruce), because different woods will give some changes in readings. You don't, however, need highly accurate readings (such as you

For good insurance on costly paint jobs use this

Electronic Moisture Tester

By HAROLD P. STRAND

BEFORE repainting your house, you should know how much moisture there is on or just below the old paint surfaces. If there is much moisture, the new paint you apply may peel off in a short time. The cure, of course, would be to scrape off the old paint, and let the sun and air dry out the excess moisture before you apply the new paint.

But how do you find out how much moisture is in the wood, and how do you know when this amount is too much? Sometimes, of course, simply feeling it with your hand will tell you whether it is damp. Sometimes, however, this "hand test" will tell you nothing. The actual surface may seem dry and yet $\frac{1}{16}$ in. below the surface there is plenty of moisture, which, in time, will work out to the surface and ruin the new paint job.


This simple tester (Fig. 1) shows you how much moisture is below the surface of the wood. Parts for the tester cost about \$9, which is a small amount to pay in order to make sure an expensive house repainting job will last.

How the Tester Works. This tester has pointed steel electrodes (Fig. 2), which are in the grid circuit of a simple vacuum tube amplifier (Figs. 3 through 5). The amount of resistance in the material to be tested varies with the moisture content; the more moisture, the lower the resistance. When the grid circuit is closed by pressing the pointed steel electrodes into the surface you are testing, a positive voltage is applied to the grid causing the tube to conduct, and the amplified value indicating relative moisture con-




Tester is calibrated by sticking probes into a thoroughly saturated area of soft wood. Then adjust control to read full scale on meter, which represents 100% moisture content.

**SCHEMATIC
DIAGRAM**

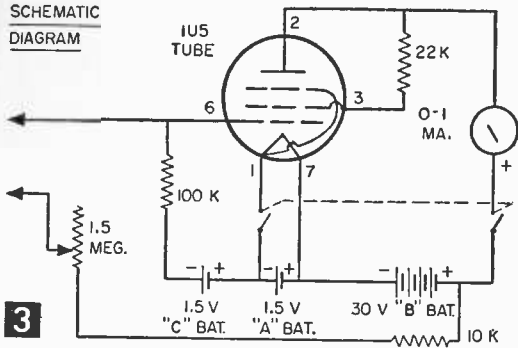


3

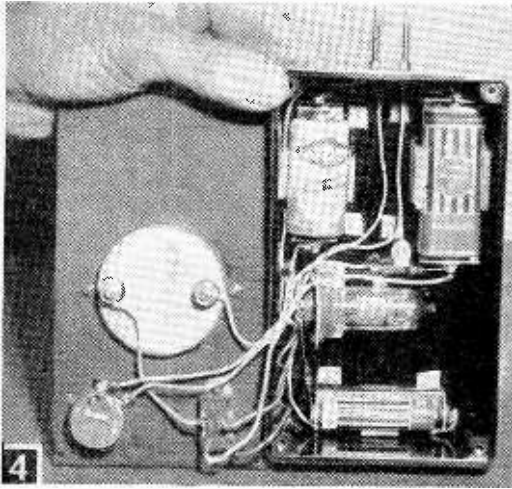

4

5 PICTORIAL DIAGRAM

BACK VIEW OF PANEL

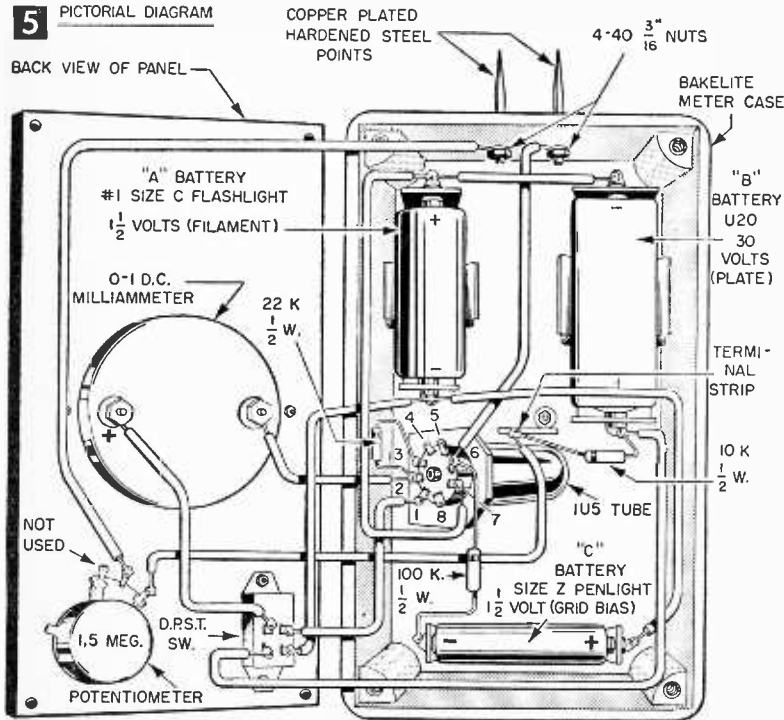

MATERIALS LIST—MOISTURE TESTER


No.	Description
1	Bakelite meter case 2 x 3 3/4 x 6 1/4" Lafayette MS-216
1	1U5 miniature tube
1	7-pin miniature socket (Amphenol Type 147-500 or equivalent)
1	Milliammeter, 0-1 ma. Shurite Model 950, Stock #9300Z
1	slide switch, D.P.S.T. #SW-16
1	Control, 1.5 megohm, Mallory Midgetrol, IRC Q type or similar, linear taper terminal strip, 1—terminal chassis type (also called tie points or mounting strips)
1	10,000-ohm 1/2 watt resistor
1	100,000-ohm 1/2 watt resistor
1	22,000-ohm 1/2 watt resistor
1	battery holder for one size Z penlight cell
1	battery holder for one size C or #1 flashlight cell
1	battery holder for one 30 volt Burgess U-20 B battery
1	miniature knob for 1/4" shaft
1	30-volt Burgess U-20 B battery
1	1 1/2-volt penlight Z cell
1	1 1/2-volt flashlight C cell
Above parts can be supplied by Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y. or in New England from their branch at 110 Federal Street, Boston, Mass.	
1	piece drill rod .108-.110" dia., about 2 1/2" long (Points)
1	piece black Bakelite 1/8 or 3/32" thick x 3 1/2" x 6" (Panel)
1	Bakelite rod stock, 3/4" diam., 3/4" long (for remote handle—see Fig. 1)
1	piece phosphor bronze or hard brass about .012-.014" x 1/4" x 3/8" (contact pieces in plastic block)
2	pieces drill rod .108-.110" about 2 3/8" long (points for remote handle if desired)
Misc. screws, nuts, hook-up wire, and solder	

might get with the expensive bridge-circuit type commercial meters) when your only problem is to test a surface to be painted. Tests with this meter have shown that readings over about 10% moisture present an unfavorable condition for painting.

Building the Tester.

Cut a piece of 1/8 in. thick black Bakelite to fit neatly in the recess in the open top side of the meter case. Or you could, instead, use 1/8 in. Masonite hardboard for this panel, if you finish it with black lacquer or enamel (using several rubbed coats for a good smooth black surface) to resemble Bakelite. Rub the final coat lightly with fine steel wool for a satin finish.

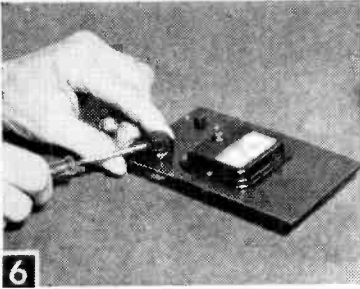You'll need a 2 3/16 in. diameter hole in the front panel (Fig. 7A) for the meter. If your front panel is cut down from a larger piece, you'll find it easier to cut this hole first in the



6


Parts fitted to front panel.

larger piece, using a circle or fly cutter in the drill press. Also cut the $\frac{3}{8}$ in. diameter hole for the potentiometer. To make the rectangular hole for the slide switch, first lay it out on the panel with a scribe, drill several small holes within the area, and dress opening to size with a small file.


Note drilled holes for two small machine screws which hold switch in place (Fig. 7A), and the corner holes for screws that hold panel to case. Match these carefully to holes in case before drilling. To adapt case holes for 4-40 screws, drill $\frac{1}{4}$ in. down in bottom of existing case holes with #43 and then tap them 4-40. Use $\frac{1}{2}$ in. long 4-40 binder or button-head plated screws in these corner holes. When all openings have been made, mount meter, switch and potentiometer on front panel (Fig. 6).

Make the two pointed steel electrodes from drill rod, about .108-109 in. diameter, which is threaded at one end for 4-40 and (after shaping to points at the other ends) hardened (Fig. 7B). If you can, have these points copper- (or cadmium-) plated in some plating shop to provide good contact and freedom from corrosion.

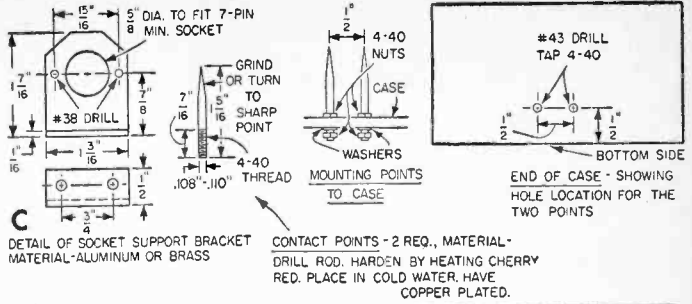
The parts to be fitted in the bottom of the case (Figs. 4, 5 and 8) are three battery holders, an angle bracket support for the tube socket and a 1-terminal terminal strip. Secure these parts with fh 4-40 screws and nuts, with the heads countersunk flush at the other side. Bend up the socket



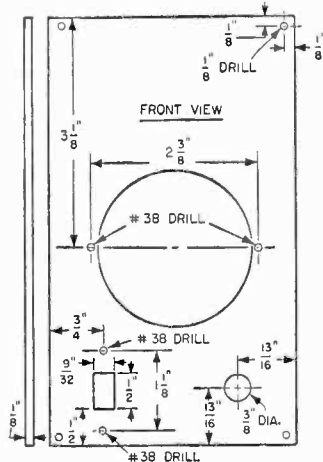
C DETAIL OF SOCKET SUPPORT BRACKET MATERIAL-ALUMINUM OR BRASS CONTACT POINTS - 2 REQ., MATERIAL - DRILL ROD. HARDEN BY HEATING CHERRY RED. PLACE IN COLD WATER. HAVE COPPER PLATED.



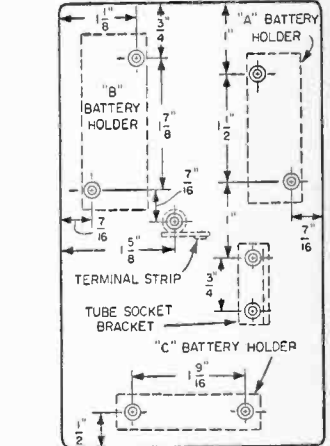
7A FRONT PANEL DRILLING - MATERIAL BAKELITE OR MASONITE, BLACK



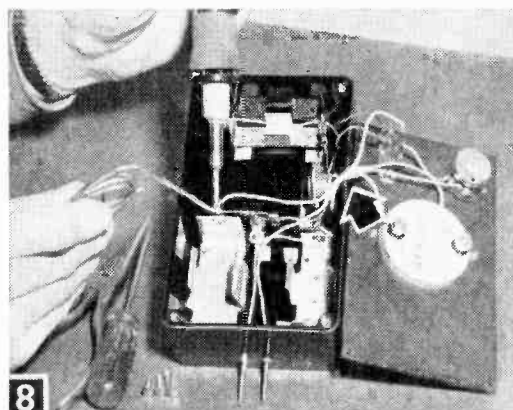
B BOTTOM VIEW OF CASE - HOLE LOCATIONS USE #33 DRILL, C SINK FOR 4-40 FH SCREWS CHECK HOLE LOCATIONS IN BAT. HOLDERS BEFORE DRILLING. THEY MAY DIFFER FROM ABOVE



8

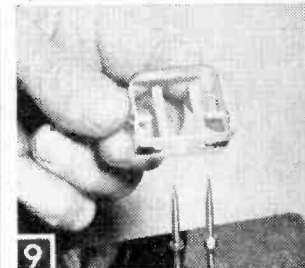

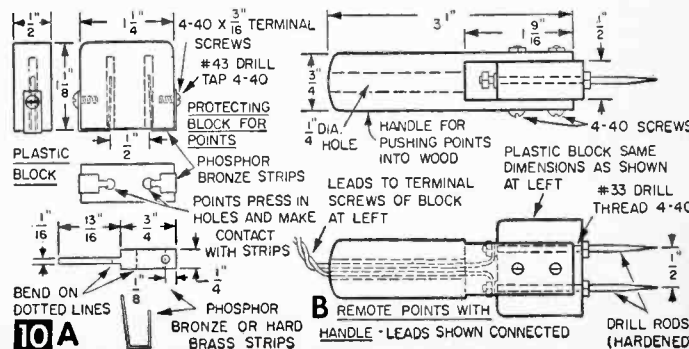Above, plastic block protects sharp points of electrodes. Left, making final solder joint on case wiring. Note tape (arrow) used to group wires for easy handling.



10A REMOTE POINTS WITH HANDLE - LEADS SHOWN CONNECTED DRILL RODS (HARDENED)

bracket (Fig. 7C) from aluminum or other soft stock about .062 in. thick with a 5/8 in. hole for the socket body and two #44 holes for the 2-56 screws and nuts which attach socket to the bracket. Drill two #33 holes in the bracket base for securing it to the case.

The wiring (Figs. 3 and 4) is done with #24-26 plastic covered hook-up wire. Solder all joints, except those at the steel points and the meter terminals, where clamping nuts are used. Make wiring to panel long enough so panel can be laid open as in Fig. 8, for working on the connections.


Note in Fig. 4 that, on the back connections of the double-pole single-throw slide switch, one side is used to open the B-battery circuit and

the other side opens the filament circuit. The *Shurite* meter is well adapted for this layout, as its shallow body assures clearance with the fixed parts, if you locate these parts exactly as shown.


To protect the pointed steel electrodes, make up a plastic block as shown in Figs. 9 and 10A. This block can serve a dual purpose by fitting thin strips of phosphor bronze or hard brass in the holes, with their ends terminating in screws at the sides. You can then employ a remote set of points in a Bakelite handle (shown in Fig. 10B) with leads connecting from the terminal screws on the first block to the points in the second block as shown. With the aid of this extension, you can test probe in hard-to-reach areas.

Make a VHF ANTENNA

By THOMAS J. HIDLEY

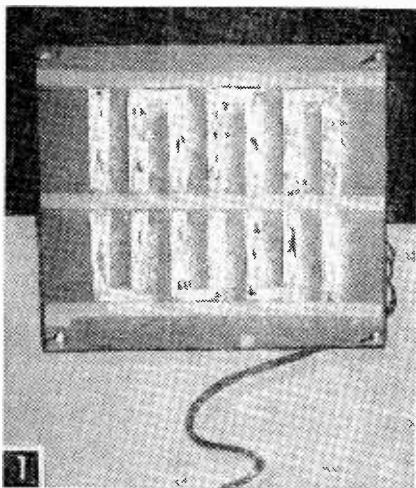

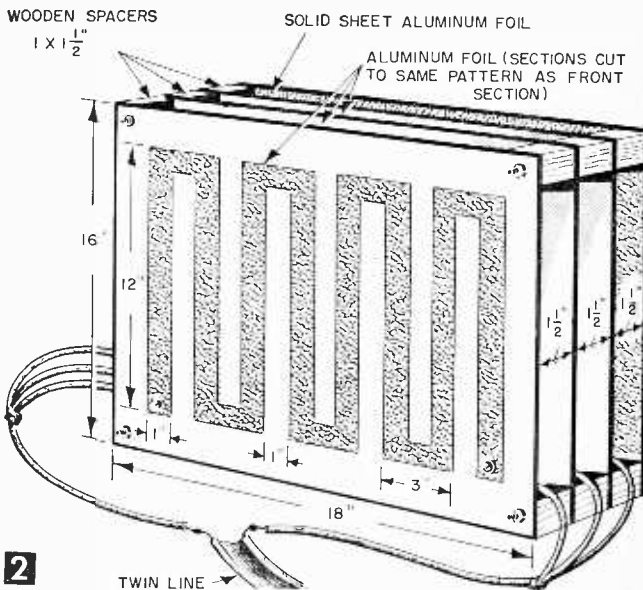Stacked in parallel, this six-bay, home-made TV antenna reaches out and drags stations in. More bays can be added if desired; this will increase signal strength.



2

FAR superior to the antenna now wired into your television set, this paralleled-stacked antenna can be constructed quickly and inexpensively

(see Materials List and Fig. 2). Begin by cutting out and cementing or taping the first three sections of aluminum foil to corrugated cardboard. Each of the three sections has aluminum foil on both sides, a total of six pieces of aluminum foil cut to the front-view pattern of Fig. 2. Cut two pieces at a time, using a safety razor blade. (Scissors will seal the edges of the foil).

At the ending and the beginning of each section, use 5/32-in. brass terminals. Connect one 6-in. length wire to one terminal, another wire to the terminal on the other end on all sections.

The last section is a solid piece of aluminum

foil, no connections, which stops interference from the opposite direction.

With all four sections completed, assemble, using 1 x 1 1/2-in. wood spacers, drilled out with a 1 3/4-in. drill. Bolt together with 6-in. bolts. Solder three wires and one end of the twin line together as shown in Fig. 2. Do this at both ends of the assembly.

The length of the aluminum foil totals 100-in. per side for a total of 200 in. per section. The grand total is 600 in. If 100 in. of foil per section side is too long for your locality, shorten each section.


MATERIALS LIST—VHF TV ANTENNA

No. Req'd.	Description	No. Req'd.	Description
4 pcs	corrugated cardboard 16 x 18"		terminals), 12 brass washers
1	roll aluminum foil 18" wide	1	roll masking tape
4	3/16 x 6" bolts, 8 washers	6 pcs	#16 insulated wire, 6" long
6	5/32 x 3/4" brass bolts (used as	5 ft	twin line


Miniature Tube Guide

The following chart contains electronic, physical and circuit application data on all miniature electronic tubes in general use. The numbers under the heading "Base Connections" refer to the base diagrams below the chart


Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Over-all Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
OA2	Gaseous v regulator	OD3/VR150	Cold	—	—	11	25 $\frac{1}{8}$	Voltage regulator	185 min.	150v
OB2	Gaseous v regulator	OC3/VR105	Cold	—	—	11	25 $\frac{1}{8}$	Voltage regulator	133 min.	108v
OG3	Gaseous v regulator	—	Cold	—	—	11	21 $\frac{1}{8}$	Voltage regulator	125 max.	85v
1A3	Vhf diode	—	Cath.	1.4	.15	7	21 $\frac{1}{8}$	H-w rect. or det.	117	—
1AB6	Pentagrid converter	—	Fil.	1.4	.025	57	25 $\frac{1}{16}$	Converter	67.5	67.5
1AC6	Pentagrid converter	—	Fil.	1.4	.050	57	21 $\frac{1}{8}$	Converter	67.5	67.5
1AE4	Pentode, sharp cutoff	—	Fil.	1.25	.1	21	21 $\frac{1}{8}$	Voltage amplifier	90	90
1AF4	R-f pentode	—	Fil.	1.4	.025	21	21 $\frac{1}{8}$	Voltage amplifier	90	90
1AF5	Diode-pentode	—	Fil.	1.4	.025	22	21 $\frac{1}{8}$	Voltage amplifier	90	90
1AH5	Diode, a-f pentode	—	Fil.	1.4	.025	22	25 $\frac{1}{16}$	Voltage amplifier	64	—
1A4	R-f pentode	—	Fil.	1.4	.25	21	25 $\frac{1}{16}$	Voltage amplifier	85	Rs-39
1AX2	H-w rectifier	1X2A	Fil.	1.4	.65	126	21 $\frac{1}{16}$	High-voltage rectifier	25K	—
1C3	Triode	1LE3	Fil.	1.45	.05	19	21 $\frac{1}{8}$	Voltage amplifier	90	—
1E3	Uhf triode	—	Fil.	1.25	.22	87	25 $\frac{1}{16}$	Oscillator, volt. amp	150	—
1L4	R-f pentode, sharp cutoff	1N5GT	Fil.	1.4	.05	21	21 $\frac{1}{8}$	Voltage amplifier	90	90
1L6	Pentagrid converter	1LA6	Fil.	1.4	.050	55	21 $\frac{1}{8}$	Voltage amplifier	90	67.5
1R5	Pentagrid converter	1A7GT	Fil.	1.4	.05	31	21 $\frac{1}{8}$	Converter	90	45
1S4	Power amp pentode	1Q5GT	Fil.	1.4	.1	32	21 $\frac{1}{8}$	Converter	90	67.5
1S5	Diode, a-f pentode	—	Fil.	1.4	.05	22	21 $\frac{1}{8}$	Power output amp	45	45
1T4	R-f pentode, remote cutoff	1P5GT	Fil.	1.4	.05	21	21 $\frac{1}{8}$	Power output amp	67.5	67.5
1U4	R-f pentode, sharp cutoff	1N5GT	Fil.	1.4	.05	21	21 $\frac{1}{8}$	Detector and volt. amp	67.5	67.5
1U5	Diode, a-f pentode	—	Fil.	1.4	.05	26	21 $\frac{1}{8}$	Voltage amplifier	45	45
1U6	Pentagrid converter	—	Fil.	1.4	.025	55	21 $\frac{1}{8}$	Voltage amplifier	67.5	67.5
1V2	H-w diode	—	Fil.	0.625	.3	123	25 $\frac{1}{16}$	Detector and volt. amp	90	45
1W4	Power amp pentode	1LB4	Fil.	1.4	.05	15	21 $\frac{1}{8}$	Rectifier	62.5	62.5
1X2	H-w rectifier	1B3GT/8016	Fil.	1.25	.22	126	21 $\frac{1}{16}$	Power amplifier	90	90
1X2A	H-w rectifier	1B3GT	Fil.	1.25	.22	126	21 $\frac{1}{16}$	Flyback voltage rectifier	15K	—
1X2B	H-w rectifier	—	Fil.	1.25	.2	126	21 $\frac{1}{16}$	Rectifier	20K	—
1Z2	H-w rectifier	—	Fil.	1.5	.4	46	21 $\frac{1}{16}$	Flyback voltage rectifier	22K	—
2AF4	Uhf triode	6AF4	Cath.	2.35	.600	59	21 $\frac{1}{8}$	Rectifier	7800	—
2B25	H-w rectifier	—	Fil.	1.4	.11	3	21 $\frac{1}{16}$	950 mc. osc.	100	—
2C4	Triode thyatron	—	Cath.	2.5	.6	8	21 $\frac{1}{16}$	Voltage amplifier	80	—
2C51	Twin triode	7F8	Cath.	6.3	.3	63	19 $\frac{1}{4}$	Rectifier	1000	—
								Rectifier	350	—
								Voltage amplifier	150	—

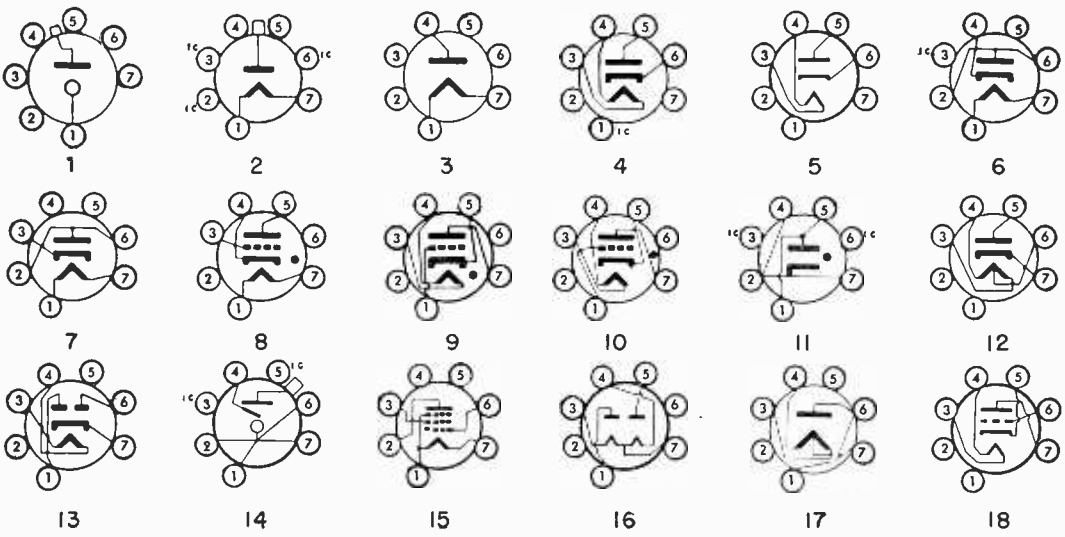


Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Overall Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
2D21	Tetrode thyratron	2050	Cath.	6.3	.6	40	2 1/8	Relay service	1300	—
2E30	Beam pentode	—	Fil.	6.0	.65	50	2 5/8	Power amplifier	250	250
2T4	Low-mu triode	6T4	Cath.	2.35	.600	59	1 3/4	Oscillator, volt. amp.	80	—
3A2	H-w rectifier	—	Cath.	3.15	.22	111	2 13/16	High-voltage rectifier	18K	—
3A4	Power amp pentode	—	Fil.	2.8	.1	34	2 1/8	Power output amp	135	90
				1.4	.2			Power output amp	150	90
3A5	Twin triode	—	Fil.	2.8	.11	35	2 1/8	Voltage amplifier	90	—
				1.4	.22					
3AL5	Twin diode	6AL5	Cath.	3.15	.600	25	1 13/16	F-m discriminator	—	—
								Rectifier	150	—
3AU6	R-f pentode, sharp cutoff	6AU6	Cath.	3.15	.600	39	2 1/8	Voltage amplifier	100	100
								Voltage amplifier	250	150
3AV6	Duplex diode, high-mu triode	6AV6	Cath.	3.15	.600	43	2 1/8	Detector and volt. amp	100	—
								Detector and volt. amp	250	—
3B4	Vhf beam pentode	—	Fil.	2.50	.165	53	2 1/8	Power amplifier	—	—
			Tap	1.25	.330			Power amplifier	150	135
3BC5	R-f pentode	6BC5	Cath.	3.15	.600	36	2 1/8	Voltage amplifier	100	100
								Voltage amplifier	250	150
3BE6	Pentagrid converter, remote cutoff	6BE6	Cath.	3.15	.600	48	2 1/8	Converter	100	100
								Converter	250	100
3BN6	Gated-beam disc.	6BN6	Cath.	3.15	.600	56	2 5/8	F-m discriminator	80	60
3BY6	Pentagrid amplifier	6BY6	Cath.	3.15	.600	48	2 1/8	Syn. separator and clipper	10	25
								Voltage amplifier	200	150
3BZ5	High-gm, semi-remote cutoff, pentode amplifier	6BZ5	Cath.	3.15	.600	49	2 1/8			
3C4	Power output pentode	—	Fil.	1.4	.05	27	2 3/16	Power amplifier	64	64
								Power amplifier	85	85
3CB6	R-f pentode, remote cutoff	6CB6	Cath.	3.15	.600	49	2 1/8	Voltage amplifier	200	150
			Fil.	1.4	.05	27	2 3/8	Power output amp	67.5	67.5
3E5	Power amp pentode	—	Fil.	2.8	.025			Power output amp	90	90
				1.4	.1			Power output amp	90	90
3Q4	Power amp pentode	3Q5GT	Fil.	2.8	.05	33	2 1/8	Power output amp	90	90
				1.4	.1			Power output amp	90	90
3S4	Power amp pentode	3Q5GT	Fil.	1.4	.1	33	2 1/8	Power output amp	90	67.5
				2.8	.05			Power output amp	90	67.5
								Power output amp	67.5	67.5
								Power output amp	90	90
3V4	Power amp pentode	3Q5GT	Fil.	2.8	.05	27	2 1/8	Power output amp	67.5	67.5
				1.4	.1			Power output amp	90	90
4BQ7A	Double triode	6BQ7A	Cath.	4.2	.600	74	2 5/16	Voltage amplifier	150	—
4BZ7	Vhf twin triode	6BZ7	Cath.	4.2	.600	74	2 5/16	Voltage amplifier	150	—
5A6	Beam pentode	—	Fil.	5.0	.23	116	2 5/8	R-f power amp and frequency multiplier	—	—
5AM8	Diode-pentode	6AM8	Cath.	4.7	.600	107	3 1/16	1-f amplifier	200	150
5AQ5	Beam pentode	6AQ5	Cath.	4.70	.600	44	2 5/8	Power output amplifier	180	180
								Power output amplifier	250	250
5BK7A	Twin triode	6BK7A	Cath.	4.7	.600	74	2 5/16	Voltage amplifier	150	—
5J6	Twin triode	6J6	Cath.	4.7	.600	37	2 1/8	Voltage amplifier	100	—
5T8	Triple diode, triode	6T8	Cath.	4.7	.600	112	2 5/16	Det. and Volt. amplifier	100	—
								Det. and Volt. amplifier	250	—
5U8	Triode-pentode	6U8	Cath.	4.7	.600	71	2 5/16	Pentode volt. amp	250	110
								Triode volt. amp	150	—
5X8	Triode-pentode	6X8	Cath.	4.7	.600	75	2 5/16	Converter:	—	—
								Triode oscillator	150	—
								Pentode mixer	150	150
6AB4	Uhf triode	—	Cath.	6.3	.15	18	2 1/8	Voltage amplifier	250	—

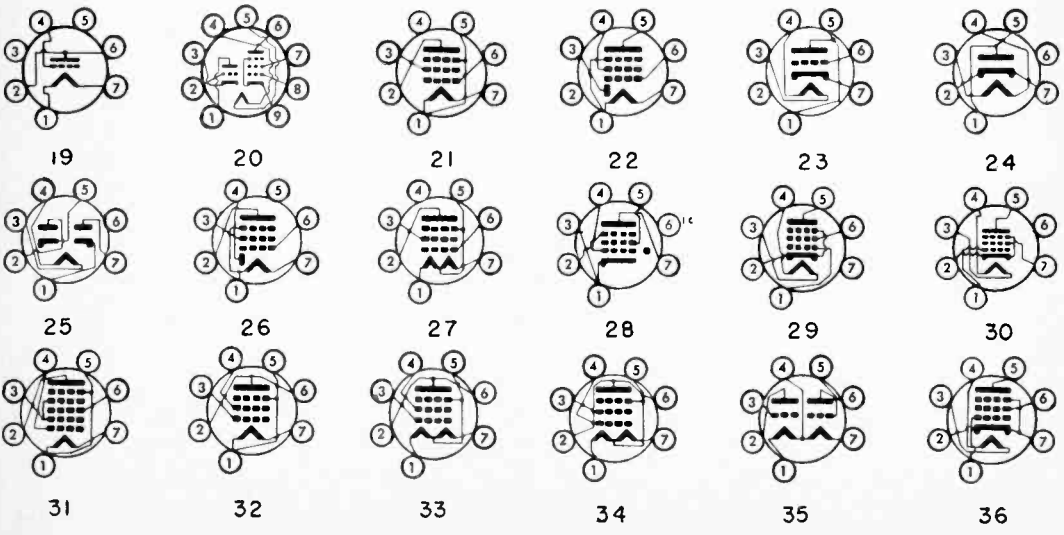

Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Over-all Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
6AB8	Triode-pentode	—	Cath.	6.3	.3	80	2 3/8"	Triode: A-f pre-amplifier and osc. Pentode: Synch. sep. or output amp	100	—
6AD8	Double diode, pentode	—	Cath.	6.3	.3	122	2 3/8"	Voltage amplifier	200	200
6AE8	Triode, hexode	—	Cath.	6.3	.3	65	2 1/4"	Frequency converter	250	85
6AF4	Uhf triode	—	Cath.	6.3	.225	59	2 1/8"	950 mc. osc. Voltage amplifier	100	—
6AF4A	Medium-mu triode	6AF4	Cath.	6.3	.225	59	1 3/4"	950 mc. osc.	100	—
6AG5	R-f pentode, sharp cutoff	6SH7GT	Cath.	6.3	.3	36	2 1/8"	Voltage amplifier	100	100
6AH6	R-f pentode, sharp cutoff	6AC7	Cath.	6.3	.45	39	2 1/8"	Voltage amplifier	250	150
6AJ4	Uhf triode	—	Cath.	6.3	.225	97	1 3/4"	Voltage amplifier Triode volt. amp. Grounded-grid amp (900 mc.)	300	150
6AJ5	R-f pentode, sharp cutoff	—	Cath.	6.3	.175	36	1 3/4"	Power output amp	150	150
6AJ8	Triode-heptode	—	Cath.	6.3	.3	100	2 5/8"	Class AB power amp Heptode mixer Triode volt. amp	28	28
6AK5	R-f pentode, sharp cutoff	—	Cath.	6.3	.175	36	1 3/4"	Power output amp	180	75
6AK6	Power amp pentode	—	Cath.	6.3	.15	39	2 1/8"	Power output amp	250	R-22K
6AK8	Triple diode, triode	—	Cath.	6.3	.45	112	2 3/8"	Detector and volt. amp	100	—
6AL5	Twin diode	6H6GT	Cath.	6.3	.3	25	1 13/16"	Detector and volt. amp F-m discriminator Rectifier	250	—
6AM4	High-mu uhf triode	—	Cath.	6.3	.225	97	1 3/4"	Grounded-grid mixer	150	—
6AM5	Power amp pentode	—	Cath.	6.3	.2	30	2 1/8"	Power output amp	150	250
6AM6	R-f pentode	—	Cath.	6.3	.3	54	2 1/8"	Voltage amplifier	250	250
6AM8	Diode-pentode	—	Cath.	6.3	.45	107	2 5/16"	1-f amplifier	200	150
6AN4	High-mu uhf triode	—	Cath.	6.3	.225	59	2 1/8"	Grounded-grid mixer	200	—
6AN5	Power amp pentode	6AG7	Cath.	6.3	.5	36	2 1/8"	Power amplifier	120	120
6AN6	Quadruple diode	—	Cath.	6.3	.2	38	2 1/8"	Rectifier	117	—
6AN7	Triode, hexode, converter	—	Cath.	6.3	.23	119	2 5/8"	Converter	250	85
6AN8	Medium-mu triode, sharp-cutoff pentode	—	Cath.	6.3	.45	20	2 5/16"	Triode voltage amplifier Pentode voltage amp	300	150
6AQ4	Triode	—	Cath.	6.3	.3	60	2 1/8"	Grounded-grid amplifier	250	—
6AQ5	Beam pentode	6V6GT	Cath.	6.3	.45	44	2 5/8"	Power output amp Power output amp	180	180
6AQ6	Duplex diode, high-mu triode	6T7G	Cath.	6.3	.15	43	2 1/8"	Detector and volt. amp	250	250
6AR5	Power amp pentode	6K6GT	Cath.	6.3	.4	29	2 3/8"	Power amplifier Power amplifier	180	180
6AS5	Beam pentode	7A5	Cath.	6.3	.800	52	2 3/8"	Power amplifier	250	250
6AS6	R-f pentode, dual control, sharp c.o.	—	Cath.	6.3	.175	49	1 3/4"	Power amplifier Voltage amplifier	150	117
6AS8	Diode, sharp-cutoff pentode	—	Cath.	6.3	.45	110	2 3/8"	Video amplifier	120	120
6AT6	Duplex diode, high-mu triode	6Q7GT	Cath.	6.3	.3	43	2 1/8"	Detector and volt. amp Detector and volt. amp	100	—
6AT8	Medium-mu triode, sharp-cutoff pentode	6X8	Cath.	6.3	.45	110	2 5/16"	Converter: Triode oscillator Pentode mixer	250	—
6AU6	R-f pentode, sharp cutoff	6SH7GT	Cath.	6.3	.3	39	2 1/8"	Converter: Triode oscillator Pentode mixer Voltage amplifier Voltage amplifier	150	150
									100	100
									250	150

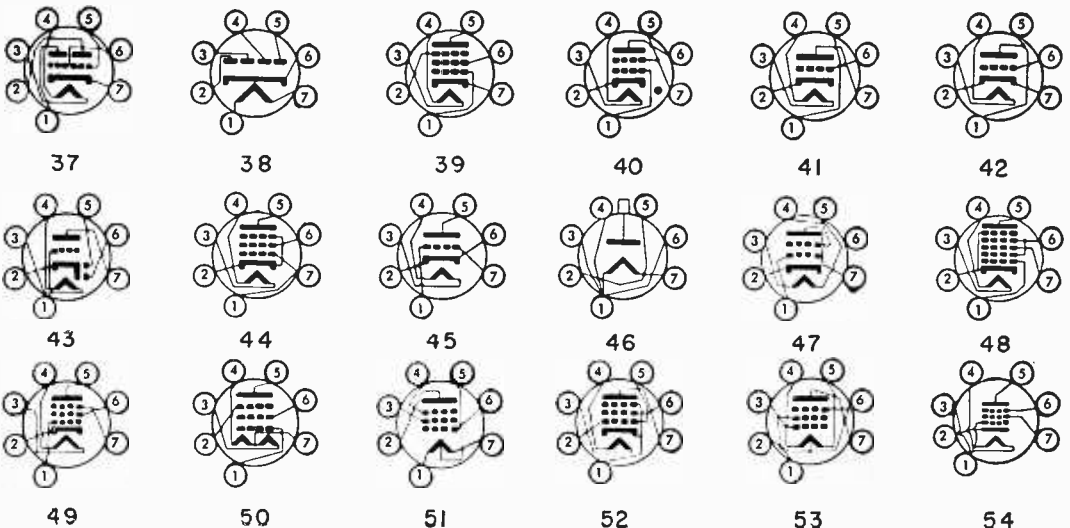


Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Overall Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
6AV4	Double diode	6X4	Cath.	6.3	.95	13	2 $\frac{5}{8}$ "	F-w rectifier	1250	—
6AV6	Duplex diode, high-mu triode	6SQ7GT	Cath.	6.3	.3	43	2 $\frac{1}{8}$ "	Detector and volt. amp	100	—
6AX7	Twin triode	12AX7	Cath.	6.3/3.15	3/0.6	66	2 $\frac{1}{16}$ "	Detector and volt. amp	250	—
6BA6	R-f pentode, remote cutoff	6SG7GT	Cath.	6.3	.3	39	2 $\frac{1}{8}$ "	Voltage amplifier	100	—
6BA7	Pentagrid converter	6SB7Y	Cath.	6.3	.300	64	2 $\frac{5}{8}$ "	Voltage amplifier	250	100
6BC4	Uhf medium-mu triode	—	Cath.	6.3	.225	109	1 $\frac{1}{4}$ "	Voltage amplifier	100	100
6BC5	R-f pentode	—	Cath.	6.3	.3	36	2 $\frac{1}{8}$ "	Voltage amplifier	250	150
6BC7	Triple diode	—	Cath.	6.3	.45	81	—	Rectifier	5	—
6BD6	R-f pentode, remote cutoff	6SK7GT	Cath.	6.3	.3	39	2 $\frac{1}{8}$ "	Voltage amplifier	100	100
6BD7	Double-diode, triode	—	Cath.	6.3	.23	127	2 $\frac{5}{8}$ "	Voltage amplifier	250	100
6BE6	Pentagrid, converter, remote C.O.	6SA7GT	Cath.	6.3	.3	48	2 $\frac{1}{8}$ "	Converter	100	100
6BE7	Heptode converter	—	Cath.	6.3	.2	67	2 $\frac{3}{8}$ "	Converter	250	100
6BF5	Pentode	—	Cath.	6.3	.2	44	2 $\frac{5}{8}$ "	Conv. f-m det., a-m amp/	250	100
6BF6	Duplex diode medium-mu triode	6SR7GT	Cath.	6.3	.3	43	2 $\frac{5}{8}$ "	Power amplifier	225	225
6BH5	Pentode, remote c.o. variable mu	—	Cath.	6.3	.2	82	2 $\frac{5}{8}$ "	Voltage amplifier	250	R-90M
6BH6	R-f pentode sharp c.o.	—	Cath.	6.3	.150	49	2 $\frac{1}{8}$ "	Voltage amplifier	100	100
6BJ5	Pentode	—	Cath.	6.3	.64	30	2 $\frac{3}{4}$ "	Voltage amplifier	250	150
6BJ6	R-f pentode remote cutoff	6SS7GT	Cath.	6.3	.15	49	2 $\frac{1}{8}$ "	Power amplifier	250	250
6BJ7	Triple diode	—	Cath.	6.3	.45	81	2 $\frac{1}{16}$ "	Voltage amplifier	100	100
6BK5	Beam pentode	—	Cath.	6.3	.2	93	2 $\frac{5}{8}$ "	Voltage amplifier	250	250
6BK6	Duplex diode high-mu triode	—	Cath.	6.3	.3	43	2 $\frac{5}{8}$ "	Voltage amplifier	100	—
6BK7	Twin triode	12AV7	Cath.	6.3	.45	74	2 $\frac{1}{16}$ "	Cascode amplifier	100	—
6BK7A	Twin triode	6BK7	Cath.	6.3	.45	74	2 $\frac{1}{16}$ "	Cascode amplifier	150	—
6BM5	Power amp pentode	—	Cath.	6.3	.45	44	2 $\frac{5}{8}$ "	Voltage amplifier	150	—
6BN6	Gated-beam disc.	—	Cath.	6.3	.3	56	2 $\frac{5}{8}$ "	Power amplifier	250	250
6BN7	Double triode	—	Cath.	6.3	.75	74	2 $\frac{5}{8}$ "	F-m discriminator	80	60
6BQ7	Double triode	—	Cath.	6.3	.4	74	2 $\frac{3}{16}$ "	Voltage amplifier	Sec. 1 250	—
6BQ7A	Double triode	—	Cath.	6.3	.4	74	2 $\frac{3}{16}$ "	Voltage amplifier	Sec. 2 120	—
6BR7	H-f pentode, sharp. c.o.	6J7	Cath.	6.3	.15	84	2 $\frac{1}{16}$ "	Voltage amplifier	100	100
6BS5	Beam power amplifier	—	Cath.	6.3	.75	89	2 $\frac{5}{8}$ "	Voltage amplifier	250	100
6BS7	Sharp-cutoff h-f pentode	6BR7	Cath.	6.3	.150	84	2 $\frac{1}{32}$ "	A-f power amplifier	100	100
6BT6	Duplex diode hi-mu triode	—	Cath.	6.3	.3	43	2 $\frac{5}{8}$ "	Voltage amplifier	250	100
6BU6	Duplex diode low-mu triode	—	Cath.	6.3	.3	43	2 $\frac{5}{8}$ "	Voltage amplifier	100	—
6BV7	Double diode, pentode	—	Cath.	6.3	.8	94	2 $\frac{5}{8}$ "	Voltage amplifier	250	—
6BW6	Beam pentode	—	Cath.	6.3	.45	76	2 $\frac{5}{8}$ "	Power amplifier	180	180
								Power amplifier	250	250
								Power amplifier	180	180
								Power amplifier	250	225
								Power amplifier	315	225

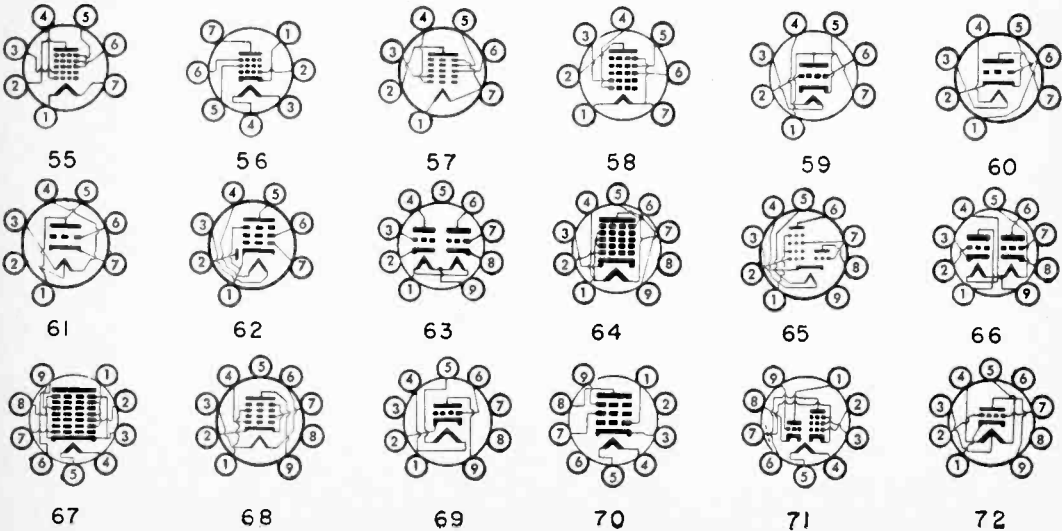


Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Over-all Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
6BW7	R-f pentode	---	Cath.	6.3	.150	77	2 1/8"	Voltage amplifier Voltage amplifier	180 250	180 250
6BX4	F-w rectifier	---	Cath.	6.3	.6	13	2 3/8"	Rectifier	1350	---
6BX6	R-f pentode	---	Cath.	6.3	.3	77	2 5/8"	Voltage amplifier	170	170
6BY6	Pentagrid amplifier	---	Cath.	6.3	.3	48	2 1/8"	Sync. Separator clipper	10	25
6BY7	R-f pentode	---	Cath.	6.3	.3	77	2 5/8"	Wide-hand amplifier	250	100
6BZ6	High-gm, semi-remote cutoff, pentode amplifier	---	Cath.	6.3	.3C	49	2 1/8"	Voltage amplifier	200	150
6BZ7	Vhf twin triode	6BQ7	Cath.	6.3	.4	74	2 3/8"	Voltage amplifier	150	---
6C4	Power triode	6J5GT	Cath.	6.3	.15	23	2 1/8"	Voltage amplifier Voltage amplifier	100 250	---
6CB6	R-f pentode sharp cutoff	---	Cath.	6.3	.3	49	2 1/8"	Voltage amplifier	200	150
6CF6	Sharp-cutoff pentode	---	Cath.	6.3	.3	49	2 1/8"	Voltage amplifier	200	150
6CG6	Pentode, remote c.o.	---	Cath.	6.3	.3	39	2 1/8"	Voltage amplifier	250	150
6CH6	R-f pentode	---	Cath.	6.3	.75	83	2 5/8"	Video output amplifier	250	250
6CJ6	Pentode	---	Cath.	6.3	.05	79	3 1/8"	Audio output amplifier Horizontal sweep amp.	250 70	250 170
6CK6	R-f pentode	---	Cath.	6.3	.71	78	3 1/8"	Video output amplifier	250	250
6CL6	R-f pentode	---	Cath.	6.3	.65	95	2 5/8"	Power amplifier	250	150
6CM6	Beam pentode	---	Cath.	6.3	.45	104	2 5/8"	Vert. deflection amp.	250	250
6CQ6	Variable-mu h-f pentode	---	Cath.	6.3	.2	54	2 1/8"	Voltage amplifier Voltage amplifier	250 250	100 250
6CR6	Diode-pentode	---	Cath.	6.3	.3	62	2 1/8"	Audio amplifier	250	100
6CS6	Dual control heptode	---	Cath.	6.3	.3	48	2 1/8"	Sync. separator	10	30
6D4	Triode thyatron	---	Cath.	6.3	.25	10	2 1/8"	---	320	---
6DB6	Sharp cutoff r-f pentode	---	Cath.	6.3	.3	49	2 1/8"	Color demodulator	150	150
6DC6	Semi-remote c.o. pentode	---	Cath.	6.3	.3	49	2 1/8"	Voltage amplifier	200	150
6DE6	Sharp-cutoff pentode	---	Cath.	6.3	.3	49	2 1/8"	Voltage amplifier	200	150
6J4	Triode, uhf grounded grid	---	Cath.	6.3	.4	41	2 1/8"	Voltage amplifier Voltage amplifier	100 150	---
6J6	Twin triode	---	Cath.	6.3	.45	37	2 1/8"	Voltage amplifier	100	---
6M5	Power amp pentode	---	Cath.	6.3	.71	118	3 1/8"	Power output amp	250	250
6N4	Triode uhf	---	Cath.	6.3	.2	45	1 3/4"	Voltage amplifier	180	---
6N8	Duplex diode, pentode	---	Cath.	6.3	.3	122	2 5/8"	Voltage amplifier	250	85
6Q4	Grounded grid triode	---	Cath.	6.3	.48	121	2 5/8"	Voltage amplifier	250	---
6R4	Uhf triode	---	Cath.	6.3	.2	120	2 5/8"	Voltage amplifier	150	---
6R8	Triple diode, triode	---	Cath.	6.3	.45	112	3 1/8"	Voltage amplifier	250	---
6S4	Triode	---	Cath.	6.3	.6	69	2 5/8"	Voltage amplifier	250	---
6S4A	Triode	6S4	Cath.	6.3	.60	69	2 5/8"	Voltage amplifier	250	---
6T4	Low-mu triode	---	Cath.	6.3	.225	59	1 3/4"	Oscillator, volt. amp	80	---
6T8	Triple diode triode	---	Cath.	6.3	.450	112	2 3/8"	Det. and voltage amp. Det. and voltage amp.	100 250	---
6U3	Diode	---	Cath.	6.3	.9	91	3 1/8"	Damper diode	4000	---
6U8	Triode-pentode	---	Cath.	6.3	.45	71	2 1/8"	Pentode volt. amp Triode volt. amp	250 150	110
6V3	H-w rectifier	---	Cath.	6.3	.75	85	2 3/8"	Rectifier Rectifier	350 350	---
6V4	F-w rectifier	---	Cath.	6.3	.6	117	3 1/8"	Damper diode	6000	---
6V8	Triple diode triode	---	Cath.	6.3	.45	73	2 1/8"	Rectifier Voltage amplifier	350 250	---
6X4	Double diode	---	Cath.	6.3	.6	13	2 5/8"	Voltage amplifier F-w rectifier	250 650	---
6X8	Triode pentode	---	Cath.	6.3	.45	75	2 1/8"	F-w rectifier Converter: triode oscillator Pentode mixer	900 150 150	Cap. Choke ---




73

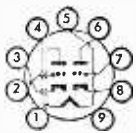

74

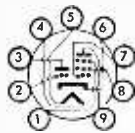

75

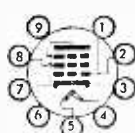


76



77




78

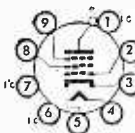

79



80

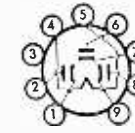

81




82




83




84

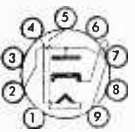

85

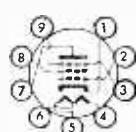

86

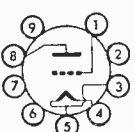

87



88




89




90


Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Over-all Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
9BM5 9BW6	Power amp pentode Beam pentode	6BW6	Cath. Cath.	9.5 9.45	.3 .3	44 76	2 5/8 2 5/8	Power amplifier Power amplifier Power amplifier Power amplifier Voltage amplifier	250 180 250 315 250	250 180 250 225 —
12A4	Medium-mu triode	—	Cath.	12.6 6.3	.3	72	2 5/8	—	—	—
12AH8	Triode-heptode	—	Cath.	12.6 6.3	.15 .3	92	2 5/8	Converter: Heptode Oscillator	250 100	100
12AL5	Twin diode	12H6GT	Cath.	12.6	.15	25	1 1/2	F-m discriminator Rectifier	117	—
12AQ5	Beam power amplifier	12V6GT	Cath.	12.6	.225	44	2 5/8	A-f power amplifier Class A-1 A-f power amplifier Class A-1	180 250	180 250
12AT6	Duplex diode high-mu triode	12Q7GT	Cath.	12.6	.15	43	2 1/8	Detector and volt amp Detector and volt amp	100 250	—
12AT7	Twin triode	—	Cath.	12.6 6.3	.150 .300	66	2 3/8	Voltage amplifier Voltage amplifier	100 250	—
12AU6	R-f pentode sharp cutoff	12SH7GT	Cath.	12.6	.15	39	2 1/8	Voltage amplifier Voltage amplifier	100 250	100 150
12AU7	Twin triode	12SN7GT	Cath.	12.6 6.3	.15 .3	66	2 3/8	Voltage amplifier Voltage amplifier	100 250	—
12AV6	Twin diode high-mu triode	12SQ7GT	Cath.	12.6	.150	43	2 1/8	Detector and volt. amp Detector and volt. amp	100 250	—
12AV7	Double triode	—	Cath.	12.6 6.3	.225 .45	66	2 3/8	Voltage amplifier Voltage amplifier	100 150	—
12AW6	R-f pentode sharp cutoff	—	Cath.	12.6	.15	49	2 1/8	Voltage amplifier Voltage amplifier	100 250	100 150
12AX7	Twin triode	12SL7GT	Cath.	12.6 6.3	.150 .300	66	2 3/8	Voltage amplifier Voltage amplifier	100 250	—
12AY7	Double triode	—	Cath.	12.6 6.3	.150 .30	66	2 3/8	Voltage amplifier	250	—
12AZ7	Double triode	—	Cath.	12.6 6.3	.225 .45	66	2 3/8	Voltage amplifier Voltage amplifier	100 250	—
12B4	Low-mu triode	—	Cath.	12.6 6.3	.3 .6	72	2 5/8	Voltage amplifier Vertical sweep amp	150 250	—
12B4A	Low-mu triode	12B4	Cath.	12.6 6.3	.3 .6	72	2 5/8	Voltage amplifier Vertical sweep arm	150 250	—
12BA6	R-f pentode remote cutoff	12SG7GT	Cath.	12.6 6.3	.15 .6	39	2 1/8	Voltage amplifier Voltage amplifier	100 250	100
12BD6	R-f pentode remote cutoff	12SK7GT	Cath.	12.6	.15	39	2 1/8	Voltage amplifier Voltage amplifier	100 250	100
12BE6	Pentagrid converter remote c.o.	12SA7GT	Cath.	12.6	.15	48	2 1/8	Voltage amplifier Converter	250 100	100
12BF6	Duplex diode low-mu triode	12SR7GT	Cath.	12.6	.15	43	2 1/8	Converter Detector and volt. amp	250 250	100
12BH7	Double triode	6SN7GT	Cath.	12.6 6.3	.3 .6	66	2 5/8	Voltage amplifier Vertical sweep amp.	250 350	—
12BK5	Beam pentode	6BK5	Cath.	12.6	.600	93	2 5/8	Power amplifier	100	250
12BK6	Duplex diode high-mu triode	—	Cath.	12.6	.15	43	2 5/8	Voltage amplifier Voltage amplifier	250 250	—
12BN6	Gated-beam disc.	—	Cath.	12.6	.15	56	2 5/8	F-m discriminator	80	60
12BT6	Duplex diode high-mu triode	—	Cath.	12.6	.15	43	2 5/8	Voltage amplifier Voltage amplifier	100 250	—
12BU6	Duplex diode low-mu triode	—	Cath.	12.6	.15	43	2 5/8	Voltage amplifier Voltage amplifier	100 250	—

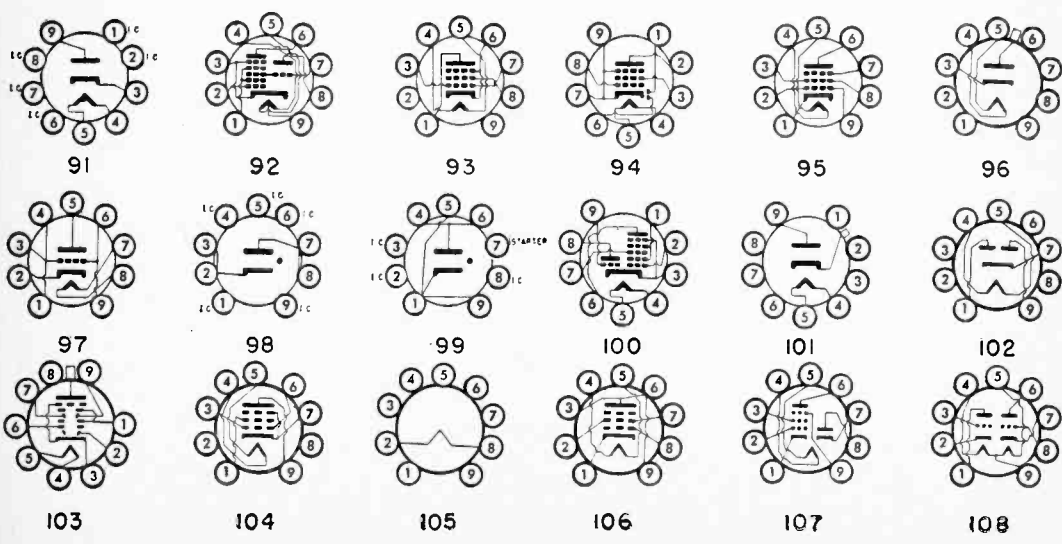

Type Designation	Description	Prototype	Cathode Heater & Filament Ratings			Base Connections	Over-all Height	Circuit Application	Typical Operating Voltages	
			Type	Volts	Amps				Plate	Screen
12BY7	R-f pentode	—	Cath.	12.6	.3	56	2 1/2	Video amplifier	250	150
12BY7A	R-f pentode	12BY7	Cath.	12.6	.3	56	2 1/2	Video amplifier	250	150
12BZ7	Twin triode	12AX7	Cath.	12.6	.3	66	2 1/2	TV sync. amplifier	250	—
12CM6	Beam Pentode	—	Cath.	12.6	.225	104	2 1/2	Power amplifier Class A1	180	180
12G4	Triode	—	Cath.	12.6	.150	23	2 1/2	Power amplifier, Class A1	315	225
12H4	Triode	—	Cath.	12.6	.150	61	2 1/2	Voltage amplifier	90	—
12X4	F-w rectifier	6X4	Cath.	12.6	.3	13	2 1/2	Voltage amplifier	250	—
15A6	R-f pentode	—	Cath.	15	.3	78	3 1/16	Voltage amplifier	90	—
16A5	R-f pentode	—	Cath.	16.5	.3	90	3 1/16	Voltage amplifier	250	—
17Z3	Diode	—	Cath.	17	.3	101	3 1/16	Rectifier	650	Cap
19AQ5	Beam pentode	—	Cath.	18.9	.15	44	2 1/2	Rectifier	900	Choke
19C8	Triple diode, triode	—	Cath.	18.9	.15	112	—	Video output amplifier	180	180
19J6	Twin triode	—	Cath.	18.9	.150	35	2 1/2	Power output amp	170	170
19T8	Triple diode	—	Cath.	18.9	.150	112	2 1/2	Power output amp	200	R-680
19V8	Triple diode, triode	—	Cath.	18.9	.15	73	2 1/2	Damper diode	4500	—
19X3	H-w rectifier	—	Cath.	19.0	.3	91	3 1/16	Power amplifier	180	180
19X8	Triode-pentode	—	Cath.	18.9	.15	75	2 1/2	Power amplifier	250	250
19Y3	H-w rectifier	—	Cath.	19.0	.3	91	3 1/16	Voltage amplifier	100	—
21A6	R-f pentode	—	Cath.	21.5	.3	79	3 1/16	Voltage amplifier	100	—
25BK5	Beam pentode	6BK5	Cath.	25	.3	93	2 1/2	Detector and volt. amp	100	—
26A6	R-f pentode	—	Cath.	26.5	.07	39	2 1/2	Detector and volt. amp	250	—
26BK6	remote cutoff Duplex diode	—	Cath.	26.5	.07	43	2 1/2	Voltage amplifier	26.5	26.5
26C6	high-mu triode	—	Cath.	26.5	.07	43	2 1/2	Voltage amplifier	250	100
26CG6	low-mu triode	—	Cath.	26.5	.07	93	2 1/2	Voltage amplifier	100	—
26D6	remote cutoff Pentode, remote c.o.	—	Cath.	26.5	.07	48	2 1/2	Voltage amplifier	250	—
26Z5W	remote cutoff Pentagrid converter, remote cutoff	—	Cath.	26.5	.07	48	2 1/2	Detector and volt. amp.	26.5	—
35B5	Twin diode	—	Cath.	26.5	.2	16	2 1/2	Detector and volt. amp.	250	150
35C5	Beam pentode	35L6GT	Cath.	35	.15	44	2 1/2	Converter	250	150
35W4	Beam pentode	35L6GT	Cath.	35.0	.150	52	2 1/2	Converter	26.5	26.5
45Z3	H-w rectifier	35Z5GT	Cath.	35	.15	12	2 1/2	Converter	250	100
50A1	H-w rectifier	—	Cath.	45	.075	6	2 1/2	H-w rectifier	325	Cap
50B5	Beam pentode	—	Cath.	50	.15	44	2 1/2	H-w rectifier	450	Choke
50C5	Beam pentode	50L6GT	Cath.	50.0	.150	52	2 1/2	Power amplifier	110	110
117Z3	H-w rectifier	117Z4GT	Cath.	117	.04	5	2 1/2	Rectifier	117	110
								Rectifier	117	—

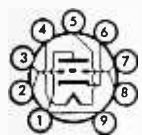

109

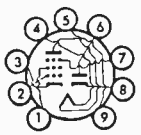


110




111



112

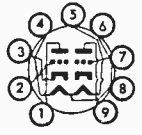

113

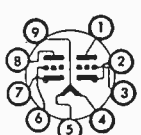

114



115



116




117




118



119

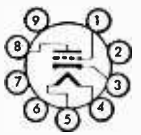


120

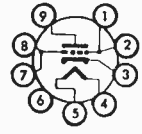


121



122

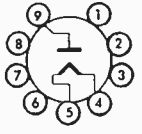


123

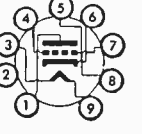

124



125

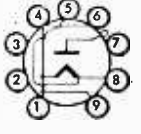

126

Getting the Most From Plastic Cases

By FORREST H. FRANTZ, SR.



Since plastic cases melt readily, you can emboss them with a heated ice pick (use letters printed on white sheet placed inside case as guide), filling the embossing with India ink or gold ink for attractive panels.

SMALL plastic cases have become very popular as enclosures for electronic devices because of their extremely low cost and the minimum amount of work required in preparing them for use. They can be obtained from a number of sources. Some hardware stores stock them, they are frequently used to package electronic parts, and quite often to box gift products. Indeed, these plastic cases have become so popular for electronic construction that one radio parts distributor (Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y.) lists them in its catalog among other electronic supplies.

The smallest case listed by Lafayette is 1 x 1 $\frac{5}{8}$ x 2 $\frac{1}{8}$ in. (MS-156; cost, 9¢). This case has a ball type hinge and the two halves are easily separated. Several other sizes with the ball type hinge are available, the largest (MS-159) being 1 x 2 $\frac{5}{8}$ x 3 $\frac{5}{8}$ in. This range of sizes will accommodate almost any transistor construction project and many simple vacuum-tube projects. A number of additional plastic cases—some with handles—are available in larger sizes for housing more complex or bulkier equipment.

These plastic cases are clear. Sometimes, however, it is desirable to have an opaque case which will have decorative beauty by virtue of its color. All right, simply paint the inside of the case. Spraying usually gives a smooth finish, a crinkled effect can be obtained by brushing on a thick coat of enamel inside the case and then, when it is partially dry, molesting the painted surface with irregular brush marks. If the brush marks are made deep enough to leave clear openings in the paint, a second coat of paint of a different color over the first produces a two-color, mottled effect.

Before you paint the case, wash it in lukewarm, soapy water, rinse, and dry it thoroughly. If you fail to do this, you may find the paint flaking off after a short time or you may find that there are very obvious finger prints between the plastic case and the paint coat.

Painting should be done before construction holes are made; so should decoration of the cabinet with aluminum foil, colored paper, plastic, leather, or cloth, if you plan that. Such decorating material can be applied inside or outside the case. Aluminum foil and cloth are acceptable out-


side case decorations; fasten them with suitable cement (Duco will hold cloth to plastic, but a "to-metal" cement such as Pliobond is required for aluminum foil). If the decorative material is to be fastened inside the case, back the cloth, paper or foil with a moderately stiff piece of paper or cardboard. Don't use cement. The control knobs fastened to the plastic case hold the interior decoration in place. If you mark dial scales with

India ink on a piece of filing card cut to fit inside of the case you will have an attractive scale that will never get dirty.

If you attach aluminum foil to a plastic case, the equipment in the case is shielded. The shield connection to the equipment's chassis ground is made through a volume control case or hex nut contact to the foil. If the equipment does not include a volume control, use a lug under a machine screw or nut introduced specifically for grounding purposes.

In using any of the "fasten-to" decorative approaches, cut required holes in the material after it's fastened. To make small round holes up to about $\frac{1}{2}$ in. dia., use a heated ice pick to make small pilot holes, then ream these to size with a taper reamer. To make larger round holes or square holes, use a heated knife or hacksaw blade. Or equip a soldering iron with a pointed cutter attachment made from a piece of tin can. The cutter can be made for either the quick-heat type of iron or a conventional soldering iron. (The size of the cutter attachment and the method of attaching it to the iron may have to be determined experimentally to get the right amount of heat transfer for easy cutting without excessive melting of the plastic.) Trim the edge build-up on the sides of the hole with a pocket knife and smooth with a file.

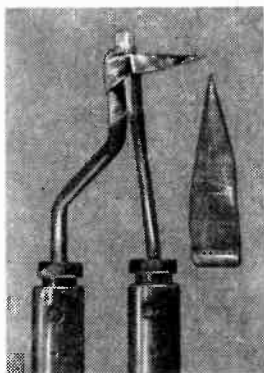To emboss a monogram and dial marks on the case, use a heated ice pick.



A soldering iron can be equipped with a tin-can scrap tip for cutting large holes in plastic cases.



WHITE'S RADIO LOG

An up-to-date broadcasting directory
AM, FM, TV and Short-Wave Stations

Vol. 36

No. 1

Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and, of course, only information available up to press-time could be included. Copyright 1959 by Science and Mechanics Publishing Co., 450 East Ohio St., Chicago 11, Ill.

QUICK REFERENCE INDEX

U.S. and Canadian AM Stations by Frequency 161
 U.S. and Canadian AM Stations by Location 170
 U.S. and Canadian AM Stations by Call Letters 178
 Mexican and Cuban AM Stations 185
 World-Wide Short-Wave Stations 186
 Canadian Short-Wave Stations 188
 United States FM Stations 188
 Canadian FM Stations 190
 United States Television Stations 190
 Canadian Television Stations 191

U. S. and Canadian AM Stations by Frequency

U.S. stations listed alphabetically by states within groups, Canadian stations precede U.S. Abbreviations: Kc., frequency in kilocycles; W.P., watt power; d—operates daytime only. Wave length is given in meters

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
540—555.5											
CBK Regina, Sask.		5000d	CFRA Ottawa, Ont.		5000	WKBN Youngstown, Ohio		5000	KBHS Hot Springs, Ark.		5000d
KVIP Redding, Calif.		1000d	CJKL Kirkland Lake, Ont.		5000	WNAX Yankton, S. Dak.		5000	KFXM San Bernardino, Cal.		1000
KFMB San Diego, Calif.		5000	CFOS Owen Sound, Ont.		1000	WFAA Dallas, Tex.		5000	KCSJ Pueblo, Colo.		1000
WGTO Cypress Gardens, Florida		5000d	WDOF Dothan, Ala.		5000d	WBAP Ft. Worth, Tex.		5000	WDLP Panama City, Fla.		1000
KBRV Soda Springs, Idaho		500d	KYUM Yuma, Ariz.		1000	KLUB Salt Lake City, Utah		5000	WAGA Atlanta, Ga.		5000
KWMT Ft. Dodge, Iowa		1000d	KSFO San Fran., Calif.		5000	KVI Seattle, Wash.		5000	KGB Honolulu, Hawaii		5000
WDVM Pocomoke City, Md.		500d	KLZ Denver, Colo.		5000	WMAM Marinette, Wis.		250	KID Idaho Falls, Idaho		1000
WCXG Canonsburg, Pa.		250d	WQAM Miami, Fla.		5000	580—516.9					
WDXN Clarksville, Tenn.		250d	WIND Chicago, Ill.		5000	CFCL Timmins, Ont.		1000	WKZO Kalamazoo, Mich.		5000
WRIC Richlands, Va.		1000d	WMIK Middleboro, Ky.		500d	CJFX Antigonish, N.S.		5000	WROW Albany, N.Y.		5000
550—545.1											
CFNB Fredericton, N.B.		5000	WGAN Portland, Maine		5000	CKPR Ft. William, Ont.		5000	WGTM Wilson, N.C.		5000
CFBR Sudbury, Ont.		1000	WHYX Springfield, Mass.		1000	CKUA Edmonton, Alta.		1000	KUGN Eugene, Oreg.		5000
CHLN Three Rivers, Que.		5000	WMIC Monroe, Mich.		500d	CKY Winnipeg, Man.		5000	WARM Scranton, Pa.		5000
CKPG Prince George, B.C.		250	WEBC Duluth, Minn.		5000	WTUS Tuskegee, Ala.		5000	WMBS Uniontown, Pa.		1000
KENI Anchorage, Alaska		5000	KWTO Springfield, Mo.		5000	CKNA Tucson, Ariz.		5000	KFC Austin, Tex.		5000
KAFY Bakersfield, Calif.		5000	KMON Great Falls, Mont.		5000	KMJ Fresno, Calif.		5000	KSUB Cedar City, Utah		1000
KRAI Craig, Colo.		1000	WGAI Elizabeth City, N.C.		1000	KUBC Montrose, Colo.		5000	WLVA Lynchburg, Va.		1000
WGGA Gainesville, Ga.		5000	WFIL Philadelphia, Pa.		5000	WDBO Orlando, Fla.		5000	KHQ Spokane, Wash.		5000
KFRM Concordia, Kansas		5000d	WIS Columbia, S.C.		5000	WGAC Augusta, Ga.		5000	600—499.7		
WHYX Springfield, Mass.		1000	WHBQ Memphis, Tenn.		5000	KFXD Nampa, Idaho		5000	CFCF Montreal, Que.		5000
WCBI Columbus, Miss.		1000	KFDM Beaumont, Tex.		5000	WILL Urbana, Ill.		5000d	CFCH North Bay, Ont.		1000
KSD St. Louis, Mo.		5000	WJLS Beckley, W.Va.		5000	KSAC Manhattan, Kans.		5000	CFQC Saskatoon, Sask.		5000
KOPR Butte, Mont.		5000	570—526.0						CFOR Vancouver, B.C.		5000
WGR Buffalo, N.Y.		5000	CKEK Cranbrook, B.C.		1000	WTAG Worcester, Mass.		5000	CKOL Truro, N.S.		1000
WDBM Statesville, N.C.		500d	CKCQ Quesnel, B.C.		1000	WELO Tupelo, Miss.		1000	WIRB Enterprise, Ala.		1000
KFYR Bismarck, N. Dak.		5000	CJEM Edmundston, N.B.		1000	WHP Harrisburg, Pa.		5000	KLS Flagstaff, Ariz.		5000
WGGA Gainesville, Ga.		5000	WCAS Gadsden, Ala.		5000d	WKAQ San Juan, P.R.		5000	KVCV Redding, Calif.		1000
KQAC Corvallis, Oreg.		5000	KCNO Alturas, Calif.		1000	WRKH Rockwood, Tenn.		500d	KFSD San Diego, Calif.		5000
WHLM Bloomsburg, Pa.		500	KLAC Los Angeles, Calif.		5000	KDVA Lubbock, Tex.		500d	WICC Bridgeport, Conn.		1000
WPAB Ponce, F.R.		5000d	WGMS Washington, D.C.		5000	WCHS Charleston, W.Va.		5000	WPDQ Jacksonville, Fla.		5000
WPAW Pawtucket, R.I.		1000d	WACL Waycross, Ga.		5000	WKTY LaCrosse, Wis.		1000	WMT Cedar Rapids, Iowa		5000
KMWI Waukegan, Ill.		1000	WKYB Paducah, Ky.		1000	590—508.2					
KCRS Midland, Tex.		5000	WVMI Biloxi, Miss.		1000d	CFAR FlinFlon, Man.		1000	WYFE New Orleans, La.		1000d
KTSA San Antonio, Tex.		5000	KGRT Las Cruces, N. Mex.		1000d	CFAR Huntsville, Ont.		1000	WST Caribou, Maine		5000d
WDEV Waterbury, Vt.		5000	WMCA New York, N.Y.		5000	CKRS Jonquiere, Que.		1000	WCAO Baltimore, Md.		1000
WVA Harrisonburg, Va.		5000	WSYR Syracuse, N.Y.		5000	VOCM St. Johns, N.F.		10000	WTAC Flint, Mich.		5000
WSAU Wausau, Wis.		5000	WWNC Asheville, N.C.		5000	WRAG Carrollton, Ala.		1000d	KGZJ Kalispell, Mont.		2000
			WMSN Raleigh, N.C.		500d				WSJS Winston-Salem, N.C.		5000

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KCSJ	Jamestown, N.D.	5000	670-447.5			KCBS	San Francisco, Calif.	5000	KDBM	Dillon, Mont.	1000
WFRM	Coudersport, Pa.	10000	WMAQ	Chicago, Ill.	5000	KWBV	Colo. Sprngs., Colo.	2500	WKDN	Camden, N.J.	1000
WAEI	Mayaguez, P.R.	1000	680-440.9			KVFC	Cortez, Colo.	1000	KTOW	Okla. City, Okla.	2500
WREC	Memphis, Tenn.	1000	CFHA	Edmonton, Alta.	5000	WKIS	Orlando, Fla.	5000	KPDQ	Portland, Oreg.	1000
KROD	El Paso, Tex.	5000	CHLO	St. Thomas, Ont.	1000	KYME	Boise, Idaho	5000	WCHA	Chambersburg, Pa.	1000
KERB	Kermit, Tex.	1000	CJOB	Winnipeg, Man.	1000	WVLN	Olney, Ill.	2500	DZPI	Manila, P.I.	1000
KTBB	Tyler, Tex.	1000	CKGB	Timmins, Ont.	5000	KBQE	Oskaloosa, Iowa	2500	WDSB	Dillon, S.C.	1000
610-491.5			KNBC	San Fran., Calif.	5000	WNOF	Newport, Ky.	1000	WEAB	Greer, S.C.	2500
CHNC	New Carlisle, Que.	5000	WPIN	St. Petersburg, Fla.	1000	TAJO	Gannett Bridge, Mass.	5000	KDDO	Dumas, Tex.	2500
CJAT	Trail, B.C.	1000	WCTT	Corbin, Ky.	1000	KPBM	Carlsbad, N.Mex.	1000	KBHM	Brigham City, Utah	1000
CKKL	Thompson, Man.	1000	WCBM	Baltimore, Md.	1000	WGSN	Huntington, N.Y.	1000	WVSU	Crewe, Va.	1000
CKTB	St. Catharines, Ont.	5000	WNAC	Lawrence, Mass.	5000	WMBL	Morehead City, N.C.	1000	WHTN	Huntington, W.Va.	1000
WSGN	Birmingham, Ala.	5000	WDBC	Escanaba, Mich.	1000	WPAQ	Mount Airy, N.C.	1000	WDOX	Waupaca, Wis.	1000
KAYL	Lancaster, Pa.	1000	KFEQ	St. Joseph, Mo.	5000	KRMG	Tulsa, Okla.	5000	810-370.2		
KFCR	San Francisco, Calif.	5000	WINR	Binghamton, N.Y.	1000	WVCH	Chester, Pa.	1000	KGO	San Francisco, Calif.	5000
WCKR	Miami, Fla.	5000	WRVM	Rochester, N.Y.	2500	WBS	Santurce, P.Rico	1000	KCMO	Kansas City, Mo.	5000
WCEH	Hawkinsville, Ga.	5000	WPTF	Raleigh, N.C.	5000	WBAW	Barnwell, S.C.	5000	WGY	Schenectady, N.Y.	5000
KUAM	Agana, Guam	1000	WVPA	San Juan, P.Rico	1000	WIRJ	Humbolt, Tenn.	2500	WKBC	Newark, N.C.	1000
KESE	Iowa Falls, Iowa	250	WMPB	Memphis, Tenn.	1000	WJTG	Tullahoma, Tenn.	2500	WFCB	Charlotte, N.C.	1000
WRUS	Russellville, Ky.	5000	KENS	San Antonio, Tex.	5000	KTRH	Houston, Tex.	5000	WEDO	McKeesport, Pa.	1000
KDLT	Duluth, Minn.	5000	KOMW	Omaha, Wash.	1000	750-399.8		WBYV	Waynesville, N.C.	1000	
WDAF	Kansas City, Mo.	5000	690-434.5			WSB	Atlanta, Ga.	5000	WBMJ	Baltimore, Md.	1000
KOJM	Havre, Mont.	1000	CBU	Vancouver, B.C.	1000	WMD	Baltimore, Md.	1000	KMMJ	Grand Island, Neb.	1000
WGIR	Manchester, N.H.	5000	CBF	Montreal, Que.	5000	KMMJ	Grand Island, Neb.	1000	WMMJ	Portsmouth, N.H.	1000
KGGM	Albuquerque, N.Mex.	5000	WVOK	Birmingham, Ala.	5000	KXEL	Portland, Oreg.	1000	KSEO	Durant, Okla.	2500
WAYS	Charlotte, N.C.	5000	WVNA	Flagstaff, Ariz.	1000	WFDX	Clarksburg, W.Va.	1000	820-365.6		
WTVN	Columbus, Ohio	5000	KEYT	Tucson, Ariz.	2500	760-394.5		WAIT	Chicago, Ill.	5000	
WVPL	Philadelphia, Pa.	5000	WISR	Butler, Pa.	1000	KGU	Honolulu, Hawaii	1000	WGBD	Chicago, Ill.	5000
KILT	Houston, Tex.	5000	WADS	Ansonia, Conn.	5000	WJR	Detroit, Mich.	5000	WIKY	Evansville, Ind.	2500
KVNU	Logan, Utah	1000	KBLI	Blackfoot, Idaho	1000	WPCS	Tarboro, N.C.	1000	WOSU	Columbus, Ohio	5000
WLSL	Roanoke, Va.	5000	KGFF	Coffeyville, Kans.	1000	770-389.4		KIKI	Honolulu, Hawaii	250	
KEPR	Kennewick, Wash.	5000	WTIX	New Orleans, La.	5000	KUOM	Minneapolis, Minn.	5000	WFAA	Dallas, Tex.	5000
620-483.6			KSST	St. Louis, Mo.	1000	WCAL	Northfield, Minn.	5000	WBAP	Ft. Worth, Tex.	5000
CKCK	Regina, Sask.	5000	KRGO	Prineville, Oreg.	1000	WEW	St. Louis, Mo.	1000	830-361.2		
KJAR	Phoenix, Ariz.	5000	KUSD	Verona, S.Dak.	1000	KOB	Albuquerque, N.Mex.	5000	WCCO	Minneapolis, Minn.	5000
KNGS	Hanford, Calif.	1000	KULA	Honolulu, T.H.	1000	WABC	New York, N.Y.	5000	KBOA	Kennett, Mo.	1000
KSTR	Grand Junction, Colo.	5000	KHEY	El Paso, Tex.	1000	KXA	Seattle, Wash.	1000	WNYC	New York, N.Y.	1000
WSUN	St. Petersburg, Fla.	5000	KPET	Lamesa, Tex.	250	780-384.4		840-356.9			
WTRP	LaGrange, Ga.	1000	KZEY	Tyler, Tex.	2500	WBM	Chicago, Ill.	5000	WKAB	Mobile, Ala.	1000
KWAL	Wallace, Idaho	1000	WCYB	Bristol, Va.	1000	WJAG	Norfolk, Neb.	1000	WKBN	New Britain, Conn.	1000
KMNS	Sioux City, Iowa	1000	WNNT	Marsaw, Va.	2500	WCCK	Dunn, N.C.	1000	WHAS	Louisville, Ky.	5000
WTMT	Louisville, Ky.	5000	WELD	Fisher, W.Va.	5000	WBBO	Forest City, N.C.	1000	WYPO	Stroudsburg, Pa.	2500
WLBZ	Bangor, Maine	5000	700-428.3			KSPI	Stillwater, Okla.	2500	850-352.7		
WJDX	Jackson, Miss.	5000	WLW	Cincinnati, Ohio	5000	WARR	Arlington, Va.	1000	CKVL	Verdun, Que.	5000
WNEW	Newark, N.J.	5000	710-422.1			790-379.5		CKRD	Red Deer, Alta.	1000	
WHEN	Syracuse, N.Y.	5000	CJSP	Leamington, Ont.	2500	CBY	Corner Brook, N.F.	1000	WYD	Birmingham, Ala.	1000
WDNC	Durham, N.C.	5000	CFRG	Gravelbourg, Sask.	5000	KCMR	Newcastle, N.B.	1000	KOA	Denver, Colo.	5000
KGW	Portland, Oreg.	5000	WKRG	Mobile, Ala.	1000	CKSO	Sulbury, Ont.	5000	WRUF	Gainesville, Fla.	5000
WHJB	Greensburg, Pa.	1000	KMPC	Los Angeles, Calif.	5000	WTUG	Tuscaloosa, Ala.	5000	WEAT	W. Palm Beach, Fla.	1000
WCAY	Cayce, S.C.	5000	KMYR	Denver, Colo.	5000	KCEI	Tucson, Ariz.	5000	KILA	Hilo, Hawaii	1000
WATE	Knoxville, Tenn.	5000	WGBS	Miami, Fla.	5000	KOSY	Texarkana, Ark.	1000	WHDH	Boston, Mass.	5000
KWFT	Wichita Falls, Tex.	5000	WRDM	Rome, Ga.	1000	KDAN	Eureka, Calif.	5000	WKCB	Muskogee, Mich.	1000
WCAX	Burlington, Vt.	5000	KEEL	Shreveport, La.	1000	KABC	Los Angeles, Calif.	5000	KFUD	St. Louis, Mo.	5000
WWRN	Beckley, W.Va.	1000	WOR	New York, N.Y.	5000	WLBE	Leesburg, Fla.	1000	WKJX	Raleigh, N.C.	1000
WTMJ	Milwaukee, Wis.	5000	DZRH	Manila, P.I.	1000	WFFA	Pensacola, Fla.	1000	WJW	Cleveland, Ohio	5000
630-475.9			WKJB	Mayaguez, P.Rico	1000	WXII	Atlanta, Ga.	1000	WEEU	Reading, Pa.	2500
CFCO	Chatham, Ont.	1000	WTPR	Paris, Tenn.	2500	WGRB	Cairo, Ill.	1000	WABA	Asuadilla, P.R.	1000
CHLT	Sherbrooke, Que.	5000	KGNC	Amariilo, Tex.	1000	KXXX	Colby, Kans.	5000	WRAP	Norfolk, Va.	5000
CFYJ	Charlottetown, P.E.I.	5000	KVYV	Edinburg, Tex.	250	WGR	Louisville, Ky.	5000	KTAC	Tacoma, Wash.	1000
CJET	Smith Falls, Ont.	1000	KIRO	Portland, Wash.	5000	WRUM	Rumford, Me.	1000	860-348.6		
KCRC	Winnipeg, Man.	5000	WDSM	Superior, Wis.	5000	WSGW	Saginaw, Mich.	1000	CJBC	Toronto, Ont.	5000
KCOV	Kelowna, B.C.	1000	720-416.4			KGHL	Billings, Mont.	5000	WHRT	Hartselle, Ala.	2500
CKYL	Peace River, Alta.	1000	WGN	Chicago, Ill.	5000	WVNO	Watsonton, N.Y.	1000	WAMI	Opp, Ala.	1000
WAVU	Alberta, Ala.	1000	730-410.7			WLSV	Wellsville, N.Y.	5000	WKFB	Fort Worth, Tex.	5000
WJDB	Thomasville, Ala.	1000	CJNR	Beind River, Ont.	1000	WTNC	Thomasville, N.C.	1000	KOSE	Oseola, Ark.	1000
KJNO	Juneau, Alaska	1000	CKAC	Montreal, Que.	5000	WKLM	Wilmington, N.C.	5000	KWRP	Warren, Ark.	2500
KVMA	Magnolia, Ark.	1000	CKDM	Dauphin, Man.	1000	KXGO	Fargo, N.Dak.	5000	KTRB	Modesto, Calif.	1000
KIDD	Monterey, Calif.	1000	CKLG	Ne. Vancouver, B.C.	1000	KWIL	Albany, Oreg.	1000	WKCO	Cocoa, Fla.	1000
KHOW	Denver, Colo.	5000	KFRD	Anchorage, Alaska	1000	WABE	Allentown, Pa.	500	WDMG	Douglas, Ga.	5000
WMAI	Washington, D.C.	5000	KBMW	Athens, Ala.	1000	WVFC	Charlotte, N.C.	5000	WWR	Worcester, Mass.	2500
WSAV	Savannah, Ga.	5000	KNYB	Newport, Ark.	1000	WEAN	Providence, R.I.	1000	WPGC	Muscatine, Iowa	2500
KIDO	Boise, Idaho	5000	WKTG	Thomasville, Ga.	1000	WBDB	Bamberg, S.C.	1000	KOAM	Pittsburg, Kans.	1000
WLAP	Lexington, Ky.	5000	KBLR	Goodland, Kans.	1000	WETB	Johnson City, Tenn.	1000	WSON	Henderson, Ky.	5000
KTIB	Thibodaux, La.	500	WFMY	Madisonville, Ky.	2500	WMC	Memphis, Tenn.	5000	WAYE	Dundalk, Md.	5000
WJMS	Ironwood, Mich.	1000	WMTG	Vanceville, Ky.	1000	KTHT	Houston, Tex.	5000	WBSB	Gt. Barrington, Mass.	2500
KXOK	St. Louis, Mo.	5000	WVWB	Wilmington, N.C.	1000	KFYD	Lubbock, Tex.	5000	KJNF	New Ufm, Minn.	1000
KOH	Reno, Nev.	5000	WVFL	Scranton, Pa.	5000	WVTV	Winston-Salem, N.C.	1000	WFMJ	Farmont, W.Va.	1000
KLEA	Lovingsville, N.Mex.	500	WVPR	Providence, R.I.	5000	WTAR	Norfolk, Va.	5000	WMO	Farmont, W.Va.	1000
WIRC	Hickory, N.C.	1000	KGFX	Pierre, S.Dak.	250	KVOS	Bellingham, Wash.	1000	WAMO	Homestead, Pa.	2500
WVFD	Wilmington, N.C.	1000	KPOA	Honolulu, T.H.	5000	KTRY	Spokane, Wash.	5000	WTEL	Philadelphia, Pa.	2500
WEPL	Scranton, Pa.	5000	WMCN	San Antonio, Tex.	1000	WEAU	Washingon, Wis.	5000	WLBG	Laurens, S.C.	2500
WVJR	Providence, R.I.	5000	KZUN	Opportunity, Wash.	5000	800-374.8		WVVK	Knoxville, Tenn.	1000	
WVPL	Providence, R.I.	5000	640-468.5			CHAB	Moose Jaw, Sask.	1000	WMTS	Murfreesboro, Tenn.	2500
WVPR	Providence, R.I.	5000	CBN	St. John's, N.F.	1000	CKOK	Penticton, B.C.	1000	KFTS	Ft. Stockton, Tex.	2500
WVPT	Providence, R.I.	5000	WFI	Los Angeles, Calif.	5000	CFOB	Ft. Frances, Ont.	1000	KPR	Portland, Ore.	2500
WVPS	Providence, R.I.	5000	W01	Ames, Iowa	5000	CJQB	Bellefonte, Ont.	1000	KSFA	Nacogdoches, Tex.	1000
WVPU	Providence, R.I.	5000	WHKK	Akron, Ohio	1000	CHRC	Quebec, Que.	5000	KONO	San Antonio, Tex.	5000
WVQV	Providence, R.I.	5000	WNAD	Norman, Okla.	1000	CJAD	Montreal, Que.	1000	KWHO	Salt Lake City, Utah	1000
WVWV	Providence, R.I.	5000	650-461.3			VOWR	St. Johns, N.F.	1000	WEVA	Emporia, Va.	1000
WVXV	Providence, R.I.	5000	WSM	Nashville, Tenn.	5000	WHOS	Decatur, Ala.	1000	WDAY	Oak Hill, W.Va.	1000
WVYV	Providence, R.I.	5000	KRCT	Baytown, Texas	2500	WMGY	Montgomery, Ala.	1000	WFOX	Milwaukee, Wis.	2500
660-454.3			660-454.3			KINY	Juneau, Alaska	5000	870-344.6		
KFAR	Fairbanks, Alaska	1000	CFXA	Edmonton, Alta.	250	KAGH	Groesett, Ark.	2500	KIEV	Glendale, Calif.	2500
KOWH	Omaha, Neb.	5000	KBLT	Toronto, Ont.	5000	KVOM	Morrilton, Ark.	2500	KAIM	Kaimuki, Hawaii	1000
WROA	New York, N.Y.	5000	WBAW	Montgomery, Ala.	5000	KHIL	Brighton, Colo.	2500	WVWL	New Orleans, La.	5000
WESC	Greenville, S.C.	5000	KUEQ	Phoenix, Ariz.	1000	WLAD	Danbury, Conn.	5000	WKAR	E. Lansing, Mich.	5000
KSKY	Dallas, Tex.	1000	KBIG	Avallon, Calif.	1000	WMBM	Miami Beach, Fla.	1000	WHCU	Ithaca, N.Y.	1000
162 WHITE'S RADIO LOG			740-405.2			WSUZ	Palatka, Fla.	1000	WGTL	Kannapolis, N.C.	1000
			CBXA	Edmonton, Alta.	250	WJAT	Swainsboro, Ga.	1000	KJIM	Ft. Worth, Tex.	2500
			KBLT	Toronto, Ont.	5000	KXID	Iowa City, Iowa	1000	WFLD	Farmville, Va.	1000
			WBAW	Montgomery, Ala.	5000	WBOK	New Orleans, La.	1000	880-340.7		
			KUEQ	Phoenix, Ariz.	1000	WCCM					

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WRRZ	Cinton, N.C.	1000d	KREX	Grd. Junction, Colo.	5000	WNCG	Barnesboro, Pa.	5000	WCAP	Lowell, Mass.	1000d
WRFD	Worthington, Ohio	5000d	KLML	Duran, Colo.	1000	WPEN	Philadelphia, Pa.	5000	WPBC	Minneapolis, Minn.	1000d
890—336.9											
WLS	Chicago, Ill.	50000	WMEG	Eau Gallie, Fla.	1000d	WSPA	Spartanburg, S.C.	5000	WAPP	McComb, Miss.	1000d
WHNC	Henderson, N.C.	1000d	WGST	Atlanta, Ga.	5000	KWAT	Watertown, S.Dak.	1000d	KMBC	Kansas City, Mo.	5000
KBYE	Okl. City, Okla.	1000d	KAHU	Waipahu, Hawaifi	1000d	WAGG	Franklin, Tenn.	1000d	KSGM	Ste. Genevieve, Mo.	5000
900—333.1											
CKTS	Sherbrooke, Que.	1000	WMOQ	Metropolis, Ill.	5000	KDXX	Denison, Tex.	500	KICA	Clovis, N.Mex.	1000
CHML	Hamilton, Ont.	5000	WBAA	W. Lafayette, Ind.	5000	KPRC	Houston, Tex.	5000	KMIN	Grants, N.Mex.	1000d
CHND	Sudbury, Ont.	1000	KFNF	Shenandoah, Iowa	1000d	KSEL	Lubbock, Tex.	1000d	WTRY	Troy, N.Y.	5000
CJBR	Rimouski, Que.	1000d	WTGW	Whitesburg, Ky.	1000d	WJRI	Richmond, Va.	1000d	WKLM	Wilmington, N.C.	5000d
CKJL	St. Jerome, Que.	1000	WHXY	Hogansau, La.	1000d	WJST	Seattle, Wash.	5000	WAAA	Win. Salem, N.C.	1000d
CJVI	Victoria, B.C.	1000d	WMFL	Bogalusa, Mich.	5000	WKAZ	Charleston, W.Va.	5000	WONE	Dayton, Ohio	5000
CKBI	Prince Albert, Sask.	1000d	KDHL	Faribault, Minn.	1000	WSHE	Sheboygan, Wis.	500d	WILK	Wilkes-Barre, Pa.	5000
CJGX	Yorkton, Sask.	1000d	KWAD	Wadena, Minn.	1000	960—312.3					
WATV	Birmingham, Ala.	1000d	KRAM	Las Vegas, Nev.	1000	CFAC	Calgary, Alta.	5000	KSCV	Richfield, Utah	5000
WDOZ	Ozark, Ala.	1000d	KOLO	Reno, Nev.	1000	WHWS	Halifax, N.S.	1000d	WFHG	Bristol, Va.	5000
KFRB	Fairbanks, Alaska	2500	KQEO	Albuquerque, N.Mex.	1000	CKWS	Kingston, Ont.	5000	WUBT	Yakima, Wash.	1000d
KHOZ	Harrison, Ark.	1000d	WTTM	Trenton, N.J.	1000	WBRC	Birmingham, Ala.	5000	KCTB	Manltowoc, Wis.	1000d
KBIF	Centerville, Calif.	1000d	WKRT	Cortland, N.Y.	1000d	WMOZ	Mobile, Ala.	1000	WPRE	Prairie du Chien, Wis.	5000
WJWL	Georgetown, Del.	1000d	WSKN	Saugerties, N.Y.	1000d	KAVR	Apple Valley, Calif.	5000d	990—302.8		
WSWN	Belle Glade, Fla.	1000d	WBBB	Burlington, N.C.	5000	KNEZ	Lompoc, Calif.	500	CBW	Winnipeg, Man.	50000
WMOP	Ocala, Fla.	1000d	WMNI	Columbus, Ohio	500	KROW	Oakland, Calif.	1000	CBT	Grand Falls, N.F.	1000
WCCA	Calhoun, Ga.	1000d	KGAL	Lebanon, Oreg.	1000d	WELI	West Haven, Conn.	1000d	WWWF	Fayette, Ala.	1000d
WCJY	Macon, Ga.	250d	WKVA	Lewistown, Pa.	1000d	WCM	Sebring, Fla.	1000d	WTCB	Flomaton, Ala.	500d
WVJY	Savannah, Ga.	1000d	WJAR	Providence, R.I.	1000d	WRFC	Athens, Ga.	5000	KTCT	Tucson, Ariz.	10000d
KSIR	Wichita, Kan.	250	WTND	Orangeburg, S.C.	1000d	WSBT	South Bend, Ind.	5000	KIIS	Pittsburgh, Calif.	5000
WKYW	Louisville, Ky.	1000d	WLIV	Livingston, Tenn.	5000	KMA	Shenandoah, Iowa	5000	KLIR	Denver, Colo.	1000d
WLSI	Pikeville, Ky.	1000d	KELP	El Paso, Tex.	1000	WPRT	Prestonsburg, Ky.	1000d	WBZY	Torrington, Conn.	1000d
KREH	Oakdale, La.	250d	KECK	Odesa, Tex.	1000	KROF	Abbeville, La.	1000d	WHD	Orlando, Fla.	10000
WCME	Brunswick, Maine	500d	KCKW	Tex. City, Tex.	5000	WBQC	Salisbury, Md.	5000	WDWD	Dawson, Ga.	1000d
WATG	Gaylord, Mich.	1000d	KXLY	Spokane, Wash.	5000	KLTF	Little Falls, Minn.	5000	WCZA	Carthage, Ill.	1000d
KTIS	Minnetonka, Minn.	1000d	WMMN	Fairmont, W.Va.	5000	WABG	Greenwood, Miss.	1000	WITZ	Jasper, Ind.	1000d
WDDT	Greenville, Miss.	1000d	WOKY	Milwaukee, Wis.	1000	KFVS	Cape Girardeau, Mo.	1000	KAYL	Storm Lake, Iowa	250d
KFAL	Fulton, Mo.	1000d	930—322.4			KNEB	Scottsbluff, Neb.	1000	KRSL	Russell, Kans.	250d
KJSK	Columbus, Neb.	1000d	CFBC	Saint John, N.B.	5000	KWYK	Farmington, N.Mex.	1000d	WJMR	New Orleans, La.	250d
WOTW	Nashua, N.H.	1000d	CJCA	Edmonton, Alta.	5000	WEAV	Plattsburg, N.Y.	5000	KCLP	Rayville, La.	250d
WBRV	Boonville, N.Y.	500d	CJDN	St. John's, N.F.	1000d	WFTC	Kingston, N.C.	1000d	WABD	Waynesboro, Miss.	250d
WSPN	Saratoga Sprngs., N.Y.	250d	WETO	Gadsden, Ala.	1000d	KWFS	Rooster, Ohio	5000	KRMD	Monett, Mo.	250d
WAYN	Rockingham, N.C.	1000d	KTKN	Ketchikan, Alaska	1000d	KGWA	Evans, Okla.	1000d	WSPX	Artesia, N.Mex.	1000
WIAM	Williamston, N.C.	1000d	KAPR	Douglas, Ariz.	1000d	WHYL	Carlisle, Pa.	1000d	WEEB	Southwestern Pines, N.C.	1000d
KFNW	Fargo, N.Dak.	1000d	KHJ	Los Angeles, Calif.	5000	WAND	Kan. Pa.	500d	WJEH	Gallipolis, Ohio	1000d
WAND	Canton, Ohio	500d	KLUP	Durango, Colo.	5000	WATS	Sayre, Pa.	1000d	WTIG	Massillon, Ohio	250d
WFRD	Fremont, Ohio	500d	KWSB	Mont. Del.	500d	WBEU	Beaufort, S.C.	5000	WIBG	Philadelphia, Pa.	10000
KLAD	Klamath Falls, Oreg.	1000d	WJAX	Jacksonville, Fla.	5000	WBMC	McMininville, Tenn.	5000	WVSC	Somerset, Pa.	250d
WCPA	Clearfield, Pa.	1000d	WKXY	Sarasota, Fla.	1000d	KIMP	Mt. Pleasant, Tex.	5000	WPRR	Mayaguez, P.R.	1000d
WXXV	Knoxville, Tenn.	250d	WMGR	Sanbridge, Ga.	5000d	KKIC	San Angelo, Tex.	5000	WAKN	Aiken, S.C.	1000d
WCDR	Lebanon, Tenn.	250d	KSEI	Pocatello, Idaho	5000	KGOV	Govt. Utah	5000	WNOX	Knoxville, Tenn.	1000d
KALT	Atlanta, Tex.	1000d	WTAD	Quincy, Ill.	5000	WDBJ	Roanoke, Va.	5000	KWEM	Memphis, Tenn.	1000d
KMCO	Conroe, Tex.	500d	WKCT	Hotlyng Green, Ky.	1000	KALE	Richland, Wash.	1000	KTRM	Beaumont, Tex.	1000d
KFLD	Floydada, Tex.	250d	WFMD	Friederick, Md.	1000	WTCH	Shawano, Wis.	1000	KAML	Kenedy, Tex.	250
KCLW	Hamilton, Tex.	250d	WREB	Holyoke, Mass.	500d	970—309.1					
WAFG	Staunton, Va.	1000d	WBCK	Battle Creek, Mich.	1000	CKCH	Hull, Que.	5000	KSYD	Wichita Falls, Tex.	10000
KUEN	Wenatchee, Wash.	250d	WLSJ	Jackson, Miss.	5000	WERH	Hamilton, Ala.	5000d	KTUT	Utah, Idaho	1000d
WATK	Antigo, Wis.	250d	KWOC	Poplar Bluff, Mo.	1000	WTBF	Troy, Ala.	5000	WNRV	Narrows, Va.	1000d
910—329.5											
CJVD	Drumheller, Alta.	1000	KODI	Kalisisp, Mont.	5000d	WVTV	Vero, Fla.	5000	WANT	Richmond, Va.	1000d
CKLY	Lindsay, Ont.	1000	KOGA	Ogallala, Neb.	5000d	KNEA	Jonesboro, Ark.	1000d	WKLJ	Sparta, Wis.	250
CBT	Ottawa, Ont.	5000	WNRH	Rocheater, N.H.	5000d	KBIS	Bakersfield, Calif.	1000	1000—299.8		
CFJC	Kamloops, B.C.	1000	PAT	Patuxent, N.J.	5000	KCHV	Chandler, Calif.	1000d	CKBW	Bridgewater, N.S.	1000
CHRL	Bellevue, Que.	1000	WBEN	Buffalo, N.Y.	5000	KBEE	Modesto, Calif.	1000d	CKTG	Okl. City, Okla.	5000
KPHO	Phoenix, Ariz.	5000	WIST	Charlotte, N.C.	5000	KFEL	Pueblo, Colo.	1000d	CKTA	Coleman, Tex.	5000
KLCN	Boyerfield, Ark.	5000d	WRRF	Washington, N.C.	5000	WFLA	Tampa, Fla.	5000	KGRI	Henderson, Tex.	250d
KAMD	Camden, Ark.	1000	WEOL	Elyria, Ohio	1000	WVDP	Deatour, Ga.	5000d	WHWB	Rutland, Vt.	1000d
KDEO	El Cajon, Calif.	1000	WKY	Oklahoma City, Okla.	5000	KHBC	Hilo, Hawaii	1000	KOMO	Seattle, Wash.	50000
KLX	Oakland, Calif.	5000	WCNR	Bloomsburg, Pa.	1000d	KBOP	Burbur, Idaho	1000d	1010—296.9		
KOXR	Oxnard, Calif.	1000d	KSDN	Aberdeen, S.D.	5000	WYAY	Springfield, Ill.	5000	CBX	Edmonton, Alta.	5000d
KPOF	Fort. Denver, Colo.	5000	KDET	Center, Tex.	1000d	WAVE	Louisville, Ky.	5000	CFRB	Toronto, Ont.	50000
WHAY	New York, Conn.	5000	KITE	San Antonio, Tex.	5000d	KSyl	Alexandria, La.	1000	KVNC	Winslow, Ark.	1000
WPA	Pitt City, Fla.	1000d	KENY	Bellingham-Ferndale Wash.	1000d	WCSH	Portland, Maine	5000	KLRA	Little Rock, Ark.	1000d
WGAF	Valdosta, Ga.	5000	WSAZ	Huntington, W.Va.	5000	WAMD	Aberdeen, Md.	5000	CKCF	Calif. Calif.	1000d
WSUI	Iowa City, Iowa	5000	WBLB	Auburndale, Wis.	5000d	WESO	Southbridge, Mass.	1000d	CKMJ	Palm Sprngs, Calif.	1000
WLCB	Baton Rouge, La.	5000	940—319.0			WVTV	Vero, Fla.	5000	KSAY	San Fran., Calif.	1000d
WABI	Bangor, Maine	1000	CBM	Montreal, Que.	50000	WKHM	Kathlamet, Mich.	1000	WCNU	Crestview, Fla.	1000d
WDFC	Flint, Mich.	5000	CJGX	Yorkton, Sask.	10000	KOBI	Billings, Mont.	5000	WZRO	Jacksonville Beach, Fla.	1000d
WDOC	Meridian, Miss.	5000	CJIB	Vernon, B.C.	1000	KJLT	N. Platte, Neb.	5000d	WEAS	Deatur, Ga.	5000d
KOYN	Billings, Mont.	1000d	KFRE	Fresno, Calif.	50000	WNTA	Newark, N.J.	5000	WCSI	Columbus, Ind.	5000
KRIM	Roswell, N.Mex.	5000	WINZ	Miami, Fla.	1000d	WEBR	Buffalo, N.Y.	5000	KSMN	Mason City, Iowa	1000d
WLAS	Jacksonville, N.C.	5000d	WMAZ	Macon, Ga.	1000d	WCNH	Norwich, N.Y.	500d	KIND	Independence, Kans.	250d
KCJB	Minot, N.Dak.	1000	WMIX	Mt. Vernon, Ill.	1000	WRCS	Ashokite, N.C.	1000d	KDLA	DeRidder, La.	1000d
WPFB	Middletown, Ohio	1000	KIDA	Des Moines, Iowa	1000	WRTT	Canton, N.C.	1000d	WSD	Baltimore, Md.	1000d
KGLC	Miami, Okla.	1000	WESA	Charleroi, Pa.	250	WDAY	Fargo, N.Dak.	5000	KCHI	Chillicothe, Mo.	250d
KURY	Brookings, Oreg.	500	WPRN	San Juan, P.R.	1000d	WATH	Athens, Ohio	1000d	KJCF	Festus, Mo.	250d
WAVL	Anolio, Pa.	1000d	KLYN	Amarillo, Tex.	1000	KAKC	Tulsa, Okla.	1000	KRVN	Lexington, Nehr.	25000d
WSBA	York, Pa.	1000	950—315.6			KNOK	Fl. North, Tex.	5000	KLAS	Las Vegas, Nev.	5000d
WPRP	Ponce, P.R.	5000	CKNB	Campbellton, N.B.	1000	WYIP	York, Pa.	5000	WJEC	Warlock, N.Y.	50000
WORD	Spartanburg, S.C.	1000	CKBB	Barrie, Ont.	5000	WYVD	Pineville, W.Va.	1000d	WABZ	Albermarle, N.C.	1000d
WJHL	Johnson City, Tenn.	5000	WRMA	Montgomery, Ala.	1000d	WHA	Madison, Wis.	5000d	WELS	Kingston, N.C.	1000d
WEPG	S. Pittsburgh, Tenn.	500d	KXJK	Forrest City, Ark.	5000d	980—305.9					
KRIO	McAllen, Tex.	1000	CFSA	Forest City, Ark.	5000d	CKNW	New Westminster, Brit. Columbia	5000	WORM	Savannah, Tenn.	250d
KRRV	Sherman, Tex.	1000	KAHJ	Auburn, Calif.	500d	CPFL	London, Ont.	5000	KAMQ	Amarillo, Tex.	5000
KALL	Salt Lake City, Utah	1000	KIMN	Denver, Colo.	5000	CBV	Quebec, Que.	5000	KMLW	Marlin, Tex.	250d
WRNL	Richmond, Va.	5000	WFBS	Ft. Walton Beh., Fla.	1000d	CKRM	Peterboro, Ont.	5000	WCH	Charlottesville, Va.	1000d
WHYE	Roanoke, Va.	1000d	WLOF	Orlando, Fla.	5000	CKFB	Regina, Sask.	5000	WMEY	Marion, Mo.	1000d
KORD	Pasco, Wash.	1000d	WGTA	Summerville, Ga.	1000d	WKLF	Clinton, Ala.	5000	WSPT	Stevens Pt., Wis.	1000d
KQDE	Renton, Wash.	1000d	WGOV	Valdosta, Ga.	5000	KINS	Eureka, Calif.	5000	1020—293.9		
KVAN	Vancouver, Wash.	1000d	KBOB	Boise, Idaho	5000	KEFP	Fresno, Calif.	500d	KPOF	Los Angeles, Calif.	5000
WWSM	Hayward, Wis.	1000d	KLER	Orange, Idaho	500d	KFWB	Los Angeles, Calif.	5000	WCIL	Cbandale, Ill.	1000d
WDDR	Sturgeon Bay, Wis.	5000	WAAF	Chicago, Ill.	1000d	KGLN	Glenwood Sprngs., Colo.	1000d	WPED	Pearia, Ill.	1000d
920—325.9											
CJCH	Halifax, N.S.	10000	WXLW	Indianapolis, Ind.	5000d	WSUB	Groton, Conn.	1000	KDKA	Pittsburgh, Pa.	50000
CKNX	Winaham, Ont.	2500	KOEL	Oelwein, Iowa	1000	WRC	Washington, D.C.	5000	1030—291.1		
WCTA	Adulafia, Ala.	2500	KJRG	Newton, Kans.	500d	WDVH	Gainesville, Fla.	5000d	WBZ	Boston, Mass.	50000
WVWR	Russellville, Ala.	1000d	WBLV	Barbourville, Ky.	1000d	WDTT	Marianna, Fla.	5000			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
(1290—232.4)											
WCOW	Sparta, Wis.	1000d	WATR	Waterbury, Conn.	1000	KIST	Santa Barbara, Calif.	250	KOLE	Port Arthur, Tex.	250
1300—230.6			WGMA	Hollywood, Fla.	1000	KOMY	Wasanville, Calif.	250	KTXL	San Angelo, Tex.	250
CBAF	Moncton, N.B.	5000	WJHP	Jacksonville, Fla.	5000	KDEN	Denver, Colo.	250	KVFN	N. of Victoria, Tex.	250
CRH	Richmond Hill, Ont.	5000	WHIE	Griffin, Ga.	1000d	KVRH	Salida, Colo.	250	WTWN	St. Johnsbury, Vt.	250
WLS	Tallahassee, Fla.	1000d	WNEG	Toccoa, Ga.	1000d	WNHC	New Haven, Conn.	250	WSTA	Charlotte Amalie, V.I.	250
WTCS	Searcy, Ark.	1000d	WKAN	Kanacka, Ill.	1000d	WOK	Washington, D.C.	250	WKEY	Covington, Va.	250
KROP	Brawley, Calif.	1000	KLWN	Lawrence, Kans.	5000	WTAN	Clearwater, Fla.	250	WHAP	Hopewell, Va.	250
KYNO	Fresno, Calif.	1000	WBRT	Bardstown, Ky.	1000d	WRD	Daytona Bch., Fla.	250	WJMA	Orange, Va.	250
KWKW	Pasadena, Calif.	1000	WBWF	Windsor, Ky.	1000d	WRD	Daytona Bch., Fla.	250	KAGT	Anacortes, Wash.	250
KVOR	Colo. Sprngs., Colo.	1000	KVHL	Hollywood, Fla.	1000d	WTSY	Marianna, Fla.	250	KPIR	Pecos, N.M.	250
WVZ	New Haven, Conn.	1000	WICO	Salisbury, Md.	5000	WQXT	Palm Beach, Fla.	250	KAPA	Raymond, Wash.	250
WMTB	Tampa, Fla.	5000d	WARA	Attleboro, Mass.	5000	WGAU	Athens, Ga.	250	KMEL	Wentatchee, Wash.	250
WMTM	Moultrie, Ga.	5000d	WILS	Lansing, Mich.	1000	WAKE	Atlanta, Ga.	250	WHAR	Clarksburg, W.Va.	250
WIMO	Winder, Ga.	1000d	WOMJ	Marquette, Mich.	5000d	WBBQ	Augusta, Ga.	250	WEPM	Martinsburg, W.Va.	250
KOZE	Lewiston, Idaho	5000	WPCP	Houston, Miss.	1000d	WGA	Cedartown, Ga.	250	WMON	Montgomery, W.Va.	250
WTAQ	LaGrange, Ill.	500	WRJW	Pitcaune, Miss.	5000d	WTK	Clinton, Mo.	250	WWE	Welch, W.Va.	250
WFRX	W. Frankfort, Ill.	1000d	KXLF	Clayton, Mo.	5000	KPST	Preston, Idaho	250	WVIT	Ladysauke, Wis.	250
WHLT	Huntington, Ind.	5000	WWHG	Hornell, N.Y.	5000d	WSOY	Decatur, Ill.	250	WFRH	Wis. Rapids, Wis.	250
WMTT	Terre Haute, Ind.	5000	WAGY	Forest City, N.C.	500d	WJPF	Herrin, Ill.	250	KOWB	Laramie, Wyo.	250
KGLO	Mason City, Iowa	5000	WCOG	Greensboro, N.C.	5000	WJOL	Joliet, Ill.	250	WKOR	Worland, Wyo.	250
WBLG	Lexington, Ky.	1000	KQDY	Minot, N.Dak.	1000d	WTRC	Bedford, Ind.	250			
WIBR	Baton Rouge, La.	1000	WHOK	Lancaster, Ohio	1000d	WLBC	Muncie, Ind.	250	1350—222.1		
KLUE	Shreveport, La.	1000d	WHOE	Clinton, Okla.	1000d	KROS	Clinton, Iowa	250	CHOV	Pembroke, Ont.	1000
WFBR	Baltimore, Md.	5000	WAFR	Frankfort, Pa.	5000	KLIL	Estherville, Iowa	250	CJDC	Dawson Creek, B.C.	1000
WJDA	Quincy, Mass.	1000d	WAMP	Pittsburg, Pa.	5000	KCKN	Kansas City, Kans.	250	CHGB	St. Anne de la Pociatere, Que.	1000
WQD	Grand Rapids, Mich.	5000	WSCR	Scranton, Pa.	5000	KSEK	Pittsburg, Kans.	250	CKLB	Oshawa, Ont.	5000
WREB	Jackson, Mo.	5000	WRIO	Rio Piedras, P.R.	5000	WCHI	Ashland, Ky.	250	KCFN	Kentville, N.S.	1000
KMMO	Marshall, Mo.	1000d	WRMS	Columbia, S.C.	1000	WMBB	Bedford, Ind.	250	CHRR	Richmond, N.S.	5000
KBRM	CoCook, Nebr.	1000d	KELO	Sioux Falls, S.Dak.	5000	WKEY	Richmond, Ky.	250	WGAD	Gadsden, Ala.	5000
WTNJ	Trenton, N.J.	250d	WKIN	Kingsport, Tenn.	5000d	KGAN	Bastrop, La.	250	KWFC	Fort Springs, Ark.	1000
WOSC	Fulton, N.Y.	1000d	KXYZ	Houston, Tex.	1000d	KRMD	Shreveport, La.	250	KLYD	Bakersfield, Calif.	1000d
WGOL	Goldsoor, N.C.	1000d	KDYL	Salt Lake City, Utah	5000	WABM	Houlton, Maine	250	KCKC	San Bernardino, Calif.	500
WSYD	Mt. Airy, N.C.	5000	WLLY	Richmond, Va.	1000d	WNBH	New Bedford, Mass.	250	KRSR	Santa Rosa, Calif.	1000
WVIZ	Cleveland, Ohio	5000	KXRO	Aberdeen, Wash.	1000	WBRK	Pittsfield, Mass.	5000	KGBD	Bedford, Colo.	5000
WVMO	Mt. Vernon, Ohio	5000	KHIT	Walla Walla, Wash.	1000d	WLEW	Bad Axe, Mich.	250	WNLK	Norwalk, Conn.	5000
KOME	Tulsa, Okla.	5000	1330—225.4			WLAW	Grand Rap., Mich.	250	WPCT	Putnam, Conn.	1000d
KRMW	The Oalles, Oreg.	1000d	CBH	Halifax, N.S.	100	WVSE	Hillsdale, Mich.	100	WDFC	Dade City, Fla.	1000d
WTIL	Mayaguez, P.R.	1000	WRDS	Scottsboro, Ala.	1000d	WTFE	Manistee, Mich.	250	WRPB	Warner Robins, Ga.	1000d
WCKJ	Greer, S.C.	1000d	KMOP	Tucson, Ariz.	500d	WAGL	Genoa, Mich.	250	KRLC	Lewiston, Idaho	5000
KOLY	Mobridge, S.Dak.	1000d	KFAO	Los Angeles, Calif.	1000d	WMBN	Petoskey, Mich.	250	WEEK	Peoria, Ill.	1000
WREB	Meriden, Conn.	5000d	WARM	Pt. Pinos, Fla.	1000d	WEXL	Royal Oak, Mich.	250	WJLD	Salem, Ill.	1000
WMAK	Nashville, Tenn.	5000	WYSE	Lakeland, Fla.	5000	KDLM	Detroit Lakes, Minn.	250	WIOU	Kokomo, Ind.	5000
KVET	Austin, Tex.	1000	WBEY	Milton, Fla.	5000d	WEVE	Eveleveth, Minn.	250	KRNT	Des Moines, Iowa	5000
KTFY	Brownfield, Tex.	1000d	WMEN	Tallahassee, Fla.	5000d	KROC	Rochester, Minn.	250	KMAN	Manhattan, Kans.	5000
KOL	Seattle, Wash.	5000	WMLT	Dublin, Ga.	1000d	WFLM	Wilmar, Minn.	250	WLOU	Louisville, Ky.	5000d
WCLG	Morgantown, W.Va.	1000d	WEAW	Evansville, Ind.	1000d	WJMB	Brookhaven, Miss.	250	WSMB	New Orleans, La.	5000
WKLK	St. Albans, W.Va.	1000d	WRAM	Monmouth, Ill.	1000d	WAML	Laurel, Miss.	250	WHMI	Howell, Mich.	5000
1310—228.9			WRBR	Rockford, Ill.	1000d	KXEO	Mexico, Mo.	250	KDIO	Ortonville, Minn.	1000d
CKOY	Ottawa, Ont.	5000	WJPS	Evansville, Ind.	5000	KSMO	Salem, Mo.	250	WCMF	Pine City, Minn.	1000d
WHEP	Foley, Ala.	1000d	KWVL	Waterloo, Iowa	5000	KICK	Springfield, Mo.	250	WKOZ	Kosciusko, Miss.	5000
WJAM	Marion, Ala.	5000d	KFHW	Wichita, Kans.	5000	KCAP	Helena, Mont.	250	KCHR	Charleston, Mo.	1000d
KBZ	Mesa, Ariz.	5000	WMOR	Morehead, Ky.	1000d	KPK	Livingston, Mont.	250	WLNH	Laconia, N.H.	5000d
WXXK	Malvern, Ark.	1000d	KVOL	Lafayette, La.	1000	KATL	Miles City, Mont.	250	WBCA	Corning, N.Y.	1000d
WKBR	Oakland, Calif.	1000d	WASA	Hayre deGrace, Md.	1000d	KBTk	Missoula, Mont.	250	WHIP	Moresville, N.C.	1000d
KTKR	Taft, Calif.	5000	WCRB	Waltham, Mass.	5000	KFTG	Fremont, Nebr.	100	KDDI	Bismarck, N.D.	5000
KFKA	Greeley, Colo.	1000	WCRB	Chnt. Mo.	1000d	KGFW	Kearney, Nebr.	250	WADC	Akron, Ohio	5000
WICH	Norwich, Conn.	1000	WLOL	Minneapolis, Minn.	5000	KSID	Sidney, Nebr.	250	WCHI	Chico, Ohio	1000d
W00D	Deland, Fla.	5000d	WRCR	Minneapolis, Minn.	5000	KORK	Las Vegas, Nev.	250	KRRD	Duncan, Okla.	250
W00C	Wauchula, Fla.	5000	WJPR	Greenville, Miss.	1000	WDRR	Hanover, N.H.	250	KTLQ	Tahlequah, Okla.	500d
W00E	Wausau, Wis.	1000d	W00D	Meridian, Miss.	1000d	W00D	Atlantic City, N.J.	250	W0RK	York, Pa.	5000
WBRO	Waynesboro, Ga.	1000d	K00K	Will Springs, Mo.	5000	KABQ	Albuquerque, N.Mex.	250	WDAR	Darlington, S.C.	5000
WBKM	West Point, Ga.	1000	KGAK	Gallup, N.Mex.	5000	KSIL	Silver City, N.Mex.	250	WGSW	Greenwood, S.C.	1000d
KLIX	Twin Falls, Idaho	1000	W00D	Rockford, Ill.	1000d	W00B	Auburn, N.Y.	250	KXJY	Jasper, Tex.	1000d
WISH	Indianapolis, Ind.	5000	W00E	Westfield, N.Y.	5000	W00T	Towsonville, N.Y.	250	W00C	Waco, Tex.	1000d
K00K	Keokuk, Iowa	5000	W00H	Oswego, N.Y.	1000d	WJOC	Jamestown, N.Y.	250	W00D	Bedford, Va.	1000d
W00L	Madisonville, Ky.	5000	W00I	Troy, N.Y.	1000	WUSJ	Lockport, N.Y.	250	W00E	Norton, Va.	5000d
W00C	Freshburg, Ky.	5000d	W00J	Findlay, Ohio	1000d	WWSA	Massena, N.Y.	250	W00Y	Portsmouth, Va.	5000
KIKS	Sulphur, La.	500	W00K	Wellston, Ohio	5000	WALL	Middletown, N.Y.	250	W00Z	Portage, Wis.	1000d
KUZN	W. Monroe, La.	1000d	W00L	Portland, Oreg.	5000	WIRY	Pittsburg, N.Y.	250			
W00B	Portland, Maine	1000d	W00M	Bellevue, Pa.	500	WJRI	Lenoir, N.C.	250	1360—220.4		
W00R	Worcester, Mass.	5000	W00N	Eric, Pa.	5000	WJTB	Lumberton, N.C.	250	W00V	Jasper, Ala.	1000d
W00M	Dearborn, Mich.	1000d	W00O	Lant Conway, S.C.	1000d	W00X	Oxford, N.C.	250	W00W	Monroeville, Ala.	1000d
KRBI	St. Peter, Minn.	1000d	W00P	Greenville, S.C.	5000	W00Y	Washington, N.C.	250	WELR	Roanoke, Ala.	5000
W00X	Hattiesburg, Miss.	1000d	W00Q	Greenville, Tenn.	1000d	W00Z	Wilmington, N.C.	250	KRUX	Glendale, Ariz.	5000
KFSB	Joplin, Mo.	5000	W00R	Dyersburg, Tenn.	500d	W00A	Winston-Salem, N.C.	250	KLYR	Clarksville, Ark.	5000
KFBG	Great Falls, Mont.	5000	KTRM	Cameron, Tex.	5000	KGPC	Grafton, N.D.	250	KFFA	Helena, Ark.	1000
WJLK	Asbury Park, N.J.	250	KSWB	Rockwell, Tex.	5000	WATG	Ashland, Ohio	250	KVIB	Modesto, Calif.	1000d
W00M	Camden, N.J.	250	KINE	Kingsville, Tex.	1000d	W00B	Athens, Ohio	100	KRCK	Ridgecrest, Calif.	1000d
WVIP	Mt. Kisco, N.Y.	1000d	K00K	Tyler, Tex.	1000d	W00C	Springfield, Ohio	250	KGB	San Diego, Calif.	1000
WTLB	Utica, N.Y.	1000	WBTM	Danville, Va.	5000	WSTV	Stuebenville, Ohio	250	WDRG	Hartford, Conn.	5000
W00A	Asheville, N.C.	5000	WESR	Tasley, Va.	1000d	KIHN	Hugo, Okla.	250	W00S	Jacksonville, Fla.	5000d
W00C	Charlotte, N.C.	1000	KFKF	Bellevue, Wash.	1000d	K00Y	Okl. City, Okla.	250	WKAT	Miami Beach, Fla.	5000
W00I	Durham, N.C.	1000	WETZ	New Martinsville, W. Va.	1000d	K00O	Corvallis, Ore.	250	WIOD	Sanford, Fla.	500d
KNOX	Grand Forks, N.Dak.	5000	WHBL	Sheboygan, Wis.	1000d	W00N	Gran. Pass, Oreg.	250	WINT	Winter Haven, Fla.	1000d
WFAH	Alliance, Ohio	1000d	K00E	Love, Lauder, Wyo.	1000	KIHR	Hood River, Oreg.	250	W00A	Asheville, N.C.	5000
KNPT	Newport, Oreg.	1000	1340—232.7			KFIR	North Bend, Oreg.	250	WLBK	DeKalb, Ill.	5000
W00D	Beaufort, Pa.	1000	CFGB	Goose Bay, Nfld.	250	WFBG	Altoona, Pa.	250	WVMC	Mt. Carmel, Ill.	5000
W00S	Ephrata, Pa.	1000	CFSL	Weyburn, Sask.	250	WCVI	Connellsville, Pa.	250	KXGI	Fort Madison, Iowa	1000d
WNAE	Warren, Pa.	5000d	CFYK	Yellow Knife, N.W.Terr.	250	WSAJ	Grove City, Pa.	250	K00J	Sioux City, Iowa	5000
W00D	Kingstree, S.C.	5000d				W00I	Okl. City, Pa.	250	KBTO	El Dorado, Kans.	500d
W00D	Chattanooga, Tenn.	5000				W00P	Philadelphia, Pa.	250	WFLW	Monticello, Ky.	1000d
WDXI	Jackson, Tenn.	5000				W00R	Reading, Pa.	250	K00B	Knoxville, Tenn.	1000d
KZIP	Amarillo, Tex.	1000d				W00S	Wilkes-Barre, Pa.	250	KVIM	New Iberia, La.	1000d
WBR	Dallas, Tex.	5000	CHAD	Amos, Que.	250	W00T	Williamsport, Pa.	250	KTLD	Tallulah, La.	5000
K00L	Yonkers, N.Y.	5000	CHRD	Yonmouth, N.S.	250	W00U	Waco, Tex.	250	W00B	Dundalk, Md.	5000d
W00E	Fairfax, Va.	5000	CHRD	Ormondville, Que.	250	W00V	Charleston, S.C.	250	WLYN	Lynn, Mass.	1000d
W00L	Newport News, Va.	5000	CJQC	Quebec, Que.	250	W00W	Rock Hill, S.C.	250	W00M	Kalamazoo, Mich.	5000
KARY	Prosser, Wash.	1000d	CKOX	Woodstock, Ont.	250	W00X	Sumter, S.C.	250	KLRS	Mountain Grove, Mo.	1000d
WIBA	Madison, Wis.	5000	WKUL	Cullman, Ala.	250	KJVD	Huron, S.D.	250	W00N	Newtown, N.J.	5000
			W00J	Florence, Ala.</							

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KLGR	Redw. Falls, Minn.	100	KIMO	Independence, Mo.	1000d	WPEP	Taunton, Mass.	1000d	WALB	Albany, Ga.	1000
WLOX	Bloom, Miss.	250	WLAC	Nashville, Tenn.	5000d	WDEW	Westfield, Mass.	1000d	WLAJ	Lafayette, Ga.	5000d
WLD	Cleveland, Miss.	250	KCTX	Chidress, Tex.	250d	WMRP	Flint, Mich.	1000d	WNMP	Winston, Ill.	1000d
WHOC	Philadelphia, Miss.	250	KSTV	Stephenville, Tex.	250d	WURF	Grand Rapids, Mich.	1000d	WQUB	Galesburg, Ill.	5000d
WELQ	Tupelo, Miss.	250	KGSA	Spokane, Wash.	5000d				WGEE	Indianapolis, Ind.	5000d
WVIM	Vicksburg, Miss.	250	WAUX	Waukesha, Wis.	250d	KMRS	Morris, Minn.	1000d	WPCC	Mid. Vernon, Ind.	500d
KDMO	Carthage, Mo.	250				KLEX	Lexington, Mo.	250d	KWBG	Boone, Iowa	500d
KTRT	Rolla, Mo.	250	1520—197.4			WFLR	Dundee, N.Y.	1000d	KVGB	Great Bend, Kans.	5000
KDRO	Sedalia, Mo.	250	KACY	Port Hueneke, Calif.	250	WBUZ	Fredonia, N.Y.	250d	WLBK	Lebanon, Ky.	1000d
KBOW	Butte, Mont.	250	WHOW	Clinton, Ill.	1000d	WNCA	Siler City, N.C.	1000d	KEVL	White Castle, La.	1000d
KVCK	Wolf Point, Mont.	250	KSIB	Creston, Iowa	1000d	WOT	Campbell, Ohio	250d	WTVB	Coldwater, Mich.	5000
KBON	Omaha, Neb.	250	WKWB	Buffalo, N.Y.	5000d	WCLW	Mansfield, Ohio	250d	WDQG	Marine City, Mich.	1000d
WLDB	Atlantic City, N.J.	250	WBIT	Minneapolis, N.Y.	250d	WPTW	Piqua, Ohio	250d	WVAV	Van Wert, Ohio	5000d
KRSN	Los Alamos, N.Mex.	250	KOMA	Oklahoma City, Okla.	5000d	KTAT	Frederick, Okla.	250d	WKJ	Jackson, Miss.	5000d
KRTN	Raton, N.Mex.	250	KGON	Oregon City, Oreg.	1000d	KBWC	Forest Grove, Oreg.	1000d	KDEX	Dexter, Mo.	1000d
WCSS	Amsterdam, N.Y.	250	WWWV	Rio Piedras, P.R.	250	KOHU	Hermiston, Oreg.	1000d	KPRS	Kansas City, Mo.	1000d
WBTA	Batavia, N.Y.	250				WBUX	Doylestown, Pa.	1000d	KMAM	Tulorosa, N.Mex.	1000d
WKNY	Kingston, N.Y.	250	1530—196.1			WAKU	Latrobe, Pa.	1000d	WEHH	Elmira Heights, N.Y.	500d
WICY	Malone, N.Y.	250	KFBK	Sacramento, Calif.	5000d	WMLP	Milton, Pa.	1000d	WNYS	Salamanca, N.Y.	1000d
WDLC	Port Jervis, N.Y.	250	WCYK	Cincinnati, Ohio	5000d	WFGN	Gatney, S.C.	250d	WGTC	Fresno, N.C.	5000d
WOLF	Syracuse, N.Y.	250	KGBT	Harlingen, Tex.	5000d	WLSL	Loris, S.C.	1000d	WAKR	Akron, Ohio	5000
WSSB	Durham, N.C.	250				WHLP	Centerville, Tenn.	1000d	WSRW	Hillsboro, Ohio	500d
WFLB	Fayetteville, N.C.	250	1540—195.0			WCLE	Cleveland, Tenn.	1000d	KHEN	Henryetta, Okla.	500d
WLOE	Leaksville, N.C.	250	ZNS	Nassau, B.W.I.	5000	WTRB	Ripley, Tenn.	250d	KTIL	Tillamook, Oreg.	250
WRNB	New Bern, N.C.	250	KPOL	Los Angeles, Calif.	1000d	KZL	Muleshoe, Tex.	250d	WXRF	Guayama, P.R.	1000
WSTP	Salisbury, N.C.	250	WSMI	Litchfield, Ill.	1000d	KTER	Terrell, Tex.	250d	WCBG	Chambersburg, Pa.	5000d
KNDK	Hettinger, N.Dak.	250	WBIL	Brooklyn, Ind.	250d	KWCR	Coal Salt Lake City, Utah	500d	WDRF	Custer, Pa.	1000d
KOVC	Valley City, N.Dak.	250	WLDI	LaPorte, Ind.	250d	WYTI	Rocky Mount, Va.	500d	WABC	Auburn, S.C.	5000
WBEX	Chillicothe, Ohio	250	KXEL	Waterloo, Iowa	5000d	WEER	Warrenton, W.Va.	500d	WACA	Camden, S.C.	1000d
WSRS	Cleveland Hgts., Ohio	250	KNEK	McPherson, Kans.	250d	WAPL	Appleton, Wis.	1000d	WDBL	Springfield, Tenn.	1000d
WOHI	E. Liverpool, Ohio	250	KLIC	Parsons, Kans.	250d				KGAS	Carthage, Tex.	1000d
WMOA	Marietta, Ohio	250	WDON	Wheaton, Md.	250d	1580—189.2			KERC	Eastland, Tex.	500d
WWRN	Marion, Ohio	250	WPRR	Albany, N.Y.	5000d	CBJ	Chicoutimi, Que.	1000d	KYOK	Houston, Tex.	5000
KWRW	Guthrie, Okla.	100	WIFM	Elkin, N.C.	250d	WJHB	Taladeaga, Ala.	1000d	KCBD	Lubbock, Tex.	1000
KBIX	Muskogee, Okla.	250	WJMO	Cleveland, Ohio	1000d	KPCA	Marked Tree, Ark.	250d	KEUS	Mexia, Tex.	500d
KBKR	Baker, Oreg.	250	WJMJ	Philadelphia, Pa.	1000d	KWIP	Merced, Calif.	500d	KANN	Anniston, Ala.	1000d
KBNR	Roseburg, Oreg.	250	WPTS	Pittston, Pa.	1000d	KDAY	Santa Monica, Calif.	1000d	WZLZ	Richmond, Va.	5000d
KBZY	Salem, Oreg.	250	WPME	Punkasutwey, Pa.	1000d	KPIK	Colorado Sprgs., Colo.	5000d	KTIX	Seattle, Wash.	5000d
WESB	Bradford, Pa.	250	WADK	Newport, R.I.	1000d	WJL	Ft. Lauderdale, Fla.	1000	WSWV	Platteville, Wis.	1000d
WAZL	Hazleton, Pa.	250	KCUL	Ft. Worth, Tex.	1000d	WIOK	Mount Dora, Fla.	1000d	WTRW	Two Rivers, Wis.	1000d
WARD	Johnstown, Pa.	250	KGBC	Galveston, Tex.	1000	WCLS	Columbus, Ga.	1000d	1600—187.5		
WLAN	Lancaster, Pa.	250	KIWW	San Antonio, Tex.	250d	WLBA	Gainesville, Ga.	5000d	CHVC	Niagara Falls, Ont.	5000
WBCB	Levittown, Pa.	250	WTKM	Hartford, Wis.	500d	WDQN	DuQuoin, Ill.	250d	WEUP	Huntsville, Ala.	1000d
WRRF	Lewiston, Pa.	250	1550—193.5		WBBA	Pittsfield, Ill.	250d	WAPX	Montgomery, Ala.	1000	
WMGW	Meadville, Pa.	250	CBE	Windsor, Ont.	1000d	WKID	Urbana, Ill.	250d	WST	Fresno, Calif.	1000d
WNBT	Wellsville, Pa.	250	WAAY	Huntsville, Ala.	5000	WCNB	Connerville, Ind.	250d	KWOW	Pomona, Calif.	1000d
WMDD	Fajardo, P.R.	250	KOBY	San Fran., Calif.	1000d	WJVA	South Bend, Ind.	250d	KUBA	Yuba City, Calif.	1000
WGD	Chester, S.C.	250	KENT	Shreveport, La.	1000	WAMW	Washington, Ind.	250d	KLAK	Lakewood, Colo.	1000
WNRB	Greenville, S.C.	250	KRES	St. Joseph, Mo.	5000	KCHA	Charles City, Iowa	250d	WKEN	Dover, Del.	500d
KORN	Mitchell, S.Dak.	250	WLOA	Bradnock, Pa.	1000d	WFMA	Davenport, Iowa	250d	KTKX	Atlantic Beach, Fla.	1000d
WOPJ	Bristol, Tenn.	250	WBSC	Bennetsville, S.C.	1000d	KBSN	Denison, Iowa	500d	WKWF	Key West, Fla.	500
WDXB	Chattanooga, Tenn.	250	1560—192.3		WXXL	Manchester, Ky.	250d	WGOA	Winter Garden, Fla.	1000d	
WJMJ	Lewisburg, Tenn.	250	CFRS	Simcoe, Ont.	250d	WPKY	Princeton, Ky.	250d	WST	Eminence, Mo.	500d
WDXL	Lexington, Tenn.	250	KPMC	Bakersfield, Calif.	1000d	KLVU	Haynesville, La.	250d	WBTO	Linton, Ind.	500d
WATO	Oak Ridge, Tenn.	250	WBYS	Canton, Ill.	250d	KLOU	Lake Charles, La.	1000	WARU	Peru, Ind.	1000d
KNOW	Austin, Tex.	250	KSWI	Council Bluffs, Iowa	500d	WPGC	Bradbury Hgts., Md.	1000d	KLGA	Algonia, Iowa	5000d
KIBL	Beeville, Tex.	250	WQXR	New York, N.Y.	5000d	WFMF	Fitchburg, Mass.	1000d	KCRG	Cedar Rapids, Iowa	5000
KBST	Big Spring, Tex.	250	WTNS	Coshocton, Ohio	1000d	WAMY	Amory, Miss.	500d	KMDD	Ft. Scott, Kans.	500d
KHUZ	Borger, Tex.	250	WTO	Toledo, Ohio	1000d	WGLC	Centreville, Miss.	1000d	WNES	Central City, Ky.	500d
KNEL	Brady, Tex.	250	WENA	Bayamon, P.R.	250	WESY	Leland, Miss.	250d	WTL	Empire, N.Y.	500d
KSAM	Huntsville, Tex.	250	KHBR	Hillsboro, Tex.	250d	KBIA	Columbia, Mo.	250d	KFNV	Ferriday, La.	1000d
KVOZ	Laredo, Tex.	250	1570—191.1		KNIM	Maryville, Mo.	250d	KFLT	Golden Meadow, La.	1000d	
KVQG	Littlefield, Tex.	250	CHUB	Nanaimo, B.C.	1000d	WCNV	Washington, N.J.	500d	KLVI	Vivian, La.	500d
KPLT	Paris, Tex.	250	CFRY	Portage la Prairie, Manitoba	250d	KHAM	Albuquerque, N.Mex.	1000d	WINX	Rockville, Md.	1000d
KGKB	Tyler, Tex.	250	CFBI	Sidney, N.S.	1000	WPAC	Patchogue, N.Y.	5000d	WBOS	Brookline, Mass.	5000
KVVC	Vernon, Tex.	250	CFOR	Orillia, Ont.	1000	KZKY	Albemarle, N.C.	250d	WTYM	East Longmeadow, Mass.	5000d
KVOG	Ogden, Utah	250	WCRL	Oneonta, Ala.	250d	WTVN	Tryon, N.C.	250d	WHRY	Ann Arbor, Mich.	1000
WIK	Newport, Vt.	250	WRWJ	Seima, Ala.	1000d	WKLO	Columbus, Ohio	1000d	WTRU	Muskegon, Mich.	5000
WVCA	Capecor, Va.	250	WRCV	Lodi, Calif.	1000d	KLTR	Blackwell, Okla.	250d	WKDL	Clarksdale, Miss.	1000d
WVEC	Hampton, Va.	250	KACE	Riverside, Calif.	1000d	WCQY	Columbia, Pa.	500d	WLAW	Laurel, Miss.	5000d
WAYB	Waynesboro, Va.	250	KLOV	Loveland, Colo.	250d	WANB	Waynesburg, Pa.	250d	KATZ	St. Louis, Mo.	5000
KBRO	Bremerton, Wash.	250	WTFB	Aburndale, Fla.	1000d	WYCL	York, S.C.	1000d	KTTN	Trenton, Mo.	500d
KLOG	Kelso, Wash.	250	WJWE	Ward Ridge, Fla.	250d	WMSR	Manchester, Tenn.	1000d	WONG	Oneida, N.Y.	1000d
KENE	Toppensish, Wash.	250	WOKZ	Alton, Ill.	1000d	WTUC	Union City, Tenn.	250d	WRL	Woodside, N.Y.	1000d
KTEL	Walla Walla, Wash.	250	WFRE	Freeport, Ill.	1000d	KGAF	Gainesville, Tex.	250d	WGIV	Charlotte, N.C.	1000d
WHMS	Charleston, W.Va.	250	WBEE	Harvey, Ill.	1000d	KIRT	Mission, Tex.	1000d	WIDU	Fayetteville, N.C.	1000d
WTCB	Fairmont, W.Va.	250	WTAY	Robinson, Ill.	250d	KTLU	Rusk, Tex.	500d	WFRG	Reidsville, N.C.	1000
WLOH	Princeton, W.Va.	250	WLOF	Frankfort, Ind.	250d	KWED	Seguin, Tex.	1000d	WBLV	Springfield, Ohio	1000d
WGEZ	Beloit, Wis.	250	WAWK	Kendallville, Ind.	1000d	KEVA	Shamrock, Tex.	500d	KUSH	Cushing, Okla.	1000d
WLXC	LaCrosse, Wis.	250	WLRB	Low Albany, Ind.	1000d	WFLA	Daniels, Tex.	5000d	KASH	Evans, Oreg.	1000
WLCM	Medford, Wis.	250	KMCD	Fairfield, Iowa	250d	WUPV	Pulaski, Va.	5000d	WHOL	Allentown, Pa.	500d
WOSH	Oshkosh, Wis.	250	KJFJ	Webster City, Iowa	250d	WPTN	Watertown, Wis.	250d	WEZN	Elizabethtown, Pa.	5000
KIML	Gillette, Wyo.	250	KNDY	Marysville, Kans.	250d	1590—188.7		WFIS	Fountain Inn, S.C.	1000d	
KTRT	Thermopolis, Wyo.	250	KWSY	Pratt, Kans.	250d	WATM	Atmore, Ala.	1000d	WUGS	N. Augusta, S.C.	500
KGOS	Torrington, Wyo.	250	WVAB	Abile, La.	500d	WVNA	Tusumbia, Ala.	5000d	WKBJ	Milan, Tenn.	1000d
			WKKS	Vanceburg, Ky.	250d	KPBA	Pine Bluff, Ark.	1000d	KBOR	Brownsville, Tex.	1000
1500—199.9			WMBL	Abile, La.	500d	KJSO	San Jose, Calif.	1000	KWEL	Midland, Tex.	1000
CHUC	Port Hope, Ont.	1000	KLLA	Leesville, La.	250d	KUDU	Ventura, Calif.	1000	KCFH	Cuero, Tex.	500d
KXRX	San Jose, Calif.	1000	KMAR	Winsboro, La.	500d	WBRY	Waterbury, Conn.	5000	KMAE	McKinney, Tex.	1000
WTOP	Washington, D.C.	5000d	WAQE	Towson, Md.	1000d	WILZ	St. Petersburg Beach, Fla.	1000d	KGOT	Orange, Tex.	1000
WJBK	Detroit, Mich.	1000d				WDAT	S. Daytona Beh., Fla.	1000d	KBBC	Centerville, Utah	1000d
KSTP	St. Paul, Minn.	5000d							WBDF	Virginia Gch., Va.	1000d
KTXO	Sherman, Tex.	250							WHWH	Whiting, W.Va.	5000d
									WCWC	Ripon, Wis.	5000d
1510—199.1											
CKOT	Tillsonburg, Ont.	1000d									
KASK	Ontario, Calif.	250d									
KTIM	San Rafael, Calif.	1000d									
KUDY	Littleton, Colo.	1000d									
WKAI	Macomb, Ill.	250d									
WMEX	Boston, Mass.	5000									

Watch for Volume Eight of the RADIO-TV EXPERIMENTER

50 new projects for electronics experimenters! Plus the latest revision of White's Radio Log
On Sale September 1st (Handbook No. 562, 75c)

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Burns, Oreg.	WDOT 1400	Charlottetown, P.E.I.	WELK 1010	Colonial Heights, Va.	WPVA 1290	The Dalles, Oreg.	KSXY 800
Butler, Pa.	WJOY 1230 A		WINA 1400 M	Colorado City, Tex.	KVMC 1320	Dalton, Ga.	WFAA 1190
Butte, Mont.	KRNS 1230	Chatham, Ont.	CFCY 630	Colo. Sprgs., Colo.	KRDO 1240	Danbury, Conn.	WFAA 570 A
	WBUT 1050	Chatanooga, Tenn.	WAGC 1450 M		KPKI 1580	Danville, Ill.	WFAA 520 N
	WISR 680	Cheboygan, Mich.	WAFD 1500 A		KVKS 1300 C	Danville, Ky.	KBCD 450 N
	KBOW 1490 C	Cheektowaga, N.Y.	WNIA 1230		KWBY 740	Darlington, S.C.	KRMW 1300 A
	KOPR 550 M	Chehails, Wash.	KITI 1420		KYSN 1460 M	Davenport, Iowa	KODL 1440 A
	KXLF 1370	Chelan, Wash.	KDZ 1240		WAIN 1270	Dawson, Ga.	WBLJ 1230 M
Cadillac, Mich.	WATT 1240 M	Cheraw, S.C.	WCRE 1420		WCJU 450 M	Dawson Creek, B.C.	WRCD 1430
Caguas, P.R.	WNEL 1450	Chester, Pa.	WDRF 1590		KFRU 1400 A	Dayton, Ohio	WLAD 800
	WRDL 1450	Chester, Pa.	WVCH 740		KBIA 1500	Dayton, Tenn.	WDAN 980
	WVJP 1110	Cheyenne, Wyo.	WG20 1490		WOS 560 N	Daytona Beach, Fla.	WHIR 1230 M
Cairo, Ill.	WGRA 790	Chicago, Ill.	WFCB 1240 A		WCS 400 A	Daytona Beach, Fla.	WBTM 1330 A
Cairo, Ill.	WKRO 1490		WVAD 1370 M		WMS 1320 C		WDVA 1250 M
Calderwell, Idaho	KGIL 800		WVAF 1370 M		WNOK 1230		WILA 1580
Calera, Ala.	WAYE 1370		WVAG 950		WOIC 1470		WIDR 1350
Calgary, Alta.	KICO 1490		WVAT 820		WJGD 2280		WKDM 1050
	CFAC 960		WVBB 780 C		WKRM 1340		WOC 1420 N
	CFCN 1060		WVBC 820		WRBL 1420 C		KFMA 1580
	CKXL 1140		WVCF 1000		WGBA 1270 M		KSTT 1170 M
Calhoun, Ga.	WCGA 900		WVCR 1240		WCLS 1580		WDWD 990
Camas, Wash.	WFLA 1480		WVCD 820		WCSJ 1010		CJDC 1350
Cambridge, Md.	WCEM 1240		WVCE 1240		WACR 1050		WHIO 1290 C
Cambridge, Mass.	WTAD 740 A		WVCF 1000		WCBJ 550 M		WHIO 1290 C
Cambridge, Ohio	WILE 1270		WVCL 1000		WCBS 1300		WING 1410
Camden, Ark.	KAMD 910		WVCM 1400		WCBS 550 M		WJVS 980
Camden, N.J.	WCAM 1310		WVCO 1240		WCS 400 A		WVNT 1210
	WKDN 800		WVCP 1280		WMI 920		WDNT 1280
Camden, S.C.	WACA 1590		WVCS 1300		WOSU 820		
Camden, Tenn.	WCFL 1220		WVCT 1420		WTVN 610		
Camerton, Tex.	KMIL 1330		WVDB 1150		WVVO 1580		
Camilla, Ga.	WCLB 1220		WVDC 1240		WVW 1340		
Campbell, Ohio	WHOT 1570		WVDE 1240		WVX 1340		
Campbellville, Ky.	WTCO 1450		WVDF 1240		WVY 1340		
Campbelltown, N.B.	CKNB 950		WVDS 1240		WVZ 1340		
Camrose, Alta.	CFCW 1230		WVDT 1240		WVZ 1340		
Canon City, Colo.	KRNL 1400		WVDF 1240		WVZ 1340		
Canonsburg, Pa.	WCAN 1240		WVDF 1240		WVZ 1340		
Canton, Ga.	WCHK 1240		WVDF 1240		WVZ 1340		
Canton, Ill.	WBYS 1560		WVDF 1240		WVZ 1340		
Canton, Miss.	WDOB 1370		WVDF 1240		WVZ 1340		
Canton, N.C.	WWTI 970		WVDF 1240		WVZ 1340		
Canton, Ohio	WAND 900		WVDF 1240		WVZ 1340		
	WCWM 1060		WVDF 1240		WVZ 1340		
	WHBC 1480 A		WVDF 1240		WVZ 1340		
Cape Girardeau, Mo.	KFVS 960		WVDF 1240		WVZ 1340		
	KGMO 1220		WVDF 1240		WVZ 1340		
	WCIL 1020		WVDF 1240		WVZ 1340		
Carbondale, Ill.	WCIL 1020		WVDF 1240		WVZ 1340		
Carbondale, Pa.	WCIL 1020		WVDF 1240		WVZ 1340		
Caribou, Maine	WFST 600		WVDF 1240		WVZ 1340		
Carlisle, Pa.	WHYL 960		WVDF 1240		WVZ 1340		
Carlsbad, N.Mex.	WCAR 1240		WVDF 1240		WVZ 1340		
	KPBM 740		WVDF 1240		WVZ 1340		
Carmel, Calif.	KTEE 1410		WVDF 1240		WVZ 1340		
Carmi, Ill.	WROY 1460		WVDF 1240		WVZ 1340		
Carrizo Springs, Tex.	KBEEN 1450		WVDF 1240		WVZ 1340		
	KCIM 1380		WVDF 1240		WVZ 1340		
Carroll, Iowa	WRAL 960		WVDF 1240		WVZ 1340		
Carrollton, Ala.	WLBW 1100		WVDF 1240		WVZ 1340		
Carrollton, Ga.	WLBW 1100		WVDF 1240		WVZ 1340		
Carson City, Nev.	KPTL 1400		WVDF 1240		WVZ 1340		
Cartersville, Ga.	WBHF 1450 M		WVDF 1240		WVZ 1340		
Carthage, Ill.	WCAD 990		WVDF 1240		WVZ 1340		
Carthage, Mo.	KDZO 1490		WVDF 1240		WVZ 1340		
Carthage, Tex.	KCAS 1590		WVDF 1240		WVZ 1340		
Caruthersville, Mo.	KCRJ 1370		WVDF 1240		WVZ 1340		
Casa Grande, Ariz.	KPIN 1260		WVDF 1240		WVZ 1340		
Casper, Wyo.	KSPR 1470 C		WVDF 1240		WVZ 1340		
	KATI 1400		WVDF 1240		WVZ 1340		
	KVOC 1230 A-M		WVDF 1240		WVZ 1340		
Cayce, S.C.	WCAY 620		WVDF 1240		WVZ 1340		
Cedar City, Utah	WCUB 590		WVDF 1240		WVZ 1340		
Cedar Rapids, Iowa	KCRG 1600 M		WVDF 1240		WVZ 1340		
	KPIG 1450		WVDF 1240		WVZ 1340		
	WMT 600 C		WVDF 1240		WVZ 1340		
Cedartown, Ga.	WGAA 1340		WVDF 1240		WVZ 1340		
Center, Tex.	KDET 930		WVDF 1240		WVZ 1340		
Centerville, Iowa	KCOG 1400		WVDF 1240		WVZ 1340		
Centerville, Tenn.	WESA 1570		WVDF 1240		WVZ 1340		
Centerville, Utah	KBBC 1600		WVDF 1240		WVZ 1340		
Central City, Ky.	WENS 1600		WVDF 1240		WVZ 1340		
	WMTA 1380		WVDF 1240		WVZ 1340		
Centralia, Ill.	WCNT 1210		WVDF 1240		WVZ 1340		
Centralia & Chehalis, Wash.	KELA 1470		WVDF 1240		WVZ 1340		
Centreville, Miss.	KCSA 1580		WVDF 1240		WVZ 1340		
Chadron, Neb.	KCSR 1450		WVDF 1240		WVZ 1340		
Chambersburg, Pa.	WCHA 800		WVDF 1240		WVZ 1340		
	WCBG 1590		WVDF 1240		WVZ 1340		
Champaign, Ill.	WDWS 1400		WVDF 1240		WVZ 1340		
Chanute, Kans.	KCRB 1460		WVDF 1240		WVZ 1340		
Chapel Hill, N.C.	WCHE 1350		WVDF 1240		WVZ 1340		
Charleroi, Pa.	WESA 1570		WVDF 1240		WVZ 1340		
Charles City, Iowa	KCHA 1580		WVDF 1240		WVZ 1340		
Charleston, Ill.	WEIC 1270		WVDF 1240		WVZ 1340		
Charleston, Mo.	KCHR 1350		WVDF 1240		WVZ 1340		
Charleston, S.C.	WCSC 1390 C		WVDF 1240		WVZ 1340		
	WHAN 1340 A-M		WVDF 1240		WVZ 1340		
	WTP 730		WVDF 1240		WVZ 1340		
	WQSN 1450		WVDF 1240		WVZ 1340		
	WTMA 1250 N		WVDF 1240		WVZ 1340		
Charleston, W.Va.	WCWA 1400		WVDF 1240		WVZ 1340		
	WCBS 580 C		WVDF 1240		WVZ 1340		
	WHMS 1490 A		WVDF 1240		WVZ 1340		
	WKAZ 950		WVDF 1240		WVZ 1340		
	WTP 1240 M		WVDF 1240		WVZ 1340		
Charlotte, Mich.	WCER 1390		WVDF 1240		WVZ 1340		
Charlotte, N.C.	WBT 1110 C		WVDF 1240		WVZ 1340		
	WAYS 610 A		WVDF 1240		WVZ 1340		
	WGIV 1600		WVDF 1240		WVZ 1340		
	WKTC 1310		WVDF 1240		WVZ 1340		
	WST 930 M		WVDF 1240		WVZ 1340		
	WST 1240 N		WVDF 1240		WVZ 1340		
	WVOK 1480		WVDF 1240		WVZ 1340		
Charlotte Amalie, V.I.	WST 930 M		WVDF 1240		WVZ 1340		
Charlottesville, Va.	WSTA 1340		WVDF 1240		WVZ 1340		
	WCHV 1260 A		WVDF 1240		WVZ 1340		

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Dubuque, Iowa	KDTH	1370	A
Duluth, Minn.	WDQB	1490	M
Dumas, Tex.	WRFX	1080	C
Duncan, Okla.	KRHD	1350	M
Dundalk, Md.	WAYE	860	
Dundee, N.Y.	WBBB	1360	
Dunkirk, N.Y.	WFLR	1570	
Dunn, N.C.	WDOE	1410	
Du Quoin, Ill.	WCKB	780	
Durango, Colo.	WDQP	1580	
Durham, N.C.	WDNC	620	C
Dyersburg, Tenn.	WSSR	1490	
Eagle Pass, Tex.	WTIK	1310	A
Eastland, Tex.	WDSG	1450	
E. Lansing, Mich.	KEPS	1270	
E. Liverpool, Ohio	WELP	1360	
East Longmeadow, Mass.	KERC	1590	
E. Palatka, Ga.	WKAR	870	
E. St. Louis, Ill.	WOHI	1490	A
Easton, Pa.	WTJM	1000	
Eaton, Pa.	WTJM	1000	
Eatonville, N.J.	WAMV	1490	M
Eau Claire, Wis.	WEEX	1230	
Eau Gallie, Fla.	WEST	1400	N
Edenton, N.C.	WHTG	1410	
Edinburg, Tex.	WEAU	790	N
Edmonds, Wash.	WEAU	790	N
Edmonton, Alta.	WECL	1090	M
Edmundston, N.C.	WMEG	920	
Emingham, Ill.	WCDJ	1260	
Elberton, Ga.	KURV	710	
El Cajon, Calif.	KGDN	630	
El Campo, Tex.	CKBT	1010	
El Centro, Calif.	CHFA	680	
El Dorado, Ark.	CJCA	930	
Elkhart, Ind.	CKUA	560	
Elkins, N.C.	CJEM	570	
Elkins, W.Va.	WCRG	1000	
Elko, Nev.	WSGC	1400	
Elmhurst, Wash.	KDEO	910	A
Elmira, N.Y.	KULP	1390	
Elmira Heights-Horseheads, N.Y.	KXO	1230	M
El Paso, Tex.	KAMP	1430	
El Paso, Tex.	KROD	600	C
El Paso, Tex.	KHEP	920	
El Paso, Tex.	KOYE	1150	
El Paso, Tex.	KSET	1340	M
El Paso, Tex.	KTSM	1380	N
El Paso, Tex.	WELY	1450	
El Paso, Tex.	KELY	1230	
El Paso, Tex.	WEOL	930	
El Paso, Tex.	WESB	1600	
El Paso, Tex.	WROE	1400	
El Paso, Tex.	WEVA	860	
El Paso, Tex.	WLEM	1250	
El Paso, Tex.	WENE	1430	A
El Paso, Tex.	KGMC	1150	
El Paso, Tex.	KCRC	1390	A
El Paso, Tex.	KGWA	960	M
El Paso, Tex.	WWRB	1600	
El Paso, Tex.	WGSA	1310	
El Paso, Tex.	KULF	730	
El Paso, Tex.	WERC	1260	A
El Paso, Tex.	WICU	1330	N
El Paso, Tex.	WJET	1400	
El Paso, Tex.	WLEU	1420	
El Paso, Tex.	WWRB	1600	
El Paso, Tex.	WDBC	1600	
El Paso, Tex.	KOWN	1450	
El Paso, Tex.	KLIL	1340	
El Paso, Tex.	WCPH	1220	
El Paso, Tex.	WULA	1240	M
El Paso, Tex.	KORE	1450	M
El Paso, Tex.	KASH	1600	A
El Paso, Tex.	KUGN	590	N
El Paso, Tex.	KEUN	1490	M
El Paso, Tex.	KINS	980	C
El Paso, Tex.

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
	KDUB 1340	McComb, Miss.	WHNY 1250 A	Moncton, N.B.	CBAF 1300	Natchez, Miss.	WVOL 1470
	KFYD 790 C	McCook, Nebr.	WAPF 980	Monett, Mo.	CKCW 1220		WMIS 1240 N
	KLL 1460 M	McGehee, Ark.	KBRL 1300 M	Monmouth, Ill.	KRMD 990		WNAT 1450 M
Ludington, Mich.	KSEL 950 A	McKeesport, Pa.	KVSA 1220	Monroe, Ga.	WRAM 1330	Natchitoches, La.	KNOC 1450 M
	WKLA 1450 A		WEDD 100 C	Monroe, La.	WMRE 1490	Needles, Calif.	KFSF 1340
	KRBA 1340 A		WCKC 1360		KMLB 140 A-N	Neenah, Wis.	WNAM 1280
	KTRF 1420 M	McKenzie, Tenn.	WHDM 1440		KLIC 1230 M	Neilsen, Wis.	WCCN 1370
Lumberton, N.C.	WAGR 1480	McKinney, Tex.	KMAE 1600		KNOE 1390	Nelson, B.C.	CKLN 1390
	WTSB 1340 M	McMinnville, Ore.	KNCM 1200	Monroe, Mich.	WMIC 560	Neon, Ky.	WNKY 1480
	WLVA 590 A	McMinnville, Tenn.	WBMC 960	Monroe, N.C.	WMAP 1060	Neosho, Mo.	KBTN 1420
Lynchburg, Va.	WWD 1390 M-N		WM 1230 M	Monroe, Wis.	WEKZ 1260	Nevada, Mo.	KNEM 1240
	WBRG 1050 A	McPherson, Kans.	KNEK 1540	Monroeville, Ala.	WMFC 1360	New Albany, Ind.	WLRP 1570
	WBYN 1450 A	McRae, Ga.	KDAX 1410	Monterey, Calif.	WMCB 630	New Albany, Miss.	WNAU 1470
Lynn, Mass.	WKAI 1510	Meadville, Pa.	WMGW 1490		KMBY 1240 C	Newark, N.J.	WNTA 970
Macomb, Ill.	WBML 1240	Medford, Mass.	WHIL 1430	Montevideo, Minn.	KDMA 1450 A		WACK 1420
Macon, Ga.	WCYR 900	Medford, Oreg.	KMED 1440 N	Monte Vista, Colo.	KSLV 1240		WAB 1280
	WIBB 1280		KBOY 730	Montgomery, Ala.	WBAM 740		WNRJ 1430
	WMAZ 940 C	Medford, Wis.	KYJC 1230 A-C		WCOV 1170 C		WVJN 620
	WNEX 1400 A-M	Medicine Hat, Alta.	WIGM 1490 M		WAPX 1600 A	Newark, Ohio	WCLT 1430
	WBMC 1400		CHAT 1270		WHYY 1440 N	New Bedford, Mass.	WBMS 1420
	KHOT 1250		WMNB 1240 M		WRMA 950		WBH 1340 M
Macon, Miss.	WMAF 1230	Melbourne, Fla.	WHBQ 560 M	Montgomery, W.Va.	WMON 1340 M	New Bern, N.C.	WHIT 1450 M
Madera, Calif.	WYTH 1250	Memphis, Tenn.	WHER 1430		WMON 1340 M	Newberry, S.C.	WRNB 1490
Madison, Fla.	WORX 1270		WMC 790 N	Monticello, Ark.	KHBM 1430	New Britain, Conn.	WKGB 1420
Madison, Ga.	WHA 970		WDLA 1070	Monticello, Ky.	FWLW 1360	New Britain, Conn.	WHAY 910
Madison, Ind.	WIBA 1310 N		WDIA 1070	Montpelier, Que.	CKBM 1490 A		WKBN 840
Madison, Wis.	WISC 1480 A-M		WFPS 580		WSKI 1240	New Brunswick, N.J.	WCTC 1450
	WKOW 1070 C		WHHM 1340 A	Montreal, Que.	CBF 690		WGNV 1220
Madison, Tenn.	WFOW 1430		WLOK 1380		CBM 940 N	Newburgh, N.Y.	WGNV 1220
Madisonville, Ky.	WFNW 730		WREC 600 C		CFCF 600	Newburyport, Mass.	WNBP 1470
	WTTL 1310	Mena, Ark.	KENA 1450		CHLP 1410	New Carlisle, Que.	CHNC 1240
	WSJC 1280	Nenomonie, Mich.	WAGN 1340 A		CJAD 800	Newcastle, N.B.	CKNR 790
Magee, Miss.	KVMA 630 M	Nenomonie, Wis.	WNNE 1360		CJMS 1290	New Castle, Pa.	WKST 1280 M
Magnolia, Ark.	KTCB 1470	Merced, Calif.	KIPW 1380		CKAK 730 C	Newcastle, Wyo.	KASL 1240
Malden, N.Y.	WICY 1490 M	Meriden, Conn.	WMMW 1470	Montrose, Colo.	KUBC 580	New Glasgow, N.S.	CKEK 1230
Malden, Ark.	KBOK 1310	Meridian, Miss.	WCOC 910 C	Montrose, Pa.	WPFL 1250	New Haven, Conn.	WAVZ 1300
Malvern, Ark.	WJNF 1230		WDAL 1330	Moorhead, Minn.	WHIP 1350		WELI 960
Manassas, Va.	WDFR 1370		WNOX 1240	Moosehead, Minn.	KVOX 1280 M		WVLC 1340
Manchester, Conn.	WXL 1580		WOKK 1450 A	Morsejaw, Sask.	CHAB 800	New Iberia, La.	KNC 240
Manchester, Ga.	WFEE 1370		WJIC 1340	Morhead City, N.C.	WMOR 1330		WKVM 1360
Manchester, Ky.	WGIR 610 C	Mesa, Ariz.	KBUZ 1310		WMBL 740	New Kensington, Pa.	WKPA 1150
Manchester, N.H.	WKBH 1240	Metropolis, Ill.	WMOK 920	Morgan City, La.	KMRC 1430	New London, Conn.	WNLC 1490 M
	WMSR 1580	Mexia, Tex.	KBUS 1590	Morgantown, N.C.	WMNC 1430	New Martinsville, W.Va.	WVZ 1330 M
	KSAO 580	Mexico, Mo.	KXEO 1340 M	Morgantown, W.Va.	WVAJ 1440 N	Newman, Ga.	WFOT 1400 N
	KMAN 1350	Mexico, Pa.	WJUN 1220	Morrilton, Ark.	WCLG 1300	New Orleans, La.	WDSU 1280 N
Manistee, Mich.	DZPI 1800 M-C	Miami, Ariz.	KIKO 1340	Morris, Minn.	KMRS 1570		WBW 1230
	DZRH 710 N	Miami, Fla.	WGBR 710 C	Morristown, N.J.	WMTR 1250		WJM 990
Manitou Springs, Colo.	WTFE 1340		WCKR 610 N	Morristown, Tenn.	WCRI 1150 M		WJK 800
	KCMS 1490		WFFC 1220		WMTN 1300		WNDE 1060
Manitowac, Wis.	WCUB 980		WAME 1260	Moscow, Idaho	KRPL 1400		WMSB 1350 A
	WOMT 1240 M		WQIE 1140	Moses Lake, Wash.	KSEM 1470		WNS 1450
	KYSM 1230 N		WMAM 560	Moultrie, Ga.	KWIO 290		WTL 690
	KTOE 1420 A		WSPK 1450		WMGA 1400		WXX 870 C
Manning, S.C.	WYMB 1410		WINZ 940		WMTM 1300		WYFE 600
Marion, La.	KDBC 1360	Miami, Okla.	KGCL 910	Moundsville, W.Va.	WMOD 1370	Newport, Ark.	KNBY 1280
Mansfield, Ohio	WLAN 1400	Miami Beach, Fla.	WMET 1490		WMLR 1360	Newport, Ky.	WNPT 740
	WCLW 1570		WKAT 1360 M-A	Mountain Grove, Mo.	KLRS 1370	Newport, Oreg.	KRPT 1340
	WYTS 1340 M		WBMB 800	Mountain Home, Ar.	KTLO 1490	Newport, R.I.	WADK 1540
Marietta, Ga.	WTOT 980	Michigan City, Ind.	WMS 1420	Mt. Airy, N.C.	WPAQ 740	Newport, Tenn.	WLK 1270
Marietta, Ohio	WFOM 1230	Middlesboro, Ky.	WNK 560		WSDY 1300 M	Newport, Vt.	WIKE 1490
Marion, Ga.	WBIE 1050	Middletown, Conn.	WCN 1150	Mt. Carmel, Ill.	WVMC 1360	Newport News, Va.	WGH 1310 A
Marion, Ind.	WNOA 1490 M	Middletown, N.Y.	WALL 1340	Mt. Clemens, Mich.	WBRB 1430		WYUO 1270
Marion, Ky.	WDOG 1590	Middletown, Ohio	WPFB 910		WBRB 1430	New Rochelle, N.Y.	WFES 1460
Marion, La.	WMAA 1500 N	Midland, Mich.	WMDN 1490		WIDK 1580	New Smyrna Beach, Fla.	FSB 1230 M
Marion, Ill.	WJAM 1310	Midland, Tex.	KCRS 550 A	Mt. Jackson, Va.	WSIG 790	Newton, Iowa	KCOB 1280
Marion, Ind.	WGGH 1150		KJCB 1160	Mt. Kisco, N.Y.	WVIP 1310	Newton, Kans.	KJRG 950
Marion, N.C.	WBAT 1400 C		KWEL 1600	Mt. Pleasant, Mich.	WCEN 1150	Newton, Miss.	WBKN 1410
Marion, N.D.	WMRI 860	Milan, Tenn.	WKAB 1600		WCEN 1150	Newton, N.J.	WNJ 1360
Marion, Ohio	WBRM 1250	Miles City, Mont.	KATL 1340 M	Mt. Pleasant, Tex.	KIMP 960	Newton, N.C.	WNCC 1230
Marion, S.C.	WBR 1490 A	Milford, Del.	WKSB 930	Mt. Shasta, Calif.	KMST 920	New Ulm, Minn.	KNJ 860
Marion, Va.	WNEV 1010	Milford, Mass.	WMRC 1490	Mt. Sterling, Ky.	WMT 1150	New Westminster, B.C.	CKNW 990
Marked Tree, Ark.	KPCA 1580	Milledgeville, Ga.	WMVG 1450	Mt. Vernon, Ill.	WMIX 940		WABC 770 A
Marksville, La.	KAPB 1370	Millington, Tenn.	WHRY 1220	Mt. Vernon, Ind.	WPCO 1590	New York, N.Y.	WBXN 1380
Marquette, Mich.	KMLV 1010	Millville, N.J.	WVBB 1440	Mt. Vernon, Ky.	WRVK 1460		WBXN 1380
Marshall, Mich.	WDMJ 1320 M	Milton, Fla.	WMLP 1570	Mt. Vernon, Ohio	WMVO 1300		WCBS 880 C
Marshall, Mo.	KMMO 1300	Milton, Pa.	WEMP 1250	Mt. Vernon, Wash.	KBCR 1430		WVFD 1330
Marshall, N.C.	WMMH 1460	Milwaukee, Wis.	WFOX 860 M	Muleshoe, Tex.	KJUL 1380		WHOM 1480
Marshall, Tex.	KMHT 1450		WTR 1340		KZOL 1570		WINS 1010
	KADD 1410		WISN 1150 A		WJAY 1280		WLBB 1190
Marshalltown, Iowa	KFBJ 1230		WVH 1250	Muncie, Ind.	WLBC 1340 C		WVGA 570
Marshallville, Wis.	WDLB 1450	Minden, La.	WTK 920	Murfreesboro, Tenn.	WMNS 1450		WVGM 1050
Martin, Tenn.	WCMT 1410	Mineral Wells, Tex.	KORC 1140		WMTS 860		WVNE 1130
	WEPM 1340	Mineola, N.Y.	WKIT 1520	Murphyboro, Ill.	WMTS 860		WVNY 830
	WHEE 1370	Minneapolis, Minn.	KEVE 1440		WMTS 860		WOR 710 M
	WMVA 1450 N		WCO 830	Murray, Ky.	WNBS 1340		WVU 1280
Marysville, Calif.	KMYC 1410 M		WLOI 1330	Murray, Utah	KMUR 1230		WVQR 1360
Marysville, Kans.	KNDY 1570		WMIN 1400	Muscateine, Iowa	KWPC 860		WRCA 680 N
Marysville, Mo.	KNIM 1580		WPBG 1130	Muscle Shoals City, Ala.	WLAY 1450	Niagara Falls, N.Y.	WHLD 1270
Marysville, Tenn.	WCAP 1400		WPDC 980	Muskegon, Mich.	WKBZ 850 A		WJLL 1440
Mason City, Iowa	KGLO 1300 C		WTCN 1280 A		WMU 890	Niagara Falls, Ont.	CHVC 1600
	KRIB 1490		KTIS 900	Muskogee, Okla.	KBIX 1490 A		WNIL 1290
	KSMN 1010	Minot, N.Dak.	KLUN 770		KMU5 1380	Niles, Mich.	WVGA 780
Massena, N.Y.	WMSA 1340 A		KLP 1390 M		WMYB 1450	Nogales, Ariz.	KNOG 1340 C
Massillon, Ohio	WTFG 990		KQDY 1320		WYB 1230 A	Norfolk, Neb.	WTAR 790 C
Matawan, W.Va.	CKBL 1250		KCJ 910 C	Nacogdoches, Tex.	KXSA 660	Norfolk, Va.	WVMS 1050
Mattoon, Ill.	WLBH 1370	Mission, Kans.	KBKC 1480		KFXD 580		WNOR 1230
Matteawan, P.R.	WAE 600	Mission, Tex.	KTRT 1580		CHUB 570		WRAP 850
	WRA 710	Missoula, Mont.	KGV 1290 C		WNAK 730	Norman, Okla.	WNAD 640
	WORA 1150		KXLL 1450 N		KYON 1440		KNOR 1400
	WPR 990	Mitchell, S.Dak.	KORN 1490 M		WNOG 1270	Norristown, Pa.	WNAR 1110
	WTTL 1300	Moab, Utah	KURA 1450		WNRV 990	N. Adams, Mass.	WNAB 1230
	WTKT 1050	Moberly, Mo.	KNCM 1210 C		WOTK 840	N. Augusta, S.C.	WVAG 780
	WNGO 1320	Mobile, Ala.	WALA 1410 N		WVOT 900	N. Battleford, Sask.	CJNB 1460
Mayfield, Ky.	WMY 1420		WAB 1480 A		WSMN 590	North Bay, Ont.	CFCH 600
Mayfield, N.C.	WFTM 1240 M		WKB 840		WVOT 900	North Bend, Oreg.	KFR 1340 C
Mayville, Ky.	KTM 1400		WKR 710 C		WVOT 900	Northfield, Minn.	WCAL 770
McAlester, Okla.	KNED 1150		WMOZ 960		WVOT 900	Northampton, Mass.	WHMP 1400 M
	KRI 910 M	Mobridge, S.Dak.	KOLY 1300		WVOT 900		KNLR 1380
McAllen, Tex.	KCMR 1450	Mouton, Calif.	KTRB 860		WVOT 900		KXLR 1150
McCamey, Tex.			KBEE 970		WVOT 900		
			KFIV 1360 A		WVOT 900		
			WQUA 1230 A		WVOT 900		
			JVKM 1340 M		WVOT 900		

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
North Platte, Nebr.	KVLC 1050 KJLT 1240 N	Palmdale, Calif.	KPAL 1450 KUTY 1470	Pleasanton, Tex.	WBRY 1340 M KBPO 1380	Radcliff, Ky.	WRJN 1400 A WSAC 1470
No. Vancouver, B.C.	CKLG 730 N	Palo Alto, Calif.	KIBE 1220	Pleasantville, N.J.	WDOV 1400	Radford, Va.	WRAD 1460
N. Vernon, Ind.	WOCH 1460	Pampa, Tex.	KPDN 1340 M	Plymouth, Mass.	WPLM 1390	Raleigh, N.C.	WKIX 850 A WPTF 680 N
N. Wilkesboro, N.C.	WKBC 810 WNVA 1350 M	Panama City, Fla.	KHHH 1230 WDLP 590 WPCF 1400 M	Plymouth, Wis.	WPLY 1420		WMSN 570 WRAL 1240 WRIT 990
Norton, Va.	WVNA 1350 M	Panama City Beach, Fla.	WTHR 1480 WSCM 1290	Pocahontas, Ark.	KPOC 1420	Rapid City, S. Dak.	KRTN 1490 A KRSD 1340
Norwalk, Conn.	WNLK 1350	Paragould, Ark.	KDRS 1490	Pocumoke City, Md.	WVDM 540	Raton, N. Mex.	WRBV 1360
Northampton, Conn.	WICH 1310	Paris, Ill.	WPRS 1440	Ponca City, Okla.	KBOW 1600	Ravenswood, W. Va.	WMOV 1360
Norwich, N.Y.	WCNH 970	Paris, Ky.	WKXL 1440	Ponce, P.R.	WBBZ 930 M WPRP 1210	Rawlins, Wyo.	KRAL 1240 M
Oakdale, La.	WKCL 1280	Paris, Tenn.	WTPR 710		WEUC 1420	Raymond, Wash.	KAPA 1340
Oak Grove, La.	WOAY 860	Paris, Tex.	KPLT 1490 A KFVY 1250 WCFE 050		WPAB 550 WLEO 1170 WISO 1260	Raymondville, Tex.	KSOX 1240
Oak Hill, W. Va.	KLX 910	Parkersburg, W. Va.	WPAP 1450 C WCOM 1230 A	Pontiac, Mich.	WPON 1460	Rayville, La.	WEUE 850 A
Oakland, Calif.	KROW 960 KWBR 1310 WOPA 1490	Park Falls, Wis.	WPFJ 1450	Portage, Wis.	WPDR 1350	Reading, Pa.	WHUM 1240 C WRAW 1340 N
Oak Park, Ill.	WATO 1490 M	Parsons, Kans.	KLKC 1540	Portage la Prairie, Man.	CFRY 1570	Redding, Calif.	KRDG 1230 M KPAD 1270
Oak Ridge, Tenn.	WOKE 1290 CHWO 1250 WMPJ 900	Pasadena, Calif.	KALI 1430 KPPC 2440 KXKA 1110 KWKW 1300	Port Alberni, B.C.	KCNM 1450	Red Bluff, Calif.	KBLF 1490
Oakville, Ont.	CHWO 1250	Pasadena, Tex.	KLVL 1480	Portales, N. Mex.	KENM 1450	Red Deer, Alta.	CKRD 850
Ocala, Fla.	WMPJ 900 WTMC 1290 N WHYS 1370	Pasagoula, Miss.	KORD 910	Port Angeles, Wash.	KONP 1450	Redlands, Calif.	KCAL 1410
Oceanside, Calif.	KUDE 1320	Pasco, Wash.	KPKW 1340	Port Arthur, Ont.	CFPA 1230 KOLE 1340 KPAC 1250 M	Red Lion, Pa.	WGCB 1440
Oceano, Tex.	KECK 920 KOSA 1230 KOYL 1310 C KRIG 1140	Paso Robles, Calif.	KPRL 1230 M	Port Arthur, Tex.	KTIP 1450 A CHUC 1500	Redmond, Oreg.	KPRB 1240
Oelwein, Iowa	KOEL 950	Patchogue, L.I., N.Y.	WALK 1370 WPAC 1580	Porterville, Calif.	CHUC 1500	Red Wing, Minn.	KCUE 1250
Ogallala, Nebr.	KOGA 930	Paterson, N.J.	WPAK 930	Port Hope, Ont.	CHUC 1500	Redwood Falls, Minn.	KLGR 1490
Ogden, Utah	KLO 1430 M KVOG 1490	Pauls Valley, Okla.	KVLH 1470	Port Huron, Mich.	WHLS 1450 WTHH 1380 A	Reedsburg, Wis.	WRDB 1400
Ogdenburg, N.Y.	WSLB 1400 M	Pawtucket, R.I.	WPAW 550 A	Portland, Ind.	WDLG 1490	Regina, Sask.	CBK 540 CKBK 620 CKRM 980
Oil City, Pa.	WKRR 1340	Payette, Idaho	KEOK 1450	Portland, N.Y.	WPGW 1440	Reidsville, N.C.	WFRC 1600 A WVFC 1200
Oklahoma City, Okla.	KLPR 1140 KOCC 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peace River, Alta.	CKYL 630	Portland, Maine	WCSD 970 N WGAN 560 C WPT 1210 A WPR 1490 A-M	Remsen, N.Y.	WRM 1480
Okmulgee, Okla.	KHGB 1240	Peos, Tex.	KIUN 1400 M	Portland, Oreg.	KBPS 1450 A KLIG 1290 KEX 190	Reno, Nev.	KOH 630 N KATO 1340 M KOL 920 C KONE 1450 KDOT 230
Old Saybrook, Conn.	WHS 1420	Peekskill, N.Y.	WLNA 1420		KGW 620 A KGIN 970 C KEM 1410	Renton, Wash.	KRKB 1230
Olean, N.Y.	WMSN 1360	Pekin, Ill.	WFSI 1140		KPDQ 800 KPOJ 1330 M KWJ 1080 KXL 750	Rhineland, Wis.	WOBT 1240
Olney, Ill.	WVLD 740	Pell City, Ala.	WFHK 1430	Richfield, Utah	WVCO 1410	Rice Lake, Wis.	WJMC 1240
Olympia, Wash.	KGY 1240 M KITT 1440	Pembroke, Ont.	CHOV 1350	Richland, Wash.	KALE 960	Richfield, Utah	KVC 980
Omaha, Nebr.	KBN 1490 KFAB 1110 N KODO 1420 KOWH 660 KSWI 1560 M-A WOW 590 C	Pendleton, Oreg.	KWRK 1240 A KUBE 1050 KUMA 1290 WBOJ 960	Richland, Wash.	WRCO 1450	Richland, W. Va.	WRIC 1440
Omaha, Wash.	KOMW 680	Pensacola, Fla.	WBRS 1450 C WNVY 1230 WCOA 1370 N WFFA 790	Richlands, Va.	WRIC 1440	Richmond, Ind.	WEKY 1390 A
Oneida, N.Y.	WDRG 1600	Perry, Fla.	WPED 1020	Richmond, Ky.	WRIC 1440	Richmond, Va.	WANT 990 WBBL 1480 WEZL 1590
O'Neill, Nebr.	WOL 1400	Perry, Ga.	WPED 1020	Post, Tex.	KPOS 1370		WLEE 1480 N WLLY 1320
Ontonaga, Ala.	WCR 1570	Perryton, Tex.	WBYN 980	Poteau, Okla.	KLCO 1280	Richmond Hill, Ont.	CJRH 1300
Ontonaga, N.Y.	WDDS 730	Peru, Ind.	WARU 1600	Potsdam, N.Y.	WPDM 1470	Richwood, W. Va.	WMNF 1280
Ontario, Calif.	KASK 1510	Petaluma, Calif.	KAFP 1490	Pottstown, Pa.	WPAZ 1370	Ridgecrest, Calif.	KRKS 1240
Ontario, Oreg.	KSRV 1380	Peterborough, Ont.	CHEX 980	Pottsville, Pa.	WPPA 1360 M WPPA 1360 M	Rimouski, Que.	CJRS 900
Opelika, Ala.	WPHO 1400 A	Petersburg, Va.	WSSV 1240 M	Poughkeepsie, N.Y.	WPPA 1360 M WPPA 1360 M	Rio Piedras, P.R.	WRIO 1320
Opelousas, La.	KSLO 1230	Petersburg, Va.	WSSV 1240 M	Powell, Wyo.	WKIP 1450 A		WWWV 1520
Opp, Ala.	WAMI 860	Peterson, Mich.	WMBN 1340	Poynette, Wis.	WISU 1280	Ripley, Tenn.	WTRB 1570
Opportunity, Wash.	KZUN 630	Phenix City, Ala.	WPCN 1460	Prairie du Chien, Wis.	WRE 940	Ripon, Wis.	WCWC 1600
Orange, Mass.	WCAT 1390	Philadelphia, Miss.	WCAO 1490	Pratt, Kans.	KWSK 1570 N	Riverhead, N.Y.	KRV 1390
Orange, Tex.	KOGT 1600	Philadelphia, Pa.	WDAU 1210 C WDAU 1480 WFIL 560 A WHAT 1340 WIBG 960	Prescott, Ariz.	KYCA 1490 N KNOT 1450 KZOK 1340	Riverside, Calif.	KPRO 1440 KACE 1570
Orange, Va.	WJMA 1340	Philadelphia, Pa.	WDAU 1210 C WDAU 1480 WFIL 560 A WHAT 1340 WIBG 960	Presque Isle, Me.	WAGM 1450	Riverton, Wyo.	KJRL 1450 M
Oranburg, S.C.	WDIX 1150 A WNTD 920	Philadelphia, Pa.	WDAU 1210 C WDAU 1480 WFIL 560 A WHAT 1340 WIBG 960	Preston, Idaho	KPST 1340	Riviere du Loup, Que.	CFJP 1480
Oregon City, Oreg.	KGO 1570 N	Philadelphia, Pa.	WDAU 1210 C WDAU 1480 WFIL 560 A WHAT 1340 WIBG 960	Pretonsburg, Ky.	960 WDOC 1310		WELR 1360
Orlando, Fla.	CFDR 1570 WDBO 580 C WHOO 990 M WHOF 1270 WHY 950 WKIS 740	Philipsburg, Pa.	WPHB 1260	Price, Utah	KOAL 1230 M	Roanoke, Ala.	WELR 1360
Ormond Beh. Fla.	WQO 1380	Phoenix, Ariz.	WPHB 1260 KIFN 860 KON 1400 KHAT 1480 KHET 1280 KOY 550 A KOOL 960 C KPHO 910 A KUEQ 740 KRIZ 1230	Prichard, Ala.	WAIP 1270	Roanoke, Va.	WRIS 1410 M WHYE 910 WROV 1240 A WLSL 610 N
Ortonville, Minn.	KDIO 1350	Picayune, Miss.	WRJW 1320	Prince Albert, Sask.	CKBI 900	Roanoke Rapids, N.C.	WCRT 1370 M
Osage Beh. Mo.	KRMS 1150	Piedmont, Ala.	WPID 1280	Prince George, B.C.	CKPG 550	Roaring Springs, Pa.	WKMC 1230 M
Oseola, Ark.	KOSE 860	Pierre, S. Dak.	KGFX 630	Prince Rupert, B.C.	CKPG 550	Roberval, Que.	CHRL 110
Oshawa, Ont.	CKLB 1350	Pikeville, Ky.	WPKF 900	Princeton, Ind.	WBRV 1250	Robinson, Ill.	WTAY 1570
Oskosh, Wis.	WOSH 1490	Pine Bluff, Ark.	KCLA 1400	Princeton, Ky.	WPKY 1580	Rochester, Minn.	KROC 1340 N
Oskaloosa, Iowa	KRSC 1450		KOTN 1490 M	Princeton, N.Y.	WPKY 1580		KWEB 1270
Othello, Wash.	WCY 1430		KPBA 1590	Princeton, Va.	WLOH 1490 A	Rochester, N.H.	WWNH 980
Ottawa, Ill.	KOFO 1220		WCMP 1350	Princetonville, Oreg.	KRCO 630	Rochester, N.Y.	WDBF 1360 M WHAC 1440 M WHCC 1480 C WRYM 680
Ottawa, Kans.	CBDO 910		WMLF 1230	Prosser, Wash.	WEAN 790 M		WSAY 1370
Ottawa, Ont.	CFRA 560 CKOY 1310		WVVO 970	Providence, R.I.	WHIN 1110 WGE 1290 WJAR 920 N WPRO 630 C		WVET 1280 A
Ottumwa, Iowa	KBIZ 1240 A		WVVO 970		WJRA 920 N WPRO 630 C WRIB 1220 A WRIB 1220 A		WROK 1440 A WRRR 1350
Owatonna, Minn.	KRFJ 1390		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Owego, N.Y.	WEBO 1330		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Owensboro, Ky.	WOMI 1490 M WVJS 1420 A		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Owen Sound, Ont.	CFOS 560		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Oxford, Mich.	WOAP 1080		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Oxford, Miss.	KSUH 420		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Oxford, N.C.	WOXF 1340		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Oxnard, Calif.	KOXR 910		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Ozark, Ala.	WOZK 900		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Paducah, Ky.	WKYB 570 N WPAD 1450 C		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Painesville, Ohio	WPVL 1460		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Painesville, Ky.	WSPF 1490 M		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Palatka, Fla.	WSUZ 800		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Palestine, Tex.	KNET 1450		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Palm Beh., Fla.	WXQT 1340 A		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350
Palm Sprrgs., Calif.	KCMJ 1010 C KDES 920		WVVO 970		WVRO 630 C WRIB 1220 A WRIB 1220 A		WRRR 1350

U. S. and Canadian AM Stations by Call Letters

Canadian stations follow U.S. list, on p. 185

C.L., call letters; Kc., frequency in kilocycles

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
U. S.											
KAAA	Kingman, Ariz.	1230	KBKW	Aberdeen, Wash.	1450	KCRA	Sacramento, Calif.	1320	KEYJ	Jamestown, N.Dak.	1400
KABC	Los Angeles, Calif.	790	KBLA	Burbank, Calif.	1490	KCRB	Channahon, Kans.	1430	KEYS	Corpus Christi, Tex.	1440
KABR	Aberdeen, S. Dak.	1220	KBLF	Red Bluff, Calif.	1490	KCRC	Enid, Okla.	1500	KEYV	Provo, Utah	1410
KACE	Riverside, Calif.	1500	KBLI	Blackfoot, Idaho	690	KCRE	Crescent City, Calif.	1240	KEYW	Williston, N.Dak.	1360
KACT	Andrews, Tex.	1360	KBLM	Hot Springs, Ark.	1470	KCRG	Cedar Rapids, Iowa	1600	KFAB	Omaha, Neb.	1410
KACY	Port Hueneme, Calif.	1520	KBLN	Goodland, Kans.	730	KCRS	Midland, Tex.	550	KFAC	Los Angeles, Calif.	1110
KADA	Ada, Okla.	1230	KBLR	Big Lake, Tex.	1290	KCRT	Trinidad, Colo.	1240	KFAL	Fulton, Mo.	900
KADO	Marshall, Tex.	1410	KBLT	Big Bend, Texas	1400	KCRV	Caruthersville, Mo.	1370	KFAM	St. Cloud, Minn.	1450
KADY	St. Charles, Mo.	1460	KBLU	Montezuma, Colo.	1400	KCS	Chadron, Neb.	590	KFAR	Fairbanks, Alaska	660
KAFP	Petaluma, Calif.	1490	KBLV	Bozeman, Mont.	1290	KCTI	Gonzales, Tex.	1450	KFAY	Fayetteville, Ark.	1250
KAFY	Bakersfield, Calif.	350	KBM	Benson, Minn.	1290	KCTX	Childress, Tex.	1510	KFBC	Great Falls, Mont.	1310
KAGE	Winona, Minn.	1380	KBMW	Breckinridge, Minn.	1450	KCUB	Tucson, Ariz.	1290	KFBI	Wichita, Kans.	1240
KAGH	Crossett, Ark.	800	KBMX	Coalinga, Calif.	1470	KCUE	Red Wing, Minn.	1250	KFBK	Sacramento, Calif.	1530
KAGI	Grants Pass, Oreg.	1340	KBMY	Billings, Mont.	1240	KCUL	Fort Worth, Tex.	1540	KFDM	Amarillo, Tex.	1440
KAGT	Anacortes, Wash.	1340	KBN	Bend, Oreg.	1400	KCV	Colville, Wash.	1270	KFDR	Grand Coulee, Wash.	1400
KAGR	Yuba City, Calif.	1450	KBNZ	Luneta, Colo.	830	KCVR	Lois, Calif.	1450	KFE	Pueblo, Colo.	970
KAHU	Waipahu, Hawaii	950	KBOA	Kennett, Mo.	740	KCYL	Lampasas, Tex.	1570	KFD	St. Joseph, Mo.	580
KAIM	Kaimuki, Hawaii	970	KBOE	Oskaloosa, Iowa	950	KD	Fort Bragg, Calif.	610	KFFA	Holena, Ark.	1360
KAIR	Tucson, Ariz.	1490	KBOJ	Boise, Idaho	1310	KD	Duluth, Minn.	790	KFGQ	Boone, Iowa	1260
KAIJ	Grants Pass, Oreg.	1270	KBOK	Malvern, Ark.	1490	KD	Eureka, Calif.	580	KFH	Wichita, Kans.	1330
KAKC	Tulsa, Okla.	970	KBOL	Boulder, Colo.	1490	KD	Santa Monica, Calif.	1580	KFI	Los Angeles, Calif.	640
KAKE	Wichita, Kan.	580	KBOM	Mandan, N.Dak.	1270	KDB	Manchester, Calif.	1490	KFIR	North Bend, Oreg.	1360
KAKL	Alexandria, La.	960	KBON	Omaha, Neb.	1390	KDB	Mansfield, Ohio	800	KFIZ	Floreston, Wis.	1450
KALE	Richland, Wash.	1230	KBOP	Pleasanton, Calif.	1600	KDB	Dillon, Mont.	1400	KFJB	Marshalltown, Iowa	1510
KALG	Alamogordo, N.Mex.	1230	KBOW	Butte, Mont.	1490	KDBS	Alexandria, La.	1410	KFJJ	Klamath Falls, Oreg.	1150
KALI	Pasadena, Calif.	910	KBOY	Medford, Oreg.	1240	KDBS	Dumas, Tex.	800	KFJM	Grand Forks, N.Dak.	1370
KALL	Salt Lake City, Utah	910	KBOX	Dallas, Tex.	1480	KDD	Decorah, Iowa	1240	KFJZ	Ft. Worth, Tex.	1270
KALM	Thayer, Mo.	1290	KBR	Portland, Oreg.	1450	KDE	Albuquerque, N.Mex.	1150	KFKA	Greenville, Colo.	1310
KALT	Atlanta, Tex.	900	KBR	Brookings, S.Dak.	1430	KDE	Denver, Colo.	920	KFK	Lawrence, Kans.	1250
KALV	Alva, Okla.	1490	KBR	Brookings, S.Dak.	1430	KDE	Palmer, Calif.	930	KFLD	Floydada, Tex.	900
KAMD	Camden, Ark.	1430	KBR	Brookings, S.Dak.	1430	KDE	Center, Tex.	1590	KFLJ	Waldenburg, Oreg.	1380
KAML	Kenedy, Tex.	990	KBR	Brookings, S.Dak.	1430	KDE	Dexter, Mo.	1240	KFLW	Klamath Falls, Oreg.	1450
KAMO	Roers, Ark.	1390	KBR	Brookings, S.Dak.	1430	KDE	Durango, Colo.	1350	KFLY	Corvallis, Oreg.	1250
KAMP	El Centro, Calif.	1430	KBR	Brookings, S.Dak.	1430	KDE	Faribault, Minn.	1520	KFMA	Davenport, Iowa	1580
KAMQ	Amarillo, Tex.	1210	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFMB	San Diego, Calif.	540
KANA	Anacortes, Mont.	1030	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFMJ	Tulsa, Okla.	1050
KANB	Shreveport, La.	1300	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFML	Denver, Colo.	1390
KANC	Corsicana, Tex.	1340	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFMO	Flat River, Mo.	1240
KANE	New Iberia, La.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFNP	Shenandoah, Iowa	920
KANN	Sinton, Tex.	1590	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFN	Ferriday, La.	1600
KANP	Anoka, Minn.	1470	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFNR	Fargo, N.Dak.	1240
KANQ	Jonesville, La.	1480	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFOR	Lincoln, Neb.	940
KAKO	Lake Charles, La.	1340	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFOX	Long Beach, Calif.	1280
KAPA	Raymond, Wash.	1340	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFPW	Ft. Smith, Ark.	1230
KAPB	Marksville, La.	1370	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFQD	Anchorage, Alaska	730
KAPR	Douglas, Ariz.	930	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFRB	Fairbanks, Alaska	900
KARC	Atchison, Kan.	1470	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFR	San Francisco, Calif.	610
KAR	Little Rock, Ark.	920	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFR	Roseburg, Tex.	980
KARM	Fresno, Calif.	1430	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFR	Kansas City, Mo.	550
KART	Jerome, Idaho	1400	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFR	Longview, Tex.	1370
KARY	Prosser, Wash.	1310	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFR	Columbia, Mo.	1400
KASA	Eik City, Okla.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFS	Ft. Smith, Ark.	950
KASH	Eugene, Ore.	1600	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFSB	Joplin, Mo.	1310
KASI	Ames, Iowa	1430	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFSD	San Diego, Calif.	1220
KASK	Ontario, Calif.	1510	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFSG	Los Angeles, Calif.	900
KASL	Newcastle, Wyo.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFT	Ft. Stockton, Tex.	860
KASB	Albany, Minn.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFTM	Ft. Morgan, Colo.	1400
KASO	Minden, La.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFV	Paris, Tex.	1250
KAST	Astoria, Ore.	1370	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFV	Las Vegas, N.Mex.	1230
KATE	Albert Lea, Minn.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFV	Cape Girardeau, Mo.	850
KAT	Casper, Wyo.	1400	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFWB	Los Angeles, Calif.	960
KAT	Miles City, Mont.	1340	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFXD	Nampa, Idaho	580
KATR	Renov, Nev.	1400	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFXM	San Bernardino, Calif.	590
KATO	Corpus Christi, Tex.	1030	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFY	Bonham, Tex.	1420
KATY	San Luis Obispo, Calif.	1340	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFY	Blackfoot, Tex.	790
KATZ	St. Louis, Mo.	1600	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KFY	Blacksburg, N.Dak.	550
KAV	Austin, Minn.	1480	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGA	Spokane, Wash.	140
KAV	Carlsbad, N.Mex.	610	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGAF	Gainesville, Tex.	1580
KAVI	Rocky Ford, Colo.	1320	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGAL	Gallup, N.Mex.	930
KAVL	Lancaster, Calif.	960	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGAL	Lebanon, Oreg.	1260
KAVR	Apple Valley, Calif.	960	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGAS	Garfield, Tex.	1340
KAWL	York, Neb.	1370	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGB	San Diego, Calif.	1360
KAWT	Douglas, Ariz.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGBC	Galveston, Tex.	1540
KAYE	Puyallup, Wash.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGBT	Harting, Tex.	1530
KAYF	Storm Lake, Iowa	990	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGBX	Springfield, Mo.	1260
KAYO	Seattle, Wash.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGC	Sidney, Mont.	1480
KAYS	Hays, Kans.	1150	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGE	Georgetown, N.Mex.	1250
KAYT	Rupert, Idaho	970	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGEM	Edmonds, Wash.	1230
KBAL	San Saba, Tex.	1410	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGEM	Boise, Idaho	1140
KBAM	Longview, Wash.	1270	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGEM	Tulare, Calif.	1370
KBAR	Burley, Idaho	1230	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGER	Georgetown, Calif.	1390
KBAS	Benton, Ark.	690	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Kalispell, Mont.	610
KBBB	Borger, Tex.	1600	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Shawnee, Okla.	1450
KBBC	Centerville, Utah	600	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGFJ	Los Angeles, Calif.	1230
KBBS	Buffalo, Wyo.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGFJ	Roswell, N.Mex.	1400
KBCH	Oceanlake, Oreg.	1400	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Kearney, Neb.	1340
KBCJ	Bossier City, La.	1220	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Pierre, S.Dak.	630
KBC	Grand Prairie, Tex.	730	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Albuquerque, Kans.	690
KBCB	Waxahatchie, Tex.	1390	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGF	Pueblo, Colo.	1350
KBCE	Modesto, Calif.	970	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGH	Little Rock, Ark.	1250
KBEL	Idabel, Okla.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGHL	Billings, Mont.	790
KBEN	Carrizo Sprngs., Tex.	1450	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGHM	Brookfield, Mo.	1470
KBHM	Branson, Mo.	1220	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGI	San Fernando, Calif.	1450
KBHS	Hot Springs, Ark.	590	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGK	White Castle, Colo.	1490
KBIA	Columbia, Mo.	1580	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGL	Tyler, Tex.	480
KBIF	Fresno, Calif.	900	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGL	San Angelo, Tex.	960
KBIG	Avallon, Calif.	970	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGL	Miami, Okla.	910
KBIM	Roswell, N.Mex.	910	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGL	Glenwood Sprngs., Colo.	980
KBIS	Bakersfield, Calif.	970	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230	KGL	Mason City, Iowa	1300
KBIT	Muskogee, Okla.	1240	KBR	Brookings, S.Dak.	1430	KDE	Ortonville, Minn.	1230			
KBIZ	Ottumwa, Iowa	1490	KBR	Brookings, S.Dak.	1						

C.I.	Location	Kc.	C.I.	Location	Kc.	C.I.	Location	Kc.	C.I.	Location	Kc.
KGLU	Safford, Ariz.	1480	KJCK	Junction City, Kans.	1420	KMUL	Muleshoe, Tex.	1380	KOVE	Lander, Wyo.	1330
KGMB	Honolulu, Hawaii	590	KJET	Jennings, La.	1290	KMUR	Murray, Utah	1230	KOVD	Provo, Utah	960
KGMC	Englewood, Colo.	1150	KJEF	Beaumont, Tex.	1380	KMUS	Muskogee, Okla.	1380	KOWB	Laramie, Wyo.	1340
KGMO	Cape Girardeau, Mo.	1220	KJFJ	Webster City, Iowa	1570	KMYJ	Walluku, T. H.	550	KOWH	Omaha, Nebr.	660
KGMS	Sacramento, Calif.	1380	KJFM	Ft. Worth, Tex.	870	KMYC	Marysville, Calif.	1410	KOWL	Lake Tahoe, Calif.	1490
KGNB	New Braunfels, Tex.	1420	KJLT	North Platte, Nebr.	970	KMYR	Denver, Colo.	630	KOWN	Escondido, Calif.	1450
KGNC	Amarillo, Tex.	710	KJMA	Juneau, Alaska	1480	KNFJ	Fredericksburg, Tex.	1340	KOXR	Ornard, Calif.	910
KGND	Dodge City, Kans.	1370	KJOE	Shreveport, La.	970	KNKR	Salt Lake City, Utah	1280	KOYR	Phoenix, Ariz.	550
KGO	San Francisco, Calif.	810	KJOY	Stockton, Calif.	1280	KNAL	Victoria, Tex.	1410	KOYE	EI Paso, Tex.	1150
KGOS	Oregon City, Oreg.	1520	KJRW	Seattle, Wash.	950	KNBA	Vallejo, Calif.	1190	KOYL	Odessa, Tex.	1310
KGOS	Torrington, Wyo.	1490	KJRW	Newton, Kans.	950	KNBC	San Francisco, Calif.	680	KOYN	Billings, Mont.	910
KGPC	Grafton, N. Dak.	1340	KJSC	Columbus, Nebr.	900	KNBX	Kirkland, Wash.	1050	KOZE	Lewiston, Idaho	1300
KGRI	Henderson, Tex.	1000	KKEY	Vancouver, Wash.	1150	KNBY	Newport, Ark.	1280	KPZJ	Cheban, Wash.	1220
KGRN	Grinnell, Iowa	1410	KKIS	Pittsburg, Calif.	950	KNCK	Concordia, Kans.	1330	KOZY	Grand Rapids, Minn.	1060
KGRH	Gresham, Oreg.	1230	KKOG	Ogden, Utah	730	KNCF	Motley, Mo.	1230	KPAC	Port Arthur, Tex.	1250
KGRT	Las Cruces, N.Mex.	570	KKLA	Albany, Calif.	570	KNCO	Garden City, Kans.	1050	KPAL	Palm Springs, Calif.	1450
KGT	Fresno, Calif.	1600	KKLD	Klamath Falls, Oreg.	900	KNDC	Hettinger, N. Dak.	1490	KPAM	Portland, Oreg.	1410
KGU	Honolulu, Hawaii	760	KKLA	Lakewood, Colo.	1600	KNDY	Marysville, Kans.	1570	KPAN	Hercford, Tex.	860
KGVL	Greenville, Tex.	1400	KLAM	Carovada, Alaska	1450	KNEA	Janesboro, Ark.	970	KPAP	Redding, Calif.	1270
KGVV	Missoula, Mont.	1290	KLAS	Las Vegas, Nev.	1230	KNEB	Scottsbluff, Nebr.	960	KPAB	Banning, Calif.	1490
KGW	Portland, Oreg.	620	KLBM	La Grande, Oreg.	1450	KNED	McAlester, Okla.	1150	KPAC	Chico, Calif.	1060
KGWA	Enid, Okla.	960	KLBN	Blytheville, Ark.	910	KNEL	Bartley, Tex.	1490	KPBA	Pine Bluff, Ark.	1500
KGY	Olympia, Wash.	1240	KLCO	Clifton, Okla.	1280	KNEP	Newada, Mo.	1240	KPBM	Carlsbad, N.Mex.	740
KGYN	Guymon, Okla.	1420	KLEC	Leighton, N.Mex.	630	KNEP	Pastry, Tex.	1450	KPCD	Marked Tree, Ark.	1580
KHAM	Albuquerque, N.Mex.	1580	KLEE	Ottumwa, Iowa	1480	KNEU	Provo, Utah	1450	KPDN	Pampa, Tex.	1840
KHAS	Hastings, Nebr.	1230	KLEM	LeMars, Iowa	1410	KNEW	Spokane, Wash.	790	KPDQ	Portland, Oreg.	1300
KHAT	Phoenix, Ariz.	1480	KLEN	Killeen, Tex.	1050	KNEX	McPherson, Kans.	1540	KPEL	Spokane, Wash.	1380
KHBC	Hilo, Hawaii	970	KLEO	Wichita, Kans.	1480	KNEZ	Lompoc, Calif.	960	KPEG	Lafayette, La.	1420
KHBB	Okmulgee, Okla.	1240	KLER	Orofino, Idaho	950	KNGS	Hanford, Calif.	1220	KPEK	San Angelo, Tex.	1420
KHBM	Munticello, Ark.	1430	KLEX	Lexington, Mo.	1570	KNIM	Marysville, Mo.	1580	KPKR	Grand Rapids, Minn.	1290
KHBR	Hillsboro, Tex.	1560	KLFT	Golden Meadow, La.	1600	KNIT	Abilene, Tex.	1280	KPET	Lamesa, Tex.	890
KHCD	Clifton, Ariz.	1420	KLGN	Logan, Utah	1600	KNLR	N. Little Rock, Ark.	1380	KPHO	Phoenix, Ariz.	910
KHEM	Big Springs, Tex.	1270	KLGN	Logan, Utah	1600	KNOC	Natchitoches, La.	1450	KPIO	Cedar Rapids, Iowa	1350
KHEN	Henryetta, Okla.	1590	KLGR	Redwood Falls, Minn.	1490	KNOE	Monroe, La.	1390	KPIK	Colorado Surgs., Colo.	1580
KHEP	Phoenix, Ariz.	1280	KLMO	Le Roy, La.	1230	KNOG	Nogales, Ariz.	1340	KPIN	Casa Grande, Ariz.	1260
KHEY	EI Paso, Tex.	690	KLIF	Dallas, Tex.	1190	KNOK	Ft. Worth, Tex.	970	KPKW	Pasco, Wash.	1340
KHFH	Sierra Vista, Ariz.	1420	KLIJ	Jefferson City, Mo.	950	KNOR	Norman, Okla.	1400	KPLC	Lake Charles, La.	1470
KHHH	Pampa, Tex.	1230	KLIE	Estherville, Iowa	1340	KNOT	Prescott, Ariz.	1450	KPLD	Dallas, Texas	1460
KHIL	Brighton-Fort Lupton, Colorado	800	KLIN	Lincoln, Nebr.	1340	KNOW	Austine, Tex.	1490	KPMC	Bakersfield, Calif.	1560
KHIT	Walla Walla, Wash.	1320	KLIR	Denver, Colo.	900	KNOX	Grand Forks, N. Dak.	1310	KPOC	Honolulu, T.H.	630
KHJ	Los Angeles, Calif.	930	KLIX	Twin Falls, Idaho	1310	KNPT	Newport, Ore.	1310	KPOF	Peachantans, Ark.	1420
KHMO	Hannibal, Mo.	1070	KLIZ	Brainerd, Minn.	1540	KNJ	New Ulm, Minn.	860	KPPC	Denver, Colo.	910
KHOB	Hobbs, N.Mex.	1280	KLKC	Parsons, Kans.	1540	KNJH	Houston, Tex.	1380	KPKD	Portland, Oreg.	1330
KHOG	Fayetteville, Ark.	1450	KLLA	Leesville, La.	1570	KNWS	Waterloo, Iowa	1020	KPKS	Scottsdale, Ariz.	1440
KHOK	Garden, Colo.	1250	KLLB	Lubbock, Tex.	1470	KNX	Los Angeles, Calif.	1070	KPLR	Los Angeles, Calif.	1540
KHON	Honolulu, T.H.	1360	KLMO	Longmont, Colo.	1570	KOA	Denver, Colo.	850	KPOP	Los Angeles, Calif.	1020
KHOT	Madera, Calif.	1230	KLMR	Lamar, Oreg.	1030	KOAC	Corvallis, Oreg.	550	KPOR	Quincy, Wash.	1370
KHOW	Denver, Colo.	630	KLMS	Lincoln, Nebr.	1480	KOAL	Price, Utah	1230	KPOS	Post, Tex.	1370
KHOZ	Harrison, Ark.	900	KLMX	Clayton, N.Mex.	1450	KOAM	Pittsburg, Kans.	860	KPOW	Powell, Wyo.	1260
KHQ	Spokane, Wash.	590	KLOG	Ogden, Utah	1430	KOB	Albuquerque, N.Mex.	1030	KPPC	Padadena, Calif.	1240
KHSL	Chico, Calif.	1290	KLOG	Kelso, Wash.	1490	KOBE	Las Cruces, N.Mex.	1450	KPQ	Wenatchee, Wash.	560
KHUB	Fremont, Nebr.	1340	KLOH	Pipestone, Minn.	1400	KOBY	San Francisco, Calif.	1550	KPRB	Redmond, Oreg.	1240
KHUZ	Borger, Tex.	1490	KLDK	San Jose, Calif.	1050	KOCA	Kilgore, Tex.	1240	KPRD	Livingston, Mont.	1340
KHVV	Honolulu, Hawaii	1640	KLOS	Los Angeles, Calif.	1170	KODY	Oklahoma City, Okla.	1230	KPRP	Livingston, Mont.	1340
KIAL	Astoria, Oreg.	1230	KLOS	Albuquerque, N.Mex.	1450	KODE	Joplin, Mo.	1230	KPRL	Paso Robles, Calif.	1230
KIBE	Palo Alto, Calif.	220	KLOU	Lake Charles, La.	1580	KODI	Cody, Wyo.	1400	KPRS	Riverside, Calif.	1440
KIBH	Seward, Alaska	1340	KLOV	Loveland, Colo.	1570	KODL	The Dalles, Oreg.	1440	KPSR	Kansas City, Mo.	1580
KIBL	Beeville, Tex.	1490	KLPK	Lake Providence, La.	1050	KODY	North Platte, Nebr.	1240	KPSO	Fallurrias, Tex.	1290
KIBS	Bishop, Calif.	1230	KLPW	Minot, N. Dak.	1390	KOEL	Oelwein, Iowa	950	KPTT	Preston, Idaho	1340
KICA	Clovis, N.Mex.	980	KLPK	Okla. City, Okla.	1140	KOFA	Yuma, Ariz.	1240	KPTL	Carson City, Nev.	1400
KID	Spencer, Iowa	1240	KLPW	Union, Mo.	1440	KOFE	Fultman, Wash.	1020	KPVA	Van Nuys, Wash.	1790
KICK	Springfield, Mo.	1340	KLRA	Lawrence, Ark.	1010	KOFO	Ottawa, Kans.	2220	KPVA	Camas, Wash.	940
KIDG	Calexico, Calif.	1490	KLRS	Little Mountain Grove, Mo.	1360	KOFY	San Mateo, Calif.	1050	KQD	Renton, Wash.	1910
KIDH	Idaho Falls, Idaho	590	KLTF	Little Falls, Minn.	960	KOGA	Ogallala, Nebr.	930	KQDI	Bismarck, N.D.	1350
KIDD	Monterey, Calif.	630	KLTR	Longview, Tex.	1280	KOGT	Orange, Tex.	1600	KQDY	Minot, N. Dak.	1320
KIDO	Boise, Idaho	630	KLTR	Blackwell, Okla.	1580	KOH	Reno, Nev.	630	KQEK	Albuquerque, N.Mex.	920
KIEM	Eureka, Calif.	1480	KLTZ	Glasgow, Mont.	1240	KOHU	Hermiston, Oreg.	1230	KQEL	Lakeview, Oreg.	1230
KIEV	Glendale, Calif.	870	KLUB	Salt Lake City, Utah	570	KOIN	Omaha, Nebr.	1290	KQF	Pittsburg, Pa.	1410
KIFJ	Idaho Falls, Idaho	1260	KLUB	Exton, Oreg.	1240	KOIN	Portland, Oreg.	970	KRAC	Alamogordo, N.M.	1270
KIFN	Phoenix, Ariz.	860	KLVY	Haynesville, La.	1580	KOJM	Havr, Mont.	610	KRAI	Craig, Colo.	550
KIFW	Sitka, Alaska	1230	KLVY	Leadville, Colo.	1230	KOKA	Shreveport, La.	980	KRAK	Stockton, Calif.	1140
KIHN	Hugo, Okla.	1340	KLVV	Vivian, La.	1600	KOKE	Austin, Tex.	1370	KRAL	Rawlins, Wyo.	1240
KIHO	Sioux Falls, S. Dak.	1270	KLVL	Pasadena, Tex.	1480	KOKO	Warrensburg, Mo.	1450	KRAM	Las Vegas, Nev.	920
KIHR	Hood River, Oreg.	1340	KLVT	Levelland, Tex.	1230	KOKX	Keokuk, Iowa	1450	KRAY	Haystack, Wash.	1790
KIJV	Huron, S. Dak.	1340	KLWN	Lawrence, Kans.	1320	KOKY	Little Rock, Ark.	1440	KRBA	Lufkin, Tex.	1440
KIKI	Honolulu, Hawaii	830	KLWJ	Lawrence, Mo.	1230	KOL	Seattle, Wash.	1300	KRBC	Abilene, Tex.	1370
KIKM	Minto, Ariz.	1340	KLWD	Duncan, Calif.	910	KOLE	Tucson, Ariz.	1450	KRBI	St. Peter, Minn.	1350
KIKS	Sulphur, La.	1310	KLYD	Bakersfield, Calif.	1350	KOLE	Port Arthur, Tex.	1340	KRBO	Las Vegas, Nev.	1010
KILE	Galveston, Tex.	1400	KLYK	Spokane, Wash.	1230	KOLL	Quannah, Tex.	1150	KRCK	Ridgecrest, Calif.	900
KILD	Grand Forks, S. Dak.	1440	KLYN	Amarillo, Tex.	940	KOLJ	Libby, Mont.	1230	KRCD	Prineville, Oreg.	690
KILT	Houston, Tex.	610	KLYR	Clarksville, Ark.	1360	KOLR	Reno, Nev.	920	KRCY	Bellingham, Wash.	1790
KIMA	Yakima, Wash.	1460	KLYZ	Denver, Colo.	560	KOLS	Pryor, Okla.	1490	KRDD	Redding, Calif.	1230
KIML	Gillette, Wyo.	1490	KMA	Shenandoah, Iowa	960	KOLT	Scottsbluff, Nebr.	1320	KRDO	Colorado Springs, Colo.	1240
KIMO	Independence, Mo.	1510	KMAC	San Antonio, Tex.	630	KOLY	Mubridge, S. Dak.	1300	KREU	Dubuqa, Calif.	1240
KIMN	Denver, Colo.	950	KMAE	McKinney, Tex.	1600	KOMA	Okla. City, Okla.	1520	KREB	Berkeley, Calif.	1400
KIMP	Mt. Pleasant, Tex.	960	KMAK	Fresno, Calif.	1340	KOMB	Cottage Grove, Oreg.	1400	KREH	Oakdale, La.	900
KIND	Independence, Kans.	1010	KMAM	Tulsa, N.Mex.	1590	KOME	Tulsa, Okla.	1300	KREI	Farmington, Mo.	800
KINE	Kingsville, Tex.	1330	KMAN	Manhattan, Kans.	1350	KOMF	Seattle, Wash.	1300	KREL	Baytown, Tex.	970
KING	Seattle, Wash.	1090	KMAP	Bakersfield, Calif.	1490	KOML	Omaha, Neb.	1000	KREK	Waukegan, Ill.	1400
KINS	Eureka, Calif.	980	KMAR	Winnaboo, La.	1570	KOMY	Watsonville, Calif.	1340	KRES	St. Joseph, Mo.	1530
KINY	Juneau, Alaska	800	KMBC	Kansas City, Mo.	1450	KONO	Reno, Nev.	1450	KREW	Sunnyside, Wash.	1250
KIOA	Des Moines, Iowa	940	KMBJ	Junction, Oreg.	1240	KONV	Visalia, Calif.	1400	KREX	Grand Junction, Colo.	920
KIOB	Bay City, Tex.	1270	KMBY	Monterey, Calif.	1570	KONI	Phoenix, Ariz.	1400	KRFQ	Owatonna, Minn.	1390
KIPA	Hilo, Hawaii	110	KMCD	Fairfield, Iowa	1260	KONP	San Antonio, Tex.	860	KRGI	Grand Island, Neb.	1480
KIRO	Seattle, Wash.	710	KMCM	McMinville, Oreg.	900	KONR	Port Angeles, Wash.	1450	KRGV	Waukegan, Ill.	1290
KIRT	Mission, Tex.	1580	KMCO	Conroe, Tex.	1600	KODK	Billings, Mont.	970	KRHD	Duncan, Okla.	1350
KIRX	Kirkville, Mo.	1450	KMED	Medford, Oreg.	1400	KODL	Omaha, Nebr.	960	KRIB	Mason City, Iowa	1490
KISD	Sioux Falls, S. Dak.	1230	KMED	Medford, Oreg.	1400	KODM	Omaha, Nebr.	1420	KRIC	Beaumont, Tex.	1450
KIST	Santa Barbara, Calif.	1240	KMLH	Marshlee, Minn.	1450	KODS	Coos Bay, Oreg.	1250	KRIG	Odessa, Tex.	1410
KIT	Yakima, Wash.	990	KMHT	Marshall, Tex.	1450	KOPR	Butte, Mont.	520	KRIO	McAllen, Tex.	910
KITE	San Antonio, Tex.	930	KMIL	Cameron, Tex.	1330	KOPY	Alice, Tex.	1070	KRIZ	Phoenix, Ariz.	1230
KITI	Chehalis, Wash.	1440	KMIN	Grants, N.M.	980	KORB	Bryan, Tex.	1240	KRPF	Miles City, Mont.	1150
KITO	N. Bernardino, Calif.	1290	KMJ	Fresno, Calif.	580	KORC	Mineral Wells, Tex.	910	KRKO	Los Angeles, Calif.	1380
KIUL	Garden City, Kans.	1240	KMLB	Monroe, La.	1440	KORD	Paris, Wash.	1010	KRKO	Everett, Wash.	1380
KIUN	Pecos, Tex.	1490	KMLW	Marlin, Tex.	750	KORE	Eugene, Oreg.	1450	KRKS	Ridgecrest, Calif.	1240
KIUP	Durango, Colo.	1290	KMMJ	Grand Island, Nebr.	1300	KORK	Las Vegas, Nev.	930	KRLC	Lawton, Idaho	1350
KIUY	Crockett, Tex.	1400	KMMO	Marshall, Mo.	1260	KORN	Mitchell, S. Dak.	1490	KRLD	Dallas, Tex.	1080
KIYW	San Antonio, Tex.	1040	KMNS	Sioux City, Iowa	1360	KORT	Grangeville, Idaho	1230	KRLN	Canon City, Colo.	1400
KIXL	Dallas, Tex.	1540	KMTC	Tacoma, Wash.	1360	KOSA	Odessa, Tex.	1230	KRLW	Walnut Ridge, Ark.	1320
KIXX	Provo, Utah	1400	KMON	Great Falls, Mont.	560	KOSE	Oseola, Ark.	860	KRMD	Shreveport, La.	740
KIYI	Shelby, Mont.	1150	KMOP	Tucson, Ariz.	1330	KOSY	Aurora, Colo.	1430	KRMG	Tulsa, Okla.	740
KJAY	Atlantic, Iowa	1220	KMOR	Orville, Calif.	1340	KOTA	Rapid City, S. Dak.	1380	KRMO	Monett, Mo.	990
KJAN	Topeka, Kans.	1440	KMOX	St. Louis, Mo.	1120	KOTR	Pine Bluff, Ark.	1490			
KJBC	Midland, Tex.	1350	KMPC	Los Angeles, Calif.	710	KOTS	Deming, N.M.	1230			
KJBS	San Francisco, Calif.	1100	KMRC	Morgan City, La.	1430	KOTV	Valley City, N. Dak.	1490			
KJCF	Festus, Mo.	1010	KMRS	Morris, Minn.	1570						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KRMS	Osage Beach, Mo.	1150	KTAC	Tacoma, Wash.	850	KWVY	Waverly, Iowa	1470
KRNV	The Dalles, Ore.	1300	KTAE	Taylor, Tex.	1260	KWVW	Waverly, Iowa	1470
KRNO	San Bernardino, Calif.	1240	KTAR	Phoenix, Ariz.	1570	KWVX	Farmington, N.Mex.	900
KRNR	Roseburg, Ore.	1490	KTAT	Frederick, Okla.	600	KWVY	Wynne, Ark.	1400
KRNS	Burns, Ore.	1290	KTBB	Tyler, Tex.	590	KWVZ	Sherridan, Wyo.	1210
KRNT	Des Moines, Iowa	1350	KTBC	Austin, Tex.	1480	KWVW	Waco, Tex.	1400
KRNY	Kearney, Neb.	1340	KTBD	Malden, Mo.	1410	KWVU	Kearney, Neb.	1400
KRRC	Rochester, Minn.	1300	KTBE	Baylorville, Ark.	1490	KWVQ	Seattle, Wash.	1400
KRDD	El Paso, Tex.	900	KTBF	Fort Smith, Ark.	1410	KWVW	Seattle, Wash.	1400
KRDF	Abbeville, La.	600	KTBE	Carmel, Calif.	1490	KWVX	Seattle, Wash.	1400
KRDR	Senora, Calif.	1450	KTEF	Walla Walla, Wash.	4400	KWVY	Seattle, Wash.	1400
KRDP	Brawley, Calif.	1300	KTEG	Temple, Tex.	1570	KWVZ	Seattle, Wash.	1400
KRDS	Clinton, Iowa	1260	KTEH	Terrill, Tex.	1220	KWVW	Seattle, Wash.	1400
KRDX	Oakland, Calif.	1360	KTEI	Livingston, Tex.	1200	KWVX	Seattle, Wash.	1400
KRDY	Crookston, Minn.	1400	KTEJ	Twin Falls, Idaho	1240	KWVY	Seattle, Wash.	1400
KRDZ	Sacramento, Calif.	1400	KTEK	Texarkana, Tex.	1300	KWVZ	Seattle, Wash.	1400
KRPL	Moscow, Idaho	1460	KTEF	Brownfield, Tex.	1200	KWVW	Seattle, Wash.	1400
KRRV	Sherman, Tex.	910	KTEH	Thermopolis, Wyo.	1290	KWVX	Seattle, Wash.	1400
KRSC	Othello, Wash.	1450	KTHS	Little Rock, Ark.	1040	KWVY	Seattle, Wash.	1400
KRSD	Rapid City, S.Dak.	1340	KTHT	Houston, Tex.	790	KWVZ	Seattle, Wash.	1400
KRSL	Russell, S.Dak.	490	KTHU	Thibodaux, La.	630	KWVW	Seattle, Wash.	1400
KRSN	Los Alamos, N.Mex.	1490	KTHV	Tillamook, Ore.	1510	KWVX	Seattle, Wash.	1400
KRTN	Raton, N.Mex.	1490	KTIM	San Rafael, Calif.	1500	KWVY	Seattle, Wash.	1400
KRTR	Thermopolis, Wyo.	1490	KTIP	Porterville, Calif.	900	KWVZ	Seattle, Wash.	1400
KRUN	Ballinger, Tex.	1400	KTIS	Minneapolis, Minn.	1500	KWVW	Seattle, Wash.	1400
KRUS	Ruston, La.	1490	KTIX	Seattle, Wash.	990	KWVX	Seattle, Wash.	1400
KRUX	Glendale, Ariz.	1360	KTJN	Hobart, Okla.	1420	KWVY	Seattle, Wash.	1400
KRVN	Lexington, Neb.	1010	KTKN	Ketchikan, Alaska	930	KWVZ	Seattle, Wash.	1400
KRWV	Forest Grove, Ore.	1570	KTKR	Taft, Calif.	1310	KWVW	Seattle, Wash.	1400
KRXK	Rexburg, Idaho	1230	KTKT	Basin, Wyo.	980	KWVX	Seattle, Wash.	1400
KRXL	Roseburg, Ore.	1240	KTKU	Tullulah, La.	1360	KWVY	Seattle, Wash.	1400
KRYS	Corpus Christi, Tex.	1360	KTLN	Denver, Colo.	1280	KWVZ	Seattle, Wash.	1400
KSAC	Manhattan, Kans.	580	KTLO	Mtn. Home, Ark.	1490	KWVW	Seattle, Wash.	1400
KSAL	Salina, Kans.	1150	KTLQ	Tahlequah, Okla.	1350	KWVX	Seattle, Wash.	1400
KSAM	Huntville, Ind.	1490	KTRJ	Rusk, Tex.	1580	KWVY	Seattle, Wash.	1400
KSAN	San Francisco, Calif.	1450	KTRK	Twin Falls, Idaho	1240	KWVZ	Seattle, Wash.	1400
KSAY	San Francisco, Calif.	1010	KTRM	McAlester, Okla.	920	KWVW	Seattle, Wash.	1400
KSBB	Salinas, Calif.	1380	KTRN	Santa Barbara, Calif.	1250	KWVX	Seattle, Wash.	1400
KSBC	Liberal, Kans.	1270	KTRP	Falls City, Neb.	1230	KWVY	Seattle, Wash.	1400
KSBD	Sioux City, Iowa	1360	KTRQ	Tucumcari, N.Mex.	1400	KWVZ	Seattle, Wash.	1400
KSCE	Scottsbluff, Calif.	1080	KTRR	Tacoma, Wash.	1420	KWVW	Seattle, Wash.	1400
KSD	St. Louis, Mo.	540	KTRS	Lawton, Okla.	1480	KWVX	Seattle, Wash.	1400
KSDA	Redding, Calif.	1400	KTRT	Mankato, Minn.	1420	KWVY	Seattle, Wash.	1400
KSDN	Aberdeen, S.Dak.	930	KTRU	Lawton, Okla.	1480	KWVZ	Seattle, Wash.	1400
KSDO	San Diego, Calif.	1130	KTRV	Henderson, Nev.	1280	KWVW	Seattle, Wash.	1400
KSEI	Pocatello, Idaho	930	KTRW	Oklahoma City, Okla.	1490	KWVX	Seattle, Wash.	1400
KSEK	Pittsburg, Kans.	1340	KTRX	Okla. City, Okla.	800	KWVY	Seattle, Wash.	1400
KSEL	Lubbock, Texas	1450	KTRZ	Modesto, Calif.	860	KWVZ	Seattle, Wash.	1400
KSEM	Moses Lake, Wash.	1450	KTRC	San Fe. N.Mex.	1400	KWVW	Seattle, Wash.	1400
KSEO	Durant, Okla.	750	KTRD	Lufkin, Tex.	1420	KWVX	Seattle, Wash.	1400
KSET	El Paso, Tex.	1340	KTRF	Thief River Falls, Minn.	1230	KWVY	Seattle, Wash.	1400
KSEW	Sitka, Alaska	1400	KTRH	Houston, Tex.	740	KWVZ	Seattle, Wash.	1400
KSEY	Seymour, Tex.	1230	KTRI	Sioux City, Iowa	1340	KWVW	Seattle, Wash.	1400
KSFA	Naacogdoches, Tex.	1340	KTRM	Beaumont, Tex.	990	KWVX	Seattle, Wash.	1400
KSFE	Needles, Calif.	560	KTRN	Wichita Falls, Tex.	1290	KWVY	Seattle, Wash.	1400
KSFO	San Francisco, Calif.	980	KTRP	Bastrop, La.	450	KWVZ	Seattle, Wash.	1400
KSGM	Ste. Genevieve, Mo.	1520	KTRQ	San Antonio, Tex.	550	KWVW	Seattle, Wash.	1400
KSIB	Credon, Iowa	1340	KTRR	El Paso, Tex.	1380	KWVX	Seattle, Wash.	1400
KSID	Sioux, Neb.	1450	KTRS	Trenton, Mo.	1600	KWVY	Seattle, Wash.	1400
KSIG	Crowley, La.	1430	KTRT	Rolla, Mo.	1490	KWVZ	Seattle, Wash.	1400
KSJA	Gladsware, Tex.	1340	KTRU	Springfield, Mo.	1400	KWVW	Seattle, Wash.	1400
KSIL	Silver City, N.Mex.	1400	KTRV	Tucson, Ariz.	1400	KWVX	Seattle, Wash.	1400
KSIM	Sikeston, Mo.	900	KTRW	Tulia, Tex.	1250	KWVY	Seattle, Wash.	1400
KSIR	Wichita, Kans.	1050	KTRX	Lookout Mountain, Okla.	1450	KWVZ	Seattle, Wash.	1400
KSIS	Sedalia, Mo.	1450	KTRZ	Turlock, Calif.	1390	KWVW	Seattle, Wash.	1400
KSJW	Woodward, Okla.	1230	KTUT	Tooele, Utah	990	KWVX	Seattle, Wash.	1400
KSJX	Corpus Christi, Tex.	1590	KTW	Seattle, Wash.	1250	KWVY	Seattle, Wash.	1400
KSJY	Jamestown, N.Dak.	660	KTXJ	Jasper, Mo.	1350	KWVZ	Seattle, Wash.	1400
KSJO	San Jose, Calif.	1160	KTXK	San Angelo, Tex.	1340	KWVW	Seattle, Wash.	1400
KSJY	Dallas, Tex.	1390	KTXL	Sherman, Tex.	1500	KWVX	Seattle, Wash.	1400
KSJZ	Salt Lake City, Utah	1160	KTYM	Inglewood, Calif.	1460	KWVY	Seattle, Wash.	1400
KSJM	Salem, Ore.	1230	KUBA	Yuba City, Calif.	1600	KWVZ	Seattle, Wash.	1400
KSJN	Opelousas, La.	1230	KUBC	Montrose, Colo.	580	KWVW	Seattle, Wash.	1400
KSJY	Monte Vista, Colo.	1240	KUCB	Fontaine, Colo.	1050	KWVX	Seattle, Wash.	1400
KSKA	Santa Maria, Calif.	1250	KUCD	Oceanside, Calif.	1450	KWVY	Seattle, Wash.	1400
KSKL	Seminole, Tex.	1010	KUDE	Great Falls, Mont.	1450	KWVZ	Seattle, Wash.	1400
KSMN	Mason City, Iowa	1340	KUDL	Kansas City, Mo.	1380	KWVW	Seattle, Wash.	1400
KSMO	Salem, Mo.	1450	KUDM	Ventura, Calif.	1590	KWVX	Seattle, Wash.	1400
KSNY	Snyder, Tex.	1460	KUDY	Littleton, Colo.	1510	KWVY	Seattle, Wash.	1400
KSO	Des Moines, Iowa	1280	KUEQ	Phoenix, Ariz.	1400	KWVZ	Seattle, Wash.	1400
KSOA	Arkansas City, Kans.	1240	KUGN	Eugene, Ore.	740	KWVW	Seattle, Wash.	1400
KSON	San Diego, Calif.	1280	KUIK	Hillsboro, Tex.	1360	KWVX	Seattle, Wash.	1400
KSDO	Sioux Falls, S.Dak.	1140	KUIJ	Walla Walla, Wash.	1420	KWVY	Seattle, Wash.	1400
KSP	Salt Lake City, Utah	1370	KUKJ	Ukiah, Calif.	1400	KWVZ	Seattle, Wash.	1400
KSOX	Raymondville, Tex.	1240	KUKL	Willow Springs, Mo.	1330	KWVW	Seattle, Wash.	1400
KSPA	Santa Paula, Calif.	1400	KUL	Honolulu, T.H.	690	KWVX	Seattle, Wash.	1400
KSPJ	Stillwater, Okla.	780	KULB	Phonix, Wash.	730	KWVY	Seattle, Wash.	1400
KSPK	Diboll, Tex.	1260	KULC	El Campo, Tex.	1290	KWVZ	Seattle, Wash.	1400
KSPR	Casper, Wyo.	1400	KULP	Penitente, Ore.	1380	KWVW	Seattle, Wash.	1400
KSPS	Sandpoint, Idaho	1400	KUNO	Corpus Christi, Tex.	1380	KWVX	Seattle, Wash.	1400
KSRK	Socorro, N.Mex.	1290	KUOA	Siloam Springs, Ark.	1290	KWVY	Seattle, Wash.	1400
KSRD	Santa Rosa, Calif.	1350	KUOM	Minneapolis, Minn.	770	KWVZ	Seattle, Wash.	1400
KSRV	Ontario, Ore.	1330	KUR	Idaho Falls, Idaho	980	KWVW	Seattle, Wash.	1400
KSTY	Sulphur Springs, Tex.	1280	KURV	Edinburg, Utah	1450	KWVX	Seattle, Wash.	1400
KSTA	Columbia, Tex.	1000	KURY	Brookings, Ore.	910	KWVY	Seattle, Wash.	1400
KSTB	Breckenridge, Tex.	1430	KUSD	Vermillion, S.Dak.	690	KWVZ	Seattle, Wash.	1400
KSTL	St. Louis, Mo.	630	KUSH	Cushing, Okla.	1600	KWVW	Seattle, Wash.	1400
KSTN	Stockton, Calif.	1420	KUSN	St. Joseph, Mo.	1270	KWVX	Seattle, Wash.	1400
KSTP	St. Paul, Minn.	1500	KUYA	Yakima, Wash.	980	KWVY	Seattle, Wash.	1400
KSTR	Grand Junction, Colo.	620	KUVR	Holdrege, Neb.	1470	KWVZ	Seattle, Wash.	1400
KSTT	Davenport, Iowa	1170	KUZN	W. Monroe, La.	1310	KWVW	Seattle, Wash.	1400
KSTV	Stephenville, Tex.	1510	KVAN	Vancouver, Wash.	910	KWVX	Seattle, Wash.	1400
KSUB	Cedar City, Utah	500	KVCK	Wolf Point, Nebr.	1450	KWVY	Seattle, Wash.	1400
KSUE	Susanville, Calif.	1240	KVCL	Winfield, La.	1270	KWVZ	Seattle, Wash.	1400
KSUM	Fairmont, Minn.	1370	KVCR	Redding, Calif.	600	KWVW	Seattle, Wash.	1400
KSUN	Bisbee, Ariz.	1230	KVCS	San Jacinto, Calif.	920	KWVX	Seattle, Wash.	1400
KSVC	Richfield, Utah	980	KVEL	Vernal, Utah	1230	KWVY	Seattle, Wash.	1400
KSWP	Artesia, N.Mex.	990	KVEN	Ventura, Calif.	1450	KWVZ	Seattle, Wash.	1400
KSWA	Granby, N.Mex.	1560	KVET	Austin, Tex.	970	KWVW	Seattle, Wash.	1400
KSWI	Council Bluffs, Iowa	1380	KVFC	Cortez, Colo.	740	KWVX	Seattle, Wash.	1400
KSWO	Lawton, Okla.	1380	KVFD	Fort Dodge, Iowa	1400	KWVY	Seattle, Wash.	1400
KSWR	Roswell, N.Mex.	1230	KVFB	Great Bend, Kans.	1590	KWVZ	Seattle, Wash.	1400
KSYC	Yreka, Calif.	1490	KVHL	Homer, La.	1320	KWVW	Seattle, Wash.	1400
KSYD	Wichita Falls, Tex.	970						
KSYL	Alexandria, La.	970						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WAKE	Atlanta, Ga.	1340	WBBZ	Ponca City, Okla.	1230	WCBI	Columbus, Miss.	550	WCUE	Akron, Ohio	1150
WAKN	Aiken, S.C.	990	WBCA	Bay Minette, Ala.	1500	WCBL	Benton, Ky.	1290	WCUM	Cumberland, Md.	1230
WAKR	Akron, Ohio	1590	WBCE	Bay Pines, Fla.	1490	WCBM	Baltimore, Md.	680	WCVA	Culpeper, Va.	1490
WAKU	Latrobe, Pa.	1470	WBCH	Hastings, Mich.	1220	WCBO	St. Helen, Mich.	1590	WCVI	Conneville, Pa.	1340
WALA	Mobile, Ala.	1510	WBCK	Battle Creek, Mich.	930	WCBS	New York, N.Y.	880	WCVS	Springfield, Ill.	1450
WALB	Albany, Ga.	1590	WBCC	Bay City, Mich.	1440	WCBT	Roanoke Rapids, N.C.	1230	WCWC	Ripon, Wis.	1600
WALD	Waterboro, S.C.	1220	WBCE	Christiansburg, Va.	1200	WCBY	Cheboygan, Mich.	1240	WCYD	Dayton, Ohio	690
WALE	Fall River, Mass.	1400	WBCT	Union, S.C.	1460	WCCE	Hartford, Conn.	1240	WCYN	Cynthiana, Ky.	1400
WALK	Patchogue, N.Y.	1370	WBEC	Pittsfield, Mass.	1430	WCCL	Lawrence, Mass.	800	WDAD	Indiana, Pa.	1450
WALL	Middletown, N.Y.	1340	WBED	Leitersville, Pa.	1570	WCCL	Lawrence, Mass.	1370	WDAM	Tampa, Fla.	1250
WALM	Albany, Mich.	1260	WBEL	Elizabethtown, Tenn.	1240	WCDD	Carbondale, Pa.	1440	WDAL	Meridian, Miss.	1490
WALO	Humacao, P.R.	1240	WBEO	Beloit, Wis.	1380	WCDE	Rocky Mount, N.C.	810	WDAR	Darlington, S.C.	1350
WALT	Tampa, Fla.	1110	WBEP	Buffalo, N.Y.	930	WCDF	Waco, Tex.	1420	WDAS	Philadelphia, Pa.	1480
WALY	Herkimer, N.Y.	1420	WBET	Brockton, Mass.	1460	WCEN	Cambridge, Md.	1240	WDAT	South Daytona Beach, Fla.	1590
WAMD	Aberdeen, Md.	970	WBEU	Beaver Dam, Wis.	960	WCEN	Mt. Pleasant, Mich.	1150	WDAY	Fargo, N. Dak.	970
WAME	Miami, Fla.	1200	WBEV	Beaver Dam, Wis.	960	WCER	Charlottesville, Mich.	1390	WDBE	Escanaba, Mich.	880
WAMI	Opp, Ala.	860	WBEX	Chicklothe, Ohio	1490	WCFC	Chicago, Ill.	1270	WDBF	Delray Beach, Fla.	1420
WAML	Laurel, Mich.	1340	WBFC	Fremont, Mich.	1490	WCFC	Clifton Forge, Va.	1480	WDBJ	Roanoke, Va.	960
WAMM	Flint, Mich.	1420	WBFD	Bedford, Pa.	1310	WCFC	Clifton Forge, Va.	1480	WDBL	Springfield, Tenn.	1590
WAMO	Homestead, Pa.	860	WBGE	Chaple, Fla.	1240	WCFC	Clifton Forge, Va.	1480	WDBM	Statesville, N.C.	550
WAMP	Pittsburgh, Pa.	1320	WBGR	Jesup, Ga.	1370	WCFC	Clifton Forge, Va.	1480	WDBO	Orlando, Fla.	580
WAMS	Wilmington, Del.	1380	WBHB	Fitzgerald, Ga.	1240	WCFC	Clifton Forge, Va.	1480	WDBQ	Ubuque, Iowa	1440
WAMV	E. St. Louis, Ill.	1490	WBHC	Hampden, S.C.	1270	WCFC	Clifton Forge, Va.	1480	WDFD	Dayton, Ohio	1350
WAMW	Washington, Ind.	1340	WBHD	Hamlet, N.C.	1450	WCFC	Clifton Forge, Va.	1480	WDFR	Dayton, Ohio	1470
WAMY	Amherst, Mich.	1380	WBHP	Huntsville, Ala.	1230	WCFC	Clifton Forge, Va.	1480	WDGR	Tarpon Springs, Fla.	1470
WANA	Annisson, Ala.	1490	WBIA	Augusta, Ga.	1230	WCFC	Clifton Forge, Va.	1480	WDRH	Hanover, N.H.	1340
WANB	Waynesburg, Pa.	1580	WBIE	Marietta, Ga.	1050	WCFC	Clifton Forge, Va.	1480	WDRE	Greenville, Miss.	900
WANC	Canton, Ohio	900	WBIG	Greensboro, N.C.	1470	WCFC	Clifton Forge, Va.	1480	WDDY	Gloucester, Va.	1420
WANE	Ft. Wayne, Ind.	1450	WBIL	Leesburg, Fla.	1470	WCFC	Clifton Forge, Va.	1480	WDEC	Americus, Ga.	1290
WANN	Annapolis, Md.	1190	WBIR	Booneville, Miss.	1420	WCFC	Clifton Forge, Va.	1480	WDEF	Chattanooga, Tenn.	1370
WANS	Anderson, S.C.	1280	WBIR	Booneville, Miss.	1420	WCFC	Clifton Forge, Va.	1480	WDFC	Dayton, Ohio	1470
WANT	Richmond, Va.	990	WBIS	Bristol, Conn.	1440	WCFC	Clifton Forge, Va.	1480	WDFF	Wilmington, Del.	1150
WAOK	Atlanta, Ga.	1380	WBIV	Bedford, Ind.	1340	WCFC	Clifton Forge, Va.	1480	WDEW	Waterbury, Vt.	550
WAOW	Vincennes, Ind.	1450	WBIZ	Eau Claire, Wis.	1400	WCFC	Clifton Forge, Va.	1480	WDEW	Westfield, Mass.	1570
WAPA	San Juan, P.R.	680	WBKH	Hattiesburg, Miss.	950	WCFC	Clifton Forge, Va.	1480	WDGJ	Minneapolis, Minn.	1130
WAPP	McComb, Miss.	980	WBKN	Newton, Miss.	1410	WCFC	Clifton Forge, Va.	1480	WDIA	Memphis, Tenn.	1070
WAPG	Acadia, Fla.	1480	WBKV	West Bend, Wis.	1470	WCFC	Clifton Forge, Va.	1480	WDIG	Dothan, Ala.	1450
WAPI	Birmingham, Ala.	1470	WBLC	Belleville, Mo.	1420	WCFC	Clifton Forge, Va.	1480	WDIV	Dayton, Ohio	1350
WAPL	Apule, Ala.	1370	WBLE	Batesville, Miss.	1290	WCFC	Clifton Forge, Va.	1480	WDKD	Kingstree, S.C.	1310
WAPD	Chattanooga, Tenn.	1150	WBLF	Bellefonte, Pa.	1330	WCFC	Clifton Forge, Va.	1480	WDKN	Dickson, Tenn.	1260
WAPX	Montgomery, Ala.	1600	WBLG	Lexington, Ky.	1300	WCFC	Clifton Forge, Va.	1480	WDLA	Walton, N.Y.	1270
WAQE	Towson, Md.	1570	WBLJ	Dalton, Ga.	1230	WCFC	Clifton Forge, Va.	1480	WDLB	Marshfield, Wis.	1450
WARA	Attleboro, Mass.	1320	WBLO	Evergreen, Ala.	1470	WCFC	Clifton Forge, Va.	1480	WDLT	Port Jervis, N.Y.	1490
WARB	Covington, La.	730	WBLS	Batesburg, S.C.	1430	WCFC	Clifton Forge, Va.	1480	WDLR	Panama City, Fla.	590
WARD	Johnstown, Pa.	1490	WBLS	Batesburg, S.C.	1430	WCFC	Clifton Forge, Va.	1480	WDNG	Douglas, Ga.	860
WARE	Ware, Mass.	1240	WBLY	Wilmington, N.C.	1420	WCFC	Clifton Forge, Va.	1480	WDNJ	Marquette, Mich.	1320
WARF	Jasper, Ind.	1490	WBLY	Springfield, Ohio	1600	WCFC	Clifton Forge, Va.	1480	WDNC	Durham, N.C.	620
WARK	Hagerstown, Md.	1490	WBMA	Beaufort, N.C.	1400	WCFC	Clifton Forge, Va.	1480	WDNE	Elkins, W.Va.	1240
WARR	Arlington, Va.	780	WBMC	McMinville, Tenn.	960	WCFC	Clifton Forge, Va.	1480	WDNG	Annisson, Ala.	1450
WARM	Scranton, Pa.	590	WBMD	Baltimore, Md.	750	WCFC	Clifton Forge, Va.	1480	WDNT	Dayton, Tenn.	1370
WARN	Ft. Pierce, Fla.	1350	WBMK	West Point, Ga.	1240	WCFC	Clifton Forge, Va.	1480	WDOR	Protestantsburg, Ky.	1310
WARU	Perry, Ind.	1000	WBML	Wilmington, N.C.	1420	WCFC	Clifton Forge, Va.	1480	WDDC	Chattanooga, Tenn.	1310
WASA	Havre de Grace, Md.	1330	WBNC	Conway, N.H.	1050	WCFC	Clifton Forge, Va.	1480	WDDK	Kingstree, S.C.	1310
WASK	Lafayette, Ind.	1450	WBND	Boonville, Ind.	1540	WCFC	Clifton Forge, Va.	1480	WDDP	Dothan, Ala.	1450
WATA	Boone, N.C.	1450	WBNS	Columbus, Ohio	1460	WCFC	Clifton Forge, Va.	1480	WDDQ	Dothan, Ala.	1450
WATC	Gaylord, Mich.	900	WBNX	New York, N.Y.	1380	WCFC	Clifton Forge, Va.	1480	WDDR	Sturgeon Bay, Wis.	910
WATE	Knoxville, Tenn.	620	WBNY	Buffalo, N.Y.	1430	WCFC	Clifton Forge, Va.	1480	WDDT	Dayton, Ohio	1470
WATG	Ashland, Ohio	1340	WBQB	Galax, Va.	1480	WCFC	Clifton Forge, Va.	1480	WDDU	Durham, N.C.	620
WATH	Athens, Ohio	970	WBQB	Galax, Va.	1480	WCFC	Clifton Forge, Va.	1480	WDDV	Dover, Del.	1410
WATK	Antigo, Wis.	900	WBQF	Virginia Beach, Va.	1600	WCFC	Clifton Forge, Va.	1480	WDDW	Dayton, Ohio	1370
WATM	Attmore, Ala.	1590	WBOK	New Orleans, La.	800	WCFC	Clifton Forge, Va.	1480	WDDX	Dayton, Ohio	1370
WATN	Watertown, N.Y.	1240	WBOP	Pensacola, Fla.	980	WCFC	Clifton Forge, Va.	1480	WDDY	Dayton, Ohio	1370
WATO	Oak Ridge, Tenn.	1490	WBOS	Brookline, Mass.	1600	WCFC	Clifton Forge, Va.	1480	WDDZ	Dayton, Ohio	1370
WATP	Marion, S.C.	1430	WBOW	Terre Haute, Ind.	1230	WCFC	Clifton Forge, Va.	1480	WDEA	Dayton, Ohio	1370
WATR	Waterbury, Conn.	1380	WBOW	Terre Haute, Ind.	1230	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WATS	Sayre, Pa.	960	WBPA	Philadelphia, Pa.	1230	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WATT	Cadillac, Mich.	1240	WBPP	Lock Haven, Pa.	1230	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WATV	Birmingham, Ala.	900	WBRR	Mt. Clemens, Mich.	1430	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WATW	Ashland, Wis.	1400	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WATZ	Alpena, Mich.	1450	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAUC	Wauchoha, Fla.	1310	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAUD	Auburn, Ala.	1430	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAUG	Augusta, Ga.	1350	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAUW	Waukesha, Wis.	1510	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVE	Louisville, Ky.	970	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVI	Dayton, Ohio	1210	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVL	Apollo, Pa.	910	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVN	Stillwater, Minn.	1230	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVO	Avondale Estates, Ga.	1420	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAWP	Avon, Ohio	1420	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAWU	Albertville, Ala.	630	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAVY	Portsmouth, Va.	1350	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAWZ	New Haven, Conn.	1300	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAWK	Kendallville, Ind.	1570	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAXE	Zarephath, N.J.	1390	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAXZ	Chino Beach, Fla.	1370	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAWY	Chippewa Falls, Wis.	1150	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYB	Waynesboro, Va.	1490	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYE	Dundalk, Md.	860	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYN	Rockingham, N.C.	900	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYS	Charlotte, N.C.	610	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYT	Waycross, Ga.	1230	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAYZ	Waynesboro, Pa.	1380	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAZA	Bainbridge, Ga.	1360	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAZF	Yazoo City, Miss.	1430	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WAZL	Hazleton, Pa.	1290	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAA	West Lafayette, Ind.	920	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAB	Babylon, N.Y.	1440	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAC	Cincinnati, Tenn.	1340	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAL	Baltimore, Md.	1090	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAM	Montgomery, Ala.	740	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAP	Ft. Worth, Tex.	570, 820	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAR	Bartow, Fla.	1460	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAT	Marion, Ind.	1400	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAX	Wilkes-Barre, Pa.	1240	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAY	Barnesville, S.C.	740	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBAY	Green Bay, Wis.	1360	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBBA	Pittsfield, Ill.	1580	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBBC	Burlington, N.C.	920	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBCC	Flint, Mich.	1330	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBCE	Rochester, N.Y.	1450	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBBI	Abingdon, Va.	980	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBBI	Richmond, Va.	1450	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.	1480	WDEB	Dayton, Ohio	1370
WBBI	Chicago, Ill.	780	WBRT	Bardonia, N.Y.	1320	WCFC	Clifton Forge, Va.</				

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WEEK	Peoria, Ill.	1350	WFNC	Fayetteville, N.C.	1390	WHA	Madison, Wis.	970	WIAM	Williamston, N.C.	900
WEEL	Fairfax, Va.	1310	WFNM	DeFuniak Springs, Florida	1460	WHAB	Baxley, Ga.	1260	WIBA	Madison, Wis.	1310
WEPP	Pittsburgh, Pa.	1080	WFNS	Burlington, N.C.	1150	WHAI	Greenfield, Mass.	1240	WIBC	Indianapolis, Ind.	1070
WEER	Warrenton, Va.	1570	WFBO	Marietta, Ga.	1430	WHAL	Shelbyville, Tenn.	1400	WIBG	Philadelphia, Pa.	1470
WEU	Reading, Pa.	850	WFBR	Horseshoe, Miss.	1230	WHAM	Rochester, N.Y.	1180	WIBM	Jackson, Mich.	1450
WEEG	Easton, Pa.	1230	WFBS	Milwaukee, Wis.	1400	WHAN	Charleston, S.C.	1340	WIBR	Baton Rouge, La.	1300
WEGC	Concord, N.C.	1410	WFBO	Fort Payne, Ala.	1400	WHAR	Chapel Hill, N.C.	1340	WIBU	Poynette, Wis.	1240
WEHH	Elmira Heights, N.Y.	1590	WFBO	Atlantic City, N.J.	1450	WHAS	Louisville, Ky.	1340	WIBV	Belleville, Ill.	1260
WEIC	Charleston, Ill.	1270	WFBR	Hammond, La.	1400	WHAW	Weston, W.Va.	1450	WIBC	Ashtabula, Ohio	970
WEIM	Fitchburg, Mass.	1280	WFBR	Reidsville, N.C.	1430	WHAY	New Britain, Conn.	910	WICC	Bridgeport, Conn.	600
WEIN	Wairton, W.Va.	1430	WFBR	Freeport, Ill.	1570	WHAY	Troy, N.Y.	1330	WICH	Norwich, Conn.	1310
WEIS	Scranton, Pa.	530	WFBR	Coudersport, Pa.	600	WHB	Seima, Ala.	710	WICK	Seranton, Pa.	1400
WEKR	Fayetteville, Tenn.	1240	WFBR	Fremont, Ohio	900	WHBC	Salta, Ohio	1480	WICO	Salisbury, Md.	1320
WEKY	Richmond, Ky.	1340	WFBR	Savannah, Ga.	1230	WHBF	Rock Island, Ill.	1270	WICE	Eric, Pa.	1480
WEKZ	Monroe, Wis.	1260	WFBR	Franklin, N.C.	1050	WHBG	Harrisonburg, Va.	1360	WICY	Malone, N.Y.	1480
WELC	Welch, W.Va.	1150	WFBR	Caribou, Maine	960	WHBI	Newark, N.J.	1280	WIDU	Fayetteville, N.C.	1600
WELD	Fisher, W.Va.	690	WFBR	Kingston, N.C.	1400	WHBL	Sheboygan, Wis.	1330	WIEU	Elizabethtown, Ky.	1400
WELI	New Haven, Conn.	960	WFBR	London, Ky.	1400	WHBM	Hempstead, N.Y.	1100	WIFM	Elkin, N.C.	1540
WELK	Charlottesville, Va.	1400	WFBR	Lauderdale, Fla.	1400	WHBN	Hartford, Conn.	1420	WIGM	Medford, Wis.	1490
WELL	Battle Creek, Mich.	1400	WFBR	Maysville, Ky.	1240	WHBT	Harriman, Tenn.	1230	WIGP	Decatur, Ga.	970
WELM	Elmira, N.Y.	1400	WFBR	Front Royal, Va.	1450	WHBU	Anderson, Ind.	1240	WIKB	Windsor, Mich.	1230
WELO	Tupelo, Miss.	1490	WFBR	Ft. Walton Beach, Florida	1260	WHBY	Appleton, Wis.	1230	WIKC	Bogalusa, La.	1300
WELP	Easley, S.C.	1360	WFUR	Huntsville, Ala.	1270	WHCC	Waynesville, N.C.	1400	WIKY	Newport, Vt.	420
WELR	Roanoke, Ala.	1360	WFUR	Grand Rapids, Mich.	1570	WHCC	Sparks, Ill.	1230	WILE	Evansville, Ind.	890
WELS	Kingston, N.C.	1010	WFVG	Fredricksburg, Va.	1230	WHCU	Ithaca, N.Y.	1400	WILS	St. Louis, Mo.	1580
WELT	City, Fla.	1450	WFVG	Ft. Camden, N.C.	1460	WHDF	Houghton, Mich.	1400	WILN	Danville, Va.	1430
WEMB	Erwin, Tenn.	1420	WFVW	Camden, Tenn.	1460	WHDH	Boston, Mass.	850	WILM	Galesburg, Ill.	1090
WEMP	Milwaukee, Wis.	1250	WFYC	Alma, Mich.	1280	WHDL	Olean, N.Y.	1450	WILP	Williamsville, Conn.	1400
WENA	Bayamon, P.R.	1560	WGAA	Cedartown, Ga.	1340	WHDM	McKenzie, Tenn.	1440	WILK	Wilkes-Barre, Pa.	980
WENC	Whiteville, N.C.	1220	WGAC	Augusta, Ga.	580	WHEB	Portsmouth, N.H.	750	WILU	Urbana, Ill.	580
WEND	Baton Rouge, La.	1380	WGAD	Gadsden, Ala.	1350	WHFC	Rochester, N.Y.	1460	WILM	Wilmington, Del.	1480
WENE	Endicott, N.Y.	1430	WGAF	Yaldosta, Ga.	910	WHFD	Springfield, Mass.	620	WILN	Frankfort, Ind.	1570
WENK	Union City, Tenn.	1240	WGAI	Easton, N.C.	580	WHFE	Worcester, Mass.	620	WILS	Sanford, Mich.	1320
WENN	Bessemer, Ala.	1450	WGAL	Lancaster, Pa.	1490	WHFR	Memphis, Tenn.	1430	WILZ	St. Petersburg Beach, Florida	1590
WENT	Madison, Tenn.	1430	WGAP	Portland, Maine	560	WHFB	Benton Harbor, Mich.	1060	WIMA	Lima, Ohio	1150
WENT	Gloversville, N.Y.	1340	WGAP	Maryville, Tenn.	1400	WHGC	Cicero, Ill.	1450	WIMO	Winder, Ga.	1300
WENY	Elmira, N.Y.	1230	WGAR	Cleveland, Ohio	1220	WHGR	Houghton L., Mich.	1290	WIMS	Michigan City, Ind.	1420
WEOA	Evansville, Ind.	1400	WGAT	Athens, Ga.	1340	WHHH	Warren, Ohio	1440	WINA	Charlottesville, Va.	1400
WEOK	Port Jervis, N.Y.	1380	WGAV	Waltham, Mass.	1340	WHHY	Montgomery, Ala.	1440	WINC	Chicago, Ill.	1400
WEOU	Elyria, Ohio	930	WGBA	Columbus, Ga.	1270	WHHM	Memphis, Tenn.	1340	WIND	Kenmore, N.Y.	1490
WEPG	S. Pittsburgh, Tenn.	910	WGBB	Freeport, N.Y.	1240	WHIE	Griffin, Ga.	1320	WINF	Manchester, Conn.	1230
WEPM	Martinsburg, W.Va.	1340	WGBE	Evansville, Ind.	1280	WHIM	Medford, Mass.	1430	WING	Dayton, Ohio	1410
WERC	Eric, Pa.	1260	WGBG	Greensboro, N.C.	1400	WHIN	Gallatin, Tenn.	1010	WINI	Murphysboro, Ill.	1420
WERD	Atlanta, Ga.	860	WGBR	Goldsboro, Pa.	910	WHIO	Dayton, Ohio	1290	WINK	Port Myers, Fla.	1240
WERE	Cleveland, Ohio	1800	WGBS	Miami, Fla.	710	WHIP	Mooresville, N.C.	1350	WINL	Tampa, Fla.	1010
WERH	Hamilton, Ala.	970	WGBR	Red Lion, Pa.	1440	WHIR	Danville, Ky.	1230	WINR	Binghamton, N.Y.	680
WERI	Westerly, R.I.	1230	WGCD	Chester, S.C.	1410	WHIS	Bluefield, W.Va.	1440	WINS	New York, N.Y.	1010
WESA	Charleroi, Pa.	940	WGCM	Gulport, Miss.	1240	WHIT	New Bern, N.C.	1450	WINT	Winter Haven, Fla.	1360
WESB	Bradford, Pa.	1490	WGEN	Geneva, Ala.	1150	WHIZ	Zanesville, Ohio	1240	WINX	Rockville, Md.	1600
WESC	Greenville, S.C.	660	WGEA	Indianapolis, Ind.	1590	WHJB	Greensburg, Pa.	620	WINY	Miami, Fla.	940
WESO	Southbridge, Mass.	970	WGEN	Chicago, Ill.	1390	WHJC	Matawan, W.Va.	1360	WIOK	Mount Dora, Fla.	1360
WESR	Tasle, Va.	1400	WGES	Gettysburg, Pa.	1450	WHK	Cleveland, Ohio	1420	WION	Ionia, Mich.	1430
WEST	Easton, Pa.	1400	WGEZ	Beloit, Wis.	1490	WHKK	Akron, Ohio	640	WIOW	Kokomo, Ind.	1350
WESX	Salem, Mass.	1230	WGFV	Covington, Va.	1430	WHKL	Hendersonville, N.C.	1450	WIP	Philadelphia, Pa.	610
WESY	Leland, Miss.	1580	WGFJ	Gainesville, Ga.	550	WHKY	Hickory, N.C.	1280	WIPC	Lake Wales, Fla.	1280
WETB	Johnson City, Tenn.	790	WGGG	Gainesville, Fla.	1230	WHLB	Virginia, Minn.	1440	WIPR	San Juan, P.R.	940
WETO	Gadsden, Ala.	930	WGGH	Marion, Ill.	1150	WHLD	Niagara Falls, N.Y.	1270	WIPS	Tienden, N.Y.	1250
WETU	Wetumpka, Ala.	1250	WGGI	Salamanca, N.Y.	1590	WHLF	South Boston, Va.	1400	WIRA	Fort Pierce, Fla.	1400
WETZ	New Martinsville, West Virginia	1330	WGGJ	Newport News, Va.	1310	WHLI	Hempstead, N.Y.	1100	WIRB	Enterprise, Ala.	600
WEUC	Ponce, P.R.	1420	WGHM	Skowegan, Maine	1150	WHLL	Wheeling, W.Va.	1600	WIRC	Hickory, N.C.	630
WEUP	Huntsville, Ala.	1600	WGHN	Grand Haven, Mich.	1370	WHLN	Northampton, Pa.	550	WIRE	Indianapolis, Ind.	1430
WEVA	Emporia, Va.	860	WGL	Galesburg, Ill.	1400	WHLP	Centerville, Tenn.	1570	WIRJ	Humboldt, Tenn.	740
WEVD	New York, N.Y.	1330	WGLC	Indianapolis, Ind.	1590	WHLS	Port Huron, Mich.	1450	WIRK	Wagram Beach, Fla.	1290
WEVE	Evletts, Minn.	1340	WGLD	Geneva, Ala.	1150	WHLT	Huntington, Ind.	1390	WIRD	Ironton, Ohio	1230
WEW	St. Louis, Mo.	770	WGLM	Charleston, W.Va.	1300	WHMA	Anniston, Ala.	1300	WIRY	Plattsburg, N.Y.	1340
WEWO	Laurinburg, N.C.	1080	WGLN	Fort Wayne, Ind.	1250	WHMB	Hickory, N.C.	1350	WIS	Columbia, S.C.	560
WEXL	Royal Oak, Mich.	1340	WGLT	Cincinnati, O.	1580	WHMC	Charleston, W.Va.	1490	WISC	Madison, Wis.	1480
WEYL	Sanford, N.C.	1290	WGLU	Hollywood, Fla.	1320	WHND	Henderson, N.C.	890	WISE	Asheville, N.C.	1310
WEZB	Homewood, Ala.	1320	WGMS	Washington, D.C.	570	WHNY	McComb, Miss.	1250	WISK	St. Paul, Minn.	1590
WEZE	Boston, Mass.	1260	WGNI	Chicago, Ill.	720	WHO	Des Moines, Iowa	1040	WISL	Shamokin, Pa.	1480
WEZZ	Richmond, Va.	1600	WGN	Wilmington, N.C.	1450	WHOA	San Juan, P.R.	1400	WISN	Milwaukee, Wis.	1580
WEZN	Elizabethtown, Pa.	1600	WGNM	Murfreesboro, Tenn.	1450	WHOC	Philadelphia, Miss.	1490	WISO	Ponce, P.R.	1260
WEZY	Cocoa, Fla.	1480	WGNW	Newburgh, N.Y.	1220	WHOL	Allentown, Pa.	800	WISP	Butler, Pa.	680
WFAA	Dallas, Tex.	570, 820	WGNX	Winter Garden, Fla.	1600	WHOM	New York, N.Y.	1490	WIST	Charlotte, N.C.	780
WFAH	Alliance, Ohio	1310	WGOL	Goldsboro, N.C.	1300	WHOO	Orlando, Fla.	980	WISV	Viroqua, Wis.	1360
WFAK	Farrell, Pa.	1470	WGOW	Georgetown, Ky.	1580	WHOP	Hopkinsville, Ky.	1230	WITA	San Juan, P.R.	1140
WFAS	White Plains, N.Y.	1230	WGPA	Bethlehem, Pa.	1100	WHOS	Decatur, Ala.	800	WITB	Baltimore, Md.	1230
WFAU	Augusta, Me.	1340	WGPC	Cary, Ga.	1450	WHOT	Camptell, Ohio	1570	WITT	Lewisburg, Pa.	1010
WFAV	Falls Church, Va.	1220	WGR	Buffalo, N.Y.	590	WHOW	Clinton, Ill.	580	WITY	Danville, Ill.	980
WFBC	Greenville, S.C.	1330	WGRA	Cairo, Ga.	950	WHPB	Belton, S.C.	1390	WIV	Esper, Ind.	990
WFBD	Fernandina Bch., Fla.	1570	WGRC	Louisville, Ky.	790	WHPE	High Point, N.C.	1070	WIVC	Christiansburg, Va.	1040
WFBB	Altona, Pa.	1340	WGRD	Grand Rapids, Mich.	1410	WHRT	Hartsville, Ala.	860	WIVV	Vieques, P.R.	1370
WFBL	Syracuse, N.Y.	1290	WGRF	Aquadella, P.R.	1340	WHRV	Ann Arbor, Mich.	1600	WIVY	Jacksonville, Fla.	1050
WFBM	Indianapolis, Ind.	1800	WGRM	Greenwood, Miss.	1240	WHSC	Hartsville, S.C.	1450	WIZE	Springfield, Ohio	1340
WFBR	Baltimore, Md.	1300	WGRS	Summerville, Tenn.	1390	WHSN	Huon, N.Y.	930	WIZZ	Streator, Ill.	1250
WFBS	Ft. Walton Bch., Fla.	950	WGRY	Gary, Ind.	260	WHSP	Hayden, N.C.	1230	WJAC	Norfolk, Va.	1400
WFDF	Flint, Mich.	910	WGSA	Savannah, Ga.	1400	WHST	Hattiesburg, Miss.	1230	WJAG	Norfolk, Va.	1400
WFDR	Manchester, Ga.	1370	WGSM	Huntington, N.Y.	740	WHTE	Taliedega, Ala.	1250	WJAK	Jackson, Tenn.	1460
WFEA	Manchester, N.Y.	1370	WGST	Atlanta, Ga.	920	WHTE	Watson, N.J.	1410	WJAM	Marion, Ala.	1310
WFEB	Sylacauga, Ala.	1340	WGSV	Guntersville, Ala.	1270	WHTN	Huntington, W.Va.	800	WJAR	Providence, R.I.	920
WFEC	Miami, Fla.	1340	WGTA	Greenwood, S.C.	1350	WHUC	Cookeville, Tenn.	1400	WJAS	Pittsburgh, Pa.	1320
WFEM	Fitchburg, Mass.	1580	WGTC	Greenville, N.C.	950	WHUD	Hudson, N.Y.	1240	WJAT	Swainsboro, Ga.	800
WFGN	Gaffney, S.C.	1570	WGTL	Kannapolis, N.C.	870	WHUN	Reading, Pa.	1240	WJAX	Jacksonville, Fla.	930
WFGH	Bristol, Va.	980	WGTN	Wilson, N.C.	590	WHVF	Wausau, Wis.	1530	WJAY	Mullins, S.C.	1080
WFHK	Pell City, Ala.	1430	WGTN	Georgetown, S.C.	1400	WHVH	Henderson, N.C.	1450	WJAZ	Albany, Ga.	1250
WFHR	Wis. Rapids, Wis.	1340	WGUP	Cypress Gardens, Fla.	540	WHVR	Hanover, Pa.	1280	WJBB	Beloyleville, Ala.	1230
WFIC	Sumter, S.C.	970	WGU	North Augusta, S.C.	1600	WHY	Rutland, Vt.	1000	WJBC	Bloomington, Ill.	1230
WFIL	Philadelphia, Pa.	1330	WGV	Geneva, N.Y.	1260	WHYB	Bogalusa, La.	910	WJBD	Salem, Ill.	1350
WFIS	Fountain Inn, S.C.	1600	WGV	Greenville, Miss.	1260	WHYH	Roanoke, Va.	910	WJBE	Detroit, Mich.	1500
WFIV	Fairfield, Ill.	1390	WGW	Selma, Ala.	1340	WHYK	Carlisle, Pa.	960	WJBO	Baton Rouge, La.	1150
WFKA	Franklin, Ky.	1490	WGW	Asheboro, N.C.	1260	WHYN	Springfield, Mass.	1370	WJBS	DeLand, Fla.	1490
WFKY	Frankfort, Ky.	970	WGY	Schenectady, N.Y.	810	WHYS	Ocala, Fla.	1370	WJBW	New Orleans, La.	1230
WFLA	Tampa, Fla.	1400	WGVY	Greenville, Ala.	1380	WIAC	San Juan, P.R.	580	WJCD	Seymour, Ind.	1390

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WJCM	Sebring, Fla.	960	WKLM	Wilmington, N.C.	980	WLDI	LaPorte, Ind.	1540	WMP5	Memphis, Tenn.	680
WJDA	Quincy, Mass.	1300	WKLO	Louisville, Ky.	1080	WLOK	Memphis, Tenn.	1480	WMP7	So. Williamsport, Pa.	1450
WJDB	Thomasville, Ala.	650	WKLY	Elkton, N.C.	1440	WL0L	Minneapolis, Minn.	1330	WMR3	Greenville, S.C.	1490
WJDX	Jackson, Miss.	620	WKLY	Paris, Ky.	1440	WL0N	Lincolnton, N.C.	1050	WMR6	Milford, Mass.	1490
WJDY	Salisbury, Md.	1470	WKLY	Hartwell, Ga.	980	WLOS	Asheville, N.C.	1380	WMRE	Monroe, Ga.	1490
WJEF	Grand Rapids, Mich.	1230	WKLL	Kalamazoo, Mich.	1470	WLOU	Louisville, Ky.	1350	WMRF	Lewisport, Pa.	1490
WJEH	Gallipolis, Ohio	990	WKMC	Roaring Sprs., Pa.	1370	WLOW	Portsmouth, Va.	1470	WMRM	Marion, Ind.	860
WJEL	Hagerstown, Md.	1240	WKMF	Flint, Mich.	1470	WLOX	Biloxi, Miss.	1240	WMRN	Marion, Ohio	1490
WJEM	Vadosta, Ga.	1150	WKMH	Dearborn, Mich.	1310	WLOX	Suffolk, Va.	1450	WMRO	Aurora, Ill.	1280
WJER	Dover, Ohio	1450	WKMI	Kalamazoo, Mich.	1360	WLPO	LaSalle, Ill.	1270	WMRP	Flint, Mich.	1570
WJET	Erie, Pa.	1450	WKMT	Kings Mtn., N.C.	1220	WLPR	New Albany, Ind.	1520	WMSA	Masena, N.Y.	1340
WJGD	Columbia, Tenn.	1290	WKNB	New Britain, Conn.	840	WLS	Chicago, Ill.	870	WMSC	Columbia, S.C.	1380
WJHB	Talladega, Ala.	1580	WKNE	Keene, N.H.	1290	WLSC	Loris, S.C.	1520	WMSV	Sylva, N.C.	1400
WJHL	Johnson City, Tenn.	910	WKNY	Saginaw, Mich.	1210	WLSD	Big Stone Gap, Va.	1420	WMSL	Leicester, Ala.	1480
WJHO	Opelika, Ala.	1400	WKNY	Kingsport, N.Y.	1490	WLSE	Wallace, N.C.	1200	WMSR	Raleigh, N.C.	570
WJIG	Tullahoma, Tenn.	740	WKOA	Hopkinsville, Ky.	1480	WLSH	Lansford, Pa.	1410	WMSR	Manchester, Tenn.	1320
WJIM	Lansing, Mich.	1240	WKOB	Souky, Pa.	1240	WLSI	Pikeville, Ky.	900	WMST	Mt. Sterling, Ky.	1150
WJIV	Savannah, Ga.	900	WKOP	Binghamton, N.Y.	1360	WLSM	Louisville, Miss.	1270	WMTA	Cedar Rapids, Iowa	600
WJJC	Commerce, Ga.	1160	WKOW	Madison, Wis.	1070	WLSV	Wellsville, N.Y.	1370	WMTA	Central City, Ky.	1380
WJJD	Chicago, Ill.	1440	WKOX	Framingham, Mass.	1190	WLTC	Gastonia, N.C.	790	WMTA	Vanceville, Ky.	1340
WJLE	Niagara Falls, N.Y.	1490	WK0Y	Bluefield, W.Va.	1240	WLVA	Lynchburg, Va.	590	WMTA	Manistee, Mich.	1300
WJLM	Lewisburg, Tenn.	1490	WK0Z	Kosciusko, Miss.	1350	WLW	Cincinnati, Ohio	700	WMTA	Moultrie, Ga.	1300
WJKO	Springfield, Mass.	1600	WKPA	New Kensington, Pa.	1150	WLYC	Williamsport, Pa.	1050	WMTR	Morrilton, N.J.	1250
WJLB	Detroit, Mich.	1400	WKPT	Kingsport, Tenn.	1400	WLYN	Lynn, Mass.	1400	WMTS	Murfreesboro, Tenn.	860
WJLD	Homewood, Ala.	1400	WKRC	Cincinnati, Ohio	550	WMAF	Madison, Mich.	1400	WMU5	Muskegon, Mich.	1090
WJLK	Asbury Park, N.J.	1310	WKRG	Mobile, Ala.	710	WMAG	Forest, Miss.	860	WMU6	Greenville, S.C.	1260
WJLS	Beckley, W.Va.	560	WKRM	Carroll, Tenn.	1340	WMAJ	State College, Pa.	1450	WMVA	Martinsville, Va.	1450
WJMA	Orange, Va.	1340	WKRO	Carro, Ill.	1490	WMAK	Nashville, Tenn.	1300	WMVB	Millville, N.J.	1450
WJMB	Brownhaven, Miss.	1340	WKRS	Waukegan, Ill.	1220	WMAL	Washington, D.C.	630	WMVG	Milledgeville, Ga.	1450
WJMC	Rice Lake, Wis.	1240	WKRT	Cortland, N.Y.	920	WMAM	Marinette, Wis.	570	WMVJ	Wilmington, Ohio	1300
WJMJ	Philadelphia, Pa.	1540	WKRR	Oit City, Pa.	1340	WMAN	Mansfield, Ohio	1400	WMVY	Myrtle Beach, S.C.	1450
WJMO	Cleveland, Ohio	1540	WKSB	Milford, Del.	930	WMAP	Manro, N.C.	1060	WMYN	Mayodan, N.C.	1420
WJMR	New Orleans, La.	990	WKSR	Pulaski, Tenn.	1420	WMAQ	Chicago, Ill.	670	WMYR	Ft. Myers, Fla.	1410
WJMS	Ironwood, Mich.	630	WKST	New Castle, Pa.	1200	WMAS	Springfield, Mass.	1450	WNAB	Bridgeport, Conn.	1450
WJMW	Athens, Ala.	730	WKTC	Columbia, N.C.	1310	WMAX	Grand Rapids, Mich.	1480	WNAC	Boston, Mass.	680
WJMX	Florence, S.C.	970	WKTF	Warrenton, Va.	1420	WMAY	Springfield, Ill.	970	WNAD	Norman, Okla.	1310
WJNJ	Jackson, N.C.	1240	WKTH	Thomasville, Ga.	730	WMAZ	Macon, Ga.	940	WNAE	Warren, Pa.	1400
WJNO	W. Palm Beach, Fla.	1230	WKTL	Sheboygan, Wis.	950	WMBA	Ambridge, Pa.	1400	WNAG	Warren, Pa.	1400
WJOB	Hammond, Ind.	1230	WKTM	Mayfield, Ky.	1050	WMBC	Macon, Miss.	1470	WNAN	Nashville, Tenn.	1330
WJOC	Jamestown, N.Y.	1340	WKTP	South Paris, Maine	1450	WMBG	Richmond, Va.	1380	WNAP	Nanticoke, Pa.	730
WJOD	Ward Ridge, Fla.	1570	WKTX	Atlantic Beach, Fla.	1600	WMBH	Joplin, Mo.	1450	WNAM	Neanah, Wis.	1280
WJOI	Florence, Ala.	1340	WKTY	Ladson, Wis.	580	WMBI	Chicago, Ill.	1110	WNAR	Norristown, Pa.	1110
WJOL	Joliet, Ill.	1340	WKUL	Carlisle, N.C.	1340	WMBL	Morehead City, N.C.	740	WNAT	Natchez, Miss.	1450
WJON	St. Cloud, Minn.	1260	WKVA	LeWiston, Pa.	920	WMBM	Miami Beach, Fla.	800	WNAU	New Albany, Miss.	1430
WJOT	Lake City, S.C.	1260	WKWB	San Juan, P.R.	810	WMBN	Peteoskey, Mich.	1400	WNAV	Areton, S. Dak.	570
WJOY	Burlington, Vt.	1230	WKWF	Key West, Fla.	1600	WMBR	Jacksonville, Fla.	1460	WNBK	Binghamton, N.Y.	1290
WJPA	Washington, Pa.	1450	WKWX	Wheeling, W.Va.	1400	WMBU	Uniontown, Pa.	590	WNBH	New Bedford, Mass.	1340
WJPD	Ishpeming, Mich.	1240	WKXL	Concord, N.H.	1450	WMC	Memphis, Tenn.	790	WNBP	Newburyport, Mass.	1470
WJPF	Herrin, Ill.	1340	WKXY	Knoxville, Tenn.	990	WMCA	New York, N.Y.	570	WNBS	Murray, Ky.	1340
WJPG	Green Bay, Wis.	1440	WKY	Yonkers, N.Y.	930	WMCC	New York, N.Y.	570	WNBT	Wellsboro, Pa.	1490
WJPR	Greenville, Miss.	1330	WKYK	Okla. City, Okla.	930	WMCC	Church Hill, Tenn.	1260	WNBZ	Saranac Lake, N.Y.	1490
WJPS	Evansville, Ind.	1300	WKYB	Paducah, Ky.	570	WMCK	McKeesport, Pa.	1600	WNCA	Siler, N.C.	1570
WJQS	Jackson, Miss.	1430	WKYR	Keyser, W.Va.	1270	WMCW	Harvard, Miss.	1220	WNCC	Barnesboro, Pa.	950
WJRW	Detroit, Mich.	760	WKYU	Louisville, Ky.	900	WMD	Fajardo, P.R.	1490	WNDB	Daytona Beach, Fla.	1150
WJRD	Tuscaloosa, Ala.	1150	WKZ	Kalamazoo, Mich.	590	WMDN	Midland, Mich.	1490	WNEB	Syracuse, N.Y.	1260
WJRI	Lenoir, N.C.	1340	WLAC	Nashville, Tenn.	1510	WMEG	Eau Gallie, Fla.	920	WNEC	Worcester, Mass.	1230
WJSB	Crestview, Fla.	1050	WLAD	Danbury, Conn.	800	WMEN	Tallahassee, Fla.	1330	WNEG	Tacoa, Ga.	1320
WJTN	Jamestown, N.Y.	1240	WLAF	LaFollet, Tenn.	1460	WMET	Miami Beach, Fla.	1490	WNEH	Live Oak, Fla.	1260
WJUN	Mexico, Pa.	1580	WLAK	Lakeland, Fla.	1430	WMEV	Marion, Va.	1010	WNEK	Central City, Ky.	1600
WJVA	South Beach, Ind.	850	WLAL	Lake Land, Fla.	1470	WMFC	Monroeville, Ala.	1360	WNEW	New York, N.Y.	1130
WJWL	Georgetown, Del.	900	WLAM	Lewiston, Maine	1470	WMFD	Wilmington, N.C.	630	WNEX	Macon, Ga.	1400
WJWS	South Hill, Va.	1370	WLAN	Lancaster, Pa.	1390	WMFG	Hibbing, Minn.	1240	WNGD	Mayfield, Ky.	1320
WJXN	Jackson, Miss.	1450	WLAP	Lexington, Ky.	610	WMFH	High Point, N.C.	1450	WNHC	New Haven, Conn.	1340
WJZM	Clarksville, Tenn.	1400	WLAR	Rome, Ga.	1430	WMFI	Daytona Beach, Fla.	1450	WNIA	Cheektowaga, N.Y.	1510
WKAB	Mobile, Ala.	1510	WLAR	Arens, Tenn.	1490	WMFR	High Point, N.C.	1230	WNIC	Arietta, Pa.	1290
WKAC	Macon, Ga.	1450	WLAT	Conway, S.C.	1300	WMFS	Chattanooga, Tenn.	1260	WNIS	Siler, N.C.	1570
WKAL	Rome, N.Y.	1450	WLAV	Grand Rapids, Mich.	1340	WMFT	Terre Haute, Ind.	1300	WNJR	Newark, N.J.	1430
WKAM	Goshen, Ind.	1460	WLAW	Muskegon, Mich.	1450	WMGA	Moutrie, Va.	1400	WNKY	Neon, Ky.	1480
WKAN	Kankakee, Ill.	1320	WLBA	Gainesville, Ga.	1580	WMGM	New York, N.Y.	1050	WNLA	Indianola, Miss.	1380
WKAP	Allentown, Pa.	1320	WLBB	Carrollton, Ga.	1390	WMGR	Bainbridge, Ga.	930	WNLC	New London, Conn.	1490
WKAQ	San Juan, P.R.	580	WLBC	Muncie, Ind.	930	WMGW	Meadville, Pa.	1490	WNLK	Norwalk, Conn.	1590
WKAR	East Lansing, Mich.	1370	WLBE	Ellettsville, Ind.	860	WMGY	Montgomery, Ala.	800	WNMF	Evansport, N.C.	1580
WKAT	Maumee, Fla.	1490	WLBS	Laurens, S.C.	790	WMIC	Monroe, Mich.	1340	WNNA	Newton, N.C.	1530
WKAW	Glasgow, Ky.	850	WLBT	Mattoon, Ill.	1170	WMID	Atlanta, Ga.	1140	WNNT	Newton, N.J.	1360
WKAZ	Charleston, W.Va.	910	WLBU	Bowling Green, Ky.	1410	WMIE	Hamlet, Fla.	1140	WNNT	Warsaw, Va.	690
WKBC	N. Wilkesboro, N.C.	850	WLBU	DeKalb, Ill.	1360	WMIL	Midleboro, Ky.	560	WNNE	New Orleans, La.	1060
WKBB	La Crosse, Wis.	1410	WLBU	Auburndale, Wis.	930	WMIL	Milwaukee, Wis.	1290	WNNG	Naples, Fla.	1270
WKBI	St. Mary's, Pa.	1400	WLBN	Lebanon, Ky.	1580	WMIN	Mpls.-St. Paul, Minn.	1450	WNOK	Columbia, Va.	1230
WKBJ	Milan, Tenn.	1500	WLBR	Bangor, Maine	620	WMIP	Iron Mountain, Mich.	1400	WNOP	Port Jervis, N.Y.	740
WKBL	Covington, Tenn.	570	WLCK	Scottsville, Ky.	1250	WMIS	Natchez, Miss.	1240	WNOR	Norfolk, Va.	1230
WKBN	Youngstown, Ohio	1230	WLCM	Lancaster, S.C.	1360	WMIX	Mt. Vernon, Ill.	940	WNOS	High Point, N.C.	1590
WKBO	Harrisburg, Pa.	1490	WLCO	Eustis, Fla.	1240	WMJM	Cordele, Ga.	1490	WNOW	York, Pa.	1250
WKBR	Manchester, N.H.	1240	WLCS	Baton Rouge, La.	910	WMJP	Pineville, Ky.	1230	WN0X	Knoxville, Tenn.	990
WKBV	Richmond, Ind.	1490	WLCS	Atlantic City, N.J.	1580	WMML	Milton, Pa.	570	WNPS	New Orleans, La.	1450
WKBW	Buffalo, N.Y.	1520	WLDB	Atlantic City, N.J.	1180	WMMS	Sylacauga, Ala.	1290	WNPT	Tuscaloosa, Ala.	1250
WKCB	Muskegon, Mich.	950	WLDB	Atlantic City, N.J.	1180	WMML	Dublin, Ga.	1440	WNRB	Windsor, N.C.	1280
WKCB	Berlin, N.H.	830	WLDB	Atlantic City, N.J.	1180	WMML	Millville, N.J.	1240	WNRS	Woodscock, R.I.	1380
WKCT	Bowling Green, Ky.	1320	WLDB	Atlantic City, N.J.	1180	WMML	Millbourne, Pa.	1400	WNRW	Narrows, Va.	1260
WKDA	Nashville, Tenn.	1240	WLDB	Atlantic City, N.J.	1180	WMML	Marshall, N.C.	1460	WNRL	Laurel, Miss.	990
WKDK	Newberry, S.C.	1240	WLDB	Atlantic City, N.J.	1180	WMML	Fairmont, W.Va.	920	WNRT	Newark, N.J.	1290
WKDL	Clarksdale, Miss.	1600	WLDB	Atlantic City, N.J.	1180	WMML	Bath, Maine	730	WNVA	Norton, Va.	1350
WKDN	Clarkden, N.J.	800	WLDB	Atlantic City, N.J.	1180	WMML	McMinnville, Tenn.	1230	WNVY	Pensacola, Fla.	1370
WKDX	Hamlet, N.C.	1400	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	WNVC	New York, N.Y.	1530
WKDY	Kewanee, Ill.	1500	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	WNVA	Salamanca, N.Y.	1590
WKEL	Wayne, Del.	1450	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	WNVT	Portsmouth, Ohio	1260
WKEU	Griffin, Ga.	1450	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0AI	San Antonio, Tex.	1200
WKEY	Covington, Va.	1340	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0AP	Oak Hills, W.Va.	1080
WKEN	Knoxville, Tenn.	1340	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0AY	Waco, Mich.	860
WKHM	Jackson, Mich.	970	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0B1	Jacksville, Fla.	1360
WKIC	Hazard, Ky.	1430	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0B2	Randyland, Wis.	1240
WKID	Urbana, Ill.	1560	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0B3	Davenport, Iowa	1420
WKIK	Covington, Md.	1370	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0C5	W. Yarmouth, Mass.	1240
WKIP	Poughkeepsie, N.Y.	1450	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0CH	North Vernon, Ind.	1460
WKIS	Orlando, Fla.	740	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0HI	E. Liverpool, Ohio	1490
WKIT	Mineola, N.Y.	1520	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0HO	Toledo, Ohio	1470
WKIX	Raleigh, N.C.	850	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0HP	Hellfontaine, Ohio	1390
WKJB	Mayaguez, P.R.	710	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0HS	Shelby, N.C.	730
WKJG	Fort Wayne, Ind.	880	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0IA	Ames, W.Va.	640
WKKO	Cocoa, Fla.	1570	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0IB	Saline, Mich.	1290
WKKS	Vanceburg, Ky.	1450	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0IC	Columbia, S.C.	1470
WKLA	Ludington, Mich.	1450	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0KE	Oak Ridge, Tenn.	1290
WKLK	St. Albans, W.Va.	1300	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470	W0KI	Meridian, Miss.	1450
WKLE	Washington, Ga.	1370	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470			
WKLK	Clanton, Ala.	960	WLDB	Atlantic City, N.J.	1180	WMML	Meriden, Conn.	1470			
WKLK	Cluquet, Minn.	1230	WLDB	Atlantic City, N.J.	1180	WMML</					

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WOKJ	Jackson, Miss.	1590	WQAM	Miami, Fla.	560	W5FC	Somerset, Ky.	1240	WTMA	Charleston, S.C.	1250
WOKY	Albany, N.Y.	1460	WQBC	Vielsburg, Miss.	1420	WSFT	Thomaston, Ga.	1220	WTMC	Ocala, Fla.	1290
WOKZ	Milwaukee, Wis.	920	WQIB	Meridian, Miss.	1390	W5GA	Savannah, Ga.	1400	WTMJ	Milwaukee, Wis.	1290
WOL	Washington, D.C.	1570	WQJK	Jacksonville, Fla.	1240	W5GC	Elberton, Ga.	1400	WTMT	Louisville, Ky.	1150
WOLF	Syracuse, N.Y.	1490	WQK	Brevelton, S.C.	1480	W5GN	Birmingham, Ala.	610	WTMP	Tampa, Fla.	1620
WOLS	Florence, S.C.	1230	WQKN	Winston, N.C.	1450	W5GO	Saginaw, Mich.	740	WTNT	Thomasville, N.C.	920
WOMI	Owensboro, Ky.	1490	WQUA	Moline, Ill.	1230	W5GK	Stagsville, N.C.	1490	WTRD	Orangeburg, S.C.	920
WOMT	Manitowish, Wis.	1240	WQUB	Galesburg, Mo.	1590	W5GL	Baltimore, Md.	1010	WTRN	Frederick, N.J.	1300
WOND	Pleasantville, N.J.	1400	WQXI	Atlanta, Ga.	790	W5GM	Mount Jackson, Va.	790	WTNS	Coshocton, Ohio	1560
WONE	Dayton, Ohio	980	WQX	Ormond Bch., Fla.	1380	W5IP	Paintsville, Ky.	1490	WTNT	Tallahassee, Fla.	1450
WONG	Onondaga, N.Y.	1230	WQXR	New York, N.Y.	1560	W5IR	Winter Haven, Fla.	1490	WTOB	Winston-Salem, N.C.	1380
WONN	Lakeland, Fla.	1230	WQXT	Palm Beach, Fla.	1540	W5IV	Pekin, Ill.	1140	WTOC	Savannah, Ga.	1290
WONW	Denahoe, Ohio	1280	WRAC	Racine, Wis.	1460	W5J	Douville, Tenn.	980	WTOE	Toledo, Ohio	1560
WOOD	Grand Rapids, Mich.	1300	WRAD	Radford, Va.	590	W5JC	Magee, Miss.	1280	WTRP	Spring Pine, N.C.	1470
WOOF	Dothan, Ala.	560	WRAG	Carrollton, Ala.	590	W5JM	St. Joseph, Mich.	1400	WTRR	Sanford, Fla.	1400
WOOG	Washington, D.C.	1340	WRAK	Williamsport, Pa.	1400	W5JN	Winston-Salem, N.C.	600	WTRS	Lawrence, Mo.	1280
WOOD	Deland, Fla.	1310	WRAL	Raleigh, N.C.	1230	W5JK	Montpelier-Barre, Vt.	1240	WTRT	Stanton, Va.	1240
WOOW	Washington, N.C.	1340	WRAM	Monmouth, Ill.	1340	W5KN	San Jose, Calif.	1490	WTRV	Washington, O.C.	1500
WOPA	Oak Park, Ill.	1490	WRAP	Norfolk, Va.	850	W5KP	Asheville, N.C.	1230	WTRW	Torrington, Conn.	1490
WOPR	Bristol, Tenn.	1490	WRAP	Norfolk, Va.	850	W5KY	Miami, Fla.	1430	WTRX	Marianna, Fla.	980
WOR	New York, N.Y.	710	WRAY	Princeton, Ind.	1250	W5LB	Ogdensburg, N.Y.	1400	WTRX	Paris, Tenn.	710
WORR	Mayaguez, P.R.	1150	WRBC	Jackson, Miss.	1300	W5LJ	Jackson, Miss.	930	WTRX	Latrobe, Pa.	1480
WORC	Worcester, Mass.	1310	WRBL	Columbus, Ga.	1420	W5LM	Salem, Ind.	1220	WTRX	Ridge, Tenn.	1570
WORL	Spartanburg, S.C.	910	WRCA	Washington, D.C.	980	W5LN	Roanoke, Va.	610	WTRX	Elkhart, Ind.	1340
WORK	York, Pa.	1350	WRCA	New York, N.Y.	680	W5LO	Nashville, Tenn.	650	WTRX	Bradenton, Fla.	1490
WORL	Boston, Mass.	950	WRCA	New York, N.Y.	680	W5LP	New Orleans, La.	1350	WTRX	Trone, Pa.	1290
WORM	Savannah, Tenn.	1010	WRCD	Richland, Wis.	1450	W5LQ	Sanford, Fla.	1400	WTRX	Dyersburg, Tenn.	1330
WORX	Madison, Ind.	1270	WRCS	Ahokie, N.C.	970	W5LR	Litchfield, Ill.	1540	WTRX	LaGrange, Ga.	620
WOSC	Fulton, N.Y.	1300	WRCV	Philadelphia, Pa.	1060	W5LS	Nashua, N.H.	1590	WTRX	Sanford, Fla.	1400
WOSH	Oskosh, Wis.	1490	WRDB	Reedsburg, Wis.	1400	W5MT	Sparta, Tenn.	1050	WTRX	Lawrence, Mo.	1280
WOSU	Columbus, Ohio	820	WRDD	Augusta, Maine	1400	W5NJ	N.J. Bridgeton, N.J.	1240	WTRX	Two Rivers, Wis.	1590
WOTR	Corry, Pa.	700	WRDW	Augusta, Ga.	1480	W5NT	Sandersville, Ga.	1490	WTRX	Bellaire, Ohio	1290
WOTW	Nashua, N.H.	900	WREB	Holbrook, Mass.	930	W5NU	Seneca, N.Y.	1150	WTRX	Troy, N.Y.	980
WOUR	Athens, Ohio	1340	WREC	Memphis, Tenn.	600	W5NY	Schenectady, N.Y.	1240	WTRX	Brattleboro, Vt.	1450
WOV	New York, N.Y.	1280	WREL	Lexington, Va.	1450	W5OC	Charlotte, N.C.	1240	WTRX	Lumberton, N.C.	1340
WOVE	Welch, W.Va.	1340	WREM	Remsen, N.Y.	1480	W5OD	Henderson, Ky.	860	WTRX	Hanover, N.H.	1400
WOW	Omaha, Neb.	590	WREN	Topeka, Kans.	1250	W5OE	St. Ste. Marie, Mich.	1230	WTRX	Dover, N.H.	1270
WOWI	Florida, Fla.	1240	WREY	Reidsville, N.C.	1220	W5OF	Decatur, Ill.	1340	WTRX	St. Petersburg, Fla.	1380
WOWD	Ft. Wayne, Ind.	1190	WRFB	Worthington, Ohio	880	W5OG	Spartanburg, S.C.	950	WTRX	Ciarento, N.H.	1230
WOWF	Oxford, N.C.	1340	WRFD	Worthington, Ohio	880	W5OH	Sarasota, Fla.	1450	WTRX	Vero Beach, Fla.	1490
WOWK	Ozark, Ala.	900	WRFS	Alexander City, Ala.	1050	W5OI	Toledo, Ohio	1370	WTRX	Port Huron, Mich.	1310
WPAB	Ponce, P.R.	550	WRGA	Rome, Ga.	1470	W5OJ	Saratoga Sprgs., N.Y.	900	WTRX	Wilmington, Del.	1290
WPAC	Patchogue, N.Y.	1580	WRGR	Starkes, Fla.	1490	W5OK	Springfield, Mass.	1270	WTRX	Trenton, N.J.	980
WPAD	Paducah, Ky.	1450	WRGS	Rockersville, Tenn.	1370	W5OL	Stevens Pt., Wis.	1010	WTRX	Watertown, Wis.	1580
WPAG	Ann Arbor, Mich.	1050	WRH	Richmond, Va.	910	W5OM	Ourham, N.C.	1410	WTRX	Westminster, Md.	1470
WPAL	Charleston, S.C.	730	WRHI	Rock Hill, S.C.	1340	W5ON	Ourham, N.C.	1410	WTRX	Bloomington, Ind.	1370
WPAM	Pottsville, Pa.	1450	WRIB	Providence, R.I.	1220	W5OO	Wesley, Ohio	1490	WTRX	Union City, Tenn.	1580
WPAQ	Mount Airy, N.C.	740	WRIC	Richlands, Va.	540	W5OP	Hillsboro, Ohio	590	WTRX	Union City, Tenn.	1580
WPAP	Parkersburg, W.Va.	1450	WRIG	Wausau, Wis.	1400	W5OQ	Durham, N.C.	1490	WTRX	Tupelo, Miss.	580
WPAT	Patonsville, N.J.	930	WRIO	Rio Piedras, P.R.	1320	W5OS	Sumter, S.C.	1340	WTRX	Tuskegee, Ala.	1380
WPAX	Pawtucket, R.I.	550	WRIS	Roanoke, Va.	1410	W5OT	Starkville, Miss.	1230	WTRX	Wilmington, Del.	1290
WPAY	Thomasville, Ga.	1240	WRIS	Roanoke, Va.	1410	W5OU	Petersburg, Va.	1240	WTRX	Coldwater, Mich.	1590
WPAY	Portsmouth, Ohio	1400	WRJA	Lanette, Wis.	1390	W5OV	Charlottesville, Va.	1340	WTRX	Waterbury, Maine	1490
WPAZ	Pottstown, Pa.	1370	WRJV	Riverhead, N.Y.	1400	W5OW	Woodstock, Va.	1230	WTRX	Columbus, Ohio	610
WPBC	Minneapolis, Minn.	980	WRJW	Picayune, Miss.	1320	W5OX	Wilmington, N.C.	1490	WTRX	Thomas, Ga.	1240
WPCC	Clinton, S.C.	1400	WRKD	Rockland, Maine	1450	W5OY	Wilmington, N.C.	1490	WTRX	Auburndale, Fla.	1570
WPCE	Panama City, Fla.	1400	WRKE	Rockwood, Tenn.	580	W5OZ	St. Augustine, Fla.	1420	WTRX	Johnsburg, Vt.	1340
WPCL	Putnam, Conn.	1350	WRKM	Rockwood, Tenn.	580	W5P	Salisbury, N.C.	1490	WTRX	W. Spfld., Mass.	1450
WPDM	Potsdam, N.Y.	1470	WRKN	Montgomery, Ala.	950	W5Q	Sturgis, Mich.	1230	WTRX	Rock Hill, S.C.	1150
WPDQ	Jacksonville, Fla.	600	WRM	Titusville, Fla.	1050	W5R	Stuart, Va.	1450	WTRX	East Longmeadow, Mass.	1600
WPDR	Portage, Wis.	1350	WRMN	Elgin, Ill.	1410	W5S	Groton, Conn.	1420	WTRX	Trion, N.C.	1580
WPDX	Clarksville, W.Va.	750	WRNB	New Bern, N.C.	1490	W5U	Oxford, Miss.	1420	WTRX	Marianna, Fla.	1340
WPFA	Florida, Fla.	1220	WRNL	Richmond, Va.	910	W5UI	Iowa City, Iowa	910	WTRX	Eufaula, Ala.	1240
WPFL	Montpelier, Pa.	1250	WROR	Gulport, Miss.	1390	W5UN	St. Petersburg, Fla.	620	WTRX	Lockport, N.Y.	1340
WPEN	Philadelphia, Pa.	950	WROR	Galena, Miss.	1450	W5UO	Seaford, Del.	1280	WTRX	Bethesda, Md.	1120
WPEO	Peoria, Ill.	1020	WROR	Daytona Beach, Fla.	1340	W5UP	Palatka, Fla.	800	WTRX	Chattanooga, Tenn.	1430
WPEP	Taunton, Mass.	1570	WROK	Rockford, Ill.	1440	W5V	Harrisonburg, Va.	550	WTRX	Coral Gables, Fla.	740
WPET	Greensboro, N.C.	950	WROR	Rome, Ga.	710	W5V	Crewe, Va.	800	WTRX	Chester, Pa.	740
WPF	Pennington, N.J.	790	WRON	Ronceverte, W.Va.	1400	W5W	Belle Glade, Fla.	900	WTRX	Hampton, Va.	1490
WPF	Middletown, Ohio	910	WRON	Scottsboro, Ala.	1330	W5X	Platteville, Wis.	1590	WTRX	Rochester, N.Y.	1280
WPF	Park Falls, Wis.	1450	WROR	Albany, N.Y.	590	W5Y	Rutland, Vt.	1380	WTRX	Vicksburg, Miss.	1490
WPGC	Bradbury Hghts., Md.	1580	WROR	Albany, N.Y.	590	W5Z	Montpelier, Vt.	1300	WTRX	Kisco, N.Y.	310
WPGW	Portland, Ind.	1440	WROR	Clarkdale, Miss.	1450	W5AA	Sylvania, Ga.	1490	WTRX	Caracas, V.Z.	1110
WPHB	Phillipsburg, Pa.	1260	WROY	Carmi, Ill.	1460	W5AB	Syracuse, N.Y.	570	WTRX	Owensboro, Ky.	1420
WPKY	Princeton, Ky.	790	WRPB	Warner Robbins, Ga.	1350	W5AC	Tabor City, N.C.	1370	WTRX	Columbus, Ohio	1580
WPL	Piedmont, Ala.	1280	WRR	Dallas, Tex.	1310	W5AD	Flint, Mich.	930	WTRX	Lexington, Ky.	590
WPL	Huntington, W.Va.	1470	WRR	Washington, N.C.	930	W5AE	Quincy, Ill.	600	WTRX	Oney, Ill.	740
WPLM	Plymouth, Mass.	1390	WRR	Washington, N.C.	930	W5AF	Worcester, Mass.	560	WTRX	St. Carmel, Ill.	1360
WPLY	Plymouth, Wis.	1420	WRR	Washington, N.C.	930	W5AG	Tallahassee, Fla.	1270	WTRX	Wilson, N.C.	1420
WPM	Pennsacoway, Pa.	1540	WRR	Washington, N.C.	930	W5AH	Tallahassee, Fla.	1270	WTRX	Wilson, N.C.	1420
WPMP	Pascagoula, Miss.	1580	WRS	Saratoga Sprgs., N.Y.	1280	W5AI	Clearwater, Fla.	1340	WTRX	Tusculum, Ala.	1590
WPNC	Plymouth, N.C.	1470	WRS	Warsaw, Ind.	1480	W5AJ	Cambridge, Mass.	740	WTRX	Newark, N.J.	620
WPNF	Brexford, N.C.	1460	WRT	Altoona, Pa.	1240	W5AK	LaGrange, Ill.	1300	WTRX	Birmingham, Ala.	690
WPNX	Phenix City, Ala.	1460	WRU	Gainesville, Fla.	850	W5AL	Norfolk, Va.	790	WTRX	Nashville, Tenn.	1470
WPN	Pontiac, Mich.	1460	WRU	Rumford, Maine	790	W5AM	Bryan, Tex.	1150	WTRX	Vidalia, Ga.	970
WPOP	Hartford, Conn.	1410	WRU	Utica, N.Y.	1150	W5AN	Springfield, Ill.	1240	WTRX	Liberty, N.Y.	1240
WPOR	Portland, Maine	1490	WRU	Russellville, Ky.	610	W5AO	Robinson, Ill.	1570	WTRX	Wilson, N.C.	1420
WPPA	New York, N.Y.	1330	WRU	Richmond, Va.	1140	W5AP	Tuscaloosa, Ala.	1230	WTRX	Logan, W.Va.	1290
WPPA	Pottsville, Pa.	1360	WRV	Mt. Vernon, Ky.	1460	W5AQ	Troy, Ala.	970	WTRX	Stroudsburg, Pa.	840
WPPR	Massasoit, P.R.	900	WRVM	Rochester, N.Y.	680	W5AR	Cumberland, Md.	1450	WTRX	Somerset, Pa.	990
WPRC	Lincoln, Ill.	1370	WRW	Kissimmee, Fla.	1570	W5AS	Ft. Monmouth, N.J.	990	WTRX	Grafton, W.Va.	1260
WPRE	Prairie Du Chien, Wis.	980	WRX	Selma, Ala.	1420	W5AT	Tell City, Ind.	1230	WTRX	Waynesburg, S.C.	920
WPR	Prestonsburg, Ky.	960	WSAC	Roxboro, N.C.	1430	W5AU	Traverse City, Mich.	1400	WTRX	Vineland, N.J.	1360
WPR	Providence, R.I.	630	WSAC	Cincinnati, Ohio	1360	W5AV	Minneapolis, Minn.	1280	WTRX	W.C. Gary, Ind.	1270
WPRP	Ponce, P.R.	910	WSAJ	Grove City, Pa.	1340	W5AW	Campbellsville, Ky.	1450	WTRX	Bremen, Ga.	1440
WPRS	Paris, Ill.	1440	WSAL	Louisport, Ind.	1230	W5AX	Ashtand, Ky.	1420	WTRX	Waterbury, Conn.	1240
WPRW	Massasoit, P.R.	900	WSAM	Lawrence, Mo.	1400	W5AY	Fairmont, W.Va.	1490	WTRX	Washington, D.C.	1260
WPRY	Perry, Fla.	1400	WSAN	Allentown, Pa.	1470	W5AZ	Whitefish Bay, Wis.	920	WTRX	New Rochelle, N.Y.	1460
WPT	Raleigh, N.C.	680	WSAR	Fall River, Mass.	1480	W5BA	Philadelphia, Pa.	860	WTRX	Washington, N.C.	1430
WPT	Albany, N.Y.	1540	WSAT	New Smyrna Beach, Fla.	1230	W5BB	Jackson, Ala.	1290	WTRX	Hornell, N.Y.	1320
WPTS	Pittsboro, Pa.	1540	WSAU	Savannah, Ga.	630	W5BC	Terre Haute, Ind.	1480	WTRX	Lauderdale, Fla.	1580
WPTW	Piqua, Ohio	1570	WSAV	Rochester, N.Y.	680	W5BD	Terre Haute, Ind.	1480	WTRX	Baltimore, Md.	1400
WPTX	Lexington Pk., Md.	920	WSAZ	Union, W.Va.	930	W5BE	Hartford, Conn.	1340	WTRX	Canton, N.C.	970
WPV	Pulaski, Va.	1580	WSBA	Atlanta, Ga.	750	W5BF	Tifton, Ga.	1340	WTRX	W. Spfld., Mass.	1450
WPVA	Colonial Hghts., Va.	1290	WSBB	New York, N.Y.	910	W5BG	Massillon, Ohio	900	WTRX	Detroit, Mich.	950
WPVL	Painesville, Ohio	1460	WSBB	New Smyrna Beach, Fla.	1230	W5BH	Durham, N.C.	1310	WTRX	Brooksville, Fla.	1450
WQAM	Chicago, Ill.	1240	WSBB	New Smyrna Beach, Fla.	1230	W5BI	Mayaguez, P.R.	1300	WTRX	Winchester, Ky.	1380
WQBC	Vielsburg, Miss.	1420	WSBT	St. George, N.Y.	860	W5BJ	Taylorville, Ill.	1410	WTRX	New Orleans, La.	870
WQIB	Meridian, Miss.	1390	WSBU	South Bend, Ind.	960	W5BK	Charleston, W.Va.	1240	WTRX	Asheville, N.C.	570
WQJK	Jacksonville, Fla.	1240	WSCM	Panama City Beach, Fla.	1290	W5BL	New Orleans, La.	1350	WTRX	Rochester, N.H.	930
WQK	Brevelton, S.C.	1480	WSD	East Point, Ga.	1260	W5BM	East Point, Ga.	1260	WTRX	Beckley, W.Va.	820
WQKN	Winston, N.C.	1450	WSE	Jackson, Tenn.	1390	W5BN	Staten Island, N.Y.	1390	WTRX	Statesboro, Ga.	1240
WQUA	Moline, Ill.	1230	WSE	Hartford, Wis.	1540	W5BO	Hartford, Wis.	1540	WTRX	Watertown, N.Y	

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WWFA	Williamsport, Pa.	1340	CBX	Edmonton, Alta.	1010	CHRD	Drummondville, Que.	1340
WWFP	Palatka, Fla.	1260	CBXA	Edmonton, Alta.	740	CHRL	Roberval, Que.	910
WWRI	W. Warwick, R.I.	1450	CBY	Corner Brook, Nfld.	1090	CHRS	St. John's, Nfld.	570
WWRL	Woodside, N.Y.	1600	CFAB	Windsor, N.S.	1450	CHSJ	Saint John, N.B.	1150
WWSC	Glens Falls, N.Y.	1450	CFAC	Calgary, Alta.	960	CHUB	Nanaimo, B.C.	1570
WWSR	St. Albans, Vt.	1420	CFAM	Altona, Man.	1290	CHUC	Port Hope, Ont.	1500
WWSW	Wooster, Ohio	960	CFAN	Flin Flon, Man.	590	CHUM	Toronto, Ont.	1050
WWSW	Pittsburgh, Pa.	970	CFBC	Saint John, N.B.	950	CHVC	Niagara Falls, Ont.	1600
WWTB	Tampa, Fla.	1300	CFBR	Sudbury, Ont.	580	CHWK	Chilliwack, B.C.	1270
WVVA	Wheeler, W.Va.	1400	CFBS	Montreal, Que.	600	CHWO	Oakville, Ont.	800
WWVB	Jasper, Alta.	1360	CFCH	North Bay, Ont.	600	CIAD	Montreal, Que.	1250
WWWF	Fayette, Ala.	990	CFCL	Timmins, Ont.	580	CIAT	Trail, B.C.	610
WWWR	Russellville, Ala.	920	CFCN	Calgary, Alta.	1060	CIJAV	Port Alberni, B.C.	1240
WWWW	Rio Piedras, P.R.	1520	CFCO	Chatham, Ont.	630	CIBC	Toronto, Ont.	860
WWXL	Manchester, Ky.	1580	CFCW	Camrose, Alta.	1230	CIBQ	Belleville, Ont.	800
WVVO	Pineville, W.Va.	970	CFCY	Charlottetown, P.E.I.	630	CIBR	Rimouski, Que.	900
WXAL	Dempolis, Ala.	1400	CFDA	Victoriaville, Que.	1380	CIDA	Edmonton, Alta.	930
WXGI	Richmond, Va.	1400	CFDG	Grande Prairie, Alta.	1050	CICB	Sydney, N.S.	1270
WXLJ	Dublin, Ga.	1440	CFDQ	Gravelbourg, Sask.	1230	CICJ	Halifax, N.S.	920
WXLW	Indianapolis, Ind.	950	CFDJ	St. Joseph d'Alma, Que.	1270	CICK	Stratford, Ont.	1240
WXOK	Baton Rouge, La.	1260	CFBT	Brampton, Ont.	1090	CICD	Dawson Creek, B.C.	1350
WXRF	Guayama, P.R.	1500	CFBJ	Kamloops, B.C.	910	CJEM	Edmundston, N.B.	570
WXXX	Hattiesburg, Miss.	1310	CFBK	Brockville, Ont.	1450	CJET	Smiths Falls, Ont.	630
WY2B	Detroit, Mich.	1270	CFBL	Schefferville, Que.	1230	CJFJ	Riviere du Loup, Que.	1400
WYCL	York, N.S.	1170	CFBN	Fredericton, N.B.	550	CJFG	Antigonish, N.S.	580
WYDE	Birmingham, Ala.	850	CFNS	Saskatoon, Sask.	1170	CJGH	Yorkton, Sask.	940
WYFE	New Orleans, La.	600	CFOB	Fort Frances, Ont.	800	CJHJ	Vernon, B.C.	940
WYLD	New Orleans, La.	940	CFOR	Orillia, Ont.	1570	CJIB	Sault Ste. Marie, Ont.	1050
WYMB	Manning, S.C.	1410	CFOS	Owen Sound, Ont.	560	CJKL	Kirkland Lake, Ont.	560
WYSE	Lakeland, Fla.	1330	CFPA	Port Arthur, Ont.	1230	CJLS	Yarmouth, N.S.	1340
WYSR	Franklin, Va.	1250	CFPL	London, Ont.	980	CJMS	Montreal, Que.	1280
WYTH	Madison, Ga.	1250	CFPR	Prince Rupert, B.C.	1240	CJMT	Chicoutimi, Que.	1420
WYTI	Rocky Mount, Va.	1570	CFQC	Saskatoon, Sask.	600	CJNB	N. Baskin, Sask.	1270
WYUW	Newport News, Va.	1270	CFRA	Ottawa, Ont.	560	CJNR	Blind River, Ont.	680
WYVE	Wytheville, Va.	1280	CFRB	Toronto, Ont.	1010	CJOB	Winnipeg, Man.	680
WYZE	Atlanta, Ga.	1480	CFRC	Kingston, Ont.	1490	CJOC	Lethbridge, Alta.	1220
WZIP	Covington, Ky.	1050	CFRG	Gravelbourg, Sask.	710	CJON	St. John's, Nfld.	930
WZKY	Albemarle, N.Dak.	1580	CFRN	Edmonton, Alta.	1260	CJOR	Vancouver, B.C.	600
WZOB	Ft. Payne, Ala.	1250	CFRS	Simcoe, Ont.	1560	CJOY	Guelph, Ont.	1450
WZOK	Jacksonville, Fla.	1320	CFRY	Portage la Prairie, Man.	1570	CJQC	Quebec, Que.	1340
WZRO	Jacksonville Beach, Florida	1010	CFSL	Weyburn, Sask.	1340	CJRH	Richmond Hill, Ont.	1300
WZYX	Cowan, Tenn.	1440	CFUN	Vancouver, B.C.	810	CJRW	Kenora, Ont.	1220
			CHAB	Moose Jaw, Sask.	400	CJRW	Summerside, P.E.I.	1240
			CHAD	Amos, Que.	1340	CJSO	Sorel, Que.	1320
			CHAT	Medicine Hat, Alta.	1270	CJSP	Leamington, Ont.	710
			CHED	Edmonton, Alta.	1080	CJVI	Victoria, B.C.	900
			CHFG	Granby, Que.	1450	CKAC	Montreal, Que.	730
			CHFE	Peterborough, Ont.	980	CKAR	Rimouski, Que.	590
			CHFA	Edmonton, Alta.	680	CKBB	Barrie, Ont.	950
			CHFB	St. Anne de Pocatiere, Que.	1350	CKBC	Bathurst, N.B.	1400
			CHLN	Three Rivers, Que.	550	CKBI	Prince Albert, Sask.	900
			CHLO	St. Thomas, Ont.	680	CKBL	Matane, Que.	1250
			CHLP	Montreal, Que.	1410	CKBM	Montmagny, Que.	1490
			CHLT	Sherbrooke, Que.	680	CKBW	Bridgewater, N.S.	1000
			CHML	Hamilton, Ont.	900	CKCH	Hull, Que.	970
			CHNC	New Carlisle, Que.	610	CKCK	Kenora, Sask.	620
			CHNS	Sudbury, Ont.	900	CKCL	Truro, N.S.	670
			CHNO	Halifax, N.S.	960	CKCQ	Queensl. B.C.	500
			CHOK	Sarnia, Ont.	1070	CKCR	Kitchener, Ont.	1490
			CHOV	Chouinot, Ont.	1350	CKCV	Quebec, Que.	1280
			CHOW	Welland, Ontario	1470	CKCW	Moncton, N.B.	1220
			CHRC	Quebec, Que.	800	CKCY	Sault Ste. Marie, Ont.	1400
						CKDA	Victoria, B.C.	1220
						CKDH	Amherst, N.S.	1400

Canada

CBA	Sackville, N.B.	1070	CHLN	Three Rivers, Que.	550	CKBL	Matane, Que.	1250
CBAF	Moncton, N.B.	1300	CHLO	St. Thomas, Ont.	680	CKBM	Montmagny, Que.	1490
CBE	Windsor, Ont.	1550	CHLP	Montreal, Que.	1410	CKBW	Bridgewater, N.S.	1000
CBF	Montreal, Que.	690	CHLT	Sherbrooke, Que.	680	CKCH	Hull, Que.	970
CBG	Gander, Nfld.	1450	CHML	Hamilton, Ont.	900	CKCK	Kenora, Sask.	620
CBH	Halifax, N.S.	1330	CHNC	New Carlisle, Que.	610	CKCL	Truro, N.S.	670
CBJ	Sydney, N.S.	1140	CHNS	Sudbury, Ont.	900	CKCQ	Queensl. B.C.	500
CBK	Chicoutimi, Que.	1580	CHNO	Halifax, N.S.	960	CKCR	Kitchener, Ont.	1490
CBK	Regina, Sask.	540	CHOK	Sarnia, Ont.	1070	CKCV	Quebec, Que.	1280
CBT	Toronto, Ont.	740	CHOV	Chouinot, Ont.	1350	CKCW	Moncton, N.B.	1220
CBM	Montreal, Que.	940	CHOW	Welland, Ontario	1470	CKCY	Sault Ste. Marie, Ont.	1400
CBT	St. John's, Nfld.	910	CHRC	Quebec, Que.	800	CKDA	Victoria, B.C.	1220
CBQ	Ottawa, Ont.	990				CKDH	Amherst, N.S.	1400
CBT	Grand Falls, Nfld.	640						
CBU	Vancouver, B.C.	850						
CBV	Quebec, Que.	980						
CBW	Winnipeg, Man.	990						

Mexican and Cuban AM Stations

Abbreviations: C.L., call letters; Kc., frequency in kilocycles; W.P., watt power

Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.				
Mexico															
BAJA CALIFORNIA															
Ensenada	XEPF	1400	250	Piedras Negras	XEMJ	920	1000	Camajuani	CMHD	890	1000				
Mexicali	XED	1050	5000		XEMU	560	5000	Ciego de Avila	CMJY	760	1000				
	XEAA	1340	250	Sabinas	XEBK	610	5000	Habana	CMW	550	2500				
	XEAO	910	250	Saltitillo	XESJ	1250	500		CMQ	590	1500				
	XECL	990	5000	Torreón	XESG	1510	1000		CMQ	630	25000				
	XEGE	1570	1000	Villa Acuna	XEBP	1310	5000		CMCO	660	1000				
Tijuana	XEC	1310	250		XEDH	1340	250		CMCB	690	50000				
	XAC	690	50000		XERF	1570	15000		CMCD	740	10000				
	XEAU	1470	5000	DISTRITO FEDERAL									CMCH	790	10000
	XEAZ	1270	500	Mexico City	XEL	1260	5000		CMCZ	830	5000				
	XEBG	1550	1000		XEN	690	20000		CMBL	860	15000				
	XEGM	950	2500		XEQ	940	15000		CMCR	910	10000				
	XEMO	860	5000		XEW	900	25000		CMCF	950	5000				
	XEXX	1420	2000		XEX	730	50000		CMCG	980	5000				
CHIHUAHUA															
Chihuahua	XEM	1390	500		XEFR	1180	5000		CMCA	1010	5000				
	XEBU	620	1000		XEJP	1510	10000		CMCB	1060	10000				
	XEBW	1280	1000		XELA	830	10000		CMCA	1150	10000				
	XEFI	1440	1000		XELM	1440	5000		CMCB	1330	1000				
	XERA	1490	250		XEMX	1820	5000		CMKJ	730	5000				
Ciudad Camargo	XEHA	580	1000		XENK	620	5000		CMKM	560	5000				
Ciudad Delicias	XEBN	1240	250		XEYO	1090	50000		CMKV	600	1000				
	XEKJ	1340	250		XEPH	590	5000		CMKD	970	1000				
	XEF	1420	250		XEQK	1350	1000		CMCD	1290	1000				
	XEJ	970	5000		XEQR	1030	10000		CMZ	1550	5000				
	XEP	1300	500		XERC	790	1000		CMAB	760	5000				
	XEFV	1240	250		XERB	1110	5000		CMAN	840	5000				
	XELO	800	150000		XERS	1500	5000		CMQ	920	1000				
	XEWG	1490	250		XERP	660	10000		CMHJ	570	1000				
	XEYC	1460	1000		XESM	1470	10000		CMHQ	640	15000				
	XEJS	1150	500		XEUN	860	5000		CMHW	810	1000				
Hidalgo	XETX	1010	250	DURANGO									CMHO	1310	1000
N. Casas Grandes				Durango	XEDU	860	1000		CMHM	1130	1000				
COAHUILA															
Ciudad Acuna	XEKD	1010	1000	NUEVO LEON									CMHT	990	1000
Moclova	XEMF	1260	250	Linares	XER	1260	250		CMDA	650	1000				
				Monterrey	XEG	1050	150000		CMKC	770	1000				
					XEL	1420	1000		CMKW	800	2000				
					XET	990	5000		CMKU	850	2000				
					XEAR	1480	1000		CMKN	930	1000				
					XEAW	1280	1000		CMKJ	1170	1000				
					XEFB	630	5000								
					XEMR	1370	300								
					XEOK	920	500								

SAN LUIS POTOSI

San Luis Potosi XEWA 540 150000

SONORA

Agu Prieta XEQA 1490 250

Cananea XEFH 1310 1000

Ciudad Obregon XEFQ 980 500

Hermosillo XEEX 1430 1000

Magdalena XEBH 920 3000

Naco XEDL 1250 500

Nogales XEDM 1580 5000

Santa Ana XEHQ 590 500

XEDJ 1450 100

XETM 1350 1000

XEHF 1570 5000

XEAB 1400 250

XEAD 1450 250

XEAB 1400 250

XEO 970 1000

XEAM 1450 250

XEAT 1340 250

XEAS 1410 250

XEBK 1340 100

XEDF 790 1000

XEF 960 1000

XERG 090 2500

XEXO 1550 50000

XEOR 1390 1000

XERT 590 5000

XEFD 1170 1000

XEFW 810 50000

TAMAULIPAS

XEO 970 1000

XEAM 1450 250

XEAT 1340 250

XEAS 1410 250

XEBK 1340 100

XEDF 790 1000

XEF 960 1000

XERG 090 2500

XEXO 1550 50000

World-Wide Short-Wave Stations

Active and Most Commonly Heard in U. S., Listed by Frequency

(For all Canadian Short-Wave Stations, see separate listing, p. 188) Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000); C.L. call letters. Due to malfunction of transmitter, interference by other stations, jamming, variance in propagational conditions, or reallocation of frequencies, stations may use other frequencies than those given.

The abbreviation (VOA) denotes Voice of America.

The symbol ● denotes stations beaming regular evening broadcasts to the United States.

Kc. C.L. Location	Kc. C.L. Location	Kc. C.L. Location	Kc. C.L. Location
3275 VP4RD Port-of-Spain, Trinidad	6009 HJFC Armenia, Colombia	8235 HRD2 La Ceiba, Hond.	9525 ZBW3 Victoria, Hong Kong
3300 Belize, Brit. Honduras	6010 GRB London, England	8235 Karachi, Pakistan	9527 Warsaw, Poland
3320 YVQG Barcelona, Venez.	6010 OLRA2 Prague, Czecho.	8248 Budapest, Hungary	9530 Honolulu, Hawaii
3330 YVQL El Tigre, Venez.	6010 XEO1 Mexico, Mex.	8285 TGQT Guatemala, Guat.	9530 Manila, Philippines
3340 YVMV Caracas, Venez.	6015 PRA8 Recife, Brazil	8295 OTM1 Leopoldville, Belgian Congo	9530 KCBR Delano, Cal., U.S.A.
3350 YVKT Caracas, Venez.	6018 HJCC Bogota, Col.	8295 TGLA Guatemala, Guat.	9530 WABC New York, U.S.A.
3360 YVOC San Cristobal, Vz.	6020 Ktsw, U.S.S.R.	8320 Baden, Germany	9531 COCO Havana, Cuba
3360 ZQI Kingston, Jamaica	6020 Radio Free Europe, Munich, Germany	8322 COCW Havana, Cuba	9535 HER4 Bern, Switzerland
3365 Grenada, Windward Is.	6020 KNBH(VOA) Dixon, Calif.	8335 TGTA Guatemala, Guat.	9535 SBU Stockholm, Sweden
3370 YVMI Maracaibo, Venez.	6020 XEUV Vera Cruz, Mex.	8335 HRP1 San Pedro Sula, Hond.	9540 VL9 Melbourne, Aus.
3380 YVQR Puerto La Cruz, Vz.	6024 Brazzaville, Fr. Eq. Africa	8374 CSA21 Lisbon, Port.	9540 LG2 Wellington, N. Zeal.
3390 YVKK Caracas, Venez.	6025 Radio Nederland	8405 TGOA Queszaltenango, Guat.	9543 XYZ Rangoon, Burma
3400 YVKK Caracas, Venez.	6025 HJLW Ciudad Trujillo, D.R.	8450 OCY Santa Clara, Cuba	9548 XETT Vera Cruz, Mex.
3410 YVMK Cabimas, Venez.	6030 Stuttgart, Germany	8632 HC2RL Guayaquil, Ecu.	9550 HVI Vatican City
3420 YVVE Merida, Venez.	6030 DZHE Manila, P.I.	8660 HROW Tegucigalpa, Hond.	9550 Paris, France
3440 YVLI Maracaib, Venez.	6030 XEKW Morelia, Mex.	8758 YNVP Managua, Nic.	9550 OLRA3 Prague, Czecho. ●
3460 YVLE Valencia, Venez.	6030 HPS Panama, Pan.	8790 ZJM6 Limassol, Cyprus	9550 Grenada, Windward Is.
3480 YVLE Puerto Cabello, Vz.	6035 GWS London, England	8830 4XB21 Tel Aviv, Israel	9555 OIX2 Pori, Finland
3490 YVRA Maturin, Venez.	6035 XYZ Rangoon, Burma	8870 HC4EB Mantla, Ecuador	9555 XETT Mexico, Mex.
3620 YVLG Maracaib, Venez.	6037 San Jose, Costa Rica	9105 Paris, France	9560 IBD2 Kawaoki, Japan
3980 Suva, Fiji Islands	6040 GSY London, England	9112 CR4AA Praia, Cape V. Isls.	9560 London, England
4650 HC2AJ Guayaquil, Ecu.	6040 KCBR Delano, Calif.	9120 GRM London, England	9560 Paris, France
4752 YVMA Maracaibo, Venez.	6040 Tangier, Tangier	9135 BED7 Taipei, Formosa	9560 WLVO Cincinnati, U.S.A.
4768 HJEF Cali, Colombia	6040 WLDW Cincinnati, U.S.A.	9135 MCM London, England	9560 WRCA New York, U.S.A.
4775 HJBG Bucaramanga, Col.	6045 YDF Djakarta, Indonesia	9145 Radio Free Europe	9565 Kosmoskol, U.S.S.R.
4783 HJAB Barranquilla, Col.	6050 HIIN Ciudad Trujillo, D.R.	9150 GRT London, England	9565 YK3B Recife, Brazil
4790 YVQC Ciudad Bolivar, Vz.	6050 GSA London, England	9155 Moscow, U.S.S.R.	9570 Algiers, Algeria
4797 HJFU Armenia, Colombia	6054 HJEX Cali, Colombia	9175 VUD Delhi, India	9570 GWX London, England
4800 YVME Maracaibo, Venez.	6055 HER2 Bern, Switzerland	9180 JOA Tokyo, Japan	9570 KCBR(VOA) Delano, Calif.
4805 YVSM Manaus, Brazil	6060 GSW London, England	9185 GRK London, England	9570 Bucharest, Rumania
4810 YVMB Maracaibo, Venez.	6060 KNBH(VOA) Dixon, Calif.	9200 GWZ London, England	9570 Rome, Italy
4815 HJBB Cucuta, Col.	6060 Tangier I, Tangier	9205 Warsaw, Poland	9580 GSC London, England
4820 XEJG Guadalajara, Mex.	6060 WDSI New York, U.S.A.	9210 GWL London, England	9580 VLB9 Shepparton, Aus.
4820 YVNB Coro, Venez.	6065 SBO Motala, Sweden	9210 HE13 Bern, Switzerland	9585 Madrid, Spain ●
4830 YVVO San Cristobal, Vz.	6065 XEXE Mexico City, Mex.	9222 Budapest, Hungary	9590 Hiversum, Neth. ●
4835 HJKE Bogota, Colombia	6065 JOB Tokyo, Japan	9230 GSW London, England	9590 WABC New York, U.S.A.
4840 YVQI Valera, Venez.	6070 GR London, England	9240 Moscow, U.S.S.R.	9590 GRY London, England
4845 CSA93 Ponta Delgada, Az.	6075 KGEI San Fran., U.S.A.	9240 Paris, France	9600 KCBR Delano, Cal., U.S.A.
4848 HJGF Bucaramanga, Col.	6080 Munich III, Germany	9250 GWI London, England	9600 (KRCA San Fran., U.S.A.)
4850 YVMS Barquisimeto, Vz.	6081 OAX4Z Lima, Peru	9255 Prague, Czechoslovakia ●	9600 Leningrad, U.S.S.R.
4855 HJFN Neiva, Colombia	6085 ORU Brussels, Belgium	9257 JKH Tokyo, Japan	9605 HP5J Panama, Pan.
4860 IJK Tokyo, Japan	6085 VP4RD Port-of-Spain, Trinidad	9260 GSO London, England	9605 JKL2 Tokyo, Japan
4860 YVPA San Felipe, Venez.	6085 ZYK2 Recife, Brazil	9260 Moscow, U.S.S.R.	9605 Radio Free Europe, Lisbon, Portugal
4865 PRCS Belem, Para, Brazil	6090 GWM London, England	9260 GWN London, England	9607 Athens, Greece
4865 HJFA Pereira, Colombia	6090 WL16 Sydney, Australia	9285 KJK Tokyo, Japan	9610 VLX9 Perth, Australia
4871 HJBG Cucuta, Colombia	6092 Radio Luxemburg	9285 TAS Ankara, Turkey	9610 ZLC8 Rio de Janeiro, Brazil
4880 YVKF Caracas, Venez.	6095 Horby, Sweden	9290 VUD Delhi, India	9610 LY8 Oslo, Norway
4892 YVKB Caracas, Venez.	6095 Radio Free Europe	9295 Moscow, U.S.S.R.	9610 XERQ Mexico, Mex.
4895 HJCH Bogota, Col.	6095 ZYB7 Sao Paulo, Brazil	9300 Radio Free Europe, Bulgaria, Germany	9615 Voice of Amer., Tangier
4895 PRF6 Manaus, Brazil	6095 HJFK Pereira, Colombia	9300 Athens, Greece	9615 VLBS Shepparton, Aus.
4897 VLX3 Perth, Australia	6100 Belgrade, Yugoslavia	9315 YSD San Salvador, Salv.	9618 WRCA New York, U.S.A.
4900 YVUE Ciudad Bolivar, Vz.	6100 WRCA New York, U.S.A.	9320 GRJ London, England	9618 TIDCR San Jose, C.Rica
4903 HJAG Barranquilla, Col.	6110 GSL London, England	9325 BEC36 Taipei, Formosa	9620 Horby, Sweden ● (Nov. to Febr. only)
4907 YVMM Coro, Venez.	6112 HIJZ Ciudad Trujillo, D.R.	9350 Moscow, U.S.S.R.	9620 Paris, France
4910 IJKI Nazaki, Japan	6115 Berlin, Germany	9350 San Salvador, Salv.	9620 Wilmington, N.Z.
4915 ACera, Ghana	6120 HC2FB Guayaquil, Ecu.	9355 ZAA Tirana, Albania	9625 XEBT Mexico, Mex.
4915 YVKK Caracas, Venez.	6120 ZJ14 Limassol, Cyprus	9363 SUX Cairo, Egypt	9625 GWO London, England
4917 HI9B Santiago, Dom. Rep.	6120 Tangier, Tangier	9393 HLIKA Pusan, S. Korea	9625 VP4RD Port-au-Spain, Trinidad
4919 VLM4 Brisbane, Aus.	6120 WRCA New York, U.S.A.	9395 Alicante, Spain	9630 HJIC Bogota, Colombia
4930 HJAP Cartagena, Col.	6122 HJWH Panama, Pan.	9405 HJFK Camaguey, Cuba	9630 HJ4J Delhi, India
4940 YVKK Barquisimeto, Vz.	6124 HRQ San Pedro Sula, Hond.	9405 COCQ Havana, Cuba	9630 Rome, Italy
4950 ZQI Kingston, Jamaica	6125 GWA London, England	9455 COKG Santiago, Cuba	9635 Munich, Germany
4951 Dakar, Senegal	6130 XEUZ Mexico, Mex.	9455 Voice of Zion, Tel Aviv, Israel	9635 Voice of Amer., Tangier
4960 YVQA Cumana, Venez.	6130 Radio Spain ●	9455 COB7 Havana, Cuba	9640 Accra, Ghana
4967 HJAE Cartagena, Col.	6130 COCD Havana, Cuba	9455 HED Cali, Colombia	9640 West Germany Radio, Cologne ●
4970 YVJK Caracas, Venez.	6130 Port Moresby, New Guinea	9455 HJLW Ciudad Trujillo, D.R.	9640 DZH2 Manila, P.I.
4980 YVMO Maracaibo, Vz.	6140 Munich, Germany	9463 TAP Ankara, Turkey	9640 GVZ London, England
4993 HIA Santiago, D.Rep.	6145 HJDE Medellin, Col.	9480 Moscow, U.S.S.R.	9645 Karachi, Pakistan
5010 Grenada, Windward Is.	6147 PRL9 Rio de Janeiro, Br.	9490 KUJ39 Agana, Guam.	9645 LL8 Oslo, Norway
5014 PJC3 Willimstad, Curac.	6150 GRW London, England	9504 OAX4J Lima, Peru	9645 TIFC San Jose, C.Rica
5020 HJFW Manizales, Col.	6150 TGAZ Guatemala, Guat.	9505 COBC Havana, Cuba	9646 HVI Vatican City
5023 HJFE Santiago, D.Rep.	6150 HJIK Bogota, Colombia	9369 Madrid, Spain	9650 Honolulu, Hawaii
5030 YVKK Caracas, Venez.	6160 Honolulu, Hawaii	9380 Khabarovsk, U.S.S.R.	9650 Moscow, U.S.S.R.
5045 ZYP23 Petropolis, Brazil	6165 Munich, Germany	9400 OTM2 Leopoldville, Belgian Congo	9650 Tangier, Tangier
5050 YVKD Caracas, Venez.	6165 GWK London, England	9410 GRI London, England	9650 WDSI(VOA) Brentwood, N. Y.
5053 HI2L Ciudad Trujillo, D.R.	6165 HER3 Bern, Switzerland ●	9440 Brazzaville, Fr. Eq. Africa	9654 OT2 Leopoldville, Belgian Congo
5055 HIJW Medellin, Col.	6167 4VCM Port-au-Prince, H.	9440 GRY London, England	9655 JKC12 Nazaki, Japan
5075 HJKH Sutatenza, Colom.	6170 Munich, Germany	9463 TAP Ankara, Turkey	9656 4VEH Cap-Haitien, Haiti
5085 PZHS Paramaribo, Surinam	6170 HJLW Ciudad Trujillo, D.R.	9480 Moscow, U.S.S.R.	9656 EQC Teheran, Iran
5088 HRN Tshwane, Hand.	6170 KCBR Delano, Cal., U.S.A.	9504 OLRB3 Prague, Czecho.	9660 GWP London, England
5120 HRA Tegucigalpa, Hond.	6170 YVKO Caracas, Venez.	9505 HOLA Colon, Panama	9660 VL9B Brisbane, Aus.
5940 Khabarovsk, U.S.S.R.	6172 ZIM5 Limassol, Cyprus	9505 JBD Kawaoki, Japan	9665 HOU3 Bern, Switzerland
5940 Moscow, U.S.S.R.	6175 XEXA Mexico, Mex.	9510 VYHJ Barquisimeto, Ven.	9668 TGNB Guatemala, Guat.
5952 TQNA Guatemala, Guat.	6180 LRM Mendoza, Argentina	9510 GSB London, England	9670 Munich, Germany
5960 HJCF Bogota, Colombia	6180 Ashkabad, U.S.S.R.	9515 KNBH(VOA) Dixon, Calif.	9670 Voice of Amer., Tangier
5965 Shanghai, China	6180 GRG London, England	9515 TAT Ankara, Turkey	9670 Moscow, U.S.S.R.
5969 HVI Vatican City	6182 TGBW Guatemala, Guat.	9520 Colombo, Ceylon	9675 PW London, England
5970 HI4T Ciudad Trujillo, D.R.	6185 KCBR(VOA) Delano, Calif.	9520 HJFK Bogota, Colombia	9680 Paris, France
5981 HAT Georgetown, Br.Gui.	6185 HJCT Bogota, Colombia	9520 OZF Skamlebak, Denmark ●	9680 XEQQ Mexico, Mex.
5985 Radio Free Europe, Munich, Germany	6190 Frankfurt, Germany	9520 VLT9 Port Moresby, British New Guinea	9680 VUD Delhi, India
5990 TGJA Guatemala, Guat.	6190 IJRT Puerto Plata, D.R.	9520 WLWO Cincinnati, U.S.A.	9680 Moscow, U.S.S.R.
5995 HO50 Panama, Panama	6190 WRCW New York, U.S.A.	9525 GWJ London, England	9680 Voice of America, Tangier
6005 Berlin, Germany	6195 GRN London, England		
6005 HP5K Colon, Panama	6195 Honolulu, Hawaii		
	6200 Paris, France		
	6215 SP13 Warsaw, Poland		

Kc. C.L. Location
 9680 VLR9/VLH9 Melbourne, Australia
 9685 Paris, France
 9685 WLWO Cincinnati, U.S.A.
 9690 LRA Buenos Aires, Arg.
 9690 GRX London, England
 9690 Moscow, U.S.S.R.
 9690 Singapore, Malaya
 9695 KJW2 Kawachi, Japan
 9700 GWY London, England
 9700 WDSI New York, U.S.A.
 9700 Sofia, Bulgaria
 9700 Voice of America, Tangier
 9700 WLWO Cincinnati, U.S.A.
 9700 KCBR Delano, Cal., U.S.A.
 9700 FZFB F., U.S.S.R.
 9710 Moscow, U.S.S.R.
 9710 Dakar, Fr., W. Africa
 9710 YDF6 Jakarta, Indonesia
 9710 Rome, Italy
 9715 Cairo, Egypt
 9716 Moscow, U.S.S.R.
 9720 CGE1 Leipzig, Ger.
 9720 PRL7 Rio de Janeiro, Brazil
 9730 French Equatorial Africa
 9730 Nanking, China
 9730 DZH7 Manila, P.I.
 9730 Leipzig, Germany
 9735 H12T Ciudad, Trujillo, D.R.
 9740 CSA29 Quito, Ecuador
 9743 HC1B Quito, Ecuador
 9745 HC1B (Missionary Station), Quito, Ecuador
 9745 ORU Brussels, Belgium
 9760 CR7BE Lourencia Marques, Mozambique
 9765 TGWA Guatemala, Guat.
 9770 ORU Brussels, Belgium
 9770 PRL4 Rio de Jan., Brazil
 9780 Rome, Italy
 9785 Monte Carlo, Monaco
 9825 GRH London, England
 9833 Budapest, Hungary
 9833 CGE1 Leipzig, Ger.
 9865 YDF8 Jakarta, Indonesia
 9915 GRU London, England
 9966 Brazzaville, Fr. Eq. Africa
 10058 SUV Cairo, Egypt
 10195 Paris, France
 10220 PSH Rio de Janeiro, Brazil
 10268 XRR4 Peking, China
 10270 SD12 Quito, Ecuador
 10272 CSA29 Lisbon, Portugal
 10390 CSA92 PontaDelgada, Azores
 1455 Peking, China
 1475 ZNX52 Barbadoes, B.W.I.
 1513 Tangier, Morocco
 1515 Peking, China
 1515 Leninrad, U.S.S.R.
 1640 All India Radio, Delhi
 1650 Peking, China
 1670 Bangkok, Thailand
 1680 HJCG Bogota, Colombia
 1680 GRG London, England
 1685 Peking, China
 1695 HPSA Panama, Panama
 1700 GWY London, England
 1702 Paris, France
 1705 JOA4 Tokyo, Japan
 1705 SBP Motala, Sweden
 1710 Moscow, U.S.S.R.
 1710 Voice of America, Tangier
 1710 YUD7 Delhi, India
 1710 WLWO Cincinnati, U.S.A.
 1714 ZIM7 Limassol, Cyprus
 1715 HE15 Bern, Switzerland
 1718 Athens, Greece
 1720 PRL8 Rio de Janeiro, Brazil
 1720 Radio Portugal
 1720 OTM4 Leopoldville, Belgian Congo
 1720 ORY2 Brussels, Belgium
 1724 HNG Baghdad, Iraq
 1725 COCY Havana, Cuba
 1730 GVV London, England
 1730 KGE1 San Fran., U.S.A.
 1730 Hiversum, Nether.
 1730 CE1173 Santiago, Chile
 1735 BE06 Taipei, Formosa
 1735 LKQ Frederikstad, Nor.
 1735 Radio Free Europe, Ger.
 1740 Moscow, U.S.S.R.
 1740 Warsaw, Poland
 1740 WRUL Boston, U.S.A.
 1742 CE1174 Santiago, Chile
 1750 GSD London, England
 1755 Radio Portugal
 1760 Moscow, U.S.S.R.
 1760 OLR4B Prague, Czech.
 1760 Voice of America, Tangier
 1760 VLA11/VLB11 Shepparton, Aus.
 1760 VUD7/II Delhi, India
 1764 CR7BH Lourencia Marques, Mozambique
 1770 GVU London, England
 1770 YDE/YDF7 Jakarta, Indonesia
 1775 Radio Poland
 1780 BBC London, England
 1780 Moscow, U.S.S.R.
 1780 XEQH Mexico, D.F.
 1780 ZLS Wellington, N.Z.
 1790 WDSI(VQA) New York
 1790 GWY London, England
 1790 VUD Delhi, India
 1790 WRUL Boston, U.S.A.
 1790 Voice of America, Tangier

Kc. C.L. Location
 11795 West Germany Radio, Cologne
 11795 YDF3 Djakarta, Indonesia
 11795 WRUL Boston, U.S.A.
 11795 Radio Pakistan, Karachi
 11795 ELWA Monrovia, Liberia
 11800 KJ14 Tokyo, Japan
 11800 GWH London, England
 11800 Brussels, Belgium
 11810 Moscow, U.S.S.R.
 11810 Radio Sweden (except—Nov. to Febr.)
 11810 Rome, Italy
 11810 VLA11 Shepparton, Aus. (Morning Program)
 11815 Warsaw, Poland
 11820 GSN London, England
 11820 XEBR Hermosillo, Mex.
 11825 KJ16 Tokyo, Japan
 11825 Moscow, U.S.S.R.
 11825 ZYK3 Recife, Brazil
 11830 FZSA Saigon, Indo-C.
 11830 Moscow, U.S.S.R.
 11830 Voice of America, Tangier
 11830 WBOU(VQA) New York, U.S.A.
 11830 WDSI(VQA) New York, U.S.A.
 11835 CXAI9 Montevideo, Uru.
 11835 PR03 Yokohama, Jap.
 11840 VLW11 Perth, Australia
 11840 OLR4A Prague, Czech.
 11840 LRT Tucuman, Argentina
 11845 Karachi, Pakistan
 11847 Paris, France
 11850 VLB11 Shepparton, Aus.
 11850 ORU Brussels, Belgium
 11850 GNC Guatemala, Guat.
 11850 VLD11 Delhi, India
 11850 LKJ Oslo, Norway
 11855 DZH9 Manila, Philippines
 11855 Radio Free Europe, Lisbon, Portugal
 11860 GSE London, England
 11860 KJ16 Tokyo, U.S.A.
 11865 CR6RA Luanda, Angola
 11865 HER5 Bern, Switzerland
 11870 Munich, Germany
 11870 KNBH San Fran., U.S.A.
 11870 Voice of America, Tangier
 11870 WRUL Boston, U.S.A.
 11875 Radio Prague, Czech.
 11875 Radio Portugal
 11880 Moscow, U.S.S.R.
 11880 LRS Buenos Aires, Arg.
 11880 VLGI1/VLH11 Melbourne, Aus.
 11880 Horby, Sweden
 11880 XEHH Mexico, Mex.
 11880 WGD London, England
 11880 SBP Stockholm, Sweden
 11885 APK3 Karachi, Pakistan
 11890 Moscow, U.S.S.R.
 11890 GWW London, England
 11890 KZFJ Manila, P.I.
 11890 WBOU New York, U.S.A.
 11895 FH83 Dar-es-Salaam, Fr. W. Af.
 11895 Radio Portugal
 11895 Manila, Philippines
 11900 CE1190 Valparaiso, Chile
 11900 CXAI0 Montevideo, Uru.
 11900 HCA1B Calvary Radio Ministry
 11900 XEXE Mexico City, Mex.
 11900 Rome, Italy
 11910 Budapest, Hungary
 11910 Karachi, Pakistan
 11915 Radio Netherlands
 11915 Damascus, Syria
 11915 HC1B Quito, Ecuador
 11915 Radio Portugal
 11918 BE04 Taipei, Formosa
 11924 FZSA Saigon, Vietnam
 11930 GVX London, England
 11935 Warsaw, Poland
 11937 Bucharest, Rumania
 11950 Radio Netherlands
 11950 YSAK Y. Salav, Salvador
 11955 GSD London, England
 11960 Moscow, U.S.S.R.
 11964 Lisbon, Portugal
 11970 Brazzaville, Fr. Eq. Africa
 11972 TIHH San Jose, C. Rica
 11975 Colombo, Ceylon
 11980 BE04 Taipei, Formosa
 11985 CSA32 Lisbon, Portugal
 11998 CE1180 Santiago, Chile
 12040 GRV London, England
 12095 GRF London, England
 12175 TFJ Reykjavik, Iceland
 14492 Radio Moscow
 14690 PSH Rio de Janeiro, Brazil
 15050 EFA Addis Ababa, Eth.
 15050 V3USE Forest Side, Mauritius
 15060 Peking, China
 15070 GWC London, England
 15095 HVJ Vatican City
 15100 CSA39 Lisbon, Portugal
 15100 Moscow, U.S.S.R.
 15100 EPB Teheran, Iran
 15105 KGE1 San Fran., U.S.A.
 15105 OAX4X Lima, Peru
 15110 GWG London, England
 15110 Moscow, U.S.S.R.
 15115 HC1B Quito, Ecuador
 15120 Colombo, Ceylon
 15120 Moscow, U.S.S.R.

Kc. C.L. Location
 15120 Rome, Italy
 15120 Warsaw, Poland
 15125 CSA36 Lisbon, Portugal
 15130 Voice of America, Tangier
 15130 WABC New York, U.S.A.
 15130 WLWO Cincinnati, U.S.A.
 15130 KCBR(VQA) Delano, Calif.
 15130 WBOU Under Brook, N. J., U.S.A.
 15135 Radio Japan, Tokyo
 15135 PRB23 Sao Paulo, Brazil
 15140 GSF London, England
 15150 YDC Djakarta, Indonesia
 15150 ZYK Recife, Brazil
 15150 OAX4 Lima, Peru
 15150 CE1515 Santiago, Chile
 15155 SBT Motala, Sweden
 15156 ZYB9 Sao Paulo, Brazil
 15160 VUD5/7 Delhi, India
 15160 VLB15 Shepparton, Aus.
 15160 TAU Ankara, Turkey
 15165 WLWO Cincinnati, U.S.A.
 15165 ZYK7 Fortaleza, Brazil
 15170 LKV Oslo, Norway
 15170 TGWA Guatemala, Guat.
 15170 Moscow, U.S.S.R.
 15175 LLM Oslo, Norway
 15180 GSO London, England
 15180 Moscow, U.S.S.R.
 15185 DZH2 Islamabad, Den.
 15190 OAX5/11 Lima, Peru
 15190 OIX4 Pori, Finland
 15195 TAQ Ankara, Turkey
 15200 Moscow, U.S.S.R.
 15200 VLA15/VLC15 Shepparton, Aus.
 15205 XESC Mexico, Mexico
 15205 Voice of America, Tangier
 15210 Munich, Germany
 15210 GWU London, England
 15210 WBOU(VQA) New York, U.S.A.
 15210 VLG15 Melbourne, Aus.
 15220 Hiversum, Neth.
 15220 ZL10 Wellington, N.Z.
 15225 IBD3 Kawachi, Japan
 15228 Komsomolsk, U.S.S.R.
 15230 GWD London, England
 15230 Moscow, U.S.S.R.
 15230 OLR5A Prague, Czech.
 15230 VLB15 Melbourne, Aus.
 15230 WRUL Boston, U.S.A.
 15235 BE03 Taipei, Formosa
 15235 JOB5 Tokyo, Japan
 15240 Radio China (Canton)
 15240 Belgrade, Yugoslavia
 15240 KRCA San Fran., U.S.A.
 15240 Paris, France
 15240 VLB15 Melbourne, Aus.
 15240 WGD London, U.S.A.
 15250 Bucharest, Rumania
 15250 Voice of Amer., Manila, P.I.
 15250 WLWO Cincinnati, U.S.A.
 15250 Voice of Amer., Tangier
 15260 GSI London, England
 15260 Karachi, Pakistan
 15270 KCBR Delano, Cal., U.S.A.
 15270 Munich, Germany
 15270 WBOU(VQA) New York, U.S.A.
 15270 Sverdlovsk, U.S.S.R.
 15280 Munich, Germany
 15280 ZL4 Wellington, N.Z.
 15280 Moscow, U.S.S.R.
 15285 Voice of Amer., Tangier
 15285 CR7BG Lourencia Marques, Mozambique
 15285 WBOU(VQA) New York, U.S.A.
 15285 WRUL Boston, U.S.A.
 15290 LRA Buenos Aires, Arg.
 15290 VLW05/9 Delhi, India
 15295 Voice of Amer., Tangier
 15300 DZH8 Manila, P.I.
 15300 GWR London, England
 15300 Singapore, Malaya
 15305 HER6 Bern, Switzerland
 15305 PR03 Yokohama, U.S.S.R.
 15310 KCBR Delano, Calif.
 15310 GSF London, England
 15320 VLG15 Melbourne, Aus.
 15320 Moscow, U.S.S.R.
 15320 OLR5B Prague, Czech.
 15325 Rome, Italy
 15330 KGE1 San Fran., U.S.A.
 15330 Radio Bulgaria
 15330 WLWO Cincinnati, U.S.A.
 15335 Brussels, Belgium
 15335 Karachi, Pakistan
 15340 Moscow, U.S.S.R.
 15340 KCBR Delano, Cal., U.S.A.
 15340 Voice of Amer., Tangier
 15345 Athens, Greece
 15345 Formosa Radio
 15347 LRA Buenos Aires, Arg.
 15350 Paris, France
 15350 WRUL Boston, U.S.A.
 15350 WLWO Cincinnati, U.S.A.
 15350 VLD8 Delhi, India
 15355 Radio Luxembourg
 15360 London, England
 15360 Moscow, U.S.S.R.
 15364 ZYC9 Rio de Jan., Brazil
 15365 Radio Netherlands
 15390 Moscow, U.S.S.R.
 15390 Radio China (Canton)
 15400 Paris, France
 15400 Rome, Italy

Kc. C.L. Location
 15405 DMQ15 Cologne, West Germany
 15405 PZC Paramaribo, Surinam
 15410 Moscow, U.S.S.R.
 15420 Paris, France
 15420 Brazzaville, Fr. Eq. Africa
 15425 Radio Netherlands
 15435 GSD London, England
 15440 Moscow, U.S.S.R.
 15445 Radio Netherlands
 15450 GRZ London, England
 15595 Brazzaville, Fr. Eq. Africa
 15620 Madrid, Spain
 15680 Peking, China
 1720 GVP London, England
 17710 GRUL Boston, U.S.A.
 17715 GRA London, England
 17720 LRA5 Buenos Aires, Arg.
 17730 GVW London, England
 17750 WRUL Boston, U.S.A.
 17750 Rome, Italy
 17760 WGED Schenectady, U.S.A.
 17760 GSO New York, U.S.A.
 17770 KCBR Delano, Cal., U.S.A.
 17770 Rome, Italy
 17770 Voice of America, Tangier
 17770 Radio Sweden, Stockholm
 17775 Hiversum, Netherlands
 17780 VUD10/11 Delhi, India
 17780 GSO New York, U.S.A.
 17780 Voice of Amer., Manila, P.I.
 17784 HER7 Bern, Switzerland
 17785 JOA Tokyo, Japan
 17790 GSG London, England
 17795 WLWO Cincinnati, U.S.A.
 17800 KNBH San Fran., U.S.A.
 17800 WLWO Cincinnati, U.S.A.
 17800 GSD London, England
 17800 Radio Poland
 17800 KRHO Honolulu, Hawaii
 17800 Stockholm, Sweden
 17800 OIX5 Pori, Finland
 17800 Rome, Italy
 17805 D216 Manila, P.I.
 17810 Formosa Radio, Ecuador
 17810 GSD London, England
 17810 Moscow, U.S.S.R.
 17815 WRUL Boston, U.S.A.
 17820 Colombo, Ceylon
 17825 LLN Oslo, Norway
 17825 VAV Ankara, Turkey
 17825 Radio Japan, Tokyo
 17830 Voice of Amer., Ecuador
 17830 WDSI(VQA) New York, U.S.A.
 17835 Karachi, Pakistan
 17840 Radio Sweden
 17840 Brazzaville, Fr. Eq. Africa
 17840 Moscow, U.S.S.R.
 17840 HVJ Vatican City, Aus.
 17840 HVJ Vatican City, Aus.
 17850 Paris, France
 17860 ORU3 Brussels, Belgium
 17865 Damascus, Syria
 17870 CSA44 Lisbon, Portugal
 17890 HC1B (Missionary Station), Quito, Ecuador
 17910 Grenada, Windward Is.
 18250 TETO Paris, France
 18450 United Nations Radio, Geneva, Switzerland
 20088 Moscow, U.S.S.R.
 21460 KNBH (VOA) Dixon, Calif.
 21470 GSH London, England
 21470 Hiversum, Netherlands
 21480 Paris, France
 21500 WRCA New York, U.S.A.
 21510 VUD5 Delhi, India
 21520 HER8 Bern, Switzerland
 21520 WLWO Cincinnati, U.S.A.
 21520 GSD London, England
 21540 BU2 Shepparton, Aus.
 21550 GST London, England
 21560 Moscow, U.S.S.R.
 21560 Rome, Italy
 21570 WDSI(VQA) New York, U.S.A.
 21580 Horby, Sweden
 21590 WGED Schenectady, N.Y.
 21610 WLWO(VQA) Cincinnati, U.S.A.
 21620 Colombo, Ceylon
 21640 GRZ London, England
 21650 WLWO Cincinnati, U.S.A.
 21650 GSD London, England
 21670 LLP Oslo, Norway
 21675 GVR London, England
 21680 VLB21 Shepparton, Aus.
 21690 Voice of America, Tangier
 21700 VUD10 Delhi, India
 21710 GVS London, England
 21730 WBOU(VQA) New York, U.S.A.
 21740 KCBR Delano, Cal., U.S.A.
 21740 KGE1 San Fran., U.S.A.
 21740 Paris, France
 21750 GVT London, England
 25615 OE138 Linz, Austria
 25640 GSD London, Switzerland
 25650 DMQ25 Cologne, West Germany
 25670 GSD London, Stockholm
 25675 Radio Australia, Melbourne
 25750 GSD London, England
 26080 GSK London, England

Canadian Short-Wave Stations

Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000); C.L., call letters

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
5970	CBNX	St. John's, Nfld.	6130	CHNX	Halifax, N.S.	11705	CBFY	Montreal, Que.	15190	CKCX	Montreal, Que.*
5970	CKNA	Montreal, Que.*	6150	CKRO	Winnipeg, Man.	11705	CKXA	Montreal, Que.*	15255	CKSR	Montreal, Que.*
5990	CHAY	Montreal, Que.*	6160	CBUX	Vancouver, B.C.	11720	CBFL	Montreal, Que.	15275	CKBR	Montreal, Que.*
6005	CFXC	Montreal, Que.	6160	CHAC	Montreal, Que.*	11720	CHOL	Montreal, Que.*	15320	CKCS	Montreal, Que.*
6010	CJXC	Sydney, N.S.	9520	CBFR	Montreal, Que.*	11720	CKRX	Winnipeg, Man.	17210	CHSB	Montreal, Que.*
6030	CFVP	Calgary, Alta.	9585	CKLP	Montreal, Que.*	11760	CBFA	Montreal, Que.*	17335	CHRX	Montreal, Que.*
6060	CKRZ	Montreal, Que.*	9610	CBFX	Montreal, Que.	11900	CKEX	Montreal, Que.*	17820	CKRG	Montreal, Que.*
6070	CFRZ	Toronto, Ont.	9610	CHLS	Montreal, Que.*	11945	CKEX	Montreal, Que.*	17865	CHYS	Montreal, Que.*
6080	CKFX	Vancouver, B.C.	9630	CBFO	Montreal, Que.	15090	CKLX	Montreal, Que.*	21600	CKRP	Montreal, Que.*
6090	CBFW	Montreal, Que.	9630	CKLO	Montreal, Que.*	15105	CKUS	Montreal, Que.*	21710	CHLA	Montreal, Que.*
6090	CKOB	Montreal, Que.*	9710	CHLR	Montreal, Que.*	15190	CBFZ	Montreal, Que.	*Transmitter at Sackville, New Brunswick.		

United States FM Stations

(Territories and possessions follow states) Abbreviations: C.L., call letters; Mc., megacycles (for frequency in kilocycles change decimal point to comma and add two zeros); asterisk (*) indicates educational station

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.			
ALABAMA														
Albertville	WAVU-FM	105.1	San Jose	KSJO-FM	92.3	Macon	WMAZ-FM	99.1	Dubuque	WHO-FM	109.3			
Alexander City	WRFS-FM	106.1	San Mateo	KCSM	90.9	Newnan	WCOH-FM	96.7	Iowa City	WDBQ	103.3			
Andalusia	WCTA-FM	98.1	Santa Ana	KWIZ-FM	96.7	Savannah	WTOC-FM	97.3	Mason City	KSUI	91.7			
Anniston	WHMA-FM	100.5	Santa Barbara	KRCW	97.5	Swainshoro	WJAT-FM	101.7	Mason City	KGLO-FM	101.1			
Birmingham	WAPI-FM	99.5	Santa Clara	KSCU	90.1	Toccoa	WLET-FM	106.1	Muscatoine	KWPC-FM	99.7			
	WSFM	93.7	Santa Monica	KCRW	89.9	ILLINOIS						Storm Lake	KAYL-FM	101.5
Clanton	WKLF-FM	100.9	Stockton	KDWC	98.3	Chicago	WBBW-FM	96.3	Waverly	KWAR	89.1			
Cullman	WFMC-FM	101.1	COLORADO						Anna	WRAJ-FM	92.7			
Decatur	WHOS-FM	102.1	Boulder	KRNW	97.3	Bloomington	WJBC-FM	101.5	Bloomington	WJBC-FM	101.5			
Homewood	WJLN	104.7	Colorado Springs	KRCO	91.3	Carmi	WROY-FM	97.3	Chicago	WDBS-FM	97.5			
Lanett	WRLD-FM	102.9	Denver	KFML-FM	98.5	Champaign	WBBW-FM	96.3	Chicago	WBEZ	91.5			
Mobile	WKRQ-FM	99.9	Manitou Springs	KCMS-FM	102.7	Chicago	WBEZ	91.5	Chicago	WCLM	101.9			
Tuscaloosa	WTBC-FM	95.7	CONNECTICUT						Chicago	WDFH	95.5			
	WUOA	*91.7	Brookfield	WGHF	95.1	Decatur	WSEL	104.3	Chicago	WDFH	95.5			
ARIZONA														
Globe	KWJB-FM	100.3	Danbury	WLAD-FM	98.3	Dekalb	WSOY-FM	102.1	Chicago	WDFH	95.5			
Mesa	KYLE-FM	104.7	Hartford	WHCN	105.9	Elgin	WEPS	88.1	Chicago	WDFH	95.5			
Phoenix	KEFE	95.5	Meriden	WMMW-FM	95.7	Elmwood Park	WXFM	105.9	Chicago	WDFH	95.5			
	KFCA	*88.5	New Haven	WNHC-FM	99.1	Evanson	WEAW	105.1	Chicago	WDFH	95.5			
Tucson	KFMM	99.5	Stamford	WSTC-FM	96.7	Harrisburg	WBGQ-FM	99.5	Chicago	WDFH	95.5			
ARKANSAS														
Blytheville	KLCN-FM	96.1	Storrs	WHUS	*90.5	Jacksonville	WBJC-FM	99.5	Chicago	WDFH	95.5			
Ft. Smith	KFPW-FM	94.9	DELAWARE						Macomb	WBIK	91.3			
Jonesboro	KBTM-FM	101.9	Dover	WDOV-FM	94.7	Mattoon	WLBH-FM	96.9	Chicago	WDFH	95.5			
Mammoth Springs	KASU	91.9	Wilmington	WDEL-FM	93.7	Mt. Vernon	WMIX-FM	94.1	Chicago	WDFH	95.5			
Siloam Springs	KAMS	103.9	Washington	WJBR	99.5	Oak Park	WOPA-FM	102.3	Chicago	WDFH	95.5			
	KUOA-FM	105.7	DISTRICT OF COLUMBIA						Olney	WVLF-FM	92.9			
CALIFORNIA														
Atherton	KPEN	101.3	Washington	WASH-FM	97.1	Paris	WPRS-FM	98.3	Chicago	WDFH	95.5			
Bakersfield	KERN-FM	94.1	Washington, D.C.	WOL-FM	98.7	Quincy	WGEN-FM	105.1	Chicago	WDFH	95.5			
Berkeley	KQXR	101.5	Washington	WASH-FM	97.1	Rockford	WROK-FM	97.5	Chicago	WDFH	95.5			
	KQFA	94.1	Washington	WASH-FM	97.1	Rock Island	WHRF-FM	98.9	Chicago	WDFH	95.5			
	KPFZ	*80.3	Washington	WASH-FM	97.1	Springfield	WTAX-FM	103.7	Chicago	WDFH	95.5			
	KRE-FM	102.9	Washington	WASH-FM	97.1	Urbana	WILL-FM	*90.9	Chicago	WDFH	95.5			
Claremont	KSPC	*90.7	Washington	WASH-FM	97.1	INDIANA								
Eureka	KRED-FM	96.3	Washington	WASH-FM	97.1	Bloomington	WFUI	*103.7	Chicago	WDFH	95.5			
Fresno	KARM-FM	101.9	Washington	WASH-FM	97.1	Columbus	WCSE-FM	98.3	Chicago	WDFH	95.5			
	KMJ-FM	97.9	Washington	WASH-FM	97.1	Connersville	WCNB-FM	100.3	Chicago	WDFH	95.5			
	KRFM	93.7	Washington	WASH-FM	97.1	Crawfordsville	WBBS-FM	106.3	Chicago	WDFH	95.5			
Glendale	KFMF	97.1	Washington	WASH-FM	97.1	Elkhart	WCMR-FM	95.1	Chicago	WDFH	95.5			
	KUTE	101.9	Washington	WASH-FM	97.1	Evansville	WKRY-FM	104.1	Chicago	WDFH	95.5			
Long Beach	KFOX-FM	102.3	Washington	WASH-FM	97.1	Gary	WEVC	91.5	Chicago	WDFH	95.5			
	KLON	*88.1	Washington	WASH-FM	97.1	Goshen	WGPS	90.7	Chicago	WDFH	95.5			
	KNOB	97.9	Washington	WASH-FM	97.1	Greencastle	WGBE	91.7	Chicago	WDFH	95.5			
Los Angeles	KABC-FM	95.5	Washington	WASH-FM	97.1	Hammond	WJOD	92.3	Chicago	WDFH	95.5			
	KCBS	105.9	Washington	WASH-FM	97.1	Hartford City	WHCI	*91.9	Chicago	WDFH	95.5			
	KCBH	98.7	Washington	WASH-FM	97.1	Huntington	WVSH	91.9	Chicago	WDFH	95.5			
	KFCF	92.3	Washington	WASH-FM	97.1	Indianapolis	WAJC	*104.5	Chicago	WDFH	95.5			
	KGLA	103.5	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KHJ	101.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KMLA	100.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KNX-FM	93.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KPBQ	104.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KPOL-FM	93.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KRRM	94.7	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KRKD-FM	96.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KUSC	91.5	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KXLU	*88.7	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KHOF	99.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Marysville	KMYC-FM	99.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Modesto	KBEE-FM	103.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KTRB-FM	104.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Oakland	KAFE	98.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Ontario	KASK-FM	93.5	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Pasadena	KPCS	89.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
Sacramento	KCR4-FM	95.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KFBZ-FM	96.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KGMS-FM	100.5	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KJML	95.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KXOA-FM	107.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
San Bernardino	KVCR	*91.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
San Diego	KFSF-FM	94.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KDWD	98.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KTTT	105.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KSDS	*88.3	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
San Francisco	KALW	*91.7	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KCBS-FM	98.9	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
	KDFC	102.1	Washington	WASH-FM	97.1	Indianapolis	WJMS	95.5	Chicago	WDFH	95.5			
FLORIDA														
Daytona Beach	WNDB-FM	94.5	Athens	WGAU-FM	102.5	Terre Haute	WTHI-FM	99.1	Greenfield	WHAJ-FM	98.3			
Gainesville	WRUF-FM	*104.1	Atlanta	WABE	*90.1	Wabash	WWSK	*91.3	Lowell	WHEJ-FM	99.5			
Jacksonville	WJAX-FM	95.1		WAGA-FM	103.5	Warsaw	WRSW-FM	107.3	New Bedford	WBSM-FM	97.7			
	WZFM	96.9		WGIA-FM	92.9	Washington	WFLM	106.5	New Bedford	WBNH-FM	98.1			
	WMBR-FM	96.1		WSB-FM	95.3				S. Hadley	WMHC	88.5			
	WCKR-FM	97.3		WUFG-FM	105.7									
	WGBS-FM	96.3		WBQQ-FM	103.7									
	WTHS	91.7		WRBL-FM	93.3									
	WVMT-FM	93.9		WUN-FM	103.9									
	WKAT-FM	93.1		WLAG-FM	104.1									
	WNET-FM	93.9												
	WDBO-FM	92.3												
	WHOO-FM	96.5												
	WORZ	100.3												
	WQXT-FM	97.9												
	WDLR-FM	98.9												
	WFSU-FM	91.5												
	WDAE-FM	100.7												
	WFLA-FM	93.3												
	WPKM	104.7												
	WTUN	*88.9												
	WPRK	*91.5												
Winter Park														
GEORGIA														

Canadian FM Stations

C.L., call letters, Mc., megacycles (For frequency in kilocycles, change decimal point to comma and add two zeros)

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Brantford, Ont.	CKPC-FM	92.1		CKLC-FM	99.5		CFRA-FM	99.9		CFRB-FM	99.9
Cornwall, Ont.	CKSF-FM	104.5		CKWS-FM	96.3	Quebec, Que.	CHRC-FM	98.1		CHFI-FM	98.1
Edmonton, Alta.	CJRN-FM	100.3	Kitchener, Ont.	CKCR-FM	96.7	Rimouski, Que.	CJBR-FM	101.5		CJRT-FM	91.1
	CJCA-FM	99.5	London, Ont.	CFPL-FM	95.9	St. Catharines, Ont.			Vancouver, B.C.	CBU-FM	105.7
	CKUA-FM	98.1	Montreal, Que.	CFB-FM	95.1	Sydney, N.S.	CKTB-FM	97.7	Verdun, Que.	CKVL-FM	96.9
Ft. William, Ont.	CKPR-FM	94.3		CBM-FM	100.7	Timmins, Ont.	CJCB-FM	94.9	Victoria, B.C.	CKOAF-FM	98.5
Halifax, N.S.	CHNS-FM	96.1	Oshawa, Ont.	CFCF-FM	106.5	Toronto, Ont.	CKGB-FM	94.5	Windsor, Ont.	CKLW-FM	93.9
Kingston, Ont.	CFRC-FM	91.9	Ottawa, Ont.	CKLB-FM	93.5		CBC-FM	99.1	Winnipeg, Man.	CJOB-FM	103.1

United States Television Stations

(Territories and possessions follow states). C.L., call letters; Chan., channel number; asterisk (*) indicates educational station.

Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.	Location	C.L.	Chan.
ALABAMA			New Haven	WNHC-TV	8	IOWA			MINNESOTA		
Andalusia	WAIQ-TV	*2	Waterbury	WATR-TV	53	Ames	WOL-TV	5	Alexandria	KCMT	7
Birmingham	WAFI-TV	13	DIST. OF COLUMBIA			Cedar Rapids	KCRG-TV	9	Austin	KMMT	6
	WBIO-TV	*10	Washington	WMAL-TV	7	Davenport	WMT-TV	2	Duluth	KDAL-TV	3
Decatur	WBRC-TV	6		WRIC-TV	4	Des Moines	WOC-TV	6	Minneapolis	WDSM-TV	6
Dolhan	WMSL-TV	23		WTOP-TV	9		KRNT-TV	8		WCCT-TV	4
Florence	WTVY-TV	6		WTTG	5	Fart Dodge	WHO-TV	13		WTFC-TV	11
Mobile	WOWL-TV	15	FLORIDA			Mason City	KGLO-TV	3	Rochester	KSTP-TV	5
Montgomery	WALA-TV	10	Daytona Beach	WESH-TV	2	Ottumwa	KTVO	3	St. Paul	KTCV-TV	*2
	WKRQ-TV	5	Fort Myers	WINK-TV	11	Sioux City	KTIV	4	MISSISSIPPI		
Munford	WCOV-TV	20	Gainesville	WUFT-TV	*5	Waterloo	KWTV	9	Columbus	WCBI-TV	4
	WSFA-TV	*12	Jacksonville	WFGA-TV	12		KWWL-TV	7	Hattiesburg	WDAM-TV	9
ALASKA				WJCT	12	KANSAS			Jackson	WJTV	12
Anchorage	KENI-TV	2		WJXT	4	Engen	KTVG	6		WLBT	3
	KTVA	11	Miami	WCKT	7	Grand City	KLGD	11	Meridian	WTOK-TV	11
Fairbanks	KFAR-TV	2		WPST-TV	10	Goodland	KBLR-TV	10		WCCT-TV	30
	KTFF	11		WTHS-TV	*2	Great Bend	KCKT	2	Tupelo	WTWV	9
Juneau	KINY-TV	8		WDBO-TV	6	Hays	KAYS-TV	7	MISSOURI		
ARIZONA			Orlando	WLOF-TV	9	Hutchinson	KTWH	12	Cape Girardeau	KFVS-TV	12
Phoenix	KOOL-TV	10	Palm Beach	WPTV	5	Pittsburg	KOAM-TV	7	Columbia	KHNL-TV	7
	KPHO-TV	5	Panama City	WJDM-TV	7	Topeka	WBWB-TV	13	Hannibal	KHGG-TV	7
	KTVK	3	Pensacola	WEAR-TV	3	Wichita	KAKE-TV	10	Jefferson City	KRCG-TV	13
	KVAR	12	St. Petersburg	WSUN-TV	38		KARD-TV	3	Joplin	KODE-TV	12
Tucson	KGUN-TV	12	Tampa	WFLA-TV	8	KENTUCKY			Kansas City	KCMO-TV	5
	KOLD-TV	13		WEDU	3	Lexington	WLEX-TV	18		KMBC-TV	9
	KVOA-TV	4	W. Palm Beach	WEAT-TV	12	Louisville	WKYT	27		WDAF-TV	4
Yuma	KIVA	11	GEORGIA				WAVE-TV	3	Kirksville	KRTO	3
ARKANSAS			Albany	WALB-TV	10	Paducah	WPK-TV	*15	St. Joseph	KFEQ-TV	2
El Dorado	KTVE	10	Atlanta	WAGA-TV	5		WHAS-TV	11	St. Louis	KETC	*9
Ft. Smith	KNAC-TV	5		WSB-TV	2		WQXL-TV	41		KSD-TV	5
Little Rock	KARK-TV	4		WETV	*30	LOUISIANA				KTU	2
	KTHV	13	Augusta	WLVJ-TV	30	Alexandria	KALB-TV	5		KCPD	11
	KATV	7		WLVJ-TV	30	Baton Rouge	WAFB-TV	28	Sedalia	KDRD-TV	6
Texarkana	KCMC-TV	7	Columbus	WRDL-TV	4	Lafayette	WBRZ	2	Springfield	KTTT-TV	10
CALIFORNIA				WTVM	28	Lake Charles	KLFY-TV	10		KYTV	3
Bakersfield	KBKA-TV	29	Macon	WMAZ-TV	13	Monroe	KPLC-TV	7	MONTANA		
	KERO-TV	10	Savannah	WSAV-TV	13	New Orleans	KNOC-TV	23	Billings	KOOK-TV	2
Chico	KHSL-TV	12	Thomasville	WTOC-TV	11		KLSE	*13	Butte	KGHL-TV	8
El Centro	KEM-TV	3		WCTV	6		WDSU-TV	6	Glendive	KXLF-TV	4
Eureka	KIEM-TV	3	IDAHO				WJMR-TV	20	Great Falls	KFBB-TV	5
	KVIQ-TV	6	Boise	KBOI	2	Shreveport	WWL-TV	4		KRTV	3
Fresno	KFRE-TV	12		KIDD-TV	7		WYVE	*8	Helena	KXLJ-TV	12
	KJEO	47	Idaho Falls	KID-TV	3		KSLS-TV	12	Kalispell	KULR	9
	KJM-TV	24	Lewiston	KLEW-TV	3		KTBS-TV	3	Missoula	KMSO-TV	13
Los Angeles	KABC-TV	7	Nampa	KOIX-TV	6	MAINE			NEBRASKA		
	KOP	13	Twin Falls	KLIX-TV	11	Bangor	WABI-TV	5	Hastings	KHAS-TV	5
	KHJ-TV	9	ILLINOIS			Poland Spring	WLBZ-TV	2	Hay Springs	KDHU-TV	4
	KNXT	2	Champaign	WCIA	3	Portland	WMTW-TV	8	Hayes Center	KHPL-TV	6
	KRCA	4	Chicago	WBBM-TV	2	Presque Isle	WCSH-TV	13	Kearney	KHOL-TV	13
	KTLA	5		WGBK	7	MARYLAND			Lincoln	KOLN-TV	10
Oakland	KTTU	17		WGN-TV	9	Baltimore	WJZ-TV	13	North Platte	KUON-TV	*12
Redding	KVIP-TV	7		WNBQ	5		WBAL-TV	11	Omaha	KNOP	2
Sacramento	KBET-TV	10		WTTW	*11	Salisbury	WBAR-TV	11		KMTV	7
	KCRA-TV	3	Danville	WDAZ-TV	24		WBOC-TV	16		KETV	7
Salinas	KSBW-TV	8	Decatur	WVTP	17	MASSACHUSETTS			North Platte	KNOP	2
San Diego	KFMB-TV	8	Harrisburg	WSIL-TV	3	Adams	WDCD	19	Omaha	KNOP	2
	KFSD-TV	16	La Salle	WEEQ-TV	35	Boston	WBZ-TV	4		KMTV	7
(Tijuana, Mex.)	KGO-TV	7	Peoria	WEEK-TV	48		WGBH-TV	*2		KNOP	2
San Francisco	KPIX	5		WMBD	31		WHDH-TV	5		KNOP	2
	KQED	*9		WTVH	19		WNAAC-TV	7		KNOP	2
	KRDN-TV	4	Quincy	WGM-TV	10		WRP	32		KNOP	2
San Jose	KNTN-TV	11	Rockford	WREX-TV	13	Greenfield	WHYN-TV	40		KNOP	2
San Luis Obispo	KSBJ-TV	6		WTVJ	39	Springfield	WWLP	22		KNOP	2
Santa Barbara	KEY-TV	3	Rock Island	WHBF-TV	4	Worcester	WWOR-TV	14		KNOP	2
Stockton	KOVR	13	Springfield	WICS	20	MICHIGAN				KNOP	2
			Urbana	WILL-TV	*12	Bay City	WNEM-TV	5		KNOP	2
COLORADO			INDIANA			Cadillac	WWTV	13		KNOP	2
Colorado Springs	KKTU	11	Bloomington	WTTV	4	Detroit	WJBK-TV	2		KNOP	2
	KRDO-TV	13	Elkhart	WSJV-TV	28		WTVS	*56		KNOP	2
Denver	KBTU	9	Evansville	WFIE-TV	2		WWJ-TV	4		KNOP	2
	KLZ-TV	7		WHEI-TV	5		WXYZ-TV	9		KNOP	2
	KOA-TV	4		WTVV	7		CKLW-TV	9		KNOP	2
	KRMA-TV	*6		WANE-TV	15		WOOD-TV	8		KNOP	2
	KTVR	2		WKJG-TV	33		WKZD-TV	3		KNOP	2
Grand Junction	KREX-TV	5		WPTA	21		WJIM-TV	6		KNOP	2
Montrose	KREY-TV	10		WFEM-TV	13		WDMJ-TV	6		KNOP	2
Pueblo	KCSJ-TV	5		WLWI	13		WKNX-TV	57		KNOP	2
CONNECTICUT				WISH-TV	3		WPBN-TV	7		KNOP	2
Bridgeport	WICG-TV	43		WFAM-TV	59					KNOP	2
Hartford	WITC-TV	3		WLBC-TV	49					KNOP	2
New Britain	WNBC	30		WNDU-TV	22					KNOP	2
				WSBT-TV	22					KNOP	2

FREE-ANY 3

of these superb COLUMBIA and EPIC

STEREOPHONIC or MONAURAL RECORDS

if you join the Columbia [®] Record Club now—and agree to purchase 4 selections during the coming 12 months



1. Johnny sings What I Do, Warm, While We're Young, 9 more



2. This vivid musical painting has become an American classic



3. 16 favorites—Sweet Violets, Down by the Old Mill Stream, etc.



4. Pianistic fireworks abound in these two romantic scores




5. Where or When, The Way You Look Tonight, Be My Love, 9 more




6. 43 hits for listening and dancing—in the smooth Lanin style



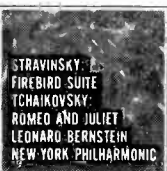7. The ingratiating Miss Holliday in her biggest Broadway hit



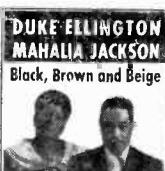8. Bernstein's exciting performances of two colorful scores




9. The finest performance ever of the Duke's masterpiece



10. A truly magnificent performance of this majestic symphony



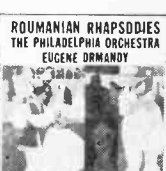11. The great tunes from Rodgers and Hammerstein's fabulous hit



12. The two fiery Rumanian Rhapsodies—plus 2 more works

Now you can acquire the world's finest stereophonic AND high-fidelity monaural recordings—at truly substantial savings! And as a dramatic demonstration of the Club's money-saving Bonus Plan—you may have, at once, ANY 3 of the sixteen records shown here, FREE . . . available in your choice of stereophonic sound OR monaural high fidelity!

Your only membership obligation is to purchase four selections from the almost 200 Columbia and Epic records to be offered in the coming 12 months.

After buying four selections, you receive your choice of a Columbia or Epic Bonus record (stereo or monaural) free for every two additional selections you buy.

HOW THE CLUB OPERATES

You enroll in any one of the six Club Divisions:

If you have stereo equipment you enroll in either the Stereo Classical or Stereo Popular Division.


If you have monaural equipment you enroll in any one of four Divisions: Classical; Listening and Dancing; Broadway, Movies, Television and Musical Comedies; Jazz.

Each month you receive, free, the Club Magazine which describes all forthcoming selections. You may accept or reject the selection for your Division, take any of the other records offered (stereo or monaural), or take NO record in any particular month. You may discontinue membership at any time after purchasing four records.

The records you want are mailed and billed to you at the regular list price: Popular Monaural Selections, \$3.98; Classical Monaural, \$4.98; all Stereo Records, \$5.98—plus a small mailing charge.

To receive your three stereo or monaural records FREE, mail the coupon today!

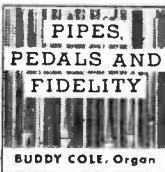COLUMBIA [®] RECORD CLUB
Terre Haute, Indiana




13. Organist Buddy Cole Plays 11 tunes—Mine, Caravan, Carioca, etc.



14. Cugat's greatest hits—Besame Mucho, Tico-Tico, Brazil, 9 more



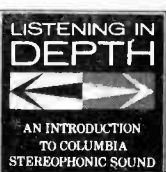15. The most popular of Tchaikovsky's lovely, melodic symphonies



16. Available in stereo only. 16 popular and classical selections

FREE — ANY 3 — MAIL COUPON NOW

COLUMBIA [®] RECORD CLUB, Dept. 246-1
Terre Haute, Indiana

Please send me as my FREE gift the 3 records whose numbers I have circled at the right — and enroll me in the following Division of the Club: (check one box only)

MONAURAL DIVISIONS		STEREO DIVISIONS	
<input type="checkbox"/> Classical	<input type="checkbox"/> Broadway, Movies, Television and Musical Comedies	<input type="checkbox"/> Stereo Classical	<input type="checkbox"/> Stereo Popular
<input type="checkbox"/> Listening & Dancing			
<input type="checkbox"/> Jazz			

I agree to purchase four selections from the almost 200 stereophonic and monaural records to be offered during the coming 12 months, at regular list price plus small mailing charge. For every two additional selections I accept, I am to receive a Columbia or Epic Bonus record (stereo or monaural) of my choice FREE.

Name..... (please print)
Address.....

City..... Zone..... State.....

CANADA: prices slightly higher, address 11-13 Soho St., Toronto 2B
If you want this membership credited to an established Columbia or Epic record dealer, authorized to accept subscriptions, fill in below:

Dealer's Name.....


Dealer's Address..... 215-2

© Columbia Records Sales Corp., 1959 © "Columbia," [®] "Epic," [®] Marcas Reg.

CIRCLE 3 NUMBERS BELOW:

(Also indicate here whether you want your 3 records in stereo or monaural)

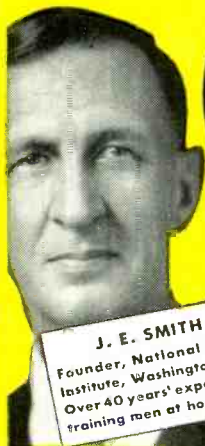- STEREO L-50
- MONAURAL L-49
- 1 9
- 2 10
- 3 11
- 4 12
- 5 13
- 6 14
- 7 15
- 8 16



J. E. SMITH
 Founder, National Radio
 Institute, Washington D.C.
 Over 40 years' experience
 training men at home.

Mail Postage-Free Card for
SAMPLE LESSON FREE
 Shows you how easy, practical it is to
**Train at Home for Good
 Radio-Television Jobs**

**Oldest and Largest Home Study Radio-
 Television Training School. N.R.I. has
 Trained Thousands for Good Pay Jobs**

Since 1914 . . . for more than 40 years—N.R.I. has been training ambitious men at home in spare time for Radio-TV. Let us send you a sample lesson to help prove you can keep your job and TRAIN AT HOME in your spare time for better pay and a brighter future. We will also send N.R.I.'s 64-page catalog to show you that Radio-Television is today's field of OPPORTUNITY for properly trained men.

Television Making Good Jobs, Prosperity

The technical man is looked up to. He should be. He does important work, is respected for what he knows, gets good pay for it. There are splendid opportunities for the man well trained in Radio-Television Servicing or Broadcasting. Government, Aviation, Police, Ship, Micro-Wave, Relay, Two-Way Communications for buses, taxis, trucks are growing Radio-TV fields, making more good jobs.

N.R.I. is the Tested Way to Better Pay


N.R.I. Training is practical, thorough. You get the benefit of N.R.I.'s 40 years' experience. Many successful N.R.I. men start without any knowledge of Radio, many without a high school education. Find out what Radio-Television training can mean to you. Make the first move today toward becoming one of that select group—a Radio-TV Technician. Send postage-free card for Actual Lesson and 64-page Catalog, both FREE. NATIONAL RADIO INSTITUTE, Dept. 9CB3, Washington 16, D. C.

**N.R.I. Sends Equipment
 for Practical Experience**



Nothing takes the place of practical experience. That's why N.R.I. training is based on LEARNING-BY-DOING. N.R.I. training includes kits of parts which you use to build equipment and get practical experience on circuits common to both Radio and Television. Shown at

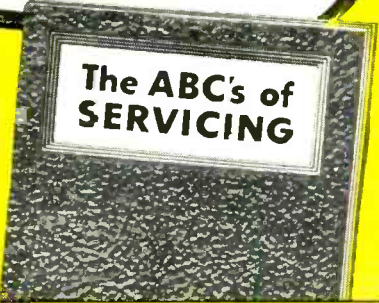left is Low-power Broadcasting Transmitter you build as part of N. R. I. Communications Course. FREE Catalog shows other equipment you get, things you learn.



WHAT N.R.I. GRADUATES DO AND SAY



**Has Own Radio-TV
 Business**

"We have an appliance store with Radio-TV servicing. During Army service, NRI training helped me get top rated job."—W. M. WEIDNER, Fairfax, S. D.



**Chief Engineer
 with FCGU**

"I am Chief Engineer with station and also have my own spare time servicing business."—R. BARNETT, Bismarck, N. D.



**Paid for Instruments
 from Earnings**

"I am doing very well in spare time. Sometimes have three TV jobs waiting, also fix car Radios."—G. F. SEAMAN, N. Y., N. Y.

See Other Side

FIRST CLASS
 Permit No. 20-R
 (Sec. 34.9, P.L.&R.)
 Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed in The United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

Washington 16, D. C.



Learn Radio-Television

Servicing or Communications by Practicing at Home in Spare Time

N.R.I. SENDS KITS with which you practice building circuits, common to Radio and Television. You LEARN-BY-DOING. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC Receiver shown here.

2 BOOKS FREE

Mail Postage-Free
Card for Sample Lesson
and 64 Page Catalog



Fast Growing Field Offers You Good Pay, Success, Bright Future

Bigger than ever and still growing. That's why Radio-Television has special appeal to ambitious men not satisfied with their future prospects. More than 4,000 Radio and TV Stations use trained technicians. 150 million home and auto Radios and 40 million TV sets must be kept in service. Color TV promises added opportunities. There are good jobs, bright futures in Radio-TV Servicing or Communications. Training PLUS Opportunity is the ideal combination for success. Plan now to get into Radio-TV. The technical man is looked up to, does important work, gets good pay. Keep your job while training. With N.R.I. you learn at home in spare time. N.R.I. is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.



J. E. SMITH,
Founder, N.R.I.

Many Good Jobs in Radio-TV Servicing
and Communications for T-ained Men



 **See Other Side**

CUT OUT AND MAIL THIS CARD NOW

Sample Lesson & 64-Page Catalog

Both FREE

NO STAMP NEEDED—WE PAY POSTAGE

NATIONAL RADIO INSTITUTE
Dept. 9CB3, Washington 16, D. C.


Mail me Sample Lesson and 64-page Catalog. (No salesman will call. Please write plainly.)

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

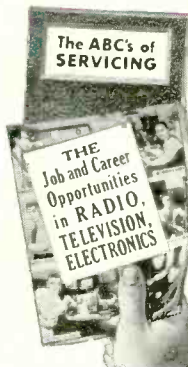ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL



**Start Soon to Make \$10—\$15 a
Week Extra in Your Spare Time**

Soon after enrolling, many N.R.I. students start to earn \$10, \$15 a week in spare time fixing sets for friends and neighbors. Some make enough to start their own full time Radio-TV shops. Easy-to-understand lessons teach you basic principles. You LEARN-BY-DOING on N.R.I. equipment which "brings to life" things you study.

Find out what N.R.I. offers. Study fast or slow—as you like. Diploma when you graduate. Mail postage-free postcard now. ACTUAL LESSON FREE. Also 64-page catalog that shows opportunities, equipment you get. Cost of N.R.I. courses low. Easy terms. NATIONAL RADIO INSTITUTE, Dept. 9CB3, Washington 16, D. C.