SCIENCE and 25 Electronic Projects

D) [O] ___ EXPERIMENTER

75c Spring '63

WHITE'S RADIO LOG

OVER 14,000 LISTINGS WITH 600 CHANGES AM-FM-TV STATIONS WORLD-WIDE SHORTWAVE

How to-

Throw TV Sound To Remote Radio

Build a Transistor Tester for \$4

Make Photofloods Out of Light Bulbs

Read AC Current On a Voltmeter

Now a Quarterly!

Centralized Home Intercom **Needs No Warmup or Switch**





TROUBLE SHOOTING WITH THE SIGNAL TRACER

YOU GET A VALUABLE ELECTRONICS LAB

ntaining ports by RCA, MALLORY, PYRAMID, CENTRALAB, STACKPOLE, TRIM and other relighte manufacturers, Retail value of parts olone is MORE THAN 25 DOLLARS

PLUS A COMPLETE ELECTRONICS COURSE

You REALLY LEARN ELECTRONICS. The progressive "learn by doing" American Basic Science Club system is the easiest, most thorough and most exciting way to a solid background in electronics. Basis erjough for beginners rewarding enough for experts.

Nowhere else is a course of this scope available at this LOW PRICE!

ENTHUSIASTIC MEMBERS WRITE:

"basic principles unforgettably learned"...

It is only after having completed the experi-ments in your kits that I can say I have truly of electronics, JOHN R. KANIA 2 trekelog Ave., Yonkers S. N. Y.

"your kits are interesting and rewarding" . . .

I am an electronics student in the Air Force and find your kits interesting and rewarding. We have not covered mything life the school that you have not covered in fire kits. JOHN G. OILL, Keegler Air Force Stase. Hiloxi.

"for ahead of friend taking another course" . . .

A friend of mine is taking a correspondence rourse in electronics, and I have learned most from your first two kits than he has in twenty leasons, RAY 28, BILODEAU, 729 Exchange St. Leoningter, Mass.

"the number of concepts presented

You, kits offer a range of experiments usually performed only in the better high schools and college laboratories. The number of concepts presented, and the clarity and concepts necessary development is amazing. R. M. MELM. Professor of Physics and State Concepts and Concepts a

Available in One Complete Shipment or Divided into 4 Monthly Kits as Shown

KIT 1 - DC AND AC CIRCUITS

Equip. for 26 Projects Including: · Electroscope · Electro Magnet Galvanometer AC Buzzer Demagnetizer • Relay • Solenoid Coin Tosser . Safety AC Power Supply with Isolation Transformer

Subjects Covered Include:

 Magnetic Fields
 Electron Theory • Electric Charge • Direct Current • Electro-Chemistry • Alternating Current . Inductance

• Transformer Principles FREE with kit 1 - Surprise "Mystery Box"

KIT 2 - RESISTANCE, CAPACITANCE AND RECTIFICATION

Equip. for 18 Projects Including: • Strobe Light • Thermocouple

- Wheatstone Bridge * Voltmeter · AC Rectifier · DC Power Supply
- Subjects Covered Include: · Ohm's Law · Power Formulas
- Rectification Resistance Neon Glow Tubes • Capacitance • Filter Circuits
- FREE with kit 2 Electric Soldering Iron

KIT 3 - AMPLIFIERS AND OSCILLATORS

Equip. for 14 Projects Including: • Two Stage Amplifier • Capacitance Burglar Alarm • Proximity Detector • High Speed Strobe Light . Ripple Tank Wave Generator • Code Practice Oscillator Subjects Covered Include: • Vacuum Amplifier Tubes • Voltage Amplification . Oscillator Circuits . Frequency and Wave Length Sound Waves, Pitch and Resonance

FREE with kit 3 — "Steps to a Ham License" Manual KIT 4 - AUDIO AMPLIFICATION AND RADIO

Equip. for 7 Projects Including: Microphone and Audio Amplifier

· Broadcast Radio · Short Wave Radio . Signal Tracer . Continuity Tester • Transmitter

Subjects Covered Include:

· Audlo Amplifiers · Amplitude Modulation • Radio Theory • Regenerative Circuits • Tuning Circuits

FREE with kit 4 - Radio-TV Service Manual

ALL	FOUR	KIŤS IN	ONE	SHIPMENT	ONLY \$	17	80 POSTPAID
					7 Harrison 12.		

OR-YOU CAN GET THE FOUR KITS. ONE A MONTH PAY \$395 PLUS COD POSTAGE ONLY SEND \$200 WITH ONLY COUPON ON RECEIPT OF EACH KIT

ALL SHIPMENTS ON 10 DAY APPROVAL YOUR SATISFACTION OR YOUR MONEY BACK. WE KNOW YOU WILL BE AMAZED AND DELIGHTED.

USE THIS "NO RISK" COUPON FOR EITHER PAID IN FULL OR MONTHLY PLAN - AMERICAN BASIC SCIENCE CLUB, Inc., 501 E. Crockett, San Antonio 6, Texas-

- Send me ABSClub's Electronics Lab in four kits one a month, I enclose \$2.00 and will pay \$3.95 plus COD Postage on arrival of each kit. I understand that all kits will be on 10 day approval with full refund guaranteed and also that I may cancel unshipped kits at any time.
 - Send me ABSClub's Electronics Lab (all four kits) in one shipment. I enclose \$17.80 full payment, postage paid to me, I understand that this will be on a 10 day approval with full refund guaranteed.

ADDRESS.....

CITY and STATE

PICK YOUR OWN SUCCESS STORY FROM THIS PAGE

These are the true stories of people who seemed trapped in routine, low-pay shaky jobs. Handicapped by lack of proper training, they couldn't get the things they wanted out of life—more money, a job they liked, security and happiness.

They are a small sample of the thousands of men and women—young and old—who turn to I. C. S. for help. Their will-to-learn plus I. C. S. training have changed the course of their lives.

Are you discouraged with your job and pay and feel you can't improve yourself because of lack of specialized education? Well, these men and women were in the same boat. With I. C. S. training, one of these success stories could be about you.

1. C. 5. is the oldest and largest correspondence school. 250 courses. Business, industrial, engineering, academic, high school. One for you. Direct, jobrelated. Bedrock facts and theory plus practical application. Complete lesson and answer service. No skimping. Diploma to graduates.



Wins \$3000 contest—"After my I. C. S. courses I secured a new position." says Mr. Cecil Rhodes. "My income has more than doubled and I recently won a \$3000 sales contest."



From clerk to Assistant Estimator, thanks to I.C.S. 'Any way you look at it.' writes Mrs. Edna James. 'the time and money one spends for I. C. S. Courses will be repaid a thousandfold.'



"As a college graduate, I found I.C.S. very valuable." Robert Lee took the I.C.S. Course in Advertising, is now Promotion Manager for a large corporation. "I.C.S. got mestarted on the way up," he says.



Reports 20% increase in salary? Gregory C. Johns says, "I. C. S. training gave me unlimited opportunity! I have completed one course, and am now enrolled in Practical Plumbing."

3 FREE BOOKLETS—a 36-page pocket-size guide to advancement, a gold mine of tips on "How to Succeed." Also a big catalog outlining opportunities in your field of interest and a sample I.C.S. lesson.

Clip coupon here-and take your first big step to real success! I.C.S., Scranton 15, Penna.

Fully Accredited Member Wational Home Study Council


INTERNATIONAL CORRESPONDENCE SCHOOLS Box J3781A, Scranton 15, Penna, (in Hawaii: P. O. Box 418, Honolulu, In Canada: I C S. Canadian Ltd. Montreal) Without cost or obligation, rush me FREE Success Kit, with 3 valuable booklets: (1) How to Succeed; (2) opportunity booklet about the fleid I've checked below; (3) Sample I.C.S. Lesson. ARCHITECTURE and ☐ Transmission Lab. Technician Nuclear Energy Industrial Practical English Shorthand Stenographio BUILDING TRADES Air Conditioning Architecture Telemetering Instrument Technician Practical Electrician Practical Lineman | Nuclear English | Plastics | Pulp, Paper HIGH SCHOOL (Diploma) AVIATION High School General High School Math High School Math Secretarial High School Vocational College Preparatory Aero Engineering Aircraft Drafting Aircraft Mechanic STEAM and DIESEL POWER Arch Intecture Arch Drawing Building Contracting and Estimating Carpentry & Millwork Heating House Planning Painting Plumbing CIVIL ENGINEERING Boiler Inspector Civil Engineering Construction Engrg. **FLECTRONICS** Automation Basic Electronics Electronic Computers Electronics Technician Hi-Fi Stereo and BUSINESS Construction Engrg. Highway Engineering Reading Structural Blueprints Sanftary Engineering Structural Engineering Surveying & Mapping Accounting Cost Accounting Public Accounting Bus. Administration Executive Training Marketing Personnel-Labor Relations Engineering Stationary Diesel Engineering Steam Engineering MECHANICAL and SHOP Gas and Electric Welding Industrial Engineering Sound Systems Industrial Electronics Ultrasonics Industrial Industrial Instrumentation SUPERVISION ART and DESIGN Foremanship—Supry'n Personnel—Lab. Rel'ns Commercial Art Fashion Illustrating Interior Decorating DRAFTING Architectural Electrical and Electronic Mechanical Sheet Metal Relations Relations Programming for Digital Computers Purchasing Agent Real Estate Satesmanship Sales Mgmt. Traffic Mgmt. ENGINEERING TV-RADIO Machine Design Machine Shop Practice Radio and TV Servicing Magazine Illustrating Show Card & Sign Painting Sketching and Painting (Professional) Machine Shop Practi Mechanical Engineering Reading Shop Blueprints Tool Design Toolmaking Safety Engineering Chemical Civil Electrical Mechanical License TV Techniclan Practical Radio-TV Engineering ELECTRICAL Elec. Appliance Servicing Electrical Engineering AUTOMOTIVE Auto Body Rebuilding Auto Electric Technician Automobile Mechanic Engine (Gas & Diesel) Engine Tune-Up ENGLISH and WRITING Electrical Engineering Elect. Eng. Technician Elec. Motor Repairman Industrial Electronic Technician MISCELLANEOUS ☐ Better Business CHEMICAL Analytical Chemistry Chem. Engineering General Chemistry Writing Introductory Technical Writing Short Story Writing Railroad Textile SECRETARIAL Other (please specify) ☐ Clerk-Typist☐ Professional Secretary Home Address_ City Occupation Employed by Working Hours_ Special low rates to members of U.S. Armed Forces!

RADIO-TV EXPERIMENTER

No. 620

A SCIENCE and MECHANICS Handbook

Spring 1963 Edition

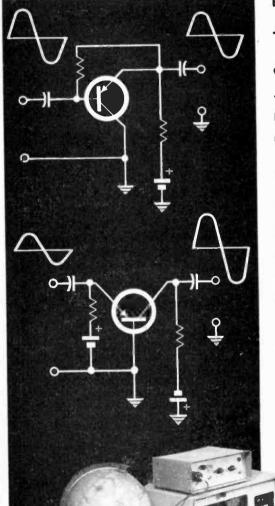


B. G. DAVISPublisher
JOEL DAVISAssistant Publisher
Garry WinterEditor-in-Chief
Joe DaffronManaging Editor
Bill WadkinsArt Editor
Leroy R. KietzmanProduction Editor
DON A. TORGERSENEditor
Byron G. WelsElectronics Editor
Lynell A. Johnson Associate Editor
John O. BastasArt Associate
John Neenan Production Assistant
Delores HenkelmanProduction Assistant

Cover by Harold R. Stluka

RADIO-TV EXPERIMENTER, Volume 15, No. 1, is published quarterly by SCIENCE AND MECHANICS PUBLISHING CO., a subsidiary of Davis Publications, Inc. Editorial, Business and Subscription Offices: 505 Park Ave., New York 22, N.Y.; one-year subscription (four issues), \$3.00 domestic, \$4.00 foreign. Advertising Offices: New York: 505 Park Ave., Pt 2-6565; Chicago: 450 E. Ohio St., WH 4-0330; los Angeles: 6363 Wilshire Blvd., 653-5037. Application for second-class postage rates is pending at New York, N.Y. and at additional mailing offices. Copyright 1962 by Science and Mechanics Publishing Co.

These men are getting practical training in NEW Shop-Labs of

ELECTRICITY

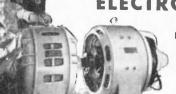

ELECTRONICS ON REAL

Motors—Generators
—Switchboards—
Controls—Modern
Appliances—
Automatic
Electronic
Control Units

TELEVISION

RADIO ELECTRONICS
ON REAL

TV Receivers—
Black and White
and Color
AM-FM and
Auto Radios
Transistors
Printed Circuits
Test Equipment

COYNE

in Chicago—prepare for today's TOP OPPOR-TUNITY FIELD. Train on real full-size equipment at COYNE where thousands of successful men have trained for over 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. Employment Service to Graduates.

START NOW—PAY LATER—Liberal Finance and Payment Plans. Part-time employment help for students.

GET FREE BOOK—"Guide to Careers" which describes all training offered in ELECTRICITY and TELE-VISION-RADIO ELECTRONICS—no obligation; NO SALESMAN WILL CALL.

Conne Electrical School, 1501 W. Congress Parkway Chartered Not For Profit • Chrcago 7, Dept. 13-8

MAIL COUPON OR WRITE TO

COYNE ELECTRICAL SCHOOL
Dept. 13-B-New Coyne Building
1501 W. Congress Pkwy., Chicago 7, IM.
Send BIG FREE book and details of all the training
you offer.

Nome	
Address	 _

State

COYNE offers LOW COST TELEVISION TELEVISION TO COLOR TV RADIO - COLOR Training in Spare Time AT HOME

The future is YOURS in TELEVISION!

A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you MODERN-QUALITY Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is MODERN TELEVISION TRAINING including Radio, UHF and Color IV. No Radio background or previous experience needed. Personal guidance by Coyne Staff. Practical Job Guides to show you how to do actual servicing jobs—make money early in course. Free Lifetime Employment Service to Graduates.

COYNE

CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT
1501 W. Congress Parkway • Chicago 7, Dept. 13-H9

B. W. COONE, In., President Couns—the Institution bekind this training... the largest, oldest, best equipped residential school of its kind, Founded 1899.



Send Coupon or write to address below

for Free Book

and full details, including easy Payment Plan. No obligation, no salesman will call.




COYNE Television Home Training Division

Dept. 13-H9, New Coyne Building
1501 W Congress Parky., Chicago 7, III.
Send Free Book and details on how I can get
Coyne Quality Television Home Training at
low cost and easy terms.


Name		
Address		
City	State	

CONTENTS

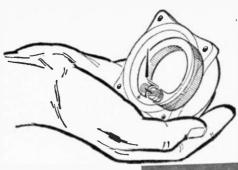


COVER	STORY
-------	-------

Centralized Home Intercom
Centralized nome tindicom
FEATURE STORIES
Electronic Plano; It Never Needs Tuning 44
Selecting the Right Short Wave Received
WHITE'S RADIO LOG (New Listing Incl. Over 400 Changes)
All U.S. and Canadian AM, FM, and TV Stations;
All U.S. and Canadian Am, rm, and 10 States 159 Mexico, Cuba, Worldwide Shortwave
FOR THE HAM AND DXER
Power Distribution Center
Two Tube Long Wave Receiver
Shorty 80-40-15 Meter Antenna121
Shorty 80-40-15 Meter America
EXPERIMENTING, TEST EQUIPMENT, AND THE SHOP
Space Station Super Workbench
A A TARAGE LIGAS TOUR VOICE
AC Experiments with Series Citation 86 Determining the Velocity of Sound
Voltage Calibrator and Switch
Voltage Calibrator and Switch
Voltage Calibrator and 94 Meters and Multimeters99
Meters and Multimeters 99 Using Positive Feedback 130
Troubleshooting interference
SPECIAL PROJECTS
Low Cost Photo Lights
Wireless Remote TV Sound
Neon Flicker Lamp147
Neon Flicker Lamp147 Thermistor Thermometer147
DEPARTMENTS AND PUZZLES
Electronics Numbergram
Electronics Numbergram
Ham Radio Anagram Puzzie
FOOKING GARLIAGE LIGHT LIGHT

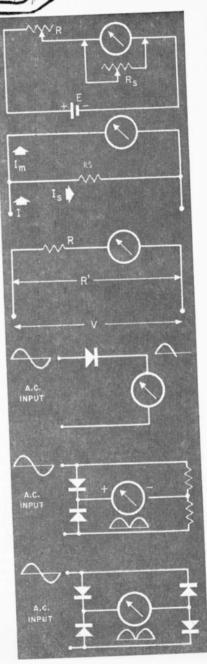

RCA training at home can be the smartest investment you ever made

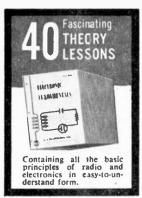Look what you get in the Course in Radio and Electronic Fundamentals








15 KITS

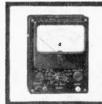to build a Multimeter, AM Receiver and Signal Generator. Kits contain new parts for experiments, integrated so as to demonstrate what you learn in the lessons and to help you develop technical skills. Each kit is fun to put together!



MULTIMETER

PLUS ALL THIS AT NO EXTRA COST...

A sensitive precision measuring instrument you build and use on the job. Big 4½" meter with 50 microamp meter movement, 20,000 obms-per-volt sensitivity d-c, 6,667 a-c.



AM RECEIVER

Have the satisfaction of building your own radio receiver with this highquality 6-tube superheterodyne set. Big 5" speaker, fine tone!



SIGNAL GENERATOR

A "must" for aligning and trouble-shooting receivers. Build it for your own use. 170 KC to 50 MC fundamental frequencies for all radio and TV work.

Also, comprehensive, fully-integrated home study courses in • Television Servicing • Color Television • Automation Electronics • Transistors • Communications Electronics • Computer Programming • Electronic Drafting. Stake out your future in electronics

with any one of this wide variety of courses. Practical work with the very first lesson! Pay-only-as-you-learn! No long-term contracts to sign! No monthly installments required. Pay only for one study group at a time, if and when you order it!

SEND FOR FREE HOME STUDY CATALOG TODAY!

RESIDENT SCHOOL COURSES in Los Angeles and New York City offer comprehensive training in Television and Electronics. Day and Evening classes. Free Placement Service. Catalog-free on request.



A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics RCA INSTITUTES, INC. Home Study School, Dept. R X-1.3 A Service of Radio Corporation of America 350 West Fourth Street, New York 14, N.Y.

Without obligation, rush me the FREE 64-page illustrated booklet "Your Career in Electronics" describing your electronic home study training program. No salesman will call.

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

BECOME A RADIO

Build 10-20 Radio and Electronic Circuits at Home

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making rock-bottom price. Our Kit is designed to training. You will learn radio theory, constructively the most modern process. The second process of the rock process of th

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well will find business or a job with while investment. "Edu-kit a worth-while investment, many thousand of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, 20 cannot make a misulfest at your cannot make a misulfest at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educatory principle of "tearn by Doing." Therefore you construct, kit was steemed to principle of "tearn by Doing." Therefore you construct, learn schematics, story of the practice trouble-shooting—all in a closely integrated progress of the progression of the progression

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variance circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variance controlled to the control of the control

NOW! TRAIN AT HO

USE COUPON ON NEXT PAGE ORDER DIRECT FROM AD

CON RESISTO BONUS E () = =

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms aeradios. You will learn home, portable aeradios. You will learn how the professional Signal Tracer, you call see the professional Signal Tracer, you call signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stataits, of 25 Poplar Pl., Waterbury,

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself, I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kita are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Radio-TV Club."

Robert L. Shuff. 1534 Monroe Ave., Muntington. W. Vai. "Thought I would drop you a few Innes to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit Liserally swell, and finds the trouble, if there is any to be found."

Choose From These Popular "Edu-Kit" Models

#10A: 10 Circuits \$14.95

#15A: 15 Circuits \$19.95

#16A: 16 Circuits (includes Printed Circuitry) \$22.95

#20A: 20 Circuits (includes Printed Circuitry and 4 Advanced Circuits) \$26.95

TECHNICIAN for only \$14

THE NEW IMPROVED DELUXE

Progressive Radio "Edu-Kit"

is now ready

NOW INCLUDES

- 12 RECEIVERS
- **3 TRANSMITTERS**
- SQ. WAVE GENERATOR
- AMPLIFIER
- SIGNAL TRACER
- SIGNAL INJECTOR
- CODE OSCILLATOR

PRACTICAL HOME RADIO COURSE

only

SCHOOL INQUIRIES INVITED

Unconditional Money-Back Guarantee

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

radio course.

By popular demand, the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.



TRAINING ELECTRONICS TECHNICIANS SINCE 1946

EXTRAS

- . SET OF TOOLS
- . SOLDERING IRON
- ELECTRONICS TESTER
- . PLIERS-CUTTERS
- . ALIGNMENT TOOL
- WRENCH SET
- . VALUABLE DISCOUNT CARD
- . CERTIFICATE OF MERIT
- . TESTER INSTRUCTION MANUAL
- . HIGH FIDELITY GUIDE . QUIZZES
- TELEVISION BOOK RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

You Will Find That The Progressive Radio "Edu-Kit" Is Perfect

- * FOR anyone who wishes to learn more about radio construction, theory and servicing.
- · · FOR anyone who is looking for an interesting hobby.
- FOR anyone who would like to learn radio but does not have time to attend regular school hours.
- · · FOR anyone who wants to start studying for a high-paying radio
- FOR anyone who wishes to start in Television.

Please RUSH my Progressive Radio "Edu-Kit" to me. BE SURE TO INCLUDE all the FREE EXTRAS and BONUS RESISTOR and CON-DENSER KITS. MODEL desired.....

☐ Send "Edu-Kit" postpaid. 6 enclose remittance in full.
☐ Send "Edu-Kit" C.O.D. 1 will pay postage.

Send me FREE additional information describing "Edu-Kits."

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 512NN, Hewlett, N. Y.

Abraham Marcus, co-author of famous best-seller "Elements of Radio" makes amazing offer!



RFPAIR



FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

were it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually most sloof fixing radios and TV sets, just return the books to us and pay not a penny! Mean the sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-tell you what to do in 1:2:3 fashion. For example, one of the point of the first few chapters of the TV bool. For example, one for business—tell you what to do in 1:2:3 fashion. For example, one for business—the first few chapters of the TV bool. For example, one for business—the first few chapters of the TV bool. For example, one for business—of the two pays of all service calls, the first few chapters of the TV bool. For example, one for business—DNTT WAIT! You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even Wheneyou decide to keep them, you pay on easy terms. Mail the coupon now.

COUPON THIS

	Prentice-Hall, Inc., Dept. 5747-A1 Englewood Cliffs, New Jersey Please send me Abraham Marcus' TV & RADIO REPAIR COURS (3 volumes) for 10 days FREE examination. Within 10 days will either return it and owe nothing, or safter 1 have used it of 85,60, plutul. MONTH, if I am not satisfied I may return and you will refund my first payment. Or I will keep the cours and you will refund my first payment. Or I will keep the cours months. 85,25 less than if books were bought individually.	it it ie it
	Name	٠
	Address Zona Stata	•
Į	CityZoneState	

WHAT YOU GET IN THESE **3 GIANT VOLUMES**

ELEMENTS OF TELEVISION

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Material 19 inch color receiver. the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned radio-frequency tuner—AC-DC superheterodyne receiver-etc.

RADIO SERVICING Theory and Practice. Here is everything RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments, such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.

RECOME A

- → HOW TO BECOME A RADIO AMATEUR
- ★ THE RADIO AMATEUR'S LICENSE MANUAL
- * LEARNING THE RADIOTELEGRAPH CODE
- * OPERATING AN AMATEUR RADIO STATION

Only S For All Four Postpaid Booklets

All you need to know to get your ham license is contained in these four booklets, written by amateurs, for amateurs, and published by the amateurs' own organization. Easy to understand, yet thorough, these ARRL publications are truly your GATEWAY TO AMATEUR RADIO.

AMERICAN RADIO RELAY LEAGUE. Inc. West Hartford 7, Connecticut

Name		
Street	• • • • •	
CityState		

TRANSISTOR IGNITION



now available as a

2 TRANSISTOR 2 DIODE

Why pay more for less?

YOU can have ALL the FUTURISTIC ADVANTAGES of TRANSISTOR ELECTRONIC IGNITION NOW at LOWEST COST by assembling this TESTED KIT yourself. COMPLETE set of parts to build WARD circuit in February Science and Mechanics. Includes 2 POWER TRANSISTORS, 2 1-watt ZENER DIODES, FINNED aluminum HEAT SINK, High-ratio COIL, TRANSFIRE DECAL, ballast, leads, and all hardware. EVERYTHING needed for a PROFESSIONAL JOBI Makes a \$70 Conversion at HALF the cost.

TKX-2 with 250:1 coil. 30kv output. \$34.95

T5KX-2 with 400:1 coil. 40kv output. \$39.95

TKX-1 1 transistor with 400: 1 coil 30kv ...\$29.95

Above kits wired and plastic potted—add \$15.
Negative-ground only. Point insulation kit for positive-ground—\$2.50 pp.

TX250 heavy duty Coil 250:1 (3 lbs.) \$9.95

T400 High-efficiency Coil 400:1 (3 lbs.) \$9.95

Ready-to-install Conversions

You can also get TOP MILEAGE. HIGHEST PERFORMANCE, LONG POINT AND PLUG LIFE, IMPROVED STARTING with one of our wired TRANSFIRE systems. These include HER-METICALLY SEALED AMPLIFIER, 400:1 COIL, and BAL-

LAST.

Model T 6 or 12 v. Negative-ground 30kv. \$39.95

Model T2 Two-transistor model T. \$44.95

Model T5 Special 40kv Negative-ground. \$59.95

Model T5 Two-Transistor Model TS. \$49.95

Model TP 30kv 6 or 12 v. Positive-ground. \$54.95

Model TP 30kv 1 DIRECT INSTALLATION. \$69.95

Marine and other models available too. Custom Designs.

Full time of parts at LOWEST PRICES. Free lists. Dealer

Opportunities. Specify car, Specify car, voltage, and grounding when ordering. Cash orders over \$30 prepaid. \$5 deposit COD's.

PALMER ELECTRONICS LABORATORIES, INC. CARLISLE 29, MASS. AL 6-2626



Now Prepare for GOOD JOB OPPORTUNITIES IN **ELECTRONICS** Faster—with

1. METER — Transistorized, Portable, AC-DC Multimeter

2. SCOPE - 5-inch New Streamlined Commercial-Type Oscilloscope

3. ELECTRO-LAB* - For 3-Dimension Circuit Building

To help you get ready F-A-S-T-E-R ... and THOROUGHLY ... for good paying job opportunities in the fast growing Electronics field, DeVry Technical Institute now presents the newest and finest training advantages in its over 30 years of experience. Now . . . AT HOME . . in your spare time, you prepare with "industry-type" home laboratory equipment. To provide real PRACTICAL EXPERIENCE, you build a quality Transistorized Meter and a 5-inch industrial-type Oscilloscope work with small, 3-dimensional circuits on DeVry's new Design Console . . . use highly instructive home training movies . . . and follow up-to-date lessons with many time-saving fold-out diagram sheets.

Little wonder DeVry men qualify for such fine opportunities in Space-Missile Electronics, Automation, Computer Work, Radio-TV, Industrial Controls, and other fields.

You learn PRACTICAL techniques important in today's Space Age industry, because you build many compact circuits with the streamlined Electro-Lab, using exclusive solderless "modular connectors." You perform over 300 construction and test procedures in all! Your self-built test equipment has function grouped controls, meter scales color-keyed to the panel markings-much like instruments used on today's jobs. What's so important, the home laboratory and the test equipment are YOURS TO KEEP!

NDUSTRY NEEDS TRAINED MEN Through this remarkable 3-way method,

DeVry Tech has helped thousands of ambitious men prepare for good jobs or their own profitable full-time or part-time service shops. It is the newest in a long series of PRACTICAL training alds that we have pioneered and developed in more than three decades of experience, Sound interesting? Then see how DeVry Tech may help YOU. Mail the coupon today.

From RADIO to SPACE-MISSILE ELECTRONICS

DeVry's training goes all the way from radio repair . . . to space-missile elec-tronics. That's the range of subjects covered in its programs AT HOME or in its well-equipped training centers in Chi-cago and Toronto. You fearn up-to-date techniques, working with new equip-ment, modern texts, movies—one of today's finest combinations of training equipment . . . geared for RESULTS!

EMPLOYMENT SERVICE When you complete the program, Devry's efficient Employment Service ready to help you get started. There is no extra charge-ever-for this aid. ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

TECHNICAL INSTITUTE TORONTO





ı	MAIL COUPO	N FOR I	FREE F	ACT:
Ī	DEVRY TECHNICAL INSTI	TUTE	RTE-1-T	208
1	Please give me your two Earnings" and "Electronic	free booklets, "s in Space Trave	Pocket Guid	de detail

the following opportunity fields (check one or more): Space & Missile Electronics Television and Radio Microwaves

" Trademark &

Radar Automation Electronics

Camputers
Broadcasting
Industrial Electronics

Name		Age
Address	PLEASE PRINT	_Apt
	Tine .	Chala

Check here If you face military service. Canadian residents: Write DeVry Tech of Canada, 970 Lawrence Avenue West, Toronto 19, Ontario

Weller **Heavy Duty Soldering Kit**

Features a professional DUAL HEAT gun. Two trigger positions let you switch instantly to low 240-watt or high 325-watt heat to suit the job. By using high heat only when necessary, you prolong tip life. Heat and spotlight come on instantly when trigger is pulled. Included: Soldering tip. Smoothing tip. Cutting tip. Tip-changing wrench. Solder. Instructions. Plus break-proof plastic case which can be used as a lunch, fishing tackle or tool box. Model D-550PK.



S BARGAINS ECTRONI

RCA 6032 IMAGE-CONVERTER TUBE

Combined with suitable optical systems, this 3-electrode tube permits viewing of scene with infrared radiation. Scene to be viewed is imaged by optical objective upon semi-transparent photocathode. Spectral resp., S-1; good response up to about 1200A. Max. ratings, absolute, grid #2, 20,000 VDC or peak AC, grid #1,2700.



\$9.95 nad.



Rated 2.4 amp hr. Approx. dimensions: 3½" l. x 1¾" w. x 2½" h. Weight: 1 lb. 3 oz. (plastic case) Dry-charged. \$2.50

POTTER & BRUMFIELD RELAY

#SM5LS SPDT 8,000 ohm 11/16 111/ dia. long. Approx



weight 1 oz. Hermetically sealed. Standard 7-pin miniature base. \$2.00

MINOR SWITCH

10-position, 3-pole with stopper coll and reset coil stopper con and reset con 6-12 volts D.C. off-normal non-bridging wiper ap-prox. dimensions: 4" long x 4\%" high x 1\%" wide, weight: 1 lb. \$9.95

NICKEL CADMIUM BATTERY 1.2 VOLTS

Rechargeable thousands of Recha times, sintere Alkaline storage battery sintered-plate. Flat voltage curve during discharge. Will hold charge for long period of time. High discharge rate up to

6-ampere-hour capacity. Dimensions:
6" high; 2" wide; ½" thick. Approx.
wt.: 6 oz. Uses potassium hydroxide. (30% Electrolite)

SIGMA EXTRA-SENSITIVE PRECISION RELAY-SERIES SF

Extremely precise, rugged DC general-purpose sensitive pc general-purpose server, relay. Balanced armature, single-pole, double-throw. Suitable for wide range of

adjustments. Dimensions: $1\frac{1}{3}\frac{n}{x_1}\frac{1}{5}\frac{1}{6}\frac{n}{n}$ high. Weight: $4\frac{1}{4}$ oz. 5F-10,000 S: 10,000 coll ohms. Operates 1.0 ma DC \$4.95 5F-16, 000-S: 16,000 coil ohms. Operates 0.5 ma DC \$5.95

POWER TRANSFORMER

Output: 12, 24, 36 volts. Input: 100 volts, 60 cycles, single-phase. Will handle 21/2 amps. Steel case is hermetically sealed. $3\frac{1}{2}$ "x2\%"x4\%". Wt.: 31/4 pounds.

DIRECT-READING MAGNETIC COMPASS



Full-floating eard, compensating magnets, and dial light avail. In 6 or 12-v. butb, Luminous dial. Mixd. by Bendix-Pioneer, 3\%" x 5\% bs. \$8.50 postpaid.

SILICON RECTIFIERS

All rectifiers listed at maximum peak inverse voltage ratings; approximate forward voltage drop, 1.5 volts. CLERK PO

1N1446	.075 1	amp.	100 rolts	, 50
1N1447	.075	amp.	200 volts	.60
1N1448	.075	amp.	300 volts	.75
1N1449	.075	amp.	400 volts	.85
1N1450	5	amp.	100 volts	1.00
1N1451	- 5	amp.	200 volts	1.25
1N1452	5	amp.	300 volts	1.50
1N1453	5	amp.	400 volts	2.00
1N1454	25	amp.	100 volts	3.00
1N1455	25	amp.	200 volts	3,50
1N1456	25	amp.	300 volts	4.50
1N1458	35	amp.	100 volts	3,50
1N1459	35	amp.	200 volts	4,00
1N05P7	50	amp.	50 volts	6.00
1N1462	50	amp.	100 volts	7,00
1N1466	75	amp.	100 volts	10.00
1N1467	75	amp.	200 volts	11.00
1N1468	75	amp.	300 volts	12.50
1N05V7	150	amp.	50 volts	16.50
1N1474	150	amp.	100 volts	17.00

X-BAND POWER LEVEL TEST SET, TS-36/AP



\$2.95

Brand new, in original packing, with accessories. Measures 10 to 30 dbm. 8700-9500 mg

\$14 95

All prices FOB Pasadena unless No COD's othermise noted.

2176 E. Colorado St., Pasadena, Calif Murray 1-7393

New Model 161 UTILITY TESTER®

FOR REPAIRIN

As an electrical trouble shooter the Model 161:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Will test all TV tubes (including picture tubes) for open filaments. and burned out tubes.
- Measures A.C. and D.C. Voltages.

(Both 110 Volt and 220 Volt lines)

- Will measure current consumption (amperes) while the appliance under test is in operation.
- Incorporates a sensitive directreading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.

As an Automotive Tester the Model 161 will test:

● Both 6 Volt and 12 Volt Storage Batteries ● Generators ● Starters ● Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers ■ Cigarette Lighters
 ■ Stop Lights
 ■ Condensers
 ■ Directional Signal Systems ● All Lamps and Bulbs ● Fuses ● Heating Systems ● Horns ● Also will locate poor grounds, breaks in wiring, poor connections, etc.



SO EASY!



tester's cord in outlet, cur-consumption of appliance is direct on meter when line is connected to receptacle on Witn receptacle iron takes



Control circuits of most furnaces use 24 volts obtained from step-down transformer Here's how to check room thermostat to see if wires to it are live.



READ THIS!



Test Storage Batteries READ THIS!



Simply insert tube in appropriate socket then follow procedure as outlined in our manual.



Small 50 ohn indicates



Test Circuit Breakers READ THIS!

INCLUDED FREE!!

This 56-page-book-practically a condensed course in electricity. Learn by doing.

Just read the following partial list of contents:

What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage current, registance and leakage • How to test all electrical appliances and motors using a simplified trouble-shooting technique.

How to test all TV tubes; also simple procedure for determining which specific tube (or tubes) is causing the trouble.

How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 161 comes complete

with above-book and test leads. Only

You don't pay for the Model 161 until AFTER you have examined it in the privacy of your home!

Try it for 10 days before you buy. If completely satisfied then send \$5.00 and pay the balance at the rate of \$5.00 per month until the total price of \$22.50 (plus small P.P. and budget charge) is paid. If not completely satisfied, return to us, no explanation necessary.

ACCURATE INSTRUMENT CO., INC.

Dept. D-230, 911 Faile St., New York 59, N.Y.

Please rush me one Model 161. If satisfactory I agree to pay \$5.00 within 10 days and balance at rate of \$5 per month until total price of \$22.50 (plus small P.P. and budget charge) is paid. If not satisfactory, I may return for cancellation of account.

Name			
Address		_	
City	Zone	State	



CHRISTY TRADES SCHOOL, Dept. T-611 3214 W. Lawrence Ave., Chicago 25 Send me 3 Free Books and Special Form for PAYING LATER from EARNINGS MADE WHILE LEARNING. NAME. Age....



12 WATT TRANSISTOR AMPLIFIER \$ 95 Each Plus

Postage

A beautifully engineered 12 watt Transistor Amplifier for music systems, public address, paging, and many other uses. Complete with husky A.C. power supply. Uses two power transistors with thermister bias protection. Input impedance—16 ohms, ouput impedance—200 ohms. Line to feed any desired number of speakers at remote points if desired. Two volts across 16 ohm input drives to full 12 watt output. Room for additional stages if desired to increase gain. These amplifiers built to run continuous duty. Chassis 91/4"1 x 29/4" x 47/8" high. New, original manufacturer packing. Shipping weight, 12 lbs.

TRANSISTOR BROADCASTER

A unique 2 Transistor Phono Oscillator which plays thru any broadcast band. Radio will operate mike or phono pickup. Originally designed to add Stereo to regular monaural system and prica at \$16.75 each. SPECIAL CLOSE-OUT RRICE ONLYeach \$2.50



FREE CATALOG

WRITE FOR YOUR COPY OF BIG ELECTRONIC PARTS BARGAINS. MAILED ANYWHERE IN U.S.A.

CAPITOL COMMODITIES CO. INC.

4757 N. Ravenswood Ave., Chicago 40, Illinois PHONES: LO 1-3355



ideas?

you'll find you are in for tempting big reports on all the worthwhile new mobile homes and travel trailers—colorful "camera tours" through America's most exciting parks—expert articles for your more enjoyable and profitable mobile home living. For new subscribers, mail the coupon below.

THE NEXT 10 ISSUES \$2.69

505 PARK AVEN	IUE NEW YORK 22, N. Y
YES Enter my the money- the next 10	Introductory subscription a saving rate of only \$2.69 for issues.
☐ Payment encl	osed Bill me late
_ ,	
Name	
Name(r	please print)
Name	
Name(r	



LATEST SAMS BOOKS FOR EVERYONE IN ELECTRONICS



USE THIS HANDY ORDER FORM

7000 GROSS		Servicing Electronic Organs. Describes typical circuits for each section of the organ. Includes special chapters on tuning, adjustment and accessories. Full typible shooting describe.
E		troubleshooting details. Order ORG-1, only \$4.95
DESCRIPTION OF STREET		Having Fun with Transistors. Thirteen fun-filled, useful construction projects using simple transistor circuits. Easy to build—wonderful variety of practical
E E		projects and games. Order THF-1, only \$2.50
THE EXPONENTS MACHINE		Air Conditioning Installation & Maintenance. Describes theory and operation of all types of air conditioners; central, room, auto—tells how to install, repair and maintain. Order ACM-1, only
H		Sams PHOTOFACT Guide to TV Troubles, Causes of
STATES STREET, N		more than 90% of TV troubles can be isolated in minutes by following the procedures described in this book; shows symptoms, analysis checks and where to look for troubles. Order PFG-1, only\$2.50
28		Transistor Substitution Handbook, Shows over 13,600
00000		direct substitutions; includes basing diagrams, polar-
100		ity indications and manufacturers for over 4000 transistor types. Order SSH-3, only\$1.50
2010		Computer Basics: Solid-State Computer Circuits, Followup
50	ш	to the famous Sams "Computer Basics" 5-volume
		work. Describes latest use of semiconductors in
		today's computers. Order CSS-6, only\$4.95
8		All 6 "Computer Basics" Volumes \$27.00
I		Amateur Radio Antenna Handbook. Tells how to select
20 %		the best antenna system for optimum performance.
Name of		Details theory, antenna design, construction and application. Order AMA-1, only \$2.95
200		
E STATE		How to Read Schematic Diagrams, RSD-1\$1.50
3000		Basic Electronics Series: Transistor Circuits, BET-1 2.95 1962 Test Equipment Annual, TEA-2
0000		Modern Dictionary of Electronics, DIC-1 6.95
K		ABC's of Radiotelephony. ABT-1
1200		ABC's of Electronic Organs. ECO-1
100		ABC's of Synchros & Servos, ASE-1 1.95
100		Radio Receiver Servicing, RS-2
S.13m6		101 Ways to Use Your Oscilloscope, TEM-2 2,50
1		



Address

FREE! Ask for the Sams Booklist, describing over 200 important books.

FREE! Index to Photofact, world's finest circuit data on 53,000 TV & radio models.

HOWARD W. SAMS & CO., INC.

Order from any Electronic mail to Howard W. Sams & 4300 W. 62nd St., Indiana	Co., Inc	c., Dept. A.143
Send books checked above	. \$	enclosed.
☐ Send FREE Booklist.	☐ Send	Photofact Index
Name		

City Zone State

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

NEW see the SCIENCE and MECHANICS

10 foot King Size Push-Pull Steel Tape \$2.75

Developed for making difficult upright and horizontal measurements. Wide blade can be extended for easier, more accurate work. Chrome plated die cast case. ¾ inch tempered steel blade has bonderized white enamel finish on both sides. Blade marked in eighths and sixteenths in large easy-to-read jet black. "Quick-conversion" foot and inch markings on blade. Self-adjusting end hook assures accurate inside and outside measurements. EXTRA: free tape holster complete with belt clip included. Only \$2.75 each.



Science and Mechanics PRODUCTS DIVISION

505 PARK AVE./NEW YORK 22, N. Y.

Please send me King Size
Push-Pull SCIENCE and MECHANICS Tapes at \$2.75 each. I am enclosing full payment.

					(ple	ase p	rint)		
Add	ress	S							
City					Zor	1e	Sta	te	
	Add	10%	for	Can	adian	and F	oreign o	rders	F1620

Pick the course for your career...

Electronics Technology



A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.

Electronic Communications



Mobile Radio, Microwave and 2nd Class FCC Preparation are just a few of the topics covered in this "compact" program . . . Carrier Telephony too, if you so desire.

First Class FCC License



If you want a 1st Class FCC ticket quickly, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.

Broadcast Engineering



Here's an excellent studio engineering program which will get you a 1st Class FCC License and teach you all about Program Transmission and Broadcast Transmitters.

Get A Commercial FCC License ...Or Your Money Back!

A Commercial FCC License is proof of electronics skill and knowledge. Many top jobs require it ... every employer understands its significance. In your possession, an FCC Commercial Ticket stamps you as a man who knows and understands electronics theory . . . a man who's ready for the high-paid, more challenging positions.

Cleveland Institute home study is far and away the quickest, most economical way to prepare for the FCC License examination. And that's why we can make this exclusive statement:

The training programs described above will prepare you for the FCC License specified. Should you fail to pass the FCC examination after completing the course, we will refund all tuition payments. You get an FCC License . . . or your money back!

Before you turn this page, select the program that fits your career objective. Then, mark your selection on the

Cleveland Institute of Electronics

1776 E. 17th Street, Dept. EX-1 Cleveland 14, Ohio



Accredited Member

coupon below and mail it to us today. We'll send you . without obligation . . . complete details on our effective Cleveland Institute home study. Act NOW . . . and insure your future in electronics.

1776 E. 17th St., Dept. EX-1	f Electronics
Cleveland 14, Ohio	Ham to 0
Please send FREE Career Informa- tion prepared to help me get ahead in Electronics, without further obligation.	How to Succeed in Electronics
CHECK AREA OF MOST INTEREST—	A STATE OF THE PARTY OF THE PAR
☐ Electronics Technology ☐ Fig.	rst Class FCC License
☐ Industrial Electronics ☐ El	ectronic Communications
Broadcast Engineering	other
Your present occupation	
Name (please print)	Age
Address	



- □ STEREO & MONO HI-FI □ TEST INSTRUMENTS ☐ HAM GEAR ☐ CITIZENS TRANSCEIVERS □ WALKIE-TALKIES
 □ TRANSISTOR RADIO
- · All easy-to-build with complete, step-by-step, beginner-tested pictorial instructions
- · All tremendously economical cost 50% less than comparable wired units
- uncompromisingly engineered

 All professional quality — CATALOG - Mail coupon today - - -

EICO Electronic Instrument Co., Inc. 3300 Northern Blvd., L.I.C. 1, N.Y. Please send FREE catalog and name of neighborhood dealer. Name



Send for

City_ _Zone___State_

Address

RTE-63a

URPLUS

DC SUPPLIES

Operate from 115 volts 60 cycle; are complete with Transformer, Rectifier, Capacitor, Switch, Line Cord, Pilot Light, Line Fuse, etc. Indicated ratings are for load conditions.

Dual output 12/11 or 21/28 Dual output 12/11 or 21/22 VDC (r 6 amps Size 7 x 65 x 13 Vt 17 lbs x #1'S-12/24VDCGA KIT l'arts \$20.00—Wired

| STK | π | 13 | W| | 17 | Ibs |
| STK | π | 18 | 2/24 VDC 6A | K1T |
| Output | 12/14 VDC 66 | 6A | Size 5½ x 3½ x 5";
| WI | 15 | Ibs | STK | π | FS | 12 VDC 6A | K1T |
| Output | 24/28 VDC | 6A | Size 5½ x 3½ x 5";
WI	15	Ibs	STK	π	FS	12 VDC 6A	K1T
Output	24/28 VDC	6A	A	S	x	5½ x	5½ x
WI	12	Ibs	STK	π	TS	21 VDC 7A	K1T
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x	5½ x	
Output	24/28 VDC	6A	A	S	x		
Output	24/28 VDC	6A	A	S	x		
Output	24/28 VDC	6A	A	S	x		
Output	24/28 VDC	6A	A	S	x		
Output	24/28 VDC	6A	A	S	x		
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A	S			
Output	24/28 VDC	6A	A				
Output	24/28 VDC	6A	A				
Output	24/28 VDC	6A					
Outpu							



		\mathbf{R}	D	10	SA	L	ES
2133 ELI	DAF	D	Box	1105	· LIM	A,	OHIO

i	FAIR RADIO SALES Dept. 20—P. O. Box 1105—Lima, Ohio—U.S.A.	
i	NAME:	
_	ADDRESS:	-
	CITY:STATE:	

NOW! EARN YOUR A. S. USE

DEMAND FOR ELECTRONIC ENGINEERING TECHNOLOGISTS EXCEEDS SUPPLY! Enroll with a nationally-recognized leader in electronics education. ECPD Accredited Technical Institute curricula in Electronic Engineering Technology and Commercial Broadcast Technology. Complete career preparation for booming fields of ELECTRONICS—COMMUNICATIONS—BROADCASTING—COMPUTER TECHNOLOGY—COMPUTER PROGRAMMING. College level resident and home-study courses. Coeducational, Up-to-date laboratories feature IBM. BENDIX and UNIVAC electronic computers and data processing equipment. SEND COUPON FOR COMPLETE CATALOG.

CENTRAL TECHNICAL INSTITUTE 1644 Wyandotte, Kansas City 8, Mo. Address... _Zone_ State_ CHECK INTERFST [] Resident [] Home Study

When Answering

Advertisements Say

You Saw It In

RADIO-TV EXPERIMENTER



GET YOUR First Class Commercial F. C. C. LICENSE IN 12 WEEKS!

Is the course proven?

A high percentage of our fulltime resident students get their 1st class licenses within 12 weeks from the time they start the course. Intensive FCC license training is our specialty — not just a sideline.

Is the course complete?

The Grantham course covers all the required subject matter completely. Even though it is planned primarily to lead directly to a first class FCC license, it does this by TEACHING you electronics.

Is the course "padded"?

The streamlined Grantham course is designed specifically to prepare you to pass certain FCC examinations. All of the instruction is presented with the FCC examinations in mind. If your main objective is an FCC license and a thorough understanding of basic electronics, you want a course that is right to the point — not a course which is "padded" to extend the length of time you're in school. The study of higher mathematics or receiver repair work is fine if your plans for the future include them, but they are not necessary to obtain an FCC license.

Is It a "coaching service"?

Some schools and individuals offer a 'coaching service" in FCC license preparation. The weakness of the "coaching service" method is that it presumes the student already has a knowledge of technical radio. On the other hand, the Grantham course "begins at the beginning" and progresses in logical order from one point to another. Every subject is covered simply and in detail. The emphasis is on making the subject easy to understand. With each lesson, you receive an FCC type test so you can discover daily just which points you do not understand and clear them up as you go along.



Is the school accredited?

Accreditation by the National Home Study Council is your assurance of quality and high standards. Grantham is accredited.

Is it a "memory course"?

No doubt you've heard rumors about "memory courses" and "cram courses" offering "all the exact FCC questions." Ask anyone who has an FCC license if the necessary material can be memorized. Even if you had the exact exam questions and answers, it would be much more difficult to memorize this "meaningless" material than to learn to understand the subject. Choose the school that teaches you to thoroughly understand — choose Grantham School of Electronics.

THE GRANTHAM FCC License Course in Communications Electronics is available by CORRESPONDENCE or in RESIDENT classes.

For further details concerning F C.C. licenses and our training, send for our FREE booklet

Accredited by the National Home Study Council rantham Schoo (Moil in envelope or poste on postal card) To: GRANTHAM SCHOOL OF ELECTRONICS NATIONAL HEADQUARTERS OFFICE 1505 N. Western Ave., Hellywood 27, Calif. 3123 Gillham Road Ans Marine Street 1505 N. Western Ave. Kansas City 9, Mo. Washington 6, D. C. Les Angeles 27, Calif. Seattle 4, Wash. (Phone: ST 3-3514) Please send me your free booklet telling haw I can get my com-(Phone: MA 2-7227) (Phone JE 1-6320) (Phone: HO 7-7727) mercial F.C.C. license quickly. I understand there is no obligation and no salesman will call, FIRST CLASS F.C.C. LICENSE IN 12 WEEKS Grantham resident schools are located in four major cities - classes in F. C. C. license preparation are offered at all locations. New day classes begin Address _ every three months, and new evening classes begin four times a year. City MAIL COUPON NOW - NO SALESMAN WILL CALL ☐ Home Study, ☐ Resident Classes E3A

CITIZENS BAND SALE!!! COMMAND GP-1 GROUND PLANE ANTENNA. Solid Alum, radials, heavy duty, Reg. \$16...SALE COMMAND CB SILENCER KIT—Model SN-3 (15-pc. mobile neise suppression kit: contains tuneable generator suppressor, spark plug and distributor suppressors, gen. cond. feed-thrus)....SALE \$4.99 COMMAND 3X LIMITER KIT 3 FILTERS (HI-PASS, LO-PASS, LINE)..SALE \$3.99 COMMAND CONTACT II Reg. \$12 102" Whip + Spring + Body Mount....... SALE \$6.89 SAVE ON ULTRA-LO-LOSS FOAM COAX CABLE!!! | 50 ft.—RGSBu Coax Cable | SALE \$2.49 | | 100 ft.—RGSBu Coax Cable | SALE \$3.99 | | 50 ft.—RGBu Coax Cable | SALE \$4.95 | | 100 ft.—RGBu Coax Cable | SALE \$4.95 | Check items wanted. Return ad or order with check or money order. Include postage, excess refunded. SQc service charge on orders under \$5.00. Beams and 102" white shipped Railway Express. S0% deposit on C.O.D. 8 D CE DEALERS: Write for Quantity Prices! GROVE ELECTRONIC SUPPLY COMPANY 4109 W. Belmont Avenue, Chicago 41, Illinois Ph. AV 3-6160 ☐ Rush Items checked ☐ Send FREE catalog of giant CB Values Name (please print)



ON SALE NOW! most newsstands



Woodworkers Encyclopedia—618

A must guide for every handyman working with wood. Over 42 heavily illustrated and detailed articles show you how to work with various kinds of woods to achieve prohow to work with various kinds of woods to achieve pro-fessional results, with special sections devoted to the use of many types of tools as they apply to specific projects. Accurate and easy to follow how-to-do-it instructions for scores of different operations in the workshop. A few of the informative articles you'll enjoy reading and actually doing are:

- Radial-Arm Saw Savy
- Safety Sticks for Your Circular Saw
- Clamping Irregular Work Modern Multi-Purpose Workbench
- Tricky Methods of **Decorating Plywood**
- Glues for Homecrafters
- Carving Wood Kitchenware
- · Mini-Turning on the Lathe Sewing Machine Jigsaw
- Projects . Do Your Picture Framing
- at Home

Home Built Power Tools-619

A real money saving how to handbook that gives the home craftsman step-by-step instructions for making power tools from salvage, surplus and/or inexpensive items found around his workshop or in the supply store. Each project is illus-trated with complete and accurate diagrams. A materials list is also provided to help you reduce building time and ensure a finished tool that will meet with all your requirements. A few of the power tool projects featured in this handbook are:

- Making Shaped Cutters from Steel

- from Steel
 Shop Bench Spot Welder
 Handy Cement Mixer
 Power Filing and Saber
 Sawing Machine
 Switches to Lock Power
- Tools
- Portable Air Compressor
- Speed Reducer for Bigger Boring
 Slitting Saw Arbor
 Portable Drill Doubles as
- Multi-Purpose Tool Build Your Own Belt
- Sander

Pick up a copy at your newsstand or send \$1.00 to include postage and handling with coupon below

Handbook New York	Division, 50 22, New Yo	include postage	lue
1	618	619	
NAME	(PLEAS	E PRINT)	
ADDRESS			
CITY	7	ZONE STA	TE

The Same School That Originated The RTS BUSINESS PLAN

Proudly Presents

A SPECIAL COMPACT COURSE COVERING ALL THREE PHASES OF

The Entire Course Is Made Up Of The Following:

- . 35 LESSONS COVERING BASIC AND INTERMEDIATE ELECTRONICS
- · 9 EQUIPMENT KITS COMPLETE WITH TUBES AND BATTERIES
- · SOLDERING IRON
- . 25 LESSONS COVERING THESE ADVANCED ELECTRONIC SUBJECTS:

Thyratron Tubes . Semiconductors . Electronic Symbols and Drawings • Voltage-Regulators . Electronic-Timers · Control Systems · X-Rays · Photoelectric Devices · Dielectric Heating · Geiger Counters · Pulse Circuitry · Clippers and Limiters · Multivibrators . Electronic Counters . Radar · Magnetic Amplifiers · Analog-Computers . DC Amplifiers . Digital Computers · Storage Systems · Input and Output Devices . Servomechanisms . Telemetering

- . 60 EXAMINATIONS
- . IINLIMITED CONSULTATION SERVICE
- KIT MANUALS
- . DIPLOMA UPON GRADUATION

BASIC . INTERMEDIATE . ADVANCED

DESIGNED FOR THE BUSY MAN OF TODAY

This is MODERN training for the MODERN man. You'll find no "horse and buggy" methods here. Every page of this streamlined course is dewoted to important Electronics principles and practical projects. You'll be amazed how fast you grasp Basic Electronics the RTS way. RTS has combined modern THEORY and PRACTICE to make this the finest training program of its kind available!

SATISFIES NOVICE, TECHNICIAN OR HOBBYIST

Whether you're new to Electronics or an old "pro," chances are you'le find this to be the ideal course for you. The novice will appreciate the completeness of the training. It starts with the most basic considerations, covering each important point thoroughly, yet concisely. The technician will enjoy the practical review of fundamentals and profit from the 25 advanced subjects covered.

RTS GIVES YOU "TOP MILEAGE" FOR YOUR TRAINING DOLLAR

The price quoted below buys EVERYTHING—there are no extras to pay for RTS has gone 'all out" to give you the best training value in America. Why pay hundreds of dollars for training such as we offer when it's available for this LOW PRICE? If you can find a better training bargain

CAN BE COMPLETED IN MONTHS INSTEAD OF YEARS
Some students will complete this course with "Jet-Like" speed but we allow up to two years if your circumstances require it. You study at your own rate. You are ENCOURAGED but not pushed. You'll find the lessons professionally written LET US SEND YOU ONE OF THESE LESSONS ALONG WITH YOUR CAREER BOOKLET SO YOU CAN SEE FOR YOURSELF. NO OBLIGATION!

AND MUCH MORE ...

RTS' Membership In The Association of Home Study Schools is your assurance of Reliability, Integrity and Quality of Training.



RTS ELECTRONICS DIVISION EGS E. ROSECRANS AVENUE LOS ANGELES 59, CALIFORNIA





Coupon

NO SALESMAN WILL CALL!



DON'T LOSE OUT - FIND OUT!

KIT WILL BE RUSHED TO YOU THE SAME DAY THEY ARE RECEIVED!

RTS ELECTRONICS DIVISION Dept RTE 3 E15 E. ROSECRANS AVENUE LOS ANGELES 59, CALIFORNIA

Rush me full information by return mail. (Please Print)

Address State City

ENROLL ME NOW

SEND MORE FACTS

New Ram Jet Engine Burns Gasoline!

Powerful continuous



Powerful Electric Generator

Cost U. S. Gov't \$20,001 While They Last \$3.95-Brand New!

Cost U. S. Gov't \$20.00! While They Last Generates Up To 100 Votts. generate electricity, to ring bells, light up lights, as a medical battery, deliver territe electric shock as joke, many electrical experiments. Hand crank or gear classroom uses, etc. Hand crank or gear companies. Powerful almon magnets (alone worth more than total cost). Ready for use, Postpaid \$3.95.

Underwater Electronic Potential Supplied to the cost of the cost

Postpaid \$3.95.
Underwater Electronic Detector
Gov't Surplus. Cost \$200.00; Special \$7.95,
Brand new. Use as detector or use parts for
other devices such as mike, pick-up, etc. Wt. 30 lbs. F.O.B. Detroit. Only.

Johnson Smith Company, Dept. 230. Detroit 7, Michigan

Johnson Smith Company, Dept. 230. Detroit 7, Michigan

POWERFUL NEW INVENTION, ONLY 2" LONG

SHOOTS THRU 100 PAGES-THIS BOOK!



MAKE THIS TEST . . . Load your 'BB Shot' and fire against this magazine. Notice that it drives BB's through more than 160 pages. Though only 2" long x 1" in diameter, this pocket-size device has amazing power and accuracy. Use it for targets, pests and hunting. Scientifically designed for high power, operating ease and safety.

FREE! Cone and FREE Target, BB's and Automatic BB Dispenser . . all for only \$1.98 ppd. 3 for \$5.00 ppd. Money Back Guarantee. Not sold to N. Y. C. residents or minors.

GRAYSON PROD., INC., Dept. D-19, 210 Fifth Ave., N.Y. 10, N.Y.

City State....



LEARN ELECTRONICS with a TEACHING MACHINE

You learn easily and quickly, step by step, at home, at your own pace. Teaching Machines and Programed Learning are the most important advances in educational techniques for 50 years or more. Said to be: "The most significant aid to learning since the invention of movable type." A.I.E.T., established over a quarter-century ago, has more than 25,000 successful graduates. Now, A.I.E.T. is the first technical institute to offer home training through Teaching Machines and Programed Learning.

LABORATORY KITS, Practical, learn-by-doing training projects include test equipment useful after graduation.

EXCELLENT CAREERS IN THE ELECTRONICS INDUSTRY AWAIT TRAINED MEN. Qualify for a career in electronics in the Best, Fastest, Most Efficient way possible, at home in your spare time. Write now for full details.

TUTORMATIC DIVISION

AMERICAN INSTITUTE OF ENGINEERING & TECHNOLOGY 1135-45 W. Fullerton Pkwy. - Chicago 14, Illinois

Surplus Sun Battery & Photocell \$1.00



Brand new. Sav. 300%. Genuine famous braud account of the control of the control

Johnson Smith & Co.

Dept. 230

Detroit 7. Michigan

Hypnotize Fast with Hypno-Matic



Amazing Hypno-Matic invention only \$1.00. Eyecarching hypnotic device operates on rotating
tion for QUICK HYPNOTIC TRANCE. Easily concealed in borket or hand. Control people during
snell & afterwards, too! With 2 books on hypnotiam: uses dangers, post-hypnotic control, selfhypnotism for correcting bad habits & easier
thermore, oriented habits & easier
thermore, oriented habits & easier
postpostpaid.

Postpaid.

Johnson Smith & Co., Dept. 230 Detroit 7, Michigan

TRANSISTOR RECEIVER KIT

Critical resistors, condensers and transistors are pre-mounted. Oscillator and IF cans come factory aligned so no equipment is needed for alignment. Powerful 14 watt output. Circuit is designed for long-life battery operation. Comes complete with 9 volt battery, earphone and leather carrying case. Schematic and parts layout diagram included.
Only \$18.95 postpaid. Send check or money order.
NIPPON OVERSEAS

TV REPAIR BOOKLET-FREE

To Prospective Customers for Tubes and Parts "Professional TV-Radio Servicing for Everyone" Reveals tricks of the trade. Shows how anyone can quickly diagnose any trouble-professionally, easily, accurately. No hit or miss, no guess work. Booklet is yours for the asking. No strings attached, no gimmicks,

CENTURY ELECTRONICS, Dept. RT-1 Box 327 Hicksville, L. I., N. Y. P. O. Box 327



delightful, exciting

FANTASTIC OFFER ALL TEN MOVIES IN 8mm FOR ONLY (16mm-\$4)

The movie buy of a lifetime! Ten subjects, all different, brand new and thrilling, and all yours for only 20c each. You must be delighted or your money back! Rush \$2 (cash, check or money order) to: SENSATIONAL MOVIE OFFER

Box 69856, Dept. G-13 West Hollywood 69, Calif.

EXPERIMENTERS ● AMATEURS ● HOBBYISTS

Save real money on radio parts. Write today

for big free catalog of government surplus electronic materials, many items priced at 90% below list. All are new unless otherwise indicated. Here's a sample:



\$12.95

FOR SACRAMENTO

ELECTRONICS

SEND FOR CATALOG TODAY P.O. BOX 6188 CCC SACRAMENTO, CALIFORNIA POWER SUPPLY FOR RECEIVERS, AMPLIFIERS ETC.

POWER SUPPLY FOR RECEIVERS, AMPLIFIERS ETC.

RA-42 rectifier power supply designed for use with the BC-639.

Here's your chance to pick up a beoutful reck-mounting power supply for a song We've seen these advertised as high as 339 50; load of our law price. Line and plate circuits are fused and this supply may be operated from 115 volt or 200-250 volt, 60 cycle AC Plate voltage is about 250 of better than 100 mils with an auxiliary 3 amps at 6 3 volts for heavest than 100 mils with an auxiliary 3 amps at 6 3 volts for heaves. Filter is dual section with two choices and 2 sect, hemmetically seeled capacitier. Recrifter is 5V4. This and comes complete with dust cover and is used but looks just like new inside; outsides may be all shifty blamshad. We have a few units that are dirty and married from handing without proper pocking; while these last Mey ore priced or just 39 93. Overall height is 37", depth behind panel is only 6:1/4" over dust cover. All connections are on rear chassis agron. Shipping weight 35 pounds. Buy three for a hundred pound shipment at \$34.95. (L-14)

VACUUM TUBE VOLT METER KIT (6-INCH METER) RMS and p. to p. scale. Input imped. 12.2 megs. Professional performance and appearance. Kit: \$31.95
Assembled: \$44.95





"CUSTOM 70" TV SET KIT—Excellent sensitivity. Transformer power supply; 3 stages of 1F. In-cludes slimline cabinet, 19 inch picture tube everything. Kit Price: \$135.00

TRANSISTOR RA-DIO KIT -Superb tone and sensitivity. No deland sensitivity. No delicate printed circuits. Attractive, durable case, All U.S. made parts. Kit: \$25.50





5-INCH WIDE BAND OSCILLOSCOPE KIT—For black-white, color, AM-FM and electronic applications. High intensity trace Extremely stable sync. Advanced design. Kit: \$89.50 Kit: \$89.50 | Assembled: \$139.50 |

Get your FREE 1963 CATALOG

from CON

It's full of exciting new electronic kits of highest quality. Many items available in both kit or assembled form. Home entertainment items that make perfect family gifts or test instruments for the technician who appreciates quality and high performance. Tools, too, to make your work easier, faster. And you'll like the reasonable prices and convenient payment plans which make CONAR Kits easy to own. Mail coupon for new 1963 Catalog now.



division of NATIONAL RADIO INSTITUTE

Mail this Coupon

GUARANTEE Parts and performance guaranteed by NRInearly 50 years of pioneering in

Electronics.

CONAR 3939 Wisconsin Ave., N.W. Washington 16, D.C.

AP 3C

Send me your new 1963 CONAR KIT CATALOG

Name		
Address		
City	_Zone	_State

ELECTRONIC SURPLUS BARGAINS

100 Disc Ceramic Cond. Asstd
CK-722 Transistors
Silicon Diodes 500 ma. 400PIV3/1.00
Ptd. Circuit Boards Copper Laminate 3 x 108/1.00
Germ. Rect. 5 amp 200 PIV1.00
Snooperscope tube see in dark #60326.50
SNIPERSCOPE M3 SEE IN DARK
Ceramic Magnets, stronger than Alnico12/1.00
Infra Red filter 5½ inch
K-25 Camera, Govt. cost \$1,200
IBM Modular Stack (computer)1.00
IBM Memory plane, 200 bit5.00
IBM Memory plane, 8,000 bit
Transistor Battery Eliminator Kit
Miniature Mike Buttons4/1.00
Nickel Cadmium btry. 1.2v. 4 amp. hr1.95
Philco SB-100 Type Osc. Transistor3/2.00
Periscope Prism
Treasure Hunters: PRS-3 metal locator, with
btry
28 volt DC 4 amp. power supply, operates from
115v 60 cycle. Unused surplus, govt. cost
\$55012.50
Solar Bank Kit five cells With Instructions\$1.50

All material FOB Lynn, Mass. (you pay shipping). Minimum order \$5.00. These are a few selected bargains from our giant 60 page catalog of Government Surplus Material. Send 10r coin or stamps for your illustrated catalog.

JOHN MESHNA, JR. 15 Allerton St. Lynn, Mass. TRODUCTORY


DOUBLE **BONUS!**

BONUS #1 WORTH OF .00 RADIO-TV PARTS!!!

BONUS #2 POLY PAK OF YOUR CHOICE LISTED BELOW

Write for Catalog. Cut out and mail with check or money order; plus postage, C.O.D.'s 25%

P.O. Box 942X So. Lynnfield, Mass.

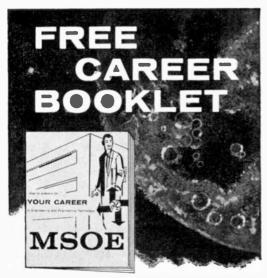

To guide you to a successful future in

ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL **ENGINEERING**

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

MISSILES . AVIONICS . AUTOMATION SALES . DEVELOPMENT **ELECTRICAL POWER · ROCKETRY** RADAR · RESEARCH

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

MILWAUKEE SCHOOL OF ENGINEERING

MAIL COUPON TODAY!
Milwaukee School of Engineering Dept. RTX-163 1025 N. Milwaukee St., Milwaukee, Wis. Please send FREE "Your Career" booklet I'm interested in Electronics Radio-TV Computers Electrical Engineering Mechanical Engineering
Name Age PRINT
Address
CityZoneState I'm eligible for veterans education benefits. Discharge date



Send for FREE OSCILLATOR CIRCUIT Catalog #962

Citizen Band Class "D" Crystals

3rd overtone — .005% tolerance — to meet all FCC requirements. Hermetically sealed HC6/U holders. ½" pin spacing, .050 pins. (Add 15c per crystal for .093 pins).

pins).
ALL 23 CHANNELS IN STOCK: 26.965, 28.975, 26.985, 27.005; 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.135, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225, 27.225.
Matched crystal sets for ALL CB units (Specify equipment make and model numbers)

make and model numbers)\$5.90 per set-

RADIO CONTROL CRYSTALS

In HC6/U HOLDERS-SIX FREQUENCIES

ENGINEERING SAMPLES and small quantities for prototypes now made at either Chicago or Fort Myers plants with 24 hour service. IN CHICAGO, PHONE GLadstone 3-3555 IF YOUR PARTS DEALER DOESN'T STOCK Texas Crystals, order direct and send us his name.

RUSH YOUR ORDER NOW TO

Div. of Whitehall Electronics Corp. 1000 Crystal Drive, Fort Myers, Florida Dept. P-102 Phone WE 6-2100

FOR SHIPMENT VIA FIRST CLASS MAIL AT NO EXTRA COST ATTACH THIS ADVT. TO YOUR ORDER!

DO-IT-YOURSELF

ILLUSTRATED CATALOG



à

Now you can get simple easy-to-understand plans for building boats, electrical equipment, models of gas and steam engines, famous firearms, antique automobiles, toys, games, cabin trailers, many other projects. In all, 212 useful things you can build. It's easy! It's fun! And you can save money! Send now for this

brand new catalog.
SCIENCE AND MECHANICS CRAFTPRINT DIVISION 505 Park Avenue, New York 22, N. Y. Enclosed is 25¢ which I understand will be refunded to me with my first order. Please send me the new 1962 edition of the Science and Mechanics Craftprint Catalog.
NAME (PLEASE PRINT) ADDRESS
CITYZONESTATE

A MUST TOOL FOR EVERY HOME CRAFTSMAN




This specially designed S&M Transfer Tool is a "must" for every home craftsman. Now, you can trace your full-size Craft Prints directly onto the wood—faster, easier, and more accurately, too.

The toothed wheel perforates the Craft Print and outlines your cutting edge in a series of pin-point marks. The S&M Transfer Tool is easily guided along any line—straight or curved.

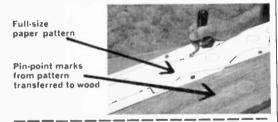No craftsman can afford to be without a Transfer Tool. You shouldn't be without it another day. Order your S&M Transfer Tool now—use the coupon below. Only \$2 each, postpaid.






SCIENCE and MECHANICS Product Division

505 Park Avenue / New York 22, N. Y.

Enclosed is my payment of \$_____. Please send me_____S&M Transfer Tools. (\$2.00 each in U.S.A., \$2.25 in Canada and all other countries.)

Name	(pleas	e print)
Address		
City	ZoneState	620

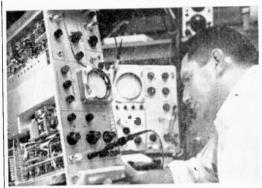

You Can PREPARE NOW For ELECTRONICS TECHNICIAN TELEVISION BROADCASTING F. C. C. LICENSE

No previous technical experience or advanced education needed!

Now is the time to learn a skill that can put you ahead. In either civilian or military life, the trained technician is in demand for the better jobs—the higher ratings.

Opportunities are great in many Electronic fields.

Our up-to-the-minute training prepares you at home, in your spare time. Covers basic and advanced electronics, and trains you for FCC license exam. Modern electronic project kits for home assembly are provided.

FREE SAMPLE LESSONS: We will send you Lessons 1 and 2, without cost or obligation. See for yourself how quickly you grasp electronic principles.

You can get all the facts on our training program, and information about age and requirements necessary for employment as an Electronics Technician. Mail the coupon or write to ELECTRONICS DIVISION, Northwest Schools, Dept.NX-1E, 1221 N. W. 21st Ave., Portland 9, Oregon.

Send today for y	our FREE LESSON
Please send me, without SONS and all the facts of	. 21st Ave., Portland 9, Ore. obligation, your FREE LES- the training checked below:
Name	
Address	
City	State
Nearest Phone	Age

Coming in the Feb. Issue



"The monthly magazine for craftsmen"

Do-it-yourselfers will also be interested in:

- Knowing what adjustments and repairs to make when your power steering starts giving you trouble so you can save by not having to pay a big repair bill.
- An informative article that gives you tips and graphic illustrations on how to make bevel cuts for turning corners.
- Techniques used to plane lumber to size in your own workshop so you can always be assured of the right size.

Fact or Fiction ...

Robots have proven they are better than humans in exploring space and duplicating man's physical actions in research and industry. Therefore, it's only logical he become part of man's family and help raise his children.

Atomic Artillery ...

These technically "obsolete" atomic cannons facing East out of West Germany may be the reason why we are having a war of words, not armament. Each cannon, as you can see in the article, is precision built to deliver optimum devastation with bullseye accuracy.

Weapons Against Crime...

Is it possible that our police departments are using out-dated, antiquated weapons against a modern crime arsenal? "Is the Police Revolver Outmoded?" gives the hard-hitting facts.

On Sale December 27th

AT ALL NEWSSTANDS



Classified MARKET PLACE

For Information on Classified ads—to be included in our next RADIO-TV EXPERIMENTER HANDBOOK and other Handbooks—write C. D. Wilson, Mgr., Classified Advertising, SCIENCE and MECHANICS HANDBOOK DEPT., 505 Park Ave., New York 22, N. Y.

ADDITIONAL INCOME

MAKE \$25-50 week, clipping newspaper items for publishers. Some clippings worth \$5.00 each. Particulars free. National, 81 Knickerbocker Station. New York 2.

CENTRAL Nevada 10 acres including minerals. \$30.00 down, \$10.00 monthly. \$300.00 full price. Owner, Box 2372. Van Nuys. Calif.

\$100 WEEKLY possible. Compile mailing lists and address envelopes for advertisers. Home-spare time. Particulars free. National Service, 81, Knickerbocker Sta., New York City 2.

ATHLETIC EQUIPMENT & BODY BUILDING EQUIPMENT

WEIGHT Exercising Equipment. Free literature. Ed Jubinville, Holyoke, Mass.

AUTHOR'S SERVICE

LOOKING FOR A Publisher? Learn how we publish, promote, distribute your book. Free Booklet H-1. Vantage Press, 120 West 31st, New York 1.

PUBLISH your book! Join our successful authors; publicity advertising promotion, beautiful books All subjects invited. Send for free appraisal and detailed booklet, Carlton Press, Dept. SMA, 84 Flifth Avenue, New York City 11.

AUTOMOBILES & MIDGET CARS

AUTOMOBILE Catalogs, photos. Antique, modern, Hobby Club. Information Free. Enthusiasts, Box 451G, Mt. Clemens,

BUSINESS OPPORTUNITIES

ASSEMBLE Artificial Lures at home for stores. Materials supplied Free. Profitable! Write: Lures, Ft. Walton Beach, Fla.

PAWNBROKER. Be one. I'll teach you. Amazing profits. Pawnbroker Thayer. Bath. Maine.

MAKE Mail Order pay. Get "How To Write a Classified Ad That Pulls." This handbook tells how, with examples: Includes certificate worth \$2.00 toward classified ad in S & M. Send \$1.00 to C. D. Wilson, Science and Mechanics, 505 Park Ave., New York 22, N. Y.

BUY IT WHOLESALE

"FREE Merchandise!" 350.000 Items "Wholesale!" Goldmine, 240-S, Planetarium Station, New York City 24.

CAMERA & PHOTO SUPPLIES

AT last! Build you own supersensitive light meter from complete kit with easy to follow instructions. Uses newest cadmium sulfide light cell, shows ASA speeds 3 to 25,000. F stops .7 to 90 measures accurately moonlight to bright sunlight. Send \$19.95 to Kit Division, Science and Mechanics, 505 Park Ave., New York 22, N. Y. Money completely refunded if Kt returned within ten days for any reason.

DO IT YOURSELF

FIREPLACE in your home—simply and econom-cally done. Install it yourself with plans in our Home Modernization Handbook ±615. 35 Do-lt-yourself improvements. A real help in keeping house and garage in top shape. Send \$1.00 to Handbook Dlv. Science and Mechanics, 505 Park Ave., New York 22, N. Y.

EARTHWORMS

BIG Money Raising Fishworms and Crickets. Free Literature. Carter Farm-O. Plains. Georia.

ELECTRICAL EQUIPMENT & SUPPLIES

COMPLETE kit with easy to follow instructions for building a high precision all purpose tachometer. 3 ranges. Measures speeds on tape recorder. lathes, cutting tools, auto engines, model plane engines, many more uses. Only \$16.95. If not completely satisfied, kits may be returned within ten days for a complete refund. Kit Division, Science and Mechanics, 505 Park Ave., New York 22, N. Y.

EMPLOYMENT INFORMATION

OVERSEAS Jobs. List \$1.00. Universal. P. O. Box 682, (A), Kenosha, Wisc.

FOR INVENTORS

PATENT Searches—48 hour airmall service, \$6.00, including nearest patent copies. More than 200 registered patent attorneys have used my service. For Free invention protection forms and sample patent application, write Miss Ann Hastings, P.O. Box 176, Washington 4, D. C.

THOUSANDS of expert answers to your patent questions. 160 pages covering marketing, attorney's fee, clinics, searches, many other subjects. Send \$1.00 for "Inventor's Handbook" #600 to Handbook Div. Science and Mechanics, 505 Park Ave., New York 22.

PATENT Searches, including copies of related U. S. patente, \$6.00. Inventors, attorneys, manufacturers use my "World-wide" ai-mail service, "Invention Record" form and Information Every Inventor Needs, sent free. Miss Hayward, 1029 Vermont Ave., N. W., Washington S. D. C.

HOME WORKSHOP SUPPLIES

ANSWERS to your woodworking problem? We've got them in Woodworker's Encyclopedia No. 618. How the pros use tools. A must book. Send \$1 to Science and Mechanics, 505 Park Ave., New York 22. New York.

HYPNOTISM

NEW concept teaches you self-hypnosis quickly! Free literature. Smith-McKinley, Box 3038, San Bernardino, Calif

MATHEMATICS

FUTURE System of Mathematics, Guaranteed. \$1.00. Knowledge, 2900-9th St., Rock Island 19, Ill.

MISCELLANEOUS

CATALOG of all Science and Mechanics Craftprints. Send 25¢ to cover postage and Handling to Craftprint Div. Science and Mechanics, 505 Park Ave.. New York 22.

MONEYMAKING OPPORTUNITIES

INCOME From Oil Can End Your Toil! Free Book, Maps! National Petroleum, Pan-American Building-SM, Miami 38, Florida.

MUSIC & MUSICAL INSTRUMENTS

PIANO Technic Simplified. \$1.25. Waiter Kazaks. 234 East 58th Street, New York 22.

STEREO Music Center—beautifully made from complete step-by-step plans in Furniture Handbook #616A. 40 Useful projects for attractive additions in every room in the house. Send \$1.00 to Handbook Div., Science and Mechanics, 505 Park Ave.. New York 22, N. Y.

PATENT SERVICE

PATENT Searches—48 hour airmail service, \$6.00, including nearest patent copies. More than 200 Registered patent attorneys have used my service. For Free invention protection forms and sample patent application, write Miss Ann Hastings, P.O. Box 176, Washington 4, District of Columbia.

NO Letter to write! Special "Invention For Sale" form presents your idea to buyers. 6 for \$1.00. Science and Mechanics. Craft Print Div., 505 Park Ave., New York 22. New York.

PETS-DOGS, BIRDS, RABBITS, HAMSTERS, ETC.

MAKE big money raising rabbits for us. Information 25¢, Keeney Brothers, New Freedom, Penna.

PHOTO-FINISHING, ETC.

A Free Roll of Kodak Film with each developing and printing. Guaranteed Quality send for free mailers. Economy Photo Service, Dept. S. P. O. Box 111. Albany, New York

POWER TOOLS

HOME-BUILT Power Tools No. 619 shows you how to make 23 practical attachments. Also 17 complete tool projects. Real challenge to all craftsmen. Send \$1 to Science and Mechanics, 505 Park Ave.. New York 22, N. Y.

PRINTING, MIMEOGRAPHING & MULTIGRAPHING

ECONOMICAL Printing, Business, Personal, Free Catalog, Golden Glades, Box 64-18R. Miami 64, Fla.

RADIO & TELEVISION

GOVERNMENT surplus receivers, transmitters, snooperscopes. Catalog 10¢ Meshna, Małden 48, Mass.

CONVERT any Television to Supersensitive, Big-Screen Oscilloscope. No electronic experience necessary. Only minor changes required. Illustrated plans \$2.00. Reico, Dept. TV, Box 10563, Houston 18, Texas.

START YOUR OWN BUSINESS

SERVICE Business—Everyone likes to refinish furn ture but hates removing old finishes. We have pioneered the stripping business and helped over 60 men become independent using our exclusive process. For brochure write Bix. Box 8719. Kansas City 14. Mo.



Low Cost
PHOTO LIGHTS

Voltage booster operates common lamps as photofloods for color

By BRICE WARD

HE common household light bulb is designed to run on 120 volts, but feed it higher voltage and you've got a lamp that burns like an expensive photolamp at a fraction of the cost.

If you live where the power company supplies free exchange bulbs, you can save enough to pay for a booster in a few months,

Cameraman shoots color portrait using studio booster. A combination of 50, 100 and 150 watt house lamps gives him well balanced main light, side lights and background lights.

and best of all, you'll never be unable to shoot just because you burnt out your last photoflood. You can always get common houselamps at the corner drugstore, but you may not be able to get floods.

Of course, lamp life is reduced. A household bulb is designed to last several thousand hours at ordinary voltage. At the higher voltages used in this booster, the same lamp will last as long as a photoflood, three or four hours. By using the warmup circuit every time, and being careful not to jar the lamps while they are burning, you can extend lamp life considerably. Also, the booster enables you to use a variety of lamp sizes, shapes, and colors not available in photofloods to create special effects for color portraits, or special illustrative shots.

Two circuits are shown (Figs. 7 and 8). The portable booster will drive a 100 watt lamp (or two 50 watt lamps) to provide the equivalent of 300 watts of photoflood power. It has a 50% duty cycle and can be run up to half an hour, pro-

vided that you allow equal time for cooling, or add vents and a fan. Cost of parts as shown is less than \$15.00. The studio unit will handle a load of 500 watts, to produce lighting equal to four #2 photofloods. Parts should cost no more than \$29.00.

The Portable Booster fits into a 3 x 4 x 5in. aluminum minibox. Use a sharp scriber The studio unit, shown without metal grill cover has a main switch, and two slide switches. To use the unit, you warm the lamps a few moments, switch to OPERATE, and then to the 3200 or 3250 K settings. Outlets are on the rear.

to lay out the panel. Drill inside your layout lines making a line of holes as close together as possible. Break out the center and file the edges of the holes smooth. Then use the outlets and switches as templates to drill the mounting holes. A Keystone #139 battery holder acts as a heat sink for the rectifiers, and makes them easy to hook up. Enlarge the battery holder mounting holes to 3/16-in. Then mount the rectifiers. Make sure the battery clip fits snugly around the rectifier body, and that the rectifier shoulders are tight against the edge of the clip.

One rectifier, the MR-326 has a cathode-to-



MATERIALS LIST-PORTABLE BOOSTER

Amt.

Size and Description

- 20 mfd, 500 volt capacitors, Mallory type 83, Allied #17L246 10 mfd, 500 volt capacitors. Mallory type 81, Allied #17L245
- rectifier, Motorola MR-326, 18 amp. 1
- 1 rectifier, Motorola MR-326R, 18 amp.
- DPST switches, type SW325, Allied #35B920
- heat sink (battery box) Keystone #139, Allied #54J042
- #6 fiber washers, Allied #42N771
- line cord, Belden 17126S. Allied #49T211
- chassis mounting sockets, Cinch-Jones #2R2, Allied #40H830
- aluminum minibox, Bud CU-2105-A, Allied #80P397
- Allied No.'s refer to catalog of Allied Radio Corporation, 100 N. Western Avenue, Chicago 80, III.

MATERIALS LIST-STUDIO BOOSTER

Amt.

Size and Description

200 mfd. 150 volt capacitors, Mallory type 496, Allied #17L519

rectifiers, Motorola MR326 250 ohm, 200 watt resistor, Ohmite Dividohm, Allied #1MM830 extra sliders for above. Allied #75M882 3 PDT switches, Continental-Wirt SW369, Allied #35B922

SPST toggle switch, Arrow-Hart and Hegeman 82601, 15 amp, Allied #33B837

Anited #30B07 chassis mounting as sockets, Cinch-Jones, 282, Allied #40H830 double fuse clip, Littelfuse 357002, Allied #52B297 Drake Postlite neon indicator, Allied #78E062 8 amp 3AG fuses, Allied #52B248 12 x 7 x 4" Bud Minibox case, #CU-2111-A, Allied #80P353


line cord, 6 foot, Belden 17126S, Allied #49T211


Allied numbers refer to stock numbers in Allied Catalog #210A

case connection, while the MR-326R has anode connected to case. These connections are made at the clip and through the clip to the battery box frame. Since this clip is electrically hot, the battery box must be insulated from the case by mounting on spacers and washers.

The rest of the wiring is easy—just make sure that the capacitor

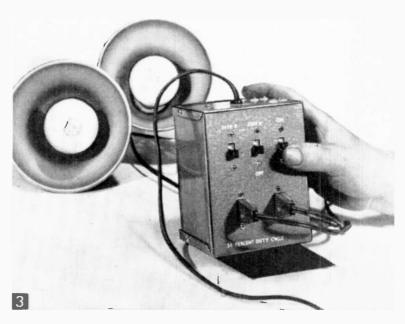The portable booster drives two 50 watt lamps. The circuit works well on movie light bars. Because the capacitors carry a heovy load, duty cycle is 50 percent.



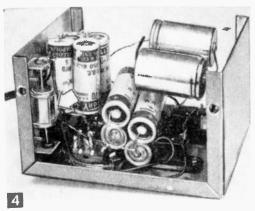


Inside the portable case, arrow shows power rectifiers mounted in battery clip used as heat sink. Capacitors are taped in place after assembly.


plus leads connect to the MR-326R center lead.

Operation. On low setting, run your lamps only a few minutes. The lowest-light output settings put the greatest load on the capacitors. The best way to get maximum lamp life, and to prevent blowing a capacitor is to use 5 to 10 second pauses at the low positions, just enough time to warm the lamps before applying the full voltage. The portable unit uses an unusual circuit principle, that of overloading a voltage doubler to obtain voltage control. Since doubler circuits usually have very poor regulation characteristics, voltage control can be obtained by reducing the capacitance below a certain critical value.


Capacitance of 20 mfd. in each leg with the 100 watt load effectively holds voltage down to about 120 volts. Throwing in the additional 10 mfd. per leg raises the voltage to 165 volts. Add another 10 mfd. capacitor per leg, and you have 185 volts for the 3450°K light output. Because these capacitors are just right for the rated load of 100 watts, no attempt should be made to change lamp size. This would affect the output voltages.

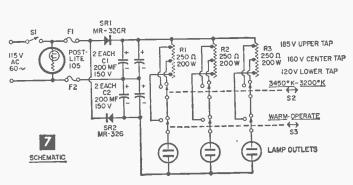The Studio Unit, unlike the portable boost-



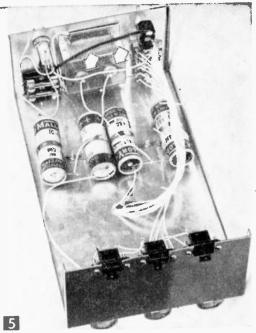

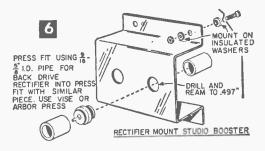Studio unit is easy to wire. Arrow shows rectifiers mounted on aluminum heat sink bracket. Capacitor polarity is important and must be correct. For heavy duty use, add a small fan and ventilating holes.



er can be used with various combinations of bulbs, because it is a more standard voltage doubler circuit and is designed for optimum operation with no excess load on the capacitors. Three large bleeder resistors (Fig. 2)

control the output voltages and kill un-needed power. During the operation, these bleeders will get hot enough to burn the hands. They should be covered at all times with screening on a metal frame. The entire unit should be cooled with a fan (see Materials List) if you plan to use the booster for long shooting sessions. Construction is similar to the small unit. Mount the parts on a 12 x 7 x 4-in. Minibox. Instead of the battery clip

mounting, press fit the rectifiers into an aluminum plate (Fig. 6) to get better heat dissipation. In this circuit, the rectifiers carry almost half the full-rated current, and thus must have more adequate cooling unless the booster is always used on very short duty cycles.

With all wiring complete and checked, set the taps on the resistors in the approximate positions as shown in Fig. 2. Connect your lamps, the same total wattage that will normally be used, and measure the voltage at each tap with a voltmeter.

Tap #1 on each resistor should read 120 volts with the switch in the warm-up position. Tap #2 on each resistor should read 160 volts with the first switch in the operate position and the second switch set on 3200K. Tap #3 on each resistor should read 185 volts in the operate and 3450 position. These voltage settings are approximate. Advanced professional photographers will want to

MR - 326 R HOV IO MF 500 V 450\ 50 V 500\ 50 V PORTABLE UNIT MR-326

> check light output with an accurate color temperature meter.


> Whenever you adjust these taps, be sure that all power is off including the wall plug, and that the capacitors are discharged. Use a pair of test leads and a resistor to discharge the capacitors. Then loosen the screw on the resistor's tap ring until it is completely free and move in the desired direction. Retighten and check voltage, repeating this procedure until the voltages are correct.

> Usually, satin finished aluminum produces the best light for color. The reflecting surface should be smooth, and neutral in color.

Paint Phone Plug Prongs



Flexible Prod Finger Guards

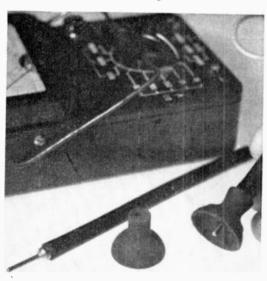


- When an ear-plug type transistor radio earphone operates intermittently, check the plug contacts that fit into the earphone. The tiny prongs may not be making contact inside the phone. A small amount of printed circuit silver paint daubed on them tightens and improves electrical contact. Solder tinning the prongs is almost impossible without melting the plastic plug insulator.—John A. Comstock.
- There's no radio-electronics technician who hasn't at one time or another let his fingers get too close to test-prod tips. You can forget the dangers of such shocking experiences by punching holes in small rubber suction cups and slipping them over your test-prod tips as shown. Because these guards are flexible. you will have no trouble putting the prods down in cramped wiring and touching test points.-John A. Comstock.

Build a Power Distribution Center

and put your entire ham shack to bed with one flip of a switch

By HOWARD S. PYLE, W70E

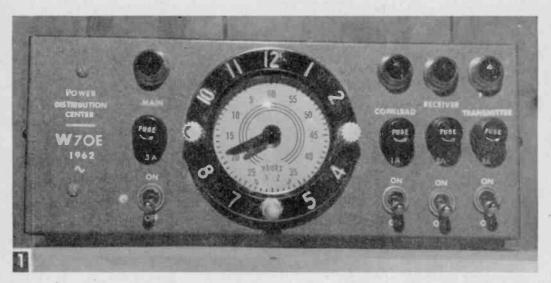

OW many times have you groped for this and that switch at the end of a long evening of ham activity, dragged your weary bones to your pallet and, the next day, found that you had turned off the transmitter the night before, but left your Conelrad unit and receiver merrily drawing juice to heat your shack? Too many times, we'll bet!


Why don't you spend a couple of hours to

fix yourself up with a power distribution center, which will assure you at bedtime that the mere flick of one switch puts you in the clear for an undisturbed night's sleep?

This is not a major project, but it does provide you with a convenience which you'll wonder how you did without. At the same time, it gives you a central unit into which you can plug all of your ham gear, knowing



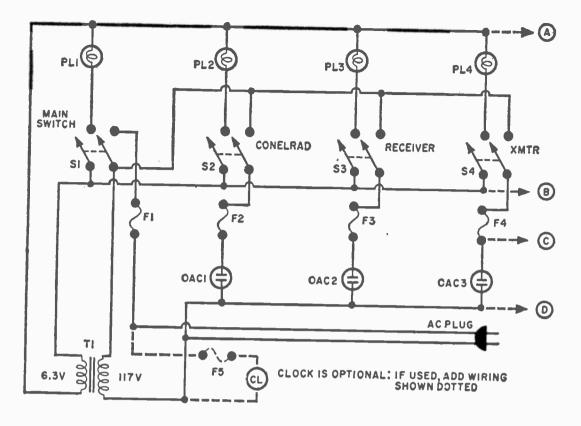Rear view of power distribution center. If additional outlets are desired, slight relocation of the clock fuse and ac cord entrance will provide space for them.



(A) (B) (C) AND (D) REPRESENT WIRING EXTENSIONS FOR ADDITIONAL CONTROL CIRCUITS

3 SCHEMATIC

that at the end of a session, the mere flip of a switch takes you "off the air" completely. It also eliminates the monkey-business of a number of straggling ac cords running to the most convenient outlet plus maybe a few 'cube-taps' to provide the additional ac combinations which you need.

You can accomplish all of this easily and simply by providing a central point to which your ac can run from every single piece of equipment in your shack. Just one main switch will kill every individual circuit in connection with your ham activities except, perhaps, your electric clock.

Simplicity of Construction. If you have been able to pass an examination for a ham license, you should be able to figure this project out by examining the schematic diagram. Actually, all that you have to keep in mind is that you want individual switching and fusing of each piece of equipment which you propose to use, plus the ability to switch them all off by means of one switch. If you use an electric clock, as the author did, you will naturally want to eliminate the clock from main switch control so that it will continue running all day. Aside from that, you

are faced with a most simple and conventional design problem followed by a bit of mechanical work and some elementary wiring.

The unit illustrated here represents that which the author felt was adequate for his requirements. They were simple, involving only control of the ac supply to a receiver, transmitter, and a Conelrad monitor.

Some readers may even question the necessity for switching the Conelrad unit, using the argument that such an item is a necessity only when the ham station is in a position to transmit signals on the air. This, then, would

MATERIALS LIST-POWER DISTRIBUTION CENTER

Desig. PL1, PL2, PL3, PL4 S1, S2, S3, S4 F1, F2, F3, F4, F5

T1 OAC1, OAC2, OAC3


ACP 6 ft. CL Misc. Description
pilot light holder (Allied 52E545)
bat handled toggle switch (Allied 34B647)
insert fuse holder, Buss HKP (Allied
53B475)
transformer, Triad E 1437 (Allied 660058)

transformer, Triad F-14X (Allied 64G954) 2-pole female outlet, Amphenol 61F (Allied 40H677)

ac cord and plug (Allied 49T230)

rubber feet, rubber grommet for ac cord, decals for lettering, LBM chassis box #144 or equivalent

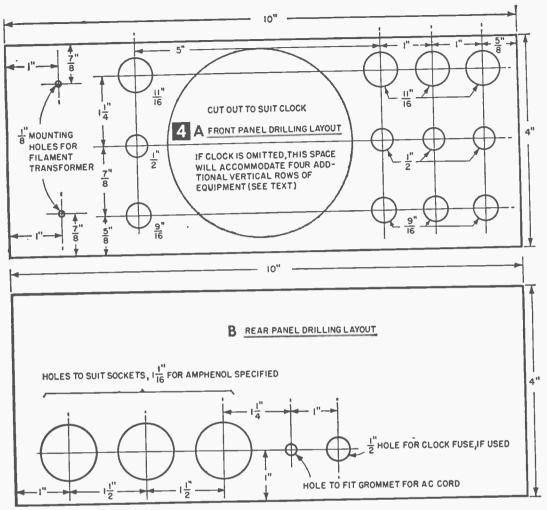The above materials can be purchased from Allied Radio Corp., 100 N. Western, Chicago 80, 111.



lead to the natural assumption that the Conelrad monitor could well be wired in parallel with the transmitter ac supply source, thereby eliminating one switch, the ac outlet, and the pilot light combination from the circuit.

To be sure, this is perfectly acceptable. But in the author's case it was desirable to have the Conelrad monitor merely as a broadcast receiver with which to listen to news and entertainment while working around the shack or on the adjacent work bench, without the transmitter, receiver, or other accessories being activated. The choice is yours. Determine what your own individual requirements are, and then design around them. For example, you may already have an adequate clock (remember, FCC insists that you keep an accurately timed log). If so, you need not consider such as part of your distribution center. Instead, use the space intended for a clock for extra switches, fuses, and pilot lights for additional equipment.

We are attempting to supply here, both

from the standpoint of mechanical drilling dimensions and schematic wiring, what the author chose for his own modest ham station. You may need several additional circuits, both 117-volt and 6.3-volt ac, with their related pilot lights, switches and fuses, if your station equipment embraces other apparatus such as an external modulator, a self-powered VFO, maybe a coaxial relay or two. That is where the design problem rests entirely with you. What you do with it in the way of expansion, and what have you, is "your baby."

We might mention, too, that you are by no means limited to the parts specified in the materials list. They happen to be those chosen by the author, and proved to be entirely adequate and satisfactory. Maybe your own "junk-box" or some other available source of supply can produce equivalent items which you can well use. If so, use them. The real measure of a good ham is the extent to which he can bring his imagination, ingenuity, and resourcefulness into play.



see what's new in

top buys in TAPE RECORDING

latest values in
CITIZENS BAND &
SHORTWAVE RADIOS

SAVE MOST ON:

000000

- Everything in Stereo Hi-Fi
- New All-Transistor Stereo
- KNIGHT® Super-Value Hi-Fi
- Tape Recorders & Tape
- Citizens Band 2-Way Radios
 Transistor & FM AM Padios
- Transistor & FM-AM Radios
- Phonographs & RecordsHam Station Equipment
- PA Systems, Intercoms
- Latest Test & Lab Instruments
- TV Tubes, Antennas, Accessories
- Parts, Tubes, Transistors, Books, Tools





See special products and values available only from Allied—plus all the famous makes!



exciting build-your-own

NO MONEY DOWN: Now! Get More
Buying Power with your
Allied Credit Fund Plan!

Satisfaction guaranteed or your money back

ALLIED RADIO

The World's Largest Electronic Supply House

SEND FOR YOUR COPY TODAY!

ALLIED RADIO, Dept. 71-33-A 100 N. Western Ave., Chicago 80, III.

☐ Send FREE 1963 ALLIED Catalog

Name_

Address _____

City_____State____

Add parts until you've built

Space Station

-Super Workbench for Your Shop

By JAMES JOSEPH

PACE engineers have come down to Earth to hand the home craftsman an out-ofthis-world workbench.

Dubbed Space Station by its designers, space-minded (and space-saving) engineers at

Hughes Aircraft Co., this compact, first-of-itskind workbench begins with a basic work table, adds more than 30 bolt-on bins, shelves, jigs, and fixtures that put hundreds of parts and scores of tools within finger's reach, and converts in a jiffy to such specialized homecrafts as electronics, model-making, gemmology, or wookworking.

Electronics. Fitted for the hobbyist or professional repairman, Space Station racks an array of miniature parts-bins and swivel cups (small, removable plastic "pigeon-holes") that hold upwards of 350 different parts. There's also a 110-volt outlet for your soldering iron, plus special reel fixtures that hold spooled wire or solder. Built into the bench are a compartmented "wire" box that holds various sizes of most-used wire and a viselike jig designed to support at convenient work level a single electronic circuit board or an entire chassis.

Model-Making. To quick-switch from electronics to modeling, simply substitute a slip-in formica work surface for the electronic holding-jig and clip a bottle rack to the basic bench's angle-iron superstructure. Result: Neatly stacked and ready to use are your liquid essentials—lacquer, solvents, plastic



Here's a version of the Space Station as assembled by an electronic hobbyist. Note wire box at left, swivel parts bins, spools for solder and wire.

cement, and dope.

Gemmology. Gem-craftsmen need light, and you get it from a quickly attached, nonglare, overhead fluorescent fixture that bathes the bench's work surface with 160 footcandles of illumination.


General Fix-It Bench. For the household handyman "specialized" to handle all home fix-it chores, Space Station's slide-out plastic drawers, tool holders, and revolving bins segregate upwards of 350 different repair parts-from electric motors to tiny washers yet hold them within quick reach.

A 10-Year Job. Hughes spent 10 years and some half a million dollars developing Space Station. It was designed for the kind of dayto-day bench versatility required of Hughes's own missile-component and electronic production. More than a thousand of the benches -some specialized for complex electronic assembly, some for mechanics, some for routine maintenance—are currently in use at Hughes' far-flung plants.


Says Harold W. Emmons, of Hughes's Ground System Group, Fullerton, Calif.,

which is marketing Space Station:

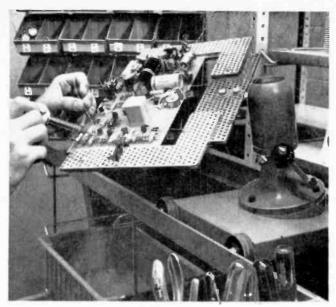"We designed the workbenches strictly for our own needs. But so many other industries



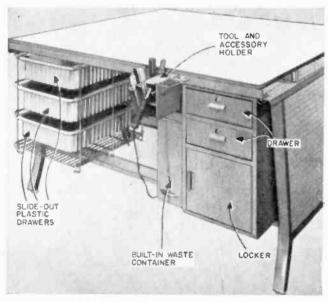Power arm mounted on a dolly conveyor lets you angle and position work for convenience. You cover track with a formica top when not in use. "Swiss cheese" fixture that holds circuit board here costs about \$19.



This is the bosic bench, costing about \$100.

wanted them that we decided to make them available—to individuals, as well as to industry."

Fitted with every available rack, bin, accessory, and add-on, a Space Station carries a \$350-\$400 price tag. It's doubtful, however, that any home craftsman would need every accessory. Actually, \$100 buys you the basic bench shown above (fitted with a 4x5-ft. formica top, three 22x7x5-in. slide-out plastic

drawers, built-in waste container, tool and accessory holder, and a two drawer-and-locker storage section). Once you've set up the basic unit—which comes ready to bolt-assemble—you can add accessories as you need them.

Rundown on Add-On's. Bench lights (a 5-ft. fluorescent fixture with two tubes) bolt on and cost \$32. You can add an ash tray and coffee-cup holder for just 90¢. For electronics, you'd want a revolving small-parts holder (swivelmounted metal frame with space for 40 clip-on plastic cups, 20 on each side of the revolving benchtop unit). The swivel frame runs \$5; plastic cups cost 25 or 50¢ each, depending on whether they're 4 or 8 in. wide. Invest another 8¢—for a divider to separate each cup into two parts—and you can double their utility. Special cup-fitting name clips (on which you can write a part's name or number) cost just 8¢ each.

"Everything on this bench," said one Hughes shopman, "has its special place. And everything fits—clips-on, bolts-on, or slips-in. Together, they make super-bench about the most versatile work sta-

tion ever."

Take "Power Arm," one of the optional fixtures. Substituting for the usual bench vise, it resembles the pan-head atop your camera tripod. "Power-arm swivels and turns whatever you're work-

ing on.

Fix an electronic chassis to power arm's "Swiss cheese" jig clamp, and you can tilt and turn it in any direction, through a full circle (360°) horizontally, or 180° vertically. The smallest of the four available power arms can hold and swivel projects weighing up to 15 lbs. and is priced at \$9.50. The strongest can swing 70 lbs. and costs \$30.

For the experimenter or modelmaker who wants to sit down, there are four special bench

chairs, 21-27 in. high. There's also a unique four-wheel "dolly" (\$9.90)—a kind of in-the-

bench conveyor (upper photo).

Hughes engineers call the Space Station "a new tool." Home craftsmen who've bought the basic unit and are building toward a shopman's dream call it an out-of-this-world workbench. And that description should do until something better comes along, which is improbable.



Centralized Home Intercom

Single amplifier permits all-master system

By W. F. GEPHART

THE requirements for home intercoms are somewhat different than those designed for businesses. If you have ever thought of installing an intercom system in your own home, you should have considered the following points.

 The majority of the stations should be masters. Due to movement in the house, calls may have to be originated from any

station.

 It should be instant-operating. Due to limited usage, it should require no warmup time, so it can normally be turned off, minimizing operating and maintenance costs.

3. Called stations should be able to talk without using a switch. Since house-holders don't sit at desks, they should be able to answer without going to the unit and operating a switch.

 Individual stations should not require ac power. This gives greater station location flexibility and simplifies wiring.

Cost should be reasonable. Home needs should not require excessive expense. System should be ac powered. This reduces operating costs and avoids having to remember battery replacement.

The unit described in this article meets all of the above requirements, and was designed specifically for home use. Since it is a "single channel" system, it is not entirely adaptable for businesses, and can handle only one call at a time. This unit has four masters and one substation, but the basic plan can handle anywhere from two to 23 stations in any combination of masters and substations.

The total cost of the unit shown, using surplus relays, was about \$80. To duplicate it as nearly as possible in commercial units would run from \$125 up, depending on the manufacturer and features desired. The savings in the centralized system can be realized in the cost of the amplifier and power supply parts—about \$40. If a separate amplifier were provided for each master station, (which would eliminate the need for relay switching), each master station would cost about \$50.

The centrally-located amplifier power sup-



Since stations do not require ac power, they can be mounted almost anywhere. This one was mounted above the phone.

ply control unit (Fig. 1B) can be placed in an attic, basement, or closet. The location should be selected for minimum length cable runs to each master station. The amplifier is turned off and on, and switched to various stations by relays, which are controlled at the master stations.

Operation. Since the system can be adapted to accommodate a number of stations, let's review the operation and switching system by referring to the schematic, Fig. 2. Notice that the power transformer (T1) primary is connected to the ac line at all times, so that positive dc voltage (24 volts) is connected to pin 8 of Ryl and pin 6 of Ry2 thru Ry6 at all times.

Now, assume that station 1 wants to call station 3. First, the amplifier is turned on by closing S2 on station 1. Cable lead 3 is ground (or minus 24 volts), and closing S2 grounds the arm of S3. Since we have set this to station 3, cable lead 8, which goes to pin 5 of Ry4, is grounded, and Ry4 closes. Positive voltage, on contact 1 of the relay, goes through contact 2 and R2, applying voltage to the amplifier.

One side of the speaker in station 1 (LS1) is grounded to cable lead 3, and the other side has two paths. One goes through cable lead 1 to contact 7 of Ry2, but since this relay is open, this path is useless. The other path goes through the lower half of S2 to cable lead 6, and to contacts 8, 13 and 4 of Ry2.

Since Ry2 is open, the path continues through contact 14 to contacts 2 and 4 of Ry1, and then to the output transformer, so station 1 is on LISTEN.

Now let's see how the sound gets from station 3 to station 1. The station 3 speaker (LS3) has one side grounded, and two paths for the other side. One path goes to S8, which is open, and the other goes to cable lead 1 at station 3, and then to contact 7 of Ry4, which is now closed. This connects to contacts 8, 13 and 4. Contact 8 goes back through the cable to S8, which is open. Contact 13 is floating, since the relay is closed, but contact 4 connects with contact 3 which goes to contacts 7 and 5 on Ry1, and from there to the amplifier input transformer. Therefore, any sound in the room where station 3 is located will get to the amplifier input through this path, and from the amplifier output to the speaker at station 1 as outlined above.


For station 1 to talk to station 3, the PRESS TO TALK switch (S1) is pressed. This places ground on pin 1 of Ry1, closing it, which reverses the speaker connections to the amplifier, so LS1 is then connected to the input, and LS3 to the output. Releasing the switch opens Ryl, restoring the original condition, so station 1 can listen. No switch manipulation is required at the called station, so the person being called does not have to be near the station. The system is sensitive enough that a normal speaking voice can be picked up anywhere in the average room.


A Pilot Light Circuit, consisting of R1, L2 and C3, is included, although it is not vital. It helps prevent leaving a station on inadvertently, which would immobilize the system for others. Since pilot light current flows in the cable with voice circuits, well-filtered dc must be used, and a separate filter system (L2 and C3) is used to avoid exceeding the current capacity of the main choke (L1). The pilot light in the master station making the call goes on when one side is grounded by closing the ON-OFF switch (S2, S5, S8, etc.).

Substations, such as station 5, work on a simpler -procedure. Setting the selector switch (S3, S6, S9, etc.) closes Ry6 when set on station 5 and master is turned on. The upper contacts of this relay supply amplifier voltage, and the lower contacts connect the substation speaker (LS5) directly to contact 7 of Ry1, and from there to the input or output of the amplifier, depending on the position of Ry1.

Stations within the house should usually be master stations, and those at outside doors should always be substations. In some cases, it may be desirable to put substations in nurseries or children's rooms, so that calls cannot be initiated or adult conversations in other rooms overheard.

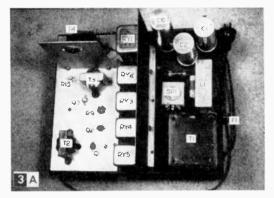Privacy Switches. Station 4 includes a PRIVACY switch (S13). Normally, as soon



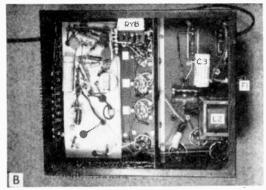

(A) Top view of surplus power transformer and plug in capacitors. Note the shield between the power supply and the amplifier and relays. (B) Bottom view showing shielding between power supply and amplifier and relays.

as you turn the unit on, you are in LISTEN condition to the station selected. To permit privacy in bedrooms, this switch (in the position shown) cuts the speaker in the station out of the circuit, and connects a buzzer (Z) into the circuit. One side of the buzzer is connected to the positive pilot light voltage through the top contacts of S13, and the other side is connected to one side of the coil of Ry5 through cable lead 4.

When this station is called, the Ry5 closes by having one side of its coil grounded. This ground also appears on one side of the buzzer, and it goes on. When the person in the room wants to answer, he throws S13 to the other position, which stops the buzzer and connects the speaker in the circuit. Operation is then normal. Upon completion of the conversation, S13 can be returned to the position shown, putting the buzzer back in the circuit for a future call, and cutting the speaker out.

The output transistor (Q4) will draw a high current without a speaker across the output transformer. If a PRIVACY switch is to be used often, or included in many units, it might be well to connect a load resistor (R18) as shown by dotted lines, to reduce this current.

With this understanding of the system, it can be seen that one multi-contact relay (Ry2 through Ry5) and one 10-contact terminal board (TB1 through TB4) are required for each master station, and one DPST relay (Ry6) and one 2-contact terminal board (TB5) are required for each substation. The limit of 23 stations is imposed by the maximum size selector switch (S3, S6, etc.) available.

DC Relays should be utilized, since ac actuating voltage in the cable would create excessive hum. Low power relays should be used to minimize the energizing current required, and should be sealed, since attics and basements are usually dusty. If sealed relays are not used, they should be placed under the chassis or homemade dust covers should be

made for them.

The master station relays must have two A contacts (single pole, normally open), and one C contact (single pole, double throw). The substation relay must have two A contacts, and the talk relay must have two C contacts.


The relays used in the unit shown are surplus 24-28-volt dc relays, with a 300-ohm coil, and draw about 80 ma. The master relays have three A and one B (single pole, normally closed) contacts, but one A and the B contact were wired together to make a C contact. The contact numbers are shown solely for explanatory purposes. Since this coil voltage is an aircraft standard, many suitable relays are available on the surplus market.

Installation Suggestions. No specific dimensions or layouts are shown, since the exact extent of the unit will depend on the number of stations to be used. Provide adequate ventilation for the power transformer (T1) and rectifier (SR1), since they have voltage on them at all times. When the system is on standby (all masters OFF), it draws about 6 watts.

Use two fuses in the power supply. One (F1) is for the ac line and will blow if the transformer or rectifier shorts out; and the other (F2) protects the transformer and rectifier if a capacitor or other component shorts out.

Place the amplifier section away from the power supply to minimize hum induction. Keep the AF transformers well apart, and mounted at right angles to each other, to minimize AF feedback. Mount the power transistor (Q4) on a heat sink made of a 3x4-in. piece of aluminum, insulated from the chassis.

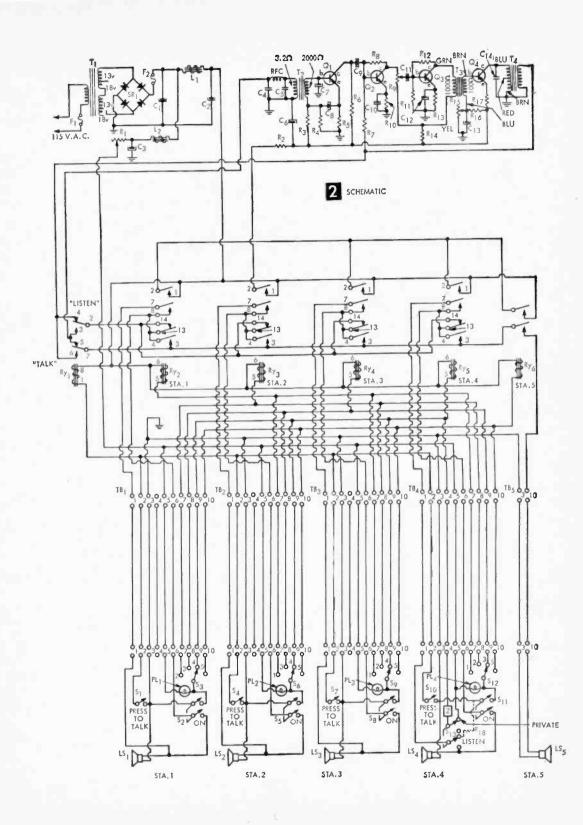The exact size of capacitor C7 will depend on the length and routing of the cables, as to hum pick-up. In the unit shown, the value of C7 is 10 mfd, which greatly reduces hum pick-up from the line yet doesn't seem to affect appreciably gain or tone.



	ILS LIST—HOME INTERCOM
223 W. Madison St., (
Desig.	Description
R1	500-ohm, 10-w adjustable resistor (Newark
R2	13F518) 100-ohm, 5-w resistor (Newark 13F150)
R3	.33-meg. resistor 15.000-ohm resistor
R5	3600-ohm resistor
R7	.1-meg. resistor .39-meg. resistor
R8	.68-meg. resistor 10.000-ohm potentiometer, Mallory U-20
	(Newark 9F104)
	3300-ohm resistor 4700-ohm resistor
R12	10,000-ohm resistor
R14	270-ohm resistor 330-ohm resistor
R15	1500-ohm 2-w w.w. pot., Clarostat 43-1500 (Newark 9F776)
R16	39-ohm resistor
R17 R18	1-ohm, 2-w resistor (Newark 13F060) 3.3-ohm, 2-w resistor (Newark 13F060)
C1, C2, C3, C13	3.3-ohm, 2-w resistor (Newark 13F060) 500-mf, 50-v capacitor Sprague TVA-1315 (Newark 18F975)
C4, C5	100-mmf, capacitor Cornell-Dublier 15F5T1 (Newark 15F1226)
C6	(Newark 1511226) 2000-mf. 15-v. capacitor Cornell-Dublier BR-20001 (Newark 15F166)
C7	BR-20001 (Newark 157-166) See text
CS. C9. C11	10-mf, 25-v. capacitor Sprague TVA-1204 (Newark 18F154)
C10, C12	50-mf, 25-v, capacitor Sprague TVA-1206
T1	18-13-0-13-18-v. 9A transistor power transformer, Stancor TP-1 (Newark 1F441)
T2	2K to VC output transformer, Stancor A-3332 (Newark 1F276)
Т3	100-ohm to 1K interstage transformer,
T4	100-ohm to 1K interstage transformer, Stancor TA-3 (Newark 1F429) 48-ohm to VC output transformer, Thordar- son TR-61 (Newark 2F524)
L1	son TR-61 (Newark 2F524) 2.8-hy, 300-ma. choke, Stancor C-2334 (Newark 1F177)
L2	13-hy, 65-ma. choke, Stancor C-1708 (New-
F1	ark 1F158)
F2	1/4-amp 3AG fuse (Newark 27F652) 3/4-amp 3AG fuse (Newark 27F655)
RFC	2.4-mh. choke, Miller 4666 (Newark 59F304)
Q1, Q2 Q3	2N169 (Newark 21F348) 2N214 (Newark 21F4506)
Q4	2N307 (Newark 21FX6159)
SR1	36 VAC, 1.5A rectifier, Int. Rect. J29B1 (Newark 21F810)
RY1	DPDT Contacts, 24 volt dc coil (See Text)
@Ry6	DPST contacts, 24v dc coil (See Text)
*S1, S4, S7, S10	(Newark 21F810) DPDT Contacts, 24 volt dc coil (See Text) 2A & 1C contacts, 24-v dc coil (See Text) DPST contacts, 24v dc coil (See Text) SPST push button switch, C-H 8411K4 (Newark 23F260) or SPST spring-return toggle. H&H 81045-FB (Newark 23F002) DPST toggle switch, H&H 20902-CX (Newark 23F012)
*\$2, \$5, \$8, \$11	toggle, H&H 81045-FB (Newark 23F002) DPST toggle switch, H&H 20902-CX (New-
*S3, S6, S9, S12	ark 23F012) 1-pole, 5-pos. rotary switch, Mallory 3215J
#\$13	(Newark 22F052) DPDT toggle switch, H&H 20905-FR (New-
	ark 23F015)
+PL1, PL2, P13, P14	#48 pilot light (Newark 25F107)

MATERIALS LIST-HOME INTERCOM

Fuse Holders, Surface Type (Newark 27F-754), chassis type (Newark 27F752) * one required for each master station @ one required for each substation # one required for each master station with PRIVACY switch In addition to the above, a chassis and cover, such as an amplifier foundation kit, will be required for the main unit, and suitable cabinets required for stations.

#Z High frequency buzzer (Newark 46FX002)
LS1, LS2, LS3, LS4 4" 3.2-ohm speaker (Newark 56F252)
*TB1, TB2, TB3, TB4 10-contact term. strip, Cinch 17-10 (New-

2-contact terminal strip, Cinch 17-2 (New-ark 29FX552) jeweled pilot light holders (Newark 25F-

ark 29FX560)

350)

Relays may be secured from Universal Relay Corp., 42 White St., N. Y. 13, N. Y. An unsealed relay for Ry2 through Ry5 (2A, 1C contact, 24-y coil) is their ARC type 55342, Cat. #R171 @ \$1.50 each. Many others are available.

Three adjustments are required when the unit is wired. After the amplifier is wired and checked, connect speakers to the input and output, and insert a milliammeter in the power lead (going to R2). Place the speakers in separate rooms so there can be no acoustic feedback between them. Connect one relay coil to the power supply so it will draw current, and connect the amplifier power lead. Adjust R15 so the amplifier draws about 170 ma, being sure that you are not also measuring the relay coil current. This will give an output of better than 1 watt, and will mean that about 250 ma flow through choke L1 on LISTEN and about 330 ma on TALK. The latter is in excess of the choke rating, but will not hurt for short periods.

A second adjustment is the pilot light supply resistor R1. Set the tap on R1 at full resistance; and, with the set-up outlined above, connect a #48 pilot light between the R1 tap and ground. Using a high resistance voltmeter, adjust this tap until there is about 1.8 volts across the pilot light. This lower-thanrated value is suggested to minimize burnouts due to the surge when the unit is turned

The last adjustment is the volume control R9. With the connections outlined above, gradually turn R9 so the arm approaches the Q2 collector lead. If the speakers are properly separated, you should be able to turn it all the way up without getting a feedback howl. If you can't, there is feedback within the amplifier. To correct this, first try increasing the size of R7, then try additional shielding. If the howl persists, and wiring is correct, the feedback is probably due to parts placement.

Later, when the unit is placed at its centralized location and all cables are connected, R9 can be adjusted for desired volume.

Stations can either be built into small radio cabinets available from suppliers or, homemade cabinets can be used. Since ac power is not required at the stations, they may be either wall-mounted, or placed on tables, whichever is more convenient.

Since only low voltage is carried in the cables, regular multiple-conductor intercom cable can be used, such as Belden 8443 through 8449, 8456, and 8457. This is available in 3 through 10-conductor, and in 12-con-

For master stations without the PRIVACY switch, you will need cable with 5 conductors plus 1 for each station to be called. The PRIVACY switch requires one more conductor, and all substations require 2-conductor cables.

Shielding is not required unless it is expected that you will have runs in excess of 75 ft. between a station and the control unit. In such cases, it might be necessary to have conductors 1 and 6 shielded.

Misc.

Puzzled By

Cryptic Citizens Band Messages? Here's what they mean



F YOU happen to eavesdrop on a citizens band radio some evening, you might hear cryptic messages that sound something like this:

"Advise 10-20."

"Cicero near Cermak."

"10-15 Raid at Polly's."

"10-4."

"10-16 three bombs."

"10-19 stake out, 10-12 heat's on."

"10-4."

What you're hearing isn't really a dramatic police episode, nor is it the audio portion of an old TV show. Deciphered by Jack Catterall, technical services manager for Raytheon Co.'s Distributor Products Division, the conversation reported above is translated as:

"Where are you now?"

"I'm on Cicero Avenue near Cermak."

"Will you please pick up a can of Raid at Polly's store?"

"OK."

"I went to the store as you requested and picked up three insecticide bombs."

"Hurry home, we're having a steak cookout. The guests are here and the fire is started."

"OK."

Businessmen, taxi drivers, wives with grocery lists, and people with car pool problems all seem to be talking like policemen, Catterall observes. With almost a half million citizens band users throughout the nation,

many have adopted the police radiotelephone abbreviations to shorten their conversations.

The "hamsters," as citizens band operators sometimes call themselves, have generally agreed on the following more commonly used signals.

- 10-1 Reception poor; can't understand you (pronounced ten one)
- 10-2 Reception good
- 10-3 Affirmative, will do
- 10-4 OK or yes
- 10-5 Need your assistance to relay a message, or I am relaying a message
- 10-6 Busy, can't talk now
- 10-7 Going off the air
- 10-8 Coming on the air, station is manned
- 10-9 Repeat your last message
- 10-10 Finished transmitting
- 10-12 Officials or visitors are present
- 10-13 Give me road and weather information
- 10-15 Make a pick up of.....at......
- 10-16 | have picked up.....
- 10-18 Do you have a message for ma
- 10-19 Return to station
- 10-20 Position report
- 10-21 Call me by telephone
- 10-23 Arrived at scene
- 10-24 Finished with last assignment
- 10-33 I have an emergency message
- 10-37 What is your call sign and name
- 10-70 Fire



Electronic Piano

Steel reeds and transistors replace strings.

Piano never needs tuning

By BILL McHUGH

SIT down at the keyboard, play a few chords and you are pleasantly surprised. Usually a small piano implies a sacrifice in tone quality, but this one sounds very close to what you hear from a good spinet.

Let's try the action. It's not an expensive

FIG. 1: This is the portable model Wurlitzer electronic piano. Amplifier and speakers are built-in. Foot pedal controls the sustain while keyboard knobs control volume and vibrato rheostats. Heart of electronic piano (left) is Swedish steel Sandvik reed . . . this one for a middle tone is about 2½ inches long. It bolts to the reed bar, hole at right for that purpose. Tip weight is ground or filed in reed pitch adjustment at factory.

piano, so we can hardly hope for concert hall touch—but we're amazed! This piano is agile! Your fingers fly over keys that feel even and nimble. It certainly is not a sluggish keyboard.

Opening the top lid (Fig. 3) we find something unlike anything we've ever seen in a piano. Maybe this is the "piano of the future." It is one of the few breakthroughs in piano design in a long time.

The piano has no strings! Sound comes from steel reeds and they

never need tuning.

So what? Well, ask any concert pianist, or recording artist, and he'll tell you that when you want to play fine music, you have to tune a grand piano before every performance. Traditional pianos have one or more metal strings for every note. The strings are arranged like a harp, on a heavy massive iron casting with a tension that can run into tons of pull. Tune the piano, and it is only a matter of time until the tension on the strings, plus changes in temperature, pressure and humidity cause it to slip out of tune.

If you live where the temperature is even year around, tuning every 6 months may be enough. But a piano on the stage of a night club, a theatre, a music school, in the tropics, the arctic . . . any place where the instrument gets lots of use, is an engineering problem now solved by the new Wurlitzer reed principle.

A fringe benefit of interest to any entertainer is a spectacular reduction in weight. The average small home-size piano weighs 400 to 600 pounds. Only experienced

movers can lug such a weight from place to place. The new electronic piano is not exactly a lightweight at 80 pounds, but a man and a boy can put it in a station wagon and move it. There is nothing fragile about the portable model . . . it is a tough piece of machinery,

and we saw proof of the fact that it can take a lot of moving.

The real news is for parents, landlords, and neighbors. Since the piano is electronic, and its sound emits from a loudspeaker, all you have to do for quiet operation is plug in the earphone jack. Then junior can practice all night if he wants, while the rest of the world sleeps. Probably every composer, musician, and pianist has tried one time or another to muffle, baffle, soft pedal, or otherwise kill the sound of a practice piano. But nothing seems to work, because if you dampen

the strings of the conventional piano, you also change the response (bounce-back) of the hammers and the keyboard feel can be so different that practice is a waste of time.

Another factor in practice is a psychological one. What music student likes to broadcast practice boners to the whole neighborhood? The ribbing that every young pianist takes from family and friends is enough to cause many potentially fine musicians to stop taking lessons and start watching TV as a life-long hobby. To develop skills as a pianist takes hundreds of hours of concentrated study and practice. The electronic circuits and earphone attachments now make this possible in crowded apartments, in college practice rooms, and in the ordinary home. Professional musicians report that they can rehearse new numbers anywhere—in hotels, and even on stage with curtain up. Flip the switch and the sound is completely private.

The heart of the new invention is a Sandvik Swedish steel reed (Fig. 1). When the pianist strikes the key, the felt hammer hits the reed causing it to vibrate as in Fig. 4. The touch closely resembles that of a conventional grand piano because the "action", (hammer mechanism) is mechanically and functionally similar.

The reed vibrates at a pre-set pitch. One reed can produce only one pitch, for example middle C is a standard 261.626 cycles per second. The tip of the reed is weighted with

FIG. 4: Photo shot at 1/10th secand shows the arc of the hammer striking steel reed and bouncing away. Engineers used high speed cameras to perfect this new piano action which duplicates grand piano response.

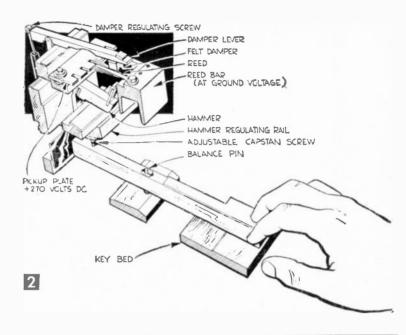




FIG. 3: Looking inside top of electronic piano you can see how the damper lever (lifted away) controls sound. Like a standard piano, as long as you press key, damper remains up. When key is released felt damper drops down to stop vibratian af reed below.

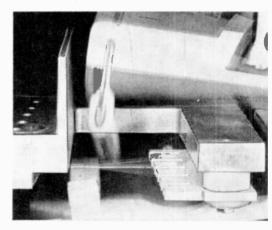






FIG. 5: Console home style electronic piano costs less than \$500, yet has complete 64-note standard keyboard and pedals. At keyboard side are volume and vibrato control knobs. Electronic amplifier (inset) operates on 9 transistors, delivers over 10 watts audio.

a lead mass. By filing or grinding away tiny amounts of this weight, factory technicians working with precise frequency measuring equipment establish the pitch. Once set, it stays right on the note. Should the reed ever break, a rare happening, you will be able to buy a replacement for less than 50 cents.

Electronic Function. All the reeds, one for each key of the piano, are bolted securely at one end to the cast aluminum reed bar (Fig. 3). When they are at rest, the reeds are centered slightly below the slotted cavities of the pickup plate. This pickup plate is charged at a plus 270 volts dc while the reeds are at zero or at ground voltage.

The piano in effect is a big capacitor. It is similar to the variable capacitors (condensers) used to tune a radio. When the piano is not playing, the reeds are in a neutral position and capacity is very low. The hammer strikes a reed and as it starts to vibrate, the tip swings upward. Capacity increases until the reed travels through the slot and slightly beyond. At that point the capacity starts to decrease until the reed reaches the end of its upward swing. Now as it starts to travel downward back through the pickup plate capacity again increases. This action repeats itself for every cycle . . . from 50 to





FIG. 6: Eighty-pound portable piano (left) can be used outdoors, on boats, in army camps without ac power. Entertainer Marian McPartland (above) uses Wurlitzer electronic transistor piano at Savoy Hilton, New York. Battery power pack will be available in early 1963.



FIG. 7: Electronic piano installation at Ball State Teachers College, Muncie, Indiana, equals 13 separate practice rooms. Students hear private com-



ments and only their own piano on phones. Instructor can demonstrate on main unit, connecting individually to any student, or to entire class by means of control.

2093 times per second depending on which note of the piano you are playing.


The varying voltage feeds through a load resistor, is then amplified through a transistor amplifier (a less expensive tube amplifier is also available) and fed to the loudspeaker. Pianos are equipped with the standard sustain pedals, and volume controls. In the portable model, the volume control is on the keyboard; in the home model, a pedal controls volume. But there is also a second rheostat control which controls the vibrato section of the amplifier. By adjusting this

control, you can obtain effects from Hawaiian guitar to vibraphone.

The amplifier puts out enough sock to fill a small auditorium. Wide open, the electronic piano will deliver considerably more sound volume than a standard spinet. External speaker jacks, and a jack for input permit a wide variety of electronic hookups. For example, a musician can rig his electronic piano so pre-recorded music plays through the piano speaker system along with what he plays. A musician could easily play duets with himself!



FIG. 8: Electronic piano design (right) shows reduction in weight and cost. Wood framing which supports heavy cast iron plate and soundboard of con-

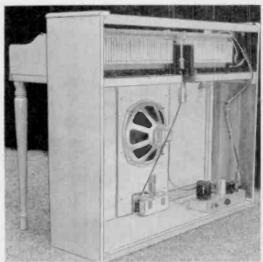


ventional piano (left) is eliminated. New piano is 1/6th the weight. Electronic amplifier delivers more sound than standard piano, produce special effects.

College Radio Stations

Over 250 of these stations broadcast unlicensed in the AM band

By DON A. TORGERSEN

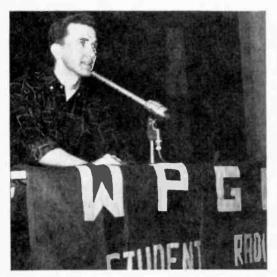



WPGU at the University of Illinois dedicates its broadcasting to the "best in music, news, and sports."

LTHOUGH seldom publicized as a broadcasting medium, the college radio station has become an important function in more than 250 college and university communities. These stations not only provide a reliable source of news and entertainment to the community, but also supply the broadcasting industry with a number of highly trained personnel, most of whom are acquiring degrees in radio and television, journalism, advertising, and engineering.

College radio stations broadcast on the AM band, and can usually be heard on any AM radio in the vicinity—even car radios and portables. By means of a special engineering principle called "carrier current," the college station is able to deliver a powerful, high quality signal to the community without being heard much beyond the boundaries of the campus itself.

Carrier current is a technique whereby transmitters, instead of being coupled to antennas, are coupled directly to the power lines of dormitories and resident halls. This same engineering technique completely solves the noisy reception problems which reduce the listenability of other stations in many of the new, steel-and-concrete, fluorescentlighted dormitories now being constructed. Very often, the college station may supply the only strong signal going into these build-



(A) Usually, an engineer and an announcer work as a team to produce a show.

ings. One student engineer described carrier current in this way: "You might say that what a person hears on his radio is controlled

interference' in the power lines."

Unlicensed Broadcasting. What is peculiar about these stations is that they operate unlicensed. This is due to a provision in part 15 of the Rules and Regulations of the Federal Communications Commission, which states that a transmitting device may operate in the broadcast band with a signal strength of 15 microvolts per meter, at a distance of one wavelength divided by two pi (157,000 feet/frequency in kilocycles) from any radiating source. Any such transmitter may operate unlicensed so long as it does not interfere with regularly licensed stations. Citizens band communication is another type of transmission governed by this provision.

Two such stations are WPGU (University of Illinois, 610 kc, Champaign-Urbana) and WRCT (Radio Carnegie Tech, 900 kc, Pittsburgh). These stations are staffed, managed, and operated entirely by undergraduate students as an extracurricular activity independent of formal school administration. WRCT has a staff of over 125 students, while over 200 students run the

affairs of WPGU.

Most of the equipment has been designed and constructed by the students themselves.

Photos by Ed Wahl



(B) But some announcers do their own engineering.

By keeping abreast of the latest developments in the electronics industry, the students have been able to design high fidelity units with a frequency response higher than that allowed for other AM stations in the same



An announcer gathers the latest news from a UPI teletype network.

area, since the commercially licensed stations are required to suppress their high frequencies. WRCT uses seven transmitters conveniently located that broadcast flat within 2 db up to 15,000 cps, and range in power from 10 to 75 watts output with a total output of about 150 watts.

Other facilities at WRCT include four studios, two of which are audio participation studios; remote equipment for live or recorded programs; and audio equipment to handle stereo recordings at 33 and 45 rpm, monophonic recordings and electrical transcriptions (lateral to 16 in.) at 33, 45, and 78 rpm. Their tape recording equipment consists of half track at 7½ and 15 ips, full or half track tape playback at 7½ and 15 ips, and cartridge tape machines. To round out their studios, they employ United Press International radio news service, NBC radio network, citizens band transceivers, and beep telephones.

WIIT (Illinois Institute of Technology, 610 AM, 91.9 FM, Chicago) has experimented with dual broadcasting of AM and FM channels, and has even tried multiplex. An engineer describing the power of their two transmitters boasted, "We load 'em up with

20,000 milliwatts."

Programming at these stations often covers as much as 133 hours per week. It includes classical, popular, folk, and show music, news, press conferences, drama, and play by play broadcasts of football and basketball games.

In times of emergency, the college radio station will often serve as an auxiliary to national networks. In May of 1962, when a tornado struck Rantoul, Ill., after a severe wind and rainstorm, the news staff of WPGU sent dispatches, both taped and telephoned, for use by UPI and ABC.

Financing these stations, since they are not for profit, is not much of a problem. Some of them are supported in part by grants from the student body, and in part, since they are not classified as educational stations, by the sale of commercial time to local merchants as well as many national advertisers. WPGU, which is financially self-sufficient, solicits a certain amount of its advertising through a New York agency, and actually realizes a small profit at the end of the year. This profit is turned back into the Illini Publishing Co. for use in other campus information activities.

Training. Although these stations are not required to have licensed technicians on their staffs, WRCT has imposed its own requirements, and 12 staff members hold first class radio telephone licenses. WRCT conducts regular classes in order to prepare their technicians and announcers for FCC examinations.

At WPGU, before a prospective announcer

is even placed on probationary status, he is given an audition to see if his voice is suitable for radio work, and to make sure that he will not tense up or freeze in front of a mike. To become a staff announcer, he must pass a written test and a simulated-broadcast examination under stress. One of the favorite techniques of the practical test is to tell the announcer that something has gone wrong



Making a spot check on the taping of a news broadcast.



The record library at WPGU contains almost 20,000 records.

with the record deck after he has introduced a record, and force him to ad lib for several minutes.

In testing engineers, it is better to face them with actual engineering predicaments. Tape decks can be bumped to the wrong speed, or transmitters in certain buildings can be mysteriously shut off. The hardest test for an engineer is known as the "flip-segue." This antic requires him to turn a record over after a number has been played, and im-



Station personnel design and maintain most of the equipment. These technicians are checking out a malfunctioning transmitter with an ascilloscope.



After 19 hours of continuous daily broadcasting, a weary engineer puts the station to bed at the master control panel.


mediately play a number in the middle of the opposite side. Whereas the standard time for this maneuver is 15 seconds, one ambitious engineer at WPGU has got it down to a split lightning four seconds.

Not all staff members are males. At least one-fourth of the staff at WPGU is composed of coeds. Besides being valuable as copywriters and production managers, several coeds have joined the engineering staff so that they can engineer the shows that their boy-friends announce.

WPGU actually owns the largest record library in the state of Illinois south of the Chicago area. There are almost 20,000 records locked up in the record library. With several bands to each record, this adds up to over 125,000 selections.

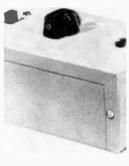To give the station a touch of personality, famous stars such as Tennessee Ernie Ford, Pat Boone, the Four Lads, Shelley Berman, and Connie Francis send short taped spot promotions to the station. In summing things up, Pat Boone said, "This is Pat Boone. I don't know a whole lot about WPGU, but they do have good taste in music. They play my records."





\$4 Transistor Tester Uses

By ROBERT E. KELLAND

THIS neat looking transistor tester costs \$4 or less, going by current catalog prices, and you can probably build it for half

that much by using scrap parts.

The unit checks transistors either on the bench or in the circuit, and results are adequate for most service and experimental needs. The advanced electronics expert needs a complete range of tests to pin down the detailed performances of any semiconductor, and so might find this tester wanting. But it is surprising to see what can be done by using this simple tester along with manufacturer's transistor spec books.

The tester will work with any VOM or VTVM that has $R \times 1$ and $R \times 100$ ohmage scales. The ohmmeter provides the indicating meter, and also eliminates the need for a separate power supply for the tester.

Build the Tester in a 5¼ x 3 x 2½-in. gray hammertone aluminum utility box. Photos show a transistor socket mounted on the top panel for testing out-of-circuit transistors. If you want to add a power transistor socket, there is plenty of room, but you will have to rearrange the available space. The pin jacks on the end of the box are for testing

transistors in circuits, and you will need three color coded alligator clip test leads. For transistor work, the small size clips are the best.


Follow the chassis layout (Fig. 3), as you cut the holes for the sockets, switches, and jacks. Ready-painted chassis should be protected with cloth when clamped in your vise. Exact measurements are not given for the tube sockets since various brands will differ in size. Less expensive wafer sockets salvaged from old radio sets will also fit.

The chassis has two pin jacks for the prods of the ohmmeter. If your meter has banana or alligator clips as prods, substitute the proper jacks to fit. Two 5-way binding posts

would also serve this purpose.

Use #22 solid insulated wire to hookup the connections on the chassis, and then connect the tube sockets with flexible stranded insulated wire.

How It Works. A transistor consists basically of two diodes; the collector-base diode and the emitter-base diode. By measuring the forward and back resistance of these two diodes and comparing the results you get an indication of transistor condition. Checking resistance between the emitter and the collector will indicate leakage or "break down" of the transistor base. When checking the diodes, a high ratio between the forward and back resistance will indicate a good

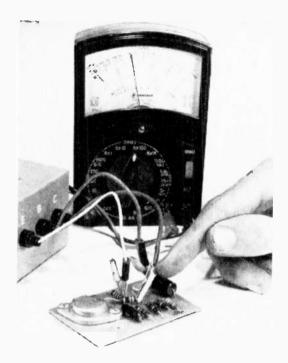

Your VOM

diode. Many technicians and experimenters rely on their ohmmeter to make these measurements, but connecting the ohmmeter leads to the transistor and reversing them at least half a dozen times is time consuming and often leads to incorrect results. The simple switching circuit used in this tester makes these measurements easy.

Using the Tester. Zero adjust your ohmmeter on the R x 100 scale and plug the prods in the tester. Polarity of the prods is not important since the DPDT slide switch reverses meter polarity. Now you can set the rotary

MATERIALS LIST-TRANSISTOR TESTER No. or Size and Description Amt. Reg. 1000 ohm ½ watt carbon resistor (#1MM000)* DPDT slide switch (#36B148) DP 3 Pos. non-shorting rotary switch (#35B235, knob R1 \$1 \$2 supplied) J1, 2, insulated tip jacks (#41H115) 3, 4, 5 alligator clips (#45H171) tip plugs (#41H200) transistor socket, 3 pin (#40H294) 1 1 8 pin octal tube socket, retainer ring mount (#40H058) 9 pin miniature tube socket (#22H594)
7 pin miniature tube socket (#22H567)
chassis, aluminum minibox 5'4x3x2!/8" gray hammerī tone finish (#80P348) Misc. #22 solid insulated hookup wire. Stranded insulated wire. Screws, nuts, solder

* All numbers from Allied Radio, 1963 Cat. 220. Address 100 N. Western Ave., Chicago 80, III.

Fig. 1-1A: S & M consultant Mort Friedman (far left) checks tester plugged into inexpensive Monarch VOM. Monufacturers transistor manual provides reference. Tronsistors can be inspected in seconds and graded for relative performance. Use short probe leads (left) with miniature alligator clips for checking transistors in wired circuit. This setup has been used for production inspection and proves fast and practical. An otherwise time-consuming test is accomplished without using expensive laboratory gear. Delicate low power transistors are protected from burnout by 1K resistor in tester.



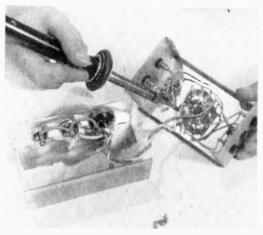


Fig. 2: Tube filament checking sockets are optional. Wire your chassis connections with solid hookup wire, and use flexible wire for the tube socket connections.

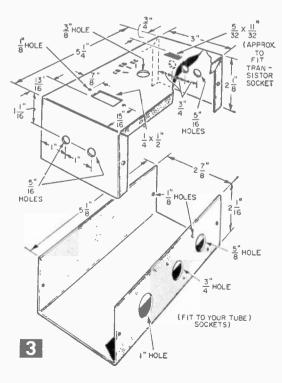

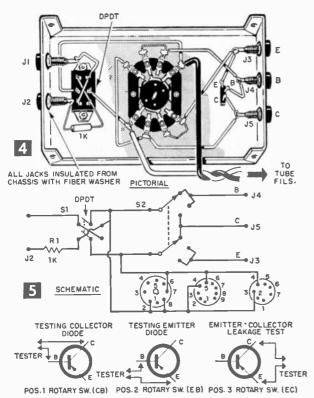

EMITTER-COLLECTOR LEAKA	GE*	
-------------------------	-----	--

Transistor	Meter	Scale	Minin	num Read	ings
RF-IF-Conv.		R x 100		6000 0	hms
Low Power Audio		R x 100		1500 0	hms
High Power		R x 1		1050 0	hms
Transistors Removed	from Circ	uit-Tested	Room Ten	np.	

NOTE: Readings Are 1000 Ohms Higher than Actual Transistor Resistance Because of R1

* Cut out and cement to meter case. (Courtesy of Delco, Div. G. M.)

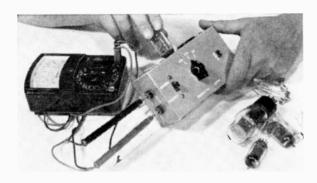


Fig. 6: Tube checking circuits on side of box are handy extra feature for radio and TV servicemen working on sets in homes. Binding posts for other kinds of tests can be added to this handsome case.

switch to position CB (Collector Base) and insert a transistor in the socket. Your ohmmeter should indicate either a very high resistance between 200K and 1 megohm or a very low resistance, 1500 ohms or less. All readings are 1,000 ohms higher than the actual transistor resistance because of current limiting resistor R1. Changing the polarity with switch S1 should immediately give you a different resistance, lower or higher. A high ratio in the two readings indicates a good collector diode.

The second position of the rotary switch EB (Emitter Base) measures resistance of the emitter to base diode. The pair of readings should be similar to the collector base diode.


Position EC of the rotary switch tests the emitter-collector leakage. Readings lower than those indicated in Table A indicate breakdown or shorting of the base. This seldom happens with low power transistors running on normal voltages. Changing the polarity reverse switch should give you a different reading, but both readings should be higher than those listed. For permanent reference, cut out Table A and cement it to the underside of the Tester Case for quick reference.

Both PNP and NPN transistors are tested in the same way. In the circuit testing will produce different sets of readings on the meter, but your low resistance readings should be about the same or slightly lower. High end readings will decrease to 2K to 100K depending on the shunt resistance present in the circuit being tested. A ratio of 5 to 1 indicates a good transistor. For example, a reading of 1200 and 2000 ohms is actually a 5 to 1 ratio, because you must subtract the 1,000 ohm value of R1 from each. If a transistor shows bad in the circuit, remove and confirm your test out of the circuit. The leakage test cannot be taken with the transistor in circuit.

A Caution. Some ohmmeters can deliver enough current to ruin transistors, and for this reason R1 is included in the circuit as a current limiting device. Except for power transistors on which you can use any ohmmeter scale, always use the R x 100 meter scale. High impedance ohmmeters are best suited as the current supply is generally much lower, and the accuracy of the meter itself is better. Resistor R1 also limits current when testing low-volt tube filaments. This test is simple continuity, and a reading indicates a good filament. Check a tube manual for proper filament connections.

54

Read AC Current with Your Voltmeter

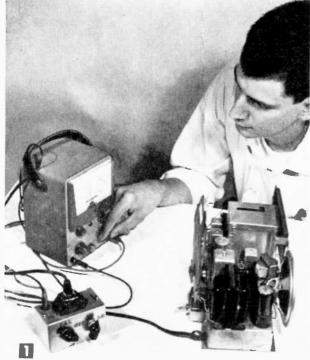

Author Lucos demonstrates haw "Mini-Amp" and sensitive VTVM can be used to abserve small changes in power consumed by radia. Unsteady reading indicates defective parts.

N OLD transformer that may be kicking around your scrap box is all you need to read ac amperage. The ordinary VOM (volt-ohmmeter) or VTVM (vacuum tube voltmeter) usually has a dozen or so scales ranging in ohms, volts, and dc amps, but it won't read ac current! This is a measurement most meters can't handle, and yet it is very important in many radio or appliance service jobs and on the electronic design bench.

The "Mini-Amp" pickup coil, made of a transformer (Fig. 8) is similar in principle to the clamp-on ammeters commonly used by electricians. The measuring head couples to the line by induction, so you can read the ac amperage consumed by a motor or appliance without having to cut into the power wire! Any ordinary ammeter has to be wired right into the circuit in series with the appliance every time you want to take a reading.

There are two ways to build the probe head. The split core magnet can be used directly to read large currents from 1 to 25 Pickup coil converts VOM to AC current reading instrument

By ALFRED R. LUCAS


amps ac. The voltage induced in the transformer winding is proportional to the current, so you simply connect the transformer to your ac voltmeter, and read on a calibrated scale (Fig. 2). A more sensitive ac current meter can be built (Fig. 1) for less than \$5.00. Calibrated properly, it will perform as well as instruments costing \$100 or more. Depending on the quality of your VOM, sensitivity can extend down as far as the microamp range and up to heavy appliance currents as high as 25 amperes and more.

Altering the Transformer is your first step. No specific transformer is listed since you can use any audio output transformer that has E-type core construction similar to the one shown in Fig. 8. Such transformers are common in radios and amplifiers. Dismantle by bending back the transformer cover tabs as in Fig. 8. Next remove the two retainers with long nose pliers. Remove the coil and place it over one of the side legs of the transformer core (Fig. 8).

Replace the frame by bending one of the mounting tabs straight and pushing it over the core and through the transformer coil. Finally, remove the primary leads of the transformer (usually heavier solid wires). The transformer modification is now complete.

If you are building the simplified model (Fig. 2) solder two test cord leads to the secondary windings and solder the plugs, PLI and PL2, to the other ends. This finishes the construction of version one.

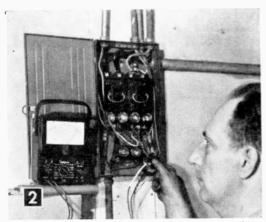The more sensitive version of the pickup coil uses the same transformer and a printed circuit amplifier. Mount the transformer so




S&M consultant, Erving Edell checked out this method of reading power consumed in home circuits. It was easy to trace circuits, in any part of the building. The VOM is far more sensitive than the usual electrician's instrument and even a 25 watt test lamp added to an existing amperage on the dial was clearly seen on the meter's calibrated scale.

that the core piece fits snugly against the side of the case. If necessary shim the fit with thin strips of wood. Mount all other parts (Fig. 9) except the amplifier chassis. Wire in the wall receptacle, splitting the two-conductor line core, and running only one of the wires through the gap in the transformer core. Then wire the circuit-board amplifier according to Fig. 3.


Insulate circuit board with electrical tape and wire it into the circuit under the switch as in Fig. 9. Complete construction by using the grounded side of R3 as a common terminal.


Calibration. Before using either unit, a conversion table or tape-on scale must be made for the VOM or VTVM. There are two ways to make this calibration. Several known currents must be sent through Mini-Amp

and the output voltages recorded. These currents can be obtained by placing known resistors in series with the line. Knowing the line voltage, the current is given by Ohm's Law as the voltage divided by the resistance. In using this method be sure to use a resistor with a high power rating. If you have a variable transformer, the entire process can be done with one resistor. Simply change the voltage by step-wise amounts and calculate the current at each point. Different size light bulbs can also be used with slightly less accuracy. The current through them is found by dividing their power rating by the line voltage. Current ratings appear in catalogs available from the lamp manufacturers.

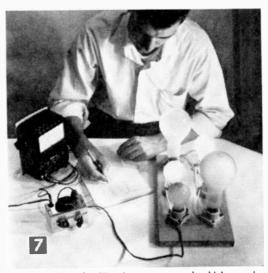

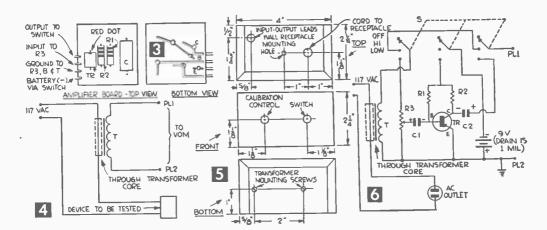This method of calibrating ammeters should be used only if you have no power resistor and variable transformer. Lamp wattages in various combinations will give you an accurate enough reading to plot a scale. Accuracy will be within 5 percent, provided that you keep your incoming line voltage steady.




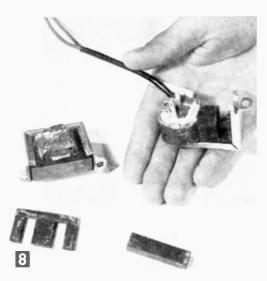

The completed pickup fits in the palm of the hand. To read amperes, you pass the conducting wire through the open side of the transformer. Top left is transformer (common in radios) before alteration.

Calibrate the high scale first. Put the selector switch in the "HI" position and set the VTVM or VOM to the lowest ac voltage range. Send increasing known currents through Mini-Amp and record the position on the voltmeter scale for each one. If a higher current scale is desired, turn the VTVM or VOM to the next higher ac voltage range and calibrate it in a similar manner.

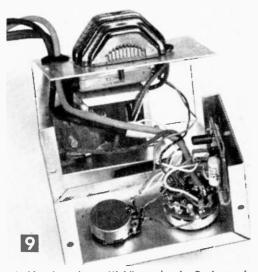To calibrate the low range, select a value



Inside view shows Mini-Amp chassis. Device to be tested plugs directly into receptacle on top. Power line (arrow) feeds through opening in transformer. Transformer secondary winding output is amplified and feeds to test leads. R3 is common terminal.

	MATERIALS LIST-MINI-AMP
Amt. Reg	. Size and Description
	Simplified model for higher currents
1	modified audio output transformer of your choice (see text)
1 or 2	plug(s) to fit voltmeter
	Amplifier model for any current range
1	5 mfd. 15 volt miniature capacitor, Cornell Dubilier 405
	(Allied #18L159) C2
1	9 volt battery (Burgess 2U6 or equiv.)
1	5 mfd. 6 volt miniature capacitor, Mallory TT6X5 (Allied
	#18L769) C1
1	680 K 1/2 watt resistor
1 1 1	10K 1/2 watt resistor
1	10K carbon potentiometer linear taper, !RC Q11-116
	(Allied #30M306)
1	4 pole, 3 position, non-shorting rotary switch, Mallory
_	3243J (Allied #34B357)
1	CK722 transistor
1	aluminum case, Bud Mimibox CU-3003A (Allied #80P363)
1	modified audio output transformer of your choice (see text)
1	battery connector, Cinch-Jones Type 50 (Allied #54J037)

plug(s) to fit voltmeter

of full scale current from 50 milliamps to 10 amps. With the VTVM or VOM set on the lowest scale, Mini-Amp in the "LO" position, and the selected current flowing through Mini-Amp, adjust the calibration control until the voltmeter reads full scale. Mark this setting of the calibration control with a piece of tape. Calibrate the remainder of the scale in exactly the same manner as the high scale.

wall power receptacle (baseboard mounting type)

The simplified Mini-Amp is also calibrated in the same manner as the high scale of version one, only in this case one lead of the load must be placed in the opening of the core, and the core piece placed over it to close the gap. A more permanent arrangement can be made if an extension cord is split, and one of the wires is run through the core with the core piece fastened permanently in place. Then the device to be tested can be simply plugged into the extension cord. You can calibrate as many different scales as you need by simply employing a different setting of the calibration control for each one

Suction Fastener for Soldering Pencil



• A rubber suction cup attached to your soldering pencil's handle by means of a cable clamp comes in mighty handy at times. For example the pencil can be suction-fastened to any smooth tool or toolbox or other object for difficult jobs requiring more than two hands. Or it could be fastened to the side of a chassis when standing idle while building or servicing.—John A. Comstock.

DX America

Maybe you've monitored five continents, logged 100 countries, verified stations on the other side of the world, but what about our own United States?

By C. M. STANBURY II

NE of the best things about DXing America is that you can start right in, using any ordinary AM radio you may have around the house. At night, find a place where you will disturb other members of the household the least, plug in, and get set to listen.

Tune away from local stations, push the volume up, and look for a weak signal: you will soon have your first "logging." With just a simple receiver, especially after midnight, you will be able to log 50-kw clear channel stations (see White's Radio Loc, page 159) up to 1000 miles away. The better your receiver, of course, the more you will hear.

One improvement you should make, if you can, is the addition of an outdoor antenna, as long and as high as possible. Most receivers are provided with means for attaching such an addition: if yours is not, simply connect the antenna to the terminal of the built-in loop with a .05-mfd. capacitor. If the terminal is difficult to locate, any competent repairman can help you. Make sure the bare antenna wire is not grounded against a metal window frame or tree limbs.

If you live in an apartment and cannot erect an outdoor antenna, the copper pipes of a heating system make an excellent substitute. Even a piece of copper screening in a

window helps.

When and What. At sunset, and again around sunrise, numerous daytime stations can be heard as they sign off and on again. This type of listening is not easy, as two or three stations are often heard simultaneously, but careful monitoring can produce a bagful of calls logged. It just takes practice.

During the evening, distant U. S. reception is usually limited to clear channel broadcasters and a few regional outlets. (A regional station is one that operates with 1 or 5 kw at night.) The clear channel powerhouses are excellent targets for the beginner, as almost all verify, and they are good sources of news.

From midnight until 5 a.m., DX is possible on almost any channel, even the "graveyard" spots—1230, 1240, 1340, 1400, 1450, and 1490 kc—where a number of low-powered stations transmit. DX will not be possible, of course, on frequencies where local and semi-local stations operate all night. In recent years allnight stations have become the broadcast band DXer's primary problem; coast-to-coast

reception is still possible, however, and includes daytime stations that are permitted to

test during the night.

Targets. Broadcast band DXers have many different goals. Some try to verify all 50 states (or often just the 48, due to the great distances involved in shooting for Alaska and Hawaii); Eastern listeners wanting to log the Pacific coast, by the way, should start with KFI, Los Angeles, on 640 kc.

Other DXers' are more interested in logging and obtaining QSL's from 500-, 1000-, or 1500-watt stations—and on up the ladder. Maybe you'll want to try for at least one station on

each frequency.

Another interesting target is on-the-spot news coverage. This includes such things as state primaries of national interest, like Gen. Edwin A. Walker's try for the governorship of Texas. The Dallas-Fort Worth clear channel transmitter on 820 kc (shared by WBAP and WFAA) carried a Walker speech live, then later the vote count as returns came in.

During local emergencies stations that normally sign off around midnight may operate all night; WCOV, Montgomery, Ala., on 1170 kc, was widely received during the Ku Klux Klan integration riot. If the emergency is serious enough, such as flood or hurricane, even daytime stations broadcast continuously.

On the lighter side, distance listening is a boon to the sports fan. Clear channel stations often carry baseball, football, and basketball


games of national interest.


The procedure for BCB news hunting is quite direct. Get to know what locations can be heard when, and which channels are clearest during the early morning hours. Then, when something is up, determine from WHITE'S RADIO Loc what stations are in the area, and look for those most likely to be heard.

QSL Hunting. While broadcast band stations do not answer reception reports quite as readily as their short wave cousins, at least 75% do verify in one way or another.

It is important to remember that AM stations, with the exception of some clear channel broadcasters, derive no revenue from the distant listener, and therefore verify only out of courtesy. Never demand a QSL: politely request it, and be sure your report is accompanied by return postage.

Although reports are usually answered by

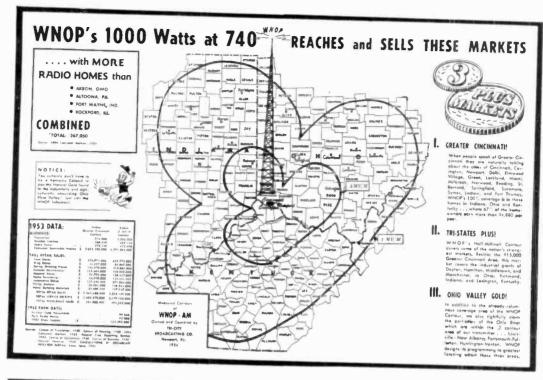

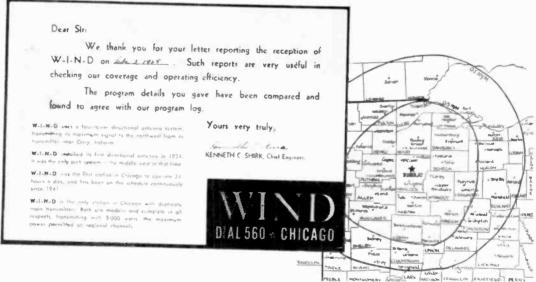

The majority of AM broadcasters verify in one way or another, and some QSL's are very elaborate, like these maps from WNOP, 740 kc, Newport, Ky., and WFIN, 1330 kc, Findlay, Ohio. The postcard from WIND, 560 kc, Chicago, measures 7x10 in.

the chief engineer of the station, and it is a good idea to address them to him, write in plain English, so that anyone at the station can understand and answer it. Do not use QRM to indicate interference or QRN instead of static.


Describe the program heard, and try to in-

clude the names of a few advertisers and the times of their spots (impossible, of course, when a test is logged). Describe your equipment and pinpoint your location—unless you live in a large city whose location is well known. The more distant the reception, the better your chance for a reply.

Three-Way Listening Dynamite

Tune in on the most controversial of all foreign broadcasters

By C. M. STANBURY II

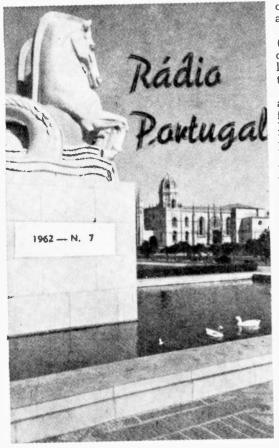

Radia Partugal's manthly program guide, sent free to those who report.

MONG the most outspoken short wave stations on the air today are Radio Cairo, the Voice of the West from Lisbon, and Radio Katanga. SWL's in the U. S. cannot agree as to whether each is ally or enemy, hero or villain. The reasons for the confusion are easily come by.

Radio Cairo. A few years ago this one followed the Communist line very closely; since then, however, the English language broadcasts at least have shifted strongly toward the neutral center. On June 22, 1962, for example, during Radio Cairo's English news beamed to West Africa (on 17690 kc at 1420 EST), there were numerous quotes from Secretary of State Dean Rusk, plus a long item

on British fears over a Chinese Communist arms build-up.

On July 12, the English news to Europe (11915 kc, 1645 EST) played up the withdrawal of U. S. troops from Thailand. Needless to say, Moscow and company did every-

thing possible to minimize this.

On the other side of the coin, every day at 1200 EST Cairo switches a transmitter from 17920 to 17895 kc and calls itself Radio Free Africa, a simulated clandestine station. Its broadcasts on this frequency are designed to stir up rebellion in such places as Kenya and Rhodesia—a legitimate cause, perhaps—as well as the Congo: and for the last named, Cairo's chief selling point is Patrice Lumumba, a communist martyr seldom mentioned by moderates and rightists in Africa. Maybe Radio Cairo hasn't reformed after all!

Before you jump to that conclusion, however, note that Radio Moscow is on the same channel, also beaming to Africa, throughout the entire period of Radio Free Africa operation (in English until 1230 EST). In effect, Moscow is jamming RFA: you figure it out.

The Voice of the West is a special English language transmission for North America by the Portuguese National Radio (Emissora Nacional). EN, as it is known in SWL circles, probably uses more names than any other station: for English to Africa and Asia it becomes Radio Lisbon, and its monthly program guide bears the title Radio Portugal (Fig. 1).

On March 7, 1962, shortly after inauguration of this North American service, the Voice of the West signed on with a musical "V" for victory, launched an attack against the new Italian government, and then turned its guns on President Kennedy, finishing up with this: "There are some people who believe Kennedy is holding off nuclear tests until his family—Jackie, Robert, and Ted—are safely at home."

The above is a typical sample. Even the use of the "V" for victory is controversial: this was the rallying call transmitted by Allied stations during World War II. Although Portugal did lease bases in the Azores to the U. S.—a year and a half before the end of the war—she remained neutral throughout the conflict.

Claims are made on VOW for Lisbon's nonracialism, which is supposed to set it apart from other fascist nations—such as South Africa. On March 5, however, Africa was described as a "racial hodgepodge" which, if given independence, would return to its "hazy origins."

Such sentiments have made the Voice popular with some American right wing groups, and its stock is boosted with them by statements like "Democratic governments have been proven incapable of upholding the might of great empires," and that there are Communist advisors around the American Secretary of Defense. However, on May 25, in answer to a listener's question, VOW described Portugal's all-encompassing system of state medicine, considered by these same rightists to be the mark of a socialist society.

Broadcasts are beamed to North America every night at 2100 and 2245 EST on 6025 and 6185 kc; if neither frequency is heard, try 9740, an alternate channel. Of the three stations discussed here, Lisbon is by far the

most easily received.


The Voice of the West is anxious for reports, and any listener who submits one is likely to have a song dedicated to him; this is partly to give the impression that the broadcasts have a large number of supporters in the U. S.

One veteran SWL describes it this way: "They send me two or three program schedules every month, enclosing reception report forms which I do send back once a month as a matter of courtesy . . . don't listen too much to them, not in love with their comments." This listener had a selection dedicated to him on June 6, after being thanked over the air for his "letter."

Radio Katanga. During the first week of July, 1962, the Elisabethville government's powerful international transmitter returned to the air, after a silence of more than six months—it had been destroyed by the UN force on December 6, 1961. Radio Katanga is the station which on May 7, 1961, while supposedly representing a legitimate African government, emphasized that white South African troops were being employed against colored UN forces: five days later, it was



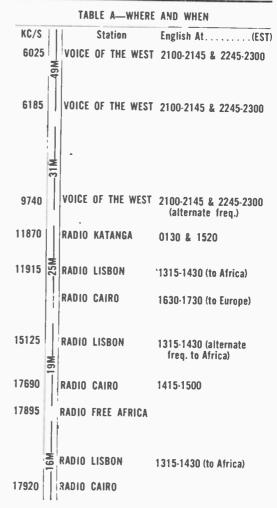QSL card from Emissora Nacional (alias Radio Portugal, Radio Lisbon, and the Voice of the West).



quoting in detail UN charges against the racial policies of South Africa and Portugal.

The resurrected RK—which still quotes the South African government—is even less predictable. On July 19, 1962, it quoted a long statement by the UN representative in Elisabethville which concluded with an accusation against Radio Katanga itself, charging it with following one line on its European broadcasts and another—against integrat on into the Congo—on its African service. RK made no attempt to deny the charge: either it is the most honest broadcasting organization in the world—or is trying to convince its listeners of this—or there is a civil war going on right inside the station.

Without a doubt, Radio Katanga offers the most surprising listening within our torrid triangle. It can be heard on 11870 kc, with news in English at 130 and 1520 EST.



Selecting the Right Short Wave Receiver


By JERRY SKELLY

When you buy that communications receiver, be sure to get a set of head-phones for it. By excluding outside noises, they make for better listening. They also make wee-hour DXing more acceptable to the other members of your family.

Photos courtesy Allied Radio Corp., Chicogo

HORT wave listening can be one of the most enjoyable and informative of hobbies, but only if you have adequate equipment—a receiver that covers the right bands, has the sensitivity to pull in weak signals, and can separate stations that are close together on the dial.

By learning what makes a receiver a top

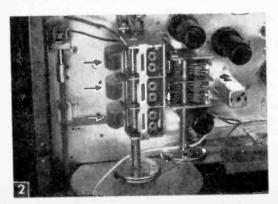

performer, you can compare the sets on the market and select the one you want. Keep in mind that the purchase of a communications receiver is something of an investment. A good one depreciates slowly and after four or five years may still be worth half its cost. So resist any temptation to buy off-brands or marginal-performance sets merely because they are low-cost. Stick with widely known names such as those in the table on page 64.

In the table we've listed 12 already-assembled and four kit-type receivers that, together, account for most of the communications receivers sold today. All of them are superheterodynes and use a time-proved circuit that converts the signal frequency to an "intermediate frequency" where large amounts of stable amplification can be applied.

To determine haw many r.f. stages a set has, look inside and count the gangs on the tuning capacitor. Set shown here has three gangs (arrows), which means there is one r.f. stage. Just two gangs means no r.f. stage, while a four-gang capacitor indicates two r.f. stages.

We'll explain each of the performance features listed in the table, so that you can see how each contributes to the set's performance. And you can use the same information to judge sets that aren't in the table, such as models that are no longer built but may still be found in some stores.

Many of the performance features are given in manufacturers' brochures or mail order catalogs, which means you can get a

good idea as to a set's quality even before going to a store and trying it out.

How Many Tubes? The first thing to check is the number of tubes. In general, the more tubes, the better the receiver—and the higher the cost. The number of tubes reflects the number of amplifying stages and is a rough index of how much "guts" a set has.

Get the Right Bands. If you want to use


Get the Right Bands. If you want to use your set for all types of listening—news broadcasts from foreign countries, music, radio amateurs or "hams", police calls, aircraft, or Russian satellites—you should steer clear of receivers that cover only the radio amateur bands. Instead you will want a set that, like the sets in the table, has general coverage and will bring in all the bands (Fig. 3, 4).

An R.F. Stage? At least one radio frequency stage is desirable, because it gives the received signal some preamplification before it is subjected to the relatively noisy process of conversion to the intermediate frequency of the superhet. This contributes to the set's sensitivity by helping boost the signal over the noise.

An r.f stage also reduces annoying image response. (A strong signal may be received at two different points on the dial, one of them the correct frequency and the other, the "image", incorrect. Receivers with good image rejection attenuate the image below hearing level. You can easily determine how many r.f. stages a receiver has, even when it doesn't tell you in the catalog, by counting the numer of gangs, or sections, on the tuning capacitors (Fig. 2).

At Least Two I.F. Stages? Intermediate frequency amplifier stages (don't confuse them with the r.f. stages) provide most of a superhet's sensitivity and much of its selectivity—or the ability to separate stations.

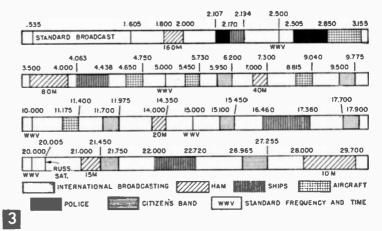The i.f. amplifiers operate at a lower fre-



Drawing shows all the broadcast bands and what can be heard on them. A receiver with general coverage (such as in Fig. 4A) will bring in all of these.

Receivers with non-continuous dials, as in Fig. 4C, will pick up only some.

quency than the signal (usually at $455 \ kc$), and at that frequency tubes and transformers can be designed to give tremendous amounts of stable amplification.

The receiver you buy should have at least two i.f. stages. One stage is barely adequate, and will mean low sensitivity. You can determine how many i.f. stages a set has by checking the set's specifications in a catalog or by looking at its schematic diagram (Fig. 5).

Sensitivity. A sensitive receiver pulls in the weaker signals clearly and is a great help in DXing—trying to pick up distant signals.

Receiver manufacturers do not publish sensitivity ratings, and you would have to be an electronics engineer to figure them out yourself, but the number of i.f. and r.f. stages a set has will give you a rough idea of sensitivity. You'll note from the table that we have evaluated the sets for sensitivity and rated each as either Fair, Good or Excellent.

Selectivity is also difficult to determine unless you're a radio expert. Besides separating close-together stations, it aids the reception of weak signals close to strong ones and improves the ratio of signal to noise. As with sensitivity, look for i.f. stages; we have rated each set in the table as Fair, Good or Excellent in selectivity.

BFO for Code and Satellites. If you want to listen for Morse code (CW) or signals from satellites, your set should have a beat frequency oscillator (BFO). Normally, code signals are poorly audible. The BFO is a special circuit which—when you turn it on—"beats" with the code to give an easy-to-read musical pitch to the dots and dashes.

Receivers with BFO will have markings on the front panels such as "Code," "CW," "Pitch Control" or "BFO Pitch."

Other Valuable Features include an "S" meter, a noise limiter, an antenna trimmer, a crystal calibrator and a phono input:

Performance Guide to Communications Receivers										
Manufacturer Model No.	Price	Number of Tubes (5)	Frequency Range in, Mcs.	R. F. Stages		Sensi- tivity	Selec- tivity	S Meter	Antenna Trimmer	Internal Crystal Calibrato
National NC60	59.95	5	.540-30	0	1	F	F	No	No	No
Hallicrafters S108	139.95	8	.540-34	1	2	G	F	No	No	No No
Hallicrafters SX110	169.95 + 12.95 spkr	8	.540-34	1	2	G	E	Yes	Yes	15.95
Hammarlund HO100AC	199.00 + 14,95 spkr	10	.540-30	1	2	E	E	Yes	Yes	extra No
Hallicrafters (4) SX62A	395.00 + 19.95 spkr	16	.540-108	2	3	E	E	No	No	No
Heath-Kit AR-3	29.95 (1)	5	.550-30	0	1	F	F	No	Yes	No
Knight-Kit R-55	59.95	6	.540-36	0	2	G	F	No	Yes	No
Knight-Kit	99.95	9	.540-30	1	2	E	E	12.95 extra		No
Heath-Kit GC-1A	109.95 (2)	10 Tr.	.550-32	1	3	E	G-E	Yes	Yes	No
Lafayette HE-30	wired — 99.95 kit — 79.95	9		1	2			Yes	No	No
Lafayette	wired — 79.95 kit — 64.50	9		1	2			Yes	NO	1 140

Note (1):Cabinet \$4.95 extra.

Note (2): Supplied with batteries. A-C power supply is \$9.95

extra.

Note (3): Uses 10 transistors and 6 semiconductor diodes.

Note (4): The SX62A hos a hi-fl audio system. Also covers the

standard FM band. Note (5): Includes rectifiers and voltage regulator tubes. All models have BFO's, and all have noise limiters except NC60. All models are current, made by standard brand manufacturers with national distribution. Price is subject to change. Excise tax is included; but shipping charges and sales tax, if any, must be added.

• The "S" meter occupies a distinctive place on the front panel (if the set has such a meter) and is calibrated from 1 to 9; in some cases, the meter will be marked "Carrier Level." The calibrations indicate the strength of the received signal and are helpful for on-the-nose tuning, since signal strength is greatest when tuning is correct. Not an absolute necessity for average listening, this feature is found on only the more expensive receivers.

 Noise limiter. This circuit minimizes the effect of extraneous electrical noises. If the receiver has one, a front panel switch will be marked "Noise Limiter" or "ANL" (for Auto-

matic Noise Limiter).

• Antenna trimmer. This is another front panel control which almost always is marked either "Antenna" or "Antenna Trimmer." Important to top performance, it tunes the antenna and the receiver input circuit together for better signal energy transfer. (You will have difficulty getting clear reception on distant stations without a good out-door antenna. Weaker signals may represent an energy of less than a few millionths of a millionth of a watt. Give your receiver a break by collecting as much as possible of this energy in a good antenna before asking the receiver to go to work on it.)

 Crystal calibrator. Inevitable variations in mass-produced parts, together with changes in temperatures, humidity and line voltage, produce inaccuracies in the tuning dial scale.
 A good way to overcome this is by use of a

precision frequency source and its harmonics as dial calibration reference points. The receiver can then be adjusted to bring in stations at the correct spot on the dial. Receivers that provide internally for a crystal calibrator have a "Calibrate" marking on a front panel switch.

• Phono input. This is an unessential extra that permits the use of the receiver's amplifier and speaker with accessory record changers. FM tuners and such (Fig. 6).

ers, FM tuners and such (Fig. 6).

Finding the Right Dealer. You can check out a receiver for the preceding features merely by looking at a catalog or brochure.


But you should also put it through its paces to see how it performs. This can be done only by going to a dealer (or by purchasing a set through a mail order house with a moneyback guarantee if you're not satisfied).

It's important to select your dealer carefully. Check your classified telephone directory for names of radio parts jobbers or ask a local radio amateur where he shops.


Be wary of department stores and jobbers who serve radio-TV servicemen exclusively, because your dealer should have a service department to back up a new set's guarantee. He should also have a wide selection of sets.

Through the Paces. Once you are ready to give a receiver its on-the-air test, turn it to short wave broadcast and amateur signals. These should be heard on one band or another at any time of the day or night. If you can't hear any signals, try another set.

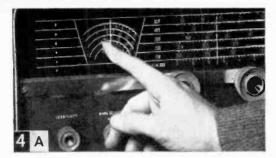Next, rotate the band selector switch. Some



Here's how you can easily tell if a set has general coverage, will pick up all the bands shown in Fig. 3. In 4A, finger points to 4.5 megacycles, which is at extreme left of the second band on the dial. In 4B, finger points to 4.6 megacycles, which is on extreme right of the third band; thus there is no gap between the bands. In 4C, though, note that the top band runs from 3.5 to 4.0, while the band below it picks up at 7.0. This receiver covers only the ham bands.

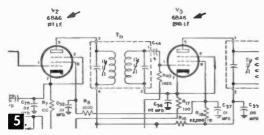

It's easy to tell how many i.f. stages a communications receiver has. Just take a close look at its schematic diagram. The stages (arrows) will be clearly labeled as shown in this section of a typical schematic. This set has two i.f. stages.

signals or noise should be heard on all bands. No band should be 100% dead.

Now, after tuning in a station, rotate all the controls and throw all the switches—one by one—listening carefully as you do so. Each control or switch should have some audible effect on what you hear.

Potentiometer controls should not give scratchy sounds when they are turned. If one does, it probably is worn or defective.


Last, turn the tuning dials over their entire range. They should move easily with no noticeable slack motion or backlash.


What About Portables? If you don't need the portability that comes with a transistorized receiver, you probably would do well to avoid it and buy a regular tube set. The less expensive of the transistor models—those costing up to about \$90—do not have the sensitivity of a comparable tube set.

The more expensive transistor portables charge a high premium for the combination of portability and good performance—yet may lack many features desired by DXers.

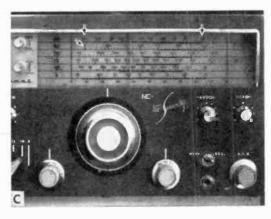Buy a Used Set? A used receiver may be a good buy, but only if it comes with the standard 90-day new set guarantee—in writ-





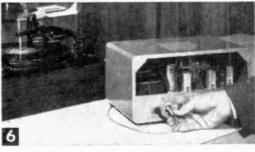

Receivers with a phonograph input will have the word "Phono" on a front panel switch position, but the jack will be on back of the set as shown here.

Don't confuse the "Phono" jack with "Phanes"—which designates the headphone jack as shown in Fig. 1.

ing—covering parts and labor. Used sets should be purchased only from those jobbers who have service facilities and will give you an additional guarantee in writing—stating that you can get a full refund within 10 days if you are not satisfied with the set.

If you plan on buying a used receiver, you should look for the same features listed in the table, but be sure to give it a real wring-out during the on-the-air check. If possible, take an experienced radio amateur along when you go to buy the set. He'll probably be able to assess it for you pretty well.

Experimenter's **Transistor** Breadboard


By ART TRAUFFER


RANSISTORS and small diodes are fragile and easily ruined by excessive handling. With this miniature breadboard you can instantly test circuits in any combination without soldering and unsoldering leads.

The power transistor is mounted on a copper bracket which doubles as a heat sink, and the clips are marked so vou can't make a mistake in your connections. Size and placement of the parts are not critical. For the base use a 6 x 2 x ½-in. piece of wood. Mount the clips with 3/8-in. rh wood screws. Solder a general purpose diode (Sylvania 1N34A or equal) directly to a pair of the


clips. Solder three short wire leads to the terminals of a three transistor socket, and run these leads to the three Fahnestock clips.

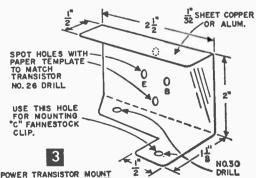Bend the power-transistor bracket from ½2-in. sheet copper. The "C" clip goes over the long ear of the bracket. Mount the power transistor (Motorola 2N555, RCA 2N301 etc.) directly to the copper surface, using two \%2 x 3/8-in. rh machine screws and nuts. Do not



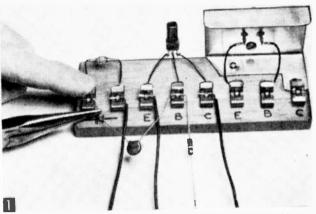

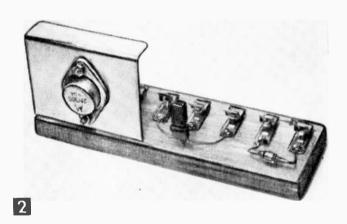Front view shows breadboard set up as crystal detector with one stage of audio. Rear view shows power transistor bolted directly to copper heat sink mount. Engrave the symbols with a ball point pen.



MATERIALS LIST-EXPERIMENTER'S TRANSISTOR BREADBOARD

Amt.	Size and Description
1	general-purpose germanium diode (Sylvania 1N34A, etc.)
1	general-purpose PNP transistor (Raytheon CK722, etc.)
1	AF power amplifier transistor (Motorola 2N555, RCA 2N301, etc.)
1	Raytheon CK722 transistor socket
2	terminal clips for power transistor
1	4 x 21/2 x 1/32" sheet copper (heat sink for power transistor)
2	6-32 x 3/8" th with hex nuts
8	3/4 x \$/16" Fahnestock clips
9	round-head wood screws 3/8" long
1 pc	6 x 2 x 1/2" hardwood

solder directly to the emitter and base pins on the power transistor. Use lugs removed from a miniature tube socket.

If you work with more complex circuits, you'll find that several of these boards will be handier than one large breadboard.



It's New - It's Big - It's Better Than Ever It's From the "World's Hi-Fi & Electronics Shopping Center"

The exciting, all-new 1963 Lafayette Catalog features thousands of items for the audiophile, experimenter, technician, hobbyist, serviceman

. Citizens Band, Tape Recorders, Stereo Hi-Fi. Ham and Amateur Equipment, and much more. No Money Down on Lafayette's Budget Plan

ONLY LAFAYETTE OFFERS THESE OUTSTANDING EXTRAS: VSATISFACTION GUARANTEED OR MONEY REFUNDED VLOWEST PRICES EXCLUSIVE LAFAYETTE KITS VLARGEST STOCK SELECTION VBUY THE EASY-WAY WITH EASY-PAY ...

LAFAYETTE FM/AM STEREO MPX TUNER



89.50

- Tuned RF Stage; Duplex 3 Gang Tun-Duplex 3 uame ing Condenser
- quency Control and Noise Filter

LAFAYETTE HE-20C C.B. TRANSCEIVER



109.50

- Officially Approved For Use in Canada
- For Use in Canada 8 Crystal Control-led Receive and Transmit Positions

LAFAYETTE 10-TRANSISTOR C.B. "WALKIE-TALKIE"



33.95 each, 2-for-62.90

HE-29B

- 50% More Power-ful—Extra RF Stage Receives and
- Transmits up to 2 Miles

LAFAYETTE "SQUELCHER"



- · Noise Eliminator and Squelcher
 - Improves Recep-Transceivers

LAFAYETTE 4-TRACK STEREO TAPE DECK.



Built-in Transistorized Stereo Record/Play Preamps Records Sound-on-

Sound

	L ORD					
111	Jericho	Turnpil	ie, Syo	sset, I	L. I.,	N. Y



Jamaica, N. Y. New York, N. Y. Bronx, N. Y. Scarsdale, N. Y.

Newark, N. J. Plainfield, N. J. Paramus, N. J. Boston, Mass.

Natick, Mass.

LAFAYETTE RADIO ELECTRONICS, Dept. EXA-3 n

.O. Bo	x 10, Syosset, L. I., N. Y.	
] \$	enclosed for Stock No.	

shipping charges collect.

Address


the Send me Free 1963 388-Page Lafayette Catalog



Zone.

AC Experiments with Series Circuits

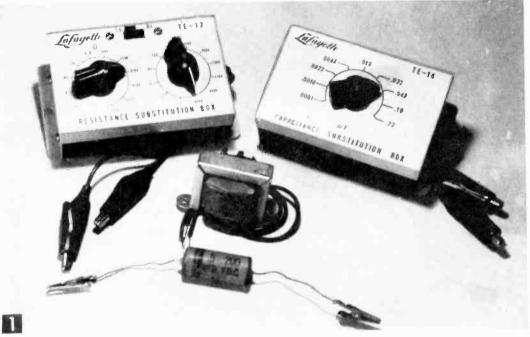Why voltage, unlike that in dc, can often be much greater than the amount applied—10 tests you can make with simple, safe, and inexpensive equipment



These basic passive components plus a 6.3-volt transformer and an ac voltmeter are all that's needed for some challenging ac experiments.

By FORREST H. FRANTZ SR.

LTERNATING current (ac) circuits are excitingly different from direct current (dc) circuits. The dc circuit situation with a steady voltage applied at a relatively long time after any switching has occurred, is influenced only by the circuit resistance. But in a circuit operated from an ac power source, capacitance and inductance also influence steady state conditions.

The sum of voltages across the elements in series ac circuits add up to a voltage greater than the applied voltage if inductance and/or capacitance are present. And that voltage can be many times the applied voltage if inductance and capacitance with proper value relationships exist in the circuit.

Equipment Used. You can conduct the experiments that follow with capacitance and resistance substitution boxes (available at most radio shops) or, if preferred, you can just as readily use loose capacitors and re-

For the inductance, we used an inexpensive


universal output transformer with the sec-


ondary left open (no connections).

In addition to these components forming the passive elements of the series ac circuit (Fig. 1), you'll need a power source and ac voltmeter. Any 6.3-volt filament transformer can provide the power. It provides an exact frequency of 60 cycles since the power line frequency is well regulated.

The low voltage is preferable because it keeps the larger voltages which you'll encounter at resonance down to about 35 volts. If you were to use a 25-volt power supply, the voltage across the capacitor at resonance would be close to 150 volts! A transformer has the additional safety feature of isolating the circuit from the ac line and preventing accidental shock if you should become grounded in any way.

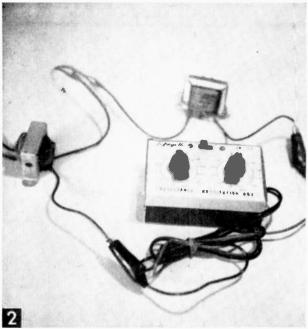Many experimenters have their own voltmeter. I used a Heathkit MM-1. If you wish to buy one, you might check the catalogs of the mail order houses and kit companies for a meter to fit your needs and pocketbook. You should select a vacuum-tube voltmeter (VTVM) or a multimeter with an ac sensitivity of 5000 ohms per volt or better. You'll



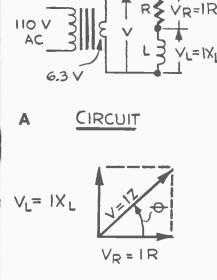

Series R-L arrangement.

have considerable error if you use a meter with only 1000-ohm per volt sensitivity.

Series Resistance: Inductance (R-L) Circuit

First connect the resistance substitution box and the inductance in series, using brown and blue leads, then connect the leads to the transformer 6.3-volt secondary as in Fig. 2A. Measure the voltage across the coil (IXL—current times reactance) and the voltage across the resistor (IR—current times resistance) for R values of 1000, 2200, 4700, 6800, and 10,000 ohms. Record IXL and IR.

You'll note that IXL plus IR is greater than V (measure V) for most values of R. Why is this so? Can you deduce anything about ac circuits from your data?

PROJECT 1

Vector Diagrams. Here's a partial explanation: Current lags the induced voltage in an inductive circuit. The amount of lag is defined by a *phase* angle (\ominus) and is 90° for a pure inductance. The phase angle in a resistance is 0°, so resistor current and voltage are in phase.

These relationships show up in a vector diagram, as in Fig. 2B. IR and IXL are drawn to scale for a typical set of R and L values, with IXL leading IR by 90°. Now the value of IXL is the magnitude of the reactive voltage only and should be symbolized more properly as VL. If the vector diagram is completed, the voltage V is the resultant. The angle between V and IR is the phase angle (⊕).

Now, draw the vector diagrams for the data

you took previously, ignoring the measured value of V. You might, for example, let 1 in. equal one measured volt. Complete the diagrams to solve for V, then compare the values thus obtained with that of the measured V. You'll note that there's a difference. Why is this so? Write a short explanation as to why you may have obtained these seemingly erroneous answers, then put it aside for comparison with the explanation which will be given later.

ECTOR

DIAGRAM


PROJECT 2

Understanding Circuit Computations. The preceding project has probably alerted you to some of the possible computations for this circuit. First, the vector addition of VL (which is IXL) and VR (which is IR) to obtain the resultant V (which is IZ as will be seen shortly), can be solved analytically. Units used are V. volts; \bigcirc , degrees; I, amperes; XL, ohms; R, ohms, and L, henries:

- (1) $V = \sqrt{V_R^2 + V_L^2}$
- (2) $\tan \Theta = VL/VR$ The fact is that
- (3) $V_L = IX_L$ and
- (4) V_R = IR have already been mentioned. From this,
- $(5) I = V_R/R$
- (6) $X_L = V_L/I$

Now, what is XL? It is the inductive reactance of the coil. The inductive reactance is a function of the inductance of the coil and the frequency of the applied voltage.

(7) $X_L = 2\pi fL$

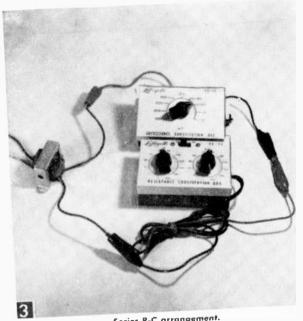

Series R-C arrangement.

For our experiment, the frequency f is 60 cycles. Therefore $2\pi f$ is 377 for our problems. I'll use 377 wherever $2\pi f$ is involved in most subsequent formulas and calculations and leave substitution of $2\pi f$ when a different frequency is to be used as a student responsibility. Then, for our case

(8) $X_L = 377L$, and

(9) L = XL/377

Now what about this "Z" bit? Z is the impedance of the circuit in ohms. It is the vector sum of the resistance and the reactance. Hence,

(10) $Z = \sqrt{R^2 + XL^2}$, and

(11) $tan \Theta = XL/R$

Note that equations 1 and 2 are equations 10 and 11 with all terms multiplied by I. Hence,

(12)V = IZ, and

 $(13) \quad Z = V/I$

Has any of this explanation given you a clue as to why you got erroneous results in Project 1? PROJECT 3


Examples of Circuit Computation. At this point, let's try an example. Take the data for the series circuit where R = 4700 ohms. I got values of $V_R = 4.2$, and $V_L = 3$. Applying the formulas presented in Project 2, and rounding off to two significant figures:


 $V = \sqrt{4.2^2 + 3^2} = 5.2 \text{ volts}$ (1) from $\tan \Theta = 3/4.2, \Theta = 35.6^{\circ}$ (2) from

I = 4.2/4700 = .0009 amp(5)XL = 3/.0009 = 3300 ohmsfrom (6) from

L = 3300/377 = 8.8 henries(9)Z = 5.2/.0009 = 5800 ohms from (13)

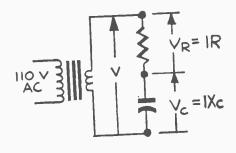from $Z = \sqrt{(4700)^2 + (3300)^2}$ (10)check



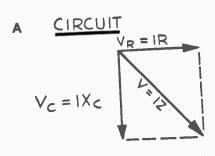

VECTOR DIAGRAM

The latter check equals 5700 ohms, which is adequate since we've been rounding off numbers. Why equations 10 and 13 check while measured V and computed V don't check will be explained in the next project.

At this point, perform the computations, using your data for R = 2200 ohms.

PROJECT 4

The Fallacy. Use the ohmmeter function of your multimeter to measure the resistance of L, while L is disconnected from the circuit. You'll find the resistance is roughly 200 ohms. This should give you the first clue to the difference between the computed V and the calculated V. In calculating V, we assumed that L was a pure inductance. In practice, however, this is impossible because a length of wire exhibits resistance.


Furthermore, when a length of wire is wound into a coil, there is capacitance between turns. In the case of our experiment, the capacitance between turns introduces more error than the resistance of the coil.

There is an additional error due to the loading of the circuit by the meter during the measuring process. This error plus others mentioned above introduces an error of about 8% to 15% in the measured and calculated values of V.

Series Resistance:

Capacitance (R-C) Circuit

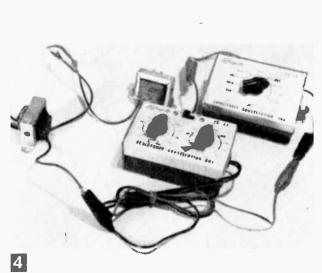If the facts of practicality in the preceding projects are puzzling you may relax and smile for what comes next. The inductance and resistance associated with practical capacitors is negligible at 60 cycles. Consequently, a practical capacitor looks like an ideal capaci-





tor. In experiments described here, then, the error will be due to meter-loading during measurement only. For a 5000-ohm-per-volt meter this should be less than 8%.

Connect the circuit as shown in Fig. 3. Set R at 6800 ohms on the resistance bex. Record Vc and VR for C = .1, .22, .5, and 72 microfarad (mfd). Note that the capacitance box is disconnected and the external .5 mfd capacitor is used for the .5 mfd measurements. The .5 mfd capacitor is connected across the capacitance box (set to .22) to make the .72 mfd measurements. Measure V and record the value.

Vector Diagram for R-C Circuit is shown in Fig. 3B. Note that the Vc vector is directed downward. Current leads in a capacitive circuit.


Draw vector diagrams for this data as you did for the data in Project 1. Then determine V from the vector diagrams. The error between the measured V and the calculated V is much smaller.

PROJECT 6

Understanding Circuit Computations. The applicable formulas are:

- $(14) \quad V = \sqrt{VR^2 + VC^2}$
- (15) $tan \Theta = Vc/VR$
- (16) $V_C = IX_C$
- (17) $V_R = IR$
- (18) $I = V_R/R$
- (19) Xc = Vc/I
- (20) $X_c = 1/(2\pi fC)$
- (21) $X_{\rm C} = 1/(377 \ {\rm C})$ (for f = 60 cycles)
- (22) C = 1/(377 XC) (for f = 60 cycles)

A CIRCUIT

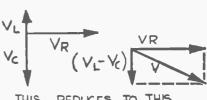

THIS REDUCES TO THIS

B VECTOR DIAGRAM

- (23) $Z = \sqrt{R^2 + Xc^2}$
- (24) $tan \Theta = XC/R$
- $(25) \quad V = IZ$
- (26) Z = V/I

These units are V, volts; I, amperes; R, ohms; Xc, ohms, C, farads, and Z, ohms.

The matter of making most of the computations is pretty much in line with the examples of Project 3. The generation of a group of examples corresponding to the set for the R-L circuit given in Project 3 is a good exercise for the student. There is considerable similarity in most cases.

PROJECT 7

Another Experiment. Adjust circuit capacity to .72 mfd. Then record V_R and V_C for R = 2.2K, 4.7K, and 6.8K.

Now you can draw vector diagrams for this data. Compare the values of V obtained from the vector diagrams with the measured values of V.

If you wish additional practice, you may perform the computations for all sets of data. The more problems you do, the better you get to understand the subject. With this experimental set-up, you can get a large amount of dage for practice problems.

Series Resistance-Inductance-Capacitance (R-L-C) Circuit

Hook up the series R-L-C circuit as in Fig. 4 and 4A. Set R=2200 ohms and record VL, Vc, and VR for C=.1, .22, 15, and .72 mfd. Measure and record V.

In the vector diagram (Fig. 4B), you can see that VL and Vc are 180° out of phase and hence can assume large values. What is happening here? The capacitor and inductor al-



ternately store and dump energy on each other. A special relationship exists between Vc and VL at resonance, a phenomena that we'll discuss later

PROJECT 8

Draw the vector diagrams for the series R-L-C circuit.

PROJECT 9

New Formulas and Practice. The formulas presented earlier apply for the most part. However, there are new formulas for $\hat{
m V}, \, \ominus$, and Z:

MATERIALS LIST-AC EXPERIMENTS

capacitance, .1 to .7 mfd (Lafayette TE-16 capacitance substitution box, \$2.95, and a Sprague 2EP-P50.5 mfd., 200-v. capacitor, 36¢). inductance (Use the brown and red leads on Lafayette TR-12 output transformer, \$1.19). Tape or keep the red lead out of the wiring. Leave the secondary open. resistance, 1K to 10K (Lafayette TE-17 resistance substitution box, \$3.95). 6.3-v. filament transformer (Lafavette TR-11 89c). Description Desig. C

(Lafayette TR-11, 89¢). 6.3-v. filament transformer (Lafayette TR-11, 89¢). AC voltmeter, 5000 ohms per volt or better sensitivity. (Heathkit MM-1, \$33.95). Least expensive suitable unit is Lafayette TK-10, \$11.95.

Sources: Lafayette Radio, 111 Jericho Turnpike, Syosset, L. I., N. Y. Heath Co., Benton Harbor, Mich.

 $V = \sqrt{VR^2 + (VL - Vc)^2}$ (27)

 $tan \ominus = (VL - Vc)/VR$ (28) $Z = \sqrt{R^2 + (XL - Xc)^2}$

(29) Now you can perform a complete group of computations for one set of your data.

PROJECT 10

Resonance. Removing R from the circuit will change the circuit to that shown in Figs. 5 and 6. Then adjust C till Vc reaches a maximum value. Note that Vc will be somewhere between 30 and 40 volts. On measuring VL, you will find it is nearly equal to Vc.

When VL = Vc, the circuit is in resonance. This occurs when XL = Xc. A relationship of interest at the resonant frequency fo is:

(30) fo = $1/(2\pi \sqrt{LC})$

The manipulation of this formula to solve for L and for C is left as an experimenter exercise.

We haven't used an ideal inductance, so you'll notice some errors (seeming contradictions) in some of the voltages computed. But since we went into that subject in relative detail earlier, you're prepared for it at this point and know why it occurs.



Two-Tube Long Wave Receiver

This compact ac-dc receiver features good sensitivity, better than average selectivity, and simplified construction. It has an adjustable tuning range of 85 to 550 kc. and is easily modified for broadcast-band reception


By JOE A. ROLF, K5JOK

THE circuit of this economical receiver (see Fig. 4) employs two miniature high-gain TV tubes. The 6AN8 is a regenerative detector; the pentode section of the 6AU8 is an audio amplifier. The triode of the 6AU8 serves as an ac-dc type rectifier.

The heart of the circuit is the detector, a regenerative cathode-follower type commonly known as the "Regenode." If you're not familiar with this hybrid circuit, here's how it works: The pentode section of the 6AN8 is a conventional grid-leak detector, with the exception of the signal grid which is separated from the tuned antenna circuit by the cathode-follower connected triode section of the tube. This arrangement permits a degree of selectivity not possible with the detector

grid connected directly to the antenna circuit, since the signal-grid loads the tuned circuit and reduces its Q, or selectivity ability. The cathode-follower isolates the detector from its input circuit and allows a great improvement in selectivity. The circuit operates smoothly, is easily adjusted, and eliminates hand-capacity effects common to most regenerators. These advantages are particularly desirable in a LW receiver.

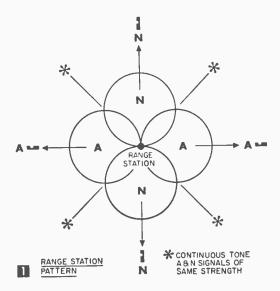Since hand capacity does not affect operation, an all-wood chassis constructed with simple hand tools can be used. Chassis details are shown in Fig. 5. Large holes (for tube sockets and controls) can be made with a coping saw; fastener holes can be made with a hot ice-pick in the absence of a drill. A



YOU'LL be pleasantly surprised at the number of interesting signals to be heard below the standard broadcast band, though at first they may sound like nothing but jumbled dots and dashes intermixed with weird howls and squeals. Careful listening, however, will reveal this apparent bedlam to be important communication services which make unusual listening and challenging DX.

The main divisions of the 10 Kc. to 535 Kc. band are shown in Table A. It is occupied mainly by aeronautical and marine services, although 150-535 Kc. is part of the standard BC band in Europe and Asia. However, without discounting the possibility of logging some of these BC stations, the marine and aeronautical stations are of prime interest to most LW listeners.

What to Listen To on LW

The long waves provide up-to-the-minute reports on weather and flying conditions, code practice and some good DX

The most popular are the navigational aids, or radiobeacons, heard between 200 Kc. and 405 Kc. Some are marine beacons, others aeronautical. Both employ very slow amplitude modulated code and are easily distinguished from one another by their signals.

Marine beacons usually transmit their call signs continuously in an omni-directional pattern. In some cases the call, consisting of from two to four letters or numerals, is separated by a number of dashes. Many marine beacons can be heard constantly over a considerable range, while the less powerful can be logged at great distances under favorable conditions.

Aeronautical range stations transmit a combination A-N signal in a four-leaf pattern like that of Fig. 1. They identify themselves every thirty seconds and employ two pairs of antennas to obtain the four-leaf radiation pattern. The transmitter is operated continuously and is alternately switched between the two antenna systems so that an A (dit dah) is radiated in the directions marked A in Fig. 2, and an N (dah dit) in the directions marked N. Midway between the A and N patterns, the signals merge as a steady tone which aircraft follow to or from the station. If the pilot leaves this course, he will hear either the A or the N.

These radiobeacons offer an unlimited

metal chassis will afford more compact construction, but a wooden panel and cabinet should be used to avoid accidental grounding of the chassis.

Construction is not critical and will pose no difficulty if the general layout shown in Figs. 2, 3, and 5 is followed. Keep RF and AF leads separated and away from ac leads. This is best accomplished by wiring the filaments and power supply first, then the AF and detector stages.

Ground connections are made to solder lugs mounted to the socket and tuning capacitor fasteners. Components R4, R6, R9 and R10 mount on a 7-lug terminal strip at the rear underside of the chassis (see Figs. 3 and 4). The filter capacitor, C11, can be wedged between the 6AU8 socket and chassis leg, or secured with a mounting clip. Two sections of this capacitor are used in the power supply

filter, the third is used as a cathode bypass for the audio stage.

Other components under the chassis, except R3, C7 and C9, mount to respective tube sockets. Capacitor C9 is connected from J2 to the grounded terminal on R5. Resistors R3 and C7 connect to a machine screw and solder lug placed between L1 and C2. One lead of L2 connects to a solder lug on the same screw on the chassis top.

The antenna trimmer, C1, is secured by the antenna terminal mounting screw as shown in Fig. 3. This component requires only infrequent adjustment, but it can be mounted on the front panel for easier access, if desired.

Inductance L1, a standard TV replacement coil, is mounted last. Before inserting the core, as explained in the manufacturer's instruction leaflet, thread on the 16-in. mounting clip and remove 1/2 in. from the slotted

Frequency (Kc.) Communications Service Sunset Skip Night DX

Radionavigation		
Fixed Public Services and Coastal-Marine CW	none	
Aeronautical Beacons and Communications	Hone	4 am
Marine Radiobeacons		to
Aeronautical Beacons and Communications	10 pm	7 am
Radio Direction Finding	to	,
Coastal and Marine CW	2 am	
International Calling and Distress Frequency	2–4 hours	11 pm
Misc. Radiobeacons	sunset	7 am
	Fixed Public Services and Coastal-Marine CW Aeronautical Beacons and Communications Marine Radiobeacons Aeronautical Beacons and Communications Radio Direction Finding Coastal and Marine CW International Calling and Distress Frequency	Fixed Public Services and Coastal-Marine CW Aeronautical Beacons and Communications Marine Radiobeacons Aeronautical Beacons and Communications 10 pm Radio Direction Finding Coastal and Marine CW International Calling and Distress Frequency after

Note: Frequencies between 150 Kc. and 535 Kc. also used by foreign

source of unusual DX. At first sight, these stations seem to offer poor DX since most are relatively low powered and have a daytime range of less than 200 miles. However, their range is greatly increased at night—best times for night DX are given in Fig. 1. These hours will vary somewhat with the seasons, with the choicest DX being heard from early fall to late spring.

Above 325 Kc. sunset skip is often heard for a half-hour during early darkness. Notable examples are PJG, 343 Kc. in the Netherlands Antilles; ASN, 350 Kc. on Ascension Island; and SWA, 406 Kc. from Swan Island.

Since beacons identify continuously or every thirty seconds, less than a minute is required to log a station. However, in order to determine the locations of the stations you TABLE B-STATION LISTS

The Airman's Guide Superintendent of Documents, Washington 25, D. C. 25¢ per copy. A bi-weekly publication listing all U. S. aeronautical radio beacons.

Location Identifiers Superintendent of Documents, Washington 25, D. C. \$1.50 for copy and one-year supplement service. General listing of all domestic beacons.

Broadcasting Stations Superintendent of Documents, Washington 25, of The World, Part 11, According to Casting stations.

Air Navigation Radio Aids

Department of Transport, Air Service Branch, Ottawa, Ontario, Canada. Complete list of Canadian Radio Beacons, published every two months.

Radio Facility Charts ACIC. USAF, 2nd & Arsenal Streets, St. Louis
—Caribbean & 18, Mo. One year subscription \$3.50. Listing of Caribbean & South American beacons.

Radio Navigational Hydrographic Office, U. S. Navy. An annual publication listing worldwide marine beacons.

List of Coast Stations Secretary General, International Telecommuni-(4.10 Swiss francs) cations Union, Geneva, Switzerland. Very com-List of Ship Stations plete listings of worldwide stations. (12.30 Swiss francs) List of Call Signs

(21 Swiss francs)

hear, you need a reference log listing the stations you are interested in. Such listings can be purchased (see Table B).

Range stations also transmit verbal weather reports for air fields in their area 15 minutes before and 15 minutes after the hour.

In addition to radiobeacons, many CW stations operate on long waves for maritime, aeronautical, and public service communication. For the CW enthusiast, these are interesting to copy and the slower stations, sometimes sending as slow as eight words a minuite, provide plenty of code practice. Many good DX signals can be heard between 415 Kc. and 500 Kc., particularly on the 500 Kc. international calling and distress frequency. The frequencies below 200 Kc. are also widely used by public service and maritime CW stations.

end of the core adjustment screw, otherwise it will protrude below the chassis when the coil is mounted. Clamp the section to be removed in a vise and cut it off with a hacksaw, then cut a new screwdriver slot. Take care not to break or fracture the fragile ferrite coil.


Inductance L2 consists of 35 turns of #26 (or smaller) enameled wire scramble-wound over a 1/16 in. ID tube which slides freely over L1. If not available, this form can be made by winding four or five layers of moist gummed tape, sticky side out, over L1. When dry, slip the tube off and trim to proper length with a razor blade. With L2 in place, secure L1 to the chassis with a bead of Duco cement.

For maximum sensitivity, the position of L2 on L1 should be adjusted for the individual receiver. This simple adjustment is well

worth the effort and can be made with a long antenna, 455 Kc signal generator, or a BCB receiver with a 455 Kc intermediate frequency. If possible, use a signal generator or BCB receiver, since this will permit adjustment of L2 and the core of L1 at the same time.

Short out L2 temporarily by connecting a short piece of wire from the R3-C7 solder lug to pin No. 7 of the 6AN8 socket. Turn the core adjustment screw full counterclockwise and connect the antenna, signal generator, or BCB receiver to the antenna terminal.

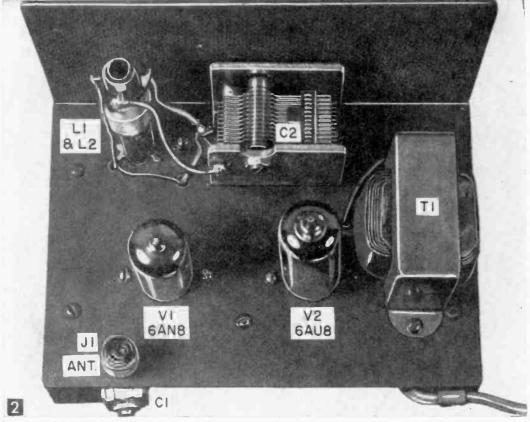If a BCB set is used, tune to a strong BCB station and turn the set's volume down. Connect a short piece of insulated wire to your LW receiver antenna terminal and place it near the underside of the BCB set's IF tube socket or IF transformer to hear the 455 Kc IF signal of the BCB receiver.



Topside of the receiver's Masonite chassis. The antenna coil, L1, is mounted so that its slug is adjusted from below the chassis.

MATERIALS LIST-LONG WAVE RECEIVER

	to 180 mmf trimmer capacitor	R10	2.2 K, 1 watt
C2 1	LO to 365 mmf variable capacitor, standard single-gang TRF type	J1 J2	antenna terminal post, or Fahnestock clip standard phone jack
C3 .0	Ol mfd disc ceramic	Li	Long Wave: Merit MWG-9 Width or Linearity coil, .3 to
	.00 mmf mica	-1	12 ma., tapped (see text)
	001 mmf disc ceramic		Broadcast: Ferri-loopstick BCB antenna coil (see text)
	500 mmf mica	L2	Long Wave: 35 turns #26, or smaller, enameled wire
C7 .0	Ol mfd disc ceramic		scramble wound on 1/16" ID x 3/2" form (see text)
	Ol mfd disc ceramic		Broadcast: 3 turns #26, or smaller, enameled wire on ad-
	0047 mfd disc ceramic		justable form (see text)
	Ol infd disc ceramic	RFC1	2.5 mh. RF choke (National R-100, or equivalent)
C11 4	10-40-40 mfd, 150 wv capacitor, 3-section electrolytic filter	SW1	on R7
R1 6	capacitor (Cornell-Dubilier BBRT 44415, or equivalent) 5.8 K, 1/2 watt resistor	Tl	filament transformer, 6.3 vct, 1.2 amp (Stancor P-6134 or equivalent)
	meg, 1/2 watt	T2	optional-for speaker use only; 5000/3.2 ohm, 3 watt, 40
	3 K. 1/4 watt		ma, output transformer. (Merit A-3026, or equivalent)
	58 K. 1 watt	Vl	6AN8
	meg, 1/4 watt volume control with SPST switch (Mallory	V2	6AU8
	U-53 Midgetrol with US-26 switch, or equivalent)	1 pc	1/8 x 41/2 x 6" Masonite (panel)
	.00 K, 1/2 watt	1 pc	a x 4 x 6" Masonite (chassis top)
R7 1	LOO K. Va watt, volume control (Mallory U-41 Midgetrol,	2 pcs	pine strip, 3/4 x 11/8 x 4" (chassis sides)

With the volume control at maximum and the regeneration control set at half-scale, place the tuning capacitor about 85% open and turn L1's core clockwise until the 455 Kc signal is heard. Adjust the regeneration control for maximum volume and mark its position. This is the detector's most sensitive

Description


point and will determine the position of L2. Remove the jumper across L2 and slide the coil up or down over L1 until regeneration (signal distortion) occurs just above the point previously marked on the regeneration control. If the detector fails to regenerate, reverse the leads on L2.

Description


Desig.

R8

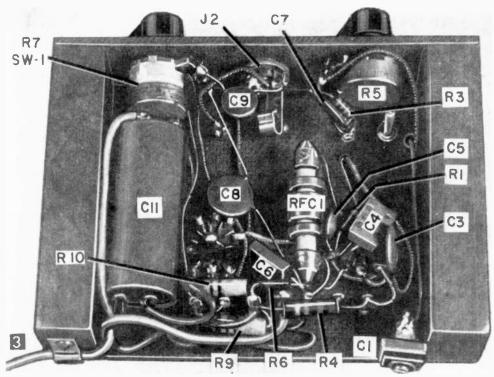or equivalent) 82 ohm, 1/2 watt 5.6 K, 1 watt



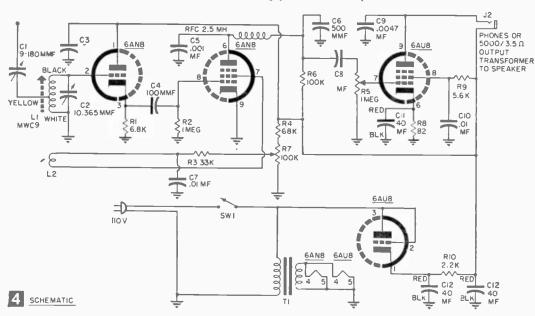
Under-chassis view, showing placement of components.



This receiver's tuning range, from 85 to 550 Kc, is covered in two adjustments of the core on L1. When set to receive 550 Kc at C2's minimum capacity, the receiver will tune down to about 200 Kc. The range from 85 to 200 Kc is tuned when the slug is almost fully inserted into L1. Overlap on both bands will

permit easy bandchanging once the operator is familiar with the stations heard around 200 Kc. On the lower band, L2 may require slight readjustment for best reception of weak signals.

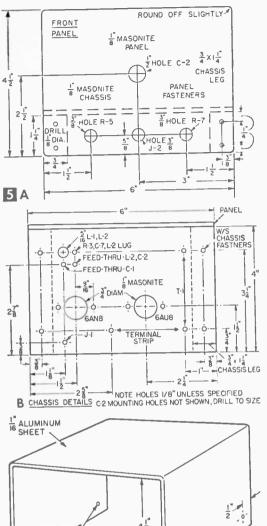For BCB reception, a ferri-loopstick is used for L1. Inductance L2 consists of three turns



W/S FASTNERS INTO CHASSIS LEG


6" INSIDE

C OPTIONAL CHASSIS COVER

and adjustment is similar to that of LW operation. The lead from C1 should be connected to the grid end of the loopstick.

A high, long-wire antenna will give best all-'round LW reception, though a short length of wire will give satisfactory local reception. Capacitor C1 should be adjusted for best reception on each band and the receiver should not be grounded.

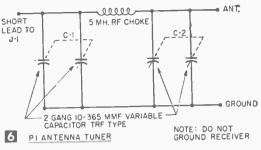In some localities, interference from strong BCB stations may be bothersome, a trouble commonly encountered with LW receivers having only a single tuned circuit. Such in-




terference can be minimized by reducing the antenna coupling or, in severe cases, by the use of the simple Pi antenna tuner (shown in Fig. 6). The tuner can be built on a small pine block. Adjust C1 and C2 for minimum BCB interference.

Four or five feet of hookup wire is sufficient antenna for BCB reception. The receiver will give good loudspeaker volume on the BC band and on the stronger LW stations. Due to the low power used by most LW stations, however, headphones are recommended for serious LW listening. For speaker operation plug a 5000-3.5 ohm, 3-watt, output transformer into J2.

Inverted Brush Cleans Gun's Tip

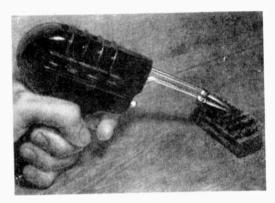• To keep the tip of your soldering gun clean of scale, woodscrew-fasten a brass-bristle suede shoe brush to one end of your workbench. Wipe the soldering-gun tip across the brush occasionally to keep it clean for efficient soldering.—J.A.C.



Why Inside Gun-Tip Care?

• To receive maximum soldering efficiency and long-tip life, be sure that cleaning and tinning operations of your soldering gun's tip also include the *inside* surfaces of the tip. A gun's tip that is maintained on the outside, but allowed to deteriorate on the inside, is sure to give lowered soldering efficiency and it will shorten tip life.

Versatile Code Practice Equipment

By HOWARD S. PYLE

HE teaching of code to a group of students is made easy with this control unit. The control unit (Fig. 1) with connections to a key and an ac supply line, is a keved audio oscillator of variable tone and volume, with the resultant tone reproduced in a loud speaker with sufficient audibility to handle a group of up to thirty students.

The control unit is housed in a Hamcab #12. Layout the front panel, chassis and the rear panel according to Fig. 2 and cut the holes for the components. Several holes in the sides of the cabinet are also required. Mount the components (see Materials List). Wire the

unit according to the schematic, Fig. 3. The isolation transformer is mounted inside the cabinet.

When you have completed the control unit and have selected a space for the students' table (Fig. 4), make the table of plywood, suitably supported. Wire the table in accordance with schematic (Fig. 5) and Fig. 6.

Through the plug P-1, provided on the table cord, connect the table wiring to the instructor's control unit through the multi-terminal jack, J-2. With the instructor's switch S-2 in the LOCAL position, the audio oscillator is keyed and the reproduction emanates from the loud speaker. All of the table circuits are now connected to the control unit through the cord and plug. Any student whose toggle switch SX is placed in the A position, now has his key in parallel with the instructor's and he, too, may then key the oscillator.

One or all students may be so switched in through their SX switches and have keying control of the oscillator, with loud speaker reproduction. The instructor may then send to all students or work with any one or more students two-way, with the rest of the class monitoring.




This control panel is a versatile aid in group code instructions.


Any two or more students may work each other, simulating on-the-air operation and, as the reproduction is still from the loud speaker, the remainder of the class may still monitor all sending and, if desired, may break in on the communication as can the instructor

Now let's throw the instructor's switch S-2. to the REMOTE position. This immediately disconnects the loud speaker from the circuit and at the same time shorts the instructor's key, thereby producing a continuous, steady audio tone which is fed through J-2 and P-1 to the tables and made available to all students through their keys and head telephone receivers, provided each student has thrown his toggle switch SX to the B position. The second switch S at each student position, if all thrown to the ON position, will parallel all positions, and the same conditions existing when the instructor's switch S-2 was in the LOCAL position will appear except that reproduction will now be in the head telephone receivers rather than through the loud speaker.

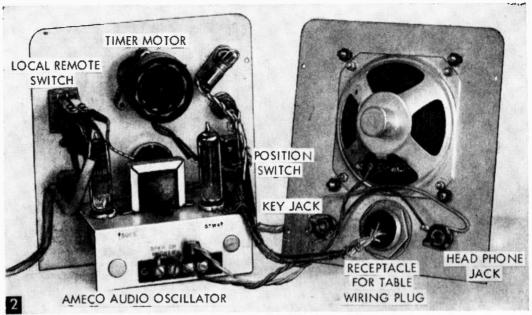Suppose now that we leave the instructor's switch, S-2, in the Remote position and that



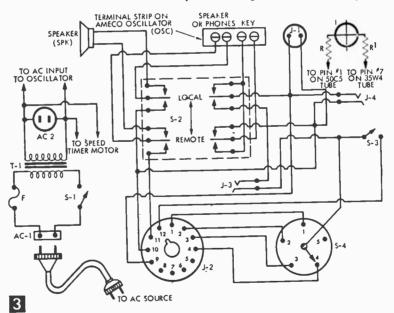Parts layout and wiring of instructor's control panel



all student switches S are placed in the open position. Each student may then practice sending by himself with reproduction in only his own headphones and without interfering with any other student who may be engaged the same way. In other words, each and every student may conduct sending practice and listen to himself in his headphones while all other students are doing likewise simultaneously and with no inter-position interference.

Now, suppose student #2 wants to work

two-way with student #3 at the same time that all of the others are engaged in independent individual sending practice. Student #2 need merely throw his switch S to the ON position which will parallel him with student #3 and they may then work together without causing or receiving interference from any of the others! Perhaps student #4 wants to join this group (#2 and #3). He merely asks student #3 to close his S switch to the ON position and he, too, is in!

Student #1 may come in also, if desired, merely by closing his

S switch to ON.

And the instructor may listen to any individual student, any pair or more who may be working together and may break in on any position or any group of paralleled positions by merely placing his monitor position selector switch S4 on the single position he wishes to monitor or work, or to any of the positions which are paralleled.


The speed timer is a standard electric clock movement and motor—in this case a new Telechron from one of the mail order

electronic supply houses (cost \$1.95) without hands or face. The octagon shaped dial shown in the photos is made by removing the clear plastic cover from a box of dressmaker's pins purchased at the local variety store. Give it a coat of black enamel and fit small white decals, procurable at any amateur radio supply store, to indicate the 15, 30, 45 and 60 second points. A light strip of aluminum is cut and fitted to the central shaft of the clock driving mechanism or a standard sweep hand may be procured from a local watchmaker. This makes one revolution every 60 seconds; five times around equals five minutes and enables the instructor to time code speed.


The audio oscillator is an Ameco or other brand purchased in kit form and the cabinet discarded after removing the speaker. Unfortunately these oscillators are of the ac-dc type and require installation of a small 1/1 ratio isolation transformer on the inside of the control cabinet, feeding the oscillator,

clock motor and an ac outlet from the secondary side and with the primary connected externally to the 115 ac line through the power switch and fuse on the control panel. The ac outlet AC-2, of conventional chassis mounting type, is installed on the side of the cabinet to provide a convenient point at which to plug in the ac supply to an automatic tape transmitter, if one is used. If you use a tape transmitter (such as Instructograph) the contacts of the tape transmitter are paralleled across the instructor's key through a two conductor cord and plug with a matching socket mounted on one side of the control cabinet.

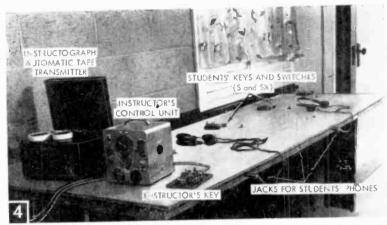For the indicator lamp (I) use an NE-51 neon bulb connected through a 47 K resistor



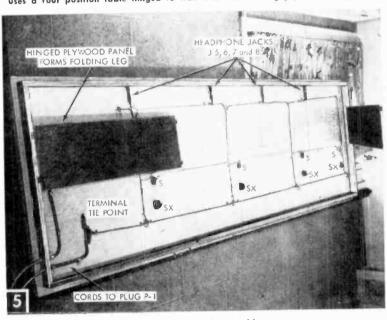Complete equipment as set up in the author's home class-room. This arrangement uses a four position table hinged to wall and with folding plywood wing legs.



Wiring of the students' table.

in each leg, to pin 1 of the 50C5 tube and to pin 7 of the 35W4. The NE-51 element will not fire until the neon gas has become sufficiently heated, which will take a few seconds. Conversely, the bulb will also require a few seconds to extinguish after the ac switch is placed in the off position. This is an added safety factor in that the false indication that the unit is still hot allows any stray high voltage in the oscillator to bleed off before you touch exposed terminals.

If, due to use of high impedance headphones (2000 ohms) with the oscillator, there is an annoying undertone of audio feed-back when unkeyed, place a 670-ohm (not critical value) 1/2 watt resistor across each headphone jack.

MATERIALS LIST—GROUP CODE EQUIPMENT INSTRUCTOR'S CONTROL UNIT Design. Description AC-2 T-1 110 V. AC chassis type receptable (Amphenol 61-F) 115/115 V. isolation transformer (Triad N-51X) panel mounted fuse holder, insert type (Buss H-CP) panel mounted fuse holder, insert type (Buss MAP)
SPST bat-handled toggle sws. (Cutler-Hammer 8098)
recessed 115 V. AC plug (Cinch-Jones 2RP)
4" PM dynamic speaker (incld. in Ameco oscil. kit)
code practice oscillator (Ameco CPS-KL Deluxe)
locking type lever switch (Switchcraft 60012-L)
open circuit phone jacks (Mallory LA-1 Midget) S-1/S-3 AC-1 5PK OSC J-3/J-4 1.2 terminal Jack (Amphenol Military type AN up to 8 students or Cinch-Jones Series 300) single contact, male microphone receptacle. Insu-late from cabinet with extruded fibre washers. (Walsco 1882 or equivalent) 5.4 rotary switch (Mallory 3215J for 4 students, 32112J for 8 students) Jewel light assembly with NE-51 neon bulb (Drake 10)

ATK-ohn resistors, 1/2-watt

Cabinet with chassis—mount chassis upside down
in cabinet to form rigid base plate. (Hamcab 12,
L. M. Bender Co., 2528 W. 9th 5t., L. A. 6, R-R1


Calif. or supplier) SPEEDTIMER Telechron electric clock motor with sweep hand PRACTICE TABLE EQUIPMENT (FOR 4 STUDENTS)

P-1 plug to match J-2 on Instructor's control unit. SPST toggle switches-1 for each student (Cutler-Hammer 8098)

SPDT toggle switches—1 for each student (Cutler-Hammer 7140) Sx KFY5

military surplus or builder's choice midget open-circuit phone jacks (Mallory LA-1) J-5, J-6, etc. 670-ohm, 1/2-watt swamping resistors, one for each

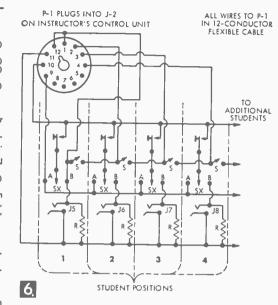12-conductor (for up to 8 students) flexible cable to reach from table to J-2. Conductors may be unshielded. (Belden 8747 intercom cable)




Wiring for one four-position table; additional tables are wired identically.

Fast Turn for Large Knobs



 When the turning ratio of a large knob on a receiver is too slow, a rubber suction cup will solve the problem. Place the cup directly in the center of the knob and use it as an additional knob for fast tuning. A bottle-cap force-fitted into the cup (or over the cup) will make turning easier and improve appearance.-J. A. C.

Stickers Solve Tape Troubles

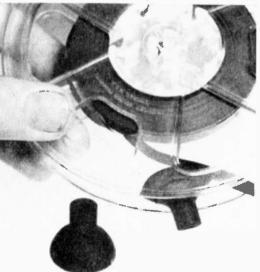

 Need a good pair of recording tape spool locks for your tape recorder? A pair that isn't easily misplaced when not in use? Two medium-size rubber suction cups—the type with open tops—are ideal for this purpose. The cups are easy to slip over the spindles to hold the spools, or they may be used as wedges to hold tape on the spools. When they aren't in use, you can store them neatly on the tape deck by means of suction. They might be used this way as holders for your regular spool locks.-J. A. C.

CABLE

ELECTRONIC NUMBERGRAM

By JOHN A. COMSTOCK

THIS puzzle is especially for those electronics hobbyists who are fascinated by numbers and calculations. This should keep you busy the rest of the day! When you have worked out the problems presented by the clues, and filled in the right numbers, turn to page 158 for the solution.

ACROSS

- Year Hertz proved radio possible.
- 4. Frequency in Citizens Band set aside for radio-telephone.
- Maximum efficiency commonly obtained in actual practice when an amplifier is operated class B.
- 8. Last TV channel in UHF group.
- 9. Wire left on 1000-ft. spool after you have run a line 300 ft. long.
- Frequency of a parallel tuned circuit tuned to 3600 kc after inductance has been reduced by half and capacitance doubled.
- Lowest useful frequency in radio spectrum for accurate and reliable communications (in kilocycles).
- Second harmonic of a 400-meter wavelength signal, expressed in kilocycles.


- 14. Voltage across a capacitor that has been connected to a source of 100 volts, then removed and connected in parallel with another capacitor of the same value.
- 16. Largest AWG wire gauge.
- 17. 2.71 x 10-6 henries expressed in microhenries.
- 19. Image frequency of a superhet when tuned to 1450 kc and IF is 465 kc.
- 21. Total capacitance of three capacitors—
 4, 6, and 12 microfarads connected in parallel.
- 23. Third harmonic of 5 kc.
- 25. Voltage drop across series resonant circuit when capacitive reactance and inductive reactance are 175 ohms each, resistance is 65 ohms, and applied voltage is 248 volts.
- Width of commercial FM broadcast channel in kilocycles.

- 27. Inductive reactance of a 2-henry choke at a frequency of 3000 cps.
- 29. Amount of resistance in ohms when a voltage of 100 volts will maintain a current of 10 amps.
- 30. .000005 amp converted to milliamps.
- 34. The number of years required for radium to lose onehalf its energy.
- 35. Decimal multiplier used when you have the peak value of a sine wave, but want to find the average value.
- 36. Velocity in kilometers of a 20-mc signal having a wavelength of 15

DOWN

- Received signal frequency of a superhet when IF is fixed at 176 kc and mixer oscillator is cperating at 1586 kc.
- 2. Dah-dah-dah-dit-dit, dah-dah-dit-dit, dah-dah-dah-dahdah.
- 3. Second harmonic of 300 kc.
- Xc of a .01-mfd capacitor at a frequency of 3000 cps.
- .080 millihenries expressed in microhenries.
- Cutput frequency of a 5-mc transmitter expressed in kilocycles.
- Lower limit of medium-frequency band in kilocycles.
- 11. .0006 microfarads converted to micro-microfarads.
- 14. Total resistance of 15 ohms, 30 ohms, and 5 ohms, connected in series.
- 15. Color burst frequency in megacycles.

- Oscillator frequency in kilocycles of a transmitter having an output signal of 16880 kc and three doubler stages.
- Number of equalizing pulses transmitted per field in monochrome TV.
- Wattage reference level in watts of 0 decibels.
- 21. Number of joules in 24-watt seconds.
- 22. Radiated output in watts of a station when transmitter output is 1 kilowatt, line loss is 50 watts, and antenna power gain is 3.
- 24. Theoretical field strength in mc per mile at 200 miles when 100 mc per mile is measured at 100 miles.
- 25. Applied voltage when two resistors are connected in series, the value of one 50 ohms, the other with a voltage drop of 50 volts; current flow is 3 amps.
- 26. Value of negative bias on a tube when grid resistor is 2000 ohms, grid current 10 milliamps.
- 27. Upper limit in megacycles of UHF band.
- 28. Wavelength in meters of a 4-mc transmitter signal.
- Year radar was first used to make contact with moon.
- 31. Current flow in amperes when a resistor drops a voltage of 10 volts and the power dissipated is 270 watts.
- 32. Total number of electrical degrees that plate current flows in α class "A" amplifier.
- 7 x 10² micromicrofarads in ordinary notation.
- 34. Value of a resistor color-coded brown, blue, black.

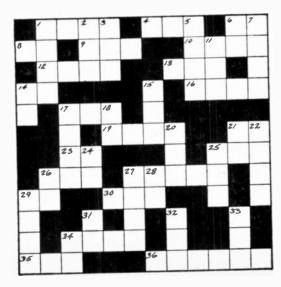


Experimentally Determining the Velocity of Sound

This experiment may be performed with equipment available to physics students, or by the home experimenter with a preamp, AC voltmeter and audio signal generator


By FRANK WOODS, Jr.

OUND is propagated by longitudinal waves consisting of alternate compressions and rarefactions of air as shown in Fig. 1b. If a sine wave of voltage (solid line Fig. 1c) is applied to the terminals of a loudspeaker (an electrical to sound transducer). the air in front of the speaker will have the pressure distribution shown in 1b at a given instant of time. The pressure at a given point will of course vary with time, and a microphone or speaker placed at that point will react to these changes in pressure. This reaction to the pressure will produce a waveform of electrical voltage at the terminals of the microphone or second speaker that is a copy of the solid line of Fig. 1c, except that it will be smaller in magnitude and will be displaced in time, as shown by the dotted line in Fig. 1c.

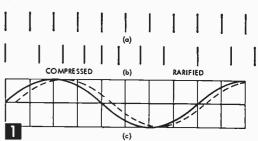If a source speaker and receiver speaker are a whole multiple of one wavelength apart, the receiver waveform will be in time with the source speaker signal. The measurement of this distance would be difficult to perform accurately. A wavelength — the distance



- The normal positions of particles of air (a) are changed upon becoming the carrier of a sound wave—they are alternately compressed and rarifled (b). If the sound source is a speaker producing a wave represented by the solid line in (c), a receiver speaker would receive a copy of this wave slightly later (dotted line).
- Lissajous figures for two voltages of same frequency. The angles given refer to the differences in phase between the vertical and horizontal input voltages where 1 cycle time is considered equal to 360°.
- Oscilloscope method for determining the velocity of sound. Transformer cores are connected to common connection to minimize hum pick-up.

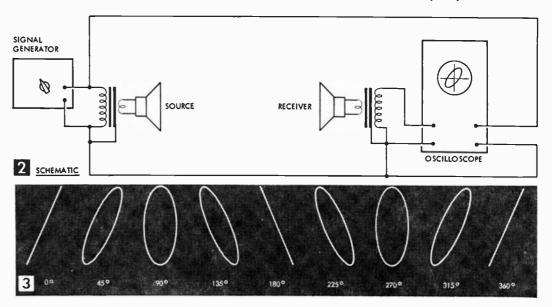

through which a cycle of sound is distributed at a given instant of time-may be determined more accurately in another way. A cycle corresponds to a complete excursion from nominal to maximum to nominal to minimum to nominal air pressure. Suppose the position of the receiver speaker relative to the source speaker is adjusted for a given time relationship between source and receiver voltage. If the receiver speaker is moved away from the source speaker the time relationship will change, till at some new position the voltage waveforms of source and receiver voltage bear the original time relationship. The distance that the receiver must be moved to attain the original time relationship is a wavelength.


The relationship between the velocity of sound (v), the frequency (f), and the wavelength (w) is v equals fw. Thus, if wavelength and frequency are known, the velocity of sound in air may be computed. An audio signal generator may be used as a sinusoidal voltage source speaker driver. The frequency may be read from the signal generator dial. Wavelength may be determined by the method described in the previous paragraph.

All that remains is to find the time relationship between source and receiver signals.


There are two good methods of determining the time or phase relationships between two voltages of the same frequency. One of these methods requires an oscilloscope and employs Lissajous figures. The other employs an ac voltmeter in a comparison circuit. Since the receiver voltage is small, an audio millivoltmeter such as the Heathkit AV-3 or an amplifier driving an ac voltmeter should be employed if the latter method is used. (The "Hi-Qual Preamp," ideal for this experiment, appeared in Radio-TV Experimenter #569 available from Science and Mechanics, 505 Park Ave., New York 22, for \$1 including postage and handling.

Oscilloscope Method. The experiment is diagrammed in Fig. 2 and shown visually in Fig. 4. The loudspeakers may be inexpensive ones such as the 4-in. Lafayette SK-25. The transformer secondaries should match the speaker voice coils and the primaries may have any impedance value from 2K to 25K. A high impedance is preferable for the receiver circuit since the transformer is reverse connected and a voltage step-up results. The Stancor A3327 (25K to 4 ohms) is an excellent choice. If an audio signal generator which does not have sufficient power output to drive the speaker audibly is used, connect an audio amplifier between the signal generator and the source drive transformer. Connect the receiver transformer input to the vertical input of the oscilloscope, and the source signal to the horizontal input.

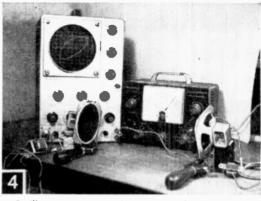Fasten the speakers in hand vises and support them at the same height. Set the signal



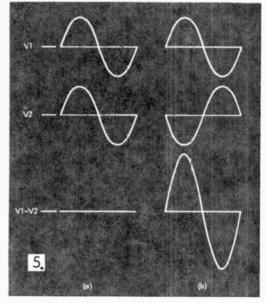Oscilloscope set-up for determining velocity of sound.



In the meter method, V1 and V2 in phase result in minimum voltmeter reading (a), while V1 and V2 180° out of phase (b) give maximum voltmeter reading.

generator for 500 cycles and adjust the output till an audible signal comes from the source speaker. Adjust the oscilloscope controls to display the Lissajous figure. Move one of the speakers relative to the other till the 0° waveform of Fig. 3 is observed. Measure and record the distance between the speakers, in ft. Now increase the distance till the 360° waveform of Fig. 3 appears Measure this distance, and subtract from it the first distance, which gives the wavelength of the signal. The velocity of sound in ft./sec. may then be computed from v=fw.

The velocity of sound is known to be 1,054 ft./sec. plus $1.1 \times$ the temperature in degrees F. Thus, in a room at 70° F, the velocity of sound is 1,131 ft./sec. The accuracy of the experimental results may then be computed:

$$\% \text{ error} = \frac{v - v'}{v'} \times 100\%$$

where v is the experimental value and v' is the known value.


The author's experiment produced fairly accurate results. The wavelength at 1000 cycles was 1.167 ft. Thus v was 1,167 ft./sec. The room temperature was 80° F. The value of v' therefore was 1,142 ft./sec. The error was +2.2%. The experiment was repeated with the signal generator set at 500 cycles. The measured wavelength was 2.29 ft. The slide rule computed value of v was 1145 ft./sec. The error was 0.26%. Note that the accuracy improved considerably when a longer wavelength was involved.

Meter Method. The difference of two sine waves of equal amplitude and frequency for 0° and 180° phase relationships is shown in Fig. 5, and this leads to a method of finding sound wavelength with more common equipment. Either an audio millivoltmeter or an ac voltmeter is needed, the latter requiring an amplifier such as the "Hi-Qual Preamp," referred to earlier, as a driver. The value of voltage which an ac meter will


read does not give an indication of phase relationships. But, since the value which the meter will indicate is a function of peak value, the differencing principle may be employed to determine phase relationships. The schematic is shown in Fig. 6 and the set-up in Fig. 7.

The signal generator drives the source loudspeaker. A 1K potentiometer (R), in the original apparatus a Clarostat 58C1-1000, is connected across the signal generator output. Its purpose is to allow the adjustment of the voltage between the slider and the common connection to the receiver to be approximately equal to the voltage at the output of the preamp. This is accomplished by measuring the voltage across the preamp output with the voltmeter and then connecting the voltmeter across the potentiometer to make the adjustment of R. The two sets of connection terminals for this adjustment are designated M1 and M2 in Fig. 6. After this adjustment has been made the meter is connected in the circuit as shown.

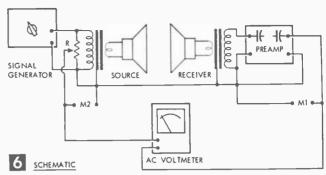With the meter connected as shown in Fig. 6, receiver and source voltage buck each other (subtract). This process causes the meter to read minimum voltage when both voltages are in phase (5a) and maximum voltage when both voltages are 180° out of phase (5b). Thus, the receiver speaker is moved through



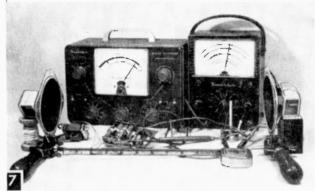Schematic for determining velocity of sound with an ac voltmeter.
(If audio millivoltmeter used, preamp not needed.)



Set-up for voltmeter method of finding speed of sound.


one wavelength when the meter indication goes from min to max to min or from max to min to max. The distance measurements, frequency used and the computations are the same as those required with the oscilloscope method.

Shockproof Switch Covers



To avoid any possible shock from the bathandles of toggle switches, place plastic test-clip insulators over them. These insulators are also good dust covers to prevent particles of metal and other foreign materials from entering the switch mechanism.

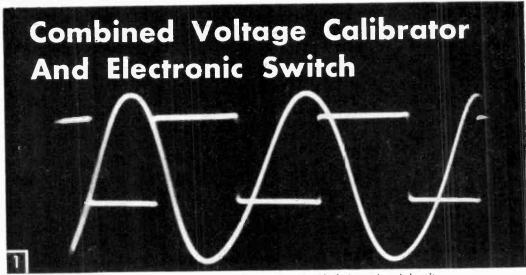The covers enable one to throw the switch safely and easily, and to distinguish from tilt, whether the switch is on or off.—J. A. C.



Sine and square wave seen simultaneously with aid of electronic switch unit.

Single unit multiplies oscilloscope usage

By W. F. GEPHART


THE unit shown in Fig. 2 combines two useful 'scope accessories: 1) an electronic switch which permits viewing of two signal patterns simultaneously (Fig. 1), and 2) a voltage calibrator, allowing the 'scope to be used for ac voltage measurements. The first accessory, the switch, permits both the input and output of an amplifier to be viewed together to check fidelity, for example. The second accessory, the voltage calibrator, gives the magnitude of a signal as the wave form is viewed.

Our unit has a special switching system that permits the calibrated voltage signal to be one of the signals seen simultaneously.


An electronic switch switches signals so fast that both images appear on the oscilloscope together, due to the persistence of the cathode ray tube. A multivibrator type oscillator switches amplifier tubes "on" and "off" so they conduct alternately. Separate signals are fed into each amplifier tube, whose output is common. This output is actually both signals, presented alternately.


Figure 3 shows the schematic, in which V1 is a twin triode multivibrator. It generates square waves, with frequencies between about 20 and 2000 cycles, as set by SW1 and R15, the frequency controls. The multivibrator drives the grids of a second twin triode (V2), which acts as a switching tube. The two plates of the multivibrator are connected to the two grids of the switching tube. Since the signals on the plates of V1 are 180° out of phase, the two halves of V2 conduct alternately. The output of the multivibrator is a square wave and quite high. Thus, when the

plate of V1a is positive, the grid of V2a is positive and V2a conducts. At the same time, the plate of V1b and grid of V2b are negative,

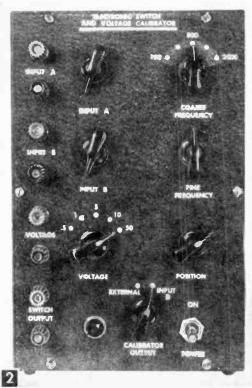

Front view of the completed unit.

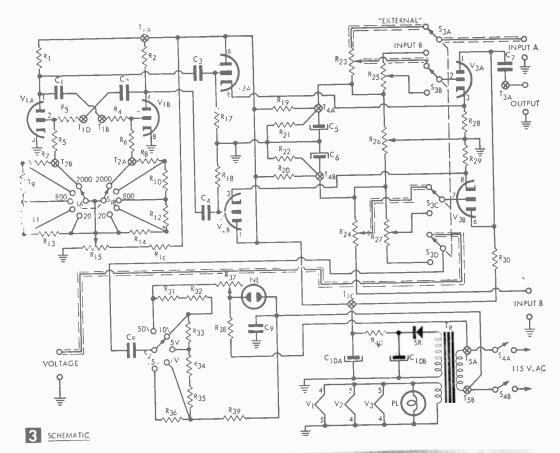


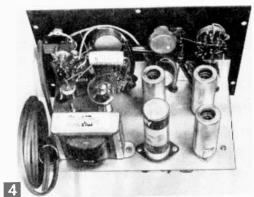

Back-of-panel view shows miniature pots mounted by stiff wire leads.


which prevents V2b from conducting. At the half-cycle point, the situation instantly reverses (since the multivibrator is a square wave generator), and V2b conducts and V2a cuts off.

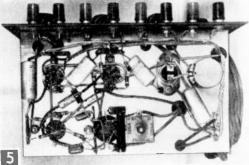As the two halves of V2 alternately conduct, the current they draw flows through the cathode resistors (R28 and R29) of V3a and V3b. The twin triode amplifier (V3) is two ordinary amplifiers, biased at a normal op-



Under-chassis view shows shielded lead attached to common negative lead of binding posts.

erating point by cathode bias. If the cathodes of the switching tube were not connected to their cathodes, both halves of V3 would amplify equally. However, as the two halves of V2 draw current, this current flowing through the related cathode resistor of V3a or V3b biases that half of the amplifier tube (V3) to cut-off. In this way, the two halves of the amplifier tube (V3a and V3b) are alternately switched on and off at a rate equal to the multivibrator frequency. Therefore, the two input signals take turns appearing at the out-

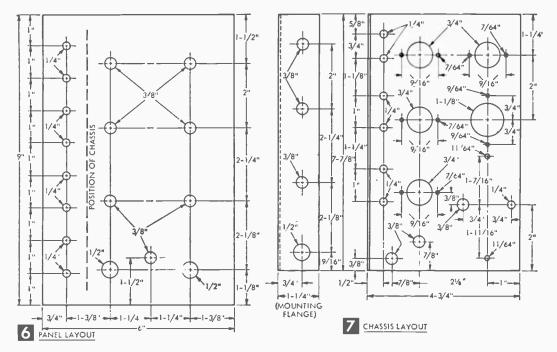

put terminals. But, due to the persistence of the fluorescence of the CR tube and the rapid switching rate, both signals appear on the CRT at the same time.

By adjusting the dc potential of the grid of the amplifier tubes, the position on the CRT screen of each signal can be changed. This is done by having a dc voltage from twin voltage dividers R19-R21 and R20-R22 across potentiometer R26 (Position). Adjusting this control varies the voltage on each grid by changing the grounding point.

The voltage calibrator section uses a neon bulb to get square waves at line voltage frequency. Neon bulbs ignite at a certain voltage, and if a resistor is connected in series with the bulb, the voltage drop across the bulb will be constant. The ignition voltage of the NE32 bulb used is approximately 60 v., and gives square waves of 60 v. in this circuit. On the positive half of the cycle, the voltage increases until the ignition point (about 60 v.) is reached. The tube then fires, and starts drawing current. As the voltage increases, more current is drawn, but the voltage drop across the resistor in series with the tube (R38) holds the voltage across the tube constant. As the voltage passes the peak and decreases below the ignition point, the bulb goes out, and current stops flowing through the resistor. The voltage drop across the tube then follows the pattern of the cycle, and the process is repeated on the negative half of the cycle. In this way, fairly good square waves are obtained.

The ignition voltage is reduced to a reference level by R37, and subsequently divided


for other ranges by R31 through R35. For oscilloscope use, these levels are usually set at peak-to-peak values rather than the RMS values shown on meters.


Switch S3 and potentiometers R25 and R27 permit the output of the calibrator to be used as one of the electronic switch inputs. The usual method of using a calibrator is to note the height of the calibrator pattern, remove it and connect the signal to the 'scope, and compare the heights of the patterns. By switching the calibrator output into the electronic switch, the calibrator voltage pattern remains on the screen to be compared directly with the signal pattern.

Potentiometers R25 and R27 are required to keep conditions constant when using the calibrator through the electronic switch. If the calibrator were fed directly into Input-B terminals, the output of V3b would vary with the setting of B-gain and the amplification of V3b. Potentiometer R27 is set so the output of V3b is equal to the input.

Since the magnitude of the signal to be measured must not be altered in this case, potentiometer R25 is set so that the output of V3a is equal to the input, making it a 1:1 amplifier. This prevents the electronic switch from affecting the magnitude of the signal whose voltage is to be measured by comparing it with the calibrator signal.

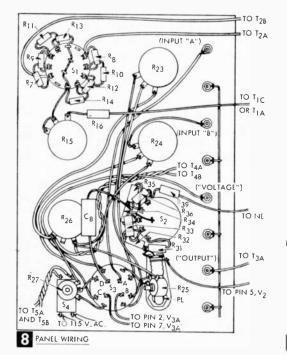The unit is built on a vertical arrangement to minimize bench space required, as shown in Figs. 4 and 5. The panel and chassis layouts are shown in Figs. 6 and 7, with pictorial wiring shown in Figs. 8 and 9. Notice that R25 and R27 are miniature units, supported



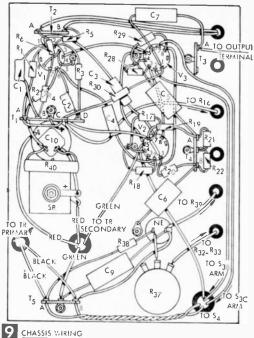

by stiff (#16) wire leads.

The power supply and filaments are wired first, followed by the neon bulb circuit. In mounting resistors on the voltage switch (S2), be sure they will clear the neon bulb. No particular care is required in wiring, except that certain leads (as shown on the schematic) should be shielded, and care used that the grounded shield does not short out any terminals.

After wiring, output of the calibrator must be set. Connect a vacuum tube voltmeter between R37 and ground, and set the voltage switch S2 on 50. Calibration should be for peak-to-peak voltages, so the reading on the VTVM should be .3535 of the values shown on S2. Turn the unit on, and adjust R37 so the voltmeter reads 17.7 v., which is .3535 of the 50 v. indicated on S2. Due to the divider, other readings will be appropriate.

Next, potentiometer R27 should be set. With Calibrator Output S3 on External, set Voltage S2 on 5, and connect the Voltage terminals to the vertical input of the 'scope.

MATERIALS LIST—'SCOPE CALIBRATOR AND SWITCH (All resistors 1/2 watt and 10% unless shown)

Desig.	Description	Desig.	Description
R1, R2	51K, 5%	C1, C2	.001 mfd., 200 v.
R3, R4	12K	C3, C4	.047 mfd., 200 v.
R5, R6	.22 meg.	C5. C6	25 mfd., 25 v. electrolytic
R7, R8	1 meg.	C7, C8, C9	.5 mfd., 200 v.
R9, R10	3.3 meg.	C10	40-40 mfd., 150 v. electrolytic (Mallory FP-221 or
R11, R12	4.3 meg., 5%		equiv.)
R13, R14	5.1 meg., 5%	S1	2-pole, 5-pos. rotary switch (Coarse Freq.) Mallery
R15	.1 meg. potentiometer (Fine Frequency)		3226J
R16	.15 meg.	S2	1-pole, 5-pos, rotary switch (Voltage) Mallory 3215J
R17. R18	.1 meg.	S3	4-pole, 2-pos. rotary switch (Calibrator Output)
R19, R20	.33 meg.		Mallory 3242J
R21, R22	15K	\$4	DPST toggle switch (Power)
R23, R24	.1 meg. potentiometer (Input A and Input B)	PL	6.3 v., .15 amp. pilot light (#40 or #47)
R25, R27	1 meg. miniature potentiometer (Clarostat Series 48)	SR	65 ma. selenium rectifier
R26	50K potentiometer (Position)	T	power transformer, 120 v. @ 50 ma., 6.3 v. @ 1 amp.
R28, R29	1000 ohm		(Merit P-3045)
R30	33K, 1 watt	NE	NE 32 neon bulb
R31	68K, 1%	V1, V2, V3	
R32	12K. 1%		5 x 6 x 9" utility cabinet (Bud CU-1099)
R33	10K. 1%		three 9-pin miniature sockets
R34, R35	4K, 1%		neon bulb socket
R36, R39	1K. 1%		pilot light holder
R37	50K potentiometer		8 binding posts
R38 R40	10K		7 knobs
N40	250 ohm, 10 watt, wirewound		miscellaneous hardware

Turn both units on, and adjust the vertical gain control on the 'scope to give a pattern of convenient height, and note the height of the image on the CRT. Do not touch the vertical

gain control on the 'scope after this.

Move the leads from the 'scope to the Output terminals, set Frequency controls S1 and R15 to mid-position, and adjust Position R26 so a single trace appears on the CRT. Switch Calibrator Output to Input-B and adjust R27 so that the trace height on the CRT is the same as the voltage trace height found above. Seal R27 shaft with nail polish.

To set R25, feed a low gain signal from an AF oscillator or other unit into the vertical input of the 'scope, adjust the vertical gain for a convenient height, and note the trace height. Then connect the 'scope to the Output Terminals instead of the signal source and adjust the Position control to get a single


trace on the CRT.

Remove the neon bulb and set S3 to Input-B. Connect the AF oscillator to Input-A terminals, and adjust R25 to give the same trace height as given when the signal was connected directly to the 'scope. Seal R25 shaft with nail polish and replace the neon bulb.

It will be found that adjustment of the position control will affect signal magnitudes somewhat, so the voltage calibrator section

Improved Razor-Blade Detector

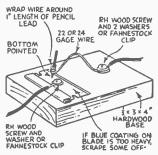• Here is a more rugged version of the familiar foxhole razor-blade "crystal" detector. The original was a piece of pencillead bridged across the edges of two razor-blades and sometimes used by G.I's in fox-



holes to pick up local broadcasting stations. This was fairly sensitive, but it was very difficult to hold an adjustment, as the least vibration or jar caused the lead to rock and roll on the blade edges, resulting in erratic and noisy reception. For the arrangement shown, blue 'steel single edge or double edge blades (such as *Pal* razors) seem to be the most sensitive, but many other blades also have sensitive spots on them. Use with a conventional circuit and a good antenna and ground.—Arthur Trauffer.

Removing Enamel Wire Insulation

• To remove enamel insulation on magnet and hook-up wire quickly and cleanly, wrap a piece of sandpaper around the wire and give a twisting, rotary motion.—E. L. Burner.


should be used through the electronic switch section only when approximate results are sufficient. When using the unit in this manner, the Position control should be set so the signal pattern is superimposed over the voltage calibrator pattern, and ready comparison can be made. Also, most accurate results can be obtained when the two signals are superimposed. For more precise work, the electronic switch section is not used. Output from the Voltage terminals is connected to the 'scope, the vertical gain set, and trace height noted. The leads from the Voltage terminals are removed, and the signal is then connected directly to the 'scope. A comparison of the trace height produced by the signal, with the noted height of the voltage calibrator trace will then give a precise peak-to-peak voltage measurement.

In using the electronic switch, the two signals to be viewed are connected to Input A and Input B, and the Output is connected to the vertical input of the 'scope. The frequency controls of both the 'scope and the electronic switch are adjusted for proper frequency and the gain controls on the switch adjust the individual trace heights. By use of the Position control on the switch, the two patterns can be shown separately or superimposed (as in Fig. 1).


Pointed-End for Radio Ground Pipe

• A simple pointed end makes it easier to drive a radio ground pipe. Insert the lathe-turned point into the bottom end of the pipe to keep dirt from plugging the pipe. Holes drilled through the pipe for soil wetting reduce electrical resistance between ground pipe and soil.—ARTHUR TRAUFFER.

Solderless Tube Sockets

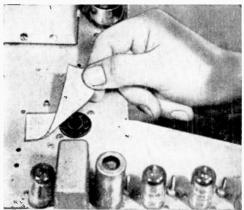

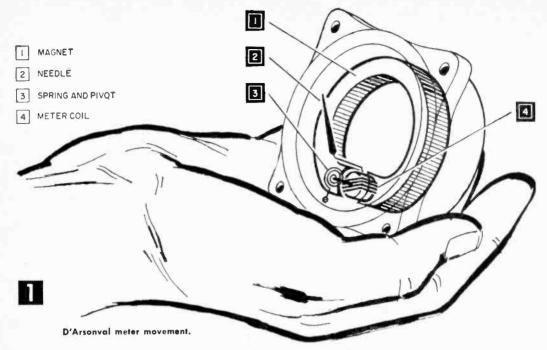• When soldering on top side of radio or TV chassis, dropping solder in an open tube socket can cause trouble. Eliminate this possibility by placing a strip of wide adhesive tape over the open socket.—H. LEEPER.



Meters and Multimeters

By FORREST H. FRANTZ, SR.

THE type of meter we are concerned with has an electromagnetic mechanism known as a d'Arsonval movement. From it I'll show you how to make voltmeters and ammeters and ohmmeters.

How Meters Work. The d'Arsonval meter (Fig. 1) contains a permanent magnet, a coil that is free to rotate about its pivot axis, a needle attached to the coil and a spring that resists displacement of the coil from zero and tends to restore the coil to zero.

The torque that causes the coil to turn is developed when a current passes through the meter coil. The amount is proportional to the current passing through the meter coil. The coil and needle are supported by low friction bearings so that mechanical resistance is low. The pole pieces conduct the flux from the magnet poles and the circular iron core over which the coil rotates. This core and the curved pole piece faces assure that the magnet's flux is always cutting the coil windings at right angles.

The most common basic d'Arsonval meter movement is the 0-to-1 milliampere dc meter.

Designing Your Own Meter Instruments. Assume for simplicity in the examples, that all of the work is being done with a 0-1 ma. meter. The resistance of the meter, if not

known, can be determined by the circuit of Fig. 2. Adjust pot R, which is connected as a high resistance rheostat, for full scale meter deflection. Connect shunt RS across the meter terminals, and adjust it until the meter deflection is reduced to half scale. The resistance to which RS is adjusted is the resistance of the meter movement. The resistance of RS may be measured with an ohmmeter or Wheatstone bridge.

Once you know the basic movement (I_m) and the resistance (R_m) of the meter, you can increase the current range with a shunt resistance $(R_s$ in Fig. 3.). The value of the shunt resistance for a new range is determined using these formulas:

(a) $I_s = I - I_m$


(a)
$$I_s = I - I_m$$


(b) $R_s = R_m \left(\frac{I_m}{I_s}\right)$

You can buy a 1% shunt resistor, or you can make the shunt by winding insulated resistance or magnet wire on a form, such as a matchstick or a Bakelite bobbin. Or you can use a rheostat, adjust it to the proper resistance, and lock it with a cement seal between the shaft and bushing. Most shunt resistance values will be so low, though, that it's best to wind your own.

In designing an extended-range meter

- Circuit for measuring meter resistance. With RS out of the circuit adjust R for full-scale meter deflection. Then cannect RS across the meter as shown and adjust it till the meter reads half scale. The meter resistance is equal to the value to which R is adjusted.
- 3 Extending the range of a current meter with a shunt resistance.
- Canverting a milliammeter to a valtmeter with a series resistance.

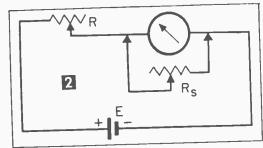

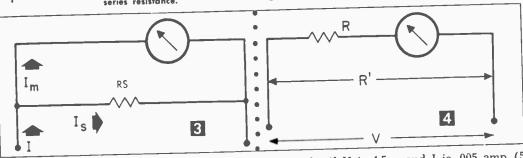

using a basic meter movement, try to select a range that is a convenient multiple of the meter scale range. Multiples of 10 are best since you can read the meter directly, and have to supply only the decimal point. Two and five are the next best choices for scale number multipliers, and of course, multiples of 10 can be used with these also. (Same applies to voltmeters.)

The circuit for converting a milliammeter to a voltmeter is given in Figure 4. These formulas are used:

(a)
$$R' = \left(\frac{V}{I_m}\right)$$

(b) $R = R' - R_m$

By connecting a switch (Fig. 5) you can make a multi-range voltmeter.

These current range extensions and voltmeter conversions are solved by applying Ohm's law. In the ammeter application of Fig. 3, the meter and shunt are in parallel. Thus, the voltage across the meter equals the voltage across the shunt. Therefore, the current through the meter times the meter resistance equals current through the shunt times the shunt resistance. And the current into the combination equals shunt plus meter current. The voltmeter arrangement of the second problem (Fig. 4) was based on the idea that the current through the shunt must equal the current through the meter, and the sum of the voltage drops across the meter and the series resistor equals the voltage drop across the combination.


What about measuring resistance with a meter? There are several approaches. The first (Fig. 6) utilizes an ammeter and a voltmeter to measure the current through, and the voltage across, an unknown resistance R_x. Then R_x is calculated from Ohm's law. For


example, if V is 4.5 v and I is .005 amp (5 ma.), using:

 $R_x = -\frac{V}{I}$. Then $R_x = \frac{4.5}{.005}$, and $R_x = 900$ ohms.

This method is cumbersome, so let's see if we can get around it. If we know the voltage E of the battery, do we need to measure V? No, if R, is much greater than the resistance of the meter measuring the current I. This leads us to the circuit of Fig. 7, where a pot P is employed to adjust the voltage V to a value around which we'll design our ohmmeter. Assuming that we'll use a 1-ma, 27ohm meter movement, as before, we'll want the resistance of P to be about 500 ohms. This choice is made on the assumption that the current from the battery should be 10 or more times the current through the meter, for accurate results. The resistance across A and B is zero, if we short these terminals. Therefore the resistance of R and the meter should be 5v (the design voltage) divided by the meter current, .001 amp. Resistance R, therefore, is 5000 ohms, minus the meter resistance of 27 ohms, or 4973 ohms. Since 5000 and 4973 ohms differ by only about 1/2%, you can let R equal 5000 ohms without noticeable error. The ohms scale may be calculated in terms of the I scale on the meter by assuming different values of R, using this formula:
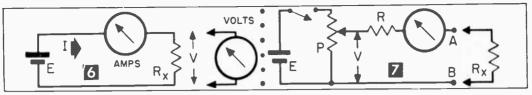
$$\begin{split} \mathbf{I} &= \frac{\mathbf{V}}{\mathbf{R} + \mathbf{R}_{\star}} \\ \mathbf{Thus, } \mathbf{R}_{\star} & \text{in ohms} & \mathbf{I} \text{ in ma.} \\ & 0 & 1.000 \\ & 500 & 0.909 \\ & 1000 & 0.832 \\ & 2000 & 0.715 \\ & 3000 & 0.625 \\ & 4000 & 0.555 \\ & 5000 & 0.500 \end{split}$$



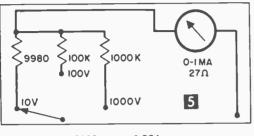

8000	0.384
10,000	0.333
15,000	0.250
20,000	0.200
30,000	0.143
50,000	0.091
100,000	0.048
200,000	0.024

You can compute additional values yourself. Note that the half-scale meter deflection is equal to R for any meter combination which uses this arrangement. That's a handy piece of information for estimates, before you begin design. The ohm readings may be obtained using a table such as that above, or an ohms scale may be pasted on the meter glass. The switch S is turned on only when the ohmmeter is being used.

The potentiometer P may be made up of a 100-ohm pot in series with a 400-ohm, fixed resistance. This arrangement makes the zero resistance adjustment less critical. You can double battery life by doubling the value of P (use a 200-ohm pot and an 800-ohm resistance) with a decrease in accuracy that's

negligible.

To convert a basic dc meter movement for ac measurements, rectifiers are used. Their difference in forward and back resistance is so great that we generally assume a rectifier acts as a switch. The rectifier circuit of Fig. 8A, not often used with meters, conducts during only half the ac input cycle. The full-wave half bridge of 8B passes current during all of the input cycle. A 2.7K resistor for each R works well with most germanium diodes. The output current is about 0.72 times the input current. The full bridge of Fig. 8C passes current during the entire input cycle also, but presents a greater output for a given input current. The output current is 0.9 times the input current.

The rectifiers may be germanium diodes or copper oxide types. Germanium diodes are more readily available and cover a broader range of frequencies. The GE 1N64, Sylvania


- A simple 3-range valtmeter. Resistance values were obtained by the methad of Fig. 4 and rounded off ta practical values.
- 6 Determining resistance by the valt-current (Ohm's law) method.
- A simple ohmmeter circuit. In the example in the text, P is 500 ohms. For less critical zero adjustment, substitute (for P) a 100-ahm pat in series with a 400-ohm resistor.

IN34A and the Raytheon IN66 are suitable. The shunt resistances for current meters and the series resistances for voltmeters of the ac variety may be determined in the same way as they were determined for dc instruments, but bear in mind that the transfer factor of the rectifier arrangement alters the value of the ac voltage required for full scale deflection, and that the apparent meter resistance is changed, too. Use the circuit of Fig. 2 for experimentation, considering the rectifier input terminals as the meter terminals and an ac voltage source instead of a battery to determine the apparent meter resistance. The current through the meter is the voltage across R divided by the resistance of R. Then, the formulas of Fig. 3 and 4 can

be applied.

Multimeters. There are many meter kits available at low prices. They're called VOM (volt-ohm-milliammeter) or multimeter kits and are good for measuring ac and dc current and voltage, and for measuring resistance. Although many factors enter into the choice of a meter kit, the primary consideration is meter sensitivity: the number of ohms resistance that the meter movement and the series resistance present between the input terminals of the meter, divided by the corresponding voltage range. This is expressed in ohms/volt. This number is a function of meter movement current for full scale deflection. A 1-ma meter has a sensitivity of 1000-ohms/volt; a 200 microamp. meter has a sensitivity of 5000 ohms/volt; and a 50 microamp, meter has a sensitivity of 20,000ohms/volt.

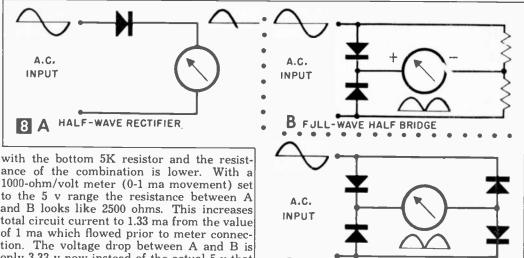The sensitivity is important, because when you connect a voltmeter into a circuit to make a measurement, you're connecting a resistance across the circuit. If you connect too low a resistance across the circuit, you'll draw enough current from the circuit to get a wrong voltage reading. Figure 9 illustrates what can happen. When you connect the meter across AB, its resistance is in parallel



Meter rectifier circuits.

FULL-WAVE FULL BRIDGE

with the bottom 5K resistor and the resistance of the combination is lower. With a 1000-ohm/volt meter (0-1 ma movement) set to the 5 v range the resistance between A and B looks like 2500 ohms. This increases total circuit current to 1.33 ma from the value of 1 ma which flowed prior to meter connection. The voltage drop between A and B is only 3.33 v now instead of the actual 5 v that would exist under normal circuit conditions—a big error. However, if a 20,000 ohm/volt meter were used to make the measurement, the resistance paralleling R2 would be 100,000 ohms on the 5-v range, and the resistance between AB would be 4760 ohms. The total current through the circuit would be 1.023 ma, and the voltage between A and B would be 4.87 volts, very close to exact.

Using a Multimeter. My young son uses his meter to check the resistance of a toy motor. If it's open, the needle reads infinite resistance (no deflection). Sometimes he checks his toy motors by using them as generators, switching the meter to a low dc voltage or current range and looking for a meter deflection as he rotates the motor shaft.

The motor used as a generator with a meter indicating output voltage across or current through a resistance makes a good rpm indicator for lathes, drills, motors and engines (including cars). The same scheme may be used for a speedometer for bicycles or a child's wagon. Equipped with a propeller or vane that is outfitted to face into the wind or equipped with anemometer type cups, this same electrical arrangement may be used to measure wind speed. The hook-up of Fig. 10 may be used for any of these applications. The size of the series rheostat must be determined experimentally and may include a series resistance in the meter if you use the dc voltage range of a VOM for the meter. A more versatile approach is to use a dc current

Usually the pot adjustment can be made to calibrate the meter so the existing meter scale with a suitable fraction or multiple of 10 will provide the desired range of rpm or mph. Sometimes, though, you'll have to provide a paper and ink scale, and you'll have to figure out the mechanical coupling.

A multitester's ac volts range can be used


with an audio amplifier to produce an audio millivoltmeter, a sound survey meter or an applause meter (Fig. 11A). Figure 11B shows resistance-capacitance meter coupling, and 11C shows transformer coupling to the meter. You can rig up a calibration template for the amplifier volume control so you can use it as you'd use a range switch. You can use the meter's decibel or voltage scales.

The ac voltmeter ranges may be used to measure capacitance of paper, oil or mica dielectric capacitors. Use the circuit arrangement of Fig. 12. Adjust the pot till the voltages at A and B are equal Then disconnect the pot and measure its resistance R. For the capacitance in microfarads, substitute the value of R in this formula:

$$C = \frac{1,000,000}{377R}$$

This circuit works best with higher ac voltages, but 30 v is the top, safe limit. (The voltages across C and R won't add up to the applied voltage.) Get the 60-cycle ac voltage from a transformer—either a filament transformer or a train transformer will do. And, don't use this arrangement to measure low-voltage electrolytic capacitors, or you may ruin them! You can use a 6.3-v transformer in the circuit to test electrolytic capacitors rated 100 v or more, without damage.

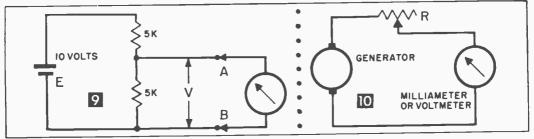Beginners can use a meter to get a good understanding of electricity. Use it to find out: What happens when you connect batteries in series and parallel; what happens to the battery voltage when you decrease the resistance connected to it; what happens to the voltage and current when resistors are connected in series or parallel; how to apply



Ohm's law; the difference in the resistance of a light bulb before it's turned on and after it has been on a while. Incidentally, never use the ohms scales to measure resistance in a circuit under power. Always disconnect the voltage from the circuit before you measure resistance.

The resistance ranges may be used to check light bulbs and lamp wiring. If the ohmmeter needle deflects at all on the low ohm range, the bulb (or lamp wiring with a good bulb in the lamp and the switch on) isn't open and if the meter needle doesn't hit zero, the bulb or lamp isn't shorted. In the case of a table or floor lamp, if you get this kind of indication, everything's good, except that you're not sure that the switch will work. When you turn the switch off, the meter needle will return to its normal rest position if the switch is operating properly. This is the technique for trouble-shooting radios, electrical appliances and home and car electrical wiring.

Another example of the continuity check just outlined is locating tubes with open heaters in a radio or TV. If none of the tubes in an ac-dc (transformerless) radio light up when the radio is on, the probable cause of trouble is an open tube heater. An open tube heater will also cause a TV set to be inoperative, but won't necessarily prevent all tubes from lighting up. To check tube filaments for


Using an amplifier with an ac voltmeter as an audio millivoltmeter, sound survey meter or an applause meter (a); R-C coupling meter to amplifier (b); and meter-cannected amplifier output transformer (c).

- 9 Illustrating how a low sensitivity voltmeter upsets low current circuit operation and gives false readings (see text).
- A toy motor used as a generator in this simple circuit has many practical uses. Determine R experimentally.

opens, use the ohmmeter test leads across the heater pins (power disconnected). The pin numbers may be obtained from tube manuals.

An ac voltmeter is useful in checking ac line voltages, transformers, circuit wiring, oscillator output, model railroad and toy circuits and for numerous other applications. The dc voltmeter is useful in checking batteries (check them for voltage with the normal load connected), checking dc power supplies, trouble-shooting in radios and car wiring, and for numerous other applications. You should have little difficulty in voltage measurement.

Current measurements are not used as commonly in routine trouble-shooting and experimenting, but are becoming more important with the advent of the transistor. The important thing to remember in making dc current measurements is that the meter is connected in series with source and load. That is, one of the leads connects to the source of voltage and the corresponding connecting point on the device that is receiving power. You might look at it as simply cutting one of the leads in the circuit and connecting the current meter to the lead ends that you've created. The microampere range on the meter is also useful as a current detector in Wheatstone bridge circuits.

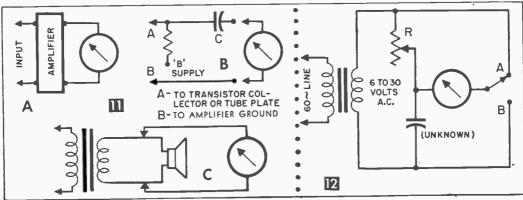

Using Positive Feedback

By C. F. ROCKEY

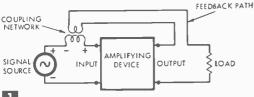


DIAGRAM OF AMPLIFIER EMPLOYING FEEDBACK


NE of the truly valuable techniques available to the small-receiver designer is positive feedback, or regeneration. Most small receiver projects utilize it; in fact, all truly sensitive receivers using less than five tubes or transistors probably apply this principle.

Positive feedback owes its effectiveness to the reduction of circuit losses which it accomplishes. All apparatus contributes some loss of energy to a radio signal as it passes through; even one inch of hookup wire has measurable resistance. This unavoidable extraction of signal energy reduces both the available amplification and the selectivity of a receiver. Positive feedback takes a little of the relatively strong signal appearing in the output of an amplifier and transfers it around to the input, overcoming some of the losses in the circuit (Fig. 1).

Thus the losses of the circuit are reduced, and in effect the resistance of the tuning circuit or other circuit is reduced. In the case of the tuning circuit, since selectivity is an inverse function of its resistance, the tuning curve will be sharpened considerably (Fig. 2).

By "positive" feedback is meant that the feedback path and coupling network are arranged to make the feed-back voltage add to the original signal voltage at any instant. Such a connection enhances the gain and reduces the bandwidth of the circuit involved.

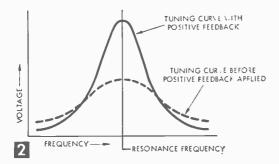The additional gain is expressed in this formula:



$$\begin{array}{l} \text{Gain with} \\ \text{Positive Feedback} = \frac{\text{Normal gain}}{1 - \text{Normal gain}} \\ \times \text{Feedback Ratio} \end{array}$$

The feedback ratio is the ratio of the voltage fed back over the output voltage. It is always a number smaller than one.

Even though you've let your algebra slip, you can still see that as the feedback ratio (amount of voltage fed-back, in effect) is increased the denominator of the fraction grows smaller. And as the denominator grows smaller, you will recall, the whole quantity becomes larger, since the numerator remains constant. This means that a comparatively small amount of feedback will give a large increase in gain.

Suppose we have an amplifier with a normal, non-feedback gain of five. Now, let us arrange that 1/10 of the amplifier's output voltage will be additively (positively) fedback into the input. Substituting these values into our equation we see that:


Gain with Feedback =
$$\frac{5}{1 - (5 \times \frac{1}{10})} = \frac{5}{\frac{5}{10}} = 10$$

Thus we see that even this comparatively small amount of feedback has doubled the actual amplification of our system. Some calculated gain values obtained from this same hypothetical amplifier with various values of feedback are tabulated below:

Ratio (Feedback Voltage)	Effective Circuit Amplification
Without Feedback	5.0
0.05	6.7
0.10	10.0
0.125	13.7
0.150	20.0
0.175	40.0
0.195	200.0

The value of feedback is limited by the fact that when the product of the normal gain times the feedback ratio becomes equal to one, the system breaks into oscillation. As the feedback is increased toward the maximum value, the circuit adjustment becomes exceedingly critical. But positive feedback makes it possible to obtain as much amplification from one tube or transistor as would be gotten from two or three without it, so it is well worth the drawbacks.

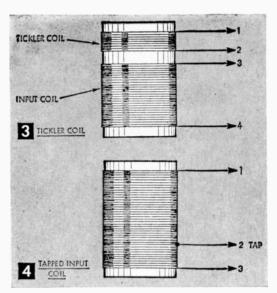Positive feedback is always employed in the



higher frequency circuitry of a receiver, since the bandwidth-limiting action makes its use in the audio section inadvisable. While most often employed in the detector circuit, regeneration often also improves the operation of if or rf amplifiers; here it increases both sensitivity and sharpness of tuning to a marked degree.

In any case, the requirements for successful application of positive feedback may be summarized as follows:

- 1. The feedback must add to the signal input voltage at all times. This means the phasing or polarity of the coupling circuit must be correct.
- 2. The magnitude of the feedback's effect must be under perfect control and smooth at all times.
- 3. Normal control of feedback must have a minimum effect upon the frequency to which the circuit is tuned.

Most often, an inductive feedback system is used wherein the energy is transferred via a magnetic field.

The first method of inductive feedback employs a tickler coil, connected in series with the output circuit and coupled magnetically to the tuned input coil. If the two coils, tickler and input coil are wound in the same direction and on the same form, they must be connected according to Fig. 3 and Table A.

The tickler coil should be spaced as closely to the input coil as possible, and should contain the fewest possible turns, determined by experiment.

Another commonly-used arrangement for providing positive feedback is by the use of a tapped input coil. This is shown in Fig. 4, connections in Table B.

Again, exact placement of the tap along the coil must be determined experimentally in new designs; in most cases, however, the

TABLE A-TICKLER COIL CONNECTION	
	e

Type of	Connection Numbers			
Circuit	1	2	3	4
Vacuum Tube Grounded Cathode	Plate	B+	Ground	Grid
Vacuum Tube "Hot" Cathode	Ground	Cathode	Ground	Grid
Grounded Emitter Transistor	Emitter	Battery	Ground	Base
Grounded Base Transistor	Battery	Collector	Ground	Emitter

TABLE B-TAPPED INPUT COIL CONNECTIONS

Type of	Coni	nection Numbers	
Circuit	1	(Tap)2	3
Vacuum Tube Grounded Cathode	Plate	Cathode	Grid
Vacuum Tube "Hot" Cathode	Grid	Cathode	Ground
Grounded Emitter Transistor	Collector	Emitter	Base
Grounded Base Transistor	Collector	Emitter	Base

number of turns between connections one and two will be appreciably greater than between two and three.

Although physical arrangements may vary, other taps may be used in certain applications, particularly with transistors, but the identical principles apply in coil connections.

Control of the effects of feedback is most often accomplished by controlling the gain of the circuit rather than by varying the feedback coupling. This is because most feedback variations tend to influence the tuning of the circuit at the same time.

The most widely-used method for controling the effect of feedback involves varying of either the dc plate voltage (with triodes) or the screen-grid voltage (with pentode tubes). With transistors, current practice involves variation of the dc base bias in most instances. This is practically done with a well-bypassed volume control potentiometer. When set up properly, these means provide absolutely smooth and reproducible control of the effects of feedback with a minimum of influence upon circuit tuning. This, along with a little circuit savvy and shielding, suffices for requirement three that we stated earlier.

From the operational standpoint, these two rules should be observed:

- 1. For maximum gain, adjust the effective feedback as closely to the oscillation point as possible. The oscillation-point is manifested by a click or plunk, followed by evidences of instability or reduction or gain as the feedback is advanced.
- 2. If for any reason it is desirable to operate the circuit in an oscillating condition; as for CW radiotelegraph reception with the simple receiver, for instance, again always operate as close to the oscillation-point as expedient.



STEREO MUSIC CENTER

Complement your electronic finery by matching its beautiful sound with a handsome hardwood cabinet far below cost of its manufactured counterparts

By CHILTON E. PARKER

RUE stereo—two high fidelity units operating together—is a wonderful experience, especially when you have purchased quality equipment in kit form at substantial savings and successfully wired the project. But you're really only halfway along the road to complete enjoyment of your achievement until you house all of the components in a lastingly-beautiful hardwood cabinet.


A cabinetmaker will custom-build such an elaborate enclosure for you at a price to match its handsomeness. For somewhat less, you may be able to "pick up" a fine cabinet of adequate dimensions at a large furniture store or radio shop. And, you can realize still more savings by building the 7½-ft.-long cabinet shown in Figs. 1 and 12, if your home shop is equipped with good hand tools and a few power tools. Its clean, simple styling will allow placement with practically any type of home furnishings, save the most extreme contemporary pieces.

Though solid and veneer cherry was selected as the primary wood, you can easily substitute any other hardwood that suits your taste or is more available in your area. Inner

frames and base pieces are of pine. All details have been worked out so that only a minimum of shop equipment is required. Power tools used include a table saw, ½-in. drill press, a borrowed or rented router, and portable drill. Special tools used were a Stanley doweling jig and a set of Sears screw pilot drills.

Before ordering materials give special consideration to your speaker enclosures, as size will govern the dimensions of the cabinet. The speaker units in Fig. 2 have an overall height of 30 in. and can accommodate enclosures with a maximum height of 24 in. plus padding. A great many kits on the market will fit these dimensions comfortably.

The Cabinet Base, constructed in two distinct operations, consists of a sub-assembly and final surface assembly. Lay out pieces of pine for the sub-base as in Fig. 3A. For the long end pieces, rip a 10-ft. 1x8 into two boards, 3½ and 3% in. wide. Put the boards together to be sure they will be cut square and trim them to 86¾ in. long. From the remaining parts of this ¾-in. stock, cut out four 3½ x 15-in. pieces; also cut three 2x4

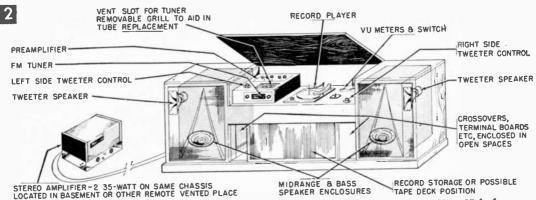

Minimum acceptable distance for placement of speakers is 6 ft., which provides a stereo zone 11 to 17 ft. from front of cabinet. Low- and mid-range speakers are spaced on 6-ft, centers. Tweeters are placed further out to extend the stereo listening area.

pieces to the same length. A simple way to ensure squareness is to cut the pieces slightly oversize and clamp together, trimming all seven ends at the same time.

Drill for two #8 x 1½-in. flathead (fh) screws on the ends of the long pieces as in Fig. 3A. A wood screw pilot bit will do a faster, more efficient job than ordinary drill bits. Glue and screw the 34-in. side pieces to the ends, then line up the three 2x4 pieces and repeat the operation. Before the glue dries, make sure all corners are perfectly square. After glue has set, assemble the two remaining inner pieces.

The Inner Frames are next (Fig. 4A). Cut two 48-in. pieces each out of two 8-ft. 1x8 pine boards, then rip these 3 in. wide. Now cut out an 18-in. and a 28-in. length out of each of the four 3x48-in. lengths. Measure 5%2 in. from the center of each of the shorter pieces and, with the saw blade set at half the thickness of the wood, rabbet the ends for Note: After assembling right and left speaker frames and end pieces, fit and glue 1/16-in. veneer strip as

a half-lap miter joint. Measure 9% in. from center of the longer pieces and rabbet these ends. If no other means, line up the edges on the edge of your saw table to check that corners are square.


Now you can glue and clamp the frames together then drill for and install two #8 x 34-in. fh screws at each joint. Unclamp the

frames, now slightly oversize, and let dry.

Use of Plywood. We cut our principal wood sections out of a 4x8-ft. sheet of 3/4-in. sliced lumber core cherry plywood available through cabinet shops and lumber dealers nationally. Ask your source to rip your sheet into two pieces, one being 181/4 x 96 in. It will then be easier to handle when you finish sawing it at home. This piece should be cut from the side and edge having the most beautiful grain.

Put your best hollow ground or planer blade on your table saw and set the rip fence at 1711/16 in. These blades give amazingly

shown in detail B, Fig. 7. SUB-BASE A ALL MATERIALS - PINE COUNTERSINK FOR -3 1/2 (2 EACH END ON E) 3 CABINET END PIECE - 2 REQ. V4"CHERRY PIECE TOP & BOTTOM OUTSIDE FRAME MEMBER 2 REQ - SOLID CHERRY - GLUE TO - 1""
ABBET IN CABINET END PIECE.
ABBET IN CABINET END PIECE.
ABBET IN CABINET END PIECE.
ABBET IN CABINET END PIECE. TE - AFTER ASSEMBLING RIGHT & LEFT SPEAKER FRAMES ND PIECES VENEER STRIP SHOWN IN DETAIL B. FIG. T FITTED & GWED B SPEAKER FRAME & END PIECES

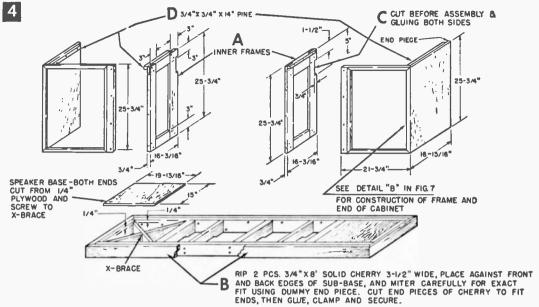

Caution: Assemble subframe before gluing. After checking for squareness, cut X-braces for each end. Disassemble, glue, and complete assembly, including braces. Check for perfect squareness.

smooth surfaces but must be exactly parallel to the rip fence; otherwise gum pick-up and resultant heat burn the wood and rapidly dull the blade.

Parts of the same width are cut at the same time, resulting in fewer settings of the saw and perfect fitting during assembly. With the fence set at $17^1 \frac{1}{16}$ in., rip the narrow piece of plywood. Set this piece aside, now cut the two end pieces as one piece of wood $16\frac{7}{8}$ in. wide and 53 in. long. Next cut a panel $21\frac{1}{2}$ x $43\frac{1}{8}$ in. which will be the base for the control center and front piece of the cabinet. Turn the saw blade to a 45° angle and miter the front edge as in Fig. 6A. The long narrow piece left is reversed for use as the front of the inner portion of the cabinet.

Take two $34 \times 5 \times 96$ -in. pieces of solid cherry and rip them to $3\frac{1}{2}$ in. wide (we asked our source of supply to plane one edge, which makes the sawing operation easier and gives a perfectly finished top edge). Also cut two pieces $34 \times 3\frac{1}{2} \times 19$ in. for the ends of the base. Miter the ends, then glue and screw this "veneer" to the sub-base as in Fig. 4B.

This can be accomplished with only four clamps. Line up one side perfectly and clamp, making sure the loose end pieces fit properly. Drill pilot holes every 18 in. on a line 1 in. from both edges. The holes should be staggered so there is approximately 9 in. between screws. Now remove clamps, apply glue and carefully reclamp back in position. Install screws, remove clamps, and follow the same procedure with the three other pieces. Cut a strip of cherry 1/8 x 3/4 in. from one of the remaining 8-ft. pieces, trim to length,

clamp, and glue onto the long piece of the subframe that was cut to 3% in. width. Be extremely careful not to let any surplus glue ooze onto an outside surface.

Cut the 16% x 52-in. plywood in half and then trim the two pieces together to a length of 25% in. (Fig. 3C). While cutting this dimension, cut the inner frames (Fig. 4A) to 25% in. long by 16% in wide. It is imperative that these four pieces be identically square.

Select the graining that you prefer to be exposed on the end pieces. On the inside of what is to be the front, rabbet the edge on both pieces as in detail B in Fig. 7.

Speaker Framing Stock. Cut four pieces of 34×34 -in. cherry 24 in. long, two pieces of the same stock 26 in. long and two 34×24 -in. pieces 30 in. long. Bevel all of these pieces on one side 18° as in Fig. 3B. Trim the two 30-in. lengths to 26 in. and the four 24-in. pieces to 204 in. long. Do this by first mitering one end, then carefully measuring to the other end and mitering it. Trim the two $34 \times 24 \times 30$ -in. pieces to 2534 in. with the miter being cut last as in Fig. 3B.

Next put the two 26-in. long pieces through the saw and remove ½6 in. of the face (detail B in Fig. 7) to compensate for ½6-in. veneer to be attached later.

Now glue and clamp these pieces, one each, into the rabbets of the already cut end pieces. Scrap from the 18° angle cuts can be used to get a square clamping surface. Once these are dry, cut miter and, using the edge of your saw table or other square surface, clamp and glue one of the 20¼-in. pieces as in a picture frame construction (Fig. 6B). Since both the

bottom and top edges will be covered, drive a $\#8 \times 1\frac{1}{2}$ -in. fh screw from the bottom pulling the corners together. This produces a "professionally" tight joint without special clamps.

Join another 20¼-in. piece in the same manner and when glue has dried, take one of the 2½-in. x 25¾-in. pieces and complete the frame, again screwing from top and bottom. Using the other pieces of end stock, assemble

your second frame.

Draw a light guide line 1½6 in. from the edge across the front of the base (front edge has the ¼-in. strip of cherry glued in) and ¼ in. in from the edge of each end. Set the ends and speaker frames on the guide lines. Then carefully measure, cut, and trim the inner frames. Tack the frames together, trimming both at the same time. While they are tacked, cut a notch ¾ in. deep by ½ in. wide (Fig. 4C). Use a thread or light string stretched across the end pieces at the front and back corner to check that all four: the two inner frames and end pieces, are the same height and in line.

Cut eight pieces of ¾-in.-square white pine glue strips. Attach them to top and bottom of each end panel and inner frame as in Figs. 4D and 6B, using glue and #8 x 1½-in. fh

screws. Check that edges are flush.

Just before gluing end panels in place, mark and cut dadoes for knife hinges on each end as in Fig. 6C. Replace in position, drill four pilot screw holes in both the lower glue strips of the end piece and inner frame. Glue and screw in place as in #2 of Fig. 6B, and wipe off any excess glue immediately.


Through the bottom of the speaker platform, drill three screw pilot holes and drive three screws to pull the bottom member of the speaker frame down to the base (#3 of Fig. 6B). Drill and screw the inner and speaker frames together after squaring up. Repeat these operations to assemble and glue

the remaining end.

Control Center Construction. Cut a 7½ x 48-in. piece of ¾-in. cherry plywood for the control center back piece. Notch ends and cut dadoes as in Fig. 6D and observe the 45¾-in. dimension, which is critical. Trial fit back piece into the inner frame notches, and check that the edge should be ¾2 in. lower than the top of the inner frames (critical). Glue and screw the back piece in place.

Cut and dado both sides of the control center as in Fig. 6E, using a router or saw and chisels. Carefully position these sides; glue and clamp. Drill holes for and drive #8 x 1½-in. fh screws. Dadoes must match those in the back piece as in Figs. 8 and 9. Properly mounted, side pieces will be ½6 in. below the top of the inner frames.

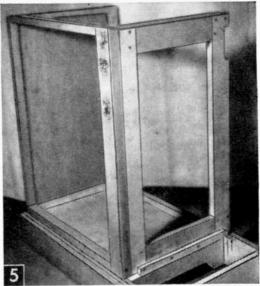The previously cut control center base and front (Fig. 6A) can now be installed. Slide the base in place into the side piece dadoes as



Lap-jointed inner frame is supported by heavy member of sub-base. Pine components are concealed by solid and veneer cherry in finished cabinet.

in Figs. 10 and 11 so that mitered front edge is flush with front of the sides. At this point, front and side dadoes were marked as in Fig. 6F to fit our tuner and preamp case. Check yours and modify the panel as needed.

Remove the base, make the marked dado and other cuts. Also cut out the record player mounting hole on the other side according to a template supplied by the manufacturer. In addition, lay out and cut any holes you may need for control switches and meters (Fig. 6G). While doing this, be careful not

to dent or scar the mitered edge.

Now trial fit the previously cut front piece (Fig. 6A) to the base. Once satisfied, apply glue carefully to the side panel dadoes and slide the base in position. You've no doubt noticed that the dadoes are slightly wider than the ¾-in. base thickness. After checking that dadoes for tuner and preamp case line up drive wedges in from the underside to push the base up tight. Allow to dry.

Apply glue to mitered edge of the installed control center base and its front piece, place latter in position, and secure with two #8 x 1½-in. fh screws on each end. Use wood clamps to draw into position, then screw wood strips to base and front inside. Allow to dry.

Record Compartment. A number of remnant pieces were splined together here to reduce waste or scrap to a minimum. Spline cuts were made the same way as other dadoes, with a saw blade making as many runs as needed for proper width.


Cut the floor for the record storage compartment from ¾-in. plywood as in Fig. 7A, dadoing and rabbeting the underside to receive the cross members of the base and cut-

ting %-in. wide dadoes with a router bit for partitions and back.

Partitions are shaped from %-in. birch plywood and finished with cherry strips splined and glued to the front as in Fig. 7C. If you wish, partitions can be left square so dadoes can be cut with a table saw and hand chisel.

dado to fit over compartment back.

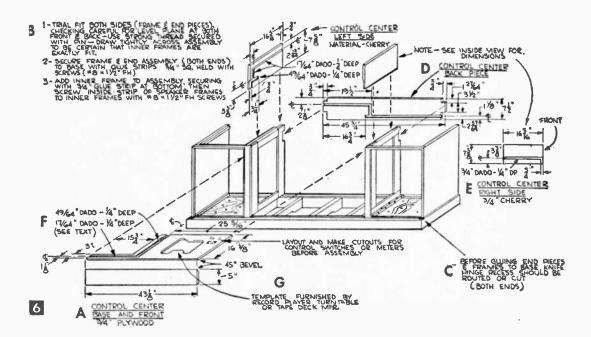The Tuner-Preamp Case is cut from solid cherry stock, except for the front and top which are ¼-in. cherry veneer. Dimensions given in Fig. 14A are about ¾-in. longer than the ¼-in. dadoes on the control panel base. This allows them to be easily inserted in



Cut two $16^{11}/_{16} \times 18^{1}/_{8}$ -in. pieces from the $^{3}/_{4}$ -in. plywood sheet for end panels, then dado and notch as in Fig. 7D. Cut and dado the solid cherry front and rear top pieces and the birch plywood back as in Fig. 7E.

Glue and screw the record compartment to the frame (Fig. 14). Cut a $\frac{3}{4}$ x $\frac{3}{4}$ x 3-in. guide block for the top of the record compartment and install it with glue and screws to the inside of control panel front piece as in Fig. 11. Now you can apply glue to bottom dado on left side of record compartment, slide it into position as in Fig. 14 and attach to base of compartment and guide block.

Cut a ¾ x ¾ x 33¾-in. spacer strip from scrap pine and secure it flush with the bottom of control panel front piece and butting against left side of the compartment.


Glue the vertical dado on the left side of compartment, the dado in the rear of bottom piece, and both dadoes in the right side. Position compartment back and assemble the right side similar to the left. In order, glue compartment dadoes and place them in position; glue and screw front partition, holding bar in forward notches cut in sides; glue and screw rear bar in rear notches in sides, and

place. Rout or drill and chisel the end piece to receive the lid support. No dimensions are given for the preamplifier or tuner cutouts as there are many slight variations and manufacturers supply their cwn mounting instructions. Also, the position of the tuner's cooling panel may change in order to improve ventilation or for easier tube replacement.

We found the following method easiest for setting and gluing the finished blanks in place. First glue and slide the top in position, then the side. Depth of side is cut approximately 1/16 in. short of total height. After the side is in place, slip in a filler strip to bring it to proper height so the miter edge of top and side meet. The strip should be about 1 in. shorter than total length of the dado.

Glue and slip in the front. A number of small clamps are a real asset here. Since this is a focal point of the finished cabinet, be sure to lift all glue that may ooze from the joints. Edges around the tuner vent and preamp are optional. These are ¼ in. square and are glued and screwed to the top after the selected preamp and other equipment were set in for fitting.

Panel Door Building. There are 13 nar-

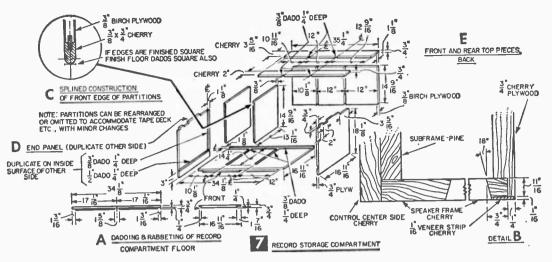

row doors attached accordion style by concealed hinges. All wood is ¾-in. solid cherry except for the ¼-in. inner frames. To simplify the job, cut all similar parts at the same time. Set up a cutoff gauge on your saw, clamp strips to cut six at a time, making sure the cross feed is perfectly square.

Cut 26 pieces $1\frac{1}{4} \times 25\frac{3}{4}$ in. for the sides, 26 pieces $1\frac{1}{4} \times 4\frac{1}{4}$ in. for the ends, 13 pieces $1 \times 4\frac{1}{4}$ in. for the centers, and 26 pieces $3\frac{15}{6} \times 10\frac{3}{4}$ in. for the insert panels, all from $3\frac{1}{4}$ -in.


solid cherry. Run off 85 ft. of ¼-in. stock to be machined in two basic operations. Set the saw blade ¼ in. high and dado the strips ¼ in. wide as in detail A of Fig 15.

You'll need a molding head cutter to round both edges of the ¼-in. stock, such as


Sears #9H-2352.

Make a jig by taking a strip of scrap wood about ¾ in. thick and 4 in. wide. Saw a dado ½ in. deep on it with the width just enough to allow the ¼-in. stock to slide through

	MATERIALS LIST-ST	EREO MUSIC	CENTER
No. Req.	Size and Description	No. Req.	Size and Description
1 pc.	3/4 x 71/2" x 10' pine (sub-base framing)	200	3/8" D. x 11/2" long spiral hardwood dowel pins (Crafts- man, 92¢)
1 pc.	15% x 35% x 48" pine (sub-base framing)	9 prs.	36 x 1" Soss invisible hinges for doors (Crattsman
2 pcs.	3/4 x 71/2 x 96" pine (inner frames)	2 5.2.	#0100, \$2.39 with screws. For this quantity, it is
1 pc.	3/4 x 51/2 x 60" pine (glue strips)		cheaper to order 12 pairs of hinges at \$21.50.)
1 pc.	34 x 48 x 96" lumber core cherry plywood (top, ends, control center back piece, record compartment floor)	2 prs.	\$\frac{5}{6} \times 15\frac{7}{6}" reversible knife hinges (Craftsman #1595, 54¢)
1 pc.	34 x 48 x 48" lumber core cherry plywood (control center base and front piece, record compartment end panels)	1	48" long piano (continuous) hinge 11/16" wide when opened, with screws (lid hinge)
1 pc.	1/4 x 24 x 36" cherry plywood (speaker platforms)	1	lid support (#9379J, left hand style, used in project available from Lussky, White & Coolidge, 216 W.
1 pc.	1/4 x 16 x 20" cherry plywood (tuner-preamp control box top, front)		Monroe St., Chicago 6, III. Price \$2.68. Cheaper type is new type of adjustable friction brass plated
2 pcs.	3% x 24 x 36" birch plywood (record compartment par- titions, back)		support with nylon roller to hold lid at any height. Available as #7074 from Craftsman, 42¢)
	All wood listed below is solid cherry	3	1/4" D. x 1/2" long magnets with 1/2" D. steel disk contacts (door closers—available for \$1.90 from J. F.
2 pcs.	3/4 x 5 x 96" (finished base, long pieces)		Simpson Co., 4754 W. Washington St., Chicago 44,
2 pcs.	3/4 x 31/2 x 39" (finished base, end pieces)		III.)
4 pcs.	3/4 x 21/2 x 30" (speaker frame strips)	1 lb.	casein stainless glue (Craftsman #524C, 85¢)
1 pc.	$3/4 \times 31/2 \times 18''$ (side of tuner-preamp box)	1 pt.	contact bond cement (Craftsman #CBP10, \$1.49)
7 pcs.	3/4 x 51/2 x 36" (door sides, ends, centers)	1 qt.	pigmented wlping stain, French provincial (Craftsman #202, \$1.77)
7 pcs.	3/4 x 315/16 x 35" (door insert panels)	1 qt.	wiping stain reducer (Craftsman #205, 94¢)
2 pcs.	3/4 x 75/8 x 167/16" (control center sides)	1 doz-	$\#10 \times 1\frac{1}{2}$ " flathead (fh) screws
13 pcs.	1/4 x 11/2 x 72" (door inner panels)	1 gross	#8 x 11/2" fh screws
Note: Solid cherry available at Craftsman Wood	1 gross	#8 x 11/4" fh screws	
	Service Co., 2727 S. Mary St., Chicago 8, III. Order the 96" lengths and the $\frac{1}{2} \times \frac{1}{2} \times 72$ " strips sepa-	16	#8 x 3/4" 1h screws
the 96" lengths and the 1/4 x 1/2 x 72" strips separately. An order for 18 sq.ft. of 3/4" cherry dimension stock in 42" lengths and random widths (4" to 8") should be sufficient to cut all other solid pieces. Latest catalog (1962, #28) price is 55¢ per sq.ft.	2 pcs. Misc.	24x29" grille cloth (speaker sections) cherry veneer edging '416" wide, 1 pt. linseed oil, 1 pt. turpentine, insulation for speaker cabinets, 1 box 36" brads, 1 box 1/4" tacks	

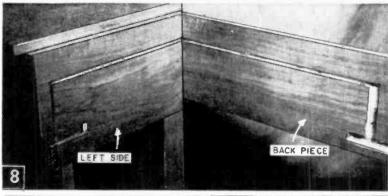

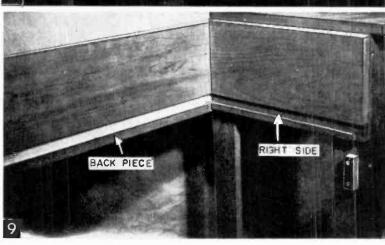Views of left and right sides of control center back piece, after fitting side pieces. Note perfect match of dadoes at each end. Right side piece is cut about 1 in. narrower than recommended in Fig. 6E.



easily. Now change the saw blade for molding cutters and measure carefully so that when the cutters are raised, one of the beads will be exactly centered in the dado on the guide board. Raise cutters enough to place a rounded edge on stock and run both sides.

To shape the insert panels, change to a molding cutter shape such as that of Sears #9H-3202 (Fig. 15). Since there is a lot of wood to remove, take three passes to do it.

As you will be cutting against the grain on the ends and there will be slight splintering on the edge, cut the ends first and sides last. This will leave a smooth-finished edge as the splintered portion will be cut away.

Clamping Jig for Dowel Work. Now construct a clamping jig—flat, and with a surface at least 28x36 in. Cut two 3x28-in. pieces of scrap pine and attach them to the base, leaving 28½ in. between the inside edges. Cut a 1½-in. wide strip into two wedges. Lay the pieces for four doors in position: two 1¼ x 4¼-in. pieces for ends, one 1 x 4¼-in. piece for the middle.

With the pieces in alignment, lightly drive the wedges into position and mark the dowel guide lines: two for each side top and bottom, and one each side for the center. A Stanley dowel jig and the complete directions that come with it make easy work of this. To cut dowel holes, we used a Delta \%-in. spur drill bit with \\\'/2-in. shank.


Mark all door sides and cross members as in Fig. 15 and then drill. Place glue in one side of each door only and tap in dowel pins (the prepared kind, 3/8-in. diameter and 1½ in. long). Place dry dowels on the other side and carefully tap together.


Again, lift excess glue. Complete four doors in this manner and place in press, driving wedges in fairly snug. As the wedge pressure will tend to raise the doors in the middle, place a board on top, and weights, such as old barbells. Allow to dry. Complete the other doors the same way.

Sand the surfaces flush with medium production paper and finish off with a fine grade. A slight surface variation is possible.

The frames (still with one side not glued) are now ready for fitting with inner frames. For a perfect fit, miter these individually for each opening. Cut all inner frames, then label and bind each set of four separately. We suggest this individual-fit method since it is quite unlikely that each door will have precisely the same measurement.

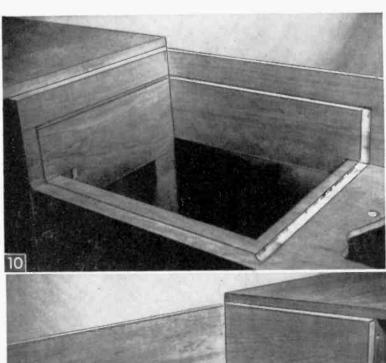With the frames intact, apply glue and position inner frames, then secure each end piece



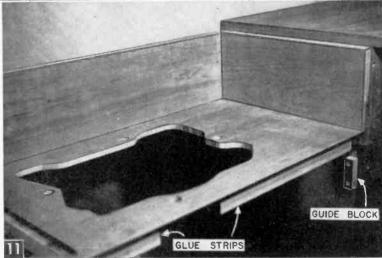

View of control center base during trial fit to check all cuts with equipment selected. Changes should be made and checked again before securing this panel in place. Front panel of base is removed here, exposing gluing strips at joint with bevel of base, also the small guide block for top of the record compartment.

with two \(^{3}\mathbb{e}\)-in. brads and each side piece with three brads. Use a small counterpunch to set the brads. Be sure not to glue the miter of the inner frame of the loose side on the door frame—let it dry thoroughly.

Now tap the loose side out and trial-fit completed panels in their respective positions. They should go in freely, not sloppily. Trim any panel edges that need it and, working in groups of four, apply glue carefully to the inner frame dado. When the two panels are in place, glue the loose side and tap into position. Remove dowels, glue these holes, and put the dowels back in place, tapping slowly and with care.

Considerable pressure builds up in the dowel holes and the wood will split unless the glue is allowed to pass by the sides of the dowels. You will be wise to have a partner ready to lift any glue that may ooze out. This type of glue sets rapidly and you cannot

handle both operations on four doors alone.

Now lay the four doors in the wedge vise, set weights on top, and drive home the wedges. This will bring on more oozing of glue, so be ready for it. Use strips of aluminum foil on the bottom and under weights. Finish the remaining doors in like fashion.

Multiple Door Assembly. Lay out the 13 doors across the floor, arrange them for most pleasing appearance, then number them. Rabbet doors numbered 2, 3, 6, 7, 11, and 12 as in the three details in Fig 16A. Install a ¼ x ¾-in tongue in the rabbets of doors numbered 3, 6, and 11 to lock the sections closed.

Doors 1 and 13 are routed or chiseled out at top and bottom for knife hinges, while the others are hung on Soss invisible hinges. The dowel jig makes installation of this type hinge extremely simple.

When closed, these hinges have %4-in. spacing between their faces, so take this into ac-



Completed stereo music center with doors and top open to reveal control and speaker area cabinetry.




Without cabinet, the equipment looks like this: preamp over one speaker enclosure, amplifiers (to be remotely installed as in Fig. 2) over the other, record player. Tuner and tweeters not shown.

count when trimming the sides of all doors. When the doors are laid out, the outside edge of end doors should be flush with the respective end panels of the cabinet. The ¾-in. spacing is also carried into the rabbeted edges to allow freedom of opening. Trim ends of doors to 25% in., which will allow ¼6 in.

clearance at top and bottom.

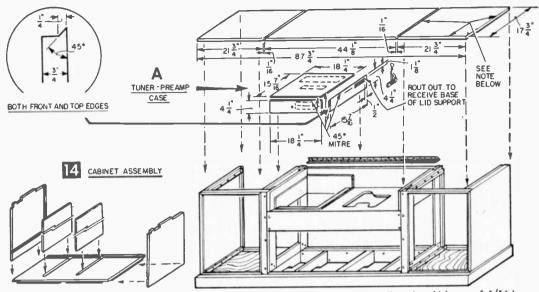Working with two adjoining doors at a time, measure and mark a line on each one 3¼ in. from the top and bottom. Then, measuring toward the middle, mark at ½, ¾, and 1¼ in. Drill at these points with a ½-in. drill, following instructions furnished with the



Note: Dimensions given for top panels are finished measurements. Be sure to allow for thickness of 1/16-in.

veneer strip to be added on front and side edges of all three pieces.

hinges for depth and cleanout. Tap hinges in place, drill pilot holes and secure with screws. Finish the hinge installation for the four sets of doors and lay aside.

Check a radial saw to be sure its cut is perfectly square, then take the piece of cherry plywood blank previously earmarked for the top and cut it into three pieces: two 21% in. long and the other 44 in. long.


Final Assembly. Overall length of the cabinet should be 87¾ in. If any variance, allow for it in the center panel before gluing any veneer strips. Using a scrap 8-ft. piece from the base as a straightedge, cut three pieces of cherry veneer ⅓6 in. thick and ⅙6 in. wide. Attach the veneer to all exposed plywood edges on front and sides, using contact cement. Sand edges flush.

Glue and screw gluing blocks in place on the inside top (flush) edges of outer panels and inner frames. After they are dry, apply glue to the two top end panels, clamp them in position, drill pilot holes from underneath through the blocks and secure with $\#8 \times 1\frac{1}{4}$ -in, fh screws.


Screw a 44-in. length of piano hinge in position on the control compartment back panel. Rabbet the inside rear edge of the center top panel, previously cut and adjusted for length, to accept a flush mounting of the piano hinge. Set the panel in place, mark and screw to hinge, using only a few screws until you get it properly centered.

Place the lid support in position in the routed-out side of the preamp-tuner cabinet (Fig. 14A) to locate and drill an adjusting hole through the back panel. Adjust the tension; install support with screws.

| 13 DOOR ASSEMBLY | 26 INSERT PANELS | 13 CENTERS | 26 ENDS | 26 SIDES | 52 INNER FRAMES (SIDES) | 52 INNER FRAMES (SIDES) |

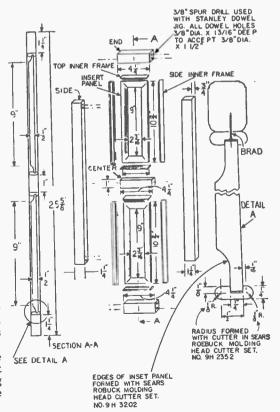


DENOTES: PAIR SOSS

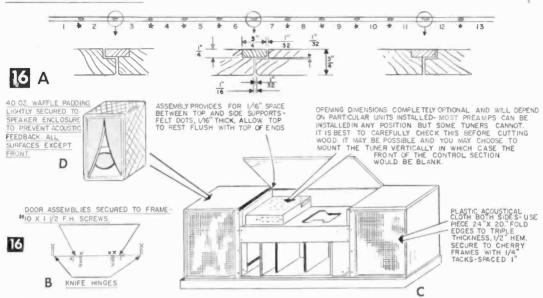

Opening dimensions depend on style and make of units to be installed. Most preamps can be installed in any position but some tuners cannot. Check units before cutting wood. You may, if possible, choose to mount the tuner vertically, in which case the control section would be blank.



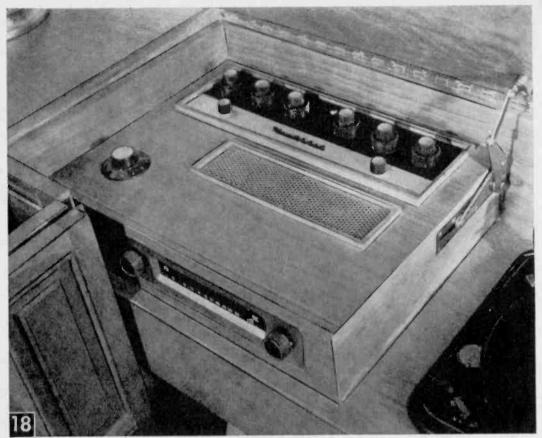Completed control section and record compartment. Note tiny magnet recessed in front panel. Strong enough to hold doors closed, it releases with a slight pull.



Tuner-preamp case in place. Note ventilator panel and single dial at left which controls tweeter mounted in top outside corner of speaker cabinet adjoining. Tension of bracket can be set to hold lid open as desired.

Using knife hinges, secure both sets of end doors in position. Lay a ½6-in. spacer on the base and set the remaining doors in place, using ½6-in. shims behind doors 4 and 10. Wedge lightly in position and drill six pilot holes on each side from the rear of the cabinet (doors 4 and 10). Insert #10 x 1½-in. fh screws (Fig. 16B), check alignment, and drive them home tightly.

Apply a cap strip of veneer in front of the exposed edge of the piano hinge, using con-

tact cement.

Small magnets only of ¼ in. diameter, and ½ in. long can be imbedded in ¼-in. holes in the cabinet as in Fig. 17 to keep the free doors closed. Small metal plates can be cut into the doors to make contact. Only a 2½-lb. pull will open the doors.

Finishing the Cabinet is a pleasure—there's no long and drawn-out painting or pumice polishing. Remove two center door sections for staining and oiling, then replace.

To complete the cherry finish, we used French provincial pigmented oil stain, cutting it well with the reducer recommended for it. Test it first on scrap pieces to be sure of the correct degree of color depth.

Apply the stain (½ pt. of stain plus 1 pt. of reducer) by dipping a soft, lintless cloth in the can and wiping it over the surface. Remove any excess left standing on the wood and use only the stain immediately absorbed. After a 24-hour wait for drying, apply a liberal coating of linseed oil and turpentine (2:1) with a clean, soft rag. Wait five minutes, then rub briskly to remove any excess oil. This will give a very rich, non-glossy appearance.

Remember not to start with a too-dark finish. With each subsequent oiling (every three or four months), the finish has darkened slightly. No polishes are needed since the oil application cleanses the wood and con-

tinues to protect it.

After the finish, select your grille cloth for the speaker sections and purchase enough to cut two 24x29-in. pieces. Turn the edges over ¾ in. and stitch the edges to triple thickness. Fasten in place with ¼- or ¾-in. tacks. Start at top and bottom centers, stretching the cloth as you tack toward the edges.

Since vibration from the speaker cabinets can be transmitted to both tuner and record player, the least you should do is insulate the bottom. We used 40-oz. rug wafile padding



Completed right side of control panel includes two meters and switch as well as another tweeter control.



Medium and low-range speakers come with this enclosure. Tweeter, control and crossover on top will be mounted in cabinet outside this enclosure.

tacked all around except for the front (Fig. 16D).


If you're using tweeters as we did, install them first, then slide in woofer enclosures. Install the other components, re-balance your record player, and you're in business.

Soldering with Immersion Heater

In a pinch, the occasional electronic builder, serviceman, or experimenter can solder wire connections with an immersion heaterlike the one shown. Simply wedge the wires between



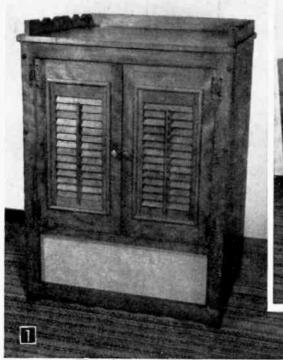the heater coil turns and plug the heater in intermittently until the joint gets hot enough. Use the heater to aid heating large work when your iron or gun isn't large enough to handle the job.—John A. Comstock.





This Early American styled cabinet combines modern living with an old design to give you a piece of furniture that is both decorative and functional.

Early American

TV Cabinet

Any portable or table TV set becomes a handsome console model when installed in this Early American styled cabinet

By RAY AYERS

NJOY the beauty of a console TV without paying the high cabinet price by customizing a cabinet that sheathes your present portable or table model set. Even an old TV chassis can be brought up-to-date by installing it in this Early American styled cabinet.

This particular cabinet was designed to house a table model Motorola, but with a few dimensional changes any model can be adapted to it. If the controls of your set are mounted on the side, an access panel can be made


(Fig. 2A) to permit convenient operation.

First Measure the TV you are going to enclose; then make the necessary dimensional changes directly on Fig. 2 so you won't have to double check every measurement when cutting the materials.

Next, cut the birch (see Materials List) for the front framework and rails to size (Fig. 2). Then shape the ¾ x ¾-in. hardwood corner support blocks for the top shelf. Duplicate the scrolled designs used on the lower part of the front framework and sides, and top rails (Fig. 4) on cardboard, so the de-

sign can later be transferred to the wood. The design can be fashioned with a saber or coping saw.

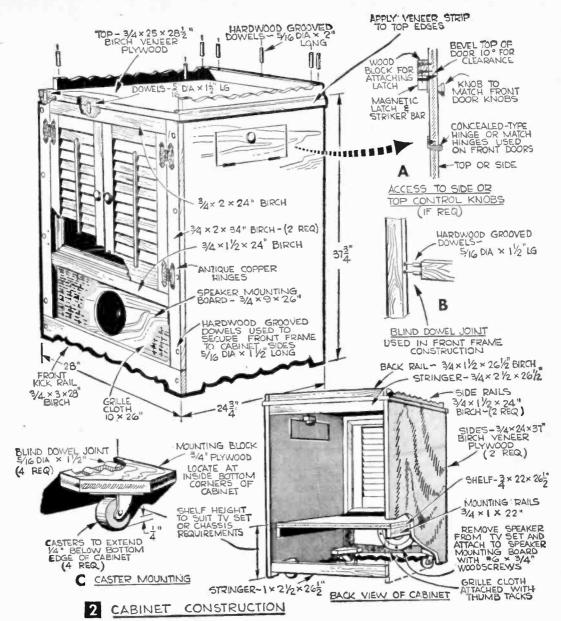Use blind dowel joints (Fig. 2B) to assemble the front framework. Dowel centers are preferable when spotting the holes in the frame pieces. For greater accuracy in matching the 16 x 34-in. holes, bore them in the horizontal members first. Groove all dowels to allow trapped air and Blue-Bird white glue to escape. Remove the squeezed-out adhesive



immediately with a moist cloth. Be sure the framework is squared when you set it aside

Cut the Top Shelf so it overhangs the cabinet by ½ in. on the sides and ½ in. on the front and back. This is the only piece of plywood that will have exposed edges; but these edges will later be covered with veneer. Other components that have to be cut from the ¾-in. birch veneer plywood are the sides, TV shelf and mounting rails, and the speaker mounting board. The two stringers used for added support in the back (Fig. 2) can be cut from plywood or 1 x 2½-in. hardwood.

Disconnect the speaker and use it as a template to locate the center cut-out and mounting holes in the speaker mounting board. Grille cloth can be made from dyed burlap or can be bought in 12 x 36-in. lengths from many radio and TV supply outlets.

Grille material used in Fig. 1 is described as "Tan with Bronze Threads," pattern 811, and was purchased from Allied Radio, 100 N. Western Ave., Chicago 80. After stretching the cloth across the mounting board, use thumb tacks to hold it in place. When attaching the speaker to the board with wood screws, be sure you don't damage the paper



MATERIALS LIST— EARLY AMERICAN TV CABINET

No.	
Req. 3 pc 1 pc 2 pc 1 pc 1 pc 1 pc 1 pc	34x1/2x261/2" birch hardwood 34x2x24" birch hardwood 34x2x34" birch hardwood 34x3x28" birch hardwood

Use frame, side rails back rail frame (horiz.) frame (vert.) frame corner blocks stringers speaker mounting board top, sides, TV shelf, mounting rails louver doors

1 pc. 2 pr. Misc.

1/16×60" hardwood dowel 31/2" long "H" type antique ham-mered hinges (Sears & Roebuck Co.) #5 and #6 wood screws, 1½" fin-ishing nails, grille cloth and thumb tacks, casters, Glu Bird glue, Miniwax stain, Weldwood veneer, louver

doors.


3 APPLYING VENEER

After cutting the scrolled design on the sides (Fig. 4), and, if necessary, the side access opening (Fig. 2A), attach the TV shelf mounting rails to the sides with 11/4-in. flathead (fh) wood screws. Use 11/2-in. finishing nails to fasten the sides to the top, and countersink these fasteners when attaching the stringers to the sides so the nails can be covered with wood filler. The nails used to attach the top to the sides are covered by the scrolled side rails.

Molding used to mask the old TV cabinet should not interfere with the viewing area. It should also fit flush against the installed set, which should be back far enough so the standard size louvered doors can close.

The ½x 2-in. cove molding used in Fig. 1 was shaped from solid stock, with all corners mitered. Attach it to the front framework by first drilling 1/8-in. pilot holes, then fasten with glue and woodscrews.

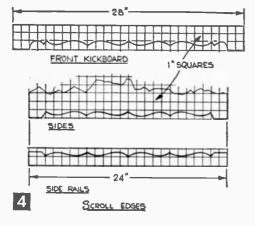Use furniture clamps to hold the frame against the assembled sides and top when you drill the 11/2 x 1/6-in. dowel holes. Attach the top to the front with a dowel in front of each side rail (Fig. 2), and with two blind dowel



joints that are positioned 834 in. from the sides of the top. Drill the holes for the blind dowel joint 1/2 in. into the plywood top and 1 in. into the birch frame.

Make the cabinet mobile by attaching casters (Fig. 2C). The 34-in. plywood caster blocks should be large enough so the casters clear the cabinet when it turns.

The type of flooring you have will determine how far the casters should extend below the cabinet. A 1/4-in. clearance between cabinet and caster is enough on tiled floors or on carpeting not backed with a thick pad. Use 1½-in. dowels to hold the caster mounting blocks in place.

While the cabinet is still resting on the top, glue the 3/4 x 3/4-in. corner blocks in the angles formed where the top meets the front, and the back stringer.


Final Step is to install the TV shelf and the top rails. Position the shelf and drill two pilot holes on each side so 11/2-in. fh wood screws can be driven in to add further support to the cabinet.

Cut the scrolled design on the side rails (Fig. 4), then attach them to the top with 5/16 x 2-in. dowels. The back rail fits between the side rails, and is held in place with three dowels.

The Weldwood veneer strip used to cover the exposed edges of the top can be applied with glue and pressed in place with a small block (Fig. 3). An excellent bond can be assured if a hot iron is run over the strip immediately after it is positioned. After the glue sets, trim any surplus veneer edge with a razor blade and sand smooth. Since the veneer strip is so thin, no mitering is required, only a light sanding and rounding of the edges.

Lightly sand the cabinet with a fine abrasive paper and slightly round off the edges. After thoroughly cleaning the wood surfaces. apply a light coat of Miniwax Early American stain. Brush on two coats of clear lacquer. Rub on several coats of paste wax.

A Musical Annunciator

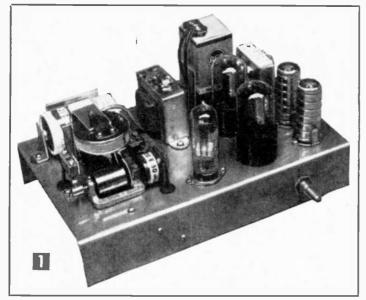

With this device hooked into your front door-bell circuit, you substitute the soft, tinkling tones of a music box for the jangle of bell, rasp of buzzer or raucous cling-clang of chimes

By HARTLAND B.
SMITH, W8VVD


An electronically amplified Swiss musical movement (at left front) makes a pleasant daar annunciator.

THE heart of this annunciator is its Swiss musical movement. Powered by a miniature 110-v, shaded-pole motor, this movement will play a 20-second excerpt from one of your favorite melodies. (The available tunes range from Adeste Fideles to the Third Man Theme, so you should have little difficulty in finding a composition to suit your taste.)

If this tiny music maker is to be heard throughout your home, however, some form of amplification must be employed—and the amplifier must be ready to operate the instant the front door button is pressed.

For economy's sake, no power should be drawn by the unit during standby periods. Consequently, heater-type vacuum tubes cannot be used. The choice, therefore, lies between battery tubes and transistors. Despite continued transistor price reductions, the capacitors, transformers, etc. needed for transistor circuitry are still relatively expensive. In contrast, the parts required for a vacuum-tube amplifier are quite reasonable and, in addition, many are likely to be found in the average experimenter's junk box. For this reason, the unit shown in Fig. 1 utilizes filament-type tubes rather than transistors.

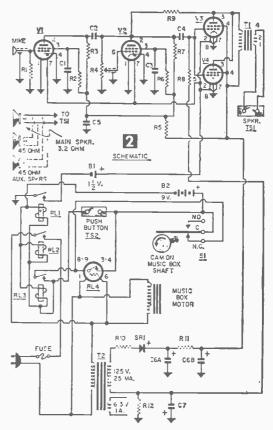An inexpensive high-output crystal lapel mike converts the sound produced by the musical movement into electrical impulses. These impulses are fed to the control grid of vacuum tube V1 (see Fig. 2). A dynamic mike cannot be employed at this point, be-



cause it would be sensitive to the hum resulting from the magnetic field that surrounds the motor. A vibration pickup mike, as used for electric guitars and similar musical instruments is also impractical, because of its sensitivity to the mechanical noises generated as the motor and its associated gearing operates.


Because of this mechanically generated noise, a relatively shockproof bracket (see Fig. 6) must be used to mount the mike. This bracket makes use of a small section of plastic sponge to deaden vibrations which would otherwise travel up the mount and excite

the mike.


In most respects, the four-tube amplifier is of conventional design. Since the power capability of a single 3Q5GT is rather limited, two of these tubes are operated in parallel. The extra 3Q5GT provides a very useful increase in power output. Parallel, instead of push-pull operation was chosen because no phase inverter tube is needed and an inexpensive output transformer can be employed. Preliminary tests of the completed amplifier showed that its overall gain was so high that there was a tendency toward self-oscillation when the volume control was well advanced, but the addition of resistor R9 (see Fig. 2) provided sufficient inverse feedback to lower the gain and completely eliminate the oscillation problem. The use of inverse feedback also improved the frequency response

and minimized distortion in the output stage. When the annunciator is first plugged into the line, no power can be drawn because relay RL2 is open. However, as soon as the pushbutton is pressed current from the 9-v battery will flow through the coils of RL1, RL2, and RL3. Relay RL2 closes and applies 110 volts to the primary of T2, to the heater of delay relay (RL4), and to the motor of the musical movement. Relay RL1 closes and applies filament power to the tubes. The amplifier becomes operative at once and the tones of the musical movement are heard via loudspeakers placed in convenient spots throughout the home.

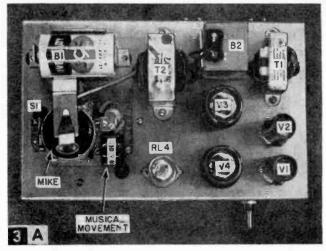Relay RL3 also closes at the instant the button is pressed. The contacts of RL3—as long as RL4 or S1 remain closed—act as a short across the pushbutton. Thus, current continues to be supplied to the coils of RL1, RL2 and RL3 via the contacts of RL3, even



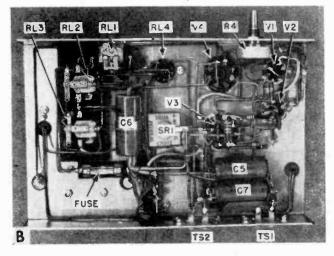
Top-chassis (above) and bottom-chassis (below) views of annunciator circuitry.



after the visitor stops pressing the button.

As the unit operates, the heater in RL4 warms up. After a period of approximately 10 seconds, it becomes so hot that the bimetal arm in RL4 bends far enough to open the normally closed contacts of this relay. At the moment, this action has no effect on the operation of the musical movement or amplifier because the points of RL4 are paralleled by those of S1, the miniature snap action switch operated by the cam on the shaft of the musical movement. As soon as the 20second tune has been completed, the cam opens S1, breaking the current path from the 9-v battery to the coils of RL1, RL2 and RL3. The relays open and the entire unit shuts down until such time as it is reactivated by the push-button.

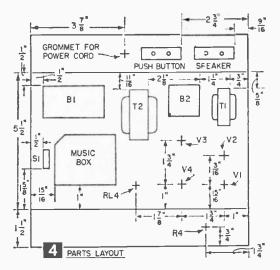The cam on the music box is constructed from a short length of volume control shaft and a 6-32 machine screw (see Fig. 5). This



cam must be so positioned that it actuates the lever of S1 when the tune on the barrel has been completed.

The power transformer T2 in Fig. 3A happens to be a surplus unit designed to provide 125 v at 25 ma and 6.3 v at 1 amp. A suitable substitute would be a Knight 62G008 which furnishes 125 volts each side of center-tap,

Desig. R1, R6, R8

R2

R9

R10

R11

R12

R4 R5

RL4

Ϊī Ť2

B1 B2

SR1 Sl T\$1, T\$2

Fuse

V1, V2 V3, V4

Musical movement

R3, R7

SHAFT EXTENSION N.O. ON DRUM OF MUSIC N.C. B MOVEMENT 6-32 X 1 = ACTUATING LEAF SPRING MACHINE SCREW OF SWITCH SUPPORT BKT. LENGTH OF 4 SHAFT 5 ALUMINUM CUT FROM OLD VOLUME STRIP CONTROL . DRILLED LENGTHWISE TO SLIP OVER MUSICAL MOVE-MENT SHAFT. DRILL AND TAP FOR 6-32 SCREW METHOD OF ACTUATING SI $\times 1\frac{1}{2} \times \frac{1}{2}$ CUT FROM SOFT PLASTIC SPONGE 2 00 2" 4

SHOCK PROOF MOUNT FOR MICROPHONE

MICROPHONE

MOUNTING HOLE

BAND OF SCOTCH ELEC. TAPE

plus 6.3 v. Only half of the high-voltage secondary on the 62G008 should be employed with the center-tap going to R12 and one end of the high-voltage winding going to R10. Since the other end of the secondary and the 6.3-v leads are not required, clip them short and insulate with electrical tape.

The two small batteries B1 and B2 are subjected to so little use in this particular device that they can be expected to have almost shelf life. Consequently, the battery cost per month will be insignificant.

Constructed on a 1½ x 5½ x 9-in. aluminum chassis, the amplifier is easy to wire since there is plenty of room between the components for the tip of a soldering iron. The armatures of the three small relays are directly connected to the frames. Therefore, RL2 and RL3 should be insulated from the chassis. Figure 3B shows how these relays are mounted on a thin sheet of Bakelite. Any easily worked plastic can be substituted for the Bakelite.

No knob is needed on the shaft of R4. Once the volume has been set to the desired level, no further adjustment is necessary. Battery B1 is kept in place with a home-made battery holder (or use a commercially built holder, such as a Keystone type 175). Two L-shaped brackets bent from small pieces of aluminum clamp battery B2 in position. Since the No. 5

```
MATERIALS LIST-MUSICAL ANNUNCIATOR
```

Description
2.2 megohm, ½ watt (Allied 1MM000)
1 megohm, ½ watt (Allied 1MM000)
220,00C ohm, ½ watt (Allied 1MM000)
330,00C ohm, ½ watt (Allied 1MM000)
75 ohm, ½ watt (Allied 1MM000)
560 ohm, ½ watt (Allied 1MM000)
330 ohm, ½ watt (Allied 1MM000)
500,00C ohm volume control (Allied 29M773)
33,000 ohm, 1 watt (Allied 1MM020) Description 33,000 ohm, 1 watt (Allied 1MM020) .01 mfd. disc ceramic capacitors (Allied 11L437) 12 mf., L50-v electrolytic capacitor (Allied 15L194) C1, C2, C3, C4 C5 C6 20-20 mf., 150 v electrolytic capacitor (Allied 151247) 100 mf., 15 v electrolytic capacitor (Allied 161236) Sigma 11F-1000G-SIL SPDT Relay (Allied 75P068) RL1, RL2, RL3 Amperite 115C10T miniature delay relay (Allied 75PP296) Knight power transformer 125-0-125 v, 25 ma; 6.3 v, 1 amp (Allied 6260081 021000)
11/2 v sire D A battery (Allied 80J903)
9 v battery VS-305 (Allied 80J838)
Federal 1002A, 65 ma. rectifier (Allied 4A606)
Unimax USML SPOT Subminiature leaf switch (Allied 34B848)
2 screw ferminal strip (Allied 41H505) Crystal lapel Mike (Lafayette PA-9) for 1 size D cell (Lafayette MS-175) 3AG 1/2 amp (Allied 52B232) 1U5 tube Battery Holder 3Q5GT tube Reuge ELR 1.18 110 v. 60 cps with extended shaft. From Novelties of Oistinction, 131 West 42nd St., New York 36, N. Y., or direct from the manufacturer, Reuge S.A., 26, Rue des Rasses, Ste. Croix, two octal tube sockets (Allied 40H058) one 9-prong miniature socket for RL4 (Allied 41H534) two 7-prong tube sockets with shield (Allied 40H194) two 134" tube shields (Allied 40H198) open-end chassis $1\frac{1}{2} \times 5\frac{1}{2} \times 9$ " (Allied 80P440) fuse clip (Allied 52B292) three terminal tie-point strip (Allied 41H501) 5" loudspeaker, 3.2-ohm voice coil (Allied 81D617) wall baffle for 5" speaker

wire, power plug, assorted 4-36 and 6-32 screws and nuts Components available from Allied Radio Corp., 100 N. Western Ave., Chicago 80, Illingis, and Lafayette Radio 111 Jericho Turnpike, Syosset, L. f., N. Y.

pin on a 1U5 and the No. 1 and 6 pins of a 3Q5GT are not connected to elements within the tubes, those terminals on the sockets can be used as convenient tie points to support resistors and capacitors. Grid bias for the 3Q5GT's is obtained from the voltage drop across R12. Capacitor C7, the bias filter capacitor, must be wired with its positive terminal grounded.


Locate the amplifier where output from the speakers cannot get back into the microphone to produce acoustical feedback—put it in the basement or, if you have no basement, in a utility room. Wherever you put the amplifier, make certain that it is out of reach of your youngsters. With the exception of the terminals on the motor of the musical movement, which ought to be insulated with electrical tape, all high voltages appear only on the under side of the chassis. A fuse has been included as a protection against overheating which might result from a shorted component.

Once it has been permanently installed, plug the amplifier into the power line and run a pair of wires from TS2 to a pushbutton near the front door. Run a second pair of wires from TS1 to the main speaker which may be a 4-in. or 5-in. unit with an impedance of 3.2 ohms. Mounted in a wooden baffle, this speaker can be placed at a convenient point in the most lived-in section of your

home.

Overall volume in any one part of the house need not be high, since additional speakers can be placed in those areas where the sound of the main speaker does not penetrate adequately. These extra speakers can be wired in parallel with the main speaker as shown in Fig. 2. Since the desired volume level at remote locations will normally be less than that of the main speaker, intercom replacement units with 45-ohm voice coils will work effectively in these spots. Each intercom speaker will give adequate acoustical output to cover a room or two, but because of the relatively high impedances involved, even when several are connected in parallel. they will not seriously shunt the 3.2-ohm main speaker.

The electronically amplified music box, as a replacement for an ordinary door bell or chime has a number of important features, in addition to its basic one of providing pleasant music. Unlike the ordinary bell or solenoid-operated chime, it plays for a period of 20 seconds, whether or not the pushbutton is held down. The sound of a doorbell is usually of rather short duration and is often masked by noises around the house. On the other hand, the continued output from the music box tends to get through such distractions as children's voices, loud hi-fi's, clacking typewriters, and pounding hammers.

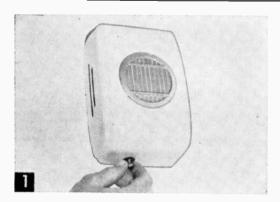


Door Bell Silencer

ERE'S a simple way of silencing that door bell so that it won't wake babies taking afternoon naps.

Obtain a small twist switch with threaded shaft and nut for mounting from your hardware store. Remove the cover or housing from your door bell and drill a hole through it large enough to pass the threaded shaft on the switch (Fig. 2). Make sure the switch parts inside the housing won't interfere with the bell mechanism.

Remove the wire coming from the bell

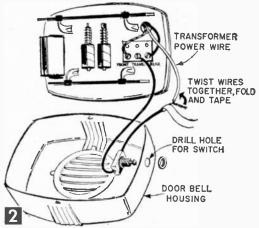

transformer from its terminal and connect one of the pigtail wires on the switch to the transformer terminal. Then connect the transformer wire to the other pigtail wire on the switch by twisting them together and taping.


You don't have to turn off the house current for this job—house bell circuits carry only 6 volts.

Replace bell housing, and have someone press door bell button so you will know if the switch is in the "on" or "off" position.

SHORTY:

the Compact 3-Band Antenna

By JOE A. ROLF, K5JOK

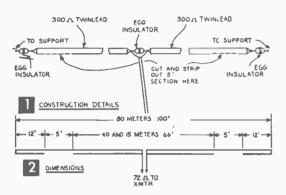

IMITED in antenna space? Here is an inexpensive three-band system that will fit the average backyard and is ideal for the novice amateur operator since it's designed for 80, 40, and 15 meters.

The system is constructed with 300-ohm television twin lead and consists of a 40- and

80-meter dipole with the same feed line at the center. The entire system is "shrunk" to 100 ft. by bending the 80-meter section back 12 ft. at each end. There is no noticeable sacrifice in performance.

Construct the antenna to the dimensions of Fig. 2, using a grade of TV twin lead such as Belden 8230 that is strong enough to stand the stress. Start by cutting two 50-ft. lengths of twin lead and attaching an egg insulator to one end of each piece. Tie the other ends to a single insulator to form the center feed point as in Fig. 1.

From each outer end, measure back 12 ft. toward the center, then remove a 5-ft. section of conductor from one side of the twin lead. Attach the feed line and the system is ready to go on the air.

Either 72-ohm coax or twin lead may be used for feeding the system. A 72-ohm twin lead reduces the weight which the antenna must support and keeps the system electrically balanced. There's an advantage to coax, however, in that it reduces feed line radiation and will prove easiest to connect to most transmitters. If neither is available, a good grade of plastic lamp cord can be used.

You should obtain adequate results with this antenna system of 80, 40, and 15, and it will also work fairly well on 20 and 10 meters. But for the best overall performance, use an

antenna tuner, if available.

Patch Up Test Clips




• When small, bare uninsulated test clips are used on 'hot' wires connected to live circuits, insulate the clips with rubber-tire patching. When ordinary clip insulators aren't available, tire-patching covers come in mighty handy. Simply sandwich the clip between two of the patches and bring the outer edges together and squeeze. The adhesive on the patching is sufficient so you won't need to use rubber cement.—J. A. C.

Rubber-Mount Treble Speaker

 Rubber suction cups are ideal shockmounts for treble loudspeakers. They make good mechanical mounts and acoustically isolate the speaker frame from cabinet panels which tend to accentuate the bass frequencies. Attach the cups to the speaker frame with screws (get the kind of cups having threaded inserts or screws) and to the cabinet panel with rubber or service cement.—John A. Ccmstock.

Easy Color Coding

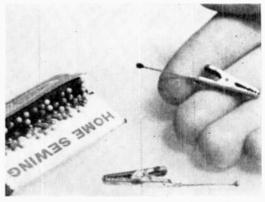

• Perhaps the easiest way to color-code test clips used for marking circuit wires or parts to aid servicing is to attach a colored dressmaker s pin to each clip. The colored head of the pin sticks out like a sore thumb against wiring. What's more the pins are inexpensive and available in dozens of colors.—J. A. C.



S&M Boat Designer Bill Jackson demonstrates search method. A 26-in. loop is wired into a 100-ft. cable made of lamp cord. When the coil approaches the metal object, a change in tone is heard.

Underwater Metal Locator

Pinpoints Submerged Treasure



This small coil locates pipes buried in walls, floors, and concrete and can also be used to search for buried metal objects.

By JAMES E. PUGH JR.

Craft Print Project No. 341

HETHER you are searching for a lost outboard motor or sunken loot, this easy-to-build underwater metal locator can make an otherwise impossible job both productive and interesting.

Just drop your search coil overboard, make a few easy tuning adjustments, then start searching. As the submerged coil nears a metal object, a tone is heard in the earphones. Since the detector responds to both ferrous and non-ferrous metals it is possible to locate nearly any metal object at the bottom of bays, rivers, lakes, and streams.

A low-frequency inductance bridge circuit minimizes the effect of water and cable length on sensitivity. This makes it possible to use an inexpensive unshielded cable, a 100-ft. length of rubber covered lamp cord between control box and search coil. If your treasure lies in deeper water this cable can be lengthened to 500 or 600 ft. with only a minor circuit adjustment. Similarly, it can be shortened to as

little as desired if you plan to work in shallow water or on dry land.

Besides the many possible underwater applications, this metal detector with a smaller coil can be used by landlubbers for finding buried pipes and tanks, shell fragments in old battlefields, ore deposits near the surface of the ground, and metal in lumber, logs, and livestock feed.


Transistorized circuitry is used for minimum weight, maximum battery life, and greatest resistance to mechanical shock. The inexpensive penlight size cells, easy to obtain, last about 100 hours in the oscillator and 200 hours in the amplifier section.

Detection range depends on size of the object, skill of the operator, and type of metal. Iron, steel, lead, and aluminum can be detected at a greater range than brass and copper. A small camera can be found at about 1 foot from the coil and a large outboard motor


at about 4 feet. Maximum range is about 5 feet.

Drill the Case as shown in Fig. 3. Holes are the same on the front and back, for mounting of controls and jacks. Wire the battery clips in series. and solder each lug to its eyelet to avoid a possible source of trouble later. Bend each end of the battery clips inward to obtain a firm connection with each battery as a high resistance contact can cause noisy and erratic operation. Put a dab of red paint near the positive terminal of each clip and fasten the battery holders in the case. Mount the other parts in the case and wire the negative battery terminals to the two switch sections.

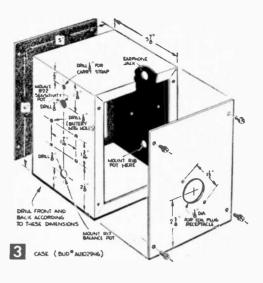Start construction of the two plastic chassis (Figs. 5 & 6) by drilling all holes and mounting the terminal lugs. Mark C, B, E, +, and - near the transistor and battery connections. Identify the lugs on both sides to help avoid wiring errors and to make circuit tracing easy. Position the larger parts and wire. Solder resistors, capacitors, and interconnecting wires next and the 1% resistors



	MATERIALS LIST-ELECTRONIC METAL LOCATOR
Parts	Size and Description
V1	2N217 PNP transistor, RCA (Newark 21F7004)
V2 V3	2N647 NPN transistor, RCA (Newark 21FX7105) 2N270 PNP transistor, RCA (Newark 21F7010)
V4. 6	2N649 NPN transitor, RCA (Newark 21F7/106)
V5	2N408 PNP transistor, RCA (Newark 21F7019)
T1, 2	20,000 to 1000 ohm transistor transformer, Argonne AR-104 (Lafayette
Т3	AR-104) 500 ct to 500 ohm ct transistor transformer, Argonne AR-162 (Lafayette
10	AR-162)
L2 L1	5.4 Hv variable inductor, UTC VIC-15 (Newark 3F414) search coil (info. for 3 sizes of search coils in Sept. '62 S&M))
Cl	.006 MF, 100-v., ElMenco 1DP-1-602 (Newark 14F1001)
C2, 3, 7, 8	.25 MF, 100-v., EJMenco 1DP-3-254 (Newark 14F1021)
C4, C10	.1 MF, 100-v., ElMenco 1DP-2-104 (Newark 14F1017)
C5 C6	.01 MF, 100-v. ElMenco 1DP-1-103 (Newark 14F1004) 1400 to 3055 MMF mica paddler, ElMenco 315 (Newark 14F817)
Č9	.0075MF, 100-v., ElMenco 1DP-1-752 (Newark 14F1003)
C11	.05 MF, 100-v., ElMenco 1DP-2-503 (Newark 14F1013)
R1	$1.2K$, $\frac{1}{2}$ w, 10% carbon (Lafayette RS-10)
R2 R3	2.7K, 1/2 w, 10% carbon (Lafayette RS-10)
R4. 5	2K potentiometer, linear taper, Mallory U-6 (Lafayette VC-419) 10K. 1/2w, 10% carbon resistor (Lafayette RS-10)
	2.2K, 1/2 w, 10% carbon resistor (Lafayette RS-10)
R7	2.2K. V_2 w, 10% carbon resistor (Lafayette RS-10) 3.9K, V_2 w, 10% carbon resistor (Lafayette RS-10) 26 82K, V_2 w, 10% carbon resistor (Lafayette RS-10)
R8. 20, 23, 2 R9	26 82K, 1/2w, 10% carbon resistor (Lafayette RS-10)
R10	56 ohm, $\frac{1}{2}$ w. 10% carbon resistor (Lafayette RS-10) 18K. $\frac{1}{2}$ w, 10% carbon resistor (Lafayette RS-10)
R11	3.3K. V ₂ w. 10% carbon resistor (Lafavette RS-10)
R12	330 ohm. 1/2 w. 10% carbon resistor (Lafavette RS-10)
R13 R14	500 ohm, ½ w, 1% deposited carbon, Aerovox CP½ (Lafayette CP-½) about 1.5 megohm, ½ w, 10% carbon (see text) (Lafayette RS-10)
R15	91K 1/2 w 1% denosited carbon Aerovov CPI/2 (Latayette KS-1U)
R16	91K. 1/2 w, 1% deposited carbon, Aerovox CP1/2 (Lafayette CP-1/2) 11K. 1/2 w, 1% deposited carbon, Aerovox CP1/2 (Lafayette CP-1/2)
R17	20K potentiometer, linear taper, IRC Q 11-119 (Lafayette VC-940)
R18	250 ohm, potentiometer, linear taper, IRC Q 11-201 (Lafayette VC-961)
R19. 21, 24, R22	25 4.7K, ½-w, 10% carbon (Lafayette RS-10) 5K potentiometer, audio taper, Mallory U-12 (Lafayette VC-423)
S1, 2	DPST switch, mounted on R22, Mallory US-27 (Lafayette VC-524)
	6-v batteries)8-1/2-volt Burgess 930 cells) (Lafayette BA-174)
2	battery holders for 4 type Z cells (Lafayette MS-182)
1	6x5x4" gray hammertone aluminum box, Bul AU1029hG (Newark 91F718)
2	rubber headphone cushions (Lafayette MS-34)
8	1/4" dia. x 3/4" threaded bushings, 6-32 thread (Newark 31F973)
2 8 3 4 1 2 33	1/2" skirted knobs, Davies 4104 (Newark 26F024) 5%" dia. rubber feet (Lafayette P-252)
i	shoulder strap and mounting hardware (at camera store)
2	31/2 x 33/4 x 1/32" Bakelite sheet
	Turret terminal lugs, USECO 1350C for 3/32" chassis (Radio Shack 16J432)
J1 J2	female receptacle, Amphenol 61-MIP-61F (Newark 39F116)
P1	phone jack, Switchcraft 11 (Newark 39F782) male plug, rubber covered (Newark 36F864)
P2	phone plug, Switchcraft 220 (Newark 39F768)
Phones	5000 ohm magnetic headphones, Cannon AM-15-5 (Lafayette ME-32)
Misc.	Note: Standard 2K phones will also work
m 136.	wire screws, nuts, washers, solder lugs, gaskets, rosin core solder

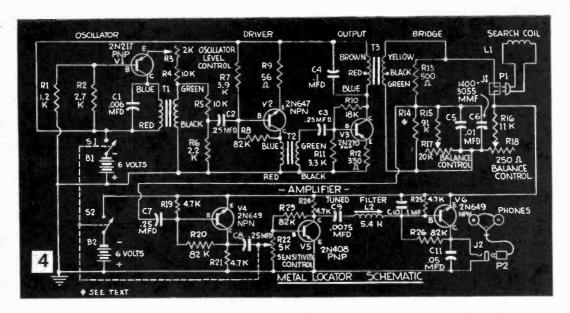


and transistors last. Hold these smaller parts with long nosed pliers to avoid damage from heat, being especially careful with the transistor and the 1% resistors.

Solder the wires connecting these two chassis to the jacks, batteries, switches, and controls to the chassis leaving adequate length to connect to the desired points. Trim and tin the ends, then when the chassis are mounted in place they can be soldered to the various parts in the case without risking damage to the small parts.

After all chassis wiring is completed, but

before mounting in the case, clean the rosin off with alcohol. Then spray thoroughly with CRC 2-26 waterproofing solution. Allow excess to drip off and carefully wipe with a clean, dry cloth. Be careful that you don't wipe the color code off the resistors. Spray the various controls (protect openings with tape) wipe off the excess, and then mount the chassis in the case and solder all interconnecting wires. Remove the headphone covers and diaphragms and spray the inside and cords. Wipe dry and reassemble.

Make gaskets for both control box covers

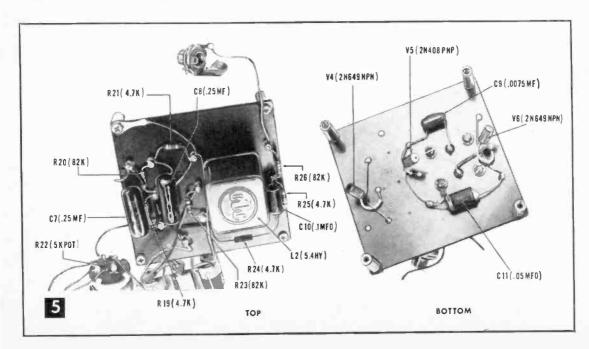


from rubber electrical tape or a thick gasket material. Fasten to the covers, and if you use the rubber tape, apply talcum powder to the upper surface to prevent its sticking to the case.

Principle of Operation. Transistor V1 (Fig. 4) is a stable, low distortion audio oscillator operating at approximately 1000 cps. Transformer T1 provides feedback as well as coupling from V1 to V2. R3 controls the oscillator feedback, thus the signal level and purity.

A voltage divider consisting of R5 and R6 reduces the input to V2 to a suitable level so as to help keep the waveform free from dis-

stability during temperature change at the least cost.

When the bridge is balanced, the signal transferred through it from the oscillator to the amplifier is minimum. When the search coil is brought near a metal object its inductance changes. This unbalances the bridge and permits some of the signal available across the secondary of T3 to be transferred to the amplifier where its level is increased and fed to the headphones. Therefore, as metal is approached a 1000-cycle note will be heard in the headphones—the closer and larger the metal the louder the signal will be.

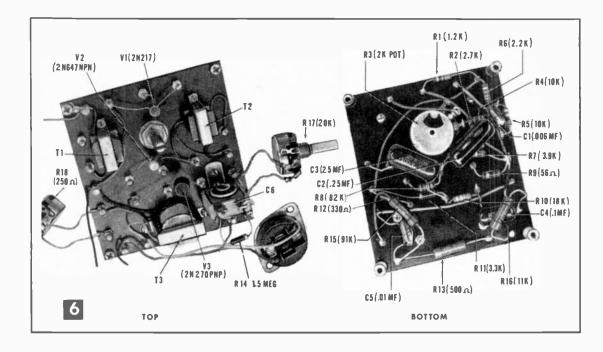

tortion. Transistor V2 amplifies the signal and isolates the oscillator from the output stage. This isolation improves oscillator stability since it prevents any change in the bridge circuit from reflecting back to the oscillator.

The output stage increases the voltage level to the bridge circuit for maximum detection sensitivity at the lowest harmonic distortion.

The bridge is a conventional Maxwell inductance bridge with the search coil L1 used as its inductive arm. Balance is obtained by comparing C5, C6, R14, R15, and R17 with L1. C6 is a trimmer capacitor used to compensate for manufacturer's variation in C5. It makes it possible to balance R18 at any convenient point of its range. Deposited carbon resistors at R13, R15, and R16 give maximum bridge

An adjustable filter consisting of C9 and L2 is tuned to 1000 cycles. It helps to increase the sensitivity by reducing the harmonics of the 1000 cycle note, thus makes small changes in the signal level more easily noticed. It also helps reduce 60-cycle pickup when operating the search loop near ac lines.

Capacitors C4 and C11 resonate with T3 and the headphones, respectively, to further improve the sensitivity by increasing the signal to harmonic ratio.

Separate batteries are used for the oscillator and amplifier sections to avoid coupling the signal from oscillator to amplifier through any circuit external to the bridge. This gives a better null when the bridge is balanced and maintains optimum sensitivity.

administration of the second of the second s

Now we shall describe the construction and use of three search coils that operate with the electronic detecting circuit. The largest coil (Fig. 7A) is designed for underwater use, while the 7-in. coil is intended for use on land in finding buried pipes and cables. The small, 2¾-in. coil will locate nails and even large tacks buried under plaster, or in auto tires.

Let's Start with the 17½ x 26½-in. oval search coil. Steam and bend the wood loop to shape (Fig. 8). But the ends together

a small rod through its hub so it will unwind easily without kinking. The rod can be held in a vise or with a cardboard box to keep it from shifting.

Pull about 1 ft. of the wire through one of the 1/16-in. holes in the frame and anchor by looping around the edge of the frame and back through the hole. Tape this end of the wire down to the inner face of the coil frame to keep it out of the way until the coil is

wound.

Wind one turn about 1/8 in. from the edge





Working from a boat or dock the large loop finds lost outboard motors, cameras and even keys. A small loop wound on a plastic tumbler detects nails and pipes in the wall.

and glue the 5-in. strip of wood on the inner surface of the frame. Clamp tightly to dry. When dry, sand and drill a 1/16-in. hole about 3/12 in. from each edge of the frame where the 5-in. joint is fastened.

If you prefer an easier way, the inner hoop from an 18 x 27-in. quilting frame (available at Sears, Roebuck) can be used instead. Trim the wood brace on the inner surface down to ¼ in., drill the ¼6-in. holes, and it's ready.

Winding the Coil. Find a clean, comfortable place to work, perhaps over a rug or heavy canvas to avoid scraping the insulation off the wire. Arrange the spool of wire with

of the frame and tape in place at 5-in. intervals. With the frame supported across the knees, rotate the frame with one hand and lay the wire on with the other hand. Press the wire in place with the thumb of the hand rotating the frame. Wind 10 turns and place strips of masking tape across these turns at 10-in. intervals. Every 10 to 15 turns, temporarily fasten the winding end down with masking tape and move these strips over to prevent wires from slipping off. Halfway through, and at the end of each layer, check that all wires are pressed together firmly, but do not push the outer turns off the frame.

Put 50 turns on the first layer. After adjusting the winding evenly on the frame, tape it down firmly with masking tape at 5-in. intervals. Remove the temporary strips of tape and save them for the next layer.

Start the First Turn of the second layer in slightly from the last turn of the first layer and tape. Wind 47 turns for the second layer, keeping it taped down as you go as with the first layer. Tape firmly in place at 5-in. intervals between the strips holding the first layer.

Repeat this procedure for a third layer of 44, a fourth of 41, and a fifth of 38 turns. The five layers total 220 turns. Loop the end of the last turn through the second 1/16-in. hole, tape the entire winding-down firmly, and the winding is done.


Next, assemble the search coil terminal strip up to the first nut (Fig. 8A). Tighten these nuts securely and tape this section of the terminal strip to the coil frame. Cut the coil wires, leaving 3 to 4 in. of slack, and care-

fully solder to the lugs. Fasten securely to the terminal strip with the second lock washer and nut, and tape the wires down, making sure there are no sharp bends or kinks.

Fiber Glass Tape and Resin coating waterproofs the coil. Add white coloring to the resin to make the coil visible in the water and to help avoid the chance of damaging it when not in use.

Follow the manufacturer's mixing instructions exactly. Work in a clean, warm, dry place (75-80°), but not in the sun. After mixing the activator with the resin, you will have to work fast, because the mix jells in 30 minutes. Until then, the resin is fluid and easy to work, but as it starts to set it stiffens rapidly.

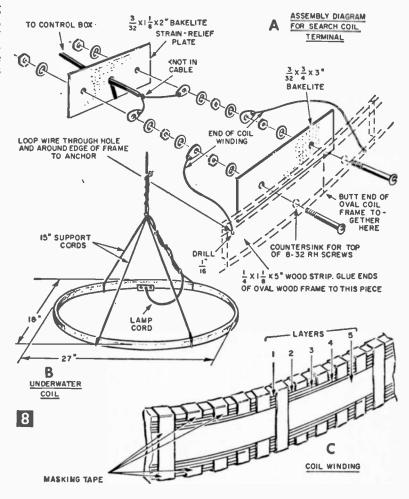
Roll the fiber glass tape into a small roll for easy handling. Keep hands away from the eyes, and keep children away. Fiber glass is safe and easy to use if you are careful, but



the tiny glass particles can irritate eyes and skin.

Open the resin and pour into a pint jar that can be sealed. With everything ready, pour 4 oz. of the resin into a small can, mix in about 1 teaspoonful of the white coloring, add the exact amount of activator, and stir thoroughly.

Using a 1-in. Paint Brush, generously coat the area around the wood brace and terminal strip, and about 1 ft. beyond with resin. Hook the fiber glass tape end over the terminal strips as an anchor and spiral-wind the tape to the end of the resin-coated section. Wrap snugly and overlap the windings about 2 in. Coat another 10 in. of the coil and frame with resin and wind on more tape to cover. Repeat until the entire coil has been covered. Overlap the start of the winding with one or two turns and tie the end down with a long strand of fiber glass taken from one edge of the tape.

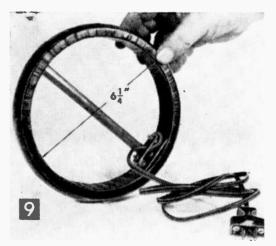

Seven inch coil detects pipes in walls, beams in concrete and small metal objects such as keys, and watches. Assembly steps are as follows:

- 1. Make 7" O.D., 6¼" 1.D. x 1½" cylindrical coil form by jig sawing out of solid wood, or of glued up sheets of plywood.
- Drill holes for terminal strip as for large coil.
 Install ½ x 6¼" wood handle.
- 4. Wind ½ lb. #28 Nyclad wire, 473 turns total, same way as large coil. Only first turn each laver.
- 5. Check balance with bridge circuit at least 3 feet from any metal object.
- To use with other coils, add about 10 turns and trim for balance at same control settings.

Now press the tape down around the terminals so that none is on or above the top surface of the 8-32 nuts. Clip off all loose threads from the tape edges and apply a heavy coat of resin to the entire surface of the tape. Work it in thoroughly with the brush, making sure all holes and seams are filled. If there are any large holes, fill with small threads of fiber glass mixed with resin. Wipe the threads of the 8-32 screws and the upper face of the nuts with a wet cloth to remove excess resin. Hang the coil in a warm dry place, and wash tools and hands with hot water and soap.

The Resin Will Harden in 24 hours. File all rough spots and connect the cable and strain relief plate. Now mix about 2 oz. of resin with the required amount of activator and stir in about ½ teaspoonful of white coloring for the second coat. Dry 24 hours and apply a third coat consisting of 1 oz. of resin, the specified amount of activator, and ½ teaspoonful of color.

Use a small amount of the resin to fill in all slots in the corners of the aluminum case for waterproofing. After drying, file smooth

and cover with grey paint.

Fasten the Completed Search Coil to the lamp cord cable with four 15-in. supporting cords (Fig. 8B), allowing slack to avoid strain

	MATERIALS LIST METAL LOCATER COILS
	LARGE COIL
Amt.	Size and Description
1	1/4 x 11/8 x 70" wood strip or 18 x 27" wood quilting hoop (Sears Roebuck Cat. No. 25K5510)
1	1/4 x 1/8 x 5" wood strip
î pc.	Bakelite, 1/14 x 11/8 x 2"
1 pc.	Bakelite, 3/4 x 3"
1	Fiberglass tape kit (Sears Roebuck Cat. No. 6K5787)
l pkg.	White resin color (Sears Roebuck Cat. No. 6K5764)
3 sets	Wire footage markers, 1-33; 34-66; 67-99. (Newark #30F200, #30F201 and #30F202)
1 lb.	#26 Nyclad magnet wire, Belden HNC 8079 (1260 ft.) Allied #48T092
100′	#18 lamp cord, Consolidated type POSJ (Allied #48T760)
1	16-oz. can CRC-2-26 (Northern Mining Equipment Co., Box 836, Hibbing, Minn.) For waterproofing headphones and control box,
	7-IN. COIL
_	
1	circular wooden or plastic coil form approx. 7" O.D., 6!4" I.D., x 11/2"
1	1/2 x 61/4" wood dowel to fit above as handle.
1/2 lb.	(Allied Radio #48 TO 43)
1/2'	Rubber covered lamp cord
	Bakelite strip, 5/8 x 11/2"
1 2	Bakelite strip % x 1%"
2	6-32 x 3/4" fh machine screws, nuts and washers for
M isc.	terminals
MINE.	Masking tape, plastic electrical tape, wood screws, appliance plug.
	SMALL COIL
•	
1	8 oz. plastic tumbler, 21 1/32" at top, 21 1/32" 0.D. at base. Konite #209, Plastics Manufacturing Co., 2700 S. Westmoreland, Dallas 33, Tex. Available
675'	restaurant supply houses.
Misc.	#29 Formwar Magnet Wire (Allied Radio #48T144) male appliance plug, lamp cord for cable, plastic elec- trical tape

on the terminal strip. Apply markers to the cable every foot for measuring depth. The reel on which the cord is supplied can be used in the boat, provided you add a grommet to a hole near the hub and feed about 4 ft. of the inner end of the cable through.

Operating Adjustments. With the search coil and headphones connected, set R3 for minimum output. Then balance the bridge for least signal. This balance adjustment is a step-by-step process. Alternately adjust the two balance controls for minimum output until the 1000-cycle note can not be heard. Practice until you can balance in five steps

Then adjust R3 slowly until you hear a distinct high-pitched note. This is a harmonic of the 1000-cycle note. Back R3 down until this note is barely noticeable. When you are approaching balance, the harmonic becomes predominant; when balance is reached, the 1000-cycle note will not be heard—only the harmonic will come through. Control R3 should now be near its mid-point.

If you have an oscilloscope, check for a 5-volt peak-to-peak signal across the bridge input. Then unbalance the bridge by rotating one of the balance controls off toward one end. The core of L2 is now adjusted for maximum output.

With the search coil in water and no metal nearby, adjust C6 until the balance point on R18 falls near the center of rotation. Also

check that the second balance control (R17) is near center. When the search coil is removed from the water, the balance controls will need to be readjusted, but the balance points should not be too near one end of their rotation. If R17 is too far off, trim by changing the value of R14. Normally this resistor will be near 1½ megohms. If you plan to use the metal locator on dry land, balance adjustments must be made with the coil in air and no metal nearby.

Check the adjustments again, then lock L2 adjustment screw with a dab of cement.

Operation in Water. For best results with any metal locator, it is necessary to practice adjustment and search procedure. Improper

use can cut your range in half.

This metal locator was designed to be used in boats. Or a diver can manipulate the search coil; while a helper operates the control box above. The large oval loop produces a field that combines the advantages of larger and smaller diameter loops. It will detect objects ranging from a camera to an outboard motor and—at close range—coins and keys. If there are strong water currents, tie small bags of sand to the loop frame for additional weight.

With the control box on a shoulder strap, one hand is free to manipulate the search coil while the other adjusts the controls. Lower the coil into the water, and while well away from all metal objects, adjust the two balance controls for minimum earphone signal. Then set your sensitivity control so the harmonic and amplifier noise are clearly but not loudly heard. If the sound is too loud, your car will not readily detect the 1000-cycle

note when you approach metal.

Lower the search coil to the bottom, then raise it slightly, the distance depending on the size of the lost object. For example, if you are seeking a small camera, the search coil should be about 1 ft. from bottom. For outboard motors, about 3 ft. would be right. As you search, frequently drop the coil until it hits bottom, taking note of your cable depth markers, since there may be deep drop-offs on the bottom.

If there is a considerable difference between air and water temperature, you will have to readjust your balance controls (mostly R17) during the first few minutes, because temperature changes affect the search coil resistance. When the coil stabilizes at water temperature, only an occasional re-balance will be needed.

As soon as you suddenly hear the 1000-cycle note, it is likely the search coil is near metal. Move the coil back and forth over that spot to get an idea of how large the object is, and where the signal is maximum. Raise the coil, and mark the find with an anchor and marker float to guide diving or grappling. Many small ferrous objects can be pulled up



Small coil locates nails and tacks in walls and tires. A $\frac{1}{4}$ brad can be detected at 2 inches.

- Wind coil on 8-oz plastic tumbler available at hardware stores. Diameter is approx. 2 19/32".
- Drill lateral holes through tumbler and feed stiff wires through as guides for winding.
- Wind about 950 turns #29 Formvar Magnet wire, and trim for balance setting to match other coils.

4. Cover with plastic electrical tape.

with high powered magnets.

The detector will also indicate the kind of metal. Small ferrous objects will cause the bridge to unbalance in one direction, while non-ferrous objects will cause an opposite unbalance. A difficulty arises because objects the size of the coil and larger cause just the opposite effect. By first estimating size of the object, you can judge the type of metal.

After locating a metal object, readjust R17 for an approximate null. Then adjust R18 for null, noting which way it has to be rotated from its original setting. It is labeled to show the direction of rotation for small items; for large objects, this indication will be reversed.

• Craft Print No. 341 in enlarged size for building the underwater metal locator is available at \$3. Order by print number. To avoid possible loss of coin or currency in the mail, we suggest you remit by check or money order (no CODs or stamps) to Craft Print Div., SCIENCE and MECHANICS, 505 Park Ave., New York 22, N. Y. Please allow three to four weeks for delivery. Special quantity discount! If you order two or more craft prints (this or any other print), you may deduct 25¢ from the regular price of each print.

Shield Simplifies Soldering

Soldering in crowded wiring of a circuit is simplified if the upper portion of a waxed milk carton is used as



a shield. This helps avoid touching adjacent parts with the hot soldering iron or gun tip, helps you concentrate on the work, and often catches excess drops of solder.—John A. Comstock.


Trouble-Shooting Interference

How to discover the source and eliminate noise in a radio or amplifier

By FORREST H. FRANTZ, Sr.

We usually differentiate interference as either hum, buzz, squeal, noise, distortion or station interference. Sometimes these are due to faults in the gear, sometimes to external sources. Frequent internal causes are: open, shorted or leaky capacitors, intermittent connections, intermittent short circuits, defective tubes and dampness. The antenna-ground system is also a frequent trouble spot. Externally caused disturbance is often traced to switches, thermostats, advertising signs, motors, radio stations and high voltage lines.

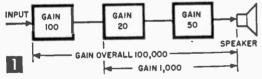Let us look, first, at hi-fi audio amplifiers, remembering that this discussion is applicable also to the AF section of radios. Then we will cover radios specifically.



Hum introduced in first stage is amplified more than hum introduced in subsequent stages.


Audio Amplifiers. Amplifiers may exhibit interference in the form of hum, buzz, squeal, noise or distortion.

Hum in an amplifier is usually caused by insufficient shielding of the amplifier input circuit. The various stages of an amplifier have individual gains, which multiply as shown in Figure 1. The first stage usually has the highest gain. Thus, the gain from the first stage to the loudspeaker is much greater than the gain from any succeeding stage to the loudspeaker. If even a small portion of an amplifier input lead is unshielded, it acts as a capacitor to the ac line though it may be many feet away. A small amount of alternat-


ing current can therefore feed into the amplifier. The high gain of the amplifier multiplies this minute voltage into a sizeable signal at the loudspeaker.

Hum due to poor input shielding is easily recognized, since the loudness of the hum will decrease as the volume control setting is decreased. There are several steps to pinpointing and curing this. First, dress the input lead close to the chassis. The input lead can be traced from the input connector and usually goes to the high volume control terminal (possibly through a capacitor) as shown in Figure 2. The center terminal of the volume control goes to the grid of the input tube (possibly through a capacitor). In some amplifiers, a preamp stage precedes the volume control. If the input tube is glass, a shield may cure hum. Next, check the shell to chassis ground connection of the input connector. Then check the connection from the external input plug to the braided shield which encircles the unit's input lead (Figure 3). An open can cause hum.

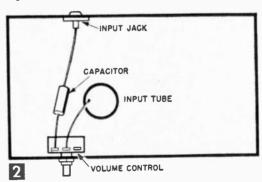Sometimes, in cheap construction, unshielded leads are used, and should be replaced. An open circuit from shield to ground or at the chassis connector results in loss of gain because the shield is frequently the chassis ground return conductor. Finally, check the ground connection at the remote input device and look for short lengths of



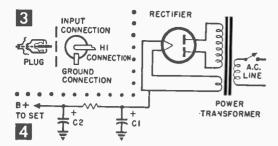Leads likely to pick up hum. Remedy is to substitute shielded cable, dressed close to chassis.



 A broken shield or disconnection from plug ground or a faulty or open input jack can cause hum pickup.
 Filter capacitor (C1), which if open, causes hum in amplifier power supply. Leaky power supply output filter capacitor (C2) will cause hum or squeal.

input lead which may be unshielded.

Hum which occurs at all volume settings is often due to defective filter capacitors in the amplifier power supply, as shown in Figure 4. (The rectifier tube is connected to the power transformer and the high voltage electrolytic capacitors.) To test the filtering, bridge a 10 mfd. electrolytic (watch the polarity) across C1. The voltage rating should be equal to or greater than that of C1. If hum decreases, you're on the right track. Disconnect C1, and connect a replacement capacitor of the same or greater voltage and the same capacity in the circuit. If the hum is substantially reduced, replace C1 permanently. Otherwise, connect the original C1 back into the circuit, and bolster the filtering action with the 10 mfd. capacitor that scored the original improvement. If this isn't enough, try a 40 mfd. capacitor of adequate voltage rating across C2.

Caution! Don't work on an amplifier that has been used in the last few minutes—wait

until capacitors discharge.

If you still haven't cured the hum, check for cathode to heater leakage in tubes, poor connections to chassis ground within the amplifier, and open or partially open capacitors elsewhere in the circuit (can usually be found by bridging with another capacitor).

Squeal in amplifiers may be due to open filter or bypass capacitors, which can be traced by employing the capacitor bridging technique described previously. Another cause of squeal is feedback caused by a high level signal lead being too close to an early amplifier stage lead—shorten the lead and

dress it close to the chassis.

Noise may be due to a bad volume control, a microphonic, shorted or intermittent tube (which can often be located by tapping with a pencil eraser) or a rubbing loudspeaker voice coil (most readily checked by substitution of another speaker). Noise can also be caused by an intermittent capacitor (thump and jiggle the suspect), by poor connections which may be loose or intermittently shorted,

by intermittently shorting output or interstage transformer windings or by arcs across rectifier or output tube sockets (usually indicated by a charred section of tube socket or a visible arc during operation).

Distortion in amplifiers is usually caused by leaky coupling capacitors (C4 in Figure 5). Coupling capacitors may be checked by substitution, but this requires disconnecting one end of the original capacitor. Other sources

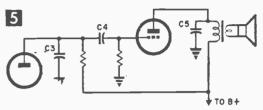


Plate bypass capacitors (C3 and C5) or coupling capacitor (C4) if leaky can cause distortion.

of distortion are leaky power supply output filter capacitors (C2 in Figure 4) and leaky bypass capacitors. Plate bypass capacitors (C3 and C5 in Figure 5) are likely offenders. In each of these cases, one end of the original capacitor must be disconnected before substitution of a similar capacitor is attempted. Another frequent cause of distortion in amplifiers is a gassy tube. Output tubes are the usual offenders.

Radios. Radios are subject to all the amplifier disturbances described, and the same solutions apply. In addition to amplifier trou-

bles there are other possibilities.

Hum caused by some strong local radio station can usually be cured by connecting a 0.05 mfd., 600 v. capacitor from one side of the ac line to chassis ground as shown in Figure 6A. If the set is ac-dc (no power transformer), the capacitor should be connected from the set side of the switch to the opposite side of the line as shown in Figure 6B.


Buzzing is due to external sources such as neon signs, motors, or high voltage lines.

Squeals may be caused by any of the things already discussed under audio amplifiers or may be due to open bypass capacitors, long unshielded RF or IF leads or other causes. Long leads on IF transformers are frequent causes of squealing.

Noise may be due to internal or external trouble. If the set uses an external antenna,



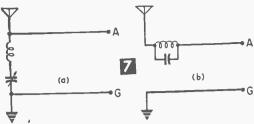Suppressing a strong local station by connecting .05 mfd capacitor from one side of line to chassis ground for ac radio (a) and from set side of the switch to opposite side of line for AC-DC radio (b).



Suppressing an unwanted station with a wave trap, a tuned circuit across the antenna ground terminals

(a) or in series with the antenna terminal (b).

disconnect it, and short the antenna terminal to ground. If the noise persists, it's in the receiver. Arc in the power supply, intermittent connections almost anywhere in the set or defective tubes are possibilities. Next, check the antenna by disconnecting it and connecting 20 ft. of wire to the antenna terminal. Noise in an antenna may be due to poor or corroded connections at the antenna, lightning arrestor, feed-in to the building, a break in the lead-in under the insulation or to the antenna or lead-in contacting metal such as the storm gutter.

Assuming noise to be external to the receiver, a capacitor connected as shown in Figure 6A or 6B may be helpful if your receiver doesn't already have one. If this doesn't help, try tracking down the external causes

which were mentioned early in this article. For example, if noise occurs around meal times, it may be an electric stove or other appliance. Or, say the noise occurs only in winter—could be the thermostat.

The type of noise your receiver picks up is also a clue to its origin. Switches, relays, thermostats and poor electrical connections cause intermittent noise. Motors and industrial and medical electronic equipment produce a buzz or whine in nearby radios. High voltage lines produce a hum or buzz with a super-imposed crackle in radios. High voltage line noise is continuous, and the crackling is worse in damp weather.

A battery receiver, that has automatic volume control (which you must disconnect for this purpose) and a directional loop antenna, is helpful in tracking down noise.

When the source of noise is located, a commercial filter installed at the source of the noise will usually cure the trouble. These filters usually consist of capacitors or capacitors and inductors.

Distortion is usually due to AF section trouble. Refer to the previous discussion of distortion in connection with audio amplifiers.

An interfering radio station can be eliminated by a wave trap, a tuned circuit across the antenna-ground terminals (Figure 7A) or in series with the antenna terminal (Figure 7B) tuned to the frequency of the interfering station.



Wireless Remote TV Sound

Easily constructed unit permits private listening

By W. F. GEPHART



With TV speaker silent, the sound is picked up remotely by an earphone-equipped transistor radio.

VER wish the TV set had earphones when the kids were watching a Western, or when someone is trying to sleep in the next room? It can be done, but usually requires a long cord stretching across the room to the earphones or a small speaker. It also requires an earphone, or extra speaker, and limits the movement of the listener.

With this little transistorized oscillator, the main TV speaker can be cut off, and the sound picked up anywhere in the room with an ordinary radio. If a transistor radio is used, the earphone can be used for complete privacy or the speaker used for listening in a small area. Even with an ac-dc radio, the sound can be cut down so that it doesn't bother others.

The unit, similar to a wireless phono oscillator, is mounted on the back of the TV set, and is turned on by a switch accessible at the top of the back of the cabinet. This switch also connects the TV sound to the unit, and

cuts the TV speaker out.

The circuit (Fig. 4) consists of a transistor oscillator (TR1), operating in the broadcast band, which can be tuned to a blank spot on the radio dial. It also has an AF transistor modulator (TR2), and an optional power supply. It can be built for less than \$10 without the power supply, and for about \$15 with the power supply.

Through the use of an adapter for the TV audio tube, connections to the TV set can be made without modifying the TV set wiring. In some cases power from the TV set can be picked up for the unit, and in other cases, the standard 9-volt transistor battery is used. Since only 5 ma is drawn by the unit, a battery will last from several months to a year, depending on usage.

Circuitry. There are two general types of circuitry used in TV audio output stages, as explained in Fig. 3. The unit will work with any of these circuits, but battery power must

be used if the TV set uses a circuit similar to 3C, or if the cathode voltage in circuits 3A or 3B is less than 13.5 volts. To determine the circuitry used and the cathode voltage, secure the adapter mentioned in the materials list, and solder the leads together.


Plug the adapter into the audio tube socket, and the audio tube into the adapter. (Typical audio tubes in TV sets are 5BQ5, 6AQ5, 6BQ5, 6V6, etc. Usually the tube location guide pasted on the back or inside the set will tell which is the audio output tube).

With the set on, measure the voltage between the cathode pin on the adapter and the set chassis. If it is relatively low (25 volts or less), the circuitry is probably similar to Fig. 3A or 3B and a self-powered oscillator can be used. If the voltage is relatively high (90 volts or more), the circuitry is probably similar to Fig. 3C, and a battery supply must be used for the oscillator. Even if Fig. 3A or 3B circuitry is used, a battery supply must be used if the cathode voltage is less than 13.5 volts.


Construction. Most of the parts are mounted on a 2x2-in. piece of Bakelite. The author used a surplus terminal board, but a similar mounting can be made as shown in Fig. 7. This board is wired first, and then mounted in the box with either a battery or power supply, as shown in Fig. 8.


Since this unit must work with various TV sets, some modifications may have to be made. The volume control (R1) can be eliminated in most cases, and in some cases it loads the oscillator enough to reduce the output depending on the size of the grid resistor in the TV set. Obviously, R4 is not needed


	MATERIALS LIST-REMOTE TV SOUND
Desig.	Description
R1	1-meg potentiometer (Mallory U-54; Allied 29M777) (see text)
R2	.15-meg, 1/2-w, 10% resistor (Allied 1M M000)
R3	47K. I/2.w. 10% resistor (Allied 1MMUOU)
Cl	10-mfd, 450-v capacitor (Sprague TVA-1705; Allied 15L225)
C2	10-mfd, 25-y capacitor (Sprague TVA-1204; Allied 15L205)
C3	01.mfd, 50-y capacitor (Sprague S-10; Allied 15L996)
C4	270-mmf, capacitor (Cornell-Dubilier CD15-5T27; Allied
C5	100-mmf, capacitor (Cornelf-Dubilier CD15-5T1; Allied 20L023) or 25-280 mmf trimmer (Allied 60H343) (see text)
L1	Loopstick antenna (Miller 705A; Allied 60H893)
S1	4-pole, 2-pos. rotary switch (Mallory 3242J; Allied 348356)
TR1	Sylvania 2N1265
TR2	Sylvania 2N1264 Parts Below Required If Power Supply Used
R4	1500-ohm w.w, potentiometer (IRC WPK1500; Allies
C6	500-mfd, 25-v capacitor (Sprague TVA-1209; Allied 151869)
C7	500-mmfd, 15-v capacitor (Sprague TVA-1162; Allied
L2 Misc.	20-hy, 15-ma choke (Stancor C-1515; Allied 64G058) 3 x 4 x 5" Minibox (Bud CU-2105A), 7-pin min. socke adapter (Vector TX-7M), knob, two terminal tie point miscellaneous hardware Above parts available from Allied Radio Corp., 100 N Western, Chicago 80, 111.

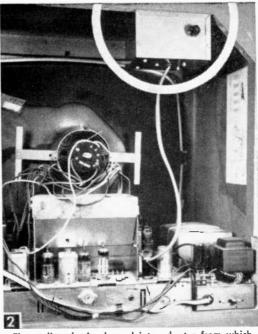

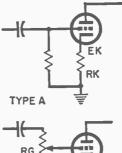The audio tube is plugged into adapter from which cable leads to unit attached at top of TV cabinet.



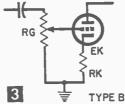

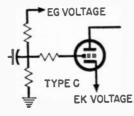


This type is also found as half of a push-pull output circuit. Cathode voltages (E_k) vary from about 7 to 172 volts, depending on tube and manufacturer. Cathode resistors (R_k) vary from about 200 to 560 ahms, depending on tube and manufacturer.

This is essentially the same as type A, except that the volume cantral $\{R_c\}$ is in this stage. Cathode valtages $\{E_k\}$ vary fram about 5 to 16.5 valts, depending on tube and manufacturer. Cathode resistars $\{R_k\}$ vary from about 82 to 680 ahms, depending on tube and manufacturer.

Grid voltages (E_E) run from 120 to 135 volts (pasitive), depending an tube and manufacturer. Cathade voltages (E_k) run from 135 to 150 volts (positive), depending an tube and manufacturer. (These combinations give a negative grid bias of about 15 volts.)

Typical Audio Output Tubes 5AQ5 6BQ5 12C5 6AQ5 6DG6 12CU5 6V6

Types of Output Circuits

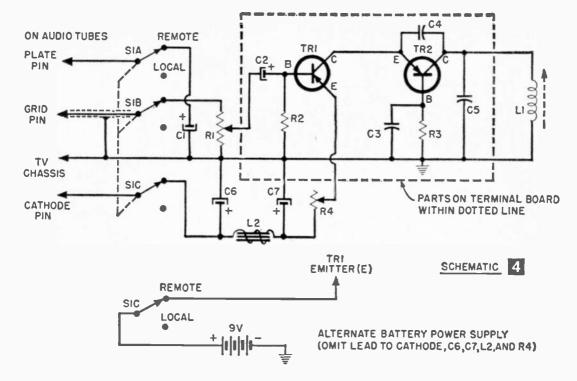


when battery power is used.


A small loopstick is used for L1, but larger units give better range. The one shown was later replaced with a larger one, and C5 changed to a 280-mmf trimmer. Small loopsticks, such as the Superex "Ferri-loopstick" (shown in the pictures), "Vari-Loopstick," and Miller #2002 or #2007 are compact and adjustable, but have limited range. Larger units, such as the Superex "7-in. Loopstick," and Miller #705 and #2000 take more room and will require an adjustable trimmer for C5, but will give greater range. These units will also permit the addition of a length of wire for an antenna without appreciably al-

tering the oscillator frequency. Where space is available, the larger units are recommended.


Adjustments. When the box is in place and connected, the only adjustment required is the frequency setting. Turn the TV set on, and set to a channel. When it has warmed up and the sound is good, switch to a vacant channel.

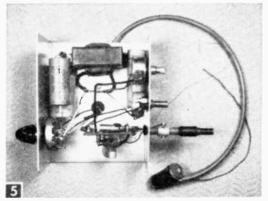Place a small radio on the TV set, and turn the knob on the unit to the REMOTE position. Gradually tune the radio through the broadcast band until you hear a whistle. Tune the radio to the center of the whistle, and then switch the unit to LOCAL to verify



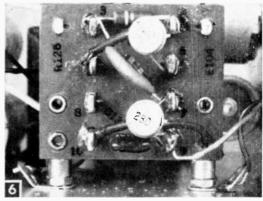

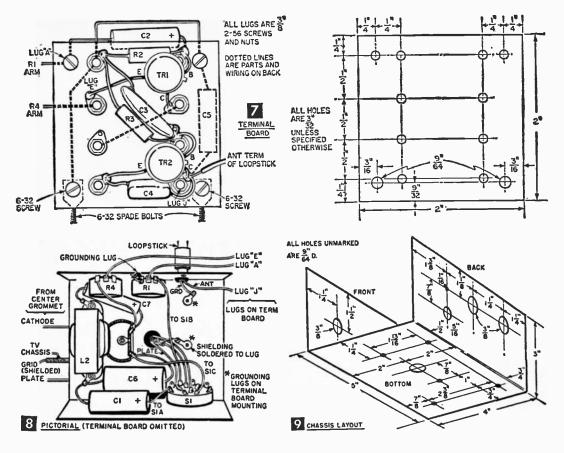Interior view of unit showing power supply, cord, and adapter. When battery is used, it is placed where choke and capacitors are located. Close-up of terminal board showing resistors and capacitors.



that the whistle is from the unit, as indicated by the whistle stopping.

If the output seems weak, and appears above $1100\ kc$ on the radio dial, retune for half the frequency shown. This is to make sure that you are not picking up the 2nd harmonic of the oscillator. If, with a weak signal, the radio is tuned below $1100\ kc$, raise the oscillator frequency by moving the slug farther out of the coil or loosening the trimmer condenser, and make the test to be sure you are tuned to the fundamental frequency.

Once the proper frequency is found, turn the unit to LOCAL, and turn the radio volume all the way up without moving the dial setting. Make sure there are no stations on the frequency that will interfere with operation. This test should be made at night when reception is best.

If the oscillator is not tuned to a blank spot on the dial, its frequency can be changed by adjusting the slug in the coil (L1) on small units, or adjusting the trimmer (C5) on large coils. Moving the slug farther in the coil (or closing the trimmer) decreases frequency, and the reverse increases it.

Once the oscillator has been set to a blank spot on the dial, turn the TV set to a channel, adjust the sound to the desired level, and turn the unit on REMOTE. You should then pick up the TV sound on the radio, and can adjust the radio volume as desired. If, even at low radio volume and proper tuning, the sound is distorted, potentiometer R1 will have to be included, so that the sound input to the unit can be reduced.

You will find that, as you move the radio away from the TV set, the signal weakens. This can be minimized by attaching a 6- or 8-ft. piece of wire to the loopstick antenna post. If a small loopstick is used, this will change the frequency, so the radio or oscillator will have to be retuned. With transistor radios, position of the radio will also have an effect on signal strength as you move away from the TV set.

By eliminating C1, and using a high-gain radio, this unit can sometimes be of help to those with impaired hearing. It is often necessary for them to turn the TV sound up to a point uncomfortable for others. In some cases (where C1 is omitted) the TV sound can be adjusted to a comfortable level for all, the unit turned on, and the hard-of-hearing person can listen on an earphone-equipped radio set to the desired volume. With C1 omitted, the TV speaker remains in operation, even with the unit set on REMOTE.

HAM RADIO ANAGRAM

F AMATEUR radio is your hobby, you will have loads of fun working this puzzle. Those in other branches of electronics will have almost as much fun trying to figure out the lingo that isn't so familiar to them. After you think you have all the correct answers, turn to page 158 for the solution.

ACROSS:

- 1. Radio-frequency effect
- 10. No
- 11. Same as #2 down
- 12. Positive terminal of grid bias voltage source
- 13. Famed manufacturer of electronics gear (abbr.)
- 15. Changeable current (abbr.)
- 16. Positive grid of a vacuum tube (abbr.)
- 18. Wire tiedown point
- 20. The maximum input
 ---- permitted
 for operating a
 transmitter with a
 novice class license
 is 75 watts
- 23. Short for crystal
- 24. Voltage (abbr.)
- 25. Capacitance (abbr.)
- 26. Power output (abbr.)
- 27. Are you troubled by atmospherics?
- 30. Tube and associated components
- Many beginners learn to send code with one
- 34. Current used
- Federal radio communications regulating agency (abbr.)
- 37. Transmitter stage (abbr.)
- 38. You are QRMing
- 39. Not a regular wire circuit (abbr.)
- 40. Wife
- 41. Type of national defense (abbr.)


- 42. Abbreviation for #51 down
- 43. Quadrature-phase subcarrier signal
- Current that is not undecided which way to flow (abbr.)
- 47. Going out of the network
- 49. - hams should join the ARRL
- 51. Bunch of interconnected relay
- 52. Letter symbol for power
- 53. The strength of your signal is
- 54. Intentional loss
- 56. Send your information "QNC"
- 58. Type of magnet (abbr.)
- 59. - directional antennas radiate equally well in all directions
- 61. Cathode resistor (abbr.)

- 62. Radiotelephone
- 63. Class of amateur radio license

DOWN:

- 1. Wave reflection phenomenon from ionosphere
- 2. One thousand watts (abbr.)
- 3. Broken or open circuit connection (abbr.)
- 5. Volume compensating circuit (abbr.)
- 6. Antenna support
- 7. Not far away
- 8. Current in vacuum tube cathode circuit (abbr.)
- 9. What's your - -
- 14. Switch (abbr.)
- 17. Deck switch
- 19. Type of earthly radio wave
- 21. Operator

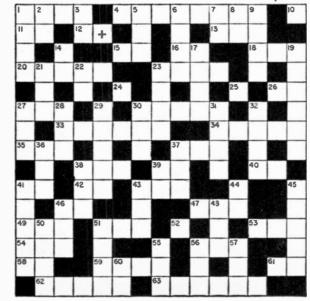- 22. Resistor voltage drop (abbr.)
- 23. Short for something that generates and emits
- 27. Means network isn't busy
- 28. Major broadcasting network (abbr.)
- 29. Odor associated with electrical discharge in air
- 30. Short for says
- 31. Magnetically induced circulating
- 32. K-King, L-Lewis,
- 36. Could
- 37. Modulated continuous waves (abbr.)
- 38. Signal concerning network communications
- 39. Circuit etched on wafer (abbr.)
- 41. Series-tuned
 Colpitts oscillator
- 43. Stop transmitting
- Not a distant oscillator (abbr.)
- 45. Ham's lair
- 46. Received
- 48. Type of transistor (abbr.)
- 50. Light source
- 51. Inert gas
- 55. It is α - to say amateur operators aren't of great help in time of α national emergency
- 56. Shall I send a series of VVV
- 57. How many telegrams have you received?
- 60. Objective case of pronoun I, or the one who wrote this puzzle!



A Handy Home Appliance Tester

\$6.50 electronic box will check out electrical units up to 15 amps at 125VAC

By JAMES ROBERT SQUIRES

PPLIANCE testing can be as simple as you make it. The little unit shown in Fig. 1, simplicity itself, can be used as the basic tool for a lot of tests that locate

many appliance faults.

Most modern appliances provide a product name plate giving either total current drawn by the unit or total power consumed in its normal operation. New appliances will draw current in the general range of the same plate value. Older appliances usually draw less current as the heating elements age. Older appliances that require longer heating times or in general do not do the job in the time allotted are wasting electricity. The location and repair of these faulty units will soon pay for the slight expense of making this tester.

It will cost approximately \$6.50 to build this unit. With it you can test all electrical appliances up to 15 amps at 125 vac with safety. As you know, these little boxes can attract all kinds of little gimmicks such as test points, and extra switches, in a hurry. Since these add to cost and construction time, they

were not included.

Construction of the appliance tester is straightforward (Fig. 2) and it can be done in a few evenings. Close the aluminum minibox and fold a piece of white paper tightly over the flanged cover. Anchor the paper with cellulose tape. Also allow the paper to cover one end of the box. Now draw a center line on the paper as shown in Fig. 3, then locate the five cross points on the paper as indicated.

The SPDT switch requires a ¹⁵/₂-in. hole, the neon light grommet one of ⁵/₆-in. diameter. The 2-in. circular opening for the 0-15 ammeter is best cut with a chassis punch. Other useful ways to cut the hole are satisfactory, providing they leave a clean hole and



Just plug your appliance into the tester. An 8-ampere reading on the dial indicates normal operation of the iron, but an intermittent movement of the needle would indicate a faulty contact in the cord connector.

do not mar the shiny aluminum face.


You will need two rectangular holes for the Cinch-Jones ac sockets. The simplest way I have found to start the rectangular hole is to drill the two ¼-in. holes in two places as indicated in Fig. 3. Then, using the socket as a pattern, lay out the rectangle on the paper. Now, with a small square file and the socket as a fitting template, file the rectangle to size. Again with the socket as pattern, lay out the mounting holes and drill them. These mounting holes were not laid out before, so that any error made in drilling or filing the rectangular holes would not be added to the position of the predrilled mounting holes. Drill a ½-in. hole for the power cord grommet.

Wrap one of the neon lamp pigtails around the pigtail of the 56K resistor and solder the joint. Wrap the other neon pigtail around one end of a 5-in. piece of No. 22 shielded wire—then solder. Slip a 2-in. piece of sleeving over the joint and butt up against the


glass of the NE2E bulb.

Remove any of the white layout paper and



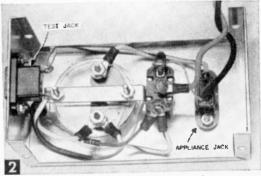

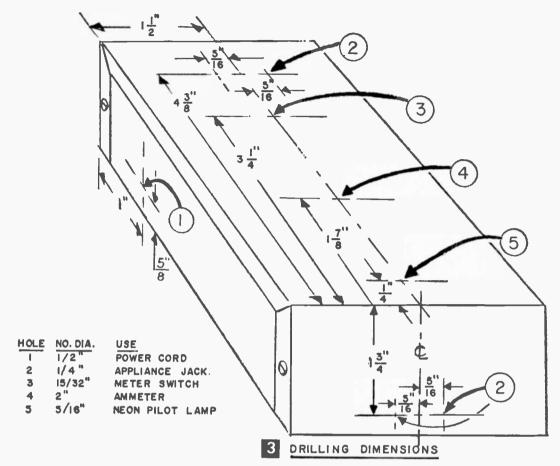Interior view of tester showing parts placement.



cellulose tape left on the chassis. Insert the 3/8-in. neon grommet in its hole, moisten the neon tube glass with water, and slip into the grommet. Allow about 1/4-in. of neon tube to project above the chassis.

Mount the Shurite meter, taking care to square and center the meter face with the Minibox sides. Now mount the SPDT switch and the two Cinch-Jones sockets. Strip 6 in. of outer rubber protective insulation from the power cord. Dampen the outer rubber of the power cord, insert the power grommet in its hole, then slip the power cord about ¾-in. into the grommet. A tight fit here assures a firm hold of the power cord at the grommet.

Disassemble the double-fused plug and, with a small round file, file the edges to permit the plug cover to close over the power cord. Strip, solder, and attach the wires to the plug. Reassemble the plug and insert two Buss ABC15 (3AB) fuses into the plug.


Wiring the Tester. It is always good practice to tin stranded wires before using the solderless connector crimp tool. Be certain to use internal lock-tight washers under every screw and nut used in the circuit. With exception of the neon circuit, work with #16 stranded wire throughout. The long length

of power cord wire inside the box will allow servicing of the instrument.

Attach a solderless connector to one wire of the power cord pair and connect it to the center screw terminal of the SPDT switch, as in Figs. 2 and 4. Connect the other wire of the power cord pair to the left terminal, as viewed from the rear of the appliance jack. Also connect the wire from the neon pigtail to this terminal and solder. Connect a length of wire from the right screw terminal of the switch to the right terminal of the meter.

Using solderless terminals or solder where necessary, connect a wire from the left side of the test jack to the left side of the ammeter. On this same terminal of the meter, connect a wire to the left screw terminal of the SPDT switch. Also connect the pigtail of the 56K resistor to this switch terminal. Complete wiring of the tester with the connection of the right terminal of the test jack to the right terminal of the appliance jack. Using a small piece of #16 wire, short the two male pins of the ac plug together at the terminals to form the shorting plug.

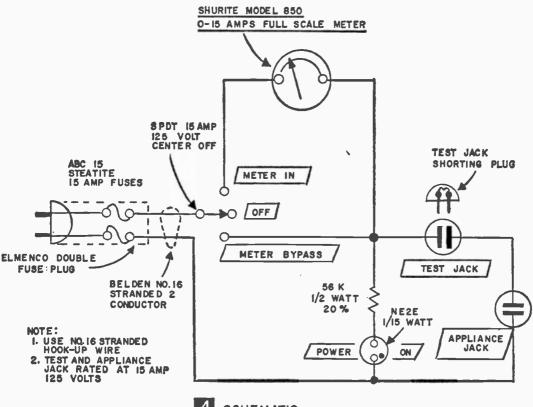A word of caution before continuing. This tester might well be constructed from assorted parts lying around the work bench.



SCHEMATIC

However, operating ratings for all components used in the model are 15 amps at 125 vac. Any random bench parts used should equal or exceed this rating. As an example, table lamp zip cord should not be used. For your own safety, be very sure to use the components that meet the ratings given above.

Using the Appliance Tester. It is only necessary to assume or measure the approximate value of the ac line voltage applied to the tester. That is, you must decide that input voltage is nearest to 100 volt, 113 volt, or 125 volt. When the appliance is turned on, the 0-15 ac ammeter will indicate a current flow.


Chart No. 1 shows the power consumed for a choice of one of the three approximate line voltages. This chart plots meter current in amperes versus power consumed at the appliance jack in watts.


As an example, assume you have selected the 113-vac house voltage as being the closest to your own voltage. With the appliance plugged into the tester, you then read 10 amps on the meter. By sliding your finger up to the 10-amp line on the chart to the point where it crosses the 113-vac curve, you have found the power consumed by the appliance. It is indicated to the left of the chart on the horizontal line which also crosses the 113-vac curve. The Shurite ammeter movement is accurate to within 5% and is close enough for all measurements used here.

Plug the appliance to be tested into the ac receptacle marked appliance jack. Be certain that a shorted ac plug is plugged into the receptacle marked test jack. The SPDT switch mounted under the meter is the on-off meter selector switch. In meter bypass position, the meter is not in the ac circuit. In the meter position, all appliance current will flow through the meter. The meter bypass is used to prevent damage to the meter when appliances that may have a short are tested. It has another use to be mentioned in a moment.

Safety Features. Additional trust may be placed in the tester because of many safety features built into the unit. Both sides of the ac line are fused. This prevents excessive current in the event one side of the line is shorted to a good ground such as a water pipe. The fuses are 3AB medium time lag, steatite-case, heavy-duty fuses. They offer more protection in the event of direct shorts to fuse holders in the ac plug. Fuses are removed from the double fuse plug by pushing them out through a small hole to the rear of the plug.

With the meter selector switch in either

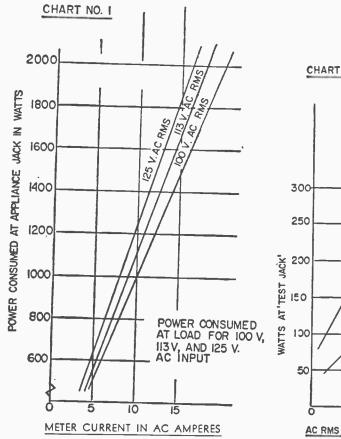

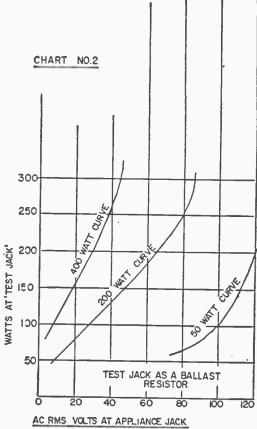

meter bypass or meter in position, the NE2E glows brightly. The Shurite model 850 plastic meter case enables the operator to see the neon glow from many angles. When working in dark corners, the neon provides enough light to illuminate the meter face. The test jack shorting plug need not be in its socket for the neon power on light to warn of ac voltage on. The tester can be used either horizontally or vertically as it is convenient. The power cord is No. 16 heavy duty 15 amp. 125-volt cord, so it should not heat under these maximum load conditions.

To measure appliance currents less than 3 ac amps with more accuracy than possible with the 0-15 amp meter movement, the test jack is used. Simply throw the meter selector switch to meter bypass, remove the male shorting plug, and plug an ac ammeter of your choice in the test jack. With an 0 to 3 ac ammeter plugged in, all appliances drawing more than 350 watts should not be checked. Line voltages supplied by the power company vary during the day and night. Often the complaint that an appliance does not get hot enough for the evening meal, a fry pan for example, may be traced to a lower ac line voltage to the appliance during this peak

load time. The tester has provisions to test appliances under these reduced voltage conditions. Again, the shorting plug is removed and an ordinary table lamp plugged in the test jack.

Chart No. 2 gives the reduced voltage at the appliance jack when using the various wattage bulbs in the lamp socket. The values given are approximate and are only for reference. The range of possible loads is wide and actual ac rms. voltage at the appliance jack should be found by experimentation. The chart shows that the reduced-voltage feature is most useful for small loads in the 50- to 150-watt range. This includes radios, hi fi's, amplifiers, small industrial systems, and P.A. systems.

Chart No. 2 also shows that for very large loads, 400 watts or greater, the ac voltage at the appliance jack will be very small, on the order of 20 volts or less. Electrical devices using timers such as toasters require careful checks to assure that all components are working.


In conclusion, it cannot be stated too often: Currents and voltages used in this appliance tester are lethal, and caution is the byword at all times.

The Torpedo

A portable capsule radio the young experimenter can build



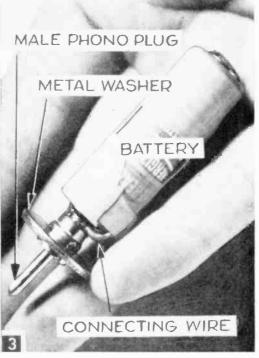A young experimenter listens intently to the World Series on his newly built Torpedo radio.



The battery and plug fit together and comprise the switch that energizes the radio.

By HOMER L. DAVIDSON


THE Torpedo consists of just 10 small components soldered together and sealed in plastic. Local broadcast stations are heard across the band with plenty of volume. A phono male and female plug combination forms a simple on-off switch. Simply clip the capsule radio to a metal object and you're in business. The cost is less than \$5, including the earphone.


The antenna coil is a ferrite-core type with a .000330 mfd fixed capacitor to tune the broadcast band. By removing the threads

from the core shaft, the coil can be pushed in and out, selecting your favorite station.


A fixed crystal rectifies the RF signal and also couples the signal to the base of the first transistor. The emitter terminal of TR1 is grounded. Capacitor C2 couples the audio signal to the base of TR2 for greater amplification. R1 serves as the plate load for the collector circuit of TR1. Any 1000- to 3000-ohm earphone can be used in the collector circuit of TR2. SW1 is a female phone socket with the male jack fastened to the small battory.

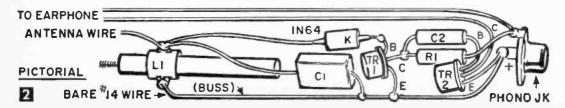Construction. Take a solid piece of No. 14



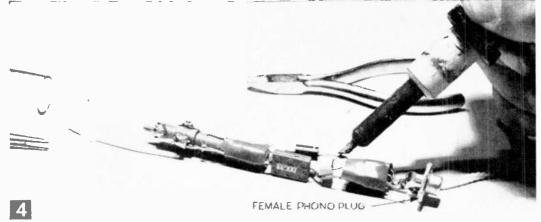

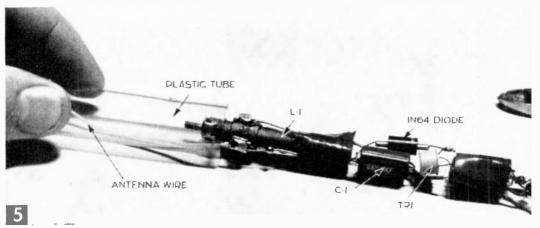Be careful not to let the heat of the soldering iron damage a transistor.



A section of plastic tubing acts as the shell that encases the radio elements.


"buss" wire and cut it to 4 in, in length. This wire serves as a common ground and can be picked up from a local supplier. First scrape off the rubber insulation and clean for good bonding. Run the solid wire to one side of the connecting lug on L1. Place L1 parallel to the ground wire. Fasten the silver mica capacitor to the grounded side and also to the antenna side of L1. All of these components are mounted in a straight and narrow line so they will go inside a ¾-in. plastic tube. Use of a pencil soldering iron is suggested, as the small components are mounted very close together.

Solder the crystal detector to the antenna lug on L1 and to the base of the first transistor. Use longnose pliers to dissipate the heat when soldering the crystal and transistors into the circuit. It is best to start at the front of the circuit, mounting and then soldering each component into place. Solder C2 and R1 together first before soldering them to the collector terminal of TR1. A good soldering joint is made and less heat applied to the

transistor all at once. Connect the other end of the coupling capacitor to the base of TR2. Ground the emitter terminal to the base wire. Remove the plug from the earphone and solder one wire to the R1 and SW1 junction. Refer to pictorial diagram, Fig. 2, for ease in wiring. Use spaghetti and plastic tape where needed.

The battery is a 4.5-volt Eveready miniature type with a male phono plug soldered

Deele	MATERIALS LIST—THE TORPEDO Description
Desig.	
L1	ferrite antenna coil, micrometer adjustment (Lafayette
	MS299)
C1	.000330 mfd silver mica capacitor
C2	2.mfd, 6.v. electrolytic miniature capacitor (Lafayette
62	CF100)
R1	4700-ohm, 1/2-w. resistor (Lafayette RS10)
TR1, TR2	2N408 transistor, RCA or equivalent
XTAL	1N64 diode
1	1000- to 3000-ohm earphone (Lafayette AR50)
1	switch, male and female phono jack, and plug (La-
A	
	fayette MS167, MS168)
1	4.5-v. Eveready battery
Misc.	plastic tubing, wire, and Epoxy Cement bonding kit
	(G. C. Electronics Cc., Rockford, III.)
	Above parts available from Lafavette Radio, 111 Jericho
	Turnpike, Syosset, N. Y.

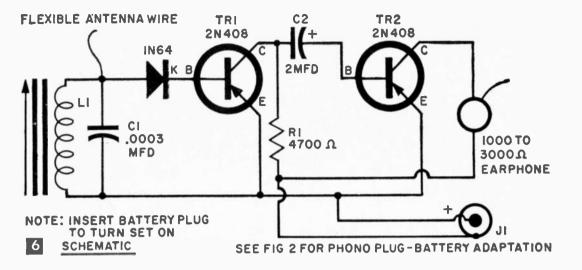

to one end. File a V-notch in the wire end of the male plug, run a small flexible wire to the prong end, and solder into place. Place a piece of spaghetti over the wire where it comes out of the V-notch so the wire will not short out. Solder a small washer to the male plug and in turn solder to the negative terminal of the battery. Take the wire lead and solder to the positive terminal of the 4.5-volt battery.

Slip the metal clip off the coil end, and the ferrite rod will come out with it. Unscrew the threaded slug and file or grind off threads.

This will let the slug move in and out of the coil, tuning in the broadcast stations. Solder a metal washer to the rod after placing it in the coil assembly. This washer will serve as a tuning knob.

Testing Your Torpedo. Clip the antenna wire to an outside antenna or metal object and plug in the battery. Move the ferrite rod in or out until a station is heard. When the slug is pushed all the way in, you are selecting the lower part of the broadcast band. When it is pulled all the way out, you are selecting the higher end of the band.

In case the receiver does not work, first check the wiring carefully to be sure that no soldering mistakes were made. If a milliammeter is handy, insert the meter in series with one lead of the battery and check the circuit drain. The capsule radio pulls only 1 ma of current. Place the soldering iron tip on the base of TR2 when the iron is plugged in, and a 60-cycle hum should be heard. Go to the base of TR1 and do the same thing. A louder hum should be heard.

Check to see if the connection from the crystal diode cathode is made to the base of TR1. Most of these crystal diodes are marked either with a line or a K at the cathode end. Also, a loud click or scratchy noise should be heard when the antenna lead is hooked to a

metal object.

Final Assembly and Sealing. The radio is now ready to be mounted in the plastic container. Cut a piece of ¾-in. plastic tubing about 5 in. long. File the ends down smooth. Slip the small chassis into the tube from the ferrite coil end. Let the coil stick out about ½ in. and the female phono plug about ¼ in. Now wrap two layers of masking tape around the coil end and let the tape stick up from the plastic tube about ½ in.

The unit is now ready to be sealed with fiber glass plastic which comes in two separate tubes. Mix a small amount at a time on a piece of board. Take a knife blade or a screw-driver blade and place the mixture inside the masking tape. Push it down tight so that a good solid bond is made. Do not let the fiber glass get in the hole in the female phono plug or the antenna coil. When the plastic sets and becomes hard, the components will not pull apart. Do one end at a time. Let the mixture set overnight or for at least eight hours. Follow the directions for correct method of mixing. They will be found on the tube container.

There are several types of fiber glass plastic available. They can be purchased at hardware stores, boat supply stores, or radio wholesale houses. After the plastic sets, pull off the masking tape. If there are a few drips or dents in it, run a small amount into the crevices and let that set. Plastic fiber glass does not need heating to harden. Both ends of The Torpedo are sealed in the same way.

After the ends are sealed and formed, use a file to smooth them. Round off the rough corners. To make the plastic capsule look like a professional job, place several rings of masking tape around the container. Then from a spray can apply the desired color of paint. Remove the masking tape when dry, and The Torpedo is ready for hard use.

Neon Flicker Lamp


Here's a decorative night light that doubles as a conversation piece

THIS flickering neon lamp can be an assuring nighttime companion in your child's bedroom, a gift for the man who has everything, or a piece for milady's dressing table. It costs only a few dollars to build, requires very little power, and will operate for a few cents a year.

The novelty of this lamp is its flicker. As rectifier D1 (see Fig. 2) converts ac line voltage into pulsating direct current, capacitor C1 charges to a steady dc value approaching peak voltage. This is the dc voltage required for the operation of the neon glow lamp multivibrator, which consists of resistors R1 and R2, capacitor C2, and neon lamps X1 and X2.

When dc voltage is applied to the glow lamp multivibrator, one of the lamps fires the one with the lowest starting potential. Since the terminal of capacitor C2, which is connected to the glowing lamp, has a lower potential than the other capacitor terminal, the capacitor will charge up until the voltage on its terminal reaches the firing potential of the non-conducting neon lamp. At that point, the second lamp fires and the other lamp extinguishes. Now the process repeats itself with C2 charging in the opposite direction, and the operation is repetitive.

 Construction Details. The housing for the lamp, a miniature kerosene lamp, can be




bought at five-and-dime stores or at variety import stores. I obtained mine at an import store for 47¢.

Punch a small hole in the bottom of lamp's fuel reservoir with an ice pick, and enlarge it to about \%-in. with a taper reamer or by using successively larger drills. Insert a rubber grommet in this hole.


Pass the line cord through the grommet, and bring it out through the filling hole at the top of the reservoir. Strip the insulation from the ends of the cord, and expose about \%-in. of bare copper wire.

Use the sequence of pictures in Fig. 3 to guide you with the wiring. Keep the leads of the capacitors and resistors as short as possible to minimize the possibility of short circuits, and be sure to use rosin core solder and a clean, well-tinned iron.

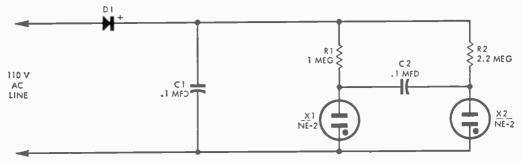Remove the wick from its holder by removing the wick screw. Then assemble the two neon lamps and insert the insulated hookup wires through the wick holder. Connect these to the base circuit.



Wiring and Construction Sequence.

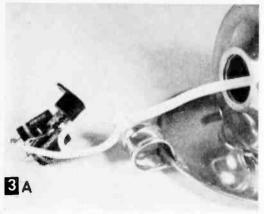


Wire base circuit.



Assemble the two neon lamps.



Replace the wick with the neon lamps.

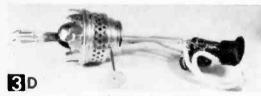

Connect lamps to base circuit.



Put base circuit in reservoir and wick holder on top.



Replace the chimney and it's ready to flicker.

	MATERIALS LIST-NEON FLICKER LAMP
Desig.	Description
C 1, C2	.1 mfd, 200-volt metalized paper capacitors (Lafayette 3CG-804)
D1 R1 R2 X1, X2	selenium rectifier (Lafayette MS-887) 1 meg. ½-watt carbon resistor 2.2 meg. ½-watt carbon resistor NE-2 neon lamps (GE)
Misc.	ac line cord and plug, miniature kerosene lamp (avail- able at variety stores) The above parts, except for the kerosene lamp, can be obtained from Lafayette Radio, 111 Jericho Turnpike,

Svosset, N. Y


Plug the unit into ac line voltage to check operation. If the circuit has been wired properly, the glow will shift from one lamp to the other continuously. In order to alter the speed of the flicker, you will have to change the value of capacitor C2. By making C2 smaller, the lamp will flicker faster. Make C2 larger, and the lamp will flicker slower. After you have checked out the operation, unplug the circuit. Then fasten the lamp leads to the wick holder with Duco cement.

Insulate all exposed metal parts of the base circuit with electrical tape, and cram the base circuit into the lamp reservoir. Put two turns of reverse twist in the lamp leads to the base. and screw the wick holder on the reservoir

Finally, adjust the lamp positions, put the chimney in place, and you've completed the job.-Frank Woods, Jr.

Fire Extinguisher Chases Radio Bugs

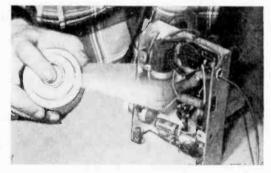 The chilling effect of a carbon dioxide fire extinguisher will help you locate a defective part in a radio circuit that plays erratically. Often a set works fine for a few minutes after you turn it on, and then suddenly misbe-



haves or goes dead. The trouble may be a part that expands with heat after current has been flowing through for a few moments. Spray suspicious parts with CO, gas one at a time. The intense cold will contract a defective component so it can work normally.

You can also use Charg-A-Can Freon #12 with a suitable adapter (sold by refrigeration supply houses). However do not use carbon tetrachloride fire extinguishers since the fumes are highly toxic.—T. A. BLANCHARD.

Thermistor Thermometer

Conduct experiments in changing temperature with a compact lab instrument you can build for less than \$10

By FORREST H. FRANTZ Sr.

TRANSDUCERS are devices that sense energy in one form and convert it to another form. The thermistor senses changes in temperature and responds with changes in resistance. The changes in resistance can be converted to changes in electrical current in a circuit.

The unit described in this article demonstrates the operation of a thermistor; change in temperature is indicated by a change in electrical meter reading. It was originally designed as a demonstration unit and a conversation piece, but some simple experiments are described here, as well as a method of calibration, which will suit it for use as a laboratory thermometer.

The circuit is shown in Fig. 3. R3, the thermistor, is one of the arms of a Wheatstone bridge; R1 in parallel with R2 is another arm, and R4 and R5 are the other arms. The 50-microamp meter M is the bridge null and small temperature change indicator.

The thermistor's resistance is a function of temperature. When temperature increases, the thermistor resistance decreases, and vice







Energy changes are clearly indicated as the meter.

versa. A bridge circuit with a sensitive meter will detect smaller temperature changes than a less sensitive one, as the change in resistance for each degree of change in temperature is small.

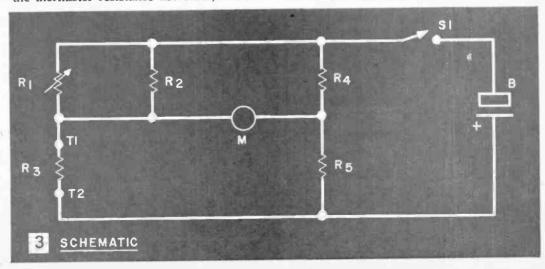Construction. Drill the metal case as shown in the layout (Fig. 4). Saw the shaft of R1 to



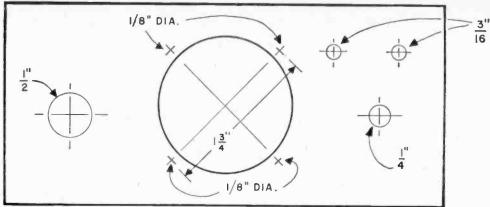

4 DRILLING DIMENSIONS

FRONT VIEW

a length of % in. Mount the switch S1, the potentiometer R1, the terminals T1 and T2, and the meter M on the front panel of the case (see Fig. 5A). T1 and T2 must be insulated from the panel.

Mount the battery holder on the back panel (see Fig. 5B). Wire the instrument with the

help of Figs. 3 and 5.


Use. Fasten the thermistor R3 in the terminals T1 and T2. Turn the instrument on and adjust R1 for mid-scale meter deflection.

Now, touch the thermistor: the meter reading should increase. If the meter reading decreases, reverse the meter connections. In other words, the meter deflection should be in the direction of temperature change.

The terminals T1 and T2 have been provided so the thermistor can be used for remote temperature reading. Attach wire leads of the required lengths for the desired appli-

One experimental demonstration is to show the change in meter reading when the thermometer is touched with the hand or an ice cube; another is to place a drop of cigarette lighter fluid on the thermistor, and note the cooling effect as the fluid evaporates. If the thermistor is placed at the focus of a parabolic reflector, the instrument may be used as an infrared detector. The sensitivity is limited, however.

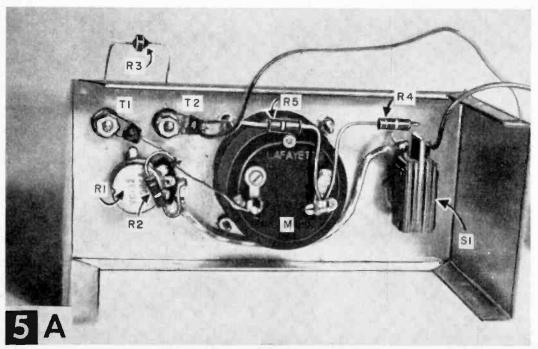If you care to calibrate the thermometer,




Interior view showing components and wiring.

miniature knob (Lafayette MS-185) Parts for this project are available from Lafayette Radio, 111 Jericho Turnpike, Syosset, L. I., N. Y.


you can use it as an experimental quantitative instrument.

Calibration. This requires calibration of R1. With a triangular file, make a groove in the edge of the knob. Fill the groove with contrasting India ink to provide an index. Prepare a paper scale with a 1-in. diameter circle marked on it, and fasten it to the case with Carter's rubber cement.

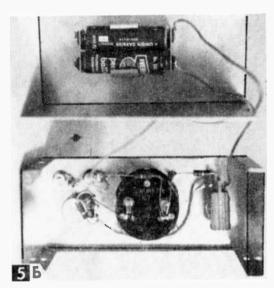Place the thermistor (equipped with extension leads connected to T1 and T2) in ice water (Fig. 6). Adjust R1 for zero meter



Mount batteries on the back of the case.

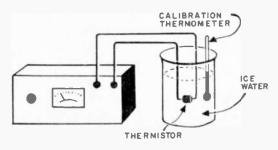

THERMISTOR THERMOMETER BRIDGE

reading, and place a calibration mark on the paper scale and mark it 0 (for zero degrees Centigrade).


Heat the water gradually, stirring constantly, until the meter deflects full scale. Adjust R1 for zero meter reading, note the calibration thermometer reading, and enter it beside the calibration mark for the new R1 setting. Repeat this process up to boiling point of the water, and R1 will be calibrated in steps

Reading the R1 setting plus the interpolated value of the meter reading to the next higher R1 calibration will give you the temperature. The precision of the instrument will approach that of the calibration thermometer used.

Earphone Volume Reducer



• To reduce the volume of an earphone of the "earplug" type when using the phone in conjunction with a set that has insufficient volume reduction at its lowest setting (this happens often near stations) slip a soft rubber grommet over the phone. This keeps it from fitting into your ear so far, yet still allows it to fit firmly. The lengthened distance between phone diaphragm and ear drum lowers the volume several db's.—John A. Comstock.

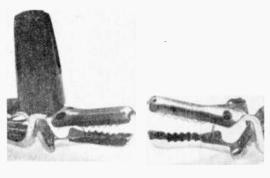

"Clara, you've been shopping again!"

LOOKING OVER NEW PRODUCTS



C-B Walkie Talkie


A super het transceiver with exact crystal control for both receive and transmit channels on the 27-mg citizens band. Using four transistors and a diode, we feed 80 milliwatts of power to the 10-section telescoping antenna.

No license is required and the unit can be operated by anybody. The range is one mile under normal conditions, increased when conditions are optimum, such as over water. The finger tip push to talk switch provides high speed break-in operation. Comes complete with blue and black metal case with leather carrying case, crystals, and six penlight cells. Priced at \$19.95 each or two for \$38.95 from Lafayette Radio Electronics Corp., Dept. RTE, 111 Jericho Turnpike, Syosset, N. Y.

Tube Tester Kit

Called the Grid Circuit Analyser Tube Tester, this kit will test 10- and 9-pin miniatures, 12-pin compactrons, 7- and 5-pin nuvistors, 9-pin novals, novars, octals and loctals, plus many industrial and European types. It checks for inter element shorts, cathode emission at optimum pre-selected plate loads, gas content and grid emission, as well as picture tubes by means of cathode emission. The new kit sells for \$49.95, or wired and tested, for \$67.95. Paco Electronics, Dept. RTE, 70-31 84th St., Glendale 27, N. Y.



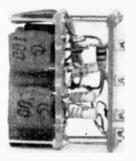

Tiny Transceiver

Designed for use by missile refueling teams, fire fighting crews or warehouse operations, this unit provides hands-free communications for people working in noisy or hazardous areas.

The radio consists of a single package, no larger than a package of cigarettes. It contains a crystal controlled transmitter and a receiver, powered by two rechargeable batteries. The unit is attached to the user by a clip, light belt or nylon cord. A voice operated switch turns the unit to transmit only when the user talks. It operates in the 25-50-mg range. ITT Kellogg, Dept. RTE, 320 Park Ave., New York 22, N. Y.

LOOKING OVER






15-In. Speaker

This three-way hi-fi speaker features a 5 lb. ceramic magnet. It is custom built in England. The three elements are axially mounted and the woofer section is vacuum constructed. It is plastic terminated with free edge cone suspension to eliminate standing waves and surround resonances. The woofer cone resonance is 25 cycles.

The overall frequency response is 20 to 20,000 cps with a power capacity of 50 watts. The impedance is 16 ohms. \$64.50 from Lafayette Radio Electronics Corp., Dept. RTE, 111 Jericho Turnpike, Syosset, N. Y.

Amateur Receiver

The frequencies from 550 kilocycles to 30 megacycles are covered in four bands by this new communications receiver. Front panel controls consist of on/off volume, main tuning, band selector and phone-CW switch. A front panel headphone jack permits quiet listening. Plugging in the low impedance phones automatically disconnects the built-in 4-in. speaker. The unit uses three tubes and a silicon diode for five-tube performance. The slide rule dial and wrinkle finish cabinet make for a professional appearing receiver. Operates on 105-125 volts, 50/60 cycles. \$39.95. Lafayette Radio Electronics Corp., Dept. RTE, 111 Jericho Turnpike, Syosset, N. Y.

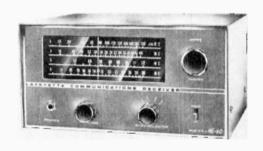



Sound Spectrometer

This acoustical device helps isolate sounds and their levels. It not only tells you how loud sounds are, measured in decibels, but also in what frequency range they fall. The new model has been modified to meet ASA specifications which require a low frequency cutoff at 45 cycles. It was originally designed with conventional octave bands, the first band having a cut-off sharply at 37.5 cycles.

The unit is finding great acceptance in industry because of its convenient weight, size and simplicity of operation. Industrial Acoustics Co., Dept. RTE, 341 Jackson Ave., New

York 54, N. Y.

LOOKING OVER NEW PRODUCTS

Stereo Amplifier

A headphone output on the front panel of this new amplifier permits constant monitoring of all program sources. A tape monitor switch and special inputs and outputs are included for the tape recording enthusiast. A derived third channel output is provided to drive a power amplifier for extension speakers.

Amplifier provides 15 watts per channel, hum and noise are 70 db down. Intermodulation distortion is 0.5%, harmonic distortion is 0.8%. Unit measures 15½ wide, 5¼ high, 13¼ deep. Accessory case available in walnut, mahogany or leatherette covered metal. Model 200 stereo amplifier is available from H. H. Scott, Inc., Dept. RTE, 111 Powder Mill Rd., Maynard, Mass.





Page-Reply And Music

In addition to providing music as a background for employees, this unit also permits selective paging and reply facilities. The music can be programmed to start and stop at the time sequences chosen by the user. Music sources are available either from tapes or FM tuners.


An additional feature of the system is a tone generator which signals various increments in the working day, such as coffee breaks and lunch periods. Fisher Berkeley Corp., Dept. RTE, 1475 Powell St., Emeryville 8, Calif.


Pegboard Kit

The secret of this kit is the peg itself which may be inserted wherever two leads are to be connected. When a project is in development, the leads are inserted between the brass peg and the flexible sleeve surrounding it. Also the design becomes more firm, temporary connections are replaced by soldering the leads to the brass tips. Virtually no components are lost as no soldering is done until the design is well organized.

The kits are ideally suited to classroom instruction, as well as electronic development laboratories. The kits are available in three standard sizes, 5x8, 8½x11, and 11x14 in. Accessories include buss strips and anchor inserts for holding sockets and bulky components. Priced from \$2.50 to \$9. Laguna Labs, Dept. RTE, 2319 S. Coast Blvd., Laguna

Beach, Calif.

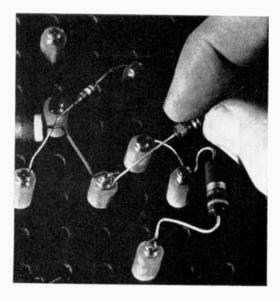


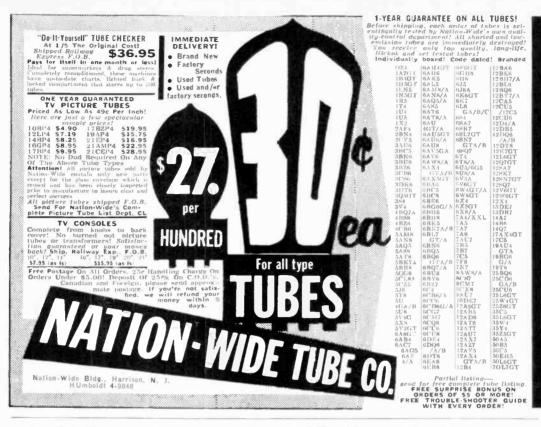

Build Better Boats with S&M FULL-SIZE Patterns



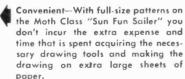Insure Accuracy—Full-size patterns on the "Minimax" duplicate the originals used by the designer when he built the first "Minimax". Each component can be cut to exact size for a perfect fit in final assembly.





Complete plans for each one of these popular boats are available at:

\$8



Save Time—Ready to use when you are ready to begin. Full-size patterns on critical parts in the "Sea Flea" enable you to use time generally spent on drawing full-size patterns in hours of enjoyment on this hair-trigger action surfboard that provides you with the utmost in sailing sport.

SCIENCE and MECHANICS, Dept. 2234 Craft Print Division
505 Park Avenue, New York 22, New York Enclosed is \$ for FULL-5IZE plans that cost \$8
each on the: #346Sun Fun Sailer #347Minimax #348Sea Flea
Please allow four weeks for delivery. For special handling, including first class mail delivery, add 50¢ per item ordered.
Name(PLEASE PRINT)
Street
City Zone State


ORDER YOUR 1963 S&M HANDBOOKS



Use the coupon below to insure yourself that you will receive each issue of the S&M Handbooks you want—direct to your mail box. No chance of missing a single copy, if you order by mail. Here's the complete 1963 line-up. Your copies will be mailed to you, postpaid, as they are published during the months shown below. Allow four weeks for delivery of 1962 editions.

1962 Edition 609 596	JANUARY 620—Radio-TV Experimenter 621—Car Repair Handbook 622—Income Opportunities 623—Gun Handbook	1962 Edition 611 592 594 597	624—Home Workshop Handbook	1962 Edition 593 613	MARCH 628—Boat Builder's Handbook 629—Electrical Handbook 630—Fisherman's Manual 631—How To Buy Or Sell
612 618 599	APRIL 632—Radio-TV Experimenter 633—Car Repair Handbook 634—Woodworker's Encyclopedia 635—Camping Handbook	377	MAY 636—Home Workshop Handbook 637—1001 How-To Ideas 638—Home Repair Handbook 639—Careers and Jobs	607 600 601	Your House JUNE 640—Boat Builder's Handbook 641—Inventor's Handbook 642—Water Sports Handbook 643—Auto Racing Handbook
	JULY 644—Radio-TV Experimenter 645—Car Repair Handbook 646—Woodworker's Encyclopedia 647—Home Appliance Repairs 648—Kitchen & Bath Improvements	608	AUGUST 649—Home Workshop Handbook 650—1001 How-To Ideas 651—Science Experimenter 652—Do-It Yourself Plumbing 653—Surplus and Salvage Projects	610	SEPTEMBER 654—Boat Builder's Handbook 655—Electrical Handbook 656—Junior Mechanics Handbook 657—Elementary Electronics 658—Christmas Suggestions.
	OCTOBER 659—Radio-TV Experimenter 660—Car Repair Handbook 661—Woodworker's Encyclopedia 662—Radio-TV Repairs 663—Photography Guide	615	NOVEMBER 664—Home Workshop Handbook 665—1001 How-To Ideas 666—Furniture Handbook 667—Crafts & Hobbies 668—Home Modernization Handbook	619	DECEMBER 669—Boat Builder's Handbook 670—Home-Built Power Toois 671—Engine Handbook 672—Small Investor's Guide 673—Small Home Plans

SCIENCE and MECHANICS	Handbooks ordered below. The Handbooks are to be shipped to me as they are published.
HANDBOOKS	
50 5 PARK AVENUE	Name(Please print)
NEW YORK 22, N.Y.	Address
	CityState

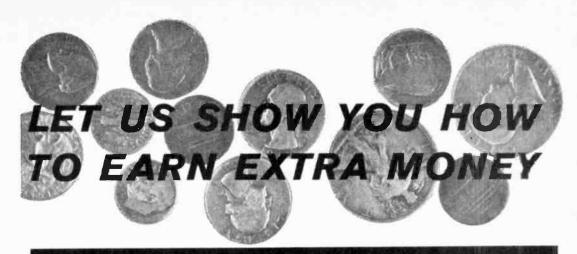

No inventory—no investment on your part

world for direct sales representatives...a world in which you can achieve your favorite goals. Here is a world where you will earn extra money to buy the things you want and need. A world where your earnings are obtained in a dignified, pleasant and self-satisfying manner.

And your selling is made easy for you, too! Your friends, and neighbors, people you work or study with—all of these people—and more are your prospects for additional income.

Do you want more information . . . it's yours for the asking. Please fill out all the blanks on the coupon below It's your first step to making all those extra dollars.

Pete Reynolds - Davis Publication		rk Avenue • New York 22, N. ars. Please send me details.	Υ.
NAME	(Please Print)		_
CITY		STATE	_
PRESENT PRINCIPAL OCCUPATION			

Your Best Newsstand Investment

Proven money-making enterprises are featured in this volume of INCOME OPPOR-TUNITIES. Advantages, responsibilities and rewards of working with a franchise are compared to the responsibilities of "going it alone." You can get first-hand information through the success stories that show the growth of ideas that have resulted in high profit ventures by handling an exclusive line yourself or having others work for you on a full- or part-time basis. This volume is really an investment because it will show you where solid profits can be obtained. Buy it now and read about the high returns available in:

COMPANIENT A Successful Small Business

ODDOTTUNITIES

Ond Successful Small Business

and Successful Small Business

The Rewards in Franchising

Smart Selling by Mail Order

Marketing Food Specialties

Tooling Up for Rental Profits

Trading Workshop Ideas for Cash

Dozens of Tested Ways to Boost

Earnings with a Small Investment

- Electrical Repairs
- Auto Seat Covering
- Lapidary Retailing
- Writing for Trade Magazines
- Travel Agenting

- Tool Rental
- Odd-Jobbing
- Marketing Food Specialties
- Position Placing for Profit
- Selling by Mail-Order

SCIENCE AND MECHANICS MAGAZINE Handbook Division, 505 Park Avenue New York 22, New York

Enclosed is \$1 to include postage and handling for *Income Opportunities* #622. Please allow four weeks for delivery. For special handling, including first class mail delivery, add 50c to your order.

Name....(PLEASE PRINT)

Address....

Pick up your copy of this informative investment guide and the other how-to SCIENCE AND ME-CHANICS handbooks that are now at your newsstand, or send \$1 and the coupon at left to have it delivered to you.

ON SALE NOW! at most newsstands



#622 Income Opportunities

Dozens of successful ways to be your own boss on a full-time basis or to conduct a small business profitably on a part-time arrangement. This money-making guide reveals how many franchise operations work and the opportunities available in business ventures that require little capital investment. These articles explain how to get started in business and how to keep it operating on a profitable basis. You like a bout what is required to make money in such business opportunities

- Position Placing for Profit
- Selling by Mailorder
- Travel Agenting
- Auto Seat Covering
- Electrical Repairs

- Writing for Trade Magazines
- · Lapidary Retailing
- Odd-Jobbing
- Marketing Food Specialties
- Tool Rental

#621 Car Repair Handbook

A must guide for every weekend mechanic who wants to keep his car in like-new condition and in peak running order. You'll find many applications for the more than 20 servicing articles that give complete how-to instructions so you can use tools you already own. These articles are fully illustrated with photographs and drawings to make servicing that much easier. A partial listing of the contents includes:

- Save Your Upholstery
- Installing a Throttle Control
- How to Get More MPG
- Fire Up Your Heater
- Beat Winter No-Start
- 26 Emergency Roadside Repairs
- Take the Tap Out of Tappets
- Longer Life for Tires
- Rust Stopping Tips
- What's Wrong with Imports





#623 Gun Handbook

A fact-filled reference for targeteer, hunter and collector. Fully-illustrated volume provides you with money-saving ideas on loading your own ammo, tips on gun care and customizing. Handgun enthusiasts—both beginner and advanced—will find advice from champions and top coaches very beneficial. Rifle and shotgun buffs are briefed on latest developments in their areas and will be interested in a new weapon that fires four different sizes of ammunition. Buy it and read about:

SCIENCE AND MECHANICS MAGAZINE

- New Loads Make News
- Knock-Down: Fact or Fiction?
- How to be a Handgunner
- Build a Clay Pigeon Catapult
- Kitchen-Table Handloading
- Variable Power Scopes
- Artistry in Metal
- Sighting-In Your Rifle
- All Around Gun
- New Light on Old Kentuckys

Pick up your copies of these comprehensive volumes at your newsstand or send \$1 to include postage and handling for each guide ordered to:

SCIENCE AND MECHANICS

HANDBOOK DIVISION
505 PARK AVENUE
NEW YORK 22, NEW YORK

	mail delivery, add 50¢ per item ordered.	
i	#620 #621 #622	
i	NAME	
i	(PLEASE PRINT)	
į	ADDRESS	
	CITY ZONE STATE	

Handbook Division, 505 Park Avenue, New York 22, New York

Enclosed is \$..... to include postage and handling for the do-

it-yourself volumes circled below, at \$1 each. Please allow four

Build Yourself A One-Man Modern Biplane

Completely modern in design but based on the traditional one-man flying machine of yesteryear is the EAA sport biplane that is adaptable to home construction, easy to maintain, and costs under \$1600 (with a used engine). She is capable of carrying a 230-lb. pilot at a rate of climb of 400 ft./min. to a ceiling of 7000 ft. With an 85 hp Continental engine up front her top speed was about 130, and cruising speed around 110. The biplane design permits a larger engine-up to 125 hp. Positive response and orthodox spinning behavior are the final traits that mark her as an ideal one-man build-it-yourself flying machine.

Craft Print No. 334, comprising 8 sheets of drawings and full building instructions are available at: EAA BIPLANE

SCIENCE and MECHANICS,
Craft Print Division,
505 Park Avenue, New York 22, N. Y.
Enclosed is \$10.00 for complete plans of the EAA Biplane that include full
Enclosed is \$10.00 for complete plans of the EAA biplane that include the
building instructions. To avoid possible loss of coin or currency in mails,
remit by check or money order (no C.O.D.'s or stamps). Please allow four
weeks for delivery. For special handling, including first class mail delivery,
add 50¢ per item ordered.
Name
(PLEASE PRINT)
(PLEASE PRINT)
Street
City, Zone, State
Add 10% for Canadian and Foreign orders.

If You've Enjoyed

LOOKING

Through This
SCIENCE and MECHANICS
Handbook

You should subscribe to

SCIENCE and MECHANICS

New Subscribers: Use This Money-Saving Coupon

SCIENCE and MECHANICS	-
Please enter my subscripting SCIENCE and MECHAN	
Dissues for \$2.98 Payment Enclosed Bill me	By enclosing payment you may double this offer and receive 20 issues for \$5.96
Name(PLEASE	PRINT)
Address	
City	StateH-620

SOLUTIONS

Electronic Numbergram, page 85



Ham Radio Anagram, page 137



WHITE'S RADIO LOG

An up-to-date broadcasting directory

No. 1

Vol. 40

AM, FM, TV and Short Wave Stations

Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and, of course, only information available up to press-time could be included. Copyright 1963 by Science and Mechanics Publishing Co., a subsidiary of Davis Publications, Inc., 450 East Ohio St., Chicago 11, III.

QUICK REFERENCE INDEX

QUICK REFER	
U.S. and Canadian AM Stations	U.S. FM Stations by States187
by Frequency159	U.S. FM Stations by Call Letters190
U.S. and Canadian AM Stations	Canadian FM Stations by Location192
by Location168	Canadian FM Stations by Call Letters193
U.S. AM Stations by Call Letters177	U.S. Television Stations193
Canadian AM Stations by Call Letters 186	Canadian Television Stations194
Mexican and Cuban AM Stations186	World-Wide Short-Wave Stations195

Canadian AM Stations by Call Letters 186	
Mexican and Cuban AM Stations186	World-Wide Short-Wave Stations195
	tic and International 196
	Stations by Frequency
U.S. stations listed alphabetically by states w	ithin groups, Canadian stations precede U.S.
Abbreviations: Kc., frequency in kilocycles; W.P., watt pawe	
Kc. Wave Length W.P. Kc. Wave Length W.P.	
### Company of the co	WLES Lawrenceville, Va. WCHS Charlesten. W.Va. Sound WKTY LaCresse, Wis. Sound WKTY LaCresse, Wis. Sound WKTY LaCresse, Wis. Sound CKK
WFRB Frestburg, Md. 1000d WRKH Reckwood, Tenn. 1000d	CHML Mont Laurier, Que. 1000 WHITE'S RADIO LOG 159

Kc. Wave Length	W.P.		W.P.		W.P.		W.P.
KVMA Magnolia, Ark. K100 Monterey, Calif.	1000q	DZRH Manila, P.I. WKJB Mayaguez, P.Rico	10000	KOAN Eureka, Calif. KABC Los Angeles, Calif.	5000d 5000	KFUO St. Louis, Mo.	5000d 10000
KHOW Oenver, Colo. WMAL Washington, D.C.	5000 5000	WTPR Paris, Tenn. KGNC Amarillo, Tex.	250d 10000	WLBE Leesburg, Fla. WFUN Miami Beach, Fla.	5000 5000	WKIX Raisigh, N.C. WJW Cleveland, Ohio WJAC Johnstown, Pa,	10000
WSAV Savannah, Ga.	5000	KURV Edinburg, Tex.	250	WPFA Pensacola, Fla.	10000	WEEU Reading, Pa. WABA Aquadilla, P.R.	1000
WNEG Toccoa, Ga. KIDO Boise, Idaho	500d 5000	KIRO Seattle, Wash, WDSM Superior, Wis.	50000 5000	WQXI Atlanta, Ga. WGRA Cairo, Ga.	10000	WRAP Norfolk, Va. KTAC Tacoma, Wash,	500 5000
WLAP Lexington, Ky. KTIB Thibedaux, La.	5000 500d	720-416.4		KEST Beise, Idahe WRMS Beardstewn, III,	1000d 500d		1000
WJMS Irenwood, Mich. KDWB So. St. Paul, Minn.	1000 5000	WGN Chisago, III.	50000	KXXX Colby, Kans, WAKY Louisville, Ky, WRUM Rumford, Me.	5000d 5000	860-348.6 CHAK Inuvik, N.W.T.	1000
KXOK St. Louis, Mo. KGVW Beigrade, Mont.	5000 1000d	730410.7		WRUM Rumford, Me. WSGW Saginaw, Mich.	1000d 5000	CJBC Toronto, Ont. WHRT Hartselle, Ala,	50000
KOH Rene, Nev. KLEA Lovington, N. Mex.	5000 500d	CJNR Blind River, Ont. CKAC Mentreal, Que.	50000	WSIC Magas Miss	1000d 5000	WAMI Opp. Ala.	250d 1000d
WIRC Hickory, N.C. WMFD Wilmington, N.C.	1000d	CKDM Dauphin, Man. CKLG No. Vancouver, B.C.	10000	KGHL Billings, Mont. WWNY Watertown, N.Y. WLSV Weilsville, N.Y.	10000	KIFN Phoenix, Ariz. KOSE Osceola, Ark.	1000d
KWRO Coquille, Ores.	5000d 500d	WJMW Athens, Ala. KFQD Anchorage, Alaska	10000	WINC Thomasville, N.C.	1000d 5000	KWRF Warren, Ark. KTRB Modesto, Calif.	250d 10000
WEJL Scranton, Pa. WKYN San Juan, P.R.	5000	KSUD W. Memphis, Ark.	250d 1000d	KFGO Fargo, N.Oak, KWIL Albany, Oreg.	1000	WOWW Naugatuck, Conn. WAZE Clearwater, Fla.	250d 500d
WPRO Providence, R.I. KGFX Pierre, S.Dak.	5000 250	WKTG Thomasville, Ga. KLOE Goodland, Kans.	1000d	WAEB Allentown, Pa. WPIC Sharon, Pa.	500 1000d	WKKO Cocoa, Fla. WERD Atlanta, Ga.	1000d
KMAC San Antonio Tex. KSXX Sait Lake City, Utah	5000 1000d	WFMW Madisenville, Ky. WMTC Van Cleve, Ky.	500d 1000d	WEAN Providence, R.I. WWBD Bamberg, S.C.	5000 1000d	WDMG Douglas, Ga. WMRI Marion, Ind.	5000d 250d
KGDN Edmunds, Wash. KZUN Opportunity, Wash.	5000d 500d	KTRY Bastrop, La. WARB Covingion, La.	250d 250d	WETB Johnson City, Tenn, WMC Memphis, Tenn,	1000d 5000	KWPC Muscatine, lowa KOAM Pittsburg, Kans,	250d
640-468.5		WMMS Bath, Maine WACE Chicopee, Mass,	1000d 5000d	WMC Memphis, Tenn. KTHT Houston, Tex. KFYO Lubbeck, Tex.	5000 5000	WSON Henderson, Kv.	10000 500d
CBN St. John's, N.F.	10000	KWRE Warrenton, Mo. KWOA Worthington, Minn.	1000d	KUTA Bianding, Utah WSIG Mount Jackson, Va.	1000d	WAYE Dundalk, Md. WSBS Gt. Barrington, Mas	
KFI Los Angeles, Calif. WOI Ames, lowa	50000 5000	KURL Billings, Mont. KMGM Albuquerque, N. Mex	500d	WTAR Norfolk, Va. KGMI Bellingham, Wash.	5000 5000	KNUJ New Ulm, Minn, WMAG Forest, Miss, KARS Belen, N. Mex.	1000d 500d
WHLO Akron, Ohio WNAD Norman, Okia.	1000q	WDOS Oneonta, N.Y. WFMC Goldsbore, N.C.	10000	KNEW Spokane, Wash, WEAQ Eau Claire, Wis.	5000 5000	WFMO Fairmont, N.C.	250d 1000d
650461.3		WOHS Shelby, N.C. WMG8 Bowling Green, Ohio	1000d	800—374.8	3000	KMFR Medford, Oreg. WAMO Pittsburgh, Pa.	1000d 1000d
KORL Honolulu, Hawali WSM Nashville, Tenn,	10000 50000	KBOY Medford, Oreg.	1000d	CHAB Moose Jaw. Sask.	10000	WTEL Philadelphia, Pa. WLBG Laurens, S.C.	250d 1000d
KIKK Pasadena, Texas	250d	WNAK Nanticoke, Pa. WPIT Pittsburgh, Pa.	1000d 5000d	CKOK Penticton, B.C. CFOB Ft. Frances, Ont.	10000	WIVK Knoxville, Tenn. WMTS Murfreesboro, Tenn	1000d
660454.3		WPAL Charleston, S.C. WLIL Lengir, Tenn.	1000d	CFOB Ft. Frances, Ont. CJLX Ft. William, Ont. CJBQ Belleville, Ont.	5000 1000	KFST Ft. Stockton, Tex.	250d 250d
KMEO Omaha, Nebr. WNBC New Yerk, N.Y.	500d 50000	KPCN Grand Prairie, Tex. KSVN Ogden, Utah WPIK Alexandria, Va.	500d 1000d	CKLW Windsor, Ont,	50000 10000	KPAN Hereford, Tex. KSFA Nacogdoches, Tex.	1000d
WESC Greenville, S.C. KSKY Oallas, Tex.	10000d	WMNA Gretna, Va.	5000d 1000d	CJAD Mentreal, Que. VOWR St. Johns, N.F.	10000	KONO San Antonio, Tex, KWHO Salt Lake City,	5000
670-447.5		KULE Ephrata, Wash. WXMT Merrill, Wis.	1000d	WHOS Decatur, Ala,	1000d	WEVA Emperia, Va. WOAY Oak Hill, W.Va.	1000d
WMAQ Chicago, III.	50000	740—405.2		WMGY Montgomery, Ala. Kiny Juneau, Alaska KAGH Crossett, Ark.	1000d 5000	WOAY Oak Hill, W.Va. WFOX Milwaukee, Wis.	10000d 250d
680440.9		CBXA Edmenton, Alta,	50000	KVOM Morrilton, Ark.	250d 250d	870344.6	
CHFA Edmonton, Alta. CHLO St. Thomas, Ont.	5000d 1000	CBL Terente, Ont. WBAM Mentgemery, Ala.	50000 50000d	KUZZ Bakersfield, Calif. KOAD Weed, Calif.	250d 1000d	KIEV Glendale, Calif. KAIM Kaimuki, Hawali	250d 5000
CJOB Winnipeg, Man. CKGB Timmins, Ont.	10000	KUEQ Phoenix, Ariz. KBIG Avalon, Calif,	P00001	KBRN Brighten, Cole, WLAD Danbury, Cenn.	500d 250d	WWL New Orleans, La.	50000
KNBC San Fran., Calif. WPIN St. Petersburg, Fla.	50000 1000d	KCBS San Francisco, Calif.	50000 1000	WSUZ Palatka, Fla. WJAT Swainsboro, Ga.	1000d	WKAR E. Lansing, Mich. WHCU Ithaca, N.Y.	5000d 1000d
WCTT Corbin, Ky. WCBM Baltimere, Md.	10000	KSSS Colo. Springs, Colo. KVFC Cortez, Colo. WKIS Orlando, Fla.	1000d 5000	KXIC Iowa City, Iowa WBOK New Orleans, La.	1000d	WGTL Kannapolis, N.C. WHOA San Juan, P.R.	1000d 500 0
WNAC Boston, Mass.	50000 10000	KYME Boise, Idaho WVLN Olney, III.	500d 250d	WCCM Lawrence, Mass, KREI Farmington, Mo.	1000d	KJIM Ft. Worth, Tex. WFLO Farmville, Va.	250d 1000d
WDBC Escanaba, Mich, KFEQ St. Joseph, Mo.	5000	KBOE Oskaleosa, Iowa WNOP Newport, Ky.	250d 1000d	KDBM Dillon, Mont, WKDN Camden, N.J.	1000d	880340.7	
WINR Binghamton, N.Y. WRVM Rochester, N.Y.	1000 250d	WTAO Cambridge, Mass.	250d	KJEM Okla City, Okla.	250d	WCBS New York, N.Y.	50000
WPTF Raleigh, N.C. WISR Butler, Pa.	50000 250d	KPBM Carlsbad, N.Mex. WGSM Huntington, N.Y.	1000d	KPDQ Portland, Oreg. WCHA Chambersburg, Pa.	1000q	WRRZ Clinton, N.C. WRFD Worthington, Ohio	1000d 5000d
WAPA San Juan, P.Rico. WMPS Memphis, Tenn.	10000		100004	WDSC Dillon, S.C. WEAB Greer, S.C.	1000d 250d	890-336.9	
KENS San Antonio, Tex. KOMW Omak. Wash.	50000 1000d	KRMG Tulsa, Okla. WVCH Chester, Pa.	50000 1000d	WDEH Sweetwater, Tenn. KDDD Dumas, Tex.	1000d 250d	WLS Chicago, III. WHNC Henderson, N.C.	50000 1000d
WCAW Charleston, W.Va.	250	WIAC San Juan, P.Rice WBAW Barnwell, S.C.	10000	KBUH Brigham City, Utah WSVS Crewe, Va.	250d 5000d	KBYE Okla. City, Okla.	1000d
690—434.5	10000	WIRJ Humbolt, Tenn. WIIG Tullahoma, Tenn.	250d 250d	WKEE Huntington, W.Va. WDUX Waupaea, Wis.	1000q	900333.1	
CBU Vancouver, B.C. CBF Mentreal, Que.	10000 50000	KTRH Houston, Tex. KCMC Texarkana, Tex. WBCI Williamsburg, Va.	50000 1000	810-370.2		CKTS Sherbrooke, Que. CHML Hamilton, Ont.	1000 5000
KVNA Flagstaff, Ariz.	50000d		500d	KGO San Francisco, Calif.	50000	CHNO Sudbury, Ont. CJBR Rimouski, Que.	10000
KEVT Tueson, Ariz. KBBA Benton, Ark.	250d 250d	750-399.8	F0000	WABW Annapolis, Md. KCMO Kansas City, Mo.	250d 50000	CKJL St. Jerome, Que. CJVI Victoria, B.C.	1000
KAPI Puebio, Colo. WADS Ansonia, Conn.	250d 500d	WSB Atlanta, Ga, WBMD Baitimore, Md,	50000 1000d	WGY Schenectady, N.Y. WKBC N.Wilkesbore, N.C.	50000 1000d	CKBI Prince Albert, Sask	00001 .
WAPE Jacksonville, Fla. KULA Honolulu, Hawaii KBLI Blackfoot, Idaho	25000d 10000	WHEB Portsmouth, N.H.	10000d	WEDO McKeesport, Pa.	1000d	WATV Birmingham, Ala. WGOK Mobile, Ala. WDZK Ozark, Ala.	1000d
KGGF Coffevville, Kans.	1000d	KSEO Durant, Okla. KXL Portland, Oreg.	250d 50000	WKVM San Juan, P.R.	25000	KPRB Fairbanks, Alaska KHOZ Harrison, Ark.	10000 1000d
WTIX New Orleans, La. KTCR Minneapolis, Minn.	5000 500d	WPDX Clarksburg, W.Va.	1000d	1	5000d	KBIF Fresno, Calif. KGRB West Covina, Calif	1000d
KSTL St. Louis, Mo. KEYR Terrytown, Nebr.	1000d	760-394.5 KGU Henolulu, Hawaii	10000	WAIT Chicago, III. WIKY Evansville, Ind.	250d 5000d	WJWL Georgetown, Del. WSWN Belle Glade, Fla.	5000d 1000d
KRCO Prineville, Oreg. WXUR Media, Pa.	1000d 500	WJR Detroit, Mich. WCPS Tarboro, N.C.	50000 1000d	WEAA Dallas, Tex.	50000	I WMOP Ocala, Fia.	1000d
KUSD Vermillion, S.Dak.	1000d	WORA Mayaguez, P.R.	5000	WBAP Ft, Worth, Tex. 830-361.2	50000	WCGA Calhoun, Ga. WCRY Macon, Ga. WEAS Savannah, Ga.	250d 5000d
KHEY El Paso, Tox. KPET Lamesa, Tex. KZEY Tyler. Tex.	250 250d	770—389.4		KIKI Honolulu, Hawali	250	KTEE Idaho Falls, Ida.	1000d
WCYB Bristol, Va.	10000d	KUOM Minneapolis, Minn. WCAL Northfield, Minn.	5000d 5000d	WCGO Minneapolis, Minn.	50000 1000d	KSIR Wichita, Kan. WKYW Louisville, Ky.	250d 1000d
WNNT Warsaw, Va. WELD Fisher, W.Va.	250d 500d	WEW St. Louis, Mo. KDB Albuquerque, N.Mex.	1000d 50000	WNYC New York, N.Y.	1000	WLSI Pikeville, Ky. KREH Oakdale, La.	5000d 250d
700-428.3		WABC New York, N.Y.	50000 1000d	840-356.9	1000	KREH Oakdale, La. WCME Brunswick, Maine WATC Gaylord, Mich. KTIS Minneapolis, Minn.	1000d
WLW Cincinnati, Ohio	50000	780—384.4		WRYM New Britain, Conn	1000d	I WDDT Greenville, Miss.	1000d
710—422.3	1000d	WBBM Chicago, III,	50000	WHAS Louisville, Ky. WVPO Stroudsburg, Pa.	50000 250d	KFAL Fulton, Mo. KJSK Columbus, Nebr.	1000d
CJSP Leamington, Ont. CFRG Gravelbourg, Sask. CKVM Ville Marle, Que,	5000d	WJAG Norfolk, Neb. WCKB Dunn, N.C.	1000q	850—352.7		WOTW Nashau, N.H.	1000d
WKRG Mobile, Ala.	10000	WBBO Forest City, N.C. KEPI Stillwater, Okla.	1000d 250d	CKAL Asidum, Gus.	50000 10000	WSPN Saratoga Sprgs N	.Y. 250d
KMPC Los Angeles, Calif. KBTR Denver, Colo.	5000	WAVA Arlington, Va.	1000d	CJJC Langley Prairie, B.C WYDE Birmingham, Ala.	1000	WIAM Williamston, N.C.	1000d
KBTR Denver, Colo. WGBS Mlami, Fla. WROM Rome. Ga.	50000 1000d	770-377.3	1000	KICY Nome, Alaska	5000 50000	WCNS Canton, Ohio	500d 500d
KEEL Shreveport, La. WHB Kansas City, Mo. WOR New York, N.Y.	10000	CHB Halifax, N.S.	10000	WRUF Gainesville, Fla.	5000	WCPA Clearfield, Pa.	1000d
WOR New York, N.Y.	50000	CKSO Sudbury, Ont. WTUG Tuscaloosa, Aia.	500d	I KIMO HIIo, Hawaii	1000	WKXV Knexville, Ienn.	1000d 500d
160 WHITE'S RADIO	o Log	WTUG Tuscaloosa, Aia, KCEE Tucson, Ariz, KOSY Texarkana, Ark,	5000d		1000	KALT Atlanta, Tex.	10000

		- 00 100 . 0 05		M - 100	147 0 .	Ma Maria Laurah	W D
Kc. Wave Length	W.P.		W.P.		W.P.	Kc. Wave Length KUPI Idaho Falls, Idaho	W.P. 1000d
KMCO Conroe, Tex. KFLD Floydada, Tex.	500d 250d	CJCA Edmonton, Alta, CJON St. John's, N.F.	10000		5000	KSGM Chester, III,	500
KCLW Hamilton, Tex.	250d	I WETO Gadsden, Ala.	1000d	WBRC Birmingham, Ala.	5000	WITY Danville, III.	1000
WODY Bassett, Va.	500d	KTKN Ketchikan, Alaska KAPR Douglas, Ariz,	1000	WMOZ Mobile, Ala. WCVQ Kodiak, Alaska	1000 250	KREB Shreveport, La. WCAP Lowell, Mass.	5000d 1000d
WAFC Staunton, Va. KUEN Wenatchee, Wash,	1000q	KAPK Douglas, Ariz,	1000d	KOOL Phoenix Ariz	5000	WDMC Otsego, Mich.	500
WATK Antige, Wis.	250d	IKMI Los Anneles Calif	5000	KOOL Phoenix, Ariz. KAVR Apple Valley, Callf. KNEZ Lompoc, Callf.	5000d	WPBC Minneapolis, Minn. WAPF McComb, Miss.	1000d
		KMET Paradise, Calif, KIUP Durango, Colo. WKSB Milford, Del. WHAN Halnes City, Fla.	500d	KNEZ Lompoc, Galif. KABL Oakland, Calif.	500 5000	WAPF McComb, Miss, KMBC Kansas City, Mo.	1000d 5000
910—329.5		WKSR Milford Del	5000 500d	WELL New Haven, Conn.	5000		10000
CJDV Drumheller, Alta,	5000 1000	WHAN Haines City. Fla.	1000	WGRO Lake City, Fla. WJCM Sebring, Fla.	500d	KVLV Fallon, Nev. KICA Clovis, N. Mex. KMIN Grants, N. Mex. WIRY Troy, N.Y.	5000d
CKLY Lindsay, Ont. CBO Ottawa, Ont.	5000	WJAX Jacksonville, Fla. WKXY Sarasota, Fla.	5000	WJCM Sebring, Fla. WJAZ Albany, Ga.	1000d 5000d	KICA Clovis, N. Mex.	1000 l
CFJC Kamloops, B.C.	10000	WMGR Bainbridge, Ga.	1000 5000	WRFC Athens, Ga.	5000	WITRY Trey, N.Y.	5000
CHRL Roberval, Que. WDVC Dadeville, Ala.	1000 500d	l WGTA Summerville, Ga.	5000	KSRA Salmon, Idaho . WDLM E. Moline, III.	1000d		5000d
KPHO Phoenix, Arlz.	5000	KSEI Pocatello, Idaho	5000	WDLM E. Meline, III.	1000d	WAAA Win. Salem, N.C. WONE Dayton, Ohlo	1000d 5000
KPHO Phoenix, Arlz. KLCN Blytheville, Ark.	5000d	WTAD Quincy, III. WKCT Bowling Green, Ky	. 1000	WSBT South Bend, Ind. KMA Shenandoah, Iowa	5000	WILK Wilkes-Barre, Pa.	5000
KAMD Camden, Ark.	1000	WEMU Frederick, Md.	5000	WPRT Prestonsburg, Ky. KROF Abbeville, La.	5000d	WAZS Summerville, S.C. WRBI Winnsbore, S.C.	500d
KDEO El Cajon, Calif, KEWB Oakland, Calif, KOXR Oxnard, Calif.	5000	WREB Holyoke, Mass.	500d		1000d 5000	KDSJ Deadwood, S.Dak.	500d 1000
KOXR Oxnard, Calif.	1000d	WBCK Battle Creek, Mich.	5000 1000d	WBOC Salisbury, Md. WFGM Fitchburg, Mass. WHAK Rogers City, Mich.	1000	WSIX Nashville, Tenn.	5000
KPOF nr. Denver, Colo.	5000 5000	WSLI Jackson, Miss.	5000	WHAK Rogers City, Mich.	5000d	WSIX Nashville, Tenn. KFRD Rosenberg, Tex.	1000d
WHAY New Britain, Conn, WPLA Plant City, Fla.	10000	WSLI Jackson, Miss. KWOC Poplar Bluff Mo.	1000	KLTF Little Falls, Minn, WABG Greenwood, Miss,	500d 1000	KWVC Riebfield Utab	5000 5000
WGAF Valdosta, Ga.	5000	KOFI Kalispell, Mont. KOGA Ogallala, Nehr.	5000d 500d	KFVS Cape Girardeau, Mo.	5000	WFHG Bristol, Va. WMEK Chase City, Va. KUTI Yakima, Wasn.	500d
KBGN Caldwell, Ida. WAKO Lawrenceville, III.	1000d 500d	WWNH Rochester, N.H.	5000d	KNEB Scottsbluff, Nebr.	1000	KUTI Yakima, Wasn.	5000d
WSUI lowa City, lowa	5000	WPAT Paterson, N.J. WBEN Buffalo, N.Y	5000	KWYK Farmington, N.Mex. WEAV Plattsburg, N.Y.	5000d	WHAW Weston, W.Va. WSUB Manitowec, Wis.	1000d
WLCS Baton Rouge, La.	1000	WBEN BUTTAIO, N.Y.	5000 1000d	WAAK Dallas, N.C.	10004	WPRE Prairiedu Chien, Wis	
WABI Bangor, Maine WFDF Flint, Mich.	5000 5000	WSOC Charlotte, N.C.	5000	WFTC Kinston, N.C. WWST Wooster, Ohio	5000	990-302.8	
WCOC Meridian, Miss.	5000	WITN Washington, N.C.	5000	WWST Wooster, Ohio KGWA Enid, Okla.	10004		50000
KOYN Billings, Mont.	1000d	WEOL Elyria, Ohio WKY Oklahoma City, Okla	1000	KLAD Klamath Falls, Oreg.	5000d	CEY Corner Breck, Nfld.	10000
KYSS Missoula, Mont.	1000d 5000d	KAGI Grants Pass, Oreg.	5000	WHYL Carlisle, Pa.	5000d	WEIS Center, Ala.	250
KBIM Roswell, N.Mex. WLAS Jacksonville, N.C.	5000d	WCNR Bloomsburg, Pa.	1000d	WADP Kane, Pa, WATS Sayre, Pa.	1000q	WWWF Fayette, Ala. WTCB Flomaton, Ala.	1000d 500d
KCJB Minot, N.Dak.	1000	KSDN Aberdeen, S.D. WSEV Sevierville, Tenn.	1000 5000d	WBEU Beaufort, S.C.	10009	KTKT Tueson, Ariz.	10000
WPFB Middletown, Ohio	1000	KDET Center, Tex.	1000d	WBEU Beaufort, S.C. WBMC McMinnville, Tenn.	500d	KKIS Pittsburg, Calif.	5000
KGLC Miami, Okia. KURY Brookings, Oreg.	10000	KITE San Antonio, Tex.	5000	KIMP Mt. Pleasant, Tex. KGKL San Angelo, Tex.	1000d 5000	KGUO Santa Barbara, Calif. KLIR Denver, Colo.	. 1000d
KISN Portland, Ore.	1000	KENY Beilingham-Ferndale Wash.	10004	KOVO Provo. Útah	5000	WAZY Terrington, Conn.	1000d
WAVL Apollo, Pa.	10004	WSAZ Huntington, W.Va.	5000	WDBJ Roanoke, Va. KALE Richland, Wash.	5000	WEAB Miami, Fla.	5000
WGBI Scranton, Pa. WSBA York, Pa.	5000	KROE Sheridan, Wyo.	1000d	KALE Richland, Wash. WTCH Shawano, Wis.	1000	W 100 Orlando, Fla.	10000
WPRP Ponce, P.R.	5000	WLBL Auburndale, Wis.	5000d		1000	WDWD Dawson, Ga. W&ML Hinesville, Ga.	1000d 250d
WNCG North Charleston, 8.0	C. 500d	940-319.0		970—309.1		KTRG Honolulu, Hawali	5000
WORD Spartanburg, S.C.	5000d	CBM Mentreal, Que. CJGX Yorkton, Sask. CJB Vernon, B.C.	50000	CKCH Hull, Que.	5000	WEAZ Carthage, III.	1000d
WJCW Johnson City, Tenn. WEPG S. Pittsburgh, Tenn.	. 500d	CJGX Yorkton, Sask.	10000	WERH Hamilton, Ala. WTBF Troy, Ala.	5000d 5000	WITZ Jasper, Ind. KAYL Storm Lake, Iowa	1000d 250d
KNAF Fredericksburg, Tex.	10004		1000 250	KNEA lonesboro Ark.	1000d	KESL Russell, Kans.	250d
KRIO McAllen, Tex. KRRV Sherman, Tex.	3000 1000	KFRE Fresno, Calif, WINZ Miami, Fla. WMAZ Macon. Ga.	50000	KBIS Bakersfield, Calif.	1000	WIMR New Orleans, La.	250d
KALL Sait Lake City, Utal	5000 h	WINZ Miami, Fla.	50000	KCHV Coachella, Calif. KBEE Modesto, Calif.	5000 1000	KRIH Rayville, La. WCRM Clare, Mich.	250d 250d
WWRJ White River Junetic	DN.	WMAZ Macon, Ga.	50000 5000d	KFEL Pueblo, Colo.	10004	WABO Waynesboro, Miss,	250d
VRNI Richmond Va	5000	WMIX Mt. Vernon, III. KIOA Des Moines, Iowa	10000	WFLA Tampa, Fla.	5000	KRMO Monett, Mo.	250d
WRNL Richmond, Va. WHYE Roanoke, Va.	1000d	WYLD New Orleans, La. WJOR South Haven, Mich,	1000	WIIN Atlanta, Ga. WVOP Vidalia, Ga.	5000d 5000d	KSVP Artesia, N.Mex. WEEB Southern Pines, N.C	1000
KORD Paseo, Wash.	1000d	KSWM Aurora, Mo.	1000d 500d	KHBC Hilo, Hawaii	1000	WJEH Gallipells, Ohio	1000d
KUDY Scattle, Wash, WHSM Hayward, Wis, WDOR Sturgeon Bay, Wis,	20004	KVSH Valentine, Nehr. WFNC Fayetteville, N.C.	5000d	KAYT Rupert, Idaho	1000d	WTIG Massillon, Ohio	250d
WDOR Sturgeon Bay, Wis.	1000d	WFNC Fayetteville, N.C.	10000	WMAY Springfield, III.	1000 5000	KRKT Albany, Oreg. WIBG Philadelphia, Pa.	250d 50000
		KGRL Bend. Oreg. WESA Charleroi, Pa.	1000d 250d	KHBC Hilo, Hawaii KAYT Rupert, Idaho WMAY Springfield, III, WAVE Louisville, Ky, KSYL Alexandria, La.	0000	WVSC Somerset, Pa.	250d
920—325.9		WGRP Greenville, Pa,	1000d	WUSH Pertiane, maine	5000	WPRA Mavaquez, P.R.	10000
CFRY Portage La Prairie,	1. 1000	WIPR San Juan, P.R.	10000	WAMD Aberdeen, Md.	500 1000d	WLKW Providence, R.I. WAKN Aiken, S.C.	50000 1000d
CJCH Halifax, N.S.	10000	KIXZ Amarillo. Tex. KTON Belton, Tex.	5000 1000d	WESO Southbridge, Mass. WJAN Ishpeming, Mich.	5000d	WNOX Knoxville, Tenn.	10000
CJCJ Woodstock, N.B.	1000	KATQ Texarkana, Tex.	1000d	WKHM Jackson, Mich.	1000	WNOX Knoxville, Tenn. KWAM Memphis, Tenn.	1000d
CKCY Sault St. Marie, Ont CKNX Wingham, Ont.	2500	950-315.6		KQAQ Austin, Minn. KOOK Billings, Mont,	5000d 5000		1000 250d
WCTA Adalusia, Ala.	5000	CKNB Campbellton, N.B.	10000	KILT No. Platte, Nebr.	5000d	KAML Kenedy, Tex. KNIN Wichita Falls, Tex.	10000
WWWR Russellville, Ala.	P0001	CKBB Barrie, Ont.	10000	KVEG Las Vegas, Nev.	500d	IKUYE IDDAIA. UTAN	1000d
KARK Little Rock, Ark. KDES Palm Springs, Callf.	5000	WRMA Montgomery, Ala.	1000d	WJRZ Newark, N.J.	5000 5000	WNRV Narrows, Va. WANT Richmond, Va.	10004
KVEC San Luis Obispo, Ca	1. 1000	KXJK Forrest City, Ark. KFSA Ft. Smith, Ark.	5000d	WEBR Buffalo, N.Y. WCHN Norwich, N.Y.	500d	WKLJ Sparta, Wis.	250
KREX Grd. Junction, Colo.	5000	KAHI Auburn, Calif.	1000d	WRCS Ahoskie, N.C. WWIT Canton, N.C.	1000d	1000-299.8	
KLMR Lamar, Colo. WMEG Eau Gallie, Fla.	0001 00001	KAHI Auburn, Calif. KIMN Denver, Colo.	5000	WWIT Canton, N.C. WDAY Fargo, N.Dak.	1000d 5000	CKBW Bridgewater, N.S.	10000
WGST Atlanta, Ga.	5000	WNUE Ft. Walton Sch., Fla. WLOF Orlando, Fla.	5000	WREO Ashtabula, Ohio	5000	WCFL Chicago, III.	50000
WVOH Hazelhurst, Ga.	500wd 1800	WGTA Summerville, Ga.	5000d	WATH Athens, Ohio	1000d	WCFL Chicago, III. KTOK Okla, City, Okla,	5000
KAHU Waiphau, Hawail WGNU Granite City, III.	500d	WGOV Valdesta, Ga. KBOI Boise, Idaho	5000 5000	KAKC Tulsa, Okla. KOIN Portland, Oreg.	1000 5000	KSIA Udieman, Iex.	250d 250d
WMOK Metropolis, III,	1000d	KLER Orofino, Idaho	1000d	WWSW Pittsburgh, Pa.	5000	KGRI Henderson, Tex. WHWB Rutland, Vt.	10000
WBAA W. Lafayette, Ind. KFNF Shenandoah, Iowa	5000 1000	WAAF Chicago, III.	1000d	KASE Austin, Tax.	5000 1000d	WBMB Charlotte Amalie, Virgin Island	de inno
WTCW Whitesburg, Kv.	1000d	WXLW Indianapolis, Ind.	5000d	KNOK Et Warth Tay	1000d	KOMO Scattle, Wash.	50000
WBOX Bogalusa, La.	1000d	KOEL Colwein, Iowa KJRG Newton, Kans. WBVL Barbourville, Ky.	500d	WIVI Christiansted, V.I.	10004	1010-296.9	
KTOC Jonesboro, La. WPTX Lexington Pk., Md.	1000d 500d		1000d	WBVA Waynesboro, Va.	1000d 500d	CBX Calgary, Alta.	50000d
WMPL Hancock, Mich.	1000d		50004	WIVI Christiansted, V.I. WYPR Danville, Va. WBVA Waynesboro, Va. KREM Spokane, Wash, WWYO Pineville, W.Va.	5000	CFRB Toronto. Ont.	50000
KDHL Faribault, Minn.	1000	WWJ Detroit, Mich.	5000	WWYO Pineville, W.Va.	1000d	CFRB Toronto, Ont. KCAC Phoenix, Ariz.	500d
KWAD Wadena, Minn. KRAM Las Vegas, Nev.	1000	WORL Boston, Mass, WWJ Detroit, Mich. KRSI St. Louis Park, Minn WBKH Hattiesburg, Wiss.	.1000d	WHA Madison, Wis. WIGL Superior, Wis.	5000d 500d	KVPC Winslow, Ariz. KLPA Little Rock, Ark, KCHJ Delano, Calif.	1000
KOLO Rene, Nev.	1000			980—305.9		KCHJ Delano, Calif.	5000
KQEO Albuquerque, N.Mex	. 1000	WBER Moncks Corner, N.C. KLHS Lordsburg, N. Mex.	500d			KChr J Palm Spres., Calif.	1000
WITM Trenton, N.J. WKRT Cortland, N.Y.	1000	KLHS Lordsburg, N. Mex.	10004	CKNW New Westminster, Brit. Columbia	Lanna	KCWJ Palm Sprgs., Calif. KSAY San Fran., Calif. WChU Crestview, Fla. WZFO Jacksonville Beach.	10000d
WGHQ Kingston, N.Y. WIRD Lake Placid, N.Y.	5000d	WBBF Rochester, N.Y. WIBX Utica, N.Y. WPET Greensbere, N.C.	5000	CFPL Lenden, Ont.	10000	WZFO Jacksonville Beach.	
WIRD Lake Placid, N.Y. WBBB Burlington, N.C.	1000 5000d	WPET Greensbere, N.C.	5000d	CKGM Mentreal, Que,	10000	l Florida	2500d 50000d
WMNI Columbus, Ohio	500	KYES Roseburg, Urea.	1000d 500d	CBV Quebec, Que.	5000 5000	WGUN Decatur, Ga,	50000d
KGAL Lebanen, Oreg.	1000	WNCC Barnesboro, Pa. WPEN Philadelphia, Pa.	5000	CHEX Peterbore, Ont, CKRM Regina, Sask.	10000	KATN Boise, Idahe	1000d
WKVA Lewistown, Pa. WJAR Providence, R.I.	1000 5000	WSDA Spartanhura S.C.	5000	WKLF Clanten, Ala. WXLL Big Delta, Alaska KINS Eureka, Callf. KEAP Fresno, Callf.	1000d	WCSI Columbus, Ind.	500d 1000d
WJAR Providence, R.I. WTND Orangeburg, S.C.	1000d	KWAT Watertown, S.Dak. WAGG Franklin, Tonn. KDSX Denison, Tex. KPRC Houston, Tex.	10000	KINS Eureka, Callf.	100 5000	KSMN Mason City, Iowa KINO Independence, Kans.	
KEZU Rapid City, S.Oak.	1000d	KDSX Cenison, Tex.	500	KEAP Fresno, Calif.	500d	KDLA DeRidder, La.	1000d
WLIV Livingston, Tenn. KELP EL Paso, Tex.	1000d	KPRC Houston, Tex.	50000	MCIN ClanwoodSpres Colo	5000	WSIO Baltimere, Md.	1000d 500d
KELP El Paso, Tex. KECK Odessa, Tex. KTLW Texas City, Tex.	1000	WXGI Richmond Va.	5000d	WSUB Greton, Conn.	1000d	WMRT Lansing, Mich. WMDX Meridian, Miss.	10000
KTLW Texas City, Tex.	1000d	KIR Seattle, Wash.	5000	WRC Washington, O.C.	5000 5000d	KCHI Chillicothe, Mo.	250d
KIIN Ulympia, Wash. KXLY Spokane, Wash.	1000d 5000	WERL Eagle River, Wis.	1000d 5000	WOVH Gainesville, Fla.	10004	KXEN Festus, Mo.	50000d 25000d
KITN Diympla, Wash, KXLY Spokane, Wash, WMMN Fairment, W,Va.	5000	WKTS Sheboyean, Wis.	500d	WBOP Pensacola, Fla.	10000	KRVN Lexington, Nebr. WCNL Newport, N.H.	250d
WOKY Milwaukee, Wis.	1000	960—312.3		WSUB Greton, Conn. WRC Washington, O.C. WOYH Gainesville, Fla. WTOT Marlanna, Fla. WBOP Pensacola, Fla. WLOD Pempane Beach, Fla	. 1000d	WINS New York, N.Y.	50000
930-322.4			10000	WRLY Martwell, Ga.	6004		
CFBC Saint John, N.B.	10000	CFAC Calgary, Alta. CKNL Fort St, John, B.C.	1000	WKLY Hartwell, Ga. WPGA Perry, Ga. WRIP Ressville, Ga.	500d	WHITE'S RADIO LOG	161
-							
				-			

Kc. Wave Length W.P. Kc. Wave Length W.P. Kc. Wave Length	W.P.
WABZ Albermarle, N.C. 1000d KHMO Hannibal, Mo. 5000 KASM Albany, Minn. 1000d WMDC Hazlehurst, Miss. WHPE High Point, N.C. 1000d WXTN Lexington, Miss. 500d KBHM Branson, Mo.	. 250d 1000d
N.C. LOGODAL WMIA Arecino P.R. 500 KRMS Osage Beach, Mg. 1000d KLPW Union, Mg.	1000d
WELS Kinston, N.C. 1880 WFLI Lookout Min., Tenn. 1880 KSEN Shelby, Mont. 1880 WKBK Keene, N.H. WIOI New Boston, Ohio 1880 WDIA Memphis, Tenn. 1880 KDEF Albuquerque, N.Mex. 1880 WGNY Newburgh, N.Y.	1000a 5000d
KBEV Portland, Ores. 1000d KOPY Alice, Tex. 1000 WRUN Utlea, N.Y. 5000 WSOQ N. Syracuse, N.Y.	. 1000d
WULL Calletin Tann 1000d WGBR Goldsbore, N.C. 5000 WKEV Keldsville, N.C.	10004
	10009
KODA Hauston Text 1000d KSCO Santa Creekland, Ohio	50000
KAWA Water, Tex. 10000d WKLO Lepisville, Ky. 5000 WKLIN Handlander Pers. 5000d WCKI Campan College	250d 1000d
WMEV Marion, Va. 1000d WIFO Amberst, N.Y. 1000d WYNS Lehighton, Pa. 1000d KBLY Goldbeach, Oreg.	1000d 1000
WCST Backeley Sores W Va. 2500 WEWO Laurinburg, N.C. 10000 WDIX Orangeburg, S.C. 5000 WJUN Mexico, Pa.	1000d
WSPT Stevens Pt., Wis. 1000d WYRE Pittsburgh, Pa. 1000d WSNW Senera Township	1000q
1020—293.9 KRLD Dallas, Tex. South Carolina 1000d WFWL Camden, Tenn,	250d 1000d
WELD FOULA III. 1000 OLLO December Ont 250 WTAW Deuge Tay 1000d West Washington Tay	250d 250d
KDRA Pittsburgh, Pa. South CHRS St. Jean, Que. 1000 KCCT Corpus Christi, Tex. 1000d WLSD Big Stone Gan.	Va. 1000d
	L 5000d 250d
WBZA Springfield, Mass. 1000 KHAI Honolulu, Hawaii 5000 KIBC Midland, Tex. 10000 KOZi Chelan, Wash. WBZA Springfield, Mass. 1000 KNAI Wash. Baid, Wash.	1000d
KCTA Corpus Christi, Tex. 50000d WBAL Baltimore, Md. 50000 KOLJ Quanah, Tex. 500d 3230 243 8	s. 300u
1040 200 2 WILD Roston, Mass 1000d KRER San Antonio, 16%, 1000d 1430-473.9	10000
KHVH Honoldid, Hawaii 30000 WAJS San German P.R. 250 KAYO Seattle, Wash. 5000 CHFC Churchill, Man.	250
WASH Deerneid, Va. 1999 CFGR Gravelbourg, Sasi	ι, 250
1000d CFHR Hay River, Nwt.	100
CFGP Grande Prairie, Alta. 10000 Kr AR Sau Francisco, Carrolla Co. 2504 WISN Milwaukes, Wis. 5000 CFPA Pert Arthur, Ont.	1000
CIIC Sault Ste. Marie, Ont. 10000 WHLI Hempstead, N.Y. 10000d 1160-258.5 CKMP Midland, Ont.	Que. 250 250
CHUM Toronto, Ont. 5000 NTW Clevering Uliv Street WIID Chieses III. 50000 VOAR St. John's, Nfld.	1000
WCRI Scottsboro, Ala. 2500 1110 270 1 WAUD Auburn, Ala.	1000
NAME SUGA FOR SUGA FO	1000
KOFY San Mateo, Calif. 1000d CFTJ Galt, Ont. 250 WCOV Montgomery, Ala. 10000 WOLS Florence, Ala.	1000 250
KLMO Longmont, Colo. 250d KIPA Hilo, Hawaii 1000 KI OK San Diego, Calif 10000 WTBC Tuscalossa, Ala,	250
WISB Crestatew, Fig. 1000d WMBI Criteago, III. 5000d KOHO Honolulu, Hawaii 1000 KIFW Sitka, Alaska	250 250
WHBO Tampa, Fla. 250d WBT Charlotte, N.C. 50000 KETT Dayannert town 1000 KAAA Kingman, Ariz,	250 250
	250
WRIE Mariette Ga 500d I WVIP Capust P.R. 250 I WOULD DELUGED WASH 1000 I KCON Conway. Ark.	250 1000
WUZ Decatur, III. 100001 and Arma 1 INDIM Junesburg, Ark.	250
WNES Central City, Ky. 500d WIIST Rethesda, Md. 250d WIIST Rethesda, Wd. 250d Wd.	1000
KLPL Lake Providence, La. 2500 KMOX St. Louis, Me. 50000 WHAM Rochaster N. 50000 KIBS Bisnop, Call.	1000 250
KVPI VIIIa Platta, La. 2000 i KCI F Ciahirna, Tax. 2000 i 1 1 91	. 250
WOMR Silver Sprg. Md. 1000d WPAG Ann Arbor, Mich. 5000d 1130—265.3 KZON Tolleson, Ariz. 250 KGFJ Los Angeles, Cali KPRL Paso Robles, Cali	if. 1000
KLOH Pipestone, Minn. 1000d CKWX Vanceuver, B.C. 50000 KNRA Vallein, Calif. 250d KWC Stocking, Calif.	250 1000
WACK Columbus, wiss. 1000 KROU Dinuba, Calli, 1000 WOWO Et Wayne and Soon	lo. 250 250
VIVC Les Vages Nev 500d VWVII Chessenest Le 50000 WKUX Fram gnam, Mass. 10000 KDZA Pueblo, Colo.	250
MONO COMMENT NOTE TOUCH IN THE PROPERTY OF THE	250 1. 1000
	. 1000
WHN New York, N.Y. 50000 1140-263.0 1200-249.9 WONN Lakeland, Fla. WHS Feeselis N.C. 1000d 11140-263.0	250 1000
WLON Lincolnton, N.C. 1000d CFTK Terrace, B.C. 1000 WOAI San Antonio, Tex. 50000 WSBB New Smyrna B	ch., orida 1000
WWGP Sanford, N.C. 1000d CKXL Calgary, Alta. 1000d 1210—247.8 WNVY Pensacola, Fla.	250
KFMJ I UISE, UKIE. 1000U KRAK Sacramento, Calif. 5000U K250 TONIOUS, TONIOUS, INC. WIND W Palm Basch	1000 Fla. 250
KEED Springfield, Oreg. 1000d KGFM Reise, Idaho 10000 WKNX Saginaw, Mich. 10000d WBIA Augusta, Ga.	1000q
WBU Butter, Pa. 1000d WSIV Pekin, III. 1000d WAVE Daylor Ohio. 250d WXLI Dublin, Ga.	250 d
WSMT Sparts, Tenn, 1000d with San Juan, P.R. 500 WCAU Philadelphia, Pa. 50000 WCM WGM Savennesh Ca	1000 250
KLEN Killeen, Tex. 250d KSOO Sloux Falls, S.Dak. 10000 1220—245.8 WAYX Wayeross, Ga. KWLD Liberty, Tex. 250d KORC Mineral Wells, Tex. 250d KARR Rurley Idahe	1000
KPLA Plainview, Tex. 1000d WRVA Richmond, Va. 50000 CJOC Lethbridge, Alta, 10000 KORT Grangeville, Idal	250 he 250 1000
WEAT Gate City, Va. 250d 1150—260.7 CKDA Victoria, B.C. 10000 KRXK Rexburg, Idaho	, 1000
WBRG Lynenburg, Va. 10000 CKSA Lloydminister, Alta, 10000 CKCW Moneton, N.B. 10000 WOLLA Moline, Ill.	1000
KNBX Kirkland, Wash. 1000d CKOC Hamilton, Ont. 10000 CKSM Shawinigan, Quenec 1000 WJOB Hammond, Ind.	1000
WECK EAU CIRITS, WIS. 1000 CKTR Three Rivers, Que. 1000 WARE Follower Ale 1000 WICJ Tell City. Inc.	1,000
WLIP Renorms, Wis. 250d WBCA Bay Minette, Ala. 1000d WSA MeGehee Ark. 1000d WSA Megehee Ark. 1000d WSA Megehee Ark.	nd, 1000d wa 1000
FOOD KITP Fewler, Calif. 2500 With Deputite My	v. 1000d
1060—282.8 WRD Tuscalossa, Ala. 5000 KRLP Fowler, Calif. KLP Fowler, Calif. KLP Fowler, Calif. KLP Fowler, Calif. Calif. KLP Fowler, Calif. KLP Fowler, Calif. KLP Fowler, Calif. KLP Fowler, Calif. KLP Fowler, Calif. Calif. KLP Fowler, Calif. Calif. KLP Fowler, Calif. KLP Fowler, Calif. Calif. KLP Fowler, Calif. Calif. Calif. KLP Fowler, Calif.	10004
VILPO Temps Ariz 500 WEVD Los Angeles, Calif 5000 WDEE Hamden, Conn. 1000d WSHO New Orleans, L	_a. 1000
KPAY Chico, Calif. 10000 KIAX Santa Rosa, Calif. 5000 1 7 4 5 5 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7	250 250
WHOE New Urlears, La. Sould KGMC Englewood, Colo. 1000d WRET Miami, Fla. 250d WITH Baltimore, Md.	1000
	d. 1000 ass. 250
WMAP Monroe, N.C. 250d WHOF Canton, Ohlo 1000d WTMP Tampa, Fla. 5000d WPLK Rockmart, Ga. 500d WESX Salem. Mass. M WRCV Philadelphia, Pa. 50000 WFMP Fort Valley. Ga. 1000d WFT Themsston, Ga. 250d WNES Worcester. Mass.	1000 s. 1000
WRCV Philadelphia, Pa. 50000 WFPM Fort Valley, Ga. 10001 WIRD I Salla III 1000d WIED Grand Panide	
1070—280.2 WEM Valdosta, Ga. 50000 WKRS Waukegan, III. 1000d WKB Iron River, Mic CFAX Vletoria, B.C. 10000 WJRL Rockford, III. 5000d WSLM Salem, Ind. 1000d WMPC Lapeer, Mich.	250
CEA Sackville, N.B. 50000 KWKY Des Moines Iowa 1000 KNUR Independence, Iowa 250d WSDO Sit. Ste. Marie. CHOK Sarnia. Ont. 5000 KNL Salina. Kans. 5000 KOUR Independence, Iowa 250d WSTR Sturgis, Mich.	Mich, 1000 1000d
CHOR Sarnia, Unit Sale Salina, Kans. Soud Koro Ottawa, Kans. 250d WKLK Cloquet, Minn.	1000 Mires 100
KNX Les Angeles, Callf. 50000 WJC0 Mumferdville, Ky. WVCG Coral Gables, Fla. 1000d WJB0 Baton Rouge, La. 50000 WJB0 Baton Rouge, La. 50000 WGHM Skowhegan, Maine KFDI Wichita, Kans. 10000 WHMC Galthersburg, Md. 1000 WSME Sanford, Maine 10000 KTRF Thief Riv. Fils.	. 250 250
WVCG Coral Gables, Fia. 1000d WJBO Baton Rouge, La. 5000 KBCL Shreveport, La. 250d KYSM Mankato, Minn. WIBC Indianapplis, Ind. 50000 WGHM Skowhegan, Maine 5000d WLBI Denham Springs, La. 250d KMRS Morris, Minn.	
WED! Wishits Were 10000 William Sales and 1000 WEMF Senford Maine 1000d KTRF Thief Riv. Fils.	
WEST indiangular, was a second of the first with the first was a second of the first was a secon	1000

Kc. Wave Length	W.P.	Kc. Wave Length	W.P.		W.P.		P.
WHSY Hattlesburg, Miss.	1000	KRDO Colo. Sprgs., Colo.	250 250	WONE Elkins, W.Va. WOMT Manitowoc, Wis.	1000 250		000
WSSO Starkville, Miss. WAZF Yazoo City, Miss.	250 250	KDGO Durango, Colo, KSLV Monte Vista, Colo,	1000	WIBU Poynette, Wis.	250	KWSH Wewoka-Seminole.	
KODE Jopiln, Mo.	1000 250	WWCO Waterbury, Conn.	1000	WOBT Rhinelander, Wis. WJMC Rice Lake, Wis.	1000	Oklahoma I KMCM MeMinnville, Oreg. I	000
KLWT Lebanon, Mo. KNCM Moberly, Mo.	1000	WBGC Chipley, Fla. WLCO Eustis, Fla.	250	KFBC Cheyenne, Wyo.	1000	WWYN Erle, Pa. 5	5000 000d
KBMN Bozeman, Mont, KXLO Lewiston, Mont,	10000	WLCO Eustis, Fla. WINK Fort Myers, Fla.	250 250	KLUK Evanston, Wyo. KASL Newcastle, Wyo.	250	WISO Ponce, P.R. I	000
KLCB Libby, Mont.	250	WMMB Melbourne, Fla.	1000	KRAL Rawlins, Wyo. KTHE Thermopolis, Wyo.	1000		000d
KTNC Falls City, Nebr. KHAS Hastings, Nebr.	100 250	WFOY St. Augustine, Fla. WBHB Fitzgerald, Ga.	250		1000	KWYR Winner, S.Dak. 50	D00d
KELY Ely. Nev. KLAS Las Vegas, Nev.	250 250	WDUN Gainesville, Ga.	1000	1250-239.9 CHWO Oakville, Ont.	1000	WNOO Chattanooga, Tenn. 10 WMCH Church Hill, Tenn. 10	000d
KDOT Reno, Nev.	250	WLAG LaGrange, Ga. WBML Macon, Ga.	1000	CKBL Matane, Que.	5000	WDKN Dickson, Tenn. 10	D00d
WMOU Berlin, N.H. WTSV Claremont, N.H.	1000	WWNS Statesbore, Ga. WPAX Thomasville, Ga.	250	CKOM Saskatoon, Sask. WZOB Ft. Payne, Ala.	10000		000d
WCMC Wildwood, N.J.	100	WTWA Thomson, Ga.	250	WETU Wetumpka, Ala.	5000d	KPSO Faifurrias, Tex. 5	500 d
KALG Alamogordo, N.Mex.	250 250	KLEI Kailua, Hawaii KVNI Cosur d'Alene, Idaho	250	KAKA Wickenburg, Ariz. KWCX Willcox, Ariz.	500d 1000d		000d
KOTS Deming, N.Mex. KYVA Gallup, N.Mex.	250	KFLT Mountain Home, Idah	0 250	KFAY Fayetteville, Ark. KAJI Little Rock, Ark.	1000d	KTAE Taylor, Tex. 10	000d
KFUN Las Vegas, N.Mex. KRSY Roswell, N.Mex.	250	KWIK Pocatello, Idaho WCRW Chicago, III.	1000	KHOT Madera, Calif.	500d		5000 300d
WNIA Cheektowaga, N.Y.	1000	WEDC Chicago, III	1000d	KTMS Santa Barbara, Calif. KDHI Twenty-Nine Palms,	. 1000	KWIQ Moses Lake, Wash, 10	D000
WENY Elmira, N.Y. WHUC Hudson, N.Y.	250	WSBC Chicago, III. WEBQ Harrisburg, III. WTAX Springfield, III.	250	California	1000d	WWIS Black River Falls,	500 d
WLFH Little Falls, N.Y. WFAS White Plains, N.Y.	250 250	WTAX Springfield, III. WSDR Sterling, III.	1000	KMSL Ukiah, Calif, KICM Golden, Colo.	500d	Wis. 10	D00d
WSKY Asheville, N.C.	1000	WHBU Anderson, Ind.	250	WNER Live Oak, Fla.	1000d	KPOW Powell, Wyo.	5000
WFAI Fayetteville, N.C. WMFR High Point, N.C.	10000	KDEC Decorah, lowa KWLC Decorah, lowa	250 250	WRIM Pahokee, Fia. WDAE Tampa, Fia,	500d 5000	1270-236.1	
WISP Kinston, N.C.	1000d	KBIZ Ottumwa, Iowa	1000	WLYB Albany, Ga. WYTH Madison, Ga.	1000d		0000
WNNC Newton, N.C. WCBT Roanoke Rap., N.C.	250 250	KICO Spencer, Iowa KIUL Garden City, Kans.	1000	WIZZ Streator, III,	500d		0000 5000
KDIX Dickinson, N.Dak,	250 250	KIUL Garden City, Kans. KAKE Wichita, Kans.	250 250	WGL Ft. Wayne, Ind. WRAY Princeton, Ind.	10000	CFGT St. Joseph d'Alma,	
WCPO Cincinnati, Ohio WCOL Columbus, Ohio	250	WINN Louisville, Ky. WFTM Maysville, Ky.	1000	KCFI Cedar Falls, lowa	500d		000d
WIRO Ironton, Ohio WTOL Toledo, Ohio	250 1000d	WPKE Pikeville, Ky. WSFC Somerset, Ky.	1000	KFKU Lawrence, Kans. WREN Topeka, Kans.	5000		000d
KADA N. Of Ada. UKIA.	250	KASO Minden, La.	250	WNVL Nicholasville, Ky.	500	KDJI Holbrook, Ariz. 10	D00d
WBBZ Ponca City, Okla. KIAL Astoria, Oreg.	250 250	KANE New Iberia, La. WCOU Lewiston, Maine	250 1000	WLCK Scottsville, Ky. WGUY Bangor, Maine	500d	KADL Pine Bluff, Ark, 50 KCCK Tulare, Calif. 50	000d
KRNS Burns, Oreg.	250	WCEM Cambridge, Md.	250	WARE Ware, Mass, WWBC Bay City, Mich.	1000	WNOG Naples, Fla. 5	500d
KOOS Coos Bay, Oreg. KGRO Gresham, Oreg.	1000	WHA! Greenfield, Mass.	250	KOTE Fergus Falls, Minn.	1000d	WHIY Orlando, Fia. 50	000d 5000
KYJC Medford, Oreg. KQIK Lakeview, Oreg.	1000	WOCB W. Yarmouth, Mass. WATT Cadillac, Mich.	1000	KOTE Fergus Falls, Minn. KCUE Red Wing, Minn.	1000d 5000	WKRW Cartersville, Ga.	500d
KTDO Toledo, Dreg.	250 250	WCBY Cheboygan, Mich.	250 250	WHNY McComb. Miss. KHTN Houston, Mo.	500d		000d 000d
WBVP Beaver Falls, Pa. WEEX Easton, Pa.	1000 250	WCBY Cheboygan, Mich. WJPD Ishpeming, Mich.	1000d	WKBR Manchester, N.H. WMTR Morristown, N.J.	5000d	KNDI Honolulu, Hawaii	5000 5000
WKBO Harrisburg, Pa.	1000	WJIM Lansing, Mich. WMFG Hibbing, Minn.	1000	WIPS Ticonderoga, N.Y.	1000d	WEIC Charleston, III. 10	000d
WCRD Johnstown, Pa. WBPZ Lock Haven, Pa.	1000	WJON St. Cloud, Minn. WMPA Aberdeen, Miss.	250	WFAG Farmville, N.C. WBRM Marion, N.C.	500d 1000d	WHBF Rock Island, III,	5000 5000
WTIV Titusville, Pa.	1000	WGRM Greenwood, Miss.	250	WCHO Washington Court		WWCA Gary, Ind.	1000
WNIK Arecibo, P.R. WERI Westerly, R.I.	1000	WGCM Gulfport, Miss. WMIS Natchez, Miss.	250 250	House, Ohio KQEN Roseburg, Oreg.	500d 5000d	WORX Madison, Ind. KSCB Liberal, Kans.	000d
WAIM Anderson, S.C.	0001 b0001	KFMD Flat River, Mo.	250	WLEM Emporium, Pa,	1000d	WAIN Columbia, Ky. 10	000d
WNOK Columbia, S.C. WOLS Florence, S.C.	1000	KFMD Flat River, Mo, KWOS Jefferson City, Mo, KODE Joplin, Mo.	1000d	WPEL Montrose, Pa. WRYT Pittsburgh, Pa.	1000d 5000		000d 000d
KISD Sioux Falls, S.Dak, WAKI McMinnville, Tenn,	1000d	KNEM Nevada, Mo.	250	WNOW York, Pa.	1000d	WSPR Springfield, Mass.	5000
KSIX Corpus Christi, Tex	250	KBMY Billings, Mont. KLTZ Glasgow, Mont.	1000 250 250	WTMA Charleston, S.C. WCKM Winnsboro, S.C.	5000 500d	WXYZ Detroit, Mich. KWEB Rochester, Minn.	5000 500d
KDLK Del Rio, Tex. KNUZ Houston, Tex.	1000	KLTZ Glasgow, Mont. KBLL Helena, Mont.	1000	WKBL Covington, Tenn. WNTT Tazewell, Tenn.	1000d 500d	WVOM loka, Miss,	000d
KERV Kerryllie, Tex.	250 250	KFOR Lincoln, Nebr. KODY North Platte, Nebr.	1000	KFTV Paris, Tex. KPAC Port Arthur, Tex.	500d	KUSN St. Joseph, Mo. 10	000d
KLVT Levelland, Tex. KEEE Nacogdoches, Tex.	1000	KELK Elko, Nev.	1000 250	KPAC Port Arthur, Tex. KUKA San Antonio, Tex.	5000 500d	KBLB Sparks, Nev. 10	000d 5000
KOSA Odessa, Tex.	250 250	WSNJ Bridgeton, N.J. KAVE Carisbad, N.Mes. KCLV Clovis, N.Mes.	1000	KTFO Seminole, Tex. KANN Ogden, Utah	1000d	WDVL Vineland, N.J.	500d
KHHH Pampa, Tex. KSEY Seymour, Tex.	1000	WEBB Freeport, N.T.	250	KVEL Vernal, Utah	5000d		000d
KSST Sulphur Sprgs., Te KWTX Waco, Tex.	x. 250 250	WITM Ismestown, N.Y.	1000d	WDVA Danville, Va. WYSR Franklin, Va.	5000 1000d	WDLA Walton, N.Y.	000d
KMUR Murray, Utah KOAL Price, Utah	250 250	WVOC Liberty NV	250	WNRG Grundy, Va.	1000d		000d
WJOY Burlington, Vt. WBB! Abingdon, Va.	1000	WNBZ Saranac Lake, N.Y. WSNY Schenectady, N.Y.	1000 l	KWSC Pullman, Wash, KTW Scattle, Wash.	1000	KBOM Mandan, N.Dak.	1000 000d
WCFV Clifton Forge, Va.	10000	WATN Watertown, N.Y.	250 250	WEMP Milwaukee, Wis.	5000	KWPR Claremore, Okla,	500d
WFVA Fredericksburg, Va.	1000	WIST Charlotte, N.C.	1000	1260-238.0	*****	KAJO Grants Pass, Oreg. 5	000d
WNOR Norfolk, Va. KWYZ Everett, Wash.	1000	WONC Ellzsheth City N.C.	1000	CFRN Edmonton, Alta. DYBU Cebu. P.I.	1000	WBHC Hampton, S.C.	000d
KLYK Spokane, Wash, KREW Sunnyside, Wash,	1000	WRAL Raleigh, N.C.	1000	WCRT Birmingham, Ala. KPIN Casa Grande, Ariz.	5000d		000d
WLOG Logan, W.Va.	1000		. 250	KCCB Corning, Ark.	500d	KIOX Bay City, Tex.	000d
WTAP Parkersburg, W.Va. WHBY Appleton, Wis.	1000 250	WHIZ Zanesville, Unio	250 250	KBHC Nashville, Ark. KGIL San Fernando, Calif.	500d	KEPS Eagle Pass, 1ex.	000d
WCLU Janesville, Wis.	1000 250		250	KYA San Francisco, Calif.	5000		5000 000d
WHVF Wausau, Wis, KVOC Casper, Wyo.	1000		250 250	KSNO Aspen, Colo, WMMM Westport, Conn.	5000d	WHEO Stuart, Va.	000d
1240-241.8		KFLY Corvallis, Oreg.	1000d	WMMM Westport, Conn. WNRK Newark, Del.	500d		000d 000d
CFLM La Tuque, Que.	1000	KKID Pendleton, Oreg. KPRB Redmond, Oreg.	1000 250	WWDC Washington, D.C. WFTW Fort Walton Beach,	5000	WKYR Keyser, W.Va. 5	000d
CFNW Norman Wells,		WRTA Altoona, Pa.	1000	WAME Miaml, Fla.	1000d 5000d		500 d
OFPR Prince Rupert, B.		WHUM Reading, Pa. WKOK Sunbury, Pa.	250 250	WWPF Palatka, Fla.	1000	1280—234.2	5000
CJAV Port Alberni, B.C.	250	WBAX Wilkes Barre, Pa.	1000	WHAB Baxley, Ga. WBBK Blakely, Ga.	5000d	CIMS Montreal, Que.	0000
CJCS Stratford, Ont. CJRW Summerside, P.E.I	, 1000 , 250	WWON Woonsocket, K.I.	1000	WTJH East Point, Ga.	5000d	CKCV Quebec, Que.	0000
CKBS St. Hyacinthe, Que. CKCQ-I Williams Lake, B	250	WKDK Newberry, S.C.	250 250	KIFI idaho Falls, Idaho KWEI Weiser, Ida.	5000 1000d	WPID Pledmont, Ala. 16	000d
CKLS LaSarre, Que.	250	WBEJ Elizabethton, Tenn,	1000	KWEI Weiser, Ida. WIBV Belleville, 111,	1000d 5000		5000 000d
WEBJ Brewton, Ala.	250 250	WEKR Fayetteville, Tenn. WBiR Knoxville, Tenn.	1000	WFBM Indianapolis, Ind. KFGQ Boone, Iowa	250d	KNRY Nawnort Ark	000d
WULA Eufaula, Ala. WOWL Florence, Ala.	1000	WKDA Nashville, Tenn.	1000	KWHK Hutchinson, Kans. WXOK Baton Rouge, La.	1000d	KFOX Long Beach, Calif. KCJH San Luis Obiano, Cal. KJOY Stockton, Calif.	500d
WARF Jasper, Ala. KVRD Cottonwood, Ariz.	1000 250	KVLF Alpine, Tex.	1000	WEZE Boston, Mass.	5000	KJOY Stockton, Calif.	1000
KZOW So. of Globe, Ariz.	1000	KEAN Brownwood, Tex.	1000 250	WALM Albion, Mich. WJBL Holland, Mich.	1000 5000d	WSUK Seaford, Del.	000d
KOFA Yuma, Ariz. KVRC Arkadelphia, Ark.	250 250	KOCA Kilgore, Tex.	250	KROX Crookston, Minn, KDUZ Hutchinson, Minn.	1000	WDSP Deruniak Springs,	000d
KWAK Stuttgart, Ark. KPLY Crescent City, Calif	250	KSOX Raymondville, Tex.	250 250	WCVM Greenville Miss	1000d 5000d	WQIK Jacksonville, Fla. 56	000d
KMBY Monterey, Calif.	1000	KXOX Sweetwater, Tex.	250	WNSL Laurel, Miss. KGBX Springfield, Mo, KIMB Kimball, Nebr.	5000d 5000	WYND Sarasota, Fia.	000d 500d
KPPC Pasadena, Calif. KLOA Ridgecrest, Calif.	100 250	WSSV Petersburg, Vt.	1000	KIMB Kimball, Nebr.	10004	WIBB Macon, Ga. 5	000d
KLOA Ridgecrest, Calif. KROY Sacramento, Calif. KRNO San Bernardino,	1000	WROV Roanoke, Va.	1000	WBUD Irenton, N.J.	1000	WGBF Evansville, Ind.	5000
Californi			250	KVSF Santa Fe, N. Mex. WBNR Beacon, N.Y.	1000d 5000		000d
KSON San Diego, Calif. KSMA Santa Maria, Calif.	250		1000	WGWR Asheboro, N.C.	5000d		
KSUE Susanville, Calif.	1000	WKOY Bluefield, W.Va. WTIP Charleston, W.Va.	1000	WCDJ Edenton, N.C.	1000d	WHITE'S RADIO LOG	163

Kc. Wave Length W.	P. Kc. Wave Length	W.P. I	Kc. Wave Length	W.P.	Kc. Wave Length W	'.P.
WCPM Cumberland, Ky. 100	0d KWKW Pasadena, Calif	1000	1320—227.1		WOLD Marion, Va. 10	000d
WOSU New Orleans, La. 50 KWCL Oak Grove, La. 50	00 KVOR Colo. Sprgs Col 0d WAVZ New Haven, Co 00 WRKT Cocoa Beach, Fl	o. 1000 nn. 1000	CHQM Vancouver, B.C.	10000	WESR Tasley, Va. 10	000d
WEIM Fitchburg, Mass. 50	00 WRKT Cocoa Beach, Fl	a. 500d	CKEC New Glasgow, N.S.	5000	KFKF Bellevue, Wash, 50 KCFA Spokane, Wash, 50	100d
WFYC Alma, Mich, 100	od were Marathon, Fla.	500d 1	CJSO Serel, P.Q.	1000	KCFA Spokane, Wash, 50 WETZ New Martinsville, W.Va, 10	
WTCN Minneapolis, Minn. 50	100 W SOL Tampa, Fla.	5000d	CKKW Kitchener, Ont.	1000	W.Va. 10	000d
KVOX Moorhead, Minn. 10 KDKO Clinton, Mo. 100	00 WMTM Moultrie, Ga. 0d WNEA Newman, Ga.	5000d 500	WAGF Dothan, Ala. WENN Birmingham, Ala.	5000d	William Shoudy gall, Wis.	1000 5000
KYRO Potosi, Mo. 50	Od WIMO Winder, Ga.	10004	KRI II Yuma, Ariz	500d		,000
	Od KOZE Lewiston, Idaho	5000	KWHN Fort Smith, Ark, KRLW Walnut Ridge, Ark,	5000	1340—223.7	
KTOO Henderson, Nev. 500 KRZE Farmington, N.Mex. 500	0d WTAQ LaGrange, III. 0d WFRX W. Frankfort, II	1, 1000d	KHSJ Hemet, Calif.	1000d	CFGB Goose Bay, Nfld. I	1000 250
WADO New York, N.Y. 50	00 WHLT Huntington, Ind.	500d	KLAN Lemeore, Calif.	1000d	CFSL Weyburn, Sask.	1000
WROC Rochester, N.Y. 500	Od WMFT Terre Haute, Ind	l. 500d	KUDE Oceanside, Calif.	500 [CPYK Yellow Knife, N.W.T.	250
	100 KGLO Mason City, low	a 5000 l	KCRA Sacramento, Calif. KAVI Rocky Ford, Colo.	5000 1000d	CHAD Amos, Que, CJLS Yarmouth, N.S.	250 250
WYAL Scotland Neck, N.C. 500 WONW Defiance, Ohio	0d WBLG Lexington, Ky. 100 WIBR Baton Rouge, La	1000	WATR Waterbury, Conn.	5000	CHRD Drummondville, Que.	250
WLMJ Jackson, Ohio 100	0d KANB Shrevepert, La.	100091	WGMA Hollywood, Fla.	1000d	CJQC Quebec, Que.	250
	0d WFBR Baltimore, Md.	5000	WZOK Jacksonville, Fla. WAMR Venice, Fla.	5000	CKAR-I Parry Sound, Ont.	250
	00 WJDA Quincy, Mass. 0d WOOD Grand Rapids, N	1000d		500d 5000d	CKOX Woodstock, Ont, WKUL Cullman, Ala.	250 250
WHVR Hanover, Pa. 50	00 WRBC Jackson, Miss.	5000	WKAN Kankakee, III.	1000	WIUI Florence, Ala.	1000
WKST New Castle, Pa. 10	100 KMMO Marshall, Mo.	1000d	KNIA Knoxville, Iowa	500d		250
WCMN Arecibe, P.R. 50 WANS Anderson, S.C. 50	00 KBRL McCook, Nebr. 00 KPTL Carson City, Nev,	1000 d 5000	KMAQ Maquoketa, Iowa KLWN Lawrence, Kans,	500d 500d	KIRH Seward, Alaska	250 250
WJAY Mullins, S.C. 500	Od WAAT Trenton, N.J.	250d		1000d	KIKO Miami, Ariz,	250
WMCP Columbia, Tenn. 100	UO I WASC Fulton, N.Y.	10004	WNGO Mayfield, Ky.	1000d	KNOG Nogales, Ariz. KPGE Page, Ariz.	250
WDNT Dayton, Tenn, 100 KNIT Abilene, Tex. 50		5000d		1000d	KPGE Page, Ariz. KENT Prescott, Ariz.	250 250
KWHI Brenham, Tex. 100	Od WGOL Goldsboro, N.C. Od WLNC Laurensburg, N.C	500 1	WARA Attleboro Moss	1000d	KBTA Batesville, Ark.	1000
KLUE Longview. Tex. 100	Od WSYD Mt. Airv. N.C.	5000	WILS Lansing, Mich, WDMJ Marquette, Mich, WRJW Picayune, Miss,	5000	KAAB Hot Springs, Ark,	500
KRAN Morton, Tex. 50	00 WERE Cleveland, Ohio	5000	WDMJ Marquette, Mich,	1000	KBRS Springdale, Ark,	250
KVWG Pearsall, Tex. 50	Od WMVO Mt. Vernon, Ohi	o 500	WRJW Picayune, Miss, KXLW Clayton, Mo.	5000d 1000d	KENL Areata, Calif. KMAK Fresno, Calif KDOL Mojavo, Calif.	250 1000
KNAK Salt Lake City, Utah 50 WKDE Altavista, Va. 50	Od KDOV Medford, Oreg.	5000 5000d	KOLT Seettsbluff, Nebr	5000	KDOL Mojave, Calif.	100
WYVE Wytheville, Va. 100	Od KACI The Dalles, Oreg.	1000d	KOLT Seottsbluff, Nebr. WWHG Hornell, N.Y.	5000d	KSFE Needles, Calif. KAUR Oroville, Calif.	250
KUDY Spekane, Wash. 500	Od WWCH Clarion, Pa.	500d I '	WQSR Solvay, N.Y.	500d	KAUR Oroville, Calif. KATY San Luis Obispo.	250
KIT Yakima, Wash, 50 WVAR Richwood, W.Va. 100	00 WTHT Hazleton, Pa.	10004	WAGY Forest City, N.C.	1000 5000	California	1000
WVAR Richwood, W.Va. 100 WNAM Neenah, Wis. 50	00 WLOW Aiken, S.C.	500wd	WCOG Greensboro, N.C. WEEW Washington, N.C.	500d	KIST Santa Barbara, Calif. KOMY Watsonville, Calif.	1000
	WCKI Greer, S.C.	10004	KQDY Minot, N.Dak.	1000d	KUMY Warsenville, Calif.	250
1290232.4	WKSC Kershaw, S.C.	500d	WHOK Lancaster, Ohio	1000d	KDEN Deliver, Colo. KWSL Grand Junction, Colo.	250
CFAM Altona, Man. 100 CKSL Lenden, Ont. 50		n, 5000d		1000d	KVRH Salida, Colo.	250
CKSL Lenden, Ont. 50 WTHG Jackson, Ala, 100	na IW MAK Nashville, Tenn.	. 5000 L	WKAP Allentown, Pa.	5000	WN HC New Haven, Conn.	1000
WSHF Sheffield, Ala. 100	Dd KVET Austin, Tex.	1000	WGET Gettysburg, Pa.	1000	WOOK Washington, D.C. WSLG Clermont, Fla.	250 250
WMLS Sylacauga, Ala. 100	Od KTFY Brownfield, Tex.	1000d 1	WJAS Pittsburgh, Pa. WSCR Scranton, Pa.	5000 1000	WTAN Clearwater, Fla.	250
KEOS Flagstaff, Ariz. 10 KCUB Tueson, Ariz. 10	no IKKAS Silsbee. Tex.	500d	WUNO Rio Piedras, P.R.	5000	WTAN Clearwater, Fla. WROD Daytona Beh., Fla.	1000
KDMS El Dorado, Ark. 500	ANTROTU LOGAR, UTAR	1000	WOIC Columbia, S.C.	1000		1000
KUOA Siloam Speas. Ark. 500	Od KOL Seattle, Wash,	5000	KELO Sioux Falls, S.Dak,	5000d	WOXT Palm Beach, Fla.	250
KHSL Chico, Calif. 50 KPER Gilroy, Calif. 500	00 WCLG Morganiswii, W.V	a. 1000d		10000	WSEB Sebring, Fla.	250
KHSL Chies, Calif. 50 KPER Gilroy, Calif. 500 KMEN San Bernardine,	1210 00 0000		KVMC Colo City Tay	10004	WNSM Valparaiso-Niceville, Fla.	260
California 30	00 1310—228.9		KXYZ Houston, Tex. KCPX Salt Lake City, Utah	5000	WAKE Atlanta, Ga.	1000
KACL Santa Barbara, Calif. 500 WCCC Hartford, Conn. 50	Od CECM Pichmond Hill (50000 L	WDMS Lynchburg, Va.	1000	WGAU Athens, Ga.	1000
WTUX Wilmington, Del. 100	Od CFGM Richmond Hill, I Od WHEP Foley, Ala,	10004	WEET Richmond, Va. KXRO Aberdeen, Wash,	1000d		1000
WTMC Ocala, Fla. 50	00 CHGB St. Anne-de-la-F	ocatiere,	KXRO Aberdeen, Wash,	5000	WOKS Columbus, Ga.	1000
WSCM Panama City Beach, Florida 50		5000d		1000q	WBBI Lyons, Ga,	250
WIRK W. Palm Beh., Fla. 50		5000	WFHR Wisconsin Rapids.			1000
WDEC Americus, Ga. 100	Od IKBOK Malvern. Ark.	10004	W1s.	. 5000	KPST Preston, Idaho	250
WCHK Canton, Ga. 100	Od KIOT Barstow, Calif.	500d	1330—225.4	- 1	KSKI Sun Valley, Idaho	1000
WOKA Douglas, Ga. 100	Od KPOD Crescent City, Ca	1000	WROS Scottsboro, Ala.	1000d	WSOY Decatur, III.	1000
WTOC Savannah, Ga. 50 KSNN Pocatello, Idaho 100	00 KDIA Oakland, Calif. 0d KTKR Taft, Calif.	10000	WROS Scottsboro, Ala. KMOP Tucson, Ariz,	500d	WJPF Herrin, III. WJOL Joliet, III.	250 250
WIRL Pearia, III. 50	00 KFKA Greeley, Colo.	1000	KVEE Conway, Ark.	500d	WRIW Bedford, Ind.	1000
WCBL Benten, Ky. 500	00 WICH Norwish, Conn. 0d WDOO Deland, Fla.	5000 5000d	KLPC Lompoc, Calif.	5000	WTRC Elkhart, Ind. WLBC Muncie, Ind.	1000
KIEF Jennings, La. 100	Od I WAUC Wauchula, Fla.	500d	KFAC Los Angeles. Calif. KLBS Los Banos, Calif.	500d	KROS Clinton, lowa	250
WHGR Houghton Lake, Mich. 50	00 WBRO Waynesboro, Ga. 0d WBMK West Point, Ga	1000d	KAHR Redding, Calif.	5000d	KLIL Estherville, Iowa	100
WNIL Niles, Mich. 50 WOIA Saline, Mich. 50	Od KNUI Makawao, Hawai	1 1000 1	WARN Ft. Pierce, Fla. WYSE Lakeland, Fla.	1000d	KCKN Kansas City, Kans. KSEK Pittsburg, Kans.	250 250
KBMD Benson, Minn. 50	Od I K Lix Twin Falls, Idah	a 5000 l	WEBY Milton, Fla.	5000d	WCMI Ashland, Kv.	250
WBLE Batesville, Miss. 100		5000	WMEN Tallahassee, Fla.	5000d	WBGN Bowling Green, Ky.	250
KALM Thayer, Mo. 100	0d KDLS Perry, Iswa 00 KOKX Keskuk, Iswa	500d 5000	WMLT Dublin, Ga. WEAW Evanston, III.	5000d 5000d	WNBS Murray, Ky.	250
KOIL Dmaha, Nebr. 50	100 WITL Madisonville, Ky	. 500d	WRAM Monmouth, III.	1000d	WEKY Richmond, Ky. KVOB Bastrop, La.	250 250
WKNE Keene, N.H. 50	00 WDOC Prestonsburg, K		WRRR Rockford, III.	1000d	KRMD Shreveport, La.	250
KSRC Socorro, N.M. 100	0d KIKS Sulphur, La. 00 KUZN W. Monroe, La.	500d	WJPS Evansville, Ind.	5000 5000	WFAU Augusta, Maine	1000
	100 WLOB Portland, Maine	10000	KWWL Waterloo, lowa KFH Wichita, Kans, WYGD Corbin, Ky.	5000		1000
WHKY Hickory, N.C. 50	000 WORC Worcester, Mass	5000 h. 5000	WYGD Corbin, Ky.	5000d	WNBH New Bedford, Mass.	1000
WEYE Sanford, N.C. 100 WOMP Bellaire, Ohio 100	Od WKMH Dearborn, Micl	h 5000 l	WMUR Moreneau, Ky.	1000d	WBRK Pittsfield, Mass.	1000 250
WHIO Dayton, Ohio 50	00 KRBI St. Peter, Minn.	100004	KVOL Lafayette, La. WASA Harve deGrace, Md.	10000	WLEW Bad Axe, Mich. WLAV Grand Rap., Mich, WCSR Hillsdale, Mich. WMTE Manistee, Mich.	1000
KUMA Pendieton, Oreg. 50	00 WXXX Hattlesburg, MI	ss. t000d	WCRB Waltham, Mass. WTRX Flint, Mich.	5000	WCSR Hillsdale, Mich.	1000
KLIQ Portland, Oreg. 50	00d KESB Joplin, Mo.	5000	WTRX Flint, Mich. WLOL Minneapolis, Minn,	5000	WMTE Manistee, Mich.	1000
	DOD KFSB Joplin. Mo. DOO KFBB Great Falls. Mo: KGMT Fairbury, Nebr.	nt. 5000 500d	WIPR Greenville Miss	5000 1000	WALN Menominee, Mich.	250 1000
WFIG Sumter, S.C. 10 WATO Oak Ridge, Tenn, 5	00 WILK Asbury Park. N	.J. 250	WJPR Greenville, Miss. WDAL Meridian, Miss. KUKU Willow Springs, Mo.	10004	WEXL Royal Oak, Mich.	250
WATO Oak Ridge, Tenn. 5	KW I W CAM Camden, N.J.	250	KUKU Willow Springs, Mo.	1000d		1000
	Od KARA Albuquerque, N. Od WVIP Mt. Kisee, N.Y.	M. 1000dl	KGAK Gallup, N.Mex. WEVD New York, N.Y.	5000 5000	WEVE Eveleth, Minn, KROC Rochester, Minn.	1000
KRGV Weslaco, Tex. / 5	000 WTLB Uties, N.Y.	1000	WPOW New York, N.Y.	5000	KWLM Willmar, Minn.	1000
KTRN Wichita Falls, Tex. 5	JUU I WISE Asheville, N.C.	5000	WEBO Owana, N.Y.	1000d	i WIMB Brookhaven, Miss.	250
WAGE Leesburg, Va. 10	MOIWTIK Durham N.C.	1000	WHAZ Troy, N.Y. WUSM Havelock, N.C. WHOT Campbell, Ohio	10000	WAML Laurel, Miss. KXEO Mexico. Mo.	250 250
WKWS Rocky Mount, Va. 10	DOD KNOX Grand Forks, N	.Dak. 5000	WHOT Campbell, Ohio	500	KLID Poplar Bluff, Mo.	250
WVOW Logan, W.Va. 5	000 WFAH Alliance, Ohio	10000	WFIN Findlay, Ohio	1000d	I VOMO Calam Ma	250
KAPY Port Angeles, Wash, 10 WMIL Milwaukee, Wis. 10	Old WRED Redford Pe	5000 5000d	WKOV Wellston, Ohio WELW Willoughby, O.	500d 500wd	KICK Springfield, Mo. KCAP Helena, Mont.	250 250
WCOW Sparta, Wis. 50	00d WBFD Bedford, Pa. 00d WGSA Ephrata, Pa.	5000d	KPOJ Portland, Oreg.	5000	KPRK Livingston, Mont.	250
	000 WGSA Ephrata, Pa. 000 WNAE Warren, Pa. WDKD Kingstree, S.C.	5000d	KPOJ Portland, Oreg. WBLF Bellefonte, Pa.	500	KPRK Livingston, Mont. KATL Miles City, Mont.	1000
1300230.6	WDKD Kingstree, S.C.	5000d	WICU Erle, Pa. WLAT Conway, S.C.	5000 5000d	I KOTE Missoula, Mont.	250 500
	WDOD Chattanooga, T 000 WDXI Jackson, Tenn.	enn. 5000 5000	WFBC Greenville, S.C.	5000	KHUB Frement, Nebr. KGFW Kearney, Nebr.	1000
CBAF Moneton, N.B. 5 CJME Regina, Sask. 1	nnn IWBNT Dneida, Tenn.	1000d	WFBC Greenville, S.C. WAEW Crossville, Tenn.	1000d	KSID Sidney, Nebr.	1000
W HSA HORZ, Ala. 5	00d KZIP Amarillo, Tex.	10004	WIDD Dyserburg Tons	500d 500d	KSID Sidney, Nebr. KORK Las Vegas, Nev. KBET Reno, Nev.	250 1000
WTLS Tallassee, Ala. 10 KWCB Searcy, Ark. 10	NOW I KOYL Odessa, Tex.	5000 1000d	KSWA Graham, Tex.	500d	I W U L K Hanover, N.D.	1000
KROP Brawley, Callf. 1	000 KUBO San Antonio, To	x. 5000d	KMIL Cameron, Tex. KSWA Graham, Tex. KINE Kingsville, Tex.	1000d	I WMID Atlantic City, N.J.	1000
KYNO Fresno, Calif. 5	000 WEEL Fairfax, Va.	a. 5000	IKVKM MODADADI, 16%.	5000 1000d	KNDE Aztec, N. Mex. KRRR Ruidoso, N. Mex.	250
	WGH Newport News, V KARY Presser, Wash,	m. 1000d	KDOK Tyler, Tex. WBTM Danville, Va.	5000	KRRR Ruidoso, N. Mex. KKIT Taos, N. Mex. KSIL Silver City, N. Mex.	250 250
164 WHITE'S RADIO L	OG WIBA Madison, Wis.	5000	WRAA Luray, Va.	1000d	KSIL Silver City, N.Mex.	1000

Kc.	Wave Length	W.P.	Ke Ways Laugh	WB	I Va Ways Laurell	14/ 0		
WMBO	Auburn, N.Y.	1000	KTI O Tableaush Okla	W.P.	WALK Patchogue N.V.	W.P. 500d		W.P. 5000
WENT	Gloversville, N.Y. lamestown, N.Y.	1000	KRVC Ashland, Orag. KLOO Corvallis, Orag.	1000d		5000	WEGF Presous Isla. Ma	5000d
WUSLL	ockport, N.Y. Massena, N.Y.	250	WORK York, Pa	5000	WTAB Tabor City, N.C.	1000d 5000d	WPLM Plymouth, Mass.	1000d 5000
WALL	Middletown, N.Y.	1000	WDAR Darlington, S.C. WGSW Greenwood, S.C. WRKM Carthage, Tenn.	10004	WSPD Toledo Obio	1000d 5000	WCER Charlotte, Mich. KAOH Duluth, Minn.	1000d 500
WIRLL	Plattsburgh, N.Y.	1000	WRKM Carthage, Tenn. KCAR Ciarksville, Tex.	1000d 500d	KASI Astoria Oreg.	1000	KRFO Owatonna, Minn.	500d
WISB	Lumberton, N.C. Oxford, N.C.	1000	KTXJ Jasper, Tex.	10004	WPAZ Pottstown, Pa	10000	WROA Gulfport, Miss. WQIC Meridian, Miss.	1000d 5000d
WOOW	Greenville, N.C.	1000		5000 1000d	WIVV Vlagues D.B.	1000d	KJPW Waynesville, Mo. KENN Farmington, N.Mex.	1000d 5000
WAIR	Wilmington, N.C. Winston-Salem, N.C.	1000	WFLS Fredericksburg Va	500d	WKFD Wickford, R.I.	500d	KHOB Hobbs, N. Max	5000d
KGPC	Grafton, N.Dak. Ashland, Ohio	1000 250	WAVY Portsmouth Va	5000	WDXE Lawrenceburg, Tenn.	1000d	WEOK Poughkeepsie, N.Y. WRIV Riverhead, N.Y.	5000d
MUUB	Athens, Ohio	250		5 000d	KOKE Austin, Tex.	10004	WFBL Syracuse, N.Y. WKRK Murphy, N.C.	5000 1000d
	Steubenville, Ohio	250 1000	1360-220.4 WWWB Jasper, Ala.	1000d	KFRO Longview, Tex.	1000 500d	WKRK Murphy, N.C. WEED Rocky Mount, N.C. WADA Shelby, N.C.	5000
KOCY	Hugo, Okla, Okla, City, Okla, Sand Springs, Okla,	250 250	W LIV MODILE, Ala.	5000d	KSOP Salt Lake City, Utah	10004	WJRM Trov. N.C.	500d
KTOW	Sand Springs, Okia. Enterprise, Oreg.	250 250		10009	WHEE Martinaville, Va.	1000d 5000d	KLPM Minot, N.Dak, WOHP Bellefontaine, Dhio	5000 500d
KIHR	lood River, Oreg.	250	KRUX Glendale, Ariz,	5000 500d	WIWS South Hill, Va.	5000d 1000d	WMPO Middleport.Pomroy,	1000d
WCVI C	orth Bend, Oreg. Connellsville, Pa.	1000 250	KFFA Heiena, Ark. KFIV Modesto, Calif.	1000	WMOD Moundsville, W.Va.	1000d	WFMJ Youngstown, Ohio	5000
WSAL	Frove City, Pa.	1000		10000	KVWO Cheyenne, Wyo.	1000	KSLM Salem, Ores.	1000 5000
WHAT	Oil City, Pa. Philadelphia, Pa.	1000	KGB San Diego, Calif.	5000 5000d	1380-217.3		WLAN Lancaster, Pa. WRSC State College, Pa.	5000 1000d
WTRN	Reading, Pa. Tyrone, Pa.	250	WDRC Hartford, Conn. WOBS Jacksonville, Fla.	5000	CFDA Victoriaville, Que	1000	WISA isabella, P.R. WHPB Belton, S.C.	1000
WWPA	Wilkes-Barre, Pa. Williamsport, Pa.	1000 250	WKAT Miami Beach, Fla.	5000d 5000	CKLC Kingston, Ont.	10000 5000	WCSC Charleston, S.C. KJAM Madison, S.D.	500d 5000
WGRF	Aguadilia, P.R. Charleston, S.C.	250	WSFR Sanford, Fla. WINT Winter Haven, Fla.	500d 1000d	WRAB Arab. Ala. WGYV Greenville, Ala.	1000d	WIJS Jackson, Tenn.	5000d 5000
WRHII	Rock Hill, S.C.	1000	WAZA Bainbridge Ga	10004	KDXE N. Little Rock, Ark, KBVM Lancaster, Calif.	1000d	KULP El Campo, Tex. KBEC Waxahachie, Tex.	500d 500d
KIJA H	umter, S.C. uron, S.D.	250	WLAW Lawrencevills, Ga. WMAC Metter, Ga.	1000d 500d	KGMS Sacramento Calif	1000	KLGN Logan, Utah	1000
WBAC (uron. S.D. Rapid City, S.Dak. Cleyeland, Tenn.	1000 250	WIYN Rome, Ga. WLBK DeKaib, III.	500d	KSBW Salinas, Calif. KFLJ Walsenburg, Colo.	5000 1000d	WEAM Arlington, Va. WWOD Lynchburg, Va.	5000 5000
A IV IV IM	Columbia, Lann.	1000	WVMC Mt. Carmel, III. WGFA Watseka, III.	500d	WAMS Wilmington, Del. WLIZ Lake Worth, Fla.	5000 500d	KBBO Yakima, Wash.	1000
WKGN	Greeneville, Tenn. Knoxville, Tenn.	1000	KXGI Ft. Madison, lowa	10004	WQXQ Ormand Beh., Fla.	10000	1400-214.2	
WCDT	Memphis, Tenn. Winchester, Tenn,	1000	KSCJ Sioux City, Iewa KBTO El Dorado, Kens, WFLW Monticello, Ky.	5000 500d	WLUT St. Petersburg, Fla.	5000 5000	CKDH Amherst, N.S. CJFP Riviere-du-Loup, Que.	1000
KWKC	Abilene, Tex.	250 250	WFLW Monticello, Ky. KDBC Mansfield, La.	10004	WSIZ Oellia, Ga. KPOI Honolulu, Hawaii	5000d 5000	CKRN Rouyn, Que, CKSW Swift Current, Sask,	250 1000
KAND (Corsicana, Tex.	250	KVIM New Iberia, La.	10004	WREL South Relait III	5000	WMSL Decatur, Ala.	250
KLBK I	l Paso, Tex. Lubbock, Tex. Lufkin, Tex.	250 250	KTLD Tallulah, La, WEBB Dundalk, Md.	500d 5000d	WBZI Brazil, Ind. WKJG Ft. Wayne, Ind.	500d 5000	WXAL Demopolis, Ala. WFPA Ft. Payne, Ala.	250 250
KRBA L	Lufkin, Tex. Pampa, Tex.	250 250	WLYN Lynn, Mass. WWRO Caro, Mich.	1000d 5000	KCIM Carroll, lowa	1000	WILD Homewood, Ala.	1000
KOLE P	ort Arthur, Tex.	250	WKMI Kalamazoo, Mich. KLRS Mountain Grove, Mo.	5000	KCII Washington, lowa WMTA Central City, Ky.	500d 500d		250
WTWN	St. Johnsbury, Vt.	1000	KWRV McCook, Nebr.	1000d	WWKY Winchester, Kv.	1000d	KJKJ Flagstaff, Ariz.	250 250
WKEY	Charlotte Amalie, V.I Covington, Va.	1000		10000	WYNK Baton Rouge, La, WKTJ Farmington, Me.	500d 1000d	KXIV Phoenix, Ariz.	250 250
WHAP	Covington, Va. Hopewell, Va. Drange, Va.	1000	WWBZ Vineland, N.J. WKOP Binghamton, N.Y. WMNS Olean, N.Y.	5000	WTTH Port Huron, Mich. WPLB Greenville, Mich.	1000 500d	KTUC Tucson, Ariz. KVOY Yuma, Ariz. KELD El Dorado, Ark.	1000
KAGT A	nacortes, Wash.	250	WCHL Chapel Hill, N.C. KEYZ Williston, N.D.	10009	KAGE Winona, Minn.	1000d	KCLA Pine Bluff, Ark. KWYN Wynne, Ark.	1000
KAPA F	Pasco, Wash. Raymond, Wash.	250 250	Womi Cincinnati, Uhio	5000	WDLT Indianola, Miss,	1000 500d	KRE Berkeley, Gally,	000
WHAR	Wenatchee, Wash. Clarksburg, W.Va.	250 250	WWOW Conneaut, Ohio KUIK Hillsboro, Oreg.	500d	KUDL Kansas City, Mo. KWK St. Louis, Mo. KUVR Holdredge, Nebr.	5000 5000	KREO Indio, Calif. KQMS Redding, Calif.	250 250
WEPM	Martinsburg, W.Va. Montgomery, W.Va.	250	WPQR McKeesport, Pa. WPPA Pottsville, Pa.	5000	WBBX Portsmouth, N.H.	1000	KQMS Redding, Callf. KSLY San Luis Obispo, Cal KSPA Santa Paula, Callf.	. 250 250
MOVE	Welch, W.Va.	1000	WELP ESSIEY, S.C.	10000	WAW7 Zaranhath M I	5000	KHOE Truckee, Calif. KUKI Uklah, Calif.	1000
WRIT M	.adysmith, Wis, lilwaukee, Wis, Yheatland, Wyo,	1000 250	WLCM Laneaster, S.C. WNAH Nashville, Tenn.	10000	WFSR Bath, N.Y. WBNX New York, N.Y.	500d 5000	KUNG Visalia, Calif.	1000 250
KWOR V	Wheatland, Wyo, Worland, Wyo,	250 250	KRAY Amarillo, Tex. KACT Andrews, Tex.	500d 1000d	WTOB Winston-Salem, N.C.	5000 5000	KRLN Canon City, Colo. KDTA Delta, Colo.	250 250
1350-	-222.1		KWBA Baytown, Tex.	1000	WWIZ Lorain, Ohio WPKO Waverly, Ohio	500d 1000d	KETM Ft. Morgan, Colo, KBZZ La Junta, Colo,	250 250
CHOV P	embroke, Ont.	0001	KRYS Corpus Christi, Tex. KXOL Ft. Worth, Tex.	5000	KSWO Lawton, Okla, KMUS Muskopee, Okla,	1000	WSTC Stamford, Conn. WILI Willimantic, Conn.	1000
CKLB 0	shawa, Ont, i	0000	WBOB Galax, Va. WHBG Harrisonburg, Va.	1000d 5000d	KBCH Ocean Lake, Ores	10004	WFIL Ft. Lauderdale, Fla.	1000 250
WIWI D	entville, N.S. Demopolis, Ala.	0000	KFDR Grand Coulee, Wash, KMO Tacoma, Wash,	1000d	KSRV Ontario, Oreg. WACB Kittanning, Pa.	5000 1000d	WIRA Ft. Pierce, Fia. WR4C Jacksonville, Fia.	250 250
WGAD (Sadsden, Ala,	000d 5000	WHJC Matawan, W.Va	5000 1000d	WMLP Milton, Pa. WAYZ Waynesboro, Pa.	1000d	WRMC Jacksonville, Fla. WPRY Perry, Fla. WTRR Sanford, Fla.	1000
KLYD B			WMOV Ravenswood, W.Va. WBAY Green Bay, Wis. WISV Virouqua, Wis.	5000	WNRI Woonsocket, R.I. WAGS Bishopville, S.C.	1000d	WZRH Zephyr Hills, Fla. WCQS Alma, Ga.	250
KSRO S	anta Rosa Calif.		WISV Virouqua, Wis. WMNE Menomonie, Wis.	10001	WGUS N. Augusta, S.C.	1000q	WSGC Elberton, Ga. WNEX Macon, Ga.	1000
MULK	ueblo, Colo. Jorwalk, Conn.	1000	KVRS Rock Springs, Wyo.	1000	KOTA Rapid City, S.Dak. KFCB Redfield, S.Dak. WYSH Clinton, Tenn.	5000 500d	WMGA Moultrie, Ga.	1000
WEZY C	utnam, Conn. I ocoa, Fla,	1000	1370—218.8		WGMM Millington Tann	1000d 500d	WCDH Newnan, Ga.	1000
WDCF D	lackshear, Ga.	000d l	WBYE Calera, Ala, CFLV Valleyfield, P.Q.	1000d	KJET Beaumont, Tex. KBWD Brownwood, Tex.	1000	WGSA Savannah, Ga. KART Jerome, Idaho	250
WRWH	Cleveland, Ga. I	000d	KTPA Presentt, Ark	1000 500d	KCRM Crane, Tax	10001	KRPL Moscow, Idaho KSPT Sandpoint, Idaho	250 250
KRLCL	varner Hobins, Ga. 5 ewiston, Idaho	5000	KBUC Corona, Calif. KEEN San Jose, Calif.	1000 5000	KTSM El Paso, Tex. KMUL Muleshoe, Tex. KBOP Pleasanton, Tex.	5000 1000d	WDWS Champaign, III. WGIL Galesburg, III. WROZ Evansville, Ind.	1000
WAAP P	ewiston, Idaho Peoria, III. alem III	500 A E	KEEN San Jose, Calif. KGEN Tulare, Calif. WKMK Blountstown, Fla.	1000d 500d	KBOP Pleasanton, Tex. WSYB Rutland, Vt.	1000d 5000		1000 500
WIOU K	okomo, Ind.	5000	WKOS Ocala, Fla.	5000d	WMBG Richmond, Va.	5000	KCOG Centerville, lowa	100
KMAN N	es Moines, Iowa Manhattan, Kans,	5000 500d	WCOA Pensacola, Fla. WAXE Vero Beach, Fla.	5000 1000d	KRKO Everett, Wash. KPEG Spokane, Wash,	5000d	KVOE Emporia, Kans.	250 250
WSMB N	lew Orleans, La.	000d l	WBGR Jesup, Ga. WFDR Manchester, Ga.	5000 1000d	WBEL Beloit, Wis.	5000	WGAI marion, ind. KCOG Centerville, lowa KVFD Fort Dodge, lowa KVOE Emporia, Kans. KAYS Hays, Kans. WCYN Cynthiana, Ky, WIEL Elizabethtown, Ky,	250 250
WDEA E	lisworth, Me. I lowell, Mich.	000d	WKLE Washington, Ga. WPRC Lincoln, III.	1000d	1390—215.7		WIEL Elizabethtown, Ky,	1000 250
KDID Or	rtonville. Minn. I	0000	WTTS Bloomington, Ind.	1000d 5000	CKLN Nelson, B.C. WHMA Anniston, Ala.	1000 5000	WFTG London, Ky. WFPR Hammond, La.	250
WKOZ K	osciusko, Miss. 5	000d	WGRY Gary, Ind. KDTH Dubuque, Iowa	1000d 5000	KDQN OeQueen, Ark.	500d 1000d	KAOK Lake Charles, La. WROO Augusta. Maine	1000 250
KCHR C	harleston, Me. 1	000d	KGNO Dodge City, Kans. KALN Jola, Kans.	5000 500d	KGER Long Beach, Calif. KCEY Turlock, Calif.	5000	WIDE Biddeford, Maine WWIN Baltimore, Md.	1000
WLNH L	'Neill, Nebr. 1 aconia, N.H. 5 Princeton, N.J.	0000	WGOH Grayson, Ky.	5000d	KFML Denver, Colo.	5000 1000d	WWIN Baltimore, Md. WALE Fall River, Mass, WLLH Lowell, Mass,	250 5000 500
		2000	KAPB Marksville, La.	10000	WAVP Avon Park, Fla. WPUP Gainesville, Fia.	1000d 5000d	WHMP Northampton, Mass. WELL Battle Creek, Mich.	1000
WCBA C	orning, N.Y. Iome, N.Y. Isak Mountain, N.C.	000d	WKIK Leonardtown, Md.	500d	WGES Chicago, III. WYNR Chicago, III.		WELL Battle Creek, Mich, WILB Detroit, Mich, WHDF Houghton, Mich,	1000 250
WHIP M	lack Mountain, N.C.	500d	WGHN Grand Haven, Mich.	500d	WFIW Fairfield, III.	1000	WHOF Houghton, Mich.	250 250
WILLY W	Alson N.C.	0000	KSUM Fairmont, Minn. WDOB Canton, Miss.	10000	KCLN Clinton, Iowa	P0001	WSAM Saginaw, Mich.	250 1000
WADC A	kron. Ohio	500d 5000	KCRV Caruthersvilla Ma	1000d	KCRC Des Moines Jown	1000 500d	WMAB Munising, Mich, WSAM Saginaw, Mich, WSJM St. Joseph, Mich, WTCM Traverse City, Mich, KEYL Long Prairie, Minn.	250
WUH! CI	elina, Ohio hiilleothe, Ohio	500d	KXLF Butte, Mont, KAWL York, Nebr, WFEA Manchester, N.H.	5000 500d		0000	NETE Long Prairie, Minn.	250
KRHD D	uncan, Okla.	250	WFEA Manchester, N.H.	5000	KFRA Franklin, La,	5000d	WHITE'S RADIO LOG	165

						14.5 . 1	(c. Wave Length W.P.
F		.P. K		W.P.	wwGS Tifton, Ga.	W.P. 6	(NOT Prescott, Arlz. 250
1	VMIN MplsSt. Paul, Minn. !	000 H	KGRN Grinnell, lowa	500d	WNSH Highland Park, III. WCMY Ottawa, III.	500d H	(OLD Tucson, Ariz. 250 (ENA Mena, Ark. 250
1	VBIP Booneville, MIss.	250 K		5000d	WIRE Indianapolis, Ind. KASI Ames, Iowa	10004 1	YOR Blythe, Calif. 250 OWN Escondido, Calif. 250
١	VFDR Hattiesburg, Miss.	250 H	WLBJ Bowling Green, Ky.	5000 5000d	KMRC Morgan City, La. WNAV Annapolis, Md.	500d H	(PAL Palm Springs, Calif. 250 (TIP Porterville, Calif. 1000
1	VIQS Jackson, Miss.	250 F	KOBS Alexandria, La.	1000d	WHIL Medford, Mass. WION Jonia, Mich.	5000d h	(SAN San Francisco, Callf 1000 (VML Sonora, Calif. 250
	(FRU Columbia, Mo.	250 V	WOKW Brockton, Mass.	10000	WBRB Mt. Clemens, Mich. WLAU Laurel, Miss.	500d	(VEN Ventura, Calif. 1000 (AGR Yuba City, Calif. 100
	(SIM Sikeston, Mo. (TTS Springfield, Mo.	000 F	KLED Litchfield, Minn.	1000d 500d	KAOL Carrollton, Mo. WIL St. Louis, Mo.	500d F	(GIW Alamosa, Colo. 250 (YOU Greeley, Colo. 1000
_ 1	CARR Great Falls, Mont.	000 \	WBKN Newton, Miss.	1000d 500d	KRGI Grand Island, Nebr.	1000 V	VNAB Bridgeport, Conn. 250 VILM Wilmington, Del. 250
	(COW Alliance, Nebr.	250 N	WHTG Eatontown, N.J.	1000d 500d	WNJR Newark, N.J. KGFL Roswell, N.M. WENE Endicott, N.Y.	5000d \	WDL Washington, D.C. 250 WWJB Brooksville, Fla. 250
	(BMI Henderson, Nev. (WNA Winnemucca, Nev.	250 V	WDOE Dunkirk, N.Y. WFLM Elmira, N.Y.	1000	WMNC Morganton, N.C.	5000d \	WMFJ Daytona Beach, Fla. 1000 WSKP Miami, Fla. 250
,	WBRL Berlin, N.H. WTSL Hanover, N.H. i	000	WSET Glen Falls, N.Y. WOTT Watertown, N.Y.	1000d 5000	WDJS Mt. Olive, N.C. WRXO Roxboro, N.C.	10004	WBSR Pensacola, Fla. 1000 WSPB Sarasota, Fla. 1000
- 1	CTRC Santa Fe, N.Mex.	- 1	WSRC Durham, N.C.	b0001	WFOB Fostoria, Ohio WCLT Newark, Ohio	500d	WSTU Stuart, Fla. 250 WTNT Tallahassee, Fla. 1000
	CTNM Tueumeari, N.Mex.	250		5000d	KALV Alva, Okla. KELI Tulsa, Okla.	5000	WGPC Albany, Ga. 250 WBHF Cartersville, Ga. 1000
1	WOND Pleasantville, N.J.	000	WLSH Lansford, Pa. KOV Pittsburgh, Pa.	5000d 5000	WVAM Altoona, Pa.	1000	WCON Cornelia, Ga. 250 WKEU Griffin, Ga. 1000
,	WSLB Oadensburg, N.Y.	000	WPCC Clinton, S.C. WYMB Manning, S.C.	1000d	WFRA Franklin, Pa. WNEL Caguas, P.R.	1000	WMVG Milledgeville, Ga. 1000
_ }	WBMA Beautort, N.C.	250	WCMT Martin, Tenn.	1000d	WBLR Batesburg, S.C. WATP Marion, S.C.	5000d 1000d	WBYG Savannah, Ga. 1000 WYLD Valdosta, Ga. 1000 KENK Pavette, Idaho 250
	WSIC Statesville, N.C.	230	KBUD Athens, Tex. KBAN Bowle, Tex. KVLB Cleveland, Tex.	500d 500	KBRK Brookings, S. Dak. WFCT Fountain City, Tenn.		KEOK Payette, Idaho 250 KEEP Twin Falls, Idaho 250 WHFC Cicero, III. 1000
	WHICE Waynesville, N.C.	250	KXIT Dalhart, Tex. KAOO Marshall, Tex.	500d 500	WENO Madison, Tenn. WHER Memphis, Tenn.	1000	WKEI Kewanee, III. 1000 WCVS Springfield, III. 1000
	WMAN Mansfield, Ohlo	250	KRIG Odessa, Tex. KBAL San Saba, Tex.	1000 500d	KSTB Breckenridge, Tex. KEES Gladewater, Tex.	1000d	WANE Ft. Wayne, Ind. 500 WXVW Jeffersonville, Ind. 250
	KWON Bartlesville, Okla.	250	KNAL Victoria, Tex. WRIS Roanoke, Va.	500d	KCOM Houston, Tex.	5000	WASK Lafayette, Ind. 1000 WAOV Vincennes, Ind. 250
	KTMC McAlester, Okla, KNOR Norman, Okla,	250	WKBH LaCrosse. Wis. KWYO Sheridan. Wyo.	5000 1000	WIVE Ashland, Va. WDIC Clincho, Va. KBRC Mt. Vernon, Wash.	1000d	KUWN Cedar Rapids, Iowa 250 KWBW Hutchinson, Kans. 1000
	WEST Easton, Pa.	000	1420-211.1		WEIR Weirton, W.Va.	1000	WYCO Campbellsville, Ky. 1000 WWXL Manchester, Ky. 1000
	WHER Harrisburg, Pa.	250	CKPT Peterborough, Ont.	0001	WBEV Beaver Dam, Wis.	1000d	WPAD Paducah, Ky. 1000 KSIG Crowley, La. 1000
	WKBI St. Marys, ra.		CJMT Chicoutlmi, Que. WACT Tuscaloosa, Ala. KHFH Sierra Vista, Ariz.	5000d 1000d	1440—208.2 CFCP Courtenay, B.C.	1000	KNOC Natchitoches, La. 1000 WNPS New Orleans; La. 250
	WCOS Columbia, S.C.	1000	KPOC Pocahontas, Ark. KSTN Stockton, Calif.	1000d 5000	WHHY Montgomery, Ala. KWBY Scottsdale, Ariz.	5000d	WRKD Rockland, Maine 250 WKTQ South Parls, Maine 250
	WGTN Georgetown, S.C. W700 Spartanburg, S.C.	050	WILLS Old Savbrook, Conn.	500d 1000	KHOG Fayetteville, Ark.	1000d 5000d	WTBO Cumberland, Md. 1000 WMAS Springfield, Mass. 1000
	WHIIR Cookeville, Tenn.		WBRD Bradenton, Fla. WDBF Delray Beach, Fla. WETH St. Augustine, Fla.	5000d	KYON Napa, Calif. KPRO Riverside, Calif. KCOY Santa Maria, Calif.	1000	WATZ Alpena Township, Michigan 1000
	WGAP Maryville, Tenn.	1000	WRFB Tallahassee, Fla. WAVO Avondale Estates, Ga	5000d	WRIS Bristol, Conn.	1000 500d	WHIC Holland, Mich. 1000
	WHAL Shelbyville, Tenn, KRUN Bailinger, Tex.	250	WRBL Columbus, Ga. WPEH Louisville, Ga.	5000 1000d	WABR Winter Park, Fla.	5000 1000d	WMIQ Iron Mtn., Mich. 250 WIBM Jackson, Mich. 1000 WKLA Ludington, Mich. 250
	KBYG Blg Spring, Tex. KUNO Corpus Christi, Tex.	250 250	WLET Toccoa, Ga.	5000d 500d	WRAJ Anna, III.	5000 500d	WHLS Port Huron, Mich. 250 KATE Albert Lea, Minn, 250
	KILE nr. Galveston, Tex. KGVL Greenville, Tex.	250 250	WIMS Michigan City, Ind.	5000d 5000	WIDK Normal, III.	1000d	
	KIUN Pecos, Tex.	1000	KICK Junction City, Kans.	1000d 5000d	WROK Rockford, III.	5000 5000	WELY Ely, Minn. 1000
	KEYE Perryton, Tex. KVOP Plainview, Tex.		WHEN Harrodsburg, Ny.	1000d 5000		500d 500d	WROX Clarksdale, Miss. 250 WCJU Columbia, Miss. 250
	KDWT Stamford, Tex. KTEM Temple, Tex.	250 250	WOKW Brockton, Mass.	1000d	WCDS Glasgow, Ky.	5000 lkwd	WOKK Meridian, Miss. 1000
	KTFS Texarkana, Tex. KVOU Uvalde, Tex.	250 250	WBSM New Bedford, Mass,	1000	WEZJ Williamsburg, Ky.	1000d	WNAT Natchez, MISS. 230
	KIXX Provo, Utah WDOT Burlington, Vt. WINA Charlottesville, Va.	250 250 1000	WAMM Flint, Mich.	10004	WJAB Westbrook, Me.	5000d	
	WHHV HIIISVIIIe, Va.	250 250	WSIIH Dxford, Miss.	5000 1000d	WAAB Worcester, Mass.	5000 1000	KIRX Kirksville, Mo. 1000 KOKO Warrensburg, Mo. 250
	WHIH Portsmouth, Va. WHLF So. Boston, Va.	1000	WQBC Vicksburg, Miss.	1000 500a	WCHR Inkster, Mich	1000q	
	WINC Winchester, Va. KEDO Longview, Wash.	250 250	WOOD Omaha Nebr	10000	IIKEVE Golden Valley, Min	In. 5000	KUDI Great Falls, Mont, 1000 KXLL Missoula, Mont. 250
	KRSC Othello, Wash. KTNT Tacoma, Wash. WROY Clarkesburg, W.Va.	1000	WALY Herkimer, N.Y.	300	WSEL PONTOTOC, MISS.	1000d	KYCK Wolf Point, Mont. 1000
	WRON Ronceverte, W.Va.	0001	WLNA Peckskill, N.Y.	10000	0 WJJL Niagara Falls, N.Y.	1000d	KCSR Chadron, Nebr. 250
	WSPZ Spencer, W.Va. WKWK Wheeling, W.Va.	250 1000	WGAS S. Gastonia, N.C.	100	WBLA Elizabethtown, N.	1000d C. 1000d	WKXL Concord, N.H. 1000
	WBTH Willamson, W.Va. WATW Ashland, Wis.	1000	WHK Cleveland, Ohio	1000	KILO Grand Forks, N.D.	5000d	WEPG Atlantic City, N.J. 1000
	WBIZ Eau Claire, Wis. WDUZ Green Bay. Wis. WRJN Racine, Wis.	1000	KYNG Coos Bay, Dreg. WCOJ Coatesville, Pa.	1000 500	WHHH Warren, Ohlo KMED Medford, Oreg.	5000 5000	WCTC New Brunswick, N.J. 250 KLOS Albuquerque, N.Mex. 250 KLMX Clayton, N.Mex. 250
	WRDB Reedsburg, Wis. WRIG Wausau, Wis. KATI Caspar, Wyo.	1000	WCED DuBols, Pa.	100	0 WCDL Carbondale, Pa.	5000d	KLMX Clayton, N.Mex. 250 KOBE Las Cruces, N.Mex. 250 KENM Portales, N.Mex. 1000
	KATI Caspar, Wyo.	1000	0 WCRE Cheraw, S.C. 0 KABR Aberdeen, S.D.	1000	d WGCB Red Lion, Pa.	500d	WCLI Corning, N.Y. 1000
	1410-212.6		D WHK Cleveland, Ohio KTJS Hobart, Okla. KYNG Coos Bay, Dreg. WCOJ Coatesville, Pa. WCCED DUBois, Pa. WCCED DUBois, Pa. WCCED Conce, P.R. WCCE Cheraw, S.C. KABR Aberdoen, S.D. WEMB Erwin, Tenn. WKSR Pulaski, Tenn. KFYN Bonham, Tox. KTRE Lufkin, Tox.	5000 100	O WHHL Holly Hill, S.C.	5000 lkwd 1000d	WHOL Olean, N.Y. 1000
	CFUN Vancouver, B.C.	10000	KFYN Bonham, Tex.	100		500	WKIP Poughkeepsie, N.Y. 250 WKAL Rome, N.Y. 250 WATA Boone, N.C. 250
	CHLP Montreal, Que. WALA Mobile, Ala.	5000	IV KGNB New Braunfels, Ter.	x. 1000	d KEYS Corpus Christi, Te	x. 1000 5000	WGNC Gastonia, N.C. 1000
	WRCK Tuscumbla, Ala. KTCS Fort Smith, Ark.	100	WWSR St. Albans, Vt.	1000	d KETX Livingston, Tex.	5000 5000	WHILE Hendersonville, N.C. 1000
	KTCS Fort Smith, Ark. KERN Bakersfield, Calif. KRML Carmel, Calif.	100 500	KITI Chenaiis, wash.	5000 1000			DIKECA Rughy, N. Dak. 250
	KMYC Marysville, Calif.	500	WPLY Plymouth, Wis.	500 500	WHIS Bluefield, W.Va. 00 WAJR Morgantown, W.V 0d WJPG Green Bay, Wis.	a. 500 500	W MOH Hamilton, Ohio 250
		1000	1430—209.7		1450-206.8		KWHW Altus, Ukla.
	KCOL Ft. Collins, Colo. WPOP Hartford, Conn. WDOV Dover, Del.	5000	WEHK Pell City, Ala.	100	Od CBG_Gander, Nfld.	10 25	0 KSIW Woodward, Okla. 1000 0 KORE Eugene, Oreg. 1000
	WMYR Fort Myers, Fla. WBIL Leesburg, Fla.	1000	KHBM Monticello, Ark,	100	ad CF R Brockville, Unt.	100	0 KFLW Klamath Falls, Oreg. 250
	WRIX Griffin, Ga.	5000 1000	AL KARM Fresho, Call.	50	00 CHEF Granby, P.Q. 00 WDNG Anniston, Ala.	100	10 KBPS Portland, Ureg. 430
	WSNE Cummings, Ga. WDAX McRae, Ga. WLAQ Rome, Ga.	1000	od KOSI Aurora. Colo.	. 50 50		100	00 WDAD Indiana, Pa. 250
	WLAU Rome, Ga. WRMN Elgin, III. WTIM Taylorville, III.	1000		50 50	00 WDIG Dothan, Ala. 00 WFIX Huntsville, Ala. 00 WLAY Muscle Shoals C	Ity, bama 10	WMPT So. Williamsport, Fa. 200
			WGFS Covington, Ga.	100	000 KLAM Cordova, Alaska 00d KAWT Douglas, Ariz.	pama ivi	WMAJ State College, Pa. 250 WJPA Washington, Pa. 250 WWRI W. Warwick, R.I. 1000
	166 WHITE'S RADIO	LO	OG WRCD Dalton, Ga.	100	ou I KAW I Douglas, Ariz.	2.	A Call of the Comment of the Call of the C

Kc. Wave Length	W.P.		W.P.			W.P.	
WQSN Charleston, S.C. WCRS Greenwood, S.C.	1000	WRBB Tarpon Sprgs., Fla. WAAG Adel, Ga.	5000d	WBLU	Salem, Va, Lakewood, Wash,	5000d 1000d	WMRN Marion, Ohio 1000
WMYB Myrtle Beach, S.C. WHSC Hartsville, S.C.	1000	WDOL Athens, Ga.	1000d	KVAN	Vancouver, Wash,	1000d	KBIX Muskoges, Okla. 250
KBFS Beile Fourche, S. Dak	1000	WEGA Bome Co	1000 5000	VDAE	Madison, Wis. Cheyenne, Wyo,	5000 1000d	
KYNT Yankton, S.Dak. WLAR Athens, Tenn.	250 250	WMPP Chicago Heights, III	. 1000d	1 400	—201.2		
W MOC Chattanooga, Tenn. W DSG Dyersburg, Tenn.	250	WHUT Anderson Ind	5000 1000d	CFMR	Fort Simpson NWT.	250	WESB Bradford, Pa. 1000 WAZL Hazleton, Pa. 1000
WSMG Greeneville, Tenn.	250 250	KTRI Sloux City, Iowa KWVY Waverly, Iowa	5000 1000d	CFRC	Kingston, Ont. Kitchener, Ont.	100	WARD Johnstown, Pa. 250
WLAF LaFollette, Tenn	100	KARL Atchison, Kans.	1000	CKBM	Montmagny, Que,	1000	WBCB Levittown, Pa. 1000
WGNS Murfreesboro, Tenn. KAYC Beaumont, Tex.	1000	KLIB Liberal, Kans. WSAC Fort Knox, Ky.	500d 1000d	WANA	Anniston, Ala. Decatur, Ala.	250	WMPE Lawiston Do 1000
KBEN Carrizo Spros., Tex.	250	KPLC Lake Charles, La.	5000	WRLD	Lanett, Ala	1000 250	WMGW Meadville, Pa. 250 WNBT Wellshore, Pa. 1000 WSIB Beaufort, S.C. 100
KCTI Gonzales, Tex, KMBL Junction, Tex,	250 250	WJDY Salisbury, Md.	5000d	WHRE	Selma, Ala,	250 1000	WSIB Beaufort, S.C. 100 WGCD Chester, S.C. 250
KCVI Lampasas Tav	250 1000	WITR Westminster, Md.	1000d	KAIR	Tueson, Ariz. Hope, Ark. Mtn. Home, Ark.	250	WMRB Greenville, S.C. 1000
KMHT Marshall, Tex. KAMY McCamey, Tex.	250	WSRO Mariborough, Mass. WNBP Newburyport, Mass.	1000d 500d	KTLO	Mtn. Home. Ark	250 250	WOPI Bristol, Tenn. 1000
KNET Palestine, Tex. KSNY Snyder, Tex.	250 1000	WNBP Newburyport, Mass. WKMF Flint, Mich. WKLZ Kalamazoo, Mich.	5000			250	WDXB Chattanooga, Tenn. 1000
KURA Moab. Utah KEYY Provo, Utah	1000	KANU AROKA, MIRA	500d	KXRJ	Pine Bluff, Ark. Russellville, Ark.	250 1000	WROL Fountain City, Tenn. 250 WJJM Lewisburg, Tenn. 1000
KDXU St. George, Utah	250 250	WCHI Brookhavan Miss	1000d	IKWAC	Rakersfield Callf	1000	WOX! Levincton Tenn 1000
WSNO Barre, Vt, WTSA Brattlebore, Vt.	1000	KGHM Brookfield, Mo.	500d	KBLA	Banning, Calif. Burbank, Calif.	250 250	KNOW Austin, Tex. 250 KIBL Beeville, Tex. 250 KBST Big Spring, Tex. 250
WFTR Front Royal, Vm.	1000 250	KTCB Malden, Mo. WTKO Ithaca, N.Y.	10004	KICO	Calexico, Calif. Lake Tahoe, Calif.	250 250	KBST Big Spring, Tex. 250 KHUZ Borger, Tex. 250
WENZ Highland Springs, Va WREL Lexington, Va.	a, 250 250	WPDM Potsdam, N.Y.	10000	KTOB	Petaluma, Calif, Red Bluff, Calif.	1000	KNEL Brady, Tex. 250
WMVA Martinsville, Va.	1000	WBIG Greensbore, N.C. WPNC Plymouth, N.C.	5000 1000d	KBLF	Red Bluff, Calif. Santa Barbara, Calif.	1000	KSAM Huntsville, Tex. 250 KVOZ Laredo, Tex. 250
KBKW Aberdeen, Wash, KCLX Colfax, Wash,	1000	WIDE Spruce Pine, N.C.	1000d	LKSYC	Yraka, Calif.	1000	
KONP Port Angeles, Wash.	250	WOHO Toledo, Ohie KVLH Pauls Valley, Okia,	1000 250d	KGUC	Boulder, Colo. Gunnison, Colo.	1000 250	MCLT Paris, Tex. 250 MGKB Tyler, Tex. 250 KGKB Tyler, Tex. 250 KVWC Vernon, Tex. 250 KVWC Qden, Utah 1000 WKVT Brattlebore, Vt. 250
KAYE Puyallup, Wash. WPAR Parkersburg, W.Va.	1000 250	KVIN Vinita, Okla.	500d	KCMS	Manitou Sprgs., Colo.	100	KVWC Vernon, Tex. 250
WPAR Parkersburg, W.Va. KFIZ Fond du Lac, Wis.	250	KVIN Vinita, Okla. KRAF Reedsport, Oreg. WSAN Alientown, Pa.	5000d 5000	WTOR	Sterling, Colo. Torrington, Conn. Bradenton, Fla.	250 250	KVOG Ogden, Utah 1000 WKVT Brattlebore, Vt. 250
WDLB Marshfleid, Wis, WPFP Park Falls, Wis,	1000	WEAR Farrell, Pa.	10004	WIRL	Bradenton, Fla.	250	
WRCO Richland Center, Wis.		WWML Portage, Pa. WQXL Columbia, S.C.	500d 5000d	WMBN	DeLand, Fla. Mlami Beach, Fla.	250	WVEC Hampton Va 250
KBBS Buffalo, Wyo, KVOW Riverton, Wyo,	250 250		10000	WSKA	Milton, Fla. Starke, Fia.	250 250	WAYB Waynesboro, Va. 250
1460-205.4			5000 5000	WITE	Vero Beach, Fla.	250	KLUG Kelso, Wash. 250
CJOY Guelph, Ont,	10000	KRBC Abilene, Tex, KWRD Henderson, Tex,	500d	IWMOG	Winter Haven, Fla. Brunswick, Ga.	250 250	KENE Toppenish, Wash. 250 KTEL Walla Walla, Wash. 250
CKRB VIIIe St. Georges, Quebec	10000	KCNY San Marcos, Tex. KELA Centralla, Wash.	250d 5000	WMJM	Cordele, Ga.	1000	WTGR Charleston, W.Va. 250
CJNB N. Battleford, Sask,	10000	KSEM Moses Lake, Wash, KAPS Mount Vernon, Wash	5000	WSFB	Monroe, Ga. Quitman, Ga.	250 250	WLOH Princeton, W.Va 250
WFMH Cullman, Ala. WPNX Phenix City, Ala.	5000d 5000		5000d	WSNT	Quitman, Ga, Sandersville, Ga,	500	WGEZ Reinit. Wis 250
KZOT Marianna, Ark.	500	WJBT Wheeling, W.Va. WBKV West Bend, Wis.	500d	KTOH	Sylvania, Ga, Lihue, Hawali	250 250	WLCX LaCrosse, Wis, 1000 WIGM Medford, Wis, 1000
KCCL Paris, Ark.	500d 5000d	KTWO Casper, Wyo.	5000	KCID	Caldwell, Idaho Cairo, III.	1000 250	WOSH Oshkosh, Wis. 1000
KDON Salinas, Callf.	5000	1480-202.6		WDAN	Danville, III.	1000	WOSH Oshkosh, Wis. 1000 KIML Gillette, Wyo. 258 KLME Laramie, Wyo. 100
KVRE Santa Rosa, Calif. KYSN Colo. Sprgs., Colo.	10004	WARI Abbeville, Ala.	1000	WBBR	East St. Louis, III.	500 1000	KRTR Thermopolis, Wyo. 250 KGOS Torrington, Wyo. 1000
WBAR Bartow, Fla.	1000d	WBTS Bridgeport, Ala. WIXI Irondale, Ala.	1000d 5000d	WZOE	Oak Park, III. Princeton, Ind.	1000	1500—199.9
WZEP DeFuniak Springs, Fiorida	10004	WARR Mobile Ale	5000	WKBV	Richmond, Ind. South Bend, Ind.	1000 250	CHUC Port Hope, Dat, 1000
WMBR Jacksonville Fie	5000	KHAT Phoenix, Ariz, KGLU Safford, Ariz, KTHS Berryville, Ark	1000	KBUR	Burlington, lowa	1000	KXRX San Jose, Callf. 5000
WROY Carmi, III.	1000d	KTHS Berryville, Ark	1000	KRIB	Dubuque, iowa Mason City, Iowa	1000 250	WTOP Washington, D.C. 50000 WKIZ Key West, Fla. 250
WIXN Dixon, III.	1000d	KWUN Concord, Calif. KRED Eureka, Calif.	500d 5000	I W W A AL	Ohilliachung Mana	250	WJDN Detroit, Mien. 10000
WRTL Rantoul, III, WKAM Goshen, Ind.	250d 1000d	KRED Eureka, Calif, KYOS Merced, Calif, KWIZ Santa Ana, Calif.	5000 5000	WEKY	Topeka, Kans, Frankfort, Ky. Glasgow, Ky.	250 250	KSTP St. Paul, Minn, 50000 KPIR Eugene, Dre, 10000d
		KSEE Santa Maria, Calif. KTUX Pueblo, Colo.	1000	WKAY	Glasgow, Ky, Owensboro, Ky,	1000	WMNT Manati, P.R. 250
KCRB Chanute, Kans.		WSOR Windsor, Conn.	1000d 500d	WSIP	Paintsville, Kv.	1000	KTXO Sherman, Tex. 250 KANI Wharton, Tex. 500
WRVK Mt. Vernon, Ky,	500d 5000	WAPG Arcadia, Fla.	1000d		Bogalusa, La. Eunice, La.	250	1510-199.1
WAIL Baton Rouge, La. KBSF Springhill, La.	1000d	WTHR Panama Beach, Fla. WXIV Windemere, Fla.	500d 1000d	KCIL	Houma, La.	1000	CKOT Tillsonburg, Ont. 1000d
WEMD Easton, Md. WBET Brockton, Mass,	500d 5000	WYZE Atlanta, Ga.	5000d	WPOR	Ruston, La. Portland, Maine	1000	KALF Mesa, Ariz. 10000d KASK Ontario, Calif. 1000
WBRN Big Rapids, Mich.		WRDW Augusta, Ga, WGSB Geneva, III.	5000 1000	WTVL	Waterville, Maine Hagerstown, Md,	1000	KIRV Fresno, Callf. 500
WPON Pontiae, Mich. KDMA Montevideo, Minn.	1000	WGSB Geneva, III. WJBM Jerseyville, III. WTHI Terre Haute, Ind.	500d	WHAV	Haverhill, Mass.	250	KTIM San Rafael, Callf, 1000d KMOR Littleton, Colo. 1000
WELZ Belzoni, Miss.	1000d	WOCW Warraw Ind	1000	WTYL	Milford, Mass, W. Springfield, Mass,	250	WNLC New London, Conn. 5000
KADY St. Charles, Mo. KRNY Kearney, Nebr.	5000d	KLEE Ottumwa, Iowa KBEA Mission, Kans,	500d 1000d	WABJ	Adrian, Mich,	1000	WJRC Jollet, III. 500d WKAI Macomb, III. 250d
KENO Las Vegas, Nev.	1000	KLEO Wichita, Kans.	5000	WMDN	Adrian, Mich, Fremont, Mich, Midland, Mich,	250 1000	KEIG lowa Falls, lowa 500d
WOKO Albany, N.Y. WVOX New Rochelle, N.Y.	5000 500d	WKOA Hopkinsville, Ky. WNKY Neon, Ky.	1000d	WCBU	Whitehail, Mich.	1000	WMEX Boston, Mass. 5000 WAST Jackson, Mich. 500d WLKM Three Rivers, Mich. 500
WHEC Rochester, N.Y.	5000 1000d	WTLO Somerset, Ky.	1000d	KOZY	Alexandria, Minn, Grand Rapids, Minn, Redwd, Falls, Minn,	250 250	
WRKB Kannapolis, N.C.	500d	KANV Jonesville, Lz.	500d	KLGR	Redwd, Falls, Minn, Biloxi, Miss,	1000	WRAN Dover, N.J. 1000
WMMH Marshall, N.C. WBNS Columbus, Ohio	500d 5000	KJOE Shreveport, La. WSAR Fall River, Mass,	1000d	WCLD	Cleveland, Miss	250	WERW Brawster NV 10004
WBNS Columbus, Ohio WPVL Painesville, Ohio KELR EL Rano Okla	500d	WMAX Grand Rapids,	5000	WHUC	Philadelphia, Miss. Tupelo, Miss.	250 250	KCTX Childress, Tex. 250d
KELR El Reno, Okla. KROW Dallas, Oreg.	500 1000	WiOS Tawas City, Mich.	1000d	WVIM	Vicksburg, Miss. Carthage, Mo.	250	KGA Spokane, Wash, 50000
WMBA Ambridge, Pa. WCMB Harrisburg, Pa.			500wd	KTTR	Rolla, Mo.	1000	KGA Spokane, Wash. 50000 WAUX Waukesha, WIs. 10000d
WBCU Union, S.C. WGOG Walhalla, S.C.	1000	KAUS Austin, Minn. KGCX Sidney, Mont, KLMS Lincoln, Nebr. KWEW Hobbs, N. Mex.	1000 5000	KDRD	Rolfa, Mo. Sedalia, Mo. Butte, Mont.	250	1520-197.4
WIAK Jackson Tenn	500d 5000d	KLMS Lincoln, Nebr.	1000	KBUM	Umana, Nebr.	1000	KGHT Hollister, Calif. 500 KACY Port Hueneme, Calif. 10000
WEEN Lafayette, Tenn.	10000	WLEA Hornell, N.Y.	5000 1000d	WEMJ	Atlantic City, N.J.	250	WGNP Indian Rocks Beach,
KLLL Lubbock, Tex.	500d 1000d	WLEA Hornell, N.Y. WHOM New York, N.Y. WREM Remsen, N.Y.	5000 5000d	KRSN	Los Alamos, N Mex		F13 10004
WACO Waco, Tex, WPRW Manassas, Va.	1000	WWOK Charlotte, N.C.	5000	WCSS	Raton, N.Mex. Amsterdam, N.Y.	250 1000	WHOW Clinton, III, 5000d
WRAD Radford, Va.	500d 5000	WWOK Charlotte, N.C. WYRN Louisburg, N.C. WMSJ Sylva, N.C.	500d 5000d	WBIA	Batavia, N.Y. Kingston, N.Y.	250	WIXX Oakland Park, Fla. 1000d WHOW Clinton, III. 5000d WLUV Loves Park, III. 500d WSVL Shelbyville, Ind. 250
WRAD Radford, Va. WLPM Suffolk, Va. KCDI Kirkland, Wash.	1000	WHBC Canton, Ohio WCIN Cincinnati, Ohio	5000	WILLY	Mainne, N.Y.	1000	
	5000d 5000	WIRA Latrobe, Pa.	5000 500d	WOLE	Port Jervis, N.Y.	250 250	WRSL Stanford, Ky, 500d KXKW Lafayette, La, 500
	5000d	WTRA Latrobe, Pa. WDAS Philadelphia, Pa.	5000	WSSB	Port Jervis, N.Y. Syracuse, N.Y. Durham, N.C. Fayetteville, N.C.	250	WKBW Buffalo, N.Y. 50000
WTMB Tomah, Wis,	10004	WISL Shamokin, Pa. WSHP Shippensburg, Pa. WMDD Fajardo, P.R.	1000 500d	WILB	Leaksville, N.C.	250 250	WFYI Mineola, N.Y. 50000d KOMA Okla, City, Okla, 50000
1470—204.0		WMDD Fajardo, P.R.	5000	WRNB	Leaksville, N.C. New Bern, N.C. Rocky Mount, N.C. Sallsbury, N.C. Valdese, N.C.	1000	KGON Dregon City, Ores, 10000
	1000	KSDR Waterton, S.D. WJFC Jefferson City, Tenn.	1000d 500	WSTP	Salisbury, N.C.	250 250	WWWW Rio Piedras, P.R. 250
	10000	WJFC Jefferson City, Tenn, WLOK Memphis, Tenn, KBOX Dallas, Tex.	5000d	WSVM	Valdese, N.C.	250	1530-196.1
KZNG Hot Springs, Ark.	1000d	KLVL Pasadena, Tex.	1000	WHSL	Wilmington, N.C.	250 250	WRPM Poplarville, Miss. 1000d
KZNG Hot Springs, Ark, KBMX Coalinga, Calif, KUTY Palmdale, Calif.	500d	KDNI Spanish Fork. Utah	500d 1000d	KOVC	Valley City, N.Dak. Chillicothe, Ohio	1000	WTHM Lapser, Mich. 5000d
KZNG Hot Springs, Ark, KBMX Coalinga, Calif, KUTY Palmdale, Calif, KXOA Sacramento, Calif, WMMW Merlden, Conn, WPOM Pompano Beach, Fla.	5000	WCFR Springfield, Vt.	1000d	MIMD	Cleveland Hights. Ohlo	250	KMAM Butler, Mo. 250
WPOM Pompano Beach, Fla.	5000	WLEE Richmond, Va.	5000	WOHI	E. Liverpool, Ohio Marietta, Ohio	250	WHITE'S RADIO LOG 167

Kc. Wave Length	W.P.	Kc.	Wave Length	W.P.		Wave Length	W.P.		Wave Length	W.P.
WENG Englewood, Fla.	1000 50000	KGUL	Port Lavaca, Tex. Hogulam, Wash,	500d 1000d		Pittsfield, III. Urbana, III.	250d 250d	KTIL '	Tillamook. Oreg. Carnegie, Pa.	1000d
WCKY Cincinnati, Ohio KPBR El Paso, Tex.	10000			10000		Connersville, Ind.	250d	WCBG	Chambersburg, Pa.	5000d
KGBT Harlingen, Tex.	50000	1570	191.1		WJVA	South Bend, Ind.	100004	WEEZ	Chester, Pa.	1000
KCLR Rails, Tex. WQVA Quantico, Va.	1000d 250	CHUB	Nanaimo, B.C.	00001 b00001	KCHA	/ Washington, Ind. Charles City, Iowa	250d 500d	WYNG	Guayama, P.R. Warwick, R.I.	1000d
1540195.0			Montreal, Canada Drillia, Ont.	10000	KWNT	Charles City, Iowa Davenport, Iowa	500d		Abbeville, S.C. Camden, S.C.	1000d
ZNS Nassau, B.W.1.	10000	WCRL	Oneonta, Ala,	1000 5000d		Denison, Iowa Georgetown, Ky.	500d 10000d	KCCR	Pierre, S. Dak.	1000d
CHFI Toronto, Ont. KPOL Los Angeles, Calif.		KBRI	Selma, Ala. Brinkley, Ark.	250d	WMTL	Leitchfield, Ky.	250d	WISO	Jonesboro, Tenn. Springfield, Tenn.	5000d 1000d
KPOL Los Angeles, Calif. WSMI Litchfield, III.	50000 1000d	KBJT	Brinkley, Ark. Fordyce, Ark.	250d		Princeton, Ky. Haynesville, La.	250d 250d	KGAS	Carthage, Tex.	10004
WBNL Boonville, Ind.	250d	KKKU	King City, Calif. Lodi, Calif.	250d 1000d	KLOU	Lake Charles, La.	1000	KERC	Carthage, Tex. Eastland, Tex. El Paso, Tex.	500d 1000d
WLOI LaPorte, Ind. KXEL Waterloo, lowa	250d 50000	KACE	Riverside, Calif.	1000d	WPGC	Bradbury Hgts., Md	1, 10000 250d	KYUK	Houston, Tex.	5000
KNEX McPherson, Kans.	250d	WTWE	Loveland, Colo. 3 Auburndale, Fla.	250d 5000d	aniw	St. Johns, Mich.	1000d	KCBD	Lubbock, Tex.	1000 500d
KLKC Parsons, Kans. WDON Wheaton, Md.	250d 1000	WPAP	Fernandina Beach,		KDOM	St. Johns, Mich. Windom, Minn. Amory, Miss.	250d 5000d	KTOD	Mexia, Tex. Sinton, Tex.	1000
WPTR Albany, N.Y. WIFM Elkin, N.C.	50000	WOKC	Okeechobee, Fla.	1000d	WGLC	Centreville, Miss.	250d	WRLA	Luray, Va. I Richmond, Va.	500d 5000d
WIFM Elkin, N.C. WABQ Cleveland, Ohio	250d 1000d	WIDE	Ward Ridge, Fla.	250	WESY	Leland, Miss. Pascagoula-Moss	1000	KLFF	Mead, Wash. Scattle, Wash.	1000d
WJMJ Philadelphia, Pa.	50000d	WMES	Ashburn, Ga. Clayton, Ga.	1000d		Point, Mississippi	1000d	KETO	Seattle, Wash. New Richmond, Wis	5000d
WPTS Pittston, Pa. WPME Punxsutawney, Pa.	1000q	WEAD	Clayton, Ga. College Park, Ga.	1000d 250d	KCGM	Columbia, Mo. Eldorado Springs, N	250d	WSWV	v Platteville, Wis.	5000
WARK Newsort R I	1000d	WOKZ	Millen, Ga. Alton, III.	1000d	KNIM	Maryville. Mo.	250d	WTRW	Two Rivers, Wis.	1000d
KCUL Ft. Worth, Tex. KGBC Galveston, Tex. KBVU Bellevue, Wash.	50000d	WFRL	Freeport, III. Harvey, III.	5000d 1000d	HINM	Hammonton, N.J. Washington, N.J.	250d 500d	KCHY	Cheyenne, Wyo.	1000d
KBVU Bellevue, Wash.	1000	WTAY	Robinson, III.	250d	KRZY	Albuquerque, N.Mex		1/00	107.5	
WTKM Hartford, WIS.	500d	WILD	Frankfort, Ind.	250d	I WPAC	Patchogue, N.Y.	10000d 250d		—187.5	10000
1550—193.5		WOW	Kendallville, Ind. New Albany, Ind.	250d 1000d	WPYB	Albemarie, N.C. Benson, N.C.	500d	WELLP	Niagara Falls, Ont. Huntsville, Ala.	1000 0 5000d
CBE Windsor, Ont. WBHM Birmingham, Ala.	10000 50000d	KMCD	Fairfield, Iowa	250d 250d	WVKO	Columbus, Ohlo Blackwell, Okla	1000d	WAPX	Huntsville, Ala. Montgomery, Ala. Cottonwood, Ariz.	1000
WAAY Huntsville, Ala. WMOE Mobile, Ala.	5000	KNDY	Webster City, Iowa Marysville, Kans,	250d	WCOY	Blackwell, Okla. Columbia, Pa.	500d	KXEW	Tueson, Ariz.	1000d
WMOE Mobile, Ala. KFIF Tucson, Arlz.	50000d 50000d	KWSK	Pratt, Kans.	250d	IWEND	Ebensburg, Pa. Waynesburg, Pa.	1000d 250d	L C ST	Erespo Colif	1000d
KXEX Fresno, Calif.	500d	WARL	S Vanceburg, Ky. Amite, La.	250d 500d	WORG	Orangeburg, S.C.	1000d	KHER	y Pomona, Calif. Santa Maria, Calif. Yuba City, Calif.	1000 500d
KKHI San Fran., Calif. KDAB Arvada, Colo.	100000	KLLA	Leesville, La.	1000	WYCL	York, S.C. Colonial Village, Te	250d	KUBA	Yuba City, Calif. Lakewood, Colo.	5000 5000
WRIZ Coral Gables, Fla.	100004	WAGE	t Winnsboro, La. Towson, Md. Taunton, Mass.	1000 5000d	WLII	Shelbyville, Tenn.	1000d	WKEN	Dover, Del.	500d
WORL NAW SHIVING DED., P	10000d	WPEP	Taunton, Mass.	1000d 500d	WSKT	South Knoxville, To	enm, 250 250d	WKT)	Dover, Del. (Atlantic Beach, Fla F Key West, Fla.	. 1000d
WYOU Tampa, Fla. WSMA Smyrna, Ga.	10000d	WDEV) Beverly, Mass. V Westfield, Mass.	10000	KGAF	Denver City, Tex. Gainesville, Tex. Mission, Tex.	250d	IWHE	W Riviera Beach, Fla	i. 1000
WJIL Jacksonville, III. WCTW New Castle, Ind.	250	WMRI	P Flint, Mich.	1000d	KIRT	Mission, Tex. Rusk, Tex.	1000d 500d	WOKE	Winter Garden, Fla A Atlanta, Ga.	. 1000d
KEDD Dodge City, Kans.	1000d	WFUF	R Grand Rapids, Michigan	n 1000d	KWED	Seguin, Tex.	1000d	1 WNG/	h Nashviila, fil.	LUUUU
WIRV Irvine, Ky. WMSK Morganfield, Ky.	1000d 250d	KUXL	Golden Valley, Min	n, 500d	KBRP	Shamrock, Tex. Waco, Tex.	250d 1000	WCGC	Chicago Hgts., III. W Harvard, III.	1000d 500d
WYNE Baton Rouge, La. KOKA Shreveport, La.	5000d	KLEX	Winona, Miss. Lexington, Mo.	250d	WILA	Danville, Va. Pulaski, Va.	1000d 5000d	WBTO	Linton, Ind. J. Peru, Ind.	500d
WSER Elkton, Md.	250d	WAFS	Amsterdam, N.Y. Dundee, N.Y.	0001 b0001	WITN	Watertown, Wis.	1000d	WARL	J Peru, Ind.	1000d 5000d
WSHN Frement, Mich. WSAO Sanitobia, Miss.	1000d 5kwd	WBU2	Z Fredonia, N.Y.	250d				KCRG	Algona, lowa Codar Rapids, low	5000
KRIR Bolivar, Mo.	250	WAPO	Riverhead, N.Y. Taylorsville, N.C.	1000d 500		—188.7	5000d	WSTL) Ft. Scott, Kans. Eminence, Ky.	500d 500d
KGMO Cape Girardeau, Mo KKJO St. Joseph, Mo.	5000	WNCA	L Siler City, N.C.	1000d	WVNZ	Atmore, Ala. Tuscumbia, Ala.	5000d	KENV	/ Ferriday, La. Vivian, La.	1000d 500d
WCGR Canadalqua, N.Y.	250 500d	WCLV	V Mansfield, Ohlo V Piqua, Ohio	1000 250d	IKPBA	Pine Bluff, Ark.	1000d 5000	IWINX	Rockville, Md.	1000
WBAZ Kingston, N.Y. WBVM Utica, N.Y.	1000	KTAT	Frederick, Okla.	250d	KUDU	San Jose, Calif. Ventura, Calif.	1000	I WROS	Brookline, Mass. M East Longmeadew,	5000
WHTB Greenville, N.C. WTYN Tryon, N.C.	500d	KUUS	Pryor, Okla. Forest Grove, Oreg.	b0001 b0001	WERY	Victorville, Calif.	500d 5000	1	Mass.	
WPEG Winston-Salem, N.L	. 1000d	KOHU	l Hermiston, Oreg.	1000d	WOW	Waterbury, Conn. Y Clewiston, Fla.	500d	WHR	V Ann Arbor, Mich. J Muskegon, Mich.	t 000 5000
KUTT Fargo, N.D. WDLR Delaware, Ohio	5000d 500d	WAK	(Doylestown, Pa. U Latrobe, Pa.	1000d		St. Petersburg Beat Florida	a 1000d	WKD	L Clarksdale, Miss.	10004
KMAD Madill, Okla.	250	WFG	l Gaffney, S.C.	250d	WELE	S. Davtona Beh.,	a, 1000d	IWEER	F Columbia, Miss. St. Louis, Mo.	500d 5000
KREK Sapulpa, Okla, WLOA Braddock, Pa.	500d 1000d	WISC	Johnston, S.C. Loris, S.C.	250 1000d		Albany, Ga.	1000	KTTN	Trenton, Mo. Nebraska City, Neb	5004
WLOA Braddeck, Pa. WTTC Towanda, Pa.	500d	WHLE	Centerville, Tenn.	1000d	WIFA	Lafavette, Ga.	5000d 500d	KNCY	' Nebraska City, Neb Superior, Nebr.	r. 500d 500d
WKFE Yauco, P.R. WBSC Bennetsville, S.C.	250 10000	WCLE	Cleveland, Tenn. Ripley, Tenn.	1000d	WNM	Thomaston, Ga. P Evanston, III. Galesburg, III.	1000d	1 14/88/01	D Chalde N V	1000d
WTHB N. Augusta, S.C. KVPH Canyon, Tex.	10004	KZOL	Ripley, Tenn, Farwell, Tex.	250d 250d	WAIK	Galesburg, III. Indianapolis, Ind.	5000d 5000d	WXK	w Troy, N.Y.	500 500d
KWBC Navasota, Tex.	250d	KTER	La Grange, Tex.	250d	WPCC	Mt. Vernen, Ind.	500d	WWR	Sag Harbor, N.Y. Troy, N.Y. L Woodside, N.Y. Charlotte, N.C.	50000 1000
WYRL Bristol, Tenn. WTPI Cookville, Tenn.	1000d 250d	KWIC	Salt Lake City, Ut V Pennington Gap, V	h 5000	KWB	G Boone, lowa G Great Bend, Kans.	1000 5000	IMIDO) Payelleville, M.C.	10004
WKPT Kingsport, Tenn.	P00001	WYTI	Rocky Mount, Va.	1000d		J Labanan Kv	1000d	WFR	C Reidsville, N.C. K W. Jefferson, N.C.	0001 00001
WKBA Vinton, Va. WBOF Virginia Beach, Va	1000d 1. 5000d	WEE	R Warrenton, W.Va. L Appleton, Wis.	500d 1000d	KEVL	White Castle, La. Ocean City, Md. Coldwater, Mich.	10000 0001	KDA	K Carrington, N.Dak.	500d
WXVA Charlestown, W.Va KOQT Bellingham, Wash.	. 500d		-	10000	WTVE	Coldwater, Mich.	5000	WAQ	Ashtabula, Ohio Y Springfield, Ohio	1000d
	10004		—189.2		WMIC	3 Marine City, Mich 5 St. Helen, Mich.	. 1000d 500d	IWTTE	Time Ohio	500d
1560192.3	250d		Chicoutimi, Que. Y Talladega, Ala,	10000 1000d	IKRAL	E. Grand Forks.	n. 1000d	KUSH	Cushing, Okla. Leugene, Oreg. St. Helens, Oreg.	1000d 5000
CFRS Simcoo, Ont. KPMC Bakersfield, Calif.	10000	IKVNI	Tempe, Ariz.	10000d	WOK	Lackson, Miss.	5000d	KSTH	St. Helens, Oreg.	1000d
KIQS Willows, Calif. WBYS Canton, III. KSWI Council Bluffs, lowe	250d	KPCA	Marked Tree, Ark.	250d 1000d	KDE)	Dexter, Mo. Kansas City, Mo.	1000d		L. Allentown, Pa. V. Elizabethtown, Pa.	500d 500d
KSW1 Council Bluffs, lower	250d 1 1000d			1000d	IKCLU	Rolla, Mo.	1000d	WFIS	Fountain Inn. S.C.	1000d
WIDER Padueah, Kv.	1000	KDAY	Merced, Calif. Santa Monica, Cal.	500d 50000d	WSMI	N Nashua, N.H. A Plainfield, N.J.	5000 500d	WHB	L No. Augusta, S.C. T Harriman, Tenn.	500d 5000d
KQYX Joplin, Mo. WQXR New York, N.Y. WSDC Mocksville, N.C.	50000	KHU	M Santa Rosa, Calif.	500d	WAU	A Plainfield, N.J. B Auburn, N.Y. H Elmira Heights-	500d	WKB	J Milan, Tenn.	10000
WSDC Mocksville, N.C. WGLD Chardon, Ohio	1kwd 250d	IKPIK	Colorado Spres., Col L. Ft. Lauderdale, Fl	a. 10000	WEH	H Elmira Heights- Horseheads, N.Y.	500d	KBO	B Borger, Tex. R Brownsville, Tex.	500d 1000
WINS Coshaeton, Ohia	1000d	WVG	L Ft. Lauderdale, Fl T Mount Dora, Fla.	1000d	WGG	Horseheads, N.Y. O Salamanca, N.Y.	5000d	KWE	L Midland, Tex.	1000 500d
WTOD Toledo, Ohio KWCO Chickasha, Okla. WRSJ Bayamon, P.R.	5000d	WCLS	S Columbus, Ga. E Eastman, Ga.	1000d 500d		E Chadburn, N.C. C Greenville, N.C.	1000 500	KMA	d Cuero, Tex. E McKinney, Tex.	1000d
WRSJ Bayamon, P.R.	5000	WLB.	A Gainesville, Ga.	5000d	I WNO	B High Point, N.C.	10004	KOG	E McKinney, Tex. Orange, Tex. Centerville Utah	0001 b0001
WLVN Nashville, Tenn. KCAD Abilene, Tex.	10000d	WKK	G Glenville, Ga. D Aurora, III.	1000d 250d	I WSR1	R Akron, Ohio W Hilisboro, Ohio	500d	WHL	Centerville, Utah L Wheeling, W.Va. C Ripon, Wis.	5000d
KHBR Hillsboro, Tex.	2500	WDQ	N DuQuein, III.	250d	KHE	Henryetta, Okla.	500d	ı wcw	C Ripon, Wis.	5000d
ı	J. S.	an	d Canadia	n A	M St	ations by	Loc	atio	n	

W.P.

Wave Length

W.P. | Kc.

Abbreviations: C.L., call letters; Kc., frequency in kilocycles; N.A., network affiliation—A: American Broadcasting Co.; C: Columbia Broadcasting System, Inc.; M: Mutual Broadcasting System; N: National Broadcasting Co., Inc.

C. COMMING BIOGRAPH		,		-	
Location C.L. Kc. N.A.	Location	C.L. Kc. N.A. Location	C.L. Kc. N.A.		C.L. Kc. N.A.
Abbeville, Ala. WARI 1480 Abbeville, La. KROF 960	Aberdeen, Wash.	KSDN 930 A Adel, Ga. KBKW 1450 Adrian, Mich.	WAAG 1470 WABJ 1490 A	1	WADC 1350 C WCUE 1150 M WHLO 640 M
Abbeville, S.C. WABV 1590 Aberdeen, Md. WAMD 970	Abilene, Tex.	KXRO 1320 Aguadiila, P.R. KRBC 1470 A KCAD 1560 Ahoskie, N.C.	WABA 850 WGRF 1340 WRCS 970		KALG 1230 M KRAC 1270
Aberdeen, Miss. WMPA 1240 Aberdeen, S.Dak. KABR 1420		KNIT 1280 Aiken, S.C.	WAKN 990 WLOW 1830 D		KGIW 1450 M WALG 1590 A
168 WHITE'S RADIO LOG	Abingdon, Va. Ada, Okia,	WBB1 1230 Aitkin, Minn. KADA 1230 A Akren, Ohie	KKIN 1000 D WAKR 1590 A		WLYB 1250 WGPC 1450 C

l nombre	C . K. N .	11					
Location	C.L. Kc. N.A. WJAZ 960		C.L. Kc. N.A. WLOS 1880 N-M-A		C.L. Kc. N.A. WAIL 1460 M		C.L. Kc. N.A. KLTR 1580
Albany, Ky, Albany, Minn,	WANY 1390 KASM 1150		W8KY 1230 WWNC 570 C		WYNE 1550 WYNK 1380	Blaine, Wash, Blakely, Ga.	KARI 550 WBBK 1260
Albany, N.Y.	WABY 1400 WOKO 1460 M WPTR 1540 A	Ashland, Ky,	WCMI 1340 C WTCR 1420		WIBR 1300 WJBO 1150 N	Blanding, Utah Blind River, Ont.	KUTA 790 CJNR 730
Albany, Ores.	WROW 590 C		WNCO 1340 KWIN 1400 M KRVC 1350	Dettile Couch Mile	WLC8 910 WXOK 1260	Bloomington, III. Bloomington, Ind.	
Albemarie, N.C.	KRKT 990 WABZ 1010	Ashland, Va. Ashland, Wis,	WIVE 1430 WATW 1400	Battle Creek, Mis Baxley, Ga.	MELL 1400 A WHAB 1260	Bleemsburg, Pa.	WCNR 930 WHLM 550
Albert Lee, Minn	WZKY 1580 . KATE 1450 A	Ashtabula, Ohio	WAQI 1600 WREQ 970	Bay City, Mish,	WBCM 1440 A WWBC 1250	Blountstown, Fia. Bluefield, W.Va.	WKMK 1370 WHIS 1440 N WKOY 1240 M
Albertville, Ala. Albien, Mich.	WAVU 630 WALM 1260	Aspen, Cele. Astoria, Oreg.	KSNO 5000 D KAST 1370 M	Bay City, Tex. Bay Minette, Ala	KIOX 1270 M	Blythe, Callf. Blytheville, Ark.	KYOR 1450 A KLCN 910
Albuquerque, N.M.	KDEF 1150 A	Atchison Kana	KIAL 1230 Kare 1470	Bayamen, P.R. Baytown, Tex.	WRSJ 1560 KWBA 1360	Boaz, Ala, Begalusa, La,	WBSA 1300 WIKC 1490 N
	KGGM 610 C KOB 770 N KQEO 920 M	Athens, Ga.	WGAU 1340 C WDOL 1470	Beardstowa, III,	WBNR 1260 WRMS 790	Boise, Idaho	WBOX 920 KATN 1010
	KARA 1310 KMGM 730	Athens, Ohio	WRFC 960 WATH 970 WOUB 1840	Beatrice, Nebr. Beaufert, N.C. Beaufert, S.C.	KWBE 1450 WBMA 1400 WBEU 960		KBO1 950 C KEST 790
	KLOS 1450 KRZY 1580 A	Athens, Tenn. Athens, Tex.	WLAR 1450 M KBUD 1410	Beaument, Tex.	WSIB 1490 KFDM 560 A		KGEM 1140 M KIDO 630 N KYME 740
Aleca, Tenn. Alexander City, A		Atlanta, Ga.	WPLO 590 C WAKE 1840		KPYC 1450 KTRM 990	Bolivar, Mo, Benham, Tex,	KBLR 1550 KFYN 1420
Alexandria, La,	WRFS 1050 KALB 580 A KDBS 1410		WAOK 1380 WERD 860	Beaver Dam, Wis. Beaver Falls, Pa.	WBVP 1230	Beene, lowa	KFGQ 1260 KWBG 1590
Alexandria, Minn.	KSYL 970 N		WGKA 1600 WGST 920 A	Beckley, W. Va.	WJLS 560 C WWNR 620	Boone, N.C. Beonville, Ind.	WATA 1450 WBNL 1540
Alexandria, Va, Algona, Iowa	WPIK 730 M KLGA 1600 KOPY 1070		WIIN 970 WQXI 790 WSB 750 N	Bedford, Ind. Bedford, Fa. Bedford, Va.	WBIW 1340 WBFD 1310 WBLT 1350	Boonville, Me. Boonville, Miss. Boonville, N.Y.	KWRT 1370 WBIP 1400 A WBRV 900
Allee, Tex. Allegan, Mich.	WOWE 1580	Atlanta, Tex.	WYZE 1480 C KALT 900	Beeville, Tex. Belen, N. Wex.	KIBL 1490 KARS 860	Berger, Tex.	KHUZ 1490 M KBBB 1600
Allentown, Pa,	WHOL 1600 WAEB 790	Atlantie, Iswa Atlantie Beach, F	KJAN 1220 Ia. WKTX 1600	Belgrade, Mont, Bellaire, Ohlo	KGVW 630 WOMP 1290 M	Bosten, Mass.	WBZ 1030 WCOP 1150
Alliance, Nebr.	WKAP 1320 WSAN 1470 N KCOW 1400	Atlantic City, N	WLDB 1490 A-M	Bellefentaine, Ohl Bellefente, Pa.	WBLF 1330		WILD 1090 WNAC 680
Allience, Ohio	WFAH 1310 WCQS 1400	Atmore, Ala,	WMID 1840 A WATM 1590	Bell Fourche, S.D. Belle Glade, Fla.	WSWN 900		WEZE 1260 N WEEL 590 C
Alma, Mich. Alpena Tewnship,	WFYC 1280 Mich.	Attlebere, Mass Auburn, Ala, Auburn, Calif,	. WARA 1320 WAUD 1230 A KAHI 950	Belleville, Ont. Belleville, III. Bellevue, Wash.	CJBQ 800 WIBV 1260 KFKF 1330		WHDH 850 WMEX 1510 WORL 950 M
Alpine, Tex.	WATZ 1450 KVLF 1240 M WKDE 1280	Auburn, N.Y.	WMB0 1340 M WAUB 1590	Beilingham, Wash	KBVU 1540	Bouider, Cole.	KBOL 1490 KDEY 1360
Altavista, Va. Alton, III.	WOKZ 1570	Auburn, Wash, Auburndale, Fla Auburndale, Wis	KASY 1220 WTWB 1570		KGMI 790 A KOQT 1550	Bowle, Tex, Bowling Green, Ky	KBAN 1410 WKCT 930 A
Altona, Man, Altoona, Pa,	CFAM 1290 WFBG 1290 N WRTA 1240 A	Augusta, Ga.	WAUG 1050	Bellingham-Fernd	ale, Wash, KENY 930		WBGN 1340 WLBJ 1410 M
Alturas, Calif.	WVAM 1430 C KCNO 570		WBBQ 1340 M WBIA 1230 N WGAC 580 A	Belment, N.C. Beleit, Wis. Belten, S.C.	WCGC 1270 M-A WGEZ 1490 M WHPB 1390	Bowl, Green, Ohio Bozeman, Mont.	KXXL 1450 N KBMN 1230
Altus, Okla, Alva, Okla,	KWHW 1450 KALV 1430	Augusta, Maine	WRDW 1480 C WRDO 1400 N	Belton, Tex. Belzoni, Miss.	KTON 940 WELZ 1460	Bradbury Hets., M Braddock, Pa,	MLOA 1550
Amarillo, Tex.	KBUY 1010 M KFDA 1440 A	Aurora, Colo.	WFAU 1840 M	Bemidli, Minn, Bend, Oreg.	KBUN 1450 M KBND 1110 A	Braddecks Heights	, Md. WMHI 1370
	KGNC 710 N KIXZ 940 C	Aurora, ill,	WMRO 1280 WKKD 1580 '	Bennetsville, S.C. Bennington, Vt.	KGRI 940	Bradenton, Fla.	WTRL 1490 WBRD 1420
Ambridge, Pa.	KRAY 1360 KZIP 1310 WMBA 1460	Aurora, Mo. Austin, Minn.	KSWM 940 Kaus 1480 m Kqaq 970	Benson, Mian,	WBTN 1370 KBMO 1290 WPYB 1580	Bradford, Pa. Brady, Tex. Brainerd, Minn.	WESB 1490 M KNEL 1490
Americus, Ga. Ames, Jewa	WDEC 1290 KSAI 1430	Austin, Tex.	KNOW 1490 A KASE 970	Benson, N.C. Benton, Ark. Benton, Ky.	KBBA 690 WCBL 1290	Brampton, Ont. Brandon, Man.	KLIZ 1380 CHIC 1090 CKX 1150
Amherst, N.S. Amherst, N.Y.	WOI 640 CKDH 1400 WUFO 1080		KTBC 590 C KOKE 1370	Benton Harbor, M Berkeley, Calif.	leh.WHFB 1060 KRE 1400	Branson, Me. Brantford, Ont.	KBHM 1220 CKPC 1380
Amite, La.	WABL 1570 WAMY 1580	Avaion, Calif.	KVET 1300 M KBIG 740	Berkeley Springs,	W.Va, WCST 1010	Brattleboro, Vt.	WTSA 1450 N WKVT 1490
Ames, Que. Amsterdam, N.Y.	CHAD 1340 WAFS 1570	Avendale Estates	WAVP 1390 Ga. WAVO 1420 KNDE 1340	Berlin, N.H. Berry Hill, Tenn,	WMOU 1230 WBRL 1400 WVOL 1470	Brawley, Callf. Brazil, Ind. Breckenridge, Min	KROP 1300 A WBZ1 1380
Anaconda, Mont.	WCSS 1490 KANA 580	Babylon, N.Y.	WBAB 1440 M WGLI 1290	Berryville, Ark. Berwick, Pa.	KTHS 1480 WRRX 1280	Breckenridge, Tex Bremen, Ga.	, KSTB 1430 WWCC 1440
Anacortes, Wash, Anaheim, Calif.	KAGT 1340 KEZY 1190	Bad Axe, Mich. Bainbridge, Ga.	WLEW 1340 WMGR 930	Bessemer, Ala, Bethesda, Md,	WYAM 1450 WUST 1120	Bremerten, Wash, Brenham, Tex.	KBRO 1490 KWHI 1280 PNF 1240 M-N
Anchorage, Alaska	KFQD 730 C-A NI 550 A-M-N	Baker, Oreg.	WAZA 1360 KBKR 1490	Bethlehom, Pa. Beverly, Mass,	WGPA 1100 WMLO 1570	Brewster, N.Y.	WRRW 1510
Andalusia, Ala. Anderson, Calif.	WCTA 920 KPON 1580	Bakersfield, Cali	f. KAFY 550 M KBIS 970 KERN 1410 C	Biddeford, Maine Big Delta, Alaska Big Lake, Tex,	WIDE 1400 M WXLL 980 KBLT 1290	Bridgeport, Ala.	W B T S 1480 W B T S 1480
Anderson, Ind.	WHUT 1470 M WHBU 1240 C		KGEE 1230 KUZZ 800	Big Rapids, Mich, Big Sprg., Tex.		Brewton, Ala. Bridgeport, Ala. Bridgeport, Conn. W Bridgeton, N.J.	NAB 1450 A-M W8NJ 1240 M
Anderson, S.C. Andrews, Tex.	WAIM 1230 C WANS 1280 M		KLYD 1350 KWAC 1490		KHEM 1270 KBYG 1400 M	Bridgewater, N.S. Brigham City, Utah	CKBW 1000 KBUH 600
Annapolis, Md.	WANN 1190 WARW 810	Bellingham, Was Baldwinsyille, N.	KPMC 1560 A	Big Stone Gap, Va Biloxi, Miss,	WLOX 1490 M	Brighten, Cele, Brinkley, Ark, Bristol, Cenn,	KBRN 800 KBRI 1570
Ann Arbor, Mich.	WABW 810 WNAV 1430 WHRV 1600 M	Ballinger, Tex. Baltimore, Md.	Y. WSEN 1050 KRUN 1400 WBAL 1090 N	Billings, Mont,	WVMI 570 KBMY 1240 M KGHL 790 N	Bristel, Tena.	WBIS 1440 WOPI 1490 N WYKE 1550
Anna, III.	WPAG 1050 WRAJ 1440		WBMD 750 WCAO 600		KOOK 970 C	Bristof, Va.	WCYB 690 A WFHG 980 M
Anniston, Ala.	WANA 1490 WDNG 1450 A WHMA 1390		WCBM 680 C WFBR 1300 WITH 1230 M	Binghamton, N.Y.	KURL 730 WINR 680 N	Breckton, Mass,	WBET 1460 WOKW 1410 CFJR 1450
Anoka, Minn. Ansonia, Conn.	KANO 1470 WADS 690 M		WSID 1010 WWIN 1400 A-M	Birmingham, Ala.	WKOP 1360 M WNBF 1290 C WAPI 1070 N	Brackville, Ont, Braken Bow, Nebr, Brookfield, Me.	CFJR 1450 KCNT 1280 KGHM 1470
Antigonish, N.S.	WATK 900 CJFX 580	Bamberg, S.C. Banger, Maine	WWBD 790 WABI 910 A-M	Dirmingnam, Ala,	WAPI 1070 N WBHM 1550 WBRC 960 A	Brookhaven, Miss,	WCHJ 1470
Apolio, Pa, Apple Valley, Cal.	WAVL 910 KAVR 960		WGUY 1250 C WLBZ 620 N		WCRT 1260 A WEZB 1220	Brookings, Oreg, Brookings, 8.Dak, Brookline, Mass,	KURY 910 KBRK 1430
Appleton, WIS.	WAPL 1570 WHBY 1230 M WRAB 1380	Banning, Calif. Barboursville, Ky	KPAS 1490 V. WBVL 950		WENN 1320 M WATV 900 C	Brooksville, Fla.	WWJB 1450
Arcadia, Fla. Arcata, Calif.	WAPG 1480 KENL 1340	Bardstown, Ky, Barnesboro, Pa, Barnwell, S.C.	WBRT 1320 WNCC 950 WBAW 740		WSGN 610 WYDE 850	Brownfield, Tex. Brownsville, Tex. Brownwood, Tex.	KTFY 1300 KBOR 1600 A KBWD 1380 M
Ardmore, Okla, Arcelbo, P.R.	KVSO 1240 A WCMN 1280	Barre, Vt. Barrie, Ont.	WSNO 1450 1	Bishee, Ariz. Bishop, Calif.	WVOK 690 KSUN 1230 A	Brunswick, Ga.	KEAN 1240 WGIG 1440 A
	WMIA 1070 WN1K 1230	Barstew, Calif,	CKBB 950 KWTC 1230 A KIOT 1310	Bishopville, S.C. Bismarck, N.Dak.	KIBS 1230 A WAGS 1380 KFYR 550 N	Brusswick, Maine	WMOQ 1490 WCME 900
Arkadelphia, Ark. Arkan. City, Kans, Arlington, Fia, Arlington, Va.	KVRC 1240 M l	Bartlesville, Okla Bartew, Fla. Bassett, Va.	. KWON 1400 M WBAR 1460	Bismarck-Mandan,	KQDI 1350 N.Dak.	Bryan, Tex.	KORA 1240 M WTAW 1150
		Bassett, Va. Bastrop, La.	KTRY 730	Black Mountain, N	KBOM 1270	Buffale, N.Y.	WBUC 1460 WBEN 980 C WYSL 1400
Arvada, Colo.	WEAM 1390 KSVP 990 M KDAB 1550	Batavia, N.Y. Batesburg, S.C.	KVOB 1340 WBTA 1490 M WBLR 1430	Black River Falls,	WBMT 1350 WFGW 1010 WIs.		WEBR 970 M WGR 550 N
Ashburn, Ga. Asbury Park, N.J.	KDAB 1550 WMES 1570 WJLK 1310	Batesville, Ark. Batesville, Miss.	KBTA 1840 WBLE 1290	Blackfoot, Idane	WWIS 1260		WKBW 1520 N WWOL 1120 A
Asheville, N.C.	WGWR 1260	Bath, Maine Bath, N.Y,	WMM8 730	Blackshear, Ga. Blackstone, Va.	WBSG 1350	WHITE'S RADIO	
					·		

							C.L. Kc. N.A.
Location	C.L. Ke. N.A.	Location C.L.	Kc. N.A. Lo	cation eveland, Ga	C.L. Kc. N.A. WRWH 1350	Location	KCTA 1030 M
Buffale, Wye, Buford, Ga.	KBBS 1450	Chapel Hill, N.C. WCh Chardon, Ohio WGL	D 1560 CI	eveland, Miss.	WCLD 1490		KCCT 1150 KEY8 1440 KRYS 1360 N
Burbank, Callf, Burley, Idahe	KBLA 1490 KBAR 1280 A-M	Charles City, Iswa KCI	SA 940 1A 1580 IC 1270	eveland, Ohio	KYW 1100 WDOK 1260 M		KSIX 1230 A-M KUNO 1400
Burlington, lowa Burlington, N.C.	KBUR 1490 A WBBB 920 M	Charleston, Me. KCI	1R 1350 RC 1390 C		WERE 1300 WGAR 1220 C WHK 1420	Corry, Pa, Corsicana, Tex.	WOTR 1370 KAND 1340
Burlington, Vt.	WBAG 1150 WCAX 620 N	WOKE	1340 A-M AL 730		WABQ 1540 WJW 850 N	Cortex, Colo.	KVFC 740 WKRT 920 KOAC 550
Burnett, Tex.	WDOT 1400 WJOY 1230 A KTSL 1340	WI	SN 1450 NA 1250 N CI NW 680	leveland, Tenn.	WBAC 1340 M WCLE 1570 KVLB 1410	Corvailis, Ores.	KFLY 1240 KLOO 1850
Burns, Oreg. Butier, Ala.	KRNS 1230 WPRN 1220	WC WT	H S 580 C C	leveland, Tex, leve, Hets., Ohi	WIMO 1490 A	Coshocton, Ohio Cottage Grove, Or	WTNS 1560 8. KNND 1400
Butler, Mo. Butler, Pa.	KMAM 1530 WBUT 1050 WISR 680	W.K.	AZ 950 N C	lewiston, Fla. lifton, Ariz. lifton Forde, V	KCLF 1400 A	Cottonwood, Aria	KVIC 1600
Butte, Mont.	KBOW 1490 C	Charlotte, Mich. WC	EB 1890 C	lincho, Va. jinton, III.	WDIC 1430 WHOW 1520 KCLN 1390	Coudersport, Pa Council Bluffs,	
Cabano, Que.	KXLF 1370 N CJAF 1340 WATT 1240 M	W	YS 610 M C	linton, lowa	KROS 1340 M KDKD 1280	Covington, Ga.	CFCP 1440 WGFS 1430
Cadillae, Mich, Caguas, P.R.	WNEL 1430 WVJP 1110	W.K	TC 1310	iinton, Mo. iinton, N.C. linton, Okla.	WRRZ 880 A	Covington, La.	WARB 730 WKBL 1250 WKEY 1340 A
Cairo, Ga. Cairo, III.	WGRA 790 WKRO 1490	Charlotte Amalie, V.L.	OK 1480	linton, Tenn.	WPCC 1410 WYSH 1380 WKLK 1230	Covington, Va. Cowan, Tenn. Craig, Colo.	WZYX 1440 KRAI 550
Calais, Maine Caldwell, Idaho	KCID 1490	l WE	STA 1340	loquet, Minn. Clevis, N.Mex.	KCLV 1240	Cranbrook, B.C.	
Calera, Ala.	KBGN 910 WBYE 1370 KICO 1490 A	Charlottesville, Va. W.C	HV 1260 A	Coachella, Calif.	KICA 980 KCHV 970 KBMX 1470	1	alif. KPLY 1240 KPOD 1310 KSIB 1520
Calexico, Calif. Calgary, Alta.	CFAC 960 CBX 1010	Charlottetown, P.E.I.C	ECV 630 11	Coatesville, Pa. Cocoa, Fla.	WCOJ 1420 WKKO 860 WEZY 1350	Creston, lowa Crestview, Fla.	WCNU 1010 WJSB 1050
_	CFCN 1060 CKXL 1140 WCGA 900	Chatham, Ont. C	FCO 630 MOC 1450 M	Cocoa Beach, Fl Cody, Wyo.	WRKT 1300	Crewe, Va. A Crockett, Tex.	WSVS 800 KIVY 1290
Calhoun, Ga, Cambridge, Md Cambridge, Ma	WCEM 1240	.] """	1070 01	Coour d'Alene, l Coffeyville, Ka	ns. Kuur ooo	M Crookston, Mil A Crossett, Ark.	KAUII 000
Cambridge, Oh Camden, Ark.	KAMD 910	i w	DXB 1490 NOO 1260	Colby, Kans. Coldwater, Mic	h. WTVB 1590 KSTA 1000	Crossville, Ten Crowley, La. Cuero, Tex.	KSIG 1450 M KCFH 1600
Camden, N.J.	WCAM 1810 WKDN 800 WACA 1590	Cheboygan, Mich. W	CBY 1240 / NIA 1230	Colby, Kans. Coldwater, Mic Coleman, Tex. Coling, Wash. Coloniel Heigl	KCLX 1450 a. WEAD 1570	Culiman, Ala.	WFMH 1460 WKUL 1340 WCVA 1490 M
Camden, S. C. Camden, Tenn, Cameron, Tex.	WFWL 1220 KM1L 1330	Chehalis, Wash, Chelan, Wash,	KITI 1420 KOZI 1220 CRE 1420	Colourer	WPVA 1290	Cuipeper, Va. Cumberland, K Cumberland, M	y. WCPM 1280
Camilla, Ga.	WCLB 1220	Cherokee, Iowa	CHE 1440 SGM 980	Colonial Villag	M 2 K 1 1200	Cummings, Ga	WTB0 1450 WSNE 1410
Campbellsville Campbellton,	N.B. CKNB 950	Chester, Pa.	VEEZ 1590	Colorado City, Colo. Spres., (Colo. KRDO 1240 KPIK 1580	Cushing, Okla	L KUSH 1999
0211110001	N V WCGR 1550		GCD 1490 (FBC 1240 A (CHY 1590		KYOR 1300 KSSS 740 KYSN 1460		El. WGTO 540
Canton, us.	Cole. KRLN 1400 a. WARO 540 WCHK 1290		(RAE 1480 VWO 1370 M	Columbia, Ky.	WAIN 1270	Dade City, F M Dadeville, Als	ia. WDCF 1350 WDVC 910
Canton, III. Canton, Miss.	WBYS 1560 WDOB 1370 WWIT 970	Chicago,	VAAF 950 WAIT 820 M VRBM 780 C	Columbia, Mo	K CGM 1580	A Dalhart, Tex.	* KXIT 1410 * WAAK 960 KROW 1460
Canton, N.C. Canton, Ohio	WCNS 900 WHOF 1060		WBBM 780 C WCFL 1000 VCRW 1240	Columbia, Pa.	WCOY 1580 WCOS 1400 W18 560	A Dallas, Tex.	KRLD 1080 C KIXL 1040
Canyon, Tex.	WHBC 1480 KVPH 1550 B. Ma. KFVS 960	^	WEDC 1240 VYNR 1390		WOIC 132 WNOK 123	D C	KSKY 660 KLIF 1190
Cape Girardes Carbondale, I	KGMO 1550		WGN 720 M WIND 560 WJJD 1160	Columbia, Ter	WOXL 1470	0 1	WFAA 570 A WFAA 820 N KBOX 1480
Carbondale, F	a. WCDL 1440	,	WLS 890 A	\	M K k in 194) N (WRR 1310 M Ores KACI 1300
Carlisle, Pa. Carisbad, N.) C1	WMBI 1110 WSBC 1240		WGBA 127 WCLS 158	0 M Dalton, Ga.	KODL 1440 A WBLJ 1230 M WRCD 1430
Carmel, Calif	KRML 1410 WROY 1460	Chicago rigos, itis	WCGO 1600 KWCO 1560	Columbus, 11	WOKS 134 WCSI 101	0 Danbury, Co	nn, WLAD 800
Carnesie, Pa	WZUM 1590	Chico, Calif.	KHSL 1290 (Columbus, M	ACRISE SE	O M Danville, K	WITY 980 WHIR 1230 M
Carrington, Carrizo Sprii	N.Dak. KDAK 1600 ngs, Tex. KBEN 14 KCIM 1880		WACE 730 CBJ 1580 CJMT 1420	Columbus, O	hie WBNS 146	60 C Danville, V	a. WBTM 1830 A WYPR 970 WDVA 1250 M
Carroll, low: Carrollton, Carrollton, Carr	Ia. WRAG 59	Childrens, Tex.	KCTX 1510 KCH! 1010		WMNI 92 WOSU 82 WTVN 6		WILA 1580 S.C. WDAR 1350
Carrollton, I Carson City,	Nev. KPTL 130	Chillicothe, Ohio	WBEX 1490 WCHI 1350	Colville, Wa	WVKO 15	80 Dauphin, M 70 Davenport,	SU' CKDW 120
Cartersville, Carthage, I	GA. WKRW 127	O Chimiwacki D.O.	CHWK 1270 WBGC 1240	Commerce, G	ia. WJJC 12 III. KWUN 14	70 l	KSTT 1170 M
Carthage, M Carthage, T	B1114.	Christiansburg, Va	WAXX 1150 WBCR 1260	Concord, N. Concord, N. Concordia,	C. WEGO 14	10 Dawson, Yu 90 Dawson Cre	iek, B.C. CIDC 560
Carthage, T	III. Me. KCRV 187	Church Hill, Tenn.	WIVI 970	Conneaut, O	hio WWOW IS	50 A Dayton, Un	WHIO 1290 C WING 1410 WONE 980
Casa Grand Casper, Wy	O, KTWU 14. KATI 14	00 Cicato III. Orio	WCKY 1580	M Connelisville	a, Ind. WUND	000 Dayton, Te	MAVI 1210 MDNT 1280
Cayee, S.C	KVOC 1280 WCAY 6 Litah KSUB 5	20 C	WCIN 1480 WCPO 1280	Conway, A	44 CO CO DI 46	230 Daytona B	ezch, Fla. WNDB 1150 M-A WMFJ 1450
Cedar City Cedar Fall	s, lows KCF1 12	500 A	WKRC 550 WLW 700 N W8AI 1360	Conway, S.	H. WBNC	050 I	WROD 1840
Cedar nap	KLWN 14	50 Clanton, Ala.	WKLF 980 WCRM 990	Cookeville,	WTPL	220 Destroin.	Mich WKMH 1310 M
Cedartown	Ga. WGAA IS	Clarement, N.H.	WTSV 1230 KWPR 1270 WWCH 1300	Coos Bay,	Ores. KOOSI	230 M 420	WMSL 1400 M
Celina, Oh Center, Al Center, Te	a. WEIS	Clarksburg, W.V		M Coquille. C	il, Tenn. WLSB I Dreg. KWRO les. Fla. WRIZ I	400 Decatur, C	II. WSOY 1340 C
		400 I	WPDX 750 WROX 1450	M Continue	WVCG	070 Deceran, 1	owa KDEC 1240 KWLC 1240
Centerville Centerville Central C	ity, Ky. WNES I	Clarksville, Ark.	KLYR 136	Cordele. G	WYGO	1330 Deerfield,	Ohio WONW 1280
Centralia,	III. WCNT I	210 Clarksville Tex	WDXN 54 KCAR 135 WCLA 147	n Cordova,	AIRSER INLINI	1230 1450	Springs, Fla. WDSP 1280 WZEP 1460
Wash, Cantravil	e Miss. WGLC	580 Clayton, Ga.	WCLA 147 WGHC 157 KXLW 132	O Corner Br	ook, Nfld. CBY	790 De Kalb, 570 De Land,	Fia. WLBK 1360 WJBS 1490 WOOO 1310
Chadourn	Nebr. KCSR	800 Clayton, Mor	KFUO 85 KLMX 145	Cerning.	ANK KUUD	1350 Delano, (Callf. KCHJ 1010 Ohio WDLE 1550
Champai	an, III. WDWS	1400 C Clearfield, Pa.	WCPA 90 WTAN 134 WAZE 80	10 1	Ont. CJSS CFML	1220 Delray, B	Tex. KDLK 1230
Chanute,	Kans, KUNB	Clabuena Tex	WAZE 81 KCLE 11: WSLG 13:	20 Cerana.	11 - 11 - 11 - 11	1370 Delta, C Deming,	N.Mex. KOTS 1230
170	WHITE'S RADIC	LOG Clerment, Fla.	# OFG 19				

C. L. K. R. M. A. LocoPlon C. L. K. R. M. LocoPlon C. L. K. M.	*							
Denters Street, L. W. U.S. 1 1500 100		C.L. Kc. N.A	. Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location (C.L. Ke. N A.
Canada Face Canada Can	Demopolis, Ala,	WXAL 1400 R	4	CJCA 930	Faribault, Minn.	KDHL 920	Frederick, Md.	WFM0 980 C
Denter Late Color Soc Color	Denham Spres., I	.a. WLBI 1220	Edmundston, N.	C, CJEM 570	Farmington, Mo.	KREI 800		
Denwy Clork Color 1808 Clork Call Cal	Denison, Tex.	KDSX 950	Elba, Ala.	WELB 1350	Farmington, N.M	KWYK 960	Fredericksburg, Va.	KNAF 910 M WEVA 1280 A
C. C. C. C. C. C. C. C.	Denver, Cele.	KDEN 1840	El Cajon, Calif.	KDEO 910 A		WFAG 1250	Fredericten, N.B.	WFLS 1350 CENB 550
## 15 19 10 10 10 10 10 10 10		KHOW 630 A	El Contro, Calif.	KXD 1230 M	Farmville, Va. Farrell, Pa.	WFLO 870 WFAR 1470	Fredericktown, Mo.	
Elderde, Kam. Fig. 20 Carlotte Carlo		KLIR 990	El Dorade, Ark.	KDMS 1290	Farwell, Tex,	KZDL 1570	Fredenia, N.Y.	WBUZ 1570
Elder March Springs March Ma		KBTR 710		KELD 1400 A		KHOG 1440	Freeport, N.Y.	WGBB 1240
## Care City, Tea. KCAL 1300		KPOF 910		i, Me.	Fayetteville, N.C.	WFAI 1230 C	Fremont, Mich.	WBFC 1490
Darleder, L., R. (KDL. 1806) Darleder, L., KOL. 1806 Darleder, L., KOL. 1806 Darleder, L., KOL. 1806 N. (KOL. 1806) Darleder, M. (KOL. 1806) Dilline, M. (KOL. 1806) D		KFSC 1220	Elgin, III,	WRMN 1410		WFLB 1490 A	Fremont, Nebr.	KHUB 1340
Dariell, Mish, William Dariell, Mish, Will	Denver City, Tex.	KKAL 1580		WCNC 1240	Fayetteville, Tene	١.	Fremont, Ohie Fresno, Calif.	KARM 1436 A
Comparison Com	DeRidder, La.	KOLA 1010		n. WBEJ 1240	Forgus Falls, Mi	nn.		KBIF 900
Datroll, Mich. Wid. 1900 Clark Wid. Wid. 1900 Clark Wid. Wid. 1900 Clark Wid. Wid. 1900 Clark Wid. W	Des mutitos, 10 wa	KIDA 940 N	Elizabethtown, N	I.C.	Fornandina Beach	h. Fla.		KEAP 980
Datrolt Lakes, Michael 1999 Wilk 1999 Drafter, Mr. N. Dak, KDIX, 1230 Ditkinson, M. Dak, MDIX, 1230 Ditkinson, M. Dak, MD		KSO 1460	Elizabethtown, P.	a. WEZN 1600	Fefriday, La.	KFNV 1600		KFRE 940 C
## 150 ## 150		WHD 1040 A		WTRC 1340 N			1	KMAK 1340
## 1 200 Datrolt Lakes, Minn, KO, LM, 1300 Dileti, Tear, Mark, Collar, 1300 Dileti, Tear, Mark, Collar, 1300 Dileti, Tear, Mark, Collar, 1300 Dileti, Tear, Mark, KO, LM, 1300 Dower, Mark, M	Detroit, Mich,	WJBK 1500	Elkin, N.C.	W1FM 1540	Findiay, Ohlo	W F I N 1830	1	KYND 1800
Derirol Lakes, M.D. (C. D. 1936) Derirol Lakes, M.D. (C. D. 1936) Distant, M. (C. D. 1936) Di		WJLB 1400 WJR 760	Elkins, W.Va.	WDNE 1240 KELK 1240 M	Fitchburg, Mass.	WEIM 1280 M	Frostburg, Md.	WFRB 560
Detter, Ma. ROEK, 1930 Dilkstan, Tan. WD SN 1200 Dilkstan, Tan. WD SN		WWJ 950 N	l Eikton, Md.	WSFR 1550		WBHB 1240 M	Fulton, Me.	KFAL 900
Detter, Ma. ROEK, 1930 Dilkstan, Tan. WD SN 1200 Dilkstan, Tan. WD SN	Detroit Lakes, M	Inn.	Elisworth, Me.	WDEA 1350	l'ingreen, Arra.	KFGT 1000	FUGURY Spres. N	C.
Dickings, N. Dalb, KCINI 200 Dickings, T. Dalb, KCINI 200	Devils Lake, N. D.	ılt.	1	WENY 1280 N		KVNA 690 A	Gadsden, Ala,	WGAD 1850 A
Dillien, Mar. KDBB 600 Dillien, SC. KDBB 600 Dillien, SC. KDBB 600 Dillien, SC. WIX 600 Description WIX 600 Descri	Dexter, Me.	KDEX 1590		Y	Flat River, Me.	KFMD 1240 M		WETO 930 M WAAX 570
Dillenis, Sept. Republish	Dickinson, N.Dal	. KDIX 1230	El Paso, Tex.	KROD 600 C	Flint, Mich.	WFDF 910 N	Gaffney, S.C. 1	WFGN 1570
Disso, Ill., WIXM 1460 Doteder City, Kans, KCR0 1370 Doteder, Ala, WAGF 1320 Dover, Oble, WEEL 1320 Dover, Dels, WEEL 1320 Dover, N.J., WEEL 1320 Dover, N.J., WEEL 1320 Dover, N.J., WAGF 1320 Dover, N.J., WAGF 1320 Dover, N.J., WAGF 1320 Dover, M.J., WAGF 1320 Dover	Dillon, Mant.	KDBM 800		KPBR 1530	1	WAMM 1420	1	WGGG 1230 M
Dethan, Ala. WAG 1330 M KED 1350 M KED 1350 M KED 1350 M KELR 1460 M WOLF 1350 M KELR 1460 M KERR 1460	Dinuba, Calif.	KRDU 1130	`	KINT 1590		WMRP 1570 WKMF 1470 M	Gainesville, Ga.	WGGA 550 C
Dethen, Ala. Collaboration Florence, Ala. W. M. W. W. M. W.	Dodge City, Kans	WIXN 1460 , KGNO 1870 M	ı		Flomaton, Ata.			WLBA 1580
Deuglas, Ariz, K. April 1930 M Epity Minn. WELY 1450 M Epity Minn. WELY 1200 Emperis, R. R. K. V. WELK 1500 Deuglas, G. W. WIN 1000 Deuglas, Wys. K. WIV 1000 Deuglas, Wys. WIV 1000 Deuglas, Wys. WELK 1500 Deuglas, Wys. WELK 1500 Deuglas, Wys. WELK 1500 Deuglas, Mys. Welk 1500 Deuglas,	Dothan, Ala,		El Rene, Okla.	KTSM 1380 N		WJDI 1840 M	Gaithersburg, Mc. 1	WHMC 1156
Douglas, Ariz, K. AWT 1459 M Douglas, Ariz, K. AWT 1459 M Douglas, W. Control of the Control of		WDDF 560	l Ely, Minn.	WELY 1450 M	Florence S 7	WDWL 1240 A	Galesburg, III,	WGIL 1400
Duglas, Mys. (CA) 1310 Cover, Del. (CA) 1310 Cover, Col. (CA) 1310 Cover	Douglas, Ariz.	KAWT 1450 M	I Elvria, Dhio	WEOL 930		WYNN 540	Gallatin, Tonn.	WHIN 1010
Down	Douglas, Ga.	WDMG 860	Emperia, Kans,	KV0E 1400	Foley, Ala.	WHEP 1310	Gellipolis, Dhie Gallup, N. Mex.	WJEH 990 KGAK 1330 A
Downer, N. H. WEEN 1800 Downer, N. H. WT59 1800 Downer, Ohle WT	Douglas, Wyo,	KWIV 1050	Emporium, Pa.	WLEM 1250	Fordyce, Ark.	KBJT 1570	Galt, Ont,	KYVA 1230 CKGR 1110
Downsies, Mish. WIRAM S100 Devasjas, Mish. WIRAM S100 Easting, Mish. WIRAM S100 Ea		WKEN 1600 A	Englewood, Colo.	KGMC 1150	Forest City, N.C.	WB80 780	Galvesten, Tex.	KILE 1400
Devesters, P. WELV 1370 Drysholite, P. Welver, P. Welve	Doyer, N.J.	WRAN 1510		KCRC 1390 A	Forest Greve, Ores	I, KGGG 1570	Gander, Nfld,	CBG 1450
Drammond/life, Que. Other Discontine City of Street City of Stree	Downgiae, Mich.	W D O W 1440	Enterprise, Ala.	WIRB 600	Ft. Brage, Calif.	KAJK 950 KDAC 1280	Gardner, Mass. V	KIUL 1240 M
Dublin, Ga. WALT 1350 Efle, Pa. WWYM 1250 A WWYM	Drumheller, Alta.	CIDA 810	Ephrata, Pa.	W GSA 1310	Ft. Collins, Colo.	KCOL 1410 A	Gary, Ind.	VWCA 1270
Du Bais, Pa. WXLI 1230 Dubbiqus, Jows WXLI 1230 Dubbiqus, Jows WXLI 1230 Duristh, Minn. WJBQ 1400 WEBC 560 Duristh, Minn. WJBQ 1400 WEBC 560 NADH 1350 Durmas, Dita. CRDD 300 Durmas, Dita. CRDD 300 Durmas, Dita. CRDD 300 Durmas, Dita. WRBB 1500 Du		CHRD 1340	Ephrata, Wash, Erie, Pa,	WWYN 1260 A	Ft. Dodge, lewa	KVFD 1400 M	Gastonia, N.C.	WGNC 1450 A
Dubuque, Iowa KOTH 1370 A Duluth, Minn, KOTH 1370 A VERB 1370 A VE		WXLI 1230		WICU 1380 N WJET 1400 M	Ft. Frances, Dat,	CFDB 800	Gate City, Va.	WGAT 1050
Dultith, Minn, WOBG, 1490 N. Control 1890 N. C		KOTH 1270 A	Erwin, Tenn.			a. WFTL 1400	Geneva, Ala, \	WGEÁ 1150
Duman, Tox. Name	Duluth, Minn,	KDAL 610 C		WDBC 680 M	Ft. Madison, lowa	KXG1 1360	Geneva, N.Y. V	WGVA 1240 A
Dumas, Tex. KDDD Bod Dumean, Dilta KRM 1350 M Exheryille, lews KLIL 1340 Dumean, Dilta KRM 1350 M KVR		WEBC 560 KADH 1390	Escendide, Calif.	KDWN 1450	Ft. Myers, Fia.	WINK 1240 C	Georgetown, Ky, \	WAXU 1580
Dundals, Mg, WATE S80 Dundals, Cele, KUP S80 Dundals, Cele, KUP S80 Cele, KUP		KDDD 800	Estherville, lowa	KL1L (340	Ft. Payne, Ala,	WFPA 1400	Gettysburg, Pa.	WGET 1320 M
Dunkirk, N.Y. WPE R 1870 Dunkirk, N.Y. WDE 1410 Dunn, N.C. WCKB 780 Du Quoin, III. WDN 1580 Curange, Cele, N. GDD 1240 Curange, C		WAYE 860	Eufaula, Ala,	WULA 1240 M	Ft. Pleree, Fla.	WARN 1330	Gilrey, Calif.	KPER 1290
Durange, Cele, WCKB 780 Durange, Cele, KIUP 830	Dundee, N.Y.	WFLR 1570	Eugene, Oreg.	KPIR 1500	Ft. Saint John, B.	C. I	Giasgowater, 19X.	WKAY 1490
Durange, Cole, KUD 930 Cole, KSFD 750 Col	Dunn, N.C.	WCKB 780	}	KATR 1320		KMDD 1600	Glasgow, Ment,	WCDS 1440 D KLTZ 1240
Dursat, Okla.	Durange, Cele.	KIUP 980		KUGN 590 N	·	CFMR 1490	Giendale, Calif.	
## WSB 1490 WTK 1310 WTK 1310		K8FD 750	Euroka, Calif.	KINS 980 C	Pt. Smith, Ark,	KFSA 950 A	'Glendive, Mont, I	(XGN 1400 KGLE 590
## WTK 1310 A WTK	Jurnem, M.U.	WSRC 1410	E	KRED 1480 M		KTCS 1410 M KWHN 1820	,	WW8C 1450 A
Easle Pass, Tex, East River, Wis. WERL 950 Easley, S.C. WELP 1380 C. Grand Forks, Minn. Everett, Wash. KERC 1390 E. Liverpool, Ohio WOHI 1490 AEaston, Md. WEMD 1490 E. St. Louis, Ill. WBBR 1490 AEaston, Md. WEMD 1490 Easton, Md. WEMD 1490 Eas	Danashuan Tar-	WTIK 1310 A	Evanston, III.	WEAW 1330	Ft. Valley, Ga.	KFST 860 WFPM 1150	Glenville, Ga. Glenwood Sprgs., Co	WKIG 1580
Eagle Play, Very Wert 1950 Easley, S.C. WERL 1950 E. Grand Forks, Min. RAD 1990 E. Grand Forks, Min. KERC 1950 E. Grand Forks, Min. KERC 1950 E. Liverpool, Ohio WOH1 1490 East Longmeadew, Mass. Eastman, Ga. WTYM 1800 E. St. Louis, Ill. WBBR 1490 E. St. Louis, Ill. WBBR 1490 Easton, Md. WEMD 14		WTRO 1330	Evansten, Wye.	WNMP 1590 KLUK 1240	rt. Walten Beach,	FIA. WNUE 950	Globe, Ariz.	KGLN 960 M
Eastland, Tex, KRAD 1990 E. Lansing, Mich. WKAR 870 E. Liverpool, Ohio WOH1 1490 East Longmeadow, Mass. WTYM 1800 E. Point, Ga. E. Point, Ga. E. Point, Ga. E. Point, Ga. Easton, Pa. WEMD 1490 Easton, Pa. WEST 1400 Easton, Pa. WEST 1400 Easton, Pa. WEST 1400 Easton, Pa. WEST 1400 Easton, WHTG 1410 Easton, WHTG 1410 Easton, Pa. WEST 1400 Easton, Pa. WE	Eagle River, Wis.	WERL 950	Evansville, 1nd.	WRDZ 1400 C WGBF 1280 N	Ft. Wayne, Ind.	WGL 1250 A	Gloucester, Va. V	VDDY 1420 1. N.Y.
Eastland, Tox. KPAR 1390 E. Lansins, Mich. WKAR 870 E. Liverpool, Ohio WOH 1490 East Longmeadow, Mass. WPFE 1380 E. Moline, Ill. WDLM 360 E. Point, Ga. WTIM 1280 E. St. Louis, Ill. WBR 1490 Easten, Ma. WEMD 1490 Easten, Ma. WEMD 1490 Easten, Ma. WEMD 1490 Easten, Pa. WEST 1400 Easten, Pa. WEST 1400 Easten, Pa. WEST 1400 East Longmeadow, WEST 1400 East Louis, Ill. WBR 1460 Easten, Pa. WEST 1400 East Louis, Ill. WBR 1460 East Louis, Ill. WBR 1460 Easten, Pa. WEST 1400 East Louis, Ill. WBR 1460 Easten, Pa. WEST 1400 East Louis, Ill. WHITE 1400 East Louis, Ill. WBR 1460 East Louis,	E. Grand Forks, N	linn.		WJPS 1330 A I		WOWO 1190 WANE 1450 C	Gold Beach, Ores.	WENT 1340 C KBLY 1220
E. Linsring, Mich. WKAR 870 E. Liverpool, Ohio WOHI 1490 East Longmeadew, Mass. WTYM 1600 E. St. Louis, III., WDLM 960 E. St. Louis, III., WBBR 1490 Easton, Md. WEMD 1460 Easton, Pa. WEEX 1230 WEST 1400 Eatontown, N.J., WHT 1010 Eau Claire, Wis. WBL 1400 Eau Galille, Fia. Education, N.C., WBLD 1800 Eau Galille, Fia. Education, N.C. WBLD 1800 Edmonds, Wash. CEM 630 Edmonds, Wash. KCR 710 Edmonds, Wash. CEM 710 Edmonds, Wash. CEM 1200 ECM 710 Edmonds, Wash. CEM 720 Edmonds, Wash. CEM 740 Edmonds, Wash.		KERC 1590	Eveleth, Minn.	WEVE 1340 M KR.(0 1380	Ft. William, Dnt.	CKPR 580 I	Golden, Colo.	KICM 1250
East Longmeadew, Mass. WTYM 1800 Eastman, Ga. E. Meline, Iii. WDLM 960 E. Moline, Iii. WBBR 1890 E. St. Louis, Iii. WBBR 1890 Easten, Md. Easten, Pa. WEEM 1400 Easten, Nd. Eau Claire, Wis. Eau Claire, Wis. Eau Claire, Wis. Eau Gallie, Fia. Ebensburg, Pa. Edenton, N.C. Edenton, I.E. Earles, Va. Edenton, I.E. Edibero, Va. Edenton, Va. Edenton, Va. Edenton, Va. Edenton, Va. Edent	E. Liverpool, Ohio	WOH! 1490 A	Evergreen, Ala.	KWYZ 1230		CJLX 800		KEVE 1440 M
Eastman, Ga. E. Meline, Iii. WDLM 960 E. Point, Ga. WDLM 1250 E. St. Louis, III. WBBR 1490 A Easten, Pa. WEEX 1230 W	East Longmondow,	Mass, WTYM 1600	Fairbanks, Alaska			KCUL 1540	Geldsboro, N.C. \	WFMC 730
E. Point, Ga. E. St. Louis, III. E. St. Louis, III. WBBR I490 Easton, Md. Easton, Pa. Eatontown, N.J., Eau Claire, Wis, WEZY 1400 WBTJ 1	E. Moline, III.	WPFE 1580 WDLM 960	1	KFRB 900 C-A		KNOK 970	٧	WGOL 1800
Easton, Md. WEMD 1460 WEMD 1460 WEMD 1460 WEEX 1230 Wast 1400 Wast 1	E. Point. Ga.	WTJH 1260	Fairfax, Va.	WEEL 1310		WBAP 820 N	Goodland, Kans.	KLOE 730 M
East Claire, WIs. East Claire, WIs. WHAQ 790 East Claire, WIS. WHAQ 790 East Claire, WIS. WHAQ 790 East Claire, WIS. WHAD 790 East Claire, WIS. WHAQ 790 East Claire, WIS. WHAD 180 Fairment, W.C. WHAD 180 WHAD 180 Fairment, W.C. WHAD 180 WHAD 180 Fowler, Calif. WHAD 180 Fairment, W.C. WHAD 180 Fowler, Calif. WHAD 180 Fowler, Cali	Easton, Md.	WEMD 1460	Fairfield, Iewa	KMCD 1570	Fostoria, Ohio	WFDB 1430	Goshen, Ind. W	KAM 1460
WBIZ 1400 M WECL 1050 Eau Gaille, Fla. WMEG 920 Ebensburg, Pa. WCDJ 1580 Edenton, N.C. Edinburg, Tat. KGDN 630 Edmonton, Alta. Edmonton, Alta. Edmonton, Alta. CERN 1260 CHED 630 CHED 630 CHEA 680 WBIZ 1400 M WCDJ 1600 WGCJ 1490 A Fajardo, P.R. WMBD 1480 WFCS 1490 A WTCS 1490 A Fajardo, P.R. WFS 1600 WFCS 1490 A WTCS 1490 A Famingham, Mass, WKOX 1190 Framingham, Mass, WKOX 1190 Framkfort, Ind. WILD 1570 Frankfort, Ky. WFKY 1490 M Frankfort, Ind. WFKN 1220 Frankfort, Ky. WFKN 1220 Frankfort, Ind. WFRN 1370 KTLD 1440 C KNOX 1310 M Franklin, N.C. WFSC 1050 Franklin, Pa. WFRA 1430 Franklin, Toms. WAGG 950 CHED 630 CHED 630 CHEF 1450 WTCS 1490 A WTCS 1360 Franklin, La. KFRA 1390 Franklin, N.C. WFSC 1050 Franklin, Pa. WFRA 1430 Franklin, Toms. WAGG 950 KFGQ 790 A Franklin, Va. WYSR 1250 WHITE'S RADIO LOG 171		WEST 1400 N	Fairmont, Minn.	KSUM 1370 M	. Juniarin Orty, 181	WFCT 1430	Grafton, W.Va. W	VVW 1260
Eau Gaille, Fla. WHEG 920 Ebenaburg, Pa. Edmonton, N.C. Edinburg, Tox. Edmonton, Alta. CEXA 740 CFRN 1260 CHED 630 CHFA 680 CHFA 680 CHED 630 CHFA 630 CHFA 630 CHED 630 CHFA 630 CHED 630 CHFA		WEAQ 790 N	Fairmont, W.Va.	WMMN 920 C	Fountain Inn. S.C.	WF18 1600	Granby, Que. (CHEF 1450
Ebensburg, Pa. WEND 1580 Edenton, N.C. WCDJ 1580 Edenton, N.C. WCDJ 1580 Edinburg, Tex. KUDN 490 MSAR 1480 A Falls Church, Va. WFAX 1220 KTNC 1230 CRAN 740 CFRN 1260 CHED 630 CHFA 680 CHEA 680	Fau Gallia Sta	WECL 1050	Falardo, P.R.	WMDD 1480	Framingham, Mass	.WKQX 1190	Grande Prairie, Alta.	CFGP 1050
Edinburg, Tex. Edinburg, Tex. KIRV 710 Edinburg, Tex. KIRV 710 Edmonds, Wash. KIRV 710 Edmonds, Wash. CEXA 740 CFRN 1260 CFRN 1260 CFRN 1260 CHED 630 CHFA 680 CHFA 6	Ebensburg, Pa,	WEND 1580	Fall River, Mass,	WALE 1400 M	Frankfort, Ky.		urang Falls, Nfld. Grand Forks, N.D. I	KFJM 1370
CHAN 1260 CHED 630 CHFA 680 CH	Edinburg, Tex.	KURV 710	Falls Church, Va.	WFAX 1220	Franklin, Ky.	WFKN 1220	к	NOX 1310 M
CHED 630 KFRW 900 Franklin, Tens. WAGG 950 CHFA 680 KFGQ 790 A Franklin, Va. WYSR 1250 WHITE'S RADIO LOG 171	Edmonton, Alte.		Farge, N. Oak.	WDAY 970 N	Franklin, N.C.	WFSC 1050	Grand Haven, Mich	
CHFA 680 1 KFGO 790 A! Franklin, Va. WYSR 1250 WHITE'S RADIO LOG 171		CHED 630		KUTT 1550	Franklin, Tenn.	WAGG 950		
				Krug /90 A	rranklin, Va.	WY8R (250	WHITE'S RADIO	LOG 171

· .

Location C.L. Kc. N.A.		l	
Grand Island, Nebr. KMMJ 750 A	Harrisburg, III. WEBQ 1240 Harrisburg, Pa. WHGB 1400 A	Houghton Lake, Mich. WHGR 1290	Jasper, Ala, WWWB 1360 WARF 1240
Grand Junction, Colo.	WCMB 1460 M WHP 580 C	Houlton, Maine WHOU 1340 Houma, La, KCIL 1490 N	Jasper, Ind. WITZ 990 Jasper, Tex. KTXJ 1350
KREX 920 C KEXO 1230 A	Harrison, Ark. WKBO 1230 N KHOZ 900	Houston, Miss. WCPC 1320 Houston, Mo. KHTN 1250	Jefferson City, Mo. KLIK 950 KWOS 1240 M
KSTR 620 KWSL 1340	Harrisonburg, Va. WHBG 1360 WSVA 550 N	Houston, Tex. KCOH 1430 KILT 610	Jefferson City, Tenn. WJFC 1480
Grand Prairie, Tex. KPCW 730	Harrodsburg, Ky, WH BN 1420	KNUŽ 1230 KOOA 1010	Jeffersonville, Ind. WXVW 250 Jena, La. KCKW 1480
Grand Rapids, Mich. WJEF 1230 C	Hartford, Conn. WORC 1360 C WCCC 1290 M WPOP 1410 M-A	KPRC 950 N KTHT 790	Jennings, La. KJEF 1290
WFUR 1570	WTIC 1080 N Hartford, Wis, WTKM 1540	KTRH 740 C	Jerseyville, III. WJBM 1480
WGRD 1410 WLAV 1340 A	Hartselle, Ala. WHRT 860	KYOK 1590	Jesup, Ga. WBGR 1370 Johnson City, Tena. WJCW 910 C
WMAX 1480 M WOOD 1300 N	Hartweil, Ga, WKLY 980	Hudson, N.Y. WHUC 1230	WETB 790 M
Grand Rapids, Minn. KOZY 1490 M	Harvey, III. WBEE 1570	Hugo, Okia, KIHN 1340 Hull, Que, CKCH 970 Humacao, P.R. WALO 1240	Johnstown, N.Y. WIZR 930
Grangeville, Idaho KORT 1230 Granite City, III. WGNU 920	Hastings, Nebr. KHAS 1280	MUMDOIAT, IONN, WIKJ /40	WARD 1490 C
Grants, N. Mex. KMIN 980 Grants Pass, Oreg. KAGI 930 M	Hattiesburg, Miss. WBKH 950 WFOR 1400 N WHSY 1230 A	Huntingdon, Pa. WHUN 1150 Huntington, Ind. WHLT 1300	Joliet, III. WJOL 1340
Gravelbourg, Sask. CFGR 1230	WXXX 1810	Huntington, N.Y. WGSM 740 Huntington, W.Va. WKEE 800 M-A	Jollette, Que. CJLM 1350 Jonesboro, Ark, KBTM 1230 M
Grayson, Ky. WGOH 1370	Haveleck, N.C. WUSM 1330 Haverhill, Mass, WHAV 1490 Havre, Ment. KOJM 610 M	WSAZ 930 N WWHY 1470 M	KNEA 970
Gt, Barrington, Mass. WSBS 860 Gt. Bend. Kans. KVGB 1590 N	Havre de Grace. Md. WASA 1330	Huntsville, Ala. WBHP 1230 M WEUP 1600	Jonesboro, Tenn. WJSO 1590
Gt. Bend. Kans. KVGB 1590 N Gt. Falls, Mont. KFBB 1310 C KUDI 1450	Hawkinsville, Ga. WCEH 610 Haynesville, La, KLUV 1580	WFIX 1450 WAAY 1550 A	Jonquiere, Que. CKRS 590
KMON 560 M KARR 1400 N	Hays, Kans, KAYS 1400 Hayward, Wis, WHSM 910	Huntsville, Ont. CKAR 630 Huntsville, Tex. KSAM 1490	Joplin, Mo, WMBH 1450 M KQYX 1560 KFSB 1310
Greeley, Colo, KFKA 1310 KYOU 1450	Hazard, Ky. WKIC 1390 M Hazelhurst, Ga. WVOH 920 O	Huron, S.Dak, KIJV 1340 Hutchinson, Kans, KWBW 1450 N	Junetion, Tex. KMBL 1450
Green Bay, WIs. WBAY 1360 C WJPG 1440 M	Haziehurst, Miss. WMDC 1220 Hazieton, Pa. WAZL 1490 N-M	KWHK 1260	June, City, Kans. KJCK 1420 Juneau, Alaska KINY 800 C-A
WOUZ 1400 A Greeneville, Tenn. WGRV 1340	W [H I 1300	Hutchinson, Minn. KDUZ 1260 Idabel, Okla, KBEL 1240 Idaho Falis, Idaho KID 590 C	KJNO 630 A-M-N Kailua, Hawall KLEI 1130
Greenfield, Mass. WHAI 1240 M	Helena, Ark, Helena, Mont, KCAP 1340 M KBLL 1240 N	KIFI 1260 A-M	Kaimuki, Hawali KAIM 870
Greensboro, N.C. WBIG 1470 C	Hemet, Calif. KHSJ 1320 Hempstead, N.Y. WHLI 1100	Independence, Ia. KUPI 980 KOUR 1220	Kalamazoe, Mich. WKPR 1420 WKZO 590 C WKLZ 1470 M
WGBG 1400 A	Henderson, Ky, WSON 860 Henderson, Nev. KBM1 1400	Independence, Kans, KIND 1010 M	WKMI 1360 WKMI 1360 M
Greensburg, Pa. WHJB 620	Henderson, N.C. WHNC 890 M	Independence, Mo. KANS 1510	KOFI 930 Kamloops, B.C. CFJC 910
Greenville, Ala. WGYV 1380 Greenville, Mich. WPLB 1380 Greenville, Miss, WJPR 1330	WIZS 1450 Henderson, Tex. KGRI 1000	Indiana, Pa. WDAD 1450 C Indianapolis, Ind. WFBM 1260 A	Kane, Pa. WADP 960 Kankakee, III. WKAN 1320
WDDT 900 WGVM 1260	KWRD 1470 Hendersonville, N.C.	WGEE 1590	Kannapolis, N.C. WGTL 870 WRKB 1460
Greenville, Pa. WGRP 940 Greenville, N.C. WGTC 1590 M	WHKP 1450 A	WIRE 1430 N WISH 1310 C	Kans, City, Kans, KCKN 1340 Kansas City, Me. KCMO 810 C
Greenville, S.C. WESC 660	Henryetta, Okla, KHEN 1590 Hereford, Tex. KPAN 860 Herkimer, N.Y. WALY 1420	Indianola, Miss. WXLW 950 M	KM BC 980 A KPRS 1590
WFBC 1330 N WMRB 1490 C-M	Hermisten, Ores. KOHU 1570 Herrin, III. WJPF 1340 M	I Indian Posts Bassh Ela	KÜDL 1886 WDAF 610 N
WMUU 1260 WQOK 1440 C	Hettinger, N.Dak, KNDC 1490 Hibbing, Minn. WMFG 1240 N	Indio, Calif. KREO 1400 A	WHB 710 Kearney, Nebr. KGFW 1346 M
Greenville, Tex. KGVL 1400 Greenwood, Miss. WABG 960 A	Hickory, N.C. WHKY 1290 A WIRC 680	Inkster, Mich. WCHB 1440 International Falls, Minn.	KRNY 1460 Keene, N.H. WKNE 1290 N
Greenwood, S.C. WCRS 1450 N	Highland Park, III. WNSH 1430	Invrik. N.W.T. CHAK 860	WKBK 1220 Kelewna, B.C. CKOV 630
Greer, S.C. WEAB 800	Highland Park, Tex. KVIL 1150 Highland Springs, Va.	Iola, Kansas KALN 1370 Ionia, Mich. WION 1430	Kelse, Wash. KLOG 1490 Kendaliville, Ind. WAWK 1570
Grenada, Miss. WNAG 1400 M	WENZ 1450 High Point, N.C. WMFR 1230	laws City laws WYIC 800	Kenedy, Tex. KAML 990 Kennett, Mo. KBOA 830
Gresham, Oreg. KGRO 1230 Gretna, Va. WMNA 730	WNOS 1590 WHPE 1070	Iowa Falls, Iowa KFIG 1510 Iron Mtn., Mich. WMIQ 1450 A	Kennewick-Pasco-Richland, Wash, KEPR 610 C
Griffin, Ga. WKEU 1450 M WHIE 1320	Hillsbore, Ohie WSRW 1590 Hillsbore, Oreg. KUIK 1360 Hillsbore, Tex. KHBR 1560	Iron River, Mich. WIKB 1230 M Irondale, Ala, WIXI 1480	Kenera, Ont. CJRL 1220 Kenesha, Wis. WLIP 1050
Grinnell, Iowa KGRN 1410 Groton, Conn. WSUB 980	Hillsboro, Tex. KHBR 1560 Hillsdale, Mich. WCSR 1340 Hillsville, Va. WHHV 1400	Ironton, Ohio WIRO 1230 M	Kentville, N.S. CKEN 1350 Keckuk, Iewa KOKX 1310 Kermit, Tex. KERB 600
Grove City, Pa. WSAJ 1340	Hilo, Hawaii KHBC 970 (l Irvine, Ky. WIRV 1550 I Isabella, P.R. WISA 1390	Kerrville, Tex. KERV 1230
Guayama, P.R. WXRF 1590	Hinesville, Ga. KGML 990	WIAM 9/0	Kershaw, S.C. WKSC 1300 Ketchikan, Alaska KTKN 930 C-A
Guelph, Ont. CJOY 1460 Gulfport, Miss. WROA 1390 WGCM 1240 A	Hebart, Okla. KTJS 1420 Hobbs, N.Mex. KWEW 1480 N	Islip, N.Y. WBIC 540 Ithaca, N.Y. WHCU 870 C	Kewanee, III, WKE1 1450 Keyser, W.Va, WKYR 1270 M Key West, Fla. WKWF 1600 A-M
Gunnison, Colo. KGUC 1490 Guntersville, Ala. WGSV 1270	Holbrook, Ariz. KDJI 1270	luka, Miss. WVOM 1270	W K I Z 1500
Guthrie, Okla. KWRW 1490 Guymon, Okla. KGYN 1220	Holdredge, Nebr. KUVR 1380 Holland, Mich. WHTC 1450	Jackson, Mich, WIBM 1450 A	Killeen Tex. KLEN 1050 M Kimball, Nebr. KIMB 1260
Hagerstown, Md. WARK 1490 C WJEJ 1240 A-M	Hallister, Calif. KGHT 1520	WKHM 970 M WAST 1510 Jackson, Miss. WJDX 620 N	King City, Calif. KRKC 1570 Kingman, Ariz. KAAA 1230 A
Haines City, Fla. WHAN 930 Halevville, Ala. WJBB 1230 M	Hollywood, Fla. WGMA 1320 Holly Hill, S.C. WHHL 1440	Jackson, Miss. WJDX 620 N WJQS 1400 M WJXN 1450	Kings Mountain, N.C. WKMT 1220
Halifax, N.S. CBH 790	Holyoke, Mass. WKEB 930 Homer, La. KHAL 1320	WOKJ 1590 WRBC 1300 M	Kingsport, Tenn. WKIN 1320 WKPT 1550 N
CHNS 960 CJCH 920	Homestead, Fla. WSDB 1430 Homewood, Ala, WJLD 1400	WSLI 980	Kingston, N.Y. WBAZ 1550 M
Hamden, Conn. WDEE 1220 Hamilton, Ala. WERH 970	KZ00 1210	Jackson, Tenn. WDX1 1810 WJAK 1460	WGHQ 920 WKNY 1490 C Kingston, Ont. CFRC 1490
Hamilton, Mont, KYLQ 980 Hamilton, Ohio WMOH 1450	KHAI 1090 KPOI 1380	WTJS 1390 A	CKLC 1380 CKWS 960
CHML 900	KiKi 830 KGU 760	WAPE 690 WZOK 1320 A-M	Kingstree, S.C. WDKD 1310 Kingsville Tex. KINE 1330
Hamilton, Tex. KCLW 900	KHVH 1040 KORL 650 (M WIVY 1050 WMBR 1460 C	Kinston, N.C. WELS 1010
Hamlet, N.C. WKDX 1400 Hammond, Ind. WJOB 1230	KNOI 1270 KOHO 1170	WOBS 1360 WPDQ 600	Kirkland, Wash, KCD1 1460
Hammonton, N.J. WNJH 1580	KTRG 990 KULA 690	WQIK 1280 WRHC 1400	KNRX 1050
Hampton, S.C. WBHC 1270 Hampton, Va. WVEC 1490 Hancock, Mich. WMPL 920	Hoed River, Oreg. KIHR 1340 Heps. Ark. KXAR 1490 Hepswell, Va. WHAP 1340	WLDS 1180	Kirkland Lake, Ont. CJKL 560 Kirksville, Mo. KIRX 1450 A Kissimmee, Fla. WKBX 1220
Hanford, Calif. KNGS 620	Hopkinsville, Ky. WHOP 1230 WKOA 1480	C Jacksonville, N.C. WINC 1240 M WLAS 910	CKKW 1320
Manover, N.H. WISLISU	Hoquiam, Wash, KHOK 1560 Hornell, N.Y. WWHG 1320	Jacksonville, Tex, KEBE 1400	Kittanning, Pa. WACB 1380 Klamath Falls, Ores. KAGO 1150 M KF1 W 1450 A-C
WDCR 1340 Hanover, Pa. WHVR 1280 Harlan, Ky. WHLN 1410	WLEA 1480 Hot Springs, Ark, KAAB 1340	WZRO 1010 WZRO 1400 W	
Harlan, Ky. WHLN 1410 Harlingen, Tex. KG BT 1530 Harriman, Tenn. WHBT 1600	KBHS 590 KZNG 1470	KSJB 600 C	
	Hot Springs, S. Dak. KOBH 560 Houghton, Mich. WHDF 1400	Jamestown, Tenn, WCLC 1260	WIVK 860
172 WHITE'S RADIO LOG	Houghton, Mich. WHDF 1400	I janesvijie, Wis. WCLO 1230 M	II WATE 620 N

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Lecation	C.L. Kc. N.A.
	WKGN 1340 M	Leonardtown, Md.	WK1K 1370		KFY0 790 C		WPRA 990
	WKXV 900 M WNOX 990 C	Leihbridge, Alta.	CJOC 1220 CHEC 1090		KLLL 1460 M KSEL 950 A	Mayfield, Ky,	WTIL 1300 WNGO 1320
Kodiak, Alaska	WCVQ 960	Levelland, Tex.	KLVT 1230	Lucedale, Miss.	WHHT 1440	Mayodan, N.C.	WMYN 1420
Kokomo, Ind. Kosciusko, Miss.	W10U 1350 C WKOZ 1350 A	Levittown, Pa. Lewisburg, Pa.	WBCB 1490 WUNS 1010	Ludington, Mich.	KRBA 1340 A	Maysville, Ky. McAlester, Okla.	WFTM 1240 M KTMC 1400
Laconia, N.H.	WLNH 1350 WEMJ 1490	Lewisburg, Tenn. Lewiston, Idaho	WJJM 1490 M KRLC 1350 M	Lumberton, N.C.	KTRE 1420 M WAGR 580	McAllen, Tex.	KNED 1150 KRIO 910 M
LaCresse, Wis.	WKBH 1410 N	1	KOZE 1300		WTSB 1340 M	McCamey, Tex.	KAMY 1450
	WLCX 1490 WKTY 580 A	Lewiston, Maine	WCOU 1240 M WLAM 1470 A	Luray, Va.	WRLA 1590 WRAA 1330	McComb, Miss.	WHNY 1250 A WAPF 980
Ladysmith, Wis.	WLDY 1340 WLFA 1590	Lewistown, Mont.	KXLD 1230 M	Lynchburg, Va.	WLVA 590 A	McCook, Nebr.	KBRL 1300 M
Lafayette, Ga. Lafayette, Ind.	WASK 1450 M WAZY 1410	Lewistown, Pa.	WKVA 920 A WMRF 1490 N		WDMS 1320 WWOO 1390 M	McGehee, Ark,	KWRV 1360 KVSA 1220
	WAZY 1410 WBAA 920	Lexington, Ky.	WLAP 630 M	Lynn, Mass.	WBRG 1050 WLYN 1360	Mc Keesport, Pa.	WEDO 810 C WPQR 1360 M
Lafayette, La.	KPEL 1420 A		WBLG 1300 A WVLK 590 C	Lyons, Ga.	WBBT 1340	McKenzie, Tenn.	WHDM 1440
	KVOL 1330 N KXKW 1520	Lexington, Miss. Lexington, Mo.	WXTN 1150 'KLEX 1570	Macomb, III. Macon, Ga,	WKAI 1510 WBML 1240	McKinney, Tex. McMinnville, Ores	KMAE 1800 KMCM 1260
Lafayette, Tenn. LaFollette, Tenn.	WEEN 1460 WLAF 1450	Lexington, Nebr.	KRVN 1010		WCRY 900	McMinnville, Tenn	WBMC 960 WAKI 1230 M
LaGrande, Oreg.	KLBM 1450	Lexington, N.C.	WBUY 1440 WDXL 1490		WIBB 1280 WMAZ 940 C	McPherson, Kans.	KNEX 1540
LaGrange, Ga.	WLAG 1240 M WTRP 620	Lexington, Va. Lexington Pk., Md	WREL 1450 N	Macon, Miss.	WNEX 1400 A-M WMBC 1400	McRae, Ga. Mead, Wash.	WDAX 1410 KLFF 1590
LaGrange, III.	WTAQ 1300 KVLG 1570	Libby, Ment,	KLCB 1230 M	Madera, Cailf.	KHOT 1250	Meadville, Pa.	WMGW 1490
LaGrange, Tex. Lajunta, Colo.	KBZZ 1400 M	Liberal, Kans.	KLIB 1470 KSCB 1270	Madill, Okla. Madison, F'a,	KMAD 1550 WMAF 1280	Medford, Mass. Medford, Oreg,	WHIL 1430 KMED 1440 A
Lake Charles, La.	KLOU 1580 KPLC 1470 N	Liberty, N.Y.	W V O S 1240	Madison, Ga.	WYTH 1250		KMFR 860 KDOV 1300
1-1-024-01	KAOK 1400 M	Liberty, Tex, Lihue, Hawaii	KWLD 1050 KTOH 1490	Madison, Ind. Madison, S.D.	WORX 1270 KJAM 1390		KBOY 730
Lake City, Fla.	WDSR 1340 WGRO 960	Lima, Ohio	WIMA 1150 A WPRC 1370	Madison, Tenn. Madison, Wis.	WENO 1430 WHA 970	Medford, Wis.	KYJC 1230 A-C WIGM 1490 M
Lake City, S.C. Lakeland, Fla.	WJOT 1260 WLAK 1430 N	Lincoln, III. Lincoln, Nebr.	KFOR 1240 A		WIBA 1310 N	Medicine Hat, Alt	a. CHAT 1270
Eskeland, Fis.	WONN 1230 M		KLIN 1400 KLMS 1480		WISM 1480 A-M WKOW 1070 C	Media, Pa. Melbourne, Fla.	WXUR 690 WMMB 1240 M
Lake Placid, N.Y	WYSE 1330 . WIRD 920	Lincolnton, N.C.	WLON 1050	Madisonvilla, Ky,	WFMW 730	Memphis, Tenn.	WHBQ 560 M WHER 1430
Lake Providence, I	.a. KLPL 1050	Lindsay, Dnt. Linton, Ind.	CKLY 910 WBTO 1600	Magee, Miss.	WTTL 1310 WSJC 790		WMC 790 N
Lake Tahoe, Calif. Lakeview, Dreg.	KQ1K 1230	Litchfield, III. Litchfield, Minn.	WSMI 1540	Magnolia, Ark. Makawao, Mawaii	KVMA 630 M		WDIA 1070 WMPS 680
Lake Wales, Fla	. WIPC 1280 KLAK 1600	Little Falls, Minn.	KLFD 1410 KLTF 960	Malden, Me.	KTCB 1470		WHHM 1340 A
Lakewood, Colo. Lakewood, Wash.	KFHA 1480	Little Falls, N.Y. Littlefield, Tex.	WLFH 1280 KZZN 1490	Malone, N.Y. Malvern, Ark.	WICY 1490 M KBOK 1310		W L O K 1480 W R E C 600 C
Lake Worth, Fla. Lamar, Colo.	WLIZ 1380 KLMR 920 M	Little Rock, Ark.	KARK 920 N	Manassas, Va.	WPRW 1460	Mena, Ark,	KWAM 990 KENA 1450
Lamesa, Tex. Lampasas, Tex.	KPET 690 KCYL 1450		KAJI 1250 M KLRA 1010 A	Manati, P.R. Manchester, Conn	. WMNT 1500 . WINF 1230 C	Menominee, Mich.	WAGN 1340 A
Lancaster, Calif.	KAVL 610	١.	KLRA 1010 A KOKY 1440 (AAY 1090 C-M	Manchester, Ga, Manchester, Ky.	WFDR 1370 WWXL 1450	Menomonie, Wis, Merced, Calif.	WMNE 1360 KYOS 1480 M
Lancaster, Ohio	KBVM 1380 WHOK 1320		KVLC 1050	Manchester, N.H.	WFEA 1370 M	Meriden, Conn.	KWIP 1580 WMMW 1470
Lancaster, Pa.	WGAL 1490 N	Littleton, Colo. Live Oak, Fla.	KMOR 1510 WNER 1250		WGIR 610 C WKBR 1250	Meridian, Miss,	WCOC 910 C
Lancaster, S.C.	WLAN 1390 A-M WLCM 1360	Livingston, Mont.	KPRK 1340 M	Manchester, Tenn. Manhattan, Kans.	. WMSR 1320 KSAC 580		WDAL 1330 M WMOX 1010
Lander, Wyo. Lanett, Ala.	KOVE 1330 M WRLD 1490 A	Livingston, Tenn, Livingston, Tex,	WLIV 920 KETX 1440 KVLL 1220		KMAN 1350		WOKK 1450 A WQIC 1390
Langley Prairie, B	· C	Lloydminster, Alta.	KVLL 1220	Manistee, Mich. Manitou Springs,	WMTE 1340 Colo.	Merrill, Wis.	WXMT 730
Lansdale, Pa.	CJJC 1000 WNPV 1440	Lock Haven, Pa.	WBPZ 1230 M	Manitowee, Wis.	KCMS 1490 WCUB 980	Mesa, Ariz. Mesa, Ariz.	KBUZ 1310 KALF 1510
Lansford, Pa. Lansing, Mich.	WLSH 1410 WILS 1320	Lockport, N.Y. Lodi, Calif.	WUSJ 1340 KCVR 1570		WOMT 1240 M	Metropolis, III, Metter, Ga.	WMOK 920 WMAC 1360
Lansing, mich.	WJIM 1240 A-N	Logan, Utah	KVNU 610 M KSTU 1300	Mankato, Minn.	KYSM 1230 N KTOE 1420 A	Mexia, Tex.	KBUS 1590
Lapser, Mich.	WMRT 1010 WMPC 1230	l	KLGN 1390	Manning, S.C.	WYMB 1410 KDBC 1360	Mexico, Mo. Mexico, Pa.	KXED 1340 M WJUN 1220
LaPorte, Ind.	WTHM 1530 WLOI 1540	Logan, W.Va,	WLDG 1230 M WVOW 1290	Manning, S.C. Mansfield, La. Mansfield, Ohio	WMAN 1400 A	Miami, Ariz. Miami, Fla.	KIKO 1340 WGBS 710 C
Laramie, Wyo,	KLME 1490	Logansport, Ind.	WSAL 1230 M KKOK 1410	Maqueketa, Jowa	WCLW 1570 KMAQ 1320	miami, rja.	WCKR 610 N
Laredo, Tex.	KOWB 1290 M KGNS 1300	Lompec, Calif.	KLPC 1330 D	Marathon, Fla. Marianna, Ark.	KMAQ 1320 WEFG 1300 KZOT 1460		WFAB 990 WMBM 1220
	KVOZ 1490 M	London, Ky,	KNEZ 960 WFTG 1400	Marianna, Fia.	WTYS 1340 M		WAME 1260 A WM1E 1140
LaSalle, III. LaSarre, Que.	WLP0 1220 CKLS 1240	London, Ont.	CFPL 980	Marietta, Ga.	WTOT 980 WFDM 1230		WQAM 580
Las Cruces, N.Mex.	KOBE 1450 KGRT 570	Long Beach, Caiif.	CKSL 1290 KFOX 1280	Marietta, Chio	WBIE 1050		WSKR 1450 WINZ 940 M
Las Vegas, Nev.	KEND 1460 A	Longmont, Colo.	KGER 1390 KLMD 1050	Marine City, Mist	. WDOG 1590 '	Miami, Okla, Miami Beach, Fla	KGLC 910
	KORK 1340 M	Long Prairie, Minn	. KEYL 1400	Marinette, Wis. Marien, Ala.	WMAM 570 N WJAM 1310	miami Death, Fiz	WMBM 1490
	KRAM 920 KLUC 1050	Longview, Tex.	KFRD 1370 A KLUE 1280	Marion, III. Marion, ind.	WGGH 1150 WBAT 1400 A		WKAT 1360 C WFUN 790
Les Veens N Mey	KVEC 070	Longview, Wash.	KEDO 1400 A KBAM 1270		WMRI 860	Michigan City, Ind Middleport-Pomroy	. WIMS 1420
Las Vegas, N.Mex. Latrobe, Pa.	WPKV 1570 M	Lookout Mtn., Tenn	. WFLI 1070	Marion, N.C. Marion, Ohio	WBRM 1250 WMRN 1490 A	Ohio	WMPD 1390
LaTuque, Que,	WTRA 1480 CFLM 1240	Lorain, Ohio Lordsburg, N.Mex.	WWIZ 1380 A KLHS 950	Marien, S.C. Marien, Va.	WATP 1480 WMEV 1010 A	Middlesboro, Ky. Middletown, Conn.	WMIK 560 WCNX 1150
Laurel, Miss.	WAML 1340 N	Loris, S.C. Los Alamos, N.Mex.	WLSC 1570 KRSN 1490 A	Marion, Va.	WOLD 133	Middletown, N.Y. Middletown, Ohio	WALL 1340 WPFB 910
1	WLAU 1600 A WNSL 1260	Los Angeles, Calif.	KABC 790 A	Marked Tree, Ark Marksville, La	KAPB 1370	Midland, Mich.	WMDN 1490
Laurens, S.C. Laurinburg, N.C.	WLBG 860 WEWO 1080		KHJ 930 M	Mariborough, Mas Marquette, Mich.	s. WSRO 1470 WDMJ 1320 M	Midland, Ont. Midland, Tex.	CKMP 1230 KCRS 550 A
Lawrence, Kans.	WLCW 1300 KFKU 1250		KFSG 1150 KFWB 980	Marshall, Minn.	KMHL 1400 A		KJBC 1150 KWEL 1600
	KLWN 1320		KGFJ 1230 KFAC 1330	Marshall, Mo. Marshall, N.C.	KMMO 1300 WMMH 1460	Milan, Tenn. Miles City, Mont.	W K B J 1600
Lawrence, Mass. Lawrenceburg, Ten	WCCM 800 M n. WDXE 1370		KLAC 570]	Marshali, Tex.	KMHT 1450 KADO 1410	Militord, Del.	KATL 1340 M WKSB 930
Lawrenceville, Ga.	WLAW 1360 WAKO 910		KMPC 710 KNX 1070 C	Marshalltown, low	a KFJB 1280	Milford, Mass, Milledgeville, Ga,	WMRC 1490 WMVG 1450 M
Lawrenceville, III. Lawrenceville, Va.	WLES 580		KPOL 1540	Marshfield, Wis, Martin, Tenn.	WDLB 1450 WCMT 1410	Millen, Ga.	WGSR 1570
Lawton, Okla.	KSW0 1380 A KCCO 1050		KGBS 1020 KRKD 1150	Martinsburg, W.V Martinsville, Va.	a, WEPM 1340 WHEE 1370	Millington, Tenn.	WGMM 1380
Leadville, Colo. Leaksville, N.C.	KBRR 1230 WLOE 1490 M	Los Banos, Calif. Louisburg, N.C.	KLBS 1330 WYRN 1480	Marystown, Nfld. (WMVA 1450 N	Miliville, N.J. Milton, Fla.	WMVB 1440 WEBY 1330 M
Leamington, Ont.	CJSP 710	Louisville, Ga.	WPEH 1420		CHCM 560	·-	WSRA 1490
Leavenworth, Kans Lebanon, Ky.	WLBN 1590	Louisville, Ky.	WAVE 970 N WAKY 790 M	Marysville, Caiif. Marysville, Kans,	KMYC 1410 M KNDY 1570	Milton, Pa.	WMLP 1570 WARC 1380
Lebanon, Mo.	KLWT 1230 KGAL 920		WHAS 840 C WKLO 1080 A	Maryville, Me. Maryville, Tenn,	KNIM 1580	Milwaukee, Wis.	WEMP 1250 WFOX 860 M
Lebanon, Oreg. Lebanon, Pa.	WLBR 1270		WINN 1240 WKYW 900 C	Mason City, Iowa	WGAP 1400 KGLO 1300 C		WRIT 1340
Lebanon, Tenn. Leesburg, Fla.	WCOR 900		WLOU 1350		KRIB 1490 KSMN 1010		WISN 1150 A WMIL 1290 WOKY 920
_	WLBE 790 M WBIL 1410	Louisville, Miss.	TMT 620 A-M WLSM 1270	Massena, N.Y.	WMSA 1340 A		WOKY 920 WTMJ 620 N
Leesburg, Va. Leesville, La.	WAGE 1290 KLLA 1570	Loveland, Colo.	KLOV 1570	Massillon, Ohio	WSTS 1050 WTIG 990	Minden, La.	KASO 1240
Lehighton, Pa. Leitchfield, Ky.	KLLA 1570 WYNS 1150 WMTL 1580	Loves Park, III, Lovington, N. Mex.	WLUV 1520 KLEA 630	Matane, Que, Matawan, W.Va,	CKBL 1250 WHJC 1360	Mineral Wells, Tex. Mineola, N.Y.	WFY1 1520 D
Leland, Miss.	WESY 1580 KLEM 1410	Lowell, Mass.	WCAP 980 I	Matteon, III.	WLBH 1170	Minneapolis, Minn.	
LeMars, lowa Lemoore, Calif.	KLEM 1410 KLAN 1320	Lubbock, Tex. K	WLLH 1400 CBD 1590 M-N	Mauston, Wis. Mayaguez, P.R.	WRJC 1270 WAEL 600 WKJB 710		WMIN 1400
Leneir, N.C. Leneir, Tenn.	WJRI 1340 M WLIL 730		KDAV 580 KLBK 1340		WKJB 710 WORA 760	WHITE'S RADIO	LOG 173
, 1000.	WEIL /30						

Lecation	C.L. Ke. N.A.	Location (.L. Kc. N.A.		C.L. Kc. N.A.	Location	C.L. Kc. N.A.
	WOGY 1130 WPBC 980	Mt. Vernon, ind. Mt. Vernon, Ky.	WPC0 1590 WRVK 1460	New Rochelle, N.Y New Smyrna Beac	h, Fia.		KFABIIIO N KOIL 1290
	WTCN 1280 A KTCR 690	Mt. Vernon, Ohio Mt. Vernon, Wash.	WMV0 1300 KAPS 1470		WSBB 1230 M WORT 1550		K000 1420 KMEO 660 M
	KTIS 900 KUOM 770	Mt. Vernon, Wash, Muleshoe, Tex, Mullins, S.C.	KMUL 1380	Newton, Iowa Newton, Kans,	KCOB 1280 KJRG 950	Omak, Wash,	WOW 590 C KOMW 680
Minet, N. Dak.	KLPM 1390 M KQDY 1320	Muncie, Ind.	WJAY 1280 WLBC 1340 C		WBKN 1410 WNNJ 1360	Oneida, N.Y. Oneida, Tenn.	WMCR 1600 WBNT 1310
Mission, Kans.	KCJB 910 C KBEA 1480 KIRT 1580	Munfordville, Ky. Munising, Mich.	WLOC 1150 WMAB 1400	Newton, N.C. New Ulm, Minn,	WNNC 1230 KNUJ 860	O'Neill, Nebr. Oncenta, Ala,	KBRX 1350 WCRL 1570
Mission, Tex. Missoula, Mont,	KGVO 1290 C	Murireesboro, Tens	WMTS 860 WCVP 600	New Westminster,	CKNW 980	Onconta, N.Y. Ontario, Calif.	WD08 730 KASK 1510
	KXLL 1450 N KQTE 1340 M KYSS 910	Murphy, N.C. Murphysbere, III,	WKRK 1390 WINI 1420	New York, N.Y.	WABC 770 A WBNX 1380 WCBS 880 C	Ontario, Oreg. Opelika, Ala.	KSRV 1380 WPHO 1400 M
Mitchell, S. Dak, Moab, Utah	KORN 1490 M	Murray, Ky. Murray, Utah	WNBS 1340 KMUR 1230		WEVO 1330	Opelousas, La. Opp, Ala. Opportunity, Wash	KSLO 1230 A Wami 860 Kzun 680
Moberly, Me, Mobile, Ala,	KNCM 1230 WALA 1410 N	Muscatine, Iowa Muscle Shoals City	KWPC 860		WHOM 1480 WINS 1010 M WLIB 1190	Orange, Mass. Orange, Tex.	WCAT 1390 KOGT 1600
	WMOE 1550 WABB 1480 A	Alabama Muskegon, Mich.	WLAY 1450 WKBZ 850 A		WMCA 570 WHN 1050	Orange, Va. Orangeburg, S.C.	WJMA 1340 WDIX 1150 A
	WGOK 900 WTUF 840		WTRU 1600 WMUS 1090	1	WNEW IISO WNYC 830		WORG 1580 WTNO 920
	WKRG 710 C	Muskogee, Okia.	KBIX 1490 A KMUS 1380		WOR 710 WADO 1280	Orange Park, Fla. Oregon City, Oreg.	WAYR 550 KGON 1520 M
Mobridge, 8.0ak, Mocksville, N.C.	WMOZ 960 KOLY 1300 WSOC 1560 D	Myrtle Beach, S.C. Nacogdoches, Tex.	KEEE 1230 A		WPOW 1330 WQXR 1560	Orillia, Ont. Orlando, Fla,	CFOR 1570 WDBQ 580 C
Modesto, Calif.	KTRB 860 KBEE 970 A	Nampa, Idaho	KSFA 860 KFXD 580 KWLW 1340	Niagara Falis, N.Y	WNBC 660 N WHLD 1270		WHOO 990 M WHIY 1270
Mojave, Calif.	KFIV 1360 A KDOL 1340	Nanaimo, B.C. Nanticoke, Pa,	CHUB 1570 WNAK 730	Niagara Fails, Ont Nicholasville, Ky.	WJJL 1440 M CHVC 1600 WNVL 1250	Command Bab. Etc.	WLOF 950 WKIS 740 N
Moline, III. Monahans, Tex.	WQUA 1230 A KVKM 1330 M	Napa, Calif. Naples, Fla.	KVON 1440 WNOG 1270	Niles, Mich. Nogales, Ariz.	WNIL 1290 KNOG 1340 A	Ormond Beh., Fla. Orofino, Idaho Oroville, Calif.	WQXQ 1380 KLER 950 KAOR 1340
Moneks Corner, N	WBER 950	Narrows, Va. Nashua, N.H.	WNRV 990 WOTW 900	Nome, Alaska Norfolk, Nebr.	KICY 850 WJAG 780	Ortonville, Minn. Osage Beh., Me.	KOIO 1350 KRMS 1150
Moneton, N. B.	CBAF 1330 CKCW 1220 KRMO 990	Nashville, Ark.	WSMN 1590 KBHC 1260	Norfolk, Va.	WTAR 790 C WCMS 1050	Osceola, Ark. Oshawa, Ont.	KOSE 860 CKLB 1350
Monett, Mo. Monmouth, III, Monroe, Ga.	WRAM 1330 WMRE 1490	Nashville, Ga. Nashville, Tenn.	WNGA 1600 WKDA 1240		WNOR 1230 WRAP 850	Oshkosh, Wis. Oskaloosa, Iowa	WOSH 1490 A KBOE 740
Monroe, La.	KMLB 1440 A-N KLIC 1280 M		WLAC 1510 C WMAK 1300 WLVN 1560	Normal, 111, Norman, Okia,	WIOK 1440 WNAO 640	Oswego, N.Y. Othelle, Wash,	WSG0 1440 KRSC 1400
Monroe, Mich.	WOTE 560		WNAH 1360 N	Norman Wells, No		Otsego, Mich. Otlawa, III.	WOMC 980 WCMY 1430
Monros, N.C. Monros, Wis.	WMAP 1060 WEKZ 1260	Natchez, Miss.	WSIX 980 A WSM 650 N WMIS 1240 N	Norristown, Pa.	WNAR IIIO	Ottawa, Kans, Ottawa, Ont.	KOFO 1220 CBO 910
Monroeville, Ala. Mont Laurier, Qu	WMFC 1360	Natchitoches, La.	WNAT 1450 N KNOC 1450 N		WMNB 1230 WGUS 1380	Ottumwa, Iowa	CFRA 580 CKOY 1310 KBIZ 1240 A
Monterey, Calif. Montevideo, Mins	K100 630 KMBY 1240 C	Navasota, Tex.	WOWW 860 KWBC 1550	N. Battleford, Sasi	WFNL 1600 WTHB 1550	Owatonna, Minn.	KLEE 1480 KRFO 1390
Monte Vista, Coi Montezuma, Ga.	1. KOMA 1460 A o, KSLV 1240 WMNZ 1050	Nebraska City, Ne	KNCY 1600	North Bay, Ont. North Bend, Ores.	CFCH 600 KFIR 1840 C	Owego, N.Y. Owensboro, Ky.	WEBO 1330 WOMI 1490 M
Montgomery, Ala		Needles, Calif. Neenah, Wis. Neillsyille, Wis.	KSFE 1340 WNAM 1280 WCCN 1370	North Charleston,	S.C. WNCG 910	Owen Sound, Ont.	WVJS 1420 A CFOS 560
	WAPX 1600 N WHHY 1440 N	Nelson, B.C. Neon, Ky,	CKLN 1390 WNKY 1480	Northfield, Minn, Northampton, Mas	WCÁĽ 770	Owesse, Mich. Oxford, Miss.	WOAP 1080 WSUH 1420
	WMGY 800 M WRMA 950	Neosho, Mo. Nevada, Mo.	KBTN 1420 KNEM 1240	N. Little Rock, Ari	WHMP 1400 M	Oxford, N.C. Oxnard, Calif.	WOXF 1340 KOXR 910
Montgomery, W.\ Monticello, Ark.	WMON 1346 M	New Albany, Ind. New Albany, Miss.	WOWI 1570 WNAU 1470	North Platte, Nebi	KXLR 1150 KJLT 970	Ozark, Ala. Paducah, Ky.	WOZK 900 WKYB 570 M WOXR 1560 N
Monticello, Kv.	KHBM 1430 WFLW 1360 CKBM 1490	Newark, Oel. Newark, N.J.	WWRK 1260 WJRZ 970	No System M V	KNOP 1410 KOOY 1240 N . WSOQ 1220 M	Page Arts	WOXR 1560 N WPAO 1450 C KPGE 1340
Montmagny, Que, Montpelier-Barre	, Vt. WSKI 1240 A	N	WNJR 1430 WVNJ 620	No. Syracuse, N.Y No. Vancouver, B.I N. Vernon, Ind.	C. CKLG 730 WOCH 1460	Page, Ariz. Pahokee, Fia. Painesville, Ohio	WRIM 1250 WPVL 1460
Montreal, Que.	CBM 940 N	Newark, N.Y. Newark, Ohio New Bedford, Mass	WACK 1420 WCLT 1430	No. Wilkesbere, N Norton, Va.	.C.WKBC 810 WNVA 1350 M	Paintsville, Ky, Paiatka, Fla,	WSIP 1490 M WWPF 1260
	CFCF 600 A	New Bern, N.C.	WNBH 1340 A WHIT 1450 A	Norwalk, Conn.	WNLK 1350 WICH 1310	Palestine, Tex.	WSUZ 800 KNET 1450
	CHLP 1410 CJAD 800	Newberry, S.C.	WRNB 1490 WKOK 1240	Norwich, N.Y. Oakdale, La.	WCHN 970 Kreh 900	Palm Beh., Fia. Palm Sprgs., Call:	WQXT 1340 A
	CJMS 1280 CKAC 730 C CKGM 980	New Boston, Ohio New Braunfels, Tex	WIOI 1010 c. KGNB 1420	Oakes, N.Oak. Oak Grove, La.	KEYO 1220 KWCL 1280	B-14-1- 0-1/4	KOES 920 KPAL 1450 KUTY 1470
Montrose, Colo. Montrose, Pa.	KUBC 580 WPEL 1250	New Braunfels, Tex New Britain, Conn	WHAY 910 /	Oak Hill, W.Va. Oakland, Calif.	WOAY 860 KEWB 910 KABL 960	Paimdale, Calif. Pale Alto, Calif. Pampa, Tex,	KIBE 1220 KPON 1340 M
Mooresville, N.C. Moorhead, Minn.	KVOX 1280 M	New Brunswick, N Newburgh, N.Y. Newburyport, Mass	WGNY 1220	Oakland Park, Fia	KO1A 1310	Panama City, Fla.	KHHH 1230
Moosejaw, Sask, Morehead, Ky, Morehead City, A	CHAB 800 : WMOR 1330 I.C. WMBL 740	New Carlisie, Que,	. CHNC 610	Oak Park, III. Oak Ridge, Tenn.	WOPA 1490 WATO J290 M	Panama City Bea	eh,
Morgan City, La. Morganneld, Ky.		New Castle, Ind. Newcastle, N.B. New Castle, Pa,	CKMR 790 WKST 1280	Qakville, Ont.	CHWO 1250 WMOP 900	Fia.	WTHR 1480 WSCM 1290
Morganton, N.C.	WMNC 1430 Va. WAJR 1440 N	Newcastle, Wyo. New Glassow, N.S	KASL 1240 CKEC 1320		WTMC 1290 N WKOS 1370	Paradise, Calif, Paragould, Ark, Paris, Ark,	KMET 930 KDRS 1490 KCCL 1460
Morritton, Ark,	WCLG 1300 KVOM 800	New Haven, Conn	WELI 960	Ocean City, Md. Oceaniake, Oreg. Oceanside, Calif.	WETT 1590 KBCH 1380	Paris, III, Paris, Kv.	WPRS 1440 WKLX 1440
Morris, Minn. Morristown, N.J.	KMRS 1230 WMTR 1250 WCRK 1150 M	New Iberia, La.	WNHC 1340 KANE 1240 KVIM 1360	Ocilia, Ga. Odessa, Tex.	W812 1380 KECK 920	Paris, Tenn. Paris, Tex.	WTPR 710 KPLT 1490 A
Morristown, Tenn Morton, Tex.	WMTN 1800 KRAN 1280	New Kensington, f New London, Conf	Pa.WKPA 1150	, , , , , ,	KOSA 1230 C KOYL 1310	Parkersburg, W.V	KFTV 1250 a. WCEF 1050
Moscow, Idahe Moses Lake, Was	KRPL 1400	New Martinsville,	W.Va.	l l	KRIG 1410 M KOEL 950	l	WPAR 1450 C
Moultrie, Ga.	KWIQ 1260 WMGA 1400 A WMTM 1300	Newsan, Ga.	WETZ 1330 I WCOH 1400 I WNEA 1300	Ogden, Utah	KOGA 930 KLO 1430 M	Park Falls, Wis, Parry Sound, Ont.	WPFP 1450 CKAR-1 1340
Moundsville, W.	V& WM00 1370	New Orleans, La.	WOSU 1280 I WJMR 990 R		KANN 1250 KSVN 730	Parsons, Kans. Pasadena, Calif.	K L K C 1540 K A L I 1480 K P P C 1240
Mountain Grove, Mountain Home,	Mo. KLRS 1360 Ark. KTLD 1490		WBOK 800 WNOE 1060	Ogdensburg, N.Y.	KVOG 1490 WSLB 1400 M	Pasadena, Tex.	KWKW 1300 KLVL 1480
Mt. Alry, N.C.	WPAQ 740 WSYD 1300 M WVMC 1360		WSMB 1350 A WNPS 1450 WTIX 690	Oil City, Pa. Okeechobee, Fla. Okla. City, Okla.	WKRZ 1840 WOKC 1570 KBYE 890 A	Paseagoula-Moss	KIKK 650 Point, Miss.
Mt. Carmel, III. Mt. Clemens, I	WYMC 1360 Mich. WBRB 1430		WWL 870 (3	KLPR 1140	Pasco, Wash.	WPMP 1580 A KORO 910
Mt. Dora, Fla. Mt. Jackson, Va	WVGT 1580	Newport, Ark,	WYLD 940 F KNBY 1280	1	KOCY 1340 KOMÁ 1520 KTOK 1000 A-M	Pase Robles, Calif	KPKW 1340 f, KPRL 1230 M
Mt. Jackson, Va Mt. Kisco, N.Y. Mt. Olivo, N.C.	WVIP 1310 WOJS 1430	Newport, Ky, Newport, N.H.	WNOP 740 WCNL 1010		KJEM 800 WKY 930	Patchogue, L.1., F	1.Y. WALK 1370
Mt. Olive, N.C. Mt. Pleasant, Mt Mt. Pleasant, Te	ich. WCEN 1150 IX. KIMP 960	Newport, Oreg. Newport, R.I.	KNPT 1310 WAOK 1540	Okmuigee, Okla, Old Saybrook, Con	KOKL 1240 n. WLIS 1420	Paterson, N.J.	WPAC 1580 WPAT 930
Mt. Shasta, Cali Mt. Sterling, K Mt. Vernon, III.	I. KWSU DZU	Newport, Tenn. Newport, Vt.	WLIK 1270 WIKE 1490	Olean, N.Y.	WMNS 1360 WHOL 1450 A WVLN 740	Pauls Valley, Oki: Pawtucket, R.I. Payette, Idahe	R. KVLH 1470 WXTR 550 A KEOK 1450
MIL VOINON, III,	W M I A 940	Newport News, Va	WT10 1270	Olney, Ill. Olympia, Wash,	KGY 1240 M	Peace River, Alta.	
174 WHITE	'S RADIO LOG	New Richmond, W	WIXK 1590	Omaka, Nebr.	KITN 920 KBON 1490	Pearsail, Tex. Peces, Tex.	KIUN 1400 M

Location	C.L. Kc. N.A	Location C	C.L. Kc. N.A.	Location	C.L. Kc. N.A	. Location	C.L. Kc. N.A.
Peekskill, N.Y. Pekin, III.	WLNA 1420 WSIV 1140	Poplarville, Miss.	KLID 1340 WRPM 1530	Racine, Wis,	WRAC 1460 WRJN 1400	Rocky Ford, Colo, Rocky Mount, N.C	KAVI 1320 . WCEC 810
Pell City, Ala. Pembroke, Ont,	WFHK 1430 CHOV 1350	Portage, Pa. Portage, Wis.	WWML 1470 WPDR 1350	Radford, Va. Raleigh, N.C.	WRAO 1460 WKIX 850		WEED 1390 A WRMT 1490
Pendleton, Oreg.	KUBE 1050	1 .	CFRY 920	İ	WPTF 680 I WLLE 570	Rocky Mount, Va.	WKW8 1290
Pennington Gap,	KUMA 1290 /	Port Alberni, B.C.		Ralls, Tex.	WRAL 1240 KCLR 1530	Rogers, Ark. Rogers City, Mich	KAMO 1390
Pensacola, Fla.	WSWV 1570 WBOP 980	Portales, N.Mex. Port Angeles, Wast		Rantoul, III. Rapid City, S.Da	WRTL 1460 k. KOTA 1380	Rogersville, Tenn C Rolla, Mo.	. WRGS 1370 KCLU 1590
	WBSR 1450	Port Arthur, Ont.	KONP 1450 CFPA 1230		KIMM 1150 KRSD 1340	Rome, Ga.	KTTR 1490 WLAQ 1410 A
	WNVY 1230 WCOA 1370	A Port Arthur, Tex.	KOLE 1340 KPAC 1250 N	Raton, N Mex.	KEZU 920 KRTN 1490	A	WIYN 1360 WRGA 1470 C
Penticton, B.C. Peoria, III.	WPFA 790 CKOK 800 WAAP 1350 I	Porterville, Calif. Port Hope, Ont. Port Hueneme, Cali	KTIP 1450 /	Rawlins, Wyo.	KRAL 1240 A.R	Rome, N.Y.	WROM 710 WKAL 1450 A
		Port Huron, Mich.	WHLS 1450 WTTH 1380	Raymond, Wash. Raymondville, Te Rayville, La.	KAPA 1340 EX. KSOX 1240 KRIH 990	Ronceverte, W.Va.	WRNY 1350 WRON 1400
Perry, Fla,	WPEO 1020 N	Port Jervis, N.Y. Port Lavaca, Tex.	WDLC 1490 KGUL 1560	Reading, Pa.	WEEU 850 A	Roseburg, Oreg.	KRNR 1490 C KRXL 1250
Perry, Ga. Perry, Iowa	WPGA 980 KDLS 1310	Portland, Ind. Portland, Maine	WPGW 1440 WCSH 970 P	Redding, Callf.	WRAW 1340 A	Rosenberg, Tex.	KYES 950 KFRD 980
Perryton, Tex. Peru, Ind.	KEYE 1400 N		WGAN 560 C	, reduing, Carri,	KRDG 1230 A KAHR 1330 KQMS 1400	Rossville, Ga, Roswell, N. Mex.	WRIP 980 KRSY 1230
Petaluma, Calif. Peterborough, On	KTOR 1490	Portland, Oreg.	POR 1490 A-N KBPS 1450	'	KVCV 600 (KGFL 1430 M KBIM 910
Petersburg, Va.	t. CHEX 980 CKPT 1420 WSSV 1240 N		KISN 910 KBEV 1010	Red Bluff, Calif, Red Over, Alta.	KBLF 1490 CKRO 850	Rouyn, Que. Roxboro, N.C. Royal Oak, Mich,	CKRN 1400 WRXO 1430 WEXL 1340
Petoskay Mich	WMDN 1940		KLIQ 1290 KEX 1190	Redfield, S. Dak Redlands, Calif.	KFCB 1380 KCAL 1410	Rugby, N. Dak, Ruidoso, N.Mex,	KGCA 1450 KRRR 1340
Phenix City, Ala. Philadelphia, Mis Philadelphia, Pa.		l .	KGW 620 N KOIN 970 C	Red Lien Pa.	WGCR 1440	Rumferd, Me. Rupert, Idaho	WRUM 790 KAYT 970
	WOAS 1480 WFIL 560 A		KPAM 1410 KPDQ 800	Red Wing, Minn.	KPRB 1240 KCUE 1250	Rushton, La. Rusk, Texas	KRUS 1490 KTLU 1580
	WFLN 900 WHAT 1340		KPOJ 1330 KWJJ 1080 A	Reedsburg, Wis.	Inn.KLGR 1490 WRDB 1400	Russell, Kans, Russellville, Ala,	KRSL 990 WWWR 920
	WIBG 990 WIP 610	Port Neches, Tex. Portsmouth, N. H.	KXL 750 KPNG 1150	Reedsport, Oreg, Regina, Sask,	KRAF 1470 CBK 540	Russellville, Ark. Russellville, Ky.	KXRJ 1490 WRUS 610
	WJMJ 1540 WPEN 950 M	Partamenth Ohlo	WBBX 1380 WHEB 750 WPAY 1400 C		CJME 1300 CKCK 620	Rutland, Vt.	WHWB 1000 WSYB 1380 M
Philipsburg, Pa.	WRCV 1060 N WTEL 860	Portsmouth, Va. W	WNXT 1260 A	Reidsville, N.C.	CKRM 980 WFRC 1600 A	Sackville, N.B. Sacramento, Caiif.	CBA 1070 KCRA 1320 N KFBK 1530 A
Phillipsburg, Kan Phoenix, Ariz,	WPHB 1260 s. KKAN 1490		WPMH 1010 WAVY 1350 N	Remsen, N.Y.	WREV 1220 WREM 1480 KOH 630 N		KGMS 1880 M
, 1100111A, ATTZ.	KIFN 860 KXIV 1400 KHAT 1480	Post, Tex. Poteau, Okla.	KUKO 1370 KLCO 1280	11000, 1404.	KOH 630 N KBET 1340 M KOLO 920 C		KJAY 1430 KRAK 1140 M
	KHEP 1280 KCAC 1010	Potosi, Me. Potsdam, N.Y.	KYRO 1280 WPOM 1470		KONE 1450 KDOT 1230		KROY 1240 C KXOA 1470
	KOY 550 A	Pottstewn, Pa. Pottsville, Pa.	WPAZ 1370 WPAM 1450	Rensseiger, N.Y. Rexburg, Idaho	WEEE 1300 KRXK 1230	Safford, Ariz. Sag Harbor, N.Y.	KGLU 1480 A KATO 1230
	KPHO 910 A KUEQ 740	Poughkeepsie, N.Y.	WPPA 1360 M WEOK 1390	Rhinelander, Wis,	. WOBT 1240 WJMC 1240 M	Saginaw, Mich.	WKNX 1210
	KRIZ 1230 KTAR 620 N	Powell, Wye. KF	WKIP 1450 A OW 1260 A-M	Richfield, Utah	KSVC 980 KALE 960	Sanitobia, Miss.	WSGW 790 C WSGU 1550
Picayune, Miss. Piedmont, Ala.	WRJW 1320 WPID 1280	Poynette, Wis. Prairie du Chien,	WIBU 1240 Wis. WPRE 980	Richlands, Va.	WRC0 1450 WRIC 540 WKBV 1490 A	St. Albans, Vt. St. Albans, W.Va.	WWSR 1420 WKLC 1300
Pierre, S.Dak, Pikevlile, Ky,	KGFX 630 KCCR 1590	Pratt, Kans.	WPRE 980 KWSK 1570 KPRT 1290	Richmond, Ind. Richmond, Ky. Richmond, Va.	WEKY 1340 M	St. Anne-de-la-Poo	catiore, Que.
Pine Biuff, Ark.	WLSI 900 WPKE 1240 M KCLA 1400	Prescott, Ariz,	KYCA 1490 N KENT 1340	Kienmond, Va.	WANT 990 WBBL 1480 WRGM 1590	St. Augustine, Fla.	WETH 1420
, mo Dian, Aig.	KAOL 1270 KOTN 1490 M	Prescett, Ark,	KNOT 1450 A KTPA 1370		WLEE 1480 M WEET 1320	St. Boniface, Man. St. Catherines, Ont	CKTB 610
Pine City, Minn.	KPBA 1590 WCMP 1350		WAGM 950 WEGP 1390		WMBG 1380 A WRNL 910 C	St. Charles, Me. St. Cleud, Minn,	KAOY 1460 KFAM 1450 N
Pineville, Ky, Pineville, W.Va,	WMLF 1230 WWYO 970	Preston, Idaho Prestonsburg, Ky,	KPST 1340 WPRT 960		WRVA 1140 N WXGI 950	St. George, Utah St. Helen, Mich.	WJON 1240 KDXU 1450 WMIC 1590
Pipestone, Minn, Piqua, Ohlo	KLOH 1050 WPTW 1570	Price, Utah Prichard, Ala,	WOOC 1310 KOAL 1230 M	Richmond Hill, On Richwood, W. Va.	WVAR 1280	St. Helens, Ores, St. Hyacinthe, Que.	KOHI 1600
Pittsburg, Calif. Pittsburg, Kans,	KKIS 990 KOAM 860 N	Prince Albert, Sask. Prince George, B.C.	WSIM 1270 CKB1 900 CKPG 550	Ridgecrest, Calif.	KRCK 1360 KLOA 1240	St. Jean, Que, St. Jerome, Que,	CHRS 1090 CKJL 900
Pittsburgh, Pa.	KSEK 1340 KOKA 1020 KQV 1410 A	Prince Rupert, B.C.	CFPR 1240 WRAY 1250	Rimouski, Que. Rio Piedras, P.R.	CJBR 900 WUNO 1320 WWWW 1520	Saint John, N.B.	CFBC 930 CHSJ 1150
	WAMO 860 WJAS 1320 N	Princeton, Ky, Princeton, N.J. W	WPKY 1580 /HWH 1350	Ripley, Tenn. Ripon, Wis,	WWWW 1520 WTRB 1570 WCWC 1600	St. Johns, Mich, St. John's, Nfld,	WJUD 1580 CBN 640
	WPIT 730 WRYT 1250	Princeton, W.Va. Princetile, Oreg.	WLOH 1490 A KRCO 690	Riverheac, N.Y.	WRIV 1390 WAPC 1570		CJON 930 VOAR 1230
	WYRE 1080 M WWSW 970	Prosser, Wash. Providence, R.I.	KARY 1310 WEAN 790 C	Riverside. Calif.	KPRO 1440 KACE 1570 KVOW 1450 M	St. Johnsbury, Vt.	VOCM 590 VOWR 800
Pittsfield, III. Pittsfield, Mass.	WBBA 1580 WBEC 1420 A		WHIM III0 WICE 1290	Riverton, Wyo. Riviera Beach, Fla.	. WHEW 1600	St. Joseph, Mich. St. Joseph, Me,	WSJM 1400 KFEQ 680
Pittston, Pa.	WBRK 1340 M WPTS 1540	v	WJAR 920 N VLKW 990	Riviere du Loup, Q Roanoke, Ala.	WELR 1360	on seeds in, inter	KKJO 1550 M KUSN 1270
Plainfield, N.J. Plainview, Tex.	WERA 1590 KVOP 1400 M KPLA 1050		WPRO 630 WRIB 1220 M	Reanoke, Va.	WOBJ 960 C WRIS 1410 M	St. Joseph d'Alma,	Que. CFGT 1270
Plant City, Fla. Platteville, Wis.	WPLA 910 WSWW 1590		KIXX 1400 A KEYY 1450 KOVO 960 M		WHYE 910 WROV 1240 A WSLS 610 N	St. Louis, Me.	KATZ 1600 KFUO 850
Plattsburg, N.Y.	WEAV 960 A.N. WIRY 1340 M	Pryor, Okla.	KOLS 1570 KOZA 1230	Roanoke Rapids, N	.C. WCBT 1230 M		KMOX 1120 C KSO 550 N
Pleasanton, Tex. Pleasantville, N.J.	KBOP 1380 WOND 1400		KAPI 690 KEEL 970	Roaring Sprgs., Pa	W KMC 1370		KSTL 690 KWK 1880
Plymouth, Mass, Plymouth, N.C.	WPLM 1390 WPNC 1470	KG	HF 1350 A-M KCSJ 590 KTUX 1480	Roberval, Que. Robinson, III.	CHRL 910 WTAY 1570		KXOK 630 WEW 770 M
Plymouth, Wis. Pocahontas, Ark,	WPLY 1420 KPOC 1420	Pulaski, Tenn. V	WKSR 1420 A	Rochester, Minn.	KROC 1340 N	St. Louis Park, Min	
Pocatello, Idaho	KSE1 930 N KWIK 1240 M	Pullman, Wash.	WPUV 1580 KWSC 1250	Rochester, N.H. Rochester, N.Y.	WWNH 930 WBBF 950 M	St. Mary's, Pa. St. Paul, Minn.	KRSI 950 WKBI 1400
Pocomoke City, Md.	KSNN 1290 WDMV 540	Punxsutawney, Pa. V	KOFE 1150 WPME 1540 WINY 1350		WHEC 1460 C	St. Peter, Minn.	KSTP 1500 N KDWB 630 M Krbi 1310
Pointe Claire, Que. Pomena, Calif.	KWOW 1600	ruyallup, wash,	KAYE 1450		WRVM 680 WSAY 1370	St. Petersburg, Fia.	WPIN 680 WSUN 620 A
Pompano Beach, Fl	KKAR 1220	Quantico, Va. V Quebec, Que.	KOLJ 1150 VQVA 1530 CBV 980	Rockford, III,	WROC 1280 N WROK 1440 A	St. Petersburg Beas	WLCY 1380 M
Panes Oliver and	WLOO 980 WPOM 1470 A		CHRC 800 CJLR 1060	Rack Hill C.C.	WJRL 1150 WRRR 1330	Fla.	WILZ 1590
Ponca City, Okla, Ponce, P.R.	WBBZ 1230 M WPRP 910		CJQC 1340	Rock Hill, S.C. Rockingham, N.C.	WRHI 1340 M WTYC 1150 WAYN 900	Salamanca, N.Y. Salamanca, N.Y.	CHLO 680 WGGO 1590 WJBD 1350
	WEUC 1420 WPAB 550	Quincy, Fla. W	CKCQ 570 /CNH 1230 M	Rockingham, N.C. Rock Island, III, Rockland, Maine		Salem, Ind. Salem, Mass.	WSLM 1220 WESX 1230 M
Pontine, Mich.	W130 1200	Quincy, III. W	GEM 1440 A	Rockmart, Ga. Rock Springs, Wyo	WPLK 1220	Salem, Mo. Salem, Oreg.	KSMO 1340 KSLM 1390 A
Pontotoe, Miss. Poplar Bluff, Mo.	WPON 1460 WSEL 1440	Quincy, Mass. \Quincy, Wash.	WJOA 1300	Rockville, Md,	VRS 1360 A-M		KAPT 1220
. vpici bluff, m0.	KWOC 930	Quitman, Ga.	WSFB 1490	Rockville, Md. Rockwood, Tenn.	WRKH 580	WHITE'S RADIO	LOG 175

Location	C.L. Kc. N.A.	Location C	L. Kc. N.A.	Location C	.L. Kc. N.A.	Location C	L. Kc. N.A.
200000	KBZY 1490 N KGAY 1430		WSAF 1220 WSPB 1450 C	Sitka, Alaska	KS00 1140 A KIFW 1230 C-A	Sunnyside, Wash.	KREW 1280 KSKI 1340
Salem, Va. Salida, Colo.	WBLU 1480 KVRH 1340 M	Saratoga Springs, N	W Y N D 1280	Skowhegan, Maine	KSEW 1400	Superior, Nebr. Superior, Wis,	KRFS 1600
Salina, Kans, Salinas, Calif,	KSAL 1150 M KDON 1460		WSPN 900 CHOK 1070	Slaton, Tex. Smithfield, N.C.	KCAS 1050 WMPM 1270	ouperior, wis.	WIGL 970
Saline, Mich.	KSBW 1380 M WOLA 1290	Saskatoon, Sask.	CFQC 600 CFNS 1170	Smiths Falls, Ont. Smyrna, Ga.	CJET 630 WSMA 1550	Susanville, Calif,	WQMN 1320 KSUE 1240
Salisbury, Md.	WBOC 960 WICO 1320 A	Sault Ste. Marie,	CKOM 1250	Snyder, Tex. Socorro, N. Mex.	KSNY 1450 M KSRC 1290	Swainsboro, Ga. Sweetwater, Tenn.	WDEH 800
Salisbury, N.C.	WJOY 1470 WSTP 1490 M	Michigan Sault Ste, Marie,	W800 1230	Soda Spres., Idaho		Sweetwater, Tex. Swift Current, Sask	KXOX 1240 . CKSW 1400
**	WSAT 1280 A KSRA 960	Ontari	CKCY 920	Solvay, N.Y. Somerset, Ky,	WSFC 1240 M	Sydney, N.S.	CBI 1140 CJCB 1270
Saimon, Idaho Sait Lake City, L		Savannah, Ga.	WBYG 1450 M WEAS 900	Somerset, Pa.	WTLO 1480 WVSC 990 KVML 1450	Sylacauga, Ala,	WFEB 1340 M WMLS 1290
	KCPX 1320 N	1	WSAV 630 N WSGA 1400	Sonora, Calif. Sonora, Tex. Sorel, P.Q.	KCKG 1240	Sylva, N.C. Sylvania, Ga.	WMSJ 1480 WSYL 1490
	KNAK 1280	,	WTOC 1290 C	South Beloit, III.	CJSO 1320 WBEL 1380	Syracuse, N.Y.	WHEN 620 C WFBL 1390 M
	KSOP 1370	Savannah, Tenn. \	WORM 1010	So. Bend, Ind.	WNOU 1490 A WJVA 1580 M		WNOR 1260 WOLF 1490 A
	KWHO 860	Sayre, Pa. Schefferville, Que.	WATS 960 CFKL 1230	Southbridge, Mass, So. Boston, Va.	WSBT 960 C WESO 970	Tabor City, N.C.	WSYR 570 N WTAB 1370
San Angelo, Tex.	KWIC 1570 KTEO 1340 KGKL 960 A	Schenectady, N.Y. Scotland Neck, N.C.	WGY 810 N WSNY 1240	Southern Pines, M. (3.WEEB 990	Tacoma, Wash,	KMO 1360 KTAC 850 KTNT 1400
	KPFP 1420	Scottsbluff, Nebr,	NEB 960 A.M	South Daytona Ber Florida	WELE 1590		KVI 570 M
San Antonie, Tex.	KWFR 1280 KAPE 1480 KCOR 1350	Seettsbore, Ala.	KOLT 1320 C	So. Gastonia, N.C. So. Haven, Mich. So. Knoxville, Tenr	WJOR 940	Taft, Calif. Tahlequah, Okla.	KTKR 1310 KTLQ 1350
	KENS 680 C KBER 1150		W ROS 1330 K WBY 1440	So. Paris, Me.	WKTQ 1450	Tahoe Valley, Calif.	KTHO 590
	KITE 930	Scottsville, Ky.	WLCK 1250	So. Pittsburg, Tens	N. WEPG 910 n. Kowo see M	Talladega, Ala	WEYY 1580 WNUZ 1230 M
	KUKA 1250 KUBO 1310 KMAC 630 A	Scranton, Pa.	WEJL 630 WEBI 910 C	So. Williamsport,	KDWB 630 M Pa.	Tallahassee, Fia.	WMEN 1330 WRFB 1410
	KONO 860		WICK 1480	Spanish Fork, Uta	WMPT 1450 h KONI 1480		WTAL 1270 M WTNT 1450 C
San Bernardine, Co	KTSA 550 WOAI 1200 N	Seaford, Del.	WSCR 1320 N WSUX 1280 KWCB 1300	Sparks, Nev. Sparta, III.	KBUB 1270 WHCO 1230	Tallassee, Ala. Tallulah, La.	WTLS 1300 KTLD 1380
Jen Salmer Bline, Ci	KCKC 1350 KFXM 590	Searcy, Ark. Seaside, Oreg. Seattle, Wash.	KSRG 730 KAYO 1150 M	Sparta, Tenn, Sparta, Wis.	WSMT 1050 WKLJ 990 WCOW 1290	Tampa, Fla.	WALT 1110 WDAE 1250 C
	KRNO 1240 KMEN 1290 M	Scattle, Wasii,	KUDY 910	Spartanburg, S.C.	WZ00 1400 M		WYOU 1550 WFLA 970 N
Sandersville, Ga. San Diego, Calif.	WSNT 1490 KCBQ 1170		KING 1090 A KIRO 710 C KJR 950	Saurana taura	WORD 910 N WSPA 950 C		WHBO 1050 M WINQ 1010
San Diege, Calif.	KFMB 540 C KOGO 600 N		KOL 1300	Spencer, lowa Spencer, W.Va.	KICD 1240 WSPZ 1400	Al A4	WTMP 1150 WSQL 1300
	KGB 1360 A KSON 1240		KOMO 1000 N KETO 1590 KTW 1250	Spokane, Wash,	KGA 1510 A	Tarbore, N.C.	KKIT 1340 WCPS 760
Sandpoint, Idaho	KSDO 1130 KSPT 1400		KVI 570		KPEG 1380 KHQ 590 N		WRBB 1470 WESR 1330
Sand Spring, Okia Sandusky, Ohie	KTOW 1340 WLEC 1450 M	Sebring, Fla.	KXA 770 WJCM 960 WSEB 1340		KNEW 790 M KREM 970	Tawas City, Mich.	WPEP 1570 WIOS 1480
San Fernando, Cali: Sanford, Fla.		Sedalia, Me.	KDRO 1490 KSIS 1050	Parinadata Ash	KXLY 920 C	Taylor, Tex. Taylorsville, N.C.	KTAE 1260 WTLK 1570
Sanford, Me.	WSFR 1360 WSME 1220	Seguin, Tex. Selma, Ala.	KWED 1580 NGWC 1340 C	Springdale, Ark. Springfield, III.	KBRS 1340 A WCVS 1450 A M WMAY 970 N	Taylorville, III, Tazewell, Tenn.	WTIM 1410 WNTT 1250
Sanford, N.C.	WEYE 1290 WWGP 1050	1	WHBB 1490 WRWJ 1570	Springfield, Mass,	WTAX 1240 C	Tell City, 1nd, Tempe, Ariz,	WTCJ 1230 KUPD 1060
San Francisco, Calif.		Seminole, Tex.	KTFO 1250	opringnete, mass,	WHYN 560 C		KYND 1580 KTEM 1400 CFTK 1140
Cam.	KCBS 740 C	S.C. Seven Iles, Que.	W8NW 1150 CKCN 560	Springfield, Mo.	WSPR 1270	Torre Moute Ind	WBOW 1230 N
	KGO 810 A	Sevierville, Tenn.	WSEV 930 (1BH 1340 C.A	Springnatu, mu,	KGBX 1260 N KICK 1340 KTTS 1400 (.1	WTH1 1480 C
	KNBC 680 N KKHI 1550 M	Seymour, Ind. Seymour, Tex.	WJCD 1390 KSEY 1230	Springfield, Ohlo	KWTO 560 A	Terrytown, Nebr.	KTER 1570 Keyr 690
	K8AY 1010 K8AN 1450	Shamokin, Pa. Shamrock, Tex.	WISL 1480 KBYP 1580		WBLY 1600	Texarkana, Ark. Texarkana, Tex.	KOSY 790 M KCMC 740 A
	KSFO 560 KYA 1260	Sharon, Pa. Shawane, Wis.	WPIC 790 WTCH 960	Springfield, Oreg. Springfield, Tenn. Springfield, Vt.	WDBL 1590 WCFR 1480		KATQ 940 KTFS 1400
San German, P.R. San Jose, Calif.	WRJS 1090 KLOK 1170 KLIV 1590 M	Shawinigan, Que. Shawnee, Okla.	CKSM 1220 KGFF 1450 M	Springhill, La. Spruce Pine, N.C	KBSF 1460	Texas City, Tex. Thayer, Me.	KTLW 920 KALM 1290
	KLIV 1590 M KEEN 1370 KXRX 1500	Sheboygan, Wis,	WHBL 1330 A WKTS 950 WSHF 1290	Stamford, Conn. Stamford, Tex.	WSTC 1400 A KDWT 1400	The Dailes, Ores.	KODL 1440 KRMW 1300 KRTR 1490 M
San Juan, P.R.	WAPA 680 M	Sheffield, Ala. Shelby, Mont.	WSHF 1290 KSEN 1150 M	Stanford, Ky. Starke, Fla.	WRSL 1520 WRGR 1490	1	KRTR 1490 M KTHE 1240
	WHOA 870 WIAC 740 WIPR 940	Shelby, N.C.	WOHS 730 M WADA 1390	Starkville, Miss, State College, Pa	WS80 1230	Thief River Falls, Minn. Thetford Mines, Qu	KTRF 1230
	WKAQ 580 C WKVM 810	Shelbyville, Ind. Shelbyville, Tenn.	WSVL 1520 WHAL 1400	Statesbore, Ga.	WRSC 1390 WWNS 1240	Thibodaux, La. Themasten, Ga.	KTIB 630 WSFT 1220
	WKYN 630 WITA 1140	Shenandoah, lowa	WLIJ 1580 KFNF 920	Statesville, N.C.	WSIC 1400 WDBM 550	Thomasville Ale	WTGA 1590
San Luis Obispo, (KATY 1340	Sherbrooke, Que,	KMA 960 A CHLT 630		WTON 1240 /	Thomasville, Ga.	WPAX 1240 WKTG 730
	KCJH 1280	Sheridan, Wye,	CKTS 900 KWYO 1410 M	Stephenville, Tex. Sterling, Colo.	KGEK 1230	Thomasville, N.C. Thomson, Ga.	WKTG 730 WTNC 790 WTWA 1240 M
San Marcos, Tex,	KVEC 920 M KCNY 1470 KOFY 1050	Sherman, Tex,	KROE 930 KRRV 910 M	Sterling, III,	KOLR 1490 WSDR 1240	Three Rivers, Mich	WLKM 1510
San Matee, Calif. San Rafael, Calif. San Saba, Tex.	KTIM 1510	Shippensburg, Pa.	KTX0 1500 WSHP 1480	Steubenville, Ohio Stevens Point, Wi	WSTV 1340 N	Three Rivers, Que.	
San Saba, Tex. Santa Ana, Calif.	KBAL 1410 KWIZ 1480	Shew Lew, Ariz. Shreveport, La.	KVWM 1050 KANB 1300	Stillwater, Minn, Stillwater, Okla.	W A V N 1770	I = 1 - 1 - 1 - 1 - 1	WIPS 1250 WTTF 1600 M
Santa Barbara, Ca	I, KDB 1490 KGUD 990 KIST 1340 N	l	KBCL 1220 KCIJ 1050 C	Stockton, Calif.	KSPI 780 KJOY 1280 KSTN 1420 KWG 1230	Tiften, Ga.	WT1F 1340 WWG8 1430
	KIST 1340 N KTMS 1250 A-M	ļ	KEEL 710 KOKA 1550 M KJOE 1480 M	Storm Lake, lews	KAYL 990 CJCS 1240	Tillamook, Oreg,	KTIL 1590 CKOT 1510
Santa Cruz, Calif.	KTMS 1250 A-M KACL 1290 KSCO 1080		KREB 980	Strantor III	W LZZ 1250	Tillsenburg, Ont. Timmins, Ont.	CECL 620
Santa Fe, N. Mex.	KTRC 1400 A KVSF 1260 C	Eldam Paris	KRMO 1340 A		WVPO 840 WSTU 1450 1	Titusville, Fla. Titusville, Pa.	CKGB 680 WRMF 1050 WTIV 1230
Santa Maria, Cal.	KHER 1600	Sidney, Mont. Sidney, Nebr. Sierra Vista, Ariz.	KULA 1460 M	Stuart, Va. Sturgeon Bay, Wis	WHEO 1270 WDOR 910	Toecoa, Ga.	WLET 1420 M WNES 630
	KSMA 1240 KSEE 1480	Sikeston, Mo.	KSIM 1400	Stuttgart, Ark.	WSTR 1230 KWAK 1240 N	Toledo, Ohio	WOHO 1470 M
Santa Monies, Cal Santa Paula, Cali	i, KDAY 1580 f. KSPA 1400	Siler City, N.C. Sileam Spres., Ark.	WNCA 1570 KUOA 1290 M	Sudbury, Ont.	CKSO 790 CFBR 550		WTOD 1560 C WTOL 1230 A KTDO 1230
Santa Rosa, Calif.	KHUM 1580	Sileam Spres., Ark. Silsbee, Tex. Silver City, N. Mex.	KRAS 1300 KSIL 1340 (Suffelk, Va.	CHNO 900 WLPM 1460	Toledo, Oreg. Tolleson, Ariz.	KZON 1190
Santa Rosa, N. Me	KVRE 1460 KJAX 1150	Silver Sprgs., Md.	CFRS 1560 KTOD 1590	Sulphur Spras. T	KIKS 1310 ex. KSST 1230	Temah, Wis, Tompkinsville, Ky,	WTMB 1460 WTKY 1370
Santa Rosa, N. Me Sapulpa, Okla.	K, KSYX 1420 KREK 1550	Sinten, Tex, Sieux City, Iewa	KSCJ 1380 A		WGTA 930	Topele, Utah Topeka, Kans,	KDYL 990 WIBW 580 C
Santa Rosa, N.Me Sapulpa, Okla. Saranat Lake, N.Y Sarasota, Fla.	Y. WNBZ 1240 A WKXY 930	Slow Falls 6 5	KMNS 620 M KTRI 1470	Summerville, S.C. Sumter, S.C.	WFIG 1290 I		KEWI 1440 WREN 1250 A
	S RADIO LOG	1	KELO 1820	Suntaine D.	WDXY 1240 WSSC 1340	C Toppenish, Wash.	
TA AMILE	" wanto rod	•	KNWC 1270	l Sumbury, Pa.	W POR 1340	O. Labhanion' A Self'	ALIE ITO

	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	G.L. Ke. N.A.	Location C.L. Kc. N.
ocation oronto, Ont.	CBL 740 N	200011011	CJOR 600		WKRS 1220	Willimantie, Conn. WILI 1400
	CHFI 1540 D CFRB 1010 C	Vancouver, Wash,	CKWX 1130 M KKEY 1150	Waukegam, III. Waukesha, Wis. Waupaca, Wis.	WAUX 1510 WDUX 800 A	Williston, N.D. KEYZ 1360 Willmar, Minn. KWLM 1340
	CHUM 1050 M		KVAN 1480 WAMR 1320	Wausau, Wis,	WRIG 1400 N WSAU 550 A	Willoughby, Dhio WELW 1330 Willow Springs, Mo. KUKU 1330
	CJBC 860 CKEY 580 M	Venice, Fla. Ventura, Calif.	KVEN 1450 M		WHVF 1230	Willows, Calif. KIQS 1560
orrington, Conn.	CKFH 1430 WBZY 990	Verdun, Que.	KUDU 1590 CKVL 850	Waverly, lowa Waverly, Ohio	KWVY 1470 WPKD 1380	Wilmington, Del. WAMS 1380 WDEL 1150
•	WTOR 1490 M	Vermillion, S.Dak		Waxahachie, Tex. Wayeross, Ga.	KBEC 1390 WACL 570	WILM 1450 WTUX 1290
orrington, Wye, Towanda, Pa.	KGOS 1490 WTTC 1550	Vernal, Utah Vernon, B.C.	CJ1B 940		WAYX 1230 M	Wilmington, N.C. WMFD 630
owson, Md. Trail, B.C.	WAQE 1570 CJAT 610	Vernon, Tex. Vero Beach, Fla.	KVWC 1490 WAXE 1370	Waynesboro, Ga. Waynesbero, Miss.	WBR0 1310 WABO 990	WHSL 1490 WKLM 980
raverse City, Mici	h. WTCM 1400 WCCW 1310	Vicksburg, Miss.	WTTB 1490 A WQBC 1420 M	Waynesboro, Pa. Waynesboro, Va.	WAYZ 1380 WAYB 1490 M	Wilson, N.C. WGNI 1840
renton, Mo.	KTTN 1600	I	WVIM 1490		WRWV 970	WLLY 1350
renton, N.J.	WAAT 1300 WBUD 1260	Victoria, B.C.	CJVI 900 CFAX 870	Waynesburg, Pa. Waynesville, Mo.	WANB 1580 KJPW 1390	Winchester, Ky. WWKY 1380
rinidad, Colo.	WTTM 920 M KCRT 1240 M	Victoria, Tex.	CKDA 1220 KNAL 1410	Waynesville, N.C. Weatherford, Tex.	WHCC 1400 KZEE 1220	Winchester, Tenm. WCDT 1340 Winchester, Va. WINC 1400
roy, Ala,	WTBF 970 M	Victoriaville, Que,	CFDA 1380	Webster City, lows	KJFJ 1570	WHPL 610
roy, N.Y.	WHAZ 1330 WTRY 980	Victorville, Calif. Vidalia, Ga.	WVOP 970	Weed, Calif. Weirton, W.Va.	KDAD 800 WEIR 1430 N	Windemere, Fla. WXIV 1480 Winder, Ga. WIMO 1300
roy, N.C.	WXKW 1000	Vicques, P.R. Ville Marie, Que,	WIVV 1370 CKVM 710	Weiser, daho Welch, W.Va.	KWEI 1260 WELC 1150	Windom, Minn, KDDM 1580 Windsor, Conn. WSOR 1480
ruckee, Calif.	WJRM 1390 KHOE 1400	Ville Platte, La.	, KVPI 1050		WOVE 1340 M	Windsor, N.S. CFAB 1450
rure, N.S. ruth or Conseque	CKCL 600	Ville St. Georges	L Que. CKRB 1460	Weldon, N.C. Welland, Ontario	WCNF 1400 CHOW 1470	Windsor, Ont. CBE 1550 CKLW 800
New Mexico	KCHS 1400	Vincennes, Ind. Vincland, N.J.	WAOV 1450 M WWBZ 1360	Wellsbore, Pa. Wellston, Ohio	WNBT 1490 M	Wingham, Ont. CKNX 920 Winnemucca, Nev. KWNA 1400
ryon, N.C. ucson, Ariz,	WTYN 1550 M KTUC 1400 A		W D V L 1270	Wellsville, N.Y.	WLSV 790	Winnfield, La. KVCL 1270
	KXEW 1600 KAIR 1490	Vinita, Okla, Vinton, Va.	KVIN 1470 WKBA 1550	Wenatchee, Wash	, KPQ 560 A KUEN 900	Winner, S.Dak. KWYR 1260 Winnipeg, Man. CBW 990
	KCEE 790	Virginia, Minn.	WHLB 1400 N	Wendell-Zebulon,	KMEL 1840 M	CKRC 630 CKY 580
	KCUB 1290 M	Virginia Beh., Va Virouqua, Wis.	WISV 1360		WETC 540	CIOB 68
	KEVT 690 KOBY 940	Visalia, Calif. Vivian, La.	KONG 1400 KLV1 1600	Westaco, Tex. West Allis, Wis.	KRGV 1290 N WAWA 1590	Winnsboro, La. KMAR 1570 Winnsboro, S.C. WCKM 1250
	KMOP 1330	Wato, Tex.	WACO 1580 A KAWA 1010	W. Bend, Wis. Westbrook, Me.	WBKV 1470 WJAB 1440	Winona, Minn. KWNO 1230
	KFIF 1550 KTKT 990		KBGO 1580	West Covina, Call	f, KGRB 900	KAGE 138
ucumeari, N.Mex	KOLD 1450 C	Wadena, Minn,	KWTX 1230 M KWAD 920 M	W. Frankfort, III. West Jefferson, N	. WFRX 1300	Winena, Miss, WONA 1570 Winslow, Ariz, KVNC 1010
ulare, Calif.	KCOK 1270 M	Wadesboro, N.C.	WADE 1210 KMVI 550 N		WKSK 1600	Winston-Salem, N.C. WAAA 98
fulla, Tex.	KGEN 1370 KTUE 1260	Wailuku, Hawail Waipabu, Hawaii	KAHU 920	W. Memphis, Ark W. Monroe, La.	KUZN 1310	WAIR 134
ullahoma, Tenn. ulsa, Okia.	WJIG 740 KAKC 970	Walhalla, S.C. Wallace, Idaho	WGOG 1460 KWAL 620 M	W. Palm Beach,	FIA. WEAT 850 M	WPEG 155 WSJS 600
uisa, Okia.	KOME 1300	Wallace, N.C.	WLSE 1400		WJNO 1230 C WIRK 1290 M	WTOB 1380 (Winter Garden, Fla. WOKB 160
	KRMG 740 C KELI 1430 C	Walla Walla, Wa	KHIT 1320	West Plains, Mo.	KWPM 1450	Winter Haven, Fla. WSIR 149
	KV00 1170 N KFMJ 1050		KUJ 1420 M KTEL 1490 A	West Point, Ga. West Point, Miss	WBMK 1310 . WROB 1450 M	WINT 136 Winter Park, Fla. WABR 144
upelo, Miss.	WELO 580 M	Wainut Ridge, Ar Waisenburg, Colo.	k. KRLW 1320	Westport, Conn. W. Springfield, A	WMMM 1260 M	Wisconsin Rapids, Wis. WFHR 132
Turlock, Calif.	WTUP 1490 A KCEY 1390	Walterboro, S.C.	WALD 1220 A		WTXL 1490 A	WRNE 122
luscaloosa, Ala,	WJRD 1150 WACT 1420	Waltham, Mass. Walton, N.Y.	WCRB 1330 WDLA 1270	W. Yarmouth, Ma	WOCB 1240 M	Wolf Pt., Mant. KVCK 145 Wood River, III. WBBY 59
	WNPT 1280 A		WDLA 1270 a. WJOE 1570 WARE 1250 M	Westerly, R.I. Westfield, Mass.	WERI 1230 M WDEW 1570	Wood River, III. WBBY 59 Woodside, N.Y. WWRL 160 Woodstock, N.B. CJCJ 92
	WTUG 790 WTBC 1230 M	Warner Robbins,	Ga,	Westminster, Md	. WTTR 1470	Waadstock, Gnt. CKOX 134
Tuscumbia, Ala.	WVNA 1590 WRCK 1410	Warren, Ark.	WRPB 1350 A KWRF 860	Weston, W.Va. W. Warwick, R.I	WHAW 980 M WWRI 1450	Woonsocket, R.I. WNRI 138
Tuskegee, Ala.	WABT 580	Warren, Ohio Warren, Pa.	WHHH 1440 WNAE 1310	Wetumpka, Ala. Wewoka-Seminole	WETU 1250 Okla	WwoN 124 Wooster, Ohlo WWST 96
Twenty-Nine Pain	KDH1 1250	Warrensburg, Mc	b. KOKO 1450		KWSH 1260 A	Worcester, Mass.
Twin Falls, Idaho	KTF1 1270 N KLIX 1310 M	Warrenton, Mo. Warrenton, Va.	KWRE 730 WEER 1570	Weyburn, Sask. Wharton, Tex.	CFSL 1340 KAN1 1500	WAAB 1440 M- WNEB 123
Two Divors Wis	KEEP 1450 WTRW 1590	Warsaw, Ind.	WKCW 1420 WRSW 1480	Wheatland, Wyo. Wheaton, Md.	KY CN 1340 W O O N 1540	WORC 131 WTAG 58
Two Rivers, Wis. Tyler, Tex.	KDOK 1330	Warsaw Va	WNNT 690	Wheeling, W.Va.	WHLL 1600 WJBT 1470	Worland, Wye, KWOR 184 Worthington, Minn. KWOA 73
	KGJB 1490 M KTBB 800 A	Warwick- E.Green	WYNG 1590		WKWK 1400 A	Worthington, Ohio WRFD 88
Tyrone, Pa,	KZEY 690 WTRN 1340	Wasco, Calif. Washington, D.C.	KWSO 1050 . WGMS 570	White Castle, La.	WWVA 1170 C KEVL 1590	Wynne, Ark. KWYN 140 Wytheville, Va. WYVE 128
Ukiah, Calif.	KUKI 1400	Washington, D.C.	WMAL 630 A WOL 1450 M	White Plains, N.Y	. WFAS 1230	Yakima, Wash, KIT 128 KIMA 146
Jnien, Me.	KMSL 1250 KLPW 1220		WOOK 1340	White River June	WWRJ 910	KBB0 139
Union, S.C. Union City, Tenn.	WBCU 1460 WENK 1240		WWDC 1260 WRC 980 N	Whitehall, Mich. Whitehorse, Y.T.	WCBP 1490 CFWH 570	KUTI 98 KYAK 139
Uniontown, Pa.	WMB8 590 C	Washington, Ga.	WTOP 1500 C WKLE 1370	IW hitesburg Kv.	WTCW 920 WENC 1220	Yankton, S.D. KYNT 145 WNAX 57
Urbana, III,	WILL 580 WKID 1580 WIBX 950 C	Washington, Ind.	. WAMW 1580	Whiteville, N.C. Wichita, Kans.	KAKE 1240 M	Yarmouth, N.S. CJLS 134
Utica, N.Y.	MRAM 1250	Washington, lowa Washington, N.J	. WCRV 1580		KLEO 1480 M KFDI 1070 N	Yazoo City, Miss. WAZF 123
	WRUN 1150 WTLB 1310 A	1	WITN 930 A		KFH 1330 C KSIR 900	Yellowknife, N.W.T. CFYK 134
Uvalde, Tex.	KVDU 1400	Washington, Pa.	. WJPA 1450 M	Wishian Falls T.	KWBB 1410	York, Nebr. KAWL 137 York, Pa. WNDW 125
Val D'Or, Que. Valdese, N.C.	CKVD 1230 WSUM 1490	Washington Court	WCHO 1250	Wichita Falls, Te	KTRN 1290	I WORK 185
Valdosta, Ga.	WGDV 950 M WGAF 910 A	Waterbury, Conn.			KWFT 620 C KAKA 1250	York, S.C. WSBA 91
	WJEM 1150 WVLD 1450	1	WWC0 1240 M	Wickford, R.I.	WKFD 1370	Yorkton, Sask. CJGX 94 Youngstown, Ohio. WBBW 124
Valentine, Nebr.	WVLD 1450 KVSH 940	Waterbury, Vt. Waterloo, lowa	WDEV 550 M KXEL 1540 A	Wildwood, N.J. Wilkes-Barre, Pa	WCMC 1230 M WBAX 1240 M	W F M J 139
Vattelo, Catif.	KNBA 1190	1	KNWS 1090 KWWL 1330 M		WBRE 1340 N WILK 980 A	Ypsilanti, Mich. WKBN 57
Valley City, N. Da Valleyfield, P. R.	CFLV 1370	Watertown, N.Y.	WATN 1240	Willeox, Ariz.	KWCX 1250	Yreka, Callf. KSYC 149
Valparaiso-Nicevi	IIC, FIA. WNSM 1340		WDTT 1410 WWNY 790 C		. WBCI 740	KAGR 145
Van Buren, Ark. Van Cleve, Ky.	KFDF 1580 WMTC 730	Watertown, S.Da	k. KSDR 1480 KWAT 950 M	Williams Lake, B	.C. CKCQ-1 1240	Yuma, Ariz. KOFA 124 KBLU 132
Van Wert, Unio	WERT 1220	Watertown, Wis.	WTTN 1580	Williamson, W.V.	n. WBTH 1400 M	KBLU 132 KVDY 140 KYUM 56
Vanceburg, Ky. Vancouver, B.C.	WKKS 1570 CBU 690	Waterville, Me. Watseka, III.	WTVL 1490 A WGFA 1360	Williamsport, Pa	WRAK 1400 N	Zanesville, Ohio WHIZ 124
	CFUN 1410 CHQM 1320	Waterville, Me. Watseka, III, Watsenville, Cali Wauchula, Fla,	f, KOMY 1340	Williamston, N.C	WWPA 1340 C	Zarephath, N.J. WAWZ 138 Zephyr Hills, Fla. WZRH 140
	OHUM 1320	IR C AI	A CACALO			1
				s by Call		
				1		C.L. Location
	A -1 1000	KACE Riverside,	. Calif. 1570		s, Mo. 1460	KAGR Yuba City, Calif.
	Ariz. 1230	N KACI The Dalle	s. Oreg. 1300	KAFP Pataluma.	Calif. 1490	KAUI ANBCOLLES. WEST.
KAAA Kingman, KAAB Hot Sprin KAAY Little Ro	ek, Ark. 1094	N KACI The Dalle	s. Oreg. 1300 Tex. 1360	KAFP Petaluma, KAFY Eakersfield	Calif. 1490 f. Calif. 550	KAHI Auburs, Calif.
KAAA Kingman, KAAB Hot Sprin	ck, Ark. 1090 les. Calif. 790	NACI The Dalle KACT Andrews,	Tex. 1360 neme, Calif. 1520	KAFY Eakersfield KAGE Winona, I KAGH Crossett,	f, Calif. 550 Ninn. 1380 Ark, 800	

	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
	KAHR	Redding, Calif. Kaimuki, Hawaii	1330	KBIX	Muskogee, Okla.	1490	KCLU	Rolla Mo	1590	KELO	Sinux Falle C Det	1320
	KAIK	Lucson, Ariz.	1490	KBJT	Ottumwa, Iowa Fordyce, Ark.	1570	KCLW	Clovis, N.Mex. Hamilton, Tex. Colfax, Wash.	1640	RELP	El Paso, Tex.	920 1460
	KAJI	Little Rock, Ark. Grants Pass, Oreg.	250	REKE	Baker, Oreg	1490	KCLX	Colfax, Wash.	1450	KEIV	Fiv May	1230
	KAKA	Wickenburg, Ariz	1250	KBLA	Burbank, Calif.	1490	KCMJ	Texarkana, Tex. Palm Sprgs., Calif.	1010	KENA	Mena, Ark. Toppenish, Wash	1450 1490
	KAKE	Tulsa, Okla. Wichita, Kan.	970	KBLF	Aberdeen, Wash. Burbank, Calif. Red Bluff, Calif. Blackfoot, Idaho	1490 690	KCMO	Texarkana, Tex, Palm Sprgs., Calif. Kansas City, Mo. Manitou Sprgs., Cole	810	KEN	Anchorage, Alaska	550
	KALB	Alexandria, La				1550						1340 1450
	KALF	Richland, Wash, Mesa, Ariz.	960	KBLU	Big Lake, Tex. Yunia, Ariz. Gold Beach, Oreg.	1290	IKCNO	Alturas, Calif. San Marcos, Tex.	570 1470	KENI	Farmington M M	1200
	KALG	Alamogordo, N. Mex.	1230	KBLY	Gold Beach, Oreg.	1220	KCOB	Newton, Iowa Centerville, Iowa	1280	KENS	Las Vegas, Nev. San Antonio, Tex. Bellingham-Ferndale,	1460 680
	KALL	Pasadena, Calif. Salt Lake City, Utah	910	KBMN	Bozeman, Mont.	1230	KCOG	Centerville, Iowa Houston, Tex.	1400	KENY	Bellingham-Ferndale, Wash.	930
	NALM	Thayer, Mo. iola, Kan.	1290	KRMO	Benson, Minn. Breckingdg., Minn.	1290	KCOK	Houston, Tex. Tuiare, Calif.	1270	KEOK	Payette, Idaho Flagstaff, Ariz.	1450
	KALT	Atlanta, Tex.	900	KBMX	Coalinga, Calif.	1470	KCON	Ft. Collins, Colo. Conway, Ark.	1410	KEPR	Kennewick, Wash. Eagle Pass, Tex.	610
	KAMU	Camden, Ark.	910	IKHNO	Hend ()rea	1240	LUGAN	San Antonio, Tex.	1350	KEPS	Eagle Pass, Tex. Kermit, Tex.	1270 600
	KAML	Kenedy, Tex. Rogers, Ark.	990	KBOA	Kennett, Mo. Oskaloosa, Juwa	830	KCOY	Alliance, Nebr. Santa Maria, Calif.	1400	KERC	Eastland, Tex.	1590
	KAMP	El Centro, Calif. McCamey, Tex.	1430	KBO	Boise, Idaho	950	KCRA	Santa Maria, Calif. Salt Lake City, Utah Sacramento, Calif. Chanute, Kans.	1320	KERN	Bakersfield, Calif.	1280 1410
	KAMY	McCamey, Tex. Anaconda, Mont.	1450	KBOK	Boise, Idaho Malvern, Ark. Boulder, Colo.	1310	KCRB	Chanute, Kans. Enid, Okla.	1460	KERV	Kerrville, Tex.	1230
	KANB	SHIEVEDORY, La.	1300	KBOM	Bisniark-Mandan,		KCRG	Cedar Rapids, Iowa	1600	KEST	Eldorado Springs, Mo. Boise, Idaho	790
	KANE	Corsicana, Tex. New Iberia, La.	1340	KBON	Omaha, Nebr.	1270	KCRM	Crane. Tex	1380	KETO	Seattle, Wash.	1590
	KANI	Wharton, Tex. Ogden, Utah	1500	KBOP	Pleasanton, Tex. Brownsville, Tex.	1380	KCRT	Midiand, Tex. Trinidad, Colo.	1240	KEUN	Eunice, La. Minneapolis, Minn.	1490
	KANO .	Anoka, Minn.	1470	KBOW	Butte, Mont. Dalias, Tex.	1490	LKCSI	Caruthersville, Mo. Pueblo, Colo.	280	VEAF	White Castle, La.	1440
	KANS I	Independence, Me. Duluth, Minn,	1390	KBOY	Medford, Ores	1480 730	KCSR	Chadron, Nebr. Corpus Christi, Tex.	1450	KEVT	Tucson Ariz	690
	KAOK	Lake Charles In	1400	KBPS	Portland, Orea.	1450			1450	KEWI	Oakland, Calif. Topeka, Kans.	1440
	KAPA	Carroliton, Mo. Raymond, Wash.	1430 1340	KBRI	Mt. Vernon, Wash. Brinkley, Ark.	1570	KCUB	Childress, Tex. Tucson, Ariz. Red Wing, Minn. Fort Worth, Tex.	1510	KEXO	Portland, Oreg. Grand June., Colo.	1190
	KAPB	Marksville, La. San Antonio, Tex.	1370	KBRK	Brookings S Dak	1430	KCUE	Red Wing, Minn,	1250	KEYD	Grand June., Colo. Oakes, N. Dak. Perryton, Tex.	1220
	KAPI P	ueblo. Coio	690	KBRN	McCook, Nebr. Brighton, Colo.	000			1270	KEYJ	Jamestown, N.Dak.	1400
	KAPSI	Douglas, Ariz. Mt. Vernon, Wash.	1.470	KHRR	Bremerton, Wash. Leadville, Colo.	1490	KCYR	Lodi, Calif. Lampasas, Tex. Arvada, Colo.	1570	KEYL	Long Prairie, Minn. Terrytown, Nebr.	1400 690
	NAFI :	Satem, Ure.	1220	KBRS	Springdale, Ark. Soda Sprgs., Ida.	1340	KDAB	Arvada, Colo.	1550	KEYS	Corpus Christi, Tex.	1440
	KARA	Albuquerque, N.M.	1290	KBRX	O'Neill, Nebr. Freeport, Texas	1350	KDAD	Ft. Bragg, Calif. Weed, Calif. Carrington, N.D.	800	KEYZ	Provo, Utah Williston, N. Dak.	1450 1360
	KARLE	Atchison, Kan. Blaine, Wash,	1470 550	KBSF	Springhill, La.	1460					Williston, N.Dak. Rapid City, S.Dak. Anaheim, Calif.	920
	CARK	Little Rock, Ark. Fresno, Calif.	920	KBST	Springhill, La. Big Spring, Tex.	1490	KDAN	Duluth, Minn, Eureka, Callf, Lubbock, Tex, Santa Monica, Calif, Santa Barbara, Calif, Mansfield	790	KFAB	Omaha, Nebr. Los Angeles, Calif.	1110
	KARR	Great Falls, Mont	1400	KBTM	Batesville, Ark. Jonesboro, Ark.	1340 1230	KDAY	Lubbock, Tex. Santa Monica, Calif.	580 1580	KFAL	Los Angeles, Calif.	1330 900
	CARS E	Belen, N.M. Jerome, Idaho	860	KBTN	Neosho, Mo, El Dorado, Kans,	1420	KDB	Santa Barbara, Calif.	1490	KEAM	St. Cloud, Minn. Fairbanks, Alaska	1450
j	CARY	Prosser, Wash. Austin. Tex.	1310	KBTR	Denver, Colo. Corona, Calif.	710	KDBM	Dillen, Ment.	800	KFAX	San Francisco Calif	610
- 1	CASH I	Eugene, Ore.	16001	KBUD	Athens, lex.	1410	KUBS	Alexandria, La. Dumas, Tex.	800	KFAY	Fayetteville, Ark. Great Falls, Mont.	1250
	KASIA	mes, lowa			Brigham City, Utah Bemidji, Minn.	800 1450	KDEC	Decoran, lowa	1240	KFBC	Chevenne, Wvo	1240
- 1	(ASL N	lewcastle, Wyo.	1240	KBUR	Burlington, lowa	1490	KDEN	Albuquerque, N.Mex. Denver, Colo.	1340	KFCB	Sacramento, Calif. Redfield, S. Dak.	1530
	CASO	Albany, Minn. Hinden, La.	1150	KBUY	Burlington, lowa Mexia, Tex. Amarillo, Tex.	1590	KDEO	El Cajon, Calif. Palm Spres., Calif.	910 920	KEDA	Amarillo, Tex.	1440
1	CAST A	ASTORIA, Ure.	1370	K B U Z	Mesa, Ariz.	1310	KDFI	Center Tax	930	REDI	Wichita Kansas	1070
į	ATE A	libert Lea. Minn.	1450	KBVU	Lancaster, Calif. Bellevue, Wash.	1380	KDEY	Dexter, Mo. Boulder, Colo. Durango, Colo.	1590 1360	KFDR	Beaumont, Tex. Grand Coulee, Wash.	560 1360
			1400	KBYE	Brownwood, Tex.	1380 890	KDGO	Durango, Colo. Twenty-nine Palms,	1240		Pueblo, Colo. St. Joseph, Mo.	970
- [CATN E	diles City, Mont, Boise, Idaho Safford, Ariz,	1010	KBYG	Okła. City, Okła. Bło Spring, Tex. Shamrock, Tex.	1400		California	1250	KFFA	Helena, Ark.	1360
- 4	CATUIT	exarkana. lex.				1580	KDIA	Farlbault, Minn. Oakland, Calif.	920	KFGQ	Fargo, N.D. Boone, Jowa	790 1260
,	CATR E	Eugene, Ore. San Luis Obispo, Cal.	1320	KBZY	Salem, Oreg. LaJunta, Colo.	1490	KUIU	Ortonville, Minn, Dickinson, N.Dak,	1350	KEH	Boone, Iowa Wichita, Kans.	1330
- 1	CATZ S	t. Louis, Mo.	1600	KCAC	Phoenix, Ariz.	1010	KDJI	Holbrook, Ariz.	1230	KFIF	Tueson, Ariz.	640 1550
- 1	CAVEC	Carlsbad, N.Mex.	1240	KCAL	Abilene, Tex. Redlands, Calif. Helena, Mont.	1560	KDKA	Pittsburgh, Pa.	1020	KFIG	Tucson, Kans, os Angeles, Calif, Tucson, Ariz, lowa Falls, lowa Modesto, Calif. Fond du Lac, Wis, Marshalltown, lowa	1510
1	CAVLR	ocky Ford, Colo. ancaster, Calif.	1320	KCAP	Helena, Mont, Clarksville, Tex.	1340	KDLA	DeRidder, La. Del Rio, Tex. Detroit Lakes, Minn.	1010	KFIZ	Fond du Lac, Wis.	1450
1	CAVRA	Apple Valley, Calif.	960	KCAS	Slaton, Tex. Des Moines, Iowa	1050	KDLM	Detroit Lakes, Minn.	1340	KEIM	Grand Forks N Dak	1230 1370
- 1	CAWL	York, Neb.	1010	KCBD	Lubbock, Tex.	1390	KULK	Devils Lake, N.Dak. Perry, Iowa	1310	KFKA	Ft. Worth, Tex.	1270
- 1	CAWT	Douglas, Ariz	1450	KCBO	San Diego Calif	740	KDMA	Montevideo, Minn.	1450 1490	KEKE	Bellevue, Wash.	1330
į	CAYE	Puvallun Wach	1450	KCCL	San Fran., Calif. Paris, Ark.	1460	KDMS	El Dorado, Ark.	12901	KFLD	Floydada, Tex.	900
	CATLS	torm Lake, lowa	990	KCCR	Lawton, Okta. Pierre, S. Dak. Corpus Christi, Tex.	1050	KDOK	El Dorado, Ark. Denton, Tex. Tyler, Tex.	1330	KFLT	Walsenburg, Colo. Mountain Home, Ida	1380
H	(AYD S	Seattle, Wash.	1150	KCCT	Corpus Christi, Tex. Kirkland, Wash	1150			1340	KFLW	Klamath Falls, Oreg.	1450
ŀ	CAYT R	lays, Kans lupert, Idaho lan Saba, Tex. Longview, Wash,	970	KCEE	Trusson, Wash Tucson, Ariz Tuniock, Calif, Spokane, Wash, Cuero, Tex. Cedar Falis, Iowa	790	KDON	Windom, Minn. Salinas, Calif.	1460	KEMB	San Diego Calif	1240 540
j	BAM	Longview, Wash,	1270	KCFA	Spokane, Wash.	1330		Medford Oren			Danvar Colo	1050
ŀ	BAR E	Bowle, Tex. Burley, Idaho	1410	KCFH KCFI	Cuero, Tex. Cedar Fails, Iowa	1600 1250	KDON	Medford, Oreg. DeQueen, Ark. Sedalia, Mo.	1390	KEMO		1240
ŀ	BBA E	Burley, Idaho Benton, Ark. Borger, Tex. Centerville, Utah	690	KCGM	Columbia, Mo.	1580	KDRS	Paragould, Ark.	1490	KENV	Ferriday, La.	920 1600
1	BBC C	enterville, Utah	1600	KCHE	Cherokee, lowa	1580	KDSN	Denison, Iowa	1580	KFOR	Lincoln, Nebr	900 1240
i	BBR	Yakima, Wash, North Bend, Oreg.	1390	KCHI	bnillicotne, Mo.	1010	KDSX	Denison, Tex.	950	KEOX	Long Beach, Calif.	1280
- 1	(BBS B	luffalo, Wyo.	1450	KCHR	Charleston, Mo.	1350	KDTH	Dubuque, Iowa	1370	KFQD	Anchorage, Alaska	730 730
1	BCL S	hreveport, La.	1380	KUMS	I ruth or Consequences	1400	KDWB	Sedalia, Mo. Paragould, Ark. Deadwood, S. Dak. Denison, Iowa Denison, Iowa Denison, Tex. Delta, Colo. Dubuque, Iowa Hutchinson, Minn. St. Paul, Minn. St. Paul, Minn. St. Boorge, Utah Touche, Utah Touch, Utah Touch, Colo. Brownwood, Tex. Fresno, Calif.	630	KFRA	Franklin, La. Fairbanks, Alaska	1390 900
	UBEA N	Mission, Kans	1480	KCHY	Coachella, Calif. Cheyenne, Wyo. Caldwell, Idaho	970 1590	KDWT	Stamford, Tex.	1200	KFRC	Fairbanks, Alaska San Francisco, Calif. Rosenberg, Tex. Fresno, Calif. Kansas City, Mo.	610
-	BEE N	Andesto, Callf.	970	KCID (Caldwell, Idaho	1490	KDXU	St. George, Utah	1450	KFRE	Fresno, Calif.	980 940
- 1	BELL	tik City, Okia,	1240	KCII W	hermont la	1380	KDZA	Pueblo, Colo.	990	KFRM	Kansas City, Mo.	550 1370
1	BEN C	Carrizo Sprgs., Tex.	1450	KCIL I	fouma, La. Carroll, lowa /ictorville, Calif, Minot, N.Dak. San Luis Obispo, Cal.	1490	KEAN	Brownwood, Tex.	1240	KERII	Columbia Mo	1400
	BET A	eno, Nev.	1340	KCIN	ictorville, Calif.	1590	KEBE	Jacksonville, Tex.	1400	KESB	Joplin, Mo.	950 1310
	BFS B	ortland, Oreg. Belle Fourche, S. Dak	1450	KCIH :	Minot, N.Dak. San Luis Obisco, Cal.	910	KECK	Fresno, Calif, Jacksonville, Tex. Odessa, Tex. Dodge City, Kans.	920	KESD	Denver, Colo.	1220 600
		Caldwell, Idaho	910	KCKC	San Bernardine, Cal.	1350		Longview, Wash.	1400	KFSG	Los Angeles, Calif.	1150
-	BHC	Waco, Tex. Vashville, Ark.	1260	KCKN	Kansas City, Kans.	1340	KEEE	Springfield, Oreg. Nacogdoches, Tex. Shreveport, La.	1230	KFTM	Ft. Morgan, Colo.	860 1400
į,	BHS	Branson, Mo. lot Springs, Ark.	1220 590	KCKY	Jena, La. Coolidge, Ariz.	1480	KEEL	Shreveport, La. San Jose Calif	710	KETW	Paris, Tex.	1250 1450
	CRIE E	resno, Calif.	900	KCLA	Pine Bluff, Ark.	1400	KEEP	San Jose, Calif. Twin Fails, Idaho Gladewater, Tex.	1450	KFUN	Las Vegas, N.Mex.	1230
	CDIM L	raion, Carry,	910	KCLF	San Luis Obispo, Cal. San Bernardino, Cal. Sonora, Tex Kansas City, Kans. Jena. La. Jena. La. Pine Bluff, Ark. Cleburne, Tex. Clifton, Arlz. Clinton, Jowa Leavenworth. Kans	1400		Kallua, Hawaii	130	KFVS	San Diego, Calif. Los Angeles, Calif. Ft. Stockton, Tex. Ft. Morgan, Colo. Paris, Tex. Frederickstown, Mo. Las Vegas, N.Mex. St. Louis, Mo. Cape Girardeau, Mo. Los Angeles Calif.	850 960
1	(B 12 B	akersfield, Calif.			Clinton, lowa Leavenworth, Kans.	1410	KELD	Centralia, Wash. El Dorado, Ark. Julsa, Okla.	1470	KFWB	Los Angeles, Calif. Nampa, Idaho	080
1	78	WHITE'S RADIO L			Rails, Tex.	1530	KELL T	ulsa, Okla. Eiko, Nov.	1430	KFXM	Nampa, idaho San Bernardino, Caiif.	590
						2001		mind! (464*		NT TH	Bonham, Tex.	1420

C.L. Location		C.L. Location				C.L. Location	Kc.
KFYO Lubbock, Tex.	790	KICM Golden, Colo.	1250 1490	KLIF Dallas, Tex. KLIK Jefferson City, Me.	950	KNEL Brady, Tex. KNEM Nevada, Mo.	1490
	550 1510	KICO Calexico, Calif. KICY Nome, Alaska	850	KLIL Estherville, lowa	1340		1450
KGAF Gainesville, Tex.	1580	KID Idaho Falls, Idaho KIDD Monterey, Calif.	690	KLIP Fowler Calif.	1400	KNEW Spokane, Wash. KNEX McPherson, Kans.	790 1540
KGAL Lebanon, Oreg.	920	KIDO Boise, Idaho	630	KLIQ Portland, Oreg, KLIR Denver, Colo, KLIX Twin Falls, Idaho	1290	KNEZ Lompoc, Calif.	960 620
KGAS Carthage, Tex. KGAY Salem, Oreg.	1590 1430		870 1260	KLIR Denver, Colo, KLIX Twin Falls, Idaho	990		1320
KGB San Diego, Calif.	1360	KIFN Phoenix, Ariz.	860	KLIZ Brainerd, Minn.	1380	KNIM Marvylile, No.	1580 990
KGBC Galveston, Tex. KGBS Los Angeles, Calif.	1540 1020	KIFW Sitka, Alaska KIHN Hugo, Okla.	1230	KLLA Leesville, La.	1540 1570	KNIN Wichita Falls, Tex. KNIT Abilene, Tex.	1280
KGBT Harlingen, Tex.	1530	KIHR Hood River, Oreg.	1340	KLLL Lubbock, Tex.	1460 1490	KNND Cottage Grove, Oreg. KNOC Natchitoches, La.	1400 1450
KGBA Springheld, Mo. KGCA Rugby, N.D.	1260 1450	Kijv Huron, S.Dak. Kiki Honolulu, Hawaii	830		1050	KNOE Monroe, La.	1390
KGCX Sidney, Mont.	1480 630	KIKK Pasadena, Tex,	650 1340	KLMR Lamar, Colo. KLMS Lincoln, Nebr.	920	KNOG Nogales, Ariz,	1340 970
KGEE Bakersfield, Calif.	1230	KIKS Suiphur, La.	1310	KLMX Clayton, N.Mex.	1450	KNOK Ft. Worth, Tex. KNOP N. Platte, Nebr.	1410
KGEK Sterling, Colo. KGEM Boise, Idaho	1230	KILE Galveston, Tex, KILD Grand Forks, S.Dak.	1400	KLO Ogden, Utah KLOA Ridgecrest, Calif	1240	KNOR Norman, Okia. KNOR Norman, Okia. KNOT Presentt, Ariz. KNOW Austin, Tex. KNOW Grand Forks. N.Dak. KNOT Newport, Dre.	1450
KGEN Tuiare, Calif.	1370	KILT Houston, Tex.	610	KLOE Goodland, Kans.	730	KNOW Austin, Tex.	1490
KGER Long Beach, Calif, KGEZ Kalispell, Mont,	1390 600	KIMA Yakima, Wash. KIMB Kimball, Nebr.	1460 1260	KLOG Kelso, Wash. KLOH Pipestone, Minn.	1050	KNOX Grand Forks, N.Dak. KNPT Newport, Dre.	1310
KGFF Shawnee, Okla.	1450	KIMM Rapid City, S.D.	1150	KLUK San Jose, Calli.		KNUI Makawao, Hawaii KNUJ New Ulm, Minn.	1310 860
KGFJ Los Angeles, Calif. KGFL Roswell, N.Mex.	1400	KIMN Denver, Colo.	1490 950	KLOO Corvallis, Dreg. KLOS Albuquerque, N.Mex.	1450	KNUZ Houston, Tex.	1230
KGFW Kearney, Nebr. KGFX Pierre, 8.Dak. KGGF Coffeyville, Kans.	1340 630	KiMO Hilo, Hawaii	850 960	KLOU Lake Charles, La.	1580 l	KNWC Sieux Fails, S.D. KNWS Waterloo, Iowa	1270
KGF Coffeyville, Kans.	690		1010	KLPC Lompoc. Calif.	1330	KNX Los Angeles, Calif.	1070
KGGG Forest Grove, Oreg. KGGM Albuquerque, N.Mex.	1570 610		1090	KLPL Lake Providence. La.	1050	KOA Denver, Cole,	850 550
KGHF Pueblo, Colo.	1350	KINS Eureka, Calif.	980	KLPM Minot, N.Dak. KLPR Dkla. City, Okla.	1140	KOAC Corvallis, Oreg. KOAL Price, Utah	1230
KGHL Billings, Mont. KGHM Brookfield, Mo.	790 1470	KINT El Paso, Tex. KINY Juneau, Alaska	1590 800	KLPW Union, Mo. KLRA Little Rock, Ark.	1220	KOAM Pittsburg, Kans. KORR Oroville, Calif.	860 1340
KGHS International Falls.	- 1	KIDA Des Moines, lowa	940	KLRS Mountain Grove, Mo.	1360	KOB Albuquerque, N. Mex.	770
Minn. KGHT Hollister, Calif.	1230 1520	KIOT Barstow, Calif. KIOX Bay City, Tex.	1310	KLTF Little Falls, Minn. KLTR Blackwell, Okla.	960 1580	KOBE Las Cruces, N.Mex. KOBH Hot Springs, S.Dak.	1450 580
KGIL Şan Fernando, Calif.	1260	KIPA Hilo, Hawaii	1110	KLTZ Glasgow, Mont.	1240	KOCA Kilgore, Tex.	1240 1340
KGIW Alamosa, Colo. KGKB Tyler, Tex.	1450 1490	KIQS Willows, Calif.	1560 710	KLUB Salt Lake City, Utah KLUC Las Vegas, Nev.	570 1050	KOCY Oklahoma City, Okla. KODA Houston, Tex.	1010
KGKL San Angelo, Tex.	960	KIRT Mission, Tex.	1580	KLUE Longview, Tex.	1280	KODE Joplin, Mo.	1230 1400
KGLC Miami, Okla. KGLE Glendive, Mont.	910 590	KIRX Kirksville, Mo. KISD Sioux Falls, S.Dak.	1230	KLUK Evanston, Wyo. KLUV Haynesville, La.	1240 1580	KODI Cody, Wyo. KDDL The Dalles, Dreg.	1440
KGLE Glendive, Mont. KGLN Glenwood Spres., Colo.	980	KISN Portland, Dre.	910	KLVL Pasadena, Tex. KLVT Levelland, Tex.	1480 1230	KDDL The Dalles, Dreg. KDDY North Platte, Nebr.	1240 950
KGLO Mason City, Iowa KGLU Safford, Ariz.	1300 1480	KIST Santa Barbara, Calif. KIT Yakima, Wash.	1280	KLWN Lawrence, Kans.	1320	KOEL Oelwein, Iowa KDFA Yuma, Ariz.	1240
KGMB Honolulu, Hawali	590 1150	KITE San Antonio, Tex.	930	KLWT Lebanon, Mo.	1230 1450	KOFE Pullman, Wash. KDFI Kalispell, Mont.	1150 930
KGMI Bellingham, Wash.	790	KITN Olympia, Wash,	1420 920	KLWN Cedar Rapids, Ia. KLYD Bakersfield, Calif.	1350	KOFO Ottawa, Kans.	1220
KGMO Cana Girardaau, Mo.	1220 1386	KIUL Garden City, Kans.	1240	KLYK Spekane, Wash.	1230 980	KOFY San Mateo, Calif. KOGA Ogallala, Nebr.	1050 930
KGMS Sacramento, Calif. KGMT Fairbury, Nebr.	1310	KIUN Pecos, Tex.	930	KLYQ Hamilton, Mont. KLYR Clarksville, Ark.	1360	KOGT Orange, Tex.	1600
KGNB New Braunfels, Tex. KGNC Amarillo, Tex.	1420 710	KIVY Crockett, Tex.	1290	KLZ Denver, Colo. KMA Shenandoah, Iowa	560 960	KOH Reno, Nev. KOHO Honolulu, Hawaii	630 1170
KGNO Dodge City, Kans.	1370	KIXX Provo. Utah	1400	KMAC San Antonio, Tex.	630	KOHU Hermiston, Orea,	1570
KGNS Laredo, Tex. KGO San Francisco, Calif.	810	I KIAL AMATINO, 10A.	940 1150	KMAD Madiil, Okla.	1550 1600	KDIL Omaha, Nebr. KOIN Portland, Ores.	1290 970
KGDN Oregon City, Oreg.	1520	KJAM Madison, S.Dak.	1390		134Q	KOJM Havre, Mont.	610
KGDN Oregon City, Oreg. KGOS Torrington, Wyo. KGPC Grafton, N.Dak.	1490	KJAX Santa Rosa, Calif.	1220 1150	KMAN Butler, Mo. KMAN Manhattan, Kans.	153G 135G	KOKA Shreveport, La. KOKE Austin, Tex.	1550 1370
KGHI Henderson, lex.	940	KJAY Sacramento, Calif.	1430	i KMAQ Maqueketa, Jowa	1320- 1570	KOKL Okmulgee, Okla, KOKO Warrensburg, Mo.	1240 1450
KGRL Bend, Oreg. KGRN Grinnell, lowa	1410	KJCF Festus, Mo.	1400	KMAR Winnsboro, La. KMBC Kansas City, Mo.	980	KOKX Keekuk, lowa KOKY Little Rock, Ark.	1310
KGRO Gresham, Oreg. KGRT Las Cruess, N.Mex.	1230 570		1420 1290	KMBL Junction, Tex. KMBO Tucson, Ariz.	1450 940	IKΩL Seattle, Wash.	1440
KGST Fresno, Calif.	1600	KJEM Oklahoma City, Okla.	800	KMBY Monterey, Calif.	1246	KOLD Tucson, Ariz.	1450
KGU Henelulu, Hawall KGUC Gunnisen, Colo.	760 1490	KJF1 Webster City, Iowa	1380 1570	KMCD Fairneld, lowa KMCM McMinnville, Oreg.	1570	KOLE Port Arthur, Tex.	1150
KGUD Santa Barbara, Calif. KGUL Port Lavaca, Tex.	990 1560	KJIM Pt. Worth, lex.	870 1400	KMCO Conroe, Tex.	900	KOLO Reno, Nev. KOLR Sterling, Colo.	920 1490
KGVL Greenville, Tex.	1400	KJLT North Platte, Nebr.	970	KMED Medford, Oreg.	1446	KOLS Prvor. Okla.	1570
KGVL Greenville, Tex. KGVO Missoula, Mont. KGVW Belgrade, Mont.	1290 630		630 1480	KMEN San Bernardine, California	1296	KOLT Scottsbluff, Nebr. KOLY Mobridge, S. Dak.	1320
KGW Portland, Ores.	620	KJOY Stockton, Calif.	1280	KMEO Omaha, Nebr.	66#	KOMA Okla. City, Okla. KOME Tulsa, Okla.	1520 1300
KGWA Enid, Okla. KGY Olympia, Wash.	960 1240	KJR Seattle, Wash.	1390 950	KMER Medford, Ore.	930 860	I KIIMII MARTIIA. WASH.	1000
KGYN Guymon, Dkla. KAHI Honolulu, Hawaii	1220	KJRG Newton, Kans.	950 900	IKMCM Albunuernue N. Mex	73W	KOMW Omak, Wash. KOMY Watsonville, Calif.	680 1340
KHAK Cedar Rapids, Iowa	1380	KKAL Danver City, Tex.	1580		1330	KONE Rene, Nev.	1450
KHAL Homer, La. KHAR Anchorage, Alaska	1300 590		1490 1220	KMIN Grants, N.M. KMIS Portageville, Mo.	980	KONG Visalia, Callf. KONI Spanish Fork, Utah	1400
KHAS Hastings, Nebr.	1230	KKAS Silsbee, Tex.	1300	KMI Freena Calif	580	KONO San Antonio, Tex. KDNP Port Angeles, Wash,	860
KHAT Phoenix, Ariz, KHBC Hilo, Hawali	1480 970	KKEY Vancouver, Wash. KKHI San Francisco, Calif.	1150	KMLB Monroe, La. KMMJ Grand Island, Nebr.	1444 750	KONP Port Angeles, Wash,	1450 970
KHBM Menticelle, Ark.	1430	KKID Pendleton, Dreg.	1240	KMMJ Grand Island, Nebr. KMNS Sieux City, Iowa	620	KOOK Billings, Mont, KOOL Phoenix, Ariz,	960 1420
KHBR Hillsboro, Tex. KHEM Big Springs, Tex.	1270	KKIS Pittsburg, Calif.	990	KMON Great Falls, Mont.	568	KOOO Omaha, Nebr. KOOS Coos Bay, Oreg.	1230
KHEN Henryetta, Okla, KHEP Phoenix, Ariz.	1590	KKIT Taos, N.Mex.	1340	KMOP Tueson, Ariz.	1330	KOOS Coos Bay, Oreg, KOPR Butte, Mont, KOPY Alice, Tex, KOQT Bellingham, Wash.	550 1070
KHER Santa Maria, Calif.	1600	KKOK Lompoc, Calif.	1410	KMOX St. Louis, Mo.	1120	KOQT Bellingham, Wash.	1550 1240
KHEY El Paso, Tex. KHFH Fry, Ariz.	690 1420	KLAC Les Angeles, Calif. KLAD Klamath Falls, Oreg.	570 960	KMPC Los Angeles, Calif.	1439	KORA Bryan, Tex. KORC Mineral Wells, Tex.	1140
KHHH Pampa, Tex. KHIT Walla Walla, Wash, KHJ Los Angeles, Calif. KHMO Hannibal, Mo.	1230	KLAK Lakewood, Colo.	1600	KMRS Morris, Minn.	1230	KORD Pasco, Wash, KORE Eugene, Oreg. KORK Las Vegas, Nev. KORN Mitchell, S. Dak. KORT Grangeville, Idaho	910
KHIT Walla Walla, Wash, KHI Los Anneles, Calif.	930	KLAM Corgova, Alaska	1320	KMUL Muleshoe, Tex.	1380	KORE Eugene, Oreg. KORK Las Vegas, Nev.	1450 1340
KHMO Hannibal, Mo.	1070	KLAS Las Vegas, Nev.	1230	KMUR Murray, Utah	1230	KORN Mitchell, S.Dak.	1490 1230
KHDB Hobbs, N.Mex. KHOE Truckee, Calif. KHOG Fayetteville, Ark.	1400	KLBM La Grande, Oreg.	1450	KMVI Walluku, Hawail	550	KDSA Odessa, Tex. KOSE Osceela, Ark.	1230
KHOG Fayetteville, Ark.	1440	KLBS Los Banes, Calif.	1330	KMYC Marysville, Calif.	1410	KOSE Oscoola, Ark.	860 1430
KHDT Madera, Calif.	1250	KLCN Blytheville, Ark.	910	KNAF Fredericksburg, Tex.	910	KDSY Texarkana, Ark.	790
KHOW Denver, Colo.	630 900	KLCO Poteau, Okla.	1280 630	KNAK Salt Lake City, Utah	1280	KOTA Rapid City, S.Dak.	1380 1250
KHOK Hoquiam. Wash. KHOK Hoquiam. Wash. KHOT Madera, Calif, KHOW Denver, Colo. KHOZ Harrison, Ark, KHQ Spokane, Wash. KHQI Hemet, Calif. KHQI Chico, Calif.	590	KLEE Ottumwa, Iowa	1480	KNBA Vallejo, Calif.	1190	KOTN Pine Bluff, Ark.	1490
KHSJ Homet, Calif. KHSL Chico, Calif.	1320	KLEN LeMars. Iowa	1410	KNBC San Francisco, Calif.	1240	KUIS Deming, N.M. KOUR Independence, lows	1230 1220
KHSL Chico, Calif. KHTN Hooston, Mo.	1250	KLEN Killeen, Tex.	1050	KNBX Kirkland, Wash.	1050	KOVC Valley City, N. Dak.	1490
KHUB Fremont, Nebr. KHUM Santa Rosa, Calif.	1580	KLER Drofino, Idaho	950	KNCK Concordia, Kans.	1390	KOVD Provo, Utah	1330 960
KHUM Santa Rosa, Calif. KHUZ Borger, Tex. KHVH Honoluly, Hawali	1490	KLEX Lexington, Mo.	1570	KNCM Moberly, Mo.	1230	KOWB Laramie, Wyo.	1290 1490
KIAL Astoria, Dre.	1230	KLEF Mead, Wash.	1590	KNCY Nebraska City, Nebr.	1600	KDWN Escondido, Callf.	1450
KIAL Astoria, Dre. KIBE Pale Alte, Calif. KIBH Seward, Alaska	1220	KLGA Algena, lewa KLGN Legan, Dish	1800	KNDC Hettinger, N.Dak.	1490	KDXR Oxnard, Calif.	910 550
KIBL Beeville, Tex.	1490	KLGR Redwood Falls, Minn.	1490	KNDI Honolulu, Hawail	1270	KOSE Osceela, Ark. KDSI Aurora, Colo. KDSY Texarkana, Ark. KOTA Rapid City, S.Dak. KOTA Rapid City, S.Dak. KDTE Fergus Falis, Minn. KOTN Pine Bluff, Ark. KDTS Deming, N.M. KOUR Independenee, Iowa KOVC Valley City, N.Dak. KOVE Lander, Wyo. KOVB Laramie, Wyo. KOVB Laramie, Wyo. KOVB Laramie, Wyo. KOWL Blipu, Calif, KDWN Escendide, Calif, KDXR Oxnard, Calif, KDX ROxnard, Calif, KDY Pheenix, Ariz. KOY L Odessa, Tex. KDY Not.	1310
KIBL Beeville, Tex. KIBS Bishop, Calif. KICA Clovis, N.M. KICD Spencer, Iowa	980	KLIB Liberal, Kans.	1470	KNEA Jonesboro, Ark.	970	KDYN Billings, Mont.	910
KICD Spencer, lowa KICK Springfield, Mo.	1240	KLIC Monroe, La.	1230	KNEB Scottsbluff, Nebr.	960	WHITE'S RADIO LOG	179
		KKHI San Francisco, Calif. KKID Pendicton, Dreg. KKIN Altkin, Minn. KKIS Pittsburg, Calif. KKIS Pittsburg, Calif. KKIT Tass, N. Mex. KKJO St. Joseph, Mo. KLOK Lompec, Calif. KLAC Les Angeles, Calif. KLAC Les Angeles, Calif. KLAC Les Angeles, Calif. KLAC Les Angeles, Calif. KLAC Lakewood, Colo. KLAM Cordova, Alaska KLAN Lemoore, Calif. KLAN Lemoore, Calif. KLAS Las Vegas, Nev. KLBK Lubbock, Tex. KLEN KLEO Dotamus, Iowa KLEN Cottumwa, Iowa KLEI Kaliua, Hawali KLEM Cottumwa, Iowa KLEN Killeen, Tex. KLEO Ottumwa, Iowa KLEN Killeen, Tex. KLEO Wichita, Kans. KLER Drofino, Idaho KLEX Lexington, Mo. KLFD Litchfield, Minn, KLEG Algona, Iowa KLGA Algona, Iowa KLGA Algona, Iowa KLGA Redwood Falls, Minn, KLGA Redwood Falls, Minn, KLGA Redwood Falls, Minn, KLGR Redwood Falls, Minn, KLB Libberal, Kans. KLID Poplar Bluff, Mo.				-	

C.L.	Location		C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KOZE	Lewiston, Idaho Chelan, Wash	1300	KRLN	Canon City, Colo. Walnut Ridge, Ark.	1400	KSUE	Susanville, Callf.	1240	KUON	Minneapolls, Minn. Tempe, Ariz. Idaho Falls, Idaho	770
KOZY	Chelan, Wash. Grand Rapids, Minn.	1490	IKRMD	Shreveport, La.	1340	IKSUN	MISDAR APIZ	1370 1230	KUPI	Idaho Falls, Idaho	1060 980
KPAK	Port Arthur, Tex. Minden, La.	1250	KRML	Tulsa, Okta. Carmel, Calif.	1410	KSVC	Richfield, Utah Ogden, Utah	980 730		Moab, Utah Billings, Mont,	1450
KPAL	Palm Springs, Calif. Portland, Oreg.	1450	IKRMO	Monett, Mo. Osage Beach, Mo.	990	IKSVP	Artesia, N. Mex.	990	IKUKY	Edinburg Tex	730 710
KPAN	Hereford, Tex.	860	IKRNO	San Bernardino, Calif		KSWC	Graham, Tex. Tucson, Ariz.	1330 1550	IKUKY	Brookings, Oreg. Vermillion, S.Dak.	910 690
KPAP	Redding, Calif. Banning, Calif.	1490	KRNR	Roseburg, Oreg. Burns, Oreg.	1490	KSWI	Council Bluffs, Iowa A Aurora, Mo.	1560 940	KUSH	Cushing, Okta	1600
KPAY	Chico, Calif. Pine Bluff, Ark.	1060	IKRNT	Des Moines, Iowa	1350	IKSWO	Lawton, Okla.	1380	KUTA	St. Joseph, Mo. Blanding, Utah	790
		1590 740	KROC	Kearney, Nebr. Rochester, Minn.	1460 1340	KSXX	Salt Lake City, Utah Yreka, Calif.	630 1490	KUTI	Yakima, Wash. Fargo, N.Oak.	980
KPBR	El Paso, Tex. Marked Tree, Ark. Grand Prairie, Tex.	1530	KROD	El Paso, Tex. Sheridan, Wyo. Abbeville, La. Brawley, Calif.	600 930	KSYL	Alexandria La	970	KUTY	Palmdale, Calif.	1550
KPCN	Grand Prairie, Tex.	730	KROF	Abbeville, La.	960	KTAC	Santa Rosa, N. Mex. Tacoma, Wash. Taylor, Tex.	1420 850	KUXL	Holdredge, Nebr. Golden Valley, Minn.	1380
KPDQ	Pampa, Tex. Portland, Oreg.	1340	KROP	Brawley, Callf. Clinton, Iowa	1300	KTAE	Taylor, Tex. Tucson, Ariz.	1260 580	KUZN	W. Monroe, La. Bakersfield, Calif.	1310
KPEG	Portland, Oreg. Spokane, Wash.	1380	KROW	Clinton, lowa Dallas, Ore. Crookston, Minn.	1460	IKTAR	Phoenix, Ariz.	620	KVAN	Vancouver, Wash.	1480
KPEP	Lafayette, La, San Angelo, Tex.	1420	KROY	Sacramento, Callf.	1240	IKTBB	Frederick, Okla. Tyler, Tex.	1570 600	KVCK	Wolf Point, Nebr. Winnfield, La.	1450
KPER	Gilroy, Calif. Lamesa, Tex.	1290 690	KRPL	Moseow, Idaho Ruidoso, N.Mex.	1400	KTBC	Austin, Tex. Malden, Mo.	590 1470	KVCV	Redding, Calif	600
KPGE	Page, Ariz. Phoenix, Ariz.	1340	KRRV	Sherman, Tex. Othello, Wash.	910	KTCR	Minneapolis, Minn,	690	KVEE	San Luis Obispo, Calif Conway, Ark.	1330
KPIK	Colorado Spres., Colo.	1580	KRSD	Rapid City, S.Oak, St. Louis Park, Minn.	1400	KTDO	Fort Smith, Ark, Toledo, Oreg.	1410	KVEG	Las Vegas, Nev. Vernal, Utah	970 1250
KPIN	Casa Grande, Ariz. Eugene, Wash,	1260	KRSI :	St. Louis Park, Minn. Russell, Kans.	950 990	KTEE	Idaho Falls, Idaho Walla Walla, Wash.	900	KVEN	Ventura, Calif.	1450
KPKW	Pasco, Wash, Plainview, Tex,	1340	KRSN	Los Alamos, N. Mex.	1490	KTEM	Temple, Tex.	1490	KVFC	Austin, Tex. Cortez, Colo.	1300 740
KPLC	Lake Charles La.	1470		Roswell, N.Mex. Raton, N.Mex.	1230	KTFR	San Angelo, Tex. Terrell, Tex.	1340	KVFD	Ft. Dodge, towa Great Bend, Kans,	1400
KPLW	Paris, Tex. Union, Mo.	1490	KRTR	Thermopolis, Wyo, Ballinger, Tex.	1490	KTFI	Twin Falls, Idaho Seminole, Tenn.	1270	KVIS	eattle. Wash	570
KPLY	Crescent City, Callf. Bakersfield, Callf.	1240	KRUS	Ruston, La.	1490	KILS	Texarkana, Tex.	1250 1400	RVIL	Cottonwood, Ariz. Highland Park, Tex.	1600
KPNG	Port Meches Tex	1560	KRVC	Ruston, La. Glendale, Ariz. Ashland, Oreg.	1360 1350	IKTHE	Brownfleid, Tex. Thermopolis, Wyo.	1300	KVIM	New Iberia, La. Vinita, Okla.	1360
KPOC	Pocahontas, Ark. Crescent City, Calif.	1420	KRVN	Lexington, Nebr. Rexburg, Idaho Corpus Christi, Tex.	1010	KTHO	Tahoe Valley, Calif. Berryville, Ark.	590 1480	KVIP	Redding, Callf.	540
KPUF	Denver, Colo. Honolulu, Hawaii	910	KRYS	Corpus Christi, Tex.	1360	KTHT	Houston, Tex.	790	KAFR	Monahans, Tex. Cleveland, Tex.	1330
KPOJI	Portland, Ores	1380 1330	KRZY	Farmington, N.M. Albuquerque, N.M.	1280 1580	KTIL	Thibodaux, La. Tillamook, Oreg.	630 1590	KVLC	Little Rock, Ark, Alpine, Tex.	1050
KPOK	Scottsdale, Ariz. Los Angeles, Calif.	1440	KSAC	Manhattan, Kans. Salina, Kans.	580 1150	KTIM	Tillamook, Oreg. San Rafael, Calif. Porterville, Calif.	1510	KVLG	LaGrange. Tex.	1570
KPON	Anderson, Calif.	1580	KSAM	Huntsville, Tex.	1490	KTIS	Minneapolis, Minn,	900	KVLL	Pauls Valley, Okta. Livingston, Tex.	1470
KPOW	Quincy, Wash, Powell, Wyo.	1370 1260	KSAY	San Francisco, Calif. San Francisco, Calif.	1010	KTKN	Hobart, Okla, Ketchikan, Alaska	1420 930	KVMA	Magnolia, Ark. Colorado City, Tex.	630
KPPC	Pasadena, Calif. enatchee, Wash.	1240 560	KSBW	Salinas, Calif. Liberal, Kans.	1380 600	KTKR	Taft, Calif. Tueson, Ariz.	1310	KVML	Sonora, Calif.	1450
KPRB	Redmond, Orem.	1240	KSCJS	Sioux City, Iowa	1360	KTLD	Tullulah, La.	990 1360	KVNC	Flagstaff, Ariz, Winslow, Ariz,	1010
KPRK	Houston, Tex. Livingston, Mont.	950 1340	KSCO S	Santa Cruz, Calif. t. Louis, Mo.	1080 550	KTLN	Denver, Colo. Mtn. Home, Ark.	1280	KVNI	Coeur d'Alene, Idaho Logan, Utah	1240
KPRL	Paso Robles, Calif. Riverside, Calif.	1230	KSDN	Aberdeen, S. Dak.	930 1130	KTLQ	Tahlequah, Okla. Rusk, Tex.		KVOB	Bastrop, La. Casper, Wyo.	1340
KPRS	Kansas City, Mo.	1590	KSOR	San Diego, Calif. Waterton, S.Dak.	1480	KTLW	Texas City, Tex. McAlester, Okla.	920	KVOE	Emporia, Kans.	1230
KPSO	Pratt, Kans. Falfurrias, Tex.	1290	KSELF	Santa Maria, Calif.	1480 930	KTMC	McAlester, Okla. Santa Barbara, Calif.	1400	KVOG	Ogden, Útah Lafayette, La.	1490
KPST I	Preston, Idaho Carson City, Nev.	1340	KSEK	Pittsburg, Kans, Lubbock, Tex.	1340 950	KINC	Falls City, Nebr. Tucumcarl, N.Mex.	1230 1400	KVOM	Morritton, Ark.	800
KPUG	Beilingnam, Wash.	1170			1470	KTNT	Tacoma, Wash.	1400	KVOO	Napa, Calif. Tulsa, Okla. Piainview, Tex.	1440
KQDF	Austin, Minn. Spokane, Wash.	970 1280	KSEO	Shelby, Mont. Durant, Okla.	1150 750	KTOD	Jonesboro, La. Sinton, Tex.	920 1590	KVOP	Plainview, Tex. Colo. Springs, Colo.	1400
KUDII	Bismarck, N.D. Minot, N.Dak.	1350	KSET	El Paso, Tex. Sitka, Alaska	1340	KTOE	Mankato, Minn. Lihue, Hawaii	1420	KVOU	Uvalde, Tex.	1400 1450
KQEN	Roseburg, Oreg. Albuquerque, N. Mex.	1250 920	KSEY	Sitka, Alaska Seymour, Tex. Nacogdoehes, Tex.	1230 860	KTOK	Oklahoma City, Okla,	1000	KVOX	Moorhead Minn	1280
KOIK	akeview. Ores. Redding, Calif.	1230	KSFE	Needles, Calif.	1340	KT00	Belton, Tex. Henderson, Nev.	940 1280	KVOZ	Yuma, Ariz. Laredo, Tex. Canyon, Tex.	1400 1490
KUIL	MISSOUIA, MONT.	1400	KSGM	San Francisco, Calif. Chester, III.	560 980	KTOW	Topeka, Kans, Sand Spring, Okla,	1490 1340	KVPH	Canyon, Tex. Ville Platte, La.	1550
KOYX	ittsburgh, Pa.	1410	KSIB C	reston, lowa Sidney, Nebr.	1520 1340	KTPA	Sand Spring, Okla. Prescott, Ark. Modesto, Calif.	1370 860	KVRC	Arkadelphia, Ark.	1240
KRAC	Alamogordo, N.M. E. Grand Forks, Minn.	1270	KSIG C	rowiey, La.	1450	KTRC	Santa Fe. N. Mex.	1400	KAME	Santa Mosa, Calif.	1240
		1480	KSIM S	ilver City, N.Mex. Sikesion, Mo.	1340	KTRE	Lufkin, Tex. Thief River Falls,	1420	KVRH	Salida, Colo.	1340 1360
KRAK	Craig, Colo. Stockton, Calif. Rawlins, Wyo.	550	KSIS S	Vichita, Kans, edalia, Mo.	900		Minn	1230 990	KVSA	McGehee, Ark.	1220
KRAL	Rawlins, Wyo. Las Vegas, Nev.	1240 920	KSIW	Woodward, Okia. Jorpus Christi, Tex.	1450	KTRH	Honolulu, Hawaii Houston, Tex. Sloux City, Iowa	740	RVSH	Valentine Nahr	940
KRAN	Morton, Tex	1280	KSJB J	amestown, N. Dak.	600	KIRM	Masumont, Tex	990	KVSO		1240 1490
KRBA	Amarilio, Tex. Lufkin, Tex.	1360	KSKIS	Sun Valley, Idaho Dallas, Tex.	660	KTRN	Wichita Falls, Tex. Bastrop, La.	1290 730	KVWD	Pearsall, Tex.	1280
KRBC.	Abilene, Tex.	1470	KSL Sa	It Lake City, Utah	1160	KISA	San Antonio, Tex.	550	KVWO	Cheyenne, Wyo.	1050 1370
KRBN	t, Peter, Minn, Red Lodge, Mont,	1310 1450	KSLO C	Salem, Oreg.)pelousas, La.	1390	KTSM	Burnett, Tex. El Paso, Tex.	1340	KWAC	Bakersfield, Calif. Wadena, Minn.	1490 920
KRCO	Ridgecrest, Calif. Prineville, Dreg.	1360		Monte Vista, Colo. Santa Maria, Calif.	1240	KTTR	Rolls Mo.	1600 1490	KWAK	Stuttgart, Ark.	1240 620
KRDG	Redding, Calif. Colo. Springs, Colo.	1230	KSMN	Mason City, Iowa Salem, Mo.	1010	KTTS	Springfield, Mo.	1400	KWAM	Wallace, Idaho Memphis, Tenn, Watertown, S.Dak.	990
KROP	Readsport Ores	1470	KSNB S	Santa Barbara, Calif.	1340 1290	KTUE	Springfield, Mo. Tucson, Ariz, Tulia, Tex.	1400	KWAT	Watertown, S.Dak. Baytown, Tex.	950 1360
KRE B	Dinuba, Calif, erkeley, Calif.	1240 1400	KSNO .	Pocatello, Ida, Aspen, Colo,	1290 1260	KTW S	Pueblo, Colo, Seattle, Wash.	1480 1250	KWBB	Wiehita, Kans,	1410
KREB	Shreveport, La. Eureka, Calif.	980	KSNY S	Aspen, Colo. Snyder, Tex. ss Moines, Iowa	1450	KTWO	Casper, Wyo.	1470	KWBE	Beatrice, Nebr.	1450
KREM	Oakdale, La.	900	KSOK	Arkansas City, Kans. San Diego, Calif.	1280	KTXO	Sherman, Tex.	1350 1500	KWBW	Hutchinson, Kans.	1590 1450
KREK	armington, Mo. Sapulpa, Okla,				1140	KUAM	Agana, Guam	1400	KWCB	Searcy, Ark.	1300 1280
KREM	Sapulpa, Okla. Spokane, Wash.	970	KSOP S	Salt Lake City, Utah Raymondville, Tex. Santa Paula, Calif. tillwater, Okla.	1370	KUBA	Agana, Guam Yuba City, Calif. Montrose, Colo, Pendleton, Oreg. Oceanside, Calif.	1600	KWCO	Chickasha, Okla,	1560
KREW	Indio, Calif. Sunnyside, Wash.	1230	KSPA S	anta Paula, Calif.	1400	KUBE	Pendleton, Oreg.	1050	KWED	Rochester, Minn, Seguin, Tex.	1270 1580
KREA	Grand June Colo. Owatonna, Minn.	920	KSPL [Dibolt, Tex.				1320 1450	KWEI		1260 1600
KRES S	Owatonna, Minn, Superior, Nebr. Frand Island, Neb.	1600	KSPT S	Dibolt, Tex. sandpoint, Idaho Salmon, Idaho	1400 960	KUDL	Kansas City, Mo.	1380 1590	KWEW	Hobbs, N.Mex.	1480
KRGV	Weslasco, Tex. Duncan, Okla.	1290	KSRC S	ocorro, N. Mex.	1290	KUDY	Seattle, Wash.	910	KWFT	Wichita Falls, Tex.	620
KRIB	dason City, Iowa	1350	KSRV C	santa Rosa, Calif. Ontarlo, Oreg. olorado Springs, Colo. uiphur Springs, Tex. Coleman, Tex. Breckenridge, Tex.	1380	KUEQ	Wenatchee, Wash, Phoenix, Ariz, Eugene, Oreg.				1280 1280
KRIG C	dason City, Iowa Idessa, Tex. Rayville, La.	990	KSSS C	olorado Springs, Colo,	740	KUGN	Eugene, Oreg.		KWHK	Hutchinson, Kans.	1260
KRIO A	Ac Allen, Tex.	910	KSTA C	oleman, Tex.	1000	KUJ W	alla Walla, Wash.	1420	KWHO	Sait Lake City, Utah	860
KRKC	AcAllen, Tex. hoenix, Ariz. King City, Calif.	1230 1570	KSTH S	St. Helen's, Oreg.	1600	KUKI	Ukiah, Calif.	1250 1400	KWHW	Salt Lake City, Utah Altus, Okla. Salt Lake City, Utah Pocatello, Idaho	1450 1570
NANO	LOS Andeles, Gaill.	1150 1380	KSTL S	t. Louis, Mo.	690 1420	KUKO	Post, Tex. Willow Springs Mo				790
KRKT	Everett, Wash, Albany, Ore. Lewiston, Idaho	990	KSTP S	it. Paul, Minn.	1500 620	KULA	San Antonio, Tex. Ukiah, Calif. Post, Tex. Willow Springs, Mo. Honolulu, Hawaii Ephrata, Wash.	690	KWIN	Ashland, Oreg.	580
KRLD	Dallas, Tex.	1350	KSTT C	irand Junction, Colo, Javenport, Iowa tephenville, Tex.					KWIQ	Moses Lake, Wash. 1	580 1260
180	WHITE'S BADIO				590	KUNO	Pendleton, Oreg. Corpus Christl, Tex.	1400	KWIZ :	Santa Ana Calif	1050 1480
	WHITE'S RADIO	-0G	V20 D	w. memphis, Ark.	/30	KUOA	Siloam Springs, Ark.	1290	KM11 I	Portland, Oreg,	080

C.L. Location	Ke	C.L.	Location	¥c.	C.L.	Location	H.c.	C.L.	Location	Re.
KWK St. Louis, Mo. KWKC Abilene, Tex.	1380	KZZN	Littlefield, Tex.	1490	WARN	1 Scranton, Pa.	590	WBIW	Bedford, ind. Eau Claire, Wis.	1340
KWKC Abilene, Tex. KWKH Shreveport, La.	1340	WAAA	Winston-Salem, N.C. Worcester, Mass,	980	WARN	Ft. Pierce, Fla. Canonsburg, Pa.	1330	WBIZ	Eau Claire, Wis. Hattlesburg, Miss.	1400 950
KWKW Pasadena, Calif. KWKY Des Moines, Jowa	1300	WAAF	Chicago, III	950 1470	WARL	Peru, Ind. Havre de Grace, Md.	1600	AA R K L	NEWTOR MISS	1410
KWLC Decorah, lowa KWLD Liberty, Tex.	1240	WAAK	Adel, Ga. Dallas, N.C.	960	WASK	Lafavette, Ind.	1450	WBLA	West Bend, Wis. Elizabethtown, N.C.	1470 1440
KWLM Willmar, Minn.	1050	WAAT	Peoria, III. Trenton, N.J.	1350	WATC	Boone, N.C. Gaylord, Mich.	900	WBLF	Batesville, Miss. Bellefonte, Pa.	1290
KWLW Nampa, Idaho KWMT Ft. Dodge, Iewa	1340	WAAX	Gadsden, Ala, Huntsville, Ala	570 1550	WATE	Knoxville, Tenn,	620 970	WBLG	Lexington, Ky. Daiton, Ga.	1300
KWNA Winnemucca, Nev.	1400	WABA	Huntsville, Ala. Aguadilla, P.Rico	850	WATK	Athens, Ohio Antigo, Wis.	900	WBLO	Evergreen, Ala.	1470
KWNO Winena, Minn. KWNT Davenport, lowa	1230 1580	WABC	Mobile, Ala, New York, N.Y. Fairhope, Ala.	770	WATN	Matertown, N.Y.	1590	WBLT	Batesburg, S.C. Bedford, Va.	1430 1350
KWOA Worthington, Minn, KWOC Poplar Bluff, Mo.	730 930	WABF	Fairhope, Ala. Greenwood, Miss.	1220 960	WATO	Oak Ridge, Tenn, Marlon, S.C.	1290	WBLU	Bedford, Va. Salem, Va. Springfield, Ohio	1480 1600
KWOE Clinton, Okla, KWON Bartlesville, Okla.	1320	WABH	Greenwood, Miss, Deerfield, Va.	910	WATR	Waterbury, Conn.	1320 960	WENTA	Beaufort, N.C. McMinnville, Tenn.	960
KWOR Worland, Wyo.	1340	WABI	Bangor, Maine Adrian, Mich, Amite, La.	1490	WATT	Sayre, Pa. Cadillae, Mich.	1240	WBME	Baltimore, Md.	750
KWOW Pomona, Calif.	1600	WABU	Waynesboro Miss.	1570 990	WATW	Birmingham, Ala, Ashland, Wis.	900 1400	WBML	West Point, Ga. Macon, Ga.	1310
KWPC Muscatine, Iowa KWPM West Plains, Mo.	860 1450	WABQ	Cleveland, Ohlo Winter Park, Fla,	1540	WATZ	Alpena, Mich, Auburn, N.Y.	1450 1590		Black Mountain, N.C. Charlotte Amalie,	1350
KWPR Claremore, Okla.	1270	WABT	Tuskegee, Ala, Abbeville, S.C.	580 1590	WAUC	Wauchula, Fla. Auburn, Ala.	1310		Virgin Islands Conway, N.H.	1000
KWRA Idaho Falls, Idaho KWRD Henderson, Tex. KWRE Warrenton, Mo.	1470	WARW	Annapolis, Md.	810	WAUG	Augusta, Ga.	1050	WBNL	Boonville, Ind.	1540
KWHF Warren, Ark.	730 860	WABZ	Albany, N.Y. Albemarle, N.C.	1010	WAVE	Waukesha, Wis, Louisville, Ky,	1510 970	WBNS	Beacon, N.Y. Columbus, Ohio	1260 1460
KWRO Coquille, Oreg. KWRT Boonville, Mo.	630 1370	WACE	Camden, S.C. Kittanning, Pa.	1590	WAVL	Dayton, Ohio Apollo, Pa.	910	WBNI	Oneida, Tenn. New York, N.Y.	1310
KWRV McCook, Nebr. KWRW Guthrle, Okla,	1360	WACE	Chicopee, Mass, Newark, N.Y. Waycross, Ga.	730 1420	WAVN	Stillwater, Minn. Avendale Estates, Ga.	1220	WBOB	Galax. Va	1360 960
KWSC Pullman, Wash,	1250	WACL	Wayeross, Ga.	570	WAVE	Avon Park, Fla	1390	WBOF	Salisbury, Md. Virginia Beach, Va.	1550
KWSD Mt. Shasta, Calif. KWSH Wewoka-Seminole,	620	WACR	Waco, Tex. Columbus, Miss.	1460	WAVY	Albertville, Ala. Portsmouth, Va.	630 1350	WBOP	New Orleans, La. Pensacola, Fla.	800 980
KWSK Pratt, Kans.	1260	WACT	Tuscaloosa, Ala.	1420	WAVZ	New Haven, Conn. A West Aliis, Wis. K Kendallville, Ind.	1300	WBOS	Brookline, Mass, / Terre Haute, Ind	1600
KWSL Grand Junction, Colo. KWSO Wasco, Calif.		WADC	Akron, Ohio Wadesboro, N.C.	1350	WAW	K Kendaliville, Ind. Zarephath, N.J.	1570	WBOY	Clarksburg, W.Va. Lock Haven, Pa.	1400
KWTC Barstow, Calif.	1230	WADK	Newport, 15,1,	1540	WAXE	Vero Beach, Fla.	1370	WBKE	Mt. Clamens, Mich.	1430
KWTO Springfield, Mo. KWTX Waco, Tex.	560 1230	WADP	New York, N.Y. Kane, Pa. Ansonia, Cenn.	1280 960	WAXX	Georgetown, Ky. Chippewa Falls, Wis.	1150	WBRE	Birmingham, Ala. Bradenton, Fla.	960 1420
KWVN Concord, Calif. KWVR Enterprise, Oreg.	1480	WADS	Ansonia, Conn. Allentown, Pa.	690 790	WAYB	Waynesboro, Va. Dundalk, Md.	1490 860	WBRE	Wilkes+Barre, Pa.	1340
KWVY Waverly, Iowa KWWL Waterloo, Iowa	1470	WAEL	Mayaguez, P.Rico Staunton, Va.	900	WAYN	Rockingham, N.C. Orange Park, Fla.	900 550	WBRH	Lynchburg, Va. Pittsfield, Mass, Berlin, N.H.	1340
KWYK Farmington, N.Mex.	960	WAFS	Amsterdam, N.Y. Leesburg, Va.	1570	WAYS	Charlotte N.C.	610	WBRA	Marion, N.C. Big Rapids, Mich.	1250
KWYO Sheridan, Wvo.	1410	WAGE	Dothan, Ala,	1290	WAYZ	Waynesboro, Pa.	1230 1380	WRKU	Wavnesboro, Lia.	1460
KWYR Winner, S.Dak. KWYZ Everett, Wash.	1260	WAGG	Franklin, Tenn. Presque isle, Maine	950 950	WAZA	Clearwater, Fla.	1360 860	WBRT	Bardstewn, Ky. Boonville N.Y.	1320 900
KXA Seattle, Wash, KXAR Hope, Ark.	770 1490	WAGN	Menominee, Mich. Lumberton, N.C.	1340	WAZF	Yazoo City, Miss. Hazelton, Pa.	1230	WBRV	Brewster, N.Y. Berwick, Pa.	1510
KXEL Waterloo, lowa	1540	WAGS	Bishopville, S.C.	1380	WAZS	Summerville, S.C. Lafayette, Ind.	780	WBRY	Waterbury, Conn.	1590
KXEN St. Louis, Mo. KXEO Mexico, Mo. KXEW Tucson, Artz.	1010	WALK	Forest City, N.C. Galesburg, III,	1320 1590	WBAA	West Lafavette, Ind.	920	WBSC	Boaz, Ala. Bennetsville, S.C. Blackshear, Ga.	1550
KXEW Tucson, Ariz. KXEX Fresno, Calif.	1600	WAIL	Baton Rouge, La. Anderson, S.C.	1460 1230	WBAE	Babylon, N.Y. Cleveland, Tenn.	1440	WBSG	Blackshear, Ga. New Bedford, Mass,	1350
KXGI Ft, Madison, lowa	1360	WAIN	Columbia, Ky.	1270	WBAG	Burlington, N.C. Baltimore, Md.	1150	WBT	Charlotte, N.C.	1110
KXGN Glendive, Mont. KXIC lowa City, Iowa	800	WAIT	Winston-Salem, N.C. Chicago, III. Decatur, Ala.	820	WBAN	Montgomery, Ala,	740	WBTH	Batavia, N.Y. Williamson, W.Va. Danville, Va.	1400
KXIC lowa City, lowa KXIT Dalhart, Tex. KXIV Phoenix, Ariz.	1410	WAJR	Morgantown, W.Vz.	1490	WBAR	Ft. Worth, Tex. 570 Bartow, Fla. Marion, Ind.	1460	WBTN	Bennington, Vt.	1330
KXJK Forrest City, Ark. KXKW Lafayette, La.	950 1520	WAKE	Atlanta, Ga. McMinnville, Tenn.	1340	WHAM	/ Barnwell S.C.	1400 740	WBTO	Linton, Ind. Bridgeport, Ala,	1600
KXL Portland, Oreg.	750 1240	WAKN	Aiken, S.C. Lawrenceville, III.	990	WBAX	Wilkes-Barre, Pa. Green Bay, Wis. Kingston, N.Y.	1360	WRUC	Buckhannon, W.Va.	1460
KXLE Ellensburg, Wash. KXLF Butte, Mont. KXLJ Helena, Mont.	1370	WAKR	Akron, Ohio	1590 1570	WBAZ	Kingston, N.Y. Pittsfield, III.	1550	WBUT	Trenton, N.J. Butler, Pa.	1050
KXLL Missoule, Mont.	1450	WAKY	Latrobe, Pa. Louisville, Ky.	790	WBBB	Burlington, N.C.	920 950	WBUY	Doylestown, Pa. Lexington, N.C.	1440
KXLL Missoule, Mont. KXLO Lewiston, Mont. KXLR Little Rock, Ark.	1230	WALD	Mobile, Ala. Walterboro, S.C.	1410	WBBI	Burlington, N.C. Rochester, N.Y. Abingdon, Va.	1230	WBVA	Fredonia, N.Y. Waynesboro, Va.	1570 970
KXLW Clayton, Mo.	920	WALE	Fall River, Mass. Albany, Ga.	1400	WBBB	Blakely, Ga, Richmond, Va. I Chicago, III.	1260 1480	WBV	Barbourville, Ky. I Utica, N.Y.	950 1550
KXLY Spokane, Wash, KXO El Centro, Calif, KXOA Saeramento, Calif,	1230	WALK	Patchogue, N.Y. Middletown, N.Y.	1370	I W B B O	Forest City, N.C.	780 780	WBVF	Beaver Falls, Pa. Calera, Ala,	1230 1370
KXOK St. Louis, Mo. KXOL Ft. Worth, Tex.	630 1360	WALM	Albion, Mich.	1260	WBBQ	Augusta, Ga, E. St. Louis, III.	1340	WBYG	Savannah, Ga.	1450 1560
KAUA Sweetwater, lex,	1240	WALT	Humacao, P.R. Tampa, Fia.	1110	WBBT	Lyons, Ga. V Youngstown, Ohlo	1340	WBZ	Canton, III. Boston, Mass.	1030
KXRA Alexandria, Minn. KXRJ Russellville, Ark.	1490 1490	WAMO	Herkimer, N.Y. Aberdeen, Md.	1420 970	WBBX	Portsmouth, N. H.	1380	WBZI	Springfield, Mass. Brazil, Ind.	1030
KXRJ Russellville, Ark. KXRO Aberdeen, Wash. KXRX San Jose, Calif.	1320	WAME	Miami, Fla. Opp, Ala.	1260 860	WBBZ	Wood River, III. Ponca City, Okla.	590 1230	WEZY	Brazil, Ind. Torrington, Conn. Northfield, Minn.	990 770
KXXL Bozeman, Mont. KXXX Colby, Kans,	1450 790	WAML	Laurel, Miss, Fiint, Mich,	1340	WBCA	Bay Minette, Ala. Levittown, Pa.	1150	WCAM	Camden, N.J. Baltimore, Md.	1310
KXYZ Houston, Tex. KYA San Francisco, Calif.	1320	WAMO	Homestead, Pa. Venice, Fla.	860	WBCH	Levittown, Pa, Hastings, Mich, Williamsburg, Va,	1220 740	WCAP	Lowell, Mass, Detroit, Mich.	980
KYCA Prescott, Ariz.	1490	WAMS	Wilminotos, Del	1380	WBCK	Battle Creek, Mich.	930	WCAT	Orange, Mass.	1390
KYCN Wheatland, Wyo. KYES Roseburg, Oreg.	1340 950	WAMW	/ Washington, Ind. Amory, Miss, Anniston, Ala, Waynesburg, Pa.	1580	WBCR	Battle Creek, Mich. Bay City, Mich. Christiansburg, Va. Union, S.C.	1440 1260	WCAW	Philadelphia, Pa. Charleston, W.Va.	1210 680
KYJC Medford, Oreg. KYME Boise, Idaho	1230 740	WANA	Anniston, Ala, Waynesburg, Pa.	1490 1580	WBCU	Union, S.C. Pittsfield, Mass.	1460	WCAX	Burlington, Vt. Cayce, S.C. Carthage, Iil, Corning, N.Y.	620 620
KYME Boise, Idaho KYND Tempe, Ariz. KYNG Coos Bay, Oreg.	1580	WAND	Canton, Ohio Ft. Wayne, Ind.	900 1450	WBEE	Pittsfield, Mass. Harvey, III.	1570	WCAZ	Carthage, III.	990 1350
KVNO Fresno Callf	1300	WANN	Annapolis, Md.	1190	WBEL	Buffalo, N.Y. Moncks Corner, N.C.	1380			1590
KYNT Yankton, S.Oak, KYOK Houston, Tex. KYOR Blythe, Calif.	1590	WANS	Annapolis, Md. Anderson, S.C. Richmond, Va. Aibany, Ky.	990	WBER	Moncks Corner, N.C.	950	WCBL	Columbus, Miss. Benton, Ky.	1290
KYOR Blythe, Calif. KYOS Merced, Calif.	1450	WANY	Albany, Ky. Atlanta, Ga.	1390	WBEU	Brockton, Mass. Beaufort, S.C. Beaver Dam, Wis.	960	WCBS	Baltimore, Md, New York, N.Y. Roanoke Rapids, N.C.	680 880
KYOS Merced, Calif. KYOU Greeley, Colo. KYRO Potosi, Mo.	1450	WADY	Atlanta, Ga. Vincennes, Ind. San Juan, P.R. Riverhead, N.Y.		WBEV	Beaver Dam, Wis. Chillicothe, Dhio	1430 1490	WCBY	Roanoke Rapids, N.C. Cheboygan, Mich.	1230
KYSM Mankato, Minn. KYSN Colorado Sprgs., Colo. KYSS Missoula, Mont.	1230	WAPC	Riverhead, N.Y.	1570 690	WBFC	Fremont, Mich.	1490 1310	WCCC	Magtined Conn	1290
KYSS Missoula, Mont.	910	WAPF	Jacksonville, Fla. McComb, Miss. Arcadla, Fla.	980	WBGC	Chipley, Fla.	1240	WCCN	Lawrence, Mass. Neilisville, Wis.	1370
KYVA Gallup, N. Mex.	1230	WALL	Dirmingnam, Ala,	1480	WBGR	Beaver Dam, Wis. Chillicothe, Ohio Fremont, Mich. Bedford, Pa. Chipley, Fla. Bowling Green, Ky. Jesup, Ga. Fitzgerald, Ga. Hameton, S.C.	1340	WCC.W	Minneapolis, Minn, Traverse City, Mich, Carbondale, Pa, Edenton, N.C.	830 1310
KYW Cleveland, Ohio KZEE Weatherford, Tex.	1100	WAPL	Appleton, Wis. Chattanooga, Tenn.	1570 1150	MBHC	Hampton, S.C.	1240	MCD1 MCDL	Carbondale, Pa. Edenton, N.C.	1440
KZEY Tyler, Tex.	690 1310	WAPX	Montgomery, Ala. Towson, Md.	1600 1570	WBHF	Hampton, S.C. Cartersville, Ga. Birmingham, Ala.	1450 1550	WCDS	Glasgow, Ky.	1440
KZIP Amarillo, Tex. KZIX Fort Collins, Colo. KZNG Hot Springs, Ark.	600	WAQI	Ashtabula, Ohio	1600	WBHP	Huntsville, Ala.	1230	WCEC	Rocky Mount, N.C.	810
KZOK Prescott, Ariz.	1340			730	WBIC	Augusta, Ga. Islip, N.Y. Marletta, Ga.	540	WCEF	Parksburg, W.Va.	1050
KZOL Farwell, Tex. KZON Tolleson, Ariz.	1570	WARE	Johnstown, Pa. Ware, Mass. Jasper, Ala.	1490 1250	MRIE	Greensboro, N.C.	1470	WCEM	Cambridge, Md.	610 1240
KZOO Honolulu, Hawaii KZOT Marianna, Ark.	1210 1460	WARF	Jasper, Ala. Abbeville, Ala.	1240	WBIP	Leesburg, Fla. Booneville, Miss. Knoxville, Tenn.	1400	WCEN	Mt. Pleasant, Mich.	1150
KZOW Globe, Ariz, KZUN Opportunity, Wash.	630	WARK	Abbeville, Ala, Hagerstown, Md, Arlington, Va,	780	WBIR	Knoxville, Tenn. Bristoi, Conn.	1240	WHITE	'S RADIO LOG	181

WESP Charletts, Mich. WESP Strategied, V. V. WESP Children, C. WESP	C.L. Location WCER Charlotte, Mich.		C.L. Location		C.L. Location		C.L. Location	Kc.
## WED Cathonic Catho	WCFL Chicago, III.	1000	WDAE Tampa, Fla.	1230	WEEL Michmond Va		WFIL Philadelphia, Pa, WFIN Findlay, Ohio	
WORD Continue 1979 WORD Description 1979 WOR	WCFV Clifton Forge, Va.	1230	WUAK Columbus, Ga.	540	WEEU Reading, Pa. WEEW Washington, N.C.	850	WEIW Pairneld III	1600
W. C. Canada-fram, N. V. 1539 W. C. S. Printedich, D. C. 1540 W. C. 1540 W. C. C. 1540	WCGC Belmont, N.C.	1270	WDAL Meridian, Miss. WDAN Danville, III.		WEEK Easton, Pa.	1230	WEKN Franklin, Ky,	1220
WERT BLANTER, WICH. WORD CALL CASENDER, CO. WORD CASENDER, CO.	WCGR Canandalqua, N.Y.	1550	WDAR Darlington, S.C. WDAS Philadelphia, Pa.		WEGO Concord, N.C. WEGP Presque Isle, Maine	1410	WILA Tampa, Fla.	970
WCHO Washington Carabination Ca	WCHB Inkster Mich	800	WDAX McRae Ca	1410	WEHH Elmira Heights-		WELL Lookeut Mtn., Tenn.	1070
WCHL Charles H.S	WCHI Chillicothe, Ohio WCHI Brookhaven, Miss.	1350	WDBC Escanaba, Mich.	680	WEIC Charleston, III.	1270	WFL() Farmville Va	870
WCH, Charlet, N. V., 1998. 1500 WDB D. Debugst, Issa. 1500 WE W. Rithmond, N. V., 1500 WE W. Charletterillit, V. 1500 WDB D. Debugst, Issa. 1500 WE W. Rithmond, N. V., 1500 WE W.	WCHK Canton, Ga,		WUBJ Moanoke, Va.	960	WEIR Weirton, W.Va.	1430	WFLS Fredericksburg, Va.	1350
WELF Charleting, W. V. 200 W DOF Date City, File. 1999 WELF Shorten, W. V. 1990 WELF Shorten, W. 1990 WELF Shorten, W	House, Ohlo		WDBM Statesville N.C.	550	WEJL Scranton, Pa.	630	WENC Goldshoro, N.C.	
WEIL Ginemant, 1915. WE WE WE S. Daylors, File. WE WE WILLIAM S. Daylors, File. WE WE S. Dayl	WCHN Norwich, N.Y.	970	WDBQ Dubuque, Iowa	1490		1340	WEMD Frederick, Md.	
WEIL Ginemant, 1915. WE WE WE S. Daylors, File. WE WE WILLIAM S. Daylors, File. WE WE S. Dayl	WCHV Charlottesville, Va.	1260	WDCR Hanover, N.H.	1340	WELB Elba, Ala,	1350	WEMD Fairment, N.C.	
WCR, Grants, R.C. WCR, Milami, F.G. WCR, Milami, G.G. WCR, Milami, M.Y. WCR, Wilami,	WCIN Cincinnati, Ohio	1480	WDDW Halfway, Md.	1410	WELD Fisher, W.Va.		WENC Favetteville, N.C.	730
WCR Minn, 15, 01, 10, 10, 10, 10, 10, 10, 10, 10, 10	WCKB Dunn, N.C.	780	WDEA Elisworth, Me.	1350	WELL S. Daytona, Fla. WELL New Haven, Conn.		WENL No. Augusta, S.C.	1600
WCLE Granding, Gran, W. C. 1909 W	WCKM Winnsboro, S.C.		WDEB Pensacola, Fla. WDEC Americus, Ga.	1290	WELK Charlottesville, Va.	1010	WFOM Marietta, Ga.	1230
WCLG Danielsen, Tenn. WCLG Daresview, WCLG Dares	WCKY Cincinnati, Ohio	1530	WDEF Chattanooga, Tenp.	1220	WELM Elmira, N.Y. WELO Tupelo, Miss	1410	WEOX Milwaukee Wis	860
WCLL Greenbas, 19, 19, 19, 19, 19, 19, 19, 19, 19, 19	WCLB Camilla Ga	1470	WIDEH Sweetwater Tenn	800	WELP Easiev, S.C.	1360		1400
WCLL Greenbas, 19, 19, 19, 19, 19, 19, 19, 19, 19, 19	WCLC Jamestown, Tenn, WCLD Cleveland, Miss.	1260	WDEV Waterbury, Vt.	550	WELS Kinston, N.C.	1010	WEPM FORE Valley Ga	1150
WCLS Dameswille, Mia. 1230 WDLS Orangeburg, S.C. 1350 WEND Easten, Mad. 1460 WFR PROBLEM, D.C. 1600 WDLS Orangeburg, S.C. 1350 WDLS Marchin, Miss. 1250 WDLS Dameswill, Miss. 1250 WDLS Dameswi	WCLE Cleveland, Tenn. WCLG Morgantown, W.Va	1570	WDGY Minneapolis, Minn	1130	WELY Ely, Minn,	1450	WFRA Franklin, Pa.	1430
WCLW Manteld, Ohlo 1999 WKD Wilson, Tenn. 1999 WKD Wilson, Tenn. 1990 WKD WKD Wilson, Tenn. 1990 WKD	WCLI Corning, N.V.	1450	WDIG Dothan, Ala.	1450	WEMB Erwin, Tenn,	1420	WFRC Reidsville, N.C.	1600
WCMB Hartsburg, Pa. 1500 WKR Dickson, Tenn. 1500 WKR Dickson, Tenn. 1500 WKR Edenburg, Pa.	WCLS Columbus, Ga. WCLT Newark, Obio	1580	WDJS Mt. Olive, N.C.	1430	WEMJ Laconia, N.H.	1490	WFRM Coudersport, Pa.	600
WCME Burnwis, Malno WCME B	WCLW Mansfield, Ohio	1570	WDKN Dickson, Tenn.	1260	WENA Bayamon, P.R.	1560	WERX West Frankfort III	1300
WCBN Aretholo P.R., 130 WERN Dinon City, Ten., 1240 WFTC kinston, N.C. 1500 WERN Marches Prince City, Minn, 1350 WDT indianals, Miss, 1350 WERT Gloverville, N.Y. 1340 WFTC kinston, N.C. 1500 WERN Marchis, Prince City, Minn, 1350 WDT indianals, Miss, 1350 WERT Gloverville, N.Y. 1340 WFT Maryini, R.Y. 1340 WFT Maryini, R.	WCMB Harrisburg, Pa.	1460	WDLB Marshfield, Wis.	1450	WEND Edensburg, Pa.	1580	WFSR Bath, N.Y.	1380
WORD F Michael Co., F. M. 1980 WELL Fallaman Life 1980	WCMF Brunswick Malno	900	WULK Delaware, Ohio	1550	WENK Union Cltv. Tenn.	1240	WFTC Kinston, N.C.	960
WORD Contraville, Inc. 1489 WORD James Str. 1489 WORD James	WUMN Arecino, P.R.	1200		590	WENO Madison, Tenn.	1430	WFTL Ft. Lauderdale, Fla.	1400
WORD Contraville, Inc. 1489 WORD James Str. 1489 WORD James	WCMR Elkhart, Ind.	1270	WDMC Otsego, Mich.	980	WENY Elmira, N.Y.	1230	WFTR Front Royal, Va.	
WORD WORD WORD WORD WORD WORD WORD WORD	WCMT Martin, Tenn,	1410		860	WEOL Elyria, Ohio	930	Florida	
WCM H Gulny, Fls. 1400 WDNC Durham, N.C. 700 WERD Atlantia, B. 1. 1500 WFV Greater Spring of the Month of the	WCNB Connersville, Ind.	1580	WDMS Lynchburg, Va.	1320	WEPM Martinsburg, W.Va.	1340	WFUN Huntsville, Ala.	1450
WCMT Centralia, Ill. 210 WDDC Danton, Miss. 1370 WERR Mamilton, Ala. 970 WFW, Canden, Tenn. 1220 WCMU Crestview, Fia. 1010 WDDC Danton, Miss. 1370 WERR Canden fiver, Wiss. 300 WFY, Minan, Mich. 1380 WCMC Candelson, Comp. 1380 WDDC Danton, Miss. 1370 WERR Canden fiver, Wiss. 300 WFY, Minan, Mich. 1380 WCMC Candelson, Comp. 1380 WCMC Candelson,	WCNE Weldon, N.C.	1400	WDNC Durham, N.C.	620	WERD Atlanta, Ga	860	WIVA Fredericksburg, Va.	1230
WCDA Pensacola, Fla. 1370 WDD Denkirk, N.Y., 1310 WESS Bradford, Ps. 1300 WGO Greensboro, N.C. 1320 WDD Cleveland, Ohlo 1200 WCO Greensboro, N.C. 1320 WDD Cleveland, Ohlo 1200 WCO Greensboro, N.C. 1400 WCO Greensboro, N.C. 140	WCNL Newport, N. H.	1010	WUNG Anniston, Ala.	1450	WERM Hamilton Ala	970	WrwL Camden, Tenn.	1220
WCDA Pensacola, Flan. 1370 WCDA Pensacola, Flan.	WCNT Centralla, III.	1210	WDOB Canton, Miss.	1370	WERL Eagle River, WIs.	950	WFYI Mineola, N.Y.	
## WOD Greensborn N. C. 1520 W DOW Cleveland, Ohlo 1260 W ESN N. Augusta, S.C. 1550 W GA I Elizabeth Gity, N. C. 560 W COD Comental, Ga. 1400 W COD Cornella, Ga. 1450 W DON Alment, Ga. 1400 W COD Cornella, Ga. 1450 W DOS Onconta, N. 1400 W COD Cornella, Ga. 1450 W DOS Onconta, N. 1400 W COD Cornella, Ga. 1450 W DOS Onconta, N. 1400 W COD Cornella, Ga. 1450 W DOS Onconta, N. 1400 W COD Cornella, Ga. 1450 W DOS Onconta, N. 1400 W COD Cornella, Ga. 1450 W DOW Oweaplac, Mich. 1400 W COD Cornella, Ga. 1400 W COD Cornella, Ga. 1400 W COD Coumbia, S.C. 1400 W Dowsplac, Mich. 1400 W COD Coumbia, S.C. 1400 W Dowsplac, Mich. 1400 W COD Coumbia, S.C. 1400 W Dowsplac, Mich. 1400 W COD Coumbia, S.C. 1400 W Dowsplac, Mich. 1400 W COD Coumbia, S.C. 1400 W Dowsplac, Mich. 1400 W COD Coumbia, S.C. 1400 W COD Coumbia, S.C. 1400 W COD W COURDING, Mich. 1500 W COD Coumbia, S.C. 1400 W COD W COURBIA, Ph. 1500 W COD Coumbia, S.C. 1400 W COD W COURBIA, Ph. 1500 W COD W C	WCNX Middletown, Conn.	1150	WDOD Chattanooga, Tenn.	1310	WESA Charleroi, Pa.	940	WGAA Cedartown, Ga. WGAC Augusta, Ga.	
WCOP Newnan, Ga. 400 WDOP Catesville, Pa. 1420 WDOP Wheston, M. W. Wis. 1420 WDOP Wheston, M. W. Wis. 1420 WDOP Moston, M. W. Wis. 1420 WDOP Downson, M. W. Wis. 1420 WETZ Newson, M. W. Wis. 1420 WGBA Evansville, Ind. 1420 WGBA Evansville, Ind. 1420 WGBA Evansville, Ind. 1420 <td< td=""><td>WCOC Meridian, Miss.</td><td>910</td><td>WDOG Marine City, Mich.</td><td>1590</td><td>WESU Greenville, S.C.</td><td>660</td><td>WGAF Valdosta Ga</td><td></td></td<>	WCOC Meridian, Miss.	910	WDOG Marine City, Mich.	1590	WESU Greenville, S.C.	660	WGAF Valdosta Ga	
WCDP Boston, Mass. 150 WCDR Lebanon, Tenn, WCDR Solombia, S.C. 400 WCDR Columbia, S.C. 400 WCDR Columbia, S.C. 400 WCDR Lebanon, Tenn, WCDR Solombia, S.C. 400 WCDR Lebanon, Mills, 400 WCDR Lebanon, Tenn, WCDR Solombia, S.C. 400 WCDR Columbia, Pa. 1200 WCDR Columbia, Pa. 1200 WCDR Lebanon, Tenn, WCDR Solombia, S.C. 400 WCDR Lebanon, Tenn, WCDR McDr Solombia, S.C. 400 WCDR McDr Solombia, S.C. 400 WCDR Lebanon, Tenn,	WCOH Newnan, Ga.	1400	WDOL Athens, Ga	1470	WESO Southbridge, Mass.	970	WGAL Lancaster, Pa.	1490
WCDR Eston, Mass, 1150 WDDT Burtinston, V.s. 1400 WESY Litland, Alliss, 1630 WGCD Claumbia, S.C. 1400 WDDV Dover, Del. 1410 WEST Dibmson City, Tenn, 790 WGCD Claumbia, S.C. 1400 WDDV Dover, Del. 1410 WEST Claumbia, Tenn, 1700 WGCD Claumbia, P.s. 1580 WDDW Dover, Del. 1410 WEST Claumbia, P.s. 1400 WGCD Claumbia, P.s. 1580 WDDW Dovenglar, Mich. 1440 WETC Wendell-Zebulon, N.C. 340 WGAU Athens, Ga. 1340 WGCD Clearfield, Pa. 900 WDS Cleveland, Miss. 1410 WEST Claumbia, P.s. 1580 WEST Claumbia, P.	WCOL Columbus, Ohio	1230	WUUR Sturgeon Bay, Wis.	910	WEST Easton, Pa.		WGAP Maryville, Tenn.	
## WOOD Coumbils, SC. 1400 Dover, Del. 1410 WETB Johnson City, Tenn. 1410 WETB Wendell-Zebulion, N.C. 530 WGAU Athens, Galler City, Va. 1050 WCOW Montgomery, Ala. 1270 WDRO Hartford, Conn. 1360 WETO Galden, Ala. 1300 WCDW Description, Sc. 1400 WETD Wendell-Zebulion, N.C. 530 WGAU Athens, Galler City, Va. 1300 WETD Galden, Ala. 1300 WCDW College, Ala. 1300 WETD Galden, Ala. 1300 WCBA Gardiner, Sc. 1400 WETD Wendell-Zebulion, N.C. 540 WCDW College, Ala. 1300 WCBA Gardiner, Ala. 1400 WETD Wendell-Zebulion, N.C. 1400 WCDW College, Ala. 1400 WETD Galden, Ala. 1300 WCBA Gardiner, Ala. 1400 WETD Wendell-Zebulion, N.C. 1400 WCDW College, Ala. 1400 WETD Wendell-Zebulion, N.C. 1400 WCBA Gardiner, Ala. 1400 WETD Galden, Ala. 1400 WCBA Gardiner, Ala. 1400 WCBA	WLUP Boston, Mass.	1150	WDOS Oneonta, N.Y. WDOT Burlington, Va.	1400	WESX Salem, Mass. WESY Leland, Miss.		WGAS S. Gastonia, N.C.	1220
## WEDU Lewiston, Maine 1240 WDM DuQuoin, III. 1580 WETD Gadsden, Ala. 1500 WEDU Gadsden, Ala. 1500	WCOS Columbia, S.C.	1400 I	WDOW Dowagiac, Mich.	1440	WEIC Wendell-Zebulon, N.C.	540	WGAU Athens, Ga	
WCPA Clearthid, Fig. Soo WCPA Clearthid	WCOV Montgomery, Ala.	1170	WDRC Hartford, Conn.	1360	WETH St. Augustine, Fla. WETO Gadsden, Ala.		WGAW Gardner, Mass, WGRA Columbus Ga	1340
WCPL Houston, Miss. 1320 WDSP Defunitals Springs. 710 WEUC Phone, P.R. 330 WEUC Phone, P.R. 3120 WGSP Gelunitals Springs. 1150 WGSP Gelunitals Springs. 210 WGSP Gelunitals S	WCOW Sparta, Wis. WCOY Columbia, Pa.	1290 1580	WDSC Dillon, S.C. WDSG Dyersburg, Tenn.	1450	WETT Dream City, Md. WETU Wetumpka, Ala,	1590	WGBF Evansville, Ind.	1240
## WCPM clowberland, Ky, 1280 ## WCPD ClineInnail, Ohlo ## WCPD ClineInnail, Ohlo ## WCPD ClineInnail, Ohlo ## WCRA Empham, III, 1230 ## WDSR Lake City, Fla. 1240 ## WDSR Lake City, Fla. 1240 ## WDSR Lake City, Fla. 1240 ## WCRA Empham, III, 1090 ## WDUX Waupaca, Wis. 1400 ## WCRA Empham, III, 1090 ## WDUX Waupaca, Wis. 1400 ## WDUX Waupaca, Wis. 1400 ## WDUX Waupaca, Wis. 1400 ## WCRA Cheraw, S.C. 1420 ## WDVA Danville, Va. 1250 ## WCRI Sottsboro, Ala. 1050 ## WCRI Sottsboro, Ala. 1050 ## WCRI Wortstown, Tenn, 1150 ## WCRI Wortstown, Tenn, 1150 ## WCRI Clare, Mich. 1990 ## WDVV Uncland, N.J. 1270 ## WDVV Davison, Ga. 1900 ## WCRI Corinth, Miss. 1230 ## WCRI Corinth, Miss. 1240 ## WDVV Davison, Ga. 1900 ## WCRI Washinjam, Ala. 1250	WCPA Clearfield, Pa. WCPC Houston, Miss.	1320	WUSM Superior, Wis.		WETZ New Martinsville, West Virginia		WGBG Greensboro, N.C.	1400
WCPD Cincinnati, Ohlo 1230 WDSR Lake City, Fla. 1340 WEVD Remporia, Va. 860 WGCB Red Lion, Pa. 1440 WCPS Alma, Ga. 1400 WDSU New Orleans, La. 1230 WEVD New York, N.Y. 1330 WGCB C Chester, S.C. 1490 WCRA Embaham, III. 1090 WDUX Salmsterlie, Ga. 1240 WEVE St. Louis, Mo. 770 WGCM Gulfport, Miss. 1240 WCRI Scottsboro, Ala. 100 WDVA Green Bay, Wis. 1800 WEVE St. Louis, Mo. 770 WGEA Geneva, Ala. 1150 WCRI Scottsboro, Ala. 100 WDVH Gene Bay, Wis. 1800 WEVE Gard, Oak Mich. 1800 WEVE Gard, Oak Mich. WGEA Geneva, Ala. 1590 WCRI Onconta, Ala. 1570 WDVH Vineland, N.J. 1800 WEVE Brain, Bay, Marker 1800 WEZB Birlmaham, Ala. 1220 WGFA Watska, III. 1800 WCRZ Gram, Marker 1800 WEZB Birlmaham, Ala. 1800 WGFA Watska, III. 1800 WGFA Gainesville, Ga. 4350 WGFA Gainesville, Ga. 4350 WGFA Gainesville, Ga. 4350 WGFA Gainesville, Ga. 4350 <	WCPM Cumberland, Ky.	1280	Florida		WEUC Ponce, P.R. WEUP Huntsville, Ala	1420	WGBR Goldsboro, N. C.	1150
WCQS Alma, Ga. 460 WDN Galnesville, Ga. 1240 WEVE Eveleth, Milnn. 1340 WGCM Gulfport, Miss. 1220 WCRB Empham, III. 1900 WDUX Waupaca, Wis. 1400 WEWE Louis, Mo. 770 WGEA Geneva, Ala. 1150 WCRE Cheraw, S.C. 1400 WDVA Danville, Va. 1400 WEXE Louis, Mo. 1700 WGEA Geneva, Ala. 1150 WCRE Cheraw, S.C. 1400 WDVA Gainesville, Fla. 1900 WEXE Louis, Mo. 1700 WGEA Geneva, Ala. 1150 WCR CRIS Cortisboro, Ala. 1050 WDVH Gainesville, Fla. 1900 WEYE Sanford, N.C. 1290 WGET Gettysburg, Pa. 1320 WCR CRIS Cortisboro, Ala. 1570 WDVD Dawson, Ga. 1900 WEZE Borton, Ala. 1580 WGET Gerisboro, Mass. 1200 WGET Gerisboro, Mass. 1200 WGET Gerisboro, Mass. 1200 WGET Gerisboro, MGET	WCPO Cincinnati, Ohio WCPS Tarboro, N.C.	760	WDSU New Orleans, La.		WEVA Emporia, Va. WEVD New York, N.V.	860	WGCB Red Lion, Pa.	1440
WGRB Waltham, Mass, WGRE Cheraw, S.C., WDVA Danville, Va. WDVA Danville, Va. WDVA Danville, Va. WDVA Gainesville, Fla. 1500 WEYE Sanford, N.C. 1290 WGRA Morristown, Tenn, 1570 WGRM Morristown, Tenn, 1570 WGRM Clare, Mich. 1570 WDVD Dawson, Ga. WDVA Clare, Mich. 1570 WGRM Clare, Mich. 1570 WDVD Dawson, Ga. WDVB Champaign, Ill, WDVD Dawson, Ga. WDVB Champaign, Ill,	WCQS Alma, Ga.	1400	WDUN Gainesville, Ga. WDUX Waupaca, Wis.		WEVE Eveleth, Minn. WEW St. Louis, Mo.	1340	WGCM Gulfport, Miss,	1240
WORN Clare, Mich. 1370 WOWS Champaign, III, 1400 WZEB Boston, Mass. 1260 WGGA Gainesville, Ga. 550 WDXE Lawrenceburg, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1	WCRB Waltham, Mass, WCRE Cheraw, S.C.	1330	WDUZ Green Bay, Wis, WDVA Danville, Va.	1400		1000	WCEE Indiananalia tad	1590
WORN Clare, Mich. 1370 WOWS Champaign, III, 1400 WZEB Boston, Mass. 1260 WGGA Gainesville, Ga. 550 WDXE Lawrenceburg, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1370 WDXE Lexington, Tenn. 1370 WDXE ADMINISTRATION, Tenn. 1	WCRI Scottsboro, Ala. WCRK Morristown, Tenn.	1050	WDVH Gainesville, Fla. WDVL Vineland, N.J.		WEYE Sanford, N.C. WEYY Talladega, Ala	1290	WGET Gettysburg, Pa.	1320
WCRR Gerinth, Miss. 1330 WERR Gerinthh, Miss.	WCRL Oneonta, Ala, WCRM Clare, Mich.	1570 990	WDWS Champaign, III,			1220	WGFA Watseka, III.	1360
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCRO Johnstown, Pa. WCRR Corinth, Miss.	1230	WDXB Chattanooga, Tenn. WDXE Lawrenceburg, Tenn.	1490	WEZJ Williamsburg, Ky. WEZN Elizabethtown, Pa.	1440	WGGA Gainesville, Ga.	550
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCRS Greenwood, S.C. WCRT Birmingham, Ala	1450	WDXI Jackson, Tenn. WDXL Lexington, Tenn.	1310	WEZY Cocoa, Fla. WEAA Dallas, Tex 570	1350	WGGH Marion, III.	1150
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCRV Washington, N.J. WCRW Chicago III.	1580	WDXN Clarksville, Tenn. WDXR Paducah, Kv.	540	WFAB Miaml, Fla. WFAG Farmville, N.C.	990	WGH Newport News, Va.	1310
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCRY Macon, Ga, WCSC Charleston, S.C.	900	WDXY Sumter, S.C. WDZ Decatur, III.	1240	WFAH Alliance, Ohio WFAI Favetteville, N.C.	1310	WGHM Skowegan, Maine WGHN Grd Haven Mich	1150
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCSH Portland, Maine WCSI Columbus, Ind.	970	WEAB Greer, S.C. WEAG Alcoa, Tenn.	800 1470	WFAR Farrell, Pa. WFAS White Plains, N.Y.	1470	WGHO Kingston, N.Y.	920
WCST Berkeley Springs, W.Va. 1010 WCTA Andalusla, Ala. 920 WCTC New Brunswick, N.J. 450 WCTC Corbin, Ky. 680 WCTW New Castle, Ind. 1550 WCUB Manitowoc, Wis. 980 WCUB Manitowoc, Wis. 980 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB Cuyahoga Falls, Ohlo 1550 WCUB Clayahoga Falls, Ohlo 1550 WCUB C	WCSM Celina, Ohlo WCSR Hillsdale, Mich.	1350	WEAM Arlington, Va. WEAN Providence, R.I.	1390 790	WFAU Augusta, Me. WFAX Falls Church, Va	1340	WGIL Galesburg, III.	1400
WCUE Cuyahoga Falls, Ohio 1150 WCUM Cumberland, Md. 1230 WCVQ Culpeper, Va. 490 WCVI Connelisville, Pa. 1340 WCVP Connelisville, Pa. 1340 WCVP Murphy, N.C. 600 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Ripon, Wis. 1600 WCVC Ripon, Wis. 1600 WCVD R	WCSS Amsterdam, N.Y.	1490	WEAQ Eau Claire, Wis, WEAS College Park, Ga	790 1570	WFBC Greenville, S.C.	1330	WGIV Charlotte, N.C.	1600
WCUE Cuyahoga Falls, Ohio 1150 WCUM Cumberland, Md. 1230 WCVQ Culpeper, Va. 490 WCVI Connelisville, Pa. 1340 WCVP Connelisville, Pa. 1340 WCVP Murphy, N.C. 600 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Ripon, Wis. 1600 WCVC Ripon, Wis. 1600 WCVD R	WCTA Andalusia, Ala	920	WEAT W. Palm Beach, Fla. WEAV Plattsburg, N.Y.	850 960	WFBL Syracuse, N.Y.	1390	WGL Fort Wayne, Ind.	1250
WCUE Cuyahoga Falls, Ohio 1150 WCUM Cumberland, Md. 1230 WCVQ Culpeper, Va. 490 WCVI Connelisville, Pa. 1340 WCVP Connelisville, Pa. 1340 WCVP Murphy, N.C. 600 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Kodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Rodlak, Alaska 960 WCVQ Ripon, Wis. 1600 WCVC Ripon, Wis. 1600 WCVD R	WCTC New Brunswick, N.J.	680	WEAW Evanston, III, WEBB Baltimore, Md.	1330	WFBR Baltimore, Md.	1300	WGLD Chardon, Ohio	1500
WCWS Springheid, III. 450 WED acreesport, Fa. C. 990 WFG Black Mountains, WCWB Bristol, Va. 690 WED Rocky Mount, N.C. 990 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFH Bristol, Va. 980 WFH Bristol, Va. 980 WFH Bristol, Va. 1450 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1240 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGN WGNY NEWBURGH, N.Y. 1370	WCTW New Castle, Ind. WCUB Manitower. Wis.	1550	WEBC Duluth, Minn. WEBJ Brewton, Ala.	560 1240	WFDF Flint, Mich. WFDR Manchester, Ga	910	WGMA Hollywood, Fla.	1320
WCWS Springheid, III. 450 WED acreesport, Fa. C. 990 WFG Black Mountains, WCWB Bristol, Va. 690 WED Rocky Mount, N.C. 990 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFH Bristol, Va. 980 WFH Bristol, Va. 980 WFH Bristol, Va. 1450 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1240 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGN WGNY NEWBURGH, N.Y. 1370	WCUE Cuyahoga Falls, Ohio	1150	WEBO Owego, N.Y. WEBO Harrisburg, III.	1330	WFEA Manchester, N.Y.	1370	WGMM Millington, Tenn.	1380
WCWS Springheid, III. 450 WED acreesport, Fa. C. 990 WFG Black Mountains, WCWB Bristol, Va. 690 WED Rocky Mount, N.C. 990 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFH Bristol, Va. 980 WFH Bristol, Va. 980 WFH Bristol, Va. 1450 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1240 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGN WGNY NEWBURGH, N.Y. 1370	WCVA Culpeper, Va.	1490	WEBR Buffalo, N.Y. WEBY Milton, Fla	970	WFEC Miami, Fla, WFFE Columbia Miss	1220	WGN Chicago, III.	720
WCWS Springheid, III. 450 WED acreesport, Fa. C. 990 WFG Black Mountains, WCWB Bristol, Va. 690 WED Rocky Mount, N.C. 990 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFG Black Mountains, N.C. 1010 WED Rocky Mount, N.C. 1300 WFH Bristol, Va. 980 WFH Bristol, Va. 980 WFH Bristol, Va. 1450 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1220 WGO WGNY Newburgh, N.Y. 1240 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WGO WGNY Newburgh, N.Y. 1370 WEEL Fairfax, Va. 1310 WFH Wis, Rapids, Wis. 1320 WGO WGNY Newburgh, N.Y. 1370 WGN WGNY NEWBURGH, N.Y. 1370	WCVP Murphy, N.C. WCVD Kodlak, Alaska	600	WECL Eau Claire, WIS.	1050	WFFG Marathon, Fla.	1300	WGNI Wilmington, N.C.	1450
WCYB Bristol, Va. 699 WEED Rocky Mount, N.C. 1390 WFHG Bristol, Va. 980 WGNY Newburgh, N.Y. 1400 WEE Rensselaer, N.Y. 1300 WFHG Bristol, Va. 980 WGNY Newburgh, N.Y. 1420 WEEL Boston, Mass. 990 WFHK Pell City, Ala. 1430 WGOG Walhalla, S.C. 1460 WFHK Pell City, Ala. 1310 WFHK Wis. Rapids, Wis. 1320 WGOH Grayson, Ky. 1370 WEEL Fairfax, Va. WEEN Lafayette, Tenn. 1460 WFIG Sumter, S.C. 1290 WGOK Mobile, Ala, 900	WCVS Springfield, III.	1450	WEDO McKeesport, Pa, WEEB Southern Pines, N.C.	810	WFGN Gaffney, S.C. WFGW Black Mountains	1570	WGNO Granite City, Iil.	
WEEL Boston, Mass. 590 WFHK Pell City, Ala. 1430 WGOG Walhalla, S.C. 1460 WEEL Fairfax, Va. 1310 WFHR Wis. Rapids, Wis. 1320 WGOH Grayson, Ky. 1370 WEEN Lafayette, Tenn. 1460 WFIG Sumter, S.C. 1290 WGOK Mobile, Ala, 900	WCYB Bristol, Va.	690	WEED Rocky Mount, N.C. WEEE Rensselaer, N.Y.	1390				1520
WHITE'S RADIO LOG WEEN Lafayette, Tenn. 1460 WFIG Sumter, S.C. 1290 WGOK Mobile, Ala, 900		-	WEEL Boston, Mass. WEEL Fairfax, Va.	590 1310	WFHK Pell City, Ala. WFHR Wis, Rapids, Wis.	1430	WGOG Walhalla, S.C. WGOH Grayson, Kv.	1460
	104 WHITE'S RADIO L	UG	WEEN Lafayette, Tenn.	1460	WFIG Sumter, S.C.	1290	WGOK Mobile, Ala,	

C.L. Location	W.	C.L. Location	W a		Landin	W	CI tacattac	v .
WGOL Goldsboro, N.C.		WHMI Howell Mich	1350	WIRD	Location Ironton, Ohio		C.L. Location WIUD St. Johns, Mich.	Kc.
WGOL Goldsboro, N.C. WGOV Valdosta, Ga. WGPA Bethlehem, Pa.	950	WHMP Northampton, Mass. WHN New York, N.Y.	1400	WIRY	Ironton, Ohio / Irvine, Ky. / Plattsburg, N.Y.	1550	WILIN Mexico Pa	1220
WILL Albany, Lia	1450	WHNC Henderson, N.C.	890	TI IS		560	WIVA South Bend, Ind. WIW Cleveland, Ohio	1580 850
WGR Buffalo, N.Y. WGRA Cairo, Ga. WGRD Grand Rapids, Mich.	790	WHNY McComb, Miss. WHO Des Moines, lewa	1250	WISE	Asheville, N.C.	1390	WJWL Georgetown, Del.	900
WGRD Grand Rapids, Mich. WGRF Aguadella, P.R.	1410	WHO Des Moines, Iewa WHOA San Juan, P.R. WHOC Philadelphia Miss	870 1490	WISH	I Indianapolis, Ind.	1310	WJWT Demopolis, Ala,	1350 1450
WGRM Greenwood, Miss.	1240	WHOC Philadelphia, Miss. WHOF Canton, Ohio	1060	WISH	Shamokin, Pa. Madison, Wis.	1480	WJWT Demopolis, Ala, WJXN Jackson, Miss. WJZM Clarksville, Tenn.	1400
WGRO Lake City. Fla. WGRP Greenville, Pa.	940	WHOK Laneaster, Ohio WHOL Allentown, Pa.	1320	WISO	Ponce. P.R.	1260	WKAL Rome, N.Y.	1510
WGRY Greeneville, Tenn, WGRY Gary, Ind.	1340	WHOM New York, N.Y. WHOO Orlando, Fla.	1480	WISP	Kinston, N.C. Butler, Pa.	1230	WKAM Goshen, Ind. WKAN Kankakee, III.	1460
WGSA Ephrata, Pa. WGSB Geneva, III.	1310	WHOP Monkinsville Kv	1230	MIST	Charlotte, N.C.	1240	WKAP Allentown, Pa.	1320
WGSM Huntington, N.Y.	740	WHOS Decatur, Ala, WHOT Campbell, Ohio	800 1330		Vireuqua, Wis. San Juan, P.R.	1360		580 870
WGSR Millen, Ga. WGST Atlanta, Ga.	1570 920	WHOW Clinton, Maine	1340	WITH	Baltimore, Md. Washington, N.C.	1230	WKAT Miami Reach Fin	1360
WGSV Guntersville, Ala. WGSW Greenwood, S.C.	1270	WHP Harrisburg, Pa. WHPB Belton, S.C.	580	WITY	Danville, III	980	WKAY Glasgow, Ky. WKAZ Charleston, W.Va.	950
WGTA Summerville, Ga.	930	WHPE High Point, N.C.	1390	WIVE	Jasper, Ind. Ashland, Va.	990 1430	WKBH La Crosse, Wis.	1410
WGTC Greenville, N.C. WGTL Kannapolis, N.C.	1590 870	WHRT Hartselle, Ala.	860 1600	IWIVI	Christiansted V I	970 860	WKBI St. Mary's, Pa.	1400
WGTM Wilson, N.C. WGTN Georgetown, S.C.	1400	WHRY Ann Arbor, Mich. WHSC Hartsville, S.C.	1450	MINA	Knoxville, Tenn. Viegues, P.R. Jacksonville, Fla.	1370 1050	WKBK Keene, N.H.	1220
WGTO Cypress Gardens, Fla. WGUN Decatur, Ga.		WHSL Wilmington, N.C. WHSM Hayward, Wis,	910	IWIXI	K New Richmond, Wis.	1590	WKBN Youngstown, Ohio	1250 570
WGUS North Augusta, S.C.	1380	WHSY Hattlesburg, Miss, WHTC Holland, Mich.	1230	WISS	Dixon, III. C Oakland Park, Fla.	1460	WKBO Harrisburg, Pa. WKBR Manchester, N.H.	1230 1250
WGUY Bangor, Maine WGVA Geneva, N.Y.	1250 1240	WHTG Eatontown, N.J.	1410	WITH	l Rome, Ga. Springfield, Ohio	1360	WKBV Richmond, Ind.	1490
WGVM Greenville, Miss,	1260 1340	WHUB Cookeville, Tenn. WHUC Hudson, N.Y.	1230	WIZA	Johnstown, N.Y.	930	WKBX Kissimmea Fla	1220
WGWR Asheboro, N.C.	1260	WHUM Reading, Pa. WHUN Huntington, Pa.	1240	I WIZZ	Henderson, N.C. Streator, III.	1450 1250	WKCT Bowling Green, Ky.	850 930
WGY Schenectady, N.Y. WGYV Greenville, Ala.	1380	WHUT Anderson, Ind. WHVF Wausau, Wis. WHVR Hanover, Pa.	1470	WIAG	Westbrook, Me. Johnstown, Pa.	1440 850	WKCW Warrenton, Va.	1420
WHA Madison, Wis. WHAB Baxley, Ga.	970 1260	WHYR Hanover, Pa.	1280	IWIAG	i Morfolk, Nebr.	780	WKDE Altavista, Va.	1280
WHAI Greenfield, Mass. WHAK Rogers City, Mich.	1240	WHWB Rutland, Vt. WHWH Princeton, N.J.	1000	WIA	C Jackson, Tenn. Marion, Ala,	1460	WKDK Newberry, S.C.	1240
WHAK Hogers City, Mich. WHAL Shelbyville, Tenn,	1400	WHYE Roanoke, Va. WHYL Carlisle, Pa.	910	WIAN	i Ishpeming, Mich. R Providence, R.I.	970 920	WKDN Camden, N.J. WKDX Hamlet, N.C. WKEE Huntington, W. Va.	800
WHAL Shelbyville, Tenn, WHAM Rochester, N.Y. WHAN Haines City, Fia.	930	WHYN Springfield, Mass. WIAC San Juan, P.R.	560 740	WJAS	Providence, R.I. Pittsburgh, Pa.	1320	WKEE Huntington, W. Va.	800
WHAP Honewell Va	1340	WIAM Williamston, N.C.	900	WIAX	Swainsboro, Ga, Lacksonville, Fla, Mullins, S.C.	930	WKEN Dovec Del	1450 1600
WHAR Clarksburg, W.Va. WHAS Louisville, Ky. WHAT Philadelphia, Pa.	1340 840	WIBB Macon, Ga.	1310	YALW	Mullins, S.C. Albany, Ga.	1280 960	WKEU Griffin, Ga. WKEY Covington, Va.	1450
WHAT Philadelphia, Pa.	1340	WIBC Indianapolis, Ind. WIBG Philadelphia, Pa.	1070	IMIBE	Haleyville, Ala, Bloomington, III.	1230	WKFD Wickford, R.I.	1370
WHAV Haverhill, Mass. WHAW Weston, W.Va.	980	WIRM lockson Mich	1450	I W J B D	Salam, Ili	1350	WKGN Knoxville, Tenn. WKHM Jackson, Mich.	1340 970
WHAY New Britain, Conn. WHAZ Troy, N.Y. WHB Kansas City, Mo.	910	WIBR Baton Rouge, La. WIBU Poynette, Wis.	1300	WIRE	Detroit, Mich, Holland, Mich, Jerseyville, ill.	1260	WKIC Hazard, Ky. WKIC Urbana, III.	1390
WHBB Selma, Ala.	710 1490	WIRV Rolleville III	1260 580	WIBA	M Jerseyville, ill. I Baton Rouge, La.	1480	WKIG Glenville, Ga. WKIK Leonardtown, Md.	1580
WHBC Canton, Oblo WHBF Rock Island, III.	1480	WIBW Topeka, Kans. WIBX Utica, N.Y.	950	MIBS	DeLand, Fla.	1490	WKIN KINGSDOPT, TANK	1370
WHBG Harrisonburg, Va.	1360	WICC Bridgeport, Conn. WICE Providence, R.I.	600 1290	Mico	Wheeling, W.Va. Seymour, Ind. Sebring, Fla.	1390	WKIS Orlando, Fla	1450 740
WHBL Sheboygan, Wis. WHBN Harrodsburg, Ky.	1330	WICH Norwich, Conn. WICK Scranton, Pa.	1310				WKIX Baleigh, N.C.	850 1500
WHBO Tampa, Fia.	1050	WICO Salishury, Md	1320	WIDA	Quincy, Mass. Thomasville, Ala. Jackson, Miss. Salisbury, Md. Grand Rapids, Mich.	1300	WKJB Mayaguez, P.R.	710
WHBT Harriman, Tenn.	1600	WICU Erie, Pa. WICY Malone, N.Y.	1490	Wips	Jackson, Miss.	620	WKJG Fort Wayne, Ind. WKKD Aurora, III.	1380 1580
WHBU Anderson, Ind. WHBY Appleton, Wis.	1240	WIDE Biddeford, Maine WIDU Fayetteville, N.C.	1400	WJEF	Grand Rapids, Mich.	1230	WKKO Cocoa, Fla. WKKS Vanceburg, Ky,	860 1570
WHCC Waynesville, N.C. WHCO Sparta, III.	1400	WIEL Elizabethtown, Ky.	1400	MILH	Hagerstown Md	1240	WKLA Ludington, Mich.	1450
WHCU Ithaca, N.Y. WHDF Houghton, Mich.	870 1400	WIFM Elkin, N.C. WIGL Superior, Wis, WIGM Medford, Wis,	970	WIEN	Valdosta, Ga. Dover, Ohio	1150	WKLE Washington, Ga.	1300
WHDH Boston, Mass.	850	WIIN Atlanta, Ga.	970	WJES	Johnston, S.C.	1570	WKLE Washington, Ga. WKLF Clanton, Ala. WKLJ Sparta, Wis.	980
WHDH Boston, Mass. WHDL Qlean, N.Y. WHDM McKenzie, Tenn.	1450 1440	WIKB Iron River, Mich. WIKC Bogalusa, La.	1230	WJFC	Jefferson City, Tenn.			1230 980
WHEB Portsmouth, N.H. WHEC Rochester, N.Y.	750 1460	WIKC Bogalusa, La, WIKE Newport, Vt, WIKY Evansville, Ind,	1490 820	MIHO	Opelika, Ala,	1400	WKLM Wilmington, N.C. WKLO Louisville, Ky. WKLV Blackstone, Va.	1080
Wriee Martinsville, Va.	1370 620	WIL St. Louis, Mo. WILA Danville, Va.	1430	Will	Tullahoma, Tenn. Jacksonville, III. Lansing, Mich.	1550	WKLX Paris, Ky. WKLY Hartwell, Ga.	1440
WHEN Syracuse, N.Y. WHEO Stuart, Va. WHEP Foley, Ala.	1270	WILD Boston, Mass.	1090	I WJIV	Savannah, Ga.	900		980 1470
WHEP Foley, Ala. WHER Memphis, Tenn. WHEW Riveria Beach, Fia.	1310	WILE Cambridge, Ohio WILI Willimantie, Conn.	1270 1400	WILL	Commerce, Ga. Chicago, III. Niagara Falls, N.Y.	1160	WKMC Hoaring Sprgs,, Pa.	1370 1470
WHEY Millington, Tenn,	1600	WILK Wilkes-Barre, Pa. WILL Urbana, III.	980 580	WILM	Niagara Falls, N.Y. Lewisburg, Tenn.	1440	WKMH Dearborn, Mich, WKMI Kalamazoo, Mich,	1310
WHFB Benton Harbor, Mich. WHFC Cicero, III.	1060	WILM Wilmington Del	1450 1570	WILB	Detroit, Mich. Homewood, Ala.	1400	WKMK Blountstown, Fla.	1370
WHGB Harrisburg, Pa.	1400	WILO Frankfort, Ind. WILS Lansing. Mich.	1320	WILK	Asbury Park, N.J.	1310	WKMT Kings Mtn., N.C. WKNE Keene, N.H.	1220
WHGR Houghton L., Mich. WHHH Warren, Ohio	1440	WILZ St. Petersburg Beach, Florida	1590	WIMA	Beckley, W.Va. Orange, Va.	1340	WKNX Saginaw, Mich, WKNY Kingston, N.Y.	1210
WHHL Holly Hill, S.C. WHHM Memphis, Tenn. WHHT Lucedale, Miss.	1340	WIMA Lima, Ohlo	1150	I W J M E	Brookhaven, Miss.	1340	WKOA Hopkinsville, Ky. WKOK Sunbury, Pa.	1480
WHHY Lucedale, Miss. WHHY Hillsville, Va.	1440	WIMS Michigan City, Ind. WINA Charlottesville, Va. WINC Chicago, Ill. WIND Chicago, Ill. WINF Manchester, Conn. WING Dayton, Ohio	1420	MIWI	Rice Lake, Wis, Philadelphia, Pa. Cleveland Hgts., Ohio	1540		1360
WHHY Montgomery, Ala.	1440	WINC Winchester, Va.	1400	WIME	New Orleans, La.	990	WKOS Ocala, Fla. WKOV Wellston, Ohio WKOW Madison, Wis.	1370
WHIE Griffin, Ga. WHIH Portsmouth, Va.	1400	WIND Chicago, III. WINF Manchester, Conn.	560 1230	WIMS	tronwood, Mich. V Athens, Ala. C Florence, S.C.	630 730	WKOW Madison, Wis.	1070
WHIL Medford, Mass. WHIM E. Providence, R.I.	1430	WING Dayton, Ohio WINI Murphysboro, III.	1410	WINC	Florence, S.C. Jacksonville, N.C.	970 1240	WKOX Framingham, Mass, WKOY Bluefield, W.Va. WKOZ Kosciusko, Miss, WKPA New Kensington, Pa,	1240
WHIN Gallatin, Tenn,	1010	WINK Fort Myers, Fla.	1240	MIND	W. Palm Beach, Fla.	1230	WKPA New Kensington, Pa.	1350
WHIN Gallatin, Tenn, WHIO Dayton, Ohio WHIP Mooresville, N.C.	1350	WINN Louisville, Ky. WINQ Tampa, Fla.	1240	MIOE	Hammond, Ind. Ward Ridge, Fia.	1230	WKPR Kalamazoo, Mich. WKPT Kingsport, Tenn.	1420
WHIR Danville, Ky. WHIS Bluefield, W. Va.	1440	WINR Binghamton, N.Y. WINS New York, N.Y.	1010			1340 1340	WKRC Cincinnati, Ohio	550 710
WHII New Bern, N.C.	1450	WINS New York, N.Y. WINT Winter Haven, Fla. WINX Rockville, Md. WINY Putnam, Conn. WINZ Miami, Fla.	1360	WION	South Mayon Mich	940	WKRK Murphy, N.C.	1390
WHIZ Zanesville, Ohio	1240	WINY Putnam, Conn.	1350	MJOT	Lake City, S.C.	1260	WKRO Caire, III.	1340 1490
WHJB Greensburg, Pa. WHJC Matawan, W.Va. WHK Cleveland, Ohio	1300	WIOI NEW Boston, Onto	1010	WJDA	Washington, Pa.	1230 1450	WKPR Kalamazoo, Mich, WKPT Kingsport, Tenn, WKRC Cincinnati, Ohio WKRG Mobile, Aia, WKRK Murphy, N.C., WKRM Columbia, Tenn, WKRC Cairo, III, WKRS Waukegan, III. WKRY Cortland, N.Y. WKRW Cartersville, Ga. WKRZ Oli City, Pa.	920
WHKP Hendersonville, N.C.	1420 1450	WIOI New Boston, Ohio WIOK Normal, III, WION Ionia, Mich, WIOS Tawas City, Mich,			Isnoemine, Mich.	1240	WKRY Cartersville, Ga.	1340
WHKY Hickory, N.C.	1290	WIOS Tawas City, Mich, WIOU Kokomo, Ind.	1480	WIPE	Herrin, III. Green Bay, Wis. Greenville, Miss.	1440	WKSB Milford, Del.	930
WHK Cleveland, Onlo WHKP Hendersonville, N.C. WHKB Virginia, Minn. WHLD Niagara Falls, N.Y. WHLF South Boston, Va. WHLI Wheeling, N.Y. WHLL Wheeling, W.Va. WHLL Wheeling, Pa.	1270	WIP Philadelphia, Pa.	610	WJPS	Evansville, Ind.	1330	WKRZ Oil City, Pa. WKSB Milford, Del. WKSC Kershaw, S.C. WKSK W. Jefferson, N.C. WKSR Pulaski. Tenn.	1300 1600
WHLI Hempstead, N.Y.	1100	WIP Philadelphia, Pa. WIPC Lake Wales, Fia. WIPR San Juan, P.R.	1280 940	WIR	Detroit, Mich.	760	WKSR Pulaski, Tenn, WKST New Castle, Pa.	1420 1280
	1600 550	WIPS Ticonderoga, N.Y. WIRA Fort Pierce, Fla.	1250 1400	WJRD	Evansville, Ind. Jackson, Miss. Detroit, Mich. Joliet, III. Tuscaloosa, Ala. Lenoir, N.C.	1510	WKTG Thomasville Ge	1310 730
WHLO Akron Ohio	1410 640	WIFN San Juan, F.R., WIFN Ticonderoga, N.Y. WIRA Fort Plerce, Fla. WIRB Enterprise, Aia. WIRC Hickory, N.C. WIRD Lake Placid, N.Y.	630	WIRI	Lenoir, N.C.	1340	WKST Pulaski, Jenn. WKST New Castle, Pa. WKTC Charlotte. N.C. WKTG Thomasville, Ga. WKTJ Farmington, Maine	1380
WHIS Port Musen Mich	1570	WIRD Lake Placid, N.Y.	920	WIRM		1390	WKTQ South Paris, Maine	950 1450
WHLT Huntington, Ind.	1300	WIRE Indianapolis, ind. WIRJ Humboldt, Tenn.	740	WISB	Crestview, Fla.	1050	WKTX Atlantic Beach, Fia.	1600
WHMA Anniaton, Ala. WHMC Gaithersburg, Md.	1150	WIRJ Humboldt, Tenn. WIRK W. Palm Beach, Fia. WIRL Pecria, III.	1290	MILM	Jamestown, N.Y.	1590 1240	WHITE'S RADIO LOG	183

44		.=:-						
C.L. Location WKTY LaCrosse, Wis.	Kc. 580	C.L.	Location Loves Park, III.	Kc.	C.L. Location WMRP Flint, Mich,		C.L. Location	Kc.
WKUL Cullman, Ala.	1340	WLVA	Lynchburg, Va.	590	WMSA Massena, N.Y.	1570 1340	WOKE Winter Corden Ele	1310 1600
WKVA Lewistown, Pa. WKVM San Juan, P.R.	920 810	WLW	Nashville, Tenn. Cincinnati, Ohio	700	WMSK Morganfield, Ky.	1480 1550	WOKE Charleston, S.C.	1340 1450
WKVT Brattleboro, Vt. WKWF Key West, Fla. WKWK Wheeling, W.Va.	1600	WLYN	Albany, Ga. Lynn, Mass.	1250 1360	WMSR Manchester, Tenn	1400	WOKJ Jackson, Miss. WOKO Albany, N.Y. WOKS Columbus, Ga.	1590 1460
WKWS Rocky Mount, Va.	1400	WLYC	New Orleans, La. Williamsport, Pa.	940 1050	WMST Mt, Sterling, Ky.	600	WOKS Columbus, Ga. WDKW Brockton, Mass.	1340
WKXL Concord, N.H. WKXV Knoxville, Tenn	1450	WMAB	Munising, Mich. Netter, Ga,	1400	WMTA Central City, Kv.	1380	WOKY Milwaukee, Wis.	920
WKXY Sarasota, Fla. WKY Oklahoma City, Okla.	930 930	WMAF	Madison, Fla	1230	WMTE Manistee, Mich.	1340	WOL Washington D.C.	1570 1450
WKYB Paducah, Ky, WKYN Rlo Piedras, P.R.	570	WMAJ	Forest, Miss. State College, Pa.	1450	WMTM Moultrie, Ga.	1300	WOLF Syracuse, N.Y.	1330
WKYR Kaysar W Va	630 1270	WMAL	Nashville, Tenn. Washington, D.C.	1300 630	WMTR Morristown, N.J.	1300 1250	WUMI Uwenshoro, Kv.	1230
WKYW Louisville, Ky. WKZO Kalamazoo, Mich.	900 590	WMAN	Marinette, Wis. Mansfield, Ohlo	570 1400	WMUS Muskegon, Mich.	1090	WOMP. Bellaire, Ohlo WOMT Manitowee, Wis	1290
WKZO Kalamazoo, Mich, WLAC Nashville, Tenn, WLAD Danbury, Conn.	1510 800	WMAQ	Monroe, N.C. Chicago, III.	1060 670	WMUU Greenville, S.C. WMVA Martinsville, Va.	1260 1450	WONA Winona, Miss.	1570
	1450	WMAS	Springfield, Mass. Lansing, Mich.	1450	WMVB Millville, N.J. WMVG Milledgeville, Ga.	1440	WONE Dayton Ohio	980 1230
WLAG La Grange, Ga. WLAK Lakeland, Fla. WLAM Lewiston, Maine	1430	WMAA	Grand Rapids, Mich. Springfield, III.	970	WMVO Mt. Vernon, Ohio	1300	WONW Defiance, Ohio	1280
WLAN Lancaster, Pa. WLAP Lexington, Ky.	1390	WMAZ	Macon, Ga. Ambridge, Pa.	940 1460	WMYN Mayodan N.C.	1450	WOOF Dathan Al-	560
WLAU Rome Ga	630 1410	WMBC	Macon, Miss	1400	WMYR Ft. Myers, Fla. WNAB Bridgeport, Conn.	1410 1450	WOOO Deland, Fla.	1340
WLAS Jacksonville, N.C.	910	WMBG	Peoria, III. Richmond, Va.	1470	WNAU Boston, Mass, WNAD Norman, Okla.	680 640	WUPA Dak Park III	1340
WLAU Conway, S.C. WLAU Laurel, Miss.	1330 1600	WMBI	Joplin, Mo. Chicago, III.	1450	WNAE Warren, Pa. WNAG Grenada, Miss	1310		1490 710
WLAV Grand Rapids, Mich. WLAW Lawrenceville, Ga.	1340	WMBM	Morehead City, N.C. Miami Beach, Fla.	740 1490	WNAH Nashville, Tenn. WNAK Nanticoke, Pa.	1360 730	WORA Mayaguay D D	760 1310
WLAY Muscle Shoals, Ala. WLBA Gainesville, Ga.	1450 1580	WMBN	Petoskey, Mich. Auburn, N.Y.	1340	WNAM Neenah, Wis. WNAR Norristown, Pa.	1280	WORD Spartanburg, S.C.	910
WLBB Carroliton, Ga. WLBC Muncie, Ind.	1100	AWRK	Jacksonville, Fia. Uniontown, Pa.	1460 590	WNAT Natchez, Miss. WNAU New Albany, Miss.	1450		1350 950
WLBE Leesburg, Fla. WLBG Laurens, S.C.	790	WMC	Memphis, Tenn. New York, N.Y.	790	WNAV Annapolis, Md. WNAX Yankton, S. Dak.	1430	WORM Savannah, Tenn.	1010
WLBH Mattoon, III.	860 1170	WMCH	Church Hill, Tenn. Columbia, Tenn.	1260	WNBC New York, N.Y.	570 660	WORT New Smyrna Beach, Florida	
WLBI Denham Springs, La. WLBJ Bowling Green, Ky.	1220	WMCR	Oneida, N.Y.	1280 1600	WNBF Binghamton, N.Y. WNBH New Bedford, Mass.	1290	WOSC Fulton, N.Y.	1270 1300
WLBK DeKalb, III. WLBL Stevens Point, Wis.	1360 930	WMDC	Harvard, III. Hazlehurst, Miss.	1600 1220	WNBS Murray, Kv.	1470		1490 820
WLBN Lebanon, Ky. WLBR Lebanon, Pa	1590 1270	WMDN	Midland, Mich.	1480	WNBT Wellsboro, Pa. WNBZ Saranac Lake, N.Y.	1490	WOTT Watertown, N.Y.	1370 1410
WLCK Scottsville, Ky.	620 1250	WMEK	Eau Gallie, Fla. Chase City, Va.	920 980	WNCA Siler City, N.C. WNCC Barnesboro, Pa.	1570 950	WOTW Nashua, N.H. WOUB Athens, Ohio	900 1340
WLCM Lancaster, S.C. WLCN Laurensburg, N.C.	1360			1330	WNCG N. Charleston, S.C. WNCO Ashland, Ohio	910	WOVE Welch, W.Va	1340 590
WLCO Eustis, Fla. WLCS Baton Rouge, La.	1240 910	WMEX	Marion, Va. Boston, Mass. Monroeville, Ala.	1510	WNDB Daytona Beach, Fla. WNDR Syracuse, N.Y.	1150	WOWE Allegan, Mich.	1580 1570
WLCX LaCrosse, Wis. WLCY St. Petersburg, Fla.	1490			630 1240	WNDU South Bend, Ind.	1260	WOWI Clorence Ale	1240
WLDB Atlantie City, N.J.	1380	WMFJ	Hibbing, Minn. Daytona Beach, Fla.	1450	WNEB Worcester, Mass. WNEG Taccoa, Ga.	630	WOWW Naugatuck, Conn.	860 860
WLDB Atlantie City, N.J. WLDS Jacksonville, III. WLDY Ladysmith, Wis.	1180	WMFT	High Point, N.C. Terre Haute, Ind. Moultrie, Ga.	1230 1300	WNER Live Oak, Fla, WNES Central City, Ky.	1250 1050	WILE Deford N.C.	500d 1340
WLEC Sandusky, Ohio	1480 1450	WMGR	Bainbridge, Ga.	1400 930	WNEW New York, N.Y. WNEX Macon, Ga.	1130	WPAB Ponce. P.R.	900 550
WLEE Richmond, Va. WLEM Emporium, Pa.	1480	WMGW	Bowling Green, Ohio Meadville, Pa,	730 1490	WNGA Nashville, Ga, WNGO Mavfield, Kv.	1600	WPAC Patchogue, N.Y.	1580 1450
WLEO Ponce, P.R. WLGS Lawrenceville, Va.	1170 580	WMGY	Montgomery, Ala. Atlantic City, N.J.	800 1340	WNHC New Haven, Conn. WNIA Cheektowaga, N.Y.	1340	WPAG Ann Arbor, Mich.	1050 730
WLET Toccoa, Ga, WLEU Erie, Pa.	1420 1450			1 (40	WNIK Arecibo, P.R. WNIL Niles, Mich.	1230	WPAM Pottsville, Pa. WPAP Fernandina Beach,	1450
WLEW Bad Axe, Mich.	1340	WMIL	Middlesboro, Ky. Milwaukee, Wis. Mpls. St. Paul, Minn.	1290	WNJH Hammonton, N.J. WNJR Newark, N.J.	1580	WPAQ Mount Airy, N.C.	1570 740
WLFA Lafayette, Ga. WLFH Little Falls, N.Y.	1590 1230	AN INT I C	fron Mountain, Mich.	1450	WNKY Neon, Ky.	1480	WPAR Parkersburg, W.Va.	1450
WLIB New York, N.Y. WLIJ Shelbyville, Tenn.	1190 1580	WMIX	Matchez, Miss. Mt. Vernon, III.	940	WNLC New London, Conn. WNLK Norwalk, Conn.	1350	WPAT Paterson, N.J. WPAX Thomasville, Ga.	930 1240
WLIK Newport, Tenn. WLIL Lenoir, Tenn.	730	WMLF	Cordele, Ga, Pineville, Ky, Beverly, Mass,	1490 1230	WNMP Evanston, III. WNNC Newton, N.C. WNNJ Newton, N.J.	1590 1230	WPAZ Pottstown, Pa.	1400 1370
WLIP Kenosha, Wis. WLIQ Mobile, Ala.	1050 1360	WMLS	Sylacauga, Ala. Dublin, Ga.	1570	WNNT Warsaw, Va.	1360 690	WPCC Clinton, S.C.	980 1400
WLIS Old Saybrook, Conn. WLIV Livingston, Tenn.	920	MININB	Melbourne, Fla.	1330	WNOE New Orleans, La. WNOG Naples, Fla.	1060	WPCO Mt. Vernon, Ind.	1430
WLIZ Lake Worth, Fla. WLKM Three Rivers, Mich.	1380	WMMH	Marshall, N.C. Westport, Conn.	1460	WNOK Columbia, S.C. WNOO Chattanooga, Tenn,	1230 1260	WPDM Potsdam, N.Y.	1470
WLKW Providence, R.I. WLLE Raleigh, N.C.	990 570	WMMS	Fairmont, W.Va. Bath, Maine	920 730	WNOP Newport, Ky. WNOR Norfolk, Va.	740 1230	WPDR Portage, Wis, WPDX Clarksburg, W.Va, WPEG Winston-Salem, N.C.	1350 750
WLLH Lowell, Mass. WLLY Wilson, N.C.	1400 1350	WMMW	Meriden, Conn. Gretna, Va.	1470 730	WNOS High Point, N.C.	1590	WPEG Winston-Salem, N.C. WPEH Louisville, Ga.	1550 1420
WLMJ Jackson, Ohio	1280	WMNB	No. Adams, Mass. Morganton, N.C.	1230	WNOW York, Pa. WNOX Knoxyllle, Tenn. WNPS New Orleans, La.	990	WPEL Montrose, Pa.	1250
WLNA Peckskill, N.Y. WLNG Sag Harber, N.Y.	1600	WMNE	Menomonie, Wis,	1360	WNPT Tuscaloosa, Ala.	1280	WPEO Peorla III	1020
WLNH Laconia, N.H. WLOA Braddock, Pa.	1350 1550	WMNS	Olean, N.Y. Manati, P.R. Montezuma, Ga.	1360 1500	WNRG Grundy, Va.	1250	WPEP Taunton, Mass. WPET Greensboro, N.C. WPFA Pensacola, Fla.	1570 950
WLOA Braddock, Pa, WLOB Portland, Maine WLOC Munfordville, Ky.	1310	WMNZ	Montezuma, Ga.	1050	WNRK Newark, Del.	1260	WPFB Middletown, Ohio	790 910
	1490	WMOC	Chatlanoona, Tenn	1490	WNRG Grundy, Va, WNRG Grundy, Va, WNRI Woonsocket, R.I. WNRK Newark, Del. WNRV Narrows, Va, WNSH Highland Park, III. WNSL Laurel, Miss, WNSM Valoraries, Nicosilla	1430	WPFP Park Falls, Wis.	1580 1450
WLOE Leaksville, N.C. WLOF Orlando, Fla. WLOG Logan, W.Va. WLOH Princeton, W.Va.	950 1230	WMOD	Mobile, Ala	1370 1550	Wilder Valparatso-Hitchelle,			980 1580
WLOH Princeton, W.Va.	1490 1540	WMOG	Brunswick, Ga. Hamilton, Ohio	1490 1450	WNTT Tazewell, Tenn.	1250	WPGW Portland, Ind. WPHB Philipsburg, Pa.	1440 1260
WLOI LaPorte, Ind. WLOK Memphis, Tenn. WLOL Minneapolis, Minn. WLON Lincolnton, N.C.	1480 1330			920 1340	WNTT Tazewell, Tenn. WNUE Ft. Walton Beach, Fic WNUZ Falladega, Ala. WNVA Norton, Va. WNVL Nicholasville, Ky. WNVY Pensacola, Fla. WNXT Portsmouth. Ohio WNYC New York, N.Y. WOAL San Antonio. Tex	1230	WPIC Sharon, Pa. WPID Pledmont, Ala.	790 1280
WLON Lincolnton, N.C.	1050	WMOP	Mertopolis, III, Montgomery, W.Va. Ocala, Fla. Morehead, Ky. Berlin, N.H. Ravenswood, W.Va. Meridian, Miss.	900	WNVA Norton, Va. WNVL Nicholasville, Kv.	1350 1250	WPIK Alexandria, Va.	730
WLOU Louisville, Ky.	1380 1350	WMOU	Berlin, N. H.	1230 1360	WNVY Pensacola, Fla.	1230	WPIN St. Petersburg, Fla. WPIT Pittsburgh, Pa.	730
WLOX Biloxi, Miss.	1300	WMOX	Meridian, Miss.	1240	WNYC New York, N.Y.	830	WPKO Waverly, Ohio	1380
WLON Lincolnton, N.C. WLOU Asheville, N.C. WLOU Alken, S.C. WLOW Alken, S.C. WLOX Biloxi, Miss, WLPM Suffolk, Va. WLPO LaSalle, III, WLPS Lehighton, Pa. WIS Chicago, III	1460			960 1240	WNYC New York, N.Y. WOAI San Antonio, Tex, WOAP Owosso, Mich, WOAY Oak HIII. W.Va, WOBS Jacksonville, Fla, WOBT Rhinelander, Wis. WOC Davenport, Jowa WOCB W. Yarmouth, Mass, WOCH North Vernon, Ind. WOCK Okeechobee, Fla, WODY Bassent Va,	1080	WPIT Pittsburgh, Pa. WPKE Pikeville, Ky. WPKO Waverly, Ohio WPKY Princeton, Ky. WPLA Plant City, Fla. WPLB Greenville, Mich. WPLB Rockmart, Ga.	910
WLPS Lehighton, Pa. WLS Chicago, III.	1150 890	WMPL	Aberdeen, Miss. Lapeer, Mich. Hancock, Mich.	920	WOBS Jacksonville, Fla.	1360	WPLB Greenville, Mich, WPLK Rockmart, Ga.	1380 1220
WLS Chicago, III. WLSB Copper Hill, Tenn. WLSC Loris, S.C. WLSD Big Stone Gap, Va. WLSE Wallace, N.C. WLSH Lansford, Pa. WISH Pitevilla KV	1400 1570	AA 183 L. 188	Smithfield, N.C. Middleport-Pomroy,	1270	WOC Davenport, lowa	1420	WPLK Rockmart, Ga. WPLM Plymouth, Mass, WPLO Atlanta, Ga. WPLY Plymouth, Wis. WPME Punxsutawney, Pa. WPMH Portsmouth, Va. WPMP Pascagoula, Miss, WPMP Plymouth N.C.	1390 590
WLSD Big Stone Gap, Va.	1220	WMPP	Chicago Heights III	1390 1470	WOCH North Vernon, Ind.	1460	WPLY Plymouth, Wis.	1420 1540
WLSH Lansford, Pa. WLSI Pikeville, Ky.	1410	WMPS	Memphis, Tenn. So. Williamsport, Pa. Greenville, S.C.	680 1450	WOCK Okeechobee, Fla. WODY Bassett, Va.	900	WPMP Passanoula Miss	1010
WLSM Louisville, Miss.	1270	WMRB	Greenville, S.C.	1490 1490	WOHI E. Liverpool, Ohio WOHO Toledo, Ohio	1490	WPNC Plymouth, N.C.	1470
WLSM Louisville, Mys. WLSM Escanaba, Mich. WLSV Wellsville, N.Y. WLTC Gastonie, N. C.	790	WMRE	Milford, Mass. Monroe, Ga. Lewistown, Pa. Marion, Ind.	1490 1490	WOHI E. Liverpool, Ohio WOHO Toledo, Ohio WOHP Bellefontaine, Ohio WOHS Shelby, N.C.	1390 730	WPNC Plymouth, N.C. WPNF Brevard, N.C. WPNX Phenix City, Ala. WPOM Pompano Beach, Fia.	1460
WLTC Gastonia, N.C.	1370	WMRI	Marion, Ind.	860	WOI Ames, Iowa	640	WPON Pontiae, Mich.	1460
184 WHITE'S RADIO	LOG		Marion, Unio	1490 1280	WOIA Saline, Mich. WOIC Columbia, S.C.	1320	WPON Pontiae, Mich. WPOP Hartford, Conn. WPOR Portland, Maine	1410 1490

.

C.L. Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L. Location	Kc.
WPOW New York, N.Y. WPPA Pottsville, Pa. WPQR McKeesport, Pa.	1330	WROK	Location Rockford, III. Fountain City, Tenn. Rome, Ga. Ronceverte, W.Va. Scottsboro, Ala. Roanoke, Vs. Albany, N.Y.	1440	WSOK	Savannah, Ga.	1230	C.L. Location WTPI Cookville, Tenn. WTPR Paris, Tenn. WTRA Latrobe, Pa. WTRB Ripley, Tenn. WTRC Elkhart, Ind. WTRL Bradenton, Fia. WTRN Tyrone, Pa.	1550
WPQR McKeesport, Pa.	1360	WROM	Rome, Ga.	710	WSOL	Tampa, Fla. Henderson, Ky.	860	WTPR Paris, Tenn, WTRA Latrobe, Pa.	710 1480
WPRA Mayaguez, P.R. WPRC Lincoln, III.	1370	WRON	Ronceverte, W.Va.	1400	WS00	Sit. Ste. Marie, Mich.	1230	WTRB Ripley, Tenn.	1570
WPRE Prairie Du Chien, Wi	s. 980	WROV	Roanoke, Vs.	1240	WSOR	Windsor, Conn.	1480	WIRL Bradenton, Fla.	1490
	030	WROX	Clarksdale, Miss.	1450	WSPA	Spartanburg, S.C.	950	WIRD Dyersburg, Tenn	1340 1330
WPRP Ponce, P.R. WPRS Paris, III.	910	WROY	Clarksdale, Miss. Carmi III. Evansville, Ind.	1460	WSPB	Sarasota, Fla. Toledo, Ohio	1450	WIRL Bradenton, Fla. WIRN Tyrone, Pa. WIRN Dyersburg, Tenn. WIRP LaGrange, Ga. WIRR Sanford, Fla.	1400
WPRT Prestonsburg, Ky. WPRW Manassas, Va.	960 1460	WRPB	Warner Robbins, Ga. Poplarville, Miss.	1350	I W S P N	Saratoga Sprgs., N.Y. Springfield, Mass.	, 900	WTRU Muskegen, Mich.	1600
WPRY Perry, Fla.	1400	WRRI	Dallas, Tex.	1310	WSPT	Stevens Pt., Wis. Spencer, W.Va.	1010	WTRW Two Rivers, W	1330
WPTF Raleigh, N.C. WPTR Albany, N.Y.	680 1540	WRRZ	Rockford, III. Clinton, N.C.	1330 880		Milton, Fla.	1400		980 1450
WPTS Pittston, Pa. WPTW Pigua, Ohlo	1540	WRSA	Saratoga Sprgs., N.Y.					WTSA Brattleboro, Vt. WTSB Lumberton, N.C. WTSL Hanover-Lebanon	1340
WPTX Lexington Pk., Md. WPUP Galnesville, Fla.	920	WKSL	Stanford, Ky. Jackson, Mich.	1520	WSRW	Hillsbore, Ohio	1590	WISL Hanover-Lebanon. New Hampi WISN Dover, N.H. WISV Claremont, N.H. WITB Vero Beach, Fla. WIIC Towanda, Pa. WIIF Timn, Ohio WITH Part Huran Miel	INITE 1400
WPUV Pulaski, Va.	1580	WRSW	Warsaw, Ind.	1480	WSSC	Sumter, S.C.	1340	WTSV Claremont, N.H.	1270 1230
WPVA Colonial Hights., Va. WPVL Painesville, Ohio	1460	WRTE	Warsaw, Ind. Altoona, Pa. Rantoul, III.	250d	WSSV	Starkville, Miss, Petersburg, Va.	1230	WTTB Vero Beach, Fla.	1490
WPYB Bensen, N.C. WQAM Miami, Fla.	1580 560	WRUF	Gainesville, Fla. Rumford, Maine	850 790	WSTC	Stamford, Conn.	1400	WTTF Timn, Ohio WTTH Port Huron, Mid	1600
WQBC Vicksburg, Miss, WQDY Calais, Maine	1420 1230	WRUN	Utica, N.Y. Russellville, Ky,	1150	WSTL	Eminence Kv	1600	WITTI Madisonville My	, 1310
WOIC Meridian, Miss.	1390	WRVA	Richmond. Va.	1140	WSTR	Sturgis, Mich,	1230	WITM Trenton, N.J. WITN Watertown, Wis.	920 1580
WQIK Jacksonville, Fla, WQMN Superior, Wis,	1320	WRVM	Mt. Vernon, Ky. Rochester, N.Y. Augusta, Ga.			Massena, N.Y. Suart, Fla.	1450	WTTR Westminster, Md WTTS Bloomington, Ind. WTUF Mobile, Ala.	. 1470 1370
WQMR Silver Spring, Md. WQOK Greenville, S.C.	1050 1440	WRWD	Augusta, Ga. Cleveland, Ga.	1480	WSTV	Steubenville, Ohio	1340	WTUF Mobile, Ala.	840 790
WQSN Charleston, S.C.	1450	WRWJ	Selma, Ala.	1570	WSIJH	Oxford, Miss. Iowa City, Iowa	910	WTUG Tusealoosa, Ala, WTUP Tupelo, Miss,	1490
WQSR Solvay, N.Y. WQTE Monroe, Mich.	560	WRYM	Roxboro, N.C. New Britain, Conn.	840			620	WTUX Wilmington, Del WTVB Coldwater, Mich. WTVL Waterville, Main	1590
WQTY Arlington, Fla. WQUA Moline, III.	1220	WSAC	Pittsburgh, Pa. Fort Knox, Ky. Sarasota, Fla.	1470	WSUZ	Seaford, Del. Palatka, Fla, Harrisonburg, Va.	800	WTVL Waterville, Main WTVN Columbus, Ohio	610
WQVA Quantice, Va. WQXI Atlanta, Ga.	1250 790	WSAF	Sarasota, Fla. Cincinnati, Ohio	1360	WSVL	Shalbyville, Ind.	1520	WTWA Thomson, Ga.	1240
WQXL Columbia, S.C.	1320	WSAJ	Grove City Pa	1340	WSVN	Valdese, N.C.	1490	WTWN St. Johnsbury, V	t. 1340
WQXQ Ormond Bch., Fla. WQXR New York, N.Y. WQXT Palm Beach, Fla.	1560	WSAM	Saginaw, Mich.	1400	WSW	Belle Glade, Fla,	900	WTWN St. Johnsbury, V WTXL W. Spgfd., Mas WTYC Rock Hill, S.C. WTYM East Longmeador	1150
W KAA Luray, Va.	1340	WSAD	Allentown, Pa. Sanitobia, Miss.	1330	MOMA	Y PISTIEVILLE, WIS.	1230	N N	ass, 1600
WRAB Arab, Ala.	1380	WSAR	Fall River, Mass, nr. Salisbury, N.C.	1480	WSVR	Rutland Vt	1380	WIYN Tryon, N.C.	1550 1340
WRAD Radford, Va.	1460	WSAU	Wausau, Wis. Savannah, Ga.	550 630	WSYL		1490		1080
WRAG Carrollton, Ala, WRAJ Anna, III.	590 1440	WSAY	Rochester, N.Y. Huntington, W.Va.	1370	WTAB	Tabor City, N.C.	1370	WULA Eufaula, Ala. WUNE Baton Rouge, La	1240 1550
WRAK Williamsport, Pa. WRAL Raieigh, N.C.	1400 1240	WSAZ WSB	Muntington, W.Va. Milanta, Ga.	930 750	WTAD	Flint, Mich. Quincy, III,	600 930	WUND Rio Piedras, P. WUNS Lewisburg, Pa.	R. 1320 1010
WRAN Dover N.I.	1330	WSBA	tlanta, Ga, York, Pa, New Smyrna Beach,	910	WTAG	Worcester, Mass. Tallahassee, Fla.	580	WULA Eufaula, Ala WUNE Baton Rouge, La WUND Rio Piedras, P. WUNS Lewisburg, Pa. WUSJ Lockport, N.Y. WUSM Havelock, N.C. WUST Bethesda, Md. WYAM Altoona. Pa	1340
WRAN Dover, N.J. WRAP Norfolk, Va.	850 1340		Florida	1230	WTAN	Clearwater, Fla.	1340	WUST Bethesda, Md.	1120
WRAY Princeton, Ind.	1250	WSBS	Gt. Barrington, Mass South Bend, Ind.	860	WTAP	Parkersburg, W.Va.	1230	WVAR Richwood, W.Va.	1280
WRBB Tarpon Springs, Fla. WRBC Jackson, Miss.	1300	WSCM	Panama City Beach,				790	WVCG Coral Gables, F	1a. 1070 740
WRRI Columbus Ga	1420 980	WSCR	Seranton, Pa.	1320	WIAW	Norfolk, Va. / Bryan, Tex. Springfield, III. Robinson, III.	1240	WVEC Hampton, Va.	1490 1580
WRC Washington, D.C. WRCD Dalton, Ga, WRCK Tuscumbia, Ata,	1430	WSDB	Homestead, Fla.	1430 1560	WTAY	Robinson, III. Tuscaloosa, Ala.	1570	WVIM Vickshurg, Miss.	1490
WRCD Rienland, Wis.	970	WSDR	Sterling, III,	1240	WTBF		970	WVJP Caguas, P.R.	1110
WRCV Philadelphia, Pa.	1060	MSEL	Pontotoc, Miss,	1440	WICE	Cumperiand, Md, Flomaton, Ala. Shawano, Wis. Tell City, Ind. Traverse City, Mich. Minneapolis, Minn. Camphelisville, Ky	990	WVJS Dwensboro, Ky, WVKO Columbus, Ohio WVLD Valdosta, Ga.	1420
WRDB Reedsburg, Wis, WRDD Augusta, Maine	1400	WSER	Baldwinsville, N.Y. Elkton, Md.	1550	WICH	Shawano, Wis, Tell City, Ind.	960 1230	WVLD Valdosta, Ga. WVLK Lexington, Ky,	
WRDW Augusta, Ga. WREB Holyoke, Mass.	930	WSEV	Elkton, Md. Glen Falls, N.Y. Sevierville, Fonn.	930	WICH	Traverse City, Mich.	1400	WVLN Olney, III, WVMC Mt. Carmel, III.	740 1360
WREC Memphis, Tenn. WREL Lexington, Va.	600 1450	MPLR	Quitman, Ga. Somerset, Hy.	1490			1450		5/0
WREM Remsen, N.Y.	1480	WSFR	Sanford, Fla.	1360	WICS	Ashland, Ky. Fairmont, W.Va.	1490	WVNA Tuscumbia, Ala, WVNJ Newark, N.J. WVOE Chadburn, N.C.	1590 620
WREN Topeka, Kans, WREO Ashtabula, Ohlo	970	WSGA	Thomaston, Ga. Savannah, Ga.	1400	WIGA	Whitesburg, Ky. Thomaston, Ga.	920 1590	WVOH Hazelhurst, Ga.	920
WREV Reidsville, N.C. WRFB Tallahassee, Fla.	1220	WSGC	Elberton, Ga. Birmingham, Ala.	1400	WIEL	Philadelphia, Pa. Charleston, W. Va.	860 1490	WVOK Birmingham, Ala	1470
WRFC Athens, Ga. WRFD Worthington, Ohio	960 880	WSGO	Oswego, N.Y. Saginaw, Mich.	1440 790	WTHG	Jackson, Ala. Terre Haute, Ind.	1290	WVOM tuka. Miss.	1270 970
WRFS Alexander City, Ala.		WSHF	Sheffield, Ala. Frement, Mich,	1290	WIHM	Lapeer, Mich.	1530	WVOS Liberty, N.Y.	1240
WRGA Rome, Ga. WRGM Richmond, Va.	1590	WSHO	New Orleans, La.	1230	WIHT	Panama City, Fla, Hazleton, Pa.	1300	WVOX New Rochelle, N.	Y. 1460
WRGR Starke, Fla. WRGS Regersville, Tenn.	1370	WSIB	Shippenburg, Pa. Beaufort, S.C.	1490	WTIE	Hartford, Conn. Newport News, Va.	1080		
WRHC Jacksonville, Fla. WRHI Rock Hill, S.C.	1400	WSIC	Statesville, M.C. Baitimore, Md.	1400	WTIE	Tifton, Ga. Massillon, Ohio	900	WYSC Somerset, Pa. WYSC Somerset, Pa. WYW Grafton, W.Va. WWBC Bay City, Mich. WWBD Bamberg, S.C.	1260 1250
WRIB Providence, R.I.	1220 540	WSIG	Mount Jackson, Va, Prichard, Ala,	790 1270	WTIK	Durham, N.C. Mayaguez, P.R.	1310	WWBD Bamberg, S.C.	790 1360
WRIC Richlands, Va. WRIG Wausau, Wis.	1400 1250	WCID	Dainteullla Ma	1490	WILM	Taylorville, III.	1410	WWBZ Vineland, N.J. WWCA Gary, Ind.	1270
WRIM Pahokee, Fla. WRIP Rossville, Ga.	980	WSIV	Winter Haven, Fla. Pekin, III. Nashville, Tenn. Magee, Miss. St. Joseph, Mich.	1490	WTIX	New Orleans La	690	WWCC Bremen, Ga. WWCH Clarion, Pa.	1440
WRIS Reaneke, Va. WRIT Milwaukee, Wis.	1410	WSIX	Nashville, Tenn. Magee, Miss.	980 1280	WTJH	East Point, Ga. Jackson, Tenn.	1260	WWCO Waterbury, Con WWDC Washington, D.	n. 1240 C. 1260
	1390	WSIS	St. Joseph, Mleh, Winston-Salem, N.C.	1400	WTKM	East Point, Ga. Jackson, Tenn. Hartford, Wis. Ithaca, N.Y.	1540 1470	WWCO Waterbury, Con WWDC Washington, D. WWGP Sanford, N.C. WWGS Tifton, Ga.	1050
WRIX Griffin, Ga. WRIZ Coral Gables, Fla.	1550 1270	WSKI	Montpelier-Barre, Vt. Miami, Fla.				1370	WWHG Hornell, N.Y.	1320 /a. 1470
WRJC Mauston, Wis, WRJN Racine, Wis. WRJS San German, P.R.	1400	WSKT	Colonial Village,		WILK	Taylorsville, N.C.	12/0	WWIL Ft. Lauderdale, WWIN Baltimore, Md.	Fia. 1580
WRJW Pleavune, Miss.	1320	WSKY	Asheville, N.C.	1230	WILD	Tallasee, Ala.	1480	WWIS Black River Fall	B.,
WRKB Kannapolis, N.C. WRKD Rockland, Maine	1460 1450	WSLB	Ogdensburg, N.Y. Clermont, Fla.	1400	WTMA	Charleston S.C.	1250	WWIT Canton N.C.	Vis. 1260 970
WRKH Rockwood, Tenn. WRKM Carthage, Tenn.	580 1350	WSLI .	lackson, Miss. Salem, Ind.	930	WIMC	Tomah, Wis. Ocala, Fia. Milwaukee, Wis.	1290	WWIT Canton, N.C. WWIZ Lorain, Ohio WWJ Detroit, Mich.	1380 950
WRKT Cocoa Beach, Fla.	1300	WSLS	Roanoke, Va. Nashville, Tenn,	610	WIMP	Tampa, Fla.			1450
WRLD Lanitt, Ala,	1490	WSMA	Smyrna, Ga.	1550	WINC	Louisville, Ky. Thomasville, N.C. Orangeburg, S.C.	620 790	WWKY Winchester, Ky, WWL New Orleans, La. WWML Portage, Wis,	870
WRMA Montgomery, Ala, WRMF Titusville, Fla.	950	WSME	New Orleans, La. Sanford, Maine Greenville, Tenn,	1350 1220	WIND	Orangeburg, S.C. Coshocton, Ohio	920 1560	WWML Portage, Wis. WWNC Asheville, N.C.	1470 570
WRMN Floin III	1410 790	WSMG	Greenville, Tenn. Litchfield, III.	1450 1540	WINT	Tallahassee, Fla.	1450	WWNC Asheville, N.C. WWNH Rochester, N.H WWNR Beckley, W.Va.	930 620
WRMS Beardstown, III. WRMT Rocky Mount, N.C. WRNB New Bern, N.C.	1490	WSMN	Litchfield, III. Nashua, N.H. Sparta, Tenn. Cummings, Ga.	1590	WTOC	Savannah, Ga.	1290	WWNS Statesboro, Ga. WWNY Watertown, N.Y.	1240 790
WRNB New Bern, N.C. WRNE Wis. Rapids, Wis.	1220	WSNE	Cummings, Ga.	1410	WTOE	Savannah, Ga. Toledo, Ohio Spruce Pine, N.C. Tomah, Wis.	1470	WWOD Lynchburg, Va. WWOK Charlotte, N.C.	1390
WRNY Rome, N.Y.	1350	WSNO	Barre, Vt.	1240 1450	MIOF	Toledo, Ohlo	1460	WWOL Buffalo, N.Y.	1480
WROA Gulfport, Miss, WROB West Point, Miss,	1390 1450	WSNY	Sandersville, Ga. Seneca Twishp., S.C.	1490	WTON	Staunton, Va.	1240	WWOL Buffalo, N.Y. WWOM New Orleans, La WWON Woonsocket, R.I.	. 600 1240
WROC Rochester, N.Y. WROD Daytona Beach, Fla.	1280	WSNY	Schenectady, N.Y.	1240	WTOR	Torrington, Conn.	1490		
Dajiola Diacii, Fla.	1340	# 300	Quartotte, M.U.	930	# 1U1	Marianna, Fia.	960 [WHITE'S RADIO LOG	269

C.L.	Location		C.L.				Location	Kc.	C.L.	Location	Kc.
WWOW	Conneaut, Ohio	1360	WWY	Pineville, W.Va.	970	WYAM	Bessemer, Ala.	1450	WYSH	Clinton, Tenn.	1380
WWPA	Williamsport, Pa.	1340	WXAL	Demopolis, Ala.	1400	WYCL	York, S.C.	1580	WYSI	Ypsilanti, Mich.	1480
WWPF	Palatka, Fla.	1260	WXGI	Richmond, Va.	950	WYDE	Birmingham, Ala.	850	WYSL	Buffalo, N.Y.	1400
	W. Warwick, R.I.	1450	WXIG	Windemere, Fla.	1480	WYGO	Corbin, Kv.	1330		Franklin, Va.	1250
WWRJ	White River Junc., V				1230	WYHE	Bristol, Tenn.	1550	WYTH	Madison, Ga.	1250
WWRL	Woodside, N.Y.			Big Delta, Alaska	980	WYLD	New Orleans, La.	940		Rocky Mount, Va.	1570
WWRO	Caro, Mich.	1360		Indianapolis, Ind.	950	WYMB	Manning, S.C.	1410		Wytheville, Va.	1280
WWSC	Glens Falls, N.Y.	1450		Merrill, Wis,	730	WYND	Sarasota, Fla.		WYZE	Atlanta, Ga.	1480
WWSR	St. Albans, Vt.	1420	WXOK	Baton Rouge, La.	1260	WYNG	Warwick-East			DeFuniak Sprgs., Fla.	
WWST	Wooster, Ohio	960	WXRF	Guayama, P.R.	1590		Greenwich, R.I.	1590	WZKY	Albemarie, N.C.	1580
WWSW	Pittsburgh, Pa.	970	WXTN	Lexington, Miss,	1150	WYNK	Baton Rouge, La.		WZOR	Ft. Payne, Ala.	1250
WWVA	Wheeling, W.Va.	1170		Pawtucket, R.I.	550	WYNN	Florence, S.C.		WZOE	Princeton, III.	1490
WWWB	Jasper, Ala,	1360	WXVA	Charleston, W.Va.	1550	WYNR	Chicago, III.	1390	WZOK	Jacksonville, Fla.	1320
WWWF	Fayette, Ala.	990	WXVW	Jeffersonville, Ind.	1450	WYOU	Tampa, Fla.		W 700	Spartanburg, 8.C.	1400
WWWR	Russellville, Ala.	920	WXXX	Hattiesburg, Miss.	1310	WYPR	Danville, Va.		WZDH	Zephyr Hills, Fla.	1400
WWWW	Rio Piedras, P.R.	1520	WXYJ	Jamestown, N.Y.	1340	WYRE	Pittsburgh, Pa.	1080	WZPO	Jacksonville Beach,	1400
	Manchester, Ky.	1450	WXYZ	Detroit, Mich.	1270	WYRN	Louisburg, N.C.	1480	WZNO	Florida	1010
WWYN	Erie, Pa.	1260	WYAL	Scotland Neck, N.C.			Lakeland, Fla.				1440
				moon, moo		******	Eurorana, 11a.	1000	WEIX	Cowall, 18611.	1440
	Canadian AM Stations By Call Letters										
		- 1	ana	DION AM SI	CTI	ons.	KV CAII LA1	TAP	· (C		

Canadian AM Stations By Call Letters

				-	aidii Aiii Si	GII.	Olla	by call re	161	3		
	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
	CBA	Sackville, N.B.	1070	CFRB	Toronto, Ont.	1010	CICI	Woodstock, N.B.	920	CKGB	Timmins, Ont.	680
	CRE	Moneton, N.B. Windsor, Ont.	1300	CERC	Kingston, Ont.	1490	Cics	Stratford, Ont.	1240		Montreal, Que.	980
	CBF		690		Gravelbourg, Sask, Edmonton, Alta,	710 1260	CIDC	Dawson Creek, B.C.	560	CKGR	Galt, Ont.	1110
	CBG	Gander, Nfld.	1450	CFRS	Simcoe, Ont.			Edmundston, N.B. Smiths Falls, Ont.	630	CKKW	St. Jerome, Que. Kitchener, Ont.	900 1320
	CBH	Halifax, N.S.	790	CFRY	Portage la Prairie,		CJFP	Riviere du Loup, Que.	1400		Oshawa, Ont.	1350
	CRI S	Bydney, N.S. Chicoutimi, Que.	1140	l .	Man	. 920	CIFX	Antigonish, N.S.	580	CKLC	Kingston, Ont.	1380
	CBK	Regina, Sask,	1580 540	CETK	Weyburn, Sask. Terrace, B.C.	1340	Ciex	Yorkton, Sask. Vernon, B.C.	940	CKLD	Thetford Mines, Que.	1230
- 1	CBL 1			CFUN	Vancouver, B.C.	1410	2112	Sault Ste. Marie, Ont.	940	CKLG	N. Vancouver, B.C. Montreal, Que,	730 1570
		MCDTreal, Que.	940	ICFWH	l Whiteborse, Yukon T	570	DILD	Langley Prairie, B.C.	850	CKLN	Nelson, B.C.	1390
- 1	CBN :	St. John's, Nfld. Ottawa, Ont.	640	CFYK	Yellowknife, N.W.T.		ICIKL	Kirkland Lake, Ont.	560	CKLS	LaSarre, Que.	1240
i	CBT	Grand Falls, Nfld.	990	CHAR	Dawson, Yukon T. Moose Jaw, Sask.	1230 800	CILM	Joliette, Que.	1350	CKLW	Windser, Ont.	800
- 1	CBU	vancouver, B.C.	690	CHAD	Amos, Que.	1340	CILS	Quebec, Que. Yarmouth, N. S.			Lindsay, Ont. Mont Laurier, Que.	910 610
- 9	CBV (Quebec, Que.	980	CHAT	Medicine Hat. Alta.	1270	CJLX	Ft. Williams, Ont.	800	CKMP	Midland, Ont.	1230
- 1	CRM	Winnipeg, Man. Edmonton, Alta.	990	CHCM	. Marystown Nfld	560	CJME	Regina, Sask.	1300	CKMR	Newcastle, N.B.	790
- 7	CRXA	Edmonton, Alta.	740	CHED	Lethbridge, Alta. Edmonton, Alta.	1090	CIWE	Montreal, Que.	1280	CKNB	Campbellton, N.B.	950
i	CBY	Corner Brook, Nfld.	990	CHEE	Granby, Que.	630 1450	CINE	Chicoutimi, Que. N. Battleford, Sask.	1420 1460	CKNL	Ft. St. John, B.C. New Westminster,	970
- (CFAB	Windsor, N.S.	1450	CHEX	Paterborough, Ont.	980	CINR	Blind River, Ont,	730	CKAW	British Columbia	986
. !	CFAC	Caigary, Aita.	960	CHFA	Edmonton, Alta	680	CIOB	Winnipeg. Man.	680	CKNX	Winebam, Ont.	920
- 7	CFAR	Flin Fion, Man.	590	CHEC	Churchill, Man.	1230	Cloc	Lethbridge, Alta.	1220	CKOC	Hamilton, Ont.	1150
- i	CFAX	Victoria, B.C.	870	CHER	Toronto, Ont. St. Anne de la	1540	CION	St. John's, Nfld.	930	CKOK	Pentieton, B.C.	800
- (CFBC	Saint John, N.B.	930		Postiere Oue	1350	CION	Vancouver, B.C. Guelph, Ont.	1460	CKOM	Saskatoon, Sask, Tilisonburg, Ont,	1250 1510
		Brochet, Man.	1450	CHIC	Brampton, Ont.	1090	ClGC	Quebec, Que,	1340	CKOV	Kelowna, B.C.	630
		Sudbury, Ont, Corner Book, Nfld.	570	CHIQ	Hamilton, Ont.	1280	CJRH	Richmond Hill, Ont.	1310	CKOX	Woodstock, Ont.	1340
- i	CFCF	Montreal, Que.	600	CHLO	Three Rivers, Que. St. Thomas, Ont.	550 680	CIRL	Kenora, Ont. Summerside, P. E.1.	1220	CKOY	Ottawa, Ont.	1310
- (CECH	North Bay, Ont.	600	CHLP		1410	CISO	Sorel, Que,	1240	CKEC	Brantford, Ont. Prince George, B.C.	1380 550
- !	CFCL	Timmins, Ont.	620	CHLT	Sherbrooke, Que.	630	CJSP	Leamington, Ont.	710	CKPR	Fort William, Ont.	580
- 7	CECO	Calgary, Alta, Chatham, Ont.	1060	CHML		900	C122	Cornwall, Ont.	1220	CKPT	Peterborough, Ont.	1420
			1440	CHNC	New Carlisle, Que. Sudbury, Ont.	610	CIAI	Victoria, B.C.		CKRB	Ville St. Georges, Que.	
- (CFCW	Camrose, Alta.	1230	CHNS	Halifax, N.S.	900 960	CKAR	Montreal, Que. Huntsville, Ont.	730 590	CKED	Winnipeg, Man. Red Deer, Alta.	630 850
		Charlottetown, P.E.I.	630	CHOK	Sarnia, Ont.	1070	CKAR	-I Parry Sound, Ont.	1340	CKRM	Regina, Sask,	980
		Victoriaville, Que. Goose Bay, Nfld.	1380 1340	CHOV	Pembroke, Ont.	1350	CKBB	Barrie, Ont.	950	CKRN	Rouyn, Que.	1400
- i	CFGM		1310	CHOM		1470 1320	CKBI	Prince Albert, Sask.	900	CKRS	Jonquiere, Que.	590
- 1	CFGP	Grande Prairie, Alta.	1020	CHRC	Quebes, Que	ROO I	CKBM		1250	CKGB	Lloydminster, Alta. St. Boniface, Man.	1150
- !	CFGR	Graveidourg, Sask.	1230	CHRD	Deummandvilla Oua	1340	CKBS	St. Hyacinthe, Que.	1240	CKSL	London, Ont.	1290
- 7	CFIC	St. Joseph d'Alma, Que. Kamloops, B.C.	12/0	CHRL	Roberval, Que,	910	CKBW	/ Bridgewater, N.S.	1000	CKSM	Shawinigan, Quebec	1220
				CHRI	St. Jean, Que. Saint John, N.B.	1090	CKCH	Hull, Que,	970		Sudbury, Ont,	790
- 1	CFKL	Schemerville, Que,	1230	CHUB	Nanaimo, R.C.	1570	CKCL	Regina, Sask. Truro, N.S.	620 600	CKTR	Swift Current, Sask, St. Catharines, Ont.	1400 610
- 9	CFLM	LaTuque, Que.	1240	CHUC	Port Hone, Ont.	1500	CKCN	Seven Hes. Que.		CKTR	Three Rivers, Que.	1150
		Cornwall, Ont. Fredericton, N.B.	550	CHUM	Toronto, Ont.	1050	CKCQ	Quesnel, B.C.	570	CKTS	Sherbrooke, Que,	900
i	CFNS		1170	CHWK	Niagara Falls, Ont, Chilliwack, B.C.	1600	CKCQ	-I Williams Lake, B.C. Kitchener, Ont,	1240 1490	CKUA	Edmonton, Alta,	580
- 1	CFNW	/ Norman Wells,		ICHWO	Oskvilla Ont	1250	CKCV		1280	CKAL	Val d'Or, Que. Verdun, Que.	1230 850
		Northwest Territory	1240	CIAD	Montreal, Que	800	CKCW	Moneton, N.B.	1220	CKVM	Ville Marie, Que.	710
		Fort Frances, Ont.	1570	CJAF	Cabano, Que, Trail, B.C.	1340	CKCY	Sault Ste. Marie, Ont.	920	CKWS	Kingston, Ont.	960
- 1	CFOS	Owen Sound, Ont.	560	CIAV	Port Alberni, B.C.	610	CKDY	Victoria, B.C.	1220	CKWX	Vancouver, B.C.	1130
		Pointe Claire, Que.	1470	CJBC	Terente, Ont.	860	CKDN	I Amherst, N.S. I Dauphin, Man,	730	CKXI	Irandon, Man. Calgary, Alta.	1150 1140
- 9	CFPA	Port Arthur, Ont.	1230	CIBG	Belleville, Ont.	800	CKEC	New Glasgow, N.S.	1320	CKY V	Vinnipeg, Man.	580
- 1	CFPR	London, Ont. Prince Rupert, B.C.	980 1240		Rimouski, Que.	900	CKEK	Cranbrook, B.C.		CKYL	Peace River, Alta.	630
		Saskatoon, Sask.	600	CICE	Edmonton, Alta, Sydney, N.S.	930 1270	CKEN	Kentville, N.S. Toronto, Ont.	1350 580	VOAR	St. John's, Nfld.	1230
		Ottawa, Ont.	560	CICH	Halifax, N.S.		CKFH	Toronto, Ont.		VOWR	St. John's, Nfld. St. John's, Nfld.	590 800
					-							000

Mexican and Cuban AM Stations

Mexican stations audible in the Southwest; the more powerful Cuban stations

-				, acaibic		C 30	201114	VC31; 1116	HOLE	ρu	A CL I O	Copun	Sidilo	112	
Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.	Location	C.L.	Kc.	W.P.
- 1	Mexic	:0		CHIL				Monciova Piedras Negr		1260 920	250 1000		XEPH XEQK	1350	5000 1000
BAJA	CALIF	ORNI	A	Chihuahua	XEM XEBU XEBW	620	500 1000 1000	Sabinas Saltillo	XEMU XEBX XESJ	580 610 1250	5000 5000		XEQR	790	10000
Cuervos El Saugai	XEDY		1000 500		XEFI	580	1000		XESG	1510	1000		XERG	690 1110	250 50000
Ensenada	XEPF	1400	250 250	Ciudad Camare	XERA 10 Xeha		250 1000	VIIIa Acuna	XEBP XEDH XERF	1310	5000 250		XERH XERPM XESM	660	50000 10000 10000
Mexicali	XED	1050	5000 250	Ciudad Delicia			250	DISTRI					XEUN	860	5000
	XEAO	910	250 5000	Ciudad Juarez	XEJK		250 250	Mexico City	XEB	1220	100000	_	URANG	_	
Tijuana	XEGE	1150	1000	0,00000	XEJ	970	5000 500		XEDF XEL	970 1260	10000 5000	Durango	XEDU		1000
11/04/14	XETRA XEAU	690	50000		XEFV	1240	250		XEN	690 940	20000 150000	Linares	EVO LE	1260	250
	XEAZ	1270	5000 500	1	XEWG	1490	250		XEW	900 730	250000 500000	Monterrey	XEG	1050	150000 5000
	XEGM	950	1000 2500 5000	Hidalgo N. Casas Gran	XEJS		1000 500		XEFR		5000 10000		XEH		1000 5000
	ΧĒΧΧ		2000	N. Casas Gran	XETX	1010	250		XELZ		10000 5000		XEAR XEAW	570 1280	1000
100					AHUI				XENK	620	5000 5000		XEFB	630	5000 500
186 W	MITE'S R	ADIO	LOG	Ciudad Acuna	XEKD	1010	1000	i	XEOY	1000	50000		XEOK		

Location	C.L. Kc. V						Location	C.L.	Kc. 1			C.L. Kc.	W.P.
	IS POTOSI	' <u>'</u>		XEMS I XEMT I XEAS	1340 1410	250 250 250		CMSS	800 900		Pinar del Rio C		5000
San Luis Potos	XEWA 540 15	0000		XEBK I		100	Clenfueges Consulacion D	CMHN	680 880	1000	Č	MAN 840 MAQ 920	1000
so	NORA	- 1		XEFE	790 900	1000	Cruces Guantanamo	CMAK	1210		Sagua La Grand-	MHA 1280	1000
Agua Prieta	XEAO 1490	250		XEWL	1090 1370	2500 50000	Habana	CMW	590 550		Santa Clara (MHI 570 MHG 670	10000
Cananea	XEFH 1310 XEFQ 980	1000 500	Reynosa	XEOR		1000		CMCU	630	25000	č	MHC 1410 MHQ 640	1000
Ciudad Dbrego	XEDX 1430	1000	Rio Bravo	XERT	590 1170	5000 1000		CMBC	690	50000 10000	CI	MHW 810 MHD 1310	1000
Hermosiile	XEBH 920 XEDL 1250	5000 500	Rio Brava	XEDQ XEFW	810	50000		CMCH		5000	Saneti Spiritus	MHM 1130	1000
	XEHQ 590	50000 500	Valle Hermesa	XEVI		1000		CMBL	860	15000	C	MHT 990 MDA 1320	1000
Magdalena Naco	XEDJ 1450 XETM 1350	1000	C	uba				CMBF	950 980	5000 5000	C	MKC 770	1000
Nogales San Luis	XEHF 1870 XECB 1450	5000 250	Camaguey	CMJB	880	1000			1010	5000 10000	Ċ	MDB 680	1000 2000
Santa Ana	XEAB 1400	250		CMJL	920 960	5000 1000		CMCA	730	10000		MKW 1000 MKR 1090	2000 1000
	AULIPAS			CMJE	680	1000	Holguin	CMKJ	730 670	5000	C	MKU 630	2000 1000
Culdad Miquei Aleman	XEHI 1470 XEWD 1430	500 2000		CMJR	1030	1000	Holguin Drte	CMKM	560 600	5000	C	MKN 930 MKB 1170	1000
Cuidad Camar	XEZD 1400	250		CMJF	1340	1000		CMKV	970	1000	Victoria de las	lunas	1000
Matamores	XEO 970 XEAM 1310	1000 250	Camajuani Ciego de Avila	CMHD	890 760	1000	Marianao	CMDC	770 1560	1000 5000		MDQ 840 MKT 1520	1000
			U. S	. FN	A S	tati	ons by	Stat	es				
	A	bbrev	iatians: Mc.,				_			ianal	station		
Location	C.L.	Mc.	Location	_	L.		Location		:.L.			C.L.	Mc.
	ABAMA		H ayward I nglewood	KTY	M-FN	1 101.7	San Jose	KSJ	O-FM KRPM	92.3 98.5	,	RIDA	108.1
Albertville Alexander City	WAVU-FM WRFS-FM	105.1 106.1	LaSierra Lodi	KCV	KSD/ R-FN	97,7	San Luis Obis San Rafael	-	KTIM	96.1 100.9	Coral Gables Daytona Beach	WVCG-FM WNDB-FM	94.5
Andalusia Anniston	WCTA-FM WHMA-FM	98.1 100.5	Long Beach	KFD	KLDN	1 .88.1	San Mateo Santa Ana	KW	KCSM IZ-FM	*90.9 96.7	Fort Lauderdale	WFLM	105.9
Athens Birmingham	WAPI-EM	104.3 99.5	Los Altos	É	KNDE	97.7	Santa Barbara	a "l	KRCW	97.5	Fort Pierce	WARN WRUE-FM	98.7
	WBRC-FM WSFM	106.9 93.7	Los Angeles	KAB	KBB	1 107.5	04 01	KU	B.FM KMUZ KSCU	93.7 103.3 *90.1	Gainesville Jacksonville	WJAX-FM WMBR-FM	95.1
Clanton Culiman	WKLF-FM WFMH-FM	100.9				105.1 8 105.9	Santa Clara Santa Cruz		D-FM	99.1 99.1	Miami	WKAT-FN WCKR-FM	93.3
Decatur Homewood	WJLN	102.1		KFA	KCBH C-FR KFML	4 92.3	Santa Maria	KSM	(EYM A-FM KCRW	102.5		WGBS-FM	96.3
Huntsville Mobile	WAHR WNDA WKRG-FM	99.1 92.9 99.9		1	KGLA Kh	103.5 101.1	Santa Monica Sierra Madre		KSRF Kmax	108.1	Miami Beach	WWPB-FM WKAT-FM	101.5
Montgomery	WAJM	98.9		KN.	KML/ X-FN KPFN	4 93.1	Stockton	KST	KCVN N-FM G-FM	107.3	Deala	WAEZ-FM WMBM-FM WMDP-FM	93.9
Sylacauga Tuscumbia	WMLS-FM WVNA	98.3		KPD	L-FA	4 93.9	Turleek Ventura-Oxna	- 1	CHDM N-FM	92.9	Orlando	WDBD-FM WHOO-FM	92.3
Tuscaloosa	WTBO-FM WUDA	95.7 •91.7		KRK		4 96.3	Visalia Walnut Creek	KON	G-FM E-FM	92.9 92.1	Paim Beach	WKIS-FN WQXT-FN	100.3
Al	LASKA				KUSI	C *91.5	West Covina Woodland	-	KDWC	98.3	Pensacola St. Petersburg	WPEX-FN WGNE	l 94. l
Anchorage	KNIK KBYR-FM	105.5	Marysville	KMY	KHDI	F 99.5	1	LORA		50.0	Sarasota	WTC	99.5
AB	IZONA		Modesto	KBE	E.FA	4 103.3	Boulder		CRNW	97.3	Tallahassee	WFSU-FN WBGM-FN	1 "91.5
Globe	KWJB-FM	100.3	Monterey Mountain View	, 1	KHFI	R 96.9 C *88.5	Colorado Spri	n gs	KRCC KFMH	96.5	Tampa	WDAE-FN WFLA-FN	1 100.7
Mesa Phoenix	KBUZ-FM KELE	104.7 95.5	Newport Beacl Oakland	· .	KAFI	B 103.1 E 98.1		KVO	KSHS R-FM	92.9		WPKN	1 °88.9
	KFCA KDDL-FM KITH	*88.5 94.5 101.3	Ontario	KAS	KUD K-FR	M 93.5	Cortez Denver	KFN	KZFM IL-FM	98.5	Winter Park	WPRI	C *91.5
	KOY-FM KPHD-FM	92.5 96.9	Pasadena		KAAI KPC KAPI	R 104.7 S 89.3		KL	N-FM R-FM A-FM	100.3	Athens	DRGIA WGAU-FR	1 102.5
	KTAR-FM KYEW	98.7 93.3	Rediands	KCH	IL FI	W 96.7	Grand Junetic	n KRE	KTGM X-FM	105.1	Atlanta	WABI WPLO-FN	E *90.1
Tempe Tueson	KUPD-FM KFMM	97.9	Riverside	KLD	KPL E-FI	W 105.5	Manitou Sprin	ngs KCN	is-FM	102.7		WGKA-FN WSB-FN	92.9
	KANSAS	9000			KDU A-F	D 97.5	1	NECTI			Augusta	WAUG-FA	1 105.7
Blytheville	KLCN-FM	96.1	Sacramento	KFB	K-FI	M 96.9			W J Z Z W G H F	95.1		WRBL-FA WDUN-FA	1 103.9
Ft. Smith Jonesboro	KFPW-FM KBTM-FM	94.9				0 105.1	Danbury Hartford	,	D-FM WHCN	105.9	Lagrange Macon	WLAG-FR WMAZ-FR	4 99.1
Little Rock	KASU	91.9	1	KRA	K-FI	M 92.9		WC	CC-FM	106.9	Marietta	WBIE-FA	S 96.1
Mammeth Spi Osceela	KOSE-FM	98.1		кхо	KXR A-FI	Q 98.5 W 107.9		WRT	WSCH C-FM	*89.3	Newnan Savannah	WCOH-FA	A 97.3
Pine Bluff Sileam Sprin	KDTN-FM gs KUDA-FM	92.5 105.7	Salinas San Bernardin	KSB	W-FJ KVC	WI 102.5	Manchester	WI	IC-FM	107.9	Swainsbore Toccoa	WIAT-FR WLET-FR	
CAL	.IFORNIA			H	KEB	99.9 S *89.5	Meriden Middletown		WBMI WESU IC-FM	88.1	H.A	WAII	
Alameda Anaheim	KJAZ KEZR-FM		San Diego	KDG KFM	D-FI	W 94.1 W 100.7	Standard	WYE	3C-FM	94.3	Honolulu	KAIM-FR KVOI	< *88.1
Areata Athertes	KTOD KPEN	*90.5		KFM	X-FI	W 96.5 W 101.5	Stamford Storrs Waterbury		C-FM Whus R-FM	*90.5		KUOI	1 *90.5
Auburn Avalon	KAFI KBIQ	101.1			KJLI	T 105.3 M 98.1	1	LAWA		92.0		AHO KBOI-FA	4 97.9
Bakersfield	KERN-FM KQXR	94.1			KLR KPR	1 106.5			N-FM	94.7	Boise Lewiston	KOZE-FA	96.7
Berkeley	KPFA KPFB	94.1	San Fernando	ļ	KVFI	S *88.3 M 94.3	Wilmington		EL-FM WJBR	93.7	ILL	INOIS	
Bijou	KRE-FM KHUR	102.9	San Francisco	КВА	Y.FI	W *91.7 W 104.5		D. C.			Alton Anna	WDKZ-FR WRAJ-FR	4 92.7
Clarement Coachella	KSPC KCHQ-FM	93.7	1	KCE	38-FI	O 105.3 M 98.9 C 102.1	1	WAS	H-EM	97.1	Arlington Heig Aurora	hts WNW(0 92.7 4 95.9
El Cajon Euroka	KUFM	96.3		KED	KEA RC-FI	R 97.3			WEAN	100.3	Bloomington Carbondale	WJBC-FA WSIL	101.5 J *91.9
Fresno	KARM-FM KCIB-FM	94.5		KG	O-FI	M 103.7		WGN	WGAY 18-FM WGTB	103.5	Carmi Champaign	WROY-FR WDW8-FR	4 97.3 4 97.5
	KMJ-FM KRFM	93.7	1		KHII N-FI	P 106.9		WM/	\L.FM	107.3	Chicago	WBBM-FN WBE	2 *91.5
Garden Grove Giendale	K XQR KGGK KFMU	94.3			KSF Y-FI	R 94.9			DL-FM RC-FM DP-FM				1 101.9
diandera	KUTE				A-FI		I	WW	C-FM	101.1	WHITE'S RA	DIO LOG	187

Location	C.L.	Me.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
300011103	WDHF WEBH	95.5 93.9	Iowa City Muscatine	KSUI KWPC-FM		Plymouth	WNBH-FM WPLM-FM	98.1 99.1	NEV	ADA	
	WEFM WEHS	99.5 97.9	Sioux City Storm Lake	KDVR KAYL-FM	97.9	S. Hadley Springfield	WMHC WHYN-FM	*88.5 93.1	Las Vegas Reno	KORK-FM KNEV	97.1 95.5
٧	VENR-FM WFMF	94.7 100.3	Waverly	KWAR	89.1		W E D K W S C B	*91.7 *88.9	NEW HA	AMPSHIR	
	WEMT	107.5 98.7	Emporia	NSAS KSTE	*88.7	Waltham		94.7 102.5	Clarement Manchester	WTSV-FM WKBR-FM	106.1 95.7
	VMAQ-FM	103.5	Kansas City Lawrence	KCJC	98.1	W. Yarmouth Williamstown Winchester	WOCB-FM WCFM WHSR-FM	94.3 *90.1 *91.9	Mt. Washington Nashua	WMTW-FM WOTW-FM	94.9
	WMBI-FM ' WNIB WSBC-FM	*90.1 97.1 93.1	Manhattan Newton	KSDB-FM KJRG-FM	*88.1 92.1	Worcester	WAAB WTAG-FM		NEW	JERSEY	
	WJJD-FM □	104.3	Ottawa Parsons	KTJO-FM KPPS-FM	*88.1 *91.1	МІСІ	HIGAN		Asbury Park Bridgeton	WJLK-FM WSNJ-FM	94.3 107.7
DeKalb E. St. Louis		*91.1	Salina Topeka Wichita	KAFM KTOP-FM KFH-FM	99.9 100.3 100.3	Ann Arbor Bay City	WUOM WBCM-FM	*91.7 96.1	Camden Dover	WKDN-FM WOHA-FM	106.9 105.5
Effingham	WSEI	95.7 103.9	Wienita	KMUW KCBM-FM	*89.1	Benton Hrbr.	WHFB-FM	102.5 99.9	E. Orange Eatontown	WFMU WHTG-FM WNTI	*91.1 105.3 *91.9
Elgin	RMN-FM WEPS	94.3 *88.1	KEN1	TUCKY		Birmingham Coldwater	WHFI WTVB-FM	94.7 98.3	Hackettstown Long Branch Millville	WRLB WMVB-FM	107.1
Elmwood Park Evanston	WEAW	105.9	Ashland Central City	WCMI-FM WNES-FM	9 3 .7	Dearborn Detroit	WKMH-FM WDET-FM ' WBFG-FM		Newark	WJRZ-FM WVNJ-FM	94.7
	VYKC-FM	*89.3 *88.1 107.1	Fulton Glasgow	WFUL-FM WGGC	104.9 95.1		WCHD	98.7 105.9 106.7	New Brunswk,	WBG0 WCTC-FM	
Harrisburg \	WEBQ-FM	99.9	Hazard Henderson	WKIC-FM WSON-FM	96.5 99.5		WABX	99.5	Paterson Princeton	WPAT-FM WPRB	93.1 103.9
Jacksonville	WLDS-FM WAJP	100.5	Hopkinsville	WRLX WKOF	98.7 100.3		WGPM WJBK-FM	107.5	Red Bank South Orange	WFHA-FM WSOU	106.3 *89.5
	WJOL-FM /KAK-FM	96.7 99.9	Lexington	WBKY WLAP-FM	*91.3 94.5		WMUZ	103.5 97.9	Trenton Wildwood	WTOA WCMC-FM	97.5
Kewanee Litchfield	WKSD: WSMI-FM:	*91.9 106.1	Louisville	WFPK WFPL WFMW-FM	*91.9 *89.3 93.9		WJR-FM WOMC-FM	96.3 104.3	Zarephath NEW	WAWZ-FM MEXICO	99.1
Macomb Matteon y	VLBH-FM	91.3 96.9	Madisonville Owensboro	WNGO-FM WOMI-FM	94.7 92.5		WRMK-FM	105.1 98.7	Albuquerque	KANW KHEM	*89.1 96.3
Mt. Carmel	WSAB	94.9	Paducah	WVJS-FM WPAD-FM	96.1 96.9	E, Lansing	WWJ-FM WXYZ-FM WKAR-FM	97.1 101.1 *90.5	(s) Aztec Los Alamos	KNDE-FM KRSN-FM	94.9 98.5
Mt. Vernon \	VVMC-FM WMIX-FM VOPA-FM	94.1		WKYB-FM	93.3	Flint	WSWM	99. I *95. I	Mountain Park Roswell	KMFM KBIM-FM	97.9 97.1
Olney V	VVLN-FM WPRS-FM	92.9 98.3	Alexandria	SIANA KALB-FM	96.9	Grand Rapids	WFUR-FM WJEF-FM	102.9		YORK	
Park Forest Park Ridge	WRHS	*88. i *88. 5	Baten Rouge Monroe	WJBO-FM KMLB-FM	98.1 104.1		WLAV-FM WMAX-FM	96.9 101.3	Albany Auburn	WAMC WMBO-FM	96.1
Quiney W	/MBD-FM /GEM-FM	92.5 105.1	New Orleans	WBEH WDSU-FM	89.3 105.3	W	OOD-FM 105 WVGA-FM	104,1	Babylon	WTFM WBAB-FM	
Reskford V	VTAD-FM VROK-FM	99.5 97.5	l	WRCM	97.1 95.7	Casanvilla Mial	WXTO-FM WKLW-FM	97.9 95.7	Binghamton Brooklyn	WNBF-FM WKOP-FM WNYE	98.1 95.3 *91.5
Springfield V	VHBF-FM VTAX-FM WGGM	98.9	Shreveport	KRMD-FM KBCL-FM	96.5	Greenville, Mich Highland Pk.	WPLB-FM	107.3	Buffalo	WBEN-FM WBFO	106.5
Taylorville Urbana Wheaton	WILL-FM	95.0 *90.9 *88.1	l M	KWKH-FM AINE	94,5	Holland Houghton Lake	WJBL.FM WJGG	94.5 98.5		WEBR WGR-FM	94.5 96.9
Winnetka	WNTH	*88.1	Augusta	WFAU-FM		Interiochen Jackson	WGYA '	94.1		WBUF KWOL-FM	
INDI/	ANA WAFM	07.0	Banger Brunswick	WABI-FM WBOR	97.1 *91.1 97.7	Kalamazoo Lansing	WMCR '	102.1 97.5	Central Square	WIFE-FM WCSQ	*89.3
Bloomington	WFIU*	103.7	Caribou Lewiston	WFST-FM WCOU-FM WRJR	93.9 91.5	Midland	WMRT-FM WQDC-FM	99.7	Cherry Valley Corning Cortland	WCLI-FM WKRT-FM	101.9 106.1 99.9
Celumbus	WCSI-FM	98.3 100.3	Poland Springs Portland	WMTW-FM WLOB-FM	94.9 97.9	Mount Clemens Oak Park	WBRB-FM WLDM WOAK	95.5	DeRuyter Fimira	WOIV	105.1
Crawfordsville V Elkhart W	VBBS-FM VCMR-FM	106.3 95.1		YLAND		Royal Oak Saginaw	WOMC WSAM-FM		Floral Park Garden City	WSHS	*90.3
Evansville	WIKY-FM	100.7	Annapolis	WNAV-FM	99.1	Sturgis	WSTR-FM	103.1	Hempstead	WHLI-FM WVHC	*88.7
Ehii-	W PSR	*91.5 90.7		WXTC WAQE-FM	107.9	Brainerd	IESOTA KLIZ-FM	95.7	Hornell Ithaca	WWHG-FM WHCU-FM	97.3
Franklin / Fort Wayne Gary	WPTH	*89.3 95.1 *88.1	Baltimore	WCAO-FM	*88.1 102.7	Mankato Minneapolis	KYSM-FM KTI8-FM	103.5		WICB WEIV WVBR-FM	*91.7 103.7 101.7
Goshen Greencastie	WGCS	91.1		WCBM-FM WFMM-FM	106.5 93.1		WLOL-FM	97.1 99.5	Jamestown Kenmore	WJTN-FM WYSL-FM	93.3
Hammond Hartford City	WYCA	92.3		WRBS WSID WBAL-FM	95.1 92.3 97.9	St. Cloud	WPBC-FM WAYL KFAM-FM	96.1 104.7	Mt. Kisco New Rochelle	WRNW WVOX-FM	107.1
Huntington Indianapolis	WAJC *	*91.9 104.5		WITH-FM WSID-FM	104.3	St. Paul Worthington	KNOF KWOA-FM	95.3 94.9	New York	WABC-FM WBAI	95.5 99.5
	WAIV	107.9	Bethesda	WJMD 10 WHF8-FM	8.3(4)		ISSIPPI	0 110		WBFM WCBS-FM	101.1
W	FBM-FM WFMS WIAN	94.7 95.5 •90.1	Bradbury Heist Cumberland	nts WPGC WCUM-FM	95.5 102.9	Jackson Laurei	WJDX-FM WNSL-FM	102.9		WEVD-FM WFUV	*90.7
Jasper	WIBC-FM	93.1 104.7	Frederick Hagerstown	WFMD-FM WJEJ-FM	99.9 104.7	Meridian	WMMI	*88.1		WHOM-FM WKCR-FM WNCN	*89.9
Madison V	VORX-FM WMRI-FM	96.7 106.9	Havre de Grace	WARK-FM WASA-FM WBUZ		Clayton	SOURI KEUO-EM	99.1		WNEW-FM WNYC-FM	102.7 93.9
Muncia	WMUN	*90.7 104.1	Oakland Tacoma Park Waldorf	WGT8-FM WSMD	*91.9	Joplin Kanan Cita	WMBH-FM KSYN	96.1 92.5		WMYF	91.5
New Albany	WWHI	*91.5 *88.1	Westminster	WTTR-FM	100.7	Kansas City	KCMO-FM KBEY KTSR	94.9 104.3 *90.1		WOR-FM WOXR-FM WNBC-FM	96.3 97.1
New Castle V	VCTW-FM WYSN WRAY-FM	*91.1 98.1	MASSAC Amherst	CHUSETT: Wamf			WDAF-FM KCMK	102.1 93.3	Niagara Fails	WRFN WRVR WHLD-FM	106.7
Richmond	WGLM WSLM-FM	96.1 98.9	~	WFCR	*88.5		KCUR-FM KXTR	89.3 96.5	Olean Plattsburgh	WHOL-FM WEAV-FM	95.7 99.9
Seymour South Bend	WIOD	93.7	Boston	WBUR WBCN	*90.9	Kennett Pepiar Bluff	KBOA-FM KWOC-FM	98.9 94.5	Patchogue	WALK-FM S WPAC-FM	97.5(s) 106.1
Terre Haute	WTHI-FM WVTS 100 WSKS	99.9		WBZ-FM WCOP-FM	106.7	St. Louis	KCFM KADI WAMV-FM	9 3. 7	Peekskill Poughkeepsie	WLNA-FM WKIP-FM WEOK-FM	100.7
Wabash Warsaw V	WRSW-FM	107.3		WEEI-FM WERS	*88.9		WIL-FM	92.3		VAPC-FM I	03,9(s)
Washington West Lafayette	WFML WBAA-FM	99.1		WHDH-FM WRKO-FM WXHR	94.5 98.5 96.9		KSTL-FM KWIX	98.1	Rochester	WHFM WBBF-FM WCMF	100.1
IOV			Brockton Brookline	WBET-FM WBOS-FM	97.7 92.9	Springfield	KRFD KTTS-FM	106.9 94.7		WIRQ WROC-FM	*90.9
Ames Boone	WOI-FM KFGQ	*99.3	Cambridge	WGBH-FM WHRB-FM	*89.7 95.3	West Plains	KTXR KWPM-FM	101.5	Schenectady South Bristol	WGFM WMIV	99.5 95.1
	KHAK-FM	98. I	Fitchburg	WTBS WFGM-FM	88.1 104.7		RASKA		Springville Syracuse	WSPE	1.88*
Clinton Davenport Des Molnes		96.1 103.7 *88.1	Framingham Groenfield	WKOX-FM WHAI-FM	105.7 98.3	Kearney-Holdre	KRNY-FM	98.9		WDD8-FM WONO	100.9
Ses Munich	KDMI K80	97.3 98.5	Haverhill Lawrence	WHAV-FM WGHJ	92.5 93.7	Lincoln Dmaha	KFMQ KQAL-FM	95.3 94.3	Troy	WSYR-FM WFLY WRPI	94.5 92.3 1 *91.5
	WHO-FM		Lowell Lynn Medford	WLLH-FM WUPI-FM WISK	99.5 105.3 107.9		KFAB-FM WDW-FM KICN	99.9 92.3 96.1	Utlea Wethersfield	WRUN-FM WBIV	105.7
188 WHITE'S	S RADIO	LOG	New Bedford	WBSM-FM	97.3	Scottsbluff	KNEW-FM	94.1		WFAS-FM	

Location	C.L. Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.;	Location	C.L. Mc.
NORTH	CAROLINA	Middletown Mt Vernon	WPFB-FM WMVO-FM	105.9 93.7		WYRE-FM WILY	107.9		KARO 94.5 KOST 100.3
Albemarie Asheboro	WABZ-FM 100.9 WGWR-FM 92.3	Mt. Vernon New Concord Newark	WMCO-FM	*91.9		WJAS-FM WKJF	99.7		KQUE 102.9 KRBE 104.1
Asheville Burlington	WLOS-FM 104.3 WBBB-FM 101.1	Oxford	WMUB	*88.5 97.7		WPIT-FM WWSW-FM	94.5		KXYZ-FM 96.5 KTRH-FM 101.1
Burlington-Gra	WFNS-FM 93.9	Piqua Port Clinton	WPTW-FM WRWR-FM	95.7 94.5	Pottsville Red Lion	WPPA-FM WGCB-FM	96.1	Hilleen	KUHF *91.3 KLEN-FM 93.3
Chapel Hill	WBAG-FM 92.9 WUNC *91.5	Dartemanth	WPAY-FM WSOM-FM	104.1	Scranton	WGBI-FM WUSV	101.3	Lubbock	KSCL-FM 93.7 KBFM 96.3
Charlotte	WSOC-FM 103.5 WYFM 104.7	Sandusky Springfield	WLEC-FM WBLY-FM	102.7	Sharon State College	WPIC-FM WDFM	102.9	Marshall	KTXT-FM *91.9 KMHT-FM 97.3
Clingman's Pk. Contord, N.C.	WMIT 106.9 WEGO-FM 97.9	1	WEEC-FM WSTV-FM	100.7	Sunbury	WKOK-FM WTTC-FM	94.1 92.7	Midland Mt, Pleasant	KNFM 92.3 KIMP-FM 96.1
Durham Elkin	WONC-FM 105.1 WIFM-FM 100.9	Toledo	WSPD-FM WMHE		Tyrone		101.1 92.3	Odessa	KQIP 96.7 KWMO 99.1
Fayetteville Forest City	WFNC-FM 98.1		WTDS WTOL-FM	*91.3	Washington Waynesbero	WJPA-FM	104.3	Pampa Pasadena	KBMF-FM 100.3 KLVL-FM 92.5
Gastonia	WAGY-FM 105.3 WGNC-FM 101.9	Westerville	WTRT	99.9	Wilkes-Barre	WBRE-FM WYZZ	98.5	Plainview Port Arthur	KHBL *88.1 KFMP 93.3
Goldsboro Greensboro	WEQR 96.9 WMDE 98.7	Wooster Worthington-Co	WWST-FM		Williamsport	WLYC-FM WRAK-FM	105.1	San Antonio	KISS 99.5 KEEZ 97.3
Greenville	WQMG-FM 97.1 WWW8 *91.3	1	WRFD-FM	97.9 103.9	York	WNOW-FM	105.7		KAKI-FM 98.1 KITY 92.9
Henderson	WHNC-FM 92.5 WHKP-FM 102.5	Yellow Springs	WYSO WKBN-FM	*91.5 96.9	RHODI	E ISLAND		Sinten	KTOD-FM 101.3
Hendersonville Hickory	WHKP-FM 102.5 WHKY-FM 102.9		W9BW-FM WRED	93.3	Cranston Providence	WLOV WPJB-FM	99.9	Texarkana Tyler	KSLT 93.1
High Point	WHPE-FM 95.5 WHPS *89.3	Zanasvilla	WHIZ-FM			WICE-FM WPFM	95.5	Waco	KEFC 95.5(s) WACO 99.9
	WMFR-FM 99.5 WNOS-FM 100.3	OKLA	AMOHA			WPRO-FM WXCN	92.3	U U	TAH
Laurinburg Leaksville	WEWO-FM 96.5 WLOE-FM 94.5		KSEO-FM WAAD-FM	°90.9	Woonsocket	WWON-FM		Ephraim	KEPH *88.9 KUSU-FM *88.1
Lexington Lumberton	WBUY-FM 94.3 WTSB-FM 95.7	Oklahoma City	KOKH KIOO	*88.9	SOUTH	CAROLIN	A	Logan Provo	KBYU-FM *88.9
Raleigh	WKIX-FM 96.1 WPTF-FM 94,7		KEFM KYFM	94.7 98.9	Anderson Charleston	WCAC WCSC-FM	96.9	Salt Lake City	KLUB-FM 97.1
Reidsville	WRAL-FM 101.5 WREV-FM 102.1	Shawnee Stillwater	KRGC	*89.9	Clemson	WIMA-FM WSBF-FM	95.1 *88.1		KSL-FM 100.3
Rocky Mount	WEED-FM 92.1 WFMA 100.7	Tuisa	KSP1-FM	93.9	Columbia	WCOS-FM WNOK-FM	97.9 104.7		GINIA
Roxboro Salisbury	WRXO-FM 96.7 WSTP-FM 106.5		KIHI	95.5 97.5	Diflon	WUSC-FM WDSC-FM	*89.9	Arlington	WAVA-FM 105.1 WCCV-FM 97.5
Sanford Shelby	WWGP-FM 105.5 WOHS-FM 96,1	1	KOGM-FM	92,9	Greenville	WESC-FM WFBC-FM	92.5 93.7	Charlottesville	WINA-FM 95.3 WTJU 91.3
Statesville Tarboro	WFMX 105.7 WCPS-FM 104.3		GON		Laurens-Clinton	WMVU-FM WLBG-FM	94.5	Crewe Farmville	WSVS-FM 104.7 WFLO-FM 95.7 WFVA-FM 101.5
Thomasville Wilmington	WTNC-FM 98,3 WPRV 93.9	Eugene	KRVM KEED-FM	93.1	Rock Hill Seneca	WRHI-FM WSNW-FM	98.3 98.1	Fredericksburg Gretna	WMNA-FM 103.3
Wilson Winston-Salem	WVOT-FM 106.1 WAIR-FM 93.1		KFMY KUGN-FM KWAX	97.9 99.1	Spartanburg Sumter	WSPA-FM WFIG-FM	98.9 101.3	Hampton Farrisonburg	WVEC-FM 101.3 WEMC *91.7
	WYFS 107.5 WFDD-FM *88.1	Grants Pass	KGPO	96.9	TENI	NESSEE		Lynchburg	WSVA-FM 100.7 WWOD-FM 100.1
	W8J8-FM 104.1	Medford Oretech	KBOY-FM KTEC	95.3	Bristel	WOPI-FM	96.9	Manassas Marion	WPRW-FM 106.7 WMEV-FM 93.9
0	HIO	Portland	KOAP-FM KGMG	92.3 95.5	Chattanooga	WOOD-FM WLON	96.5 106.5	Martinsville Newport News	WMVA-FM 96.3 WGH-FM 97.3
Akron	WAKR-FM 97.5 WAPS *89.1		KGIN-FM KPDQ-FM KPFM	101.1 105.3 97.1	Cleveland Collegedate	WCLE-FM WSMC-FM	100.7 *88.1	Norfolk	WMTI *91.5 WRVC 102.5 WTAR-FM 95.7
Alliance	WCUE-FM 96.5 WFAH-FM 101.7		KPOJ-FM KQFM	98.7 100.3	Franklin Gallatin	WFLT-FM WFMG	104.5	Portsmouth	WYFI-FM 99.7
Ashland Ashtabula	WNCO-FM 101.3 WREO-FM 103.7			*89.3	Greeneville Jackson	WGRV-FM WTJS-FM WJCW-FM	94.9	Richmond	WAVY-FM 96.9 WCOD 98.1 WRFK 91.1
Athens Barberton	WOUB-FM *91.5 WDBN 94.9	PENNS	YLVANIA		Johnson City Kingsport	WKPT-FM	100.7 98.5		WRVA-FM 94.5 WRNL-FM 102.1
Bellaire Berea	WOMP-FM 100.5 WBWC *88.3	Allentown	WFMZ WAEB-FM	100.7	Knoxville	WBIR-FM WKCS	93.3	Reanoke	WDBJ-FM 94.9 WLRJ 92.3
Bowling Green Canton	WBGU *88.1 WHBC-FM 94.1	Alteona	WF8G-FM	100.1 98.1	Memphis	W M C. F M	°91.9 99.7		WROV-FM 103.7 WSLS-FM 99.1
	WCNO 106.9 WTOF-FM 98.1	Bethlehem	WGPA-FM	95.1		WMPS-FM WDIA-FM	97.1 102.7	South Boston South Norfolk	WHLF-FM 97.5 WF08 *90.5
Celina Chillicothe	WMER-FM 94.3 WBEX-FM 93.3	Boyertown	WHLM-FM WBYC-FM	106.5	Nashville	WFMB WSIX-FM WSEV-FM	97.5	Staunton	WSGM-FM 93.5 WCWM 89.1
Cincinnati	WCPO-FM 105.1 WAEF-FM 104.3	Butler	WLOA-FM WBUT-FM	96.9 97.7	Sevierville		102.1	W:nehester Weedbridge	WRFL 92.5 WXRA 105.9
	WGUC *90.9 WAKW-FM 93.3	Chambersburg 1	WHYL-FM WCHA-FM 9	5,1(s)	Abilene	KACC-FM	*01.1		INGTON
	WKRC-FM 101.9 WSAI-FM 102.7	Easton	WCED-FM WEST-FM	107.9	Alvin	KFMN KAJC-FM	99.3	Beilingham	KGM1-FM 92.9
Cleveland	KYW-FM 105.7 WXEN-FM 106.6	Erle	WEEX-FM WWYN-FM	99.9	Amarillo	KGNC-FM	93. I 98. 3	Cheney Edmunds	KEWC-FM *89.9 KGFM 105.3
			WGET-FM		Austin		06.5	Lynden Opportunity	KLYN-FM 106.5
	WBOE *90.3 WCRF 103.3		WIFI	92.5	l	KAZZ KTRC-EM	93.3		KZUN-FM 96.1
	WCRF 103.3 WDGO 95.5	Harrisburg	WHP.FM WMSP	97.3 94.9	Resument	KTBC-FM KUT-FM	95.5 93.7 *90.7	Seattle	KING-FM 98,1
	WCRF 103.3 WDGO 95.5 WDOK-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5	Harrisburg Havertown Hazleton	WHP-FM WMSP WHHS WAZL-FM	97.3 94.9 *89.3 97.9	l	KTBC-FM KUT-FM KHCB-FM KAYD-FM	*90.7 105.7 97.5	Seattle	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7
	WCRF 103.3 WDGO 95.5 WDOK-FM 102.1 WERE-FM 98.5 WGAR-FM 90.7	Harrisburg Havertown Hazleton Jenkintown Johnstown	WHP.FM WMSP WHHS WAZL.FM WIBF WARD.FM	97.3 94.9 *89.3 97.9 103.9 92.1	Big Spring Brownwood	KTBC-FM KUT-FM KHCB-FM KAYD-FM KFNE-FM KHPC	*90.7 105.7 97.5 95.3 88.1	Seattle	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7
Cleveland Hts.	WCRF 103.3 WDGO 95.5 WDOK-FM 102.1 WERE-FM 98.5 WHK-FM 100.7 WJW-FM 104.1 WNOB 107.9 WCUY-FM 92.5	Harrisburg Havertown Hazleton Jenkintown Johnstewn	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WGAL-FM	97.3 94.9 *89.3 97.9 103.9 92.1 95.5 101.3	Big Spring Brownwood Cleburne Cerpus Christi	KTBC-FM KUT-FM KHCB-FM KAYD-FM KFNE-FM KHPC KCLE-FM	*90.7 105.7 97.5 95.3 88.1 94.9	Seattle	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSN 96.5 KMCS 98.9 KOL-FM 94.1
Cleveland Hts. Columbus	WCRF 103.3 WDGO 95.5 WDGK-FM 102.1 WERE-FM 98.5 WGAR-FM 90.5 WHK-FM 100.7 WJW-FM 104.1 WNOB 107.9 WCUY-FM 92.5 WCBE *90.5 WBNS-FM 97.1	Harrisburg Havertown Hazleton Jenkintown Johnstown	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WJAC-FM WGAL-FM WDAC WLAN-FM	97.3 94.9 *89.3 97.9 103.9 92.1 95.5 101.3 94.5 96.9	Big Spring Brownwood Claburne	KTBC-FM KUT-FM KHCB-FM KAYD-FM KHPC KCLE-FM KMFM KIXL-FM KNER	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 104.5 *88.1	Seattle Spokane	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSN 96.5 KMCS 98.9 KOL-FM 94.1 KUDW 94.9
	WCRF 103.3 WDG0 95.5 WDOK-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 100.7 WJW-FM 104.1 WCUY-FM 92.3 WCBE 90.5 WBNS-FM 97.1 WCOL-FM 92.3 WOSU-FM 92.3	Harrisburg Havertown Hazieton Jenkintown Johnstown Laneastor Lebanon Meadville	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WJAC-FM WDAC WLAN-FM WLBR-FM WMGW-FM	97.3 94.9 *89.3 97.9 103.9 92.1 95.5 101.3 94.5 96.9 100.1	Big Spring Brownwood Cleburne Cerpus Christi	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KFNE-FM KHPC KCLE-FM KMEN KIXL-FM KNER KRLD-FM KLIF-FM	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 104.5 *88.1 92.5 98.7	Seattle Spokane	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSN 96.5 KMCS 98.8 KOL-FM 94.1 KUDW 94.9 KREM-FM 92.9 KXLY-FM 99.9 KHQ-FM 98.1
Columbus	WCRF 103.3 WD0 95.5 WD0 K-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WC0L-FM 92.3 W08U-FM 97.1 WC0L-FM 92.3 W08U-FM 98.7 WVK0 94.7	Harrisburg Havertown Hazleton Jonkintown Johnstown Lancaster Lebanon Meadville Montrose Oil City	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WJAC-FM WDAC WLAM-FM WDAC WLAM-FM WLBR-FM WMGW-FM WPJR WJIWR	97.3 94.9 *89.3 97.9 103.9 92.1 95.5 101.3 94.5 96.9 100.3 96.5 98.5	Big Spring Brownwood Cleburne Cerpus Christi	KTBC-FM KUT-FM KHCB-FM KAYD-FM KHPC KCLE-FM KMFM KIXL-FM KNER	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 104.5 *88.1 92.5 98.7 97.9	Seattle	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRSW 99.9 KLSN 96.5 KMCS 98.9 KOL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KCPS 90.9 KLY-FM 106.3
Columbus	WCRF 103.3 WDG0 95.5 WDOK-FM 102.1 WERE-FM 96.5 WGAR-FM 99.5 WHK-FM 100.7 WJW-FM 104.1 WOUY-FM 92.3 WCBE 90.5 WCBE 90.5 WCBL-FM 99.1 WCOL-FM 96.3 WTYN-FM 96.3 WTYN-FM 96.3 WTYN-FM 99.1	Harrisburg Havertown Hazleton Jenkintown Johnstown Lancaster Lebanon Mendville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WJAC-FM WDAC WLAM-FM WDAC WLAM-FM WLBR-FM WMGW-FM WPJR WJIWR	97.3 94.9 *89.3 97.9 103.9 92.5 101.3 94.5 96.9 100.1 100.3 96.5 98.5 92.1	Big Spring Brownwood Cleburne Corpus Christi Dalias	KTBC-FM KHCB-FM KHCB-FM KFNE-FM KHPC KCLE-FM KMFM KNER KNER KNER KRLI-FM WFAA-FM WFAA-FM KVTT KQRO	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 104.5 *88.1 92.5 98.7 97.9 101.1 102.9	Seattle Spokane	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRSW 99.9 KLKSN 96.5 KMCS 98.9 KOL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KCPS 90.9 KLAY-FM 106.3 KTNT-FM 97.3 KTOT 981.7
Columbus	WCRF 103.3 WD00 95.5 WD0K-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 100.7 WJW-FM 104.1 WNOB 107.9 WCUY-FM 90.5 WBNS-FM 97.1 WCOL-FM 92.3 WOSU-FM 98.3 WTVN-FM 98.3 WTVN-FM 98.3 WOSU-FM 99.1 WONE 104.7 WSLN 99.1	Harrisburg Havertown Hazleton Jonkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Palmyra Philadelphia	WHP-FM WMSP WHHS WAZL-FM WIBF WARD-FM WJAC-FM WDAC-FM WDAC-FM WDBC-FM WDBC-FM WMGW-FM WDW-FM WJWR WJWR WJWR WZAU-FM WPB3-FM WDAC-FM WJWR WJWR	97.3 94.9 97.9 97.9 103.9 92.1 95.5 101.3 94.5 96.9 100.1 100.3 98.5 92.1 98.1 105.3	Big Spring Brownwood Cleburne Cerpus Christi	KTBC-FM KHCB-FM KAYD-FM KAYD-FM KFNE-FM KFNE-FM KKLE-FM KNER KRLD-FM KLIL-FM KLIL-FM KRLD-FM KLIL-FM KRLD-FM KRLD-FM KRR-FM KRLD-FM KSPL-FM KSPL-FM	*90.7 97.7 97.3 88.1 94.9 95.5 104.5 92.5 98.7 97.9 101.7 102.9 106.3 95.3	Seattle Spokane	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSN 96.5 KMCS 98.9 KOL-FM 94.1 KUDW 94.9 KREM-FM 92.9 KXLY-FM 99.9 KLY-FM 99.9 KLY-FM 98.1 KCPS 90.9 KLAY-FM 106.3 KTNT-FM 97.3
Dayton Delaware East Liverpool Eaton Elyria Findlay	WCRF 103.3 WD0 95.3 WD0 6-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WH K-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WJW-FM 99.5 WGUY-FM 92.3 WBNS-FM 99.1 WCOL-FM 98.3 WJW-FM 10-FM 98.3 WJW-FM 10-FM 98.1 WGUY-FM 98.3 WJW-FM 98.1 WGUY-FM 98.3 WJW-FM 98.3	Harrisburg Havertown Hazleton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHS WAZL-FM WARD-FM WJAC-FM WJAC-FM WLAN-FM WLBR-FM WMGW-FM WMGW-FM WPEL-FM WJWR WPEL-FM WPEL-FM WJWR WPEL-FM WFM WFM WFM WFM WFM WFM WFM WFM WFM W	97.3 94.9 97.9 103.9 92.1 95.5 101.3 94.5 96.9 100.1 100.3 105.3 105.3 105.3	Big Spring Brownweed Cleburne Corpus Christi Dalias	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KFNE-FM KFNE-FM KIXL-FM KIXL-FM KIXL-FM WFAA-FM WFAA-FM KQRO KDNT-FM KODD-FM KVDD-FM KVDD-FM KVDD-FM KVDD-FM KVDM-FM	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 *88.1 92.5 98.7 97.9 101.1 *91.7 106.3 95.5 95.3 *88.5 99.9	Spokane Tacema	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 K1SW 99.9 KLSN 96.5 KMCS 98.9 KOL-FM 94.1 KUDW 94.9 KREM-FM 92.9 KXLY-FM 99.9 KHQ-FM 98.1 KCYS 90.9 KLAY-FM 106.3 KTNT-FM 97.3 KTNT-FM 97.3 KTNT-FM 97.7
Dayton Delaware East Liverpool Eaton Elyria	WCRF 103.3 WD00 95.5 WD00 4-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 100.7 WJW-FM 104.1 WNOB 107.9 WCUY-FM 90.5 WBNS-FM 97.1 WCOL-FM 92.3 WSUS-FM 98.3 WTVN-FM 98.3 WTVN-FM 98.3 WCTM 99.1 WONE 104.7 WSLN 99.1 WOHL-FM 100.5	Harrisburg Havertown Hazleton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHS WAL-FM WIBF WARD-FM WJAC-FM WJAC-FM WDAC-FM WDAC-FM WDAC-FM WDAS-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WHY WHY WHY WHY WHY WHY	97.3 94.9 *89.3 97.9 103.9 92.1 95.5 101.3 94.5 96.5 98.5 100.3 105.3 105.3 105.3 105.3 96.5 96.5	Big Spring Brownwood Cleburne Corpus Christl Dallas	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KFNE-FM KFNE-FM KIL-FM KNER KRLD-FM WFAA-FM WFAA-FM KNUT KQRO KDNT-FM KDDD-FM KSPL-FM KSPL-FM KSPL-FM KSPL-FM KSPL-FM KYMT	*90.7 105.7 97.5 88.1 94.9 95.5 104.5 *88.1 92.5 98.7 97.9 101.1 *91.7 106.3 95.3 *88.5 99.9 94.7	Spokane Tacema Yakima WEST Beckley	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRO-FM 100.7 KISW 99.9 KLKSN 96.5 KMCS 98.9 KNCL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.3 KTPS 90.9 KXLY-FM 106.3 KTNT-FM 97.3 KTWR 103.9 KNDX-FM 106.3
Dayton Delaware East Liverpool Edston Elyria Findlay Fostoria	WCRF 103.3 WD0 95.5 WD0 95.5 WD0 K-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 104.1 WNOB 107.9 WCUY-FM 92.5 WBNS-FM 97.1 WCOL-FM 92.3 W08U-FM 98.7 WYVN-FM 96.7 WYVN-FM 96.7 WYVN-FM 96.7 WONE 104.7 WSU-FM 104.3 WONE 104.7 WSU-FM 104.3 WFIN-FM 104.3 WFIN-FM 104.3 WFIN-FM 107.3 WFOB 96.7 WFRO-FM 99.3 WJEH-FM 101.5	Harrisburg Havertown Hazieton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHS WAZL-FM WJBF WARD-FM WJAC-FM WJAC-FM WLAN-FM WDAC WLAN-FM WPEL-FM WFL-FM WPS-FM WPS-FM WPS-FM WFL-FM WFL-FM WHAT-FM	97.3 94.9 *89.3 97.9 103.9 92.1 94.5 96.9 100.3 96.5 98.1 105.3 105.3 105.3 105.3 105.3 105.3 105.3 105.3	Big Spring Brownweed Cleburne Corpus Christi Dallas Denten DIBoll Dumas Et Pase	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KFNE-FM KFNE-FM KIXL-FM KIXL-FM KIXL-FM WFAA-FM WFAA-FM KSPL-FM KSPL-FM KORO KDNT-FM KODD-FM KODD-FM KODD-FM KODD-FM KSPL-FM KYBA-FM KYBA-FM KYBA-FM KYBA-FM KYBA-FM KYBA-FM KYBA-FM	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 104.5 92.5 98.7 101.7 106.3 95.5 95.3 *88.5 99.7 96.3 99.5 99.7	Spokane Tacema Yakima WEST Beckley Charleston	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRO-FM 100.7 KISW 99.9 KLKSN 96.5 KMCS 98.9 KNCL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.3 KTNT-FM 97.3 KTWR 103.9 KNTOY 91.7
Dayton Delaware East Liverpool Eaton Elyria Findlay Fostoria Fremont Gallipoils	WCRF 103.3 WD00 95.5 WD00 75.7 WD00 95.5 WD00 F-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WH K-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WCUY-FM 92.3 WBNS-FM 92.3 WCUY-FM 92.3 WCUY-FM 98.3 WCOL-FM 98.3 WTVN-FM 96.3 WTVN-FM 96.3 WTVN-FM 98.1 WCTM 99.1 WCTM 99.1 WCTM 99.1 WCTM 92.9 WFIN-FM 100.5 WFO-FM 99.3 WFIN-FM 100.5 WFO-FM 99.3 WFIN-FM 100.5	Harrisburg Havertown Hazieton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP.FM WMSP WHHSS WAZL-FM WARD-FM WJAC-FM WJAC-FM WJAC-FM WJAC-FM WJAR-FM WJAR-FM WALM-FM WPEL-FM WPEL-FM WPEL-FM WFLN WFLN WHYT WHST-FM WHYT WHST-FM WHYT WHST-FM WHYT WHST-FM WHYT WHST-FM WHYT WHYT WHYT WHYT WHYT WHYT WEN-FM	97.3 94.9 97.9 103.9 92.1 95.5 101.3 94.5 96.5 98.5 92.1 105.3 105.3 105.3 105.3 105.3 102.7 96.5 94.5 96.5 98.5 98.5 98.5 98.5	Big Spring Brownwood Cleburne Corpus Christl Dallas Denten DiBoll Dumas Et Paso Ft. Worth Gainesville	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KFNE-FM KFNE-FM KIXL-FM KIXL-FM KIXL-FM WFAA-FM WFAA-FM WFAA-FM WFAA-FM KOPD-FM KOPD-FM KOPF-FM KOPF-FM KOPF-FM KIMSP-FM	*90.7 105.7 95.3 88.1 94.9 95.5 104.5 92.5 98.7 97.9 101.1 102.9 95.3 *88.5 95.3 94.7 96.3 99.9 99.5 97.1	Spokane Tacema Yakima WEST Beekley Charleston Huntington	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRO-FM 100.7 KISW 99.9 KLKSN 96.5 KMCS 98.9 KNCL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.3 KTHY-FM 90.3 KTNT-FM 97.3 KTOY 91.7 KTWR 103.9 VIRGINIA WBKW 99.5 WKAZ-FM 98.5 WKEE-FM 100.5 WMUL 288.1
Dayton Delaware East Liverpool Eaton Elyria Findlay Festoria Frement Gallipolis Granville Greenville Hamilton	WCRF 103.3 WD0 95.5 WD0 Y-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WOEB *90.5 WBNS-FM 97.1 WCOL-FM 92.3 W08U-FM *98.7 WYVN-FM 96.7 WYVN-FM 96.7 WYVN-FM 96.7 WONE 104.7 WSU-FM 104.3 WONE 104.7 WSU-FM 104.3 WFIN-FM 104.3 WFN-FM 106.5 WFOB 96.7 WHOH 105.5 WD WB FM 91.1	Harrisburg Havertown Hazieton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHSS WAZL-FM WARD-FM WJAC-FM WHAT-FM WHAT-FM WJAC-FM WJAC	97.3 94.9 97.9 103.9 92.1 95.5 101.3 94.5 96.9 100.3 98.5 98.5 98.1 105.3 106.3 106.	Big Spring Brownwood Cleburne Corpus Christl Dallas Denten DiBoll Dumas Et Paso Ft. Worth Gainesville Harlingen Highland Pk.	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KAYD-FM KAYD-FM KHPC KCLE-FM KIXL-FM KIXL-FM KIXL-FM KNER KRLD-FM KNER KRLD-FM KYFT KQRO KDNT-FM KYFT KQRO KDNT-FM KYFT KURC-FM KYFT KIMS KYFT KIMS KYFT KIMS KAFFM KYFT KIMS KYFT KIMS KYFT KIMS KYFT KIMS KYFT KIMS KYFT KIMS KYFT KIL-FM KIL-FM KYFT KIL-FM KYFT KIL-FM KYFT KIL-FM KAFFM KYFT KIL-FM KIL-FM KIL-FM KAFFM KIL-FM KIL-FM	*90.7 105.7 95.5 94.9 94.9 95.5 *88.1 92.5 97.9 101.1 102.9 106.3 95.3 *88.5 99.9 94.7 99.5 97.9 94.7 99.5 94.7 94.5 94.5	Spokane Tacema Yakima WEST Beekley Charleston Huntington Martington Martington Margantown	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRO-FM 100.7 KIRO-FM 94.9 KLKSN 96.5 KMCS 98.9 KNCL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.3 KTNT-FM 97.3 KTOY 91.7 KTWR 103.9 VRAZ-FM 106.3 VIRGINIA WBKW 99.5 WKEE-FM 100.5 WKEE-FM 100.5 WMUL 98.1 WEPM-FM 94.3 WAJR-FM 94.3
Dayton Delaware East Liverpool Eaton Elyria Findlay Festoria Frement Gallipolis Granville Greenville Hamilton	WCRF 103.3 WD0 95.5 WD0 95.5 WD0 K-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WHK-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WJW-FM 99.5 WBNS-FM 97.1 WCOL-FM 92.3 W08U-FM 98.7 WYVN-FM 96.7 WYVN-FM 96.7 WYVN-FM 96.7 WONE 104.7 WSU-FM 104.3 WCTM 92.9 WCOL-FM 104.3 WFIN-FM 104.3 WFIN-FM 106.5 WFOB 96.7 WHOH 105.5	Harrisburg Havertown Hazieton Jenkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP-FM WMSP WHHSS WAZL-FM WARD-FM WJAC-FM WJAC-FM WJAC-FM WJAC-FM WJAC-FM WDAC-FM WDAC-FM WJAC-FM WHAT-FM WHAT-FM WJI-FM WJAC-FM	97.3 94.9 94.9 97.9 92.1 95.5 96.9 100.1 96.5 96.9 100.3 98.5 98.5 98.5 98.5 98.5 98.5 98.5 98.5	Big Spring Brownwood Cleburne Corpus Christl Dallas Denten DiBoll Dumas Et Paso Ft. Worth Gainesville	KTBC-FM KHUT-FM KHUT-FM KHYD-FM KHYD-FM KHYD-FM KHYD-FM KIXL-FM KIXL-FM WFAA-FM WFAA-FM WFAA-FM KVTT KUT-FM KVDD-FM KVDD-FM KVDD-FM KVDD-FM KVDD-FM KVBP-FM KVBP-FM KVBP-FM KVBP-FM KVIII-FM KJIM-FM KJIM-FM KJIM-FM KJIM-FM KJIM-FM KJIM-FM KHJIL-FM	*90.7 105.7 97.5 95.3 88.1 94.9 95.5 *88.7 92.9 101.1 *91.7 106.3 95.5 95.3 *88.5 99.5 94.7 99.5 102.1 102.3 102.3	Spokane Tacema Yakima WEST Beekley Charleston Huntington Martinsburg	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KIRO-FM 100.7 KIRO-FM 94.9 KLKSN 96.5 KMCS 98.9 KNCL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.3 KTNT-FM 97.3 KTWR 103.9 KNTY-FM 106.3 VIRGINIA WBKW 99.5 WKAZ-FM 96.3 WKAZ-FM 97.5 WKEE-FM 100.5 WWWL 98.1 WEPM-FM 94.3 WOAY-FM 94.1
Dayton Delaware East Liverpool Eaton Elyria Findlay Fostoria Fremont Gallipolis Granvillo Greenvillo Hamilton Hamilton Kent Laneaster Lima Marietta	WCRF 103.3 WDG0 95.5 WDOK-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WGAR-FM 99.5 WHK-FM 104.1 WOB 107.9 WCUY-FM 92.5 WBNS-FM 97.1 WCOL-FM 92.3 W08U-FM 98.7 WYVN-FM 96.7 WYVN-FM 96.7 WYVN-FM 96.7 WYVN-FM 96.7 WOLL-FM 92.9 WORL 104.7 WSLN 99.1 WOHL-FM 104.3 WFIN-FM 104.3 WFIN-FM 106.5 WFOB 96.7 WHOH 105.5 WHOH 96.8 WHOH 96.8 WHOH 96.8 WHOH 96.8	Harrisburg Havertown Hazleton Jonkintown Johnstown Lancaster Lebanen Mendville Montrose Oil City Palmyra Philadelphia	WHP-FM WMSP WHHSS WAZL-FM WARD-FM WJAC-FM WJAC-FM WDAC-FM WLAN-FM WDAC-FM WDAC-FM WDAC-FM WDAC-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WPEL-FM WFEL-FM WFEL	97.3 94.9 97.9 92.1 92.1 96.9 100.3 96.5 96.5 92.1 105.3 105.3 96.5 92.5 98.1 98.3 96.5 98.9 98.9 98.9 98.9 98.9 98.9 98.9 98	Big Spring Brownwood Cleburne Corpus Christi Dallas Denten DiBoll Dumas El Paso Ft. Worth Galnesville Harlingen Highland Pk. Hillsbore	KTBC-FM KHCB-FM KHYD-FM KHYD-FM KHYD-FM KHYD-FM KHYD-FM KHYD-FM KKHER KRLD-FM KLI-FM WFAA-FM WFAA-FM WFAA-FM WFAA-FM KVTT KUT-FM KOP-FM KOP-FM KUD-FM KHMS WBAP-FM KHFIZ-FM KHELT KHMS KHELT KHGH KHGH-FM KHUL-FM	*90.7* 105.7* 105.7* 105.7* 105.7* 105.7* 105.7* 106.5* 106.5* 106.5* 106.5* 106.3* 10	Spokane Tacema Yakima WEST Beekley Charleston Huntington Martinsburg Morgantown Oak Hill	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSW 99.9 KLSW 98.8 KOL-FM 94.1 KUDW 94.9 KXLY-FM 99.9 KXLY-FM 99.9 KXLY-FM 99.8 KHQFM 98.8 KHQFM 98.9 KLAY-FM 106.3 VIRGINIA WBKW 99.5 WKNZ-FM 99.5 WKNZ-FM 99.5 WKNZ-FM 99.5 WKNZ-FM 99.5 WKNZ-FM 99.3 WKNZ-FM 99.3
Dayton Delaware East Liverpool Eaton Elyria Findlay Festoria Frement Gallipolis Granville Hamilton Hamilton Lancaster Lima	WCRF 103.3 WD0 95.5 WD0 95.5 WD0 8-FM 102.1 WERE-FM 98.5 WGAR-FM 99.5 WGAR-FM 99.5 WH K-FM 104.1 WJW-FM 104.1 WJW-FM 104.1 WJW-FM 99.5 WG0L-FM 92.3 WG0L-FM 98.3 WG0L-FM 98.3 WG0L-FM 98.3 WTVN-FM 96.3 WYK0 94.7 WHIO-FM 99.1 WGNE 104.7 WSLN 99.1 WGNE 104.7 WFIN-FM 104.3 WFIN-FM 105.5 WGM 99.7 WFO-FM 99.3 WFIN-FM 105.5 WGM 96.7 WFRO-FM 99.3 WJEH-FM 101.5 WDUB-FM 91.3 WJEH-FM 101.5 WMW 96.7 WJEH-FM 101.5 WJWHOH-103.5 WJWH 96.7	Harrisburg Havertown Hazleton Jonkintown Johnstewn Lancaster Lebanen Meadville Montrose Oil City Paimyra Philadelphia	WHP.FM WMSP WHHSS WAZL-FM WARD-FM WJAC-FM WJAC-FM WJAC-FM WJAC-FM WDAC-FM WDAC-FM WDAC-FM WDAC-FM WHSP WJSP WJSP WJSP WJSP WJSP WJSP WJSP WJ	97.3 94.9 97.9 92.1 92.1 96.5 101.3 96.5 96.5 96.5 98.5 102.1 98.1 105.3 105.3 105.3 105.3 105.3 105.3 105.3 105.3 105.3 105.1 105.9	Big Spring Brownwood Cleburne Corpus Christi Dallas Denten DiBoil Dumas El Paso Ft. Worth Gainesville Harlingen Highland Pk. Hillsbere Houston	KTBC-FM KHCB-FM KHCB-FM KAYD-FM KAYD-FM KAYD-FM KHPC KCLE-FM KIXL-FM KNER KRLD-FM KNER KRLD-FM KNER KNIF-FM KNOT-FM KONT-FM KO	*90.7* 197.5 95.3 95.3 94.9 94.9 104.5 88.1 104.5 98.7 99.3 101.1 102.9 105.7 99.5 99.5 102.1 102.3 102.9 105.7	Spokane Tacema Yakima WEST Beekley Charleston Huntington Martinsburg Morgantown Oak Hill	KING-FM 98.1 KETO-FM 101.5 KGMJ 95.7 KIRO-FM 100.7 KISW 99.9 KLSW 99.9 KLSW 99.9 KMCS 98.8 KOL-FM 94.9 KXLY-FM 99.9 KXLY-FM 99.8 KLY-FM 99.8 KLY-FM 106.3 KNTT-FM 106.3 VIRGINIA WBKW 99.5 WKNAZ-FM 98.5 WWAZ-FM 98.5 WWUL *88.1 WEPM-FM 99.3 WAJR-FM 99.3 WAJR-FM 99.3

Location C.L. WISCONSIN

Appleton
Chilton
Colfax
Delafield
Eau Claire
Fort Atkinson
Green Bay
Greenfield Twp.
Highland WLFM '91.1 WHKW '89.3 WHWC '88.3 WHAD '90.7 WIAL 94.1 WFAW 107.3 WBAY-FM 101.1 WWCF 94.9 WHHI 91.3

Mc. | Location Highland Twp.
Janesville
La Crosse
Madison

C.L. Mc. Location

WHAA *89.9

WHAA *90.3

WHAFM *80.7

WIBA-FM *80.7

WIBA-FM 101.5

WHFM 104.1(3)

WRYB-FM 102.5

WLIN 100,7 Rice Lake

WHMIL-FM 95.7

Stevens Point Merrill Milwaukee

C.L. Mc. | Location

WJMC-FM WCOW-FM WSPT-FM

C.L.

Mc. | Location WISN-FM 97.3 WRIT-FM 102.9 WMKE 102.1 WQFM 98.3 Watertown Waukesha Wausau Wauwatosa WTMJ-FM 94.1 WEKZ-FM 93.7 WRJN-FM 100.7 West Bend Wisc, Rapids 96.3 97.1

97.9 Cheyenne

C.L. Mc. WTTN-FM 104.7 WAUX-FM 106.1 WTOS 103.7 WBKV-FM 92.5 WFHR-FM 103.3

KVOW-FM 106.3

WYOMING

U. S. FM Stations by Call Letters

Abbreviation: (s)-broadcasts stereo

Location

Ird, Cailf,
Los Angelea, Cailf,
Angelea, Cailf,
Angelea, Cailf,
Angelea, Cailf,
Angelea, Cailf,
Angelea, Cailf, C.L. KAAR Oxnard, Calif,
KABC-FM Los Angeles, Calif,
KAOL St. Louis, Mo.
KAFE Oxland, Calif,
KAFI Auburn, Calif,
KAFM Salina, Kans,
KAIM-FM Honolulu, Hawail
KALC-FM Alvin, Tex,
KAIS Newport Beach, Calif,
KAKC Tulsa, Okla,
KAKK San Antonio, Tex,
KAKK San Antonio, Tex,
KALK San Antonio, Tex,
KALK San Antonio, Tex,
KALK San Francisco, Calif,
KAMS Mammoth Spring, Ark,
KANG St. Louis, Mo,
KANT-FM Lancaster, Calif,
KANG St. Louis, Mo,
KANT-FM Lancaster, Calif,
KAPP Redonde Beach, Calif,
KAPP Redonde Beach, Calif,
KARM-FM Fresno, Calif,
KARM-FM Fresno, Calif,
KARM-FM Fresno, Calif,
KARM-FM San Luis Obispo, Calif,
KARM-FM San Luis Obispo, Calif,
KASU Jomesberra Ark,
KATY-FM San Luis Obispo, Calif,
KASU Jomesberra Ark,
KATY-FM San Luis Obispo, Calif,
KASU San Francisco, Calif,
KBBL Los Angeles, Calif,
KBBL San Francisco, Calif,
KBCA San Matca, Calif,
KBCA San Matca, Calif,
KBCA FM Monobale, Calif,
KBCA-FM Monobale, Calif,
KCBA-FM Wenbrase, Calif,
KCBA-FM Wenbrase, Calif,
KCBA-FM Wenbrase, Calif,
KCBA-FM San Francisco, Calif,
KCBA-FM San Francisco, Calif,
KCBA-FM San San San, Calif,
KCBA-FM San San, Cali

C.L. KLIR-FM Denver, Colo.
KLIZ-FM Brainerd, Minn.
KLOA-FM Ridgeerest, Calif,
KLON Long Beach, Calif,
KLRO San Diego, Calif,
KLSN Seattle, Wash, (s)
KLUB-FM Salt Lake City, Utah

KRON-FM San Francisco, Calif. KROS-FM Clinton, Iowa

C.L. Location KROW Sants Barbara, Calif.
KROY-FM Sacramento, Calif.
KROY-FM Sacramento, Calif.
KRPM San Jose, Calif.
KRSC San Jose, Calif.
KRSL Minneapolis, Minn.(s)
KRSN-FM Los Alamos, N.Mex.
KRYM Eugene, Oreg.
KSCO Santa Cruz, Calif.
KSOB-FM Salinas, Calif.
KSOB-FM Salinas, Calif.
KSOB-FM Manhattan, Kans,
KSOS San Olego, Calif.
KSEC Calif.
KSEC Calif.
KSEC Calif.
KSEC Calif.
KSEC San Olego, Calif.
KSEC San Olego, Calif.
KSEC San Olego, Calif.
KSEC San Fernando, Calif.
KSEC San San Fernando, Calif.
KSL San Fernando, Calif.
KSL San Fernando, Calif.
KSL Lauls, Mo.
KSL Tyler. Tex.
KSMA-FM Santa Maria, Calif.
KSC-FM Os Molines, lova
KSPC Claremont, Calif.
KSPL-FM Stillwater, Okla,
KSPL-FM Billwater, Okla,
KSPL-FM Billwater, Okla,
KSPL-FM Stillwater, Okla,
KSPL-FM Os Calif.
KSTL-FM St. Louis, Mo.
KSTN-FM Stockton, Calif.
KSTL-FM Mustin, Tex.
KYD Arm Austin, Tex.
KYD FM Moltawa, Kans,
KTTL-FM Modesto, Calif.
KTIS-FM Moltawa, Kans,
KTNT-FM Stockton, Tex.
KTSP Knasa City, Who,
KTXT-FM Houston, Tex.
KTSP Knasa City, Who,
KTXT-FM Houston, Tex.
KYDF FM Composite, Calif.
KUDE-FM Houston, Tex.
KUDF FM Colorade, Calif.
KUDF FM Colorade, Calif.
KULF Mel Calon, Calif.
KVLF Medwood City, Calif.
KUGN-FM Siloam Springs, Ark,
KUDO-FM Journal, Calif.
KVEC-FM Molity, Hawaii
KUDO-FM Satt Lake City, Utah
KUT FM Satt Ana, Calif.
KVIL FM Satt Ana, Calif.
KWMO-FM Worthington, Minn,
KWOC-FM Molesa, Tex.
KWOA-FM Worthing

C.L. Location KWPM-FM West Plains, Mo.

KXFM Fort Worth, Tex.

KXIK-FM Forrest City, Ark.

KXLU Los Angeles, Calif.

KXQR Fresno, Calif.

KXQR Fresno, Calif.

KXQR Fresno, Calif.

KXTR Kansas City, Mo. (s)

KXRQ Sacramento, Calif.

KXTR Kansas City, Mo. (s)

KXYZ-FM Houston, Tex.

KYA-FM San Francisco, Calif.

KYEW Phoenix, Ariz.

KYFM Oklahoma City, Okla.

KYSM-FM Mankato, Minn.

KYW-FM Cleveland, Ohio

KZAM Seattle, Wash.

KZFM Cortez, Colo,

KZOM Oklahoma City, Okla.

KZOM Seattle, Wash.

KZOM Oklahoma City, Okla.

KZOM Oklahoma, Ohlo

WAEF Syracuse, N.Y.

WAEZ HM Morpantown, W.Va.

WAIN-FM Morpantown, W.Va.

WARN-FM Morpantown, Ohlo

WACL-FM Owlahoma, Ohlo

WASA-FM Watherty, Conn.

WAUX-FM Watherty, Conn.

WAUX-FM Watherty, Conn.

WAUX-FM Watherty, Conn.

WAVY-FM Watherty, Conn.

W

Ī

WBBW-FM Youngstown, Onle
WBCB-FM Levittown-Fairless
WBCI-FM Williamsburg Ya.
WBCM-FM Bay City, Mich.
WBCN Boston, Mass,
WBEN-FM Borokton, Mass,
WBEN-FM Brokkon, Mass,
WBEX-FM Chillicothe, Ohle
WBEX-FM Chillicothe, Ohle
WBEX-FM Chillicothe, Ohle
WBEX-FM Cheage, III.
WBFG Detroit, Mich.
WBFM New York, N.Y.
WBFO Buffalo, N.Y.
WBFO Buffalo, N.Y.
WBGM Tallahassee, Fla.
WBGO Newark, N.J.
WBGM Tallahassee, Fla.
WBGO Newark, N.J.
WBGW Bowling Green, Ohle
WBIE-FM Marriette, Green,
WBGW Bowling Green, Ohle
WBIE-FM Marriette, Green,
WBIV Wethersfield, N.Y.
WBKV-FM Wethersfield, N.Y.
WBKV-FM Wethersfield, Ohle
WBMS-FM Springfield, Ohle
WBMS-FM Springfield, Ohle
WBMS-FM Columbus, Ohle (s)
WBOS-FM Brookline, Mass,
WBRS-FM Mt, Clements, Mich,
WBRC Birmingham, Ala.
WBT-FM Charlotte, N.C.(s)
WBUF Buffalo, N. N.C.(s)

C.L. Location WBVA Woodbridge, Va,
WBVP-FM Beaver Falls, Pa,
WBVC Berea, Ohio
WBZ-FM Boston, Mass,
WCAC Anderson, S.C.
WCAO-FM Baltimore, Md,
WCAU-FM Philadelphia, Pa,
WCBC-FM Andersoo, Ind.
WCBC-FM Palationer, Md,
WCBC-FM Baltimore, Md,
WCBC-FM New York, N.Y.
WCCC-FM Hartford, Conn.
WCCC-FM Hartford, Conn.
WCCV-FM Charlottesville, Va,
WCED-FM Dubois, Pa,
WCHA-FM Chambersburg, Pa, (s)
WCHD Detroit, Mie,
WCKR-FM Milliamstown, Mass,
WCHA-FM Chambersburg, Pa, (s)
WCHD Detroit, Mie,
WCKR-FM Cleveland, Tenn,
WCLI-FM Corning, N.Y.
WCLM-FM Chiesgo, Ill.
WCLO-FM Janesville, Wis,
WCLO-FM Wildwood, N.J.
WCLO-FM Wildwood, N.J.
WCMC-FM Wildwood, N.J.
WCMC-FM Wildwood, N.J.
WCMC-FM Brunswirk, Maine
WCMF-FM Rechester, N.Y.(s)
WCMI-FM Rohland, Ky,
WCMO-FM Sond, Mass,
WCOU-FM Columbus, Ohlo
WCMI-FM Columbus, Ohlo
WCM-FM Solon, Mass,
WCOU-FM Columbia, S.C.
WCOU-FM Columbia, S.C.
WCOU-FM Sparta, Wis,
WCOU-FM Sparta, Wis,
WCOU-FM Columbia, S.C.
WCOU-FM Melikhart, Ind,
WCPS-FM Tarbor, N.C.
WCH-FM Columbus, Ind,
WCSC-FM Charleston, S.C.
WCOU-FM Meliminshurg, Va,
WCMC-FM Meliminshurg, Va,
WCMC-FM Meliminshurg, Va,
WCM-FM Columbus, Ind,
WCSC-FM Charleston, S.C.
WCSL-FM Mollows, Ind,
WCSC-FM Meliminshurg, Va,
WCTM-FM Columbus, Ind,
WCSC-FM Meliminshurg, Va,
WDD-FM Mollon, S.C.
WCH-FM Mollon, S.C.
WCH-FM Meliminshurg, Va,
WDD-FM Mollon, S.C.
WDD-FM Meliminston, Del,
WDD-FM Meliminston, Del,
WDD-FM Meliminston, Del,
WDD-FM Meliminston, N.C.
WDD-FM Meliminston, N.C.
WDD-FM Meliminston, N.C.
WDD-FM Meliminston, N.Y.
WEEL-FM Wellon, N.Y.
WEEL-FM Meliminston, N.Y.
WEEL-FM

C.L. Location WERI-FM Westerly, R.I.
WERS Boston, Mass,
WESC-FM Greenville, S.C.
WEST-FM Greenville, S.C.
WEST-FM Easton, Pa.
WETN South Bend, Ind,
WETN Wheaton, III.
WEVC Evansville, Ind
WEVD-FM New York, N.Y.
WEWO-FM Laurinburg, N.C.
WFAA-FM Dallas, Tex,
WFAM-FM Alliane, Ohio
WFAN Washington, D.C.
WFAA-FM White Plains, N.Y.
WFAU-FM Magusta, Maino
WFAW Fort Atkinson, Wis.
WFBC-FM Greenville, S.C.
WFAS-FM White Plains, N.Y.
WFAU-FM Augusta, Maino
WFAW Fort Atkinson, Wis.
WFBC-FM Greenville, S.C.
WFBE Flist, Mich.
WFBG-FM Altoona, Pa.
WFBG-FM Altoona, Pa.
WFBG-FM Altoona, Pa.
WFBS-FM Whinston-Salem, N.C.
WFGE Franklin, Ind.
WFGJ Miamisburg, Ohio
WFGM Amberst, Mass.
WFDS-FM Baltimore, Md.
WFFM Cincinnati, Ohio
WFGM-FM Fitchburg, Mass,
WFDS-FM Baltimore, Md.
WFFM Cincinnati, Ohio
WFGM-FM Fitchburg, Mass,
WFHA-FM Wisconsin Rapids, WIs,
WFHD Find Plodras, P.R.
WFIG Sumter, S.C.
WFHA-FM Philadelphia, Pa.
WFIN-FM Philadelphia, Pa.
WFIN-FM Philadelphia, Pa.
WFIN-FM Philadelphia, Pa.(s)
WFLN-FM Franklin, Tenn,
WFMD-FM Frederick, Md,
WFLN-FM Franklin, Tenn,
WFMD-FM Frederick, Md,
WFLN-FM Frederick, Md,
WFLN-FM Find Wich,
WFM Chicago, III.(s)
WFM Baltimore, Md,
WFM Chicago, III.(s)
WFM Lass Orange, N.J.
WFM W-FM Madisonville, Ky.
WFM Lass Orange, N.J.
WFM W-FM Madisonville, Ky.
WFM Lass Orange, N.J.
WFM W-FM Madisonville, Ky.
WFM Lass Orange, N.J.
WFM La

C.L. Location WHEN-FM Syracuse, N.Y.
WHFB-FM Syracuse, N.Y.
WHFB-FM Beston Harbor, Mich,
WHFI West Paterson, N. J.
WHFM Rochester, N.Y.
WHS Bethesda, Md.(s)
WHHI Highland, Wis.
WHS Havertown, Pa.
WHIM-FM Dayton, Ohio
WHIZ-FM Dayton, Ohio
WHIZ-FM Dayton, Ohio
WHKY-FM Hiskory, N.C.
WHKW Chilton, Wis.
WHKD-FM Hiskory, N.C.
WHKW-FM Hiskory, N.C.
WHLD-FM Niagara Falls, N. Y.
WHLD-FM Niagara Falls, N. Y.
WHLD-FM Niagara Falls, N. Y.
WHLD-FM Niegara Falls, N. Y.
WHLM-FM Bloomsburg, Pa.
WHMA-FM Bloomsburg, Pa.
WHMA-FM Boomsburg, Pa.
WHMA-FM Bloomsburg, Pa.
WHMC-FM Henderson, N.C.
WHOG-FM Honderson, N.C.
WHOG-FM Des Moines, Jowa
WHOM-FM Naw York, N.Y.
WHOM-FM Naw York, N.Y.
WHOG-FM Des Moines, Jowa
WHOM-FM Naw York, N.Y.
WHOS-FM Decatur, Ala.
WHPE-FM High Point, N.C.
WHRFE-FM High Point, N.C.
WHR WHOS-FM Decatur, Ala.
WHPE-FM High Point, N.C.
WHR Highland Twp, Wis.
WHSA-Highland Twp, Wis.
WHSR-FM Cambridge, Mass,
WHRM Waussu, Wis.
WHSR-FM Wallson, Wis.
WHSC-FM Eatentown, N.J.
WHUS Storrs, Conn.
WHYC Colfax, Wis.
WHYN-Philadelphia, Pa.
WHYN-Philadelphia, Pa.
WHYN-Philadelphia, Pa.
WHYN-FM Springfield, Mass,
WHYY Philadelphia, Pa.
WHYN-FM Springfield, Mass,
WHYY Philadelphia, Pa.
WHE Buffalo, N.Y.
WIFE Standalophia, Pa.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Nis.
WISA-FM Midmaine, Fia.
WIRA-FM Midmaine, Fia.
WIRA-FM Midmaine, Fia.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Pa.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Pa.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Pa.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Fia.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Pa.
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Mich,
WIRA-FM Madison, Wis.
WISA-FM Midmaine, Mich,
WIRA-FM Malon, Pa.
WIRA-FM Malon, P.R.
WIFH-FM Baltimore, Md.
WIJC-FM Balton Mous, Mich,
WISC-FM Bloomington, III,
WIRA-FM San Juan, P.R.
WIFH-FM Baltimore, Md.
WIJC-FM Holand, Mich,
WIRA-FM Mannestown, N.K,
WIW-FM Moundson, N.I.
WHE-FM Midmaine, Wis.
WISA-FM Midmaine, Wis.
WISA-FM Midmaine, Wis.
WISA-FM Midmaine, Wis.
WISA-FM

C.L. Location WKIP-FM Pouphkeepsle, N.Y.
WKIS-FM Pouphkeepsle, N.Y.
WKIS-FM Pouphkeepsle, N.C.
WIKF Pittsburgh, Pa. (s)
WKLF-FM Clanton, Ala.
WKLS Marietta, Ga.
WKLW-FM Grand Rapids, Mich.
WKNA-FM Clanton, Ala.
WKNA-FM Charleston, W.Va. (s)
WKOF Hopkinsville, Ky.
WKOK-FM Sunbury, Pa.
WKOF-FM Binghamton, N.Y.
WKOK-FM Sunbury, Pa.
WKOP-FM Binghamton, N.Y.
WKOK-FM Cincinnati, Ohie
WKRG-FM Mobile, Ala.
WKRT-FM Certland, N.Y.
WKSD-FM Clantonati, Ohie
WKRG-FM Mobile, Ala.
WKRT-FM Certland, N.Y.
WKSD-FM Fambury, Conn.
WKSD-FM Sender, W.Ya.
WKYB-FM Padueah, Ky.
WLAD-FM Lagrange, Ga.
WLAN-FM Danbury, Conn.
WLAG-FM Lagrange, Ga.
WLAP-FM Lexington, Ky.
WLAY-FM Grand Rapids, Mich,
WLBG-FM Laurens-Clinton, S.C.
WLBM-FM Mattoon, Ill.
WLBG-FM Laurens-Clinton, S.C.
WLBM-FM Mattoon, Ill.
WLBG-FM Laurens-Clinton, S.C.
WLBM-FM Mattoon, Ill.
WLBC-FM Sandusky, Ohie
WLET-FM Toesca, Ga.
WLNA-FM Sparkon, Wis.
WLIN Merrill, Wis.
WL

C.L. Location WNAS New Albany, Ind.
WNAV-FM Annapolis, Md
WNBC-FM New York, N.Y.
WNBF-FM Blinghamton, N.Y.
WNBF-FM Blinghamton, N.Y.
WNBF-FM Blinghamton, N.Y.
WNBH-FM New Bedford, Mass.
WNCN New York, N.Y.
WNCO-FM Ashland, Ohlo
WNDA Huntsville, Ala. (15)
WNBD-FM Daytona Beach, Fla.
WNEM-FM Bay City, Mich. (5)
WNBC-FM Mey York, N.Y.
WNEW-FM Mew York, N.J.
WNEW-FM Mew York, N.J.
WNEW-FM Mew Haven, Conn,
WNIB Chicago, Ill.
WNO Elevaland, Ohlo (5)
WNOK-FM High Point, N.C.
WNOW-FM York, Pa.
WNOB Cleveland, Ohlo (5)
WNOK-FM High Point, N.C.
WNOW-FM York, Pa.
WNSH Highland Park, Ill.
WNSL-FM Laurel, Miss.
WMTH Winnetka, Ill.
WNYC-FM Arlington Hts., Ill.
WNYC-FM Mew York, N.Y.
WOAK Aroyal Oak, Mich.,
WOAY-FM Oak Hill, W.Va.
WOBN Westerville, Ohlo
WOCE-FM W. yarmouth, Mass,
WOHS-FM Shelby, N.C.
WOI-FM Mess, Iowa
WOIO Clincinnati, Dhie
WOC-FM Messier, N.Y.
WOKZ-FM Alton, Ill.
WOL-FM Washington, D.C.
WOMM-FM Bellaire, Ohlo
WON OS Yreause, N.Y.
WOND-FM Bellaire, Ohlo
WON OS Yreause, N.Y.
WORA-FM Mew York, N.Y.
WORA-FM Mershon, Ind.
WOS-FM Providence, R.I. (8)
WPAD-FM Paducah, Ky,
WORA-FM Pottsmouth, Ohlo (6)
WPBC-FM Minneapolis, Minn,
WPBS-Philadelphia, Pa.
WPEL-FM Montrose, Pa.
WPEL-FM Sharon, Pa.
WPEL-FM Minneapolis, Minn,
WPBS-PHIladelphia, Pa.
WPEL-FM Minneapolis, Minn,
WPBS-FM Providence, R.I.
WPRA-FM Providence, R.I.
WPRA-FM Pottsmouth, Ohlo (9)
WPAD-FM Realish, N.C.
WORMS-FM Providence, R.I.
WPRA-FM Pottsmouth, Miss,
WPAL-FM Pot

C.L. Location WQXT-FM Palm Beach, Fla.
WRAJ-FM Anna, III,
WRAK-FM Williamsport, Pa.
WRAL-FM Raleigh, N.C.
WRAY-FM Princeston, Ind.
WRBL-FM Columbus, Ga.
WRSD Baltimore, Md.
WRC-FM Washington. D.C.
WRCM New Orleans, La.
WRED Youngstewn, Ohio
WREV-FM Ashtabula, Ohio
WREV-FM Reidsville, N.C.
WRFD-FM Worthington.
Columbus, Ohio
WREV-FM Reidsville, N.C.
WRFL Winchester, Va.
WRFL Winchester, Va.
WRFL Winchester, Va.
WRFL Winchester, Va.
WRFM Woodside, N.Y.
WRFS-FM Alexander City, Ala.
WRHS Park Forest, III,
WRIJ-FM Maine, Wis.
WRJN-FM Recine, Wis.
WRJN-FM Recine, Wis.
WRJN-FM Recine, Wis.
WRJN-FM Recine, III,
WRNJ-RH Merris, III,
WRNJ-RH Morris, III,
WRNJ-RH Morris, III,
WRNJ-RH Morris, III,
WRNJ-RH Merris, WRN,
WRW-FM Morris, III,
WRNJ-FM Richmend, Va.
WRNW-FM Rockford, III,
WRNJ-FM Richmend, Va.
WRNW-FM Rockford, III,
WRNJ-FM Gains, Tex.
WRRN Warren, Pa.
WRU-FM Gainseville, Fla.
WRYS-FM Warsaw, Ind.
WRTI-FM Middlephia, Pa.
WRU-FM Gainseville, Fla.
WRVS-FM Madison, Wis.
WRV-FM Gainseville, Fla.
WRV-FM Gainseville, Fla.
WRV-FM Rechmend, Va.
WRV-FM Madison, Wis.
WRV-FM Gainseville, Fla.
WRV-FM Rechmend, Va.
WRV-FM Madison, Wis.
WRV-FM Gainseville, Fla.
WRV-FM Rechmend, Va.
WRV-FM Rechmend, Va.
WRV-FM Madison, Wis.
WRV-FM Corrish, N.C.
WRY-FM Rechmend, Wa.
WRV-FM Rechmend, Wa.
WRY-FM Corrish, N.C.
WRY-FM Rechmend, Wa.
WRY-FM Corrish, N.C.
WRY-FM Septinamed, Mich.
WSB-FM Cleansen, S.C.
WRY-FM Septinamed, Mich.
WSB-FM Maliand, Fla.
WSB-FM Cleansen, M.C.
WSB-FM Maliand, Fla.
WSB-FM Remonke, Va.
WSB-FM Remo

WBO-FM Cumberland, Md.
WTBS Cambridge, Mass,
WTCX St. Petersburg, Fla.
WTDS Toledo, Ohio
WFM Babylon, N.Y.
WTHI-FM Terre Haute, Ind.
WTIG-FM Martiord, Conn.
WTJU Charlottesville, Va.
WTMS-FM Jackson, Tenn.
WTJU Charlottesville, Va.
WTMA-FM Milvaukee, Wis.
WTMC-FM Hartiord, Conn.
WTJU Charlottesville, Va.
WTMG-FM Hartiord, Conn.
WTJU Charlottesville, Va.
WTMG-FM Savannah, Ga.
WTOF Canton, Ohio
WTOA Trenton, Ohio
WTOA Trenton, Ohio
WTOF Canton, Ohio
WTOF Canton, Ohio
WTOF FM Washington, D.C.
WTOS Wawvatosa, Wis.
WTRC-FM Elkhart, Ind.
WTOF-FM Washington, D.C.
WTOS Mawwatosa, Wis.
WTRC-FM Elkhart, Ind.
WTTY-FM Glowninster, Md.
WTTY-FM Glowninster, Md.
WTTY-FM Glowninster, Md.
WTWT-FM Columbus, Ohio
WUCB-FM Chicage, Ill.
WTWB-FM Coldwater, Mich.
WTVN-FM Columbus, Ohio
WUCB-FM Chicage, Ill.
WYM-FM Columbus, Ohio
WUCB-FM Chicage, Ill.
WYM-FM Columbus, Ohio
WUCB-FM Congel Hill, N.C.
WUOA Tuscaloosa, Ala.
WUOM Ann Arbor, Mich.
WUOT Knoxville, Tenn.
WUPL-Jynn, Mass.
WUSC-FM Columble, S.C.
WUST-FM Betheeda, Md.
WUSV Scranton, Pa.
WYMS-FM Ithaca, N.Y.
WYNG-FM Columbus, Ohio
WUSV Scranton, Pa.
WYMR-FM Haltoona, Pa.
WYMR-FM Glownbus, Ohio
WYLN-FM Glowbus, Ohio
WYLN-FM Mation, N.C.
WYM-FM Mation, N.C.
WYM-FM Mowensbore, Ky.
WWW-FM FM Mowensbore, Ky.
WYM-FM Mowensbore, Ky.
WWW-FM Mowensbore, Ky.
WWW-FM Mowensbore, Ky.
WYM-FM Mowensbo

C.L.

Location

Canadian FM Stations by Location

Cornwall, Ont. Edmonton, Alta.	CHIC-FM CKPC-FM CJSS-FM	102.1 92.1 104.5
	CFRN.FM	100.3
Ft. William.	CJCA-FM KUA-FM	99.5 98.1
	RADIO	94,3

Canadia	n FM	5ta	tior
Location	C.L.	Mc.	Loca
Hallfax, N.S. Kingston, Ont.	CHNS-FM CFRC-FM CKLC-FM	96.1 91.9 99.5	Oshav
Kitchener, Ont.	CKWS-FM CKCR-FM	96.3 96.7 100.9	Quebe Rime St. C:
Lendon, Ont. Montreal, Que,	CFPL-FM CBF-FM CBM-FM	95.9 95.1 100.7	Ont Sherb Timm

ocation	C.L.	A
	CFCF-FM	10
)shawa, Ont.	CKLB-FM	9
Ottawa, Ont.	CBO.FM	10
	CFMO-FM	9
Quebec, Que.	CHRC-FM	9
Rimouski, Que,	CJBR-FM	10
St. Catharines,		
Ont.	CKTB-FM	9
Sherbrooke, Que.	CHLT-FM	-10
limmins, Ont.	CKGB.FM	9

Mc.	Location	C.L.	Mc.
06.5	Terente, Ont,	CBC-FM	99. f
93.5		CFRB-FM	99.9
103.3		CHFI-FM	98.1
93.9		CJRT-FM	91,1
98.1	Vancouver, B.C.	CBU-FM	105.7
101.5		CHQM-FM	103.5
	Verdun, Que,	CKVL-FM	96,9
	Victoria, B.C.	CKDA-FM	98.5
	Windsor, Ont.	CKLW-FM	93.9
94.5	Winnipeg, Man,	CJOB-FM	97.5

Canadian FM Stations by Call Letters

C.L. Location
CBC-FM Toronto, Ont.
CBF-FM Montreal, Que.
CBM-FM Montreal, Que.
CBU-FM Vancouver, B.C.
CFC-FM Montreal, Que.
CFC-FM Montreal, Que.
CFPL-FM London, Ont.
CFRA-FM Ottawa, Ont.

1

C.L. Location
CFRB-FM Teronto, Ont.
CFRC-FM Kingston, Ont.
CFRN-FM Edmentos, Alta.
CHEC-FM Lethbridge, Alta.
CHEI-FM Teronto, Ont.
CHLI-FM Sherbrook. Que.
CHNS-FM Halifax, N.S.
CHRC-FM Quebec. Que.
CJBR-FM Rimouski, Que,

C.L. Location
CICA-FM Edmonton, Alta.
CICB-FM Sydney, N.S.
CIOB-FM Winnipeg, Man,
CJRT-FM Toronto, Ont.
CJSS-FM Cornwall, Ont.
CKCR-FM Kitchener, Ont.
CKOBA-FM Victoria, B.C.
CKGB-FM Timmins, Ont.
CKLB-FM Oshawa, Ont.

C.L. Location
CKLC-FM Kingston, Ont.
CKLW-FM Windsor, Ont.
CKPC-FM Brantford, Ont.
CKPC-FM FM FI, William, Ont.
CKSF-FM Ccrnwall, Ont.
CKSF-FM St. Catharines, Ont.
CKUA-FM Edmonton, Alta.
CKVL-FM Verdun, Quo.
CKWS-FM Kingston, Ont.

U. S. Television Stations

			U. .	. icicy	13	on stand	Olia				
Territories	and posse	ssic	ons follow stat	es. Chan., cl	nan	nel number; as	terisk (*) ind	dice	ates educational	station.	
Location	C.L. Ch	an.	Location .	C.L. Che	on.	Location	C.L. Che	n.	Location	C.L. Che	an.
ALAB.	AMA			KRMA-TV	•6	Danville	WICD	24	MARYL	AND	
Andalusia	WDIQ WAPI-TV	•2	Grand Junetion	KTVŘ KREX-TV	2 5	Decatur Harrisburg	WTVP WSIL-TV	17	Baltimore	WJZ-TV	18
Birmingham	WAPI-TV WBIQ	•10	Montrose Pueble	KREY-TV KCSJ-TV	10	La Salle Peoria	WEEQ-TV WEEK-TV	35 43		WBAL-TV WMAR-TV	11
Danatas	WBRC-TV	6			,		WMBD	31	Salisbury	WBOC-TV	16
Decatur Dothan	WMSL-TV WTVY	23	COÚNE	CTICUT		Quincy	WTVH WGEM-TV	19 10	MASSACH	IUSETTS	
Florence Huntsville	WOWL WAFG-TV	15 31	Bridgeport	WICC-TV	43	Rockford .	WREX-TV WTV0	13 39	Adams	WCDC	19
Mobile	WALA-TV	10	Hartferd	M 4CT-TA	18	Rock Island	WHBF-TV	- 4	Boston	WBZ-TV WGBH-TV	•2
Montgomery	WKRG-TV WCOV-TV	5 20	New Britain New Haven	WHNB-TV WNHC-TV	30 8	Springfield Urbana	WICS WILL-TV	20		WHDH-TV	5
Munford	WSFA-TV WCIQ	12	Waterbury	WATR-TV	53	IMBI	ANA		Greenfield	WNAC-TV WRLP	32
Selma	WSLA	8	DIST. OF	COLUMBIA	Δ.	INDI			Springfield	WHYN-TV WWLP	40 22
ALA:	SKA		Washington	WETA-TV	26	Bloomington Elkhart	WSJV-TV	28	Wescester	WWOR-TV	14
Anchorage	KENI-TV	2		WMAL-TV	7	Evansville	WFIE-TV WEHT	14 50	MICHI	GAN	
Fairbanks	KTVA KFAR-TV	11		WRC-TV WTOP-TV	9	Et Wayne	WTVW	7	Bay City	WNEM-TV	. 5
Juneau	KTVF KINY-TV	ΙĪ		WTTG	5	Ft, Wayne	WANE-TV WKJG-TV	33	Cadillac	WWTV WWUP-TV	13 10
		8	FLO	RIDA		Indianapolis	WPTA WFBM-TV	21 6	Cheboygan Dotsoit	WTOM-TV WJBK-TV	4 2
ARIZ			Daytona Beach	WESH-TV	.2		WLWI WISH-TV	13	D013071	WTVS	*56
Douglas Phoenix	KCDA KOOL-TV	10 *8	Fort Pierce-Vero Fort Myers	WINK-TV	19	Lafayette	WFAM-TV	16		WWJ-TV WXYZ-TV	7
	KAET KPHO-TV	*8	Gainesville Jacksonville	WUFT WFGA-TV	12	Muneie South Bend	WLBC-TV WNDU-TV	49 16	(Windsor, Ont.) Flint	CKLW-TV WJRT	9 12
	KTVK	3	240000000000000000000000000000000000000	WJCT	•7	Terre Haute	WSBT-TV WTHI-TV	22	Grand Rapids	WOOD-TV	8
Tueson	KTAR-TV KGUN-TV	12 9	Miaml	WCKT	7				Kalemazoo	WZZM-TV WKZO-TV	13
	KOLD-TV KVOA-TV	13		WLBW-TV WTHS-TV	10	10\	WA		Lansing Marquette	WLUC-TV	6
	KUAT	*6		LVTW	- 4	Ames Cedar Rapids	WOI-TV KCRG-TV	5	Onendaga WILX	-TV/WMSB	10
Yuma	KIVA	11	Oriando	WDBO-TV WLOF-TV	6		WMT-TV	2	Saginaw Trayerse City	WKNX-TV WPBN-TV	57 7
ARKA			Palm Beach Panama City	WPTV WJDM-TV	5 7	Oavenport Des Moines	WOC-TV KRNT-TV	8	MINNE	SOTA	
El Dorado Ft. Smith	KTVE KFSA-TV KFOY-TV	10 5	Pensacola St. Petersburg	WEAR-TV WSUN-TV	38		KDP8-TV '	13	Alexandria	KCMT	7
Hot Springs Little Rock	KFOY-TV KARK-TV	9	Tallahassee	W FSU-TV	٠ii	Fort Oodge	KQTV	21	Aust:n Duluth	KMMT KOAL-TV	6
LITTIO HOUR	KTHV	пŢ	Tampa	WFLA-TV WEOU	.8	Mason City Ottumwa	KGLO-TV KTVO	3		WDSM-TV	6
Texarkana	KATV KCMC-TV	6	W. Palm Beach	WTVT WEAT-TV	13	Sieux City	KTIV	9	Mankato Minneapoils	KEYC-TV KMSP	12
CALIFO	DRNIA				12	Waterloo	KWWL-TV	7		WCCO-TV WTCN-TV	-14
	KBAK-TV	29	GEO	RGIA			KWWL-ŤÝ ISAS	7	Rechester	WTCN-TV KROC-TV	11
CALIFO	KBAK-TV KERO-TV	10	GEO	RGIA WALB-TV	10	KAN Ensign	ISAS KTVC	7	Rechester St. Paul	WTCN-TV	ıî.
CALIFO Bakerefield Chico	KBAK-TV KERO-TV KLYD-TV KHSL-TV	10 17 12	GEO	RGIA WALB-TV WGTV WAGA-TV	10	KAN Ensign Garden City	KWWL-TV ISAS KTVC KGLD	7 6	Rechester St. Paul	WTCN-TV KROC-TV KSTP-TV KTCA-TV	11
CALIFO Bakerefield	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV	10	GEO Albany Athens	RGIA WALB-TV WGTV WAGA-TV WSB-TV WETV	10 *8 5 2 *30	KAN Ensign Garden City Goodland Great Bend	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT	6 11 10 2	St. Paul MISSIS Columbus	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV	11 10 5
CALIFO Bakersfield Chico El Centre Eureka	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KVIQ-TV	10 17 12 3	GEO Albany Athens Atlanta	WALB-TV WGTV WAGA-TV WSB-TV WETV WLW-A WJBF	10 *8 5	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH	8 11 10 2 7 12	MISSIS Columbus Greenwood	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV	11 10 5 2
CALIFO Bakersfield Chico El Centre	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KVIQ-TV KFRE-TV KAIL	10 17 12 3 6 30 53	GEO Albany Athens Atlanta	WALB-TV WGTV WAGA-TV WSB-TV WETV WLW-A WJBF	10 *8 5 2 *30 11 6	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH KOAM-TV	6 11 10 2 7	MISSIS Columbus Greenwood Jackson	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV WJTV	11 10 52 46 12
CALIFO Bakersfield Chico El Centre Eureka Fresno	KBAK-TV KERO-TV KLYD-TV KHSL-TV KHEM-TV KIEM-TV KYIQ-TV KFRE-TV KAIL KJEO KMJ-TV	10 17 12 3 8 6 30 53 47 24	GEO Albany Athens Atlanta Augusta Columbus	WALB-TV WGTV WAGA-TV WSB-TV WLW-A WJBF WRDW-TV WRBL-TV WTVM	10 *8 5 2 *30 11 6 12 3	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson	KWWL-TV ISAS KTVC KGLD KWHT-TV KAYS-TV KTVH KOAM-TV WIBW-TV KAKE-TV	6 11 10 2 7 12 7 13 10	MISSIS Columbus Greenwood	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV WABG-TV WLBT WOAM-TV	4 11 10 5 2 4 6 12 3 7 11
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanford	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KVIQ-TV KFRE-TV KAIL KJEO KMJ-TV KOAS-TV	10 17 12 3 6 30 53 47	GEO Albany Athens Atlanta	WALB-TV WGTV WAGA-TV WSB-TV WLW-A WJBF WRDW-TV WRBL-TV WRDA-TV WRAZ-TV	10 *8 5 2 *30 11 6 12 3 9 13	Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KOAM-TV WIBW-TV KAKE-TV KARD-TV	7 6 11 10 2 7 12 7	MISSIS Columbus Greenwood Jackson Laurel	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV WJTV WLBT WOAM-TV	11 10 5 •2 4 6 12 3 7
CALIFO Bakersfield Chico El Centre Eureka Fresno	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KVIQ-TV KFRE-TV KAIL KJEO KMJ-TV KOAS-TV KABC-TV KCOP	10 17 12 3 6 30 53 47 24 21 7	GEO Albany Athens Atlanta Augusta Columbus Macon	WALB-TV WAGA-TV WASB-TV WETV WLYA WJBF WRDW-TV WRBL-TV WMAZ-TV WSAV-TV WEGA-TV	10 *8 52 *30 11 6 12 3 9 13 *9	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KAYS-TV WIBW-TV KAKE-TV KARD-TV	6 11 10 2 7 12 7 13 10	MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV WJTV WLBT WOAM-TV WTOK-TV WTWV	4 11 10 5 2 4 6 12 3 7 11 30
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanford	KBAK-TV KERO-TV KLYD-TV KHBL-TV XEM-TV KIEM-TV KVIQ-TV KAIL KJEO KMJ-TV KAS-TV KABC-TV KABC-TV KMJ-TV KMBC-TV KMBC-TV KMBC-TV KMBC-TV KMBC-TV	10 17 12 3 6 30 53 47 24 21 7 13 9	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville	WALB-TV WGTV WAGA-TV WSB-TV WLW-A WJBF WRDW-TV WTVM WMAZ-TV WSAV-TV WEGA-TV WCTV	10 *8 5 2 *30 11 6 12 3 9 11 6	Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KOAM-TV WIBW-TV KAKE-TV KARD-TV UCKY WLEX-TV	7 6 11 10 2 7 12 7 13 10 3	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO	WTCN-TV KROC-TV KSTP-TV KTCA-TV SIPPI WCBI-TV WABG-TV WJEV WOAM-TV WTOK-TV WTOK-TV WTOK-TV WTWV	4 11 10 5 •2 4 6 12 3 7 11 30 9
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanford	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNJ-TV KNEX KNXT	10 17 12 3 6 30 53 47 24 21 7 13 9	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross	RGIA WALB-TV WAGA-TV WAGA-TV WSB-TV WETV WLW-A WJBF WRDW-TV WRBL-TV WSAV-TV WEGA-TV WEGS-TV	10 *8 52 *30 16 12 3 9 13 3 *9 11	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH KOAM-TV WIBW-TV KAKE-TV KARD-TV UCKY WKYT WAVE-TV WAVE-TV	7 6 11 10 2 7 12 7 13 10 3	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO Cape Girardeau Columbia	WTCN-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WCBI-TV WABG-TV WITV WLBT WTOK-TV WTOK-TV WTOK-TV WTWV OURI KFVS-TV KOMU-TV	4 11 10 5 2 4 6 12 3 7 11 30 9
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanford	KBAK-TV KERO-TV KLYD-TV KHBL-TV XEM-TV KIEM-TV KVIQ-TV KAIL KJEO KMJ-TV KABC-TV KABC-T	10 17 12 3 6 30 53 47 24 21 7 13 9 34 2	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross	WALB-TV WGTV WAGA-TV WSB-TV WLW-A WJBF WRDW-TV WTVM WMAZ-TV WSAV-TV WEGA-TV WCTV	10 *8 5 2 *30 11 6 12 3 9 11 6	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH KOAM-TV WIBW-TV KAKE-TV KARD-TV UCKY WLEX-TV WFY-TV WFY-TV WFY-TV WFY-TV WFY-TV	7 6 11 10 2 7 12 7 13 10 3	MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City	WTCN-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WCBI-TV WABG-TV WITV WLBT WTOK-TV WCOC-TV WTWV OURI KFVS-TV KOMU-TV KOMU-TV KRCG-TV	4 11 10 5 2 4 6 12 3 7 11 30 9
CALIFO Bakersfield Chlco El Centre Eureka Fresno Hanford Los Angeles	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KIEM-TV KOR-TV KOAS-TV KOAS-TV KABC-TV KABC-TV KMEX KMEX KMEX KMEX KMEX KRCA KTTV KTVU	10 17 12 3 6 30 53 47 24 21 7 13 9	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross	WALB-TV WAGA-TV WAGA-TV WEB-TV WEW-A WRDW-TV WRBL-TV WRSA-TV WEGA-TV WEGA-TV WEGS-TV WAII KHBC-TV	10 *8 52 *30 *11 65 *8 11 66 *8	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisviile	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH KOAM-TV WIBW-TV KARE-TV KARD-TV WLEX-TV WFPK-TV WHAS-TV WGXL-TV	7 6 11 10 2 7 12 7 13 10 3	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO Cape Girardeau Columbia Hannibal Jefferson City Joplin	WTCN-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WASG-TV WITV WOM-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV KCMU-TV KCG-TV KCG-TV	4 11 10 5 2 4 6 12 3 7 11 3 9 12 8 7 3 12
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles	KBAK-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KOAS-TV KABC-TV KABC-TV KMEX KMEX KMEX KMEX KNXT KTVU KVIP-TV KVIP-TV KVIP-TV KXTV	10 17 12 3 6 30 53 47 24 21 7 13 9 34 2	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross HA	WALB-TV WAGA-TV WAGA-TV WEN-A WIB-TV WEW-A WIBF WRDW-TV WRBL-TV WEGA-TV WEGA-TV WEGS-TV WHIGH KHBC-TV KHJK KGMB-TV	10 *8 5 2 2 *30 11 6 12 3 9 13 3 *9 11 6 *8 9 13 9	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KTVH KOAM-TV WIBW-TV KARE-TV KARD-TV WLEX-TV WHEX-TV	7 6 11 10 2 7 12 7 13 10 3 18 27 15 11 41	MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City	WTCN-TV KROC-TV KROC-TV KSTP-TV KSTP-TV WAB-TV WITV WOM-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV KCMU-TV KCMU-TV KCMU-TV KCMU-TV KCMO-TV KCMO-TV KCMO-TV	46 12 37 11 130 12 87 13 12 13 13 13 13 13 13 13 13 13 13 13 13 13
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Les Angeles Oakland Redding	KBAK-TV KERO-TV KLYD-TV KHBL-TV XEM-TV KIEM-TV KVIQ-TV KFRE-TV KOAS-TV KABC-TV KABC-TV KABC-TV KHLTV KHLTV KTVU KTVU KTVU KYTV KTVU KYTV KTVU	10 17 12 3 6 30 53 47 24 21 7 13 9 84 2 4 5 11 2 7	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross HA	RGIA WALB-TV WAGA-TV WAGA-TV WES-TV WEVA WIN-A WIBF WROW-TV WRBL-TV WAZ-TV WAZ-TV WEGA-TV WEGA-TV WEGS-TV WALB KHBC-TV KHBC-TV KHBC-TV KHBC-TV KHBC-TV	100 *88 52 *30 11 65 *8 9 13	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KOAM-TV WIBW-TV KARE-TV KARD-TV WEXT WAVE-TV WHPK-TV WHSS-TV WPSD-TV	7 6 11 10 2 7 13 10 3 18 27 3 15 11 41 6	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Joplin Kansas City	WTCN-TV KROC-TV KROC-TV KROC-TV KSTP-TV WABG-TV WIDV WOON-TV WTOV URI KFVS-TV KCMO-TV	4611052 4612371109 12877132 11259
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanferd Los Angeles Oakland Redding Sacramente	KBAK-TV KERO-TV KERO-TV KLYD-TV KHBL-TV KIEM-TV KIEM-TV KIEM-TV KOAS-TV KOAS-TV KABC-TV KTVU KVUE KVUE KVUE KVUE	10 17 12 3 3 6 50 53 47 24 21 7 10 40 *6	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hallo Honolulu	RGIA WALB-TV WAGA-TV WAGA-TV WSB-TV WETV WLW-A WJWF WRBL-TV WRBL-TV WSAV-TV WEGA-TV WCTV WEGS-TV WALB KHBC-TV KHBC-TV KHBC-TV KHBC-TV KHBC-TV KHBC-TV KONA KHWH-TV	10 * 5 2 2 * 30 1 1 6 * 8 9 1 3 9 1 3 2 4	KAN Ensien Garden City Geodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Loxington Louisville Paducah LOUIS Alexandria	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KTVH KOAM-TV WIBW-TV KARD-TV WCKT WCKT WYEX-TV WFYAS-TV WFYAS-TV WFYAS-TV WFYAS-TV WFSD-TV	7 6 11 10 2 7 12 7 13 10 3 18 27 15 11 41	MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Joplin Kansæs City Kirksville	WTCN-TV KROC-TV KROC-TV KROC-TV KSTP-IV KYCA-TV WAB-TV WAM-TV WOAM-TV WTOK-TV WTWV OKEN-TV KOMU-TV KCG-TV KCMO-TV	4623711399 128713125994315
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Les Angeles Oakland Redding	KBAK-TV KERO-TV KERO-TV KLYD-TV KHBL-TV KIEM-TV KIEM-TV KIEM-TV KOAS-TV KOAS-TV KOAS-TV KABCOP KMJ-TV KTVU KTVU KVUE KVUE KVUE KSBW-TV KCHU-TV	10 17 12 3 3 6 30 53 47 24 17 13 9 34 21 7 10 34 40 *** *** *** *** *** *** *** *** ***	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross HA	RGIA WALB-TV WAGA-TV WAGA-TV WSB-TV WETV WLW-A WJWF WRB-TV WRB-TV WARA-TV WYOG-TV WEGA-TV WEGS-TV WAII KHBC-TV KHJK KGMB-TV KONA KALA	100 *8 52 0 *30 1 6 2 3 9 1 3	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KTVH KOAM-TV WHEW-TV KARD-TV WCKT WYET WYET WYET WYET WYET WYET WYET WYE	7 6 110272713 103 18273 151416 592	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO Cape Girardeau Columbia Hannibai Jefferson City Jefferson City Jefferson City Jefferson City Jefferson St. Joseph	WTCN-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WCBI-TV WASG-TV WOOM-TV WTOK-TV WCOC-TV WTWV OURI KFVS-TV KCMO-TV	46123711052 4612371109 128713259943552
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Salinas San Bernardino	KBAK-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV	10 17 12 3 6 30 537 424 21 7 13 9 34 24 40 *6 8 18 40 **24	GEO Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hallo Honolulu	WALB-TV WAGA-TV WAGA-TV WES-TV WLW-A WAS-TV WES-TV WES-TV WEGA-TV WHOO-TV WEGA-TV WHOO-TV WEGA-TV WHOO-TV WEGA-TV WHOO-TV WEGA-TV WHOO-TV WHOO KHJK-TV KHJK KGMB-TV KHJK KGMB-TV KHJK KGMB-TV KONA KHVH-TV	10 * 8 5 2 2 * 30 11 6 8 9 13 9 13 2 2 4 3	KAN Ensien Garden City Geodland Great Bend Haye Hutchinson Pittoburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KTVH KOAM-TV WIBW-TV KARD-TV WEX-TV WKYT WAVE-TV WFFA-TV WFFA-TV WFFA-TV WFFA-TV WFFB-TV WFB-TV WFB-TV WFB-TV WFB-TV WFB-TV WFB-TV WFB-TV WFB-TV WFB-TV KATC KATC KATC KATC KATC KATC	7 8 1 1 0 2 7 1 2 7 1 3 1 0 3 1 8 7 3 1 5 1 1 1 4 6 5 9 2 3 1 0	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefierson City Joplin Kansas City Kirkswille Poplar Bluff, Mo.	WTCN-TV KROC-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WTSTP-TV WOBI-TV WOM-TV WTOK-TV WTOK-TV WTWV OURI KFVS-TV KCMO-TV	46123711052 462371109 12871325994
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Salinas San Bernardino San Diego	KBAK-TV KERO-TV KERO-TV KLYD-TV KHSL-TV XEM-TV KIEM-TV KIEM-TV KFRE-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KMEX KMEX KMEX KMEX KNXT KRCA KTTV KVIP-TV KOGO-TV KGOGO-TV	10 17 12 3 6 5 30 5 47 24 21 7 13 9 9 8 40 8 18 **24 18 **24 18 18 18 18 18 18 18 18 18 18 18 18 18	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hilo Honolulu Walluku	RGIA WALB-TV WAGA-TV WAGA-TV WSB-TV WETV WLW-A WJWF WRB-TV WRB-TV WARA-TV WYOG-TV WEGA-TV WEGS-TV WAII KHBC-TV KHJK KGMB-TV KONA KALA	100 *8 52 0 *30 1 6 2 3 9 1 3	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baten Rouge	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAY8-TV WIBW-TV WARD-TV WEX-TV WHEX-TV	7 6 1 1 0 2 7 12 7 13 10 3 18 7 3 15 1 4 1 6 5 9 2 3 10 7	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO Cape Girardeau Columbia Hannibai Jefferson City Jefferson City Jefferson City Jefferson City Jefferson St. Joseph	WTCN-TV KROC-TV KROC-TV KSTP-TV KSTP-TV KSTP-TV WABG-TV WJTV WOAM-TV WTOK-TV WCOC-TV WTWV OURI KFVS-TV KOMU-TV KCMO-TV KCMO-T	461237110522 46623711059 1287731259945
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Salinas San Bernardino	KBAK-TV KERO-TV KLYD-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTV KVIP-TV KOGO-TV KGOG-TV KGOG-TV KGOG-TV	1017 123 366 306 47 244 217 139 342 451 106 7	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hallo Honolulu Walluku	WALB-TV WAGA-TV WAGA-TV WAGA-TV WES-TV WEV WES-TV WES-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WAHI KHBC-TV KHJK KGMB-TV KGMB-TV KALA KMVI-TV AHO KBOI-TV	10 *8 52 *30 11 61 23 91 13 91 16 *8 91 32 24 37 71 2	KAN Ensien Garden City Geodland Great Bend Haye Hutchinson Pittoburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV WIBW-TV KAKE-TV KAKE-TV WAYE-TV WFPK-TV WFPK-TV WFSD-TV SIANA KALB-TV WBR KATC KLEY-TV WARE-TV KARD-TV KARD-T	7 811027273103 187311416 5923107258	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Jeplin Kansæs City Kirkswille Poplar Bluff, Mo. St. Joseph St. Leuis	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV WABG-TV WAGG-TV WTON-TV WCOC-TV WTWV OURI KFVS-TV KCMO-TV	461052 4662371109 128732125944352945211
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanferd Los Angeles Oakland Redding Sacramento Salinas San Bernardino San Diego (Tijuana, Mex.)	KBAK-TV KERO-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTVU KVIP-TV KVIP-TV KVIP-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KGG-TV KGGO-TV KGGO-TV KGGO-TV KGGG-TV	1017 123 366 306 37 47 244 211 7 103 40 *6 8 8 18 *24 8 10 6	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hilo Honolulu Walluku	WALB-TV WAGA-TV WAGA-TV WAGA-TV WES-TV WEW-A WIBF WROW-TV WRBL-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WAHIR KHBC-TV KHJK KGMB-TV KHJK KGMB-TV KALA KMVI-TV KTVB KOO-TV KTVB KOO-TV KTVB KID-TV	108522°30116123913243712 273	Ensign Garden City Geodland Great Bend Hays Huthinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette Lake Charles	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV WIBW-TV WARE-TV KARD-TV WEX-TV WFPK-TV WHAS-TV WFPK-TV WHAS-TV WFR KALB-TV WAFB-TV WAFB-TV WAFB-TV WAFB-TV WAFB-TV WAFB-TV WAFB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV KATC KLSE KOSU-TV KNOE-TV	7 8110271273103 187311416 5923107258316	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSO Cape Girardeau Columbia Hannibai Jefferson City Jefferson City Jefferson City Jefferson City Jefferson St. Joseph	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KROC-TV WABG-TV WIV WOM-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV KROC-TV KRO	461052 462371139 128713125944315294521160
CALIFO Bakersfield Chico El Centre Euroka Fresno Hanferd Los Angeles Oakland Redding Sacramento Salinas San Bernardino San Diego (Tijuana, Mex.)	KBAK-TV KERO-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTVU KVIP-TV KVIP-TV KVIP-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KCHU-TV KGG-TV KGGO-TV KGGO-TV KGGO-TV KGGG-TV	107 123 36 303 533 424 21 7 10 30 40 6 8 18 40 6 7 7 8 8 10 6 7 7 8 8 8 9 9 9 9 9 9 9 9 9 9 9 9 9 9 9	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross Hallo Honolulu Walluku Boise Idaho Falls	WALB-TV WAGA-TV WAGA-TV WAGA-TV WETV WLW-A WARL-TV WARL-TV WEGA-TV WEGS-TV WALI KALA KMVI-TV AHO KALA KMVI-TV KIFI-TV KIFI-TV	1085 520 ** 1168 ** 93 13 9 13 9 13 9 13 9 13 9 13 9 13	KAN Ensien Garden City Geodiand Great Bend Harrich Hend Harrich Hend Harrich Hend KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette Lake Charles Monroe	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAY8-TV WIBW-TV WARE-TV KARD-TV WEX-TV WFPK-TV WHAS-TV WFPK-TV WHAS-TV WFR KALB-TV WAFB-TV WA	7 8 1 1 0 2 7 1 2 7 1 3 1 8 7 3 1 5 1 1 1 4 6 5 9 2 3 1 7 2 5 8 1 3	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Jeplin Kansas City Kirksville Poplar Bluff, Mo. St. Joseph St. Leuis	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KSTP-TV WABG-TV WAM-TV WOM-TV WOOK-TV KOOM-TV	41052 462371109 128731259435216
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Salinas San Bernardino San Diego (Tijuana, Mex.) San Francisco	KBAK-TV KERO-TV KERO-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KIEM-TV KFRE-TV KFRE-TV KABC-TV KABC-TV KABC-TV KMTVU KTYUV KTYUV KVIEW-TV KVIEW-TV KVIEW-TV KVIEW-TV KVIEW-TV KOGO-TV KGGO-TV	1077123	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hilo Honolulu Walluku Boise Idaho Falls Lewiston Nampa	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WETV WLW-A WJBF WROW-TV WRBL-TV WAV-TV WAV-TV WEGA-TV WEGA-TV WEGS-TV WALB KHBC-TV KHJK KGMB-TV KALA KMVI-TV AHO KALA KMVI-TV KEOI-TV KIFI-TV KIFI-TV KIFI-TV KCIX-TV KGT-TV KCIX-TV	1085 5200 1 62 8 9 1 9 1 3 2 4 3 7 1 2 7 3 8 3 6	KAN Ensien Garden City Geodland Great Bend Haya Hutchinson Pittroburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baten Rouge 1 Lafayette Lake Charles Monroe New Orleans	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAY8-TV WIBW-TV WARE-TV KARD-TV WEX-TV WFPK-TV WHAS-TV WFPK-TV WHAS-TV WFR KALB-TV WAFB-TV WA	7 6110271271303 1873511416 592307258316348	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal	WTCN-TV KROC-TV KROC-TV KROC-TV KSTP-TV KSTP-TV WABG-TV WABG-TV WOAN-TV WTWV OURI KFVS-TV KOMU-TV KCMC-TV KFEQ-TV KFFQ-TV KFFQ-TV KFTV-T KTS-TV KTV-T KTV-T	11052 4623711 309 1287312 15994352 11603
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Salinas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Jose San Luis Obispo Santa Barbara	KBAK-TV KERO-TV KERO-TV KLYD-TV KERO-TV KLYD-TV KIEM-TV KIEM-TV KIEM-TV KIEM-TV KFRE-TV KFRE-TV KABC-TV KABC-TV KABC-TV KMEXA KRIAN KRIAN KRIAN KRIAN KRITV KTTVU KVIP-TV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KVIP-TV KOGO-TV KGO-TV KGO-TV KGO-TV KGO-TV KGO-TV KRIP-TV KRIP-TV KGO-TV KGO-TV KGO-TV KRIP-TV KGO-TV KGO-TV KGO-TV KRIP-TV KGO-TV KGO-TV KRIP-TV KRIP-TV KGO-TV KGO-TV KRIP-TV KGO-TV KRIP-TV KGO-TV KGO-TV KGO-TV KGO-TV KRIP-TV KGO-TV	10711233663005374241713945681122713940675940068	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross Hilo Honolulu Walluku Boise Idaho Falls Lewiston Nampa Twin Falls	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WETV WLW-A WLW-A WLW-A WLW-A WLW-A WLW-A WLW-A WLW-A WLW-A WARA-TV WARAL-TV KALA KALA KALA KALA KALA KALA KALA KAL	100 * 85 200 62 3 9 1 1 6 8 9 1 3 9 1 2 2 4 3 7 1 2 2 7 3 8 3 1	KAN Ensien Garden City Geodiand Great Bend Harrich Harrich Harrich KENT Lexington Louisville Paducah LOUIS Alexandria Baten Rouge 1 Lafayette Lake Charles Menden Garden Lake Menroe	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KTVH KOAM-TV WIBW-TV KARD-TV UCKY WEX-TV WFYA-TV WFYA-TV WFYA-TV WFYB-TV WFYB-TV WFB-TV WFB-TV WFB-TV KARD-TV WFYB-TV WFYB-TV WFYB-TV WFYB-TV WFYB-TV KATG-TV KATG-TV KATG-TV KNOE-TV KLSE WOSU-TV	7 6102727303 187351416 5923072831634	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibai	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KROC-TV WASG-TV WILT WOMB-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV WTOK-TV KROC-TV	4 6 1 2 3 7 1 1 0 9 1 2 8 7 1 3 2 9 4 3 5 2 1 6 10 3 2 8
CALIFO Bakersfield Chlco El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Sallnas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Luis Obispo Santa Barbara Steekton	KBAK-TV KERO-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KFRE-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTV KVIP-TV KVIP-TV KCRA-TV KVIP-TV KCRA-TV KC	10712336 30053742417739456 444571277199466 884675940	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Waycross HA Hilo Honolulu Walluku Boise Idaho Falis Lewiston Nampa Twin Falis ILLI	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WETV WLW-A WJBF WROW-TV WRBL-TV WAZ-TV WAZ-TV WEGA-TV WEGA-TV WEGS-TV WALB KALA KALA KAU-TV KAU-T	100 *8 5 2 2 3 9 1 1 1 1	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette Lake Charles Monroe New Orleans Shreveport	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAYS-TV KAYS-TV WIBW-TV KAKE-TV KARD-TV WEX-TV WYEX-TV WAST-TV WAST-TV WAST-TV KATC KLSE WOUL-TV WYES WYUE WYUE WYES KSLA-TV KTBS-TV	7 8 1 1 0 2 7 2 7 3 1 0 3 1 8 7 3 1 5 1 1 4 6 5 9 2 3 0 7 2 8 3 6 3 4 8 2	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal	WTCN-TV KROC-TV KROC-TV KROC-TV KSTP-TV KSTP-TV WABG-TV WABG-TV WOAN-TV WTWV OURI KFVS-TV KOMU-TV KCMC-TV KFEQ-TV KFFQ-TV KFFQ-TV KFTV-T KTS-TV KTV-T KTV-T	461052 462371109 128713259 44521603 2
CALIFO Bakersfield Chico El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Sallnas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Luis Obispo Santa Barbara Steckton Vista	KBAK-TV KERO-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTV KVIEM-TV KVIEM-TV KOP-TV KVIEM-TV KCHU-TV	10712336630353372445512277103400*6888475594016633	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross HA Hilo Honolulu Walluku IDA Boise Idaho Falls Lewiston Nampa Twin Falls ILLI Carbondale	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WETV WIW-A WAGA-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGB-TV WALB KABC-TV KAJK KAMB-TV KALA KMVI-TV KALA KMVI-TV KIP-TV KUX-TV KOIS-TV NOIS	108 520 1 52 1 53 9 1 1 68 9 3 3 9 3 2 4 3 7 7 2 2 7 3 8 3 6 1 8	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baten Rouge 1 Lafayette Lake Charles Monroe New Orleans MA	KWWL-TV ISAS KTVC KGLD KWHT-TV KCKT KAY8-TV WIBW-TV KAKE-TV KAKE-TV WAYE-TV WAYE-TV WAYE-TV WYEX-TV	7 8 1 1 0 2 7 2 7 3 1 0 3 1 8 7 3 1 5 1 1 4 6 5 9 2 3 0 7 2 8 3 6 3 4 8 2	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Joplin Kansas City Kirkswille Poplar Bluff, Mo. St. Joseph St. Louis Sedalia Springfield MONT Billings Butte	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KROC-TV WABG-TV WAM-TV WOM-TV WOOC-TV WTWV OR KFVS-TV KNOC-TV	411052 462371109 1287312599435211603 28455
CALIFO Bakersfield Chlco El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Sallnas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Luis Obispo Santa Barbara Steckten Vista	KBAK-TV KERO-TV KERO-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KFRE-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTV KVIP-TV KVIP-TV KCHU-TV KCU-TV KCU-TV KCU-TV KCU-TV	10 172 3 3 66 3 53 47 42 47 1 9 3 42 40 6 8 18 42 1 6 7 5 9 44 20 1 6 1 6 1 6 1 6 1 6 1 6 1 6 1 6 1 6 1 6	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross HA Hilo Honolulu Walluku IDA Boise Idaho Falls Lewiston Nampa Twin Falls ILLI Carbondale Champaign	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WES-TV WLW-A WAU-TV WARBL-TV WARBL-TV WARA-TV WAGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WEGA-TV WALB KABA-TV KALA KALA KMVI-TV KALA KMVI-TV KALA KMVI-TV KIFI-TV KLEW-TV KLIX-TV WCIA WCHU WCHU	100 *8 5 2 2 3 9 1 1 1 1	KAN Ensign Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baton Rouge 1 Lafayette Lake Charles Monroe New Orleans Shreveport	KWWL-TV ISAS KTVC KWHT-TV KCKT KAYS-TV KVYS-TV WIBW-TV KARD-TV WEX-TV WYKARD-TV WYKARD-TV WYFSD-TV KARD-TV WYFSD-TV KARD-TV WYFSD-TV INE WYUE WYLL-TV KARD-TV KARD-TV WYFSD-TV INE WCBB WABI-TV	7 61102727303 187351146 5923072583634823 165	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Jefferson City Joplin Kansas City Kirkswille Poplar Bluff, Mo. St. Joseph St. Louis MONT Billings Butte Giendive Great Falls Helena	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KROC-TV WAM-TV WOM-TV WTOK-TV WTWV OKFVS-TV KNOC-TV K	4 1052 46 237 109 287 32 59 94 35 2 94 52 16 03 284 55 32
CALIFO Bakersfield Chlco El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Sallnas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Luis Obispo Santa Barbara Steckten Vista COLO Colorado Springs	KBAK-TV KERO-TV KERO-TV KLYD-TV KEN-TV KIEM-TV KIEM-TV KIEM-TV KIEM-TV KAIL KJEO KMJ-TV KABC-TV KABC-TV KABC-TV KMEX KNXT KRCA KTTVU KVIP-TV KVIP-TV KVIP-TV KCHU-TV K	10 172 33 56 3033 474 221 73 194 30 40 6 8 8 184 2 8 10 6 7 5 9 9 4 4 0 2 1 1 6 3 15 2 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross HA Hilo Honolulu Walluku IDA Boise Idaho Falls Lewiston Nampa Twin Falls ILLI Carbondale	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WES-TV WLW-A WALB-TV WASA-TV WASA-TV WASA-TV WASA-TV WASA-TV WEGA-TV WEGA-TV WEGA-TV WACTO KONA KNON-TV KALA KNON-TV KALA KNON-TV KALA KNON-TV KIFI-TV KLEW-TV KLEW-TV KLEW-TV KLEW-TV KLEW-TV WCHU WBSM-TV WCHU WBSM-TV WCHU WBWBK	108 5 5 2 0 1 1 6 8 9 1 3 9 3 2 2 4 3 7 1 2 2 7 3 8 3 6 1 8 3 3 2 2 7	KAN Ensien Garden City Goodland Great Bend Hays Hutchinson Pitteburg Topeka Wichita KENT Lexington Louisville Paducah Louisville Paducah Louisville Lafayette Lake Charles Monroe New Orleans Shreveport MA Augusta Banger Poland Spring	KWWL-TV ISAS KTVC KWHT-TV KGLD KWHT-TV KKKTVH KOAM-TV WIBW-TV KARD-TV WWSB-TV WWYLEX-TV WYFSD-TV ISIANA KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV WAFB-TV KALB-TV KA	7 6102727303 1873151146 592307583634823 16528	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Sedalia Springfield MONT Billings Butte Giendive Great Falls	WTCN-TV WKROC-TV KSTP-TV KSTP-TV KSTP-TV WABG-TV WABG-TV WOM-TV WTWV OURI KFVS-TV KCMO-TV KFEQ-TV KFEQ-TV KFEQ-TV KFEQ-TV KSO-TV KFEQ-TV KSO-TV KFEQ-TV KSO-TV KFEQ-TV KSO-TV	4 1052 46237 109 1287 325994552 1603 284553
CALIFO Bakersfield Chlco El Centre Eureka Fresno Hanford Los Angeles Oakland Redding Sacramente Sallnas San Bernardino San Diego (Tijuana, Mex.) San Francisco San Luis Obispo Santa Barbara Steckten Vista	KBAK-TV KERO-TV KLYD-TV KLYD-TV KLYD-TV KHSL-TV KIEM-TV KIEM-TV KIEM-TV KFRE-TV KOAS-TV KOAS-TV KABC-TV KMEX KNTT KRCA KTTV KOAS-TV KMEX KNXT KRCA KTTV KOB-TV KOYP-TV KCV-TV KCV KCV-TV KCV KCV KCV KCV KCV KCV KCV KCV KCV KC	10 172 13 36 30 37 42 41 27 11 34 24 51 24 81 81 81 81 81 81 81 81 81 81 81 81 81	Albany Athens Atlanta Augusta Columbus Macon Savannah Thomasville Wayeross HA Hilo Honolulu Walluku IDA Boise Idaho Falls Lewiston Nampa Twin Falls ILLI Carbondale Champaign	WALB-TV WAGA-TV WAGA-TV WAGA-TV WAGA-TV WES-TV WES-TV WASA-TV	108 5 2 3 9 1 1 6 8 9 3 9 3 1 2 4 3 7 1 2 7 3 8 3 6 1 8 3 3 2 7 9 5	Ensien Garden City Geodland Great Bend Haya Hutchinson Pittreburg Topeka Wichita KENT Lexington Louisville Paducah LOUIS Alexandria Baten Rouge 1 Lafayette Lake Charles Monroe New Orleans Shreveport MA Augusta Banger	KWWL-TY ISAS KTVC KGLD KWHT-TY KCKT KYS-TY KTVH KOAM-TY WIBW-TY KARD-TY WEX-TY WAYE-TY KATG-TY KATG-	7 6102727303 8735146 5923072583634823 652869	St. Paul MISSIS Columbus Greenwood Jackson Laurel Merician Tupelo MISSC Cape Girardeau Columbia Hannibal Hollings Kirkswille Poplin Kansas City Kirkswille Poplin Ho. St. Joseph St. Leuis MONT Billings Butte Giendive Giendive Giendive Gient Falls Helena Kalispeli	WTCN-TV KROC-TV KROC-TV KROC-TV KROC-TV KSTP-TV WABG-TV WAM-TV WOM-TV WOOK-TV WOOK-TV KOM-TV KCG-TV KCG-TV KCG-TV KCG-TV KCG-TV KCGG-TV	411052 462371139 128731225945211603 28455329

B Allon			I a - mAlam	C.L. Chan.	I a - adla a	C.I. Chan		01 01
Location	Ç.L. CA RASKA	an.	Grand Forks	KNOX-TV 10		C.L. Chen.	Wichita Fails	C.L. Chan. KFDX-TV 3
Grand Island	KGIN-TV	п	Minet	KXMC-TV IS KMOT IO	Anderson	WAIM-TV 40		KSYD-TV 6
Hastings	KHA8-TV	5 4	Pembina, N.D.	KCND-TV 12	Charlesten	WCSC-TV 5	UTA	
Hay Springs Hayes Center	KOUH-TV KHPL-TV	6	Valley City Williston	KXJB-TV 4 KUMV-JV 8	Clemson	WSBF-FM *88.1	Ogden	KVDG-TV 9 KWCS-TV *18
Kearney Lincoln	KHOL-TV KOLN-TV	13	OH	110	Columbia	WIS-TV 10 WCCA-TV 25	Provo Sait Lake City	KLOR-TV II KSL-TV 5
Me Cook	KOMC	*12	Altron	WAKR-TV 49	Florence	WNOK-TV 67 WBTW 8	Out Land Olly	KCPX-TV 4
North Platte Dmaha	KNOP	3	Cincinnati	WCET *48 WCPO-TV 9	Greenville Spartanburg	WFBC-TV 4		KUED •7 KUTV 2
	WOW-TV	7		WKRC-TV 12 WLW-T 5		DAKOTA	VERM	ONT
Scottsbluff	KSTF	Iŏ	Cleveland	WCIN-TV 54 KYW-TV 3	Aberdeen	KXAB-TV 9	Burlington	WCAX-TV 8
NE	VADA			WEWS 5	Deadwood Florence	KDSJ-TV 5 KDLO-TV 8	VIRG	
Henderson Las Vedas	KLRJ-TV KLAS-TV	2	Columbus	WBNS-TV 10 WLW-C 4	Mitchell Rapid City	KORN-TV 5 KOTA-TV 3	Bristol Hampton	WCYB-TV 5 WVEC-TV 13
	K8H0-TV	13		W08U-TV *34	Reliance	KRSD-TV 7 KPLO-TV 6	Harrisonburg Lynchburg	WSVA-TV 3 WLVA-TV 13
Rene	KORL KOLO-TV	8	Dayton	WTVN-TV 6 WHIO-TV 7	Sioux Falls	KELD-TV II	Norfolk	WHRO-TV 15 WTAR-TV. 3
NEW H	AMPSHIRE		Lima	WLW-D 2 WIMA-IV 35	Vermilion	K800-TV 13 KUSD-TV *2	Petersburg Pertsmouth	WXEX-TV 8 WAVY-TV 10
Durham	WENH-TV		Oxford Staubenville	WMUB-TV 14 WSTV-TV 9	TEN	NESSEE	Richmond	WRVA-TV 12
Manchester	WMUR-TV	9	Tolede	WSPD-TV 13 WGTE-TV '30	Chattanooga	WDEF-TV 12 WRGP-TV 3	Roznoke	WTVR 6 WDBJ-TV 7
NEW	JERSEY		Youngstown	WTOL-TV II WFMJ-TV 2I		WTVC 9	WASHII	WSLS-TV 10
Newark	WNDT-TV	13		WKBN-TV 27 WKST-TV 33	Jackson Johnson City	WDXI-TV 7 WJHL-TV II WATE-TV 6	WASITII Bellingham	KVOS-TV 12
NEW	MEXICO		Zanesville	WHIZ-TV IS	KnexvIIIe	WBIR-TV IO	Pasco Pullman	KEPR-TV 19 KWSC-TV *10
Albuquerque	KGGM-TV KNME-TV	13	OKLAI	HOMA	Memphis	WTVK 26 WHBQ-TV 13	Richland	KNDD-TV 25
	KDAT-TV KDB-TV	7	Ada Ardmore	KTEN 10 KXII 12		WKNO *10	Seattle	KCTS-TV '9 KING-TV 5
Carlsbad	KAVE-TV	12	Enid	KOCO-TV 5 KSWD-TV 7	Nashville	WREC-TV 3 WDCN-TV *2		KIRO-TV 7 KDMD-TV 4
Clovis Roswell	KVER-TV KSW8-TV	8	Lawton Okiahoma City	KETA *13		WLAC-TV 5 WSIX-TV 8	Spokane	KHQ-TV 6 KREM-TV 2
NEW	YORK			KOKH-TV 25 KWTV 9		WSM-TV 4	Tasoma	KXLY-TV 4 KTNT-TV II
Albany	WTEN WAST	10	Tulsa	WKY-TV 4 KDTV 6	Ĭ. T I	EXAS		KTNT-TV II KPEC-TV *56 KTPS *62
	WAST WTRI WCDA	13 35		KOED-TV *11	Abilene	KRBC-TV 9 KULF-TV 12	Yakima	KTVW 13 KIMA-TV 29
Binghamton	WCDA WINR-TV	41		KVDO-TV 2	Alpine Amarillo	KFDA-TV 10	Tekime	KNDO-TV 23
Buffale	WNBF-TV WBEN-TV	12	ORE	GON		KGNC-TV 4	WEST V	IRGINIA
	WNED-TV	117	Coos Bay Corvallis	KCBY-TV II KDAC-TV *7	Austin Beaumont	KTBC-TV 7 KFDM-TV 6	Bluefield Charleston	WHIS-TV 6 WCHS-TV 8
Carthago	WGR-TV WKBW-TV WCNY-TV	7 7	Eugone	KVAL-TV IS KEZI-TV 9	Big Spring Bryan	KEDY-TV 4 KBTX-TV 3	Clarksburg Fairmont	WCHS-TV 8 WBOY-TV 12 WJPB-TV 5
Elmira New York	WSYE-TV	18	Klamath Medford	KDTI 2 KBES-TV 5	Corpus Christi	KRIS-TV 6 KZTV 10	Huntington	WHTN-TV IS WSAZ-TV 3
Mam Lork	WABC-TV WUHF-TV	3 į		KMED-TV 10	Dallas	KRLD-TV 4 KERA-TV *13	Dak HIII	WOAY-TV 4
	WNEW-TV WCBS-TV	2	Portland	KGW-TV 8	El Paso	WEAR-TV 8	Parkersburg Wheeling	WTAP-TV 15 WTRF-TV 7
	WOR-TV WPIX	Щ		KATU-TV 2 KOIN-TV 6	1	KROD-TV 4 KTSM-TV 9	WISCO	ONSIN
Plattsburg	WNBC-TV WPTZ-TV		Reseburg	KPTV 12 KPIC 4	(Ciudad Juare		Eau Claira Green Bay	WEAU-TV 13 WBAY-TV 2
Rechester	WHEC-TV WOKR-TV	10	PENNSY	LVANIA	Ft, Worth	KTVT II	dieen DE	WFRV 5
	WROC-TV WVET-TV		Altoona	WFBG-TV 10	Harlingen	WBAP-TV 5 KGBT-TV 4 KPRC-TV 2	La Crosse	WKBT 8 WHA-TV *21
Schonoctedy Syracuse	WRGB	- 6	Erio	WICU 12 W8EE-TV 35 WHP-TV 21	Houston	KHDU-TV II	Madison	WISC-TV 3
	WHEN-TV WNYS WSYR-TV		Harrisburg	WHP-TV 21 WTPA 27		KTRK-TV 13 KUHT *8	l	WKDW-TV 27 WMTV 33
Utlea	WKTV	2	Johnstown	WARD-TV 56 WJAC-TV 6	Larede Lubbock	KGNS-TV 6 KCBD-TV II	Marinette Milwaukee	WMBV-TV II WISN-TV I2
NORTH	CAROLINA	4	Laneaster Lebanon	WGAL-TV 8	Lufkin	KDUB-TV 13 KTRE-TV 9		WITI-TV 6 WMV8-TV 10
Asheville	WISE-TV WLOS-TV		Leekhaven New Castle	WBPZ-TV 32 WKST-TV 33		KMID-TV 2 KDCD-TV 18		WTMJ-TV 4 WXIX 18
Chapet Hill	WUNC-TV WBTV	3	Philadelphia	WCAU-TV 10	Monahans Odessa	KVKM-TV 9 KOSA-TV 7	Wausau	WSAU-TV 7
Charlette	W80C-TV	9		WHYY-TV *35		saument KPAC-TV 4	WYO	
Durham Greensbore	WTVD WFMY-TV	2	l	WRCV-TV 3	Richardson San Angelo	KRET-TV *23 KCTV 8	Casper Cheyenne	KTWD-TV 2 KFBC-TV 5
Greenville Raieigh	WRAL-TV	' 5		WIIC II		KACB-TV 3	Riverton	KWRB-TV 10
Washington Wilmington	WECT	6		WQED *13 WTAE 4 WNEP-TV 16		KUĀL-TV 41 KENS-TV 5 KLRN *9	PUERTO Aquadilla	WOLE-TV 12
Winston-Selem		1 12	1	WDAU-TV 22		KDNO-TV 12	Caguas	WKBM-TV II
	1 DAKOTA		Wilkes-Barre York	WBRE-TV 28 W8BA-TV 43	Sweetwater	WOAI-TV 4 KPAR-TV 12	Mayaguez	WORA-TV 5
Bismarck	KXMB-TV KFYR-TV	/ 5		ISLAND	Temple Texarkana	KCEN-TV 6	Ponce	WRIK-TV 7 WSUR-TV 9
Dickinson Farso	KDIX-TV WDAY-TV	/ 2		WJAR-TV 10	Tyler Wase	KUTV 7	San Juan	WAPA-TV 4 WIPR-TV 6
	KXGO-TV		1	WPRO-TV 12	Weslace	KRGV-TV 5	I	WKAQ-TV 2
			Cana	dian Tele	vision S	tations		
Location	C.L. C	han.	Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.
	BERTA		1	COLUMBIA	Penticton Prince George	CHBC-TV-2 13 CKPG-TV 3	Winnipes	CBWT 3 CBWFT 6
Burmis Calgary	CJLH.TV-	3 3 V 2		CFCR-TV-2 IC	Saddle Mounta	sin CHHC-TV-I 4		CJAY-TV 7
Drumheller	CHCT-T CFCN-T CFCN-TV	v á	Crescent Valley	CHAN-TV E	Trail	CBUAT II	NEW BRU	
	CBXT-T	٧ :	Enderby	CJDC-TV 5	Vernon	CHBC.TV-3 7	Campbelites Monetos	CRCD-TV 7 CKAM-TV 2
Edmonton Lethbridge	CFRN-T	V 7	Kamloons	CFCR-TV CHBC-TV		CHEK-TV 6	Saint John	CBAFT II CHSJ-TV 4
Lloydminster Medicine Hat	CHAT-T CHAT-T	V 6		CHGP-TV-1 72 CABC-TV-	LAB	BRADOR	Upsalquitch Lake	
Pivet Red Deer	CHCA-T	V E	Keremees	CHBC-TV-9 !	done bay	CFLA-TV 6	NEWFOU	NDLAND
	CHCA-TV-2	10	Nelson	CRUAT-TV-7	m A	NITOBA	Argentia	CJOX-TV 10
194 WHI	TE'S RADIO I	LOG	Oliver	CHBC-TV-3 8	Baldy Mountai	in CKOS-TV-I 8 CKX-TV 5		CBYT 5 Chek-tv 6

Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.
Grand Falls		Hamilton	CHCH-TV II	Windsor	CKLW-TV 9	Quebec	CFCM-TV 4
St. Jehn's	CJON-TV 6	Kapuskasing	CFCL-TV-I 8	Wingham	CKNX-TV 8	l	CKMI-TV 5
Stephenville	CFSN-TV 8	Kenera	CBWAT 8	DOINES	EDWARD	Rimouski	CJBR-TV 8
NOVA	COOTIA	Kingston	CKW8-TV II			Riviere du-Loup	CKRT-TV 7
NOVA	SCOTIA	Kitchener	CKCO-TV 13	l ISL/	AND	Rouyn	CKRN-TV 4
Antigonish	CFXU-TV 9	London	CFPL-TV 10	Charlottetown	CFCY-TV 13	Sherbrooke	CHLT-TV 7
Halifax	CBHT 3	North Bay	CKGN-TV 10 CKVR-TV-1 II			Three Rivers	CKTM-TV 18
,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,	CJCH-TV 5	Parry Sound Pembroke	CHOV-TV 5	QUE	BEC	CACHATO	LIEWALAN
Inverness	CJCB-TV-I 6	Peterborough	CHEX-TV 12	Carleton	CHAU-TV 5	SASKATO	MEWAN
Liverpool	CBHT-1 12	Ottawa	CBDFT 9	Carrotton	CJAO-TV-I 80	Cariyle Lake	CKDS-TV-2 7
New Glasgow	CFCY-TV-1 7	Ottawa	CBOT 4		CHSM-TV 7	East End	CJFB-TV 2
Shelburne	CBHT-2 8	l	CIDH-TV 13	Ciermont	ICFCV-TV-I 75	Moose Jaw	CHAB-TV 4
Sydney	CJCB-TV 4	Port Arthur	CKPR-TV-I 2	Esteourt	CJES-TV-1 70	Nigawin	CKBI-TV-4 2
(Yarmouth	CBHT-3 II	Sault Ste. Marie		Jongulere	CKRS-TV 12		CKBI-TV-1 2
ONI	ARIO	Sieux Lookeut	CHSL-TV 9	Matane	CKBL-TV 9		CKCK-TV 2
ONI	AKIO	Sturgeon Fails	CBFST 7	Montreal .	CBFT 2		CFQC-TV 8
Barrie	CKVR-TV II	Sudbury	CKSO-TV 5		CFCF-TV 12		CFJB-TV 5
Cornwall		Timmins	CFCL-TV 2			Val Marie	CJFB 2
Elk Lake		Toronto	CBLT 6			Wanganui	CKBI-TV-2 7
Elliot Lake	CKSO-TV-I 3	l	CFTO-TV 9	New Carlisle	CHAU-TV 5	Yorkton	CK08-T <u>V</u> Z

World-Wide Short-Wave Stations

Most international broadcasting is done within trequency limits agreed upon at international conventions. These frequency ranges are listed here, at the right, expressed both in frequency and by meter bands (wave-length).

Reception in the various bands varies according to the time of day and season of the year. Reception in the 60, 49 and 41 meter bands is best at night during the winter months. Reception in the 31 and 25 M. bands is best at night, but all year. Reception in the 19, 16, 13 and 11 M. bands is best during the day, also at night during the summer in the 16 and 19 M. bands. This listing includes only SWBC often heard in the U.S. and Canada, exclusive of those in the continental U.S.

Abbr.: AIR—All India Radio; RAI—Radiotelevisione Italiana; RTF—Radiodiffusion Television Française; VOA—Voice of America; RFE—Radio Free Europe. •denotes stations beaming evening (U.S. time) broadcasts to the U.S., †morning or afternoon broadcasts, V—varies.

Kes. Call and Location (cs. CGII GNG LOCCION 3245 YVKT, Caracas, Ven. 3255 ELBC, Monrovia, Liberia YVQL, El Tigre, Ven. 3265 ZFY Georgetewn, Br. Guiana 3280 W.I.B.S., Grenada, 3280 W.I.B.S., Grenada, Windward Is. 3285 H17T, Santo Domingo, D.R. 3290 H1/CQ, Bogota, Colombia 3295 YVOG, Trujiilo, Ven. 3300 B.H.B.S., Belize, Br. Honduras 3305 YVKX, Caracas, Ven. 3315 Fort de Franco, Martinique 3316 Frectown, Sierra Leone 3325 H15U, Santo Domingo, D.R. 3326 Kaduna, Niseria. 3925 H15U, Santo Domingo, D.I 3926 Kaduna, Nigeria 3935 YVLC, Valencia, Ven. 3936 Acera, Ghana 3975 H15B, Santiago, D.R. 3995 YVOJ, Merida, Ven. 4630 HCGBI, Quito, Eeu, 4725 Rangoon, Burma 4765 H1EF, Cali, Col. 4770 ELWA, Monrovia, Lib. 4770 ELWA, Monrovia, Lib. 4780 YVLA, Valencia, Ven. 4780 YVLA, Valencia, Ven. 4780 YVLA, Valencia, Ven. 4790 YVQN, Puerto La Cruz, Ven. 4805 ZYSS, Manaus, Braz. 4810 YVMG, Maracaibo, Ven. 4830 YVDA, San Cristobal, Ven. 4835 HJKE, Begeta, Cel.
4840v Leurence Marques, Mez.
4840 YVOi, Valera, Ven.
4845 HJGF, Bucaramanga, Cel.
4850 YVMS, Barquisimete,
Ven. 4870 Cotonou, Dahomoy Rep.
4880 YVKF, Caracas, Ven.
4895 Daker, Senegal
4895 ZYRZ2, Manaus, Braz.
4900 YVKE, Caracas, Ven.
4900 HJAC, Barranquilla, Cel.
4905 HRQN3, Puerte Certes, 4910 HCIMI, Quito, Ecua,
4910 Conakry, Guinea
4915 Acera, Ghana
4920 VLM4, Brisbano, Aus,
4920 YVKR, Caraess, Ven,
4935 HJLF, Ibague, Col.
4940 HCXZI, Guayaquil, Ecu,
4940 Abidjan, Ivory Coast
4940 YVMO, Barquisimeto,
Ven,
4945 HJCW, Rogeta Col. 4945 HJCW, Bogota, Col.
4945 Paradys, So. Afr.
4950 Dakar, Senegal
4950 YVMM, Coro, Ven.
4980 YVQA, Cumana, Ven.
4970 YVKK, Carcasa, Ven.
4972 Yaounde, Cameroon
4972 Radio La Cruz del Sur, La
4990 Lasos, Niseria 4990 Lagos, Nigeria 4990 YVMQ, Barquisimeto, Ven.

4995 CR6RZ, Luanda, Angela

1

Kcs. Call and Location

5010 HCRCX, Quite, Eeu.
5010 St. Georges, Windward Isl.
5020 Nismay, Nigar Bep.
5020 Nismay, Nigar Bep.
5030 YVKM, Caraeas, Ven.
5040 YVMM, Caraeas, Ven.
5050 YVKD, Caraeas, Ven.
5050 YVKD, Caraeas, Ven.
5053 YHGC Begota, Cel.
5875 Tegueigalpa, Hond.
5954 TiQ, Puerto Limen, C. R.
5952 TGNA, Guatemala, Guat.
5954 TiQ, Puerto Limen, C. R.
5960 HCF, Bogota, Col.
58809 YGAR, Guatemala, Guat.
5980 HDR, Port au Prince, Haiti
5983 Hilversum, Neth.
5980 HAB, Port au Prince, Haiti
5985 Hilversum, Neth.
5980 TGAR, Guatemala
5980 Habana, Cuba
5980 HAB, Port au Prince, Haiti
5985 Hort-de-France, Mart,
6000 RAIS, Berlin, Ger.
6015 PFAS, Recife, Braz,
6025 Muller, Germany
6035 HTL, Tegueigalpa, Hend.
6050 PAI, Caltanissetta, It.
6060 PAI, Caltanis, PAI
6070 PAI
6080 PAI
6090 P Kes. Call and Location 6090 Luxembourg, Lux.
6090 H12U, Santo Domingo, D.R.
6095 ZYBT, Sao Paulo, Braz.
6100 Belgrade, Yugo.
6105 X EQM, Merida, Mex.
6105 Cologne, Ger.
6110 BBC, London, Eng.
6115 ZYC7, Rie de Jan., Braz.
6120 LRXI, Buenos Aires
6120 4VEH, Cap Hartien, Haiti
6120 BBC, Limassol, Cyprus
6130 Port Moresby, New Guinea
6135 HRMF, La Celba, Hond.
6135 Papecte, Tahiti
6140 VLW6, Perth, Aus.
6145 RTF, Aliouis, France
6145 VPRL9, Rie de Jan., Braz.

Kes. Call and Location Kcs. Call and Location
6159 BEC, London, Eng.
6155 Wien, Austria
6155 FEN, Tokyo, Japan
6165 FEN, Tokyo, Japan
6160 Hik, J. Rogota, Col.
6160 Algiers, Algeria
6160 Saigon, S. Vietnam
6165 HERS, Bern, Switz.
6170 BEC, Jimassol, Cyprus
6170 BInsanore, Sing.
6170 VOA, Tanglers, Moroeco
6175 RTF, Allouis, France
6175 Cayenra, Fr., Guiana
6165 Lisben, Pert.
6185 HJCT, Bagota, Col.
6195 HIEZ, Call, Col.
6195 BEC, London, Eng.
6195 Pyongyang, N. Korea
6195 Andorra, Andorra
6200 4VHW, Port.au-Prince,
6200 4VHW, Port.au-Prince,
6305 Andorra, Andorra G305 Andorra, Andorra
G305 Andorra, Andorra
G305 Yohran, Iran
T105 Wadrie, Spain
T110 VOA, Colombo, Ceylon
T110 VOA, Colombo, Ceylon
T110 BBC, London, England
T115 Rabat, Morocco
T120 BBC, London, England
T125 Warsaw, Poland
T125 Warsaw, Poland
T145 Bamako, Mail
T150 Woscow, U.S.S.R.
T155 VOA, Tangiers, Moro.
T160 RTF, Paris, France
T170 Algiers, Alg.
T180 Bashdad. Iran 7160 RTF, Paris, France
7165 RFF, Germ.
7170 Alglers, Alg.
7180 Bashdad, Iraq
7180 Moscow, U.S.S.R.
7185 BBC, London, Eng.
7185 BBC, London, Eng.
7185 Paradys, So. Africa
7193 Bucharest, Roumania
7200 R. Malaya, Sing.
7205 YOA, Salonika, Gr.
7210 Dakar, Mail Fed.
7215 Trans World Radio, Monaco
7220 BUGAgest, Hung.
7230 BBC, London, Eng.
7240 RTF, Paris, France
7250 BBC, London, Eng.
7240 RTF, Paris, France
7255 Salger, Vietnam
7275 Mola, Sweden
7275 RAI, Rome, It.
7280 Moscow, U.S. S.R.
7290 RAI, Rome, It.
7290 Moscow, U.S. S.R.
7290 RAI, Rome, It.
7295 RFE, Ger.
7295 RFE, Ger.
7295 RFE, Ger.
7240 RTS. 7295 Marassar, Colober 7295 RFE, Ger. 7340 Moscow, U.S.S.R. 73989 Damascus, U.A.R. 7480 Poking, China 7650 YNMS, Leon, Nic. 8016 Beirut, Lebanon 9009 Tal Aziw, Israel

Aviv. Israel BC. Habana, Cuba

9009 Tel A 9360 COBC

9360 COBC. Habana, CU 9360v Madrid, Spain ● 9380v Madrid, Spain 9410 BBC, London, Eng, 9440 CP38, La Paz, Bol.

METER BANDS

4750 to 5060 kc/s (60 meter band)
5950 to 6200 kc/s (49 meter band)
7 100 to 7300 kc/s (41 meter band)
9500 to 9775 kc/s (31 meter band)
11700 to 11975 kc/s (25 meter band)
15100 to 15450 kc/s (19 meter band)
17700 to 17900 kc/s (16 meter band)
21450 to 21750 kc/s (11 meter band)
25600 to 26100 kc/s (11 meter band)

Kcs. Call and Location 9480 Paking, China
9481 Hisu, Santo Domingo, D.R.
9500 Magadan, U.S.B.R.
9500 Moscow, U.S.B.R.
9500 Moscow, U.S.B.R.
9505 PRBZ2, Sao Paulo, Braz.
9505 Pabz, Mor.
9506 Pabz, Mor.
9507 Pabz, Mor.
9508 Pabz, Mor.
9508 Pabz, Mor.
9509 Papz, Mor.
9510 London, England
9510 London, England
9510 London, England
9510 London, England
9510 Papz, Mor.
9520 Popenhagen, Den. e
9520 Port Moresby, New Guinea
9520 OAXEE, Iouitos, Peru
9520 Port Moresby, New Guinea
9520 OAXEE, Iouitos, Peru
9520 Port Moresby, New Guinea
9520 Part Moresby, New Guinea
9520 OAXEE, Iouitos, Peru
9520 Part Moresby, New Guinea
9530 AVAR, Delhi, India
9530 VOA, Courier, Rhodes
9530 VOA, Courier, Switz. e
9535 VDA, Manila, P.I.
9535 HEAR, Delhi, India
9530 VOA, Courier, Switz. e
9540 XL2, Wellington, N.Z.
9540 Kababovsk, N.S.S. R.
9540 Kababovsk, N.S.S. R.
9540 Kababovsk, N.S.S. R.
9553 KTT, Mexice City, Mox.
9553 VSS, San Salvador, E. S.
9550 KETT, Mexice City, Mox.
9565 ZYKS, Reeife, Braz.
9563 OAXER, Lima, Peru
9565 Calombo, Ceylon
9565 Calombo, Ceylon
9565 VAS, Reeife, Braz.
9580 VLAS, Melbourne, Aus.
9580 VLAS, Melbourn

```
Kcs. Call and Location

15220 Hilversum, Neth. †

15225 Taipei, Taiwan, China

15230 VOA, Colombo, Ceylon

15230 BBC, London, Eng.

15235 Beirut, Lebanen

15235 Feirut, Lebanen

15235 Feirut, Lebanen

15240 VLB15, Melbourne, Aus.

15240 Herby, Sweden

15240 Herby, Sweden

15240 Beigrade, Yugoslavla

15245 ZYE21, Beigen, Brazil

15245 ZYE21, Beigen, Brazil

15245 Leopoldville, Congo Rep.

15250 Bucharest, Rumania e

15255 VOA, Melolos, P. 1.

15250 Bucharest, Rumania e

15255 YOA, Munich, Ger.

15275 Varsaw, Poland e

15285 Pague, Czech, Mor.

15280 FEN, Tokyo, Japan

15285 Pague, Czech, Mor.

15290 VOA, Tanglers, Mor.

15290 VOA, Tanglers, Mor.

15290 VOA, Tanglers, Mor.

15290 Seirut, Lebanon

15295 Pague, Czech, Mor.

15295 NHK, Tokyo, Japan

15295 Cologne, Germany

15390 BBC, London, Eng. f

15300 Ducharest, Roumania

15391 AlR, Delhi, India

15310 AlR, Delhi, India

15315 VLC15, Melbourne, Aus.

15310 VOA, Munich, Ger.
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 RCs. Call and Location

11925 HLK6, Seoul, Kerea †
11925 Warsaw, Pel.
11925 Tashkent, U.S.S.R.
11930 BBC. London, Eng.
11935 Radio Liberty, Ger.
11940 ZPAS, Encarnation, Par.
11940 ZPAS, Encarnation, Par.
11940 Edit Colored, China
11945 Peking, China
11945 BBC, London, Eng.
11945 Cologne, Germany e
11945 BBC, London, Eng.
11950 Hilversum, Neth,
11950 BBC, London, Eng.
11950 BBC, Singapore
11960 CE1196, Santiage, Ch.
11960 Cenakry, Guinea
11965 Radio Liberty, Ger.
11965 Radio Liberty, Ger.
11975 Peking, China
11975 ELWA, Monrovia, Liberia
11980 Mescew, U.S.S.R.
12055 Peking, China
11975 Peking, China
11975 BBC, London, Eng.
12050 Miscew, U.S.S.R.
12055 Peking, China
12050 Libbon, Port,
12065 BBC, London, Eng.
15070 BBC, London, Eng.
15080 Melbourne, Australia
15085 St. Georges, Windward Isl.
15085 Paradys, So, Africa
                   Rcs. Call and Location
9640 Acera, Ghana
9640 HLK5, Seoul, Korea
9645 TIFC, San Jose, C.R.
9645 HVJ, Vatican City
9650 BBC, Limassol, Cyprus
9650 Mescow, U.S.3.R.
9650 Amman, Jordan
9655 Radie Free Europe, Ger.
9860 LRX, Buenos Aires, Arg.
9660 V.109, Brisbane, Aus.
9860 Radie Liberty, Gar.
9860 Mescow, U.S.S.R.
9667 Hargeisa, Somalia
9677 BGC, COCQ, Havana, Cuba
9678 BBC, London, Eng.
9675 NHK, Tokyo, Japan
9680 V.109, Melbourne, Aus.
9680 YEQQ, Mexico City, Mex.
9680 LRA32, Buenos Aires,
9680 LRA32, Buenos Aires,
9690 LRA32, Buenos Aires,
9690 RBC, Leaden, Eng.
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 Kcs. Call and Location
              Kcs. Call and Location
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                Kcs. Call and Location
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       Kcs. Call and Location
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                1730 LRA35, Buenes Arles, Arg.
1735 Rabat, Morocco
1735 Rabat, Morocco
1735 Rabat, Morocco
1735 Rabatorvsk, U.S.S.R.
1740 VLCII, Melbourne, Aus.
1740 CE1174, Santiago, Chile
1740 CE1174, Santiago
1740 CE1174, Santiago
1740 CE1174, Santiago
1740 CE1174, Santiago
1740 CE1174, Congo
1750 BBC, London, Eng.
1750 BBC, Singagore
1750 FEN, Tokyo, Japan
1755 FE, Europe
1755 Hilversum, Neth.
1755 Lago
1755 Lago
1756 VLBII, Melbourne, Aus.
1766 Copoldville, Congo Rep.
1760 VLBII, Melbourne, Aus.
1765 CAPS, La Paz. Bolivia
1765 Saven, E., Germany
1770 VOA, Munich, Germany
1770 VOA, Munich, Germany
1775 ZY228, Rio de Jan., Braz.
1780 VAK, Tokyo, Japan
1785 Ojakarta, Indon,

9895 Lisbon, Port.
9885 Havana, Cuba
9690 LRA32, Buenes Alres,
9690 BBC, Lendon, Eng.
9690 BBC, Singapore
9700 Sofia, Bulgaria 9
9700 Leopoldville, Conge Rep.
9700 Leopoldville, Conge Rep.
9705 Kabul, Afghan.
9710 RBC, London, Eng.
9710 RAI, Reme, It.
9720 Mescow, U.S.S.R.
9725 Europe
9725 BBC, London, England
9730 Brazzaville, Conge Rep.
9730 Leipzig, E. Ger.
9730 DZHZ, Manila, P.I.
9735 Colegne, Germany
9730 HZT, Santo Domingo, D.R.
9740 Lisbon, Port.
9740 Khabarovsk, U.S.S.R.
9745 Brussels, Belg.
9745 FYW23, Geiania, Braz.
9755 ZYW23, Geiania, Braz.
9755 ZYW23, Geiania, Braz.
9755 ZYW23, Geiania, Braz.
9756 HAbana, Cuba
9760 BBC, London, Eng.
9970 Brazzaville, Conge Rep.
9770 WEH, Cap Haltlen, Halti
9772 Oario, Enypt
9785 Peking, China
9815 St, Georges, Windward Isl.
9825 BBC, London, Eng.
9833 Budapest, Hung, ©
9840 Hanol, N, Vietnam
9840 Peking, China
1940 Peking, China
1950 Peking, China
1951 Harbon, China
1170 Disherta, Indonesia
1170 Disherta, Indonesia
1170 Disherta, Indonesia
1170 BBC, Limassel, Cyprus
11715 Brazzaville, Conge Rep.
11725 Prague, Czecho,
11730 Hiversum, Neth.
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 Arg. •
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   15070 BBC, London, Eng.
15080 Mobbourne, Australia
15085 St. Georges, Windward Isl.
15085 Paradys, So. Africa
15085 Peking. China
15105 AIR, Oehili, India
15100 XERR, Mexico. D. F., Mex.
15115 Peking. China
15110 XERR, Mexico. D. F., Mex.
15115 Peking. China
15120 Colombo. Ceylon
15120 RAI. Rome. Italy
15120 Warsaw. Poland †
15120 Warsaw. Poland †
15120 Warsaw. Poland †
15120 Filsbon. Portugal e
15130 RTF, Allouis, France
15135 PRB23, Sac Paulo, Braz.
15135 NHK, Tekyo, Japan
15135 PRB23, Sac Paulo, Braz.
15145 Peking. China
15140 BBC. London. Eng.
15145 Peking. China
15140 BBC. London. Eng.
15153 DAX4T, Lima, Peru
15155 ELWA, Monrovia, Libe.
15155 Peking. China
15155 ELWA, Monrovia, Libe.
15155 Peking. China
15155 VOA, Melelos, P. I.
15160 XEWW. Mexico City, Mex.
15160 XEWW. Mexico City, Mex.
15160 XEWW. Mexico City, Mex.
15160 Tromso. Norway
15165 ZYN7, Fortloza, Braz.
15160 Agharra, Turkey
15160 Molbourne, Australia
15170 Sadio Free Europe, Port.
15173 Dislo. Norway e
15190 Molbourne, Australia
15180 VOA, Poro, P. I.
15185 Radio Free Europe, Port.
15190 Molsow. USSR
15193 Radio Free Europe, Port.
15190 Holsinki, Finiand †
15190 Molsow. USSR
15193 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
15210 ZPA7, Asunelon, Paraguay
15215 Radio Free Europe, Port.
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                            15315 HEU6, Bern, Switz. e
15325 ZYR228, Sao Paulo, Braz.
15330 VDA, Munich, Germany
15330 VDA, Pero, P. I.
15335 VOA, Pero, P. I.
15335 VOA, Pero, P. I.
15340 Radio Liberty, Germany
15340 Habana, Cuba
15343 Talpei, Talwan, China
15343 Talpei, Talwan, China
15340 Luxembourg, Lux.
15350 Luxembourg, Lux.
15350 Luxembourg, Lux.
15370 ZYCS, Rie de Jan., Braz.
15370 ZYCS, Rie de Jan., Braz.
15375 BEC. London. Es.
15385 CAXA60, Manita, P. I.
15385 VAXA60, Manita, P. I.
15395 Radio Liberty, Germany
15405 Celopne, Germany
15405 Hilversum, Neth.
15406 VAA, Munich, Germany
15465 Paramaribo, Surinam
15475 Cairo, IIAR
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 15460v PZC, Paramariob.
Surinam
15465 Paramaribo, Surinam
15475 Cairo, UAR
15355 Pokine, China
17705 Luanda, Angola
17725 ZYR232, San Jose Dos
Campos, Brazil
17740 Pekine, China
17745 Aecra, Ghana
17780 BBC, London, England
17790 BBC, London, England
17790 BBC, London, England
17805 Brussels, Belgium
17865 Brussels, Belgium
17865 Brussels, Belgium
17865 Drussels, Portugal
17880 Lisbon, Portugal
17890 Cairo, Egypt
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           11910 Bungkok, Thai.
11915 HC/B, Quito Ecua. •
11915 Cairo, Egypt
11920 DXF2, Manila, P.I.
11920 AIR, Delhi, India
11925 ZYR78, Sao Paulo, Braz.
                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           17900 Cairo, Egypt
21620 Habana, Cuba
              11725 Prague, Czecho.
11730 Hilversum, Neth.
```

Canadian Short-Wave—Domestic and International

*Transmitter at Sackville, New Brunswick

Kc. C.L. Location	Kc. C.L. Location	Kc. C.L. Location	Kc. C.L. Location
5970 CBNX St. John's, Nfid.	6130 CHNX Halifax, N.S.	11705 CBFY Montreal, Que.	15190 CKCX Montreal, Que,*
5970 CKNA Montreal, Que.*	6160 CBUX Vancouver, B.C.	11705 CKXA Montreal, Que.*	15255 CKSR Montreal, Que.*
5990 CHAY Montreal, Que,*	6160 CHAC Montreal, Que.*	11720 CBFL Montreal, Que.	15275 CKBR Montreal, Que,*
6005 CFCX Montreal, Que.	9520 CBFR Montreal, Que,	11720 CHOL Montreal, Que.*	15320 CKCS Mentreal, Que.*
6010 CJCX Sydney, N.S.	9585 CKLP Montreal, Que.*	11760 CBFA Montreal, Que,	17710 CHSB Montreal, Que.º
6030 CFVP Calgary, Alta.	9610 CBFX Montreal, Que.	11760 CKRA Montreal, Que.*	17735 CHRX Montreal, Que.º
6060 CKRZ Montreal, Que."	9610 CHLS Montreal, Que.*	11900 CKEX Montreal, Que.*	17820 CKNC Montreal, Que.*
6070 CFRX Toronto, Ont.	9630 CBFO Montreal, Que.	11945 CKEX Montreal, Que.*	
6080 CKFX Vancouver, B.C.	9630 CKLO Mentreal, Que.*	15090 CKLX Montreal, Que.*	17865 CHYS Montreal, Que.*
6090 CBFW Montreal, Que.	9710 CHLR Montreal, Que.	15105 CKUS Montreal, Que.*	21600 CKRP Montreal, Que.*
6090 CKOB Montreal, Que.*	9740 CHFO Montreal, Que.*	1 15190 CBFZ Montreal, Que.	21710 CHLA Montreal, Que.*

RADIO-TV EXPERIMENTER —NOW QUARTERLY— Summer '63 Edition on Sale April 4

PICK THE CAREER YOU WANT IN THE WONDERFUL FIELD OF ELECTRONICS TRAIN AT HOME WITH THE LEADER

INDUSTRIAL ELECTRONICS TELEVISION-RADIO SERVICING (INCLUDES COLOR TV)



Prepares you to be an Electronic Technician in industry, business, government, military. Computers, telemetry, automation, missiles. rockets are changing our world. Course includes illustrated lessons, special training equipment sent at no extra cost.



Learn to fix radios. TV sets, hi-fi, etc. Earn spare-time inoney starting soon after enrolling. Train for money-making opportunities in your own spare-time or fulltime business or working for someone else. Special training equipment included.

TV-RADIO COMMUNICATIONS



Get actual experience as NRI prepares you for a choice of Communications fields and an FCC License. Broadcasting, microwave, radar, mobile and marine radio, navigation devices are some subjects covered. Special training equip-

FCC COMMERCIAL LICENSE



For men who want to operate or service transmitting equipment used in communications or to work on C-Band. From Simple Circuits to Broadcast Operation, this new NRI course trains you quickly for your Government exams.

Job Counselors Advise Electronics

A career in Electronics offers unlimited opportunity to men who qualify. When you train at home through NRI, there's no need to give up your job or go away to school. And there are no special requirements of previous Electronics experience or education. Train with the leader Your NRI training is backed by nearly 50 years of success Mail the postage-free card. National Radio Institute, Washington 16, D. C.

SEE OTHER SIDE

Cut Out and Mail—No Stamp Needed	Cut	Out	and	Mail—No	Stamp	Needed
----------------------------------	-----	-----	-----	---------	-------	--------



NATIONAL RADIO INSTITUTE Washington 16, D. C.

Please send me your Electronic, Radio-TV catalog without cost or obligation. I am interested in course checked below. (No salesman

will call. PLEASE PRINT.) ☐ FCC License Industrial Electronics

- Radio-TV Servicing
- Communications

Name

Address_____

_____Zonc____State_____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Approved for Veterans under Korean GI Bill

turn your hobby into a new and PROFITABLE CAREER in the fast growing field of ELECTRONICS you should investigate the NRI Home-Study Courses in Industrial Electronics, Radio-TV Servicing, Radio-TV Communications

There is an immediate and growing need for trained Technicians in many branches of Electronics. Better-than-average jobs await you. Join the thousands of NR1 graduates who have benefited from new careers in this Electronic Age. Mail postage-free card.

Turn Page for More Facts

FIRST CLASS PERMIT NO. 20-R (Sec. 34.9, P.L.&R.) Washington, D.C.

To assure ADVANCEMENT or to

BUSINESS REPLY MAIL NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY



3939 Wisconsin Avenue Washington 16, D.C.

Qualify for Higher Pay

You must be trained to qualify for higher earnings and advancement. Whichever branch of Electronics you select, you'll find that NRI training is the time-proved way to get ahead this interesting, growing industry



Training Equipment Included

Learn Electronics through "learn-bypractice" methods. At no extra cost, NRI sends special equipment that gives actual experience, makes theory easy-to-grasp, interesting. All equipment is yours to keep.



Oldest and Largest School

As the oldest and largest homestudy school of its kind, NRI can supply training at reasonable cost. Monthly payment plans. Mail postage-free card for NRI CATALOG. National Radio Institute, Washington 16, D. C.

Mail Postage-Free Card