

JAN. 31  
1931

*Converter With B Supply*

15 Cents  
Per Copy

# RADIO

REG. U.S. PAT. OFF.


# WORLD

The First and Only National Radio Weekly

462d Consecutive Issue—NINTH YEAR

PICTURE  
DIAGRAM  
OF I-A UNIT  
SW CONVERTER

## A FULLY FILTERED CIRCUIT

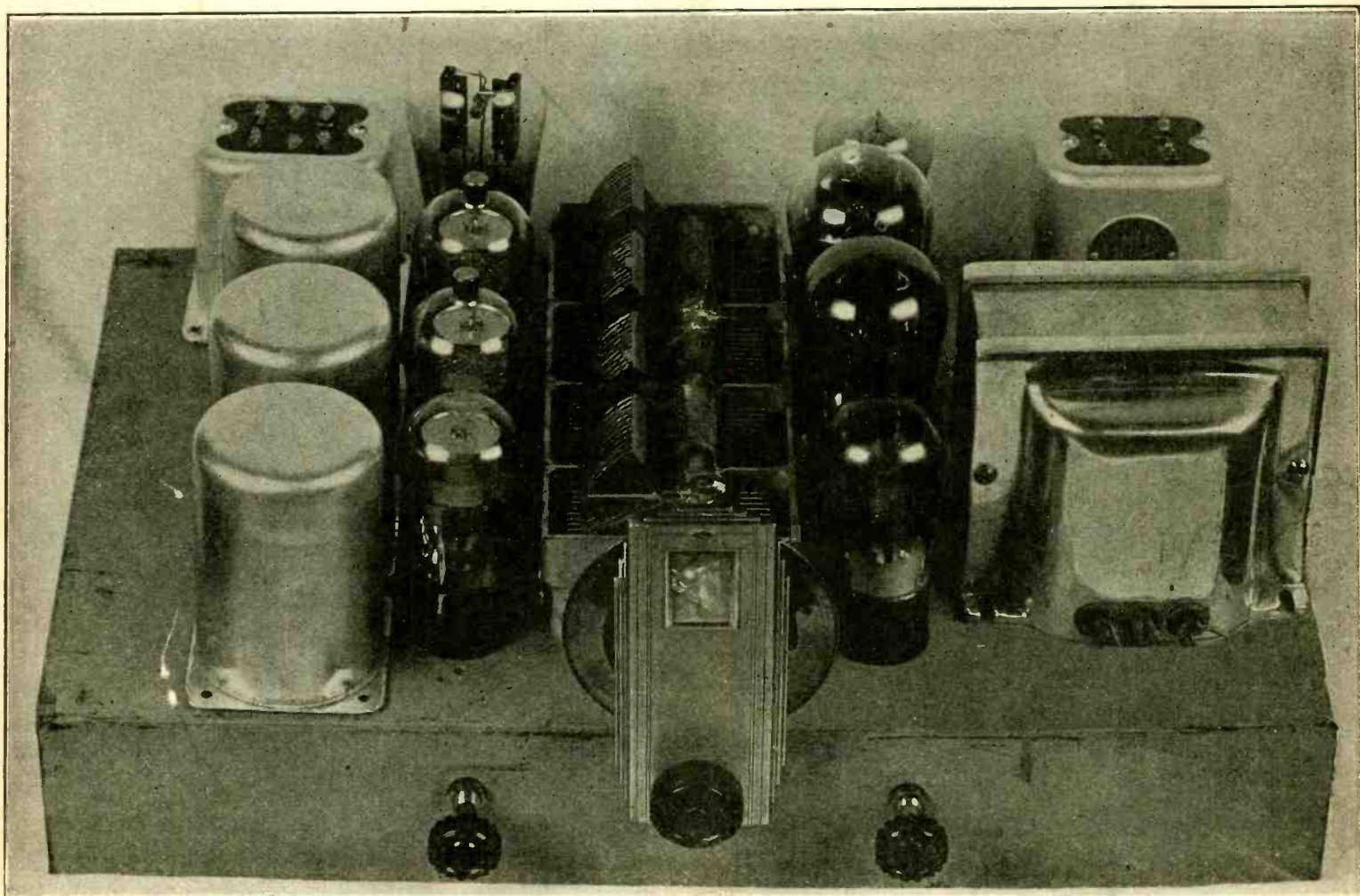

See Pages 12 and 13 for Construction of the Fully Filtered Circuit

RADIO WORLD, Published by Hennessy Radio Publications Corporation, Roland Burke Hennessy, editor; Herman Bernard, managing editor and business manager, all of 145 West 45th Street, New York, N. Y.



# Why Not "Money Back" on Tubes?

## Any Lesser Guarantee Inadequate in Present Market



Standard 201A with UX base.



227 detector and BF audio amplifier.



The AC adapter tubes permit changing a battery set to AC operation, as binding posts permit extra connections. For 226, 227 or 171A.

THE economic depression and resultant predicament of some tube manufacturers have resulted in the dumping on the market of tubes of inferior calibre, tubes that failed in the factory test for "firsts," and were sold to distress merchandise operators "as is" at a few cents apiece. These tubes often are in private brand cartons, but do not bear the name of the real manufacturer.

Rextron tubes are made by Rextron.

The estimate a manufacturer places on his tubes in the present chaotic tube market is well measured by the guarantee that backs up the tube. Replacement guarantees are encouraging but not conclusive. Nothing less than "money-back" will do now. Rextron tubes are sold on a 10-DAY MONEY-BACK GUARANTEE. Use them ten days. If not fully satisfied, return the tubes and your money will be refunded at once.

### Red-Hot Speed in Shipments!

#### GENERAL AND SPECIAL PURPOSE TUBES

(Cat. RX-1)—201A, detector, amplifier, 1/4 amp. filament	\$1.00
(Cat. RX-2)—226, amplifier for 1 1/2-v. AC on filament	1.00
(Cat. RX-3)—227, detector, amplifier; 2 1/2-v. AC on heater	1.00
(Cat. RX-4)—171A, power tube, 1/4 amp. filament; battery operation	1.00
(Cat. RX-5)—171, power tube, 1/2 amp. filament; AC	1.00
(Cat. RX-6)—240, high mu tube; battery operation	1.00
(Cat. RX-7)—120, power tube for dry cell operation	1.00
(Cat. RX-8)—UX199, detector, amplifier; long prongs	1.00
(Cat. RX-9)—UV199, detector, amplifier; short prongs	1.00
(Cat. RX-10)—112, power tube, 1/2 amp. fil.; AC operation	1.00
(Cat. RX-11)—112A, power tube, 1/2 amp. fil.; battery operation	1.00
(Cat. RX-12)—200A, special detector; highly sensitive	1.00
(Cat. RX-13)—224, screen grid AC tube; 2 1/2-v. AC on heater	1.00
(Cat. RX-14)—245, power tube for AC operation	1.00
(Cat. RX-15)—201A special RF amplifier	1.00
(Cat. RX-16)—201A special detector	1.00
(Cat. RX-17)—201A special audio amplifier for transformer	1.00
(Cat. RX-18)—201A special AF amplifier for resistance or impedance	1.00
(Cat. RX-19)—201A switch type; if one filament burns out switch on the other	1.00
(Cat. RX-20)—112 switch type	1.00
(Cat. RX-21)—171 switch type	1.00
(Cat. RX-22)—226 adapter; for converting battery sets to AC	1.00
(Cat. RX-23)—227 adapter; for converting battery sets to AC	1.00
(Cat. RX-24)—171A adapter; for converting battery sets to AC	1.00
(Cat. RX-25)—WD12, detector, amplifier; dry cell operation	1.00
(Cat. RX-26)—250, power tube; for AC operation	2.95
(Cat. RX-27)—201A, shield tube, completely bakelite encased	2.00
(Cat. RX-28)—222, screen grid tube, for battery operation	2.10
(Cat. RX-29)—Teflon television neon gas tube	3.85
(Cat. RX-30)—Photo-electric cell, 2 inches	4.50
(Cat. RX-31)—210, power tube; for AC operation	2.95

#### RECTIFIER AND CHARGER BULBS

(Cat. RX-33)—2 ampere charger bulb, old style; top connector	2.85
(Cat. RX-34)—2 ampere charger bulb; new style, base connector	2.85
(Cat. RX-35)—5 ampere charger bulb; top connector	4.95
(Cat. RX-36)—6 ampere charger bulb; top connector	4.95
(Cat. RX-37)—280 full wave rectifier	1.00
(Cat. RX-38)—281 half wave high wattage rectifier	2.95
(Cat. RX-39)—Rectifier for Freshman Master B Eliminator	1.00



The 2-ampere charger, new type.




The 2-ampere charger, with a connector at top.




High capacity charger, for 5 and 6 amperes.



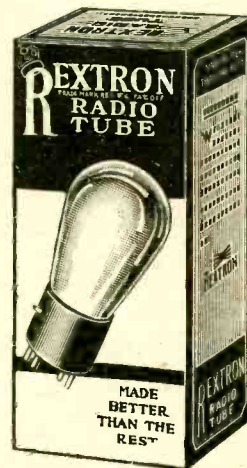
High-mu tube for battery operation, equivalent to the 240, but listed as 201A high mu.



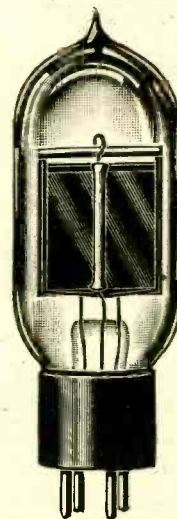Each tube is packed in an especially rugged and secure carton as precaution against damage in transit. We—NOT YOU—run the damage risk.



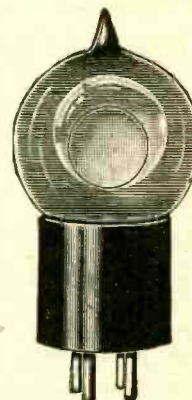One of the most popular tubes for television is the Teflon, a neon gas tube.



2-inch photo-electric cell for television transmission and for film recording of sound.

**RELIABLE RADIO CO.**  
145 West 45th Street, New York, N. Y.

Enclosed please find \$..... for which ship at once, on a 10-day money-back guarantee, the tubes checked off on list below:

- |  |   |   |   |
|--|---|---|---|
| <input type="checkbox"/> RX-1 @ \$1.00 | <input type="checkbox"/> RX-11 @ \$1.00 | <input type="checkbox"/> RX-21 @ \$1.00 | <input type="checkbox"/> RX-31 @ \$2.95   |
| <input type="checkbox"/> RX-2 @ 1.00   | <input type="checkbox"/> RX-12 @ 1.00   | <input type="checkbox"/> RX-22 @ 1.00   | <input type="checkbox"/> RX-33 @ 2.85     |
| <input type="checkbox"/> RX-3 @ 1.00   | <input type="checkbox"/> RX-13 @ 1.00   | <input type="checkbox"/> RX-23 @ 1.00   | <input type="checkbox"/> RX-34 @ 2.85     |
| <input type="checkbox"/> RX-4 @ 1.00   | <input type="checkbox"/> RX-14 @ 1.00   | <input type="checkbox"/> RX-24 @ 1.00   | <input type="checkbox"/> RX-35 @ 4.95     |
| <input type="checkbox"/> RX-5 @ 1.80   | <input type="checkbox"/> RX-15 @ 1.00   | <input type="checkbox"/> RX-25 @ 1.00   | <input type="checkbox"/> RX-36 @ 4.95     |
| <input type="checkbox"/> RX-6 @ 1.00   | <input type="checkbox"/> RX-16 @ 1.00   | <input type="checkbox"/> RX-26 @ 2.95   | <input type="checkbox"/> RX-37 @ 1.00     |
| <input type="checkbox"/> RX-7 @ 1.00   | <input type="checkbox"/> RX-17 @ 1.00   | <input type="checkbox"/> RX-27 @ 2.00   | <input type="checkbox"/> RX-38 @ 2.95     |
| <input type="checkbox"/> RX-8 @ 1.00   | <input type="checkbox"/> RX-18 @ 1.00   | <input type="checkbox"/> RX-28 @ 2.10   | <input type="checkbox"/> RX-39 @ 1.00     |
| <input type="checkbox"/> RX-9 @ 1.00   | <input type="checkbox"/> RX-19 @ 1.00   | <input type="checkbox"/> RX-29 @ 3.85   | <input type="checkbox"/> C. O. D. desired |
| <input type="checkbox"/> RX-10 @ 1.00  | <input type="checkbox"/> RX-20 @ 1.00   | <input type="checkbox"/> RX-30 @ 4.50   |   |

Name .....  
Address .....  
City ..... State .....





**BROADCASTING**  
**TELEVISION**  
**TALKING PICTURES**  
**WIRELESS OPERATING**

# WIN FAME and FORTUNE in **RADIO!**

Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to make real money in Radio—the fastest-growing, biggest money-making game on earth!

**THOUSANDS OF JOBS ARE OPEN**  
**Paying \$60, \$70 and on up to \$200 a Week**

Jobs as Designer, Inspector and Tester, paying \$3,000 to \$10,000 a year—as Radio Salesman and in Service and Installation Work, at \$45 to \$100 a week—as Operator or Manager of a Broadcasting Station, at \$1,800 to \$5,000 a year—as Wireless Operator on a Ship or Airplane, as a Talking Picture or Sound Expert—THOUSANDS of JOBS Paying \$60, \$70 and on up to \$200 a WEEK!

## Learn Without Lessons *in* 10 Weeks

You learn ALL branches of Radio at Coyne—in 10 short, pleasant weeks—NOT BY CORRESPONDENCE, but by actual work on actual Radio, Television and Sound equipment. We don't waste time on useless theory. We give you just the practical training you will need—in 10 weeks' time.

**No Books - No Lessons**  
**All Practical Work at Coyne**

Coyne is NOT a Correspondence School. We don't teach you from books or lessons. We train you on the greatest outlay of Radio, Television and Sound equipment in any school—on scores of modern Radio Receivers, huge Broadcasting equip-

ment, the very latest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you—right here in the Coyne Shops—all the actual practice and experience you'll need.

### **TELEVISION** *Is Now Here!*

And TELEVISION is already here! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television NOW can make a FORTUNE in this great new field. Get in on the ground-floor of this amazing new Radio development! Learn Television at COYNE on the very latest, newest Television equipment.

### **Talking Pictures** *A Great Field*

Talking Pictures and Public Address Systems offer thousands of golden

opportunities to the Trained Radio man. Here is a great new field of Radio that has just started to grow! Prepare NOW for these marvelous opportunities! Learn Radio Sound Work at Coyne, on actual Talking Picture and Sound Reproduction equipment.

### **Coyne is 32 Years Old**

Don't worry about a job! Coyne Training settles the job question for life. You get Free Employment Help as long as you live. And if you need part-time work while at school to help pay expenses we'll gladly help you get it. Coyne is 32 years old! Coyne Training is tested—proven beyond all doubt. You can find out everything ABSOLUTELY FREE. JUST MAIL COUPON FOR MY BIG FREE BOOK.

H. C. Lewis, Pres. **Radio Division** **Founded 1899**  
**Coyne Electrical School**  
**500 S. Paulina Street Dept. 11-9P, Chicago, Illinois**


H. C. LEWIS, President  
**Radio Division, Coyne Electrical School**  
 500 S. Paulina St., Dept. 11-9P, Chicago, Ill.

Send me your Big Free Radio Book and all details of your Special Introductory Offer. This does not obligate me in any way.

Name.....  
 Address.....  
 City..... State.....



**SCREEN GRID SHIELDED COIL, \$1.50**

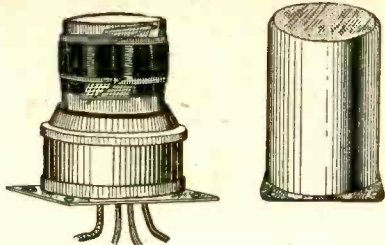


THESE shielded coils are especially suitable for screen grid circuits, but are adaptable also to other circuits.

They consist of a secondary wound on a 1 3/4" diameter bakelite tubing, a layer of moisture-proof insulating fabric, and primary wound over the secondary. The bakelite tubing is firmly embedded in a veneered base, to which an aluminum plate is attached at bottom, punctured to pass outlets and to coincide with mounting holes of the aluminum shield. The shield size is 2 11/16" x 2 11/16" x 3/8". The mounting method keeps the walls of the shield equi-distant from the coil. The outlets are: shielded wire lead to plate, red lead to B plus, dark blue lead to grid and yellow to ground. When the coil is used as antenna coupler a fixed condenser of .00025 mfd. should be in series with the aerial. The connections would be: shielded wire to fixed condenser, red and yellow both to ground and dark blue to grid. The coils are marked in matched sets of four. Thus they are of precision type, necessary for fully effectiveness from gang tuning.

The primaries are of high impedance and the coupling to the secondary is very tight. These features are desirable for high gain in multi-stage screen grid circuits. However, for circuits using other tubes, the primary turns may be easily reduced by the user to 10 turns, by cutting the primary wire near where it enters the insulating cloth, and unwinding all but 10 turns, cutting and then soldering the two wires together.

- For .0005 mfd. tuning order Cat. 40-70.....@ \$1.50
- Matched set of four for .0005 mfd. Cat. 40-70MF \$5.00
- For .00035 mfd. tuning order Cat. 40-80.....@ \$1.50
- Matched set of four for .00035 mfd. Cat. 40-80MF \$5.00

**DYNAMIC TUNER ASSEMBLY, \$1.25**

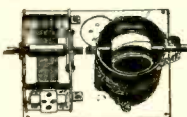

A TUNING condenser with a dynamic coil to match, mounted on an aluminum base that has socket built in. The condenser shaft goes in a dial (not furnished). The tuned circuit includes a fixed and a movable winding (rotor coil) in series. The moving coil is used as a trimmer, set once and left thus, so two separate tuning dials are made to read alike, or gang tuning is made practical. No equalizing condensers needed. Do not couple the adjoining shafts.

- For antenna circuit input to any tube fitting four-prong UX socket, or for interstage coupling for 226, 201A, 199, 240 or 230, but NOT interstage for 232 or 222, order cat. BT-L-DC @ \$1.25
- For interstage coupling for 232 and 222, order cat. BT-R-DC @ \$1.25
- For antenna circuit, as RF input to any five-prong tube, order cat. BT-L-AC @ \$1.25
- For interstage coupling for 224, order cat. BT-R-AC @ \$1.25

**DYNAMIC RF COIL, 75c**

THE dynamic coil for either .0005 mfd. or .00035 mfd. tuning. The same coil serves either capacity, as the series rotor may be set in position to increase or reduce the total secondary inductance.

- For antenna coil, all circuits, and interstage coupling for all tubes except screen grid, order cat. BT-3A @ 75c
- For interstage coupling from plate circuit of screen grid tube order cat. BT-3B @ 75c

**DIAMOND PAIR COILS, \$1.20**



The Diamond of the Air is a popular circuit using an antenna coil and a three-circuit tuner. For this circuit the standard Diamond pair of coils consists of two, wound on 3" diameters, except for rotor on smaller form. The standard pair may be obtained for .0005 or .00035 mfd. tuning. Tickler coil has single hole panel mount.

- For .0005 mfd. order SDP-5.....@ \$1.20
  - For .00035 mfd. order SDP-35.....@ \$1.20
- These coils will give extreme satisfaction and are excellent for the Diamond of the Air, being specified by Herman Bernard, the designer of the circuit.

**OTHER COILS**

- (Cat. 5-HT)—Special three-circuit tuner for .0005 mfd. tuned primary in plate circuit of a screen grid tube; untuned secondary.....\$ .95
- (Cat. 3-HT)—Same as Cat. 5-HT, except that it is for .00035 mfd. tuning.....\$ .95
- (Cat. T-5)—Standard 3-circuit tuner for .0005 mfd. where primary is for any type of tube other than plate circuit of screen grid tube.....\$ .80
- (Cat. T-3)—Same as T-5, except for .00035 mfd. condenser instead of for .0005.....\$ .80
- (Cat. 2-R5)—Radio frequency transformer for .0005 mfd. condenser where high impedance untuned primary is in plate circuit of a screen grid tube, and secondary is tuned by .0005 mfd.....\$ .60
- (Cat. 2-R3)—Same as 2-R5, except that it is for .00035 mfd. tuning.....\$ .60
- (Cat. 5-TP)—Radio frequency transformer for use where primary is tuned and placed in plate circuit of screen grid tube, while secondary is not tuned. For .0005 mfd.....\$ .55
- (Cat. 3-TP)—Same as Cat. 5-TP, except that it is for .00035 mfd. tuning.....\$ .55
- (Cat. RF-5)—Radio frequency transformer for .0005 mfd. tuning, where untuned primary is in plate circuit of any type tube except screen grid. Useful also as antenna coupler.....\$ .55
- (Cat. RF-3)—Same as Cat. RF-5, except that it is for .00035 mfd. tuning.....\$ .55

Remit with order for coils and we pay transportation. C.O.D. orders filled.

**SCREEN GRID COIL CO.**  
143 WEST 45TH STREET  
NEW YORK, N. Y.

**1-A UNIT—BP DIAMOND—FF-8  
DE LUXE CONVERTER**

The de luxe model short-wave converter, using the circuit Fig. 1 on page 10 this week, is a beautiful bakelite chassis with National modernistic dial, two tuned circuits with Hammarlund condensers, and using a total of five plug-in coils. This model, the 1-A, tunes from 15 to 600 meters and uses three screen grid tubes. Order Cat. 1-A (all parts, including filament transformer and tube base coils, but not including tubes).....\$19.87



**WRITE FOR PRICES  
ON BP-DIAMOND AND FF-8**

Polo power transformer, polished aluminum case, as specified for the FF8 (Cat. 245-PT).....\$9.50  
B supply choke coil in polished aluminum case, 100 ma. 30 henries, tapped in two places; 200 ohms DC resistance. May be used as center-tapped choke for push-pull output. (Cat. 245-CH).....\$4.00  
**ALL PARTS GUARANTEED**

**POLO ENGINEERING LABORATORIES**  
125 WEST 45TH STREET, NEW YORK, N. Y.

**The New Jiffy Tester  
Chromium-Plated Case and Accurate Meters**

A NEW and improved Jiffy Tester, improved in both performance and appearance, is Model JT-N. The meters are of the moving iron type. Tested on precise batteries, they show errors not exceeding 2%. As for appearance, the case is first copper plated, then nickel plated, then chromium plated, giving a lustrous, permanent, non-peeling non-rusting finish. It is the same finish found on hardware in fine automobiles. The handle and lock strap are genuine leather.



Jiffy Tester, Model JT-N, consists of three double-reading meters, with cable plug, 4-prong adapter, test cords and screen grid cable, enabling simultaneous reading of plate voltage, plate current and filament or heater voltage (DC or AC), when plugged into the socket of any set. The ranges are filament, heater or other AC or DC: 0-10 v, 0-140 v; plate current: 0-20, 0-100 ma; plate voltage: 0-60, 0-300 v. It makes all tests former models made. Each meter is also independently accessible for each range. The entire device is built in a chromium-plated case with chromium-plated slip-cover. Instruction sheet will be found inside. Order Cat. JT-N.

[Remit \$11.40 with order for JT-N and we will pay transportation]

**GUARANTY RADIO GOODS CO.**  
143 WEST 45th STREET (Just East of Broadway) NEW YORK, N. Y.

**Save Money on Tubes!  
Get a Guarantee Just the Same!**

QUALITY tubes at enormously reduced prices enable you to save money and obtain full satisfaction. Any tube will be replaced on request within thirty days of its sale!

These tubes are made by a manufacturer of national reputation and are not "distress merchandise." No tube is shipped until it is carefully checked on a Readrite No. 9 Radio Test Kit.

Type	List Price	Your Cost	Type	List Price	Your Cost	Type	List Price	Your Cost
<input type="checkbox"/> 201A	\$1.25	60c	<input type="checkbox"/> WD-12	\$3.00	59c	<input type="checkbox"/> 245	\$2.00	59c
<input type="checkbox"/> 226	1.75	60c	<input type="checkbox"/> 200A	4.00	59c	<input type="checkbox"/> 280	1.90	59c
<input type="checkbox"/> 199-UX	2.50	59c	<input type="checkbox"/> 171A	2.25	59c	<input type="checkbox"/> 224	3.30	59c
<input type="checkbox"/> 199-UV	2.75	59c	<input type="checkbox"/> 171AC	2.25	59c	<input type="checkbox"/> 222	4.50	95c
<input type="checkbox"/> 120	3.00	59c	<input type="checkbox"/> 112A	2.25	59c	<input type="checkbox"/> 281	7.25	95c
<input type="checkbox"/> WD-11	3.00	59c	<input type="checkbox"/> 227	2.20	59c	<input type="checkbox"/> 210	9.00	95c

250, List \$11.00, your cost, 95c.

[Remit with order for tubes and we pay postage]

**DIRECT RADIO CO.**

143 West 45th St., New York, N. Y.





Vol. XVIII. No. 20 Whole No. 462  
 January 31st, 1931  
 [Entered as second-class matter March, 1922, at the Post Office at New York, N. Y., under act of March, 1879]  
 15c per Copy. \$6.00 per Year

**NINTH YEAR**  
 Technical Accuracy Second to None  
 Latest Circuits and News

A Weekly Paper published by Hennessy Radio Publications Corporation, from Publication Office, 145 West 45th Street, New York, N. Y.  
 (Just East of Broadway)  
 Telephone, BRyant 9-0558 and 9-0559

RADIO WORLD, owned and published by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, president and treasurer, 145 West 45th Street, New York, N. Y.; M. B. Hennessy, vice-president, 145 West 45th Street, New York, N. Y.; Herman Bernard, Secretary, 145 West 45th Street, New York, N. Y.; Roland Burke Hennessy, editor; Herman Bernard, business manager and managing editor; J. E. Anderson, technical editor

# The Band Pass Diamond

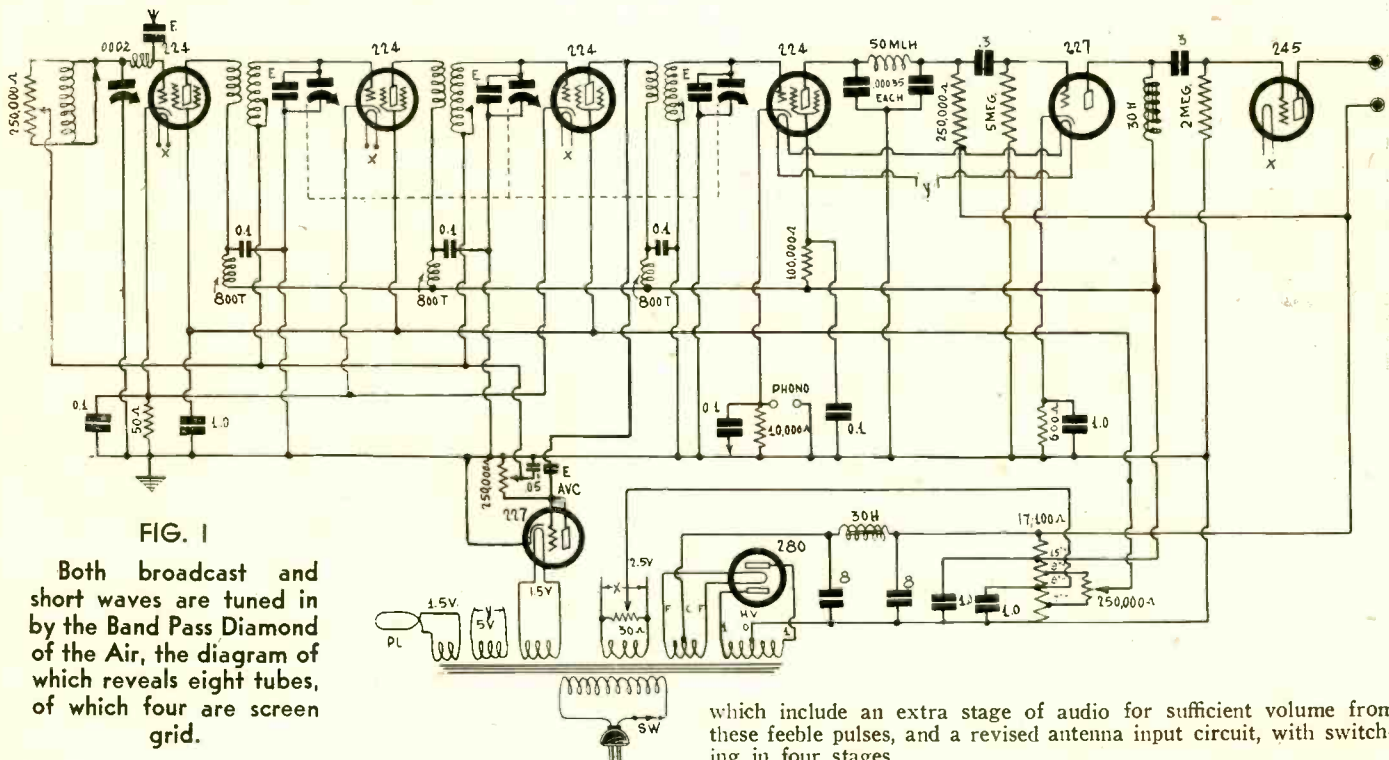


FIG. 1

Both broadcast and short waves are tuned in by the Band Pass Diamond of the Air, the diagram of which reveals eight tubes, of which four are screen grid.

**T**HERE is a surprise in the diagram of the Band Pass Filter Diamond of the Air, shown in Fig. 1, and that is the inclusion of a short-wave feature. The circuit has been shown for broadcast use, but is presented herewith with such changes as necessary to bring in short waves.

which include an extra stage of audio for sufficient volume from these feeble pulses, and a revised antenna input circuit, with switching in four stages.

The simplest way to provide for short waves is to use a switching device. You have your choice of a multiple switch, to throw four poles at one flip, or of separate switches. The choice made in the present instance was by all means for the separate switches, (Continued on next page)

## LIST OF PARTS

### Coils

- One shielded antenna coil for .0002 mfd. tuning, with switch built in.
- Three interstage couplers for .0005 mfd. tuning, tapped at 10th turn, with switch built in.
- One ¼ millihenry radio frequency choke coil.
- One 50 millihenry radio frequency choke coil.
- Three 800-turn duolateral choke coils.
- One power transformer.
- Two 30-henry choke coils (one for B filter, one for first AF).

### Condensers

- One .0002 mfd. Hammarlund junior midline condenser.
- One .0005 mfd. three-gang Scovill condenser, brass plates.
- Five Hammarlund equalizing condensers, 20-100 mmfd (three for condenser gang, one for series connection to aerial, one for AVC).
- Five blocks of triple 0.1 mfd. condensers, three condensers in each case; two blocks used with red leads interconnected for audio blocking condensers.
- Four 1.0 mfd. 200-volt condenser.
- Two Aerovox 8 mfd. dry electrolytic condensers.
- Two .00035 mfd. fixed condensers.

### Resistors

- One 50-ohm flexible biasing resistor.
- Three 250,000-ohm potentiometers.
- One 250,000-ohm metallized pigtail resistor.
- One 5 meg. metallized pigtail resistor.
- One 30-ohm center-tapped resistor.
- One 2 meg. metallized pigtail resistor.
- One 100,000-ohm metallized, pigtail resistor.
- One 10,000-ohm metallized pigtail resistor.
- One 600-ohm wire-wound resistor.
- One multitap voltage divider (17,100 ohms)

### Other Parts


- One Benjamin switch (for phonograph).
- Three moulded bakelite twin assemblies. (speaker, phonograph, antenna-ground).
- One National modernistic drum dial with 1½-volt bulb.
- One 17½ in. x 9 in. metal subpanel, with six five-prong (UY) sockets and two four-prong (UX) sockets.
- One AC switch, shaft type.
- Hardware, consisting of three milled bushings, three dozen 6/32 machine screws, three dozen nuts to match.
- Accessories: Six insulating washers for potentiometers, six soft rubber grommets.



# A Short-Wave Converter Intermediate

By J. E.

**Fig. 1**  
The circuit of a four tube short-wave converter with the power supply built in. It is especially suitable for use with broadcast receivers which are not very sensitive.

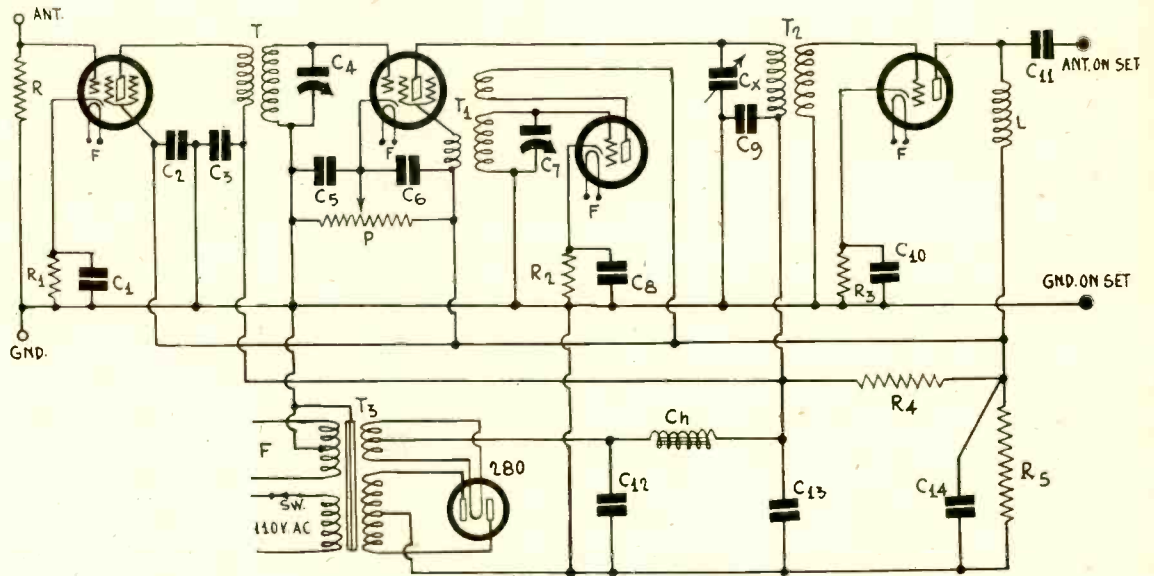

**S**HORT-WAVE converters are almost invariably successful in bringing in short-wave signals if they are connected to the receiver the proper way. Now and then a complaint is made that a converter does not produce signals when used with certain receivers. Such complaints usually result from one of three causes: first, that the oscillator does not function; second, that the receiver with which the converter is used is not sensitive enough; third, that the B supply is not correct.

Lack of oscillation is usually traced to a defective oscillator tube or to insufficient voltage on the heater or filament. Of these lack of voltage on the heater is perhaps the more common.

Failure to give results due to comparative insensitivity of the receiver with which the converter is used is most common of all, for converters are frequently used with old receivers which do not bring

in distant stations when used for broadcast reception and the sets are used in such manner with the converter that they lose a great deal of the sensitivity that they do have. The difficulty is usually in the coupling between the converter and the receiver.

## Incorrect B Supply

Many times a converter has been tested and found to work satisfactorily only to fail completely when connected up by another. In such cases the trouble almost invariably is that the converter does not get any plate voltage. Perhaps the positive lead goes to the proper voltage but the B minus may not be connected at all. In other cases the B minus is taken care of by the common ground but the B lead is not connected properly. Sometimes the lead is connected to a plate of a tube in the set in such manner as to short-circuit the signal. Sometimes the B plus outlet is connected to a screen in such way that there is a high resistance in series which causes high drop in the voltage and the converter tubes do not get enough to function.

To avoid these difficulties the converter is built with a stage of intermediate amplification with an output tube such that it matches the input impedance to the broadcast receiver and also with a B supply of its own. If a radio frequency amplifier also be built into the converter the sensitivity of the converter and the set will be satisfactory.

## Noisy Reception

Other complaints with converters are that they are noisy, and these complaints are about those that do bring in signals, that is, those that are sensitive. If the signals are noisy that is not the fault of the converter, because the noise comes in from the outside and it is only an indication that the circuit is adjusted to high sensitivity. There is no more noise in the short-wave signals than in the broadcast signals if the intensities of the signals are the same. Indeed, there may be less noise in the short-wave signals, especially on signals of less than 50 meters. In many localities the broadcast stations come in with so much noise that it is impossible to enjoy the programs, but the short-wave stations come in with practically no noise. This is particularly true in the sub-tropics in Summer.

Some persons who have got short-wave converters complain that they "do not work" but bring in only code, lots of that. Well, if a short-wave converter brings in lots of code, it works well, for the code is carried on short-waves and it could not come in if the circuit did not work. If the converter does not bring in short-wave broadcast stations it is because no such stations are working within range or, more likely, because the converter has not been tuned properly. Hence if the converter brings in code, all that is necessary is to tune properly and turn up the volume control. If still nothing comes in, except code, there is no voice-modulated station on the air at the time within range of the receiver.

The diagram in Fig. 1 is that of a converter designed especially to overcome the objections mentioned above. It has a built-in B supply so that there can be no error in connecting up the converter

## LIST OF PARTS

### Coils

- T—One set of RF transformers as described.
- T1—One set of oscillator coils as described.
- T2—One radio frequency transformer, one-to-one ratio, for .0005 mfd.
- T3—One Polo 180 volt power transformer.
- Ch—One Polo 30 henry choke coil.
- L—One 50 millihenry radio frequency choke coil.

### Condensers

- C1, C2, C3, C5, C6, C8, C9, C10—Eight Supertone 0.1 mfd. by-pass condensers.
- C4, C7—Two .0002 mfd. midget variable tuning condensers.
- C11—One .00035 mfd. fixed condenser.
- C12, C14—Two 2 mfd. by-pass condensers.
- C13—One 4 mfd. by-pass condenser.
- Cx—One .0005 mfd. tuning condenser.

### Resistors

- R—One 250,000 ohm coupling resistor.
- R1—One 300 ohm grid bias resistor.
- R2, R3—Two 1,000 ohm grid bias resistors.
- R4—One 10,000 ohm resistor for voltage divider.
- R5—One 6,500 ohm resistor for voltage divider.
- P—One 30,000 ohm potentiometer.

### Other Parts

- Four binding posts.
- Five UY sockets.
- Two UXXX sockets.
- Two dials.

### Tubes

- Two 224, two 227, one 280; total, five tubes.



# ter with B Supply and Stage Built In

Anderson

to any radio receiver, and also a filament winding so that there will be no question about adequacy of heater voltage.

It has a stage of RF ahead of the modulator so that the signals will be amplified before they are mixed with the local oscillation. It has an intermediate frequency stage after the detector so that the amplification in this level will be high even if the broadcast receiver is not sensitive by itself. Since the last tube is a 227, which has a low impedance, the coupling between the antenna circuit and the converter will be matched and there will be very little transition loss.

The circuit is essentially the same as that of the de luxe four tube converter published in the November 15th issue, which is one of the most sensitive converters operated by the writer. However, it is an improvement over that circuit in that it has a built-in power supply. That circuit had only a filament transformer.

Another change is that a resistance R of 250,000 ohms is used in the antenna circuit in place of a small choke coil. The resistance will give a greater sensitivity but the choke will pick up somewhat less static and similar interference. The resistance makes the sensitivity so much greater that it is well worth while to use it.

### Method of Modulation

The method of modulation is the same in the two circuits, that is, the oscillation is introduced into the modulator tube by way of the screen, and grid bias detection is used.

The plate circuit of the modulator tube contains a circuit tuned to the intermediate frequency. This is done for two reasons, first, to insure a high impedance load on the modulator at the intermediate frequency, and second, to provide a by-pass condenser for the high frequencies. Thus CX serves two purposes.

While it is possible to use any intermediate frequency in the broadcast band, it is best to use that at which the broadcast receiver is the most sensitive. If it is equally sensitive throughout the tuning band the intermediate frequency should be either 1,500 kc, or higher, or 550 kc, or lower. If a frequency is decided on it is possible to select a coil, the primary of T2, which will tune in the desired frequency with a midget condenser of the trimmer type. But a small condenser cannot be used to cover the entire broadcast band for the selection of any frequency therein. Hence if it desired to have the choice of any frequency from 550 to 1,500 kc, the condenser should be at least 500 mfd. It need not be represented by a control on the panel, because after the intermediate frequency once has been selected for a given broadcast receiver there is little need of changing it again so that the tuning of CX may be left fixed. Neither is it desirable to change it for every time it is changed the tuning characteristic of the RF circuit is changed and also that of the oscillator.

One side of the condenser CX is grounded and the tuned circuit is completed by means of condenser C9. If the CX is fixed it is not necessary to ground it, as it may be connected directly across the winding, but if it is a large tuning condenser it is best to connect as in the diagram.

### Controlling Volume

It is important to have a volume control on the converter even though the broadcast receiver with its volume control is close at hand, because the signal intensity range will be very large and two controls are desirable. In this circuit the control is the potentiometer P, which is connected between the screen return and ground, with the cathode of the modulator tube connected to the slider. When the slider is moved to the left, that is, toward the ground, the bias on the tube is reduced and at the same time the screen voltage is increased. The circuit will work somewhat below maximum sensitivity when the cathode is grounded and the point of maximum sensitivity will be found when the slider is a short distance to right of the ground end. As the slider is moved still farther to the right, that is, toward the positive end of the resistance, the volume will decrease and a point will be found where the set is entirely dead. Thus there is a wide volume control range.

The filament and plate voltages are supplied by a power transformer L3 and a 280 rectifier. This transformer has one 2.5 volt filament winding which supplies the four tubes in the converter and one 5 volt winding for the rectifier filament. The high voltage winding is such that the output voltage is 180 volts after the filter. This high voltage is applied to the plate of the two screen grid tubes. A voltage of 75 volts is applied to the plates of the two 227 tubes and the screens of the two 224 tubes. It is dropped from 180 to 75 in the resistance R4 of the voltage divider. R5 has a value of 10,000 ohms so that the bleeder current is 7.5 milliamperes.

Resistance R4 should have a value of 6,500 ohms, or as near that

as may be obtained by using the taps on a multi-tap voltage divider.

The plug-in coils are exactly of the same design as those in the De Luxe converter cited. The RF coil is wound on a UX form and therefore requires a UX socket. The oscillator is wound on a UY form so this requires a socket of that type. A five-prong is practical because the plate voltage on the oscillator is the same as the screen voltage on the modulator and therefore one of the prongs can be used as terminals for two windings, the tickler and the pick-up.

### Terminal Connections

The terminal connections on the RF coil T1 should be as follows: G on the coil socket to P on the RF tube socket; F minus on the coil socket to B plus 180; P on coil socket to G on the modulator, that is, to the control grid; F plus on coil socket to ground. The coil terminals on the form should be made to the prongs in the corresponding manner.

The terminal connections of the oscillator should be made as follows: G on the coil socket to G on the oscillator socket; P on the coil socket to P on the oscillator socket; K on the coil socket to ground; HP on the coil socket to B plus for the screen voltage; HK on the coil socket to G on the modulator socket. The terminals of the oscillator coil should be connected to the prongs on the base in the corresponding manner, two terminals being connected to HP.

To insure oscillation the G and the P terminals of the tuned and tickler windings should be far apart and the K and HP close together, the two windings being in the same direction. No special mode of winding the pick-up coil is necessary just so the terminals are connected to the prongs as explained. It is well, however, to put the pick-up winding on the side of the tuned winding opposite to that of the tickler so as to keep the tickler and the pick-up windings as far apart as practical.

No special mode of connecting the RF coil terminals need be observed. However, it is well to wind the coil so that the grid and the plate terminals are far apart and the ground and B plus close together.

### Number of Turns

The number of turns on the various windings depends on the size tuning condensers used. The condensers specified in the circuit cited were .000125 mfd. This is a good size. However, at this time a smaller condenser made especially for short-wave converters is available. This may be obtained in various capacities up to .0002 mfd., and this capacity is suitable. If this size condenser be used, the same coils as for the .000125 mfd. condensers may be used. The circuits will tune just as high in frequency, the different tuning ranges will overlap a little more, and the largest coil will tune a little lower in frequency.

The coils are wound on forms a little smaller in diameter than tube bases, or on forms 1.25 inches in diameter. The tuned windings on T1 and T2 are exactly the same, and the three coils in each set have seven, eleven, and sixteen turns. The corresponding primaries on T1 are three, five, and seven. The corresponding ticklers are six, nine, and ten, and the pick-up windings one, two, and three.

The size of wire on the tuned windings should be No. 22 double cotton covered. The other windings may be of smaller wire. The size is not important. Even the tuned windings can be made of wire as fine as No. 30, although it is better to use the heavier wire.

## Radio World Advertising Rates

	1 Inser.	4 consec. Inser. (each) 10%	13 consec. Inser. 12½%	26 consec. Inser. 15%	52 consec. Inser. 20%
1 page	\$150.00	\$135.00	\$131.25	\$127.50	\$120.00
½ page	75.00	67.50	65.62	63.75	60.00
¼ page	50.00	45.00	43.75	42.50	40.00
⅓ page	37.50	33.75	32.81	31.87	30.00
⅔ page	25.00	22.50	21.87	21.25	20.00
⅜ page	18.75	16.87	16.41	15.94	15.00
1 inch	5.00	4.50	4.37	4.25	4.00

Classified advertisements, 7 cents a word; \$1.00 minimum; remittance with order.

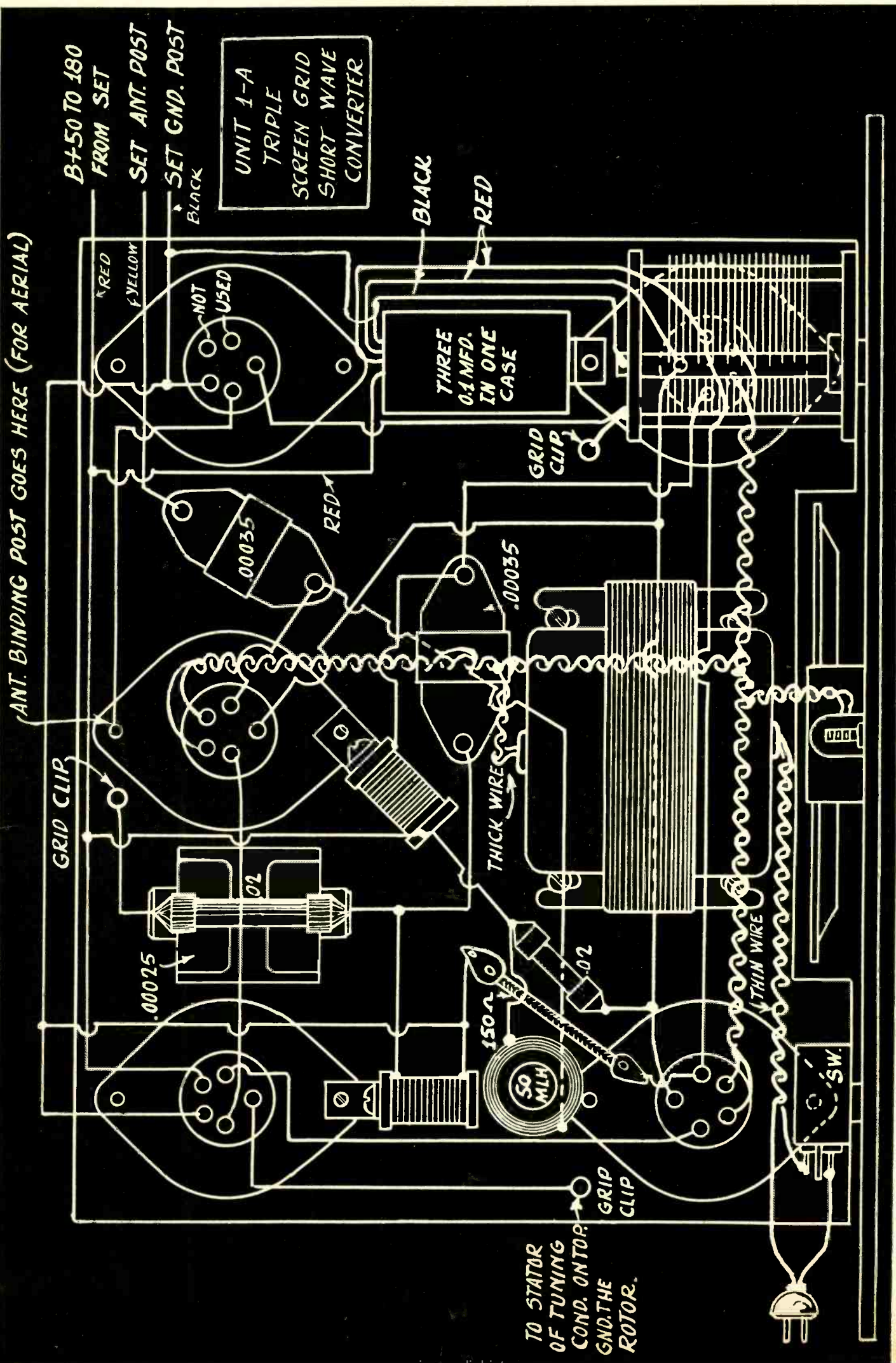
### Advertising Department

Radio World, 145 West 45th St., New York, N. Y.















# Circuit the FF-8

B. Herman

## LIST OF PARTS

### Coils

- Four shielded radio frequency transformers, Screen Grid Coil Company's Cat. 40-80
- Two 800-turn honeycomb radio frequency choke coils for plate circuits of two RF tubes
- Three 50-millihenry radio frequency choke coils
- One Amertran de luxe first stage audio transformer
- One Amertran push-pull input transformer, No. 151
- One 30-henry audio choke coil for first AF plate circuit
- One Polo 245 B choke, used as center-tapped choke in output (black and yellow for extremes, green for center)
- One Polo 245 B choke, used as B choke (black to rectifier, yellow to voltage divider, red and green to 8 mfd. condensers only)
- One Polo 245 power transformer, 110 volts, 50-60 cycles; secondaries, 2½ volts, 16 amperes; 2½ volts, 3 amperes for power tubes; 5 volts for rectifier filament; high voltage to afford 300 volts DC; all secondaries center-tapped
- Two 800-turn RF choke coils, duolateral wound

### Condensers

- One Hammarlund four-gang .00037 mfd. tuning condenser with trimmers built in
- One Hammarlund equalizer, 20-100 mmfd., for antenna series condenser
- Two blocks of triple .1 mfd., three fixed capacities in each block
- Two .1 mfd. by-pass condensers, 200-volt DC rating
- Two 2 mfd. condensers, or four 1 mfd. condensers, each pair in parallel, 200-volt DC rating, for plate circuit of first AF
- Four Aerovox 8 mfd. dry electrolytic condensers, with four brackets
- One .0015 mfd. fixed condenser
- Two .00035 mfd. fixed condensers
- One .00035 mfd. fixed condenser

### Resistors

- One 250,000-ohm potentiometer, for volume control
- Two 500-ohm wire-wound flexible biasing resistors
- Two .02 meg. pigtail metallized resistors (20,000 ohms)
- Two 50,000-ohm pigtail metallized resistors
- One 0.5 meg. pigtail metallized resistor
- One 600-ohm wire-wound biasing resistor
- One Multi-tap voltage divider, 17,100 ohms, 8th tap for screens, 15th tap for 180 volts
- One 750-ohm resistor, for biasing power tubes (10 watt)
- One 250,000 ohm potentiometer for automatic volume control circuit

### Other Parts

- One Hart and Hegeman AC switch, shaft type
- One metal subpanel, with five five-prong (UY) sockets and three four-prong (UX) sockets
- Molded bakelite twin assembly for speaker
- Molded bakelite twin assembly for phonograph
- Molded bakelite twin assembly for antenna and ground
- One National flat type modernistic dial, counterclockwise (type G), with pilot light bracket and 2½-volt lamp
- One roll of hookup wire
- Hardware, consisting of two dozen 6/32 screws and two dozen nuts to fit

### Tubes

- Two 224, three 227, one 280 and two 245; total, eight tubes

way that selectivity can be pictured or described accurately is by a curve.

The coils used are shielded. The degree of shielding actually used may be varied. If the shields are attached directly to the metal subpanel then there exists total shielding, so-called. There is still some chance of coupling between stages, but it is very slight coupling, and will not disturb a circuit like this one. In fact, if desired, the top shields, that slide over the coil, may be elevated from the subpanel to any height that installation room permits. A slight elevation has no noticeable effect. The rise should be considerably more than one inch, preferably two inches, if this method is to be introduced at all.

The way to try out this plan is to build the circuit with close shielding, then, using tubular bushings about 2 inches high with screw inside, or dowel stick with wood screws at top and bottom, to fasten the dowel to top shield and to subpanel, try out the circuit that way. There will be a slight change in the dial settings, in a downward direction (less capacity needed to resonate to any particular frequency) and the circuit may squeal

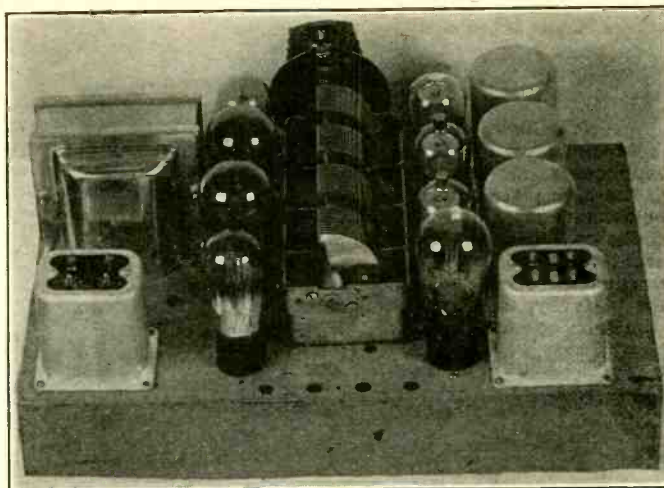


FIG. 2

How the parts are disposed on top of the subpanel is revealed.

at the high frequency end of the dial. If so, reduce the elevation of the shields a little, say ¼ inch, or until there is no squealing at any point.

The reason for this suggestion is that by altering the degree of shielding the sensitivity may be increased somewhat, since most circuits are designed so that they will not squeal at all and therefore the dampening effect of shields is pressed to the utmost, with no option for raising the effective amplification to just below the oscillation point.

## The Automatic Volume Control

It will be noticed that the primary of the radio frequency transformer that couples to the detector, instead of being left free, is returned through a condenser to the united plate and grid elements of a 227 tube, a resistor going from this joint to grounded cathode. This tube is an automatic volume control and operates on the principle of simple single-wave rectification. The direct current flows from negative grid-plate to positive cathode, so by returning the two radio frequency amplifier grids to a potential lower than grounded B minus, extra negative bias is obtained when there is a carrier. The extra bias voltage is like that of a variable C battery.

A steady bias is provided by the separate biasing resistors in the cathode leads of these two amplifier tubes, so that even when there is no carrier there will not be an absence of bias. When a carrier is tuned in, part of the second radio frequency tube's output is delivered to the automatic volume control tube, which rectifies this current. The higher the amplitude of the carrier, the greater the amount of rectified current, the voltage drop in the resistor, and the greater the bias. Thus a loud signal occasions increased bias, or decreased effective amplification (due to rise in the plate resistance), and the desired levelling effect results. Then stations may be tuned in, even strong locals, without roaring blasts. Also, this automatic volume control, or constant output level, is valuable when the set is used in conjunction with a short-wave converter, since then the fading effects that prevail on short waves are minimized, although not completely obliterated.

The detector output is filtered, with a radio frequency choke coil, and fixed condenser at both sides, so that only the audio is delivered to the first audio transformer.

## Audio Stages

Since the detector is of the power type, the plate current will be small, of the order of 1 milliampere or less, hence the high primary inductance of the first audio transformer is not shrunk by an overload of direct current. At 1 milliampere the inductance of the primary is 200 henries, which is very substantial. The transformer used was the Amertrand de luxe first stage unit.

Owing to the second audio stage, we find that the plate current must be relatively high, with the proper tube, which is a 227, and there is no way of avoiding it. The current may be as much as 10 milliamperes. This is far in excess of the amount of direct current that should be put through the primary, if the precious asset of high inductance is to be preserved, and easy saturation avoided.

It is advantageous to have a high permeability core on an audio transformer, as Amertrands have, but such cores will saturate much sooner than would an silicon steel core. The special core of the Amertran gives the advantage of higher volt-

(Continued on next page)



# Returned Quality in Filtered Set

## No Honolulu but lots of Domestic DX with Realism

(Continued from preceding page)

age in the secondary, so high permeability is somewhat akin to high amplification factor in a tube.

Although the high plate current can not be avoided, its course through the primary may be avoided, and this is done by putting an audio choke coil in the plate lead, and passing only the alternating current to the primary. Notice that the primary itself is then returned to cathode, the same return as was made for the detector plate bypass condensers, since the cathode is the datum of the tube operation.

### Push-Pull Connections

The push-pull input transformer under discussion, an Amertran 151, has the secondary in two separate windings. These are to be joined as shown, with a 50,000-ohm resistor from the low potential end of the winding to ground, in each instance, and a 2 mfd. condenser, or two 1 mfd. condensers in parallel, across the coil terminals as diagrammed in Fig. 1. The secondary terminals are numbered on the transformer, 1 and 4 going to the grids and 2 and 3 to the resistors. This special treatment of the secondary circuit is another example of filtration, and helps prevent feedback.

The audio choke in the output is a center-tapped type, which permits connection of any type speaker to the plates, without any direct current flowing in the speaker winding. In most instances a dynamic speaker will be used that has an output transformer built in, and the usual connections may be made (speaker's tipped cords to plates) without removal of the transformer from the speaker.

If a Farrand 12-G speaker is used, no output choke is necessary, as this speaker has its magnet coil center tapped. The tap is either brought out by a yellow lead, or has no wire attached to it, in which instance you must solder a connection from the maximum B plus lead, connecting tipped cords to plate.

### B Supply Filtration

The B supply is still another example of excellent filtration. The B choke permits of a so-called "choke input," whereby no condenser is next to the rectifier. Thus when the set is turned on the rectifier tube is not subjected to the high strain due to charging up a capacity, so rectifier tube life is lengthened. The connection is made, on the Polo 245 choke, by joining the black choke lead to red center lead of the 5-volt rectifier filament winding, the red, green and yellow leads of the B supply choke being connected individually to 8 mfd. electrolytic condensers. The yellow lead goes to the voltage divider.

Hence there are four connections to the choke coil, and three

of them go 8 mfd. capacities. The 180-volt lead also has an 8 mfd. electrolytic condenser, to prevent feedback, while the voltage that goes to screens, already filtered, needs only 1 mfd., of the 200-volt DC type.

The Polo 245 power transformer furnishes all the necessary voltages with margin to spare, without being overtaxed at all by the circuit.

### No Condenser Across This Resistor

The voltage divider is the Multi-Tap, but no biasing voltages are taken from it.

The power tube bias is obtained through the drop in a 750-ohm resistor, across which it would be a mistake to put a bypass condenser, since the current of a push-pull circuit is concerned. A push-pull circuit being symmetrical, there is no need for bypassing, current being equal in value but opposite in phase at any instant. A condenser would remove the stabilizing influence.

It can be seen quite readily from the foregoing discussion that the primary object was not to determine how much can be produced for the least possible cost, but what attainments may be reached, using the best parts, knowing that their cost is bound to be greater than that of indifferent parts. Nevertheless, the parts for the amplifier less tubes, should not cost more than \$50.

In the tuner it would not be economical at all to use a condenser that afforded diverse capacities in the four sections, for the tuning must be in step, or indeed it isn't really tuning, besides destroying the sensitivity and selectivity. So a Hammarlund condenser was used that has trimmers built in. The frame is die-cast aluminum and the plates are aluminum, too.

The coils are those of the Screen Grid Coil Company, as these afford the necessary inductance and capacity values for the circuit.

The choice of audio transformers just naturally fell to Amertran, since quality was the foremost consideration, while to provide power equipment that certainly would stand the strain without any sign of overload, the Polo 245 power transformer and 245 choke coil were selected.

The electrolytic condensers are those made by Aerovox and are of the dry type.

So anyone who wants a receiver that obviously is of the highest quality, that won't get Honolulu but will bring into the home the voice and music just as they are delivered to the microphone, with plenty of distance reception from continental United States, may build this receiver with utter safety and assurance. It is a receiver that will provide the highest possible delight of possession and will be a revelation to visitors to your home who perhaps never heard radio at its very best.

# FREE AID TO A NEW JOB!

SITUATIONS WANTED AND HELP WANTED ADVERTISEMENTS WITHOUT COST!

Address: Industrial Dept., RADIO WORLD, 145 W. 45th St., N. Y. C.

## SITUATIONS WANTED

**RADIO MAN WITH 8 YEARS' EXPERIENCE;** both technical and practical; 32 years of age, married, willing to go anywhere and very much interested in a foreign position. Would like connection with some reliable concern or factory. E. W. Becker, 24 Wallingford Rd., Brighton, Mass.

**SITUATION WANTED: ELECTRICAL ENGINEER,** graduate Washington University, knows radio, wishes position in radio laboratory or engineering department. Small salary to start. Louis R. Conrath, 3623 Fillmore St., St. Louis, Mo.

**RADIO TECHNICIAN, 26 YEARS OLD — 7 years'** active experience in radio service, graduate of two radio schools, with active photophone, sound and amplifier experience, desires position with firm either to act as field service man or laboratory worker. Is married but will go anywhere. Prefer south-west or Pacific coast. References on request. Has complete laboratory equipment. Address, Dougherty's Radio Laboratories, New Market, Iowa.

**EXPERT RADIOTRICIAN,** trained and graduated by National Radio Institute, high school education, four years' experience in sales and service. Desires position with manufacturing firm. Karl C. Fischer, Gen. Delivery, Knoxville, Tenn.

**CUSTOM SET BUILDER WITH INVENTIVE ABILITY** wants work in repair shop or laboratory. E. Widell, 915 N. 19th St., Saint Louis, Mo.

**CERTIFIED RADIOTRICIAN.** Also high school graduate and at present C. R. E. I. student. Can furnish satisfactory references as to character and ability. Address: H. F. Goodrich, 2020 Seminary St., Dubuque, Iowa.

**INVENTIVELY INCLINED,** and have diploma from Radio Training Association of America; would like to get in touch with radio factory with high-class laboratory. Former student in Electrical & Mechanical College of University of Kentucky. P. B. Kehoe, 2100 Lee Street, Fort Myers, Florida.

**NATIONAL RADIO INSTITUTE STUDENT** wishes position in service and installation work. Jewell test equipment. Experienced in servicing. Willing to do any kind of work. Chas. C. Stutzenberger, 228 Turner Street, Allentown, Pa.

**YOUNG, ENERGETIC MAN;** several years' experience building and servicing sets. Has worked in Westinghouse & Electric Manufacturing Co. research laboratories. Excellent references. Free to travel. Not afraid of work. Desires location that will permit of carrying on schooling in pursuit of a degree. Russell J. Ramsey, Alpine Blvd., Wilkinsburg, Pa.

**A REGISTERED RADIO TECHNICIAN** wishes position either store or factory. Anywhere in United States. Have three years' experience. Fred Kelly, 1909 4th Ave., North, Minneapolis, Minn.

**YOUNG MAN, 10 YEARS' EXPERIENCE** in designing and building of radio production test equipment, production, designing home and automobile receivers, and elimination of ignition interference in motor radios, desires position with reliable company. Best of references. F. S. Palm, 5815 W. Roosevelt Road, Cicero, Ill.

**YOUNG MAN 19, TECHNICALLY INCLINED,** desires a position as assistant in laboratory. High School education, several years experimenting with radio and chemistry; formerly radio operator; interested in research work. Melvin Kocher, Pershing, Ind.

**YOUNG ELECTRICAL ENGINEER, 25 years** of age, South American. Would like connection with radio manufacturing company to open branch in South America. Have references. D. C. Mendez, 236 Washington Ave., Brooklyn, N. Y.

**YOUNG MAN, 33 YEARS OLD,** mechanical, electrical and radio knowledge and experience, technical education, seeks position at anything. Paul Weber, 1823 Blecker St., Brooklyn, N. Y.

**SERVICE MAN,** five years' experience, with two of Chicago's largest servicing companies. 27 years old, Al man, good references. Have finest test equipment. Will go any place. Robert Murray, 1520 Howard St., Chicago, Ill.



# A Portable AC Phonograph

Motor and pickup in Handy Case Solves Home Problem, Too



View of the portable AC phonograph.

**I**F YOU have no room in your console or radio cabinet for a phonograph attachment, an arrangement like the one illustrated herewith is a good solution. A synchronous motor with the accompanying turntable is mounted on a panel that has been cut to fit a suitcase and mounted thereon. A pickup unit with a "tone arm" is also mounted on the panel, in one corner. In another corner of the panel is mounted a volume control, at a place where it is easily accessible to the operator.

When the radio programs are not satisfactory it is easy to take this portable phonograph attachment from the closet where it is normally stored and place it near the receiver, make a few connections and play what "you want when you want it."

The synchronous motor is so thin that there will be plenty of room under the panel if an ordinary suitcase is used, and there will be ample room in the lid for the pickup unit, the turntable, the volume control knob and the cord and plug. Indeed, there will even be room for a few records. The motor is designed for 60 cycles and will only run at the proper speed when connected to a line of this frequency. That makes it nearly universal in its application, for this frequency is used nearly everywhere, and in those places where other frequencies are used they are rapidly changing over to 60 cycles.

There is another application of the portable motor. Suppose a group of young folks desires to attend a dancing party at a house where there is a radio receiver not equipped with a phonograph attachment. The portable motor can be brought along in the car and set up at the home where the party is being held. This seems quite far-fetched but it is a suggestion taken from experience. Motors of this kind actually are used considerably for this purpose.

Still another use of the portable motor is for demonstration of audio frequency amplifiers and other acoustic devices. The salesmen take the motor along, together with the records wherever they wish to demonstrate.

One particular case is that of a tone control being demonstrated to prospective licensees and others interested. These carry along their own dynamotor for converting DC to AC in case their business takes them to locations where only DC is available.

## How to Connect and Work Converter

(Continued from page 10)

the heater prong next to cathode on the RF coil socket (right rear in pictorial diagram). "Heater" and "cathode" here do not refer to any tube connection, since this is a coil socket.

2. The red cable lead goes to B plus 180 volts, obtained from the receiver. However, less than 180 volts may be used. One expedient with screen grid receivers is to bare the end of this wire, turn it into a loop that will just fit over a tube prong, remove an RF screen grid tube from the receiver, slip the wire noose over the screen grid prong, and restore the tube to the receiver. This makes the screen voltage the B plus voltage. Whatever the color of the lead, it is the one coming from the heater prong next to plate in the oscillator coil socket (left rear in pictorial diagram).

3. Remove the aerial from the receiver and instead connect to the vacated antenna post of the set the yellow lead cable. No matter what the color, this is the lead emerging from one side of the .00035 mfd. condenser the other side of which goes to the 50 millihenry choke coil.

4. The aerial, removed from the receiver post, is connected instead to the solitary binding post on the converter. This post is at rear center and is used also for socket anchorage.

As for operation, it is necessary to turn on the set and also the converter, and wait until the tubes heat up. Then an inter-

mediate frequency is chosen, which is done simply by selecting some setting of the receiver. As sensitivity differs at different receiver settings, select the most sensitive position, consistent with the absence of broadcasting interference, that is, direct station pickup by the receiver to interfere with the short-wave reception. Broadcast reception will come right through, although the converter is working properly.

For broadcasts, use the very large-winding coil in the radio frequency socket, and the next largest coil in the oscillator socket. At an intermediate frequency around 1,500 kc, the lowest broadcast frequency will come in at about 90 on the converter dial, and the highest broadcast frequency at around 40 on the dial. The radio frequency tuning condenser should be rotated in searching for a station, but strong stations will be audible, in most instances, no matter what the setting of the knob-actuated condenser. After logging is established, simple rotation of the knob will bring about greatest sensitivity setting without trouble.

The same oscillator coil may be left in the socket when the highest broadcast frequency is passed, but then a coil like the one in the oscillator coil socket should be placed in the radio frequency coil socket. For the extremely high frequencies the two identical smallest coils are used. All coils are so wound as to be interchangeable on radio frequency and oscillator circuits, except the very large-winding radio frequency coil, which can be used only for broadcasts and only in the RF coil socket.

## Commercial Television Called Feasible Now

**W**ITH a number of stations now transmitting radio television programs on schedule, together with a decided indication of real showmanship about to replace haywire experimentation, the average household may be ready to consider radiovision as something more than a passing news item. What equipment is necessary? How much skill is required to snatch pictures out of the air? Such questions are becoming commonplace.

There are two answers to the first question regarding equipment, depending on who is interested, states D. E. Replogle, of the Jenkins Television Corporation. For the experimenter, there are components that may, with skill and good fortune, be assembled into a workable layout, or again a kit of matched components for ready assembly and positive results.

For the layman interested in immediate results in living room terms, there are various combinations of special television receivers and radiovisors, covering a wide range. The equipment necessary comprises a suitable receiver with which the tele-

vision signals may be tuned in and amplified with an absolute minimum of distortion, in combination with a radiovisor or device to translate signals into pictures.

The engineers have succeeded in reducing television reception to the simplest terms, so that the average layman may readily operate a properly designed outfit and receive satisfactory signals from television transmitters within service range.

Special television receivers cover the television broadcast band. A single tuning knob serves to tune in on the different wave lengths carrying television signals. The radiovisor is readily brought into proper step with the transmitted pictures and properly framed by simple adjustments. In the latest equipment, the pictures are self-synchronized so that little trouble is experienced in this respect.

The sound accompaniment, available with many television broadcasts, is being taken care of by regular broadcasting stations, so that the usual broadcast receiver may be employed for this purpose without change or additional investment.



# Principles Actuating Su

By J. E.

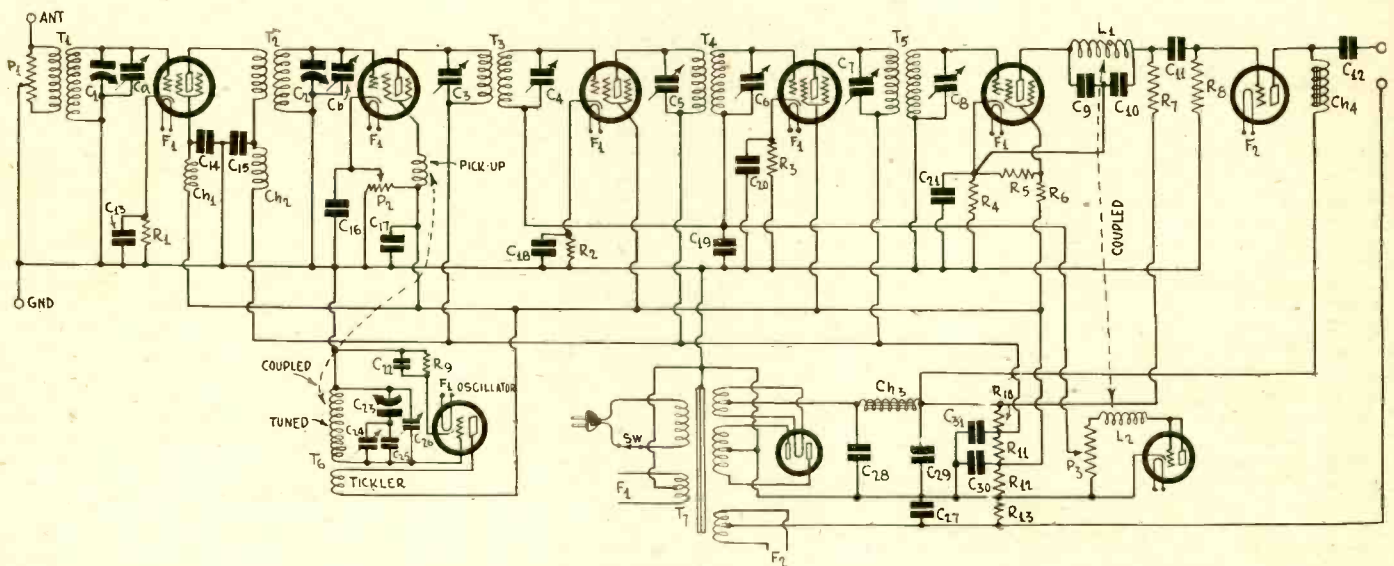


Fig. 1.

This is the circuit of a nine tube superheterodyne that is in the process of development. Not all the design features have been decided on and it will not be described for construction until the design is complete.

**P**UBLIC interest has swung to the superheterodyne again, due to the fact that the patent restrictions on this form of circuit have been lifted by the owners to the extent that licensed manufacturers are allowed to build them.

There never did exist any particular reason why the radio fans who build their own receivers should ever have lost interest in this fascinating circuit, but they did when all the manufacturers turned to tune radio frequency receivers. And now that manufacturers are free to turn out circuits of this type, the fans are going back to their first love.

Now that so many are designing superheterodynes we have a right to expect many innovations and improvements, but so far nothing outstanding has turned up. Perhaps engineers have not had time yet to develop the new ideas, but competition will bring them out without fail. So we may expect something new in the next crop of commercial receivers.

## Standardized Intermediate

In the first crop of commercial superheterodynes the intermediate frequency was 175 kilocycles, a value much higher than those used a few years ago, yet considerably lower than frequencies that have been used in many successful circuits. Why did the manufacturers uniformly choose 175 kilocycles as the intermediate frequency? Apparently because the Radio Corporation had selected this frequency and turned over the design data in full to the licensees. But why did the RCA choose 175 kc in preference to other frequencies that could have been used? The only answer that has been given is that the 175 kc channel is singularly free from commercial communication traffic. If a channel can be selected which is free from all traffic no interference need be expected from direct pickup by the intermediate frequency amplifier even if that amplifier is not shielded.

However, to look for a clear channel for use as intermediate channel in a superheterodyne is effort not well spent, for with the intense demand for channels throughout the world there is practically no channel which is not crowded with traffic. But not all channels are crowded as closely as others and not all are crowded with the same type of traffic. The 175 kc channel is said to be less productive of interference than most other channels, at least in this section of the world. Even if this be true there is no particular reason for selecting this frequency, for any interference that may result from direct pickup can be eliminated by judicious shielding. There are many other factors which must be given due consideration in selecting the intermediate frequency, and these factors are closely tied up with the purpose of the receiver.

## The Best Frequency

Scarcely a day passes on which somebody does not ask what the best intermediate frequency is to use in a superheterodyne. It must not only be simply the best, but it must be the best from all points of view. And along with this question go the questions as to which is the best intermediate frequency transformer, the best tuning condenser, the best oscillator, the optimum number of stages in,

ahead of, and following the intermediate frequency amplifier, and many other questions relating to the ne plus ultra of receivers.

If there were a best intermediate frequency it would have been found years ago and there would never have been any deviation from it. All superheterodynes subsequent to the day of discovery of that mythical frequency would have used it. It is fortunate, perhaps, that there is no best intermediate frequency, for if there were we would have no hope for making any improvements by selecting a different frequency. Likewise there is no optimum in respect to the other phases of the questions. And that, too, is fortunate, for if we had found the ultimate there would no longer be any hope of improvement, and the whole subject would become stagnate. That would mean death to interest in the superheterodyne, and even radio itself, perhaps. It would be the radio counterpart to "heat death" toward which the universe is inexorably drifting according to the pessimists of physical science.

## Phases of Superheterodyne Design

In Fig. 1 we have a circuit incorporating nine tubes, and it is of the superheterodyne type. What follows is not to be taken as a description of a superheterodyne but merely as a discussion of the various phases of a circuit of this type. The receiver is in the process of building but the final design has not yet been decided on. Much may have to be weeded out and other parts may have to be added but it will emerge as a practical superheterodyne, and just as soon as it does the constructional details will be presented.

The very first thing in the circuit is a volume control P1. Why is this placed first? Because if the volume control is put in the antenna circuit the signal intensity level will be the lowest in every part of the circuit and distortion and cross modulation will be the least possible for a given output of sound. The antenna circuit is the only logical place for a manual volume control. In most commercial receivers the manual volume control is placed in this position, but usually this is not enough so that another control has to be placed elsewhere, usually in such a manner that the grid bias on the radio frequency tubes is varied. When there are two they are placed on the same knob so that on the panel there appears to be only one.

## RF Amplifier

The first tube is a radio frequency amplifier the input circuit of which is tuned. Why is a radio frequency amplifier used ahead of the modulator tube? The same or greater gain could be obtained by making this tube an intermediate frequency amplifier placed after the modulator tube. But if it were made an intermediate frequency amplifier the circuit would be less stable since there would be three intermediate tubes and four intermediate tuners. If there is any pickup at all directly by the intermediate amplifier this would cause greater interference than if only two intermediates were used.

Moreover, using a radio frequency amplifier does not increase the difficulty of tuning because the same number of tuners would have to be used anyway in order to suppress image interference. But why not choose an intermediate frequency so that the receiver is "one-spot" and thus eliminate image interference? Because there is no such frequency and a "one-spot" super is only a fantastic



# perheterodyne Design

Anderson

dream entertained only by those who are unfamiliar with the subject. Tying the condensers together so that a given signal can only be tuned in at one spot on the dial does not make the receiver "one-spot" any more shutting the eyes hides a person from those who keep their eyes open.

The thing to do about multiple response is to accept it as inevitable and then do what is possible to minimize the trouble. If the RF tuner is reasonably sharp and if the intermediate frequency is not too low, no appreciable trouble will be experienced from multiple response. Practically there will be only one; actually there will be an infinite number of responses. Let's be practical.

## Being Practical

Since we desire to be practical on the subject of image interference, we use two radio frequency tuners ahead of the modulator tube and make these tuners as selective as we can with practical coils and condensers. Being practical requires that we gang the two variable condensers and that we put the two on the same control as the oscillator condenser. Thus condensers C1, C2, and C23 are on the same control on the panel.

Ganging the condensers cannot be done successfully by simply placing the condensers on one control. We have to make adjustments of both the fixed inductances and the minimum capacities. We have to make sure that the inductances are equal, assuming that the condensers are equal, and then adjust the trimming condensers Ca and Cb. Even that is not sufficient if the oscillator condenser is also to be on the same gang, because the oscillator will not cover the same tuning range as the radio frequency tuners.

Let us turn to the oscillator. Before we can do much about ganging the oscillator condenser to the other tuning condensers we should have a good idea of what the intermediate frequency is to be, because the frequency band covered by the oscillator depends not only on the band to be covered by the radio frequency tuners but also on the value of the intermediate frequency. As most commercial superheterodynes now use 175 kc in the intermediate channel let us use that as an illustration, and not as an admission that that is the best frequency.

Well, the radio frequency tuners are to cover the band from 550 to 1,500 kc if the receiver is for broadcast reception. It has been found that, as a rule, the higher oscillator frequency response is stronger than the lower and that it has other advantages as well. Hence the oscillator is to cover the band from 725 to 1,675 kc, which is obtained by adding 175 to the limits for the broadcast band.

## Condenser Ratios

Whatever the absolute values of the tuning condensers used, the ratio of the maximum capacity to the minimum in the radio frequency circuits must be 7.44. In the oscillator the corresponding ratio for the case under discussion must be 5.34. It is clear that if the three condensers on the same shaft are alike that both the oscillator and the RF circuits cannot be tuned without doing something to the oscillator condenser so that the capacity in that circuit does not change so fast as the capacity in either of the other circuits. We must treat the condenser so that its capacity changes in the ratio of 5.34 to one while the capacity in each of the other circuits changes in the ratio of 7.44 to one.

The first step in the treatment is to put a condenser C25 in series with the tuning condenser C23. This reduces the capacity by an amount depending on the capacity of the fixed condenser in respect to the capacity of the variable. And what is more important, it changes the rate of change of the combined capacity as the value of the variable C23 is changed. It requires a very particular value of the fixed condenser in order to get the right value of the series combination. Hence we put a midget condenser C24 across the fixed and adjust the midget until the combination of C24 and C25 has the desired value.

But this alone is not sufficient. We must establish a certain minimum capacity, and this may be entirely different from the minimum capacity of the combination C23, C4, and C25. Hence we put a midget condenser C26 across the other combination and adjust this midget until the minimum capacity of the entire combination is correct. By proper choice of the series capacity C24, C25 and the shunt capacity C26 it is possible to change the rate of change of the combined capacity as C23 varies until it has the value 5.34, the required value in our special case.

## Tied at Two Points

The rate of change of the oscillator capacity will not be just right throughout the range of C23, but the two auxiliary capacities, the series C24 and C25 and the shunt C26, will tie the circuits together exactly at two points. If these two points be chosen at suitable places, say at 600 and 1,400 kc in the broadcast band, there will be very little deviation at points in between or outside the points tied.

By tying the points is meant that the two radio frequency tuners are set at exactly 600 and 1,400 kc and the oscillator at 750 and 1,575 kc. As soon as the gang condenser is tuned a little the tun-

ing will not be exact, but may be five or 10 kc off. For all off points the oscillator will mainly determine the maximum sound, the others being off tune when a maximum occurs at any off station. The reason for this is that the intermediate frequency tuner is many times more selective than the radio frequency tuner, and the intermediate tuner selectivity appears as sharpness on the oscillator. Of course, when the tuning is off considerably, and when the RF is very sharp, even the RF tuner will contribute to the determination of the maximum, but in this case there will be a lowering of the sensitivity of the receiver.

To avoid a great diminution in the sensitivity because of detuning the radio frequency tuner must not be too selective. And it does not have to be if the intermediate frequency is 175 kc or higher because the main object of the radio frequency tuner is to suppress image response, and that means that broadcast frequencies differing by twice the intermediate frequency must be suppressed. For example, if we want to tune in a broadcast frequency of 900 kc the radio frequency tuner must be sharp enough to suppress thoroughly stations operating on 550 and 1,250 kc. It does not require a great selectivity to do that. Hence we need not worry very much about the selectivity of the two RF tuned circuits.

## Type of Oscillator

The type of oscillator to use in a superheterodyne does not make a great deal of difference. The main thing is to have an oscillator that oscillates over the entire tuning range. There is half a dozen oscillator circuits, any one of which can be used. The tuned grid-plate has been very popular with superheterodyne designers but it suffers from the fact that neither side of the tuning condenser can be grounded. For this reason it is not suitable for a circuit in which the condensers are ganged with a common grounded rotor. The tune grid oscillator is suitable in a case of this kind and for that reason it is shown in the diagram.

The most common tuned grid oscillator in superheterodynes is one in which the bias is zero and a grid leak and condenser combination is used to maintain the grid negative. Apparently the only reason for using this is that it oscillates on a lower plate voltage. In the circuit in the figure the oscillator tube is biased just as an amplifier, which is entirely satisfactory.

One important thing about the oscillator is that it should generate a wave as pure as possible so that the harmonics will be weak. If the harmonics are strong responses will occur on them as well as on the fundamental. The effect of these will be practically eliminated by the ganging of the condensers because the RF amplifier will not be in tune to any harmonic of the oscillator. But if there are harmonics in both the oscillator output and that of the radio frequency amplifier they may give rise to growling and whistling noises.

## Eliminating Harmonics

Harmonics are usually prevented in the oscillator by forcing the circuit to oscillate feebly. One way of doing this is to use the smallest tickler that will sustain oscillation at any point of the tuning range. Another is to connect only a portion of the tuned circuit in the grid, usually half. A tap is placed at the middle turn of the tuned winding and connected to the grid, or a centertapped high resistance is connected across the tuned circuit with the center connected to the grid.

Still another way is to couple the oscillator and the modulator resonantly. The only practical way of doing this is a broadcast superheterodyne is to place the pickup coil nearer the tuned circuit than the tickler and making the coupling between the tuned and pickup windings fairly loose. If either the oscillator output or the output of the RF amplifier is free from harmonics the output of the modulator will be free from troublesome harmonics.

## Type of Modulator

When a screen grid tube is used as modulator, as in the present instance, there are three main methods of coupling the pickup coil to the modulator, first, in the screen lead, second, in the control grid lead, and third, in the cathode lead. The first method is illustrated in this instance. The control grid connection is rejected because the pick-up coil is then on the live side of the second tuned circuit and there are adverse capacity effects. The cathode connection is rejected because it would require either an oscillator coil of six terminals or else a different modulator. That is, the grid bias method could not be used.

Just as it makes little difference what oscillator is used, so it makes little difference what method of coupling the oscillator to the modulator. The writer is partial to the method illustrated, mainly for practical reasons.

The pickup coil and the tuned winding of the oscillator are placed far apart in the drawing. Actually they are wound on the same form. The pickup is one side of the tuned winding and the tickler on the opposite.



**A Question and Answer Department** conducted by Radio World's Technical Staff. Only Questions sent in by University Club Members are answered. Those not answered in these columns are answered by mail.

# Radio University

Annual subscriptions are accepted at \$6 for \$2 numbers, with the privilege of obtaining answers to radio questions for the period of the subscription, but not if any other premium is obtained with the subscription.

## A Five-Tube Receiver

I HAVE a Polo 245 power transformer and a Polo choke and desire to use them in a receiver comprising three 224 tubes, one of which is the detector, a 245 output tube and a 280 rectifier. Will you kindly publish a diagram of such a circuit? Is a circuit of this type practical? I desire only local stations but I want first class quality, and it is for this reason that I wish to omit all but the last stage of audio.—J. B.

You will find such a diagram in Fig. 876. All the design values are given on the drawing to enable you to build it. For local reception this receiver is quite satisfactory, and the quality is excellent.

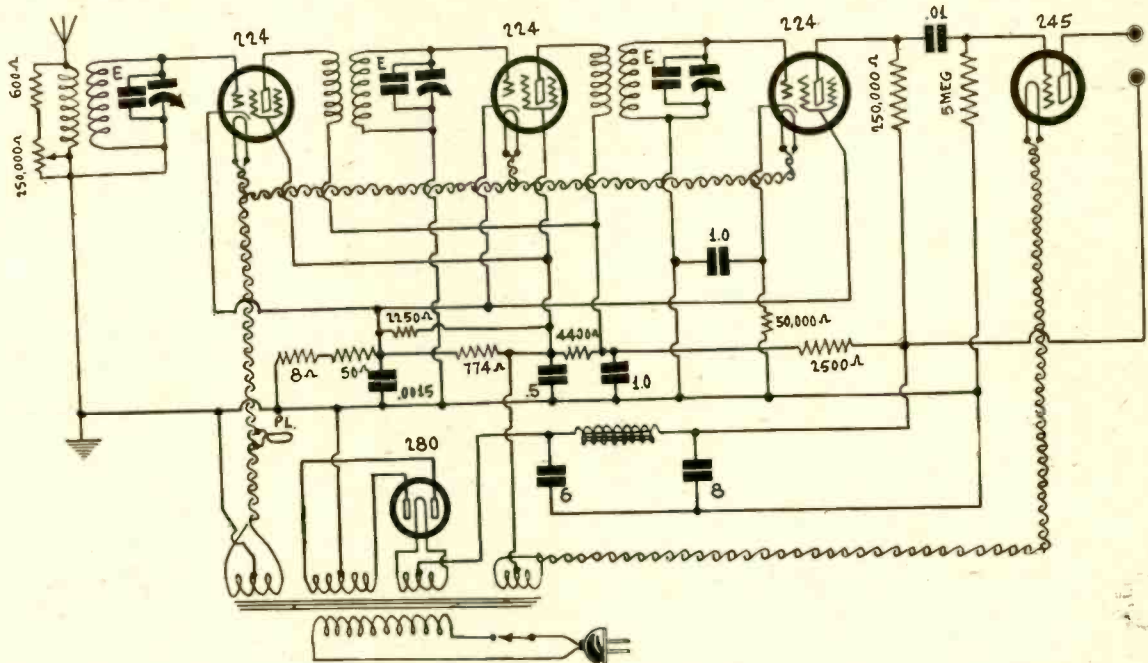


FIG. 876

A circuit for Polo parts.

this frequency and the known frequency of the station is the intermediate frequency. Repeat this process on several stations and average the results. If your oscillator condenser cannot be turned independently of the others, you can open up the live

## Hiss In Receivers

WHAT is the cause of the hissing in a radio receiver? I have noticed that it ceases in most instances when the broadcast station to which the receiver is tuned is shut down.—B. C.

There are many causes of hiss in a receiver, or in the output of a receiver. Some of the hiss originates in space and is a form of static. Then it may come from the tubes, both receiving and transmitting. Electrons are not emitted from the cathode uniformly but in a very irregular manner, and the irregularity gives rise to a hiss. Irregular conductivity of wires and grid leaks is also a source of hiss.

## Wattless Power Component

WHAT is the meaning of the wattless power component? It seems to me that it is a contradiction of terms, for if the watt is the unit of electrical power how can a power component be wattless?—W. G. L.

Sure it is a contradiction of terms and every time one sees "wattless" one inevitably thinks of "witless." But the term is well established and has a very definite meaning. When an alternating voltage is applied in a circuit containing inductance and resistance, or capacity and resistance, the current that flows either lags behind the voltage or it leads it, lagging when there is inductance and leading when there is capacity. The total power involved is the product of the voltage and the current. But since the voltage and current are out of phase by a certain amount, or by a certain time, the total power involved is not dissipated. Only that component for which the current and the voltage are in phase results in dissipation or useful work, as the case may be. For the remaining power involved the current and the voltage are 90 degrees out of phase, or a quarter period out of phase. This power is not dissipated and it does no work. Although it is measured in watts it is called wattless.

## Determining the Intermediate Frequency

WILL you kindly suggest a simple method of determining the intermediate frequency of a Superheterodyne? I have built such a circuit and it works all right but I have no idea of what the intermediate frequency is.—G. D. F.

If your oscillator condenser can be turned independently of the RF condensers, calibrate the oscillator dial against broadcast stations and plot a curve with frequency against dial settings. Then tune in a station the frequency of which you know and note the dial setting. Look on the calibration curve what frequency is represented by this setting. The difference between

side of the condenser and substitute an external condenser provided with a good dial.

## Distributed Capacity of Coils

IS there any relationship between the distributed capacity of a solenoid and the dimensions of the coil? If so, what is it and how can it be used for determining the distributed capacity?—C. T. C.

There is no definite relationship, that is one that can be used for determining accurately the distributed capacity. However, of the coil is far from other conductors the distributed capacity is approximately proportional to the diameter and it is equal numerically in micromicrofarads to the diameter in centimeters. Let us illustrate. The diameter of the coil is 3 inches. Every inch contains 2.54 centimeters. Hence the diameter of the coil in centimeters is 7.62. Therefore distributed capacity of the coil, when not close to shields and other conductors, is approximately 7.62 mmfd. This rule is only good for making estimates. It should be remembered that the capacity is higher when the coil is close to shielding and also that the distributed capacity of the coil is not the only distributed capacity in a tuned circuit connected to a tube.

## Poor Quality, Circuit Checks OK

I HAVE a receiver which gave good results for nearly a year. Then gradually it began to fall, the sensitivity and the quality going down. Now it is so bad that it is impossible to get any enjoyment out of listening in. Tubes are all OK and the circuit tests all right. What do you think is the matter?—L. N.

If the tubes are all OK and the circuit tests all right there is nothing at all wrong with the set. The poor quality must be pure imagination. But let us suppose that there is something wrong with the circuit, something that has not been tested. Since the trouble developed gradually it is due to something that deteriorated with use. Although you do not say so, I suspect that you have electrolytic condensers in your B supply and that these have dried out. Remove them and put in new condensers.

## Inspect the Antenna

FOR about a year my set gave me excellent results, but now I cannot get any distant stations. Even the locals don't come in unless I turn up the volume control to the limit, and then there is much noise. I have had two service men to look it over. One changed the detector tube and the other did something else for which he charged me five bucks. They both agreed that there was nothing wrong with the set when they got through







# The January "Proceedings"

## Studio Design, Frequency Measurement and Output Tubes Discussed

**T**HE Design and Construction of Broadcast Studios" is discussed by O. B. Hanson and R. M. Morris, of the National Broadcasting Company, New York, in the January issue of "Proceedings of the Institute of Radio Engineers." The subject is treated from the points of view of location, type of building, sound insulation, air conditioning and ventilation, acoustic treatment, lighting, decoration of studios, and technical operating requirements.

Much emphasis is placed on the acoustic treatment of the studios, to be suitable for broadcasting purposes. This treatment must be such that no sound can penetrate into the studio from outside the building nor from another studio or room. Moreover, it must be such that the period of reverberation within the studio does not exceed a certain time which has been found experimentally to give satisfactorily results. Walls, floor, ceiling, fixtures and furniture must be treated with sound absorbing material which stops echoes of all frequencies in the entire musical range. The studio should be built like a box within a box with the inner box mechanically insulated from the outer to prevent vibrations from being transmitted from the steel structure of the building to the studio.

### Size and Shape of Studio

It has been found experimentally that the dimensions of the studio to be most satisfactory both from esthetic and acoustic considerations should be approximately in the ratio 2:3:5 for the height, width, and length, respectively. Therefore the width should be 1.5h and the length, 2.5h, where h is the height of the room. The capacity of a room, in terms of number of artists, is approximately proportional to the volume. From this proportion the authors derive a formula for determining the height of a studio when the number of artists is known. This formula is height equals 5.87 times the cube root of  $N + 2.5$ , where N is the number of artists. The 2.5 is derived from the condition that the height of the studio is not to be less than 8 feet. From this formula and the previously given relations between height, width, and length all the dimensions of the studio can be determined. Illustrations of the principles of design are drawn from the New York and Chicago studios of the National Broadcasting Co.

### Accurate Measurement of Frequency

E. L. Hall, Radio Section, Bureau of Standards, describes a method of measuring transmitted wave frequencies at 5,000 and 20,000 kilocycles per second to a high order of accuracy. The method depends on the use of harmonics of standard, frequencies which are known to a high order of precision. It is estimated that frequencies of the order of 20,000 cycles per second can be measured to an accuracy of 2 parts in a million, which in this case means 40 cycles.

### Output of Tubes

C. E. Kilgour, Chief Research Engineer, Crosley Radio Corporation, contributes a paper on "Graphical Analysis of Output Tubes Performance." This paper first outlines the graphical analysis of power tube output as applied to the case of a simple resistive load and then extends the method to the case when the resistance load is different for direct and alternating current. It is shown that in this case the various load lines cannot be drawn through a common operating point because the effective plate voltage shifts when rectification occurs. The important point in this paper is the attention it calls to the error committed in deducing the output characteristics of power tubes with pure resistance loads when in fact a power tube never is operated that way in radio reception. It is either operated with a speaker in the plate circuit or with some other inductive device between the speaker and the tube. The paper outlines the correct analysis when the load is partly resistive and partly inductive and when there is a difference between the DC and the AC load. The paper deserves careful study.

J. D. Miner, Westinghouse Electric and Manufacturing Co., Springfield, Mass., contributes an interesting paper on "Power

Equipment for Aircraft Radio Transmitters." This paper covers all of the systems of power equipment now used or contemplated for supplying power to aircraft radio transmitters. The various types of power equipment are described and the advantages and disadvantages of each type pointed out. The types of power equipment discussed are (1) the wind driven generator, (2) the dynamotor, (3) the main engine driven generator, (4) the auxiliary engine generator set, (5) the combination wind driven and dynamotor, and (6) the constant speed main engine driven alternator. The discussion brings out the fact that no available type of power equipment can be regarded as entirely satisfactory, as no type of power equipment is sufficiently superior to other available types that its use can be expected to become universal. There is a pronounced tendency towards the use of main engine driven generators, and the chief obstacle to this type is that it does not provide for emergency operation.

### Polyphase Rectification

In the ordinary B supply unit for broadcast receivers the rectification is single phase, because the supply is single phase. In broadcast stations, or in many of them, polyphase supply is used. There has been very little information available on polyphase rectifiers in radio literature. There is more now than R. W. Armstrong, Westinghouse Electric and Manufacturing Co., has published a paper on "Polyphase Rectification Special Connections." Characteristics of various rectifier circuits and factors governing their selection are given in this paper. It is pointed out that, in general, the double 3-phase circuit is most desirable from the standpoint of transformer and tube capacity requirements for mercury pool type tubes and the 6-phase single Y for hot cathode mercury vapor tubes or high vacuum tubes, but that other factors may make other circuits more desirable for particular cases. Data are given 3-, 4-, 6-, and 12-phase rectifiers using T-connected transformers, so that fewer transformers are required. Since it is cheaper to build two large transformers than three smaller ones of approximately the same total capacity, the connection may permit a saving in transformer cost. The voltage doubling circuit is discussed, its relation to other single phase circuits shown, and its characteristics given as a function of the product, CR, of condenser capacity and resistance load.

### Heaviside Layer Study

P. A. de Mars, T. R. Gilliland, and G. V. Kenrick report on "Kennelly-Heaviside Layer Studies" carried out cooperatively by Tufts College, Mass., Bureau of Standards, Washington, D. C., Naval Research Laboratory, and Department of Terrestrial Magnetism. Studies were made at 1,400 kc and higher frequencies. Evidence is found in support of the existence of several ionized strata, such as postulated by Appleton and Eckersley. Numerous oscillograph records of the results obtained are given.

T. R. Gailliland reports on "Kennelly-Heaviside Layer Height Observations for 4045 kc and 8650 kc." The height is variable and falls in the range of 225 to 337 kilometers. During daylight the height is fairly constant increasing slightly from noon to sunset. After sunset the height is very irregular but increases rapidly toward midnight.

### Detection of Modulated Waves

Charles B. Aiken, Bell Telephone Laboratories, New York, contributes a mathematical paper on "The Detection of Two Modulated Waves Which Differ Slightly in Carrier Frequency." It deals with the detection of two waves, modulated with the same or with different audio frequencies, and differing in carrier frequency by several cycles or more. Both parabolic and straight line detectors are discussed and expressions are derived for all the important audio frequencies present in the output of these detectors when such waves are impressed. Interference areas that can be expected under different conditions are treated and graphs shown to illustrate the interference patterns. The inevitable appendix, characteristic of contributions from the Bell Laboratories, is there, too.

## Floor Vibration a Difficulty

Your new radio set of 1930 or 1931 model reproduces low tones as they have not been heard in former years. One problem that arises is the excessive vibration that occurs in flooring and walls. Have you ever lived in apartment house and listened to the weird effects you get from these vibrations brought to you from your neighbor's radio?

The simplest way to eliminate this is to "insulate" the radio

cabinet from the floor or wall. Thick sponge rubber feet, or "shock absorbers" will be satisfactory, or thick felt strips. Vibrations may still be present to a slight extent, but those transmitted through the legs of the cabinet or the table on which the radio is placed are the principle starting point for these low-vibration effects.

If the receiver cabinet is too close to a "vibrating" wall merely move the cabinet away to check vibration.



# STATE TAX ON SETS IS VOIDED BY U. S. COURT

Columbia, S. C.

A decision prohibiting State taxation of radio receiving set owners, as provided by a South Carolina law, has been handed down in the Federal District Court, in the first test case.

An interlocutory injunction against enforcement of the South Carolina law was granted by the Federal Court and restrains collection of the proposed taxes on radio receiving sets. The decision was made by three Federal Judges, Circuit Judge Parker of North Carolina, and District Judges Cochran and Glenn of South Carolina.

The Court's decision was made in the test case of a North Carolina broadcast station, WBT of Charlotte, brought at the instance of the Radio Manufacturers' Association. WBT contended that radio is interstate commerce and not subject to taxation by a State. The court's decision sustained the contention that the South Carolina law is unconstitutional as an interference with interstate commerce and cannot be enforced.

## Held to Be Interstate Commerce

"There can be no doubt," said the opinion, "that communications by radio constitute interstate commerce. It has been so held by numerous courts, and the decisions of the Supreme Court of the United States defining interstate commerce necessarily lead to that conclusion.

"Certainly under the facts of the present case, the plaintiff (WBT), through its broadcasting plant, is engaged in interstate commerce. The receiving sets in South Carolina are essential to the reception of the communications by the South Carolina audience. In other words, the receiving sets are absolutely essential instrumentalities of the interstate commerce in which plaintiff is engaged."

Continuing, the Federal Court said:

"Here the tax is not a general property tax, but a license tax for the privilege of using an instrument of interstate commerce."

The South Carolina law, passed last year, levied on owners of radio receiving sets a graduated tax ranging up to a maximum of \$2.50 per set. It was the first State law against owners of receiving sets. The WBT case was one of three attacks made upon the South Carolina law at the direction of the Radio Manufacturers' Association in the interests of the radio-owning and buying public, as well as the radio industry.

## Saving Estimated

John W. Van Allen of Buffalo, general counsel for the Radio Manufacturers' Association, had charge of the contest litigation, and the local proceedings were in charge of Buist & Buist, of Charleston, South Carolina.

Explaining the decision, Mr. Van Allen said:

"With forty-eight States interested in the outcome, the decision, if sustained, will save the radio set owner from possible taxation in a similar manner in forty-eight States a sum ranging somewhere from \$25,000,000 to \$50,000,000 yearly and gives the American family radio, free and unhampered by petty license tax on the privilege to tune in for information, entertainment and education."

## Literature Wanted

Readers desiring radio literature from manufacturers and jobbers concerning standard parts and accessories, new products and new circuits, should send a request for publication of their name and address. Send request to Literature Editor, RADIO WORLD, 145 West 45th Street, New York, N. Y.

- Dean Burroughs, Box 216, Wilder, Vt.
- Lenhart S. Zacune, 2405 Grand Ave., Bronx, N.Y. City.
- C. J. Dry, 1421 South 17th, Fort Smith, Ark.
- Frank Johnson, Jr., 1328 San Bruno Avenue, San Francisco, Calif.
- Harold C. Todd, Fanwood, N. J.
- S. W. Sullivan, 159 West 26th St., Erie, Pa.
- F. A. Rambie, Jr., 433 Harriman Pl., San Antonio, Texas.
- I. Kaufman, 160 Market St., Passaic, N. J.
- F. P. Jones, 1513 Vance Ave., Chattanooga, Tenn.
- Harold Dunham, 101 East Church, Oxford, Ohio.
- Louis De Marco, 1623 N. Kimball Ave., Chicago, Ill.
- Louis Laurent, Box 213, Piper City, Ill.
- John Burik, Box 121, Derry Pa.
- George C. Anderson, 2300 Shenandoah Ave., St. Louis, Mo.
- P. D. Muldoon, 898 Ellicott Square, Buffalo, N. Y.
- Edw. H. Bodenstein, Newport Schools, Newport, Ky.
- Rothert Electric Co., Cresco, Iowa.
- S. M. Nance, 215 Garrison Ave., Ft. Smith, Ark.
- J. F. Stephens, 2811 Cable Ave., Lincoln, Nebr.
- H. A. Adams, Box 294, Rutland, Vt.
- C. H. Ames, 1702 S. 52nd St., Tacoma, Wash.
- V. Wright, 622 Bloomfield Court, Birmingham, Mich.
- G. E. Hanes, Maybell, Colo.
- Peter Ambrose, 3900 E. St., Detroit, Mich.
- Robins Radio Repair, 4133 Kirby Ave., Cincinnati, Ohio.
- Oscar Hook, R. F. D. 2, Birdsboro, Pa.
- Wm. Edmondson, Pan American Union, Washington, D. C.
- Harry Knatz, 726 S. Ashland, Chicago, Ill.
- Walter O. Locke, 301 Montooth St., Pittsburgh, Pa.
- H. H. Benson, Naval Academy, Annapolis, Md.
- Dr. J. N. Bradley, 1015 Chrisler Ave., Schenectady, N. Y.
- Melvin H. Larson, W. 105 Knox Ave., Spokane, Wash.

# PASTOR'S WMBJ OWED \$115,000

Washington.

Attorney Nathan B. Williams, representing WMBJ, of Pittsburgh, that was operated by the Rev. John W. Sproul, has protested to the Federal Radio Commission against the report of Examiner Elmer W. Pratt denying renewal of the station's license. The station operated on the 1,500 kc channel, using 100 watts, and had an unlimited time schedule. The creditors of the Rev. John Sproul, including Pittsburgh Broadcasters, Inc. and William S. Walker, have sought to obtain the assignment of WMBJ at a general hearing before the Commission.

Examiner Pratt has recommended that the requested assignment be granted, and Attorney Williams objects. Exception is taken to the recommendation of the examiner with regard to the financial status of the Rev. Mr. Sproul. The past record of the station is cited as a reason why the Commission should consider the public support accorded the station, which, it is pointed out, also is the only purely local broadcaster.

The applicant admits that there were liabilities to the extent of approximately \$115,000 but submits that this was reduced by \$89,000 and that at no time was the operation of the station hampered due to debts, until the creditors seized the property, and then afterward appeared before the Commission seeking to erect it in their own name.

## KFYR POWER INCREASED

KFYR, Bismark, N. D., is now operating on 2,500 watts daytime and 1,000 watts at night. It formerly used 500 watts.

# TRADE OUTLOOK IS FAVORABLE

Chicago.

President Morris Metcalf, of the Radio Manufacturers Association, declared that prospects for 1931 in radio are more favorable. The radio industry leaders are meeting here to canvass conditions affecting prospective business and make plans for measures by the Association to promote all radio interests.

"Radio manufacturers entered the new year with practically no problem of over-production," said President Metcalf of the manufacturers national organization. "There is very little distress merchandise in radio left in the market, because 1930 manufacturing schedules were held very closely to coincide with public demand. This is in marked contrast to the conditions prevailing a year ago and most manufacturers who have survived that period now are in a healthy condition so far as inventory is concerned.

"There are many new and broad markets open to the radio industry. Radio is nowhere near the saturation point. In addition to the large normal replacement market for modern radio sets and the discarding of obsolete receivers, there is a great rural market now opening for radio sales, especially if the Federal Radio Commission grants higher power to broadcasting stations operating on clear channels.

"In addition, there is a tremendous market for the equipment of offices, factories, schools, auditoriums and other places in which radio has been comparatively little used. Special broadcasting programs for these interests already have been planned for 1931 by broadcasting interests.

"The outlook for the radio industry is not at all discouraging and with an undoubted return of better general conditions, our industry faces the future with confidence."

## Gold Seal Loses Point In RCA Tube Suit

The motion made on behalf of Gold Seal Electrical Company, Inc., manufacturer of radio vacuum tubes, for a preliminary injunction restraining the Radio Corporation of America from proceeding against the Gold Seal Company in two suits for alleged infringement of patents has been denied by Judge Nields in the United States District Court for the District of Delaware.


The Gold Seal Company charged that the patents upon which the Radio Corporation was bringing suit were held in violation of the Sherman Anti-Trust Act.

## New Corporations

- Theatre Magazine Radio Bureau, advertising agencies—Atty. E. R. Kayes, 36 West 44th St., New York, N. Y.
- Radio Auctioneers Corp., radios—Atty. W. Weisman, 276 Broadway, New York, N. Y.
- Blue Seal Sound Devices, recording apparatus—Atty. H. J. Robinson, 43 Cedar St., New York, N. Y.
- Otto Grasso Co., radios—Atty. M. Burt, 679 East 220th St., New York, N. Y.
- Parne's Radio Shop—Atty. J. Frank, Woolworth Building, New York, N. Y.
- Webster Radio Systems, broadcasting—Attys. Banzshag & Richter, 130 West 42nd St., New York, N. Y.
- Broadcast Service Corp., radio broadcasting—Attys. Byrne & Byrne, 26 Court St., Brooklyn, N. Y.
- Barty Radio Service—Atty. L. Stansky, 251 Broadway, New York, N. Y.
- Public Service Broadcasting Co., Inc., Wilmington, Del., radio broadcasting stations—Corporation Trust Co.



## Multi-Tap Voltage Divider

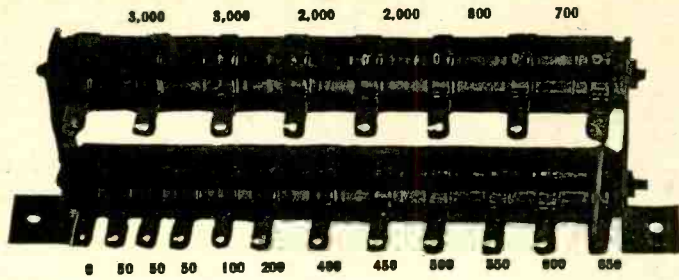

The resistance values between the twenty taps of the new Multi-Tap Voltage Divider are given above. The total is 17,100 ohms and affords nineteen different voltages.

The Multi-Tap Voltage Divider is useful in all circuits, including push-pull and star-sided ones, in which the current rating of 100 milliamperes is not seriously exceeded and the maximum voltage is not more than 400 volts. Higher voltages may be used at lesser drain. Conservative ratings. 40 watts.

**GUARANTY RADIO GOODS CO.**

143 W. 45TH ST., NEW YORK, N. Y.

The expertness of design and construction will be appreciated by those whose knowledge teaches them to appreciate parts finely made.

When the Multi-Tap Voltage Divider is placed across the filtered output of a B supply which serves a receiver, the voltages are in proportion to the current flowing through the various resistances. By making connection of grid returns to ground, the lower voltages may be used for positive bias by connecting filament center, or, in 127 and 224 tubes, cathode to a higher voltage.

If push-pull is used, the current in the biasing section is almost doubled, so the midtan of the power tubes' filament winding would go to a lug about half way down on the lower bank.

Order Cat. **MTVD**,  
List price **\$2.95**,  
\$6.50,  
net price..

## Short-Wave Converter Series

In the November 8th issue of RADIO WORLD there began a remarkable series of articles dealing with the construction of short-wave converters that really do work, and that work well. Besides, the cost of parts is low. One model, 30 to 110 meters, no plug-in coils, may be built of parts costing less than \$5, for battery operation, or for AC with extra filament transformer external, while another model, 10-200 meters, two plug-in coils, using somewhat superior parts, filament transformer built-in, can be made up by you for less than \$10. Surely these are prices within the reach of all.

Low price and high achievement go hand in hand in these designs by Herman Bernard.

The series ran in the November 8th, 15th, 22nd and 29th, and December 6th, 13th, and 20th issues. Send \$1 and we will forward these seven issues and a blueprint of the AC \$5 model.

RADIO WORLD, 145 West 45th Street, New York, N. Y.

Enclosed please find \$1.00 for which send me the November 8th, 15th, 22nd and 29th, and Dec. 6th, 13th and 20th issues, containing the series of articles on short-wave converters of extremely low price, and a blueprint of the AC \$5 model.

Name .....

Address .....

City ..... State .....

## Official Parts for Popular Circuits

Universal Short-Wave Converter, using three 227 tubes; five de luxe precision short-wave air dielectric coils, condensers, chokes, 7"x14" panel, cabinet, etc. Cat. UN-SWC @.....\$24.73

**GUARANTY RADIO GOODS CO.**

143 West 45th Street  
New York City

## RADIO MAP

OF NORTH AMERICA

22 x 22 inches, printed in two colors, bound in cover.

Shows every city from Balboa to Edmonton which has a broadcasting station.

Indexed by states, provinces and cities with key for instant location on map.

Call letters, power and frequency given for each station.

**Accurate; up-to-date**

Scale in miles gives distances between any two cities. Time zones correctly marked.

Just what you have been wanting.

**25 cents**

**THE RADEX PRESS**

1368 E. 6th St. Cleveland, Ohio

## Horn Unit \$1.95



Fidelity Unit, Cat. FDU.

The Fidelity unit is pre-eminent for horn type speakers such as exponential horns. The faintest word from a "whispering tenor" or the tumultuous shout of the crowd or highest crescendo of the band is brought out clearly, distinctly. Stands up to 450 volts without filtering.

Works, right out of your set's power tube, or tubes requiring no extra voltage source. Standard size nozzle and thread. Works great from AC set, battery set or any other set. Push-pull

or otherwise. The casing is full nickel finish, highest polish. This unit can be used in a portable without any horn attached and will give loud reproduction.

Order Cat. FDU, with 50-inch tipped cord; weight, 1/4 lbs.; size, 2 1/2-inch diameter, 2 1/2-inch height. (This is the large size) Price.....\$1.95

**GUARANTY RADIO GOODS CO.**

143 West 45th Street, New York City

## ERLA DYNAMIC CHASSIS, WESTINGHOUSE RECTIFIER—

List price \$25.00; our price \$10.50. Guaranty Radio Goods Co., 143 W. 45th St., N. Y. C.

"RADIO TROUBLE SHOOTING," E. R. Haan. 328 pages, 300 illustrations, \$3. Guaranty Radio Goods Co., 143 W. 45th St., New York.

# Quick Action Classified Ads

Radio World's Speedy Medium for Enterprise and Sales

7 cents a word—\$1.00 minimum—Cash with Order

**RESISTANCES, CONDENSERS, TRANSFORMERS, CHOKE-COILS, etc.** Write for sensational low price list. Bronx Wholesale Radio Company, 5 West Tremont Avenue, New York.

**SALESMEN WANTED. 87 MILES ON 1 GALLON OF GAS?**—Startling Vapor Gas Saver. All Autos, Motorcycles. 1 Free. Critchlow, 3360-A, Wheaton, Ill.

**PRINTING: 1000 BUSINESS CARDS \$2.75 POSTPAID.** Other printing reasonable. Samples free. Miller, (RW), Printer, Narberth, Pa.

**FOR SALE HiQ 30 CHEAP.** F. L. Hanson, Iliou, N. Y.

"A B C OF TELEVISION" by Yates—A comprehensive book on the subject that is attracting attention of radioists and scientists all over the world. \$3.00, postpaid. Radio World, 145 West 45th St., N. Y. City.

"THE PEANUT VENDOR"—Cuban novelty song, 35c, postpaid. "There's Something Missing in Your Eyes"—latest radio fox-trot song hit, 35c, postpaid. The Columbia Print, 145 W. 45th St., New York.

**GOOD VOLUME**, 4 tube, loop Auto Radio blue print 50c. Parts cost \$12 complete. Write me. C. C. Burge (Radio Engineer), 301 E. Park Blvd., Villa Park, Ill.

**RADIO COURSES**, sets, books, bargains. Stephen Plavetich, 1597 East 47th St., Cleveland, Ohio.

**BARGAINS** in first-class, highest grade merchandise. B-B-L phonograph pick-up, theatre type, suitable for home with vol. control, \$6.57; phono-link pick-up with vol. control and adapter, \$3.32; steel cabinet for HB Compact, \$3.00; four-gang .00035 mfd. with trimmers built in, \$1.95; .00025 mfd. Duhiiler grid condenser with clips 18c. P. Cohen. Room 1214, at 143 West 45th Street, N. Y. City.

**H.F.L. MASTERTONE.** List \$195. Sell \$85. World's finest radio. W. J. Reed, Aurora, Ill.

**SMALL MOTOR GEN.** 3 phase, 220 to 7 1/2 volts D.C. Like new, \$75. R. Campbell, 365 Edgewood Ave., New Haven, Conn.

"**MATHEMATICS OF RADIO.**"—A great help to everybody interested in radio. \$2 postpaid. Radio World, 145 W. 45th St., N. Y. City.

**MAGICALLY CLEANS FALSE TEETH—WATAJOY** Wonder Cleaner. Instantly removes film. Cleans and purifies plate. Approved by licensed chemist. Costs about 5c per mo. A big treat awaits you. Prepaid 25c. **WATAJOY LAB.**, Alhambra, Cal.

**HORN UNIT, \$1.95**—This is the Fidelity Unit and has stood the test of time. Guaranty Radio Goods Co., 143 W. 45th St., New York.



## A WIDE CHOICE OF PARTS

### UNSHIELDED BROADCAST COILS ON 3" DIAMETER BAKELITE

- (Cat. SGT-5)—Three circuit tuned for .0005 mfd. condenser, for use where the untuned high impedance primary is in the plate circuit of a screen grid tube. The tuned secondary may be connected to any type tube. . . . . \$ .90
- (Cat. SGT-3)—Same as above only for .00035 mfd. condenser. . . . . \$ .80
- (Cat. 5-HT)—Special three-circuit tuner for .0005 mfd. tuned primary in plate circuit of a screen grid tube; untuned secondary. . . . . \$ .95
- (Cat. 3-HT)—Same as Cat. 5-HT, except that it is for .00035 mfd. tuning. . . . . \$ .95
- (Cat. T-5)—Standard 3-circuit tuner for .0005 mfd., where primary is for any type of tube other than plate circuit of screen grid tube. . . . . \$ .80
- (Cat. T-3)—Same as T-5, except for .00035 mfd., condenser instead of for .0005. . . . . \$ .80
- (Cat. 2-R5)—Radio frequency transformer for .0005 mfd. condenser where high impedance untuned primary is in plate circuit of a screen grid tube, and secondary is tuned by .0005 mfd. . . . . \$ .60
- (Cat. 2-R3)—Same as 2-R5, except that it is for .00035 mfd. tuning. . . . . \$ .60
- (Cat. 5-TP)—Radio frequency transformer for use where primary is tuned and placed in plate circuit of screen grid tube, while secondary is not tuned. For .0005 mfd. . . . . \$ .55
- (Cat. 3-TP)—Same as Cat. 5-TP, except that it is for .00035 mfd. tuning. . . . . \$ .55
- (Cat. RF-5)—Radio frequency transformer for .0005 mfd. tuning, where untuned primary is in plate circuit of any type tube except screen grid. Useful also as antenna coupler. . . . . \$ .55
- (Cat. RF-3)—Same as Cat. RF-5, except that it is for .00035 mfd. tuning. . . . . \$ .55

### RADIO FREQUENCY CHOKES

- (Cat. 50-MLH)—A radio frequency choke coil for filtration in broadcast use, as in screen or plate leads, particularly detector plate, or in the output (plate circuit) of a short-wave converter. Mounting bracket supplied. Not shielded. . . . . \$ .47
- (Cat. QML)—A radio frequency choke for short-wave work only. Inductance, 1/4 millihenry. Wound on 3/8" diameter bakelite rod, with connecting lugs at end, and mounting bracket. . . . . \$ .47

### FILTER AND BY-PASS CONDENSERS

- (Cat. HV-1)—Compact 1 mfd. filter condenser, for use in filter section of any B supply intended to work 245 tubes, single or push-pull, and rest of tubes in receiver. . . . . \$1.50
- (Cat. HV-2)—Compact 2 mfd. condenser for 245 B supply. . . . . \$ 2.50
- (Cat. AVX-8)—Compact 8 mfd. Aerovox dry electrolytic condenser with mounting bracket, for 245 B supply. . . . . \$ 1.47
- (Cat. LV-1)—1 mfd. low-voltage condenser for by-passing, 200 v. DC rating. . . . . \$ .50
- (Cat. LV-2)—2 mfd. low-voltage condenser for by-passing, 200 v. DC rating. . . . . \$ 1.00
- (Cat. LV-4)—4 mfd. low-voltage condenser for by-passing, 200 v. DC rating. . . . . \$ 2.00
- (Cat. SUP-31)—Three 0.1 mfd. bypass condensers in one compact case, 200 v. DC rating. . . . . \$ .57

### KNOB AND DIALS

- (Cat. KNB-2)—2-inch diameter moulded bakelite black knob, no pointer; 1/4" shaft. . . . . \$ .18
- (Cat. KNB-15)—1 1/2" diameter moulded bakelite black knob, 1/4" pointer; 1/4" shaft. . . . . \$ .18
- (Cat. KNW-15)—1 1/2" diameter moulded bakelite walnut knob, with pointer; 1/4" shaft. . . . . \$ .18
- (Cat. MCD)—Marco vernier dial; moulded bakelite; black; pilot light window. . . . . \$ .80
- (Cat. NAT-H)—National velvet vernier drum dial, type H, with modernistic escutcheon, color wheel (rainbow feature). . . . . \$ 3.13
- (Cat. NAT-G)—National velvet vernier flat type dial, for use when tuning condenser shaft is at right angles to the front panel; modernistic dial; single color projection. . . . . \$ 2.05
- (Cat. NAT-VBD)—National velvet vernier black moulded bakelite circular dial, variable ratio lever 8-1 to 20-1 reads 0-100-0; with dial light and bracket. . . . . \$ 1.70

### BLUEPRINTS

- (Cat. BP-3A)—Blueprint of three-tube Supertone short-wave converter, using 227 tubes; filament transformer external; coil winding data, list of parts, schematic diagram included. . . . . \$ .25
- (Cat. BP-DLC)—Blueprint of DeLuxe short wave converter, using two National VBD dials, two Hammarlund SFL 0005, precision plug-in coils. . . . . \$ .25
- (Cat. BP-33)—Blueprint of the HB-33, seven-tube screen-grid battery set, using 222s for RF, push-pull 171A output. . . . . \$ .25
- (Cat. BP-44)—Blueprint of the HB-44, eight-tube AC screen-grid set, 245 push-pull output; screen-grid power detector. . . . . \$ .25
- (Cat. BP-SGD-4)—Blueprint of 4-tube battery Diamond of the Air, one stage RF 222, regenerative detector, two transformer audio. . . . . \$ .25
- (Cat. BP-PPBD)—Blueprint of 5-tube battery Diamond, extra tube due to push-pull output, either 112A or 171A. . . . . \$ .25
- (Cat. BP-DBX)—Blueprint of 4-tube Diamond for AC operation, screen-grid RF; no B supply, as 180-volt B eliminator is to be used. . . . . \$ .25
- (Cat. BP-UNB)—Blueprint of 4-tube Universal, with 222 RF; battery operation. . . . . \$ .25
- (Cat. BP-LIB)—Blueprint library of AC hookups. . . . . \$ .25

### GUARANTY RADIO GOODS CO.

143 West 45th Street, New York, N. Y.

Enclosed please find \$..... for which please ship at once the following:

<input type="checkbox"/> SGT-5 @ 90c	<input type="checkbox"/> LV-4 @ 2.00
<input type="checkbox"/> SGT-3 @ 90c	<input type="checkbox"/> SUP-31 @ 57c
<input type="checkbox"/> 5-HT @ 95c	<input type="checkbox"/> KNB @ 18c
<input type="checkbox"/> 3-HT @ 85c	<input type="checkbox"/> KNB-15 @ 18c
<input type="checkbox"/> T-5 @ 80c	<input type="checkbox"/> KNW-15 @ 18c
<input type="checkbox"/> T-3 @ 80c	<input type="checkbox"/> MCD @ 60c
<input type="checkbox"/> 2-R5 @ 60c	<input type="checkbox"/> NAT-H @ 3.13
<input type="checkbox"/> 2-R3 @ 60c	<input type="checkbox"/> NAT-G @ 2.05
<input type="checkbox"/> 5-TP @ 55c	<input type="checkbox"/> NAT-VBD @ 1.70
<input type="checkbox"/> 3-TP @ 55c	<input type="checkbox"/> BP-3A @ 25c
<input type="checkbox"/> RF-5 @ 55c	<input type="checkbox"/> BP-DLC @ 25c
<input type="checkbox"/> RF-3 @ 55c	<input type="checkbox"/> BP-33 @ 25c
<input type="checkbox"/> 50-MLH @ 47c	<input type="checkbox"/> BP-44 @ 25c
<input type="checkbox"/> QML @ 47c	<input type="checkbox"/> BP-SGD4 @ 25c
<input type="checkbox"/> HV-1 @ 1.50	<input type="checkbox"/> BP-PPBD @ 25c
<input type="checkbox"/> HV-2 @ 2.50	<input type="checkbox"/> BP-DBX @ 25c
<input type="checkbox"/> AVX-8 @ 1.50	<input type="checkbox"/> BP-UNB @ 25c
<input type="checkbox"/> LV-1 @ 50c	<input type="checkbox"/> BP-LIB @ 25c
<input type="checkbox"/> LV-2 @ 1.00	<input type="checkbox"/> Mail Items C. O. D.

Name .....

Address .....

City .....

State .....

## Orders-Inquiries



### POLK'S REFERENCE BOOK and Mailing List Catalog

Can be Secured by MAIL

60 pages

Send for FREE COPY

Gives counts and prices on over 8,000 different lines of business. No matter what your business, in this book you will find the number of your prospective customers listed.

Valuable information is also given as to how you can use the mails to secure orders and inquiries for your products or services.

Write for Your FREE Copy

R. L. POLK & CO., Detroit, Mich.

Largest City Directory Publishers in the World

Mailing List Compilers—Business Statistics

Producers of Direct Mail Advertising

### DEALERS and SERVICE MEN! STANDARDIZE ON



For Permanent Replacement—Accurate—Guaranteed


Write for descriptive catalogue "W"

LYNCH MFG. CO., INC., 1775 Broadway, New York

## BRACH RELAY

ONLY 99c

List price, \$4.50

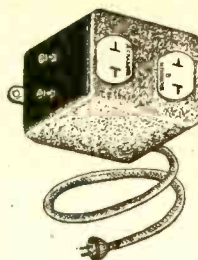


Connect relay's cable plug to 105-125 volt AC line. Connect B eliminator cable plug to relay socket so marked; connect one side of A battery to binding post, other side to A set. Then turning on your set turns on B eliminator and turns off charger, turning off set turns on charger and turns off B eliminator.

GUARANTY RADIO GOODS CO.  
143 West 45th Street  
New York City—Just E. of B'way

## RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS

7 CENTS A WORD  
\$1.00 MINIMUM  
CASH WITH ORDER
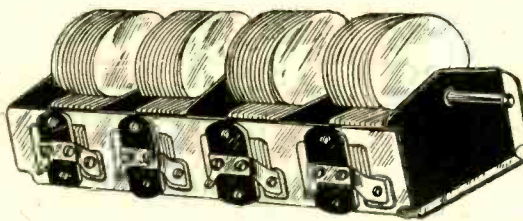
### FOUR-GANG .00035 MFD. WITH TRIMMERS BUILT IN!



This condenser, each of four sections .00035 mfd., has aluminum plates that are removable and adjustable, also a 1/4" diameter steel shaft that is removable. It is sturdy and is suitable for popular four-circuit screen grid tuners. Trimming condensers are built in. The condenser may be mounted on its bottom or side. Total overall length, including shaft, 1 1/4". Overall width, 4". The frame is steel Order Cat. 4-G

\$3.95

(Between 46th and 47th Streets)

RELIABLE RADIO COMPANY  
145 W. 45th St., N. Y. C.

## Subscribers: watch the date line on your wrapper

If the expiration date line on your wrapper indicates that your subscription has expired or is about to expire, please send in renewal so that you will not miss any copies of the paper. Subscription Dept., Radio World, 145 W. 45th St., N. Y.

# Two for the price of One

Get a FREE one-year subscription for any ONE of these magazines:

- CITIZENS RADIO CALL BOOK AND SCIENTIFIC DIGEST (quarterly, four issues).
- RADIO LOG AND LORE. Quarterly. Full station lists, cross indexed, etc.
- RADIO (monthly, 12 issues; exclusively trade magazine).
- RADIO ENGINEERING (monthly, 12 issues; technical and trade magazine).
- RADIO INDEX (monthly, 12 issues) Stations, programs, etc.
- SCIENCE & INVENTION (monthly, 12 issues; scientific magazine, with some radio technical articles).
- AMERICAN BOY—YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
- BOYS' LIFE (monthly, 12 issues; popular magazine).

Select any one of these magazines and get it FREE for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks, at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE! Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Just East of Broadway).

Your Name .....

Your Street Address .....

City .....

State .....

DOUBLE VALUE!

If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.


If renewing an existing or expiring subscription for other magazine, please put a cross in square at the beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York, N. Y. (Just East of Broadway)



# High-Grade Parts of Great Utility

**FILTER CONDENSERS**

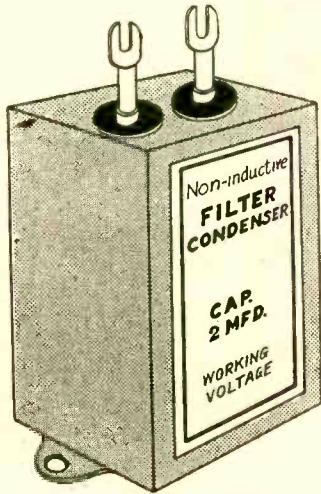


Flechthelm filter condensers for circuits using 245 output tubes, singly or in push-pull, or other circuits using lesser B voltage. Illustration is actual size. Capacities are 1 mfd. and 2 mfd. Continuous working voltage, 800 volts DC, 400 volts AC root mean square. Tested at 1,000 volts DC. Breakdown voltage 1,500 volts DC. Equipped with mounting feet.

Two condensers of 1 mfd. sent free with each 6 months' subscription at \$3.00. Order PR-HVD-1.

One condenser of 2 mfd. free with 6 months' subscription at \$3.00. (26 issues). Order PR-HVS-2.

**HAMMARLUND 100 MMFD. EQUALIZERS**

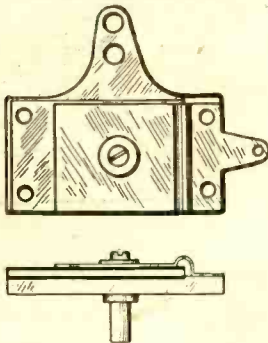

**Your Choice of NINE Meters!**

To do your radio work properly you need meters. Here is your opportunity to get them at no extra cost. See the list of nine meters below. Heretofore we have offered the choice of any one of these meters free with an 8-weeks subscription for RADIO WORLD, at \$1, the regular price for such subscription. Now we extend this offer. For the first time you are permitted to obtain any one or more or all of these meters free, by sending in \$1 for 8-weeks' subscription, entitling you to one meter; \$2 for 16 weeks, entitling you to two meters; \$3 for 26 weeks, \$6 for 52 weeks, entitling you to six meters. Return coupon with remittance, and check off desired meters in squares below.

**SOLDERING IRON**



Works on 110-120 volts, AC or DC; power, 50 watts. A serviceable iron, with copper tip, 5 ft. cable and male plug. Send \$1.50 for 13 weeks' subscription for Radio World and get these free! Please state if you are renewing existing subscription, Order PR-SO.

**AMER-TRAN AUDIO**


First stage, de luxe (illustrated), primary, in detector circuit, has 200 henrys inductance at 1 milliamperere; turns ratio, 1-to-3. Order PR-AMDL, free with 1 1/2 years' subscription at regular rate ..... \$9.60



Push-pull input transformer, turns ratio, 1-to-2 1/2; single primary; two separate windings for secondary. Order PR-AMPF, free with 2 1/2 years' subscription @ \$15.00.

These audio transformers are recognized as being predominant. They afford tone realism unexcelled and deliver fully adequate volume. You can never go wrong with Amertrans. And remember that RADIO WORLD circuits show how best to use these transformers. Read RADIO WORLD weekly.

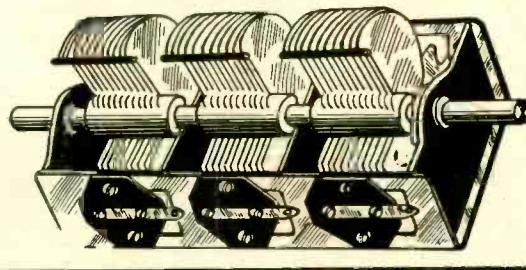**THREE-GANG SCOVILL .0005 MFD. WITH BRASS PLATES**



One of the best three-gang condensers made. Plates, utterly rigid and expertly aligned, are of brass, the most expensive metal used for this purpose. Capacity of each section, .0005 mfd. Shaft, 3/16" diameter of genuine steel, protrudes at both ends. For 1/4" diameter dial use at extension shaft (Cat. XS-4 @ 12c extra). Trimming condensers not built in, but mounting holes are provided for them. Condenser should be mounted on narrow side for drum dial operation. Rotor tension adjusters are built in. Frame is steel. Total shaft length overall 3 1/4", total frame width overall, 4 1/2". Order PR-30, free with 26 weeks' subscription @ ..... \$3.00

The most precise and rugged equalizing condenser made, with 20 mmfd. minimum and 100 mmfd. maximum, for equalizing the capacity where gang condensers are used that are not provided with built-in trimmers. Turning the screw alters the position of the moving plate, hence the capacity. Cross-section reveals special threaded brass bushing into which screw turns, hence you can not strip the thread. If you turn the screwdriver down with

accidental excess of force the screw simply stops, no injury results, as this special equalizer does not rely on the delicate thread in bakelite. The screw receptacle is strong brass. Useful in all circuits where trimming capacity of 100 mfd. or less is specified. Maximum capacity stamped on the condenser. Order PR-EQ-100, and three condensers will be shipped; subscription, three months @ \$1.50 regular rate.

**BOOKS THAT BUILD UP YOUR RADIO KNOWLEDGE TWO GREAT STANDBYS**

"Principles of Radio Communication," by Prof. John H. Morecroft, second edition. Prof. Morecroft, of the Electrical Engineering Department of Columbia University and past president of the Institute of Radio Engineers, is a noted authority. Prior electrical and mathematical knowledge required. 1,001 pages and 831 illustrations. Cloth-bound. Order PR-MPRN, free with subscription for 1 year and 34 weeks (\$8.50) @ ..... \$10.00

"Elements of Radio Communication," written in plain language, requiring little foundation knowledge of radio, is another fine Morecroft book. The book is a complete course on the elements of radio, containing much material never before published. 226 pages, 170 illustrations and a complete index. Cloth bound. This is one book you must have in your library. Order PR-MELEM, free with 26 weeks' subscription @ \$3.00

**BOOKS BY J. F. RIDER**

"Practical Radio Repairing Hints," by John F. Rider, just published. A handbook for the radio worker. No theory. No formulae. Explanations of the modern radio systems, automatic volume control circuits, new forms of voltage distribution—automobile radio sets, public address systems, etc. Order PR-PRRH, free with 26 weeks' subscription @ \$3.

"Practical Testing Systems," the first complete collection of accurate and practical testing circuits of interest to the service man, professional set builder and experimenter. Order PR-PTS, free with 3-month subscription @ \$1.50.

**AUDIO POWER AMPLIFIERS**

An understanding of audio amplifiers of all types, and of the use of tubes in audio channels, is a prerequisite today, when audio amplification is to the fore in radio, in public address systems and in the talkies.

"Audio Power Amplifiers" is the first and only book on the important subject. The authors are J. E. Anderson, M.A., former instructor in physics, University of Wisconsin, former Western Electric engineer, and for the last three years technical editor of "Radio World"; Herman Bernard, LL.B., managing editor of "Radio World." The book begins with an elementary exposition of the historical development and circuit constitution of audio amplifiers and sources of power for them. From this simple start it quickly proceeds to a well-considered exposition of circuit laws including Ohm's laws and Kirchhoff's laws. The determination of resistance values to produce required voltages is carefully expounded. All types of power amplifiers are used as examples: AC, DC, battery operated and composite. But the book treats of AC power amplifiers most generously, due to the superior importance of such power amplifiers commercially. Tube characteristic tables and curves profusely included. Cloth cover, 193 pages. Order Cat. PR-APAM with one year's subscription (52 issues) @ ..... \$6.00

**THE SUPERHETERODYNE**

This is a new volume by Anderson and Bernard dealing with the principles and practice of the Superheterodyne method of receiving. It explains the function of the oscillator, the modulator, the pre-modulator selector, and the intermediate frequency amplifier. It explains the cause of repeat points and gives methods for avoiding them or minimizing their effect. It expounds the relative advantages and disadvantages of high and low intermediate frequencies, and shows the effect of selectivity on the quality.

It illustrates various forms of oscillators and tells of the advantages of each. Different types of modulators and pick-up systems are explained and their advantages stated. Different methods of coupling in the intermediate frequency amplifier are shown. Order PR-ABSA, free with 6 months' subscription (26 issues) @ ..... \$3.00

**FOOTHOLD ON RADIO**

In simple English that any one can understand, the technical side of radio is presented by Anderson and Bernard in their book, "Foothold on Radio." Any one who can read English can understand this book. It is intended for the sheer novice. The treatment is non-mathematical. Order PR-FOR free with 16 weeks' subscription @ ..... \$2.00

**PLEASE USE THIS COUPON**

RADIO WORLD, 145 West 45th Street, New York, N. Y.

I hereby take advantage of Your extra-special premium offers and subscribe for RADIO WORLD for the number of weeks specified in the list below. Please send indicated premium. My remittance of \$..... is enclosed.

- |  |   |
|--|---|
| <input type="checkbox"/> PR-HVD-1 (26 wks., \$3.00)    | <input type="checkbox"/> PR-326-0-6 Voltmeter D.C.                  |
| <input type="checkbox"/> PR-HVS-2 (26 wks., \$3.00)    | <input type="checkbox"/> PR-327-0-50 Voltmeter D.C.                 |
| <input type="checkbox"/> PR-AMDL (1 1/2 yrs., \$9.60)  | <input type="checkbox"/> PR-23-6-Volt Charge Tester D.C.            |
| <input type="checkbox"/> PR-AMPP (2 1/2 yrs., \$15.00) | <input type="checkbox"/> PR-336-0-10 Amperes D.C.                   |
| <input type="checkbox"/> PR-EQ-100 (3 mos., \$1.50)    | <input type="checkbox"/> PR-325-0-25 Milliamperes D.C.              |
| (Three condensers supplied.)                           | <input type="checkbox"/> PR-350-0-50 Milliamperes D.C.              |
| <input type="checkbox"/> PR-APAM (1 yr., \$6.00)       | <input type="checkbox"/> PR-300-0-100 Milliamperes D.C.             |
| <input type="checkbox"/> PR-ABSH (26 wks., \$3.00)     | <input type="checkbox"/> PR-399-0-300 Milliamperes D.C.             |
| <input type="checkbox"/> PR-FOR (16 wks., \$2.00)      | <input type="checkbox"/> PR-394-0-400 Milliamperes D.C.             |
| <input type="checkbox"/> PR-PRRH (26 wks., \$3.00)     | <input type="checkbox"/> One for \$1.8 wks. Two for \$2.16 wks.     |
| <input type="checkbox"/> PR-PTS (13 wks., \$1.50)      | <input type="checkbox"/> Three for \$3.26 wks. Six for \$6.52 wks.] |
| <input type="checkbox"/> PR-MPRN (1 yr., \$8.50)       | State here how many meters.....                                     |
| <input type="checkbox"/> PR-MELEM (26 wks., \$3.00)    | <input type="checkbox"/> PR-SO (13 wks., \$1.50)                    |
| <input type="checkbox"/> PR-30 (26 wks., \$3.00)       |   |

NAME .....

ADDRESS .....

CITY ..... STATE .....

Put cross here if renewing an existing RADIO WORLD subscription, as this facilitates speedy service.