

RADIO

Servicing Course

PRACTICAL RADIO TRAINING FOR HOME-STUDY




Compiled by
M. N. BEITMAN

SUPREME PUBLICATIONS




1959

PRICE **\$2⁵⁰**


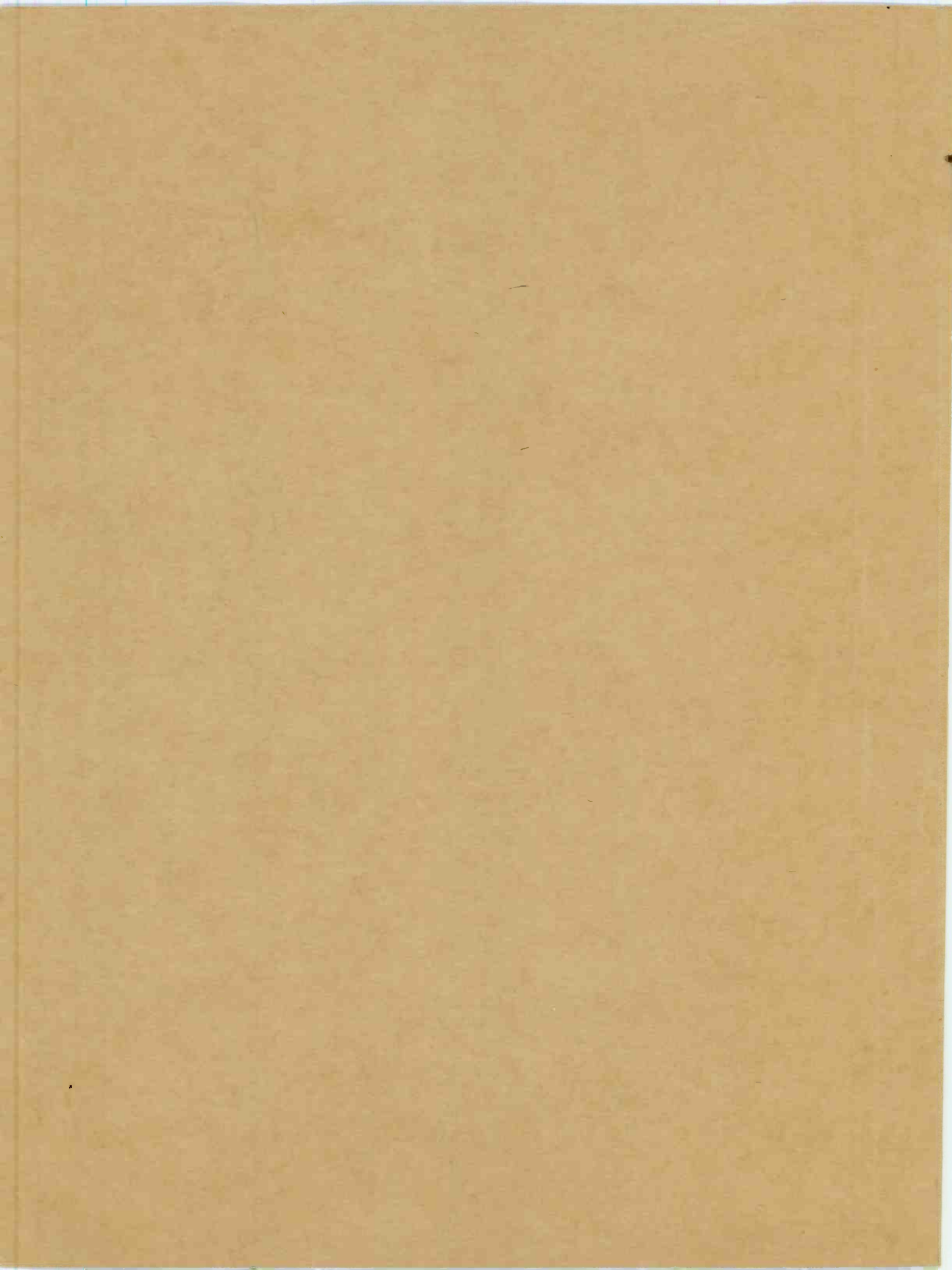





73,000,000 RADIOS TO BE REPAIRED

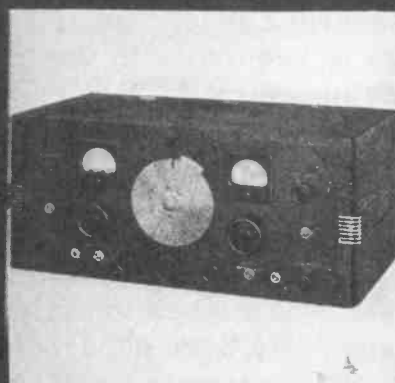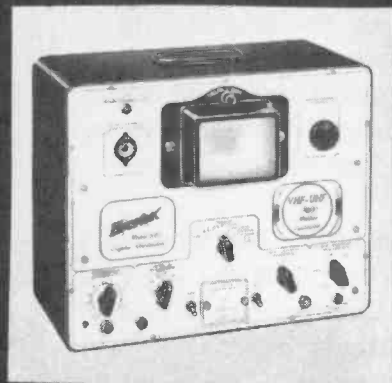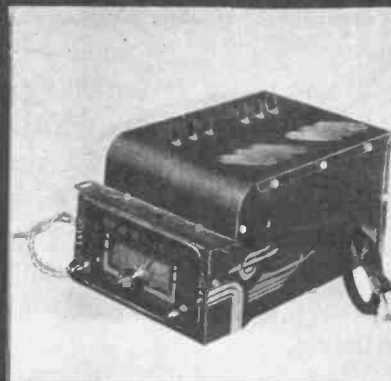

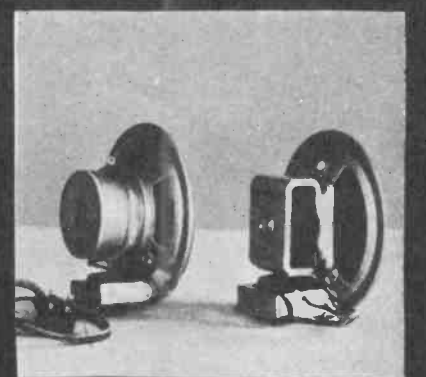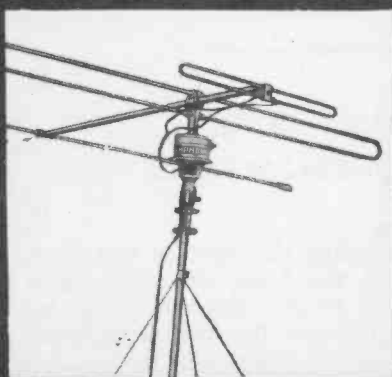HERE IS YOUR COMPLETE COURSE OF TRAINING IN RADIO SERVICING



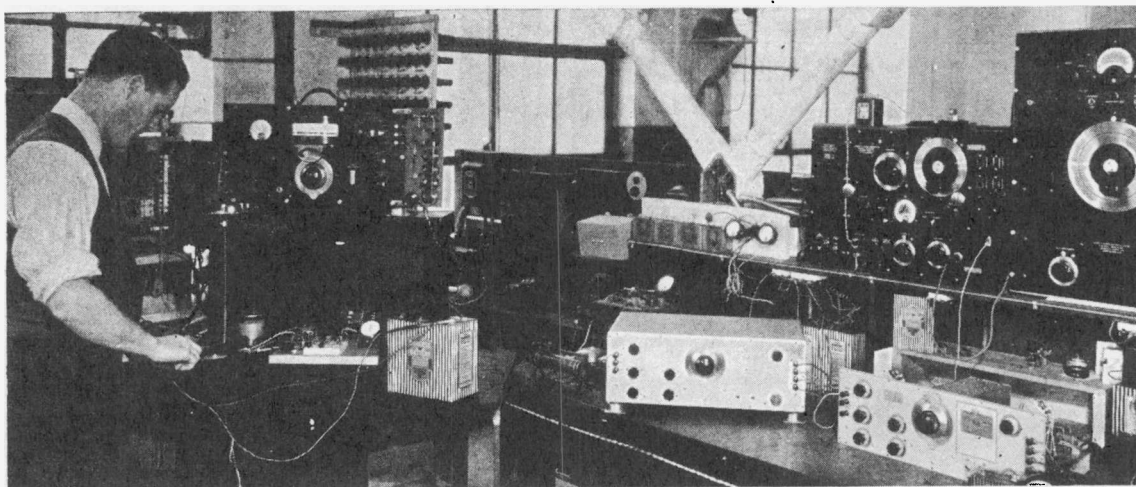

RADIO is today's opportunity field. In spite of the tremendous increase of the use of television, more radio receivers have been sold in the last few years than ever before. Amplifiers for public address use are finding extensive application and are serviced and installed by radio servicemen. The use of frequency modulation is increasing and this subject is covered in a complete lesson in this course-book. The study of television requires a background of radio knowledge and this text will give such training.

Study this course with a will to learn, slowly, going over the more difficult parts several times. Other technical radio reading will help you. Be sure to keep up with the latest developments by reading technical radio magazines. For practice build radio sets and test equipment available in kit form. Study real radio receivers and other electronic equipment whenever you have the chance.

This course is adaptable for the use of a beginner, but the subject matter goes beyond the elementary and will prove of aid to the professional serviceman who wishes to brush up on basic facts and modern service methods. We have hundreds of letters from users of the earlier editions of this course, who have expressed their thanks for the aid given them by this course. May your success in radio also improve through the study of this course.



Copyright 1955,
By SUPREME PUBLICATIONS

All rights reserved, including the right to reproduce or quote the contents of this book, or any portion thereof, in any form. Book reviews may include quotations of brief passages to illustrate the style or contents.

LESSON 1

INTRODUCTION AND FUNDAMENTAL FACTS

Originally the text to this course was prepared by the staff of instructors of the Radio Technical Institute. This material has been revised several times and brought up to date. These lessons were the stepping stones to success for thousands of men. You will enjoy and benefit through your study. Here is your complete training in radio and background for future study of television.

Although modern radios use complex circuits, their function is based on surprisingly few principles that can be easily mastered. Once the material presented in these lessons is clearly understood, you will possess the knowledge essential to be a first class radio serviceman and will be able to continue your studies in television. But you need not wait until you finish this course to begin to earn extra money servicing sets. After only a few lessons you will be ready to purchase a simple tester and begin to do some types of radio repair work.


Since the entire purpose of radio is to receive sound in the form of voice or music, a few basic facts about sound are of interest and importance to radio servicemen. Sounds must be conducted through some medium. In general, solids are good conductors of sound, but porous materials are poor conductors. Air is the most useful medium for sound conduction. In air the velocity of sound is about 1,090 feet per second, at 0° C. This velocity increases about two feet per second per degree C. The velocity in other media differs. In water the velocity of sound is about four times as great as in air.

Vibrations are either transverse or longitudinal. Water waves are transverse to the line of motion. There is no forward movement of the water itself, but there is a rising and falling motion as the water wave advances. Any single particle of water on the surface will rise and fall, but will move neither forward nor backwards.

When a body vibrates, the air immediately in front is first compressed and then released. The cone of a loudspeaker acts in this manner. In this way, a series of condensations and rarefactions is produced. This train of waves is longitudinal since it takes place in the direction of motion. There is but little movement of the air forward since each pulse communicates its energy to the air directly in front of itself.

A single cycle is completed when the vibrating body completes two vibrations (one forward and one backwards) and returns to the original position. A period is the time required to complete one such cycle. The number of cycles per second is the frequency (per second).

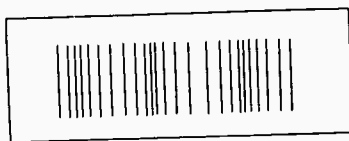As a radio serviceman you may expect to be called upon to repair and install public address amplifiers and high fidelity systems, therefore it is important to you to understand the behavior of sound in enclosed rooms. A few fundamentals will be discussed now while a more advanced lesson will deal with practical problems of this nature.



Crowded lines represent condensations, the other lines rarefactions, in this analogy of the effect of sound on a medium.

Acoustics is the science that deals with the behavior of sound. All sounds created proceed outwards in spherical waves until they strike the boundaries of the room. Upon striking the walls and other objects, sounds are absorbed, reflected, and transmitted in varying amounts depending upon the character of the object. Sound energy is diminished with each reflection because of the absorption, and this action finally results in the sound dying out. Continuous reflection has the advantage of loudness, but always introduces prolonged existence of each sound. This prolongation or reverberation is the most common acoustic fault found in auditoriums.

When you actually begin to do radio repair work you will find that for majority of repairs one or more replacement parts will be needed. All parts that may be required for replacement are sold by radio parts distributors also known as jobbers. The location of such firms may be known to you or you may be able to find their addresses in a telephone book. If you do not live in a large city, mail order houses will be glad to aid you and distribute free catalogs listing parts.

Usually you are able to secure replacement parts at 40% discount from list prices and in charging your customers you make a profit by making your bill out for the actual list price. This is a fair profit to you since you must spend time and effort in buying needed parts or carry a small stock of popular parts on hand. Of course, your service charge is in addition to any profit you may be making on the parts themselves.


It is a good idea to introduce yourself by mail or in person to a nearby jobber and secure his suggestions and assistance. You can especially benefit by his suggestion of parts that should be included in your stock so that you need not waste time each time a part is needed.

RADIO SERVICING COURSE

As a future radio serviceman you should begin reading technical radio magazines. The magazines with the greatest circulation in this field are "Radio & TV News," and "Radio-Electronics." There are other excellent magazines as well. Besides finding helpful articles in these publications you will benefit by reading the advertisements that offer lists of parts for sale as well as free catalogs.

To do actual experiments and repair of radios, you should have a place to work. This may be a basement work shop, garage, or even a corner in a kitchen. In time when you begin to do more serious and profitable radio repairing you can consider expanding to a rental location.


On page 10 you will find symbols for commonly used radio parts. While the function of these parts may not be clear to you at this time you could readily understand that these symbols are a shorthand method for illustrating parts used in radio receivers. Since in actual radio receivers these parts are interconnected with wires or with conducting surfaces in printed circuits, some method must be used in illustrating the same connections. This is done in diagrams by means of straight lines joining the parts and providing the same electrical path as exists in the radio set itself. We illustrate a simple radio circuit with the names of the parts next to most of the symbols.

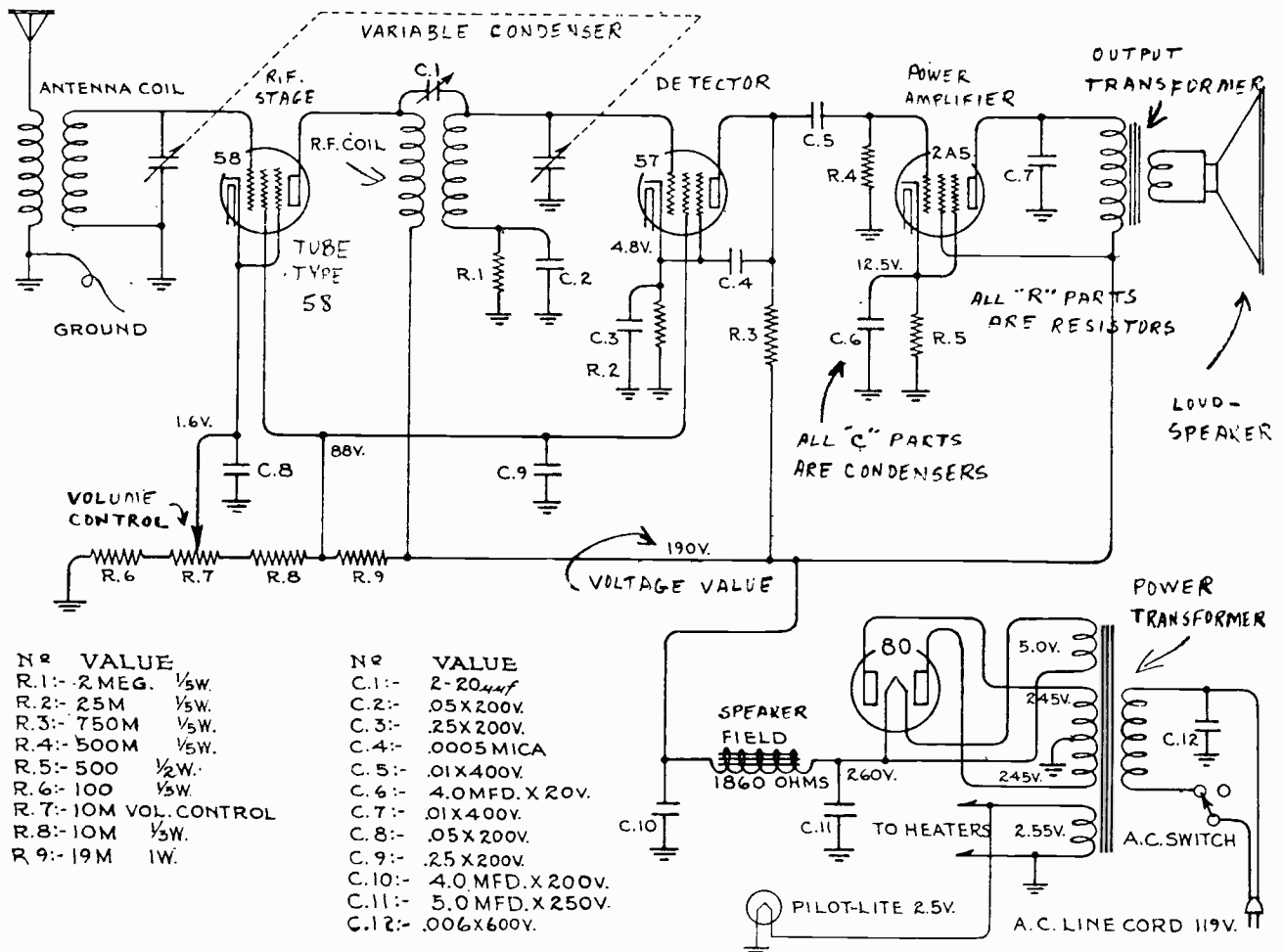

As you study this course you will realize that circuit diagrams and other service data are not only helpful but actually are essential to conserve time. As you probably know, Supreme Publications issues annually a manual covering all popular radio sets and a separate volume covering television receivers. These are low price manuals and contain practically all material that you will need in your work. Certainly they will serve well at first and the more expensive volumes of other publishers can be considered at a much later date.

Your initial tools are illustrated below. Probably you already have these tools in your possession and will not need to spend any additional funds at the present time.

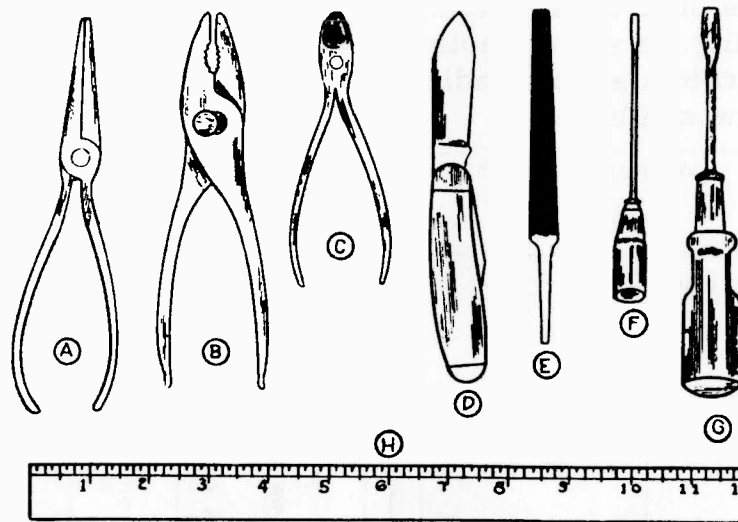Majority of connections in radio sets are made electrically secure with solder and a soldering iron is needed for disconnecting parts and for making new connections. For most radio work an electrically heated iron is employed.



These are common radio tools needed for radio repairing and construction work. (A) Long-nose pliers, (B) Gas pliers, (C) Diagonal cutters, (D) Pocket knife, (E) Flat file, (F) Small screwdriver, (G) Medium-size screwdriver, (H) Scale.

To do a good soldering job, the tip of the soldering iron must be properly shaped and tinned. Tinning an iron is a process whereby a thin, uniform layer of solder is formed upon the tip of the iron. The transfer of heat from the tip to the work occurs most easily if the surface is bright as the result of tinning. When the tip of the iron becomes "pitted" by the action of the rosin core in the solder, the iron must be filed and re-tinned. The iron can be kept clean for long periods of time by wiping the tip with a rag whenever corrosion accumulates.

The soldering iron must actually heat the joint to be soldered to a temperature that will readily melt solder. The solder will then run into

each crack in the joint and form a good electrical bond. Hot smoothly flowing solder has a bright silver luster; as it cools, its appearance changes to a duller gray, setting shortly after this change. If the joint cools with a rough surface, the soldering job is not well done; a dirty contact, improper heating, or movement of the wires may have been the cause.

It is advisable for a radio repairman to carry an inexpensive wood finishing kit obtainable at paint stores. A great deal of good will can be secured by touching up any mars or scratches that are noticeable on the cabinet of the radio being repaired. It is also possible actually to offer this service on a fee basis and this manner supplement your income.

Your first radio repair jobs will come from friends and acquaintances. Do not hesitate to accept work even at an early stage in your study. You will derive a great deal of valuable experience by trying to carry out the repair. In most cases only a simple fault may be present and you will be able to correct it. Should the job prove beyond your ability at this early stage in your career, you can make arrangements with a more experienced serviceman to take over such work from you and allow you a percentage of his charges as a commission for finding this work.

Several of the larger manufacturers of radio tubes offer shop garments and tools with the purchase of a quantity of tubes. Since a great many of repairs you will be making will require replacement of tubes, by joining one of these plans you will be able to secure various items needed to establish your business practically free of charge. Sylvania Electric Products offers imprinted stationary at a very low price. The reason that this is done is to secure the good will and publicity resulting by imprinting a small message about Sylvania tubes. We suggest that you write to this firm at Emporium, Pa.

REVIEW QUESTIONS

1. Roughly what is the speed of sound in water?
2. What happens to sound when it strikes a wall? How different is this behavior when sound strikes a cloth drape?
3. Name ten different parts used in radio sets.
4. How can you tell if a connection was properly soldered?

DO NOT RUSH YOUR PROGRESS, KNOW EVERYTHING IN THIS LESSON.

LESSON 2

E L E M E N T A R Y E L E C T R I C I T Y

For comparative purposes of the quantities that are encountered in electrical circuits, selected units are employed. These units are inter-related and are based on absolute basic reactions. Because of the nature of electricity and the associated force magnetism, we cannot measure or note these forces directly with our senses, but must resort to indirect indicators (meters, lights, etc.) operated by these forces.

Electrical current in a circuit consists of a large number of electrons flowing in a complex manner through the conductor such as a wire cord. Since electrons are negatively charged particles, the current actually consists of a motion of negative electrical charges. The measurement of quantity of current, therefore, is the measure of the sum of all the charges. An electric or magnetic charge may be measured by the force of attraction or repulsion which exists between this charge and some other charge. It is important to remember that unlike charges attract, and like charges repel.







If we connect two bodies that have different charges (one positive and one negative), a current will flow. The positive body lacks electrons, and the negative body has an excess of electrons; the current is the passage of these electrons from the negative body to the positive one.

Electro-motive force, E.M.F., which will force electrons to flow through a conductor can be generated in a number of different ways. Friction was the earliest known method, but is not used commercially today. In dynamos a conductor is moved in a magnetic field. Chemical changes generate an electrical current in batteries.

The flow of electricity is the passage of electrons between the heavier atoms of the conductor. The solid substances which conduct electricity best are the metals. Copper is the best conductor of the materials practical to employ for this purpose. Other metals, iron, alloys of nickel, have greater opposition (resistance) to the flow of electric current and find certain special applications.

It is evident that some substances are very good electrical conductors, others have greater resistance, while still others have almost no conducting properties and are called insulators. Hard rubber, bakelite, glass, porcelain are used extensively as radio insulators to separate parts that should not have electrical current flowing between them.

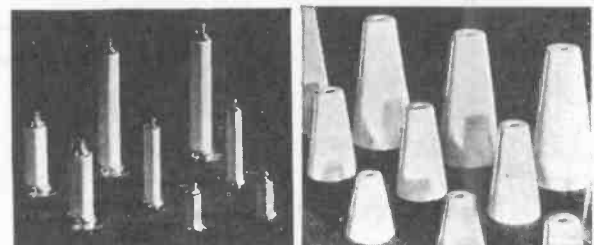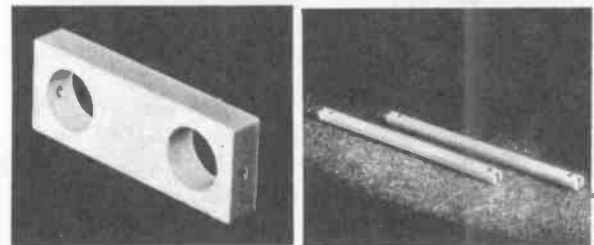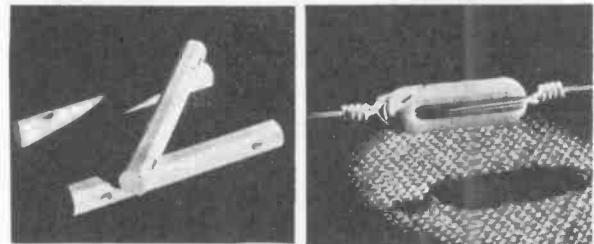
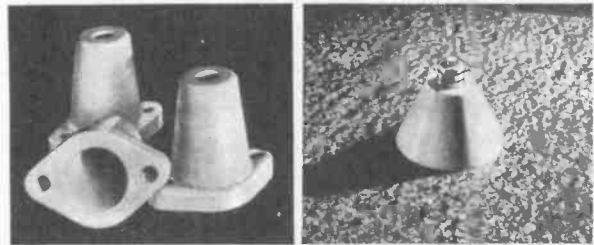
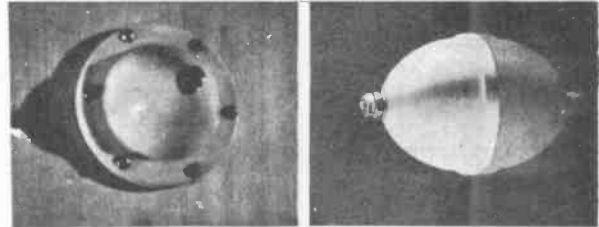
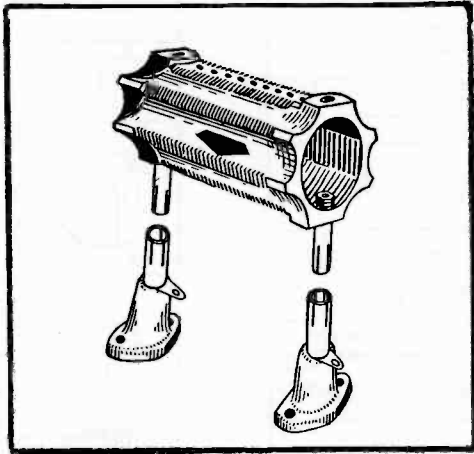
For the beginner student we have included a number of illustrations of radio parts that are excellent examples of conductors and insulators. Note the coil form which is made of special insulating material, Isotex; while the terminal jacks are of good conducting metal. The application of these parts may not be clear at this time, but will be explained later.



Many different insulators are shown on the right. These are employed for various applications in antenna systems, transmitters, and receivers. Special ceramic materials are used to reduce the electrical losses and make the units better insulators.

Every radio part, naturally, must have some conducting material. In coils we have the wire, in condensers the metal plates — and every circuit has the many parts wired and interconnected with copper hook-up wire.

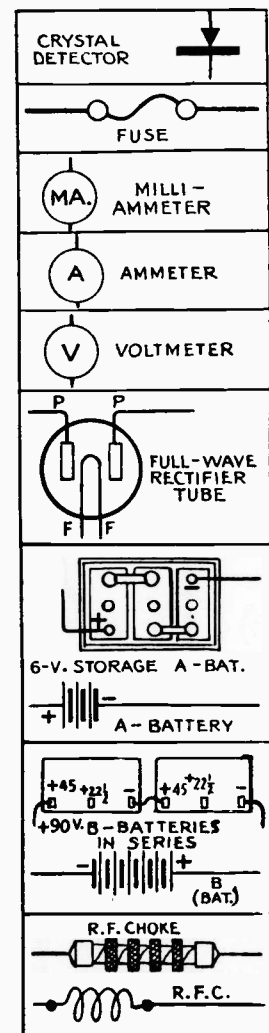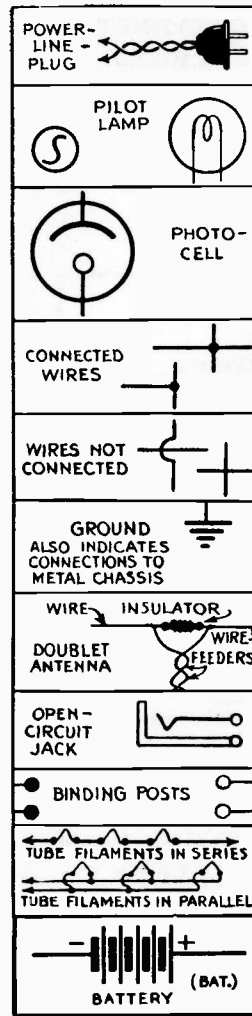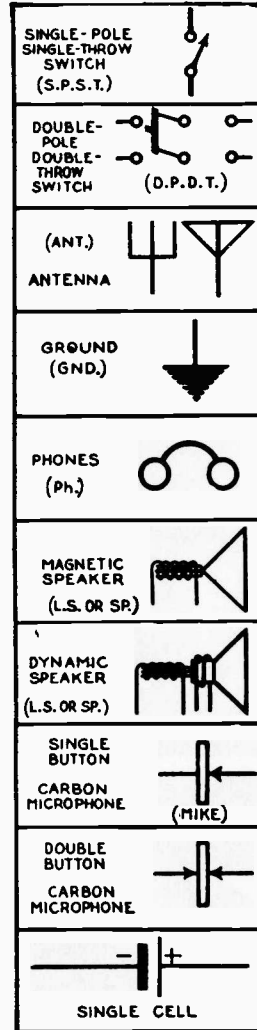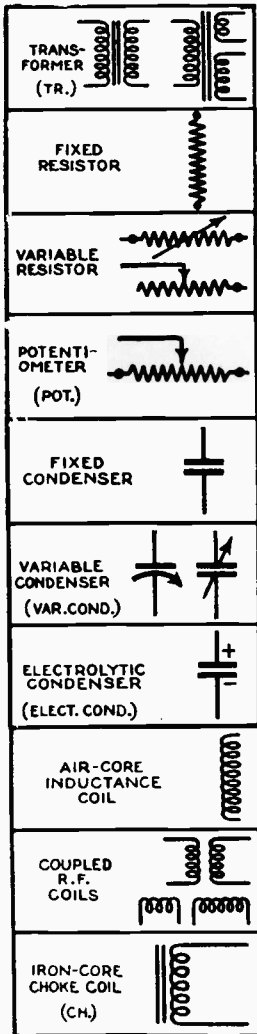The radio serviceman has his own language of radio symbols. Circuits are always shown in these symbols and the radio manuals use them. There are only a few used and once these are mastered, the understanding of radio becomes a simpler problem. These symbols will appear as we progress with the course.



Much information on new developments is presented in many technical radio magazines. You, as a future radio serviceman, should begin reading these magazines at an early stage of your career.

REVIEW QUESTIONS


1. Of what potential are electrons?
2. Name two ways an electric current can be generated.
3. Name several good conductors of electricity.
4. Make a sketch showing the connection of a fixed condenser and a fixed resistor connected to a meter.
5. Examine several circuits in radio magazines and name each part used.

LESSON 3


RADIO BATTERIES

A cell is a unit that produces electrical energy by means of chemical action. A battery is a combination of two or more cells connected in series or parallel. A primary cell is a unit that produces an electrical current because of a chemical reaction. Once the acting material is used up or an equilibrium is reached, no further appreciable current can be produced.

The ordinary flash-light battery is of this type. This "dry" cell has an outside foil of zinc that acts as the negative electrode and a center positive electrode of carbon (copper could be used instead). There is also a chemical solution in paste form. The common type "B" batteries are made up of a great number of these cells connected in series and thereby furnishing relatively high voltages. Different methods of connecting cells are illustrated below.


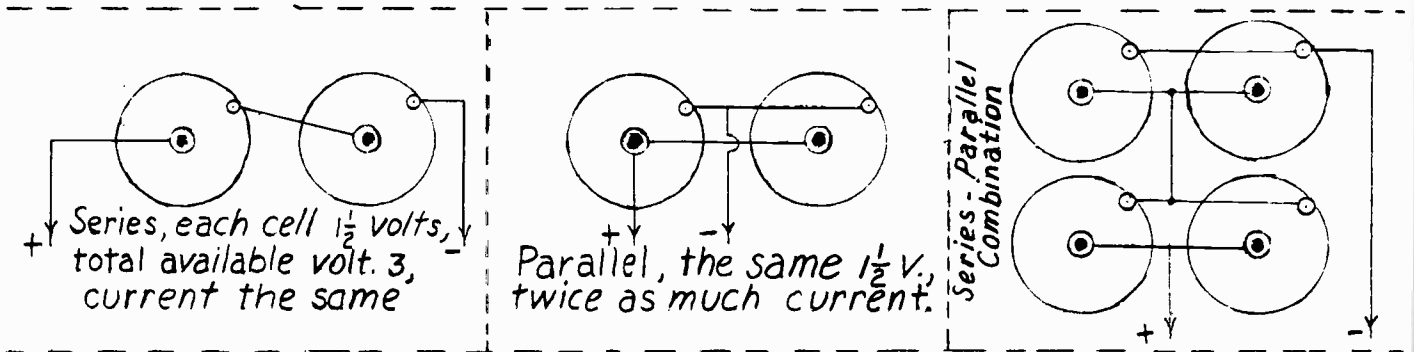


While A.C. operated receivers are used in the majority of homes, battery type radio sets are still finding widespread use in rural communities that as yet have not been electrified, and for portable use. Some house sets and all the modern auto sets obtain their operating power from a single 6 volt storage battery. Means are incorporated in the set to change the available low D.C. voltage to high voltage for plate supply requirements. Some battery sets still use "B" and "C" batteries and we refer the student to the circuit below. This is a simple set using a detector and a single audio stage.

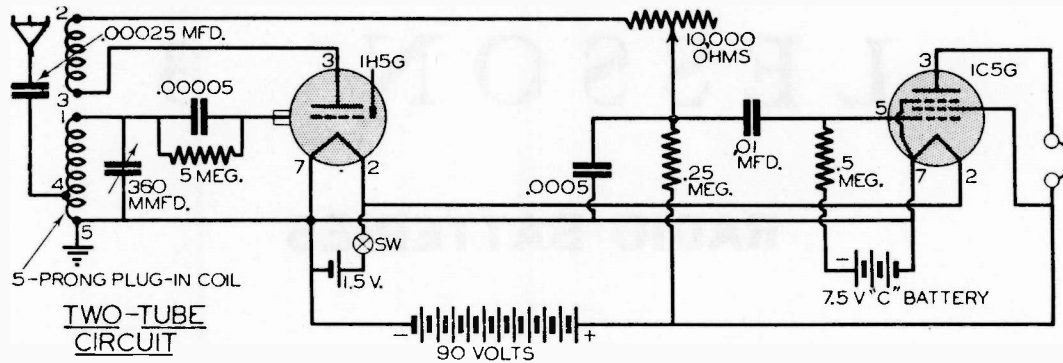

The storage battery is a secondary battery because it cannot produce an electrical current of itself, but must at first be charged. The current used for charging is stored and may be obtained when needed. The battery actually does not store electricity, it stores chemical energy created by the charging current. When the current is used during the discharge period, chemical energy is used up. Radio storage batteries are tested with a hydrometer since the specific gravity of the solution changes with the "charge" condition of the battery. The acid level should be at 1.275 when the battery is fully charged, and the battery should be recharged when the level reaches the 1.150 point.

The storage battery may be recharged by means of a charger from a 110 volt line, or a generator rotated by the wind may be used in conjunction with the battery to keep it always in operating condition. There are now also available inexpensive gasoline driven generators for quickly charging batteries.

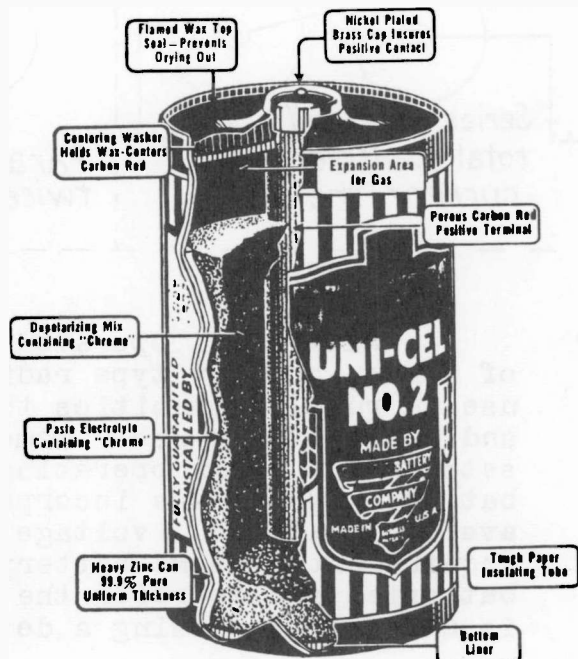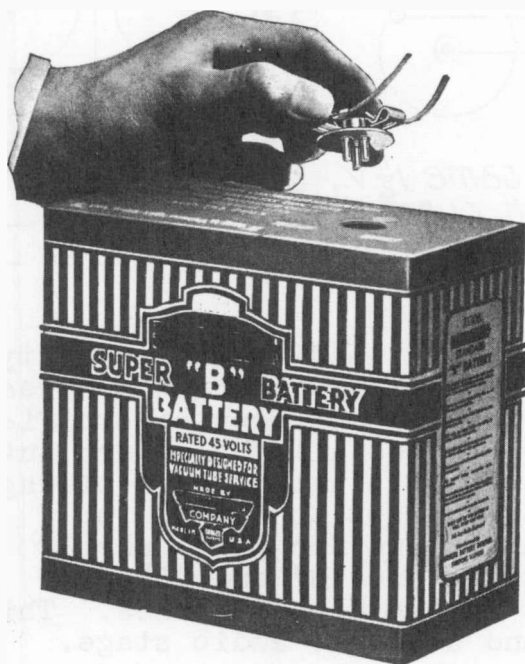

LESSON 4

CIRCUITS - MAGNETISM - ELECTROMAGNETS

A coulomb is a definite quantity of electricity just like a gallon of oil is a quantity of oil. An ampere is the rate of current flow and is the passage of one coulomb per second. For measuring small electric currents a unit, milliampere, equal to 1/1000 of an ampere is used. 1,000 milliamperes are equal to one ampere. Meters used to measure electrical current are called ammeters or milliammeters depending upon the currents they are designed to measure.

A current passes along a conductor because of an electromotive force (e.m.f.) or a potential difference. The volt is commonly used to measure potential difference and e.m.f. is often referred to as voltage.

The e.m.f. developed by a single standard dry cell, such as a flash light cell, is $1\frac{1}{2}$ volts. A single storage battery cell fully charged has a potential (voltage) slightly over 2 volts.

All conductors of electricity oppose the flow of current through them. They have electrical resistance. The unit of resistance is the ohm. In radio circuits very high resistance are sometimes encountered and the term megohm is used for 1,000,000 ohms. The student should memorize all the terms underlined as they are of prime importance in radio work. If an Encyclopedia is available at the library, the history of each term should be looked up.

NUMBERS, FRACTIONS, DECIMALS, SIMPLE FORMULAS EXPLAINED AS A TOOL

Mathematics is a symbolic way of explaining and analyzing physical occurrences. Arithmetical numbers represent quantity. Ten volts is ten times the standard measure — the volt. Numbers tell how many, is it larger or smaller, is it too small ... all these are measures of quantity. Algebraic symbols (usually letters of the English and Greek alphabet) represent specific measureable quantities. For example, E usually stands for voltage in electrical work. This is really another way of writing "voltage", i.e. we write E instead of the word voltage. In a like manner we usually write I for current, and R for resistance. Using letters saves time and greatly simplifies the writing of formulas. The Ohm's Law may be written in words as:

Voltage = Current (multiplied by) Resistance

or in symbols as $E = I \times R$

Of course, the algebraic way of writing is much simpler.

Sometimes in the same problem there are two different voltages, such as the grid and plate voltages in a vacuum tube. Here again we may use some letter, as "E", to represent voltage and use small letters after E and a little below it, to stand for grid and plate voltages respectively. As:

E_g → grid voltage

E_p → plate voltage

Many times in radio work quantities are parts of a whole unit and are called fractions. $\frac{1}{2}$ volt is a fraction of a volt. $5\text{-}1/4$ is a whole number and a fraction. The number above the line is called the numerator, and the one below the denominator. The denominator tells what part of the whole, the numerator tells how many parts.

Decimals are more convenient than fractions and, therefore, find greater application. Multiplication and division by ten or some multiple of ten simply shifts the decimal point. Fractions, of course, may be expressed as decimals, and vice versa. For example, $5\frac{2}{5}$ may be written as 5.4. The number 5, representing the whole part of the fraction, and $2/5$ changed to tenths becoming $4/10$ and written .4. In radio work, decimals are almost exclusively employed.

A number multiplied by itself is said to be squared.

$$A \times A = A^2$$

The small raised ² indicates that "A" has been multiplied by A; that is, by itself.

The square root sign $\sqrt{\quad}$ means that it is required to find a number that multiplied by itself will give the number under the $\sqrt{\quad}$ sign. For example, find $\sqrt{9}$. A number that multiplied by itself will give 9, is 3, so that:

$$\sqrt{9} = 3$$

$$3^2 = 9$$

O H M ' S L A W

We now come to an important relation between voltage, current, and resistance. It is easily seen that the greater the voltage, the larger is the number of electrons flowing or the larger is the equivalent current. But the larger the resistance, the smaller is the current. In mathematical words, the current in amperes equals the voltage in volts divided by the resistance in ohms.

$$I = \frac{E}{R}$$


where I stands for current, E for voltage, R for resistance. This equation enables us to calculate the current when the voltage and the resistance of the circuit are known. For example, in a 110 volt circuit the resistance is 10 ohms. Dividing 110 by 10, we obtain 11 amperes which is the current.

Ohm's Law may also be written as $E = I \times R$

The voltage is equal to the product of the current by the resistance. If a current of 2 amperes flows through a resistor of 6 ohms, the voltage drop is (2 x 6) or 12 volts. In some devices the voltage drop produced in a resistance is used to reduce the over all high voltage. In some other cases, the current is made to flow through a resistor purposely to create a voltage drop for some special need. This latter application is used for "C" bias in vacuum tube circuits.

By means of Ohm's Law, if the voltage and current are known, the circuit resistance may be found. For this purpose the formula below is used.

$$R = \frac{E}{I}$$

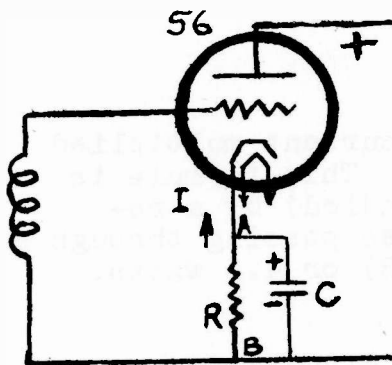

In the circuit to the left, a resistor R is used to create a negative bias on the grid of the vacuum tube. There is a constant D.C. current I passing through the tube and the associated resistor R. The A.C. component of tube-current is by-passed by condenser C. The voltage difference between points A and B, will be equal to the IR drop of the D.C. Point B will be more negative since electrons will move from point B to A, and then from cathode to the positive plate. Since the grid is connected to point

B through the coil winding of low D.C. resistance, the grid will be at IR lower potential than the cathode connected to A.

A formula is an equation used to represent a relation between a number of related factors. Usually a formula is applied to find one unknown factor when the others are known. The Ohm's Law is a simple formula:

$$E = I \times R$$

Suppose in a certain circuit we know that $I = 2$, and $R = 50$, substituting these values in the formula above, we are able to find the unknown E .

$$E = 2 \times 50$$

$$E = 100 \text{ volts}$$

In this case by knowing the current and the associated resistance and by applying the Ohm's Law formula, we were able to find the value of the voltage.

WATTAGE OR ELECTRICAL POWER

Electricity can do work or create heat and is therefore a source of power. The unit of electrical power is the watt. The watt is the power produced by one ampere flowing under the pressure of one volt. Numerically the power in watts equals the product of volts by amperes of current.

$$W = E \times I$$

where W stands for watts, E stands for the voltage, and I stands for the current. The filament of a common type 56 vacuum tube operates on $2\frac{1}{2}$ volts and requires 1 ampere of current. The filament wattage is, therefore, $2\frac{1}{2} \times 1$ or $2\frac{1}{2}$ watts. If current and voltage are known, wattage can be calculated.

By recalling from Ohm's Law that $E = IR$ and substituting in the equation above, another important formula for wattage in terms of current and resistance is obtained.

$$W = I^2R$$

This means that the wattage is equal to the current multiplied by itself, and multiplied by the resistance. This formula is useful in finding the wattage dissipated (handled) by a resistor. For example, a current of 1.5 amperes passing through a resistor of 2 ohms, dissipates $(1.5 \times 1.5 \times 2)$ or 4.5 watts. This power is actually lost as heat.

It is important in working on a radio circuit to have clearly in mind the relation existing between the different electrical factors. The Ohm's Law applies only to Direct Current, but is also applicable with certain modification to Alternating Current.

The resistance of any wire is directly proportional to its length. A piece of wire 10 feet long has twice the resistance of a similar piece 5 feet long. On the other hand, the larger the cross sectional area of the conductor the smaller is the resistance. The wire sizes are rated according to a number of different systems, but in the United States the B. & S. gauge is usually used. The larger the gauge number, the thinner is the wire. In radio work, wire sizes from # 12 to # 38 are commonly employed. Wire is obtainable with different insulation such as enamel, cotton, silk, or the combination of these materials.

Carbon composition resistors are commonly employed in radio circuits. For conveniency in determining the size of a resistor in repair work, resistors are color coded according to a standard code adopted by the R.M.A. Three indications are employed: the body, the end, and the middle dot. Ten colors are used, one for each number from 1 to 9, and 0. The table below gives color-figure code.

RESISTOR COLOR CODE

(A) (B)

RETMA COLOR CODE CHART

COLOR	VALUE	MULTIPLIER
Black	0	1
Brown	1	10
Red	2	100
Orange	3	1000
Yellow	4	10,000
Green	5	100,000
Blue	6	1,000,000
Violet	7	10,000,000
Grey	8	100,000,000
White	9	1,000,000,000

TOLERANCE CODE

Gold—±5% No Color—±20%

Silver—±10%

The ohmic value of a resistor can be determined by means of the color code. There are two standard methods of indicating this value.


In Fig. A, the body (A) and end (B) indicate the first and second digits of the value while the dot (C) indicates the multiplier to be used. The tolerance of the unit is indicated by the end color (D). For example, if the body (A) is green the number is 5; if the end (B) is grey the second number is 8. If the dot (C) is red the multiplier is 100 or two zeros should be added. The resistor is then a 5800 ohm unit. If the end (D) has no color, the tolerance is ±20%.


In Fig. B, the first two stripes indicate the first two digits; the third stripe the multiplier; the fourth stripe the tolerance. Thus, if stripe (A) is green, (B) is grey, (C) is red, and (D) is silver, the resistor is a 5800 ohm, ±10% unit.

Besides being rated in ohms, every resistance possesses another electrical rating corresponding to its power handling ability or wattage. Composition-type carbon resistors are rated from 1/4 to 2 watts depending on their size. Wire-wound resistors begin with about 5 watt size and go up to larger sizes.

The power dissipated by the resistor is changed to heat; if the heat is excessive due to overloading the resistor by more than just the normal current flow, the heat so developed may injure the resistor element. The rating commonly given is for open air mounting and where there are no close parts that may be injured by the heat. In mounting resistors in a closed chassis adjacent to other easily harmed parts, it is best not to load the resistor more than 50% of their rated wattage.

HOW TO TELL WHAT RESISTOR TO USE

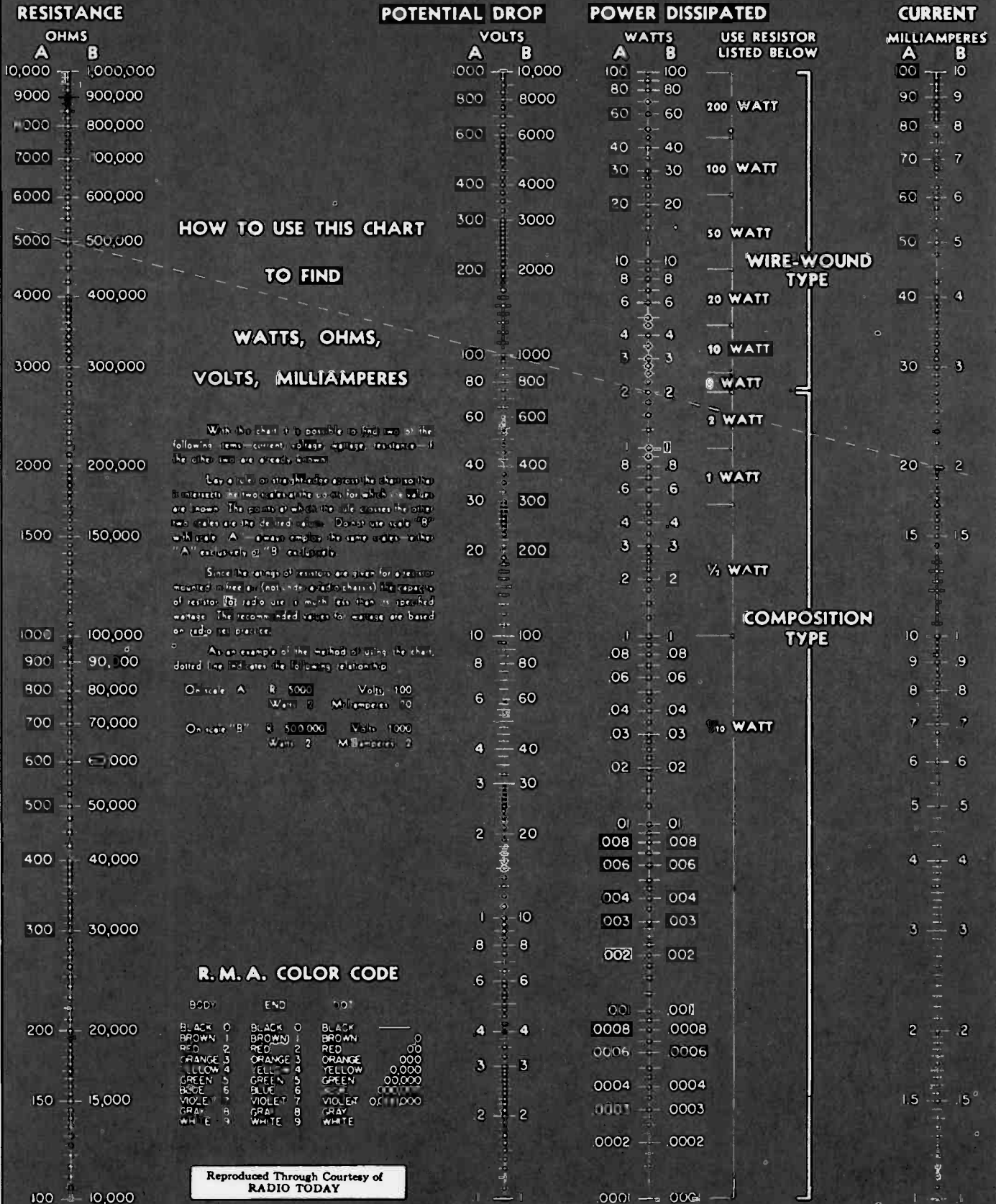

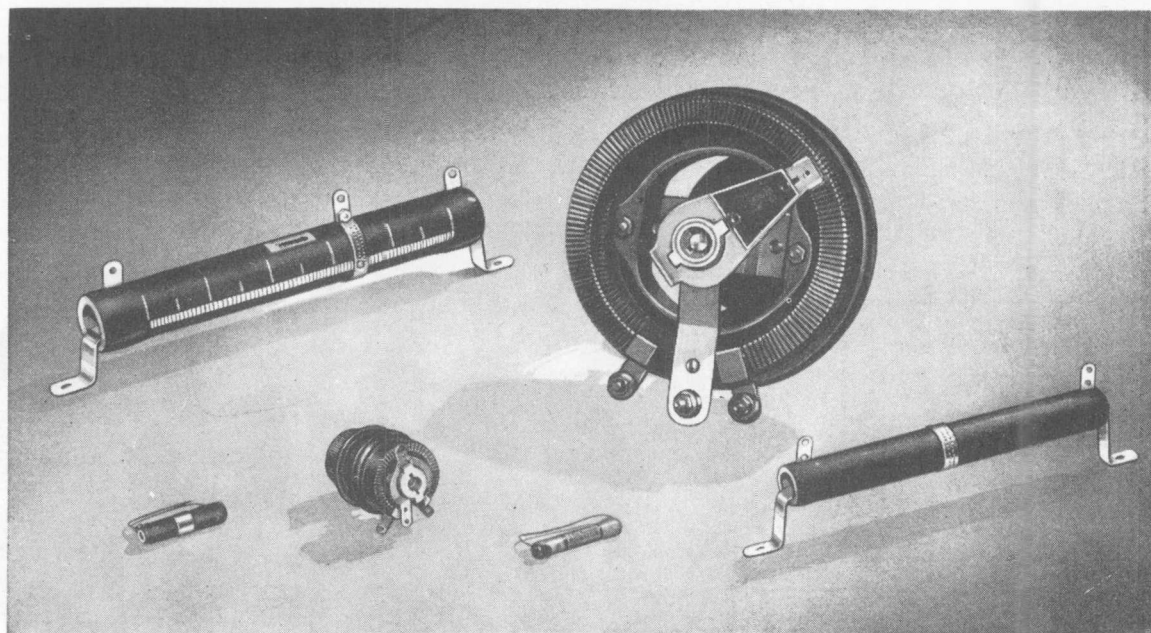

If a resistor of 3 ohms, carries a current of 2 amperes, what is the wattage dissipated?

$$W = I^2 R = 2^2 \times 3 = 2 \times 2 \times 3 = 12 \text{ watts}$$

A biasing resistor causes a drop of 30 volts, with a current of 15 milliamperes (.015 amperes). What is the wattage of the resistor?

$$W = I \times E = .015 \times 30 = .45 \text{ watts}$$

Rheostats have a single end terminal and a connection to the movable contact. Potentiometers have two end terminals and a movable arm. Volume controls are a form of variable resistors.





Resistances are used not only individually, but are combined in series, in parallel, and sometimes in more complex networks. The total resistance of two resistors R_1 and R_2 connected in series is the sum total of the individual resistances. In a like manner if more than just two resistors are connected in series, the total resistance is the sum total of all individual resistances. If we let R_s stand for the total resistance of a circuit having series resistances, than:

$$R_s = R_1 + R_2 + \dots \text{ (all the other resistors present)}$$

If in the series circuit above voltage E is impressed across the two resistors, the voltage drop across each resistor will be equal to IR_1 , and IR_2 , where I is the current. These two voltage drops together will equal to E .

$$E = IR_1 + IR_2$$

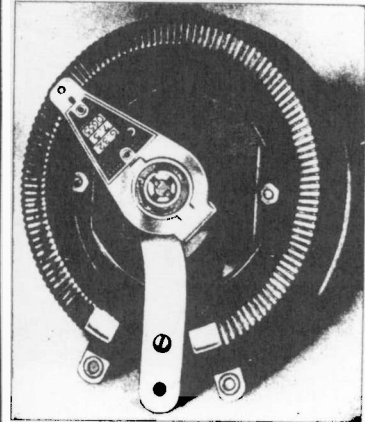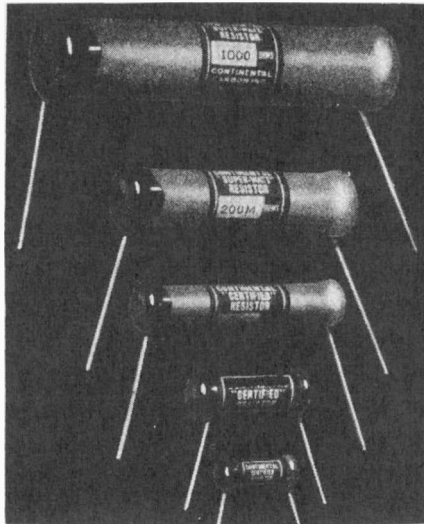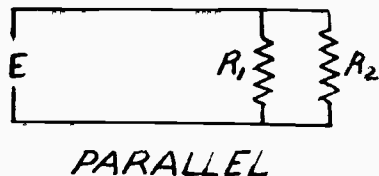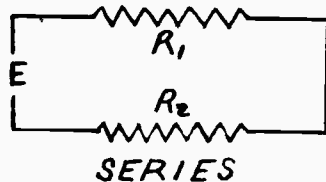The larger voltage drop will be across the larger resistance, and by selecting proper sizes for R_1 , and R_2 , E may be subdivided in any way required. Care must be taken that neither of the resistors is overloaded. The wattage formula should be applied as a test.



In a four tube midget radio set, three tubes are of the type that require 6.3 volts each, and one requires 25 volts. All these tubes are connected in series and use a current of 0.3 amperes. The total voltage required to operate all these tubes in series is the sum of the individual voltages, or 43.9 volts. We can round this figure into 44 volts. If the set is to be used on a 110 volt line (110 - 44) or 66 volts must be lost in a series resistor. Recalling Ohm's Law and solving:

$$E = I \times R_1 \qquad 66 = 0.3 \times R_1 \qquad R_1 = 220 \text{ ohms}$$

What wattage will this resistor dissipate?

Using the formula $W = I^2 R$

$$W = (.3)^2 \times 220 = .09 \times 220 = 19.8 \text{ watts}$$

A twenty watt resistor could be used, but a slightly larger size would be better. Sometimes line cords are built with the proper resistor already incorporated.

What is the total resistance of the four tubes in series?

$$R_2 = \frac{E}{I} = \frac{3(6.3) + 25}{0.3} = \frac{44}{.3} = 146.7 \text{ ohms}$$



The table on the next page and the explanation below have been reprinted from the "Aerovox Worker."

The chart covers a range which should be large enough for all radio and TV work. The ranges are from 1 to 1000 volts, from 0.1 ma. to 10 amperes, from 0.1 ohm to 10 megohms, and from 0.1 milliwatt to 10 kilowatts.

The lines are plotted on regular full logarithmic coordinate paper. Current is measured along the horizontal axis (X-axis), and voltage along the vertical axis (Y-axis). When this is done, the locus (position) of all points representing a given resistance will form a line making an angle of 45° with the X-axis. All these lines are parallel, slopping upwards to the right. All points representing the same power are situated on a straight line which makes an angle of 135° with the horizontal, slopping upwards towards the left.

A few examples will help you understand the use of this chart. Suppose the EMF in a circuit is 100 volts and the current is 100 ma.; what is the resistance of the circuit and power consumed? Beginning with the 100 ma. mark on the horizontal axis, and follow the vertical line upwards to the intersection with the horizontal 100 volt line. This junction is also the intersection of related slanting lines. Following the slant-line going upwards to the left read 10 watts for power; and following the other towards the upper right read 1000 ohms.


If a 5000 ohm resistor has a power rating of 20 watts, what is the maximum current and corresponding voltage with which this resistor may be used? Following the 5000 ohm slant line until the 20 watt slant line is reached, observe the junction point. From this point follow the vertical lines down, and interpolating by estimation read 63 ma. Then follow the horizontal lines from the junction point, and at the left read 316 volts.

The total resistance of two resistors connected in parallel is less than the resistance of either resistor. For many resistors R_1 , R_2 , R_3 , etc. connected in parallel, the total resistance

$$R_p = \frac{I}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

for only two resistors, this formula simplifies to:
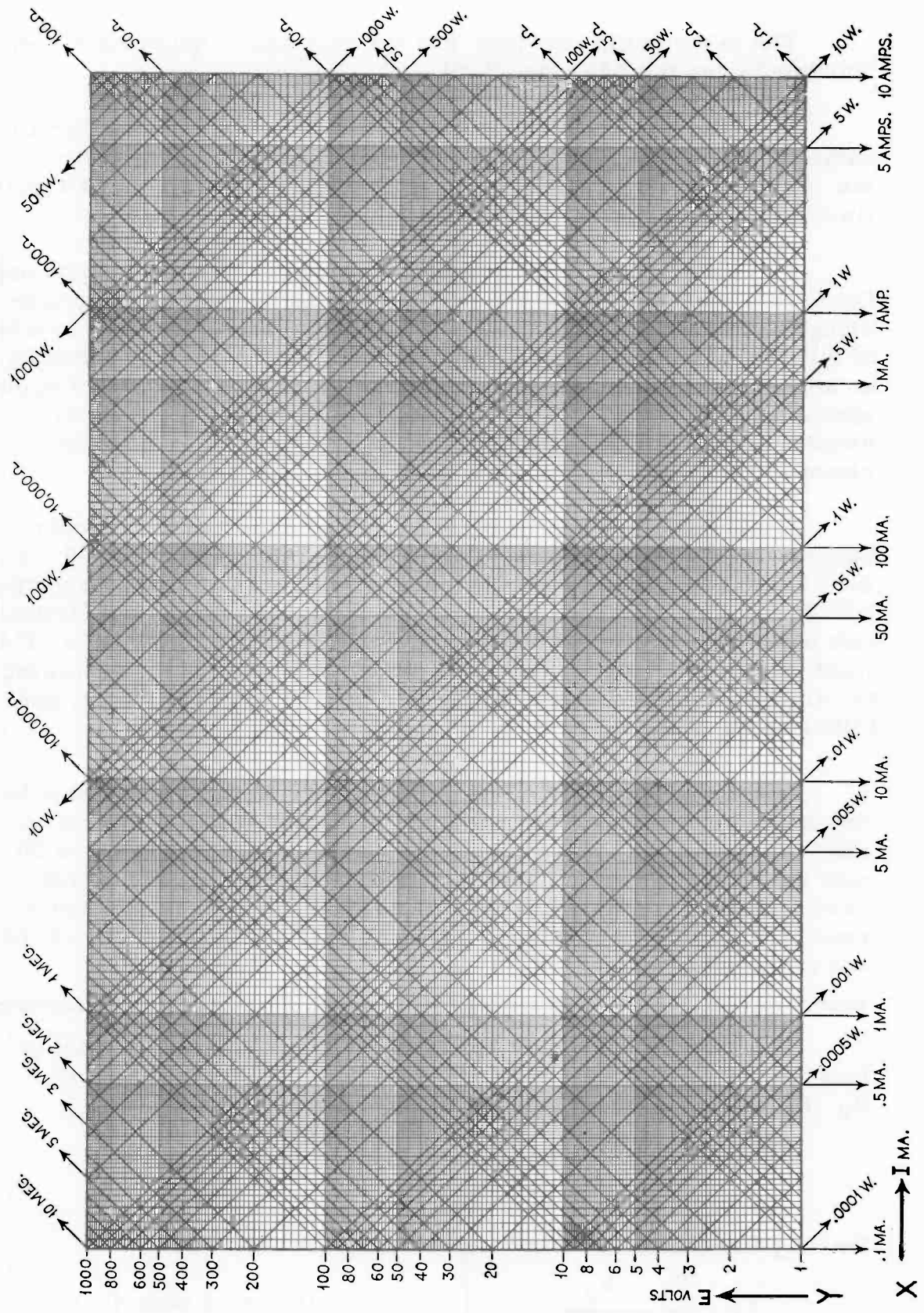
$$R_p = \frac{R_1 \times R_2}{R_1 + R_2} \qquad \text{(See also page 46.)}$$



In the preceding formula if we let $R_1 = 3$, and $R_2 = 5$ ohms,

$$R_p = \frac{3 \times 5}{3 + 5} = \frac{15}{8} = 1.875 \text{ ohms}$$

If a total current I_t flows in the circuit, only a fraction of this current will be in each resistor. However, the full voltage E will be across each resistor. The current in the resistors may be found from the formulas:


$$I_1 = \frac{E}{R_1} \qquad I_2 = \frac{E}{R_2}$$

and, of course, $I_t = I_1 + I_2$

The power handled by each resistor may be found easiest by applying the formula: $W = \frac{E^2}{R}$

In circuits where more complex combinations of resistances are present, individual parts are solved separately and combined. This process is best illustrated with an example.

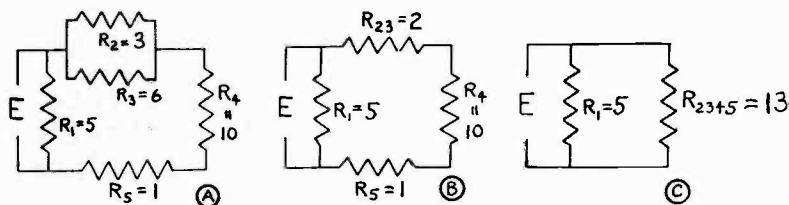In circuit A, we may consider R_2 and R_3 as parallel resistors.



Now we can replace circuit A by B, placing a single resistor R_{23} in place of R_2 and R_3 . Consider now R_{23} , R_4 , and R_5 as a single series circuit.

$$R_{2345} = R_{23} + R_4 + R_5 = 2 + 10 + 1 = 13 \text{ ohms}$$

We now can replace B, with circuit C. This circuit is a simple parallel circuit having two resistances of 5 and 13 ohms.

$$\text{Total equivalent resistance} = \frac{5 \times 13}{5 + 13} = \frac{65}{18} = 3.6 \text{ ohms}$$

This method of solving complex circuits is always used. While the steps may appear a little difficult the actual work is quite simple. The student should draw some circuits having resistors in series and parallel combinations, and solve these circuits for practice. The student may also examine the circuit diagrams in later lessons for actual examples of similar use of resistors.

M A G N E T I S M

Magnetic force plays a very important role in the operation of many radio components. Transformers of all types, phonograph pickups, loud-speakers operate on the principle of magnetism. In other fields of electricity, magnetism also is of a great importance. Being similar to electricity we cannot actually see or feel magnetism, but the effects of this force can be noticed and accurately measured.

There are certain natural magnets found already magnetized. If a piece of hard steel is stroked continuously in the same direction with a piece of natural magnet, the steel will become magnetized. For practical use, small percentage of nickel, chromium, cobalt, or tungsten are added to steel for making permanent magnets that have greater magnetic strength and other desirable properties.


Just as in the case of electrical charges,

UNLIKE MAGNETIC POLES ATTRACT EACH OTHER

LIKE MAGNETIC POLES REPEL EACH OTHER.

Also it is important to remember that the force of attraction or repulsion between two magnets is inversely proportional to the square of the distance. A north and south magnetic poles will attract each other four times as much at 1 inch distance, as at 2 inch distance. This is why the space between the field and the armature in a generator is made as small as practical.

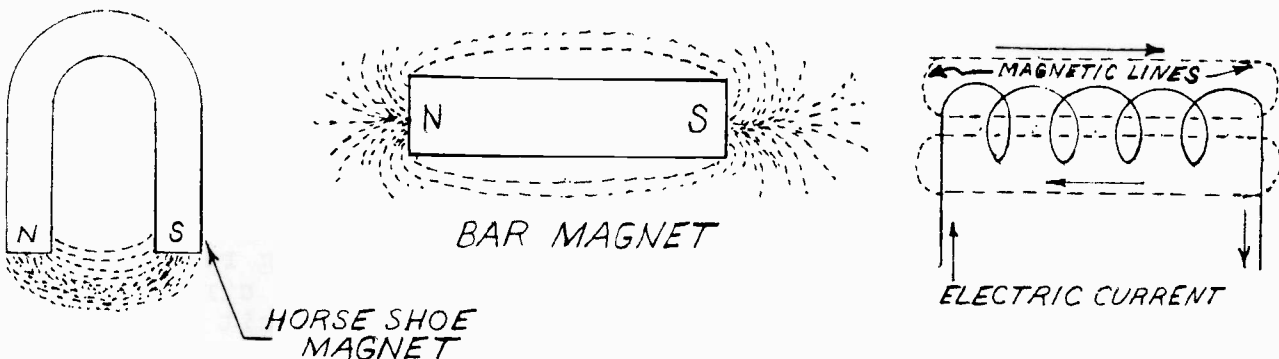If either end of a bar magnet is dipped into iron filings, most of the filings will stick to the pole indicating that the attractive force is the greatest at the poles. This magnetic effect is noticeable for a considerable distance around the magnet. This force constitutes the magnetic field and is made up of lines of force. The filings around the magnet follow the lines of force.



If a strong magnet is dipped in a barrel of nails made of soft iron, many nails will be picked up. Some nails in turn will hold other nails becoming themselves temporary magnets. However, once these nails are removed from the magnet, their magnetism will be lost. Hardened steel substances on the other hand will retain some magnetism once they are brought into contact with a magnet.

ELECTROMAGNETISM

Although many devices employed in radio circuits depend on permanent magnets for their operation, magnetism produced by the flow of electric current through a conductor finds even greater application. Every wire carrying electric current has an associated magnetic field proportional to the current strength and the arrangement of the wire.

The fact that an electric current in a conductor has an associated magnetic field may be easily proven. If a compass is held near the wire, the needle of the compass (actually a small magnet on a pivot) will take a position at right angles to the wire. If no current is present in the wire, the needle will assume its natural N - S position.

An electromagnet is made by winding a number of turns of wire in the form of a coil, a much stronger magnetic field can be created since the fields of all the individual turns will add up. Since the magnetic field of force of each turn adds to that of the next turn, the greater the number of turns of wire the coil has, the stronger will be the magnetic field.

The total magnetic flux (lines of force) depends on the number of turns and the current strength. If the current is strong, relatively few turns of thick wire will be needed to produce a given magnetic field. On the other hands, if the current is very minute, a great many turns of fine wire will be needed.

If a bar of iron is placed in the center of the coil, the iron will become magnetized when the current will flow through the coil, but will loose its magnetism once the current is stopped. This principle is used to operate relays, door bells, and other devices.


After a certain value, the effect of the applied electromagnetizing force will be diminished and, if the force is increased past a definite limit, no further effect will be noticed. The substance is then said to be saturated. For example, Wrought Iron will have a very strong flux when inserted in a coil of 10 ampere-turns. Increasing this to 20 ampere-turns only increases the lines of force per square inch from 89,000 to 97,000. At 40 ampere-turns this figure is only 106,000 lines per square inch. Saturation is reached when a further increase in ampere-turns has no effect on the flux.

ELECTROMAGNETIC INDUCTION

We have learned that an electrical current in a conductor sets up an associated magnetic field. If a conductor, connected to some indicating instrument such as a sensitive galvanometer, is moved across the magnetic field of a permanent magnet, a current will be noticed to exist in the circuit. The current will only be present while the motion continues and will be proportional to the rate of motion, the number of turns of wire being swept across, and the total flux or the number of lines of force. This principle of current generation is employed in all electrical dynamos.

It is also possible to induce a current in one conducting circuit by means of the magnetism produced by the current flowing in another associated, but not electrically connected, circuit. The flux set up by the first circuit induces a current in the second circuit. This action takes place only while the current in the first circuit is changing (increasing or decreasing), as in the case when the first circuit is connected to a source of Alternating Current (A.C.) that is periodically rising and falling. The circuits must be located closely together, that is coupled. A device used to transform electrical energy by induction is called a transformer. A transformer does not create energy, it simply separates two circuits, or steps up or down voltage. When any voltage is stepped up by means of a transformer, the current correspondingly in the same ratio is stepped down.



The coil receiving the original current is called the primary, and the coil in which the current is induced by electromagnetic induction is called the secondary. In the illustration it is evident that since only a part of the lines of force set up by the primary link the secondary coil, the current induced is not as great as would be in case all the lines of force linked the secondary. The lines of force not linking the secondary and, therefore, not being useful are termed the leakage flux. To keep the lines of force in the desired path, soft steel material is used for the core.

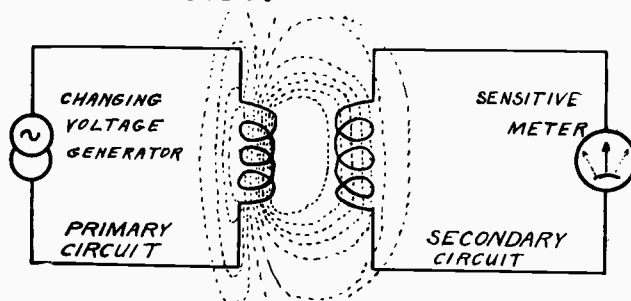

Transformers and inductors having air cores are used in radio receiving circuits where the frequencies encountered are very high and would create heavy losses due to eddy currents and hysteresis if iron cores were used. Where the frequencies are relatively low as in the case of audio frequencies, (commonly employed 30 to 12,000 cycles per second) and power frequency of 60 cycles, iron laminated cores are used.

SELF INDUCTION

An electric current flowing through a conductor sets up a magnetic field around the wire. If the current is varied, the magnetic field also varies correspondingly. This varying field sets up in the wire itself, a counter or self-induced e.m.f. which opposes any changes. A voltmeter connected in the battery circuit illustrated above to the right, will indicate the battery voltage when the key is closed. Upon again opening the key, the voltmeter will momentarily indicate a large deflection (voltage) in the opposite direction. This action indicates that the magnetic lines of force around the coil have broken down to refrain the current of the coil from changing. This effect is similar to that of inertia found in mechanical devices. Inertia tends to oppose any changes in the speed or direction of motion. The effect of self-induction is especially noticeable in a solenoid (coil) since the inductance is concentrated in a small space. The unit of inductance is the Henry. The symbol for inductance is L.

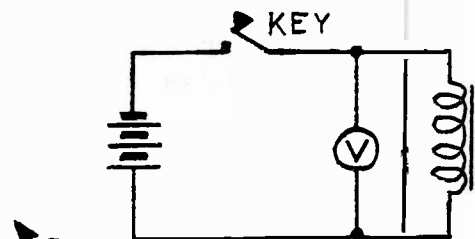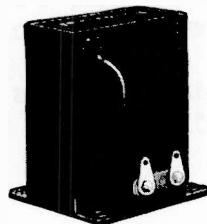

Audio chokes which may be used in this test.

The Henry is a relatively large unit and while some audio coils having special iron cores have an inductance of several hundred henries, the inductance encountered in coils used in radio frequency work and having air cores is only a small fraction of a henry. One/thousand of a henry is a millihenry, and one/million part of a henry is called a microhenry. Coils used for tuning the broadcast frequencies are in the order of 250 microhenries.

Inductive coils may be connected in series, in parallel, and in other combinations without the magnetic fields interlinking to any degree. When inductors are connected in series, the total effective inductance is the sum total of the individual inductances.

If a coil having an air core has a given current passing, a magnetic flux of a certain value will be produced. If an iron core is slipped in, replacing the air core, the electromagnet so formed will have a flux 200 times as strong. By using special nickel-iron material for the core, the strength can be made even greater. The ratio of the strength of the magnetic field with a given substance to the strength of the field when air is used as the core is the permeability. The permeability of air is taken as 1, all magnetic substances have a permeability greater than one.

REVIEW QUESTIONS

1. What does the prefix "milli" mean?
2. Since each cell in a "B" battery generates $1\frac{1}{2}$ volts, how many cells are connected in series to produce the full voltage of 45 volts? Do you understand why a "C" battery has $4\frac{1}{2}$ volts and not 5 volts?
3. Rewrite the following decimals as fractions: 0.5, 4.25, .05, 2.3, and 0.1.
4. Rewrite the following fractions as decimals: $1/10$, $3/100$, $3/50$, $3/2$, and $1/3$.
5. What is the square root of 81? Of 49? Of 2.25?
6. In a 110 volt D.C. circuit an electric bulb takes $1/2$ ampere of current. What is the resistance of the bulb? (Use the Ohm's Law relation).
7. A 100 ohm resistor is connected across a 10 volt battery. What current is being taken from the battery?
8. In Question 7, what power is being used?
9. Examining a radio circuit, estimate the current in the various resistors and calculate the voltage drops and power dissipated. You may use the chart for this purpose.
10. If a 12 ohm and a 6 ohm resistors are connected in series, what is the equivalent resistance?
11. If a 4 ohm and a 8 ohm resistors are connected in parallel, what is the equivalent resistance?
12. Make up your own complex circuit of resistors and solve it following the example given in the text.
13. On what two factors does the magnetic flux depend?
14. Make a sketch of a buzzer and battery and explain how this unit operates?
15. How are power transformers made? What materials are used and how does the transformer operate?
16. What effect does a choke coil have upon the changing current in a circuit?

LESSON 5

RADIO FREQUENCY INDUCTANCES

MUTUAL INDUCTANCE

In the section on Self-Inductance, above, the definition of "Self-Inductance," and the properties thereof were briefly explained. If, in the example of the bunched winding, half of the turns formed one circuit and the remaining half formed another circuit, a change in magnetic flux occasioned by a change in current in one winding, would induce two voltages, one in its own winding opposing the change in current, and the other in the second coil. This phenomenon of a voltage induced in the turns of one coil by a change in current in another coil is known as "Mutual Inductance."

The unit of Mutual Inductance is the "henry" defined as that value of mutual inductance in which one volt is generated across the terminals of one coil when the current in the other coil is changing at the rate of one ampere per second.


The practical units for Mutual Inductance are the same as those for self inductance, namely the Henry, Millihenry and Microhenry.

A very convenient property of mutual inductance is that the mutual inductance existing between two dissimilar coils is the same, whether the current change is in the large coil and the voltage is measured in the small one or vice versa, regardless of how dissimilar the coils may be.

This phenomenon called mutual inductance makes the formulae for inductances in series or in parallel much different from the formulae for resistances. In the latter case, the equivalent resistance of two resistances in series is the sum of the individual resistances; but in the case of two inductances in series, there may be a mutual inductance between the coils that may seriously disturb that simple relationship. If the two coils are placed so that the wires of one coil and those of the other coil occupy practically the same space, as in the case of winding the second coil as a single layer directly over the first single layer coil, or between the turns of the first coil, the overall inductance of two equal coils wound as above, will be twice the sum of the inductances of the two individual coils, if the coils are connected "Aiding" and will be practically zero if connected "Opposing." This is a special case which seldom occurs, but shows one of the extremes of mutual inductance which can influence the equivalent inductance of two coils connected in series.

The general expression for any case involving only two coils in series is: overall inductance equals the sum of the individual inductances plus or minus twice the mutual inductance. The reason for this relationship is given in the following explanation.

A current change in coil No. 1 induces in itself a voltage proportional to its inductance, and similarly in coil No. 2 a voltage proportional to the inductance of coil No. 2. The current change in coil No. 1 induces a voltage in coil No. 2 proportional to the mutual inductance between the two coils, and similarly the current change in coil No. 2 induces a voltage in coil No. 1 of the same magnitude because the mutual inductance is the same whether measured from the first to the second coil, or in the reverse direction. The overall inductance is proportional to the total voltage induced, and is consequently equal to the sum of the individual inductances plus or minus twice the mutual inductance. The "plus or minus" provision is made because the voltage induced in one coil by a current change in the other does not necessarily aid the self-induced voltage in the coil. Inductances themselves are positive, there being no negative inductances; nor, strictly speaking, are there any negative mutual inductances; but a mutual inductance may be connected into a circuit so that its effect may oppose some other effect and can be considered as a negative mutual inductance when so connected.

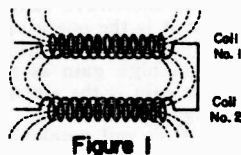

COUPLING COEFFICIENT

When two coils are arranged so that some definite mutual inductance exists, the coils are said to be magnetically coupled.

In many calculations, it is frequently convenient to express the amount of coupling as a percentage of the maximum that could possibly exist, rather than a numerical value of mutual inductance. In such a case, the term applied to this percentage is "coupling coefficient" which, for inductance, is defined as the quotient resulting from dividing the existing mutual inductance by the maximum possible mutual inductance (square-root of the product of the two separate inductances).

The losses in a coil may be divided into the following classes:

- 1— Ohmic or D.C. losses in the wire
- 2— Eddy-current losses in the conductor
- 3— Eddy-current losses in the shield
- 4— Eddy-current losses in the core material
- 5— Skin effect
- 6— Dielectric loss in the wire insulation
- 7— Dielectric loss in the terminal strip

None of these items is independent of the others, and a change to improve one usually changes one or more of the remaining factors.

Since all of the losses in a coil taken together make up the radio frequency resistance of the coil, a single number can be used to express this quantity, but the resistance alone does not give sufficient information to judge the electrical excellence of the coil. Resistance is usually the undesired quantity in a coil, and practically all coil designs attempt to make it as low as possible. Reactance is the desired characteristic of the coil and is the product of frequency, inductance and the usual multiplier, 2π . A special term has been given to the ratio of the desired to the undesired characteristic of the coil. This term is "Q" which is defined as the reactance divided by the resistance.

ANTENNA COILS

The basic types of antenna coils have high-impedance inductive, high-impedance capacitive, low-impedance inductive and low-impedance capacitive couplings. Typical values of capacity, self inductance and mutual inductance for these four types of broadcast coils are shown in Fig. 3.

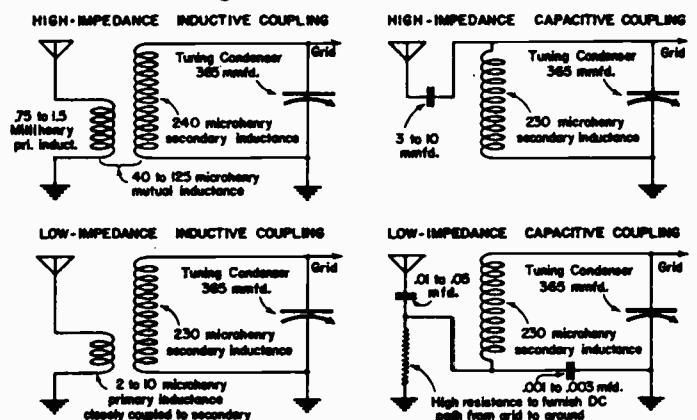


Figure 3 Typical Antenna Coils

HIGH-IMPEDANCE PRIMARY

High-impedance magnetic coupling, usually spoken of as "High-Impedance Primary" is the most universal type of coupling on the broadcast range of household receivers. It has good image ratio, reasonable gain, and, when properly designed, almost negligible misaligning of the first tuned circuit as the size of antennas is changed. With the usual design of coil, this type of coupling results in higher gain at the low-frequency than at the high-frequency end of the tuning range. Sometimes, to compensate for this deficiency at the high frequency end, a small amount of high-impedance capacity coupling is used. This capacity is connected from the antenna to the grid terminals of the coil. Its size is from 3 to 10 MMF.

It is to be noted that capacity coupling can reduce as well as raise the gain of a high-impedance magnetically coupled transformer, depending upon the polarity of the windings. If capacity coupling is to aid the magnetic coupling, a current entering the antenna terminal of the primary and the grid terminal of the secondary must go around the coil form in opposite directions, and the coupling capacity must be connected between these two points.

LOW-IMPEDANCE PRIMARY

Antenna coils with low-impedance primaries, although cheaper to manufacture than high-impedance primaries, are rare on the broadcast band of modern home radio receivers.

This type of coupling, when used with any of the conventional household antennas, gives a great deal more gain at the high-frequency end than at the low-frequency end of the tuning range. This gives rise to very poor image-ratio when used in a superheterodyne receiver.

The closely coupled low-impedance primary reflects the antenna capacity across the tuned circuit in an amount depending upon its inductance and coupling coefficient. Without attempting to derive an expression for the actual magnitude of this effect, suffice it to say that if the primary is large enough to give reasonable gain at the low-frequency end of the frequency range, the reflected antenna capacity will be so high that the secondary tuning condenser will not be able to tune to the high-frequency end of the band, and every different antenna capacity would change the amount or mis-tracking. Because of this sensitivity to changes in antenna capacity, and because of poor image ratio, the low-impedance primary is seldom used on broadcast-band antenna coils.

On short-wave coils, the low-impedance primary is used almost exclusively because the antenna gain is usually higher than with a high-impedance primary, and the antenna is usually resonant in or below the broadcast band. For this reason, the image-ratio does not suffer nearly as much as in the case of using low-impedance broadcast coils in place of coils with high-impedance primaries.

HIGH-IMPEDANCE CAPACITY COUPLING

The high-impedance capacity coupling scheme consists essentially of connecting the antenna directly to the grid end of the first tuned circuit through a capacity, usually from 1 to 10 mmf. This method of coupling has been popularly used on amateur receivers of simple design, where simplicity of coil construction was imperative, but is not used in broadcast receivers by recognized manufacturers because of the very poor image-ratio that results.

Practically speaking, the only use for high-impedance capacity coupling in a broadcast receiver is as reinforcement to a high-impedance primary, as discussed in the paragraph on "High-Impedance Primaries."

LOW-IMPEDANCE CAPACITY COUPLING

Low-impedance capacity coupling, familiarly known among radio engineers as the Hazeltine coupling system, consists of coupling the antenna directly to the junction of the low side of the tuning inductance with the high side of a high-capacity coupling condenser which is connected to ground. (See Fig. 3.) The voltage across this coupling condenser is multiplied by the resonance phenomena of the tuned circuit to give appreciable voltage at the grid.

This circuit is particularly adapted to receivers that must use a high-capacity shielded lead-in such as an automobile radio receiver. In such a circuit, the shielded lead-in is made part of the coupling capacity because of the circuit arrangement and, practically speaking, causes no loss in voltage as would be occasioned if this capacity would be connected across a high-impedance primary. For this statement to be strictly true, it is necessary that the shielded lead-in have a good power factor or else the losses in the lead will slightly reduce the effective circuit "Q," thereby bringing down the gain in the antenna coil by a corresponding amount.

This type of coil has high gain and excellent image-ratio. The drawbacks to its use are that the R.F. amplifier circuit, if used, must have a value of capacity included in its tuned circuit equal to the antenna coupling capacity in order that proper tracking may result.

R. F. COILS

R.F. coils may be divided essentially into four types: high-impedance magnetic, low-impedance magnetic, high-impedance magnetic with high-impedance capacity coupling, and choke-coupled circuits.

The high-impedance magnetically coupled R.F. coil has characteristics very similar to the high-impedance antenna coil and therefore needs little discussion.

The low-impedance magnetically coupled R.F. coil has the same deficiency as the similar antenna coil and is consequently seldom used in the broadcast range of a superheterodyne receiver. Like the antenna coil, it has possibilities for higher gain than the high-impedance type, but usually the selectivity is enough worse to rule out this type of coupling on modern receivers.


In the shortwave range, this is the most popular type of circuit, because it is the one giving the highest gain and since, with a fixed capacity of gang condenser, it becomes increasingly more difficult to obtain high gain as the frequency is increased, this circuit with its high gain is the almost universal choice in spite of its deficiencies in image-ratio.

The R.F. coil employing a high-impedance primary in combination with high-impedance capacity coupling is the most flexible design, and is popularly used for that reason. By shifting the primary resonant frequency and by changing the amount of capacity coupling together with changes in "Q" of the secondary circuit, the overall gain of an amplifier stage can be made to have almost any desired shape with respect to frequency; that is, it may give high gain in the middle, at the high-frequency end, at the low-frequency end, or almost any shape desired, to compensate for the frequency characteristics of the other stages employed in the receiver.


The choke-coupled R.F. circuit is very similar to the high-impedance primary with high-impedance capacity coupling, except that, in choke coupling, the magnetic coupling has been made zero, but design still requires that the choke have as much inductance as a primary would have, in order that the resonance of the primary circuit may fall outside of the tuning range of the secondary.

IF TRANSFORMERS

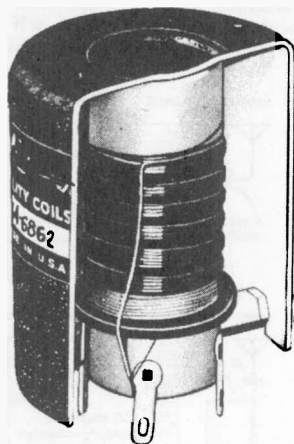Intermediate-frequency transformers used in radio receivers have taken a variety of forms and have operated at many different frequencies. They may be divided into several classes according to the number of selective circuits: untuned or self-tuned, single-tuned, double-tuned, and triple-tuned.



Courtesy Meissner Mfg. Co.

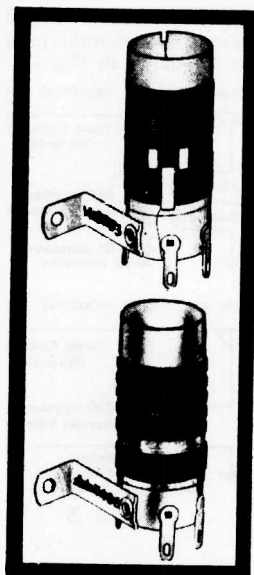


SINGLE-TUNED IF TRANSFORMERS

The single-tuned IF transformer has taken two important forms, the bi-filar coil and the double coil types.

In the former case, the two wires constituting primary and secondary are wound simultaneously, forming a coil that is a single physical unit yet having two independent circuits. The start of the primary was usually the plus "B" connection and the start of the secondary was ground. The outside of the primary was the plate connection and the outside of the secondary was the grid connection. These transformers were characterized by very high gain and comparatively little selectivity.

IF TRANSFORMER LEADS

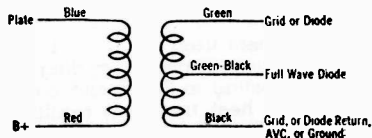


With this transformer redesigned to have two physically separate coils wound side by side, the objectionable features of leakage, corrosion and hum transfer are reduced to a very small per cent of their original importance, and transformers acceptable in today's critical market can be produced. The largest remaining objection to the single-tuned transformer is selectivity. In a low-frequency amplifier operating at 125 KC or 175 KC, the transformers are too sharp for good audio fidelity, and at the higher intermediate frequencies such as 456 KC, the transformers do not add sufficient adjacent-channel selectivity.

Single-tuned transformers may be divided into two classes according to the circuit tuned; some have their primaries tuned while the remainder have their secondaries tuned. As far as secondary voltage is concerned, there is not a great deal of difference regardless of which winding is tuned, but if there is a question of single-stage oscillation in the tube driving the single-tuned transformer, greater stability is had by tuning the secondary than by tuning the primary.

DOUBLE-TUNED IF TRANSFORMERS

The double-tuned IF transformer is, by far, the most popular type. It is simple in construction, has negligible leakage, no measurable hum transfer into diode circuits and can have its selectivity curve made as sharp as two single-tuned transformers in cascade, or can be considerably broader at the "Nose" of the selectivity curve than two cascaded single-tuned transformers, yet on the broader part of the selectivity curves maintain practically the same width as the cascaded single-tuned transformers.

If the coupling on a double-tuned transformer is made sufficiently loose, the transformer is quite selective and has a resonance curve of the same general shape as a single circuit, except sharper. As the coupling is increased, the gain will go up until the point of "critical coupling" is approached where the gain of the transformer is practically constant but the selectivity curve is changing, particularly at the "nose" of the curve. As the coupling continues to increase, first there is a decided flattening on the nose of the selectivity curve, after which continued increase in coupling produces an actual hollow in the nose of the curve. Still greater increase in coupling can spread the two "humps" and deepen the "hollow" in the nose of the response curve until a station can be tuned in at two places on the dial very close together.

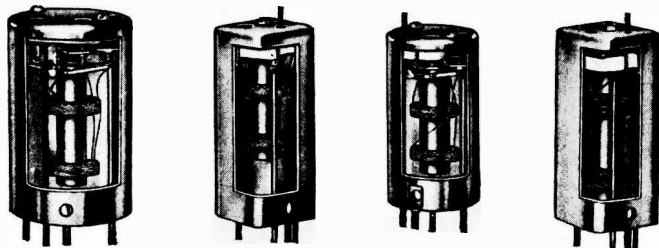

TRIPLE-TUNED IF TRANSFORMERS

Triple-tuned IF transformers have been used for two general purposes: greater adjacent-channel selectivity without increasing the number of tubes and transformers, or a better shape on the nose of the selectivity curve to produce better audio fidelity than is produced by double-tuned transformers.

CAPACITY-COUPLING IN IF TRANSFORMERS

The ordinary circuit diagram of a double-tuned IF transformer is as shown in Fig. 6, but actually the circuit in Fig. 7 is more representative of true conditions.

The capacity coupling, shown in dotted lines, is a very important part of the coupling in practically all transformers operating at frequencies above 400 KC. This statement applies with even greater emphasis as the frequency, or the "Q," of the coils is raised.

The capacity that is effective in the above mentioned "capacity coupling" is that which exists between any part of the plate end of the primary circuit and any part of the grid end of the secondary circuit; to be more specific, the capacity between the plate and grid sides of the trimmer condensers, the plate and grid ends of the coils, the plate and grid leads, the grid lead and the plate end of

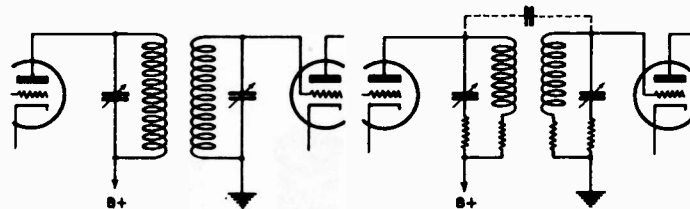


Figure 6

Figure 7

the primary coil, and between the plate lead and the grid end of the secondary coil.

The capacity between the two high-potential plates of a trimmer condenser such as the Meissner unit shown in Fig. 8 is 0.35 mmfd. if both trimmers have an even number of plates and the bottom plate of each trimmer (on the same base) is a high-potential (either grid or plate) electrode. If an odd number of plates is used on both trimmers, the capacity drops to 0.07 MMF. The difference between these two coupling capacities, amounting to only 0.28 MMF. is sufficient to make quite a difference in the gain of transformers operating above 400 KC.

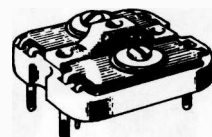


Figure 8

Double-tuned IF transformers may be built with the magnetic coupling either aiding or opposing the capacity coupling. For reasons of production economy, both coils on one dowel are usually wound simultaneously, which means they must be wound in the same direction. For reasons of production uniformity, the insides of both windings are usually chosen as the high-potential ends of the coil so that the outside (low-potential) ends of the coils will automatically act as spacers to keep the high-potential hook-up wires from approaching the high-potential ends of the coils.

Triple-tuned IF transformers, particularly output transformers where diode and plate leads both pass through the open end of the shield can, are particularly subject to gain and selectivity variations as a function of variation in capacity coupling.

As an example, in a particular triple-tuned output transformer where the plate and diode leads ran close together, it was found that in attempting to align the transformer, the middle circuit was effective as long as either the input circuit or the output circuit was out of tune, but as soon as both input and output circuits were aligned, the center circuit had a very peculiar action. If the gain of the transformer is plotted against the capacity of the middle circuit, a curve similar to Fig. 11 was obtained. From this it is seen that there is one adjustment (A) that produces an increase in the overall amplification of the transformer. At this point the center circuit is contributing to the selectivity of the transformer. At another point (B) the amplification through the center circuit opposes the capacity coupling from the input to the output winding and results in a considerable decrease in amplification. At all other settings of its tuning condenser, the center circuit is so far out of resonance that it has no effect upon the gain of the transformer, which for all practical considerations, may be assumed to be a double-tuned capacity-coupled transformer. When the capacity between the high-potential input and output leads was reduced to a very low value by keeping the leads in opposite corners of the shield can, the transformer behaved as a triple-tuned transformer should, with all three circuits effective.


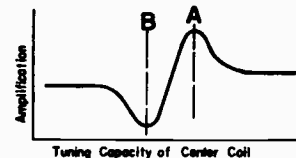


Figure 11

RADIO COILS

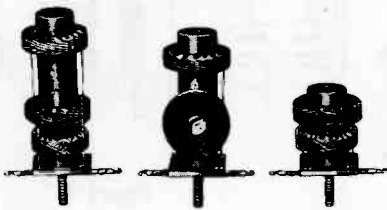
Examples of the type of coils commonly used in radio receivers are illustrated. Please read the descriptions carefully and be able to identify any of the types. Notice the advantages of each type. Selector switches are used in multi-band receivers. The loop antenna has replaced the antenna coil in most portable and midget radio sets.

TRF AND SUPERHETERODYNE COILS DUO-LATERAL WOUND




Single-section, Litz-wire-wound duo-lateral secondary. High-impedance primaries. Wound on treated hardwood dowel with bakelite terminal plate. Use with .000365 mfd. variable condenser.

HIGH GAIN SERIES

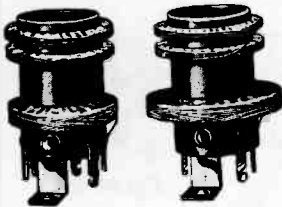

Sectional wound duo-lateral secondary, using No. 15/41. Litz-wire High-impedance primaries for uniform gain with any screen grid tubing. Wound on XXX bakelite tubing. Use with .000365 mfd. variable condenser.


IRON CORE COILS

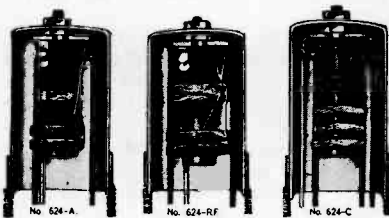

Sectional-Duo-lateral-wound on Armitte sleeves. Special iron-core provides extremely high "Q" in minimum space. Especially adapted to auto and aircraft receivers. Use with .000365 mfd. variable condenser. Antenna coil has a low-impedance primary for operation on mobile antenna equipment. R.F. Coil has high-impedance primary for maximum gain.

ment. R.F. Coil has high-impedance primary for maximum gain.

TWO BAND COILS

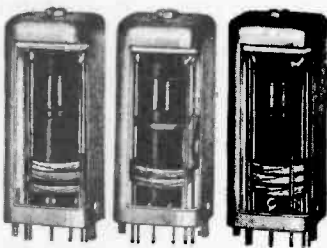

Especially designed for the constructor who wishes to build an inexpensive 2-band receiver covering standard broadcast band and either of two short-wave bands. Adaptable to Marine receivers. Wound on high-grade bakelite tubing. Assembled in aluminum shields with trimmer condensers. For use with .000365 mfd. variable condenser and 455 KC I.F. Amplifier.


AIR CORE UNSHIELDED CHOKES



Duo-Lateral-Wound, single-section, Radio Frequency Chokes are ideally suited for receiver applications wherein a moderately priced unit is required. These chokes are wound with silk-covered wire, on impregnated hard-wood dowels. A bakelite terminal plate, 1 1/8" in diameter, is fastened to the dowel with a tubular brass eyelet, providing for single-hole mounting with a #6/32 machine screw. The winding on these chokes is impregnated to prevent any moisture absorption. Inductance values accurate to within three percent.

MICA COMPRESSION TYPE DOUBLE TUNED AIR CORE

Mica-Compression trimmers used in I. F. Transformers are treated with our exclusive automatic cycling heat treatment consisting in alternately heating to 200°F and cooling to 90°F through 5 complete cycles. This heat treatment results in a much higher degree of capacity-stability, which insures perfect alignment of the I. F. Transformer under conditions of varying temperatures encountered in modern Radio receivers. **All Shields Aluminum.**

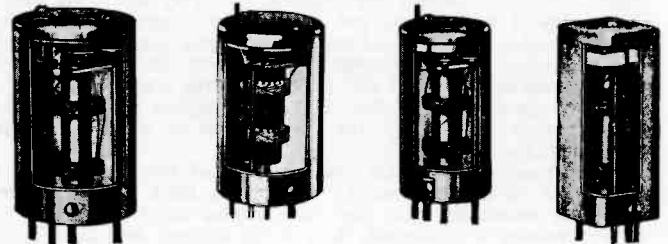


REPLACEMENT I.F. TRANSFORMERS DOUBLE TUNED




These Transformers are an essential part of the stock of every service man and dealer. In many cases they give better performance than the original unit. Only the finest materials are used. Every precaution is taken to insure a long and trouble-free life. Coils have Duo-lateral windings on treated hardwood dowels. Double tuned. Heat-Cycled, Low-Drift, Mica-Compression Trimmers. Impregnated in special moisture-resistant wax. Pre-tuned to nominal frequency. Easily identified, color-coded leads. Assembled in "Okite" finished Aluminum shields. Spade-bolt mounting.

BAND SELECTOR SWITCHES

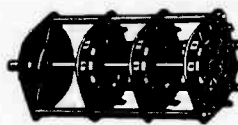


The successful operation of a multi-band receiver depends to no little degree upon the excellence of the switch used. These switches are of a positive self-cleaning type with silver plated contacts. All switches are provided with an adjustable stop.

LOOP ANTENNA

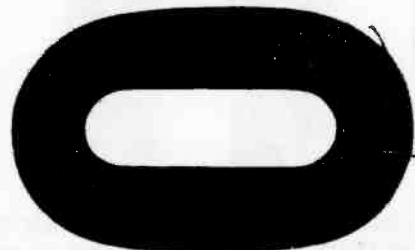

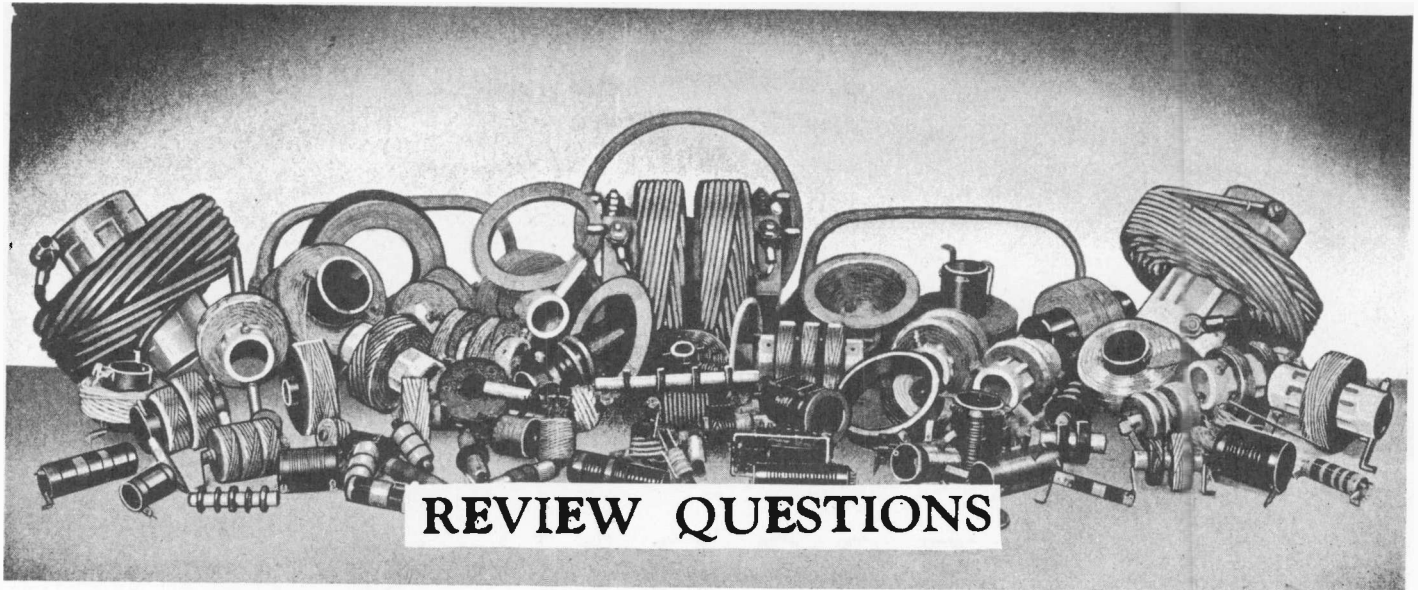Loop Antenna is applicable to most portable-receiver assemblies. The inductance of the loop is high to permit removal of turns to match different sets. The loops are wound from low-distributed capacity wire and are of the flat, pancake type of winding.




1. What is the unit of mutual inductance?
2. What three factors must be considered in designing R.F. coils?
3. Name several losses that may be present in a coil.
4. What factors determine the value of Q?
5. What is the advantage of high-impedance primaries in antenna coils?
6. What type of primary is used on short wave coils? What advantages are obtained because of this?
7. What type of IF transformers are most commonly used?
8. Why is the bi-filar type IF transformer not used very much?
9. Name some advantages of a double-tuned IF transformer.
10. Were the early "single-dial control" receivers really such? Why not? How about present day sets?
11. What new design in antenna coils eliminated the "Antenna Compensator"?
12. Why are trimmers used in gang condensers?
13. What effect will poor alignment have on the operating efficiency of a four tube receiver?
14. Make a pictorial sketch of an antenna coil.



RADIO CAPACITORS

LESSON 6

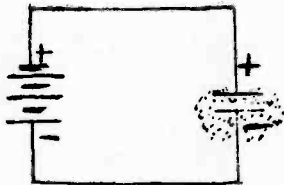


If a condenser is connected to a source of D.C. potential such as a battery, the negative side will become charged with electrons. If the battery connections are removed and the condenser shorted, a spark will jump across the point of contact, and the two plates will again be in electrical equilibrium or will be neutral. The strength of the charge will depend on a number of factors as we shall see later.

A condenser must have two plates made of conducting material, and a separation of a non-conducting material or vacuum. The material between the plates is called the dielectric.

Any insulator will serve as the dielectric, but only a limited number of insulators have characteristics that make them especially well suited for this application. Every condenser has certain losses which are almost negligible in a high quality unit.

For one thing, there is an actual resistance loss in the conducting plates of the condenser. The dielectric, while having very high insulating value, does permit a certain leakage. A practical condenser, therefore, may be assumed to be a perfect condenser with no losses, with a resistor connected in series to represent the loss in the conducting plates, and another resistor in parallel to represent the leakage. Because of the leakage loss, a charged condenser will soon lose its charge. There are also other losses, but they are not of importance from the practical point of view.

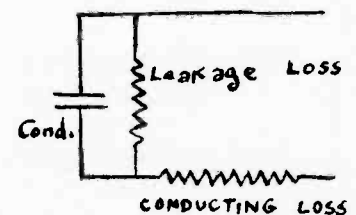The degree of ability of a condenser to store electrical charges is known as the capacity of the unit. Since the quantity of the electrical charge depends directly upon the





E.M.F. (voltage) of the source, capacity is defined in terms of not only how much charge is stored, but also in terms of how much voltage is applied. The unit of capacity is the Farad. The farad is equal to the capacity of a condenser that will store one coulomb of electricity at the pressure of one volt.

The Farad is much too large a unit for radio applications, the microfarad, or mfd. equal to one-millionth of a farad, is commonly used. Condensers of very small capacity are also rated in still smaller units of micro-microfarads or mmfd. being equal to one/millionth of a microfarad.

Condensers, similarly to resistors, may be connected in series and in parallel. When condensers are connected in parallel, the final capacity is greater than that of any condenser used in the combination. The total capacity is equal to the sum of all the individual condensers connected in parallel.

$$C_p = C_1 + C_2 + C_3 + \dots$$

Where C_p is the total capacity of units in parallel. This formulæ suggests a means of obtaining larger capacity from a number of smaller units. Each condenser used, however, must be able to withstand the applied voltage of the circuit. Should 15 mfd. be required and only 5 mfd. units be on hand, three of these may be employed and connected in parallel with equally satisfactory results as might be obtained from a single 15 mfd. condenser.

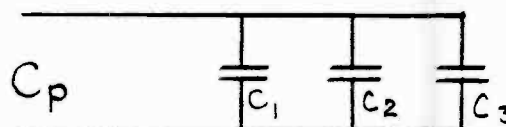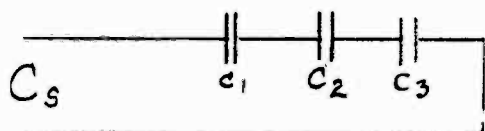

When condensers are connected in series, the final capacity of the combination is always less than that of the smallest used in the combination. It is very rarely that condensers are used in series, except when all are of the same capacity. In such cases, the total capacity


$$C_s = \frac{C}{n}$$

where n = number of condensers of capacity C , connected in series.

There are three factors affecting the capacity of a condenser.

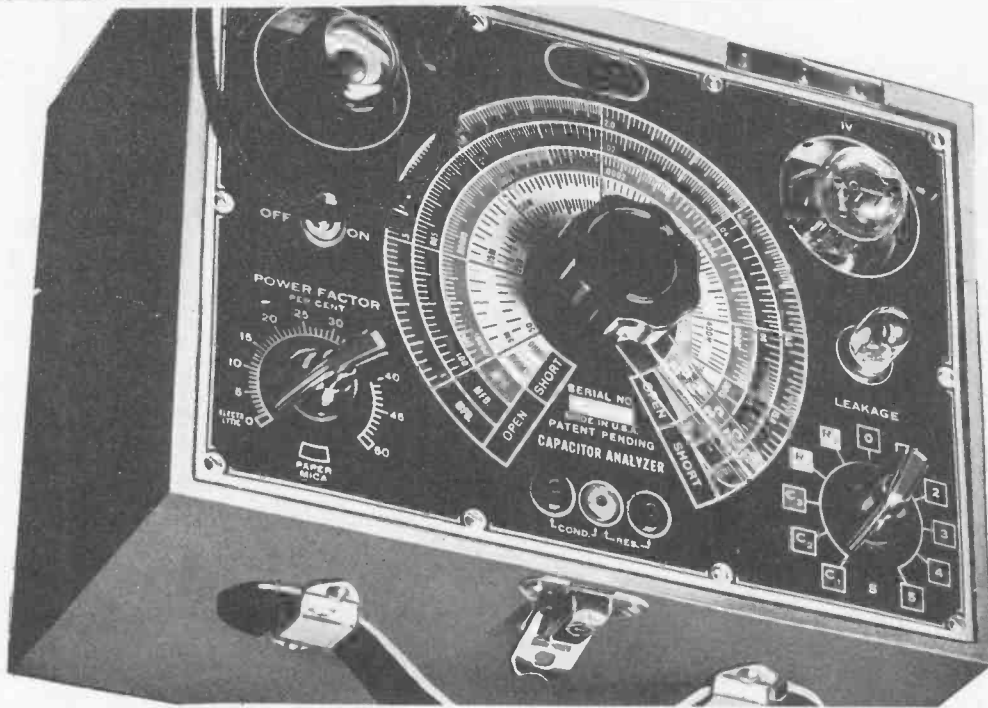- (1) The type of dielectric used
- (2) The area of the plates in contact with the dielectric
- (3) The actual thickness of the dielectric, or what is the same thing the separation between the plates.


It has been found that the capacity of a condenser using air and other substances for the dielectric changed for each definite substance used. For example, certain wax employed for the dielectric made a condenser have twice the capacity as when this same condenser had an air dielectric. Bakelite gave a value $6\frac{1}{2}$ times as large as air, etc. This property of different materials used for the dielectric of condensers is known as the dielectric constant. Air is taken as standard and its dielectric constant is assumed to be 1.



The actual capacity of different condensers may be calculated from formulas, but the serviceman uses commercial units already supplied with the capacity indicated and for the serviceman there will be little need for such calculations. Certain test analyzers have provisions for indicating the capacity of paper and electrolytic condensers directly.


FIXED CONDENSERS

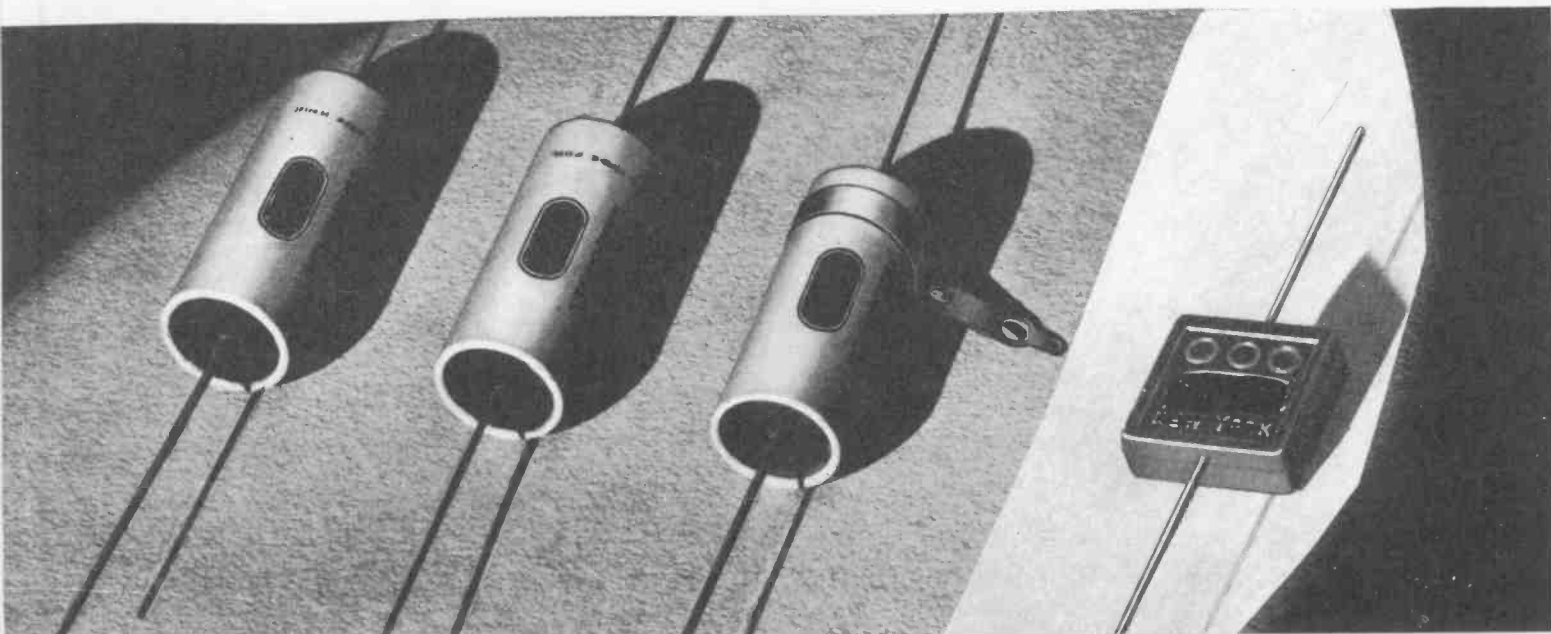Condensers commonly used in radio sets are so constructed that their capacity is fixed at one definite value. The exception is the variable condenser used for tuning the radio circuits into resonance. For low capacity, under .02 mfd., mica insulation is employed. Such condensers are molded in bakelite and are uneffected



by moisture. The value of capacity is marked on the case and for service work suitable similar replacements are easily obtained. Larger sizes are made with paper dielectric and in tubular form. We urge you to carefully note (1) the relation of capacity, breakdown voltage or the working voltage, and the physical size, (2) the general appearance of the units, and (3) the general methods used for connecting the units into the circuits.

While special condenser testers may be used to detect the faults in condensers, a simple ohmmeter will serve the purpose. A small capacity fixed condenser should test open on an ohmmeter. If the condenser has noticeable low resistance (below 50,000 ohms) or is completely shorted, the unit should be replaced. A good test is to connect the condenser momentarily to a source of D.C. potential between 25 and 100 volts. Quickly disconnect the condenser and connect the terminals together. A spark should be noted at the point of contact if the condenser is in good condition.

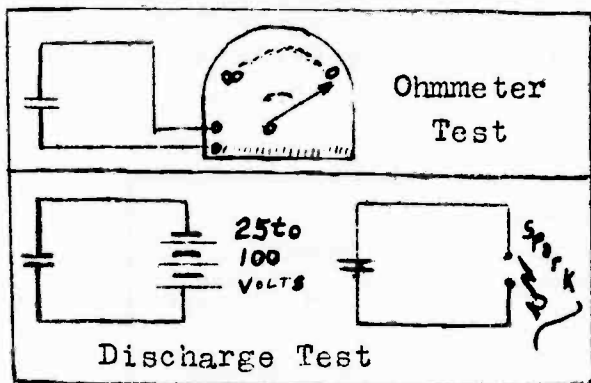

Electrolytics can be quickly tested by the ohmmeter method. They will first upon being connected show a shorted condition, but the resistance will quickly increase. The ohmmeter must be correctly connected, i.e. positive side of the battery to the positive side of the electrolytic condenser. The D.C. potential discharge test may also be used.

In replacing fixed condensers, the serviceman need not be too critical. A slight difference of capacity will ordinarily not upset the circuit and this is especially true if the unit is used as a filter. 8 or 12 mfd. units may be used for 10 mfd. However, the rated working voltage is important and must not be overworked. Condensers rated at 550 volts D.C. may be used on any voltage up to this maximum rated voltage, but not above. A.C. voltage peaks are 1.4 higher than the measured and indicated R.M.S. voltage. For example, 110 volts A.C. has peak voltage of 110×1.4 or 154 volts.

CONSIDERATIONS OF ELECTROLYTIC CONDENSERS

An electrolytic condenser is a fixed condenser of high capacity and compact size suitable for use with voltages not exceeding about 550 volts. These condensers must further be used only with D.C. or pulsating D.C. Because of these characteristics, electrolytic condensers are especially well suited for use in radio filter circuits where these advantages over paper type condensers are fully realized, and their limitations are of no consequence.

The electrolytic condenser consists of an anode to which the positive connection is made, the cathode used in conjunction with the negative connection, and the electrolyte. Aluminum is usually used as the anode in condensers for radio application. Other

metals such as tantalum and magnesium find some use; the chief advantage of tantalum being its ability to withstand acid corrosion. For the cathode either aluminum or copper is used in connection with an aluminum anode.

The dielectric film forms electro-chemically on the surface of the anode. The properties of the electrolytic condenser are due to this film formation. The exact nature of this film is not known, but it is extremely thin making possible high capacity per unit area. The capacitance of a film formed at 300 volts on aluminum is 0.12 mfd. per square inch, about eight hundred times that of a paper condenser for this voltage.


In the actual circuit when the potential is first applied, the current is only limited by the resistance of the electrolyte and the external resistance present. Naturally under this condition high currents flow. The film forms quite rapidly, however, and the leakage current drops to a safe value of about 0.2 milliamperes per microfarad. A radio rectifier circuit takes care of this leakage current without difficulty.

CAPACITOR COLOR CODE

Color	MOLDED PAPER		MOLDED MICA		CERAMIC	
	Multiplier	Tolerance	Multiplier	Tolerance	Multiplier	Tolerance
Black	1	20%	1	20%	1	20% or 2.0 μ fd.*
Brown	10		10		10	1%
Red	100		100	2%	100	2%
Orange	1000		1000	3% (RETMA)	1000	2.5% (RETMA)
Yellow	10,000	5%	10,000		10,000	
Green				5% (RETMA)		5% or 0.5 μ fd.*
Blue						
Violet						
Gray					0.01	0.25 μ fd.*
White		10%			0.1	10% or 1.0 μ fd.*
Gold	0.1	5%	0.1	5% (JAN)		
Silver		10%	0.01	10%		
None		20%				

*Capacitance less than 10 μ fd.

Capacitance is given in μ fd. Colors have same values as on resistors, except as indicated in tables. Colors (A) and (B) are for first two digits; (C) is for multiplier. (D) is for tolerance. (E) and (F) give voltage rating in hundreds of volts; (E) is used only for ratings less than 1000 volts, (E) and (F) for first two digits of ratings 1000 volts or more. Values of colors for (E) and (F) are same as in resistance values. (G) is class or characteristic of capacitor, (H), (I), and (J) give temperature coefficient. (G), (H), (I), and (J) are not listed in the tables, since this information is seldom needed by the average home builder.

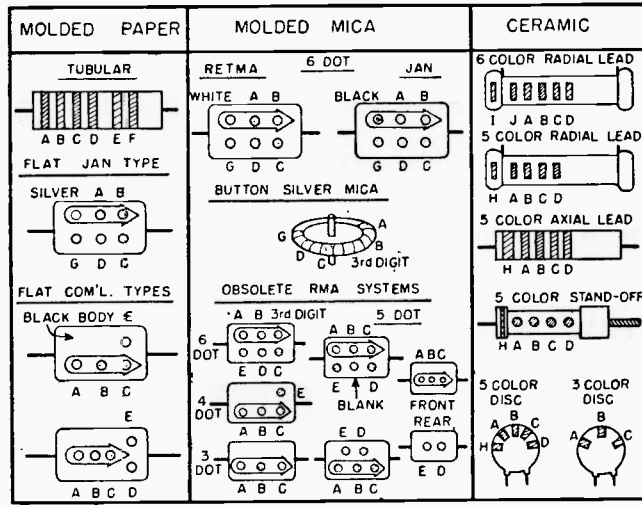

SOME IMPORTANT PRACTICAL FACTS CONCERNING CONDENSER REPLACEMENTS

When there is something wrong with the radio which you are servicing, you are almost safe in saying, "It's a condenser." Of course, there are a great many different types of condensers used in a radio set -- more condensers than any other parts. And also stresses occurring in circuits usually result in higher voltage on some condenser. Keeping this in mind, you will want to know how to find a faulty condenser and how to make the replacement quickly and inexpensively.

You know that condensers do not pass D.C. If they do, you better start replacing the condenser. Now most condensers used in circuits have a higher potential on one side than the other. Test for voltage across such units -- if there is no voltage there must be a short in the unit. You may proceed to shunt similar condenser across each unit suspected. If the condenser under test is in good operating condition, the test condenser will take a charge at the voltage impressed on the original unit. The discharge may be noticed and will be an indication that the unit is not shorted.

What about open condensers? The test suggested will take the place of the defective condenser when used in the circuit for test. Therefore, if this is the fault, during the moment the test is being made operation will be restored. Then just replace the condensers and the radio is repaired.

Are the values of condensers important? Voltage rating is important only in so far as the new unit used for replacement must have equivalent or higher rating. Notice that a higher rating can always be used. In fact it is advisable to use a replacement condenser for higher voltage rating to prevent the same fault to re-appear again.

Condensers used for by-pass purposes may be replaced by similar units but either larger or smaller in capacity. For example, a 0.1 mfd. cathode condenser can be replaced with a condenser anywhere from 0.01 to 1. mfd. capacity. Filter condensers are in the same line. Larger capacity is strongly recommended.


REVIEW QUESTIONS

1. If a total of 20 mfd. capacity is needed and only 4 and 8 mfd. units are available, how can the required capacity be obtained?
2. What three factors determine the capacity of a condenser?
3. Why cannot electrolytic condensers be used in A.C. circuits?
4. If a single section of a multi-section electrolytic condenser was at fault, would you replace the entire unit, or would you install an extra condenser to replace the damaged section? Explain why.

LESSON 7

ALTERNATING CURRENT THEORY & FILTERS

In our discussion of batteries, we talked about direct current, (D.C.). This current is of constant or varying value but flows in one direction all the time. When the magnitude of D.C. changes, there results pulsating direct current. Alternating current (A.C.) has a changing magnitude and direction. First one terminal is positive having its value rising, see chart A to B. Then the value begins to fall, but the polarity remains the same, see B to C. At C

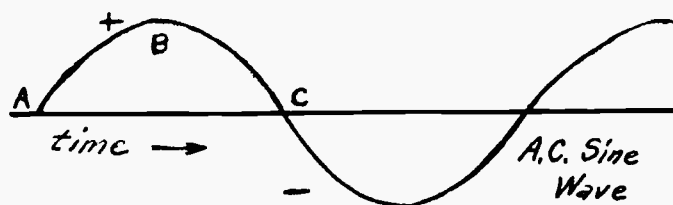

the voltage present is zero, and then it begins to rise in the opposite direction. The process is repeated, but the terminals are reversed. The usual A.C. generated forms sine waves which graphically appear as the one illustrated.

When the voltage has started from zero, has risen to its maximum value in one direction, returned to zero, risen to the maximum value in the opposite direction, and then returned to zero, one complete cycle has been completed. The common power line frequency is 60 cycles per second; this means that sixty such changes occur every second. This explains why in dealing with A.C. time must be considered.

Inductance opposes changes in current intensity. Because in an A.C. circuit the voltage is constantly varying, the current too will vary in accordance. But the inductance present will attempt to prevent a change in the current, and the current will lag behind the voltage. In a pure inductive circuit (no resistance being present), the current will lag 90° behind the voltage and no power will be used. In actual circuits, of course, resistance is always present and the phase angle by which the current will lag behind the voltage will always be less than 90° .


Since, in A.C. circuits, current changes continuously, an inductance will show a definite "resistance" or opposition to the flow of A.C. current. This opposition is known as reactance. The reactance of a coil in ohms may be calculated if the frequency F , and inductance L in henries are known.

$$\text{INDUCTIVE REACTANCE } X_L = 6.28 \times F \times L \quad (\text{in ohms})$$

Since every circuit contains resistance, in fact an inductance itself uses wire and, therefore, has resistance, both the reactance and the resistance constitute an impeding force. Please bear in mind that this opposition is equivalent to resistance in a D.C. circuit and by itself has nothing to do with the time lag. The relation between

the inductance and the resistance of the circuit will determine the angle of the lag; the frequency does not enter directly in this case. The total opposition to the current is that of the resistance and the reactance and is expressed as the impedance of the circuit, designated by the symbol Z. Impedance like reactance is expressed in ohms. The formula given is used to compute the impedance.

$$Z = \sqrt{R^2 + X_L^2}$$

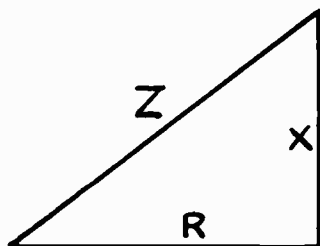

This means that the impedance Z is the hypotenuse (long, slant side) of a right triangle that has the resistance R, and the reactance X, as its two sides; see figure. From these two formulas we see that where inductance is involved, the impedance and reactance increase with the frequency.

In a radio filter circuit, the current that comes from a full wave rectifier tube contains a large 120 cycle component. It is interesting to see what impedance is offered by a 10-henry choke coil having 300 ohm D.C. resistance, to this 120 cycle component. Substituting the values and solving:

$$X_L = 6.28 \times F \times L = 6.28 \times 120 \times 10 = 7,536 \text{ ohms}$$

$$Z = \sqrt{(300)^2 + (7,536)^2} = 7,542 \text{ ohms}$$

The 120 cycle component receives a reactance from the choke of 7,536 ohms as compared to the 300 ohm resistance offered to D.C. The impedance or the combined effect of the choke's reactance and resistance is equal to 7,542 ohms.

CAPACITANCE REACTANCE

If a D.C. voltage is impressed across the plates of a perfect condenser, there will be an initial rush of current which will charge the condenser to the supply voltage. After this, there is no further flow of current if the voltage remains constant. If the plates are short-circuited, current will flow out of the condenser.

The current in a capacitance circuit tends to keep the voltage constant and leads the voltage. This is exactly opposite to the action of an inductance. Therefore, the capacitance reactance is assumed to be opposite to inductive reactance and when both appear in a circuit the following formula is applied to calculate the capacitance reactance. This formula is also used when the capacity exists in a non-inductive circuit.

$$X_c = \frac{1}{6.28 \times f \times C}$$

Here also F is the frequency and C is the capacity in farads. Use the simplified formula

$$X_c = \frac{159,236}{f \times C}$$

when C is expressed in microfarads.

If a circuit has both inductive and capacitance reactances, their effects will be opposite to each other and the larger will predominate. For example, in a 60 cycle circuit there is an inductance of 3 henries and a condenser of 10 mfd. connected in series. Figuring we find the inductance having a reactance of 1130.4 ohms, the capacitance reactance equal to 265.4 ohms. The total reactance is equivalent to $1130.4 - 265.4 = 865$. ohms and the circuit will behave inductively.

The impedance formula for circuits having capacity and resistance is similar to the one we already had where inductance was present instead of the condenser. X_c is simply substituted for X_L

$$Z = \sqrt{R^2 + X_c^2} \quad \text{in ohms}$$

If both inductive and capacitance reactances are present, X the total reactance is the algebraic sum of the two, vis:

$$Z = \sqrt{R^2 + (X_L - X_c)^2}$$

Note: X_L AND X_c are always

taken to be opposite in sign.

The student should design simple series circuits involving resistance, capacity, and inductance and apply these formulas.

FILTERS Filters are electrical circuits that show varied "shut-out" discrepancies to different frequencies present. In other words, filters change their impedance to different frequencies. By utilizing capacity and inductance (also resistance sometimes) in circuit combinations, it is possible to vary the amount of suppression of any group of frequencies. By combining a number of similar sets of filters, much sharper and more exact results may be obtained.

The use of filters in radio receivers and similar equipment is large. By-pass condensers across bias resistances, detector radio frequency chokes, and power supply chokes and condensers are but a few representative examples.

In one manner filters may be divided into four classes, depending upon the functions they are called to perform. Filters may be low pass, high pass, band pass, and band elimination types. The classification is relative to the frequencies passed or attenuated (kept out)

TUNED CIRCUITS A radio frequency air core transformer is used to couple the antenna to the radio set. In a practical input R.F. circuit, the secondary of the transformer is shunted with a variable condenser C. For practical purposes we may assume that the antenna picks up all signals equally well. These signals are transformed to the secondary with a slight voltage step up. On first appearance, the secondary of the "tuning" transformer and the condenser seem to be in a parallel circuit, however, this is not so. The voltage in the tuned circuit is induced in the windings of the secondary coil, and is in series with the winding.

RADIO SERVICING COURSE

REACTANCE AND RESISTANCE*

IN PARALLEL

When a resistance is in parallel with a reactance (either inductive or capacitive), the resultant impedance of the combination is found from the expression

$$Z = \frac{XR}{\sqrt{R^2 + X^2}}$$

Sometimes Z and R are given and X has to be found or Z and X are given and R is the unknown. In that case the equation can be solved for X and we have

$$X = \frac{ZR}{\sqrt{R^2 - Z^2}} \quad R = \frac{ZX}{\sqrt{X^2 - Z^2}}$$

In all three of the above equations X can be either inductive reactance (X=6.28 fL) or it can be capacitive in which case X=1/(6.28 f C) where f is in cycles, L in henries and C in farads.

The table, Figure 3, has been prepared to permit the finding of any one of the three quantities X, R or Z when the other two are given. When X and R are given, divide the larger of the two quantities into the smaller one and thus get a ratio less than 1. Find this ratio in the left column and multiply the number obtained in the second column by R or X whichever is the larger and find Z.

Suppose R equals 1000 ohms and X is 200 ohms, which makes X/R = .20. The table shows us that Z/R is then 0.1961. Multiplying

by R, we have Z = 0.1961 x 1000 = 196.1 ohms.

IN SERIES

The impedance, Z, of a combination resistance, R, and a reactance, X, in series is given by the equation

$$Z = \sqrt{R^2 + X^2}$$

When Z is given and either X or R is the unknown, this equation can be re-written:

$$R = \sqrt{Z^2 - X^2}$$

$$X = \sqrt{Z^2 - R^2}$$

In all these equations all three quantities are expressed in ohms and X can be either capacitive reactance (1/6.28 fC) or inductive reactance (6.28 fL).

The table, Figure 4, gives the value of all three quantities for the case that either X or Z is equal to 1. In other cases, find the ratio R/X or X/R refer to the table and find the corresponding ratio Z/X or Z/R. The table can also be used when Z is given together with one of the other quantities. It was for this reason that the table had to be extended for values of R/X or X/R from .1 to 10 since otherwise it would have been sufficient to include values from 1 upwards or downwards but not both. Example: suppose X = 1.600 ohms and R = 1,000 ohms. Then X/R = 1.6; the table shows Z/R = 1.8868. Then Z equals 1.8868 R or 1886.8 ohms.

REACTANCE AND RESISTANCE VALUES IN PARALLEL

X/R or R/X	Z/R or Z/X	X/R or R/X	Z/R or Z/X	X/R or R/X	Z/R or Z/X
0.10	0.0995	0.49	0.4400	0.88	0.6606
0.11	0.1093	0.50	0.4472	0.89	0.6648
0.12	0.1191	0.51	0.4543	0.90	0.6690
0.13	0.1289	0.52	0.4613	0.91	0.6730
0.14	0.1386	0.53	0.4683	0.92	0.6771
0.15	0.1483	0.54	0.4751	0.93	0.6810
0.16	0.1580	0.55	0.4819	0.94	0.6849
0.17	0.1676	0.56	0.4886	0.95	0.6888
0.18	0.1771	0.57	0.4952	0.96	0.6925
0.19	0.1867	0.58	0.5017	0.97	0.6963
0.20	0.1961	0.59	0.5082	0.98	0.6999
0.21	0.2055	0.60	0.5145	0.99	0.7036
0.22	0.2149	0.61	0.5208	1.00	0.7071
0.23	0.2242	0.62	0.5269	1.10	0.7400
0.24	0.2334	0.63	0.5330	1.20	0.7682
0.25	0.2425	0.64	0.5390	1.30	0.7926
0.26	0.2516	0.65	0.5450	1.40	0.8137
0.27	0.2607	0.66	0.5508	1.50	0.8320
0.28	0.2696	0.67	0.5566	1.60	0.8480
0.29	0.2785	0.68	0.5623	1.70	0.8619
0.30	0.2874	0.69	0.5679	1.80	0.8742
0.31	0.2961	0.70	0.5735	1.90	0.8850
0.32	0.3048	0.71	0.5789	2.00	0.8944
0.33	0.3134	0.72	0.5843	2.20	0.9104
0.34	0.3219	0.73	0.5895	2.40	0.9231
0.35	0.3304	0.74	0.5948	2.60	0.9333
0.36	0.3387	0.75	0.6000	2.80	0.9418
0.37	0.3470	0.76	0.6051	3.00	0.9487
0.38	0.3552	0.77	0.6101	3.20	0.9545
0.39	0.3634	0.78	0.6150	3.40	0.9594
0.40	0.3714	0.79	0.6199	3.60	0.9635
0.41	0.3793	0.80	0.6246	3.80	0.9671
0.42	0.3872	0.81	0.6289	4.00	0.9702
0.43	0.3950	0.82	0.6341	5.00	0.9807
0.44	0.4027	0.83	0.6387	6.00	0.9864
0.45	0.4103	0.84	0.6432	7.00	0.9902
0.46	0.4179	0.85	0.6477	8.00	0.9921
0.47	0.4254	0.86	0.6520	9.00	0.9939
0.48	0.4327	0.87	0.6564	10.00	0.9950


Figure 3

REACTANCE AND RESISTANCE VALUES IN SERIES

X/R or R/X	Z/R or Z/X	X/R or R/X	Z/R or Z/X	X/R or R/X	Z/R or Z/X
0.10	1.0050	0.70	1.2207	4.1	4.2202
0.11	1.0060	0.71	1.2264	4.2	4.3174
0.12	1.0072	0.72	1.2322	4.3	4.4147
0.13	1.0084	0.73	1.2381	4.4	4.5122
0.14	1.0097	0.74	1.2440	4.5	4.6098
0.15	1.0112	0.75	1.2500	4.6	4.7074
0.16	1.0127	0.76	1.2560	4.7	4.8052
0.17	1.0144	0.77	1.2621	4.8	4.9030
0.18	1.0161	0.78	1.2682	4.9	5.0009
0.19	1.0179	0.79	1.2744	5.0	5.0990
0.20	1.0198	0.80	1.2806	5.1	5.1971
0.21	1.0218	0.81	1.2869	5.2	5.2952
0.22	1.0239	0.82	1.2932	5.3	5.3935
0.23	1.0261	0.83	1.2996	5.4	5.4918
0.24	1.0284	0.84	1.3060	5.5	5.5901
0.25	1.0308	0.85	1.3125	5.6	5.6885
0.26	1.0333	0.86	1.3190	5.7	5.7871
0.27	1.0358	0.87	1.3255	5.8	5.8856
0.28	1.0384	0.88	1.3321	5.9	5.9841
0.29	1.0412	0.89	1.3387	6.0	6.0828
0.30	1.0440	0.90	1.3454	6.1	6.1814
0.31	1.0469	0.91	1.3521	6.2	6.2801
0.32	1.0499	0.92	1.3588	6.3	6.3789
0.33	1.0530	0.93	1.3656	6.4	6.4777
0.34	1.0562	0.94	1.3724	6.5	6.5764
0.35	1.0595	0.95	1.3793	6.6	6.6752
0.36	1.0628	0.96	1.3862	6.7	6.7741
0.37	1.0662	0.97	1.3932	6.8	6.8731
0.38	1.0698	0.98	1.4001	6.9	6.9720
0.39	1.0733	0.99	1.4071	7.0	7.0711
0.40	1.0770	1.00	1.4141	7.1	7.1701
0.41	1.0808	1.1	1.4866	7.2	7.2691
0.42	1.0846	1.2	1.5621	7.3	7.3681
0.43	1.0885	1.3	1.6401	7.4	7.4671
0.44	1.0925	1.4	1.7205	7.5	7.5662
0.45	1.0966	1.5	1.8028	7.6	7.6654
0.46	1.1007	1.6	1.8868	7.7	7.7646
0.47	1.1049	1.7	1.9723	7.8	7.8638
0.48	1.1092	1.8	2.0591	7.9	7.9630
0.49	1.1136	1.9	2.1471	8.0	8.0623
0.50	1.1180	2.0	2.2361	8.1	8.1615
0.51	1.1225	2.1	2.3259	8.2	8.2608
0.52	1.1271	2.2	2.4166	8.3	8.3600
0.53	1.1318	2.3	2.5080	8.4	8.4594
0.54	1.1365	2.4	2.6000	8.5	8.5588
0.55	1.1413	2.5	2.6926	8.6	8.6576
0.56	1.1461	2.6	2.7857	8.7	8.7572
0.57	1.1510	2.7	2.8792	8.8	8.8566
0.58	1.1560	2.8	2.9732	8.9	8.9560
0.59	1.1611	2.9	3.0676	9.0	9.0554
0.60	1.1662	3.0	3.1623	9.1	9.1548
0.61	1.1714	3.1	3.2573	9.2	9.2542
0.62	1.1765	3.2	3.3526	9.3	9.3536
0.63	1.1819	3.3	3.4482	9.4	9.4530
0.64	1.1873	3.4	3.5440	9.5	9.5524
0.65	1.1927	3.5	3.6400	9.6	9.6518
0.66	1.1981	3.6	3.7362	9.7	9.7512
0.67	1.2037	3.7	3.8327	9.8	9.8507
0.68	1.2093	3.8	3.9293	9.9	9.9503
0.69	1.2149	3.9	4.0262	10.0	10.0499

Figure 4

REACTANCE AND RESISTANCE IN SERIES



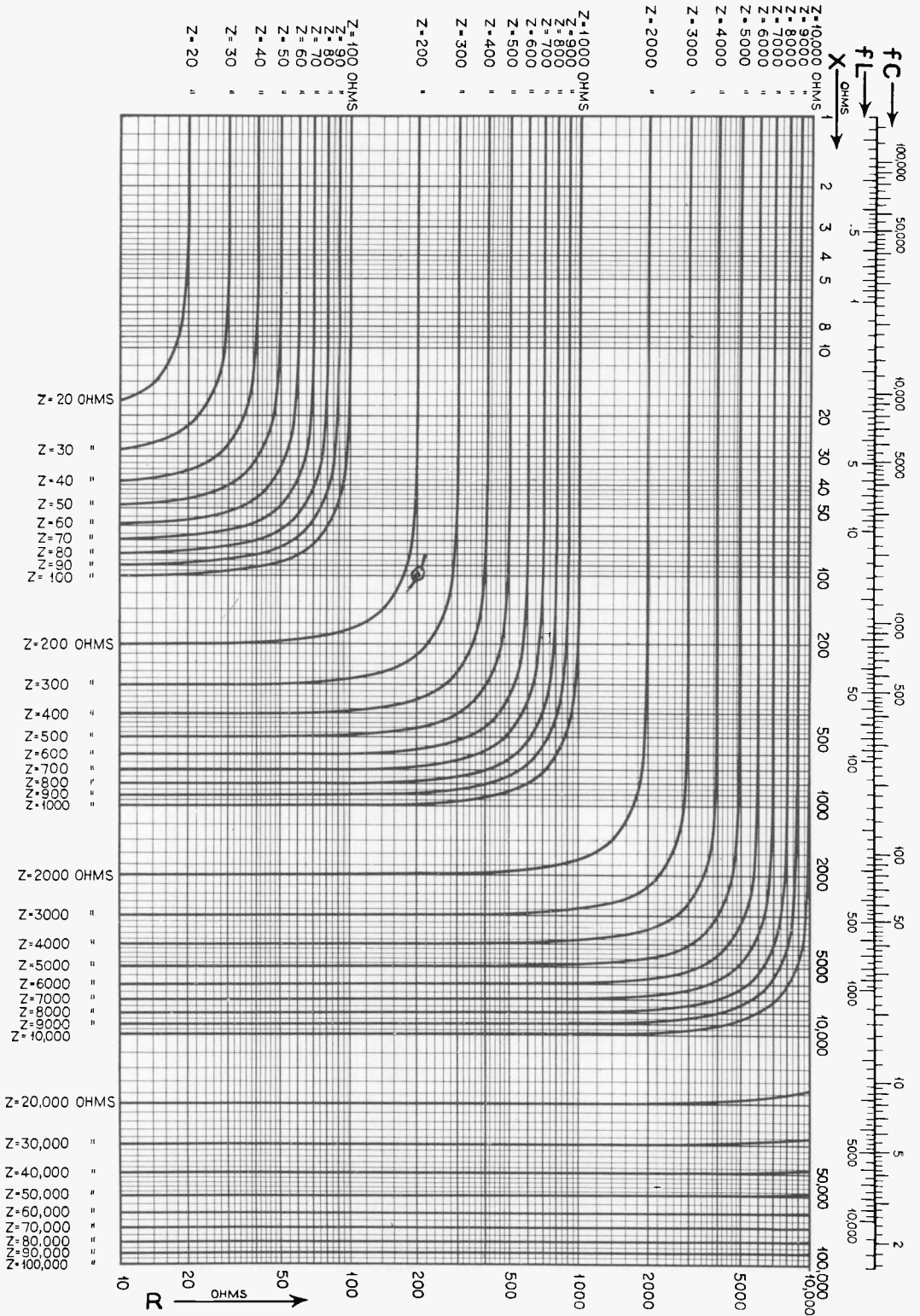


Use this graph to find impedance Z , when resistance R and reactance X , connected in series, are given. Holding the page sideways so that resistance R -scale (10 to 10,000 ohms) is at the right, you will find the reactance X -scale at the top. You will find that fC scale corresponds to X scale provided C is taken in microfarads. For example if the product of frequency f and capacity C in mfd. equals 5000, reactance X is 32 ohms. Check this above. In a similar way fL scale corresponds to the X scale values, but here L is taken in henries. For any given values of X and R , find their junction. The chart has a mark for $X=100$ and $R = 200$ ohms. Notice that this junction is close to the heavy line representing $Z = 200$ ohms, but is somewhat at a distance towards the 300 value. By interpolation you can estimate that $Z = 220$ ohms is about the right value. In this manner other problems involving X and R in series can be solved.

CAPACITY
A, B
MICRO-MICROFARADS

FREQUENCY
A B
KC MC

INDUCTANCE
A B
MICROHENRIES

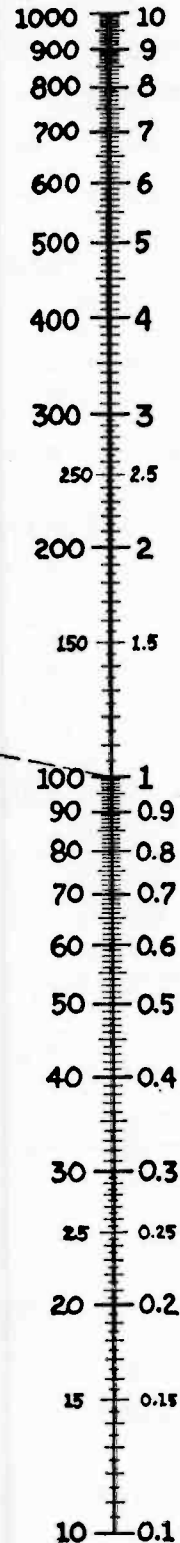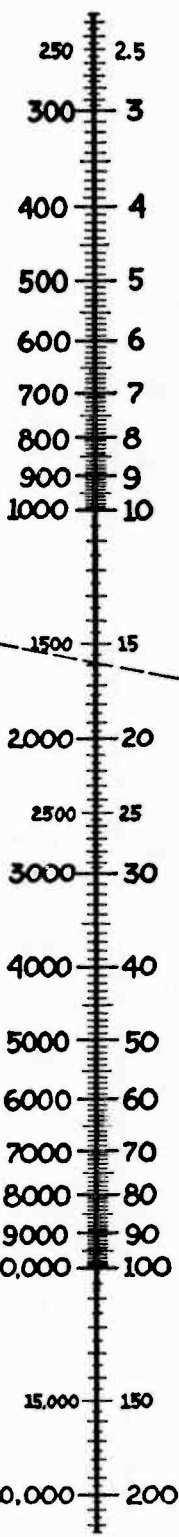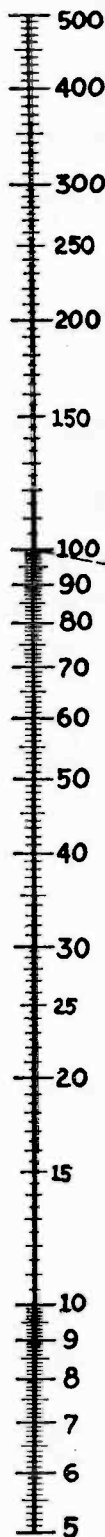

$$f_{kc} = \frac{159000}{\sqrt{C_{\mu fd} \times L_{\mu h}}}$$




*When any two of the quantities F, L, or C are known the third can be found by drawing a straight line.
Example: 100 mmfd. and 100 microhenries tune to 1590 kc. (reading all A scales) or 100 mmfd. and 1 microhenry resonates at 15.9 mc. (reading all B scales).*

HANDY RADIO FORMULAE


Direct Current Relations

VOLTS	=	$I R$	$\frac{W}{I}$	$\sqrt{R W}$
AMPERES	=	$\frac{E}{R}$	$\frac{W}{E}$	$\sqrt{\frac{W}{R}}$
OHMS	=	$\frac{E}{I}$	$\frac{W}{I^2}$	$\frac{E^2}{W}$
WATTS	=	$E I$	$I^2 R$	$\frac{E^2}{R}$


Resistance Relations

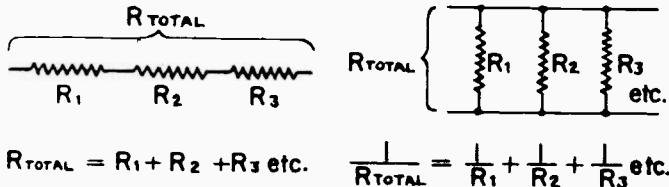


Two Resistances Only

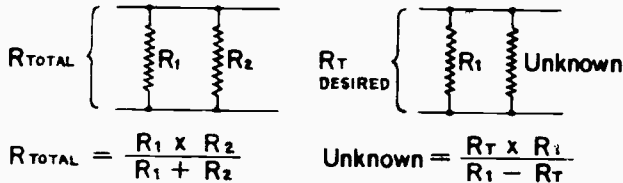


Capacity Relations

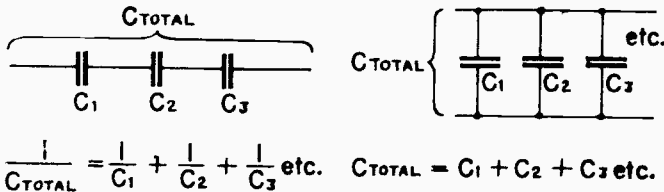



Two Capacities Only

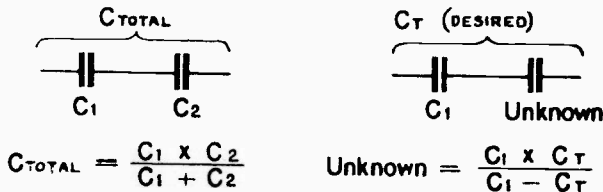

Simple Reactance

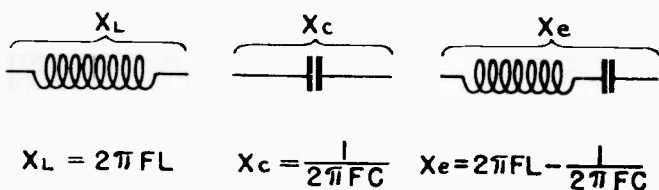


Complex Impedance

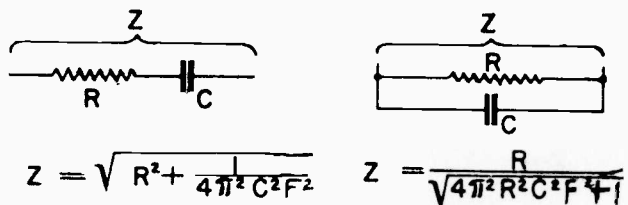
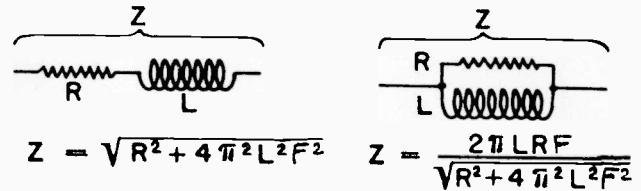


Resonance Formulae

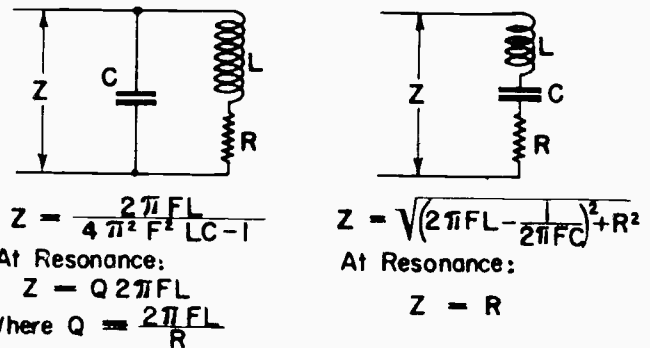$F = \frac{1}{2\pi\sqrt{LC}}$ $L = \frac{1}{4\pi^2 F^2 C}$ $C = \frac{1}{4\pi^2 F^2 L}$
 Where F is in cycles, L is in henries, and C in Farads



Coupling Coefficient

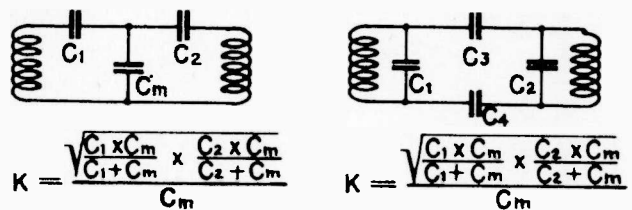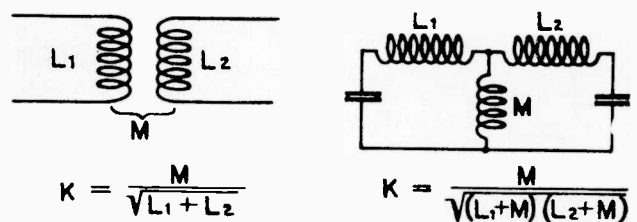

Where $C_m = \frac{C_3 \times C_4}{C_3 + C_4}$

When you have a circuit problem requiring a mathematical solution, refer to this page for an applicable formula to help you secure the correct answer.


REVIEW QUESTIONS

1. How many changes of direction does 60 cycle current have each second?
2. In an inductive circuit, does voltage lead the current?
3. What is the inductive reactance of a 20 henry choke in a 60 cycle A.C. circuit?
4. What is the total impedance if this choke is connected in series with a 1,000 ohm resistor? Work this problem and then check with the chart.
5. What reactance does a 0.1 mfd. condenser offer to 500 cycle current? What happens if a 1.0 mfd. is used instead?
6. In a series circuit, the resistance is 4 ohms, the inductive reactance 11 ohms, and the capacitive reactance 8 ohms. Find the equivalent impedance.
7. What kind of filter would be needed to eliminate the high frequencies in an audio amplifier?
8. Is it true that when a condenser and a choke are connected in series, the resulting impedance is in value smaller than the inductive reactance or the capacitive reactance taken separately? Why?
9. Set up several circuit problems and solve them with the aid of the charts included.
10. Using a coil of 220 microhenries and a condenser that can be varied from 20 to 400 micro-microfarads, what frequency coverage will be secured?
11. Refer to the "Handy Radio Formulae" listing and make up a problem with real values for each of the formulae. Then proceed to solve these problems.
12. Remembering the results obtained in problem 10, try to see the reason why several different coils must be used for all-wave coverage.

LESSON 8

Practical Aspects of Radio Servicing

In being called to repair a defective radio set you should inquire from the owner just what was observed to be wrong. Such information may be of aid to you in trouble shooting. In general, although a radio set is a complex instrument you can assume that it was in good working condition before the particular fault developed and, therefore, only a single fault must be found. This fact greatly simplifies your work since by using a simple test procedure you can isolate a section of the set at fault and then find the particular part or adjustment requiring repair.

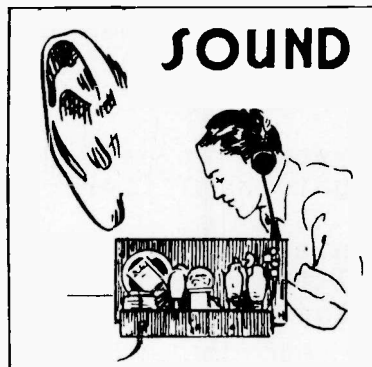

First examine the A. C. cord connection and antenna connection (if used). If found in order, the radio chassis should now be removed from the cabinet. Usually this will require the removal of front control knobs and unscrewing bolts below and in back of the cabinet.


When the set is out of the cabinet, it may be examined for any noticeable fault such as a broken grid cap, leaky condenser, or burnt out coils. You will also be able to see if the radio tubes light. In an AC-DC set one burnt out tube will prevent the filaments of other tubes from lighting. In A. C. sets using transformers, the filaments are connected in parallel and receive their operating current independently.

If your examination does not disclose any obvious fault a quick test may be made by touching with your screw driver the control grids of the various tubes. A click should be heard each time this contact is made and this click reproduced by the loudspeaker should become louder as you move from the grid of the stage next to the speaker to stages closer to the antenna. If along your testing no click is heard at a particular stage, that stage is at fault.


The test to determine if plate voltage is present may be made by taking an electrolytic condenser and making temporary contact with + lead to a point where positive plate voltage may be expected (cathode of rectifier tube, plate or screen grid of output power tube) and the negative connection to a ground or a common chassis. After making this contact, the two wires of the condenser are brought almost in contact and a spark will indicate that a voltage existed and charged the condenser. Lack of spark suggests lack of voltage.

The main reason for introducing some of these simple tests at this early stage of your study is to convince you of the ease and simplicity of finding radio faults. Once the fault is found the actual repair is usually mechanical in nature and presents no problems in itself. You should have some understanding how a radio signal is produced. At the radio station equipment is employed to produce a radio frequency signal and this in turn is modulated (varied in intensity for AM stations) by the audio frequencies resulting from the amplification of music or voice picked up by a microphone. The carrier frequency when modulated occupies a channel twice the width of the audio frequency. Since the present day broadcasting channels are 10 KC. (kilocycles) wide or 5 KC. on each side of the carrier, the program transmitted may have audio frequency up to 5,000 cycles per second.


At the receiver the antenna (which may also be a coil or loop in the set itself) is excited by all frequencies of all stations. However, only near-by stations have a pronounced effect and the combination of coils and condensers used select the desired station and discriminate against the others. The selectivity is accompanied with amplification in the R. F. and I. F. stages that precede the detector.

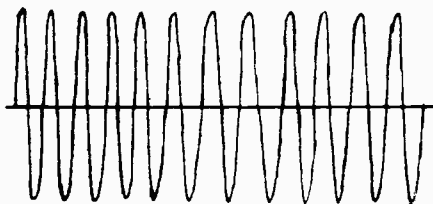

Carrier Wave

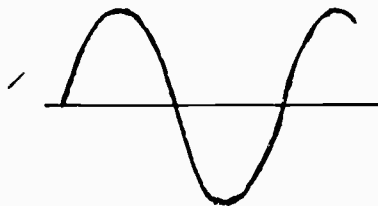


Audio Frequency

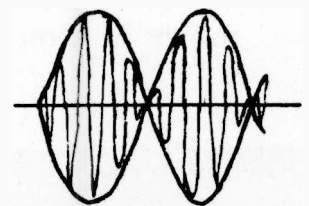

Modulated Wave

The detector removes from the modulated R. F. (or I. F.) the audio signal which in turn is further amplified in the audio stages. The audio output stage not only amplifies but also supplies power to the loudspeaker while it is excited by voltage variations. The loudspeaker, of course, is a device for changing electrical energy of audio frequencies to actual sound.

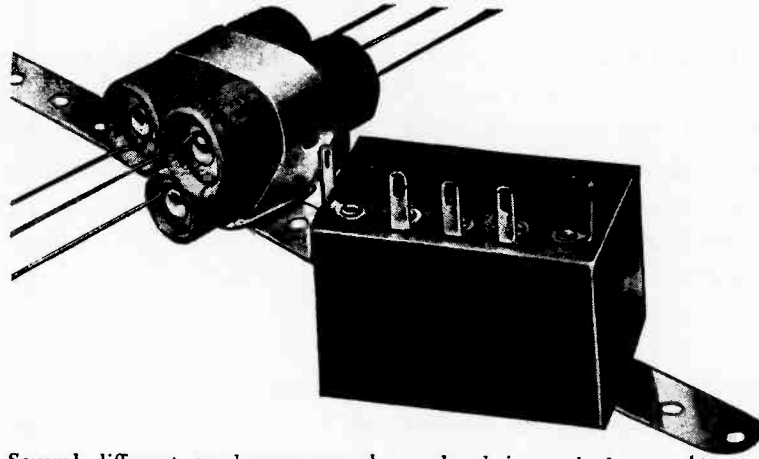Since the majority of repairs will require the removal of a defective part and the replacement of this part with one in good condition, you will




Several different condensers may be enclosed in a single container. In making a repair, only the section at fault need be replaced.

have to understand how radio parts are mechanically mounted in place. We will talk about such parts as require replacement from time to time. Items such as tube sockets, tuning condensers, etc. seldom need replacement.

Radio tubes plug into sockets and are removed with a pull upwards while a slight rocking motion is introduced. A guide pin or irregular placing of holes prevents insertion of tubes incorrectly. Some types of electrolytic condensers in more modern sets twist into position. Fuses (more commonly found on TV sets) are mounted in several different ways but usually are removed by snapping them out of the terminals.

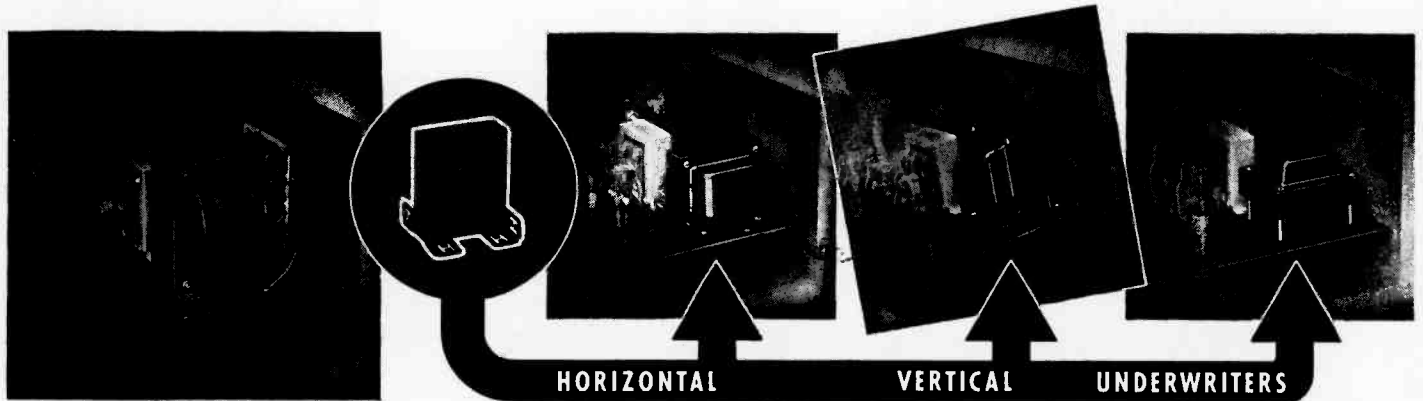Power transformers are bolted or riveted originally. Rivets in this instance or when found holding other parts that need removal must be drilled out. The replacement transformer need not be identical physically with the unit originally used in the set but should provide correct voltages. Some replacement transformers are called universal and are designed to mount in almost any position.




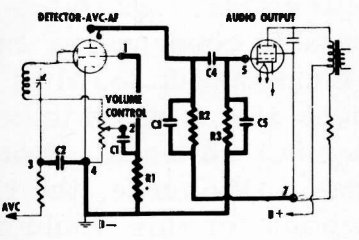
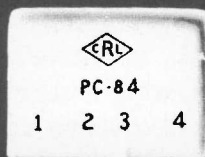
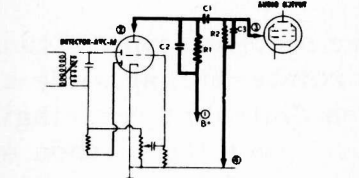
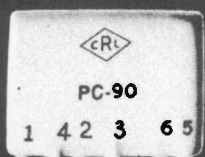
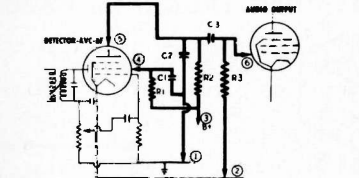
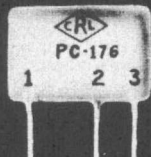
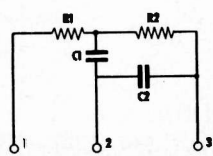
With the power transformer burned out, the set originally looked like this.

With the new Universal unit, servicing is simple—the finished product is neat. Three possible methods of mounting the unit without drilling holes, are shown. Half shell mounting is just as easy.

Parts that are mounted on pigtails (wire leads) are simply cut off and a replacement condenser or resistor mounted in their place in the same fashion. Printed circuit plates which contain several components may be replaced with suitable similar unit or just a defective component may be replaced in the circuit provided both the leads to this component are used for external wiring of the plate.

Unshielded coils are usually held in place with small brackets that are bolted to the chassis. The replacements are mounted in the same manner. I. F. transformers and other coils that are shielded should be replaced with units of identical electrical characteristics and mounted in cans of about the same physical size.

To simplify assembly at the factory and to reduce cost several resistors and condensers are combined to form a "plate." Centralab makes these units under the trade name "Couplate." A number of such units that are used in radio receivers are illustrated together with their circuits and values of parts employed.



 <p>PC-150 1 2 3 4 5 6 7</p>		<p> $R_1 = 6.8 \text{ Meg}$ $R_2 = 470\text{K}$ $R_3 = 470\text{K}$ $C_1 = 2000 \text{ mmf.}$ $C_2 = 220 \text{ mmf.}$ $C_3 + C_4 = 250 \text{ mmf.}$ $C_4 = 5000 \text{ mmf.}$ </p> <p>AUDET OUTPUT STAGE</p>
 <p>PC-84 1 2 3 4</p>		<p> $R_1 = 500\text{K}$ $R_2 = 500\text{K}$ $C_1 = .01 \text{ mfd.}$ $C_2 + C_3 = 500 \text{ mmf.}$ </p> <p>STANDARD COUPLATE</p>
 <p>PC-90 1 4 2 3 6 5</p>		<p> $R_1 = 4.7 \text{ Meg}$ $R_2 = 1 \text{ Meg}$ $R_3 = 2.2 \text{ Meg}$ $C_1 = 500 \text{ mmf.}$ $C_2 = 50 \text{ mmf.}$ $C_3 = 2000 \text{ mmf.}$ </p> <p>PENTODE</p>
 <p>PC-176 1 2 3</p>		<p> $R_1 = 82\text{K}$ $R_2 = 39\text{K}$ $C_1 = .001 \text{ mfd.}$ $C_2 = .002 \text{ mfd.}$ </p> <p>SPECIAL</p>

Tuning is needed in order to select the wanted station from the signals of all others. As you know from previous lessons this is done with a coil-condenser combination. In most radio sets the coils for any one band are fixed and the condensers are varied (capacity is changed). The inductance of the coil may be altered to permit tuning in some sets. In some push-button tuning sets, a number of semi-fixed condensers are used and are selected one at a time by means of a switch.

A gang tuning condenser is used for tuning in many modern sets. Such a unit may have two or three gangs turning on a common shaft (electrically and mechanically common), each such gang tuning a different coil. With proper adjustment (alignment), these stages will produce tuning selectivity required. In superhet sets, one such rotating gang may be somewhat smaller and is called cut-section. This section is used with the oscillator coil to give a required higher frequency to mix with the signal frequency to produce a new signal for the I.F. stages.

The rotors of a gang condenser are connected to the frame and are grounded to the chassis through the mounting bolts. The stationary plates are insulated from the frame. The terminal lugs to the stator plates are on one side or on both. Small adjustable condensers, called trimmers, may be placed on one side and are connected in parallel with the corresponding tuning gang. These trimmers are adjusted to compensate for differences in capacity of gangs and associated leads. Slotted plates permit slight bending for alignment purposes. Of course, the rotary plates must not touch stationary plates at any point for this would produce a short circuit and stop reception.

Quite often the tuning condenser or other type of tuning unit is driven with a dial cord. The pointer may rotate or may slide along a long ruler-like dial. Service data usually gives dial-cord restringing instructions for more complex applications. In most cases the method used can be figured out from the examination of the remains of the old cord or from a study of the dial, pointer, and pulleys. Dial cord should be used for replacements.

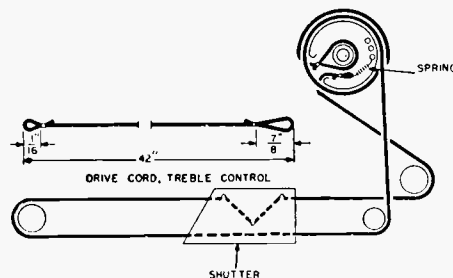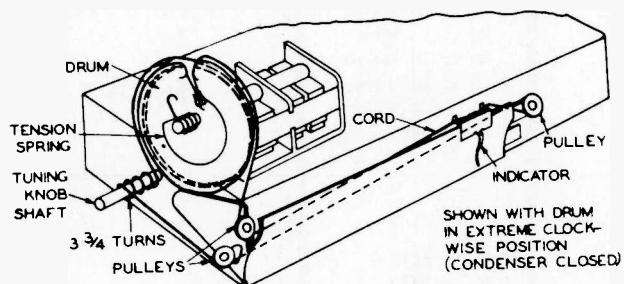

Two typical dial-cord restringing diagrams are shown above. Before putting on a new cord, see if all rotating parts turn freely. If necessary, use light oil in very small amount. You will find that a piece of tape can be of great help in holding the cord in place while you are working at another part of the dial-cord drive system.

Practically all modern auto sets provide pushbutton tuning and a great many pre-War home sets also included pushbutton tuning of various types. In the older home sets one type of pushbutton control connected trimmer condensers across coils. These trimmers were adjusted to tune specific local stations, and in this way each button automatically tuned a different station. In majority of sets buttons rotate the tuning condenser to the exact position for a particular station. This is done mechanically with a separate cam position for each station, the buttons being connected to adjustable push-rods. In other types of mechanical pushbutton tuning, gear action is combined with a rocker bar to move the tuning condenser to a pre-selected position of each wanted station.

In pushbutton tuning sets using trimmers for tuning, each set of trimmers is adjusted for one local station. The trimmers with most capacity (most plates) are used for low frequency stations, while those with least capacity are used for higher frequency stations of the broadcast band. The I. F. transformers are aligned in the usual manner and this is explained in a later lesson. Then the trimmers are adjusted for maximum signal for the corresponding station for which they are used.


On page 54 important practical facts on replacing parts and carrying out repairs in printed circuit chassis are given. This material is reprinted through the courtesy of Emerson Radio and Phonograph Corp.

In conventionally wired circuits it may be important to properly position wires moved or replaced in making a repair. In general, it is a good rule to make all connections as short as possible and to place wires close to the metal of the chassis. Do not run parallel wires carrying the actual signal, such as leads connecting to grid and plate terminals of tubes.


REVIEW QUESTIONS

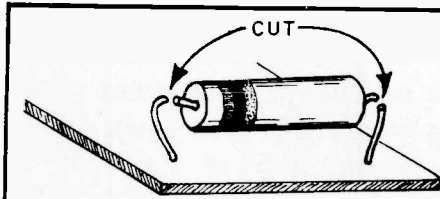1. What can be wrong with a radio set that can be repaired without removing the set from the cabinet?
2. Can a voltmeter be used to determine if plate voltage is present? Where would you make the connections for this test?
3. Examine the chassis of a radio you have at home. List at least three different methods used for mounting some of the parts.
4. Examine the printed circuit at the bottom of page 51. Note that if C2 condenser becomes open a repair can be made by wiring a .002 mfd. capacitor across terminals 2 and 3. Can a repair be made without replacing the entire plate if any one of the other components opens?


Service Hints for Replacing Parts on Printed Circuit Chassis



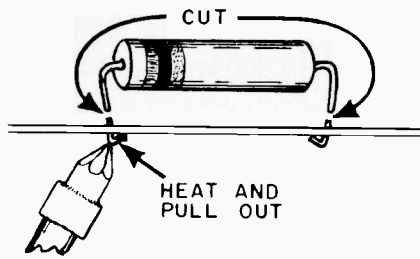Cut resistor or capacitor leads as close to the component as possible, then connect the replacement part to the remaining section of the original leads and carefully solder.



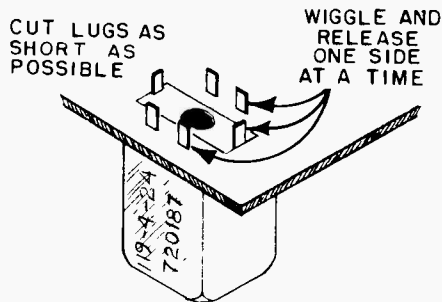
Cut resistor or capacitor leads as close to the chassis as possible. Heat connections just long enough to melt solder and remove leads from bottom one at a time. Clean area around the mounting holes and insert leads from replacement part through holes provided. Clip off excess lead, leaving a small piece to bend over and solder.



Cut transformer lugs (including spring clips) as close to chassis as possible. Heat connections (on one side) long enough for solder to melt, then wiggle loose first one side and then the other. Clean area around mounting holes and insert replacement part through same holes. Carefully resolder connections.


NOTE: The position of the part number with respect to the transformer lug numbers are fixed. When putting in a new transformer make sure the position of the part number with respect to the chassis is the same as the original.

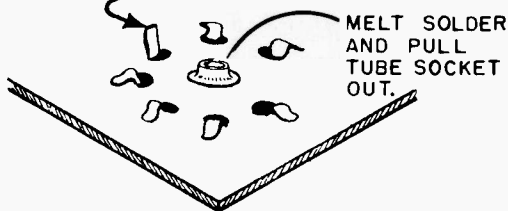HEAT, REMOVE SOLDER AND STRAIGHTEN ALL LUGS.




Melt and brush excess solder from socket pins and straighten out bent pins (one at a time). Remove solder from center ground lug of socket and remove socket (it may be necessary to reheat some of the lugs). Clean the area around mounting holes and insert new socket (with tube in it) in same holes. Bend socket lugs over and then carefully solder.

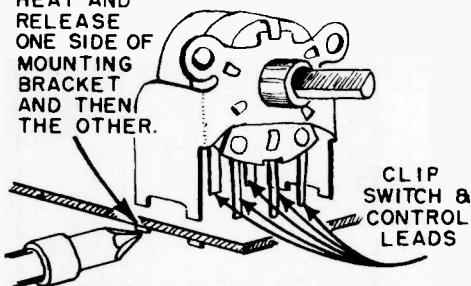HEAT AND RELEASE ONE SIDE OF MOUNTING BRACKET AND THEN THE OTHER.



Cut the volume control and a.c. switch leads close to top of chassis. Heat these clipped leads from under the chassis and pull out with long nose pliers. Melt solder around mounting bracket lugs and straighten out these lugs if bent. Clip these lugs off as close to chassis as possible. Heat and remove one side of mounting bracket and then the other. Clean area around mounting holes and insert new part, bend lugs over slightly and carefully solder all connections.

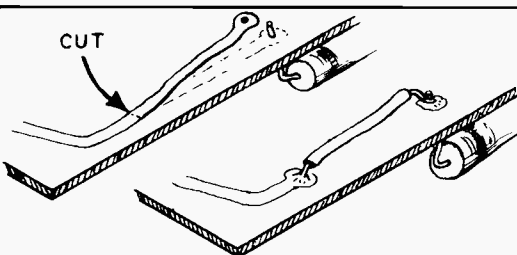



Cut off the section of the printed wiring strip that has lifted from the chassis and replace this section with a short piece of regular insulated wire. Bare wire may be used to replace short sections.

LESSON 9

RADIO TUBES

The basis of all vacuum tubes operation, be they rectifiers, or multi-purpose tubes, in glass or metal envelopes, is electron emission. Electrons are emitted from an electrically heated filament or from a covering placed over this filament and insulated from it. This later type of emission is called indirect. The element emitting the electrons is known as the cathode. Some substances are far better emitters than others. Coating a poor emitter with an oxide of certain metals may raise the emission thousand times. The emission also increases with the temperature.

In 1883, Thomas Edison discovered that when an additional electrode was placed inside an incandescent lamp and this electrode connected to a positive potential with respect to the filament, a current passed through the circuit. This is actually a simple vacuum tube of the diode type. It contains but two elements, the cathode to emit and the plate (anode) to receive the electrons. Under the influence of a positive potential applied to the plate, electrons will flow from the cathode to the positively charged plate. An increase in the plate potential will increase the plate current. The complete action is easy to analyze.

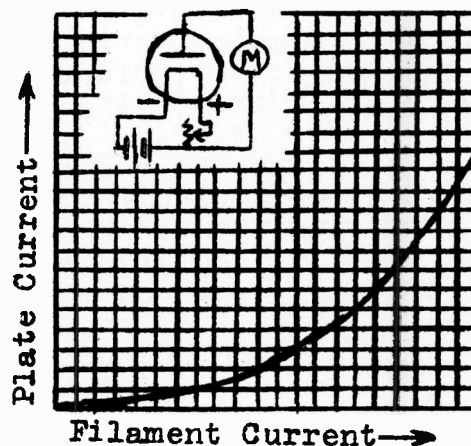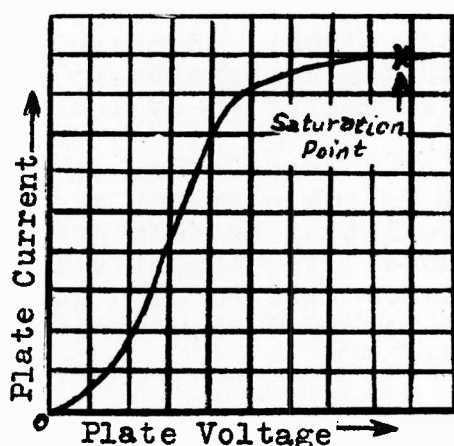

From a heated cathode many electrons venture out, forming a cloud around it. If a negative potential is applied to the plate, the electrons around the cathode will be repelled back into the cathode and no current will pass between these two elements. If, however, the plate becomes positive with respect to the cathode, the electrons around the cathode will be attracted to the plate, since unlike charges attract, and current will pass. In a rectifier an alternating current is applied, during the positive cycle current will flow, but not during the negative. In this manner the alternating current will be rectified into pulsating direct current.

Of the electrons leaving the cathode, not all, of course, reach the plate. Many return to the cathode while others remain for short periods of time between the cathode and the plate forming a space charge.

Since this charge consists of electrons, it is electrically negative and has a repelling force exerted upon other electrons and thereby impedes the passage of current between cathode and plate. By increasing the plate voltage, more electrons will be attracted and the tendency to form a space charge will be reduced.

Once the plate voltage reaches a certain maximum when all the electrons leaving the cathode are attracted to the plate, a further increase of the plate voltage will have no effect on the plate current. This maximum current is known as the saturation current.

Tubes having a third electrode for control purposes are known as triodes. This control electrode is usually called the grid because it is made of fine wire in a form of a mesh. The purpose of the grid is to control plate current. With a negative voltage on the grid, the grid exerts a force on electrons in the space between cathode and grid. This force drives the electrons back to the cathode. In this way, the negatively charged grid opposes the flow of electrons to the plate. When the voltage on the grid is made more negative, the grid exerts a stronger repelling force on the electrons and the plate current is decreased. When the grid voltage is made less negative, there is less repelling force exerted by the grid and the plate current increases. When the voltage on the grid is varied in accordance with a signal, the plate current also varies with the signal. Because a small voltage applied to the grid can control a comparatively large amount of plate current, the signal is amplified by the tube.

The grid, plate, and cathode of a triode form an electrostatic system, each electrode acting as one plate of a small condenser. The capacitances are those existing between grid and plate, plate and cathode, and grid and cathode. The capacitance between grid and plate is of greatest importance and, in high gain radio-frequency circuits, this capacitance may produce undesired coupling between the input and output circuits.

A much smaller change in the grid voltage will produce the same change in the plate current as a much larger plate voltage change. The ratio of the small change in the plate voltage (E_p) to the smaller change in the grid voltage (E_g) that will vary the plate current by an equal small amount is called the amplification factor, or μ (mu). Mathematically:

$$\mu = \frac{dE_p}{dE_g} \quad \text{where } d \text{ means the differential, a very small change.}$$

For example, a type 56 triode tube operating in a conventional circuit with

$$E_g = -13.5 \text{ volts, } E_p = 250 \text{ volts, } I_p = 5 \text{ milliamperes}$$


will have one milliampere less of plate current (I_p) by either a change of 0.87 volts in E_g , or a change in E_p of approximately 12 volts. The ratio of the two will give about 13.8 as the μ of this particular tube.

The plate resistance (r_p) of a tube is the resistance to the alternating current of a path between the plate and the cathode. It is the ratio of a small change in plate voltage (E_p) to the corresponding change in the plate current (I_p). This is:


$$r_p = \frac{dE_p}{dI_p} \quad \text{when } E_g \text{ is constant}$$

The grid may be made to assume either positive or negative values with respect to the cathode. When the grid is negative with respect to the cathode, the grid will not attract electrons and no current will flow between it and the cathode. This means that the grid will not take power from the circuit connected to it. In this manner, minute power can be used to control comparatively large plate power. Because of this and other reasons, it is desirable to keep the grid at some negative potential at all times. The negative potential applied to the grid must, therefore, be at all times larger than the greatest positive swing of the grid input voltage.


This constant negative potential is called the bias and may be obtained from batteries, but usually a section of the voltage divider is tapped off for this purpose or a resistor of a correct value is placed in the cathode return circuit and causes a drop of potential because of the passage of the direct plate current. A by-pass condenser offering very low impedance to the alternating current component of the plate current is employed to act as an easy path for all currents except the direct current component.

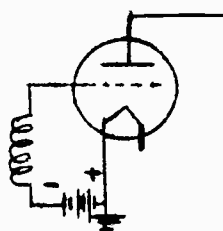

Battery Bias

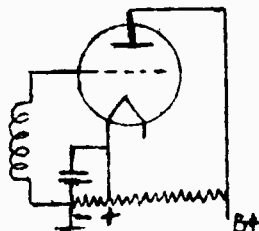

Voltage Divider Bias

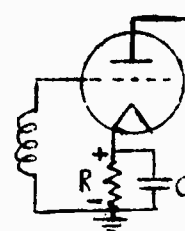

Self Bias

The detrimental effect of the grid-plate capacitance is reduced greatly by the introduction of a fourth electrode, called the screen grid, placed between the grid and the plate. This screen in ordinary application is connected to a positive potential somewhat lower than the plate potential. Since the screen voltage largely determines the electron flow, large variations in the plate voltage will have but little effect on the plate current.

Electrons striking the plate dislodge other electrons from it. This indirect emission of electrons from the plate is called secondary emission in contrast to primary emission from the heated cathode. In the diode or triode, this action does not cause any difficulties because of the absence of any positive bodies in the vicinity of the plate. In the screen grid type tetrode, however, the screen is positive and close to the plate and does attract electrons emitted by the secondary emission action. This effect lowers the plate current and limits the permissible plate swing.


This limitation in turn may be removed by a further introduction of another electrode, known as the suppressor, between the screen and the plate. The suppressor may be connected directly to the cathode or, as in some tubes for special applications, have an external prong. Since such tubes have five elements they are called pentodes.

BEAM POWER TUBES

A beam power tube makes use of a different method for suppressing secondary emission. In this tube there are four electrodes, a cathode, control grid, screen grid, and plate so spaced that secondary emission from the plate is suppressed without an actual suppressor. Because of the way the electrodes are spaced, electrons traveling to the plate slow down when the plate voltage is low, almost to zero velocity in a certain region between the screen and plate. In this region the electrons form a stationary cloud, a space charge, repelling secondary electrons emitted from the plate and cause them to return to the plate. In this manner, secondary emission is suppressed. Another feature of the beam power tube is the low current drawn by the screen, as well as economical operation.

BIAS DETECTOR

After about 1929, detectors were operated at the lower bend of their characteristic curves by using sufficient bias. Detection took place because a positive swing in the grid voltage caused a much larger increase in plate current than a corresponding decrease when an equal negative grid voltage was applied. Notice the rectification-detection that takes place in the illustrated example of a simple sine wave.

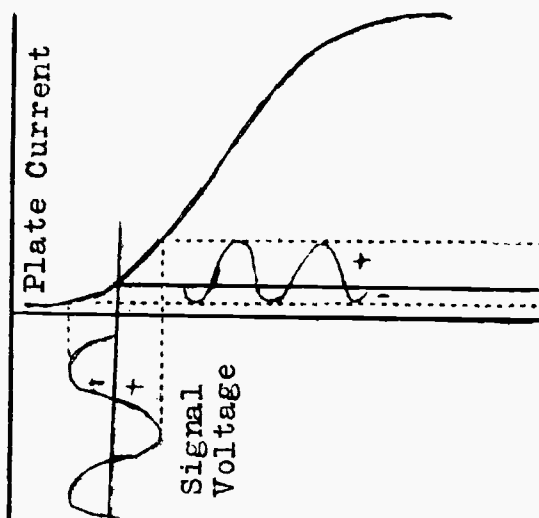

The bias may be obtained in any of the ways described previously; i.e., C batteries, voltage divider, or self biased.

GRID LEAK DETECTOR Working on a different principle, grid leak detectors were extensively used some time ago. However, these detectors have many disadvantages when considered for use in modern radio receivers and find but little present day applications.

Plate Characteristics, 46 Class A

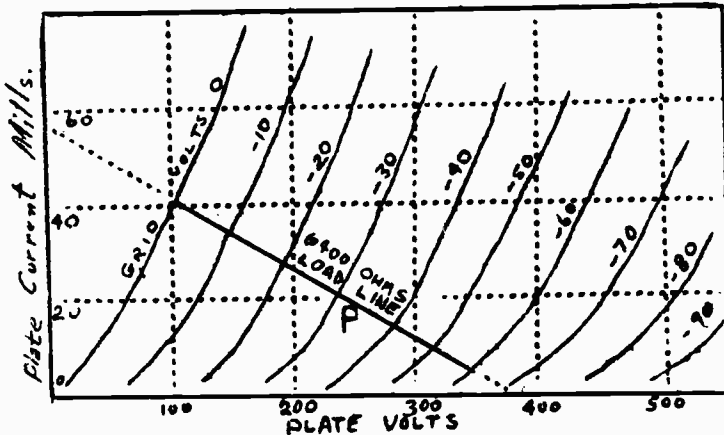


Plate characteristic curves are useful in determining the best operating conditions of a tube. The plate current is plotted as the ordinate, and the plate voltage as the abscissa. Keeping the grid potential fixed at some value, the variations in plate voltage are plotted against the corresponding variations of plate current. By repeating this process for a number of

different grid potentials, a group of similar curves are obtained, as illustrated for type 46 tube in class A operation. It will be noted that an increase in negative grid potential shifts the curve to the right.

To plot the load line having been given $E_g = -31$ volts $E_p = 250$ volts, $I_p = 22$ milliamperes, Load resistance = 6,400. First, find where the given E_p and I_p intersect, mark this point P. Place a straight edge on point P; rotate it until the value of plate voltage intersected divided by the plate current also intersected, will equal the given load resistance, 6,400 ohms in this case. The edge will cut 58 milliamperes and 371 volts at the same time. Since $371/.058 = 6,400$, this is the correct line.

If the grid swing may be considered to be between zero and the value twice the fixed bias, then the formulas below may be applied in calculating the amount of second harmonics and power output. Second harmonics are frequencies twice the signal frequency generated by the tube and usually not wanted.

At any value of grid potential, the plate current value is directly to the left of the load line and that grid potential intersection; the plate voltage is directly below this intersection. For example in the previous graph, when $E_g = -10$, the plate voltage is 150, and the plate current is about 34 milliamp.

$$\text{POWER OUTPUT} = \frac{(I_{\max} - I_{\min}) \times (E_{\max} - E_{\min})}{8}$$

$$\% \text{ 2nd HARMONICS} = 50 \times \frac{(I_{\max} + I_{\min} - 2I_{\text{average}})}{I_{\max} - I_{\min}}$$

The functions of vacuum tubes are varied. In a receiving radio set, vacuum tubes are used primarily as voltage and power amplifiers, and to a limited extent as detectors and oscillators. The current change in the plate circuit of a vacuum tube may produce a voltage variation across a resistance, a high impedance, or the impedance of the primary of an audio transformer or a R.F. transformer. If the plate current is passed through a high resistance connected between the plate and the positive side of the plate voltage supply, voltage variations will be produced in proportion to the changes in the plate current. The voltage drop will distribute itself in proportion to the resistance of the tube (r) and the load resistance (R). The voltage amplification will be a fraction of the amplification factor μ , expressed by the relation:

$$\text{Voltage Amplification} = \frac{\mu R}{r + R}$$

In case the load is an impedance Z , it may be substituted for R in the above formula.

The types 6E5, 6G5, and other tuning indicator tubes are finding extensive use in modern sets, and may be added to any radio having automatic volume control. The tube's filament is simply wired in series with other tubes in AC-DC type sets, or connected to the power transformer filament winding. Usually the transformer can easily handle an additional tube. In sets using 2.5 volt tubes, type 2E5 must be employed.

The adapter sockets supplied (as illustrated) have an internal screen resistor and are simply connected to the filament supply, B-plus point, chassis or negative return, and a point of the correct A.V.C. voltage. Complete instructions are always supplied with the unit you may purchase.



There are a great many different type of tubes used in radio sets. All these types are listed in the Sylvania tube chart beginning on page 65. A great many types are identical except for the fact that one series is for 2.5 volt operation, and another is for 6.3 volt use. Note, for example, the correspondence between types 58 and 78, or 55 and 6V7G. Also in the same series there may be many types almost alike, see 6C6, 77, and 6J7. There are tubes to serve in A.C. sets, in AC-DC sets, in battery sets, in auto sets, and for many special applications.

All the metal tubes have equivalent glass types. For example, 6K7 has a glass equivalent 6K7G. The G-type tubes may be used for

metal or vice versa, provided space permits and the glass tubes substituted are provided with shields in certain cases. There are also many G and GT type tubes not having metal equivalents, see 6K6GT, or 25A7GT.

Now you have already noticed that the first column of the chart gives type numbers. The next column tells style of bulb and class. Is the tube a triode, a pentode, or a dual type? Next is the base data. The code letters refer to base connections applicable and these are shown at the bottom of each double page. Look up type 6A8 for practice. You will note that it is a heptode (6 elements). Base connections given under 8A-1-0. You find diagram 8A and note that this tube uses a grid cap and an octal socket. The figure -1 tell you that the external shield (metal envelope) is connected to lug #1 of the socket. The next figure -0 tells you that internal shielding is not used with an outside terminal.

The filament current and voltage for each type are given in next listing. Here also is stated whether the emitter is of the cathode or filament type. The capacitances stated in the next column are average between grid-plate, input, and output. In the column marked "Use" the usual application of each type of tube is given. The average operating conditions given in other columns will permit you to check operating conditions in sets or even to design actual circuits.

In checking a stage of a radio using any one particular tube, you can refer to these characteristics. The corresponding values of voltage and current should be found within wide limits. For example, 6BA6 is used as an I.F. tube in an A.C. set with about 250 volt plate supply. Plate and screen grid current should be within ten or twenty percent of stated values. Such information can be used to find faults.




For practice, look up the information for all tubes in a few radio sets. See if the tubes are used for purposes recommended and if correct bases are used. If you have a multimeter use it to measure voltage and current of each type and compare to data given in chart.

On page 96 you will find technical information on crystal diodes. These units work in the manner of old style crystal detectors, passing current only in one direction. Crystal diodes are used in some radios, but find their greatest application in television circuits. Do not bring your soldering iron too close to these units. If you must unsolder a lead from a crystal diode, do so quickly with a small iron.

Crystal diodes have a life much longer than vacuum tubes. To test, remove one lead from circuit. Measure resistance with ohmmeter both directions (reverse leads). The reading one way should be one hundred or so times as great as the other. For 1N34 diode, your reading may be 1,000 and 200,000 ohms.

The basic type A transistor consists of a conventional crystal diode modified with an additional (second) cat-whisker contact. The two contacts are spaced close together at the point of contact with the semiconductor. Please examine the illustration of an early type A transistor, as shown below. The small metal tube is about $\frac{3}{16}$ inch in diameter and $\frac{3}{4}$ inch long; about the size of a half-watt resistor. The illustrations and much of the material on transistors in this lesson are reproduced courtesy of the Aerovox Research Worker published by Aerovox Corporation.

The basic electrical circuit of a simple transistor is shown below. The input electrode called "emitter" is maintained at a small positive potential with respect to the germanium block. The impedance in this direction is small and the small positive "bias" voltage under a volt causes an appreciable "forward" current to flow in the emitter circuit. Also, because of this low impedance to forward currents, a small increment in emitter voltage caused by a change in the impressed signal will result in a large increase in electron current flowing from the semiconductor to the cat-whisker. The static voltage-current characteristic of the emitter circuit, when considered alone, is similar to that of the typical germanium point-contact rectifier, and this is shown below at right.

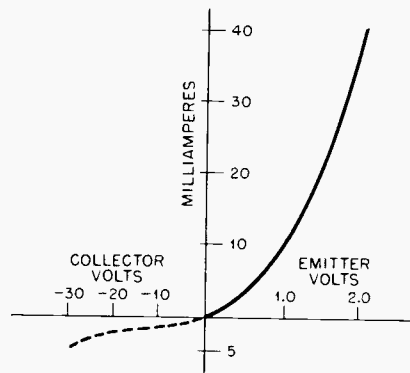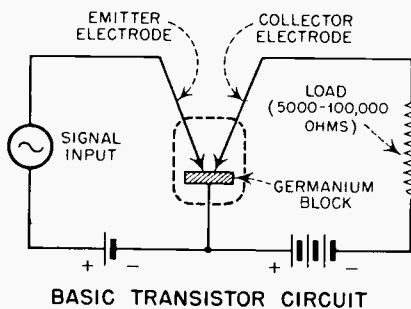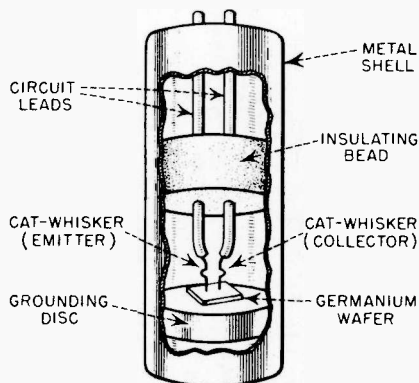


On the other hand, the "collector" or output contact of a transistor is biased negatively with respect to the germanium. At this polarity the impedance to current flow is relatively high (exceeding 10,000 ohms), so that 30 volts may be applied to the collector before appreciable "back" current flows in the semiconductor. The dotted line in the graph above represents the static characteristic of the collector circuit in the absence of the emitter.

The close proximity of the two cat-whiskers with their respective operating voltages modifies these characteristics considerably. It is the ability of the transistor to transfer an emitter voltage change to the collector circuit in the form of a resistance change that gives this device its name and comes from the words: transfer resistor. This property results in effective power gain of 100 times being possible.

Current in a semiconductor is carried in one of two possible ways. Semiconductors that have free electrons are of the n-type, while those that lack the normal amount of electrons (possess positive holes) are of the p-type. Usually the type of impurity added determines the conducting qualities.

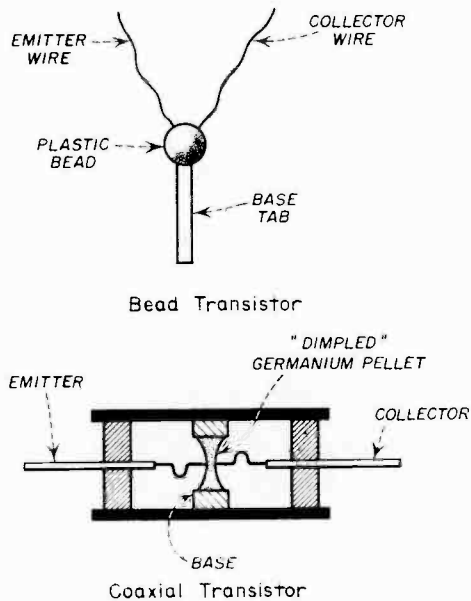Similar to the point contact type A transistor is the bead type which is essentially a miniaturized version of this type. Another form is the coaxial configuration. Here the two cat whiskers make contact with opposite sides of the semiconducting germanium made only .004 inch thick by concave grinding on both sides. See figures below.




TRANSISTOR CIRCUIT	NEAREST V.T. EQUIVALENT
<p>(a) GROUNDED BASE</p>	<p>GROUNDED GRID</p>
<p>(b) GROUNDED EMITTER</p>	<p>GROUNDED CATHODE</p>

By employing tubes that draw the same value of current (but not necessarily of the same filament voltage), it is possible to wire such tubes in series. This is a practice in AC-DC sets and eliminates the need for a power transformer. If the voltage rating of the tubes wired in series do not add up to 110 volts (line voltage), a resistor of some sort must be wired in series to produce this additional voltage drop.

Usually resistor tubes or line cords are used to produce additional voltage drop in AC-DC sets. The four or five tubes used required, as for example, 69 volts, and the remaining 46 volts of the 115 volt supply was lost in the ballast tube. At times several such tubes were used in series. In modern sets, using 12 or 14 volt series tubes requiring .15 amperes and designed to operate at fairly high voltages, all the available line voltage is used up in the tube filaments.

The serviceman does need to replace resistor tubes in older sets. Sometimes non-standard ballast tubes are used, and the actual wiring has to be altered. In almost every case the resistor in the tube is tapped for use with a pilot light of smaller current drain.

WIRE-WOUND TUBE TYPE RESISTORS

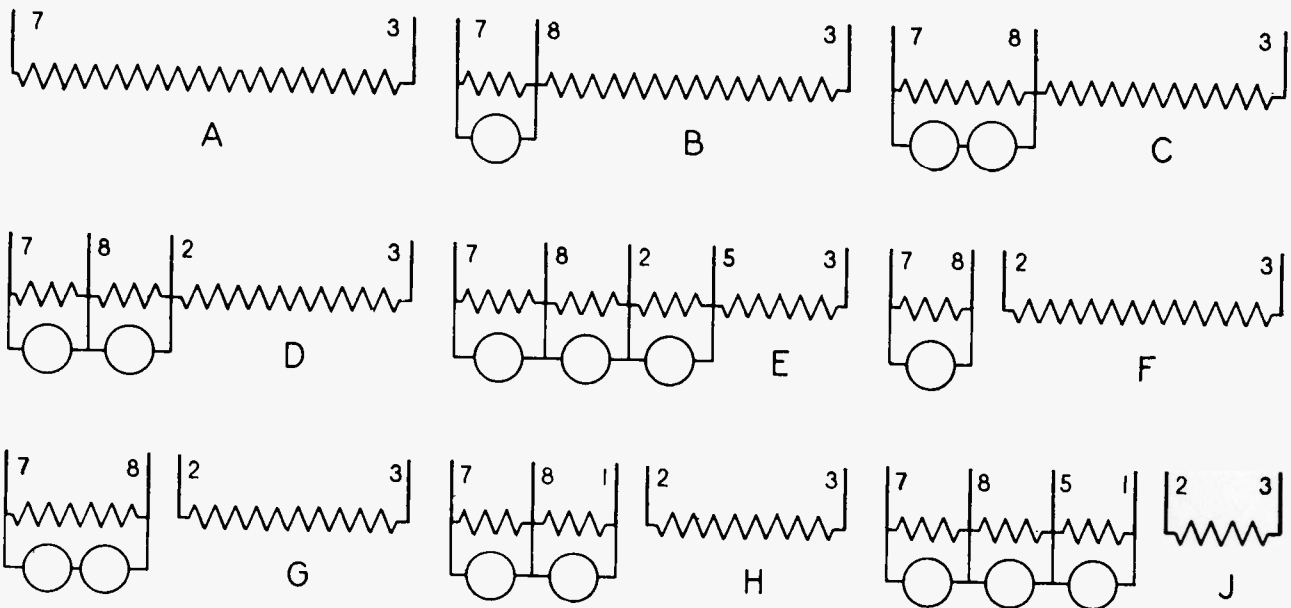

In the standard series, the first letter K means that a 6 to 8 volts, 150 ma. pilot bulb is to be used. L means a 250 ma. bulb. The number following means the voltage drop in the resistor of the tube. The last letter designates the base wiring as illustrated above. Of course, at all times a plain wire-wound resistor of proper power rating can be substituted.

REVIEW QUESTIONS

1. In the consideration of plate current and plate voltage of a vacuum tube, what is the saturation point?
2. Can any element in a tube, having a negative potential in respect to the cathode, attract electrons?
3. How does the screen grid of a tetrode reduce the capacity between the control grid and plate?
4. What is the meaning of amplification factor?
5. In radio receiving circuits, why must the control grid be biased negatively?
6. How does secondary emission take place?
7. What advantages do beam power tubes have?
8. Examining the chart, state the average amplification of triodes? Pentodes?
9. What is the advantage of metal type tubes?

SYLVANIA RADIO AND TELEVISION TUBE CHARACTERISTICS CHART

HOW TO USE THIS CHART

The types are listed in numerical and alphabetical order. The second column now lists the Bulb size or style of construction, whichever is most helpful in describing the type. Lock-in is, of course, well known, but the letters "T" and "ST" may need explaining. "T" means tubular bulb and "ST" is the dome topped bulb as now used in Type 6D6, 24, etc. The following number gives the nominal maximum diameter in eighths of inches. Subminiature types are marked T3, T2 or T1 depending on the bulb diameter.

Columns are included to show the type of emitter, (cathode or filament), and for interelectrode capacitances on those types having capacitance ratings. On converters the capacitances shown are respectively, Signal Grid to Plate; R-F Input; and Mixer Output. The capacitance values shown are for a shielded tube when the data are available, since this is the latest standard method. Except in the case of obsolete (or newly announced) types, more complete technical data may be found in the SYLVANIA Technical Manual.

The "Basing Diagram" column indicates the internal and external shield connections. For example, this column now shows the basing for Type 7A7 to be 8V-L-5. This means that the active elements are connected as shown in the base diagram 8V, and that the external shielding (in this case the Lock-in base) is connected to the lug (L) and the internal shield to pin 5. This avoids having a separate base diagram for types with a minor difference in shielding. The figures 0-0 indicate no external and no internal shielding respectively.

When replacing tubes in series string television receivers, attention should be given to the complete type number including the suffix. Prototypes should not be substituted for series string types.

Heater voltage, heater current and heater-cathode voltage ratings of the new series string tubes may, due to the requirements of such operation, differ widely from those of their prototypes. All the new series string types have controlled heater warm-up time for series string operation. In addition, heater current production tolerances have been tightened on all series string tubes to insure proper steady state voltage distribution. Two examples are shown in the following table.

	Series String Type 5AQ5	Proto-Type 6AQ5	Series String Type 6SN7GTB	Proto-Type 6SN7GTA
Series String Controlled Heater				
Warm-up Time.....	YES	NO	YES	NO
Heater Voltage.....	4.7	6.3	6.3	6.3
Heater Current (ma).....	600	450	600	600
Tolerance (ma).....	±25	±40	±25	±50
Heater-Cathode Voltage.....	200	200	200	200

It should be noted that the 5AQ5 and 6AQ5 differ in all characteristics shown except for heater cathode voltage. The 6SN7GTB and 6SN7GTA are identical except for heater current tolerance and controlled series string heater warm-up time. However, substitution of a 6SN7GTA in a series string receiver may, due to the absence of the controlled series string heater warm-up characteristic and wider heater current production tolerance, cause premature failure.

Series string types differ from their prototypes only in those characteristics necessary to insure dependable operation in series string television receivers. All other characteristics and ratings are identical to those of the prototypes.

NOTICE

This chart contains the very latest radio and television tubes in addition to many out-of-date types. It is designed to be of maximum use to servicemen as a quick reference chart.

Please note that all types listed are NOT available from Sylvania. They are included for your reference in finding substitutes, etc. Consult our price list for types currently available.

The data published here have been compiled from various sources and while believed to be accurate, no responsibility can be assumed in case of error.

Mention or reference to patented circuits does not constitute permission for their use. The license agreement under which Sylvania tubes are sold is enclosed in the tube carton.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS


Type	Construction		Emitter			Notes (1) (2) Capacitances in μf .			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Ohms Load for Rated Power Output	Unde- loaded Power Output Milli- watts	Type
	Bulb Size or Style	Class	Beams Diag.	Type	Volts	Amps.	Cyp.	Clin.												
00A	ST-14	Triode	4D-0-0	Filament	5.0	0.250	8.5	3.2	2.0	Detector	45	0	1.5	30,000	666	00A	
00B	T-5 1/2	Diode	3B0-0-0	Cold K	Voltage Regulator with starting Voltage at 155, Operating Voltage 150, Operating Current 5 to 30 Ma.	00B	
00C	ST-18	Diode	4AJ-0-0	Cold K	Voltage Regulator with starting Voltage at 100, Operating Voltage 75, Operating Current 5 to 40 Ma.	00C	
00D	ST-18	Diode	4AJ-0-0	Cold K	Relay Tube Peak Cathode Ma. = 100 D-C Cathode Ma. = 85 Max. Starter Anode Drop = 60V. Approx. Anode Drop = 70V. Approx.	00D	
00E	ST-19	Gas Triode	4V-0-0	Cold K	Switching	750	00E	
00F	T-5 1/2	Gas Pentode	0A5	Cold K	Trigger Grid Voltage = +90 Volts. Trigger Pulse Voltage = 85 Volts. Keep Alive Current = 50 μa	00F	
00G	T-5 1/2	Diode	5B0-0-0	Cold K	Voltage Regulator with starting Voltage at 115, Operating Voltage 105, Operating Current 5 to 30 Ma.	00G	
00H	ST-18	Diode	4AJ-0-0	Cold K	Voltage Regulator with starting Voltage at 195, Operating Voltage 90, Operating Current 5 Ma. Min. 30 Ma. Max.	00H	
00I	T-5 1/2	Diode	5B0	Cold K	Voltage Regulator with starting Voltage at 105, Operating Voltage 75, Operating Current 5 Ma. Min. 30 Ma. Max.	00I	
00J	ST-18	Diode	4AJ-0-0	Cold K	Voltage Regulator with starting Voltage at 180, Operating Voltage 105, Operating Current 5 Ma. Min. 40 Ma. Max.	00J	
00K	ST-19	Diode	4AJ-0-0	Cold K	Voltage Regulator with starting Voltage at 180, Operating Voltage 150, Operating Current 5 Ma. Min. 40 Ma. Max.	00K	
00L	ST-19	Gas Diode	4BL1-0	Cathode	H-W Rect. { 117 A.C. Volts Per Plate, RMS, 75 Ma. Max., 40 Ma. Min. Output Current. Starter Anode Connects to Anode thru 10 Megohms By-Pass with .002 μf	00L	
00M	T-7	Metal	4R1-0	Cathode	F-W Rect. { 300 A.C. Volts Per Plate, RMS, 90 Ma. Max., 30 Ma. Min. Output Current.	00M	
00N	T-7	Metal	4R1-0	Cathode	F-W Rect. { 300 A.C. Volts Per Plate, RMS, 110 Ma. Max., 30 Ma. Min. Output Current.	00N	
00O	T-7	Metal	4R-0-0	Cathode	F-W Rect. { 300 A.C. Volts Per Plate, RMS, 90 Ma. Max., 30 Ma. Min. Output Current.	00O	
00P	ST-14	Triode	4D-0-0	Filament	3.0	0.350	8.1	3.1	3.2	Amplifier	90 135	4.5 9.0	785 800	8.0 8.0	00P
00Q	T-5 1/2	Diode	5AP-0-3	Cathode	1.4	0.150	Detector	00Q
00R	ST-18	Pentode	4M-0-4	Filament	2.0	0.060	.007m	5.0	11.0	R-F Amp.	135 180	3.0 3.0	67.5 67.5	00R
00S	ST-18	Pentode	4M-0-4	Filament	2.0	0.060	.01m	5.0	11.0	R-F Amp.	135 180	3.0 3.0	67.5 67.5	00S
00T	ST-12	Tetrode	4K-0-3	Filament	2.0	0.060	Power Amp.	85	4.5	85	00T
00U	T-9	Power Pent.	6X-0-0	Filament	1.4	0.050	Converter	135 180	3.0 3.0	67.5 67.5	00U
00V	ST-12	Heptode	6L-0-0	Filament	2.0	0.060	10.5	9.0	Converter	135 180	3.0 3.0	67.5 67.5	00V
00W	T-9	Heptode	7Z-1-0	Filament	1.4	0.050	0.3m	7.0	10.0	Converter	90	0	90	00W
00X	Lock-in	Pentode	5B8L-0	Filament	1.2	0.130	0.95m	9.8	4.2	R-F Amp.	150	1.5	150	00X
00Y	T-3	Pentode	8CP-0-0	Filament	1.25	0.040	Power Amp.	30 45 67.5	0 0 4.5	30 45 67.5	00Y
00Z	T-3	Pentode	8CP-0-0	Filament	1.25	0.040	R-F Amp.	30 45 67.5	0 0 4.5	30 45 67.5	00Z
00AA	T-3	Pentode	8CP-0-0	Filament	1.25	0.040	.009	1.9	3.0	R-F Amp.	45	0	45	00AA
00AB	T-3 1/2	Pentode	6AR-0-0	Filament	1.25	0.100	.008m	3.6	4.4	R-F Amp.	67.5	0	67.5	00AB
00AC	T-3 1/2	Pentode	6AR-0-1A5	Filament	1.4	0.095	.008m	3.8	7.6	R-F Amp.	67.5	0	67.5	00AC
00AD	T-3 1/2	Diode Pent.	6AU-0-0	Filament	1.4	0.095	0.2	2.5	4.3	Det. Amp.	67.5	0	67.5	00AD
00AE	T-2X3	Pentode	1AG4-0-0	Filament	1.25	0.040	Power Amp.	41.4	3.6	41.4	00AE
00AF	T-2X3	Diode Pent.	1AG5	Filament	1.25	0.030	0.1	1.7	2.4	Amplifier	45	2.0	45	00AF
00AG	T-2X3	Diode Pent.	1AJ5-4-0	Filament	1.25	0.040	0.1	1.7	2.4	Det. Amp.	45	0	45	00AG
00AH	T-2X3	Pentode	1AK4-3-0	Filament	1.25	0.030	.01m	3.5	4.5	Class A7 Amp.	45	0	45	00AH
00AI	T-2X3	Diode Pent.	1AK5-4-0	Filament	1.25	0.030	0.1m	3.0	2.7	Det. Amp.	45	0	45	00AI
00AJ	T-4 1/2	Diode	9Y	Filament	1.4	0.650	Flyback	00AJ
00AK	T-9	Diode	3C	Filament	1.25	0.200	Flyback	00AK
00AL	ST-12	Pentode	4M-0-4	Filament	2.0	0.060	.007m	5.0*	11.0*	R-F Amp.	135 180	3.0 3.0	67.5 67.5	00AL
00AM	ST-12	Diode Tri.	6M-0-3	Filament	2.0	0.060	3.6	1.6	1.9	Det. Amp.	90	0	90	00AM
00AN	T-9	Heptode	7Z-1-0	Filament	1.4	0.100	0.34	7.0	7.5	Converter	90	0	90	00AN
00AO	T-9	Diode Triode Pentode	8AJ-0-7	Filament	1.4	0.100	Det. Amp.	90	0	90	00AO
00AP	T-5 1/2	Triode	5CF-0-0	Filament	1.4	0.050	1.8	0.9	4.2	Amplifier	90	0	90	00AP
00AQ	T-9	Power Pent.	6X-0-0	Filament	1.4	0.100	Power Amp.	83	7.0	83	00AQ
00AR	ST-12	Heptode	6L-0-0	Filament	2.0	0.180	0.3	10.0	10.0	Converter	135 180	3.0 3.0	67.5 67.5	00AR
00AS	ST-12	Heptode	7Z-0-0	Filament	2.0	0.180	0.26	10.0	14.0	Converter	135 180	3.0 3.0	67.5 67.5	00AS
00AT	T-3	Heptode	8CN-0-0	Filament	1.25	0.040	0.25m	6.5	4.0	Converter	30	0.0	30	00AT
00AU	T-3	Triode	8DN-0-0	Filament	1.25	0.300	2.6*	1.0*	1.0*	Amplifier	90	5.0	00AU

1D5GP	ST-12	Pentode	5Y-0-7	Filament	2.0	0.060	5.0"	12.0"	R-F Amp.	135	3.0	67.5	2.2	0.9	1 Mgr.	625	1D5GP
1D5GT	ST-12	Tetode	5R-0-4	Filament	2.0 <td>0.060</td> <td>4.4 <td>10.8</td> <td>R-F Amp.</td> <td>135</td> <td>3.0 <td>67.5</td> <td>2.3</td> <td>0.8</td> <td>1 Mgr.</td> <td>725</td> <td>1D5GT</td> </td></td>	0.060	4.4 <td>10.8</td> <td>R-F Amp.</td> <td>135</td> <td>3.0 <td>67.5</td> <td>2.3</td> <td>0.8</td> <td>1 Mgr.</td> <td>725</td> <td>1D5GT</td> </td>	10.8	R-F Amp.	135	3.0 <td>67.5</td> <td>2.3</td> <td>0.8</td> <td>1 Mgr.</td> <td>725</td> <td>1D5GT</td>	67.5	2.3	0.8	1 Mgr.	725	1D5GT
1D7G	ST-12	Heptode	7Z-0-0	Filament	2.0 <td>0.060</td> <td>0.25</td> <td>9.0</td> <td>Converter</td> <td>180</td> <td>3.0 <td>67.5</td> <td>2.2</td> <td>0.7</td> <td>350,000</td> <td>625</td> <td>1D7G</td> </td>	0.060	0.25	9.0	Converter	180	3.0 <td>67.5</td> <td>2.2</td> <td>0.7</td> <td>350,000</td> <td>625</td> <td>1D7G</td>	67.5	2.2	0.7	350,000	625	1D7G
1D8GT	T-9	Diode Triode Pentode	8AJ-0-2	Filament	1.4 <td>0.100</td> <td>.....</td> <td>.....</td> <td>Det. Amp.</td> <td>45</td> <td>0</td> <td>.....</td> <td>1.5</td> <td>2.0</td> <td>400,000</td> <td>975.4</td> <td>1D8GT</td>	0.100	Det. Amp.	45	0	1.5	2.0	400,000	975.4	1D8GT
									Power Amp.	67.5	0	0.6	77,000	395	
										90	0	0.6	55,500	450	
										45	4.5	45	1.1	43,500	575	
										67.5	6.0	67.5	3.8	300,000+	650	
										90	9.0	90	5.0	900,000+	875	
														200,000+	100	
														16,000	200	
														19,000	500	

(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, R-F input, Mixer Output.
 (4) Average contact potential bias developed across specified grid resistor.
 X Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

□ Applied through 20,000 ohms. Plate to Plate.
 * Conversion factor.
 ** Triode Operation.
 † Maximum Signal.

Plate to Plate.
 m maximum Cathode Resistor (ohms).
 † Approximate.

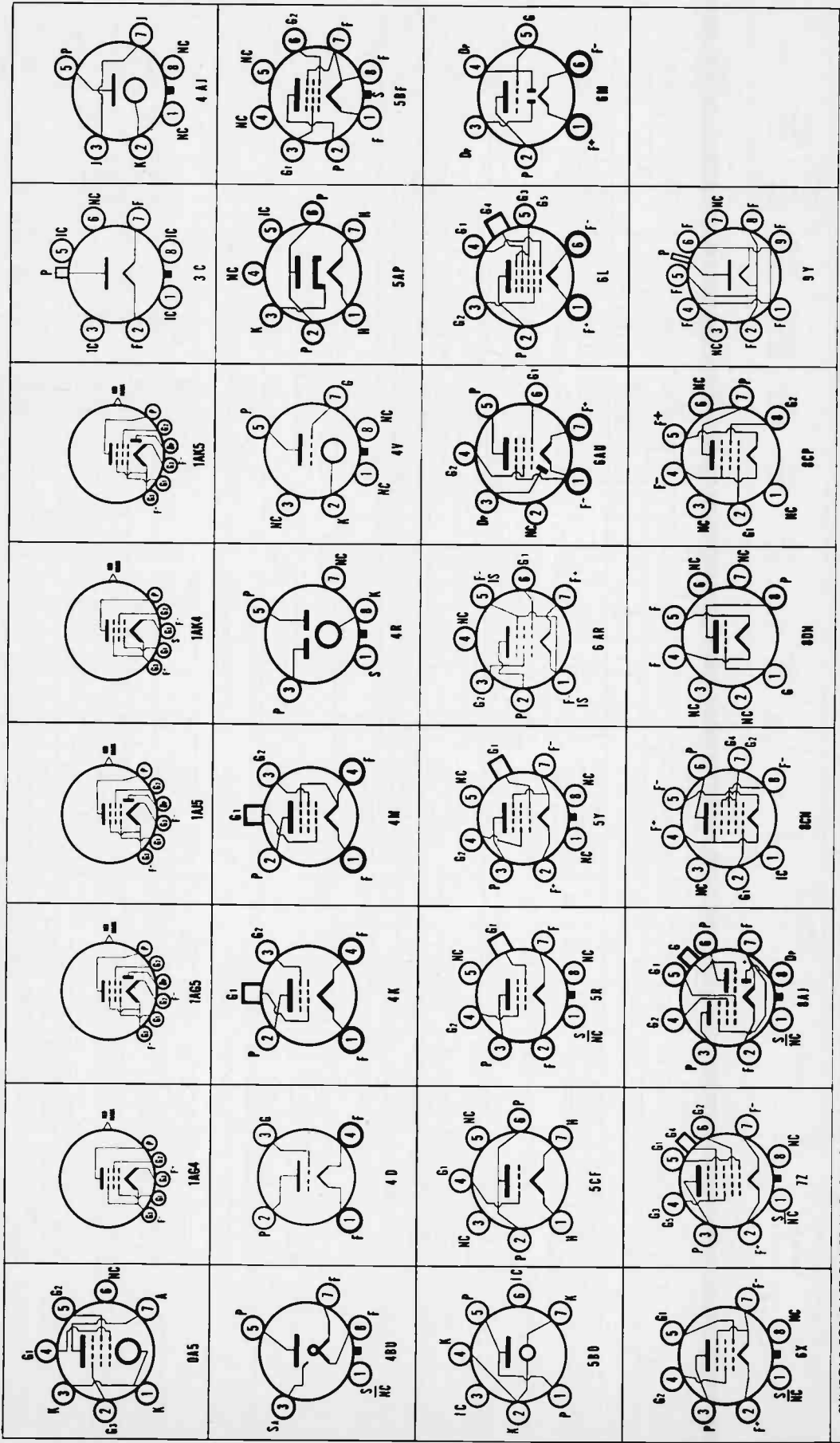


SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate, F—Filament, Fc—Filament Center, G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; HT—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper, K—Cathode, NC—No Connection, P—Plate, Rc—Ray Control, S—Metal Shell, SA—Starter Anode, T—Target, XS—External Shield, □—Top Cap, ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Note (1) (7) Capacitances in μ f.		Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Microhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milli-watts	Type
	Bulb Size or Style	Class	Beating Diag.	Type	Volts	Amps.	Cgp.												
1DN5	T-5 1/2	Diode Pent.	6BW	Filament	1.4	0.050			67.5	0	67.5	2.1	0.55	630	14.5			1DN5	
1E4G	T-9	Triode	5S-0-0	Filament	1.4	0.050	2.4	6.0	90	0.0	90	4.5	0.55	1,395	14			1E4G	
1E5GP	ST-12	Pentode	5Y-0-7	Filament	2.0	0.060	.007m	5.5	135	3.0	67.5	1.6	0.7	560				1E5GP	
1E7GT	T-9	Duo. Power Pent.	8C-0-0	Filament	2.0	0.240			180	3.0	67.5	1.7	2.0	1,600	350	84,000	575	1E7GT	
1E8	T-3	Heptode	8CN-0-0	Filament	1.25	0.040	0.4	6.0	30	0	30	0.30	0.8	115				1E8	
1F4	ST-12	Power Pent.	5K-0-0	Filament	2.0	0.180			45	0	45	0.60	1.1	400,000				1F4	
1F5G	ST-12	Power Pent.	6X-0-0	Filament	2.0	0.180			67.5	0	67.5	1.0	1.5	400,000				1F5G	
1F6	ST-12	Duodiode Pentode	6W-0-6	Filament	2.0	0.060	.007m	4.0	180	1.5	67.5	2.2	0.7	650				1F6	
1F7G	ST-12	Duodiode Pentode	7AD-0-7	Filament	2.0	0.060	.01m	3.8*	180	1.5	67.5	2.2	0.7	650				1F7G	
1F7GV	ST-12	Duodi. Pent.	7AF-0-7	Filament	2.0	0.600			180	1.5	67.5	2.2	0.7	650				1F7GV	
1G3	T-9	Diode	3C	Filament	1.25	0.200			90	6.0	90	2.3	0.55	10,700	885			1G3	
1G4GT	T-9	Triode	5S-0-0	Filament	1.4	0.050			90	6.0	90	2.3	0.55	10,700	885			1G4GT	
1G5G	ST-14	Pentode	6X-0-0	Filament	2.0	0.180			90	6.0	90	2.5	0.55	133,000	1,500	8,500	950	1G5G	
1G6GT	T-9	Duodiode	7AB-0-0	Filament	1.4	0.100			90	0.0	90	1.04	0.55	40,000	825	33	(Each Triode Class A)	1G6GT	
1H2	T-6 1/2	Diode	9D1	Cathode	1.4	0.550			90	0.0	90	2.14†	0.55	12,000†	675			1H2	
1H4GT	T-9	Triode	5S-0-0	Filament	2.0	0.060			90	4.5	90	3.5	0.55	11,000	850			1H4GT	
1H5GT	T-9	Diode Triode	5Z-1-7	Filament	1.4	0.050	1.1	0.35	135	9.0	135	3.0	0.55	10,300	900	9.3		1H5GT	
1H6GT	T-9	Duodiode Tri.	7A-0-6	Filament	2.0	0.060	3.6	1.6	180	13.5	180	3.0	0.55	240,000	275	65		1H6GT	
1J3	T-9	Diode	3C	Filament	1.25	0.200			90	0.0	90	0.8	0.55	35,000	575	50		1J3	
1J5G	ST-14	Pentode	6X-0-0	Filament	2.0	0.180			90	0.0	90	0.8	0.55	35,000	575	50		1J5G	
1J6G	ST-19	Duodiode	7AB-0-0	Filament	2.0	0.240			135	16.5	135	7.0	2.0	125,000	1,000	125	13,500	575	1J6G
1K3	T-9	Diode	3C	Filament	1.25	0.200			90	0.0	90	0.8	0.55	35,000	575	50		1K3	
1L4	T-5 1/2	Pentode	6AR-0-1A5	Filament	1.4	0.050	.008m	3.8	90	0	67.5	2.9	1.2	600,000	985			1L4	
1L6	T-5 1/2	Heptode	7DC-0-0	Filament	1.4	0.050	0.36m	7.5	90	0	45	4.5	2.0	350,000	1,085			1L6	
1LA4	Lock-in	Power Pent.	5AD-L-0	Filament	1.4	0.050			85	4.5	85	3.5	0.7	300,000	800	25,000	100	1LA4	
1LA6	Lock-in	Heptode	7AK-L-0	Filament	1.4	0.050	0.4	7.5	90	0.0	45	0.35	0.6	750,000	250A	20,000	35	1LA6	
1LB4	Lock-in	Power Pent.	5AD-L-0	Filament	1.4	0.050			67.5	6.0	67.5	3.8	0.8	300,000	875	16,000	100	1LB4	
1LB6	Lock-in	Heptode	8AX-L-0	Filament	1.4	0.050	0.1	3.8	90	0.0	67.5	4.0	0.9	800,000	100A			1LB6	
1LC5	Lock-in	Pentode	7AO-L-8	Filament	1.4	0.050	.007m	3.2	90	0.0	45	1.15	0.30	300,000	775			1LC5	
1LC6	Lock-in	Heptode	7AK-L-0	Filament	1.4	0.050	0.28	9.0	45	0.0	35	0.75	0.75	300,000	950A	45 V. Max., 1.4 Ma.		1LC6	
1LD5	Lock-in	Diode Pent.	6AX-L-8	Filament	1.4	0.050	0.18	3.2	45	0.0	45	0.55	0.12	750,000	575			1LD5	
1LE3	Lock-in	Triode	4AA-L-0	Filament	1.4	0.050	1.7	1.7	90	0.0	90	1.4	0.55	11,500	760	14.5		1LE3	
1LG5	Lock-in	Pentode	7AO-L-8	Filament	1.4	0.050	.007m	3.2	45	0	45	1.5	0.45	350,000	800			1LG5	
1LH4	Lock-in	Diode Triode	5AG-L-1	Filament	1.4	0.050			90	0.0	90	1.6	0.35	240,000	975	65		1LH4	
1LN5	Lock-in	Pentode	7AO-L-8	Filament	1.4	0.050	.007m	3.4	90	0.0	90	1.2	0.3	1.5 Mes.	800			1LN5	
1N5GT	T-9	Pentode	5Y1-7	Filament	1.4	0.050	.007m	2.8	90	0.0	90	3.4	0.7	300,000	750			1N5GT	
1N6GT	T-9	Diode Pent.	7AM-0-0	Filament	1.4	0.050			90	4.5	90	3.0	0.7	800,000	800	25,000	100	1N6GT	
1P5GT	T-9	Pentode	5Y1-7	Filament	1.4	0.050	.007m	3.0	90	0.0	90	3.3	0.7	800,000	750			1P5GT	
1Q5GT	T-9	Beam Pent.	6AF-0-0	Filament	1.4	0.100			90	4.5	90	9.5	1.3	2,900	2,900	8,000	970	1Q5GT	
1O6	T-3	Diode Pent.	8CO-0-0	Filament	1.25	0.040	.085	1.8	30	0.0	30	0.33	0.09	500,000	330			1O6	

1R4	Lock-in T-5½	H. F. Diode Heptode	4AH-2 7AT-0-0	Cathode Filament	1.4 1.4	0.150 0.050	7.0	12.0	Detector Converter	45 90	0.0 0.0	45 67.5	0.7 1.5	2.1 3.5	500,000† 400,000†	210A 280A	1R5
1S4	T-5½	Power Pent.	7AV-0-0	Filament	1.4	0.100	Power Amp.	45 90	4.5 7.0	45 67.5	3.9# 7.4#	0.8# 1.4#	100,000† 100,000†	1,250 1,575	8,000 9,500
1S5	T-5½	Diode Pent.	6AU-0-0	Filament	1.4	0.050-0.2	Det. Amp.	67.5	0.0	67.5	1.6	0.4	600,000	635	1S5
1S6	T-3	Diode Pent.	8DA-0-0	Filament	1.25	0.040	Det. Amp.	30 45	0 0	30 45	0.32 0.75	0.1 0.81	500,000 500,000	330 475	1S6

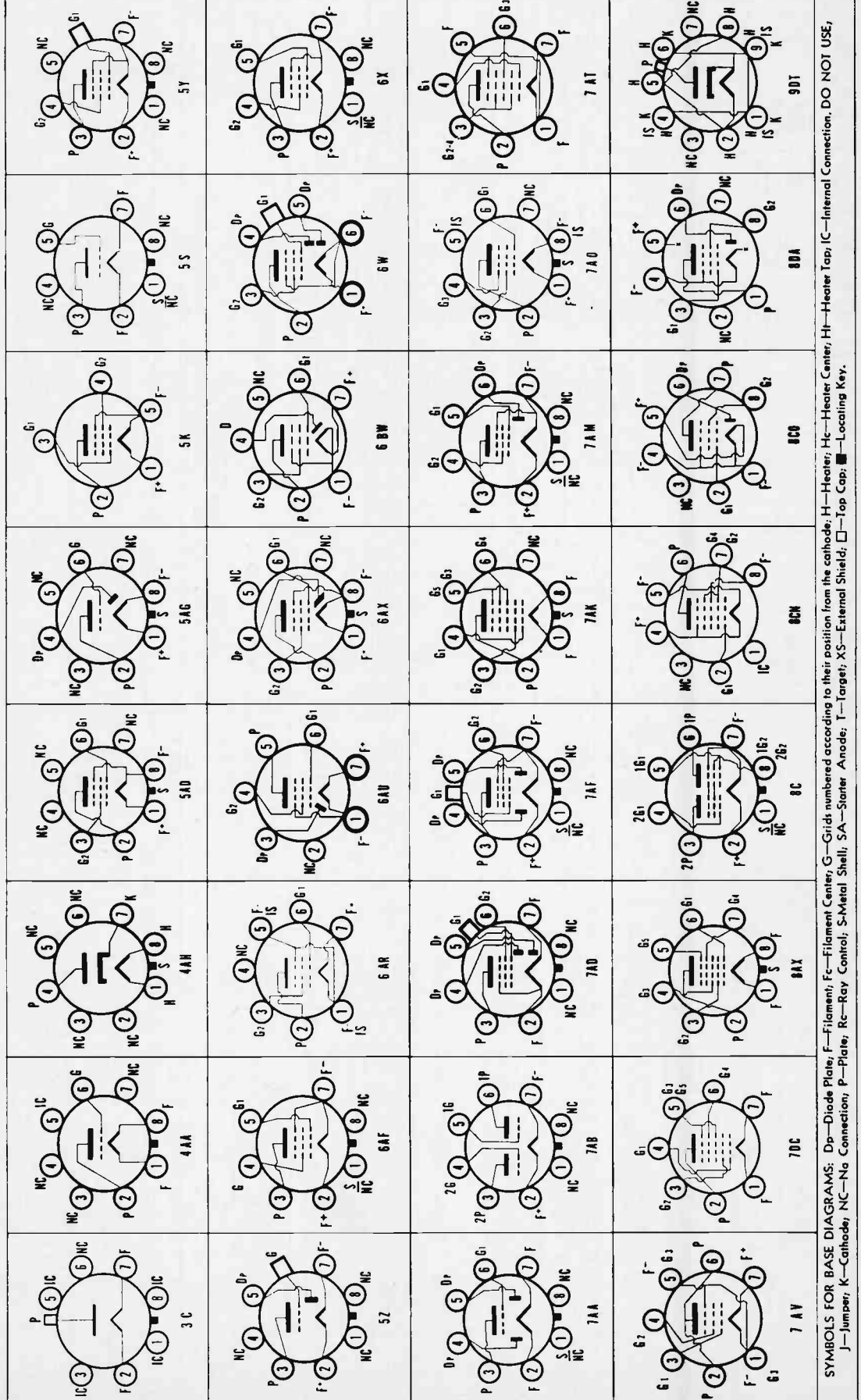(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output.
 † Per Tube or Section.
 ‡ Plate and Target Supply Voltage.
 § Applied through 20,000 ohms.
 ¶ Conversion Transconductance.
 ** Triode Operation.



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Node (*) Capacitances in p.f.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Trans-conductance Milli-mhos	Amplification Factor	Ohms for Stated Power Output	Unde-terminated Output Milli-watts	Type
	Bulb Size or Style	Class	Type	Volts	Amps.	Csp.	Cin.												
1SA6GT	T-9	Pentode	Filament	1.4	0.050	.01m	5.2	8.6	0	45	0	1.1	0.3	700,000	750	1SA6GT	
1SB6GT	T-9	Diode Pent.	Filament	1.4	0.050	0.25	3.2	3.0	0	67.5	0	2.4	0.7	600,000	950	1SB6GT	
1T4	T-5½	Pentode	Filament	1.4	0.050	.008m	3.8	7.5	0	67.5	0	1.4	0.16	700,000	665	1T4	
1T5GT	T-9	Power Pent.	Filament	1.4	0.050	0.5	4.8	8.0	0	45	0	1.7	0.7	350,000	700	1T5GT	
1T6	T-3	Diode Pent.	Filament	1.25	0.040	0	67.5	0	1.4	0.4	500,000	900	1T6	
1U4	T-3½	Pentode	Filament	1.4	0.050	.008m	3.6	7.5	0	45	0	1.6	0.45	1.0 Meg.†	600	1U4	
1U5	T-5½	Diode Pent.	Filament	1.4	0.050	0.2	3.2	2.4	0	67.5	0	0.5	0.7	500,000	960A	1U5	
1U6	T-5½	Heptode	Filament	1.4	0.025	0.4	8.0	12.0	0	45	0	0.6	0.6	500,000	275A	1U6	
1V	T-9	Diode	Cathode	6.3	0.300	395 A.C. Volts Per Plate, RMS, 45 Ma. Output Current. Condenser Input to Filter.	(Ga = 67.5 V., 1.0 Ma.)	1V	
1V2	T-6½	Diode	Filament	0.695	0.300	Television Service. RF or Flyback Supply. Peak Inverse Volts = 8,250. Output = 0.5 Ma.	1V2	
1V3	T-3	Pentode	Filament	1.25	0.040	Television Service. RF or Flyback Supply. Peak Inverse Volts = 8,250. Output = 0.5 Ma.	1V3	
1W4	T-5½	Power Pent.	Filament	1.4	0.050	Characteristics Same as Type 1A3C.	45	4.5	1.6	0.3	400,000	650	1W4	
1W5	T-3	Pentode	Filament	1.25	0.040	.01m	3.3	3.5	0	62.5	0	3.8	0.8	300,000	875	1W5	
1X2	T-6½	Diode	Filament	1.25	0.300	Television Service. RF or Flyback Supply. Peak Inverse Volts = 15 KV. Output = 1 Ma.	62.5	5.0	3.8	0.8	300,000	875	1X2	
1X3A	T-6½	Diode	Filament	1.25	0.300	Television Service. RF or Flyback Supply. Peak Inverse Volts = 17.5 KV. Output = 1 Ma.	67.5	6.0	3.8	0.8	300,000	875	1X3A	
1X3B	T-6½	Diode	Filament	1.25	0.300	Television Service. RF or Flyback Supply. Peak Inverse Volts = 22 KV. Output = 0.5 Ma.	67.5	6.0	3.8	0.8	300,000	875	1X3B	
1Y2	ST-12	Diode	Filament	1.5	0.990	15,000 A.C. Volts Per Plate, RMS, 2.0 Ma. Output Current.	90	9.0	5.0	1.0	250,000	935	1Y2	
1Z2	ST-16	Triode	Filament	2.5	2.500	16.0	7.0	5.0	H-W Rect. 7,800 Volts RMS Plate, 2.0 Ma. D.C. Output Current.	30	0.0	3.0	0.42	700,000	430	1Z2	
2A4G	ST-12	Gas Triode	Filament	2.5	2.500	S.T.-A1 Amp. 250	45.0	60.0	800	5,250	2,500	4.2	2,500	3,500	2A4G	
2A5	ST-14	Beam Pent.	Cathode	2.5	1.750	Instantaneous Forward or Inverse Anode Volts = 900 Peak Anode Amps. = 1.25 Average Anode. Current = 0.1 Amp. Max. Averaging Time = 45 Seconds. Cold Starting Time = 2 Seconds.	60.0	80-147I. Push Pull. Fixed Bias	2A5	
2A6	ST-19	Duodiode Tri.	Cathode	2.5	0.800	1.7	1.7	3.8	Relay Tube	0.9	91,000	1,100	100	2A6	
2A7S	ST-12	Heptode	Cathode	2.5	0.800	0.3m	8.5	9.0	Power Amp.	2A7S	
2AF4A	T-5½	Triode	Cathode	2.351	0.600	1.9	2.2	1.4	Characteristics Same as Type 6A7.	2AF4A	
2AF4B	T-5½	Triode	Cathode	2.351	0.600	1.9	2.2	1.4	Grid Resistor = 17.5. Plate Resistor = 220 Ohms. Grid Current = 250 µa. Type 2AF4B Has Higher Heater-Cathode Voltage Ratings Than Otherwise Identical Type 2AF4A.	100	Grid Resistor = 17.5. Plate Resistor = 220 Ohms. Grid Current = 250 µa. Type 2AF4B Has Higher Heater-Cathode Voltage Ratings Than Otherwise Identical Type 2AF4A.	2AF4B	
2B3	T-9	Diode	Filament	1.75	0.350	H-W Rect.	2B3	
2B5	T-3	Duodiode	Filament	1.2	0.360	1.2*	0.9*	1.9*	Amplifier f	90	1.0	18,700	2B5	
2B7	ST-12	Duodi. Pent.	Cathode	2.5	0.800	Characteristics Same as Type 6B7.	2B7	
2B7S	ST-12	Duodi. Pent.	Cathode	2.5	0.800	Characteristics Same as Type 6B7.	2B7S	
2B4	T-5½	Triode	Cathode	2.5	0.650	Characteristics Same as Type 6B4.	2B4	
2C1	ST-12	Duodiode	Cathode	6.3	0.600	1.6	1.6	2.0	Relay Tube	350	30	7,600	1,375	10.4	90,000	2C1	
2C2	T-9	Triode	Cathode	6.3	0.300	3.6	2.2	0.7	Amplifier	950	16.5	2C2	
2C50	T-9	Duodiode	Cathode	12.6	0.300	Amplifier f	300	10.5	6,600	3,000	20.0	2C50	
2C51	T-6½	Duodiode	Cathode	6.3	0.300	1.3	2.2	1.0	Amplifier	900	11	6,600	2,900	10	2C51	
2C52	T-9	Duodiode	Cathode	12.6	0.300	2.7*	2.3*	0.75*	Amplifier	950	2.0	6,500	5,500	3.5	2C52	
2CY5	T-5½	Tetrode	Cathode	2.41	0.600	0.7	4.5	3.0	VHF Amp.	2CY5	
2D1	T-5½	Gas Tetrode	Cathode	6.3	0.600	.08*	2.4*	1.6*	Relay Tube	400	5	2D1	
2E5	T-9	Electron Ray	Cathode	2.5	0.800	Indicator	2E5	
2E26	T-9	Beam Pent.	Cathode	6.3	0.800	.02*	12.5*	7.0*	Class C Amp.	500	40.0	185	60.0	11.0	2E26	
2S/4S	ST-12	Duodiode	Cathode	2.5	1.350	Detector	2S/4S	
2T4	T-5½	Triode	Cathode	2.351	0.600	1.7*	2.6*	0.4*	UHF Osc.	2T4	
2V3G	ST-12	Diode	Filament	2.5	5.000	H-W Rect. 6000 A.C. Volts Per Plate, RMS, 2 Ma. Output Current. Condenser Input to Filter.	2V3G	
2W3GT	T-9	Diode	Filament	2.5	1.500	H-W Rect. 350 A.C. Volts Per Plate, RMS, 55 Ma. Output Current. Condenser Input to Filter.	2W3GT	
2X3A (3)	T-9	Diode	Filament	2.5	1.500	Characteristics Same as Type 2X3	2X3A (3)	

(1) Values are given shielded unless marked with (*). (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer, Converter grid to plate, and screen grid to plate. (3) Has special mechanical and/or life characteristics. (4) Average contact potential bias developed across grid to plate, RF input, Mixer, Converter grid to plate, and screen grid to plate. (5) Controlled Heater Warm-up Time (Applies to parallel connection of types having a tapped heater.)

† Per Tube or Section.
‡ Plate and/or Section Supply Voltages.
§ Maximum Signal.
¶ Applied through 20,000 ohms.
‡ Conversion Transconductance.
†† Inode Operation.
‡‡ Maximum Signal.
‡‡‡ Inode Operation.

□ Plate to Plate.
∇ Approximate.
∞ Cathode Resistor (Ohms).

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--


SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Notes (1) (2) Capacitance in $\mu\text{f.}$			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Ohms Load for Stated Power Output	Power Output Milli- watts	Type
	Bulb Size or Style	Class	Base Disp.	Type	Volts	Amps.	Cap.												
2Z9/G84	5T-12	Diode	4B-0-0	Filament	2.5	1.500	2Z9/G84
3A2	T-6 1/2	Diode	9D1-0-1	Cathode	3.15	0.920	3A2
3A3	T-9	Diode	4A-0-7	Cathode	3.15	0.920	3A3
3A4	T-5 1/2	Pentode	7B8-0-0	Filament	1.4	0.200	0.35m	4.8	7.0	9.0	14.8	9.6	90,000	1,900	3A4
3A5	T-5 1/2	Duotriode	7B8-0-0	Filament	2.8	0.100	3A5
3A5GT	T-9	Diode Triode Pentode	8A5-0-1	Filament	1.4	0.100	0.0	9.6	4.3	9.0	30.0	3.78	8,300 Ω	1,800 Ω	15	3A5GT
3AFAA	T-5 1/2	Triode	7DK-0-0	Cathode	3.21	0.450	0.19m	2.2	1.4	UHF Osc.	3AFAA
3AL5	T-5 1/2	Duotriode	6B1-0-6	Cathode	3.151	0.600	3AL5
3AU6	T-5 1/2	Pentode	7B1-0-3	Cathode	3.151	0.600	0.035m	5.5*	5.0*	R-F Amp.	3AU6
3AV6	T-5 1/2	Duotriode Tri.	7B1-2-0	Cathode	3.151	0.600	3AV6
3B2	T-12	Diode	8GH-0-7	Cathode	3.15	0.920	3B2
3B4	T-5 1/2	Beam Amp.	7C7	Filament	9.50	0.165	0.16	4.6	7.6	VHF	3B4
3B5GT	T-9	Beam Amp.	7AP-0-0	Filament	1.4	0.100	3B5GT
3B7	Lock-in	Duotriode	7BE-L-0	Filament	2.8	0.050	3B7
3BA6	T-5 1/2	Pentode	7BK-0-2	Cathode	3.151	0.600	0.035m	5.5*	5.0*	I-F or R-F Amplifier	3BA6
3BC5	T-5 1/2	Pentode	7BD-0-2/7	Cathode	3.151	0.600	0.2	6.6	2.6	VHF Amp.	3BC5
3BE6	T-5 1/2	Heptode	7CH-0-0	Cathode	3.151	0.600	0.1m	5.5*	8.0*	Converter	3BE6
3BN4	T-5 1/2	Triode	7EG	Cathode	3.01	0.450	1.2	3.2	1.4	VHF Amp.	3BN4
3BN6	T-5 1/2	Grid Beam	7DF-0-1	Cathode	3.151	0.600	3BN6
3BU8	T-6 1/2	Duo Pentode	9FG-0-3	Cathode	3.151	0.600	G3 to P 1.9	6.0	3.0	Sync. Sep.	3BU8
3BY6	T-5 1/2	Heptode	7CH-0-0	Cathode	3.151	0.600	0.08m	5.4*	7.6*	Sync. Sep.	3BY6
3BZ6	T-5 1/2	Pentode	7CM-0-7	Cathode	3.151	0.600	0.15m	7.5	9.8	VHF Amp.	3BZ6
3C2	T-12	Diode	8FA-0-4,7,8	Filament	3.15/0.810/1.58	0.480	3C2
3CSGT	T-9	Pentode	7AP-0-0	Filament	1.4	0.100	3CSGT
3CG/XXB	Lock-in	Duotriode	7BW-0-0	Filament	2.8	0.050	3CG/XXB
3CB6	T-5 1/2	Pentode	7CM-0-7	Cathode	3.151	0.600	0.08m	6.5*	9.0*	Amplifier	3CB6
3CE5	T-5 1/2	Pentode	7BD	Cathode	3.151	0.600	0.3*	6.5*	1.9*	VHF Amp.	3CE5
3CF6	T-5 1/2	Pentode	7CM	Cathode	3.151	0.600	0.15*	6.5*	3.0*	VHF Amp.	3CF6
3CS6	T-5 1/2	Heptode	7CH-0-0	Cathode	3.151	0.600	0.05* 0.36*	7.0*	7.5*	Sync. Separator	3CS6
3CY5	T-5 1/2	Tetrode	7EW-0-2/7	Cathode	2.9	0.450	0.3	4.5	3.0	VHF Amp.	3CY5
3D6	Lock-in	Beam Pent.	68A-L-0	Filament	2.8	0.110	0.3	7.5	6.5	Power Amp.	3D6
3D21A	5T-14	Beam Pent.	68U	Cathode	6.3	1.700	3D21A
3D21B	T-12	Beam Pent.	68U	Cathode	12.6	0.950	3D21B
3DK6	T-5 1/2	Pentode	7CM-0-7	Cathode	3.151	0.600	0.2*	6.3*	1.9*	VHF Amp.	3DK6
3D16	T-5 1/2	Grid Beam	7EN-0-0	Cathode	3.151	0.600	0.2	3D16
3E5	T-5 1/2	Power Pent.	68X-0-0	Filament	1.4	0.050	3E5
3E6	Lock-in	Pentode	7CL-L-5	Filament	2.8	0.050	0.07m	5.5	7.5	R-F Amp.	3E6
3LE4	Lock-in	Power Pent.	68A-L-0	Filament	2.8	0.050	3LE4
3LF4	Lock-in	Beam Pent.	68A-L-0	Filament	1.4	0.100	3LF4
3Q4	T-5 1/2	Power Pent.	7BA-0-0	Filament	1.4	0.100	3Q4
3O5GT	T-9	Beam Pent.	7AP-0-0	Filament	2.8	0.050	3O5GT

3S4	3V4	3Z4	4A6G	4AU6	4BA6	4BC5
1-5 1/2	1-5 1/2	1-5 1/2	ST-12	1-5 1/2	1-5 1/2	1-5 1/2
Power Pent.	Power Pent.	Power Pent.	Duobridge	Pentode	Pentode	Pentode
7BA-0-0	68X-0-0	7BA	8L-0-0	7BK-0-2	7BK	7BD-0-2&7
Filament	Filament	Filament	Filament	Cathode	Cathode	Cathode
1.4	1.4	1.4	2.0	4.21	4.21	4.21
0.100	0.100	0.050	0.130	0.450	0.450	0.450
2.8	2.8	2.8	4.0	0.0035*	0.0035*	0.02
0.050	0.050	0.025	0.060	5.5*	5.5*	
5.0	5.0	5.0	5.0	5.0*	5.0*	6.6
7.0	7.0	7.0	7.0	7.0	7.0	7.0
90	90	90	90	90	90	90
Power Amp.	Power Amp.	Power Amp.	Power Amp.	R-F Amp.	R-F Amp.	VHF Amp.
100,000	100,000	100,000	96,600	Class B, Max. Signal	Class B, Max. Signal	Class B, Max. Signal
1.4	1.1	1.3	1.1	1.1	1.1	1.1
7.4	7.4	6.5	10.8	10.8	10.8	10.8
1,575	1,495	1,450	750	750	750	750
8,000	8,000	8,000	8,000	8,000	8,000	8,000
354	354	3Z4	4A6G	4AU6	4AU6	4BC5
8,000	8,000	8,000	8,000	8,000	8,000	8,000
8,000	8,000	8,000	8,000	8,000	8,000	8,000
8,000	8,000	8,000	8,000	8,000	8,000	8,000

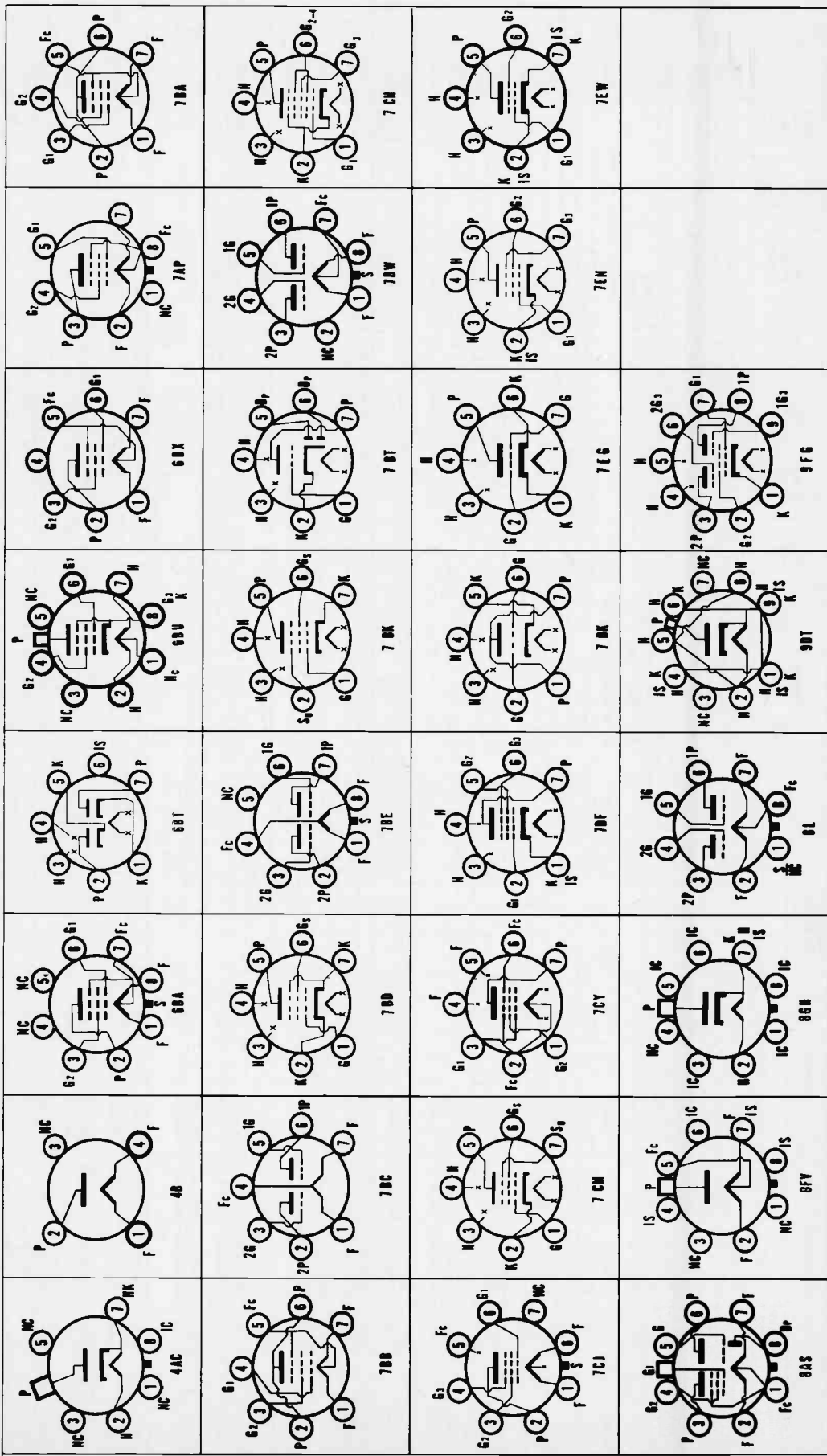(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output.
 † Controlled Heater Warm-up Time (applies to parallel connections of types having a topped heater.)
 ‡ Per Tube or Section.
 † Plate to Plate.
 ‡ Conversion Transconductance.
 †† Maximum Signal.
 ††† Those Operation.



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate, F—Filament, Fc—Filament Center, G—Grids numbered according to their position from the cathode, H—Heater, Hc—Heater Center, Ht—Heater Tap, IC—Internal Connection, DO NOT USE, J—Jumper, K—Cathode, NC—No Connection, P—Plate, Rc—Ray Control, S—Metal Shell, SA—Starter Anode, T—Target, XS—External Shield, □—Top Cap, ■—Locating Key.

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitters		Note (1) (2) Capacitances in $\mu\mu\text{f}$.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Choke Load for Stated Power Output	Unde- r- tor- ted Power Output Milli- watts	Type
	Bulb Size or Style	Clases	Beating Diag.	Type	Volts	Amps.	Cgp.												
4BC8	T-6½	Duodiode	9A J-0-9	Cathode	4.21	0.600	1.4	2.5	1.35	Class A1 Amp.	Characteristics Same as Type 6BC8. (4BC8 Designed for Series String TV Receivers.)	4BC8	
4BE6	T-6½	Heptode	7CH	Cathode	4.21	0.450	0.3*	7.0*	8.0*	Converter	Characteristics Same as Type 6BE6. (4BE6 Designed for Series String TV Receivers.)	4BE6	
4BN4	T-5½	Triode	7EG	Cathode	4.2	0.300	1.2	3.2	1.4	VHF Amp.	Characteristics Same as Type 6BN4.	4BN4	
4BN6	T-5½	Gated Beam	7DF-0-1	Cathode	4.21	0.450	Quad. F. M. Det.	Characteristics Same as Type 6BN6. (4BN6 Designed for Series String TV Receivers.)	4BN6	
4BO7A	T-6½	Duodiode	9A J-0-9	Cathode	4.2	0.600	1.15	2.85	1.35	VHF Amp.	Characteristics Same as Type 6BO7A. (4BO7A Designed for Series String TV Receivers.)	4BO7A	
4BS8	T-6½	Duodiode	9A J	Cathode	4.51	0.600	1.15	2.6	1.2	VHF Amp.	Characteristics Same as Type 6BS8. (4BS8 Designed for Series String TV Receivers.)	4BS8	
4BX8	T-6½	Duodiode	9A J	Cathode	4.51	0.600	1.4	4.9	2.6	VHF Amp.	Characteristics Same as Type 6BX8. (4BX8 Designed for Series String TV Receivers.)	4BX8	
4BZ6	T-5½	Pentode	7CM	Cathode	4.21	0.450	.015m	7.5	2.8	R-F Amp.	Characteristics Same as Type 6BZ6.	4BZ6	
4BZ7	T-6½	Duodiode	9A J-0-9	Cathode	4.21	0.600	1.15	2.5	1.35	VHF Amp.	Characteristics Same as Type 6BZ7. (4BZ7 Designed for Series String TV Receivers.)	4BZ7	
4BZ8	T-6½	Duodiode	9A J-0-9	Cathode	4.21	0.600	VHF Amp.	Characteristics Same as Type 6BZ8. (4BZ8 Designed for Series String TV Receivers.)	4BZ8	
4CB6	T-5½	Pentode	7CM-0-7	Cathode	4.21	0.450	.015	6.5	3.0	VHF Amp.	Characteristics Same as Type 6CB6. (4CB6 Designed for Series String TV Receivers.)	4CB6	
4CE5	T-5½	Pentode	7BD	Cathode	4.21	0.450	.03*	6.5	1.9*	VHF Amp.	Characteristics Same as Type 6CE5. (4CE5 Designed for Series String TV Receivers.)	4CE5	
4CS6	T-5½	Dual Control Heptode	7CH	Cathode	4.2	0.450	.07*	5.5*	7.0*	Sync. Sep.	Characteristics Same as Type 6CS6. (4CS6 Designed for Series String TV Receivers.)	4CS6	
4CX7	T-6½	Duodiode	9FC-0-9	Cathode	4.21	0.600	1.2	2.4	1.3	Amplifier	Characteristics Same as Type 6CX7. (4CX7 Designed for Series String TV Receivers.)	4CX7	
4CY5	T-5½	Tetrode	7EW-0-2,7	Cathode	4.51	0.300	.03	4.5	3.0	VHF Amp.	Characteristics Same as Type 6CY5. (4CY5 Designed for Series String TV Receivers.)	4CY5	
4DE6	T-5½	Pentode	7CM	Cathode	4.21	0.450	.015m	6.5	3.0	VHF Amp.	Characteristics Same as Type 4DE6. (4DE6 Designed for Series String TV Receivers.)	4DE6	
4DK6	T-5½	Pentode	7CM-0-7	Cathode	4.21	0.450	.02*	6.3*	1.9*	VHF Amp.	Characteristics Same as Type 6DK6. (4DK6 Designed for Series String TV Receivers.)	4DK6	
4DT6	T-5½	Gated Beam	7EN-0-0	Cathode	4.21	0.450	.02	Quad. F. M. Det.	Characteristics Same as Type 6DT6. (4DT6 Designed for Series String TV Receivers.)	4DT6	
4ES8	T-6½	Duodiode	9DE	Cathode	4.0	0.600	1.85	0.17	VHF Amp.	Characteristics Same as Type 6ES8. (4ES8 Designed for Series String TV Receivers.)	4ES8	
5A6	T-6½	Power Pent.	9L-0-0	Filament	5.0	0.930	0.1	8.5	9.5	Class B. Amp. Class C. Amp.	Characteristics Same as Type 6A6. (5A6 Designed for Series String TV Receivers.)	5A6	
5AM8	T-6½	Diode Pent.	9CY-0-0	Cathode	4.71	0.600	.015	6.0	3.4	Amp. Det.	Characteristics Same as Type 6AM8. (5AM8 Designed for Series String TV Receivers.)	5AM8	
5AN8	T-6½	Tri. Pentode	9DA-0-9	Cathode	4.71	0.600	.04m*	1.5*	2.0*	Tri. Amp. Pent. Amp.	Characteristics Same as Type 6AN8. (5AN8 Designed for Series String TV Receivers.)	5AN8	
5AQ5	T-5½	Beam Pent.	9BZ-0-0	Cathode	4.71	0.600	0.4*	8.0*	8.5*	Power Amp.	Characteristics Same as Type 6AQ5. (5AQ5 Designed for Series String TV Receivers.)	5AQ5	
5AS8	T-6½	Diode Pent.	9DS-0-7	Cathode	4.71	0.600	.02*	7.0*	2.4*	Tri. Amp.	Characteristics Same as Type 6AS8. (5AS8 Designed for Series String TV Receivers.)	5AS8	
5AT8	T-6½	Tri. Pentode	9DW-0-0	Cathode	4.71	0.600	1.5	4.7	1.0	Tri. Osc. Converter	Characteristics Same as Type 6AT8. (5AT8 Designed for Series String TV Receivers.)	5AT8	
5AV8	T-6½	Tri. Pentode	9DZ-0-7	Cathode	4.71	0.600	1.5*	2.0*	3.4*	Tri. Amp. Pent. Amp.	Characteristics Same as Type 6AV8. (5AV8 Designed for Series String TV Receivers.)	5AV8	
5AW4	T-12	Duodiode	5T-0-0	Filament	5.0	4.000	F-W Rect.	450 A.C. Volts Per Plate, RMS, 950 Ma. Output Current with Cap. Input to Filter. Peak Current = 750 Ma. Per Plate. 5AW4	5AW4	
5AX4GT	T-9	Duodiode	5T-0-0	Filament	5.0	2.950	F-W Rect.	350 A.C. Volts Per Plate, R.M.S., 150 Ma. D.C. Output Current. Condenser Input to Filter.	5AX4GT	
5AZ4	Lock-in	Duodiode	5T-L-0	Filament	5.0	2.000	F-W Rect.	300 A.C. Volts Per Plate, R.M.S., 150 Ma. D.C. Output Current. Choke Input to Filter.	5AZ4	
5B8	T-6½	Tri. Pentode	9EC-0-1	Cathode	4.71	0.600	.05m*	1.7*	6.0*	Tri. Amp. Converter	Characteristics Same as Type 6B8. (5B8 Designed for Series String TV Receivers.)	5B8	
5BE8	T-6½	Tri. Pentode	9EG-0-3	Cathode	4.71	0.600	1.8*	2.8*	1.5*	Tri. Osc.	Characteristics Same as Type 6BE8. (5BE8 Designed for Series String TV Receivers.)	5BE8	
5BK7A	T-6½	Duodiode	9A J-0-9	Cathode	4.71	0.600	1.8	3.0	1.0	VHF Amp.	Characteristics Same as Type 6BK7A. (5BK7A Designed for Series String TV Receivers.)	5BK7A	
5BO7A	T-6½	Duodiode	9A J-0-9	Cathode	5.61	0.450	1.2	2.6	1.2	VHF Amp.	Characteristics Same as Type 6BO7A. (5BO7A Designed for Series String TV Receivers.)	5BO7A	
5BR8	T-6½	Triode Pentode	9FA	Cathode	4.71	0.600	.008	5.0	3.5	Osc. Mixer	Characteristics Same as Type 6BR8. (5BR8 Designed for Series String TV Receivers.)	5BR8	
5BT8	T-6½	Duodi. Pent.	9FE	Cathode	4.71	0.600	.04m*	7.0*	2.3*	Amp. Det.	Characteristics Same as Type 6BT8. (5BT8 Designed for Series String TV Receivers.)	5BT8	
5BW8	T-6½	Duodi. Pent.	9FH	Cathode	4.71	0.600	.02m*	4.8*	2.6*	R-F or I-F Amplifier	Characteristics Same as Type 6BW8. (5BW8 Designed for Series String TV Receivers.)	5BW8	
5BZ7	T-6½	Duodiode	9A J-0-9	Cathode	5.61	0.450	1.2	2.5	1.35	VHF Amp.	Characteristics Same as Type 6BZ7. (5BZ7 Designed for Series String TV Receivers.)	5BZ7	
5CG4	T-9	Duodiode	5L	Cathode	5.0	2.0	F-W Rect.	350 A.C. Volts Per Plate, RMS, 125 Ma. Max. D.C. Output Current.	5CG4	
5CG8	T-6½	Tri. Pentode	9GF	Cathode	4.71	0.600	.02	4.8	1.6	Osc. Mixer	Characteristics Same as 6CG8 (5CG8 Designed for Series String TV Receivers.)	5CG8	
5CL8	T-6½	Tri. Tetrode	9FX	Cathode	4.71	0.600	1.8	2.7	1.2	Osc. Mixer	Characteristics Same as Type 6CL8. (5CL8 Designed for Series String TV Receivers.)	5CL8	
5CL8A	T-6½	Tri. Tetrode	9FX	Cathode	4.71	0.600	1.8	2.7	1.2	VHF Osc. VHF Amp.	Characteristics Same as Type 6CL8A. (5CL8A Designed for Series String TV Receivers.)	5CL8A	
5CM6	T-6½	Beam Pent.	9CK	Cathode	4.71	0.600	0.7	8.0	8.5	Power Amp.	Characteristics Same as Type 6CM6. (5CM6 Designed for Series String TV Receivers.)	5CM6	
5CM8	T-6½	Tri. Pentode	9FZ	Cathode	4.71	0.600	.04m	1.9	1.6	Class A1 Amp.	Characteristics Same as 6CM8. (5CM8 Designed for Series String TV Receivers.)	5CM8	
5CQ8	T-6½	Tri. Tetrode	9GE	Cathode	4.71	0.600	1.8	2.7	1.2	VHF Tri. Osc. VHF Pent. A.	Characteristics Same as Type 6CQ8. (5CQ8 Designed for Series String TV Receivers.)	5CQ8	
5CR8	T-6½	Tri. Pentode	9GJ	Cathode	4.71	0.600	1.6*	2.0*	1.4*	Tri. Amp. Pent. Amp.	Characteristics Same as Type 6CR8. (5CR8 Designed for Series String TV Receivers.)	5CR8	


5CZ5	T-6½	Beam Pent.	91N	Cathode	4.71	0.600	0.4°	6.0°	6.0°	Vert. Defl. Amp.	Characteristics Same as Type 6CZ5. (5CZ5 Designed for Series String TV Receivers).			5CZ5
5DH8	T-6½	Tri. Pentode	9EG	Cathode	5.21	0.600	1.6°	2.4°	1.4°	390	250	3.8	4,400	5DH8
5EA8	T-6½	Tri. Pentode	9AE	Cathode	4.71	0.600	1.7	3.2	1.1	Tri. VHF Amp. Pent. VHF Amp.	125	13.5	8,400	5EA8
							.03m°	6.5°	2.2°	56	56	120,000		
							.01	5	3.4			53		

(1) Values are given shielded unless marked with (*). (3) Has special mechanical end/or life characteristics.
 (2) Converter tube impedances given are signal (4) Average Contact potential bias developed across specified grid resistor.
 (5) Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

□ Per Tube or Section.
 △ Plate and Target Supply Voltage.
 † Maximum Transconductance.
 ‡ Maximum Signal.

□ Applied through 20,000 ohms.
 △ Conversion Transconductance.
 ‡ Approximate.
 † Triode Operation.

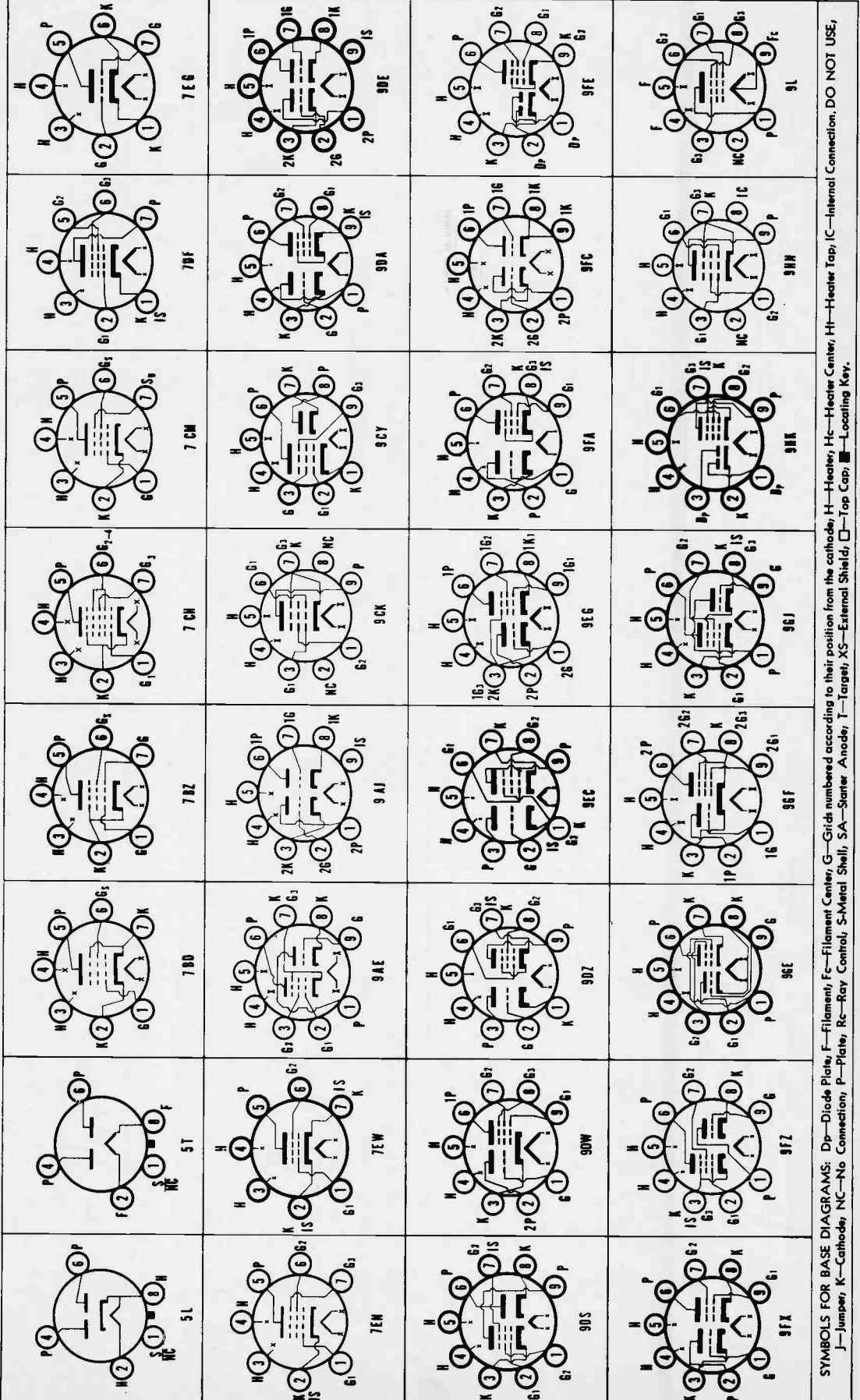⊥ Plate to Plate.
 ⊕ Cathode Resistor (ohms).




SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter; Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1)† Capacitances in μ d.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milli-watts	Type
	Bulb Size or Style	Classes	Base	Diag.	Type	Volts	Amps.												
5J6	T-5½	Duodiode	7BF-0-0		Cathode	4.71	0.600	1.5	2.6	1.6	2.6	1.0						5J6	
3R4GY	ST-16	Duodiode	5T-0-0		Filament	5.0	2.000	1.5										3R4GY	
3R4GYA	T-12	Duodiode	5T-0-0		Filament	5.0	2.000	1.5										3R4GYA	
5T4	Metal	Duodiode	5T-0-0		Filament	5.0	2.000											5T4	
5T8	T-6½	Triode	9E-0-3A7		Cathode	4.71	0.600	1.7	1.7	2.4								5T8	
5U4G	ST-16	Duodiode	5T-0-0		Filament	5.0	3.000											5U4G	
5U4GA	T-11	Duodiode	5T-0-0		Filament	5.0	3.000											5U4GA	
5U4GB	T-12	Duodiode	5T-0-0		Filament	5.0	3.000											5U4GB	
5U4WG(3)	T-12	Duodiode	5T-0-0		Filament	5.0	3.000											5U4WG(3)	
5U8	T-6½	Tri. Pentode	9AE-0-7		Cathode	4.71	0.600	1.8	2.5	3.0								5U8	
								.006m											
5V3	T-12	Duodiode	5T-0-0		Filament	5.0	3.800											5V3	
5V4G	ST-14	Duodiode	5L-0-0		Cathode	5.0	2.000											5V4G	
5V4GA	T-12	Duodiode	5L-0-0		Cathode	5.0	2.000											5V4GA	
5V6GT	T-9	Beam Pent.	7S-0-0		Cathode	4.71	0.600	0.7*	9.0*	7.5*								5V6GT	
5W4	Metal	Duodiode	5T-1-0		Filament	5.0	1.500											5W4	
5W4GT	T-9	Duodiode	5T-0-0		Filament	5.0	2.000		2.6	4.5	1.0							5W4GT	
5X3	ST-14	Duodiode	4C-0-0		Filament	5.0	2.000											5X3	
5X4G	ST-16	Duodiode	5Q-0-0		Filament	5.0	3.000											5X4G	
5X4GA	T-12	Duodiode	5Q-0-0		Filament	5.0	3.000											5X4GA	
5X8	T-6½	Tri. Pentode	9AK-0-0		Cathode	4.71	0.600	1.4	2.6	4.5	1.0							5X8	
5Y2GT	T-9	Duodiode	5T-0-0		Filament	5.0	2.000											5Y2GT	
5Y3GA	T-12	Duodiode	5O-0-0		Filament	5.0	2.000											5Y3GA	
5Y4GT	T-12	Duodiode	5O-0-0		Filament	5.0	2.000											5Y4GT	
5Z3	ST-16	Duodiode	4C-0-0		Filament	5.0	3.000											5Z3	
5Z4	Metal	Duodiode	5L-1-0		Cathode	5.0	2.000											5Z4	
5Z4GT	T-9	Duodiode	5L-0-0		Cathode	5.0	2.000											5Z4GT	
6A3	ST-16	Power Triode	4D-0-0		Filament	6.3	1.000	16.0	7.0	5.0								6A3	
6A4/LA	ST-14	Power Pent.	5B-0-0		Filament	6.3	0.300											6A4/LA	
6A5G	ST-16	Triode	6T-0-0		Cathode	6.3	1.250											6A5G	
6A6	ST-14	Duodiode	7B-0-0		Cathode	6.3	0.800											6A6	
6A7, 6A7S	ST-12	Heptode	7C-0-0		Cathode	6.3	0.300	0.3	8.5	9.0								6A7, 6A7S	
6A8	Metal	Heptode	8A-1-0		Cathode	6.3	0.300	0.6	12.0	12.0								6A8	
6A8G	ST-12	Heptode	8A-0-0		Cathode	6.3	0.300	0.26	9.5	9.5								6A8G	
6A8GT	T-9	Triode	8A-1-0		Cathode	6.3	0.300	0.26	9.5	9.5								6A8GT	
6A8A	T-5½	Triode	5CE-0-2		Cathode	6.3	0.150	1.5	2.2	1.4								6A8A	
6AB5/GN5	T-9	Electron Ray	6R-0-0		Cathode	6.3	0.150											6AB5/GN5	
6AB6G	ST-12	Duodiode	7AU-0-0		Cathode	6.3	0.300											6AB6G	
6AB7	Metal	Pentode	8N-1-1		Cathode	6.3	0.450	.015m	8.0	5.0								6AB7	
6AC5GT	T-9	Triode	6Q-0-0		Cathode	6.3	0.400											6AC5GT	
6AC6GT	T-9	Duodiode	7W-0-0		Cathode	6.3	1.100											6AC6GT	
6AC7	Metal	Pentode	8N-1-1		Cathode	6.3	0.450	.015m	11.0	5.0								6AC7	
6AD4	T-3	Triode	8DK-0-0		Cathode	6.3	0.150	0.7	1.9	3.2								6AD4	
6AD5/GT	ST-12, T-9	Triode	6O-0-0		Cathode	6.3	0.300	3.3*	4.1*	3.9*								6AD5/GT	
6AD6G	T-9	Electron Ray	7AG-0-0		Cathode	6.3	0.150											6AD6G	
6AD7G	ST-14	Tri. Pentode	8AY-0-0		Cathode	6.3	0.850											6AD7G	
6AE5GT	T-9	Triode	6Q-0-0		Cathode	6.3	0.300											6AE5GT	
6AE6G	ST-12	Duo Plate Triode	7AH-0-0		Cathode	6.3	0.150											6AE6G	

6AE7GT	1-9	Diode	7AX-0-0	Cathode	6.3	0.500	2.5	3.0	1.8	Amplifier	13.5	10.0	4,450	3,000	14	6AE7GT
6AF3	T-6½	Diode	9CB	Cathode	6.3	1.200	2.5	3.0	1.8	Amplifier	950	10.0	4,450	3,000	14	6AE7GT
6AF4	T-5½	Triode	7DK	Cathode	6.3	0.225	1.9	2.2	1.4	T.V. Dampner UHF Osc.	Maximum Peak Inverse Plate Voltage = 4,500 Volts. Maximum D.C. Plate Current = 185 Ma. 10,000 Ohms.	10.0	4,450	3,000	14	6AE7GT
6AF5G	ST-12	Triode	6Q-0-0	Cathode	6.3	0.300	2.2	2.2	1.4	Indicator	100	10.0	4,450	3,000	14	6AE7GT
6AF6G	T-9	Twin Elec. Ray	7AG-0-0	Cathode	6.3	0.150	2.2	2.2	1.4	Indicator	180	18.0	4,900	1,500	7.4	6AF5G
					6.3	0.150	2.2	2.2	1.4	Indicator	135§ (Ray Control Vols = Approx. 60 for 0° Shadow, Approx. Zero Vols for 100° Shadow.) 135§ (Ray Control Vols = Approx. 81 for 0° Shadow, Approx. Zero Vols for 100° Shadow.)	100	4,900	1,500	7.4	6AF6G

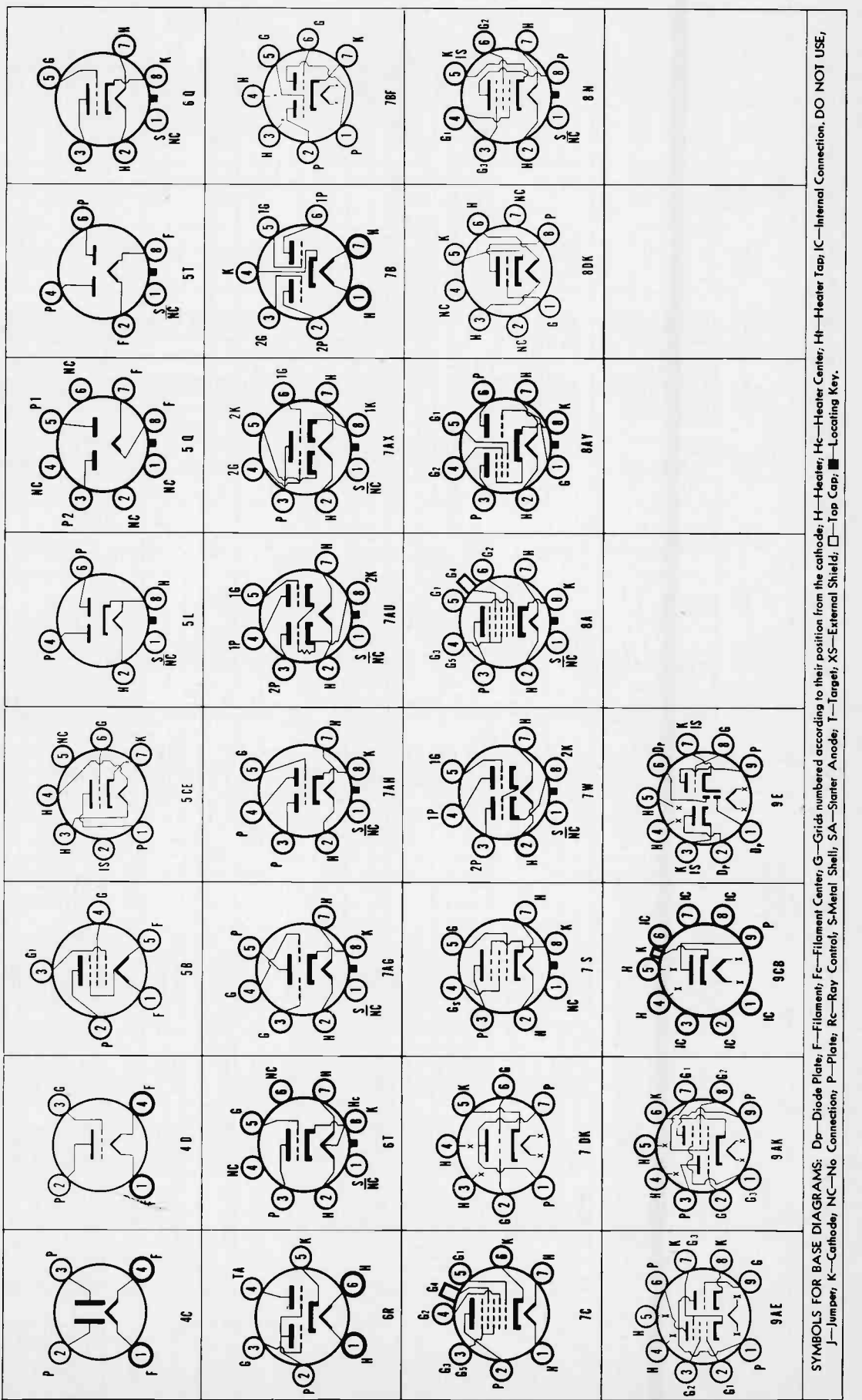(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer Output, specified grid resistor.
 † Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)
 ‡ Per Tube or Section.
 § Plate and Target Supply Voltage.
 ¶ Applied through 20,000 ohms.
 * Conversion Transconductance.
 †† Triode Operation.
 ‡‡ Plate to Plate.
 ††† Cathode Resistor (ohms).



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate, F—Filament, G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection. DO NOT USE;
 J—Jumper; K—Cathode, NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Tap Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (*) Capacitances in μ fd.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohm Load for Stated Power Output	Power Output Milli-watts	Type	
	Bulb Size or Style	Class	Basing Diags.	Type	Volts	Amps.	Cgp.													Cin.
6AG5	T-5½	Pentode	7BD-0-2A7	Cathode	6.3	0.300	.083m	6.1	2.3	100 125 150	4.5 7.3 6.5	1.4 2.1 3.0	600,000 300,000 800,000	4,500 5,100 5,000	6AG5	
6AG7	Metal	Pentode	8Y-1-3	Cathode	6.3	0.650	.06	13.0	7.5	300	30	7.0	130,000	11,000	10,000	3,000	6AG7		
6AH4GT	T-9	Triode	8EL	Cathode	6.3	0.750	4.4*	7.0*	1.7*	300	30	3.0	1,780	4,500	8	6AH4GT	
6AH5G	SI-16	Beam Pent.	6AP-0-0	Cathode	6.3	0.900	250	33	6AH5G	
6AH6V	T-5½	Pentode	7CC-0-0	Cathode	6.3	0.450	.09m	10.0	3.6	300	160	2.5	330,000	5,000	4,800	10,800	6AH6V	
6AH7GT	T-9	Duodiode	8BE-0-0	Cathode	6.3	0.300	.035m	10.0	3.6	150	160	12.5	500,000	9,000	40	6AH7GT	
6AJ4	T-6½	Triode	9BX	Cathode	6.3	0.925	195	68*	16	4,900	10,000	42	6AJ4	
6AJ5	T-5½	Pentode	7BD-0-0	Cathode	6.3	0.175	.08	4.0	2.8	98	1.0	1.0	100,000	2,500	6AJ5	
6AJ7	Metal	Pentode	8N-1-1	Cathode	6.3	0.450	300	160	10.0	1 Meg.†	9,000	9,000	6AJ7	
6AK4	T-3	Triode	8DK	Cathode	6.3	0.125	1.3	2.2	2.2	300	680*	5,300	3,800	20	6AK4	
6AK5	T-5½	Pentode	7BD-0-2A7	Cathode	6.3	0.175	.02	4	2.8	180	180	7.5	300,000	5,000	1,700	6AK5	
6AK6	T-5½	Power Pent.	7BK-0-0	Cathode	6.3	0.150	0.12*	3.6*	4.2*	180	150	2.5	200,000	2,300	10,000	1,100	6AK6	
6AK7	Metal	Power Pent.	8Y-1-3	Cathode	6.3	0.650	.06	13.0	7.5	300	30	7.0	130,000	11,000	6AK7	
6AL5	T-5½	Duodiode	6BT-0-6	Cathode	6.3	0.300	117 A.C. Volts Per Plate, RMS; 9 Ma. Output Current. 300 Ohms Min. Effective Plate Supply Impedance.	300	30.0	6AL5	
6AL6G	SI-16	Beam Pent.	6AM-0-0	Cathode	6.3	0.900	315†	6AL6G	
6AL7GT	T-9	Electron Ray	8CH-0-0	Cathode	6.3	0.150	Grid Voltage for Fluorescent C.O. = -7.0 (App.). Deflection Sens = 1.0 MM. Per Volt (App.).	10	8,700	9,800	85	6AL7GT	
6AM4	T-6½	Triode	9BX	Cathode	6.3	0.925	2.8	4.6	0.16	200	100*	6AM4	
6AM5	T-5½	Pentode	7CH-0-0	Cathode	6.3	0.300	250	13.5	2.4	130,000	2,600	16,000	1,400	6AM5	
6AM6	T-5½	Pentode	7DB-0-6	Cathode	6.3	0.300	.01	10.0	3.25	250	9.2	2.5	1 Meg.†	7,500	6AM6	
6AM8	T-4½	Diode Pent.	9CY	Cathode	6.3	0.450	.015*	6.5*	2.6*	125	56*	3.2	0.3 Meg.	7,800	6AM8	
6AN4	T-5½	Triode	7DK	Cathode	6.3	0.925	1.7*	2.9*	0.25*	200	100*	13	7,000	10,000	70	6AN4	
6AN5	T-5½	Power Pent.	7BD-0-0	Cathode	6.3	0.450	.075	9.0	4.8	180	6.0	12.0	12,500	8,000	2,500	1,300	6AN5	
6AN6	T-5½	Quadriple Di.	7BJ-0-0	Cathode	6.3	0.200	75 Volts RMS Per Plate, 8 Ma. D.C. Output Per Plate.	6AN6	
6AN7	T-6½	Tri. Hexode	9Q-0-3	Cathode	6.3	0.830	0.1	3.8	9.2	250	6AN7	
6AN8	T-6½	Tri. Pentode	9DA	Cathode	6.3	0.450	1.5*	2.0*	0.26*	200	6AN8	
6AN8A	T-5½	Beam Pent.	7BZ-0-0	Cathode	6.3	0.450	.04m*	7.0*	0.24*	125	56*	125	0.17 Meg. m	7,800	6AN8A	
6AG5	T-5½	Beam Pent.	7BZ-0-0	Cathode	6.3	0.450	0.17	8.0	11.0	250	12.5	230	45.0	4,100	5,000	4,500	6AG5	
6AG5A	T-5½	Duodiode Tri.	7BT-0-0	Cathode	6.3	0.150	1.8	1.7	1.5	100	1.0	0.8	61,000	1,150	70	5,500	2,000	6AG5A
6AG6	T-9	Duodiode Tri.	8CK-0-0	Cathode	6.3	0.300	2.8	2.3*	1.5*	250	3.0	50,000	1,300	70	6AG6	
6AG7GT	T-9	Duodiode Tri.	8CK-0-0	Cathode	6.3	0.300	2.8	2.3*	1.5*	250	2.0	44,000	1,600	70	6AG7GT	
6AR5	T-5½	Power Pent.	6CC-0-0	Cathode	6.3	0.400	250	16.5	5.7	65,000	2,400	7,000	3.2	6AR5	
6AR6	T-11	Pentode	6EO-0-0	Cathode	6.3	1.200	0.55*	11.0*	7.0*	250	18.0	3.2	68,000	2,300	7,600	3.4	6AR6	
6AS5	T-5½	Beam Pent.	7CV-0-0	Cathode	6.3	0.800	0.6*	12.0*	6.2*	150	8.5	2.0	11,000	3,200	4,500	2,800	6AS5	
6AS6	T-5½	Pentode	7CM-0-0	Cathode	6.3	0.175	.02	4.0	3.0	190	2.0	3.5	6AS6	
6AS7G	SI-16	Duo. Pwr. Tri.	8BD-0-0	Cathode	6.3	0.500	135	250*	112	980	7,000	2	6AS7G	
6AS8	T-6½	Diode Pent.	9DS-0-7	Cathode	6.3	0.450	.02*	7.0*	2.4*	200	180*	9.5	300,000	6,200	6AS8	
6A16	T-5½	Duodiode Tri.	7BT-0-0	Cathode	6.3	0.300	2.1*	2.3*	1.1*	100	3.0	51,000	1,300	70	6A16	
6A18	T-6½	Tri. Pentode	9DW-0-0	Cathode	6.3	0.450	1.5	2.4	1.0	100	58,000	1,800	40	6A18	
6A18A	T-9	Diode	4CG-0-0	Cathode	6.3	1.800	.016m	4.7	1.6	250	200*	1.6	750,000	4,600	6A18A	
6AU4GT	T-9	Diode	4CG-0-0	Cathode	6.3	1.800	T.V. Damper. P.I.V. = 4,500 Volts Abs. Max. D.C. Plate Current = 175 Ma. Max.	6AU4GT	
6AU5GT	T-9	Beam Pent.	6CK-0-0	Cathode	6.3	1.250	0.5*	11.3*	7.0*	T.V. Damper. P.I.V. = 4,500 Volts Abs. Max. D.C. Plate Current = 190 Ma. Max.	6AU5GT	
6AU6	T-5½	Pentode	7BK-0-2	Cathode	6.3	0.300	.0035*	5.5*	5.0*	100	150*	5.0	500,000	3,900	6AU6	
6AU6A	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.3	0.600	.046*	2.8*	0.32*	250	100*	3.0	100*	125	6AU6A	
6AU8	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.3	0.600	.046*	7.0*	2.6*	150	150*	17.0	7,900	5,600	40	6AU8	

(1) Values are given shielded unless marked with (*).
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output.
 (3) Has special mechanical and/or life characteristics.
 (4) Average contact potential bias developed across specified grid resistor.
 † Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)
 ‡ Per Tube or Section.
 § Plate and Target Supply Voltage.
 ¶ Maximum Signal.
 * Applied through 20,000 ohms.
 † Transconductance.
 ‡ Tube Operation.
 § Plate to Plate.
 ¶ Approximate.
 †† Maximum Signal.
 ‡†† Tube Operation.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS


Type	Construction		Emitter		Note (1) (2) Capacitance in μ f.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Ohm Load for Stated Power Output	Unde- r- tor- ted Power Output Milli- watts	Type
	Bulb Size or Style	Class	Beam Pent.	Tri. Pentode	Basins Diag.	Type	Volts												
6AUBA	T-6½	Tri. Pentode	9DX	Cathode	6.31	0.600	2.2*	0.34* 7.5*	150 ^m 200 300	82 ^m 125	9.5 17	3.4 100,000	5,300 8,000	40	40	40	6AUBA		
6AV5GT	T-9	Beam Pent.	6CK-0-0	Cathode	6.3	1.900	Instantaneous Plate Knee Voltage = 5,500 Volts. Maximum D-C Plate Current = 110 Ma. Maximum Peak Positive Pulse Voltage = 5,500 Volts. Maximum Screen Dissipation = 9.5 Watts. Maximum Plate Dissipation = 11 Watts. Maximum Screen Dissipation = 9.5 Watts.	6AV5GT		
6AV5GA	T-11 or T-19	Beam Pentode	6CK-0-0	Cathode	6.3	1.900	0.5*	14.0*	60 90 120	0 9.0 1.0	9.5 150 150	9.5 9.1 9.1	80,000 80,000 80,000	6AV5GA		
6AV6	T-5½	Duodiode Tri.	7BT-0-0	Cathode	6.3	0.300	2.1	2.3	9.5 100	0 1.0	9.5 0.5	9.5 0.5	80,000 1,950	100 100	100	100	6AV6		
6AW7GT	T-9	Duodiode Tri.	8CQ-1-0	Cathode	6.3	0.300	200 180 100	2.0 1.0 0	4.0 13.0 1.4	3.5 3.5 1.4	17,500 270,000 17,500	6AW7GT		
6AW8	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.31	0.600	2.2	3.4 1.0 1.7 10.0	200 180 150	2.0 1.0 1.0	4.0 13.0 1.4	3.5 3.5 1.4	17,500 270,000 17,500	6AW8		
6AW8A	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.31	0.600	2.2	3.4 1.0 1.7 10.0	200 180 150	2.0 1.0 1.0	4.0 13.0 1.4	3.5 3.5 1.4	17,500 270,000 17,500	6AW8A		
6AX4GT	T-9	Diode	4CG	Cathode	6.3	1.800	Instantaneous Plate Knee Voltage = 5,500 Volts. Maximum D-C Plate Current = 110 Ma. Maximum Peak Positive Pulse Voltage = 5,500 Volts. Maximum Screen Dissipation = 9.5 Watts. Maximum Plate Dissipation = 11 Watts. Maximum Screen Dissipation = 9.5 Watts.	6AX4GT		
6AX5GT	T-9	Duodiode	6S-0-0	Cathode	6.3	1.200	P.I.V. = 4,400 Volts Max., D-C Plate Current = 125 Ma. Max. 350 A.C. Volts Per Plate, R.M.S., 125 Ma. D.C. Output. Condenser Input to Filter. 450 A.C. Volts Per Plate, R.M.S., 125 Ma. D.C. Output. Choke Input to Filter.	6AX5GT		
6AX6G	5T-14	Duodiode	7Q-0-0	Cathode	6.3	2.500	350 A.C. Volts Per Plate, R.M.S., 250 Ma. Output. Condenser Input to Filter. Characteristics Same as Type 13AX7. (6AX7 Designed for Series String TV Receivers).	6AX6G		
6AX7	T-6½	Duodiode	9A-0-0	Cathode	6.3/3.151	0.600/0.300	1.7*	1.6*	6AX7		
6AX8	T-6½	Tri. Pentode	9AE-0-7	Cathode	6.3	0.450	1.8	9.5	150 250	56 ^m 180	18 110	3.5 3.5	5,000 400,000	40 4,900	40	40	6AX8		
6AZ5	T-3	Duodiode	8DF-0-4	Cathode	6.3	0.150	Plate Supply Voltage = 50 Volts, RMS, Each Plate. DC Output Current = 4 Ma. Each Plate. Capacitor Input to Filter.	6AZ5		
6AZ8	T-6½	Tri. Pentode	9ED-0-5	Cathode	6.3	0.450	1.7*	9.0*	200 300	6 180	13.0 9.5	3.0 300,000	3,300 6,300	19	19	6AZ8			
6B3	T-6½	Diode	9BD-0-0	Cathode	6.3	1.200	Maximum Peak Inverse Plate Voltage = 4,400 Volts. Maximum D.C. Plate Current = 150 Ma. Characteristics Same as Type 6A3.	6B3		
6B4G	5T-16	Triode	5S-0-0	Filament	6.3	1.000	16.0	7.0	6B4G		
6B5	5T-14	Duodiode	6AS-0-0	Cathode	6.3	0.800	Characteristics Same as Type 6B3.	6B5		
6B6G	5T-12	Duodiode Tri.	7V-0-0	Cathode	6.3	0.300	1.7	1.7	250	9.0	9.0	0.9	91,000	1,100	100	100	6B6G		
6B7	5T-19	Duodi. Pent.	7D-0-6	Cathode	6.3	0.300	6B7		
6B7S	5T-19	Duodi. Pent.	7D-6-6	Cathode	6.3	0.300	6B7S		
6B8	Metal	Duodi. Pent.	8E-1-1	Cathode	6.3	0.300	0.05m	6.0	6B8		
6B8G	5T-19	Duodi. Pent.	8E-0-8	Cathode	6.3	0.300	0.1m	3.6	6B8G		
6B8GT	5T-19	Duodi. Pent.	8E-1-8	Cathode	6.3	0.300	6B8GT		
6BA5	T-3	Pentode	8DY-0-0	Cathode	6.3	0.150	0.65	3.4	100 250	68 ^m 68 ^m	10.8 11.0	4.4 4.2	350,000 1,0 Merg.	4,300 4,400	6BA5		
6BA6	T-5½	Pentode	7BK-0-2	Cathode	6.3	0.300	0.035m	5.5*	6BA6		
6BA7	T-6½	Heptode	8CT-0-6A8	Cathode	6.3	0.300	0.19m	9.5	100 250	1.0 1.0	100 3.8	10.2 10.0	500,000 950A	6BA7		
6BA8	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.31	0.600	2.2	2.7	200 200	8.0 180	8.0 13.0	6,700 400,000	2,700 9,000	18	18	6BA8			
6BA8A	T-6½	Tri. Pentode	9DX-0-6	Cathode	6.31	0.600	2.2	2.7	200 200	8.0 180	8.0 13.0	6,700 400,000	2,700 9,000	18	18	6BA8A			
6BC5	T-5½	Pentode	7BD-0-2A7	Cathode	6.3	0.300	0.02	6.6	250 180 100	89 ^m 320 ^m 180	6.0 6.0 4.7 1.4	9,000 4,000 600,000	40 40 42	40	40	6BC5		
6BC7	T-6½	Triode Diode	9AX-0-3	Cathode	6.3	0.450	6BC7		
6BC8	T-6½	Duodiode	9A-1-0-9	Cathode	6.3	0.400	1.4	2.5	High Permeance Diode	6BC8		
6BD4	T-12	Beam Triode	8FU-0-0	Cathode	6.3	0.600	1.0*	3.8*	30,000 Max. D.C. Plate Volts. 125 Max. D.C. Grid Volts. 1.5 Ma. Max. D.C. Plate Current.	6BD4		
6BD5GT	T-9	Beam Pent.	6CK-0-0	Cathode	6.3	0.900	6BD5GT		
6BD6	T-5½	Pentode	7BK-0-2	Cathode	6.3	0.300	0.04	4.3	6BD6		
6BD7	T-6½	Duodiode Tri.	9Z-0-7	Cathode	6.3	0.930	1.3	9.4	6BD7		
6BE6	T-5½	Heptode	7CH-0-0	Cathode	6.3	0.300	0.3*	7.0*	6BE6		
6BE8	T-6½	Tri. Pentode	9EG	Cathode	6.3	0.450	1.8*	2.9*	6BE8		
6BE8A	T-6½	Tri. Pentode	9EG	Cathode	6.31	0.450	0.4*	4.4*	6BE8A		

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (7) Capacitance in $\mu\mu\text{f}$.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Output Power Watts	Type	
	Bulb Size or Style	Class	Beam Diag.	Type	Volts	Amps.	Csp.												Cin.
68G7	T-3	Duobottle	8DG-0-0	Cathode	6.3	0.300	1.5	2.0	1.6	100	8.0	7,000 \downarrow	4,800	35	68G7	
							2.0	2.0	2.0	100	8.0	7,000 \downarrow	4,800	35		
68H6	T-5 1/2	Pentode	7CM-0-7	Cathode	6.3	0.150	.0035m*	5.4*	4.4*	100	3.6	0.7 Meg. \downarrow	3,400	68H6	
							.046*	7.0*	3.8*	150	9.5	1.4 Meg. \downarrow	4,500		
68H8	T-6 1/2	Tri. Pentode	9DX-0-6	Cathode	6.3	0.600	300	15.0	150,000	7,000	68H8	
							300	15.0	150,000	7,000		
68J5	T-5 1/2	Pentode	6CH	Cathode	6.3	0.640	250	5.0	40,000	10,500	450	7,000	4,000	68J5
68J6	T-5 1/2	Pentode	7CM-0-7	Cathode	6.3	0.150	.0035m*	4.5*	5.0*	100	9.0	350,000	3,650	68J6	
68J7	T-6 1/2	Triode	9AX-0-3	Cathode	6.3	0.450	100	9.0	350,000	3,650	68J7	
68J8	T-6 1/2	Duobottle Tri.	9ER-0-0	Cathode	6.3	0.600	2.6*	2.8*	0.31*	90	4,700	2,800	88	68J8	
							90	4,700	2,800	88		
68K4	T-12	Beam Triode	8GC-0-0	Cathode	6.3	0.900	0.3*	2.6*	1.0*	250	3.5	0.1 Meg. \downarrow	8,500	6,500	3,500	68K4
68K5	T-6 1/2	Beam Pent.	9BQ-0-0	Cathode	6.3	1.200	0.6*	13.0*	5.0*	250	5.0	80,000	1,250	100	68K5	
68K6	T-5 1/2	Duobottle Tri.	7B1-0-2	Cathode	6.3	0.300	100	1.0	63,500	1,600	100	68K6	
68K7	T-6 1/2	Duobottle	9AJ-0-9	Cathode	6.3	0.450	1.9	3.0	1.1	100	1.2	6,100	6,100	37	68K7	
68K7A	T-6 1/2	Duobottle	9AJ-0-9	Cathode	6.3	0.450	1.8*	3.0*	1.0*	100	1.2	6,100	6,100	37	68K7A	
68K7B	T-6 1/2	Duobottle	9AJ-0-9	Cathode	6.3	0.450	1.8*	3.0*	0.9*	100	1.2	6,100	6,100	37	68K7B	
68L4	T-12	Diode	8GB-0-0	Cathode	6.3	3.000	150	56	4,600	9,300	43	68L4	
68L7G1	T-9	Duobottle	8BD	Cathode	6.3	1.500	6.0*	4.2*	0.9*	250	9	7,150	2,800	88	68L7G1	
68L7G1A	T-9	Duobottle	8BD	Cathode	6.3	1.500	6.0*	4.6*	0.9*	250	9	7,150	2,800	88	68L7G1A	
							250	9	7,150	2,800	88		
68L8	T-6 1/2	Tri. Pentode	9DC-0-7	Cathode	6.3	0.450	.025*	5.5*	3.8*	100	2.0	400,000	5,000	20	68L8	
68M8	T-6 1/2	Tri. Pentode	9EX-0-2	Cathode	6.3	0.780	4.0*	2.7*	4.0*	170	10.0	400,000	6,200	47	68M8	
							0.3*	9.3*	8.0*	200	35.0	400,000	6,200	47		
68N4	T-5 1/2	Triode	7EG	Cathode	6.3	0.300	1.2	3.2	1.4	150	3.0	20,000	6,400	9.5	68N4	
68N6	T-5 1/2	Triode	7DF-0-1	Cathode	6.3	0.300	150	3.0	20,000	6,400	9.5	68N6	
68N7	T-6 1/2	Duobottle	9AJ-0-0	Cathode	6.3	0.750	0.7	1.4	0.3	190	1.0	14,000	2,000	28	68N7	
68N8	T-6 1/2	Duobottle Tri.	9ER	Cathode	6.3	0.600	2.5*	3.6*	0.25*	250	1.5	91,000	3,500	75	68N8	
							250	1.5	91,000	3,500	75		
68O5	T-6 1/2	Beam Pent.	9CV	Cathode	6.3	0.760	0.5m*	10.8*	6.5*	28,000	2,500	68O5	
68O6G	5T-12	Beam Pent.	6AM-0-0	Cathode	6.3	1.300	0.6*	15.0*	7.0*	14,500	5,900	68O6G	
68O6GA	1-11	Beam Pent.	6AM-0-0	Cathode	6.3	1.300	0.6*	15.0*	7.0*	14,500	5,900	68O6GA	
68O6GT	1-9	Beam Pent.	6AM-0-0	Cathode	6.3	1.300	0.6*	15.0*	7.0*	14,500	5,900	68O6GT	
68O7	T-6 1/2	Duobottle	9AJ-0-9	Cathode	6.3	0.400	1.15	2.55	1.30	150	3.0	5,800	6,000	35	68O7	
68Q7A	T-6 1/2	Duobottle	9AJ	Cathode	6.3	0.400	1.2	2.6	1.3	150	3.0	5,800	6,000	38	68Q7A	
68R8	T-6 1/2	Triode	9FA	Cathode	6.3	0.450	1.8	2.5	1.0	150	56	5,000	8,500	40	68R8	
							.008	5.0	3.5	150	56	5,000	8,500	40		
68R8A	T-6 1/2	Tri. Pentode	9FA	Cathode	6.3	0.450	1.8	2.5	1.0	150	56	5,000	8,500	40	68R8A	
							.008	5.0	3.5	150	56	5,000	8,500	40		
68S8	T-6 1/2	Duobottle	9AJ	Cathode	6.3	0.400	1.15	2.6	1.2	100	1.0	5,000	7,900	36	68S8	
68T6	T-5 1/2	Duobottle Tri.	7B1-0-2	Cathode	6.3	0.300	250	3.0	54,000	1,300	70	68T6	
68T8	T-6 1/2	Duodi. Pent.	9FE	Cathode	6.3	0.450	.04m*	7.0*	2.3*	200	180	300,000	6,200	68T8	
68U4	T-12	Triode	8GC	Cathode	6.3	0.450	.03*	2.0*	8.0*	25,000	8.4	8.2 Meg. \downarrow	185	1,515	68U4	
68U6	T-5 1/2	Duobottle Tri.	7B1-0-2	Cathode	6.3	0.300	100	3.0	11,000	1,900	16.5	10,000	300	68U6
68U8	T-6 1/2	Duo Pentode	9FC-0-2	Cathode	6.3	0.300	G3 to P	6.0	3.0	100	0 Grid 1	180 Gr. 3	150 Gr. 1	Grid #3 Volts = -4.5	Grid #1 Volts = -2.3	68U8	
68V8	T-6 1/2	Duobottle Tri.	9FJ-0-0	Cathode	6.3	0.600	2.0*	3.6*	0.4*	200	330	5,900	5,600	33	68V8	
68W4	T-6 1/2	Duobottle	9DJ	Cathode	6.3	0.900	385 A.C. Volts Per Plate, RMS, 100 Ma. Output Current. Capacitor Input to Filter.	68W4	

68W8	1-6 1/2	Duodi. Pent.	9HK	Cathode	6.31	0.450	.02m*	4.8*	2.6*	R-F or L-F Amplifier	250	68m	110	10.0	3.5	250,000	5,200	68W8
68X7G1	T-9	Duodiode	8BD	Cathode	6.3	1.500	4.2	3.4	3.4	Maximum Peak Positive Pulse Plate Volts = 2,000 Volts. Maximum D.C. Cathode Current = 60 Ma.	68X7G1
68X8	T-6 1/2	Duodiode	9AJ	Cathode	6.3	0.400	1.4	4.9	2.6	Maximum Plate Dissipation = 10 Watts. Maximum Plate Dissipation = 42 300m	68X8
68Y5G	ST-14	Duodiode	6CN-0-0	Cathode	6.3	1.600	5.0	3.2	VHF Amp.	65	1.0	68Y5G
68Y5GA	T-12	Duodiode	6CN-0-0	Cathode	6.3	1.600	F.W. Rect.	375 A.C. Volts Per Plate, R.M.S., 175 Ma. D.C. Output Current. Condenser Input to Filter.	68Y5GA
68Y6	T-5 1/2	Heptode	7CH-0-0	Cathode	6.3	0.300	.08m*	5.4*	7.6*	T.V. Damper Sync. Separator	10 10	68Y6

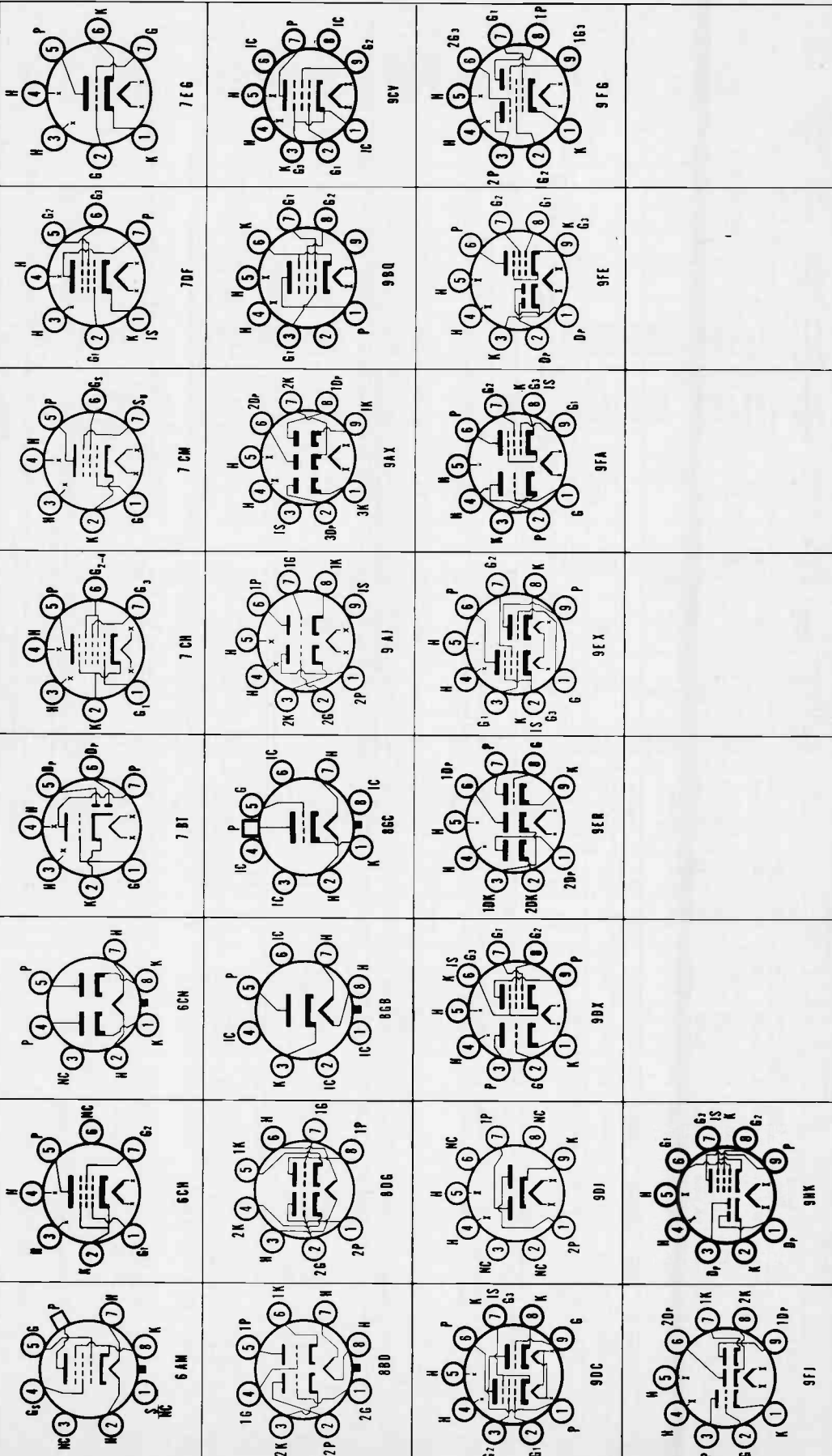(1) Values are given shielded unless marked with (*). (2) Has special mechanical and/or life characteristics. (3) Conformer specifications given are signal. (4) Average contact potential bias developed across cathode resistor. (5) Average contact potential bias developed across heater. (6) Average contact potential bias developed across heater. (7) Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)



(1) Plate to Plate.
 (2) Conversion Transconductance.
 (3) Approximate.
 (4) Triode Operation.
 (5) Applied through 20,000 ohms.
 (6) Per Tube or Section.
 (7) Plate and Target Supply Voltage.
 (8) Maximum Signal.

□ Cathode Resistor (ohms).
 ▽ Heater Operation.
 ▽ Triode Operation.
 ▽ Plate to Plate.
 ▽ Conversion Transconductance.
 ▽ Approximate.
 ▽ Triode Operation.

(1) Values are given shielded unless marked with (*). (2) Has special mechanical and/or life characteristics. (3) Conformer specifications given are signal. (4) Average contact potential bias developed across cathode resistor. (5) Average contact potential bias developed across heater. (6) Average contact potential bias developed across heater. (7) Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)

SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Tap; Ic—Internal Connection; DO NOT USE; J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; Xs—External Shield; □—Top Cap; ▽—Locating Key.

PENNY


Type	Construction		Emitter		Note (1) (*) Capacitances in μf .			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Screened Power Output	Power Output Watts	Type
	Bulb Size or Style	Class	Rating Diode	Type	Volts	Amps.	Cpn.												
6BY8	T-4½	Diode Pent.	9FN	Cathode	6.3I	0.600	.0035*	5.5*	5.0*	150 ^m	100	5.0	2.1	500,000	3,900	6BY8	
6BZ6	T-5½	Pentode	7CM-0-7	Cathode	6.3	0.300	.015m	7.5	9.8	180 ^m	150	10.6	4.3	1.0 Meg.	6,100	6BZ6	
6BZ7	T-6½	Duodiode	9AJ-0-9	Cathode	6.3	0.400	1.2	9.6	1.2	250 ^m	150	11.0	9.6	0.6 Meg.	6,100	6BZ7	
6BZ8	T-6½	Duodiode	9AJ-0-9	Cathode	6.3	0.400	1.13*	2.3*	1.35	250 ^m	150	10	5,300	8,000	6BZ8	
6CA	T-5½	Triode	6BG-0-0	Cathode	6.3	0.150	1.4	1.8	2.5	300	25	7,700	8,200	6CA	
6C5	Metal T-9	Triode	6O-1-1	Cathode	6.3	0.300	2.0	3.0	11.0	350	10.5	10,000	2,000	6C5	
6C5GT	ST-12	Pentode	6F-0-5	Cathode	6.3	0.300	.007m*	5.0*	6.5*	350	3.0	0.5	0.5	1 Meg.	1,185	6C5GT	
6C6	ST-12	Duodiode Tri.	7G-3-6	Cathode	6.3	0.300	350	3.0	100	2.0	16,000	1,250	6C6	
6C7	ST-12	Duodiode	8G-0-0	Cathode	6.3	0.300	2.6	2.6	2.0	350	3.2	92,500	1,600	6C7	
6C8G	T-6½	Triode	9MA-0-0	Cathode	6.3	1.000	0.5*	15.0*	9.0*	350	3.0	3.0	Plate Load 100,000 Ohms, Self-Bias Resistor 1,500 Ohms, Voltage Amplification 48, Output Volts 80, RMS for Inverter Service.	6C8G	
6CA4	T-6½	Beam Pent.	7CV-0-0	Cathode	6.3	1.900	110	32	16,000	8,100	6CA4	
6CA5	T-10 (SP)	Beam Pent.	8ET	Cathode	6.3	1.500	1.0*	15.5*	7.2*	185	4.5	37	6CA5	
6CA7	ST-16	Beam Pent.	8GD-0-0	Cathode	6.3	2.500	0.8*	34.0*	10.0*	175	90	5,000	9,800	6CA7	
6CB5A	T-12	Pentode	7CM-0-7	Cathode	6.3	0.300	0.4*	99.0*	10.0*	125	111	7,800	7,700	6CB5A	
6CB6	T-5½	Pentode	7CM-0-7	Cathode	6.3	0.300	.02*	6.3*	1.9*	180 ^m	150	9.5	2.8	600,000	6,200	6CB6	
6CB6A	ST-16	Beam Pent.	5BT-0-0	Cathode	6.3	2.500	0.8*	34*	9.5*	175	90	5,000	9,800	6CB6A	
6CD6A	T-12	Beam Pent.	5BT-0-0	Cathode	6.3	2.500	1.1*	92.0*	8.5*	125	75	7,800	7,700	6CD6A	
6CE5	T-5½	Pentode	7BD	Cathode	6.3	0.300	.03*	6.5*	1.9*	125	111	7,800	7,700	6CE5	
6CF6	T-5½	Pentode	7CM	Cathode	6.3	0.300	.015*	6.5*	3.0*	185	56 ^m	125	3.7	1.0 Meg.	7,600	6CF6	
6CG6	T-5½	Pentode	7BK-0-9	Cathode	6.3	0.300	.008m	5.0	5.0	250	8.0	150	9.3	780,000	9,000	6CG6	
6CG7	T-6½	Duodiode	9AJ-0-9	Cathode	6.3I	0.600	4.0*	9.3*	9.2*	125	12	6,000	6,500	6CG7	
6CG8	T-6½	Tri. Pentode	9GF	Cathode	6.3	0.450	1.5	2.4	1.0	125	9	3	3	6CG8	
6CG8A	T-6½	Tri. Pentode	9GF	Cathode	6.3I	0.450	.02	4.3	1.0	125	9	3	3	6CG8A	
6CH7	T-6½	Duodiode	9FC-0-9	Cathode	6.3	0.400	1.1	2.4	0.8	150	220 ^m	10	5,300	6,800	6CH7	
6CH8	T-6½	Tri. Pent.	9FT-0-0	Cathode	6.3	0.450	1.6*	1.9*	1.6*	200	180 ^m	150	2.8	300,000	6,200	6CH8	
6CK4	T-9	Power Triode	8JB	Cathode	6.3	1.250	6.5	8.0	1.8	250	28	40	1,200	5,500	6CK4	
6CL5	T-12	Beam Pent.	8GD	Cathode	6.3	2.500	0.7*	90.0*	11.5*	7,000	35	1,200	5,500	6CL5	
6CL6	T-6½	Power Pent.	9B7	Cathode	6.3	0.650	0.12	11	5.5	250	30	7	0.15 Meg.	11,000	6CL6	
6CL8	T-6½	Tri. Tetrode	9FX	Cathode	6.3I	0.450	1.8	2.7	1.8	185	15	5,000	8,000	6CL8	
6CL8A	T-6½	Tri. Tetrode	9FX	Cathode	6.3I	0.450	.016m	5.0	3.0	125	12	5,000	8,000	6CL8A	
6CM5	T-9	Beam Pent.	8GT-0-1A3	Cathode	6.3	1.250	1.1*	17.5*	7.7*	125	56 ^m	12	5,000	8,000	6CM5	
6CM6	T-6½	Beam Pent.	9CK	Cathode	6.3	0.450	0.7*	8.0*	8.5*	100	7	5,300	14,000	6CM6	
6CM7	T-6½	Duodiode	9ES	Cathode	6.3I	0.600	3.8*	2.0*	0.5*	250	80	4,100	4,400	6CM7	
6CM8	T-6½	Tri. Pentode	9FZ	Cathode	6.3I	0.450	1.9	1.6	0.22	180	150	50,000	2,000	6CM8	
6CN7	T-6½	Duodiode Tri.	9EN-0-3	Cathode	6.3	0.300	1.8*	1.5*	0.3*	100	1.0	54,000	1,300	6CN7	
6CO8	T-6½	Tri. Tetrode	9GE	Cathode	6.3I	0.450	1.8	2.7	1.2	125	56 ^m	12	5,000	8,000	6CO8	
6CR5	T-6½	Beam Pent.	9HC-0-0	Cathode	6.3	1.200	0.32*	12.9*	6.9*	250	22.5	150	2.1	18,000	6,000	6CR5	

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Notes (1) (2) Capacitances in μ d.			Use	Plate Vols	Negative Grid Vols	Screen Vols	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milli-watts	Type
	Beam Style	Class	Beating Diag.	Type	Volts	Amps.	Cgp.												
6CS7	T-6½	Duotriode	9EF-0-0	Cathode	6.31	0.600	2.6° 2.6°	1.8° 3.0° 0.5°	Sect. 2 Vert. Defl. Amp. Sect. 1 Vert. Osc.	250 10.5 8.5	19.0 10.5	3.450 7,700	4,500 2,200	15.5 17	6CS7	
6CS8	T-6½	Tri. Pentode	9FZ-0-3	Cathode	6.31	0.450	1.6° .02°	1.9° 6.0° 2.8°	Tri. Amp. Horiz. Amp. Power Amp.	125 125 125	12.0 13.0 3.0	5,500 7,700	4,000 7,700	22	6CS8	
6CU5	T-5½	Pentode	6AM-0-0	Cathode	6.3	1.200	0.6°	15.0°	Horiz. Amp.	180	49	10,000	7,500	6CU5	
6CU6	T-6½	Tri. Pentode	9GM	Cathode	6.31	0.450	1.6° 1.8° 3.23°	1.9° 7.1° 2.4°	Tri. Amp. Tri. Amp. Power Amp.	200 200 200	13 9.5	5,750 3,000	3,300 6,200	19	6CU6	
6CX7	T-6½	Duotriode	9FC-0-3	Cathode	6.3	0.400	1.8°	2.4	Tri. Amp.	150	9.0	6CX7	
6CY5	T-5½	Tetrtode	7EW-0-2.7	Cathode	6.3	0.200	.03	4.5	VHF Amp.	125	1.0	100,000	9,000	39	6CY5	
6CY7	T-6½	Duotriode	9EF	Cathode	6.3	0.750	1.8° 4.4°	1.5° 5.0° 1.0°	Vert. Osc. Vert. Defl. A. Amp.	250 250 250	1.2 3.0	52,000 9,700	1,300 5,400	68 5	6CY7	
6CZ5	T-6½	Beam Pent.	9HN	Cathode	6.31	0.450	0.4°	6.0°	Vert. Defl. Amp.	250 14	250 46.0	73,000	4,800	6CZ5	
6D4	T-5½	Gas Triode	5AY-0-0	Cathode	6.3	0.850	Relay Tube	350 50	Peak Cathode Current = 100 Ma. Cathode Current = 95 Ma. Approx. Volt Drop @ 95 Ma. = 16V.	6D4	
6D6	ST-12	Pentode	6F-0-3	Cathode	6.3	0.300	.007m	4.7°	Amplifier	100 250	8.0 8.2	850,000 800,000	1,500 1,400	6D6	
6D7	ST-12	Pentode	7H-5-6	Cathode	6.3	0.300	.007°	5.0°	Amplifier	135 250	3.0 3.0	600,000 400,000	385A (Ga = 135 V, 1.8 Ma.) 350A (Ga = 150 V, 0.4 Ma.)	6D7	
6D8G	ST-12	Heptode	8A-0-0	Cathode	6.3	0.150	0.2	8.0	Converter	100 100	67.5 1.5	6D8G	
6DA4	T-9	Diode	4CG	Cathode	6.3	1.200	T.V. Damper	6DA4	
6DA7	T-6½	Duotriode	9EF-0-0	Cathode	6.3	1.000	2.3° 6.9°	2.0° 5.5° 0.82°	Sect. 2 Vert. Defl. Amp.	150 150 250	17.5 40.0	1,100 7,700	2,600	6.3 20	6DA7	
6DB5	T-6½	Beam Pent.	9GR-0-0	Cathode	6.3	1.200	0.2	1.3	Vert. Defl. Amp.	200 180 125	46.0	28,000	8,000	6DB5	
6DB6	T-5½	Pentode	7CM-0-2	Cathode	6.3	0.300	.0033°	6.0°	Color Demod.	150	1.0	50,000	9,050 μ mhos when Eg 3 = -3 Vols.	6DB6	
6DC6	T-5½	Pentode	7CM-0-7	Cathode	6.3	0.300	.09°	6.5°	Amplifier	300	180	3.0	500,000	5,500	6DC6	
6DC8	T-6½	Duodi. Pent.	9HE	Cathode	6.3	0.300	.0023°	5.0°	R-F Amp.	200	1.5	100	11	3.3	6DC8	
6DE6	T-5½	Pentode	7CM	Cathode	6.3	0.300	.015m	6.5	VHF Amp.	125	56	125	15.5	4.2	6DE6	
6DE7	T-6½	Duotriode	9HF	Cathode	6.3	0.900	4.2° 8.5° 5.5°	2.2° 5.5° 1.0°	Sect. No. 2 Vert. Defl. Amp. Sect. No. 1 Vert. Osc.	150 150 250	17.5 35.0 5.5	925 8,750	2,000	6 17.5	6DE7	
6DG6GT	T-9	Beam Pent.	7S-0-0	Cathode	6.3	1.200	Power Amp.	110 200	7.5 180	110 135	49 46	4.0 2.2	6DG6GT	
6DG7	T-6½	Pentode	9BA	Cathode	6.3	0.300	.0018°	5.5°	R-F or I-F Amplifier	100 250	68 68	100 110	10.8 4.4	6DG7	
6DJ8	T-6½	Duotriode	9DE	Cathode	6.3	0.365	1.4°	3.3°	VHF Amp.	90	1.3	6DJ8	
6DK6	T-5½	Pentode	7CM-0-7	Cathode	6.3	0.300	.02°	6.3°	VHF Amp.	125	56	125	12.0	3.8	6DK6	
6DN6	T-12	Beam Pent.	5BT-0-0	Cathode	6.3	2.500	0.8°	22.0°	Horiz. Defl. Amp.	125 18 125	70	6.3	4,000	9,000	6DN6	
6DN7	T-9	Duotriode	8BD	Cathode	6.3	0.900	5.5	4.6	Sect. 2 Vert. Defl. Amp.	250 250	9.5	2,000	7,700	15.4 22.5	6DN7	
6DO3	T-12	Beam Pent.	8JC	Cathode	6.3	2.500	0.5°	23°	Horiz. Defl. Amp.	175 25 125	110	5	5,500	10,500	6DO3	
6DO6	T-12	Beam Pent.	6AM-0-0	Cathode	6.3	1.800	0.55°	15.0°	Horiz. Defl. Amp.	6,000 Max. 250	Peak Pos. Plate Vols. Max. Screen Disapp.	180 Ma. 2.4	Max. Cathode Current. 15 Watts Max. Plate Disapp.	6DO6	
6DO6A	T-12	Beam Pent.	6AM	Cathode	6.3	1.800	0.55°	15.0°	Horiz. Defl. Amp.	6,000 Max. 250	Peak Pos. Plate Vols. Max. Screen Disapp.	140 Ma. 2.4	Max. Cathode Current. 15 Watts Max. Plate Disapp.	6DO6A	
6DR7	T-6½	Duotriode	9HF	Cathode	6.3	0.900	4.5° 8.5°	2.2° 5.5° 1.0°	Sect. 2 Vert. Defl. Amp. Sect. 1 Vert. Osc.	150 150 250	17.5 35.0 5.5	925 8,750	2,000	6 17.5	6DR7	

6DS5	1-3/2	Beam Pent.	7BZ	Cathode	6.3	0.800	0.19*	9.5*	6.3*	Power Amp.	200	180 ^m	200	34.5	3.5	28,000	6,000	2,800	6DS5
6DT5	1-6/2	Beam Pent.	9HN	Cathode	6.3	1.200	0.57*	12.5*	4.9*	Vent. Defl. Amp.	250	270	200	27	3	28,000	5,800	3,400	6DT5
6DT6	1-5/2	Gated Beam	7EN-0-0	Cathode	6.3	0.300	.02	Quad. F. M. Defl. Amp.	150	560 ^m	100	1.1	2.1	150,000	6,250	6DT6
6DT8	1-6/2	Dualdiode	9DE	Cathode	6.3	0.300	1.6	2.7	1.6	Amplifier	100	270 ^m	250	3.7	15,000	4,000	60	6DT8
6DW5	1-6/2	Beam Pent.	9CK	Cathode	6.3	1.200	0.5	14	9	Vent. Defl. Amp.	250	200	10	10,900	5,500	60	6DW5	

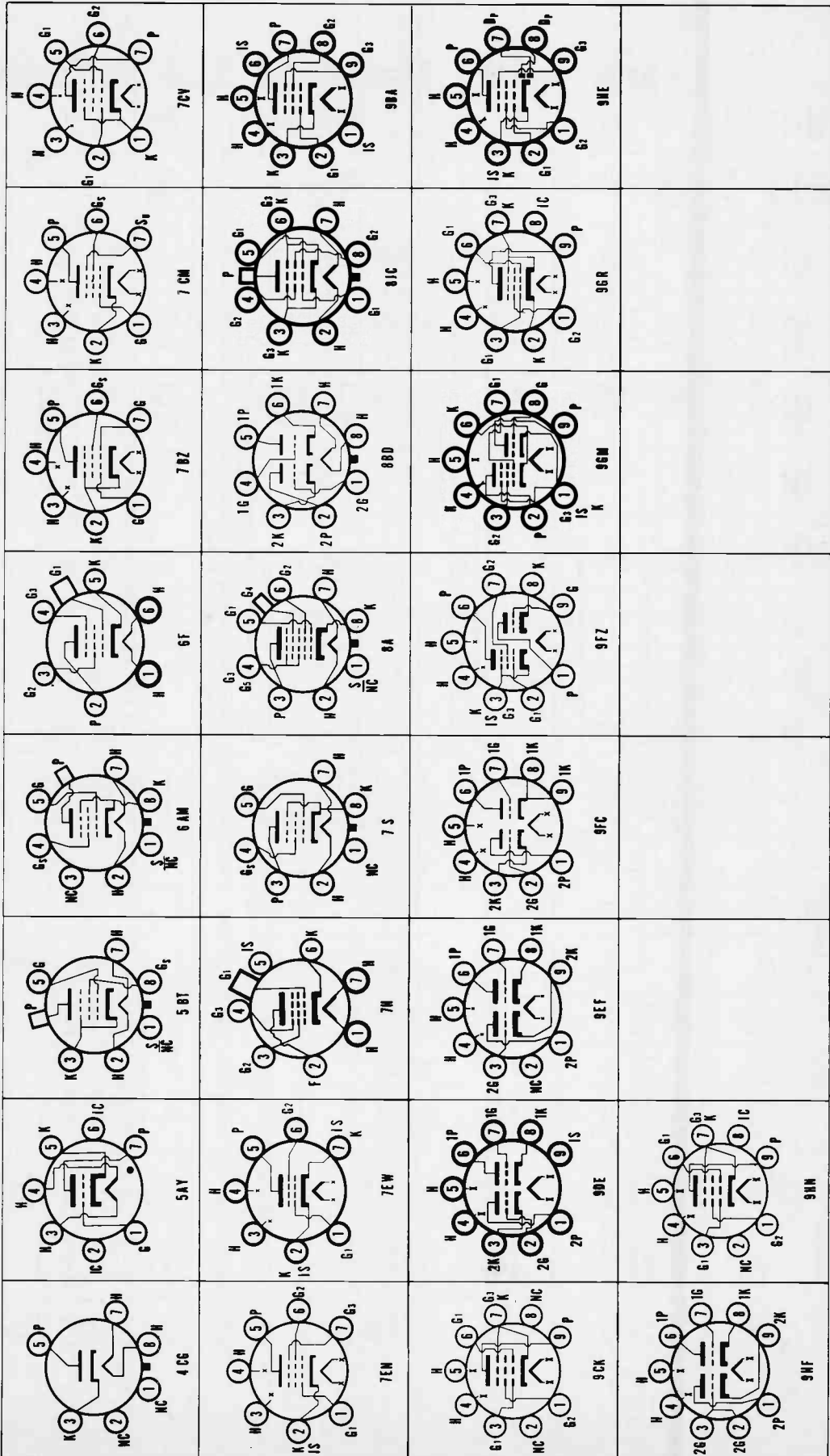(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, R₁ input, Mixer Output, and controlled heater warm-up time (applies to parallel connections of types having a tapped heater.)
 (4) Average contact potential bias developed across specified grid resistor.
 † Per Tube or Section.
 ‡ Plate and Target Supply Voltage.
 § Maximum Signal.
 ¶ Applied through 20,000 ohms.
 * Conversion Transconductance.
 † Triode Operation.
 m maximum.
 = Cathode Resistor (ohms).
 ‡ Plate to Plate.
 † Approximate.




SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate, F—Filament, Fc—Filament Center, G—Grids numbered according to their position from the cathode, H—Heater, Hc—Heater Center, Ht—Heater Tap, IC—Internal Connection, DO NOT USE, J—Jumper, K—Cathode, NC—No Connection, P—Plate, Rc—Ray Control, S—Metal Shell, SA—Starter Anode, T—Target, XS—External Shield, □—Top Cap, ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (2) Capacitances in $\mu\mu\text{f}$.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Trans-conductance Micromhos	Amplification Factor	Choke Load for Staked Power Output	Unloaded Power Output Milli-watts	Type
	Bulb Size or Style	Classes	Beating Diag.	Type	Volts	Amps.	Cgp.											
6DZ8	T-6½	Tri. Beam Pent.	6DZ8	Cathode	6.3	0.900	6DZ8
6E5	T-9	Electron Ray	6R-0-0	Cathode	6.3	0.300	6E5
6E6	ST-14	Duotriode	7B-0-0	Cathode	6.3	0.600	6E6
6E7	ST-12	Pentode	7H-5-6	Cathode	6.3	0.300	6E7
6EA8	T-6½	Tri. Pentode	9AE	Cathode	6.31	0.450	6EA8
6EB8	T-6½	Tri. Pentode	9DX	Cathode	6.3	0.750	6EB8
6EF6	T-9	Beam Pent.	7S	Cathode	6.3	0.900	0.8*	11.5*	9.0*	6EF6
6EH5	T-5½	Beam Pent.	7CV	Cathode	6.3	1.200	0.65*	17*	9*	6EH5
6EM5	T-6½	Beam Pent.	9HN	Cathode	6.3	0.800	0.7*	10*	5.1*	6EM5
6E58	T-6½	Duotriode	9DE	Cathode	6.3	0.365	1.85	0.17	VHF Amp.	90	1.2	6E58
6EW6	T-5½	Pentode	7CM	Cathode	6.3	0.400	.03	10	3.4	VHF Amp.	125	5.6*	11	6EW6
6F4	Acorn	Triode	7BR-0-0	Cathode	6.3	0.925	1.9*	9.0*	0.6*	Amplifier	80	150*	6F4
6F5	Metal T-9	Triode	5M-1-0	Cathode	6.3	0.300	2.3	5.5	4.0	Amplifier	950	9.0	6F5
6F5GT	T-9	Triode	5M-0-0	Cathode	6.3	0.300	2.8*	9.2*	3.3*	6F5GT
6F6	Metal T-9	Power Pent.	7S-1-0	Cathode	6.3	0.700	6F6
6F6G	ST-14	Pent. Triode	7E-0-6	Cathode	6.3	0.300	.008m	3.2	12.5	P.P.A.1 Amp.	315	94.0	6F6G
6F6GT	T-9	Pent. Triode	7E-6-6	Cathode	6.3	0.600	3.2*	3.9*	1.9*	P.P.A.B.2 Amp.	375	96.0	6F6GT
6F7	ST-12	Duotriode	8G-0-0	Cathode	6.3	0.200	0.4	33	8	Horiz. Def. Amp.	250	22.5	150	6F7
6F7S	T-12	Beam Pent.	6AM	Cathode	6.3	1.200	0.4	33	8	6F7S
6F8G	ST-12	Duotriode	8G-0-0	Cathode	6.3	0.600	3.2*	3.9*	1.9*	6F8G
6FH6	T-12	Beam Pent.	6AM	Cathode	6.3	1.200	0.4	33	8	6FH6
6G5	Now Known as Type 6U5	Power Pent.	7S-0-0	Cathode	6.3	0.150	6G5
6G6G	ST-12	Power Pent.	7S-0-0	Cathode	6.3	0.150	6G6G
6H4GT	T-9	Diode	5AF-0-0	Cathode	6.3	0.150	6H4GT
6H6, 6H6GT	T-9, Metal	Duotriode	7B-0-1	Cathode	6.3	0.300	6H6, 6H6GT
6J4	T-5½	Triode	7B-0-0	Cathode	6.3	0.400	3.9	4.6	0.24	Rectifier	100	6J4
6J5GT	Metal T-9	Triode	6O-1-0	Cathode	6.3	0.300	3.4	3.4	3.6	Amplifier	350	8.0	6J5GT
6J6	T-5½	Duotriode	7BF-0-7	Cathode	6.3	0.450	1.5	2.6	1.6	VHF Osc.	150	10.0	6J6
6J6A	Metal T-9	Pentode	7R-1-1	Cathode	6.31	0.450	1.5	2.6	1.0	VHF Amp./	100	50*	6J6A
6J7G	ST-12	Pentode	7R-1-1	Cathode	6.3	0.300	.005m	7.0	19.0	R-F Amp.	250	3.0	6J7G
6J7GT	T-9	Pentode	7R-1-1	Cathode	6.3	0.300	.007m	5.4	12.0	6J7GT
6J8G	ST-12	Tri. Heptode	8H-0-8	Cathode	6.3	0.300	.09m	4.4	10.0	Mixer	250	3.0	6J8G
6K4	T-3	Triode	6K4	Cathode	6.3	0.150	2.2*	9.4*	0.35*	Oscillator	950	10.0	6K4
6K5G	ST-12	Triode	5U-0-0	Cathode	6.3	0.300	2.0	9.0	5.75	Osc. Amp.	100	1.5	6K5G
6K5GT	T-9	Triode	5U-0-0	Cathode	6.3	0.300	2.8	9.9	4.7	Amplifier	350	3.0	6K5GT
6K6GT	T-9	Power Pent.	7S-0-0	Cathode	6.3	0.400	6K6GT
6K7	Metal T-9	Pentode	7R-1-0	Cathode	6.3	0.300	.005m	7.0	12.0	R-F Amp.	100	1.0	6K7
6K7GT	ST-12	Pentode	7R-0-8	Cathode	6.3	0.300	.003m	5.0	12.0	6K7GT
6K8	Metal T-9	Tri. Hexode	8K-1-0	Cathode	6.3	0.300	.03m	6.6	4.5	Mixer Osc.	250	3.0	6K8
6K8GT	ST-12	Tri. Hexode	8K-0-8	Cathode	6.3	0.300	.08m	4.6	3.8	6K8GT
6L4	Acorn	Triode	8R-1-8	Cathode	6.3	0.225	1.6*	1.8*	0.5*	Osc. Amp.	80	150*	6L4
6L5G	ST-12	Triode	6O-0-0	Cathode	6.3	0.150	2.8	9.8	5.0	Amplifier	100	3.0	6L5G

6L6	6L6G	6L6GA	6L6GB	6L6GAY	6L7	6L7G	6M3	6M4	6N6G
Metal ST-16 ST-14 T-12	Beam Peni. 7S-0-0 7S-0-0 7S-0-0	11.5°	0.9°	6.3	0.900	6.3	0.900	6.3	0.900
6L6GAY	Beam Peni. 7S-0-0	11.5°	0.9°	6.3	0.900	6.3	0.900	6.3	0.900
6L7	Metal ST-12	11.5°	0.9°	6.3	0.300	6.3	0.300	6.3	0.300
6M3	T-12	11.5°	0.9°	6.3	3.000	6.3	3.000	6.3	3.000
6M4	1-6½	11.5°	0.9°	6.3	0.710	6.3	0.710	6.3	0.710
6N6G	1-5½	11.5°	0.9°	6.3	0.800	6.3	0.800	6.3	0.800
	ST-14	11.5°	0.9°	6.3	0.900	6.3	0.900	6.3	0.900

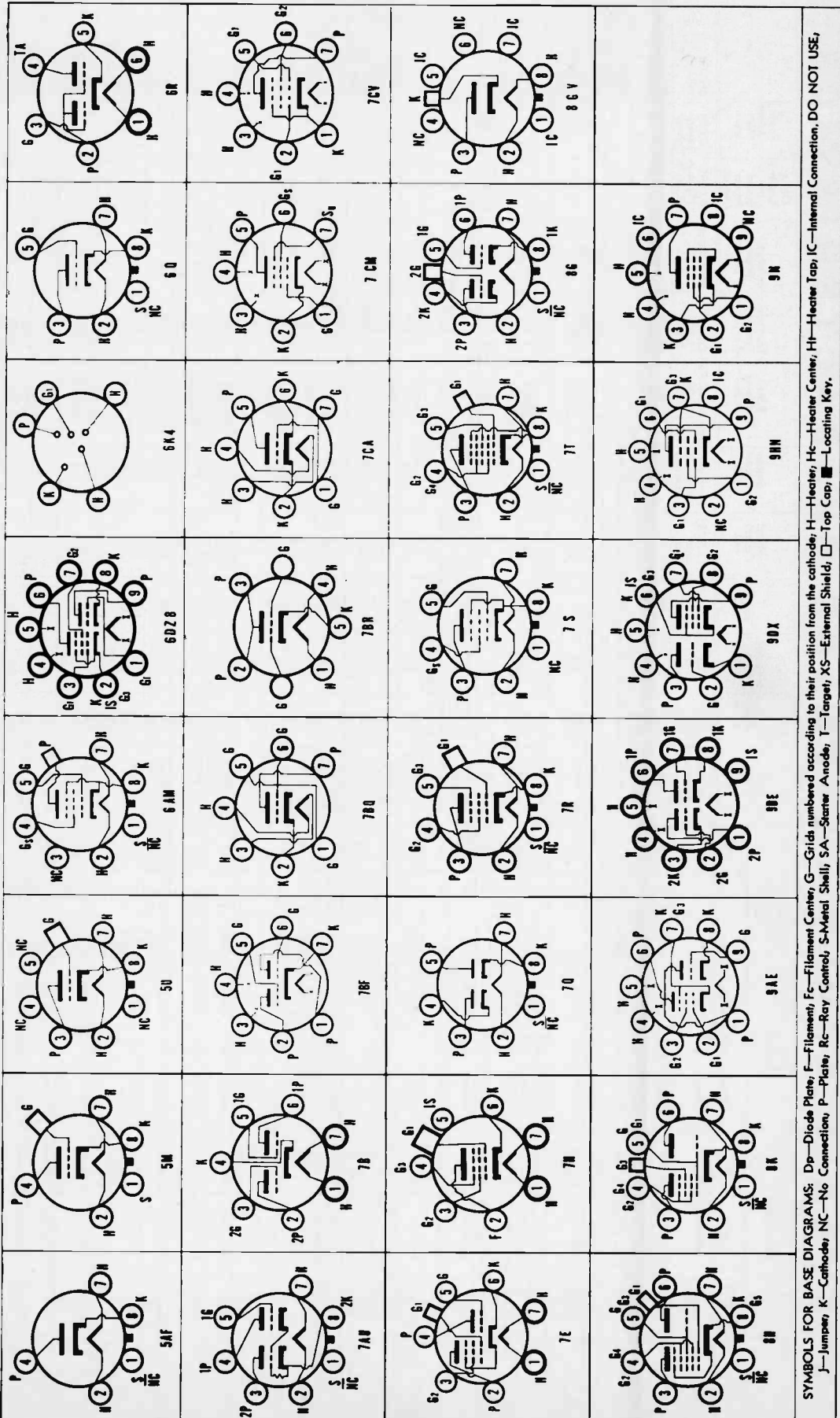(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer Output.
 (4) Average contact potential bias developed across specified grid resistor.
 X Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)




SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Hi—Heater Tap; IC—Internal Connection; DO NOT USE.
 J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES -- AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (*) Capacitances in μ fd.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohm Load for Stated Power Output	Power Output Milli-watts	Type
	Bulls Size or Style	Class	Beating Diat.	Type	Volts	Amps.	Csp.												
6N7GT 6N7	T-9 Metal	Duotriode	8B-0-0	Cathode	6.3	0.800	300 250 11,300 994	0.0 5.0 6.0 6.0	6N7GT 6N7
6N8	T-6½	Duod. Pent.	9T-0-0	Cathode	6.3	0.300	0.003m	4.0	4.6	R-F Amp.	250	1.75	1.6 Meg.	9,200	6N8
6P5GT	T-9	Triode	6Q-0-0	Cathode	6.3	0.300	0.6	3.4	5.5	Amplifier Detector	250	5.0	1,450	6P5GT
6P7G	SI-12	Pent. Triode	7U-0-8	Cathode	6.3	0.300	0.07m	9.8	19.0	R-F Amp.	250	6P7G
6Q4	T-6½	Triode	9S-0-0	Cathode	6.3	0.480	3.4	5.4	0.6m	R-F Amp.	250	1.5	6Q4
6Q7	SI-12	Duodiode Tri.	7V-1-8	Cathode	6.3	0.300	1.4	5.0	3.8	Det. Amp.	100	0.8	58,000	6Q7
6Q7GT	SI-12	Duodiode Tri.	7V-0-8	Cathode	6.3	0.300	1.5	3.2	5.0	Det. Amp.	350	1.1	58,000	6Q7GT
6R4	T-6½	Triode	9R-0-0	Cathode	6.3	0.300	1.5	1.7	0.5	Oscillator	150	3.0	5,500	6R4
6R6G	SI-12	Pentode	6AW-0-0	Cathode	6.3	0.300	0.07m	4.5	11.0*	R-F Amp.	350	7.0	1.7	800,000	6R6G
6R7	SI-12	Duodiode Tri.	7V-1-1	Cathode	6.3	0.300	3.3	4.8	3.8	Det. Amp.	250	9.0	8,500	6R7
6R7GT	T-9	Triode	7V-0-8	Cathode	6.3	0.300	2.1	9.6	5.2	Det. Amp.	250	9.0	1,900	6R7GT
6R8	T-6½	Triple Dio. Tri.	9K-0-3A8	Cathode	6.3	0.450	2.4	1.5*	1.1*	Det. Amp.	250	9.0	8,500	6R8
6S4	T-6½	Triode	9AC-0-0	Cathode	6.3	0.600	2.8*	4.2*	0.9*	Vert. Defl. Amp.	250	9.5	6S4
6S4A	T-6½	Triode	9AC-0-0	Cathode	6.3	0.600	2.6*	4.2*	0.9*	Vert. Defl. Amp.	250	9.0	6S4A
6S7	SI-12	Pentode	7R-1-1	Cathode	6.3	0.150	0.05m	4.5	10.5	R-F Amp.	125	3.0	0.75	1,950	6S7
6S7GT	SI-12	Pentode	7R-0-8	Cathode	6.3	0.150	0.08m	6.4	8.0	R-F Amp.	250	3.0	1.00	1,750	6S7GT
6S8GT	T-9	Triple Dio. Tri.	8CB-0-2	Cathode	6.3	0.300	2.0	1.2	5.0	Det. Amp.	350	0.9	1,100	6S8GT
6SA7	SI-12	Heptode	8R-1-0	Cathode	6.3	0.300	0.25m	9.5	9.5	Converter	100	2.0	100	500,000	6SA7
6SA7GT	T-9	Heptode	8AD-0-6	Cathode	6.3	0.300	0.5m	9.5	9.5	Converter	350	2.0	100	500,000	6SA7GT
6SA7GT	T-9	Heptode	8AD-1-6	Cathode	6.3	0.300	0.5m	9.5	9.5	Converter	350	2.0	100	500,000	6SA7GT
6S87Y	SI-12	Heptode	8R-1-0	Cathode	6.3	0.300	0.13m	9.6	9.2	Converter	100	1.5	100	880	6S87Y
6S87GT	SI-12	Duodiode	9S-1-0	Cathode	6.3	0.300	2.0	9.0	3.0	Amplifier	250	2.0	33,000	6S87GT
6S87GT	T-9	Pentode	8N-1-5	Cathode	6.3	0.300	0.035	9.0	7.5	R-F Amp.	250	9.0	100	3,350	6S87GT
6S87GT	T-9	Pentode	8N-1-5	Cathode	6.3	0.300	0.035m	6.0	7.5	R-F Amp.	100	1.0	100	2,500	6S87GT
6SF5	SI-12	Triode	6AB-1-0	Cathode	6.3	0.300	2.4	4.8	3.6	Amplifier	250	2.0	66,000	6SF5
6SF5GT	SI-12	Triode	6AB-0-0	Cathode	6.3	0.300	2.6	4.8	3.6	Amplifier	250	2.0	66,000	6SF5GT
6SF7	SI-12	Diode Pent.	7AZ-1-1	Cathode	6.3	0.300	0.04m	5.5	6.0	Det. Amp.	100	1.0	100	1,975	6SF7
6SG7	SI-12	Pentode	8BK-1-1	Cathode	6.3	0.300	0.03m	8.5	7.0	R-F Amp.	100	1.0	100	900,000	6SG7
6SG7GT	SI-12	Pentode	8BK-1-1	Cathode	6.3	0.300	0.04m	8.5	7.0	R-F Amp.	250	1.0	100	900,000	6SG7GT
6SH7	SI-12	Pentode	8BK-1-1	Cathode	6.3	0.300	0.03m	8.5	7.0	R-F Amp.	100	1.0	100	350,000	6SH7
6SH7GT	SI-12	Pentode	8BK-1-1	Cathode	6.3	0.300	0.04m	8.5	7.0	R-F Amp.	250	1.0	100	350,000	6SH7GT
6SJ7	SI-12	Pentode	8N-1-5	Cathode	6.3	0.300	0.05m	6.0	7.0	R-F Amp.	100	3.0	100	4,100	6SJ7
6SJ7GT	SI-12	Pentode	8N-0-5	Cathode	6.3	0.300	0.05m	7.0	7.0	R-F Amp.	100	3.0	100	4,100	6SJ7GT
6SJ7GT	SI-12	Pentode	8N-0-5	Cathode	6.3	0.300	0.05m	7.0	7.0	R-F Amp.	100	3.0	100	4,100	6SJ7GT
6SJ7GT	SI-12	Pentode	8N-0-5	Cathode	6.3	0.300	0.05m	7.0	7.0	R-F Amp.	100	3.0	100	4,100	6SJ7GT
6SK7	SI-12	Pentode	8N-1-1	Cathode	6.3	0.300	0.03m	6.0	7.0	R-F Amp.	100	1.0	100	5.3	6SK7
6SK7GT	SI-12	Pentode	8N-1-5	Cathode	6.3	0.300	0.03m	6.5	7.5	R-F Amp.	100	1.0	100	9.1	6SK7GT
6SK7GT	SI-12	Pentode	8N-1-5	Cathode	6.3	0.300	0.03m	6.5	7.5	R-F Amp.	250	1.0	100	900,000	6SK7GT
6SL7GT	SI-12	Duotriode	8BD-0-0	Cathode	6.3	0.300	2.8*	3.0*	2.8*	Amplifier#	350	9.0	44,000	6SL7GT
6SL7GT	SI-12	Duotriode	8BD-0-0	Cathode	6.3	0.300	2.8*	3.4*	3.2*	Amplifier#	350	9.0	44,000	6SL7GT
6SN7GT	SI-12	Duotriode	9BD-0-0	Cathode	6.3	0.600	3.8*	3.0*	1.2*	Amplifier	90	0	6,700	6SN7GT
6SN7GT	SI-12	Duotriode	9BD-0-0	Cathode	6.3	0.600	4.0*	3.0*	1.2*	Amplifier	250	9.0	6,700	6SN7GT
6SN7GT	SI-12	Duotriode	9BD-0-0	Cathode	6.3	0.600	4.0*	3.0*	1.2*	Amplifier	250	9.0	6,700	6SN7GT
6SN7GT	SI-12	Duotriode	9BD-0-0	Cathode	6.3	0.600	4.0*	3.0*	1.2*	Amplifier	250	9.0	6,700	6SN7GT
6SN7GT	SI-12	Duotriode	9BD-0-0	Cathode	6.3	0.600	4.0*	3.0*	1.2*	Amplifier	250	9.0	6,700	6SN7GT
6SO7	SI-12	Duodiode Tri.	8Q-1-1	Cathode	6.3	0.300	1.6	3.2	3.0	Det. Amp.	250	9.0	85,000	6SO7
6SO7GT	SI-12	Duodiode Tri.	8Q-1-3	Cathode	6.3	0.300	1.8	4.2	3.4	Det. Amp.	250	9.0	85,000	6SO7GT
6SR7	SI-12	Duodiode Tri.	8Q-1-3	Cathode	6.3	0.300	2.4	3.6	2.8	Det. Amp.	250	9.0	8,500	6SR7
6SR7GT	SI-12	Duodiode Tri.	8Q-0-3	Cathode	6.3	0.300	2.3	3.5	3.8	Det. Amp.	250	9.5	8,500	6SR7GT
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	0.04m	5.5	7.0	R-F Amp.	100	1.0	100	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0	1,950	6S87
6S87	SI-12	Pentode	8N-1-0	Cathode	6.3	0.150	1.5	2.8	3.0	Det. Amp.	250	9.0							

618	T-6 1/2	Triple	9E-0-3 & 7	Cathode	6.3	0.450	1.7	2.4	100	1.0	0.8	54,000	1,300	70	618A
618A	Diode, Tri.	6.31	0.450	1.7	6.31	0.450	1.7	2.4	250	3.0	1.0	59,000	1,200	70	618A
6UAGT	Diode	6.3	1.300	350 A.C. Volts Per Plate, R.M.S., 125 Ma. Output Current. Condenser Input to Filter.	0.8	6UAGT
6U5	Electron Ray	6R-0-0	100% (Series Plate Resistor 0.5 Meg., Target Current 1.0 Ma., Grid Bias -8.0 for 0" Shadow.)	1.0	6U5
6U6GT	Beam Peni.	7S-0-0	6.3	0.750	250% (Series Plate Resistor 1.0 Meg., Target Current 4.0 Ma., Grid Bias -22.0 for 0" Shadow.)	4.0	10,000	2,000	6U6GT
6U7G	Pentode	7R-0-8	6.3	0.300	.007m	9.0	200	3.0	100	250,000	1,500	6U7G
6U8	Tri. Pentode	9AE-0-7	6.3	0.450	1.8	2.8	100	3.0	100	800,000	1,600	6U8
6U8A	Tri. Pentode	9AE-0-7	6.31	0.450	.006	3.5	125	-1	110	200,000	5,000	6U8A

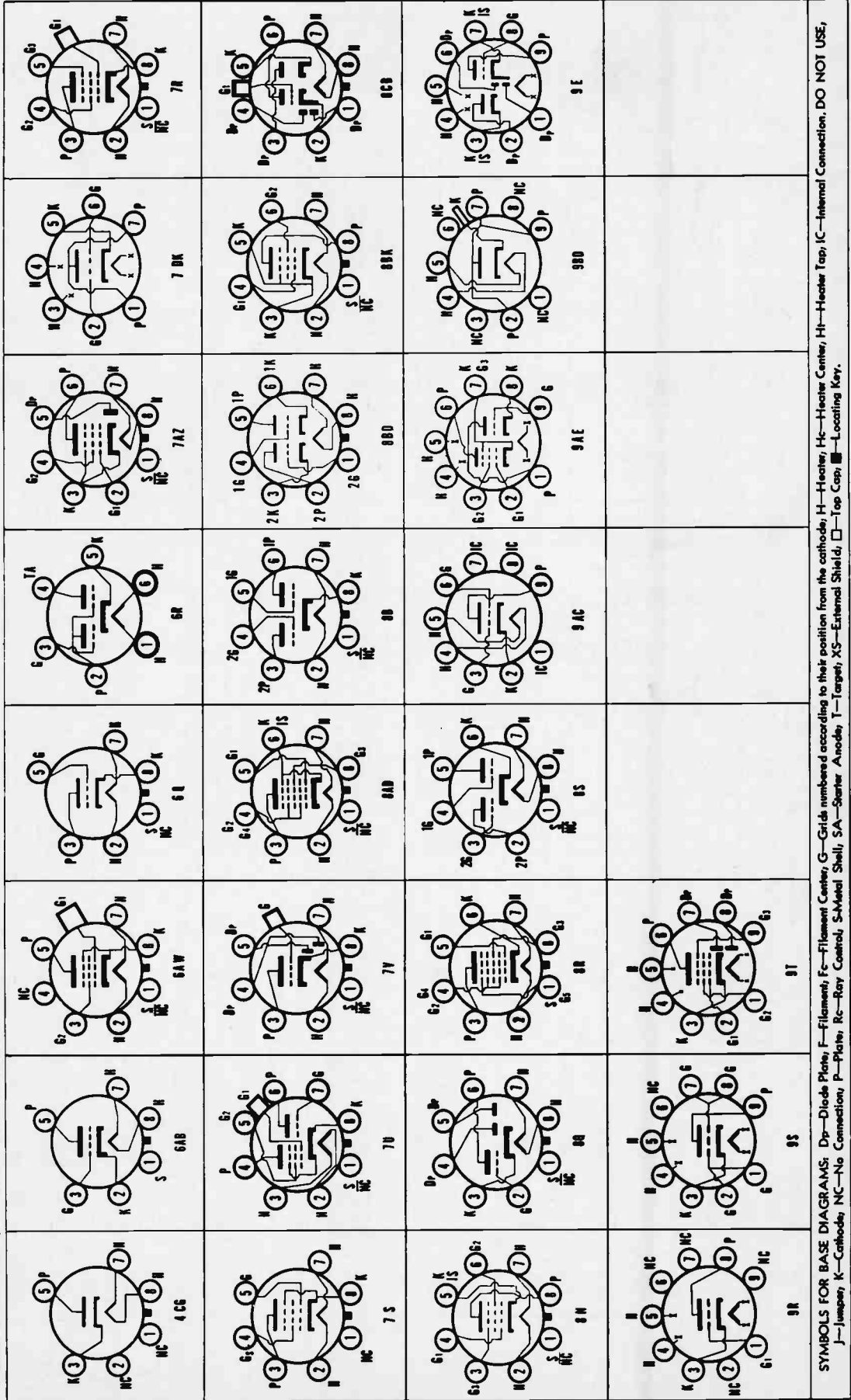(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
(2) Converter tube capacitances given are signal (4) Average contact potential bias developed across
grid to plate, RF input, Mixer, Champ.
† Maximum Signal.
‡ Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)
□ Applied through 20,000 ohms.
• Cathode to anode conductance.
* Triode Operation.
† Per Tube or Section.
‡ Plate and Control Supply Voltage.
§ Plate to Plate.
¶ Approximate.
• Triode Operation.




SYMBOLS FOR BASE DIAGRAMS: F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Tap; IC—Internal Connection. DO NOT USE,
J—Jumper; K—Cathode; NC—No Connection; P—Plate; RC—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Tap Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Note (1) (†) Capacitances in μfd .			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohm Load for Stated Power Output	Power Output Milli-watts	Type
	Bull Size or Style	Class	Beam Pent.	Type	Volts	Amps.	Cgp.	Cin.												
6V3, 6V3A	T-6½	Diode	9B	Cathode	6.3	1.750														6V3, 6V3A
6V4	T-6½	Duodiode	9A-0-0	Cathode	6.3	0.600														6V4
6V5GT	T-9	Pentode	6A-O-0-0	Cathode	6.3	0.450	0.6	9.0	10.0											6V5GT
6V6	Metal T-9	Beam Pent.	7S-1-0	Cathode	6.3	0.450	0.3	10.0	11.0											6V6
6V6GT	T-9		7S-0-0	Cathode	6.3	0.7	0.7	9.0*	7.5*											6V6GT
6V6GT	T-9		7S-0-0	Cathode	6.3	0.7	0.7	9.0*	7.5*											6V6GT
6V6GT	T-9		7S-0-0	Cathode	6.3	0.450	0.7	9.0*	7.5*											6V6GT
6V6GT	T-9		7S-0-0	Cathode	6.3	0.450	0.7	9.0*	7.5*											6V6GT
6V7G	ST-12	Duodiode Tri.	7V-0-8	Cathode	6.3	0.300	1.3	1.5	6.0											6V7G
6V8	T-6½	Triode	9A-H-0-3	Cathode	6.3	0.450														6V8
6W4GT	T-9	Diode	4C-G-0-0	Cathode	6.3	1.200														6W4GT
6W5G	ST-12	Duodiode	6S-0-0	Cathode	6.3	0.900														6W5G
6W6GT	T-9	Beam Pent.	7S-0-0	Cathode	6.3	1.200	0.8*	15.0*	9.0*											6W6GT
6W7G	ST-12	Pentode	7R-0-8	Cathode	6.3	0.150	.007m	5.0	8.5											6W7G
6X4	T-5½	Duodiode	5B-S-0-0	Cathode	6.3	0.600														6X4
6X5	Metal T-9	Duodiode	6S-0-0	Cathode	6.3	0.600														6X5
6X5GT (3)	T-9			Cathode	6.3	0.600														6X5GT (3)
6X8	T-6½	Triode Pentode	9AK	Cathode	6.3	0.450	1.5	2.4	1.0											6X8
6X8A	T-6½			Cathode	6.3	0.450	.06	4.8	1.6											6X8A
6Y5G	ST-12	Diode	4A-C-0-0	Cathode	6.3	0.700														6Y5G
6Y5	ST-12	Duodiode	6J-S-0	Cathode	6.3	0.800														6Y5
6Y6G	ST-14	Beam Pent.	7S-0-0	Cathode	6.3	1.250														6Y6G
6Y6GA	T-12			Cathode	6.3	0.600														6Y6GA
6Y7G	ST-12	Duodiode	8B-0-0	Cathode	6.3	0.600														6Y7G
6Z4	ST-12	Duodiode	3D-0-0	Cathode	6.3	0.500														6Z4
6Z5/12Z5	ST-12	Duodiode	6K-0-0	Cathode	6.3	0.800														6Z5/12Z5
6Z7G	ST-12	Duodiode	8B-0-0	Cathode	6.3	0.300														6Z7G
6Z7YG	ST-12	Duodiode	6S-0-0	Cathode	6.3	0.300														6Z7YG
7A4/XXL	Lock-in Triode	5AC-L-0		Cathode	6.3	0.300	4.0	3.4	3.0											7A4/XXL
7A5	Lock-in	6AA-L-0		Cathode	6.3	0.750	0.44	13.0	7.2											7A5
7A6	Lock-in	7DX-L-5		Cathode	6.3	0.150	.003m	6.0	7.0											7A6
7A7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.003m	6.0	7.0											7A7
7A8	Lock-in	Octode	8U-L-7	Cathode	6.3	0.150	0.15m	7.5	9.0											7A8
7AB7	Lock-in	Pentode	8B-O-L-0	Cathode	6.3	0.150	.06m	3.5	4.0											7AB7
7AD7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.600	.03	11.5	7.5											7AD7
7AF7	Lock-in	Duodiode	8AC-L-0	Cathode	6.3	0.300	2.3*	2.2*	1.6*											7AF7
7AG7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.150	.003m	7.0	6.0											7AG7
7AH7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.150	.003m	7.0	6.5											7AH7
7AJ7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.007m	6.0	6.5											7AJ7
7AK7	Lock-in	Pentode	8V-L-0	Cathode	6.3	0.800	4.0 Sutoff	12.0	9.5											7AK7
7AU7	T-6½	Duodiode	9A-0-0	Cathode	7.0/3.5†	0.300/0.600	1.5*/1.3*	1.6*/1.6*	0.4*/0.3*											7AU7
7B4	Lock-in	Triode	5AC-L-0	Cathode	6.3	0.300	1.6	3.2	3.2											7B4
7B5	Lock-in	Power Pent.	6AE-L-0	Cathode	6.3	0.400	0.8	7.4	8.0											7B5

7B6	Lock-in	Duodiode Tri.	8W-L-7	Cathode	6.3	0.300	1.6	3.0	2.4	100	1.0	0.4	110,000	900	7B6
7B7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.150	.004m	5.0	6.0	100	3.0	8.8	300,000	1,100	7B7
7B8	Lock-in	Heptode	8X-L-0	Cathode	6.3	0.300	0.2m	10.0	9.0	100	1.5	1.1	600,000	360	7B8
7C4	Lock-in	H. F. Diode	4AH-L-0	Cathode	6.3	0.150		9.5	9.0	100	3.0	3.5	500,000	360	7C4
7C5	Lock-in	Beam Pent.	6AA-L-0	Cathode	6.3	0.450	0.4	9.5	9.0	100	3.0	3.5	500,000	360	7C5

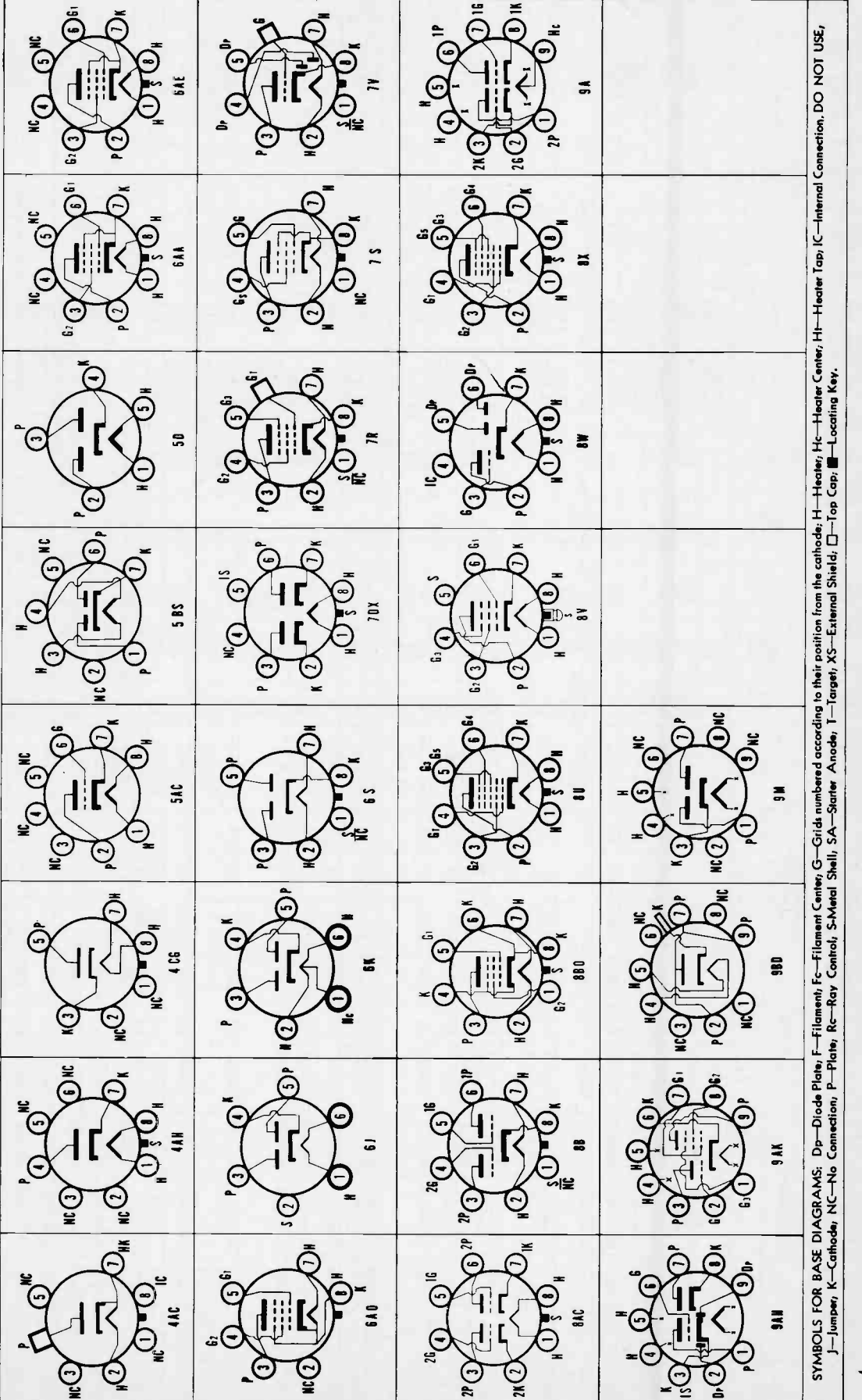(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF Input, Mixer Output, specified grid resistor.
 X Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)



m maximum Cathode Resistor (ohms).
 † Plate to Plate.
 ‡ Approximate.
 § Conversion Transconductance.
 ¶ Applied through 20,000 ohms.
 # Per Tube or Section.
 * Plate and Target Supply Voltage.
 † Maximum Signal.
 ‡ Triode Operation.
 § Conversion Transconductance.


SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Hi—Heater Tap; IC—Internal Connection; DO NOT USE, j—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; X5—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (1) Capacitances in μf .			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Plate Resistance Ohms	Transcon- ductance Microhmhos	Ampli- fication Factor	Ohms Load for Stated Power Output	Power Output Milli- watts	Type
	Bulb Size or Style	Class	Basing Diag.	Type	Volts	Amps.	Cgp.											
7C6	Lock-in	Duodiode Tri.	8W-L-7	Cathode	6.3	0.150	1.6	2.4	2.4	0.0	100	100,000	850	85	100,000	7C6	
7C7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.150	.004m	5.5	6.5	3.0	100	100,000	1,000	100	100,000	7C7	
7E5	Lock-in	Triode	8BN-L-0	Cathode	6.3	0.150	1.5	3.6	2.8	3.5	130	7E5	
7E6	Lock-in	Duodiode Tri.	8W-L-7	Cathode	6.3	0.300	1.5	3.0	2.4	3.0	100	100,000	1,500	16	100,000	7E6	
7E7	Lock-in	Duodi. Pent.	8AE-L-7	Cathode	6.3	0.300	.003m	4.6	5.5	3.0	100	100,000	1,500	16.5	100,000	7E7	
7EY6	T-9	Beam Pent.	7S	Cathode	7.21	0.600	0.7*	8.5*	7.0*	17.5	250	60,000	4,400	7EY6	
7F7	Lock-in	Duodiode	8AC-L-0	Cathode	6.3	0.300	1.6	2.4	2.0	1.0	100	65,000	1,125	70	65,000	7F7	
7F8	Lock-in	Duodiode	8BW-L-0	Cathode	6.3	0.300	1.7	2.8	1.4	2.0	100	44,000	1,600	70	44,000	7F8	
7F8W (3)	Lock-in	Duodiode	8BW-L-0	Cathode	6.3	0.300	1.6	3.0	1.7	2.0	100	50	7F8W (3)	
7G7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.450	.006m	9.0	7.0	2.0	100	800,000	4,500	7G7	
7G8	Lock-in	Duodiode	8BV-L-0	Cathode	6.3	0.300	0.15m	3.4	2.6	2.5	100	825,000	2,100	7G8	
7H7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.004m	8.0	7.0	1.5	100	350,000	4,000	7H7	
7J7	Lock-in	Tri. Heptode	8BL-L-7	Cathode	6.3	0.300	.03m	4.6	7.5	3.0	100	500,000	380A	7J7	
7K7	Lock-in	Duodiode Tri.	8BF-L-7	Cathode	6.3	0.300	1.8	2.6	3.0	2.0	100	44,000	1,600	70	44,000	7K7	
7L7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.01m	8.0	6.5	1.0	100	100,000	3,000	7L7	
7N7	Lock-in	Duodiode	8AC-L-0	Cathode	6.3	0.600	3.0	3.4	2.0	0.0	90	6,700	3,000	30	6,700	7N7	
7Q7	Lock-in	Heptode	8AL-L-0	Cathode	6.3	0.300	0.15m	9.0	9.0	2.0	100	500,000	525A	7Q7	
7R7	Lock-in	Duodi. Pent.	8AE-L-7	Cathode	6.3	0.300	.004m	5.6	5.3	2.0	100	500,000	2,100	7R7	
7S7	Lock-in	Tri. Heptode	8BL-L-7	Cathode	6.3	0.300	.03m	5.0	8.0	2.0	100	500,000	500A	7S7	
7T7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.005m	8.0	7.0	1.0	150	900,000	4,900	7T7	
7V7	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.450	.002m	9.5	6.5	160	150	300,000	5,800	7V7	
7W7	Lock-in	Pentode	8BL-L-5	Cathode	6.3	0.450	.002m	9.5	7.0	100	100,000	3,000	7W7	
7X6	Lock-in	Duodiode	7DX-L-0	Cathode	6.3	1.200	7X6	
7X7	Lock-in	Duodiode Tri.	8BZ-L-4	Cathode	6.3	0.300	7X7	
7Y4	Lock-in	Duodiode	5AB-L-0	Cathode	6.3	0.500	7Y4	
7Z4	Lock-in	Duodiode	5AB-L-0	Cathode	6.3	0.900	7Z4	
8AU8	T-6½	Tri. Pentode	9DX-0-6	Cathode	8.41	0.450	2.2*	2.8*	0.32*	8AU8	
8AU8A	T-6½	Tri. Pentode	9DX-0-6	Cathode	8.41	0.450	.046*	7.0*	2.6*	8AU8A	
8AW8A	T-6½	Tri. Pentode	9DX-0-6	Cathode	8.41	0.450	2.2	3.4	1.7	8AW8A	
8BA8A	T-6½	Tri. Pentode	9DX-0-0	Cathode	8.41	0.450	.03*	10.0*	4.5*	8BA8A	
8BH8	T-6½	Tri. Pentode	9DX-0-6	Cathode	8.41	0.450	2.4*	2.6*	3.8*	8BH8	
8BN8	T-6½	Duodiode Tri.	9ER	Cathode	8.41	0.450	2.5*	3.6*	0.32*	8BN8	
8BQ5	T-6½	Beam Pent.	9CV	Cathode	8.01	0.600	8BQ5	
8CG7	T-6½	Duodiode	9AJ-0-9	Cathode	8.41	0.450	4.0*	2.3*	2.5*	8CG7	
8CM7	T-6½	Duodiode	9ES-0-0	Cathode	8.41	0.450	3.8*	3.5*	0.4*	8CM7	
8CN7	T-6½	Duodiode Tri.	9EN-0-3	Cathode	8.41	0.225/4.21	1.8*	1.5*	0.5*	8CN7	
8CS7	T-6½	Duodiode	9EF-0-0	Cathode	8.41	0.450	2.6*	1.8*	0.5*	8CS7	

Model	Beam Pent.	Tri. Pentode	Duodiode	9EF	9DX	9HN	9DC-0-7	9A-0-0	9FA	98R8	9A8	9A7	98R8
8CY7	T-6½			7.91	0.600	1.8*	1.5*	0.3*	1.0*	5,000	8,500	40	5,200
8EB8	T-6½			8.01	0.600	4.4*	2.4	0.36	4.2	400,000	5,200	40	5,200
8EM5	T-6½			8.41	0.600	0.7*	10*	5.1*	10*	3.5	5,000	40	5,200
9A8	T-6½			9.0	0.300	0.025*	5.5*	3.8*	1.5*	18	5,000	40	5,200
9A7	T-6½			9.4/4.71	0.225/0.450	1.5	1.8	2.0	1.0	10	5,000	40	5,200
98R8	T-6½			9.45	0.300	1.8	2.5	1.0	3.5	10	5,000	40	5,200

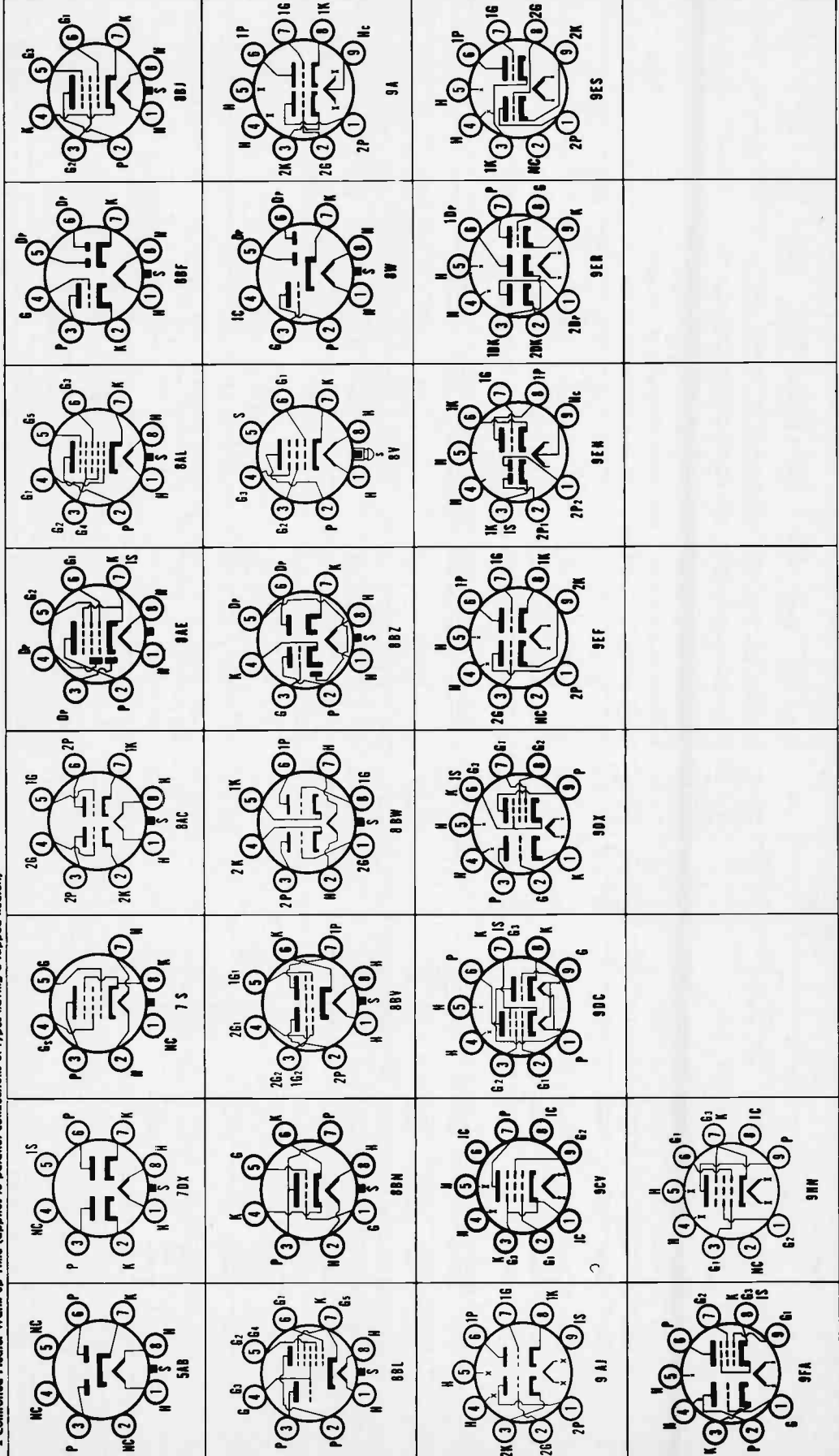(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer Output, specified grid resistor, and controlled heater warm-up time (applies to parallel connections of types having a tapped heater.)
 † Per Tube or Section.
 ‡ Plate and Target Supply Voltage.
 † Maximum Signal.
 □ Applied through 20,000 ohms.
 ‡ Conversion Transconductance.
 * Triode Operation.



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; HT—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Re—Ray Control; S—Metal Shell; SA—Starter; Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (2) Capacitance in μf .			Use	Plate Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Micromhos	Ampli- fication Factor	Other Lead for Rated Power Output	Power Output Milli- watts	Type
	Bulb Size or Style	Class	Beaming Diag.	Type	Volts	Amps.	Cap.											
9CL8	T-6½	Tri. Tetrode	9FX-0-0	Cathode	9.51	0.300	1.8 .016	2.7 5.0	1.2 3.0	Characteristics Same as Type 6CL8. (9CL8 Designed for Series String TV Receivers).								9CL8
9DZ8	T-6½	Tri. Beam Pent.	6DZ8	Cathode	9.0	0.600	Characteristics Same as Type 6DZ8. (9DZ8 Designed for Series String Receivers).								9DZ8			
9EF6	T-9	Beam Pent.	7S	Cathode	9.41	0.600	0.8*	11.5*	9.0*	Characteristics Same as Type 6EF6. (9EF6 Designed for Series String TV Receivers).								9EF6
9UBA	T-6½	Tri. Pentode	9AE	Cathode	9.451	0.300	1.8 .006	2.5 5.0	1.0 3.5	Characteristics Same as Type 6UB. (9UBA Designed for Series String TV Receivers).								9UBA
9X8	T-6½	Tri. Pentode	9AK	Cathode	9.51	0.300	1.4 .06	2.6 4.5	1.0 1.4	Characteristics Same as Type 6X8. (9X8 Designed for Series String TV Receivers).								9X8
10	ST-16	Triode	4D-0-0	Filament	7.5	1.250	7.0*	4.0*	3.0*	950 350 485 40.0	10.0 16.0 18.0	135 11.5	3.2 8,000	6,000 1,330 1,550 1,600 1,600	8.0 8.0 8.0 8.0	13,000 4,500 11,000 10,200	400 900 1,600	10
10C8	T-6½	Tri. Pentode	9DA-0-9	Cathode	10.51	0.300	1.6* .04*	2.4* 7.0*	0.2* 2.2*	Characteristics Same as Type 6C8. (10C8 Designed for Series String TV Receivers).								10C8
10DA7	T-6½	Duotriode	9EF-0-0	Cathode	10.51	0.600	2.3* 6.9*	2.0* 5.5*	0.415* 0.82*	Characteristics Same as Type 6DA7. (10DA7 Designed for Series String TV Receivers).								10DA7
10DE7	T-6½	Duotriode	9HF	Cathode	9.71	0.600	4.0* 8.5*	2.2* 5.5*	0.52* 1.0*	Characteristics Same as Type 6DE7. (10DE7 Designed for Series String TV Receivers).								10DE7
11C5	T-5½	Beam Pent.	7CV	Cathode	11.61	0.450	0.6*	1.5*	0.3*	Characteristics Same as Type 35C5. (11C5 Designed for Series String TV Receivers).								11C5
11CY7	T-6½	Duotriode	9EF	Cathode	11.1	0.450	1.8* 4.4*	5.0* 1.0*	0.3* 1.0*	Characteristics Same as Type 6CY7. (11CY7 Designed for Series String TV Receivers).								11CY7
12A4	ST-14	Triode	4D-0-0	Filament	5.0	0.950	8.5*	4.0*	2.0*	180 13.5	9.0	7.7	4,700	1,800	8.5	10,650	285	12A4
12A5	T-6½	Beam Pent.	7E-0-0	Cathode	13.6	0.300	0.3	9.0	9.0	100 180	15.0 25.0	100 45.0	3.0 3,000	1,700 4,000	30	4,500 3,300	800 3,400	12A5
12A6	Metal	Beam Pent.	7S-1-0	Cathode	13.6	0.150	Characteristics Same as Type 6A8G.								12A6			
12A6GT	T-9	Diode Pent.	7K-0-0	Cathode	13.6	0.300	Characteristics Same as Type 6A8G.								12A6GT			
12A7	ST-12	Diode Pent.	7K-0-0	Cathode	13.6	0.300	Characteristics Same as Type 6A8G.								12A7			
12A8G	T-12	Heptode	8A-1-0	Cathode	12.6	0.150	0.26	9.5	12.0	Characteristics Same as Type 6A8G.								12A8G
12A8GT	T-9	Heptode	8A-1-0	Cathode	12.6	0.150	0.26	9.5	12.0	Characteristics Same as Type 6A8G.								12A8GT
12AC6	T-5½	Pentode	7BK	Cathode	12.6	0.150	.004	4.3	5.0	12.6 0	12.6 550 μa .	900 μa .	0.5 Meg.	730	8.5	10,650	285	12AC6
12AD5	T-6½	Pentode	9AZ	Cathode	12.6	0.100	.002m*	5.1	8.1	100 2.5	100 6.0	1.75	600,000 μa .	2,200	30	4,500	800	12AD5
12AD6	T-5½	Heptode	7CH	Cathode	12.6	0.150	0.25m	8.0	13	12.6 1.6	12.6 450 μa .	1.5	360A	3,600	100	7,500	3,400	12AD6
12AD7	T-6½	Duotriode	9A	Cathode	12.6/6.3	0.325/1.8	1.7 1.7	1.6 1.9	1.9	250 2	135 9.0	1.35	69,500	1,600	100	7,500	3,400	12AD7
12AE6	T-5½	Duotriode Tri.	7DT	Cathode	12.6	0.150	2.0	1.8	1.1	12.6 0	12.6 0.75	1.4	15,000	1,000	15	13,000	550	12AE6
12AF3	T-6½	Diode	9CB	Cathode	12.61	0.600	.006*	5.5*	4.8*	Characteristics Same as Type 6AF3. (12AF3 Designed for Series String Receivers).								12AF3
12AF6	T-5½	Pentode	7BK-0-2	Cathode	12.6	0.150	.006*	5.5*	4.8*	12.6 0	12.6 1.1	0.45	0.35 Meg.	1,500	30	4,500	800	12AF6
12AG6	T-5½	Heptode	7CH	Cathode	12.6	0.150	.065m*	5.5*	7.5*	12.6 0.85	12.6 0.35	1.4	300A	3,000	100	7,500	3,400	12AG6
12AH7GT	T-9	Duotriode	8BE-0-0	Cathode	12.6	0.150	2.0 2.2	3.8 3.2	2.6 3.0	100 180	3.6 6.5	3.7 7.6	10,300 8,400	1,550 1,900	16 55	10,300 8,400	16 55	12AH7GT
12AJ6	T-5½	Duotriode Tri.	7DT	Cathode	12.6	0.150	2.0*	2.2*	0.8*	Characteristics Same as Type 6AL5.								12AJ6
12AL5	T-5½	Duotriode	6BT-0-6	Cathode	12.6	0.150	5.7*	1.8*	0.4*	Characteristics Same as Type 6AL5.								12AL5
12AL8	T-6½	Tri. Tetrode	9GS	Cathode	12.6	0.550	14.0*	13.0*	1.6*	12.6 0	12.6 0.75	1.4	13,000 480	1,000 15,000	13	13,000 480	15,000	12AL8
12AQ5	T-5½	Beam Pent.	7BZ-0-0	Cathode	12.6	0.325	0.35*	8.3*	8.2*	Characteristics Same as Type 6AQ5.								12AQ5
12AU7	T-5½	Duotriode Tri.	7BT-0-0	Cathode	12.6	0.150	2.1*	2.2*	1.1*	Characteristics Same as Type 6A16.								12AU7
12AU7A	T-5½	Duotriode Tri.	7BT-0-0	Cathode	12.6	0.150	2.1*	2.2*	1.1*	Characteristics Same as Type 6A16.								12AU7A
12AV7	T-6½	Duotriode	9A-0-0	Cathode	6.3	0.300	1.45* 1.45*	2.5* 2.5*	0.45* 0.35*	100 270*	270*	3.7	4,000	60	60	4,000	60	12AV7
12AV6	T-5½	Pentode	7BK-0-2	Cathode	12.6	0.150	.0035m*	5.5*	5.0*	Characteristics Same as Type 6AV6.								12AV6
12AV7	T-6½	Duotriode	9A-0-0	Cathode	6.3	0.300	1.5* 1.6*	1.6* 0.32*	0.4* 0.32*	Characteristics Same as Type 6AV7.								12AV7
12AV5GA	T-11 or T-12	Beam Pent.	6CK-0-0	Cathode	12.61	0.600	0.5*	14.0*	7.0*	Characteristics Same as Type 6AV5GA. (12AV5GA Designed for Series String TV Receivers).								12AV5GA
12AW6	T-5½	Pentode	7CM-0-7	Cathode	12.6	0.150	.095m*	6.5*	1.3*	Characteristics Same as Type 6AV6.								12AW6
12AX4GT	T-9	Diode	4CG-0-0	Cathode	12.6	0.600	P.I.V. = 4,400 Volts Max. D.C. Plate Current = 195 Ma. Max. (12AX4GT Designed for Series String TV Receivers).								12AX4GT			
12AX4G1A	T-9	Diode	4CG-0-0	Cathode	12.61	0.600	P.I.V. = 4,400 Volts Max. D.C. Plate Current = 195 Ma. Max. (12AX4G1A Designed for Series String TV Receivers).								12AX4G1A			

12AX7	T-6½	Duotriode	9A-0-0	Cathode	12.6 6.3	0.150 0.300	1.7* 1.7*	1.6* 0.34*	0.46* 0.34*	Amplifier#	100 250	1	2	0.5 1.2	80,000 62,500	1,250 1,600	100 100	12AX7
12AX7A	T-6½	Duotriode	9A	Cathode	12.6 6.3	0.150 0.300	1.7* 1.7*	1.6* 0.34*	0.46* 0.34*	Audio Amplifier	250 500	4.0	3.0	3.0 10.0	1,750 10,900	4,000 5,500	40 60	12AX7A
12AZ7	T-6½	Duotriode	9A-0-0	Cathode	12.6 6.3	0.150 0.300	1.3* 1.9	1.3* 2.8	0.6* 1.2	Audio Amp.#	250 500	4.0	3.0	3.0 10.0	1,750 10,900	4,000 5,500	40 60	12AZ7
12B3	T-6½	Diode	98D-0-0	Cathode	12.6†	0.600	4.0	6.2	4.2	T.V. Detector	150	1.5	3.5	3.5	6,500	6.5	12B3	
12B4	T-6½	Triode	9A-G-0-0	Cathode	12.6	0.300	4.0	6.2	4.2	Ver. Defl. Amp.	150	1.5	3.5	3.5	6,500	6.5	12B4	

(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output. (4) Average contact potential bias developed across specified grid resistor.
 † Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater).

□ Applied through 20,000 ohms.
 † Plate to Plate.
 ‡ Conversion Transconductance.
 †† Triode Operation.
 m maximum.
 = Cathode Resistor (ohms).

	4CG		6DZ8		6CK		6BT		7CH		7CK		7CY		7CA		7CB		7CC		7CD		7CE		7CF		7CG		7CH		7CI		7CJ		7CK		7CL		7CM		7CN		7CO		7CP		7CQ		7CR		7CS		7CT		7CU		7CV		7CW		7CX		7CY		7CZ		8BE		8BA		8BB		8BC		8BD		8BE		8BF		8BG		8BH		8BI		8BJ		8BK		8BL		8BM		8BN		8BO		8BP		8BQ		8BR		8BS		8BT		8BU		8BV		8BW		8BX		8BY		8BZ		9A		9AE		9AF		9AG		9AH		9AI		9AJ		9AK		9AL		9AM		9AN		9AO		9AP		9AQ		9AR		9AS		9AT		9AU		9AV		9AW		9AX		9AY		9AZ		9BA		9BB		9BC		9BD		9BE		9BF		9BG		9BH		9BI		9BJ		9BK		9BL		9BM		9BN		9BO		9BP		9BQ		9BR		9BS		9BT		9BU		9BV		9BW		9BX		9BY		9BZ		9CA		9CB		9CC		9CD		9CE		9CF		9CG		9CH		9CI		9CJ		9CK		9CL		9CM		9CN		9CO		9CP		9CQ		9CR		9CS		9CT		9CU		9CV		9CW		9CX		9CY		9CZ
--	-----	--	------	--	-----	--	-----	--	-----	--	-----	--	----	--	-----	--	-----	--	-----	--	-----	--	-----

SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grid numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection, DO NOT USE, j—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.


PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Notes (1) (†) Capacitances in μ f.		Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milli-watts	Type
	Base Size of Style	Class	Beam	Diode	Type	Volts												
12B7	1-9	New Known as Type 14A7																12B7
12BG1	1-9	Pentode Tri.	81-0-1	Cathode	12.6	0.300	0.15*	5.2	9.6*	3.0	7.0	2.0	300,000	1,800	90	(Penode Section)	12BG1	
12BA6	1-5 1/2	Pentode	78K-0-0	Cathode	12.6	0.150	.0035*	5.5*	5.5*	Characteristics Same as Type 68A6.							12BA6	
12BA7	1-6 1/2	Heptode	8CT-0-648	Cathode	12.6	0.150	.0035*	5.5*	5.5*	Characteristics Same as Type 68A7.							12BA7	
12BD6	1-5 1/2	Pentode	78K-0-2	Cathode	12.6	0.150	.004	4.3	8.3	Characteristics Same as Type 68D6.							12BD6	
12BE6	1-5 1/2	Heptode	7CH-0-0	Cathode	12.6	0.150	.004	7.0*	8.0*	Characteristics Same as Type 68E6.							12BE6	
12BF6	1-5 1/2	Heptode Tri.	781-0-0	Cathode	12.6	0.150	1.9*	1.9*	1.2*	D.C. Amp.							12BF6	
12BH7	1-6 1/2	Duodiode	9A-0-0	Cathode	6.3/12.6	0.600/0.300	2.4	3.0	2.0	Max Peak Poi. Plate Voltage = 1,500 Volts Max. D.C. Cathode Current = 30 Ma. Max. Plate Dissipation = 3.5 Watts. (12BH7A Designed for Series String TV Receiver).								12BH7A
12BK5	1-6 1/2	Beam Amp.	9BQ-0-0	Cathode	12.6	0.600	0.6*	13.0*	5.0*	Characteristics Same as Type 68K5. (12BK5 Designed for Series String TV Receiver).							12BK5	
12BL6	1-5 1/2	Duodiode Tri.	781-0-2	Cathode	12.6	0.150				1.0	0.5	80,000	1,250	100			12BL6	
12BN6	1-5 1/2	Pentode	78K	Cathode	12.6	0.150	.006	5.5	4.8	R-F Amp.							12BN6	
12BN6	1-5 1/2	Control Beam	7DF-0-1	Cathode	12.6	0.150				Class A1 Amp. F. M. Det.							12BN6	
12BO6GA	1-11	Beam Pent.	6AM-0-0	Cathode	12.6	0.600	0.8*	14.0*	6.5*	Characteristics Same as Type 68O6GA. (12BO6GA and 12BO6GTA Designed for Series String TV Receiver).							12BO6GA	
12BO6GTA	1-9	Beam Pent.	6AM-0-0	Cathode	12.6	0.600	0.6*	15.0*	7.5*	Characteristics Same as Type 68O6GTA.							12BO6GTA	
12BG6G1B	1-9	Beam Pent.	9CF	Cathode	12.6/12.6	0.325/0.330	1.9	2.8	1.0	Characteristics Same as Type 68G6G1B. (12BG6G1B Designed for Series String TV Receiver).							12BG6G1B	
12BR7	1-6 1/2	Duodiode Tri.	781-0-3	Cathode	12.6	0.150				100	270	10.0	15,000	4,900	60			12BR7
12BT6	1-5 1/2	Duodiode Tri.	781-0-3	Cathode	12.6	0.150				250	300	1.0	10,900	2,500	60			12BT6
12BU6	1-5 1/2	Duodiode Tri.	781-0-3	Cathode	12.6	0.150				100	1.0	0.8	54,000	1,300	70			12BU6
12BV7	1-6 1/2	Duodiode	9DJ	Cathode	12.6	0.300/0.600				250	3.0	3.9	11,000	1,900	16.5			12BV7
12BW4	1-6 1/2	Duodiode	98F-0-349	Cathode	12.6	0.450				100	9.0	9.5	8,500	1,500	16			12BW4
12BW7	1-6 1/2	Pentode	98F-0-349	Cathode	12.6	0.300				250	68	6.0	85,000	13,000	10,000			12BW7
12BX7	1-6 1/2	Duodiode	9A-0-0	Cathode	12.6	0.600/0.300	0.45	6.3	3.0*	Class A1 Amp. F.W. Rect.								12BX7
12C5	1-5 1/2	Beam Pent.	7CV-0-0	Cathode	12.6	0.600	0.6*	13.0*	8.5*	Sync Sep. or Amplifier								12C5
12C8	Metal	Duodi. Pent.	8E-1-1	Cathode	12.6	0.150	.003m	6.0	9.0	Power Amp. (12C5 Designed for Series String TV Receiver).								12C8
12CA3	1-5 1/2	Pentode	7CV-0-0	Cathode	12.6	0.600	0.3*	15.0*	9.0*	D.C. Amp. Power Amp.								12CA3
12CM6	1-6 1/2	Beam Pent.	9CK-0-0	Cathode	12.6	0.325	0.7	8.0*	8.5*	Characteristics Same as Type 6CA5. (12CA3 Designed for Series String TV Receiver).								12CM6
12CN5	1-5 1/2	Pentode	7CV	Cathode	12.6	0.450	0.2	12.6	4.5	Characteristics Same as Type 6CM6.								12CN5
12CR5	1-6 1/2	Beam Pent.	9HC-0-0	Cathode	12.6	0.600	0.32*	12.9*	6.9*	L.F. Amp. 12.6 [2.2Meg. 12.6 4.5								12CR5
12CR6	1-5 1/2	Diode Pent.	7EA	Cathode	12.6	0.150				Characteristics Same as Type 6CR5. (12CR5 Designed for Series String TV Receiver).								12CR6
12CS5	1-6 1/2	Beam Pent.	9CK	Cathode	12.6	0.600				9	100	9.6	800,000	9,900				12CS5
12CS6	1-5 1/2	Dual Control Heptode	7CH-0-0	Cathode	12.6	0.150	.05m	5.5	7.5	Characteristics Same as Type 6CS5. (12CS5 Designed for Series String TV Receiver.)								12CS6
12CT8	1-6 1/2	Tri. Pentode	9DA-0-9	Cathode	12.6	0.300	2.2*	2.4*	0.19*	100	0.0Gr./f1	30	700,000	950 Gr. f1	Grid #3 Volts = 0			12CT8
12CU5	1-5 1/2	Beam Pent.	7CV	Cathode	12.6	0.600	0.6*	13*	8.5*	100	1.0Gr./f1	30	1,100,000	1,350 Gr. f3	Grid #3 Volts = 1.0			12CU5
12CV6	1-5 1/2	Pentode	78K	Cathode	12.6	0.150	.05*	7.6*	6.2*	200	82	3.4	8,200	4,900	40			12CV6
12D4	1-9	Diode	4CG-0-0	Cathode	12.6	0.600				Sync. Amp. Video Amp.								12D4
12DB5	1-6 1/2	Beam Pent.	9GR-0-0	Cathode	12.6	0.600	0.2	1.3	8.0	Power Amp. (12CU6 Designed for Series String TV Receiver.)								12DB5
12DE8	1-6 1/2	Diode Pent.	12DE8	Cathode	12.6	0.200	.006*	5.5*	5.7*	Horiz. Def. Amp.								12DE8
12DF5	1-6 1/2	Duodiode	98S	Cathode	12.6	0.450				R-F Amp. T.V. Damper								12DF5
12DF7	1-6 1/2	Duodiode	9A	Cathode	12.6	0.150	1.4*	1.6*	0.4*	Characteristics Same as Type 12AX7. (Special Low Noise).								12DF7
12DK5	1-6 1/2	Pentode	9GT	Cathode	12.6	0.300	.045	9.5	2.65	R-F Amp. D.C. Amp. Driver								12DK5
12DK7	1-6 1/2	Duodiode	9HZ	Cathode	12.6	0.300				12.6	15 Meg.	1.0	4,000	5,000				12DK7
12DL8	1-6 1/2	Duodiode	9HR	Cathode	12.6	0.350	1.4*	12*	1.3*	Max. Inverse Peak Plate Voltage = 4,400 Volts. Maximum D.C. Plate Current = 135 Ma.								12DL8
12DM5	1-5 1/2	Beam Pent.	7CV	Cathode	12.6	0.450	0.55*	13.0*	9.0*	Characteristics Same as Type 6DB5. (12DB5 Designed for Series String TV Receiver.)								12DM5

12DQ6	T-12	Beam Peni.	6AM-0-0	Cathode	12.6I	0.600	0.59*	15.0*	7.0*	Horiz. Def. Amp.	Characteristics Same as Type 6DQ6. (12DQ6 Designed for Series String TV Receivers.)	12DQ6
12DQ6A	T-12	Beam Peni.	6AM	Cathode	12.6I	0.600	0.55*	15.0*	7.0*	Horiz. Def. Amp.	Characteristics Same as Type 6DQ6A. (12DQ6A Designed for Series String TV Receivers.)	12DQ6A
12DQ7	T-6½	Pentode	9BF	Cathode	12.6I / 0.300 / 0.600	0.1*	10*	3.8*	3.8*	Video Amp.	200 68 125 26 5.6 53,000 10,500 Instantaneous Plate Knee Values: EB = 40 Volt, EC = 125 Volt, EC = 0 Volt, IB = 45 Ma. and IC = 16 Ma.	12DQ7
12D57	T-6½	Duodiode Tetrode	9JU	Cathode	12.6	0.400	12.5*	13*	2*	Def. Power Amp. Driver	12.6 2.2 Meg. G1 = 12.6, 40-8T (Space-Charge Grid Operation).	800 40 12D57

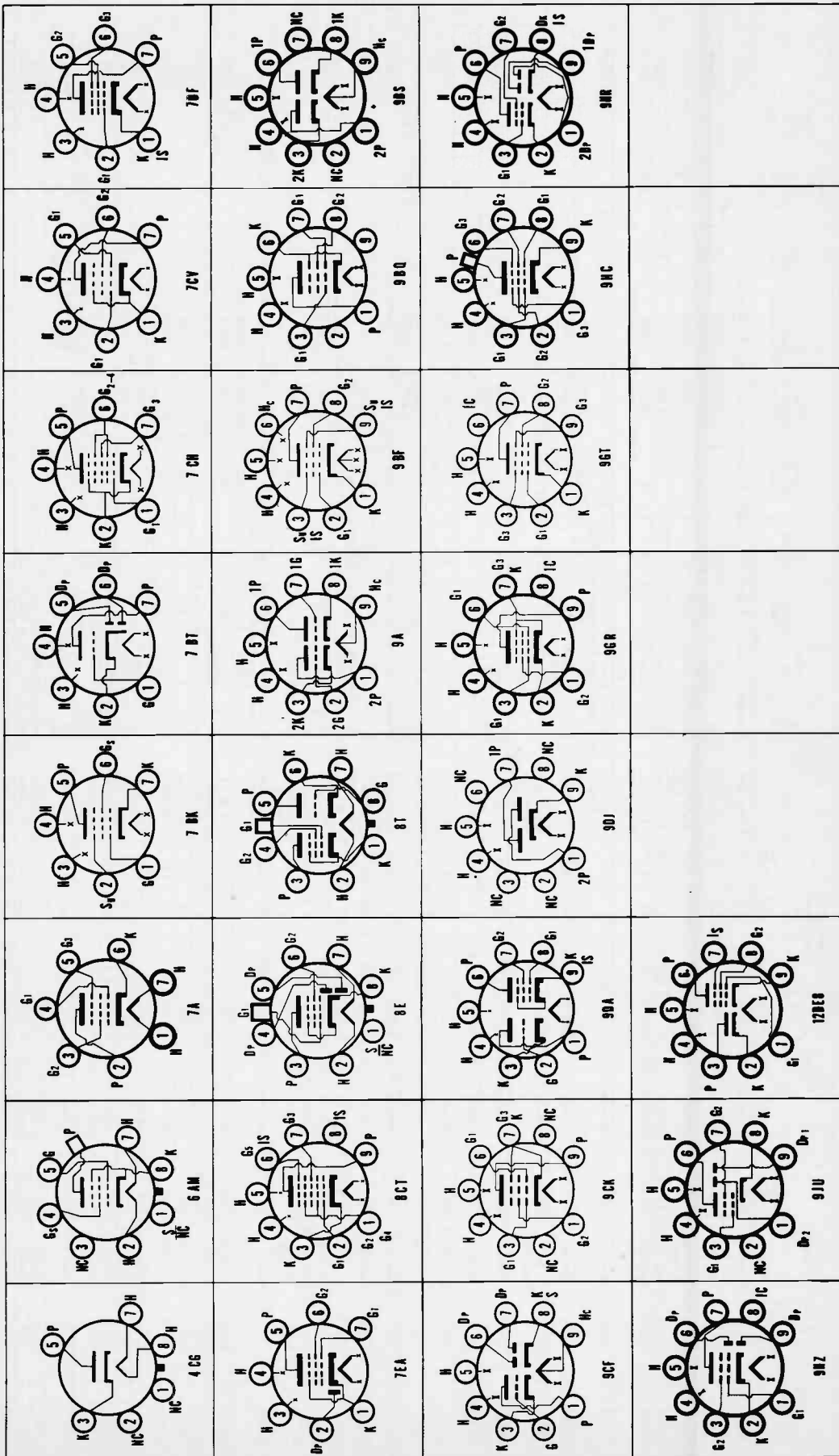(1) Values are given shaded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output, specified grid to plate.
 X Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

□ Applied through 20,000 ohms.
 † Per Tube or Section.
 ‡ Plate and Target Supply Voltage.
 † Maximum Signal.
 ‡ Triode Operation.
 †† Plate to Plate.
 ††† Cathode Resistor (Ohms).
 †††† Approximate.



SYMBOLS FOR BASE DIAGRAMS: F—Filament; FC—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; HI—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Spacer Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.


PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (†) Capacitances in μ f.		Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Microamhos	Amplification Factor	Ohm Load for Series String Power Output	Power Output Milliwatts	Type	
	Bulb Size or Style	Class	Beam Pent.	Beam Pent.	Type	Volts													Amps.
12D15	T-6½	Beam Pent.	9H-N	Beam Pent.	12.61	0.600	0.57*	12.5*	4.9*	100 250	270 ^a 200 ^b	3.7 1.0	15,000 10,000	4,000 5,500	60 60	2,700	25	12D15	
12D18	T-6½	Duodiode	9DE	Duodiode	12.6	0.150	1.6	2.7	1.6	12.6	2.2 Meg.	12.6	6,000	6,200	12D18	
12D17	T-6½	Duodiode Tri.	9JX	Duodiode Tri.	12.6	0.275	0.6*	11*	3.6*	12.6	2.2 Meg.	12.6	6,000	6,200	2,700	25	12D17	
12DV7	T-6½	Duodiode Tri.	9JV	Duodiode Tri.	12.6	0.150	1.6*	1.3*	0.38*	12.6	2.2 Meg.	12.6	6,000	6,200	12DV7	
12DV8	T-6½	Duodiode Triode	9HR	Duodiode Triode	12.6	0.375	1.2*	9*	1.0*	12.6	18 Ohm ^a G1=12.6 4.7 Meg.	6.8	54	8,500	7.6	1,250	5	12DV8	
12DW5	T-6½	Beam Pent.	9CK	Beam Pent.	12.61	0.600	0.5	14	9	12.6	2.2 Meg.	12.6	2,000	5,500	12DW5	
12DZ6	T-6½	Pentode	7BK	Pentode	12.6	0.190	0.15m*	9.5*	4.0*	12.6	10 Meg. ^a G3=0	4.5	2.2	3,800	12DZ6	
12DZ8	T-6½	Tri. Beam Pent.	6DZ8	Tri. Beam Pent.	12	0.450	12.6	10 Meg. ^a G3=0	4.5	2.2	3,800	12DZ8	
19E5GT	T-9	Triode	6Q-1-0	Triode	12.6	0.150	2.6	3.4	5.5	100 250	5.0 13.5	19,000 9,500	1,150 1,450	13.8 13.8	19E5GT
12EA6	T-5½	Pentode	7BK	Pentode	12.6	0.190	.04m*	11*	4*	12.6	10 Meg. ^a G3=0	3.2	1.4	32,000†	3,800	12EA6	
12EC8	T-6½	Tri. Pentode	9FA	Tri. Pentode	12.6	0.225	1.7	2.6	0.4	12.6	0	2.4	0.28	6,000	4,700	12EC8	
12ED5	T-5½	Pentode	7CV	Pentode	12.6	0.450	0.26	14	8.5	110 110	4.0 4.5	110 125	4 7	14,000 14,000	8,100 8,500	4,500 1,500	1,100 1,500	12ED5
12EF6	T-9	Beam Pent.	7S	Beam Pent.	12.61	0.450	0.8*	11.5*	9.0*	12.6	15 Meg. ^a	6.0	1.0	4,000	5,000	3,500	10	12EF6
12EG6	T-5½	Heptode	7CH	Heptode	12.6	0.150	0.25	6.5	12	12.6	0.8 ^a	12.6	0.4	150,000	800	12EG6
12EH5	T-5½	Beam Pent.	7CV	Beam Pent.	12.61	0.600	0.65*	17*	9*	12.6	0.8 ^a G1=10 Meg. ^a G2=0	3.2	1.4	32,000†	3,800	12EH5
12EK6	T-5½	Pentode	7BK	Pentode	12.6	0.190	.032	10	5.5	12.6	2.2 Meg. ^a	12.6	4.4	40,000	4,200	12EK6
12EL6	T-5½	Duodiode Tri.	7FB	Duodiode Tri.	12.6	0.150	1.8*	2.2*	1.0*	12.6	1.0 Meg. ^a	7.5	45,000	1,200	12EL6
12EM6	T-6½	Diode Tetrode	9HY	Diode Tetrode	12.6	0.500	12.6	15 Meg. ^a	6.0	1.0	4,000	5,000	3,500	10	12EM6
12EN6	T-9	Beam Pent.	7S	Beam Pent.	12.61	0.600	0.65*	14*	8.0*	12.6	0.8 ^a G1=10 Meg. ^a G2=0	3.2	1.4	32,000†	3,800	12EN6
12EZ6	T-5½	Pentode	7BK	Pentode	12.6	0.175	.008*	7.8*	5.5*	12.6	0.7	12.6	1.9	400,000	2,700	12EZ6
19F5GT	T-9	Triode	5M-0-0	Triode	12.6	0.150	2.8*	2.2*	3.2*	12.6	0.7	12.6	1.9	400,000	2,700	19F5GT
19F8	T-6½	Duodi. Pent.	9FH	Duodi. Pent.	12.6	0.150	0.6*	4.5	3.0	12.6	0	12.6	1.0	0.38	0.33 Meg.	1,000	19F8
12FA6	T-5½	Heptode	7CH	Heptode	12.6	0.150	0.25	7.2	12	12.6	0.5	12.6	4.5	1.0	800,000	370 ^a	12FA6
12FK6	T-5½	Duodiode Tri.	7BT	Duodiode Tri.	12.6	0.150	1.6*	1.8*	0.7*	12.6	2.2 Meg. ^a	1.3	6,200	1,200	12FK6
12FM6	T-5½	Duodiode Tri.	7DT	Duodiode Tri.	12.6	0.150	1.7*	2.7*	1.7*	12.6	2.2 Meg. ^a	1.0	7,700	1,300	12FM6
19G4	T-5½	Triode	6BG	Triode	12.6	0.150	3.4	2.6	3.2	12.6	2.2 Meg. ^a	1.0	7,700	1,300	19G4
19G8	T-6½	Duodiode	9CZ	Duodiode	12.6	0.400	12.6	0	Input Tri. 7.2 Output Tri. 7.2	8,500	2,600	2,000	25	19G8
19H4	T-5½	Triode	7DW	Triode	6.3/12.6	0.300/0.150	3.4	2.6	3.2	90 250	0 8	3,000	2,600	19H4
19H6	Metal	Duodiode	7O-1-1	Duodiode	12.6	0.150	12.6	0	3,000	2,600	19H6
19J5GT	T-9	Triode	6Q-0-0	Triode	12.6	0.150	3.8	4.2	5.0	12.6	0	19J5GT
19J7GT	T-9	Pentode	7R-1-1	Pentode	12.6	0.150	.007m	5.4	12.0	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	20	19J7GT
12J8	T-6½	Duo. Tetrode	9GC	Duo. Tetrode	12.6	0.300	0.7*	10.5*	4.4*	12.6	G2=2 G1=12.6	8	1.5	6,000	5,500	2,700	40	12J8
12K5	T-5½	Tetrode	7FD	Tetrode	12.6	0.400	12.6	G2=2 G1=12.6	8	7.5	480	15,000	7.2	800	40	12K5
19K7GT	T-9	Pentode	7R-1-8	Pentode	12.6	0.150	.007m	5.0	12.0	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	20	19K7GT
19K8	Metal	Tri. Hexode	8K-1-8	Tri. Hexode	12.6	0.150	.03m	6.6	3.5	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	40	19K8
19L6GT	T-9	Beam Pent.	7S-0-0	Beam Pent.	12.61	0.600	12.6	0	19L6GT
19L8GT	T-9	Duo. Pentode	8BU-0-0	Duo. Pentode	12.6	0.150	0.7*	5.0*	6.0*	110 180	5.5 110	5.1F 1.8F	2.8F	320,000† 160,000†	1,680† 1,150†	14,000† 10,000†	300† 1,000†	19L8GT
19Q7GT	T-9	Duodiode Tri.	7V-1-8	Duodiode Tri.	12.6	0.150	1.6	2.2	5.0	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	20	19Q7GT
12R5	T-5½	Beam Pent.	7CV-0-0	Beam Pent.	12.61	0.600	0.55*	13.0*	9.0*	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	20	12R5
19S9GT	T-9	Triple Dio. Tri.	8CB-0-2	Triple Dio. Tri.	12.6	0.150	2.0	1.2	5.0	12.6	2.2 Meg. ^a	12.6	1.2	6,000	5,500	2,700	20	19S9GT

19SA7 19SA7GT 19SC7	Metal 1-9	Heptode 8A-1-0	Cathode 12.6	0.150	0.25	9.5	Converter	Characteristics Same as Type 6SA7.
		8AD-1-6		0.5m	11.0	11.0		
		8S-1-0		2.0	3.2	3.0	Amplifier	Characteristics Same as Type 6SC7

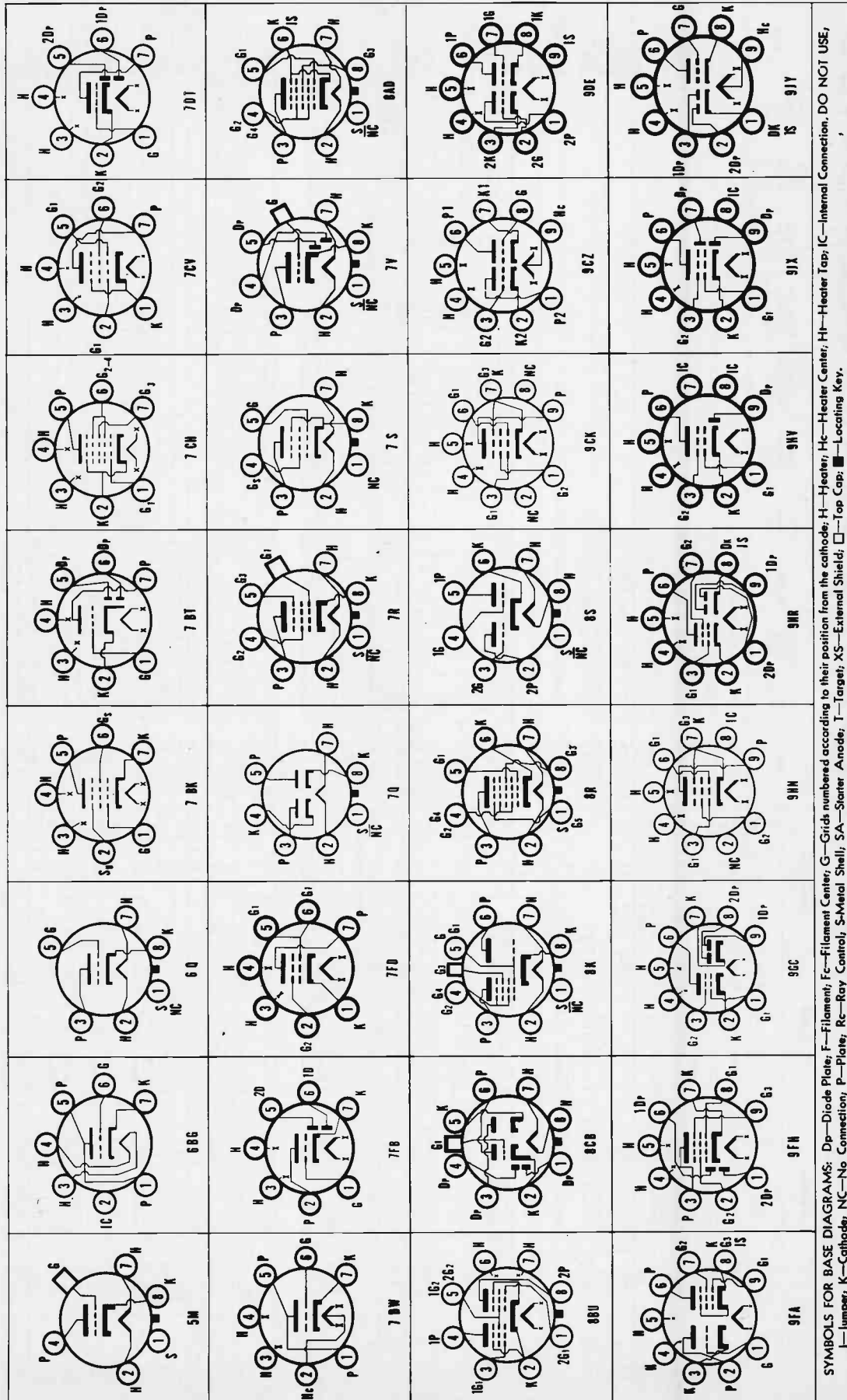(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
(2) Converter tube capacitance given are signal (4) Average Contact potential bias developed across grid to plate; RC Input; Mixer Output.
X Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

□ Applied through 20,000 ohms.
△ Conversion Transconductance.
† Plate to Plate.
‡ Approximate.
m maximum.
= Cathode Resistor (ohms).




SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction			Emitter			Note (1) (7) Capacitances in $\mu\mu\text{f}$.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milliwatts	Type		
	Bulb Size or Style	Class	Beating Diag.	Type	Volts	Amps.	Csp.	Cin.	Coef.														
19SF5	Metal T-9	Triode	6AB-0-0	Cathode	12.6	0.150	9.4	4.0	3.6	Amplifier	Characteristics Same as Type 6SF5.										19SF5		
19SF5GT																						19SF5GT	
19SF7	Metal	Diode Pent.	7AZ-1-0	Cathode	12.6	0.150	.004m	5.5	6.0	Det. Amp.	Characteristics Same as Type 6SF7.											19SF7	
19SG7	Metal	Pentode	8BK-1-1	Cathode	12.6	0.150	.003m	8.5	7.0	R-F Amp.	Characteristics Same as Type 6SG7.											19SG7	
19SH7	Metal T-9	Pentode	8BK-1-1	Cathode	12.6	0.150	.003m	8.5	7.0	R-F Amp.	Characteristics Same as Type 6SH7.											19SH7	
19SH7GT																						19SH7GT	
19SJ7	Metal T-9	Pentode	8N-1-1	Cathode	12.6	0.150	.003m	6.0	7.0	R-F Amp.	Characteristics Same as Type 6SJ7.											19SJ7	
19SJ7GT																						19SJ7GT	
19SK7	Metal T-9	Pentode	8N-1-5	Cathode	12.6	0.150	.003m	6.3	7.5	R-F Amp.	Characteristics Same as Type 6SK7.											19SK7	
19SK7GT																						19SK7GT	
19SL7GT	T-9	Duodiode	8BD-0-0	Cathode	12.6	0.150				Amplifier	Characteristics Same as Type 6SL7GT.											19SL7GT	
19SN7GT	T-9	Duodiode	8BD-0-0	Cathode	12.6	0.300	3.8*	3.0*	1.8*	Amplifier	Characteristics Same as Type 6SN7GT.											19SN7GT	
19SN7GTA	T-9	Duodiode	8BD-0-0	Cathode	12.6	0.300	4.0*	3.0*	0.7*	Vertical Osc. Amp.	Characteristics Same as Type 6SN7GTA.											19SN7GTA	
19SQ7	Metal T-9	Duodiode Tri.	8Q-1-3	Cathode	12.6	0.150	1.6	2.8	3.0	Det. Amp.	Characteristics Same as Type 6SQ7.											19SQ7	
19SQ7GT																						19SQ7GT	
19SR7	Metal	Duodiode Tri.	8Q-1-1	Cathode	12.6	0.150	1.8	4.2	3.4	Det. Amp.	Characteristics Same as Type 6SR7.											19SR7	
19SW7	Metal	Duodiode Tri.	8Q-1-0	Cathode	12.6	0.150	2.3	3.0	3.0	Det. Amp.	Characteristics Same as Type 6SR7.	26.5 Self	1.1	9.5	17	15,500	1,100	1,900	16	(2 Mes. Grid Res.)		19SW7	
19SX7GT	T-9	Duodiode	8BD-0-0	Cathode	12.6	0.300	3.6*	2.8*	0.8*	Amplifier	Characteristics Same as Type 6SX7GT.	90.0 Self				11,500	1,800	3,000	80	(.05 Mes. Grid Res.)		19SX7GT	
19SY7	Metal	Heptode	8R-1-0	Cathode	12.6	0.150	0.13*	9.5*	12.0*	Converter	Characteristics Same as Type 6SY7.	250	2.0	100	3.5	12,500	1,600	450				19SY7	
19U7	T-6½	Duodiode	7CK	Cathode	12.6	0.150	1.5	1.8	2.0	Class A1 Amp.	Characteristics Same as Type 6U7.	12.6	0	1.0	8.5	1 Mes.	1 Mes.	1 Mes.				19U7	
19V6GT	T-9	Beam Pent.	7S	Cathode	12.6	0.225	0.7	9.0	7.5	Power Amp.	Characteristics Same as Type 6V6GT.	180	8.5	180	9.0	50,000	3,700	2,000	5,500			19V6GT	
19W6GT	T-9	Beam Pent.	7S-0-0	Cathode	12.6†	0.600	0.8*	15.0*	9.0*	Power Amp. Vert. Defl. Amp.	Characteristics Same as Type 6W6GT. (19W6GT Designed for Series String TV Receivers).	250	12.5	250	4.5	50,000	4,100	5,000	5,000			19W6GT	
19X4	T-5½	Duodiode	5BS	Cathode	12.6	0.450				F-W Rect.	Characteristics same as Type 6X4.											19X4	
19Z3	T-9	Diode	4G-0-0	Cathode	12.6	0.300				H-W Rect.	325 A-C Volts Per Plate, RMS; 55 Ma. Output Current. Condenser Input to Filter.											19Z3	
13DE7	T-6½	Duodiode	9HF	Cathode	13.0†	0.450	4.0*	2.2*	0.52*	Vert. Osc. Vert. Defl. Amp.	Characteristics Same as Type 16DE7. (13DE7 Designed for Series String TV Receivers).											13DE7	
13DR7	T-6½	Duodiode	9HF	Cathode	13†	0.450	4.5*	2.2*	0.34*	S. 2 Ver. Amp. 1.0 S. 1 Ver. Osc.	Characteristics Same as Type 6DR7. (13DR7 Designed for Series String Receivers).											13DR7	
14A4	Lock-in	Triode	6AA-L-0	Cathode	12.6	0.150	4.0	3.4	3.0	Amplifier	Characteristics Same as Type 7A4.											14A4	
14A5	Lock-in	Beam Amp.	6AA-L-0	Cathode	12.6	0.150	0.4	6.8	7.0	Power Amp.	250 12.5 250 30.0 3.5 70,000† 3,000											14A5	
14A7	Lock-in	Pentode	8V-L-5	Cathode	12.6	0.150	.003m	6.0	7.0	R-F Amp.	Characteristics Same as Type 7A7.											14A7	
14AF7/XXD	Lock-in	Duodiode	8AC-L-0	Cathode	12.6	0.150	2.3*	2.2*	1.6*	Amplifier	Characteristics Same as Type 7AF7.											14AF7/XXD	
14B6	Lock-in	Duodiode Tri.	8X-L-7	Cathode	12.6	0.150	1.5	3.0	3.4	Det. Amp.	Characteristics Same as Type 7B6.											14B6	
14B8	Lock-in	Heptode	8X-L-0	Cathode	12.6	0.150	0.2m	10.0	9.0	Converter	Characteristics Same as Type 7B8.											14B8	
14C5	Lock-in	Beam Pent.	6AA-L-0	Cathode	12.6	0.225	0.4	9.5	9.0	Power Amp.	Characteristics Same as Type 7C5.											14C5	
14C7	Lock-in	Pentode	8V-L-5	Cathode	12.6	0.150	.004m	6.0	6.5	R-F Amp.	Characteristics Same as Type 7C7.	100 3.0 100 5.7	1.8	400,000†	9,975	1,575						14C7	
14E6	Lock-in	Duodiode Tri.	8V-L-7	Cathode	12.6	0.150	1.5	3.0	2.4	Det. Amp.	Characteristics Same as Type 7E6.											14E6	
14E7	Lock-in	Duodi. Pent.	8AE-L-7	Cathode	12.6	0.150	.003m	4.6	5.5	Det. Amp.	Characteristics Same as Type 7E7.											14E7	
14F7	Lock-in	Duodiode	8AC-L-0	Cathode	12.6	0.150	1.6†	9.4†	9.0†	Amplifier	Characteristics Same as Type 7F7.											14F7	
14F8	Lock-in	Duodiode	8BW-L-0	Cathode	12.6	0.150	1.6	9.8†	1.4†	Osc. Amp.	Characteristics Same as Type 7F8.											14F8	
14G6	T-6½	Duodiode Tri.	9Z	Cathode	14	0.100	1.3*	2.4*	1.3*	Det. Amp.	Characteristics Same as Type 7G7.											14G6	
14H7	Lock-in	Pentode	8V-L-5	Cathode	12.6	0.150	.004m	8.0	7.0	R-F Amp.	Characteristics Same as Type 7H7.											14H7	
14J7	Lock-in	Tri. Heptode	8BL-L-7	Cathode	12.6	0.150	.03m	4.6	7.5	Mixer Osc.	Characteristics Same as Type 7J7.											14J7	
14K7	Lock-in	Duodiode	8AC-L-0	Cathode	12.6	0.300				Amplifier	Characteristics Same as Type 7K7.											14K7	
14Q7	Lock-in	Heptode	8AL-L-0	Cathode	12.6	0.150	0.15m	9.0	9.0	Converter	Characteristics Same as Type 7Q7.											14Q7	
14R7	Lock-in	Duodi. Pent.	8AE-L-7	Cathode	12.6	0.150	.004m	5.6	5.3	Det. Amp.	Characteristics Same as Type 7R7.											14R7	
14S7	Lock-in	Tri. Heptode	8BL-L-7	Cathode	12.6	0.150	.03m	5.0	8.0	Mixer Osc.	Characteristics Same as Type 7S7.											14S7	
14W7	Lock-in	Duodiode Tri.	8BZ-L-4	Cathode	12.6	0.150	.009m	9.5	7.0	R-F Amp.	Characteristics Same as Type 7W7.											14W7	
14X7	Lock-in	Duodiode	5AB-L-0	Cathode	12.6	0.300				Det. Amp.	Characteristics Same as Type 7X7.											14X7	
14Y4	T-6½	Tri. Heptode	9Q	Cathode	14.0	0.100	1.4*	5.6*	2.4*	F-W Rect.	Characteristics Same as Type 7Y7. Except Capacitances.	100 0	10	2,800	22							14Y4	
14Y7	T-6½	Tri. Heptode	9Q	Cathode	14.0	0.100	1.4*	5.6*	2.4*	Tri. Osc.	Characteristics Same as Type 7Y7. Except Capacitances.	100 0	10	2,800	22							14Y7	
15	SI-12	Pentode	5F-0-4	Cathode	2.0	0.920	.01m	2.4*	8.0*	R-F Amp.	395 A-C Volts Per Plate, RMS; 70 Ma. Output Current. Condenser Input to Filter.	67.5 1.5	67.5 1.85	630,000	710	450						15	
15A8	T-9	Tri. Beam Pent.	8GS	Cathode	15.0†	0.600	3.4	2.6	0.9	Part Vert. Defl. Amp.	Maximum Peak Positive Pulse Plate Voltage = 1,200 Volts. Maximum D.C. Cathode Current = 40 Ma.	110 7.5	110 45.0	800,000	750	600							15A8

17AV5GA	T-11 or T-12	Beam Pent.	6CK-0-0	0.450	0.5*	14.0*	7.0*	Horiz. Defl. Amp.	Characteristics Same as Type 6AV5GA. (17AV5GA Designed for Series String TV Receivers).	17AV5GA
17AX4GT	T-9	Diode	4CG-0-0	0.450	0.6*	15.0*	7.5*	T.V. Damp. Horiz. Defl. Amp.	Characteristics Same as Type 6AX4GT. (17AX4GT Designed for Series String TV Receivers).	17AX4GT
17BQ6GTB	T-12	Beam Pent.	6AM	0.450	0.6*	15.0*	7.5*	Horiz. Defl. Amp.	Characteristics Same as Type 6BQ6GTB. (17BQ6GTB designed for Series String TV Receivers).	17BQ6GTB

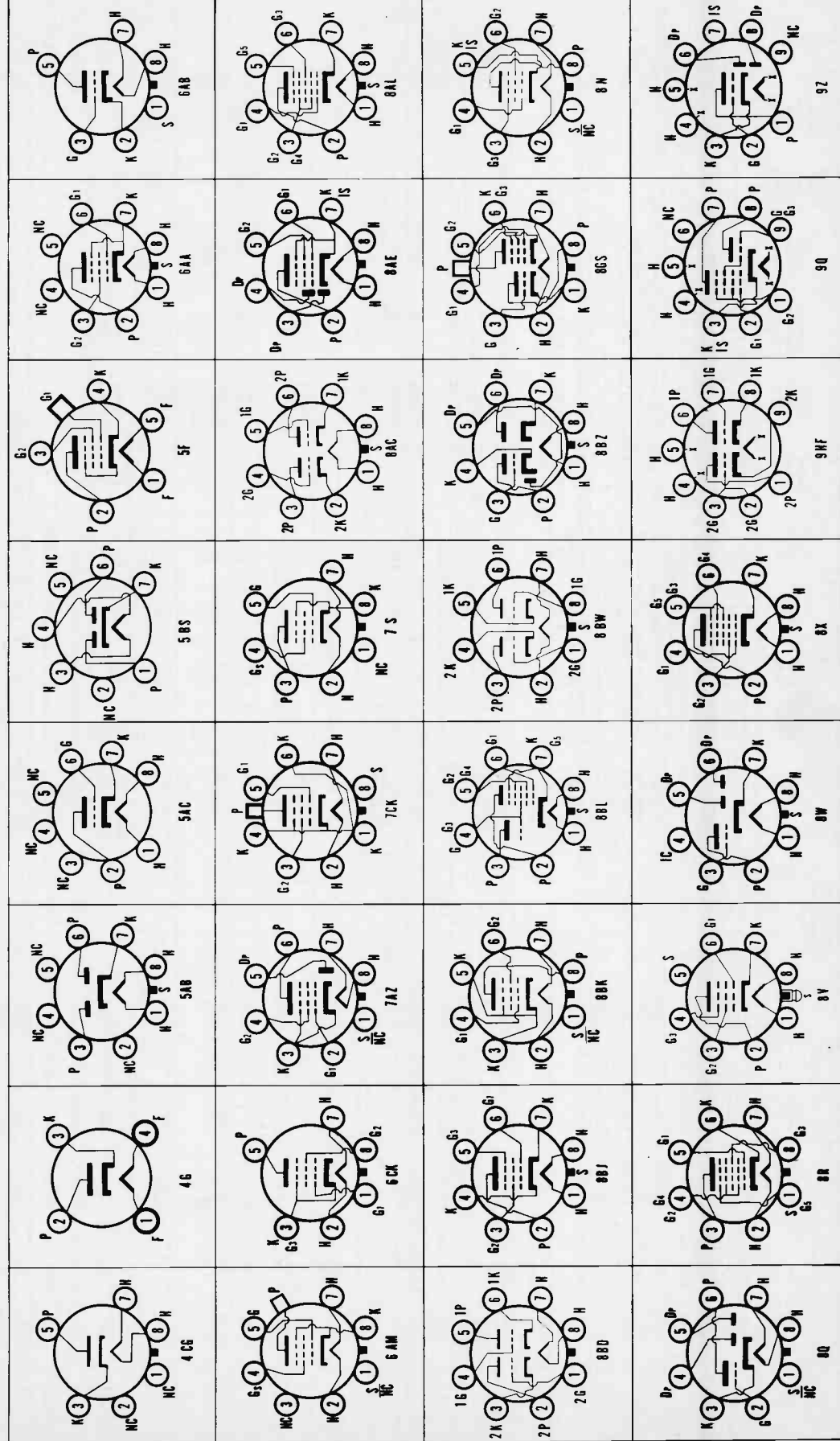(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, RF Input, Mixer Output, specified grid resistor.
 I. Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)
 # Per Tube or Section.
 § Plate and Target Supply Voltage.
 † Maximum Signal.
 ‡ Approximate.
 * Applied through 20,000 ohms.
 † Conversion Transconductance.
 ‡ Triode Operation.



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate, F—Filament, Fe—Filament Center, G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection, DO NOT USE, J—Jumper; K—Cathode; NC—No. Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (*) Capacitances in $\mu\text{f.}$			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Power Output Milli-watts	Type	
	Bulb Size or Style	Class	Beam Pent.	Type	Volts	Amps.	Cps.													Cin.
17C5	T-3½	Beam Pent.	7CV-0-0	Cathode	16.81	0.450	0.6*	13.0*	8.5*	Power Amp.	200	295	60	5	1 Meg. \downarrow	2,200	17C5		
17C8	T-6½	Pentode	9T	Cathode	17	0.100	.0025*	4.2*	4.9*	R-F Amp.	17C8		
17CA5	T-3½	Beam Pent.	7CV-0-0	Cathode	16.81	0.450	0.5*	15.0*	9.0*	Power Amp.	17CA5		
17D4	T-9	Diode	4CG	Cathode	16.81	0.450	T.V. Damper	17D4		
17DQ6	T-12	Beam Pent.	6AM	Cathode	16.81	0.450	0.55*	15.0*	7.0*	Horiz. Defl. Amp.	17DQ6		
17DQ6A	T-6½	Diode	9FK-0-0	Cathode	17.51	0.300	T.V. Damper	17DQ6A		
17L6GT	T-9	Beam Pent.	7CV-0-0	Cathode	16.81	0.450	0.55*	13.0*	9.0*	Power Amp.	17L6GT		
17R5	T-5½	Beam Pent.	7CV-0-0	Cathode	16.81	0.450	0.55*	13.0*	9.0*	Vari. Defl. Amp.	17R5		
18	ST-14	Beam Pent.	68-0-0	Cathode	14.0	0.300	Power Amp.	18		
18A3	T-9	Beam Pent.	6CK-0-0	Cathode	18.51	0.300	0.7*	13.0*	7.0*	Horiz. Defl. Amp.	18A3		
18DZ8	T-6½	Tri. Beam Pent.	6DZ8	Cathode	18	0.300	A-F Voltage Amp. and Power Amp.	18DZ8		
19	T-9	Duobiode	6C-0-0	Filament	2.0	0.260	Power Amp.	135	0.0	5-181	(Class B Operation)	10,000†	19		
19AQ3	T-5½	Beam Pent.	7BZ	Cathode	18.9	0.150	Power Amp.	19AQ3		
19AU4	T-9	Diode	4CG-0-0	Cathode	18.91	0.600	T.V. Damper	19AU4		
19AU4GTA	T-9	Diode	4CG-0-0	Cathode	18.91	0.600	T.V. Damper	19AU4GTA		
19BQ6G	ST-16	Beam Pent.	5BT-0-0	Cathode	18.9	0.300	0.34*	12.0*	6.5*	Horiz. Defl. Amp.	19BQ6G		
19BQ6GA	I-12	Tri. Beam Pent.	9E-0-0	Cathode	18.9	0.150	0.8*	11.0*	6.0*	Det. Amp.	100	1.0	0.5	19BQ6GA		
19C8	T-6½	Tri. Beam Pent.	9CA	Cathode	19.0	0.100	1.0	2.6	2.1	F.M. Tri. Osc. A.M. Hep. Converter	100	0	63	13.5	3.7	800,000	3,700	22	19C8	
19D8	T-6½	Tri. Beam Pent.	7BF-0-0	Cathode	18.9	0.150	1.5* ϕ	9.0* ϕ	0.4* ϕ	VHF Osc. Amp.	150	810	4.8	10,800	1,900	19D8	
19J6	T-5½	Duobiode	7BF-0-0	Cathode	18.9	0.150	1.7*	1.7*	2.4*	Det. Amp.	19J6		
19T8	T-6½	Tri. Beam Pent.	9E-0-3 & 7	Cathode	18.9	0.150	Det. Amp.	19T8		
19V8	T-6½	Tri. Beam Pent.	9AH-0-3	Cathode	18.9	0.150	Det. Amp.	100	1.0	0.8	54,000	1,300	70	19V8	
19X8	T-6½	Tri. Beam Pent.	9AK	Cathode	18.9	0.150	VHF Osc. Amp.	950	3.0	1.0	58,000	1,300	70	19X8	
20	T-8	Triode	4D-0-0	Filament	3.3	0.132	Power Amp.	90	16.5	2.8	7,800	450	3.5	20	
22	ST-14	Tetrode	4K-0-3	Filament	3.3	0.132	R-F Amp.	135	22.5	6.0	3,850	600	3.5	22	
24A	ST-14	Tetrode	5E-0-3	Cathode	2.5	1.750	.08m	4.0*	10.0*	R-F Amp.	135	1.5	67.5	3.7	1.3	250,000	500	185	24A	
24S	T-9	Power Pent.	7S-1-0	Cathode	25.0	0.300	.007m	5.3	10.5	Detector	180	3.0	90	4.0	1.7	400,000	1,000	400	24S	
25A6	T-9	Diode Pent.	8F-0-0	Cathode	25.0	0.300	Power Amp.	95	15.0	95	20.0	4.0	45,000	2,000	25A6	
25A6GT	T-9	Diode Pent.	8F-0-0	Cathode	25.0	0.300	Power Amp.	135	20.0	135	37.0	8.0	35,000	2,450	25A6GT	
25A7GT	T-9	Triode	6Q-0-0	Cathode	25.0	0.300	H-W Rect. Coupled Amp.	160	18.0	150	33.0	6.5	48,000	2,375	25A7GT	
25AC5GT	T-9	Beam Pent.	6CK-0-0	Cathode	25.0	0.300	0.7*	14.0*	7.0*	Power Amp.	110	15.0	100	20.5	4.0	50,000	1,800	25AC5GT	
25AV5GT	T-9	Beam Pent.	6CK-0-0	Cathode	25.0	0.300	0.5*	14.0*	7.0*	Horiz. Defl. Amp.	100	15.0	100	20.5	4.0	50,000	1,800	25AV5GT	
25AV5GA	T-11 or T-12	Beam Pent.	6CK-0-0	Cathode	25.0	0.300	0.5*	14.0*	7.0*	Horiz. Defl. Amp.	25AV5GA	
25AX4GT	T-9	Diode	4CG	Cathode	25.0	0.300	T.V. Damper	25AX4GT	
25B5	ST-12	Duobiode	6D-0-0	Cathode	25.0	0.300	Power Amp.	25B5	
25B6G	ST-14	Beam Pent.	7S-0-0	Cathode	25.0	0.300	Power Amp.	105	16.0	105	48.0	2.0	15,500	4,800	25B6G	
25B8GT	T-9	Pentode Tri.	8T-0-1	Cathode	25.0	0.150	.02	5.5	10.0	Pent. Amp.	100	3.0	100	7.6	2.0	185,000	2,000	370	25B8GT	
25BK5	T-6½	Beam Pent.	9BQ	Cathode	25.0	0.300	0.6*	13.0*	5.0	Horiz. Defl. Amp.	100	1.0	0.6	75,000	1,500	112.5	25BK5	
25BQ6GA	T-11	Beam Pent.	6AM-0-0	Cathode	25.0	0.300	0.6*	15.0*	7.5*	Power Amp.	25BQ6GA	
25BQ6GT	T-9	Beam Pent.	6AM-0-0	Cathode	25.0	0.300	0.6*	15.0*	7.5*	Power Amp.	25BQ6GT	
25C5	T-5½	Beam Pent.	7CV	Cathode	25.0	0.300	0.6*	13.0*	8.5*	Power Amp.	120	8	110	49	4.0	10,000	7,500	25C5	
25C6G	ST-14	Beam Pent.	7S-0-0	Cathode	25.0	0.300	Power Amp.	25C6G	
25C6GA	I-12	Beam Pent.	7S-0-0	Cathode	25.0	0.300	Power Amp.	25C6GA	
25CA3	T-5½	Beam Pent.	7CV-0-0	Cathode	25.0	0.300	0.5*	15.0*	9.0*	Power Amp.	25CA3	
25CD6G	ST-16	Beam Pent.	5BT-0-0	Cathode	25.0	0.600	1.0m	26.0m	10.0m	Horiz. Defl. Amp.	25CD6G
25CD6GA	ST-16	Beam Pent.	5BT-0-0	Cathode	25.0	0.600	Power Amp.	25CD6GA	

Model	Beam Pent.	Cathode	25.01	0.600	1.1*	22.0*	8.5*	Horiz. Defl. Amp.
25CD6GB	5BT-0-0	Cathode	25.01	0.600	1.1*	22.0*	8.5*	Horiz. Defl. Amp.
25CR5	9HC-0-0	Cathode	25.0	0.300	0.32*	12.9*	6.9*	Horiz. Defl. Amp.
25CU6	6AM-0-0	Cathode	25.0	0.300	0.55*	15.0*	7.0*	Horiz. Defl. Amp.
25DRGT	8AF-0-1	Cathode	25.0	0.150	3.5*	3.7*	4.5*	Det. Amp.
25DN6	5BT-0-0	Cathode	25.01	0.600	0.8*	22.0*	11.5*	Horiz. Defl. Amp.

(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output, specified and resistor.
 X Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram	Model	Diagram
4CG		4D		4K		5BT		5E		6AM		6B		6C		6CK	
6CK		6D		6DZ8		6E		7BF		7BZ		7CV		7S		8AF	
8AF		8F		8T		9AM		9AK		9BQ		9CA		9E		9FK	
9FK		9NC		9T													


Per Tube or Section. Plate and Target Supply Voltage. Maximum Signal.
 † Applied through 20,000 ohms. Conversion Inconducivance. †† Inode Operation.
 † Plate to Plate. †† Approximate. (Ohms).
 SYMBOLS FOR BASE DIAGRAMS: Dr—Diode Plate, F—Filament, Fc—Filament Center, G—Grids numbered according to their position from the cathode, H—Heater, Hc—Heater Center, Ht—Heater Tap, IC—Internal Connection, DO NOT USE, J—Jumper, K—Cathode, NC—No. Connection, P—Plate, Rc—Ray Control, S—Metal Shell, SA—Starter, Anode, T—Target, XS—External Shield, □—Top Cap, ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Note (1) (*) Capacitances in $\mu\mu\text{f}$.				Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohm Load for Stated Power Output	Power Output Milli-watts	Type	
	Barb Size or Style	Class	Beating Diag.	Type	Volts	Amps.	Cp.	Cin.	Coef													
25DQ6	T-12	Beam Pent.	6A-M-0-0	Cathode	25.0	0.300	0.55*	15.0*	7.0*	Horiz. Defl. Amp.	Characteristics Same as Type 6DQ6.										25DQ6	
25EH5	T-5½	Beam Pent.	7CV	Cathode	25	0.300	0.65*	17*	9*	S.T. A1 Amp.	Characteristics Same as Type 6EH5.										25EH5	
25F5	T-5½	Beam Pent.	7CV	Cathode	25.0	0.150	0.57*	18.0*	6.0*	Power Amp.	110	8.0	110	7.0	7.5	4,500	2,900	25F5	
25L6	Metal	Beam Pent.	7S-0-0	Cathode	25.0	0.300	Power Amp.	110	7.5	110	49.0	4.0	13,000	8,000	2,000	2,100	25L6	
25L6GT	T-9	Beam Pent.	7S-0-0	Cathode	25.0	0.300	Power Amp.	200	18.0	185	46	3.2	28,000	8,000	4,000	3,800	25L6GT	
25N6G	ST-12	Duobode	7W-0-0	Cathode	25.0	0.300	Power Amp.	110	0	110	45	7.0	(Direct Coupled)	2,300	2,000	2,000	25N6G	
25S	Now Known as Type 1B5																					
25W4GT	T-9	Diode	4C-0-0	Cathode	25.0	0.300	H-W Rect.	350	A-C	110	4.0	13,000	8,000	2,000	2,100	25W4GT	
25W6GT	T-9	Beam Pent.	7S	Cathode	25.0	0.300	0.5	15.0	9.0	Power Amp.	325	-7.5	110	32**	1,600	3,800**	25W6GT	
25X6GT	T-9	Duobode	7Q-0-0	Cathode	25.0	0.150	H-W Rect. Doubler	125	Volts RMS Per Plate, 60 Ma. D.C. Output Per Plate.	25X6GT	
25Y5	ST-12	Duobode	6E-0-0	Cathode	25.0	0.300	Doubler H-W Rect.	117	A-C	25Y5	
25Z4	Metal	Diode	5A-A-1-0	Cathode	25.0	0.300	H-W Rect.	117	A-C	25Z4	
25Z5	ST-12	Duobode	6E-0-0	Cathode	25.0	0.300	Doubler	117	A-C	25Z5	
25Z6	Metal	Duobode	7Q-1-0	Cathode	25.0	0.300	Doubler H-W Rect.	117	A-C	25Z6	
25Z6GT	T-9	Diode	7Q-0-0	Cathode	25.0	0.300	H-W Rect.	335	A-C	25Z6GT	
26	ST-14	Triode	4D-0-0	Filament	1.5	1.050	8.1*	3.8*	2.3*	Amplifier	90	7.0	9,900	935	8.3	26	
26A6	T-5½	Pentode	7BK-0-2	Cathode	26.5	0.070	.0035	6.0	5.0	R-F Amp.	26.5	Self	7,600	1,100	8.3	26A6	
26A7GT	T-9	Duo. Beam Pent.	8BU-0-0	Cathode	26.5	0.600	1.2*	16.0*	13.0*	Power Amp.	26.5	4.5	26.5	20.0*	1.9†	1,500*	5,700†	1,500*	180#	26A7GT	
26BK6	T-5½	Duobode Tri.	7BT-0-2	Cathode	26.5	0.070	Det. Amp.	100	1.0	80,000	1,950	26BK6	
26C6	T-5½	Duobode Tri.	7BT-0-0	Cathode	26.5	0.070	2.0	1.8	1.4	Amplifier	26.5	2 Megs.	69,500	1,600	26C6	
26CG6	T-5½	Pentode	7BK-0-2	Cathode	26.5	0.070	.008m	5.0	5.0	R-F Amp.	26.5	Self	15,500	1,100	26CG6	
26D6	T-5½	Heptode	7CH-0-0	Cathode	26.5	0.070	0.3	7.5	14.0	Converter Oscillator	100	1.5	100	2.8	8.0	500,000†	455 A	26D6	
27	ST-12	Triode	5A-0-0	Cathode	2.5	1.750	3.3*	3.2*	2.3*	Amplifier	250	1.5	100	3.0	7.8	1 Meg.†	475 A	27	
27S	Lock-in	Duo. Beam Pent.	8BS-L-0	Cathode	28.0	0.400	Amplifier	90	6.0	10,000	900	27S	
28D7	Lock-in	Double Diode	6BL-L-0	Cathode	28.0	0.240	Amplifier (per section) P.P.A. Total	135	9.0	9,000	1,000	28D7	
28Z5	Lock-in	Triode	4D-0-0	Filament	2.0	0.060	6.0*	3.0*	2.2*	F.W. Rect.	28	3.5	28	12.5	1.0	4,200	3,400	4,000	1,500†	28Z5	
30	ST-12	Triode	4D-0-0	Filament	2.0	0.060	6.0*	3.0*	2.2*	Det. Amp.	90	4.5	11,000	850	30	
31	ST-12	Triode	4D-0-0	Filament	2.0	0.130	Power Amp.	135	9.0	10,300	900	31	
32	ST-14	Tetrode	4K-0-3	Filament	2.0	0.060	.015m	5.3*	10.3*	R-F Amp.	135	22.5	4,100	985	32	
32L7GT	T-9	Diode Beam Pent.	8Z-0-0	Cathode	32.5	0.300	Detector	180	3.0	67.5	1.7	0.4	950,000	640	32L7GT	
33	ST-14	Power Pent.	5K-0-0	Filament	2.0	0.260	1.0*	8.0*	12.0*	Power Amp.	135	13.5	135	14.5	3.0	50,000	1,450	2,600	1,000	33	
34	ST-14	Pentode	4M-0-4	Filament	2.0	0.060	.015m	6.0*	11.0*	R-F Amp.	67.5	3.0	67.5	2.7	1.1	400,000	560	7,000	1,400	34	
EL34/6CA7	T-10 (SP)	Beam Pent.	8ET	Cathode	6.3	1.500	S.T. A1 Amp. P.P.A.B1 Amp.	450	13.5	250	100	15	15,000	11,000	2,000	11,000	EL34/6CA7	
35/51	ST-14	Tetrode	5E-0-3	Cathode	2.5	1.750	.007m	5.3*	10.3*	R-F Amp.	90	3.0	90.0	6.3	2.5	300,000	1,080	6,600†	37,000	35/51	
35/51S	Lock-in	Beam Pent.	5E-4-3	Cathode	35.0	0.150	A-F Amp.	250	3.0	90.0	6.5	2.5	400,000	1,050	35/51S	
35A5	Lock-in	Beam Pent.	6A-A-L-0	Cathode	35.0	0.150	Power Amp.	110	7.5	110	40.0	3.0	14,000†	5,800	2,500	1,500	35A5	
35B5	T-5½	Beam Pent.	7BZ-0-0	Cathode	35.0	0.150	0.4*	11.0*	6.5*	Power Amp.	110	7.5	110	40.0	3.0	34,000†	6,100	2,500	1,500	35B5	
35C3	T-5½	Diode	7ET	Cathode	35.0	0.150	0.6	H-W Rect.	117	Volts RMS Per Plate, 100 Ma. D.C. Output.	35C3
35CD6GA	T-12	Beam Pent.	5BT	Cathode	35.0	0.450	1.1*	22.0*	8.5*	Horiz. Defl. Amp.	110	7.5	110	40	3.0	5,800	2,500	1,500	35CD6GA	

35D5	Beam Pent.	9FU	Cathode 35	0.150	0.3	13.7	6.7	S.T.A1 Amp.	110 170	200 ^m 190 ^m	30 52	2.5 3	18,000 20,000	8,000 9,500	2,500 2,500	1,400 4,800	35D5
35DZ8	Th. Beam Pent.	6DZ8	Cathode 35	0.150	A-F Voltage and Power Amp.	35DZ8
35L6GT	Beam Pent.	75-0-0	Cathode 35.0	0.150	0.8*	13.0*	9.3*	Power Amp	110 200	7.5 8.0	110 110	40.0 43.0	3.0 2.0	14,000 [†] 34,000 [†]	5,800 6,100	2,500 5,000	35L6GT
35W4	Diode	5BQ-0-0	Cathode 35.0	0.150	H-W Rect.	117 A-C Volts, RMS, 60 Ma. Output Current with Panel Lamp. 117 A-C Volts, RMS, 100 Ma. Output Current without Panel Lamp.	35W4	
35Y4	Lock-in Diode	5AL-L-0	Cathode 35.0	0.150	H-W Rect.	935 Max. A-C Volts, RMS, 100 Ma. Output Current without Panel Lamp.	35Y4	

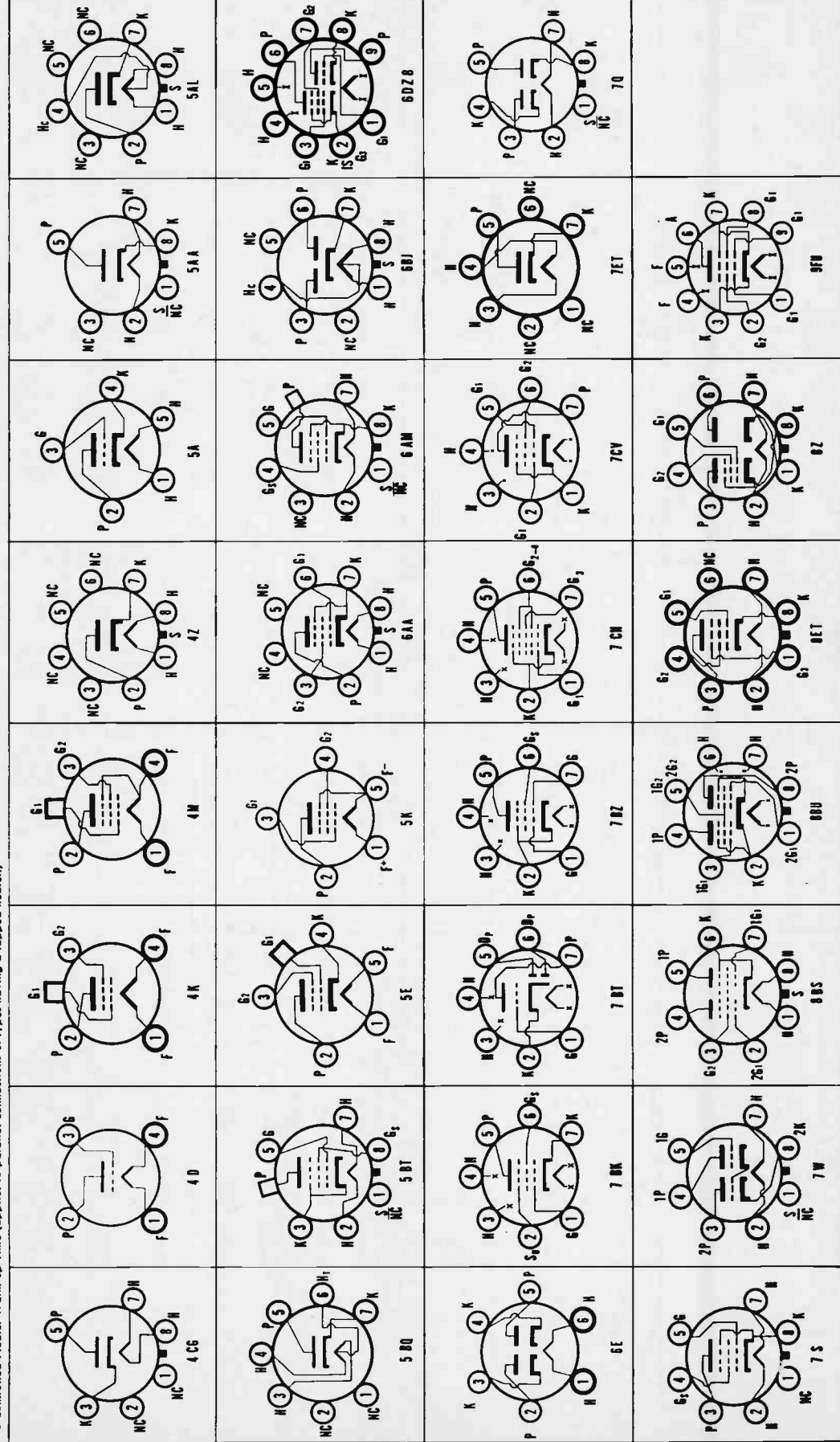(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitance given are signal grid to plate, RF input, Miler Output.
 (4) Average contact potential bar developed across specified grid resistor.
 † Maximum Heater Warm-up Time (applies to parallel connections of types having a tapped heater.)
 ‡ Per Tube of Section
 § Plate to Plate.
 ¶ Plate to Section
 †† Maximum Supply Voltage.
 ‡‡ Triode Operation.
 ††† Maximum Plate to Plate.
 †††† Maximum Cathode Resistor (ohms).
 ††††† Maximum Cathode Resistor (ohms).



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Noise (μV) Capacitances in μfd.		Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Chms Load for Stated Output	Undistorted Power Output Milliwatts	Type	
	Class	Being Disg.	Type	Volts	Amps.	Cyp.													Ch.
35Z3	Diode	4Z-L-0	Cathode	35.0	0.150	H-W Rect.	925 Max. A-C Volts Per Plate, RMS, 100 Ma. Output Current. Condenser Input to Filter.	35Z3	
35Z4GT	Diode	5A-A-0-0	Cathode	35.0	0.150	H-W Rect.	117 A-C Volts, RMS, 100 Ma. Output Current. Condenser Input to Filter.	35Z4GT	
35Z5GT	Diode	6AD-0-0	Cathode	35.0	0.150	H-W Rect.	Characteristics Same as Type 35Z4.	35Z5GT	
35Z6G	Duodiode	7Q-0-0	Cathode	35.0	0.300	Doubler	117 A-C Volts Per Plate, RMS, 110 Ma. Output Current.	35Z6G	
36	Tetrode	3E-0-3	Cathode	6.3	0.300	.007m	3.7*	R-F Amp.	135 1.5 67.5 2.8 Not Over 575,000 180 3.0 90.0 3.1 1/2 of 500,000 250 3.0 90.0 3.2 Plate Ma. 550,000 250 6.0* 90 to 95 (Plate Current to be adjusted to 0.1 Ma. with no Input Signal.)	36	
37	Triode	5A-0-0	Cathode	6.3	0.300	2.0*	3.5*	Detector Amplifier	135 9.0 985 180 13.5 985 250 18.0 985	37	
EL37	Curved Bulb	7S	Cathode	6.3	1.400	1.0*	17.5*	S.T. A1 Amp. P.P.A.B.I. Amp.	250 36 400 100-276† 13.5 13,500 11,000	EL37	
38	Power Pent.	5F-0-0	Cathode	6.3	0.300	0.3*	3.5*	Power Amp.	135 13.5 135 9.0 1.5 130,000 985 180 18.0 180 14.0 2.4 110,000 1,050 250 25.0 250 22.0 3.8 100,000 1,500	38	
38A3	Diode	98M	Cathode	38	0.100	H-W Rect.	250 A.C. Volts, RMS, 110 Ma. Max. Output Current.	38A3	
39/44	Pentode	5F-0-4	Cathode	6.3	0.300	.007m	3.5*	R-F Amp.	90 3.0 90.0 5.6 1.6 375,000 960 180 3.0 90.0 5.8 1.4 750,000 1,000 750 250 3.0 90.0 5.8 1.4 1,050 250 6.0* 90.0 5.8 1.4 1 Meg. 1,050 Eb thru 0.25 Meg Res.	39/44	
40	Triode	4D-0-0	Filament	5.0	0.350	8.0	2.8	A-F Amp. Amplifier	135 1.5 67.5 2.8 0.2 180 3.0 90.0 3.0 0.2 250 3.0 90.0 3.0 0.2	40	
40A1	Ballast	8ES	Horiz. Reg.	Avg. Operating Current—0 Ma. at 90 Volts, 150 Ma. at 40 Volts, 155 Ma. at 60 Volts.	40A1	
40B2	Ballast	8ES	Horiz. Reg.	Avg. Operating Current—140 Ma. at 90 Volts, 150 Ma. at 40 Volts, 155 Ma. at 60 Volts.	40B2	
40Z5/45Z5GT	Diode	6AD-0-0	Cathode	45.0	0.150	H-W Rect.	Characteristics Same as Type 35Z4.	40Z5/45Z5GT	
41	Power Pent.	6B-0-0	Cathode	6.3	0.400	Power Amp.	Characteristics Same as Type 6F6GT.	41	
42	Power Pent.	6B-0-0	Cathode	6.3	0.700	Power Amp.	Characteristics Same as Type 6F6G.	42	
43	Power Pent.	6B-0-0	Cathode	25.0	0.300	Power Amp.	Characteristics Same as Type 95A6GT.	43	
45	Triode	4D-0-0	Filament	2.5	1.500	7.0*	4.0*	Power Amp.	180 31.5 31.0 250 50.0 34.0 275 56.0 36.0	45	
45B5	Beam Pent.	9CV	Cathode	45.0	0.100	0.6*	12.0*	Power Amp.	100 6.7 100 43.0 3.0 23,000 9,000 170 12.5 170 70.0 5.0 23,000 10,000	45B5
45Z3	Diode	5AM-0-0	Cathode	45.0	0.075	H-W Rect.	117 A-C Volts Per Plate, RMS, 65 Ma. Output Current.	45Z3	
45Z5GT	Diode	5AM-0-0	Cathode	45.0	0.075	H-W Rect.	117 A-C Volts Per Plate, RMS, 65 Ma. Output Current.	45Z5GT	
46	Power Tet.	5C-0-0	Filament	2.5	1.750	Power Amp.	250 33.0 Tie G to P 22.0 300 0.0 Tie G to G 4.0† 400 0.0 Tie G to G 6.0†	46	
47	Power Pent.	5B-0-0	Filament	2.5	1.750	1.3*	8.6*	Power Amp.	250 16.5 250 31.0 6.0 60,000 9,500 350 22.5 350 52.0 12.0 11,000 3,900 450 29.0 450 60.0 18.0 11,000 3,900	47
48	Power Tet.	6A-0-0	Cathode	3.0	0.400	Power Amp.	95 20.0 95.0 52.0 12.0 4,000 3,900 125 22.5 100 52.0 12.0 11,000 3,900	48	
49	Power Tet.	5C-0-0	Filament	2.0	0.120	Power Amp.	135 20.0 Tie G to P 6.0 180 0.0 Tie G to G 2.0†	49	
50	Triode	4D-0-0	Filament	7.5	1.250	7.1*	4.3*	Power Amp.	300 54.0 35.0 350 63.0 45.0 400 70.0 55.0 450 84.0 55.0	50	
50A1	Ballast	9CM	Fil. Ballast	Avg. Operating Current—52 Ma. at 30 Volts, 54 Ma. at 50 Volts, 56 Ma. at 65 Volts.	50A1	
50A5	Beam Pent.	6A-L-0	Cathode	50.0	0.150	Power Amp.	100 7.5 110 49.0 4.0 13,000 8,000 200 8.0 110 50.0 4.0 28,000 8,000	50A5	
50AX6G	Duodiode	7Q-0-0	Cathode	50.0	0.300	F-W Rect.	Characteristics Same as Type 6AX6G.	50AX6G	
50B5	Beam Pent.	7BZ-0-0	Cathode	50.0	0.150	0.6*	13.0*	Power Amp.	120 8 110 49 4.0 10,000 7,500	50B5	
50BK5	Beam Pent.	9BQ-0-0	Cathode	50.0	0.150	0.6*	13.0*	Power Amp.	250 5.0 250 35 3.5 0.1 Meg. 4 2,500 3,500	50BK5	
50BM8	Tri. Pentode	9EX	Cathode	50	0.100	4.2*	2.7*	A-F Tri. Amp. Power Amp.	100 6 100 26 5 28,000 2,500 200 16 200 35 7 20,000 6,400	50BM8	
50C5	Beam Pent.	7CV-0-0	Cathode	50.0	0.150	0.6*	13.0*	Power Amp.	120 8 110 49 4.0 10,000 7,500	50C5	
50CGG	Beam Pent.	7S-0-0	Cathode	50.0	0.150	Power Amp.	Characteristics Same as Type 6CA5.	50CGG	
50CGA	Beam Pent.	7CV	Cathode	50	0.150	0.5*	15*	Power Amp.	117 A-C Volts Per Plate, RMS, 110 Ma. Output Current. Heater Top Voltage (Pin 4 to Pin 6) = 7.5 Volts.	50CGA	
50DCA	Diode	5BQ	Cathode	50	0.150	H-W Rect.	Characteristics Same as Type 6EHS.	50DCA	
50EH5	Beam Pent.	7CV	Cathode	50	0.150	0.65*	17*	S.T. A1 Amp.	Characteristics Same as Type 95L6GT.	50EH5	
50L6GT	Beam Pent.	7S-0-0	Cathode	50.0	0.150	Power Amp.	Characteristics Same as Type 95L6GT.	50L6GT	
50X6	Duodiode	7DX-L-0	Cathode	50.0	0.150	H-W Rect. Doubler	235 Volts RMS Per Plate, 75 Ma. D-C Output Per Plate. 117 Volts RMS Per Plate, 75 Ma. D-C Output.	50X6	
50Y6GT	Duodiode	7O-0-0	Cathode	50.0	0.150	F-W Rect.	Characteristics Same as Type 95Z6GT.	50Y6GT	
50Y7GT	Duodiode	8AN-0-0	Cathode	46.0	0.150	Doubler	117 A-C Volts, RMS, 65 Ma. Output with Panel Lamp. 150 A-C Volts, RMS, 65 Ma. Output Per Plate with Panel Lamp. 235 A-C Volts, RMS, 65 Ma. Output Per Plate with Panel Lamp.	50Y7GT	

SYLVANIA TUBES - AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Notes (1) (2) Capacitance in p.f.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohms Load for Stated Power Output	Undistorted Power Output Milli-watts	Type
	Bulb Size or Style	Class	Beating Dia.	Type	Volts	Amps.	Cap.	Cin.												
55N3	T-6 1/2	Diode	98M	Cathode	55	1.000	3.2*	3.2*	H-W Rect. Amplifier Detector	250 A-C Plate Volts, R.M.S., 180 Ma. Output Current.	13.5	5.0	9,500	1,450	13.8	55N3	
56	ST-12	Triode	5A-0-0	Cathode	2.5	1.000	3.2*	3.2*	Amplifier	56	
56S	T-9	Triode	5A-4-0	Cathode	2.5	1.000	3.2*	3.2*	Amplifier	Characteristics Same as Type 56.	56AS	
57	ST-12	Triode	5A-4-0	Cathode	6.3	0.400	2.8*	3.5*	R-F Amp.	57	
57S	ST-12	Pentode	6F-0-5	Cathode	2.5	1.000	.007m	5.0*	6.5*	Detector	57S	
57AS	ST-12	Pentode	6F-5-5	Cathode	6.3	0.400	.007*	5.0*	6.5*	R-F Amp.	57AS	
58	ST-12	Pentode	6F-5-5	Cathode	2.5	1.000	.007m	4.7*	6.0*	R-F Amp.	58	
58S	ST-12	Pentode	6F-5-5	Cathode	6.3	0.400	.007*	4.7*	6.0*	R-F Amp.	58S	
58AS	ST-12	Power Pent.	7A-0-0	Cathode	2.5	2.000	58AS	
59	ST-16	Power Pent.	7A-0-0	Cathode	2.5	2.000	59	
KT66	Curved Bulb	Beam Pent.	7S	Cathode	6.3	1.270	1.1*	16*	11.5*	ST-11 Amp. P.P.A.B1 Amp.	250 15 250 85 250 104-125 1	KT66
70A7GT	T-9	Diode Beam Pent.	8AB-0-0	Cathode	70.0	0.150	H-W Rect. Power Amp.	117 A-C Volts, RMS, 70 Ma. Output Current.	70A7GT	
70L7GT	T-9	Diode Beam Pent.	8AA-0-0	Cathode	70.0	0.150	H-W Rect. Power Amp.	117 A-C Volts, RMS, 70 Ma. Output Current.	70L7GT	
71A	ST-14	Triode	4D-0-0	Filament	5.0	0.850	7.5*	3.3*	3.9*	Power Amp.	71A	
75	ST-12	Duodiode Tri.	6G-0-5	Cathode	6.3	0.300	1.7*	1.7*	3.8*	Det. Amp.	75	
75S	ST-12	Duodiode Tri.	6G-5-5	Cathode	6.3	0.300	1.7*	1.7*	3.8*	Det. Amp.	75S	
76	ST-12	Triode	5A-0-0	Cathode	6.3	0.300	2.8*	3.5*	2.5*	Amplifier Detector	76	
77	ST-12	Pentode	6F-0-5	Cathode	6.3	0.300	.007m	4.7*	11.0*	R-F Amp.	77	
78	ST-12	Pentode	6F-0-5	Cathode	6.3	0.300	.007m	4.5*	11.0*	R-F Amp.	78	
79	ST-12	Duodiode	6H-0-0	Cathode	6.3	0.600	Power Amp.	79	
80	ST-14	Duodiode	4C-0-0	Filament	5.0	2.000	F-W Rect.	350 A-C Volts Per Plate, RMS, 185 Ma. Output Current.	80	
81	ST-16	Diode	4B-0-0	Filament	7.5	1.250	F-W Rect.	700 A-C Volts Per Plate, RMS, 85 Ma. Output Current.	81	
82	ST-14	Duodiode	4C-0-0	Filament	2.5	3.000	F-W Rect.	450 A-C Volts Per Plate, RMS, 115 Ma. Output Current.	82	
83	ST-16	Duodiode	4C-0-0	Filament	5.0	3.000	F-W Rect.	450 A-C Volts Per Plate, RMS, 935 Ma. Output Current.	83	
83V	ST-14	Duodiode	4AD-0-0	Cathode	5.0	2.000	F-W Rect.	375 A-C Volts Per Plate, RMS, 175 Ma. Output Current.	83V	
84/624	ST-12	Duodiode	5D-0-0	Cathode	6.3	0.500	F-W Rect.	325 A-C Volts Per Plate, RMS, 60 Ma. Output Current.	84/624	
EL84/680S	T-6 1/2	Beam Pent.	9CV	Cathode	6.3	0.760	0.5m*	10.8*	6.5*	ST-11 Amp. P.P.A.B1 Amp.	250 135 250 300 300 72-921	EL84/680S
85	ST-12	Duodiode Tri.	6G-0-5	Cathode	6.3	0.300	1.5*	1.5*	4.3*	Det. Amp.	85	
85AS	ST-12	Duodiode Tri.	6G-5-5	Cathode	6.3	0.300	1.5*	1.5*	4.3*	Det. Amp.	85AS	
KT88	ST-16	Beam Pent.	7S	Cathode	6.3	1.800	P.P.A.B1 Amp.	450 65 450 100-2401	KT88	
89	ST-12	Power Pent.	6F-0-0	Cathode	6.3	0.400	Power Amp.	89	
VR-90-105-150	T-8	Triode	4E-0-0	Filament	3.3	0.063	3.5*	2.5*	2.5*	Det. Amp.	VR-90-105-150	
X99	T-9	Triode	4D-0-0	Filament	3.3	0.063	3.5*	2.5*	2.5*	Det. Amp.	X99	
117L7/M7GT	T-9	Diode Beam Pent.	8AO-0-0	Cathode	117	0.090	Power Amp.	117L7/M7GT	
117N7GT	T-9	Diode Beam Pent.	8AV-0-0	Cathode	117	0.090	Power Amp.	117N7GT	
117P7GT	T-9	Diode Beam Pent.	8AV-0-0	Cathode	117	0.090	Power Amp.	117P7GT	
117Z3	T-5 1/2	Diode	4CB-0-0	Cathode	117	0.040	H-W Rect.	117 A-C Volts Per Plate, RMS, 90 Ma. Output Current.	117Z3	
117Z4GT	T-9	Diode	5AA-0-0	Cathode	117	0.040	H-W Rect.	117 A-C Volts Per Plate, RMS, 90 Ma. Output Current.	117Z4GT	
117Z6GT	T-9	Duodiode	7O-0-0	Cathode	117	0.075	Volt. Dbl.	117 A-C Volts Per Plate, RMS, 60 Ma. Output Current.	117Z6GT	
1838/482B	ST-14	Triode	4D-0-0	Filament	5.0	1.250	Power Amp.	1838/482B	
1837/483	ST-14	Triode	4D-0-0	Filament	5.0	1.250	Power Amp.	1837/483	
910-T	ST-16	Triode	4D-0-0	Filament	7.5	1.250	7.0*	4.0*	3.0*	Power Amp.	910-T	
417A	T-6 1/2	Triode	9V	Cathode	6.3	0.300	0.48*	9*	1.8*	UHF	417A	
485	ST-12	Triode	5A-0-0	Cathode	3.0	1.950	Det. Amp.	485	
807	ST-16	Beam Pent.	5AW-0-0	Cathode	6.3	0.900	0.2m	12.0*	7.0*	P.P.A.B1 Amp.	807	
807W	1-12	Beam Pent.	5AW-0-0	Cathode	6.3	0.900	0.2m	12.0*	7.0*	P.P.A.B2 Amp.	807W	


864	T-9	Triode	4D-0-0	Filament	1.1	0.950	5.3*	3.3*	2.1*	Det. Amp.	90	4.5	9.9	610	8.8	864
884	ST-12	Gas Triode	6O-0-0	Cathode	6.3	0.600	6.0*	2.0*	0.6*	Relay Tube	300	3.0	3.5	645	8.8	884
885	ST-12	Gas Triode	5A-0-0	Cathode	2.5	1.500	6.0*	2.0*	0.6*	Relay Tube	135	0.0	75	13,500	8.8	885
950	ST-14	Beam Pent.	5K-0-0	Filament	3.0	0.190	0.07m	3.4	3.0	Power Amp.	90	3.0	1.2	1,000	1,100	950
954	Acorn	Pentode	58B-0-0	Cathode	6.3	0.150	.007m	3.4	3.0	R-F Amp.	950	3.0	2.0	1,400	1,400	954
955	Acorn	Triode	58C-0-0	Cathode	6.3	0.150	1.3	1.0	0.4	Osc. Amp.	90	2.5	2.5	11,400	2,300	955

(1) Values are given shielded unless marked with (*). (2) Has special mechanical end (or life characteristics). (3) Plate and/or grid to plate. (4) Connect terminal bias developed across specified grid resistor. (5) Controlled Heater Warm-up Time (applies to parallel connections of types having a tapped heater).

Per Tube or Section.
 † Plate and/or Grid Supply Voltage.
 ‡ Maximum Signal.

□ Applied through 20,000 ohms.
 * Cathode Transconductance.
 † Triode Operation.

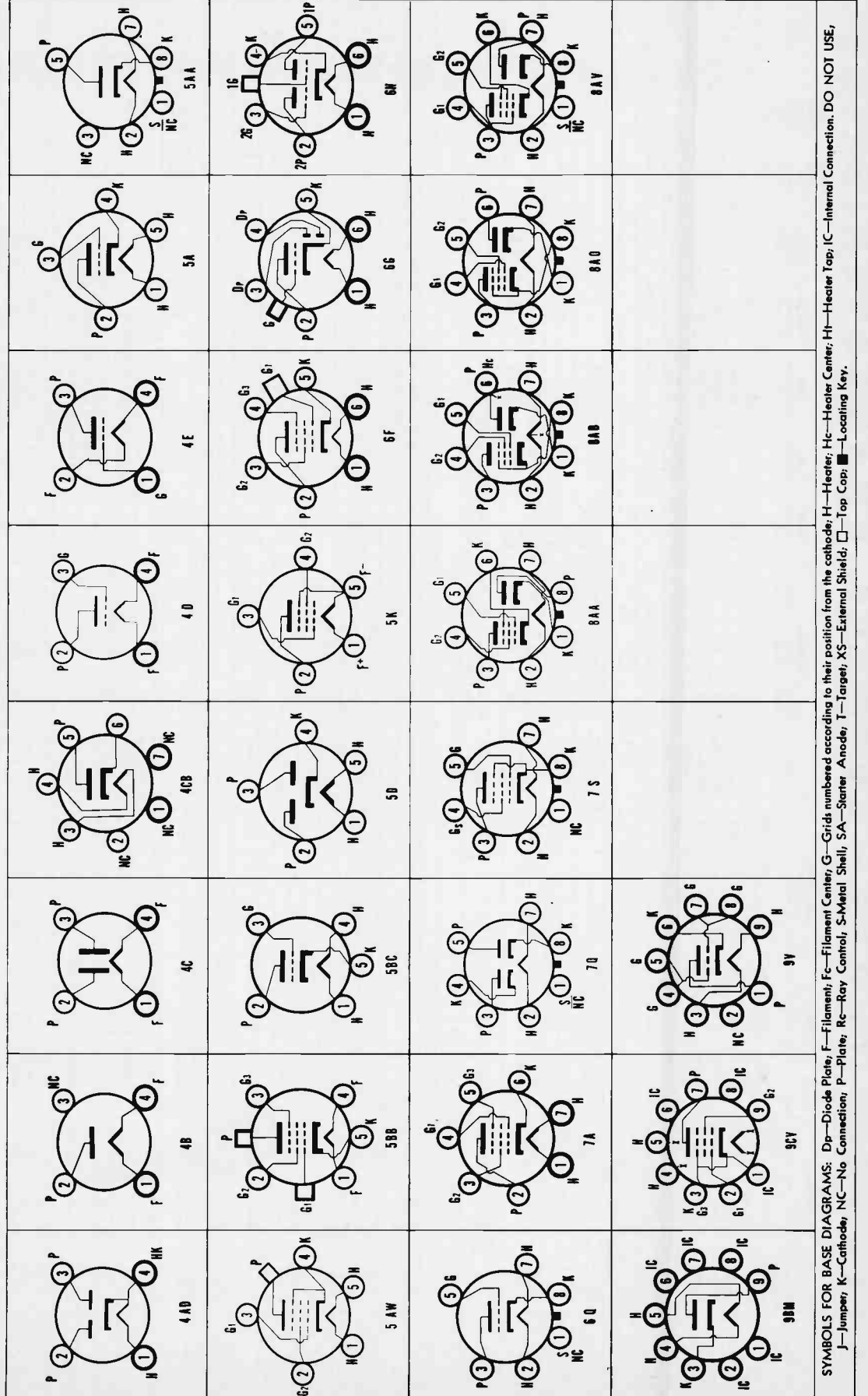‡ Plate to Plate.
 † Approximate.
 ‡ Cathode Resistor (ohms).



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; R—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNY TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (1) (2) Capacitances in μ f.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon-ductance Micromhos	Amplifi-cation Factor	Ohms Load for Stated Power Output	Unde-veloped Power Milli-watts	Type
	Bulb Size or Style	Class	Beating Diag.	Type	Volts	Amps.	Cpd.												
956	Acom	Pentode	58B-0-0	Cathode	6.3	0.150	.007m	3.4	3.0	3.0	100	6.7	2.7	700,000†	1,800	956	
957	Acom	Triode	58D-0-0	Filament	1.2	0.050	1.2	0.7	0.7	3.0	3.0	3.0	3.0	30,800†	650	957	
958-A	Acom	Triode	58D-0-0	Filament	1.25	0.100	2.6	0.6	0.8	3.0	3.0	3.0	3.0	10,000†	1,200	958-A	
959	Acom	Pentode	58E-0-0	Filament	1.25	0.050	.015m	1.8	2.9	3.0	67.5	1.7	0.4	800,000†	600	959	
FM1000	Lock-in	Heptode	FM1000	Cathode	6.3	0.300	FM1000	
1005/CK1005	Metal	Gas Diode	5AQ-0-1	Filament	6.3	0.100	1005/CK1005	
1801	Now Known as Type 7E5	1801	
1803-A	Now Known as Type 7C4	1803-A	
1804	Now Known as Type 7AB7	1804	
1806	Now Known as Type 7G8	1806	
1821	ST-12	Pentode	6F-0-5	Cathode	6.3	0.300	1821	
1822	ST-14	Beam Pent.	1822	Cathode	6.3	0.900	1822	
1823	ST-12	Pentode	4R-0-0	Filament	6.3	0.300	1823	
1829	ST-12	Tetrode	4K-0-0	Filament	2.0	0.060	1829	
1830	T-9	Triode	4D-0-0	Filament	2.0	0.060	6.0*	3.0*	2.1*	1830	
1831	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.450	.015m	8.5	6.5	1831	
1832	Now Known as Type 7G7	1832	
1836A	T-9	Diode	1836A	Filament	1.9	0.450	1836A	
1838	T-9	Duo. Beam Amplifier	88S-L-0	Cathode	8.0	0.400	1838	
1847	T-3	Diode	1847	Filament	0.7	0.065	1847	
1865	ST-12	Diode	4AJ-0-0	Cold K	1865	
1866	T-9	Diode	4AJ-0-0	Cold K	1866	
1867	T-9	Gas Triode	4V-0-0	Cold K	1867	
1873	Lock-in	Pentode	8V-L-5	Cathode	6.3	0.300	.004m	6.0	6.5	1873	
1874	T-9	Duodiode	6S-0-0	Filament	6.3	0.600	1874	
1875	ST-16	Duodiode	4C-0-0	Filament	5.0	1.750	1875	
1876	ST-16	Triode	4D-0-0	Filament	4.5	1.140	1876	
1880	Lock-in	Pentode	8V-L-5	Cathode	12.6	0.150	.004m	6.0	6.5	1880	
1884	Lock-in	Pentode	8V-L-5	Cathode	12.6	0.150	.01	5.0	6.0	1884	
1891	Now Known as Type 3B7	1891	
1893	Lock-in	Triode	4AA-L-0	Filament	1.4	0.110	1.7	1.7	3.0	1893	
1894	Now Known as Type 1R4	1894	
1899	Now Known as Type 3D6	1899	
1612	Metal	Heptode	7T-1-0	Cathode	6.3	0.300	.001m	7.5	11.0	1612	
1614	T-10 Sp.	Beam Pent.	7S	Cathode	6.3	0.900	0.4m*	10*	12*	1614	
1625	ST-16	Beam Pent.	5AZ	Cathode	12.6	0.450	0.2m*	11*	7*	1625	
1686	ST-12	Triode	6O-0-0	Cathode	12.6	0.250	4.4*	3.2*	3.4	1686	
1689	T-9	Electron Ray	7AL-0-0	Cathode	12.6	0.150	1689	
9050	ST-12	Gas Tetrode	68S-0-0	Cathode	6.3	0.600	0.26*	4.2*	3.6*	9050	
9051	ST-12	Gas Tetrode	68S-0-0	Cathode	6.3	0.600	0.26*	4.2*	3.6*	9051	
5517/CK1013	T-5½	Gas Diode	8BU	Cold K	5517/CK1013	
5590	T-5½	Pentode	78D-0-0	Cathode	6.3	0.150	.01	3.4	2.9	5590	
5591	T-5½	Pentode	78D-0-0	Cathode	6.3	0.150	.02	4.0	2.8	5591	
5608-A	ST-14	Duodiode	78-0-0	Cathode	2.5	2.000	5608-A	
5633 (3)	T-3	Pentode	5633	Cathode	6.3	0.150	.01m	4.0	2.8	5633 (3)	
5634 (3)	T-3	Pentode	5633	Cathode	6.3	0.150	.01m	4.4	2.8	5634 (3)	
5635 (3)	T-3	Duodiode	8DB-0-0	Cathode	6.3	0.450	1.2	2.6	1.6	5635 (3)	
5636 (3)	T-3	Pentode	8DC-0-0	Cathode	6.3	0.150	.015m	4.0	3.4	5636 (3)	
5637 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	1.3	2.8	3.2	5637 (3)	
5638 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.19	4.0	6.5	5638 (3)	
5639 (3)	T-3	Beam Pent.	8DL-0-0	Cathode	6.3	0.450	0.1m	9.5	7.5	5639 (3)	

(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate; RF input, Mixer Output, specified grid resistor.
 (4) Average Contact potential bias developed across sections of types having a tapped heater.)
 † Per Tube or Section.
 ‡ Plate and Target Supply Voltage.
 † Maximum Signal.
 ‡ Applied through 20,000 ohms.
 † Conversion Transconductance.
 ‡ Triode Operation.
 † Plate to Plate.
 ‡ Approximate.
 † Cathode Resistor (ohms).

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Note (*) (†) Capacitances in $\mu\mu\text{f}$.		Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Amplification Factor	Ohm Load for Stated Power Output	Power Output Milliwatts	Type
	Beam Pent. Diode	Class	Type	Volts	Amps.	Cyp.												
5640 (3)	T-3	Beam Pent.	8DL-0-0	Cathode	6.3	0.450	0.9	9.0	6.5	100	31.0	3.2	15,000	5,000	3,000	1,250	5640 (3)
5641 (3)	T-3	Diode	6CJ-0-0	Cathode	6.3	0.450	117 A-C Volts Per Plate, RMS, 45 Ma. D-C Output. Condenser input to Filter.	5641 (3)
5642 (3)	T-3	Diode	5642	Filament	1.25	0.200	0.6*	H-W Rect.	Pulse Type Rectifier for Television Service, 10,000 Volts Peak Inverse.	5642 (3)
5643 (3)	T-3	Gas Triode	8DD-0-0	Cathode	6.3	0.15	0.1	1.7	1.6	150 5 A-C	0	30	(Grid Bias Voltage 180° Out of Phase with Anode Voltage)	5643 (3)
5644 (3)	T-3	Gas Triode	4CN-0-0	Cold K	5644 (3)
5645 (3)	T-9	Triode	5645	Cathode	6.3	0.150	1.2	2.4	3.4	5645 (3)
5646 (3)	T-9	Triode	5646	Cathode	6.3	0.150	1.2	2.4	3.4	5646 (3)
5647 (3)	T-1	Diode	5647	Cathode	6.3	0.150	5647 (3)
5651	T-5½	Gas Diode	580-0-0	Cold K	5651
5654/RMSW (3)	T-5½	Pentode	7BD-0-2A7	Cathode	6.3	0.175	0.08m	4.0	2.9	Starting Voltage = 115 Volts Max. Operating Voltage = 92 Volts Max. Operating Current = 3.5 Ma. Max.	5654/RMSW (3)
5670 (3)	T-6½	Duodiode	8CJ-0-5	Cathode	6.3	0.350	1.1	2.2	1.0	H-F Amp. #	5670 (3)
5679	Lock-in	Duodiode	7CX-L5	Cathode	6.3	0.150	5679
5685 (3)	T-6½	Beam Pent.	9G-0-0	Cathode	6.3	0.900	3.8*	4.0*	0.45*	5685 (3)
5687	T-6½	Duodiode	9H-0-0	Cathode	12.6	0.450	5687
5691 (3)	T-9	Duodiode	8BD-0-0	Cathode	6.3	0.600	3.6*	2.4*	2.3*	5691 (3)
5692 (3)	T-9	Duodiode	8BD-0-0	Cathode	6.3	0.600	3.3*	2.3*	2.5*	5692 (3)
5693 (3)	Metel	Pentode	8N-1-0	Cathode	6.3	0.300	0.035m	5.8	6.8	5693 (3)
5694 (3)	ST-14	Duodiode	8CS-0-0	Cathode	6.3	0.800	5694 (3)
5702	T-3	Pentode	5702	Cathode	6.3	0.900	0.03m	4.4	3.5	R-F Amp.	5702
5703	T-3	Triode	5703	Cathode	6.3	0.200	1.15	2.7	2.1	H-F Osc.	5703
5704	T-2	Diode	5704	Cathode	6.3	0.150	VHF Det.	5704
5718 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	1.3	2.4	2.4	5718 (3)
5719 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	0.8	1.9	2.2	5719 (3)
5722	T-5½	Diode	5CB-0-0	Filament	4.9	1.600	5722
5725 (3)	T-5½	Pentode	7BD-0-5	Cathode	6.3	0.175	0.1	3.9	3.0	5725 (3)
5726/RMSW (3)	T-5½	Duodiode	8BT-0-6	Cathode	6.3	0.300	5726/RMSW (3)
5731	Acorn	Triode	58C-0-0	Cathode	6.3	0.150	1.3*	1.0*	0.4*	5731
5744	T-3	Triode	5744	Cathode	6.3	0.200	0.8	2.7	2.4	5744
5749/68A6W (3)	T-5½	Pentode	78K-0-2	Cathode	6.3	0.300	0.0035m	5.5	5.5	5749/68A6W (3)
5751 (3)	T-6½	Duodiode	9A-0-0	Cathode	6.3	0.350	1.4*	1.4*	5751 (3)
5783	T-3	Gas Diode	5783	Cold K	5783
5784	T-3	Pentode	5784	Cathode	6.3	0.200	0.03m	3.9	3.0	5784
5785	T8x3	Diode	5785	Filament	1.25	0.015	5785
5787	T-3	Gas Diode	5787	Cold K	5787
5814 (3)	T-6½	Duodiode	9A-0-0	Cathode	6.3/12.6	0.350/0.175	1.5*	1.6*	0.5*	5814 (3)
5814A (3)	T-6½	Gas Triode	4CK-0-0	Cold K	5814A (3)
5823	T-5½	Beam Pent.	75-0-0	Cathode	25.0	0.300	5823
5824 (3)	ST-14	Diode	65-0-0	Cathode	12.0	0.600	5824 (3)
5838 (3)	T-9	Duodiode	65-0-0	Cathode	6.3	0.285	5838 (3)
5839 (3)	T-9	Duodiode	65-0-0	Cathode	6.3	0.150	0.013m	4.3	3.4	5839 (3)
5840 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.013m	4.3	3.4	5840 (3)
5842	T-6½	Triode	9V	Cathode	6.3	0.300	0.55*	9*	1.8*	5842
5844	T-5½	Duodiode	78F-0-0	Cathode	6.3	0.300	2.6*	2.6*	0.5*	5844
5845	T-5½	Duodiode	5CA-0-0	Filament	5.0m	0.435	5845
5847	T-6½	Pentode	9X-0-3 & 4	Cathode	6.3	0.300	0.04m	7.1	2.9	5847
5851 (3)	T-3	Pentode	6CL-0-0	Filament	1.25	0.110	0.055	2.5	3.0	5851 (3)
5852 (3)	T-9	Duodiode	65-0-0	Cathode	2.50	0.055	5852 (3)
5853 (3)	T-9	Beam Pent.	75-0-0	Cathode	6.3	1.200	5853 (3)
5871 (3)	T-9	Beam Pent.	75-0-0	Cathode	6.3	0.450	0.7*	9.5*	7.5*	5871 (3)

(1) Values are given shielded unless marked with (*). (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer Output, and Control Grid. (3) Has special mechanical and/or life characteristics. (4) Average contact potential bias developed across specified grid resistor. (5) Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)

† Per Tube or Section. ‡ Plate and Target Supply Voltage. § Applied through 20,000 ohms. ¶ Conversion Transconductance. ** Triode Operation.

□ Plate to Plate. †† Approximate. ‡‡ Triode Operation.

SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.

PENNSYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Notes (1) (2) Capacitance In $\mu\text{f.}$			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transcon- ductance Microhmhos	Ampli- fication Factor	Ohms Load for Stated Power Output	Unde- r- tor- ted Power Output Milli- watts	Type
	Bulb Size or Style	Class	Base Dia.	Type	Volts	Amps.	Cap.	Cin.												
5879	T-6½	Pentode	9AD-0-0	Cathode	6.3	0.150	0.11m*	2.7	2.4	3	100	1.8	0.4	9,000,000†	1,000	31	5879	
5881	T-11	Beam Pent.	75-0-0	Cathode	6.3	0.900	5881	
5889	T-3	Pentode	5889	Filament	1.85	7.5Ma	5889	
5896 (3)	T-3	Duodiode	8DJ-0-4	Cathode	6.3	0.300	5896 (3)	
5897 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	1.3	2.4	2.4	100	150	1.8	0.4	9,000,000†	1,330	5897 (3)	
5899 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	0.8	1.9	2.2	100	150	1.8	0.4	9,000,000†	1,330	5899 (3)	
5900 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.15m	4.4	3.4	100	120	1.8	0.4	9,000,000†	1,330	5900 (3)	
5901 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.15m	4.4	3.4	100	120	1.8	0.4	9,000,000†	1,330	5901 (3)	
5902 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.15m	4.4	3.4	100	120	1.8	0.4	9,000,000†	1,330	5902 (3)	
5903 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	0.15m	4.4	3.4	100	120	1.8	0.4	9,000,000†	1,330	5903 (3)	
5910	T-5½	Pentode	6AR-0-5	Filament	1.4	0.050	0.08m	3.6	7.5	90	90	1.6	0.45	1,500,000†	900	5910	
5915A (3)	T-5½	Dual Control Heptode	7CH-0-0	Cathode	6.3	0.300	0.35*	5.4*	7.6*	150	0	7.5	0	Grid No. 3 Voltage = 0	5915A	
5930 (3)	T-12	Triode	4D-0-0	Filament	9.5	9.500	5930 (3)	
5931 (3)	T-12	Duodiode	5T-0-0	Filament	5.0	3.000	5931 (3)	
5932 (3)	T-12	Beam Pent.	75-0-0	Cathode	6.3	0.900	5932 (3)	
5963 (3)	T-4½	Duodiode	9A-0-0	Cathode	6.3	0.300	1.5*	1.9*	0.5*	150	0	8.3	5963 (3)	
5964 (3)	T-5½	Duodiode	7BF-0-0	Cathode	6.3	0.450	1.3*	2.1*	0.4*	100	50	9.5	5964 (3)	
5965	T-6½	Diode	9A-0-0	Cathode	6.3/	0.450/	3.0*	4.0*	0.5*	150	820	8.5	5965	
5968	T-3	Duodiode	8DQ	Filament	1.25	0.120	2.3*	0.9*	0.9*	135	3.0	4.5	0.7	5968	
5969	T-3	Duodiode	8DR	Filament	1.25	0.200	0.3*	2.5*	2.5*	135	3.0	4.5	0.6	5969	
5970	T-3	Duo Pentode	8DS	Filament	1.25	0.160	0.1*	3.3*	2.4*	45	5 Meg.	4.5	0.9	5970	
5971 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.150	1.3	2.0	2.2	100	270	10.0	5971 (3)	
5987 (3)	T-3	Triode	8DM-0-0	Cathode	6.3	0.450	3.2	3.2	5.0	100	18	9.0	5987 (3)	
6004	T-9	Duodiode	5T-0-0	Filament	5.0	3.000	6004	
6005 (3)	T-5½	Beam Pent.	7BZ-0-0	Cathode	6.3	0.450	6005 (3)	
6021 (3)	T-3	Duodiode	8DG-0-0	Cathode	6.3	0.300	1.4	2.1	100	150	6.5	6,480†	5,400	35	Count Sec. 1 = 1.3 $\mu\text{f.}$	6021 (3)	
6028	T-5½	Pentode	7BD	Cathode	20	0.050	.02	4.0	2.8	120	180	7.5	2.5	300,000	5,000	6028	
X6030	Lock-in	Diode	X6030	Filament	3.0m	0.600	90	4.0m	X6030	
6045	T-5½	Duodiode	7BF-0-0	Cathode	6.3	0.350	1.3*	2.0*	0.45*	100	50	9.0	5,940†	6,400	38	Cathodes Tied Together	6045	
6049 (3)	T-3	Pentode	8DL-0-0	Cathode	6.3	0.150	.009m	3.6	3.8	100	130	100	7.5	2.5	400,000	3,550	6049 (3)	
6053 (3)	T-3	Duodiode	8DJ-0-4	Cathode	6.3	0.300	6053 (3)	
6055 (3)	T-3	Duodiode	8DJ-0-4	Cathode	6.3	0.075	6055 (3)	
6056 (3)	T-3	Triode	8DK-0-0	Cathode	6.3	0.045	1.8*	2.8*	0.8*	96.5	Self	3.0	6056 (3)	
6080	T-12	Pentode	8DL-0-0	Cathode	6.3	0.045	.015m	4.0	3.4	96.5	Self	96.5	1.1	100,000	3,000	6080	
6080WA	T-12	Duodiode	8BD	Cathode	6.3	2.300	8*	6*	2.2*	135	250	125†	280	7,000	2	6080WA	
6082A	T-12	Duo Power Triode	8BD	Cathode	6.3	2.300	8.4*	6.2*	2.2*	135	250	125†	280	7,000	2	6082A	
6097	T-5½	Duodiode	6BT	Cathode	6.3	0.300	6097	
6110 (3)	T-3	Duodiode	8DJ	Cathode	6.3	0.150	6110 (3)	
6111 (3)	T-3	Duodiode	8DG	Cathode	6.3	0.300	1.5	1.9	0.98	100	320	8.5	4,200	4,750	30	6111 (3)	
6112 (3)	T-3	Duodiode	8DG	Cathode	6.3	0.300	1.0	1.7	0.93	100	150	0.8	38,900	1,800	70	6112 (3)	
6118 (3)	T-3	Duodiode	8DG	Cathode	6.3	0.300	1.4	5.0	0.98	100	150	0.8	58,000	1,900	70	6118	
6145	T-9	Pentode	8V-0-5	Cathode	6.3	0.600	.06m	14.0	7.5	150	0	3.4	8.0	0.1 Meg.	9,700	6145	
6146	T-12	Beam Pent.	7CK-8-1, 4, 6	Cathode	6.3	1.850	0.24*	15.9*	10.6*	600	45	180	26-200†	1.23†	6146	


PENNY TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter		Notes (1) Capacitors in μ f.			Use	Plate Volts	Negative Grid Volts	Screen Volts	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Micromhos	Anpl. Reaction Factor	Ohms Load for Stated Power Output	Power Output Milliwatts	Type
	Bulb Size or Style	Class	Basing Diagram	Type	Volts	Ampl. Series	Cpn.												
6352	T-3	Duodiode	8EY-0-0	Filament	3.0	3.00	6352	
6394A	T1-16	Duo Power Triode	8BD	Cathode	26.5	1.300	21.8*	16.7*	3.8*	6394A	
6463	T-6 1/2	Duodiode	9CZ-0-0	Cathode	6.3	0.600	5.0*	3.0*	0.6*	6463	
6486A	T-6 1/2	Pentode	9DV	Cathode	12.6	0.300	5.0*	3.0*	0.5*	6486A	
6516	T-5 1/2	Beam Pent.	6CH	Cathode	6.3	0.250	.04	4.4	3.7	6516	
6520	T-16	Duo Power Triode	8BD	Cathode	6.3	0.200	0.3m	4.25	6.5	6520	
6528	ST-16	Duo Power Triode	8BD	Cathode	6.3	2.500	9.4*	8.4*	2.2*	6528	
6550	ST-16	Beam Pent.	7S-0-0	Cathode	6.3	5.000	23.8*	17.8*	2.9*	6550	
6582A	T-6 1/2	Pentode	9EJ	Cathode	6.3	1.600	0.85*	14.0*	12.0*	6582A	
6586	T-5 1/2	Gas Diode	5BO-0-0	Cathode	6.3	0.250	.03	4.5	3.0	6586	
6626	T-5 1/2	Gas Diode	5BO-0-0	Cold K	6626	
6690 (3)	T-3	Duodiode	8GQ-0-0	Cathode	6.3	0.300	9.1m	3.9m	1.8m	6690 (3)	
6788	T-3	Pentode	8DL	Cathode	6.3	0.175	.032	2.4	3.3	6788	
6814	T-3	Triode	8DK	Cathode	6.3	0.150	1.3	2.4	3.4	6814	
6832	T-3	Duodiode	8DG	Cathode	6.3	0.400	6832	
6840	T-6 1/2	Duodiode	9CZ	Cathode	12.6	0.400	5.5*	4.0*	0.7*	6840	
6851	T-6 1/2	Duodiode	9A	Cathode	6.3	0.250	1.4*	1.6*	0.46*	6851	
6854	T-6 1/2	Duodiode	9FV	Cathode	6.3	0.500	1.7*	2.4*	1.1*	6854	
6870	T-6 1/2	Beam Pent.	9BF	Cathode	6.3	0.600	.025m*	8.5*	7.0*	6870	
6877	T-6 1/2	Power Triode	9GB	Cathode	6.3	0.800	6877	
6883	T-12	Beam Pent.	7CK-B-1A,6	Cathode	12.6	0.825	0.24*	13.5*	8.3*	6883	
6893	T-12	Beam Pent.	7CK-B-1A,6	Cathode	12.6	0.400	0.2*	12.5*	7.0*	6893	
6900	T-6 1/2	Duo Power Triode	9H	Cathode	6.3	0.900	4.0*	4.0*	0.6*	6900	
6913	T-6 1/2	Duodiode	9A-0-0	Cathode	12.6	0.450	4.0*	4.0*	0.5*	6913	
6919	T-5 1/2	Duodiode	68T	Cathode	6.3	0.300	3.4*	3.6*	0.5*	6919	
6922	T-6 1/2	Duodiode	9DE	Cathode	6.3	0.300	1.4*	3.3*	1.75*	6922	
6943	T-3	Pentode	8DC	Cathode	6.3	0.175	1.4*	3.3*	1.65*	6943	
6944	T-3	Pentode	8DC	Cathode	6.3	0.175	.015	3.0	3.0	6944	
6945	T-3	Beam Pent.	8DL	Cathode	6.3	0.350	.013	2.9	3.1	6945	
6946	T-3	Triode	8DK	Cathode	6.3	0.175	1.0*	1.6*	0.75*	6946	
6947	T-3	Duodiode	8DG	Cathode	6.3	0.350	1.2*	1.6*	0.25*	6947	
6948	T-3	Duodiode	8DG	Cathode	6.3	0.350	0.75*	1.6*	0.2*	6948	
6954	T-5 1/2	Pentode	7CM	Cathode	6.3	0.300	.0035m*	6.0*	5.0*	6954	
6955	T-6 1/2	Duodiode	9A	Cathode	6.3	0.350	1.4*	1.5*	0.5*	6955	
6958	T-5 1/2	Pentode	7BD	Cathode	12.6	0.175	1.4*	1.5*	0.4*	6958	
6973	T-6 1/2	Beam Pent.	9EU	Cathode	6.31	0.450	0.4	6	6	6973	
7001	T-5 1/2	Beam Triode	7EJ	Cathode	6.3	0.450	0.1m	7.0	8.75	7001	
7025	T-6 1/2	Duodiode	9A	Cathode	12.6	0.150	1.7*	1.6*	0.46	7025	
7027	T-12	Beam Pent.	8HY	Cathode	6.3	0.900	1.5*	10*	7.5*	7027	

SYLVANIA TUBES — AVERAGE CHARACTERISTICS

Type	Construction		Emitter			Noise (1) (7) Capacitances in $\mu\mu\text{f}$.		Use	Plate Vols	Negative Grid Vols	Screen Vols	Plate Current Ma.	Screen Current Ma.	Plate Resistance Ohms	Transconductance Microamhos	Amplification Factor	Ohms Load for Stated Power Output	Unloaded Power Output Milli-watts	Type
	Ball Size or Style	Class	Base	Type	Vols	Amps.	Csp.												
7167	T-3 1/2	Tetrode	7EW	Cathode	13.5	0.090	.03m	4.4	2.74	VHF Amp.	250	1.0	80	10	1.4	125,000	8,000	7167
7212	T-12	Beam Pent.	9EC	Cathode	6.3	1.250	0.24m*	13.5*	8.5*	P.P.A.B1 Amp. P.P.A.B1 Amp. P.P.A.B2 Amp.	600 500 600	45 40 185	1-231 2-251 22-2071	1.231 2.251 0.6-1.71	7,000 5,500 6,800	82,000 70,000 90,000	7212
7244	T-5 1/2	DuoDiode	7BF	Cathode	6.3	0.450	1.4*	3.0*	0.34* 0.28*	Tri. Amp. Pent. Amp.	100 125	30 36	9.0	6,300	6,000	7244
7258	T-6 1/2	Tri. Pentode	9DA	Cathode	13.5	0.210	1.5*	2.0*	0.26* 0.24*	Tri. Amp. Pent. Amp.	150 125	3 36	15 12	3.8	4,700 170,000	4,500 7,800	7258
9001	T-5 1/2	Pentode	7BD-0-7	Cathode	6.3	0.150	.01	3.6	3.0	R-F Amp.	350	3.0	100	2.0	0.7	1 Meq >	1,400	9001
9002	T-5 1/2	Triode	7BS-0-0	Cathode	6.3	0.150	1.4	1.3	1.1	Amplifier	350	7.0	6.3	2,900	9002	
9003	T-5 1/2	Pentode	7BD-0-7	Cathode	6.3	0.150	.01m	3.6	3.0	R-F Amp.	350	3.0	100	6.7	700,000	1,800	9003
9004	A-com	Diode	48L-0-0	Cathode	6.3	0.150	H-W Rect.	117 Vols RMS Plate, 5 Ma. D-C Output.	9004
9005	T-5 1/2	Diode	5BG-0-0	Cathode	6.3	0.150	H-W Rect.	117 Vols RMS Plate, 1.0 Ma. D-C Output.	9005
9006	T-5 1/2	Diode	68H-0-0	Cathode	6.3	0.150	H-W Rect.	170 Vols RMS Plate, 5 Ma. D-C Output.	9006
XXD	Now Listed as 1AA7/XXD																		XXD
XXFM	Now Known as Type 7X7																		XXFM
XXL	Lock-In	Triode	5AC-L-0	Cathode	6.3	0.300	Amplifier	100	0.0	10.0	7,000 8,700	3,600 2,300	XXL

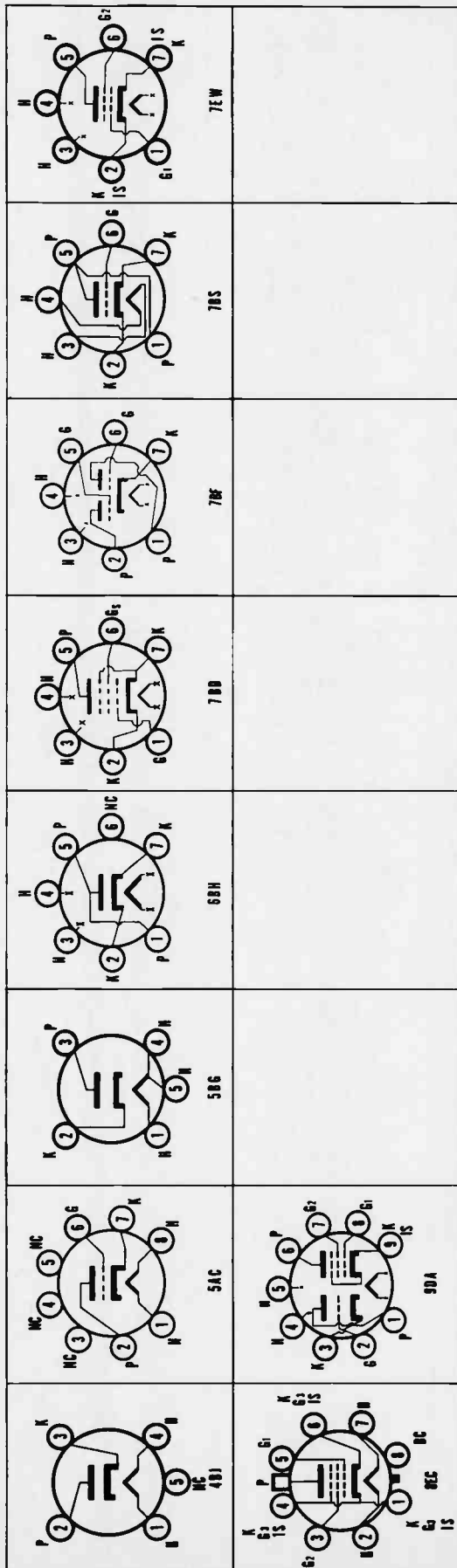(1) Values are given shielded unless marked with (*). (3) Has special mechanical and/or life characteristics.
 (2) Converter tube capacitances given are signal grid to plate, RF input, Mixer Output.
 (4) Average Contact potential bias developed across specified grid resistor.
 † Controlled Heater Warm-up Time (Applies to parallel connections of types having a tapped heater.)
 ‡ Per Tube or Section.
 § Plate and Target Supply Voltage.
 ¶ Maximum Signal.
 * Applied through 20,000 ohms.
 † Convention Transconductance.
 ‡ Triode Operation.
 †† Plate to Plate.
 ††† Approximate.
 †††† Cathode Resistor (ohms).



SYMBOLS FOR BASE DIAGRAMS: Dp—Diode Plate; F—Filament; Fc—Filament Center; G—Grids numbered according to their position from the cathode; H—Heater; Hc—Heater Center; Ht—Heater Tap; IC—Internal Connection; DO NOT USE, J—Jumper; K—Cathode; NC—No Connection; P—Plate; Rc—Ray Control; S—Metal Shell; SA—Starter Anode; T—Target; XS—External Shield; □—Top Cap; ■—Locating Key.



LESSON 10

Radio Frequency Amplification Superheterodyne Principles

The actions of tuned circuits and of vacuum tubes are utilized to select and increase the weak signals received by the antenna. The amplification in any modern radio set is accomplished at radio frequencies before detection, and at audio frequencies after detection. I.F. used is considered radio frequencies.

SELECTIVITY A radio receiver must separate the signals of any station wanted from the signals of all remaining operating stations. The degree of selectivity is the ability of the receiver to perform this function. Since the broadcast band stations are separated by 10 KC., selectivity that is sufficient to separate stations 10 KC. apart is employed.


SENSITIVITY The receiving set must also amplify the incoming signal voltage to a sufficient degree to operate the loud-speaker. The sensitivity of a receiver is the measurement of overall amplification from the antenna input to the loud-speaker connections. Sensitivity should be as large as practical; it is possible to over do this in modern high gain sets.

All noise collectively picked up by the receiver is known as the noise level. If the wanted signal has less strength than the stray impulses forming the noise level, that station cannot be received successfully. Therefore, a radio set that can "go down" to the noise level is as sensitive as is required.

FIDELITY The exactness with which the receiver reproduces speech and music is an indication of its fidelity. The radio receiver should not distort, add, change, or alter the original broadcasted sound (audio frequencies) in any way.

T. R. F. A tuned radio frequency amplification stage consists of an input tuned transformer and an output tuned transformer which also serves as the means of input for the next stage. It is possible to use a number of such T.R.F. stages pre-

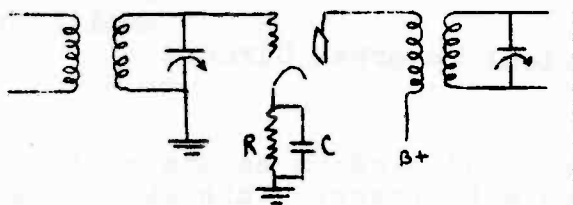ceding the detector to obtain the needed sensitivity and selectivity. The condensers used to tune the transformers are usually ganged together for single dial control. Each condenser section is identical and about .000365 mfd. capacity. Small trimmer condensers shunt each section and are adjusted to make up for the differences in capacity, etc.



TRIODE T. R. F. STAGE


VOLUME CONTROL REPLACEMENT

A large number of radio repairs center around the volume and tone control replacement. Every radio set has a volume control and a great many have tone controls. These units receive about as much handling and mechanical motion as the tuning dial and consequently do wear out with time. A volume control fault is easily detected even by the non-technical owner of the radio. It is bad practice to attempt to repair the original control, but in a few cases replacement resistor strips are available and are easily installed. For best results and time economy, a bad volume control should be replaced. To detect the fault notice if the volume change is gradual; if it is sudden, the arm does not make good contact or the resistance is worn out in spots. Another positive test is to short the different terminals of the control; if no change is noticed, the unit is at fault. Either there is an internal short, or an open circuit

The replacement of a volume control is about the easiest task servicemen come across. Look the set up in a volume control manual (available from any manufacturer of volume controls or the jobbers), obtain proper control, remove old control, install the new unit.

THE SUPERHETERODYNE PRINCIPLE

Present day receivers use in majority of cases the superhet circuit. In a superheterodyne the high carrier frequency of a desirable station is changed to a lower fixed frequency and amplified at that frequency. By a proper arrangement, it is possible to select any one station and change with the tuning equipment the frequency of that station or any other station on the same band to the same fixed frequency known as the intermediate frequency or I.F. Since the I.F. is constant, the amplifier used can be of the fixed type (no variable condensers used for tuning) and can be made more efficient (higher gain) than similar R.F. types.

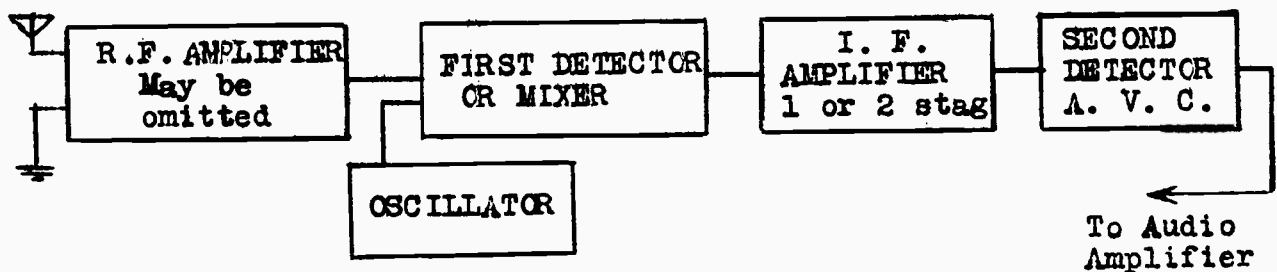


Diagrammatical Illustration of a Typical Superhet Circuit

The R.F. stage or the antenna tuned circuit separates to a limited degree the wanted signal from all others. This signal is mixed with the local oscillator signal to form the I.F. signal. The I.F. amplifier suppresses all unwanted signals and amplifies the desirable signal. A high gain may be obtained from a single I.F. stage (a gain of 75 is common).

If two different frequencies are mixed in a suitable tube, signals will be produced that are equal to the sum and to the difference of the original frequencies. For example, 650 KC. and 475 KC. will produce $650 + 475 = 1,125$ KC. and $650 - 475 = 175$ KC. Now suppose we are considering an actual case in a radio set where the I.F. amplifier is designed to pass 175 KC. (plus and minus 5 KC.) and we wish to receive a station transmitting on 650 KC. By simply adjusting the R.F. input stage to 650 KC. and the oscillator to produce a frequency of 475 KC., we will obtain 175 and 1,125 KC. frequencies. Of course, the I.F. amplifier will pass and amplify only the 175 KC. signal and the 1,125 KC. frequency will not be used. When a different station is selected, the oscillator frequency is correspondingly changed to produce the required 175 KC. I.F. signal.

AUTOMATIC VOLUME CONTROLS

There are numerous varieties of automatic volume control (A.V.C.) circuits, but they all work on the same principle. The A.V.C. arrangement is intended to maintain nearly constant the strength of the signal arriving at the detector, thus compensating for different signal strengths of different stations and for fading. It does this by varying the sensitivity of the R.F. and I.F. amplifiers. Actually A.V.C. changes the bias on these amplifier tubes to obtain this action. The actual volume is of course not kept constant because it depends on the percentage of modulation at the transmitter.

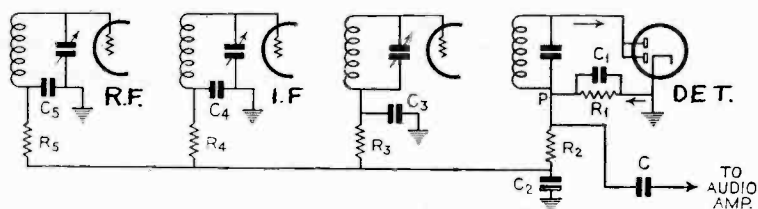

The schematic above illustrates an A.V.C. system often used in up-to-date sets. Forgetting for the moment the grid return resistors in the R.F. circuits, let us begin with the detector. The signal is rectified by a diode. Current can flow only when the diode becomes positive and the coil must then be considered as the generator. This will perhaps help to explain why the resistor R_1 will carry current in the direction of the arrow, making the point P negative with respect to the cathode and the chassis. This seems to be difficult to understand by many. The current flowing between P and the chassis consists of a direct current component, a radio frequency component, and an audio frequency component. The condenser C_1 has been placed across the resistor to pass most of the radio frequency currents and the audio frequency component is taken off to be applied to the grid by means of the coupling condenser C. The steady voltage at P, which is proportional to the strength of the incoming signal, must now be fed back to the R.F. and I.F. amplifiers, but the A.F. component must be filtered out and precautions for inter-stage coupling should be taken. This latter requirement is accomplished by the network of resistors and condensers.

The advantage of a superhet circuit comes from the use of pre-adjusted single frequency amplifiers (I.F. amplifiers) and means must be provided in such sets to convert the frequency of the station received to this intermediate frequency. This conversion is accomplished by generating a radio frequency higher than the signal and differing from it by the frequency of the I.F., and mixing this new frequency and the signal frequency in a non-linear impedance which can be provided by a vacuum tube operated over a non-linear part of its characteristic curve.

From this review, it is clear that an oscillator is needed to produce this new frequency and a mixer is required to combine these two frequencies. In the early types of superheterodyne receivers, a triode served as a local oscillator and another triode was used as the mixer. Since the mixer in such sets was operated as detector to obtain the non-linear characteristics, this tube in some literature is called the first detector while the detector used to "remove" audio signals is called the second detector.

Pentagrid converter tubes (of which 1A7, 6A7 and 6A8 are commonly encountered examples) have the electron stream influenced by both the signal and oscillator frequencies. A common cathode serves both the oscillator and mixer sections. The output is taken from the main plate. The oscillator grid is next to the cathode and the next grid serves as the oscillator anode. These elements form a triode which is connected to the oscillator coil and effects the current passing between the cathode and the main plate. Grids three and five are connected together to serve as the screen, while grid four is between them and is the control grid for the signal frequency.

Tubes of the single-ended types such as 6SA7 and 12SA7 have their elements connected somewhat differently from pentagrid converters we have just considered. Grid one nearest the cathode is here also used as the oscillator grid, but grids two and four are tied together and used as the screen, grid three is the R.F. input grid, and grid five nearest the plate is the suppressor. The oscillator coil used with such single-ended converter tubes has a single tapped winding.

Tubes such as 6J8 and 6K8 are really dual tubes, having some of their elements connected internally to provide required converter action.

REVIEW QUESTIONS


1. How is it possible to increase the sensitivity but not the selectivity of a radio receiver?
2. In a radio receiver having a 456 KC. I.F., when tuning in a station at 670 KC., what is the frequency of the oscillator?
3. Can a different AVC voltage be applied to each tube of two separate circuits? How?

LESSON 11

Power Supplies

A radio receiver requires a source of power for heating the filaments and for supplying the plate potential and grid bias. In a battery operated radio the power required is obtained from batteries of the correct voltages and capacities. The majority of the present day sets, however, are operated from power lines and require a special power supply unit incorporated into the radio chassis.

The primary function of a power supply is to furnish the required A.C. or D.C. voltages to the tubes' filaments, and also properly filtered plate supply so as to avoid hum and have satisfactory regulation. Usually the power supply also provides the necessary current for one or more speaker fields. There are power supplies for A.C. only and designed to be operated at the voltage and frequency of the supply, others for D.C. only, and still others for A.C. and D.C. combined.

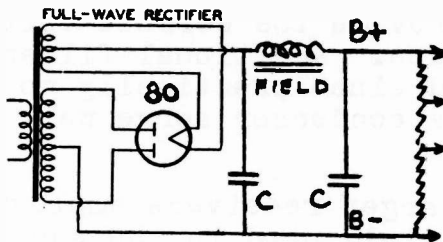


The essential parts that are employed in the simplest A.C. operated power supply are a power transformer to step the voltage up or down as needed, a rectifier tube, and one filter section consisting of a choke and two electrolytic condensers. Generally the choke can be the speaker field. The figure shows such a circuit which has become very popular. The resistance of the choke must be correctly chosen so that the total current drawn by the receiver is just sufficient to produce the required excitation in the electromagnetic field of the speaker.

This arrangement is probably the most economical one for small receivers. It is generally used with sets of relatively low sensitivity because there is only one filter section and any hum which reaches any of the early amplifying stages has only a limited amount of audio amplification. So, if this amplification is not too much, the hum in the speaker can be kept at a negligible level. Some small receivers will also be found to employ some form of hum-bucking coil in the voice coil circuit.

Note that a voltage divider consisting of high resistance units of the carbon type is used. The heavy bleeder of a few years ago is used very little now days. It is, of course, well


known that in cases where a heavy bleeder is absent, the voltage of the "B" supply will vary considerably with the current drain. The largest variation in drain is usually caused by the A.V.C. circuit which changes the bias on several tubes. In one case the plate voltage on the R.F. amplifier was 240 volts with a strong signal coming in, but dropped to 225 volts without signal. The result may be a slight shift in the oscillator frequency. Servicemen should keep these facts in mind when servicing such receivers.

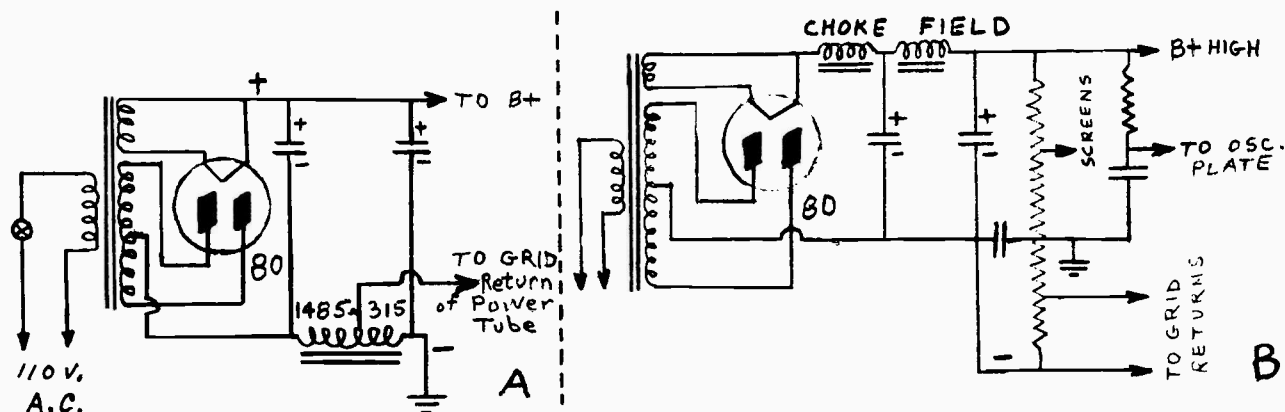

It is seen that if there is a drop of 105 volts across the speaker field; consequently when the specifications for the power transformer are made up, 105 volts must be added to the required plate voltage. This voltage drop can be utilized by placing the choke in the negative leg of the power supply and using a part of the supply for C bias. This is illustrated, next page. A tap on the field coil has been so chosen as to provide the correct voltage drop for the grid bias of the power tube. Additional filtering for the bias supply is easily provided since practically no current is taken. A high resistance and a condenser serve well for this purpose.

In B, a typical power supply for larger receivers employing two filter sections and with the speaker field used in the second section is illustrated. The filter stage ahead of the speaker field greatly reduces the hum introduced by the field itself besides lowering the hum level of the plate supply. The voltage divider serves as a bleeder to deliver semi-fixed bias to the driver stage. The output stage, however, as well as all other tubes are self biased.

AC-DC CIRCUITS

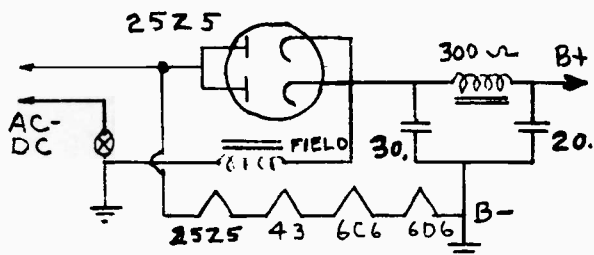


AC-DC sets employ tubes of either the 0.15 or 0.3 ampere filament current drain. The voltages vary, however, some are of the 6.3 volt type, others of the 25 volt, etc. The tubes are connected in series and a resistor is added so as to provide the required additional voltage drop. This resistor may be placed in the power cord so as to remove the heat from the chassis.

The B supply has only about 120 volts A.C. to start, so it is not possible to employ high resistance chokes. Consequently, the speaker field (if a dynamic speaker is used) cannot serve as a filter choke and is connected across the B supply. Filtering a 60 cycle supply is twice as hard as removing a 120 cycle ripple in full wave rectifiers. Reactances of the chokes are only half as much as for 120 cycles and reactances of condensers are twice as high offering a poorer path for the ripple voltage. One filter section is usually employed; large condensers are used and the choke can have larger inductance due to a relatively lower current.

Another problem with such AC-DC sets is the fact that the chassis, if tied to the B- side, becomes one side of the line and this may be the side that is not grounded. Accidental grounding of the chassis or the antenna wire would result in a short circuit. The last danger is circumvented by placing a series condenser in the antenna lead and making no provisions for a ground connection.

Newer type AC-DC sets that meet Fire Underwriters requirements, do not connect B- (plate voltage return) to the chassis in any direct way, but couple it to the chassis through a condenser, a resistor, or both.

While auto radio sets are battery operated in the sense that they secure their power from the 6 or 12-volt storage battery of the car, a power supply similar to the type we explained is still needed. By using 6.3 or 12-volt tubes, filament requirements can be obtained directly. But to obtain much higher plate voltage, the low battery voltage must be changed to interrupted D.C. (which has a behavior somewhat like A.C.), and then handled in the manner of familiar A.C. power supply.

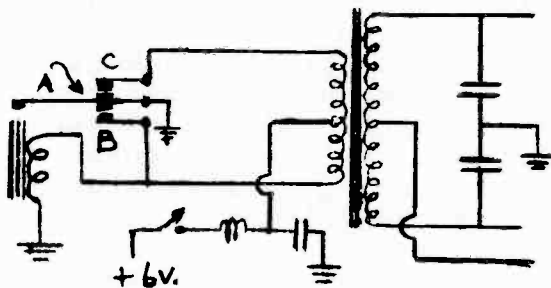


In connection with the operation of auto sets' power supplies we must carefully study the action of vibrators. The non-synchronous vibrator consists of an armature which is kept in vibration by an electromagnet on the same principle as the buzzer.

This diagram shows only the vibrator itself with the transformer and R.F. filter. When the switch is closed, current will flow through the lower half of the transformer primary and then through the magnet windings. The armature is then attracted and contact A will touch contact B, thereby short circuiting the electromagnet. The armature is then released again and swings back until contact A touches contact C. Meanwhile the electromagnet is attracting it again so that it keeps on vibrating at its own natural frequency and alternately touching contacts B and C. Now when contacts A and B are closed, the lower half of the primary is directly across the battery, which will result in a heavy current from the center tap downwards. When A touches C, the upper half of the primary is across the battery and a heavy current will flow from the center tap upwards. These two impulses

SYNCHRONOUS VIBRATORS

The armature of a synchronous vibrator closes another set of contacts which serve to rectify the current in the secondary. The figure shows this principle. When the armature moves downwards, it not only closes the primary circuit but also the secondary; when it moves up, the other halves of both the primary and secondary are closed. Buffer condensers are again employed in the secondary to improve the wave form. The usual R.F. filters and A.F. filter are used like in the other vibrator system.

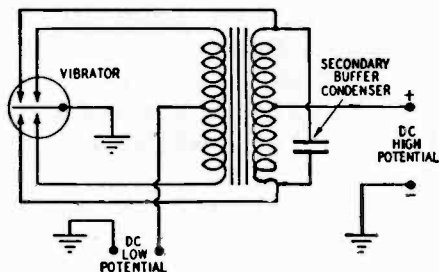

The most common fault with auto radio sets and with house sets employing vibrators, is vibrator trouble. The best procedure is to replace the unit with an exact duplicate.

Usually the vibrators are of the plug in type may be easily replaced.

A few practical service tests for A.C. operated power supplies will now be given. Determine if the power supply voltage reaches the transformer. This can be done by testing for voltage (A.C.) at the primary connections of the power transformer. Lack of voltage will suggest broken cord, poor connection at the socket, or defective switch. Next test for filament voltage, using your voltmeter or simply momentarily shorting one of the low filament windings and watching for a spark. Lack of voltage on any secondary will suggest a burned out primary winding, and this winding can be tested with an ohmmeter while the power is shut off.

Further tests may be conducted by breaking the B+ lead at the filament or cathode of the rectifier tube and measuring the amount of current consumed by the radio. If this current is very high, one filter condenser may be disconnected at a time and observing the effects produced. In case you are told by the owner of the radio that the rectifier tube needed replacements many times, suspect the input filter condenser.




The successful design of radio tubes with high voltage filaments and efficient operation with relatively low plate voltages permitted extensive use of AC-DC power supplies. In the older sets of this type, the heater voltage added up to a value considerably below the line voltage of 110 volts, and a voltage drop was produced with a line cord resistor or ballast tube. In more modern AC-DC sets, the tubes are selected so that the heater voltage adds up to the value of the line voltage and no dropping resistor is necessary. For the plate supply, use was made of half-wave rectifier or voltage-doubler circuits, and each of these will be treated from an advanced servicing point of view.

For a brief analysis of the half-wave rectifier power supply, let us first consider the action at the rectifier tube and input condenser which is made quite large in practice. While the plate of the rectifier tube is negative, it does not conduct and the current for the radio is supplied by the condenser which has been charged during the previous positive half of the cycle. When the alternating line voltage passes through the zero point and begins to supply an increasing positive potential to the plate, no conduction takes place until the sine wave positive value rises above the voltage-charge remaining in the filter condenser. Once started, this conduction lasts until the peak of the positive lobe of the sine wave is passed. When the sine wave value drops below the charge-voltage remaining in the condenser, and this occurs a short fraction of the cycle after the peak, the tube stops conducting although the positive half of the cycle is still in effect.

From this explanation, we can realize that the tube conducts over a small fraction of the cycle near the maximum point of the positive cycle. Fluctuations in the output voltage from the first condenser are less pronounced with large capacity, but a large condenser places a higher momentary load on the rectifier tube. The peak current through the rectifier tube may be many times the average of the D.C. current you may measure with a milliammeter. less than 20 mfd. in the first section of the filter when carrying out a repair. Also, condenser of metal can construction will radiate heat more efficiently than a cardboard unit. Placement away from parts which radiate heat should be your guide. The 150-volt condensers are adaptable for AC-DC supplies operated from 60 cycle A.C., but for 25 cycle use 200-volt or higher working voltage condensers will provide required safety factor.

The newly developed selenium rectifier is a natural replacement for half-wave rectifier tubes and presents several advantages. The technical facts about this new rectifier have been taken from a description of Sylvania type NC-5, but units of other makes are very similar. The actual size of the unit is 1-1/4 inches square and 11/16 inches thick and it mounts anywhere on the chassis by one bolt. Selenium rectifiers are similar in construction and performance to the copper-oxide disc rectifiers.

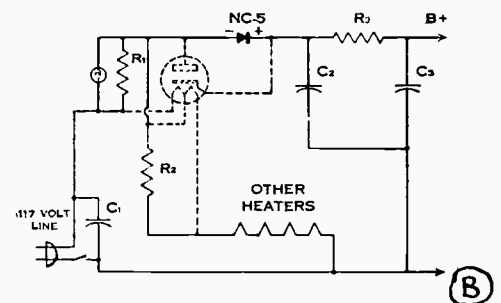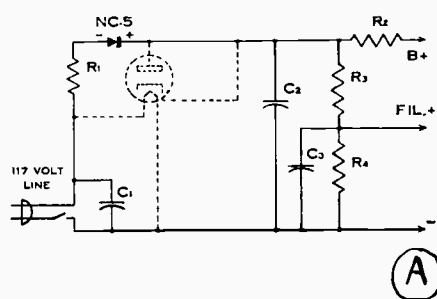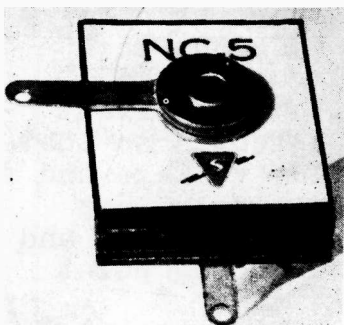The figures below show changes required when substituting a selenium rectifier for an ordinary rectifier tube in half-wave power supplies.



In Figure A, the heater circuit of the former 117 volt tube can be completely removed and the + side of the selenium rectifier connected to the cathode terminal and the minus side to the plate terminal. It is important to increase the value of the resistor R1 to restore the voltage on the tube filaments to the proper value. It would be inadvisable in this case to connect the resistor in such a place as to use additional plate voltage since the tubes are already being operated at the maximum rated voltage. The added resistance should be about 25 to 30 ohms, but may require adjusting slightly for different sets. The best way of making this adjustment is to use a 1000 ohm-per-volt meter to read the voltage across a 1.4 volt tube when the line voltage is exactly 117 volts. Adjust the resistance to get 1.3 volts under this standard condition.

Figure B shows the changes required when using the Sylvania type NC-5 as a replacement for a 35Z5 or 35Y4 rectifier tube. The important item here is R2 which must replace the rectifier tube heater in the series string. Be sure to place this so as not to overheat other parts as it will dissipate considerable heat. Table I gives the values of R2 recommended for the most common rectifier tubes.



TABLE I

Type	Heater Current	R2 Ohms	Watts	R1 Ohms
25Z5	.300	85	15	Not required
25Z6	.300	85	15	Not required
35W4	.150	200	10	10 to 25
35Y4	.150	200	10	10 to 25
35Z3	0.150	230	10	Not required
35Z4GT	0.15	230	10	Not required
35Z5GT	0.15	200	10	10 to 25
45Z5GT	0.15	270	10	10 to 25
50Y6GT	0.15	330	15	Not required
50Z7GT	0.15	330	15	10 to 25



Voltage doubler rectifier circuits have been used in many popular models. Basically there are two different circuits which produce a D.C. voltage approximately twice the A.C. line voltage. In the symmetrical type, two large capacity condensers are connected in series across the input to the filter section. Each of these condensers is also connected to a separate diode section (may be a part of 25Z5, or a separate diode rectifier) in such a manner that each half-cycle charges a different condenser. For best results, the two condensers employed should be of equal capacity or a strong 120 cycle hum will be noticed. To test for equality, shunt one condenser at a time with a 4 mfd. electrolytic and see if 120 cycle hum is reduced. If the original condensers in the set are balanced, any added capacity will increase the hum level. For added future safety when you are repairing a voltage doubler of the symmetrical type, add 25 ohm resistors in series with plate leads.

In power supplies of this type, there exists a potential difference between every cathode and heater even if one tube in the set has one filament connection grounded. Any cathode leakage in a tube will create much more trouble in a set using a voltage doubler circuit.

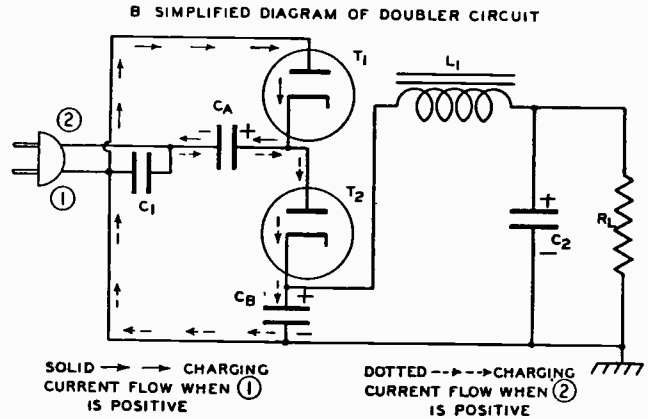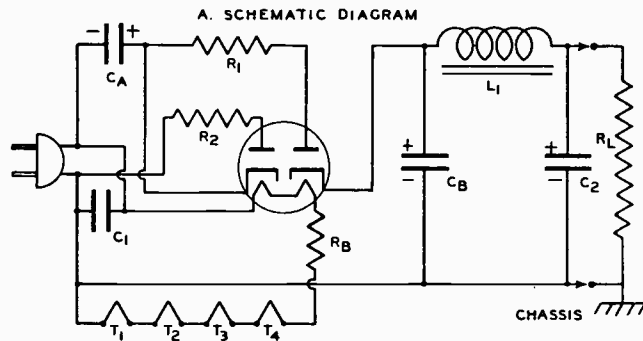SYMMETRICAL OR BALANCED TYPE OF VOLTAGE DOUBLER



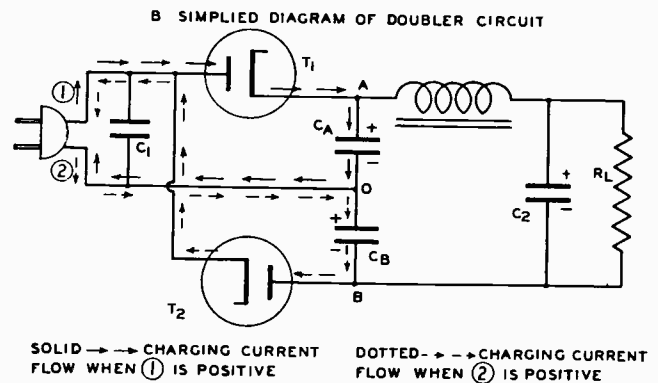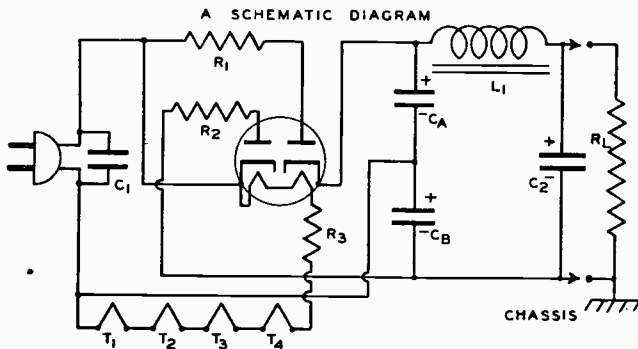COMMON LINE OR SERIES LINE FEED TYPE OF DOUBLER CIRCUIT



Courtesy P. R. Mallory & Co.

REVIEW QUESTIONS

1. Name several important reasons why batteries are not used for radio power in localities where electrical power is available.
2. What is the function of the power transformer? On what factors does the size of the transformer depend?
3. Why is the field coil of a dynamic speaker often used as the filter choke?
4. What advantage does an A.C. transformer type set have over the AC-DC radio?
5. Why are buffer condensers used in a vibrator power supply circuit? Notice that these condensers are placed in the secondary circuit at times, or sometimes connected in the primary circuit.
6. What advantage does a synchronous vibrator give?
7. What happens to the radio's response and the function of the different circuits, when the vibrator points become badly worn?


LESSON 12

Meters, Multitesters, and Tube Testers


Radio servicemen use meters as an aid in discovering faults or making adjustments in radio equipment. Knowledge of circuits permits the technician to foretell what electrical values may be expected at various sections or parts under test. Considerable variation in the values of these measurements suggest the existence of a fault which is isolated with further tests.

Electric current operates all meters and, therefore, it is current that is measured. The amount of current passing through the meter, however, is a function (depends upon) other electrical quantities (voltage, for example), and the meter scale may be calibrated directly in terms of voltage, resistance, capacitance, etc. We will review some essential fundamentals of meter construction, operation, basic circuits, and scale accuracy, before we proceed to study a few popular commercial volt-ohm-milliammeters and analyzers.

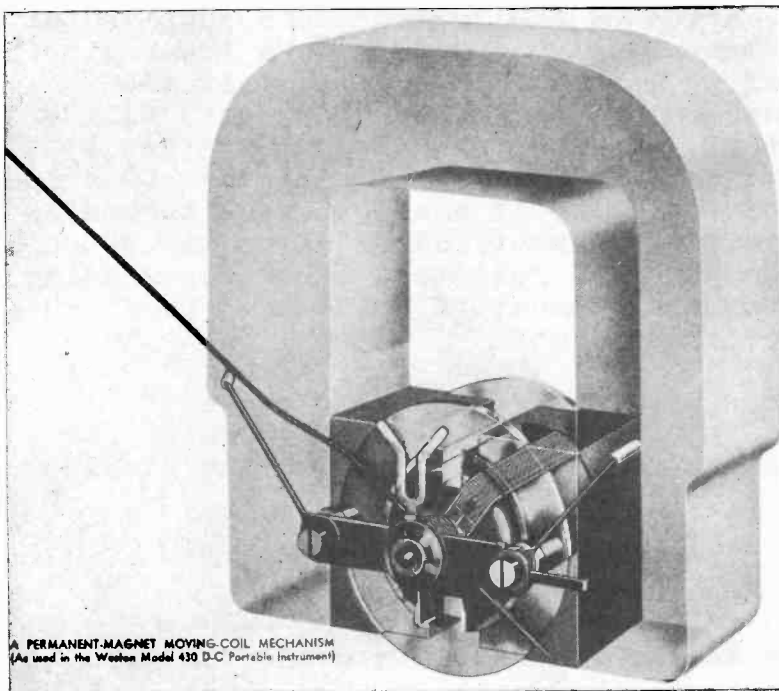The majority of today's direct current meters use D'Arsonnal type movement. This movement is sometimes called the permanent-magnet moving-coil type because of the components employed. In the two cut-away illustrations, you will notice that a large horse-shoe magnet forms the bulk of the unit. Between the pole



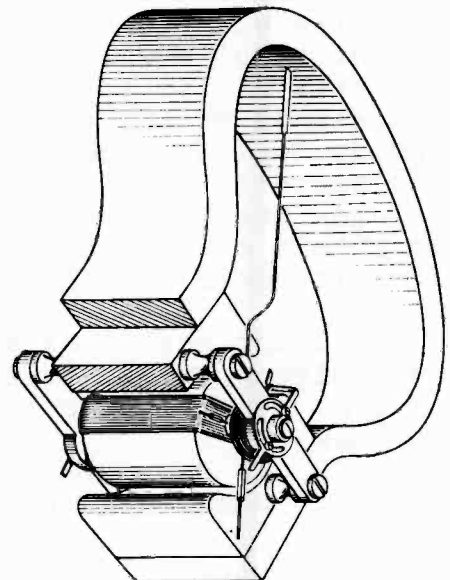A PERMANENT-MAGNET MOVING-COIL MECHANISM
(As used in the Weston Model 430 D-C Portable Instrument)



pieces, a light movable coil is suspended on pivots. The springs in front and behind the coil tend to turn the coil in opposite directions and, thereby, balance the coil and the pointer in a definite position. These springs are also used to conduct current to the coil from fixed terminals.

When the meter is used for measuring and current flows in the movable coil, an electromagnetic field is produced. This field of the electromagnet is of such a polarity that it bucks the field of the fixed horse-shoe magnet. This causes the coil to rotate to the right until the magnetic force is just balanced by the additional tension produced by the springs. The intensity of this rotating (electromagnetic) effort is proportional to the current. The actual amount of rotation, of course, depends on the design of the meter besides the amount of current present. Since the same amount of current will always rotate the coil and its attached pointer needle to a specific position, a calibrated scale can be mounted on the meter frame, behind the pointer, and used to indicate the actual value of the current present.

The movement is very finely balanced and very thin wire is used for the coil, so that little current is needed for even the maximum rotation. A great many meters used in radio testers require 1 ma. for maximum deflection. For special applications, where very minute currents must be measured or circuits must not be upset, meters of greater sensitivity, 50 micro-ampere movement, are employed.

Sensitivity of a milliammeter can be decreased by connecting shunts — resistors in parallel with the meter. The D.C. resistance of a milliammeter is marked on the instructions supplied with the instrument or can be measured with a bridge or a low-resistance ohmmeter which uses a separate meter. You know that if two resistors of equal value are connected in parallel, each will pass one-half of the total current. Let us assume our meter has a D.C. resistance of 100 ohms. We parallel it with a resistor 100 ohms and connect the combination to a circuit where we want to measure the current. The same amount of current indicated on the meter is also passing through the parallel resistor. Whatever reading we obtain on the meter, the total amount of current in the circuit under test is twice this value.

Shunt resistors are usually selected on the basis of multiplying the current scale by a factor of ten, or multiples of ten. The shunt resistor value is found by using the simple formula

$$\text{Shunt resistance} = \frac{\text{Meter resistance}}{(n-1)}$$

where n is the multiplying factor wanted to increase the current reading scale.

Scales of meters are marked off in suitable divisions to help you estimate the reading obtained. Take time to read values obtained, especially on unfamiliar meters. Even experts have wasted hours on repair jobs because of such errors.

To produce the maximum deflection in a current-measuring meter a definite voltage will be needed. This voltage, of course, will be equal to the product of the meter internal resistance and the current required for a full scale deflection. In the case where the internal resistance of the meter is 100 ohms, and the meter has zero-to-one-milliamperere movement, this voltage is 1/10 volt. ($100 \times .001$; this second figure is one milliamperere expressed in amperes).

To make this meter suitable for measuring much higher voltages, series resistors of suitable sizes are connected. If 50 volts are to be measured, as a maximum, a suitable scale is incorporated in the meter and the test prods are connected to the meter in series with a resistor of 50,000 ohms. The meter resistor of 100 ohms can be ignored since it is so small when compared to 50,000 ohms. Notice that 50 volts will just cause a current of one milliamperere to pass through the circuit. This circuit has the meter and the meter will in this instance indicate full deflection. Other value resistors used with a suitable switching method will permit the same meter to be used for many additional measurements.

The same meter incorporating a battery (or other D.C. voltage source) and a series resistor which will produce full scale deflection upon the shorting of the test prods form a high resistance ohmmeter. For example, a $4\frac{1}{2}$ volt battery may be used with an adjustable potentiometer which can provide an average value of 4,500 ohm resistance.

With this arrangement, when the prods are shorted, the circuit is completed. The meter shows maximum current, but the resistance between the prods is zero. So the point of maximum current (usually at the right) is marked 0 ohms on the ohmmeter scale. If a 4,500 ohm resistor is being measured by being connected between the prods, the current will drop to one half its previous value since the series circuit will be double its previous resistance. The meter needle will stop at the half-way mark. This point will correspond to 4,500 ohms.

An ohmmeter scale is more spread out at the right for low values and is very congested for extremely high values. The ohmmeter we described can be read for values up to about 500,000 ohms, after that the total space of the scale remaining before the infinity mark is reached is so small that no accurate reading is possible. Some ohmmeters, of course, are made to read up to several megohms. This is accomplished by using meters of greater sensitivity or by connecting higher voltage battery. If you have an ohmmeter, for example, employing a $4\frac{1}{2}$ volt battery, replacing


it with 45 volt battery and connecting an additional resistor of 40,000 ohms in series will multiply your scale (on high ohms, only) by a factor of 10.

For low resistance measurements, under 50 ohms, a shunt arrangement is used. This will be explained further as we study a few commercial units.

All meters lack perfection of accuracy. In practical work very rough reading is usually sufficient and 5% accuracy is very satisfactory. The errors are due to several causes. The meter cannot be calibrated perfectly. The scales are printed from a drawing which is based on a typical meter of the type considered. However, not all bearings, springs, magnets, and coils are exactly alike and slight variations in responding to the same current always result. The same current, therefore, may give slightly different readings in several similar meters. Errors are also due to the associated resistors and to the width of the pointer.


Always use the lowest value scale which will permit measuring values obtained. It is obvious that 7 volts can be read more accurately on a 0-10 volt scale than on the 0-100 volt scale. The meter itself is usually more accurate in the center of the scale than at the edges.

The meters we have discussed so far can be used with D.C. only. It is possible to use a regular D.C. meter for measuring alternating current or voltage with the aid of a rectifier unit. The rectifier changes A.C. to D.C. and the value of A.C. voltage or current is measured on special scales. Usually these scales are calibrated for a given A.C. frequency, and considerable variation in frequency will cause additional errors. The rectifier elements are made of copper oxide and the current is permitted to pass only in one direction.

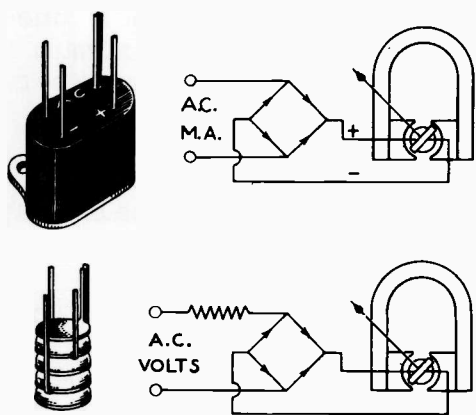


Several diagrams showing the method for connecting a four element bridge of copper oxide discs are shown on the left. These illustrations are reproduced through the courtesy of Weston Electrical Instrument Corp. It is important to realize that the sensitivity of the meter is reduced when a rectifier is used and different scales must be employed for A.C. and D.C. measurements. Any rectifier meter reads average values but is calibrated in terms of R.M.S.

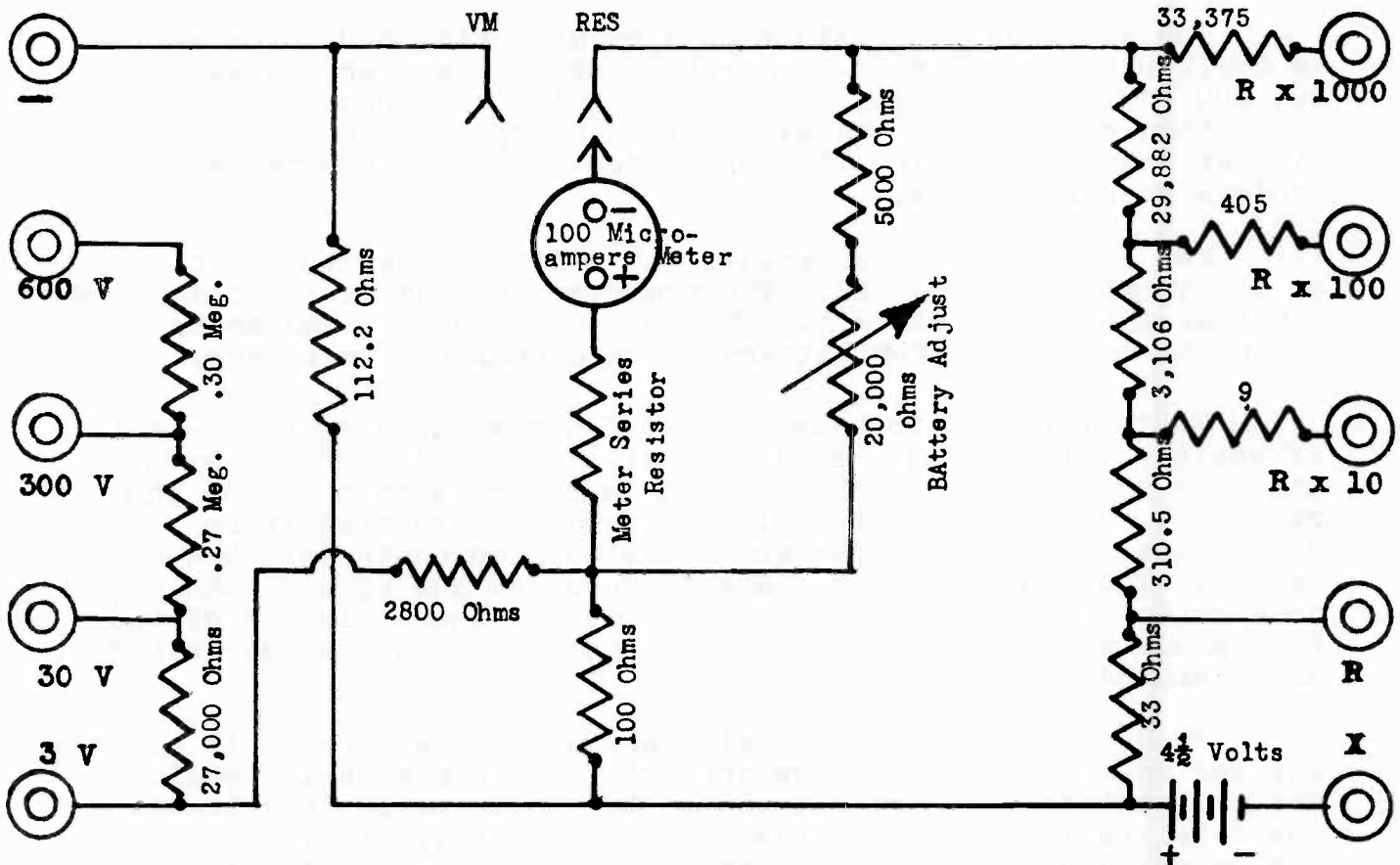A sensitive D.C. meter may be used with a thermocouple to measure alternating currents up to R.F. The current to be measured heats a small wire which is placed near a junction of two different metals. When a point of contact of two different metals is heated, a slight D.C. voltage is produced.



Because the Supreme Instruments Corp. Model 537 volt-ohmmeter uses an easy to trace circuit, we will introduce it first. The meter used is of 100 micro-ampere movement and for voltage measurements is switched to the left terminal marked VM. For all voltage measurements, the negative prod is inserted in the upper left hand terminal marked "-" minus. Let us consider the circuit when it is being used for measuring 300 volts maximum and the positive prod is connected to the jack marked 300 V. With this application, the .30 meg. resistor is not functioning, while the resistors marked .27 meg., 27,000 ohms, 2,800 ohms, "Meter Series Resistor," and the meter itself are connected in series to the prods. The meter series resistor is of a value to match the meter and give a total of 2,000 ohms. The resistors marked 100 ohms and 112.2 ohms (themselves connected in series) are in parallel with this meter circuit total resistance of 2,000 ohms. The equivalent resistance to this combination (using parallel resistance formula) is 175 ohms. The equivalent sensitivity for voltage measurements is in the order of one milliamperes — if you want the exact figure it is 1.043 milliamperes.

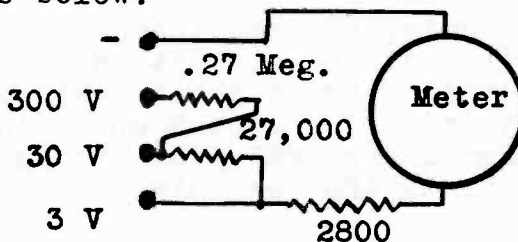A simplified equivalent circuit of what we are analyzing appears below:



The meter is considered as incorporating the associated resistors and acts as the equivalent resistor of 175Ω.

The total series resistance when measuring 300 volts maximum is 299,975 ohms, but with permissible errors may vary between 294,000 and 306,000 ohms, so that 300 volts will produce full scale deflection well within the over all accuracy of 3% to 5%. In a similar manner, the circuits formed for other voltage ranges produce proper results.

For resistance measurements the switch is set to the right, to the terminal marked RES. The ohmmeter section uses a ring-type parallel adjustment circuit. The 20,000 ohm potentiometer is needed to compensate for battery voltage variation with age.

To test for resistance values of a few hundred ohms, middle of scale about 35 ohms, use jacks marked "R" and "X." Observe that the $4\frac{1}{2}$ volts of the battery is impressed across the 33 ohm resistor. The total voltage if the prods are shorted (zero resistance), smaller values as the resistance under test becomes larger. The other resistors are of value to add up with the meter network to produce full scale deflection on short circuit of the test prods and corresponding correct reading when various resistors are measured.


When other resistance scales are used, the circuit is altered, but the re-arrangement is now correct for the new scale reading. The change introduces an alteration in the meter series circuit and the total resistance in series with the battery. If you calculate the meter current for each of the setting, you will find it can be made 100 micro-amperes for zero ohm testing on any scale and other correct values for other test considerations. The slight variations are compensated with the Battery Adjustment which alters the meter equivalent sensitivity and always has a minor effect on the total series resistance. The adjustment mentioned must be used to set zero ohms each time a new scale is used for measurements. The advantage of an ohmmeter circuit of this type lies in its adaptability in providing a single scale for several ranges.

The circuit of another multimeter is shown on the next page. This circuit is similar in some respects to the diagram just discussed, but there are several important differences.

Analyzers were popular some years ago and were intended primarily to save time in permitting the serviceman to test and discover the possible fault in a defective receiver without actually removing the chassis from the cabinet. In majority of cases, in order to make the repair, the chassis had to be removed anyway, this instrument is no longer popular and majority of servicemen make the needed tests by making contact with prods of a simpler multi-tester directly to the points in the radio chassis.

In order to use test instruments, the serviceman must have a clear notion concerning the function of the circuit he is testing and some knowledge as to the expected correct electrical values. Voltage values can be obtained by referring to the operating conditions for the different vacuum tubes employed. Resistance values can be estimated for some parts (for example, paper

condensers will show infinite resistance, coils 5 to 100 ohms) and, in the case of resistors, compared with actual markings as given. If the set is "dead," resistance tests are recommended. These usually will point to the place where the circuit is broken and prevents operation. If a radio which is being repaired has voltages at some points, the test for voltage at other points may lead to the fault which is preventing proper operation.

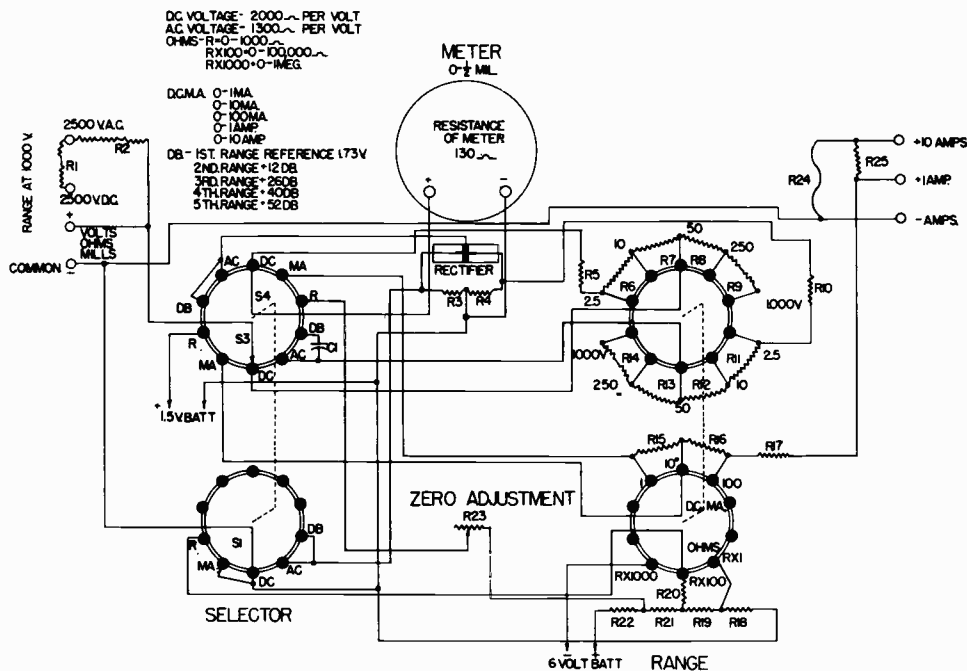


Symbol	Description
R1, R14	1 megohm, 1 watt, ±2%
R2	2 megohms, 3 watts, ±2%
R3, R4	2000 ohms, ½ watt, ±2%
R5	5000 ohms, ½ watt, ±2%
R6	15,000 ohms, ½ watt, ±2%
R7	80,000 ohms, ½ watt, ±2%
R8	400,000 ohms, ½ watt, ±2%
R9	1.5 megohm, 1 watt, ±2%
R10	1000 ohms, ½ watt, ±2%
R11	10,000 ohms, ½ watt, ±2%
R12	53,000 ohms, ½ watt, ±2%
R13	265,000 ohms, ½ watt, ±2%
R15	117 ohms, ½ watt, ±2%
R16	11.7 ohms, ½ watt, wirewound, ±2%
R17	1.17 ohms, ½ watt, wirewound, ±2%
R18	11 ohms, ½ watt, wirewound, ±2%
R19	1134 ohms, ½ watt, ±2%
R20	431 ohms, ½ watt, ±2%
R21	1137 ohms, ½ watt, ±2%
R22	10860 ohms, ½ watt, ±2%
R23	2000 ohms
R24	.013 ohm, wirewound, ±2%
R25	.117 ohm, wirewound, ±2%
C1	.5 mfd, 600 volts

Unimeter, type UM-3, is a portable unit designed for simplicity, attractive appearance and rugged construction, for the rapid and accurate measurement of volts, ohms, current and decibels as encountered in the repair of electronic equipment.

For operation in the normal ranges the test prods are plugged in the + and - jacks. Red test lead to +, black test lead to -. The most used ranges are changed by two selector switches. The left or SCALE switch selects the type of measurement desired. The right or RANGE switch selects the range of the desired type of measurement.

The SCALE and RANGE switch settings *must* not be changed while the test prods are in contact with the external circuit. This is particularly important in AC and Db. (Output) measurements and on DC above 100 volts. Rotating the range switch may cause transient voltages to be set up that are capable of ruining the rectifier, even though the duration of the voltage peak is so short that it doesn't show on the meter. *Never* change switch settings with 1000 or 2500 volts AC or DC applied to the test prods.

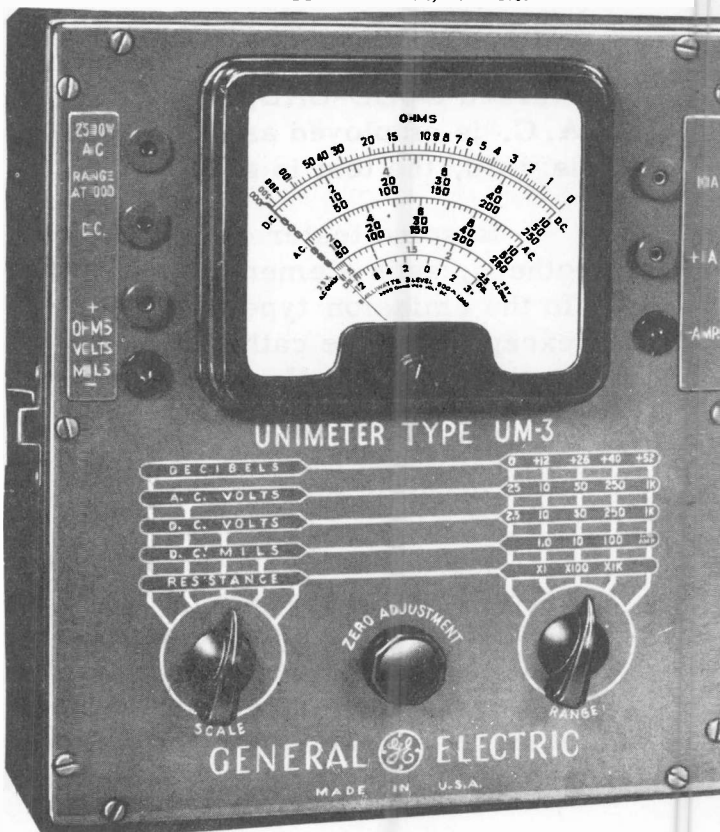A .5 mf 600 V capacitor is switched in series with the test leads for output measurements when the SCALE switch is set to decibels.



Although faults in vacuum tubes can be detected without the aid of a tube tester, to make a positive statement that a vacuum tube is in good operating condition requires the use of a good tube tester. Testing and replacing tubes constitutes a large amount of work of radio servicemen. A very large number of apparent radio receiver defects do not actually require any repairs, but merely a replacement of one or two tubes. The more accurate and the more sensitive a tube tester is, the better it will test the tubes and there will not be any chance of a tube in bad condition getting into the set to spoil the operation.

Occasionally when a tube tests defective, it will work quite well in the receiver tuned to a powerful local station. It is a rather difficult matter to convince the owner that this tube needs replacing when he can hear the receiver apparently working fine.

To convince the receiver owner that the tube in question is really defective, simply place a new tube in place of the one not testing GOOD. Tune in a rather weak distant station. Now replacing the BAD tube in the set will probably stop the reception of the weak station completely.

Different test methods are used by the various tube manufacturers. Tube checkers and testers are usually A.C. operated and employ four to as many as twenty-five sockets. The grid shift method is commonly used in the testers. The grid voltage is altered a small amount which in turn causes a corresponding change in the plate current. This change in the plate voltage is the index by which we judge the condition of the tube and this current is indicated on the meter. The tube tester meter is usually marked GOOD-BAD, so that the public can understand the results. If A.C. is employed as the grid voltage, the test is called dynamic. If D.C. is used, the test is static.

In some testers the majority of the elements are tied together; in others, each element receives a relatively correct potential for the test. In the emission type tester all the elements are tied together with the exception of the cathode and the filament. A positive potential is then applied to the collection of the remaining elements and the current passing is measured. Obviously, if the screen grid prong of a tube is completely missing, the tube may still test GOOD and this is why the grid shift dynamic testers are superior and do detect such faults.


The emission type tester is much simpler and is much cheaper in price than the dynamic type. For practical requirements, the emission test is accurate enough and does serve the purpose. Besides low emission, about the only other common defect that occurs in a tube is a short circuit between some elements. Modern tube testers of all makes incorporate a short test, placing a voltage between the different elements and using a sensitive neon bulb as the indicator.

LESSON 13

Vacuum Tube Voltmeters

As the name implies, a vacuum tube voltmeter uses a radio tube and is primarily an instrument for measuring voltage. This type of instrument falls into several different classes, each using a different basic circuit, but every type providing the main advantage of very high input impedance.

The high input impedance permits the use of the vacuum tube voltmeter for practically all voltage tests in radio equipment without upsetting the voltage values existing at these points previous to the test. For example, the exact voltage at the plate of a resistance coupled tube can be obtained. Or A.V.C. voltages can be measured accurately. If the unit is designed to measure R.F., the oscillator voltage can be measured. And, of course, all normally measurable voltages can also be measured with a vacuum tube voltmeter.

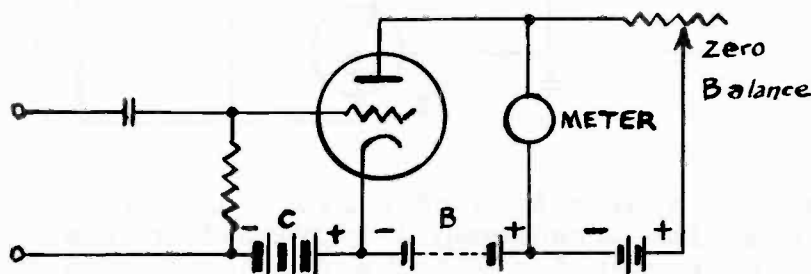


One type of vacuum tube voltmeter (VTVM) employs a vacuum tube (triode or pentode) which is operated over its curved characteristic as a detector. Under such operation, the D.C. plate current will depend on the A.C. voltage applied to the control grid. It is possible, therefore, to calibrate a milliammeter placed in the plate circuit (and which will measure the plate current) in terms of the input grid voltage. The value of plate current present when the input grid voltage is zero, can be balanced out with another, separate battery and a variable resistor circuit also connected to the same meter, but passing current in reverse. A zero adjustment is made with this circuit. A basic circuit of this type is indicated. Batteries are shown for simplicity but the same general circuit can be made to operate from a single power supply.

This type of VTVM is intended primarily for A.C. voltage measurements. It can be calibrated at some practical frequency (60 cycles for example) and will give accurate results even when used to measure R.F.

Many special arrangements are possible to secure advantages such as increased sensitivity, stability against changes due to tube's age or voltage variations, or to obtain response in a logarithmic ratio, but these circuits are not of especial interest to a radio serviceman. We shall discuss vacuum tube electronic multimeters which are special kinds of vacuum tube voltmeters designed to provide measurements of voltage, current, and resistance values commonly encountered in radio repair work.

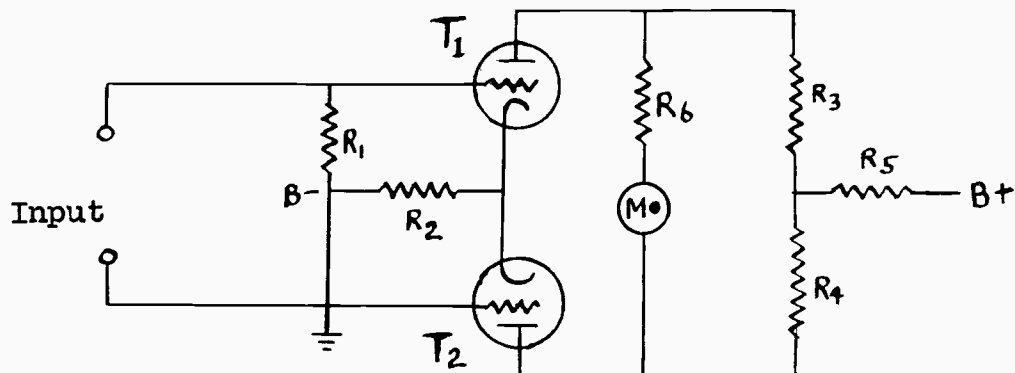Almost all electronic type volt-ohmmeters designed for use by radio servicemen employ a balanced vacuum tube circuit designed to measure D. C. voltages. The basic vacuum tube circuit employed is illustrated below. Here two similar triodes are employed in what, at first, appears to be a peculiar arrangement.



Consider the application of a D.C. voltage (of value permitted by the bias arrangement) impressed on the input terminals. For simplicity of explanation, let us further assume that the positive prod is connected to the upper terminal. This voltage will be impressed across the grid resistor R_1 of vacuum tube T_1 . The grid of this tube will become positive by the amount of this voltage. Notice that the grid of T_2 remains at ground potential at all times.

For the moment, let us return to the time just before any voltage is impressed on the input. Since there is no grid current (tubes biased negatively), each grid is essentially at ground potential — resistor R_1 simply completes the circuit to ground. The steady state plate (or cathode) current passes through R_2 and produces a voltage drop here. This voltage makes the control grids of both tubes negative with respect to the corresponding cathodes, as is required. If identical tubes are selected, the operating condition described, plus the exact similarity of plate resistors R_3 and R_4 , guarantees equal plate currents in each tube. If equal plate currents pass through equal plate resistors R_3 and R_4 , the voltage drop across each of these two resistors will be equal. These equal drops will subtract from the power supply voltage, $B+$, and the voltage present at the plate of each tube

used will be equal. Perhaps this value will be 80 volts in a practical circuit. If a sensitive meter M is connected to these points, as shown in the diagram, under the open input-terminal conditions described, no current will be present in the meter circuit. A difference of voltage, you understand, must exist to pass current through the meter.

After you clearly understand the conditions existing with no input voltage, we can proceed to consider the effects of the input voltage we mentioned before. This "positive" voltage will make the grid of T_1 less negative than it was before. This tube T_1 will pass greater current. A larger drop will occur across the plate resistor R_3 , leaving a smaller voltage at the plate of this tube — perhaps only 78 volts.

This is not all that happens. The plate current passes through the cathode resistor R_2 , and since the plate current is larger, the voltage drop across it will also be larger. This action will have a degenerative effect on the input voltage since it will produce an additional small negative bias which to a degree will nullify the application of positive input voltage to the grid of T_1 .


Also, with this increase in the cathode resistor voltage, the grid bias for T_2 will become more negative and, thereby reduce its plate current. This action in turn will have a further degenerative effect (reducing) on the amount of change produced in the voltage across the cathode resistor. Reduction in plate current of T_2 will also cause a smaller drop in the plate resistor R_4 , increasing the voltage at the plate of T_2 , perhaps to $81\frac{1}{2}$ volts. We now have a voltage difference across the meter circuit and it will indicate some new value. Resistor R_6 is used to limit the current through the meter and the meter is calibrated in terms of the input voltage.

The meter reads zero initially and is connected with proper polarity to correspond to the polarity use of the input. In some testers of this type, the meter has a center zero, and no polarity of the test prods need be observed. In other units the terminals of the meter can be reversed with a switch so that either polarity of the test prods may be used provided the corresponding setting of the switch is made.

The effect of each portion of the circuit on others was mentioned as if final conditions were affected but once, actually these actions are inter-related and cause results in a multitude of ways. Although the complete analysis of the action is difficult, equilibrium is reached instantaneously for each change, and the current through the meter is directly related to the input voltage. The degenerative effects present and the use of a balanced circuit eliminate, to a large degree, the error introduced by supply voltage variations. Observe that a change in plate voltage supply will have but little effect on the operation of the circuit.

GANGED SWITCHES
RANGE SWITCH SECTIONS
 S1A, S1B, S1C, S1D ARE GANGED.
SELECTOR SWITCH SECTIONS
 S2A, S2B, S2C, S2D, S2E, S2F ARE GANGED.

VOLTOHMYST Type No. 195

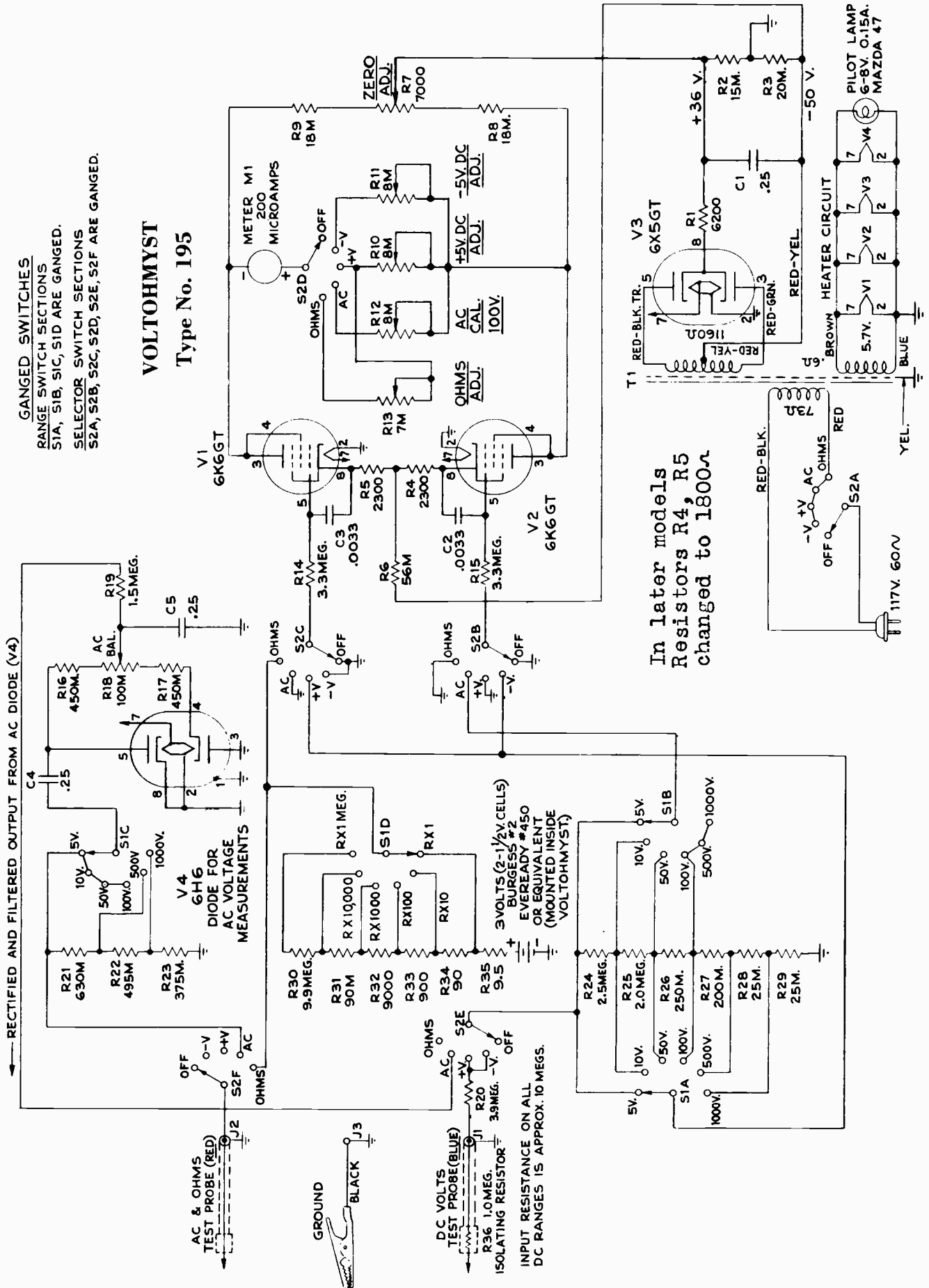

In later models
 Resistors R4, R5
 changed to 1800Ω

RECTIFIED AND FILTERED OUTPUT FROM AC DIODE (V4)

DIODE FOR AC VOLTAGE MEASUREMENTS


3 VOLTS (2-1/2V CELLS) EVEREADY #450 OR EQUIVALENT (MOUNTED INSIDE VOLTOHMYST)

INPUT RESISTANCE ON ALL DC RANGES IS APPROX. 10 MEGS.

AC & OHMS TEST PROBE (RED)

GROUND BLACK J3

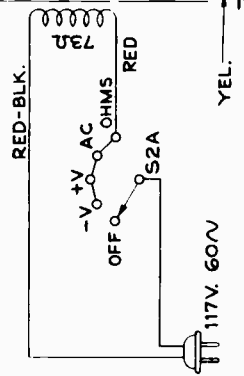DC VOLTS TEST PROBE (BLUE) ISOLATING RESISTOR R20 3.9 MEG. -V. OFF



In order to use the same circuit for measuring a wide range of voltages, a voltage divider network is incorporated in the input. Resistance measurements are made by introducing the unknown resistor in series with a small dry battery across one of the voltage inputs. Since the voltage impressed on the input circuit will depend upon the resistor value under test, additional scales can be provided to indicate the value of resistors to be tested.

To measure alternating voltage a rectifier must be provided. This may be in the form of a copper-oxide unit with correspondingly reduced sensitivity. In fact, if a copper-oxide unit is used, it is usually used directly with the meter (without the tube circuit) for A.C. measurements. In the majority of commercial instruments, a diode tube is incorporated in a special probe and serves as the rectifier. The use of a diode permits voltage measurements at high radio frequencies and preserves the advantage of high impedance input.


We will now discuss several popular commercial units which will help us to understand and apply the basic theory presented.

An instrument using the basic circuit we just studied is employed in the R.C.A. VoltOhmyst. We illustrate this circuit and will call your attention to a few special features.

As you will observe, this instrument uses a D.C. electronic vacuum tube voltmeter circuit which is characterized by excellent linearity and stability. Two type 6K6-GT tubes are linked by means of a common high resistance (R_6) and because of this coupling any change in the input voltage to the grid of one tube changes the cathode bias of the other and, as a result, the change in the plate current of one is accompanied by a simultaneous opposite change in the plate current of the other. The differential voltage this action develops across the load resistors R_8 and R_9 is applied to the meter which is calibrated in terms of the voltage applied to the grid, and in terms of resistance when the instrument is being used as an ohmmeter.

The provision of individual balance adjustments permits the switching from range to range without the need for resetting in each instance. The zero adjustment controlled by the potentiometer R_7 is employed for the initial zero setting of the meter and need be only adjusted once each time the instrument is used, unless, of course, there is considerable voltage variations.

The switching circuits at the left of the diagram employ resistance networks to provide the ranges obtainable from this instrument. Please note that the resistors in the bottom group are intended for use with D.C. ranges. The middle set of resistors is used with a small battery for resistance (ohmmeter) measurements. The circuit in the upper left hand section provides a voltage divider network to give various ranges and this circuit is

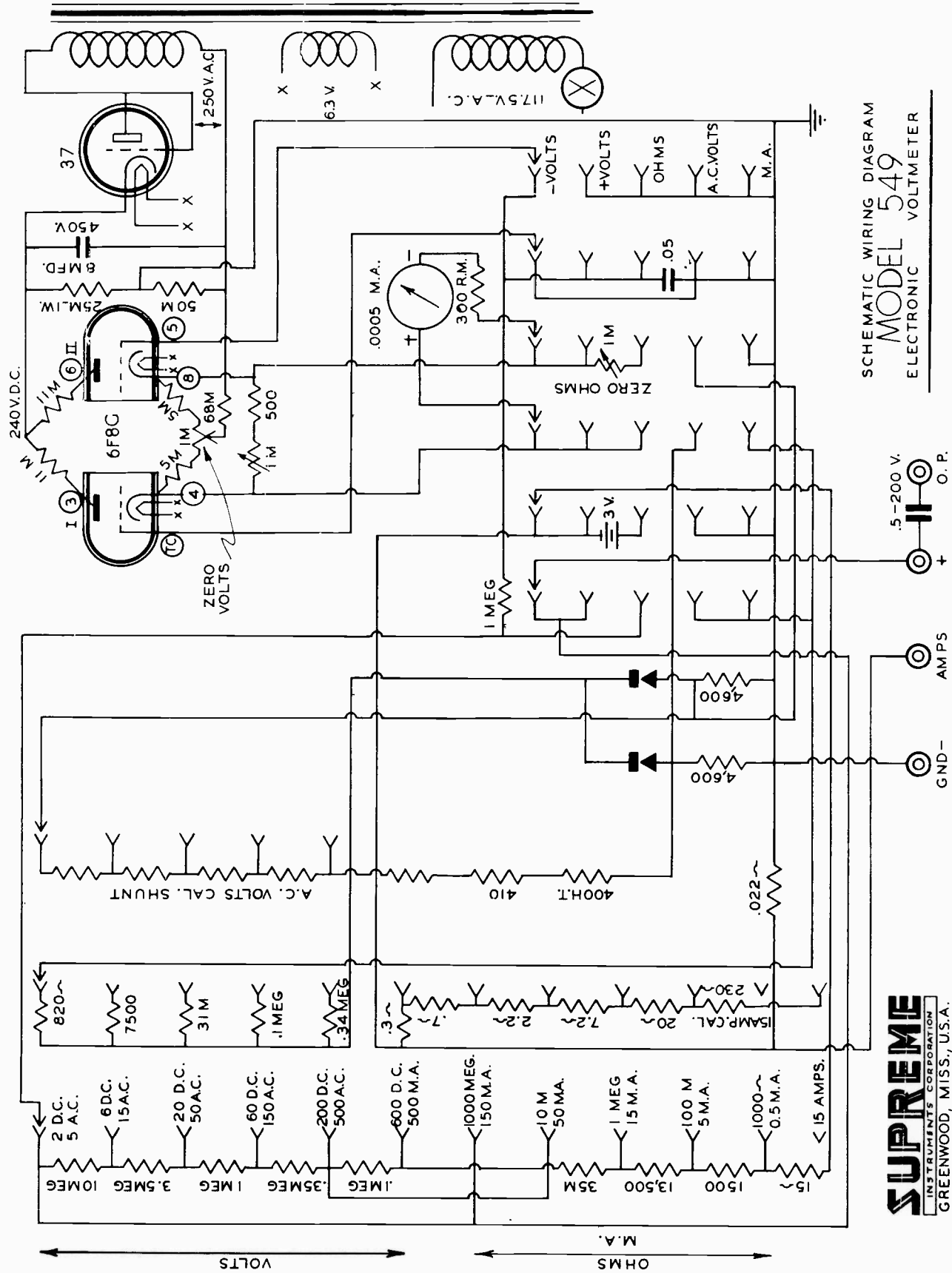

SCHEMATIC WIRING DIAGRAM
MODEL 549
 ELECTRONIC VOLTMETER

SUPREME
 INSTRUMENTS CORPORATION
 GREENWOOD, MISS., U.S.A.

NOTE: RESISTORS NOT OTHERWISE SHOWN ARE 1/2 WATT.

used for A.C. power and audio frequency measurements. The diode 6H6 tube rectifies the alternating voltage input and places the resulting rectified voltage upon the same basic VTVM circuit which, as you recall, is intended for measuring D.C. only.



Another electronic multimeter is the Supreme Instrument Corp. Model 549. In this unit, the meter used for measuring the voltage differences in the two tube balanced circuit is placed across the cathodes. This action, however, is essentially the same as in the basic circuit we have described.

You will note in studying this circuit that it is similar and the primary singular exception is the use of copper-oxide rectifiers for A.C. measurement. For these measurements, the meter is connected directly to the voltage divider network marked A.C. VOLTS CAL. SHUNT. The electronic network is not used for these measurements. The switch elements at the right bottom of the circuit are moved in tandem "up and down" to make connections for various applications of the unit.

Sylvania Electric offers to servicemen an instrument called a Polymeter which uses an electronic VTVM basic circuit of the type we discussed. A simplified circuit of this unit is shown on page 124, and you will observe certain important differences. The diode included is intended for A.C. measurements and can be used with a good degree of accuracy up to frequencies of 300 MC. This makes this instrument of value in television servicing as well. The curve on the next page indicates the accuracy obtainable at various frequencies. The D.C. voltage obtained from the diode is impressed on a balanced electronic circuit of the type we have described. The voltage differential resulting in this instance, however, is not impressed on the meter, but instead is applied to another dual function tube in a very similar circuit. A much greater voltage differential is obtained from this second set of triodes and is in turn impressed upon the meter used.

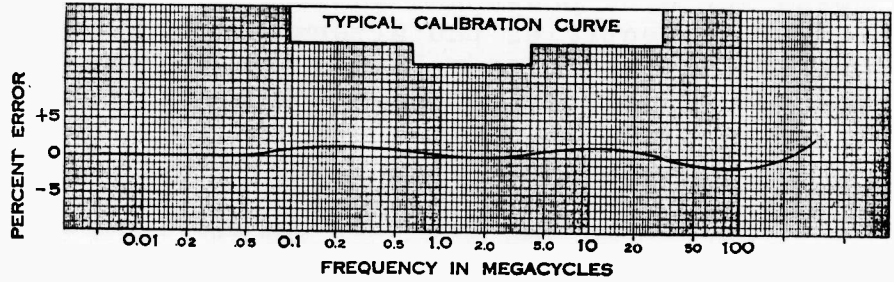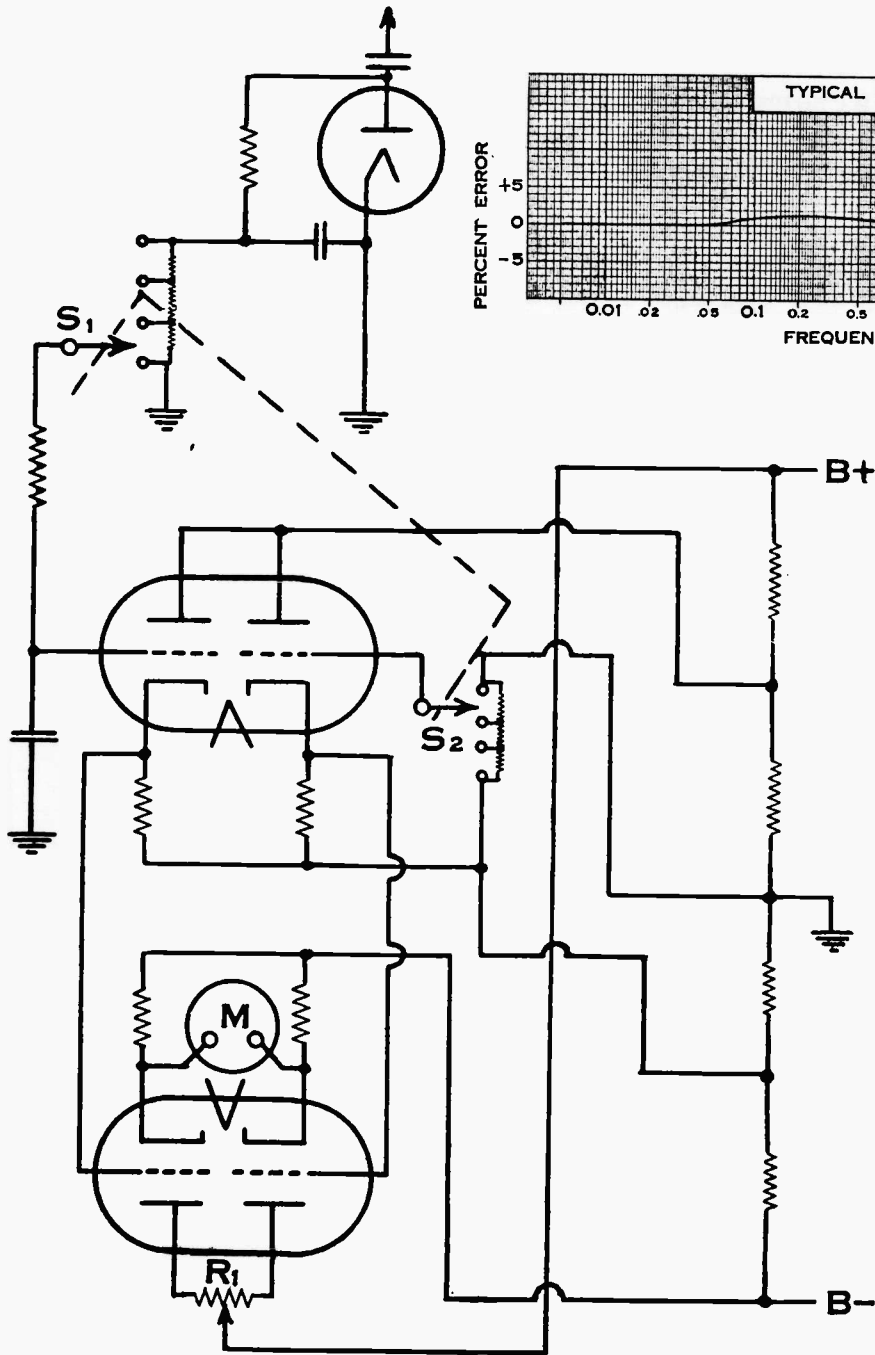The ohmmeter circuit is formed from the basic voltage input circuit with the aid of a small battery which is used to supply a voltage to the unknown resistor and the associated network. The meter reading will show the value of the unknown resistance since its scale is calibrated with consideration to the fixed network and voltage supplied by the battery.





Table

D. C. Voltages	Ohms per volt	Accuracy
0-3	5,333,333	± 3% of full scale
0-10	1,600,000	
0-30	533,333	
0-100	160,000	
0-300	53,333	
0-1000	16,000	
A. C. Voltages: Audio (capacity 40 uuf.)		
0-3	900,000	± 5% of full scale
0-10	270,000	
0-30	90,000	± 7% of full scale
0-100	27,000	
0-300	9,000	
(at frequencies up to 300 mc with probe capacity of 3 uuf.)		
A. C. Voltages: R.F. 300 mc with probe capacity of 3 uuf.)		
0-3	900,000	± 5% of full scale
0-10	270,000	± 7% of full scale
0-30	90,000	
0-100	27,000	± 10% of full scale
0-300	9,000	
Current		
0-10 amps	.015 ohms	± 5% of full scale
0-1000 ma	.150 ohms	
0-300 ma	.50 ohms	± 3% of full scale
0-100 ma	1.5 ohms	
0-30 ma	5.0 ohms	
0-10 ma	15.0 ohms	
0-3 ma	50.0 ohms	
Resistance		
0-1000 ohms	300 ma @ 0 ohms	± 6% on first half of scale
0-10,000 ohms	30 ma @ 0 ohms	
0-100,000 ohms	3 ma @ 0 ohms	
0-1 Meg.	0.3 ma @ 0 ohms	
0-10 Meg.	30 ua @ 0 ohms	
0-1000 Meg.	0.3 ua @ 0 ohms	

NOTE—RF accuracy from 100 to 300 mc is 5% greater than the above figures.

FUNDAMENTAL PROBE CIRCUIT


A table indicating the scales available, the sensitivity obtainable, and the accuracy expected, is included to give you an idea of the results that are possible with instruments of this type.

After this preliminary study, you can refer to the general circuit. Here you will note the addition of various voltage divider networks to give the needed ranges and the switching method for changing the circuit for the measurement and range wanted. Current readings are taken directly on the meter with suitable shunt resistances, but, for this purpose, the electronic

section of the unit is not employed. As you realize, the R.F. probe is employed for all A.C. measurements. Since it is not practical to design a single probe circuit to serve for high radio frequencies and at the same time measure power frequencies without error, this unit is not adaptable for A.C. frequencies below the audio spectrum.

The input impedance of 16 megohms for D.C. measurements was selected as the best compromise between the erratic behavior which may be caused through the use of a much higher value and the too low an impedance giving poor sensitivity as used in some of the earlier models of vacuum tube voltmeters. Notice that in the table the ohms-per-volt sensitivity varies with the scale used. This is not the case with some other instruments of this nature, but is of little consequence in radio service work.

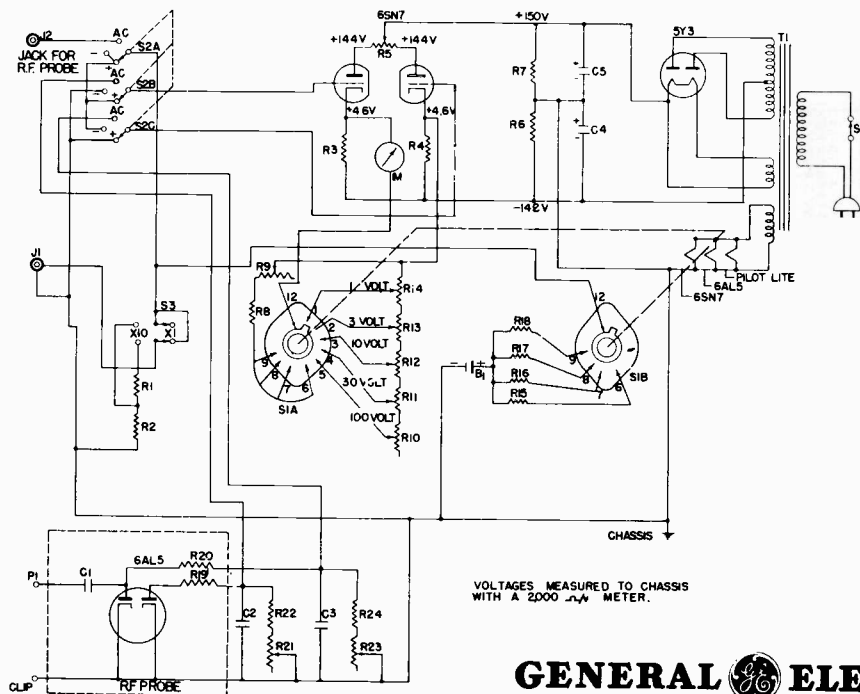The General Electric electronic volt-ohmmeter type PM-17 circuit and parts list are next presented for your study.



GENERAL ELECTRIC

A 6AL5 tube mounted in a probe is used for audio and radio frequency voltage measurements from 200 cycles to beyond 100 megacycles. Response drops below 200 cycles to a value of 5% low at 60 cycles. In audio frequency measurements the probe can be mounted in the top of the case and the test leads from the panel used instead. An ohmmeter circuit is included for convenience in measuring high and low ohmic values of resistance.

SPECIFICATIONS

D-C VOLTS: $\times 1$ range—0-1, 3, 10, 30, 100 volts. Input impedance from 30 to above 200 megohms. $\times 10$ range—0-10, 30, 100, 300, 1000 volts. Input impedance constant at 10 megohms. Input capacity on both $\times 1$ and $\times 10$ ranges 2 mmf.

A-C VOLTS: 0-1, 3, 10, 30, 100 volts. Input capacity, using test leads, approximately 100 mmf. Usable at audio and low radio frequencies. Response drops below 200 cycles to a value of 5% low at 60 cycles.

R-F VOLTS: 0-1, 3, 10, 30, 100 volts. (Same as a-c scale.) R-f measurements made using the r-f probe. Input capacity using the r-f probe is 6.6 mmf at 70 megacycles.

OHMS: $R \times 1$, $\times 100$, $\times 10K$, $\times 100K$ (K = 1000). Basic scale .2 to 1000 ohms, 10 ohms center scale. Applied voltage, all ranges, 1.5 volts.

POWER SUPPLY: 105-120 volts, 60 cycles, 30 watts input.

ACCESSORIES: (Supplied) Two alligator clips. Two pairs of leads and an r-f probe.

CASE: Steel, 8½" by 8" by 8". Sloping panel of aluminum. Instrument accessible as a unit by removing panel screws.

WEIGHT: 15 pounds.

LIST OF ELECTRICAL COMPONENTS

Symbol	Description	Rating	Tolerance
B1	No. 2 Flashlight battery	1.5 volt	
C1	Capacitor	.01 mfd	
C2	Capacitor, paper	.05 mfd, 400 volt	
C3	Capacitor, paper	.05 mfd, 400 volt	
C4	Capacitor, electrolytic	8 mfd, 250 volt	
C5	Capacitor, electrolytic	8 mfd, 250 volt	
R1	Resistor, carbon precision	1 w. 8 megohm	2%
R2	Resistor, carbon precision	1 w. 1 megohm	2%
R3	Resistor, carbon	1 w. 51K ohm	5%
R4	Resistor, carbon	1 w. 51K ohm	5%
R5	Potentiometer (zero set)	5K ohm	
R6	Resistor, carbon	1 w. 47K ohm	5%
R7	Resistor, carbon	1 w. 51K ohm	5%
R8	Resistor, carbon	¼ w. 8.2K ohm	10%
R9	Potentiometer (ohms adjust)	5K ohm	
R10	Potentiometer	750K ohm	
R11	Potentiometer	350K ohm	
R12	Potentiometer	50K ohm	
R13	Potentiometer	50K ohm	
R14	Potentiometer	15K ohm	
R15	Resistor, carbon precision	¼ w. 9 ohm	2%
R16	Resistor, carbon precision	½ w. 1K ohm	2%
R17	Resistor, carbon precision	¼ w. 100K ohm	2%
R18	Resistor, carbon precision	¼ w. 1 megohm	2%
R19	Resistor, carbon	¼ w. 3.3 megohm	5%
R20	Resistor, carbon	¼ w. 3.3 megohm	5%
R21	Potentiometer (AC zero)	10 megohm	
R22	Resistor, carbon	½ w. 6.8 megohm	10%
R23	Potentiometer	10 megohm	
R24	Resistor, carbon	½ w. 6.8 megohm	10%
R25	Resistor, carbon precision (in DC test prod)	1 megohm	2%
M	Meter	100 microammeter	2% accuracy
T1	Power transformer		

Due to the self-balancing type of circuit and the high degree of degeneration, fluctuations in line voltage and changing of tubes has little or no effect on calibrations.

In all AC-DC volts and ohms measurements, the test leads are plugged in the jack on the front panel. The 6AL5 probe is used for R.F. measurements. All functions of the instrument are obtained through the use of two selector switches. The polarity switch controls the polarity of the test prods and also switches the instrument to the ohms and A.C. circuits. The range switch selects the range of the desired measurement.

Other controls are: a zero adjustment knob to set the instrument pointer to zero, an ohms adjustment knob to set the instrument pointer to full scale on the ohms ranges, a toggle switch which acts as a power switch.

The toggle switch in the lower right corner of the panel controls the 10 to 1 voltage divider which is switched across the input to secure the higher ranges of D.C. volts. This voltage divider also provides a convenient means of securing a grid return when D.C. loading of this instrument is obtained by using an open grid input on D.C. volts X1. The grid return is through the circuit being measured.

Voltage measurements made between two points, both above ground potential, should be made using the following procedure. Measure each point separately to ground, then subtract to find the difference in potentials. This method of measuring causes no appreciable disturbance in the circuit being measured. If the negative lead, which is grounded to the instrument case, were connected to a point above ground, inaccurate readings would result due to the A.C. loading effect of the chassis and the test leads. There is also the possibility of shorting to ground.

The automatic volume control voltage developed in a receiver by the incoming signal can be measured at a number of places. Most common places are the grids of the IF amplifier tubes and the signal grid of the converter tube. This D.C. voltage, if measured anywhere along the grid return circuit on the AVC line, is a convenient output indication during receiver alignment. Resonance will produce the highest negative voltage. Polarity will be negative with respect to ground.

The D.C. voltage developed by the oscillator is always directly proportional to the strength of the oscillation. This D.C. voltage can be measured readily at the oscillator grid of the converter tube. Polarity will be negative with respect to ground.

All voltages encountered in radio service work, of course, can be measured with electronic voltmeters. Even bias cell voltage can be measured — a thing which cannot be accomplished with an ordinary voltmeter.

The discriminator voltage developed in radio receivers employing automatic frequency control can be measured directly at the discriminator and also at the grid of the oscillator control tube.

By switching to the regular D.C. voltage ranges and connecting to the limiter grid circuit, a useful means of indicating proper antenna orientation and position as well as adjusting antenna matching sections may be found. Maximum readings indicate proper antenna positions and correct matching.

The instrument is useful for measuring the D.C. voltage developed in the picture channel of a television receiver across the second detector picture load resistor. This measurement is most useful when adjusting antenna orientation and position as well as when adjusting antenna matching sections. Maximum readings indicate proper antenna position and correct matching.

The effect of a gassy tube is to put a positive charge on its control grid instead of the negative charge or no charge at all that would normally be found between grid and ground. A gassy tube will cause the entire AVC system to run positive, resulting in loss of sensitivity. You can measure the voltage directly at the control grid of the tube to determine the polarity of the charge.

The R.F. probe is useful in tracing an R.F. signal from the antenna through to the diode detector plate. After rectification by the diode tube, only the audio frequency component of the signal is left, but the R.F. probe can still be used to trace the signal through to the loud speaker. Gains or losses between stages can readily be measured.

As an example of what might be expected in the R.F. portion of a small AC-DC receiver, the following figures are given. With 100,000 microvolts of R.F. fed to the receiver through a standard I.R.E. dummy antenna, AVC voltage on the control grid of the 12SA7 tube was 5.8 volts D.C. R.F. appeared on the various tubes as follows:


12SA7 converter grid	.13 volts R.F.
12SA7 converter plate	.7 volts R.F.
12SK7 IF grid	.2 volts R.F.
12SK7 IF plate	6.4 volts R.F.
12SQ7 diode plate	3.6 volts R.F.

These figures will, of course, vary with different receivers and circuits, but in general, a minimum of 3 volts should always be found at the diode plate of the second detector.

With the aid of an R.F. signal generator, such as the General Electric SG-3A, the relative merit of similar IF., R.F. and ANT. coils and wave traps, or the frequencies to which they will tune can easily be determined.

The PM-17 electronic VTVM is set up to measure R.F. voltage and is connected to the signal generator and coil as shown in the circuit. The circuit is drawn showing an IF. coil "T." R.F. and ANT. coils are connected in the same manner.

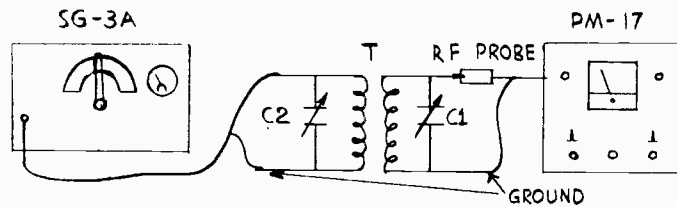
If the frequency of the coil is known, the signal generator is set on that frequency and adjusted to give an output of from 1 to 2 volts. Adjust trimmer C_1 on the coil to give the highest reading on the meter of VTVM. This reading should be noted.



Trimmer C_2 will have little or no effect on the frequency, so it can be disregarded. By connecting another similar coil in place of "T," and keeping the signal generator settings the same and peaking C_1 on the second coil, the relative merits of the two coils can be determined and the better one selected. The coil with the best "Q" produces the highest reading on the meter.

If the frequencies of the coils are unknown, connect the apparatus as before and tune the signal generator until the highest reading is obtained on the meter. The frequency can then be read on the scale of the signal generator.

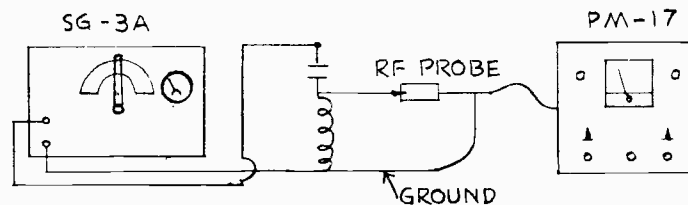The frequency or relative merit of wave traps can be determined by connecting it as shown in the circuit below and tuning the signal generator until the highest reading is obtained. The frequency of the wave trap can then be read directly on the scale of the signal generator.



By adjusting the trimmers on various coils and wave traps from minimum to maximum capacity and readjusting the signal generator to obtain the highest reading, the frequency range to which the coils can be tuned can easily be determined.

REVIEW QUESTIONS

1. What are some of the advantages of a vacuum tube voltmeter over the conventional type?
2. Why is the sensitivity of a VTVM much greater than the sensitivity of the meter employed?
3. How is it possible to measure resistance with the basis circuit used for VTVM?
4. What additional circuit parts are needed to measure radio frequencies with an ordinary VTVM?

LESSON 14

POINT-TO-POINT SERVICING

While the presence of correct voltage values at all points cannot guarantee the proper operation of the radio under examination, a wide discrepancy of even a single voltage value may suggest the cause of the existing fault. This is true in equipment which has been properly operating up to the time of the failure, and a singular fault may be rightly expected to be the cause of the trouble.

When a radio set is properly operating, it may be considered to consist of several separate inter-connected stages, each stage operating in a correct fashion. For a stage to give expected operation, certain voltage values must exist at various points. Many faults commonly causing radio failure also have a pronounced effect upon voltages present at associated junction points. The existence of these facts permits the successful application of voltage point-to-point servicing technique.

Power line frequency A.C. voltages may need checking (measurement) in the power supply input and at filament terminals — the only places where these voltages exist in most A.C. operated sets. Measurements from $2\frac{1}{2}$ to 450 volts may be needed. Radio frequency measurements are helpful in determining the degree of oscillation in a superhet, the signal strength, the stage gain, and the power output.

The preference of voltage point-to-point servicing over other methods depends on many factors which in turn depend on equipment available, fault suspected after a preliminary examination, and your personal choice. Further, a change to this servicing method may be made after another technique of radio fault finding did not lead to any conclusive results and suggested voltage point-to-point method as being more adaptable in this instance.

In general, it is best to start voltage tests by determining if correct plate voltage exists at the output of the rectifier. The various types of power supplies are discussed in a later lecture and we will, at this time, only mention at what points this test can be made and what value of voltages can be expected.

The negative prod of your voltmeter (this applies to all types) is in contact with the most negative point — this is usually the chassis. An alligator clip is handy for making this connection to the negative side, and there are clips of this type which hook into regular phone-tips of the test prods.

In some A.C. and automobile sets, the most negative point may not be the chassis. This matter may be checked easily by noting where the center-tap of the high-voltage winding is connected. This center-tap, of course, is the negative point. In the more modern AC-DC radios, the chassis is not connected directly to the negative side of the power supply. In such sets (and also in all other AC-DC types), the negative prod of your voltmeter may be connected to the power switch which is usually on the side of the power line used as the negative side. However, this is not always the case and in some sets the switch is on the positive side. The side of the line in AC-DC sets which leads to the plate of the rectifier tube is positive, so the other side of the line is negative. In battery sets, the negative B battery lead is used as the point for attaching the negative voltmeter prod. If you know that A+ is connected to B-, use A- terminal for this purpose.

The most positive point is at the cathode of the rectifier. In directly heated tubes, the filament serves as the cathode, and one side of the filament is used as the positive point before the filter. In battery sets, B+ of the battery is the point. Test at these points to determine if proper voltage is being delivered by rectifier. Here is a list of typical voltages to be expected:


Old style A.C. sets	300 to 400 volts
Recent A.C. and Auto sets	250 to 325 volts
AC-DC sets (half-wave rectifier)	115 to 135 volts

Now we can go further. Test for voltage after filter and then proceed to each tube testing for voltage at various terminals. Values expected become familiar to you from experience. A tube manual is of great help since it gives ordinary operating voltages under various conditions. Circuit diagrams include data on voltages to be expected at points used for tests.

To be efficient in using the point-to-point voltage tracing technique, you must watch for two limitations of this method and overcome them with collaborating tests or use another test technique. One limitation is wide variation in permissible values. If 200 to 300 volts is correct for a certain point in the circuit and you obtain a reading of 200, is this value to be accepted as correct? Perhaps, the set was designed to give 300 volts at the point considered, but you do not know this fact; you know that 200 to 300 is commonly used.

An answer to this type of problem is found in making further voltage measurements. If the voltage is low, something is causing it to be so, and probably voltages in the associated circuits will be definitely on the low side.

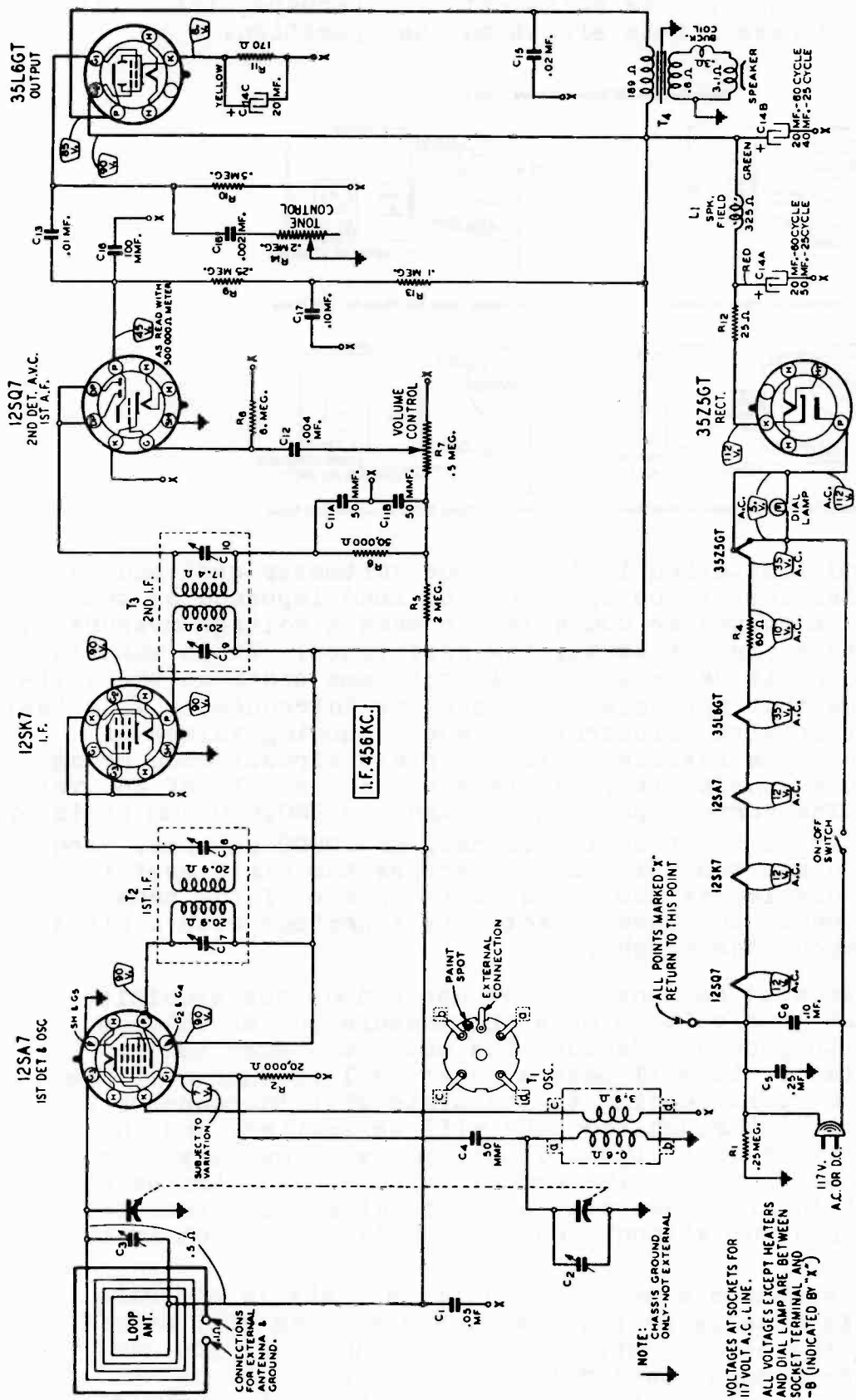
Another way to analyze this question is to ask yourself: "If this voltage really should be 300, but now measures only 200,



Besides voltage values indicated, others can be measured, but it is not probable that they will give any additional aid not offered by the suggested tests. In measuring unknown voltage, a high enough voltage scale should be selected so that no damage results even if the maximum possible voltage is encountered. If the voltage is smaller than expected, a lower scale may be selected for more accurate measurement.

The circuit of Series 5A25-S, Wells-Gardner receiver is illustrated. You will note the helpful voltage values given at various points which can be used as a guide in conducting point-to-point voltage tests. You will observe that these values are measured between the points indicated, and any point marked X. A.C. socket voltages are measured between the terminals, as indicated.

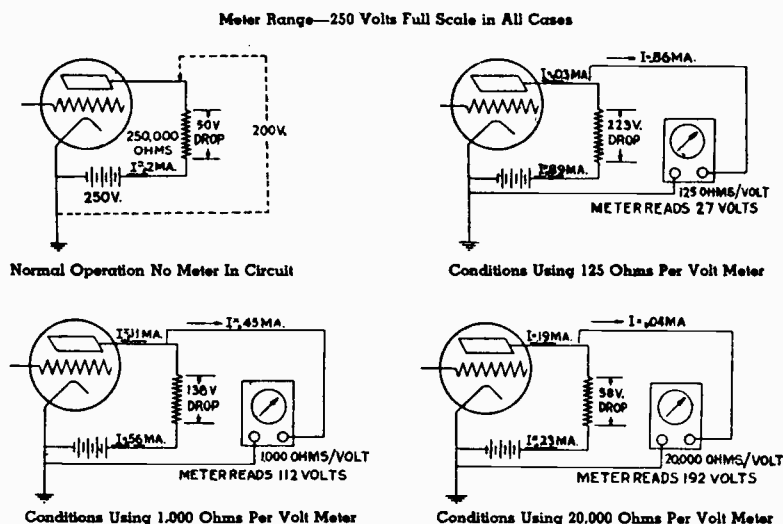would the set show the faults which exist?" Perhaps, this voltage difference should have little effect on the operation.



The second limitation is due to the voltmeter used and causes the circuit under test to be upset by the load imposed by the meter network. A voltmeter connected to make a voltage measurement is always across a circuit containing resistance. It is when the value of this circuit resistance is in the same order as the voltmeter resistance that appreciable errors are introduced. This fact will be made clear with illustrations above showing values of voltage measured in a resistance loaded plate circuit when using meters of various sensitivity. A plate voltage supply of 250 volts is indicated. The current passing through the 250,000 ohm resistor and plate circuit of the tube is 0.2 ma., or .0002 amperes. You can easily calculate the voltage drop across the plate resistor as 50 volts. This leaves 200 volts at the plate of the tube as measured to ground. The tube is actually a pentode with a plate resistance of about one megohm.

Let us see what happens when we use a none too sensitive voltmeter of 125 ohms/volt to make the measurement of voltage from the plate to ground. Because the meter has such low internal resistance, it will pass a great deal of current. The IR drop in the circuit leading to the plate will increase to 223 volts. The current through the tube will be smaller, and the voltage at the plate under these conditions will be only 27 volts. The value will be closer to the actual voltage with more sensitive meters, but in all cases will be somewhat smaller than the value actually present without the meter being connected in the circuit.

You must remember when making voltage tests in circuits where high resistance is present, that the reading will be off. By considering the circuit with the meter connected, you can estimate whether a much lower value obtained with the meter implies that the actual voltage is correct (without the meter being in the circuit), or that a fault exists.

A.C. measurements are made in testing the power supply or the existence of continuous filament circuits. In A.C. sets, voltages of various secondaries may be measured. The primary connections should indicate about 115 volts. In the "on" position, no voltage should be present across the switch; in the "off" position, you will obtain a reading almost equal to the line voltage. Filament voltage readings may be taken at the socket terminals. The voltage values should be as expected, but may be slightly higher with tube(s) out of sockets.


In AC-DC sets, filament voltage will be equal to correct value for tube employed. If the tube is burned out, your voltmeter will complete the series circuit with other tubes and will indicate the line voltage. Under this condition, the voltmeter relatively high resistance is not across any smaller resistance (filament of a tube), and almost the total drop will be across the voltmeter.

The process of translating an incorrect voltage indication to the actual fault which produces it, requires extensive understanding of the function of components included in the circuit. Normally, every component leading to the point under test is suspected and those components which could produce the results indicated by the measurement are individually tested to determine if they are the items at fault. Sometimes voltage tests at other points can be utilized for this additional testing. At other times, the parts in question may have to be tested by other methods or replaced with new components in an effort to locate the actual fault. In general, voltage point-to-point testing is best adaptable when the fault is suspected to lie in those sections of the receiver where D.C. voltage actually exists. The effect of such faults is to produce a "dead" receiver.

Resistance point-to-point testing is especially useful in determining the source of trouble in case voltage is not present in some particular section. This method, however, is adaptable for radio fault finding under other conditions and is a basic technique. The failure of a part or circuit to function properly is accompanied with a pronounced change of some resistance value. Therefore, the finding of a considerable variation from normal in a resistance measurement usually suggests what item is at fault.

To use resistance servicing method successfully, knowledge of expected resistance values for various circuit elements and their combinations is essential. Realization of equivalent resistance values obtained with elements in series and parallel must also be known. These subjects will be discussed.

An ohmmeter is employed for resistance point-to-point testing, and, for safety sake, the power in the radio under test should be shut off (or batteries disconnected) when this testing is conducted. Actually, many tests could be made with an ohmmeter while the radio power is on, but there is always a possibility of making contact across points of voltage difference and thereby damaging the meter.

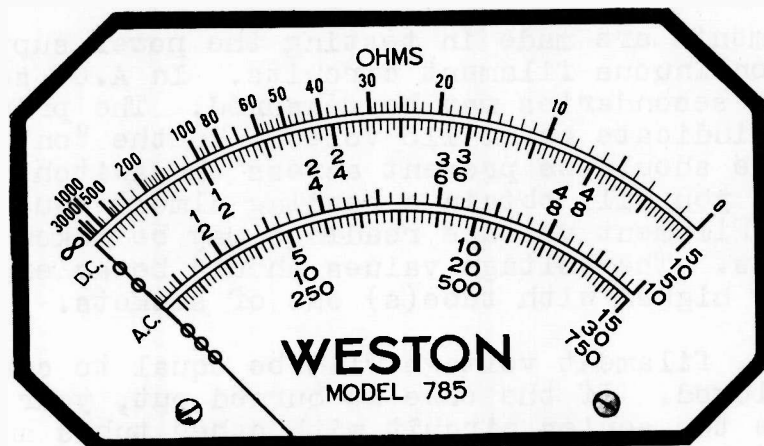FACSIMILE
SCALE

An ohmmeter should provide means for determining values commonly encountered in radio service work. However, the more popular instruments will not measure accurately above $1/2$ megohm, and higher values if present cannot be tested.


Let us review what values of resistance various components used in radio receivers will indicate when tests are made. Resistors, of course, should indicate their correct values within the expected accuracy of about 10%. You should exercise care in making certain that the resistor you are measuring is not actually shunted by others; for in that case, the combination is in parallel and an entirely different value may be obtained. This subject of parallel effects will be discussed in greater detail. If you are not certain concerning possible shunts, disconnecting one side of the resistor to be tested will eliminate this possibility.

A volume control (potentiometer) can be measured from the center tap to each side. The two values so obtained for any one setting should add up to the total resistance of the control. A control may also be tested for proper operation by connecting the ohmmeter to the center tap and one side, and rotating the shaft. The resistance should vary as the control is adjusted.

Paper and mica condensers should indicate infinite resistance implying open circuit for D.C. At times, if you test a condenser in a circuit shortly after shutting off the set, the condenser still may have a charge and will cause the meter needle to move. However, this movement will be of a temporary nature and an open circuit condition should be indicated shortly thereafter.

Variable condensers are usually shunted by coils of small resistance and will require wires to be disconnected if high resistance range of the ohmmeter is to be used for test purposes. If low resistance range is employed, you will be able to tell if the condenser is shorted (zero resistance) or if you are obtaining the value of the resistance of the coil connected in parallel.

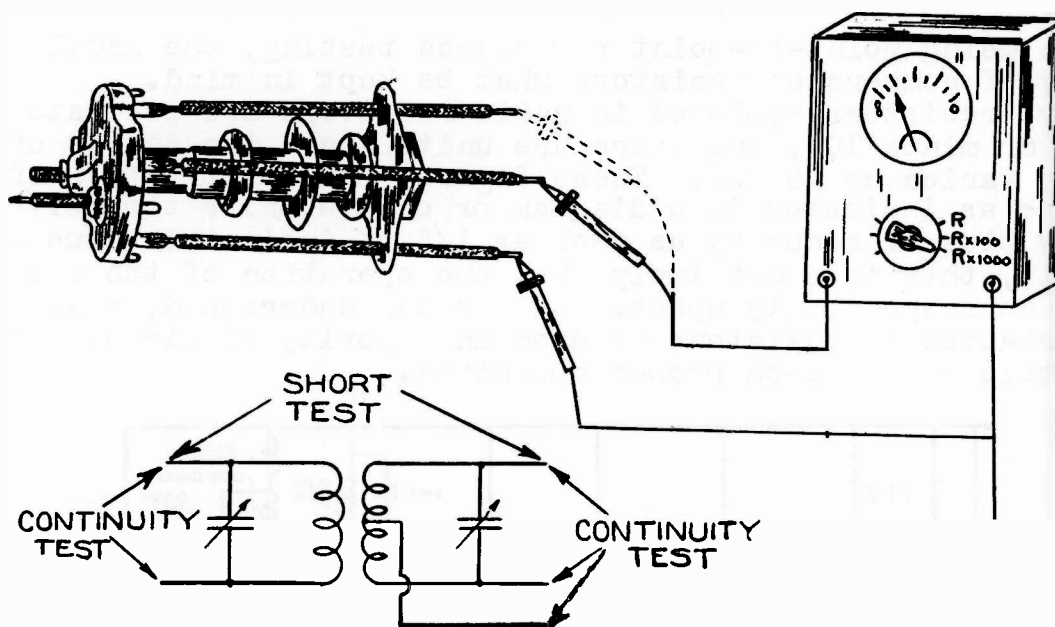Polarity must be observed in testing electrolytic condensers. The probe wired closest to the positive terminal of the ohmmeter




battery should be connected to the positive side of the electrolytic condenser being tested. Usually, upon first being connected, there will be a slight inflection of the meter needle while the condenser is charging, and then very high (almost infinity) resistance will be indicated by a good condenser.

In connection with the measurements of various coil and transformer windings, we are presenting below a table which gives values that may be expected in majority of cases. There are, you understand, exceptions to these values, and the table is given only to serve as a guide.

R.F. Coils, Primaries	10 to 65 ohms
Secondaries	1 to 10 "
Antenna Coils, Primaries	3 to 50 "
Secondaries	1 to 10 "
I.F. Coils, Primaries	20 to 200 ohms
Secondaries	20 to 200 "
Power Transformer, Primary	1 to 15 ohms
H.V. Winding ...	200 to 600 ohms
Filament Winding	Very low
Output Transformers, Primaries	300 to 800 ohms
Secondaries ..	1/5 to 8 ohms

A radio tube in good operating condition will give a value of resistance approximately equal to its filament voltage rating, divided by its current rating. The information to compute this can be obtained from your tube manual. Tests between the different tube elements should indicate open circuit, unless, of course, some of these elements are connected directly with each other or through other parts in the circuit.

In using point-to-point resistance testing, the usual accuracy of commercial resistors must be kept in mind. Normally, resistors employed in radio receivers are accurate to plus or minus 10%, but there are units where the degree of accuracy varies up to 20%. These figures mean that values of resistors as indicated in a diagram or on the units themselves may vary plus or minus by as much as 1/5 of indicated values. Naturally, this does not imply that the operation of the receiver will be correspondingly upset. As you can understand, considerable variation in resistors as used in majority of circuits will have little effect upon proper operation.

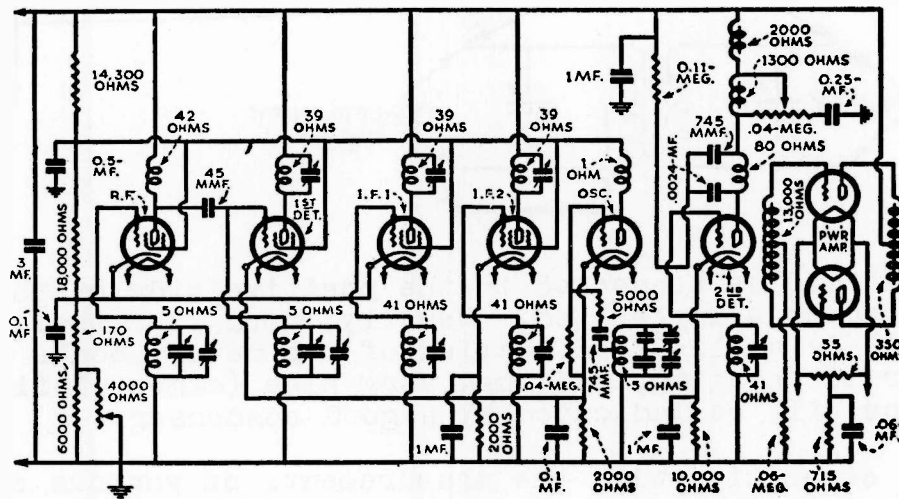

The understanding of these facts, however, is important, since when you are actually measuring resistors, you must realize that variations mentioned are normal and do not indicate possible faults. You must further understand that certain resistors may vary even a greater amount due to other causes, but even a larger variation in some circuits will not influence proper operation. In particular, resistors used in plate, grid, filter, and AVC circuits are not critical.

In proceeding to test a radio receiver, the ohmmeter should be located for easy visibility and you should hold one prod in each hand. In this manner, you can quickly make the needed contacts, and firmly holding the tips of the prods in place, observe the indication on the ohmmeter. We again caution you to watch for round about paths which may shunt the item you are intending actually to measure and may introduce errors in reading.

The circuit included above on this page is an illustration of values obtained in a typical radio set. You will note that the values of actual resistors are indicated. In the case of measuring a parallel combination, such as the 6,000 ohms fixed resistor, and the 4,000 ohms potentiometer (both located in the lower left hand corner of the schematic), one of these items has to be disconnected in order to obtain individual values and not a value for the two units in parallel.


LESSON 15

SIGNAL GENERATORS AND SIGNAL TRACERS

A signal generator is essentially a small transmitter designed to produce various frequencies required for service and laboratory work. Primarily a signal generator is used by a radio serviceman for alignment, but it is also adaptable for solving other service problems.


To mention briefly, a signal generator may be used for localizing the source of trouble in a radio receiver, detecting the stage producing distortion, testing individual parts, measuring gain, various audio and fidelity tests, and many other applications which can be used to simplify the job of a radio serviceman.

In a R.F. signal generator, an electron-coupled oscillator circuit is employed to produce adjustable radio frequencies. With this type of oscillator, the variations in the load have little effect upon the frequency. Tuning (adjustment of the frequency produced) is accomplished with a variable condenser. The tuning condenser control dial is carefully calibrated and is usually accurate to within 1%. The frequencies available are generated with several different coil-arrangements which are selected and connected to the tuning condenser of the circuit by means of a band-switch. A practical R.F. signal generator may cover frequencies from 100 KC. to 90 MC. This includes all I.F. frequencies used and also the usually employed communications frequencies. The coverage may be obtained in six or seven steps.

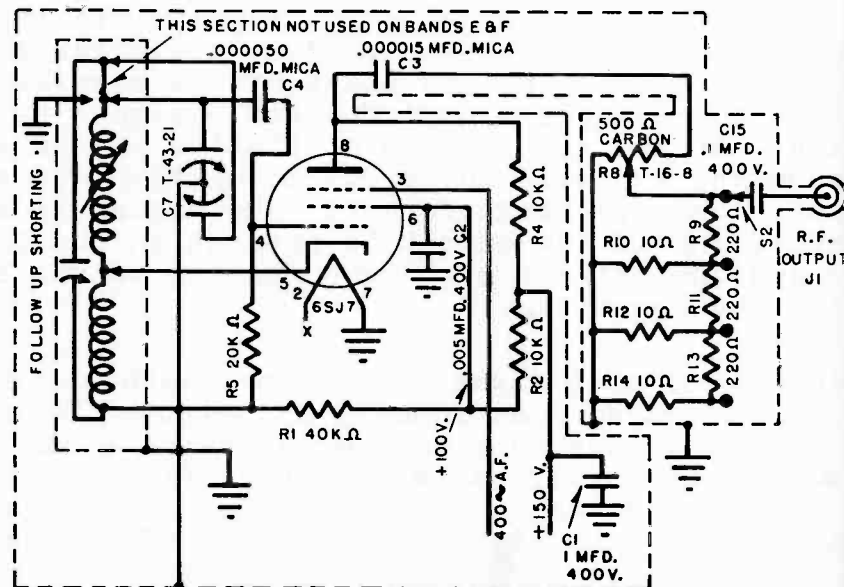

Simplified R. F. Oscillator Circuit

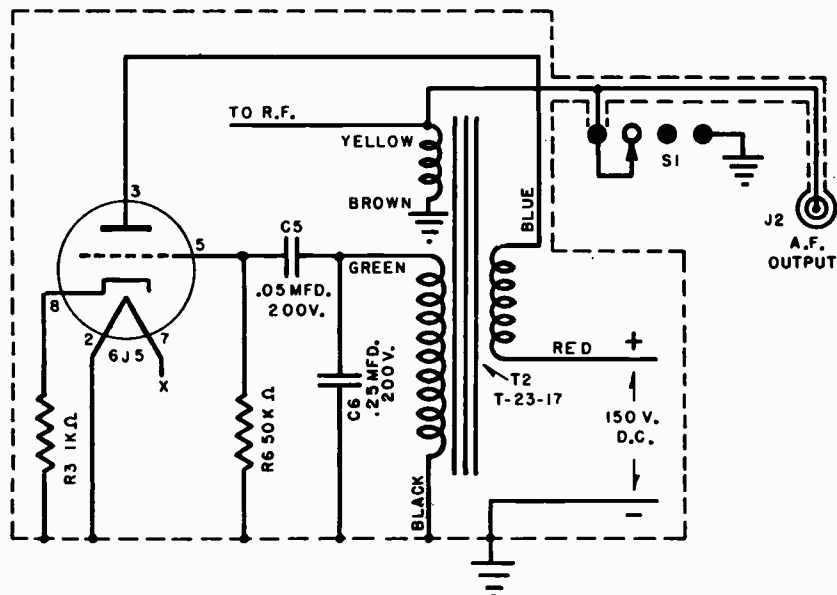In most units, the higher frequencies are not actually generated as fundamentals, but are obtained as harmonics of the highest frequency band for which L-C is actually provided.




Simplified A. F. Oscillator Circuit

A separate audio signal generator circuit is usually included in conjunction with the R.F. signal generator circuit. The audio signal produced may be of a single frequency (400 cycles commonly used), or several different frequencies may be available for selection. The intensity of the audio signal superimposed on the R.F. carrier may be controlled. This is known as the percentage of modulation and 30% is popular. Also the audio frequency output may be used separately.

A signal generator may be used for locating faults in radio receivers and as an aid for properly aligning all types of sets. With a signal generator, you can produce a similar signal to the one which can be handled by any stage of the receiver. For example, you can generate a powerful audio signal to drive the output stage. Or you can produce a relatively weak I.F., of the correct frequency and with about 30% modulation, to excite the input of the first I.F. transformer. The signal is applied to any one stage, and if the output is present in the loudspeaker, this stage and the balance of stages leading to the speaker may be assumed to be operating.

With the aid of a signal generator, each stage of a radio receiver can be tested individually and distortion can be detected. A higher accuracy in judging results can be obtained with the aid of an oscilloscope connected first to the signal generator direct and then to the output of the stage to observe effects produced on the signal. If instead of an oscilloscope, a vacuum tube voltmeter is used, stage gain can be measured.

Radio receiver audio fidelity tests are used to determine the over-all electrical fidelity characteristics of the complete receiver. This test is accomplished by applying a modulated R.F. signal to the input of the receiver and measuring the output voltage (at various modulating audio frequencies) across the loudspeaker voice coil. See sketch below which is reproduced through the courtesy of R.C.A. Manufacturing Company.

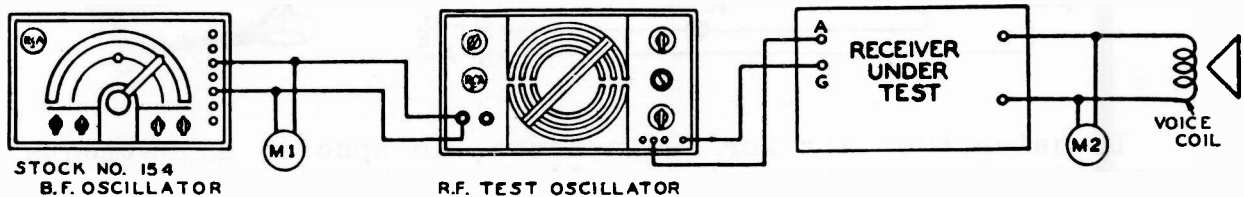



Connections for Radio Receiver Fidelity Measurements

Audio frequency signal generators are designed to produce signal frequencies between 30 to 15,000 cycles per second. Some of these units employ standard type of oscillators with the components designed to produce the required audio frequencies. Suitable inductors and capacitors for this purpose would be quite large and could be made variable only with the greatest difficulty. However, it is possible to produce audio frequencies by beating (combining in a non-linear impedance) two radio frequencies differing in frequency by the number of cycles required to produce the audio frequency. In practice, two R.F. signal generators and associated equipment are built-in a single case. One generator circuit produces a fixed R.F., while the second has its frequency variable and easily altered with a regular tuning condenser. If the frequencies of the two R.F. generators, for any one adjustment, differ (for example) by 800 cycles, then an 800 cycle audio signal is produced.

Signal Tracing Techniques

In 1945, simplified versions of signal tracing instruments were released. These lower priced instruments permitted one to listen to the existing signal at various points in the radio under test, and either incorporated a meter or had provisions for connecting a meter for comparative measurements.


The Feiler Model TS-1 is a very simple instrument and an examination of its basic schematic below will suggest its mode of operation. The capacitance-resistance input network will not upset or de-tune the circuit under test. When operated at R.F. or I.F. frequencies, this network provides correct values to convert the type 1T4 (pentode connected as a triode) to a grid leak type detector. Because of the small value condenser, the unit will produce louder signals from higher frequencies. This is just what is wanted since by operating more efficiently at R.F. than I.F., the unit can automatically adjust for the greater signal level of I.F. signal obtained from a radio under test.

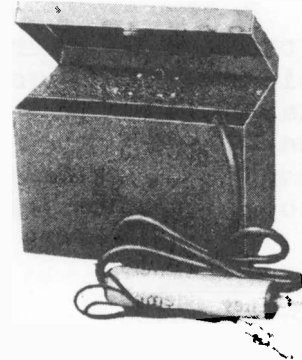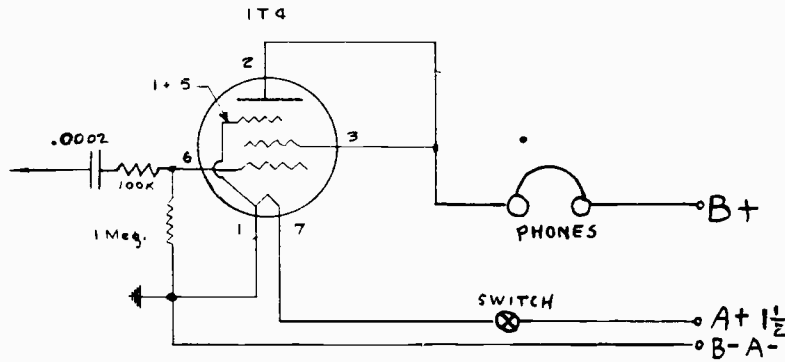

In using the unit for audio tests, no special adjustments are needed; in fact, there is no adjustments needed for any test and the probe can be touched safely to any point of the circuit. In this application, the impedance of the grid condenser and grid leak form a voltage divider network, and only a fraction of the strong incoming audio signal is impressed on the grid. The impedance of a small condenser at audio frequencies is very high; for example, at 1,000 cycles, a .0002 mfd. condenser will have an impedance of about 750,000 ohms. This automatic action is also what is wanted and the signal is reduced to a value that can be handled by the tube with its very small bias obtained from a voltage drop in the filament and from contact potential voltage.

The output from this single stage (when used with a 67½ volt plate battery) is sufficient to operate a pair of headphones. In this manner, it is possible to test for the signal at all points of a radio receiver without any adjustments at all and without risk of damaging the test unit or the radio.

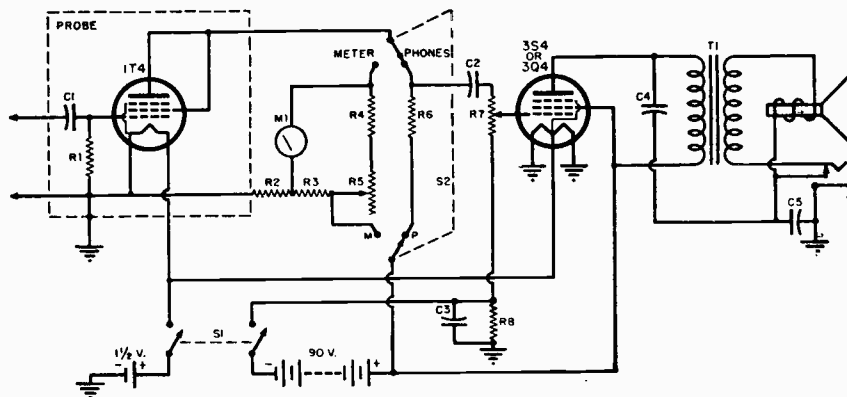The Superior Model CA-12 signal tracer was described in a past issue of RADIO NEWS and we reproduce the schematic of this unit through the courtesy of this magazine. The input arrangement is similar to the unit we just described. A meter is in-



*R*₁—20 megohm, ½ w. res.
*R*₂—20,000 ohm, ½ w. res.
*R*₃—1000 ohm, ½ w. res.
*R*₄, *R*₅—500 ohm, ½ w. res.
*R*₆—500 ohm rheostat
*R*₇—50,000 ohm, ½ w. res.
*R*₈—500,000 ohm pot.
*C*₁—0.0002 μfd. mica cond.
*C*₂, *C*₄—0.025 μfd., 200 v. cond.
*C*₃—4 μfd., 10 v. elec. cond.

*C*₅—0.02 μfd., 200 v. cond.
*S*₁—S.p.d.t. sw.
*S*₂—2-pole, 2-pos. sw.
*M*₁—0-1 d.c. milliammeter
*T*₁—Output trans., 10,000 ohms plate to voice coil
*J*₁—Closed circuit jack
I—IT4 tube
I—354 or 3Q4 tube
I—4" PM Speaker

As you progress with the test suggested, the signals should become stronger. Should any of the tests indicate a weakening of the signal, the stage preceeding this point is not operating properly and is producing a loss instead of a gain.

To locate an intermittent fault, the probe is placed on points where signal is to be expected, progressing from antenna to speaker. For each test made, try to obtain the intermittent failure, so that you can determine where the fault producing this failure lies ahead of the point under test or beyond this point. For example, if you are testing at the plate of the first I.F. tube, the turning the set on and off, shaking it, touching and pushing various parts, or doing similar things which ordinarily produce the intermittent condition, in this case do not cause the intermittent to appear in the output of the signal tracer, you can form the following deduction. Since in the test described, portions of the radio set ahead of the point under test were in the circuit serving the signal tracer output, but did not produce any intermittent indication, then these sections (ahead of the point) must be in good operating condition. The fault lies beyond the point at which you are testing. Further, tests after this point will isolate the stage and suggest the parts that may be at fault.

Test for noise, hum, or distortion is carried out in a similar manner. In alignment work, a signal tracer may be employed as the audio output indicator.

At this point we must point out to the student that a radio serviceman just like the doctor does not know it all. A physician will come across many cases completely new and baffling to him, but he will undertake to handle them by additional study and consultation with other men of his profession. The serviceman should do likewise. If the problem puzzles you, simply take the set to the shop or point out that there are a number of facts you must look up and that you will be back next day.

REVIEW QUESTIONS

1. Describe several applications of a signal generator.
2. Why is an audio signal needed in conjunction with a R.F. generator?
3. Explain why a signal tracer tests for faults "directly," while a voltmeter indicates faults "indirectly."
4. Using a circuit diagram of small modern superhet indicate points to which the signal tracer probe may be touched for test purposes.
5. How does a signal tracer detect a stage with an intermittent fault?
6. Can you think of a radio fault that could not be found with a tracer?

LESSON 16

USING AN OSCILLOSCOPE FOR SERVICING

The cathode ray oscilloscope is an indispensable tool for the radio laboratory and can be a valuable aid to a radio serviceman in performing repair work. The heart of the unit is the cathode ray tube. This we will discuss first. The need for the associated circuits then will become obvious. Sweep circuits, flat-response amplifiers, focusing arrangements will be explained before we review the technique of operating a cathode ray oscilloscope and interpretation of visual results obtained.

A cathode ray tube is a vacuum tube so designed that electrons emitted from a cathode (located at one end) are concentrated into a narrow beam. This beam is influenced by electrostatic or magnetic fields and is caused to impinge upon a screen at the opposite (wide) end of the tube. This screen becomes fluorescent at the place where the electron beam makes the impact and, as the beam varies from side to side and up and down, the image produces a pattern. The nature of the pattern depends on changes of intensity taking place in the associated electrostatic or magnetic fields.

A cathode ray tube in itself is not a complete indicating device. In order to produce a simple spot on the fluorescent screen, the proper high voltages must be applied to the various electrodes. Usually a single power transformer is used with two separate power supplies; one of conventional type and another to supply high voltages needed for the cathode ray tube.


As pointed out in the "Reference Manual" copyrighted by Allen B. Du Mont Laboratories, a source from which we will quote at length on the subjects of sweep circuits and amplifiers, the combination of the cathode ray tube and suitable power supply is enough to form the indicator element. Since the cathode ray tube is relatively an insensitive device requiring potentials of several hundred volts for full deflection, a suitable amplifier is needed to increase the usual input voltage of much lower magnitude to acceptable value.

While the amplifier will permit the study of small voltages, it will also impose limitations on the character of signals that can be transmitted by the amplifier. With the unknown signal applied directly to the deflection plates, the maximum amplitude observable will be limited only by the full scale deflection of the beam; the maximum frequency which can be applied is limited by the transit time of the beam passing between the deflection

plates, and also by the shunt capacitance between deflection plate terminals.

Applying a direct current voltage to the plates will deflect the beam proportionally to the magnitude of that voltage, and the beam will remain fixed in its deflected position until that D.C. deflection voltage is removed. Therefore, there is no low frequency limitation when direct connection is used. In fact, it is the application of a direct current voltage, controllable in magnitude, that is used to position the beam in both horizontal and vertical directions in the complete oscillograph unit.

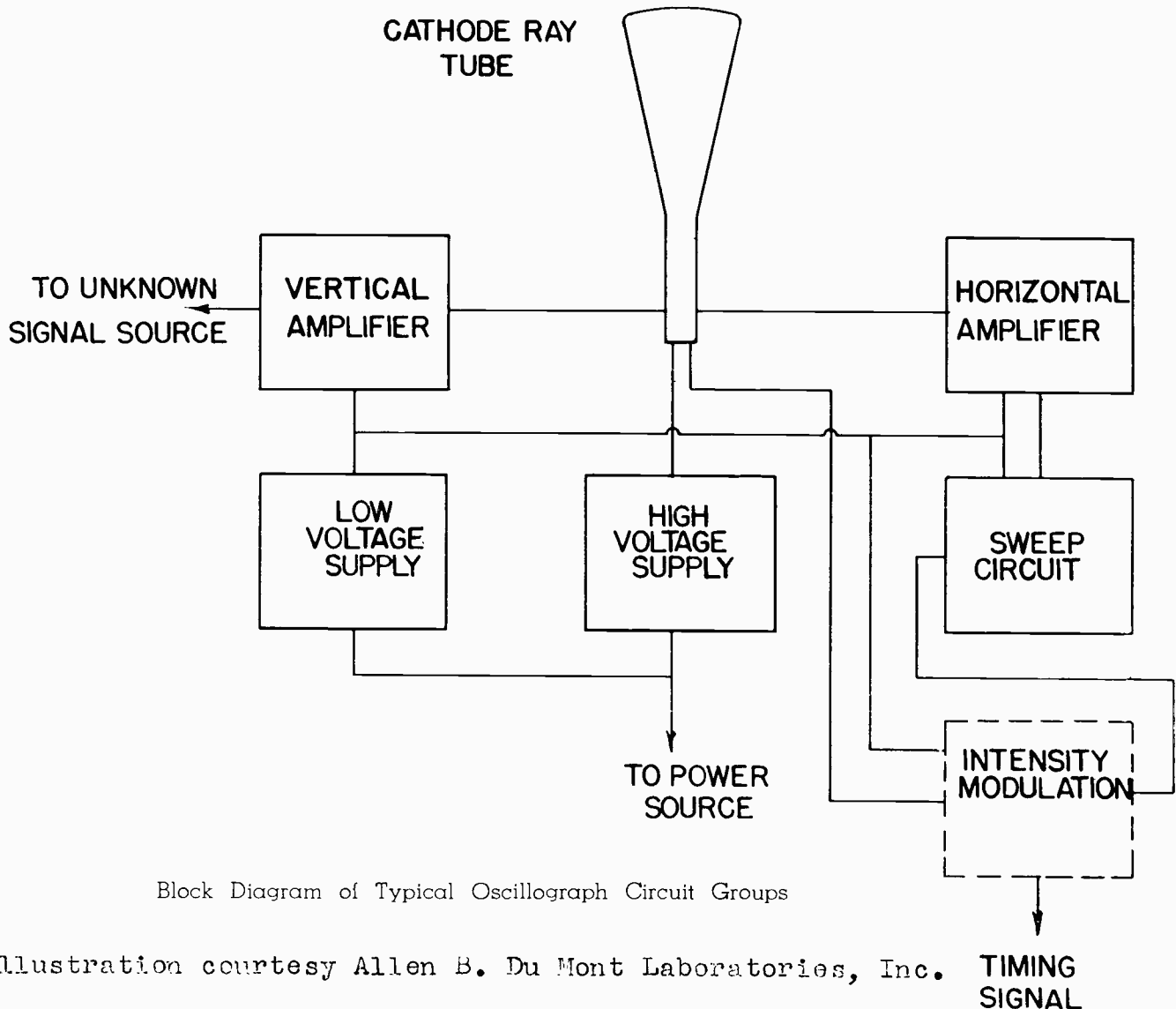When an amplifier is interposed between signal source and deflection plates, the signal will be faithfully reproduced only if the limitations of the amplifier are not exceeded. These limitations include frequency discrimination both in the amplifier and input attenuator circuits, phase distortion, and the



Block Diagram of Typical Oscillograph Circuit Groups

Illustration courtesy Allen B. Du Mont Laboratories, Inc.


maximum allowable direct current and peak input voltages. The minimum signal voltage is determined by the least amount of beam deflection which can be tolerated for effective study, and therefore by the gain of the deflection amplifier. The maximum voltage which can be applied is limited by the voltage rating of any input coupling capacitances and the voltage range of the input amplifier stage. Of course, a radio frequency signal will not be passed by an audio frequency amplifier, nor will a direct current signal be amplified by an alternating current amplifier. Attention must also be directed towards the gain or attenuation control, since the effects of the variable distributed capacitance depending on the setting of the rotor in a high resistance potentiometer can cause extreme phase and frequency distortion.

A very important consideration in choosing an oscillograph is the frequency response characteristic of the vertical axis amplifier. Many applications of an oscillograph require the observation of pulses, square waves and other non-sinusoidal waveforms. Therefore, not only must the sinusoidal response be uniform, but the transient response must permit undistorted amplification of irregular wave shapes.


This amplifier discussion thus far has been restricted largely to the vertical axis. Similarly, these considerations apply to the horizontal amplifier. For most applications, the signal applied to the horizontal deflecting plates provides for the movement of the spot at a uniform rate with respect to time. Such a signal provides the time-axis along which is plotted the unknown variable voltage. After the spot has traveled the width of the screen, it snaps back to its starting position and the process is repeated. Without going into a detailed discussion of the generator which supplies the horizontal voltage, it will suffice to say that the waveform of this time-axis deflecting voltage is usually of a saw-tooth nature, and therefore, is rich in harmonic content. Since this saw-tooth voltage is amplified by the horizontal amplifier, the frequency and phase characteristics of that amplifier should permit undistorted amplification of sinusoidal signals of frequencies extending both far above and below the saw-tooth recurrence rates. Frequently, the saw-tooth frequency range is from a few cycles per second to over 50,000 cycles per second, so that quite stringent requirements are imposed on the frequency response characteristic of this amplifier.

It is also desirable for the horizontal and vertical amplifier to have identical phase characteristics to facilitate accurate study of the relationship between two different signals, each being applied to a separate axis.

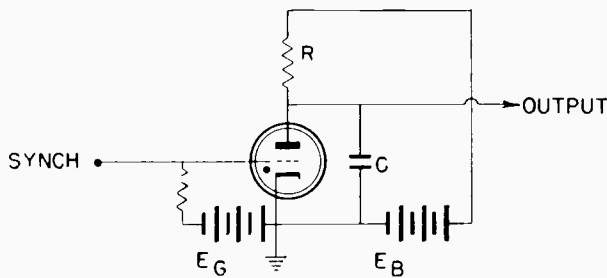The linear time-base generator or sweep oscillator is the integral part of the oscillograph unit which generates the saw-tooth voltage producing the linear time-base referred to above. The time-base is not restricted to a linear function, but can also be a sinusoidal, circular or spiral function or any other shape that may be desirable for particular applications.



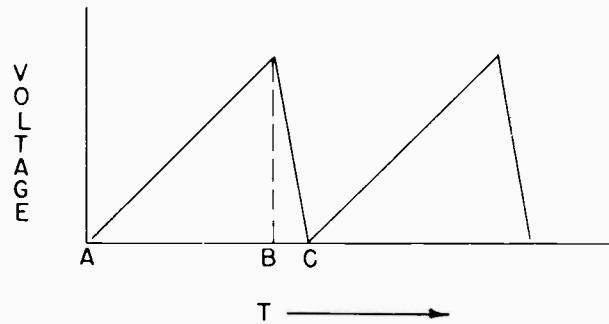Basic gas triode sweep oscillator circuit



Linear time-base voltage waveform

The saw-tooth wave is generally developed by a relaxation oscillator in which a gas discharge tube is used.

A feature of the sweep oscillator is its ability to synchronize its frequency of oscillation with the frequency of the unknown signal so that in cases of recurrent phenomena the spot begins its excursion each period at the same point on the wave of the unknown. The resulting luminescent pattern is a stabilized wave. With the pattern "locked in," the rapid retrace of the wave many times a second will give the appearance to the human eye of a "still photograph" because of the persistence of the fluorescent-phosphorescent screen on the cathode-ray tube coupled with the persistence of human vision.

The subject of blanking or intensifying the beam naturally brings to mind the application of beam intensity modulation for other purposes. In the case of television, the grid of the cathode ray tube is modulated by a voltage which causes the spot or trace to become lighter or darker in accordance with the voltage variations. This same principle may be used in oscillographs to provide timing demarcations, or reference points on the trace or pattern. These timing marks can be provided by an external oscillator or pulse generator whose frequency is known. Other times, the signal available for beam modulation is less than that needed for extinguishing the beam, and therefore, an amplifier is needed. This amplifier is commonly known as the Z-axis amplifier. A further use for this provision is to intensify the beam over portions of the trace where the writing rate of the spot is so great that the fluorescent screen is not sufficiently excited. Thus, the intensity is more uniform throughout the entire trace and photographic exposure is facilitated. Furthermore, the portion of the trace which is most interesting is often the least visible. This provision will prevent burning and damage to the fluorescent-phosphorescent screen caused by operation of the intensity control at maximum (i. e., zero bias) in an attempt to improve the total visibility.

Focusing of the fluorescent spot is accomplished by varying the ratio of the voltages applied to the two anodes. Regulation of the spot size and intensity is accomplished in some tubes through the variation of anode current of one of the

plates. Variation in the bias voltage applied to the control grid will permit this adjustment. In practical equipment, of course, these adjustments are made by means of variable resistors (potentiometers) mounted on the control panel.

We will now talk about the actual operation and application of a commercial oscilloscope. For this purpose we will discuss Supreme Corp. Model 546 unit.




The illustration of this instrument will suggest to you the physical position of the various controls, which are also indicated in the schematic diagram. The intensity control varies the brilliance of the spot. Usually this control also has the on-off switch. The focus control is used to adjust the resulting picture to a bright image and is dependent on the adjustment of anode voltages for proper electron-optical focus.

Bearing in mind that any picture or trace obtained consists of a moving dot of light, you can understand that it may be required to shift the position of the dot or the complete picture. For this purpose, the vertical position and horizontal position controls are employed. These adjustments are accomplished by varying D.C. voltages applied to both sets of deflecting plates; potentiometers R_{10} and R_{11} are used for this purpose.

The gain controls are potentiometer voltage divider networks at the input to the vertical and horizontal amplifiers. These parts are marked R_{17} and R_{18} . In the unit described, these controls are not connected unless the respective amplifier gain controls are placed in operation.

Means are provided for using the internal sweep or for changing the circuit so that an external sweep can be employed. Provisions are also incorporated for eliminating the horizontal amplifier when external sweep is employed.

In using the internal sweep, a special saw-tooth oscillator becomes connected to the circuit and produces a changing voltage which sweeps the beam across at an adjustable frequency and returns the beam from extreme right to left in a very short fraction of the total cycle. Since it is not practical to produce all frequencies in the saw-tooth oscillator with a one set of components, in the oscilloscope described, six steps are employed

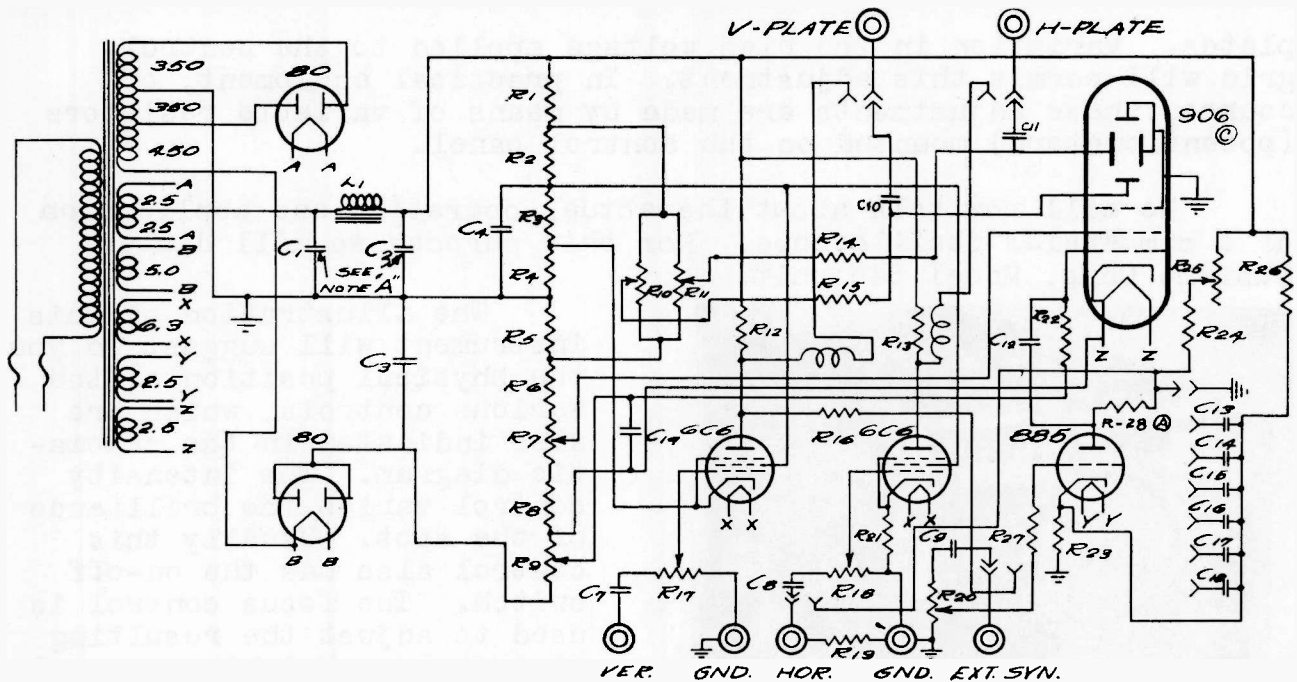


Symbol	Ohms	R-9	200,000	R-18	4 megohms	R-23	1,000	Symbol	Mfd.	C-12	50 mmfd.
R-1	25,000	R-10	4 megohms	R-19	1 megohm	R-24	1 megohm	C-3	0.5	C-13	0.37
R-2	10,000	R-11	4 megohms	R-20	15 megohms	R-25	4 megohms	C-4	8.0	C-14	0.04
R-3	10,000	R-12	50,000	R-21	1,000	R-26	100,000	C-7	0.1	C-15	0.01
R-4	220	R-13	100,000	R-22	500,000	R-27	100,000	C-8	0.1	C-16	0.0025
R-5	250,000	R-14	1 megohm			R-28	500	C-9	0.05	C-17	600 mmfd.
R-6	750,000	R-15	500,000	Symbol	Mfd.	C-1	4.0	C-10	0.5	C-18	200 mmfd.
R-7	500,000	R-16	1 megohm	C-2	4.0	C-11	0.25	C-19	0.5		
R-8	100,000	R-17	1 megohm								

covering from 15 to 30,000 cycles per second and overlapping each other for easy adjustment. Once the band of sweep frequencies, which include the frequency required is selected, the fine frequency control (potentiometer R₂₅) is used to achieve the exact adjustment.

The understanding what the various controls do will permit you to make the necessary adjustment to view any pattern obtainable from equipment under test. It is important to have the spot moving at all times in order not to burn out the fluorescent screen.

For a serviceman, a cathode ray oscilloscope is especially useful for checking voltage wave forms, as an aid in alignment, as a peak voltmeter, for measuring phase shift, for detecting and measuring distortion, for frequency measurements, and as a visual indicator in signal tracing. We will briefly describe these applications.

To study a wave form, the source of voltage is connected to the vertical amplifier and a sweep frequency is selected that will permit the viewing of a single cycle or several cycles. By eliminating the horizontal sweep from operating, the voltage input to the vertical amplifier can be measured. The actual height of the "line" produced will be in proportion to twice the peak voltage impressed. By comparing this height to some other known value of A.C. voltage, the unknown peak voltage can be estimated. In using D.C. voltage for comparison purposes, please

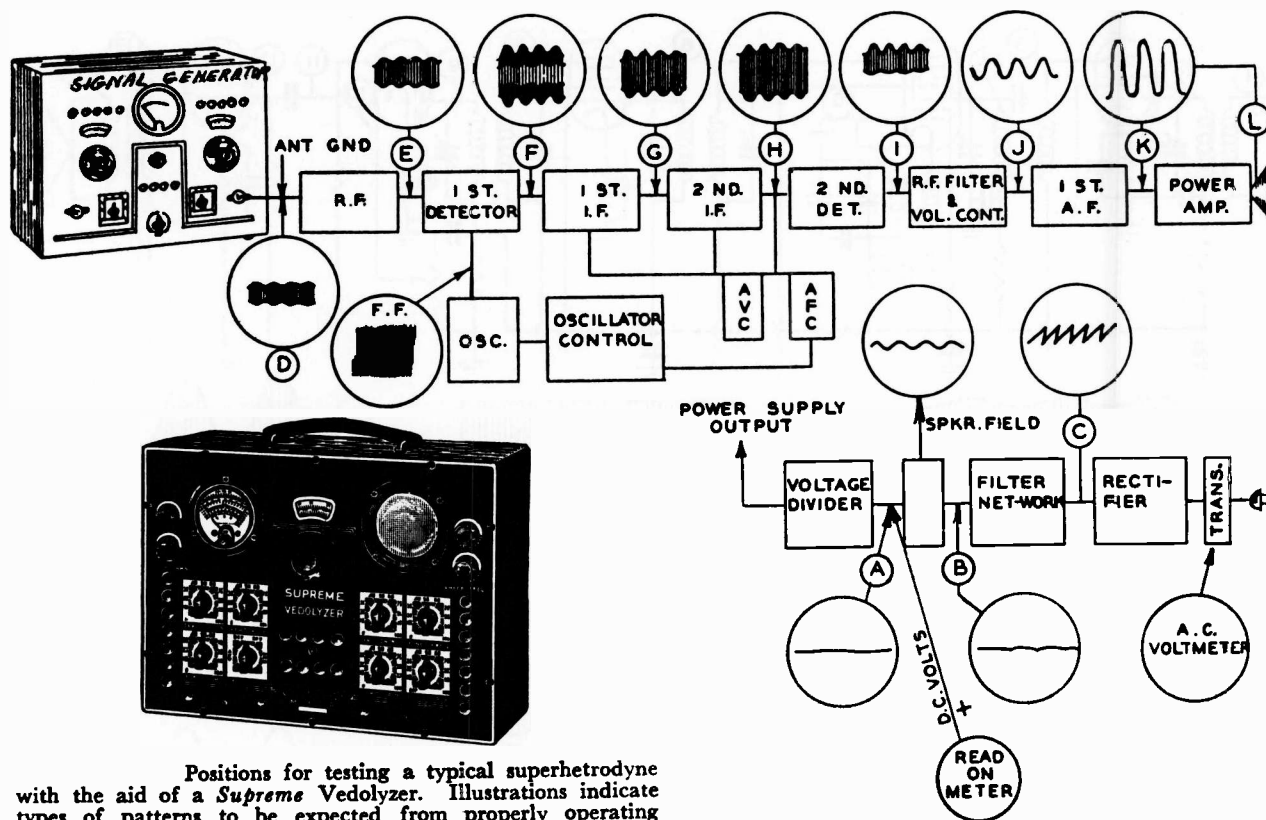


Positions for testing a typical superheterodyne with the aid of a *Supreme Vedolyzer*. Illustrations indicate types of patterns to be expected from properly operating circuits.

bear in mind that the visual line will appear only above the center mark, while for A.C. measurements, the line appears above and below and actually gives twice the height as compared to the same value D.C. A signal can be examined with the aid of a cathode ray oscilloscope before it enters a piece of equipment, and a further visual examination of this signal from the output of the equipment will indicate any changes or distortion produced by the equipment. For this purpose, special apparatus is available that will permit the examination of both patterns at the same time and, thereby, simplify the comparison.

In alignment work, with the aid of a proper sweep arrangement, the response curve can be viewed on the scope and exact adjustments carried out for best operation. This type of alignment is especially beneficial in high fidelity radio receivers and in frequency modulation equipment.

While the majority of signal tracers depend on hearing an audio signal or measuring voltage values, as indicated on a tuning-eye tube or a standard meter, additional information can be supplied by a cathode ray oscilloscope used in conjunction with the signal tracer. In fact, Supreme Instruments have built a visual type signal tracer.



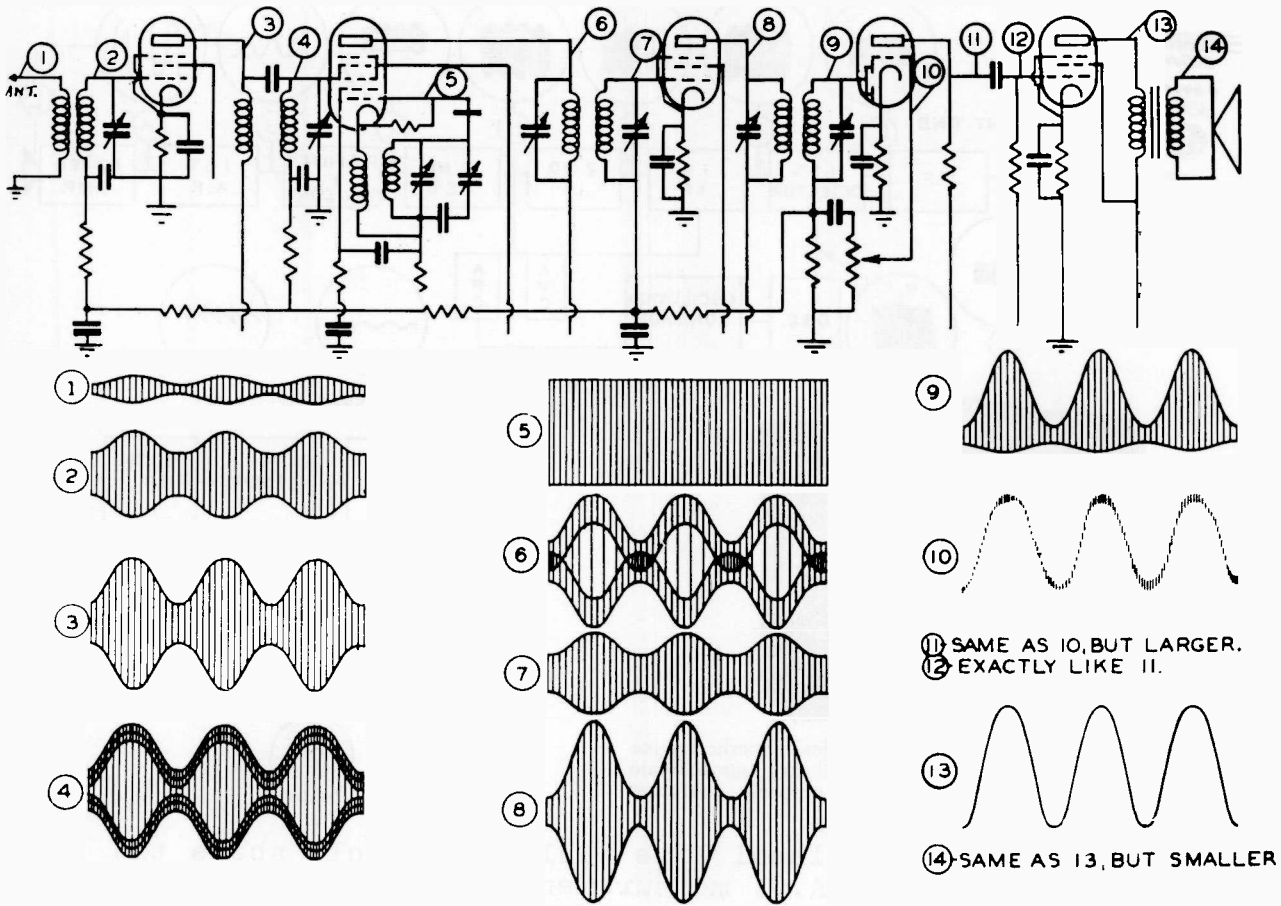
The shape of a pattern obtained on the cathode ray tube depends on the value and phase relationship of the voltages applied to the deflecting plates. These patterns are useful



for the study of voltage and phase relationship and supply information about the unknown voltage applied to one set of plates when the character of voltage applied to the other set of deflecting plates is known.

It is important to understand that the electron beam of the cathode ray tube is influenced by both sets of deflecting plates at the same time. For example, if equal sine wave voltages are applied to both sets of plates, the pattern obtained will be a line of 45 degree slope, provided the voltages are in phase. The reason for this result becomes clear, if you bear in mind that the instantaneous values of both voltages are equal at all times and the beam is shifted equally towards one of the horizontal plates and one of the vertical plates.

If two identical voltages of the same amplitude, but out of phase by 90 degrees are used instead, a circle pattern is produced. If the amplitudes are not equal, an ellipse will result. If besides the difference in amplitude, the phase differs by 45 degrees, a figure similar to an ellipse, but slanting to one side, will be produced. Figures so far considered are of the simpler Lissajou's types. From the pattern obtained on the screen of the scope, the frequency and phase relationship of the two voltages can be determined.

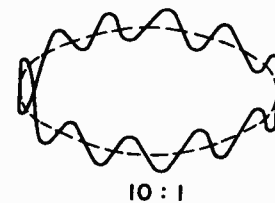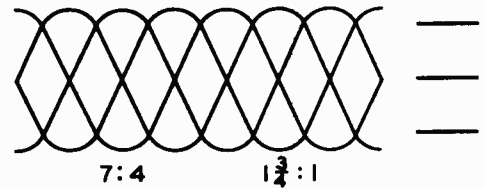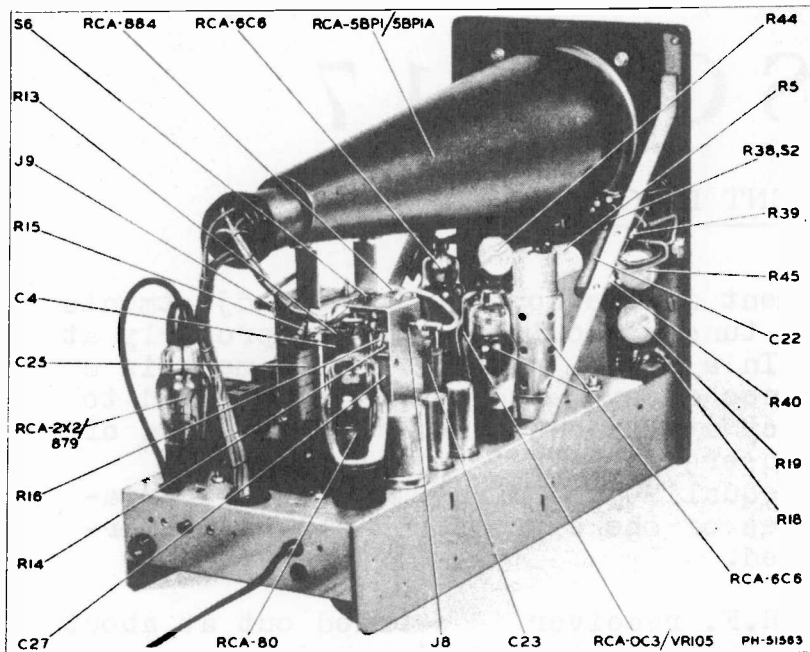

As the ratio of the frequencies increase, the pattern obtained becomes more complex. Ratios under 10 to 1, can be determined without difficulty. In general, it is difficult to judge the ratio directly from the picture without the knowledge of some tricks. One such tricky method is to count the number of horizontal lines of intersection, see illustration. Add one to this number and the result is one number of the required ratio. The other number of the ratio is obtained by counting the peaks at the top (or bottom, but not both) of the pattern.

For the study of ratios greater than 10 to 1, the wave form is produced on a circle or ellipse. A phase splitting circuit consisting of a condenser across one set of deflecting plates and a resistor across the other plates will displace the pattern around the ellipse for easy analysis.

REVIEW QUESTIONS

1. How is a pattern produced on the screen of a cathode ray tube?
2. Why must the amplifiers used in a cathode ray oscilloscope have good frequency response characteristics?
3. What are the main applications of an oscilloscope in radio servicing?
4. How is an oscilloscope used as a signal tracer?
5. How can a frequency of an unknown sine wave be determined by comparing it to one of known frequency?

LESSON 17

ALIGNMENT INFORMATION

The process of alignment is the combination of adjustments carried out to permit every tuned circuit to operate properly at each setting of the dial. In a T.R.F. receiver, alignment is a relatively simple matter since every tuned stage is intended to operate at the same frequency at any one time. Each section of a multi-gang variable condenser is shunted by a trimmer and these trimmers are used to equalize the minimum capacity variations due to stray capacities of the circuit and slight differences in inductances employed.

The alignment of a T.R.F. receiver is carried out at about 1,400 KC. and adjustment of trimmers is made to produce maximum signal. Once adjustment is made at this frequency, the receiver tuned circuits will track at lower frequencies since greater amount of capacity of the variable condenser will be in effect and any small additional differences will represent only minute fractions of this capacity.

In a superhet, as you know, the several tuned circuits function at entirely different frequencies but their adjustments are interdependent. For optimum results, the adjustments must be correctly made and carried out in the proper sequence.

The I.F. transformers are usually double tuned and will give maximum gain and best selectivity response when employed at a frequency for which these coils were designed. This frequency varies in radios of various makes and the period in which the sets were produced. In modern sets, the I.F. is between 455 and 470 KC. Some of the older sets used I.F. of 175, 260 KC., and other values.

For correct tracking, the oscillator of a superhet must generate a frequency usually above the signal frequency and differing from it by the I.F. value. When the oscillator frequency is higher, the tuning capacity must be smaller to give the required frequency range. This tuning capacity is made smaller in practical circuits by employing a cut-section condenser or by connecting a padder, which is a small semi-variable condenser, in series with the gang of a regular tuning condenser that is used for the oscillator section.

The antenna and oscillator coils (in some larger sets an R.F. coil is also used) are so designed that with a given cut-section condenser (or regular condenser and correctly adjusted padder) it is possible to adjust the trimmers at the high frequency band and have correct tracking at all other frequencies. This design, of course, is based on the I.F. used, and this is another reason why correct I.F. adjustment must be made.

In the process of tuning a superhet receiver slightly out of alignment, the oscillator section has a much more pronounced effect upon the tuning adjustment since the antenna (and R.F. if used) sections are broad enough to pass the signal of a station even if slightly detuned. Under such conditions, a given station will be received at some incorrect, but not much removed, point on the dial. At this setting, the signal of the station wanted will "ride through" the detuned antenna (and R.F. if used) sections, while the particular adjustment will produce in the incorrectly adjusted oscillator a frequency higher exactly by the I.F. of the set. This suggests that the dial reading is corrected by adjusting the oscillator section trimmer.

In performing alignment, means must exist for comparing the intensity of the output as adjustments are made. Listening to the output is one method, but it is not very reliable since the human ear is not critical to very small changes in sound intensity. If the set is equipped with a tuning indicator such as an electron-ray tube, shadow-meter, or plate milliammeter, these devices can be employed to indicate resonance. A vacuum tube voltmeter may be connected across the A.V.C. junction point and ground; with this arrangement, resonance will be indicated by maximum voltage. An A.C. voltmeter of low range can be connected across the voice coil, or a higher range of such a meter in series with a paper dielectric condenser can be inserted across the primary of the output transformer.

In sets with A.V.C., steps must be taken to nullify this action while carrying out alignment work. If you are able to carry out the alignment while feeding a very weak signal, the A.V.C. will not produce any effect under such a weak signal and the response will be directly related to accuracy of the alignment. When using a weak signal, you should have the volume control of the receiver wide open.

In sets where a stronger signal is needed, the A.V.C. by trying to keep the output intensity constant will prevent you from judging true effects of the adjustments, and in such sets A.V.C. must be prevented from operating during alignment. Where a separate A.V.C. tube is used, this tube may be removed without impairing the operation of the receiver except for lack of automatic volume control action. In other sets, it is permissible and quite a simple matter to ground A.V.C. bus to remove this action. There are sets where this simple means of nullifying A.V.C. cannot be made and in such sets you can disconnect I.F. stages grid returns from the A.V.C. and connect these returns to ground or similar point.

A signal generator is essential if the I.F. stages are out of alignment to a considerable degree. If you have another set properly operating and having the same I.F., you can couple these to carry out the I.F. adjustment without a signal generator. If the I.F. amplifier is not too far out of alignment, a signal generator lead may be connected to the signal input grid of the

oscillator. A small mica condenser is wired in series with this lead and also the ground lead. The I.F. trimmers may be adjusted in any order in such case.

In some sets, where the owner may have attempted the repair himself, you may find it impossible to get the signal through both transformers of the I.F. amplifiers. The best procedure under such circumstances is to adjust one transformer at a time. Connect the signal generator to the grid of the I.F. tube preceding the output I.F. transformer and adjust the trimmers of this transformer. You may find it necessary to find a signal generator frequency which will get through. If this frequency is above the correct I.F., turn the trimmers clockwise to increase capacity and lower the adjusted frequency of the I.F. transformer. In this manner, you can approach the correct adjustment. Then return to the converter tube and complete the adjustment of the I.F. amplifier.

There are receivers having the trimmers located apart from the coils of the I.F. transformer. A few transformers you encounter may be triple tuned, while many midgets have the second I.F. transformer of the single tuned type. In all these cases, the alignment practice is as described. As the volume output increases with improvement of gain obtained by adjusting the circuits to resonance, the volume should be reduced with the attenuator of the signal generator and not with the volume control of the set.

In carrying out the alignment of the I.F. amplifier, the turning of every trimmer should have a noticeable effect on the volume of the output or the indicator employed. Lack of such action will suggest an open coil, shorted trimmer, or a stripped adjusting screw. The factory engineers design I.F. coils so that the trimmers can give considerable variation from the optimum I.F. If you find that the trimmer adjusting screw must be tightened completely or left very loose, suspect trouble.

Although high frequency adjustment in most superhets should be performed at 1,400 KC., many manufacturers specify different frequencies and you should watch for such variations. If a station operates in your locality at the very frequency suggested for alignment, a slightly different value should be employed. In a few sets, the manufacturer's instructions give a high frequency at the end of the dial calibration for setting the oscillator trimmer and another high frequency for completing this alignment.

High frequency adjustments are made after the I.F. is aligned. A signal generator set at the correct frequency is connected to the antenna or coupled loosely to the loop of the radio with the aid of three turns of hook up wire about 8 inches in diameter. In alignment work if your signal generator provides for percentage modulation adjustment, a value between 30% and 50% will give best results.

The radio receiver dial is adjusted to a frequency corresponding to the frequency being produced by the signal generator. This is usually about 1,400 KC., but, as we have mentioned, other frequencies may be suggested by a manufacturer for certain radio sets. The adjustment of the oscillator trimmer should permit you to obtain proper response without changing the dial setting. The antenna trimmer need not be touched at this time since this circuit is broad enough to pass the signal frequency even if considerably detuned.

After the oscillator section is adjusted, the antenna trimmer adjustment is made. In radio sets using R.F. pre-selector, this stage is adjusted at the very end. You may find it advisable to go back and recheck all points of alignment including I.F. trimmers. Sometimes slight additional adjustment is possible for further improvement of response.

In superhet receivers using a cut-section condenser, no other adjustment is needed and the set should now work properly at all frequencies. In case you cannot obtain successful results at low frequencies and are certain that the alignment work has been correctly carried out with a good signal generator, adjustment at the low frequency end can be made by bending the outside plates of the variable condenser, which are notched for this purpose. You can understand that bending these plates slightly, no effective change will be produced on your high frequency adjustments, since these plates engage the stationary plates only at the lower frequencies.


In case an ordinary gang condenser is used, a padder is provided for adjustment at about 600 KC. This frequency is not critical but is recommended by most manufacturers.

In low frequency adjustment, the signal generator is set to produce 600 KC., and while the radio dial is rocked up and back past the 600 KC. point on the dial, the padder is adjusted for maximum signal. The rocking action need not be employed and the adjustment may be carried out at 600 KC. with the objective of having the signal intensity drop above and below this frequency.

A word of caution is in order to those who have not yet handled receivers that incorporated a fixed mica condenser in series with the padder. Many times this fixed condenser is the one that causes the trouble and this difficulty is not easily detected.

In radio sets providing reception on more than one band, the same procedure for adjustment of the I.F. is carried out first of all. Unless there are manufacturer's instructions to the contrary, the broadcast band is aligned next. In multi-band receivers, the trimmers may not be supplied on the variable condenser or, if they are included, may not be employed for alignment. Usually each set of coils has its own separate trimmers mounted near corresponding coils.

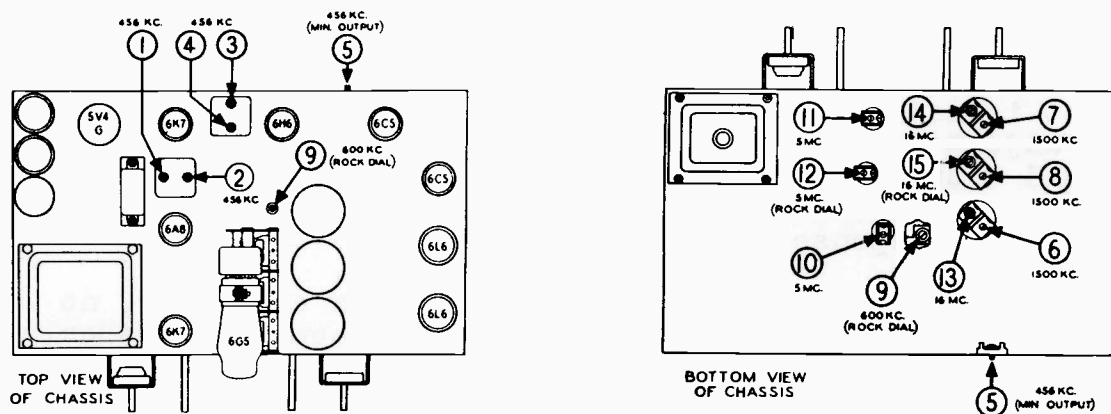If the short wave bands included have "independent" trimmers, these can be adjusted with the lowest frequency band first. In some sets, the adjustment of some one trimmer may effect an adjacent band and in such cases the alignment procedure must be carried out in the proper order.



In general, the alignment of multi-band receivers is involved because it is difficult to find the proper trimmers that correspond to the various bands. Charts similar to that illustrated are provided with circuit diagrams to permit easy location of these trimmers. Another problem is the possibility of adjusting the oscillator to produce an incorrect frequency which nevertheless will have a value that will result in new frequencies (due to harmonics) which may pass through the I.F., but not permit the receiver to operate at its maximum efficiency.

In carrying out alignment on short-wave bands, it is also helpful to know the correct frequencies for the high and low positions of the alignment. If these frequencies are not available, it is usually possible to guess by using the corresponding variable condenser position for each band after the broadcast band, but changing the wavelength switch and adjusting the signal generator to the corresponding frequency.

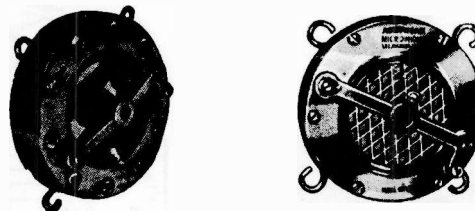
We will now consider a few possible troubles. The failure of any of the trimmers to have an effect on the response may be due to an open secondary or broken lead to the trimmer. Should you experience an improvement in response as any one trimmer is tightened, but find it impossible to tighten beyond a certain point, this shortcome will suggest that the oscillator trimmer has been tightened too far, and probably the dial scale does not read correctly. Similar trouble may occur at the other extreme when you are forced to loosen the trimmer to a point where the set screw no longer engages the threaded bushing.

LESSON 18

AMPLIFIERS, PUBLIC ADDRESS, AND HIGH FIDELITYPrinciples of PUBLIC ADDRESS SYSTEMS

When a large group of people is to be served with a common program, public address equipment finds its application. Most often a speaker's voice is amplified to a suitable volume to make him audible to all present. Radio programs and phonograph records also serve as a means of the input. If the program originates some distance from the amplifier a line is used to connect it to the input. In talking picture work a photo-cell serves as a means of input and requires a special pre-amplifier.

Essentially, a P.A. system consists of one or more of the sources of input mentioned above, the amplifier or any pre-amplifiers necessary, and the output in the form of one or more loud-speakers so placed as to take the greatest advantage of the acoustics. These various parts of P.A. systems will be taken up in detail with additional data on volume controls and measurements of related factors.




CARBON MICROPHONES

A microphone is a machine for transforming the sound waves into corresponding electrical energy. How truthfully it performs this task is the test of its excellency. Years ago a common microphone in P.A. use was the two-button type. Being a carbon microphone it depends for its operation on the varying resistance of the carbon granules with the pressure of the waves produced by sound which strikes the diaphragm. As the diaphragm fluctuates, corresponding fluctuations in the resistance of the carbon occur and vary the current passing through. In the two-button microphone, one button is placed on each side of the diaphragm and so operate exactly out of phase. This electro-acoustical push-pull arrangement gives better quality.

The thin metal diaphragm will resonate at a certain frequency and cause an increased output at this frequency. The better grade microphones have their diaphragm stretched so that resonance occurs at the upper end of the audible frequency range. This may be further reduced by air damping. The output of a two-button microphone is in the order of -40 DB; and the impedance is commonly 200 ohms per button. A transformer is used to couple this type microphone to the load.

The condenser microphone may be mentioned for its historical interest. If a variable condenser is connected to a source of potential, the charging current will vary with changes in capacity. The diaphragm of a condenser microphone constitutes one of the plates of the condenser, while the back-plate acts as the other plate. The capacity so formed is in the order of 200 micro-microfarads, and the maximum variation in capacity is only 0.01 per cent.

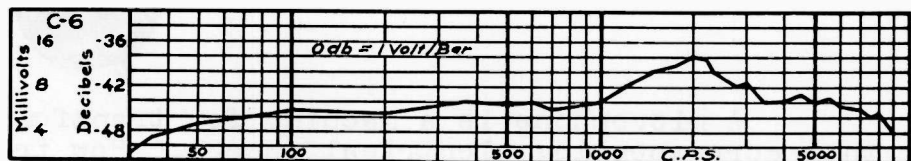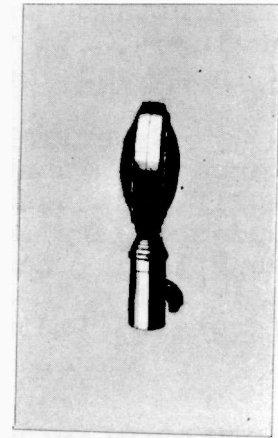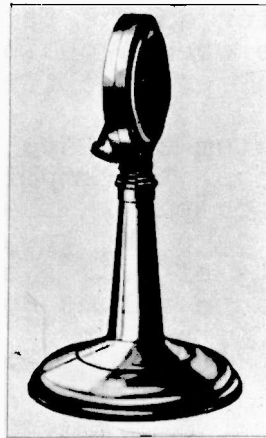Into the head of the condenser microphone is built-in a two stage resistance coupled amplifier to bring the output signal strength up to that of a two-button microphone. Batteries are usually employed as the source of condenser potential and for filament and plate supply of the pre-amplifier.



Various types of crystal microphones and a typical response curve.


The crystal microphone employs a piezo-electric crystal as a generating element. A crystal when subjected to stresses of sound waves produces corresponding changes in electrical potential generated by the crystal element. The output level of a crystal microphone is, of course, much lower than that of a carbon microphone, usually in the order of -60 DB, and requires either a suitable pre-amplifier or a main amplifier of a high gain type. The crystal microphone has absolutely no background noise and the response is not effected by the position of the microphone nor by reason of moving it about while in use.

The velocity microphone has been more recently developed and because of its excellency over the other types is finding extensive application in better public address equipment. Velocity microphones have an output of about the same value as the output of crystal type and may be obtained in high impedance types for direct coupling to the control grids of vacuum tubes.

The velocity microphone has highly directional qualities and will not pick up background noises. This greatly assists in reducing the possibility of reproducing undesirable noises. This type of microphone further has no internal "hiss noises" and possesses quite flat response characteristics over a wide audio frequency band.

As a means of radio input an ordinary tuner is utilized. This may be of the tuned radio frequency type or a superheterodyne. The latter is preferred because of its better selectivity. An automatic volume control is essential as a powerful local may literary blow the people out of the hall before the manual control is adjusted. The second detector should be of the diode type as no further audio frequency amplification outside of the final P.A. amplifier is needed. If a triode tube is used, the plate should be connected to the cathode for diode operation. Two A.V.C. circuits are illustrated below.

Phonograph records are made for rotation at 33-1/3, 45, and 78 RPM (revolutions per minute). The 78 RPM records have been made for years and are supplied in 10 and 12-inch sizes. (Children's records may be smaller). The 33-1/3 RPM records are "long playing" or LP and are also supplied in the two sizes mentioned. The 45 RPM records are made primarily by RCA and are supplied in 7-inch size. Both manual and automatic record players are available with adjustments to permit the use of a single unit for playing at any of these three speeds. The pickup needed varies for the use at these different speeds. At present it is possible to secure a pickup with a single cartridge to serve at all these speeds. A few years ago crystal pickups of reversible type were employed, and you may even find units with two distinct pickups.

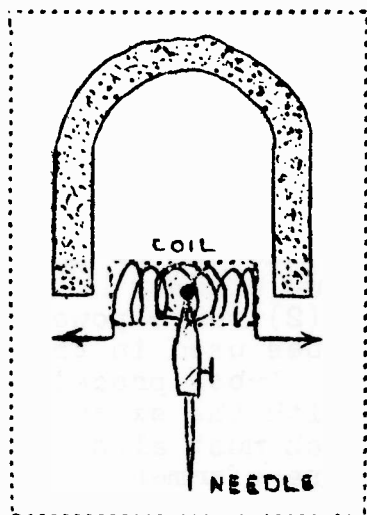


A pickup arm may consist of a permanent magnet within which is pivoted a coil of wire directly connected to the needle. As the needle works along the groove of a record, the unevenness of the grooves sets the needle in vibration. The needle being connected to the coil by mechanical means, the motion is transformed to the coil which in moving cuts the lines of force of the permanent magnet. A current is set up in the coil. This current corresponds to the recorded sound. Crystal pickups working on a different principle are also used.

One of the difficulties encountered in phonograph reproduction is needle-noise. This may be removed to an extent where it may be considered negligent by means of a band filter.

If the source of input is some distance from the amplifier, a line is used for transmission purposes. It is advisable to use

shielded cable for this purpose, thereby reducing the chance of picking up stray currents. Usually by means of transformers the impedance of the connecting line is made equal to 500 ohms. This impedance of 500 ohms is used because many standard audio frequency components are made to match this frequency.

Where the audio power must be reduced in the audio amplifier, this is accomplished with the aid of attenuation networks built up of resistive branches. All circuits possess capacity, inductance, and resistance. Of these three, only resistance does not change over wide limits of frequency and, therefore, must be adapted in the circuit for the purpose of controlling the volume. With this in mind, we may consider for practical purposes an attenuation network to consist of a combination of resistance elements, with one or more variable units. These resistance elements are used to introduce a power loss of value between certain limits when placed in the circuit between some fixed values of input and output impedances. Occasionally circuits are encountered where either or both the input and output impedances are in such a relation to the circuit that variations over wide limits in their impedances will not make a material difference in the operation. Under such conditions, one or both of the impedances may be neglected in designing the volume control network.

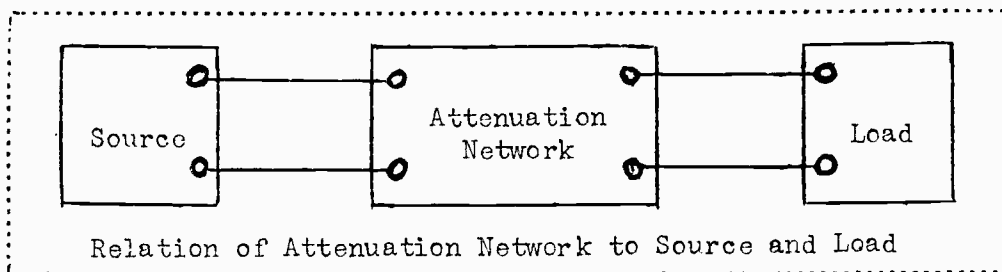

Irrespective of its application, an audio amplifier is used to amplify the frequencies of the audible range. It is possible without imposing too drastic complications to design public address amplifiers to reproduce faithfully to a marked degree audio frequencies between approximately 50 and 12,000 cycles.

Audio amplifiers are entirely dependent upon the use of the vacuum tube as an amplifier. This use falls into two classes (1) where voltage amplification is the object, and (2) where power output with little distortion is desired. Power tubes used in the last stage of an amplifier are of this latter type. Tubes preceding the power stage are primarily voltage amplifiers, with the exception of the driver stage in class "B" type amplifier which must also supply power to the grids of the last stage. The transformer connected between these stages in class "B" amplifier must be designed carefully and possess high efficiency.

The amplification ability of the tube is due to the nature of the construction which causes a small grid potential change to have the same effect upon the plate current as a much larger

plate potential change. The ratio of the change in the plate voltage (E_p) to the change in grid voltage that will vary the plate current (I_p), by an equal amount is called the amplification factor, or the Greek letter μ , as explained in Lesson 9.

The current change in the plate circuit may produce a voltage variation across a resistance, a high impedance, or the impedance of the primary of an audio transformer. With a transformer, it is possible to step up this voltage by a small ratio in the order of 3 to 1, or less. Higher ratios will demand a great deal of inductance for the secondary which will result in large capacity between the turns. This capacity would act as a shunt for high frequencies. Transformers at best can only give partially true reproduction, but may be designed to give only negligent variations in the needed audio range.

With the advent of high gain amplifiers, use of resistance coupling between stages is becoming more and more in vogue, while impedance coupling finds but little present day application. The advantage of "direct coupling" has been surpassed by the high gain tubes. If the plate current is passed through a high resistance connected between the plate and the positive side of the "B" supply, voltage variations are produced in proportion to the changes in the plate current. The voltage drop distributes itself in proportion to the resistance of the tube (r), and the load (R). The voltage amplification is a fraction of μ expressed by the relation:


$$\text{Voltage Amplification} = \frac{\mu R}{R+r}$$

From the above relation it is seen that as the load increases, voltage amplification will approach the amplification factor. The value for best results is usually suggested by the tube manufacturer. The voltage variations are coupled to the grid of the next tube through a condenser of suitable size. This size may be found approximately from the formula below, where R_g is the grid coupling resistor of the following tube, other symbols are explained above. All resistances are in ohms.

$$C = \frac{0.04(R+r)}{R_g(R+r) + rR} \text{ farads}$$

The grid resistor serves to release the electrons that may have accumulated on the grid. If this resistor is made small very little voltage will be impressed upon the grid, if unreasonably large, it will not free the electrons and cause blocking. A suitable value is suggested by tube manufacturers.

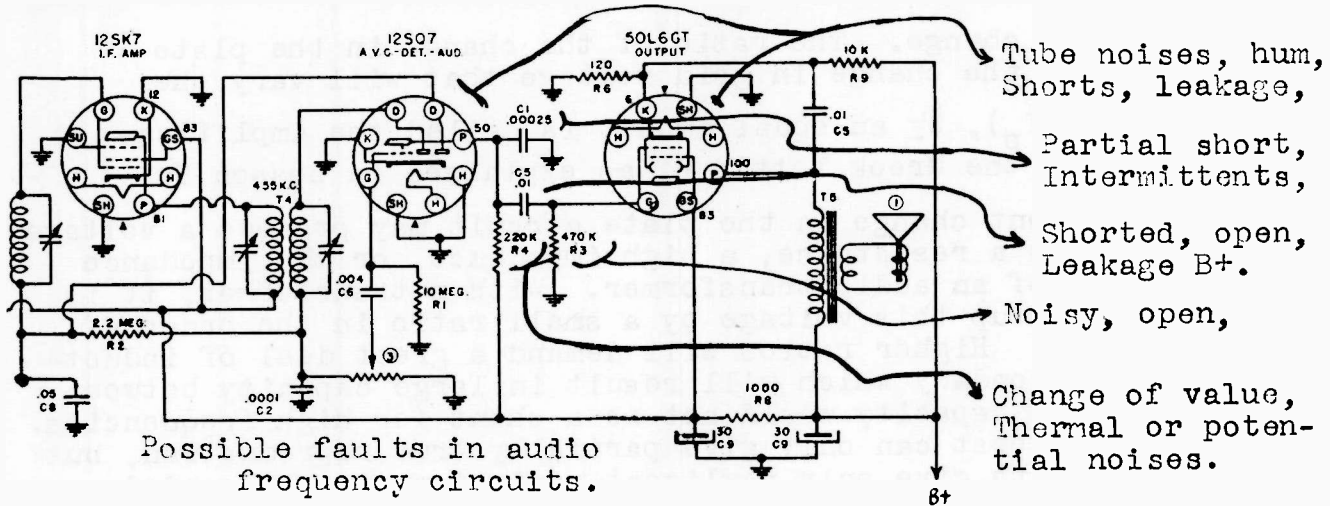The grid of a tube is biased sufficiently negative so that from the practical point of view no current flows in the grid circuit and no power is consumed there. The grid resistor does use some power which may be calculated.




The majority of faults in audio voltage amplifiers lie in the tube itself or in the coupling condenser. Generally, this stage gives little trouble. Plate coupling condensers must be of high quality, since even the slightest amount of leakage may cause the grid of the next tube to become positive.

Since a loudspeaker is an electro-acoustical device, actual power is required to operate it. For this reason, the output stage of a radio receiver uses a tube intended for power amplifier amplification. Such tubes are designed with the object of developing power, in contrast with voltage amplifier tubes in which the object is to obtain as much voltage gain as possible.

Because triode tubes in Class A are commonly used in receivers, and also for reasons of simplicity, we will first consider such an application. For any given operating condition of negative grid bias and a suitable value of plate voltage, the plate current will be of some value that can be measured or found from characteristic curves of the tube under consideration. Without a load in the plate circuit, the plate current would vary as the signal voltage would alter the instantaneous grid potential above and below the fixed bias value. This variation would follow along one of the lines (known as the static characteristic line) of the grid-voltage-plate-current curves.

The connection of a load alters these results. As the grid becomes more negative (on a negative cycle of the signal), the plate current is reduced, but not as much as under the conditions of no load. The reasons for this change is due to the fact that a reduction in the plate current reduces the voltage drop across the load and accounts for a higher voltage at the plate. This higher voltage, of course, to a degree counteracts the plate current reduction. The exact reverse of this action takes place with a positive signal. In such instance, the plate current rises less with a load connected than without.

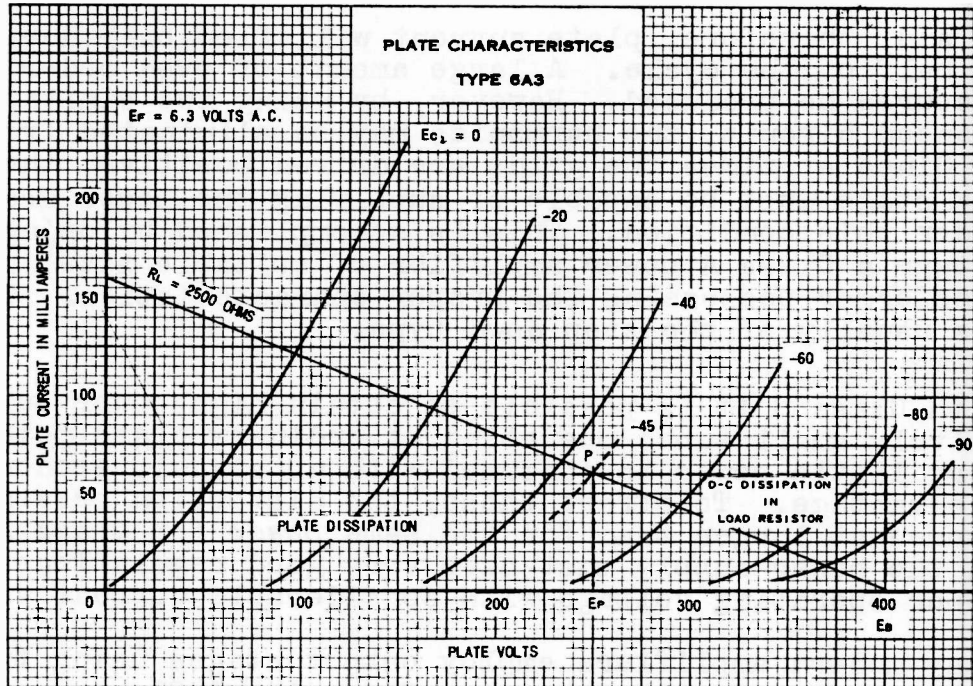The effect of a load is to change the operating line to a line called the dynamic characteristic and having a smaller slope.



The dynamic characteristic is also more nearly linear than are the characteristic curves of the tube. This linear factor is important in minimizing distortion produced by the curvature of the characteristic curve.

To keep distortion to a minimum, the practical limiting factors are the excessive curvature of the dynamic characteristic at low plate currents and the need to keep positive peaks of the signal smaller in value than the negative bias used. This latter fact is important, for if the grid is driven positive, grid current will result and will distort the input signal.

In order to obtain the maximum power output without producing distortion for reasons just stated, it is necessary to maintain a careful balance between grid bias, load impedance, plate resistance of the tube, and plate voltage. For the serviceman, this problem has been solved by tube engineers and tube manuals give the operating information required.

Distortion arises primarily from operating the tube over the curved part of its characteristics. It usually resolves itself into harmonics. Of all the harmonics, the second are of the greatest magnitude. The push-pull amplifier by cancellation reduces the even order harmonics to a very negligible figure, requires less filtering of its plate supply, and permits somewhat larger input voltage without causing distortion due to overloading.

In Class B operation the tubes are biased or designed with a sufficiently high amplification factor to cut off the plate current with no input signal. When a signal sufficient to swing the grid is introduced, the negative portion of the cycle will add only to

the bias and, therefore, plate current will flow only during the positive half of the cycle. A large amount of even order harmonics will of course be produced. However, by using two similar tubes in a balanced circuit, the harmonics may be eliminated from the output. Since at times the grids are driven positive, the preceding stage must be capable of supplying the power drawn by the grids under this condition. This is accomplished by using for a driver stage a Class A power amplifier of suitable size, coupled by a transformer possessing the proper characteristics. The transformer is usually of the step down type.

With Class B it is possible to obtain high power output with comparatively small tubes operating at ordinary plate potentials. Since very little power is consumed with no signal, economy is another advantage. To offset these, the distortion present is always somewhat larger than for the same power for Class A operation and the power supply must have very good regulations to maintain proper operating voltage with considerable current variations.

Many modern amplifiers employ output stages using tubes in an arrangement intermediary between Class A and Class B commonly called Class A-prime or Class AB. On low signals the circuit behaves as a Class A, while on powerful signals the Class B action allows the handling of large power. In this manner, the advantage of both classes is combined.

Because tubes operated in Class B cannot be self biased, it is an advantage to design these tubes so that they take almost zero current at no-signal. If tubes are employed for this class of operation that do require considerable negative grid bias, a separate power supply for this purpose is recommended. While it is best for this additional power supply to have a separate power transformer, the required power may be obtained from separate windings on the power transformer used in the main supply.

It is very difficult to make audio transformers to have uniform response in the audio band. This was the main limitation and served to hamper the popularity of such interstage arrangement. With the high gain triode or pentode type tubes, a much higher plate load is required, and, therefore, a resistor can be employed. While resistance coupling produces a certain loss of voltage instead of gain, the amount lost is easily made up by the higher gain of the tubes employed, and excellent frequency response is obtainable with a simpler arrangement.

With the use of pentodes in the output stage and with the high gain obtainable in the stages of the radio preceding the detector, very little additional audio voltage amplification is needed. In most of the modern sets, this is obtained with the aid of a single triode having a μ of 20 to 100. This triode may be incorporated with a diode detector in a single tube envelope.

LESSON 19

ADVANTAGES OF INVERSE FEEDBACK

A beam power amplifier to be truly modern should incorporate inverse feedback. It is a commonly recognized fact that low plate resistance tubes such as the 2A3 are superior from the standpoint of low distortion and good quality. With inverse feedback the high plate resistance beam power tube may be made to take on the characteristics of the low- μ triode, yet retain most of its high power sensitivity. The important advantages obtained by the use of inverse feedback are fourfold: first, reduction of wave form distortion; second, improvement of frequency response; third, reduction of hum; and fourth, reduction of "hangover" effect. The only disadvantage of inverse feedback lies in the fact that the gain is considerably reduced.

EXPLANATION OF INVERSE FEEDBACK

In the circuit of Fig. 1, a certain amount of the voltage developed in the plate circuit is fed back out of phase with the signal in the grid circuit. If without inverse feedback a certain voltage E_0 is developed across the output circuit with an input voltage E_1 , the gain of the stage is E_0 divided by E_1 . If now a certain percentage N of the voltage E_0 is fed back to the grid circuit in such a way that the voltage is out of phase with the input voltage E_1 , the total input voltage to obtain an output voltage of E_0 is $(N E_0 + E_1)$ and

the gain of the stage is $\frac{E_0}{(N E_0 + E_1)}$. The

ratio N is the percentage of the output voltage which is fed back to the input circuit. It may be readily seen that if N is large the gain of the stage depends more upon N than upon the circuit constants.

The ratio reduction in gain by the addition of inverse feedback may be readily determined by dividing the gain without feedback by the gain with feedback.

REDUCTION OF DISTORTION

As was pointed out in the above paragraph, an inverse feedback circuit feeds back a certain portion of the output voltage to the grid circuit. If distortion is introduced in the amplifier stage a certain amount of the distorted voltage will be fed back into the grid circuit and this will tend to cancel out the distortion developed

in the amplifier stage. If in the circuit of Fig. 1 a certain amount of distortion voltage B is present in the output circuit the distortion voltage fed into the grid circuit will be $N \times B$ and this quantity multiplied by the gain of the stage will give the cancelling effect of the inverse feedback. The total distortion present in the output is then equal to the sum of the distortion without inverse feedback and the distortion cancelled by the inverse feedback. In other words, if b is the distortion without inverse feedback, the total distortion, B , with inverse feedback is equal to $(b + B) \times N \times A$, where A is the gain of the stage. Evaluating B gives the quantity

$\frac{b}{1 + NA}$. In other words the distortion

is reduced by the ratio of $\frac{1}{1 + NA}$.


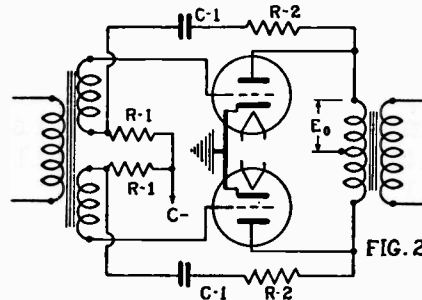


Fig. 2 shows the ordinary method of obtaining inverse feedback with the resistor-condenser method. The amount of inverse feedback is equal to $\frac{R_1}{R_1 + R_2}$ assuming

that the reactance of the condenser C_1 is negligible over the operating frequencies. However, this assumption is not necessarily true especially at the lower frequencies and the circuit of Fig. 3 is much more efficient from this standpoint. In Fig. 3 the feedback voltage is obtained from a tertiary winding on the output transformer. This method also provides a much better overload characteristic since the resistance in the grid circuit is negligible and it is quite possible to operate the tubes in the grid current region.

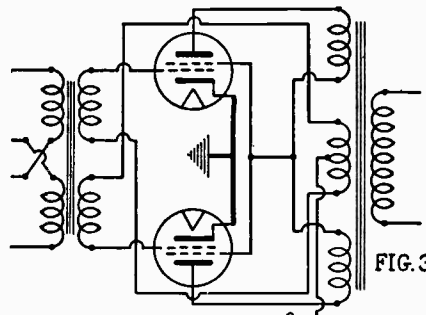

REDUCTION OF PLATE RESISTANCE

In addition to the reduction in distortion obtained by inverse feedback, there is also a reduction in the plate resistance of the tubes. A high plate resistance is a definite disadvantage in the case of a power tube which operates into a speaker load which is more or less variable depending upon the impedance of the voice coil. In the circuit of Fig. 4, it may be easily seen that the voltage E developed across the load depends a great deal upon the actual value of R_L which is the reflected impedance of the voice coil. This is due to the fact that the signal current depends almost entirely upon the high plate resistance of the tube. Since the load resistance is low in comparison to the plate resistance, the voltage developed across the load is almost directly proportional to the impedance of the load which varies appreciably with change in frequency. In Fig. 5 it may be seen that the voltage across the load does not vary so much since the signal current depends both upon the load and upon the plate resistance of the tube. If the voice coil has an appreciable amount of reactance the impedance rises with the frequency causing distortion and giving an unnatural amount of "highs." The high plate resistance is unsuitable from another view point, that of low frequency distortion which may be tolerated. This low frequency distortion is not


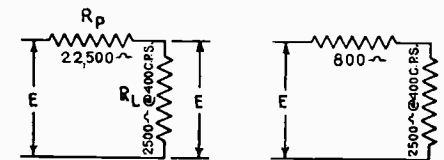


FIG. 4




FIG 5

due to the characteristics of the tubes which remain unchanged regardless of the frequency, but depends upon the magnetizing current in the output transformer. The magnetizing current is a distorted non-sinusoidal wave and this current, on flowing through the high plate resistance of the tube, develops a nonsinusoidal voltage drop across the tube which, when subtracted from the input signal, results in a distorted wave across the output. Unfortunately, most amplifiers today are measured for distortion at 400 c.p.s. where the magnetizing current is practically negligible. It is not uncommon to find beam power amplifiers without inverse feedback which have only 25 per cent of the rated power at 40 or 50 cycles. This low frequency distortion is particularly objectionable since all harmonics fall within the audible range. Inverse feedback effectively reduces the plate resistance so that the distorted voltage drop caused by the magnetizing current is exceedingly small with the result that there is very little distortion across the output circuit.

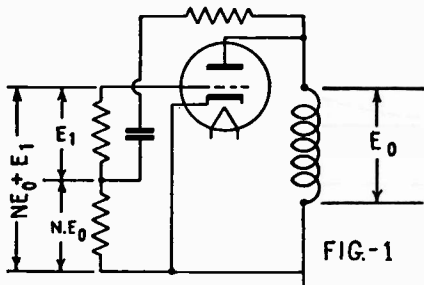

Electrodynamic & Magnetic Speakers

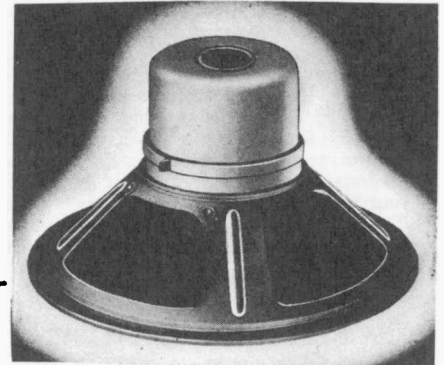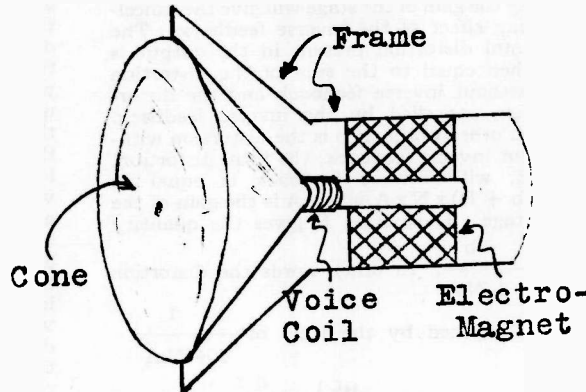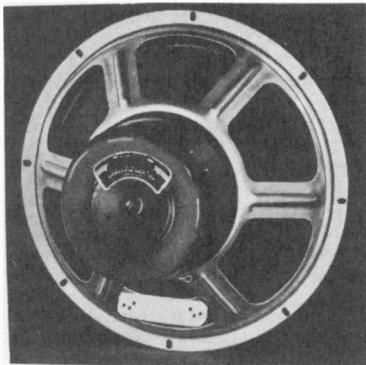
After the audio signal in electrical form is amplified, it must be changed to actual sound. The loudspeaker changes this electrical energy to acoustical energy. A magnetic field is required by all types of modern dynamic speakers and is provided by an electromagnet (field coil) or by a strong fixed magnet in the permanent magnet (P.M.) type speakers.



In the dynamic speaker a small cylindrical coil (voice coil) is attached to a paper cone. The coil is suspended in a strong magnetic field and carries the impulses from the radio set's or amplifier's output. The voice coil will move in accordance with the signal and will vibrate.

Minor troubles found in speakers can be repaired. A voice coil that touches the pole piece should be repositioned. Cone cement used can be loosened with acetone or special cement solvent. Small rips or tears in a speaker cone can be patched with cone cement. Scotch tape may be used for a temporary repair.

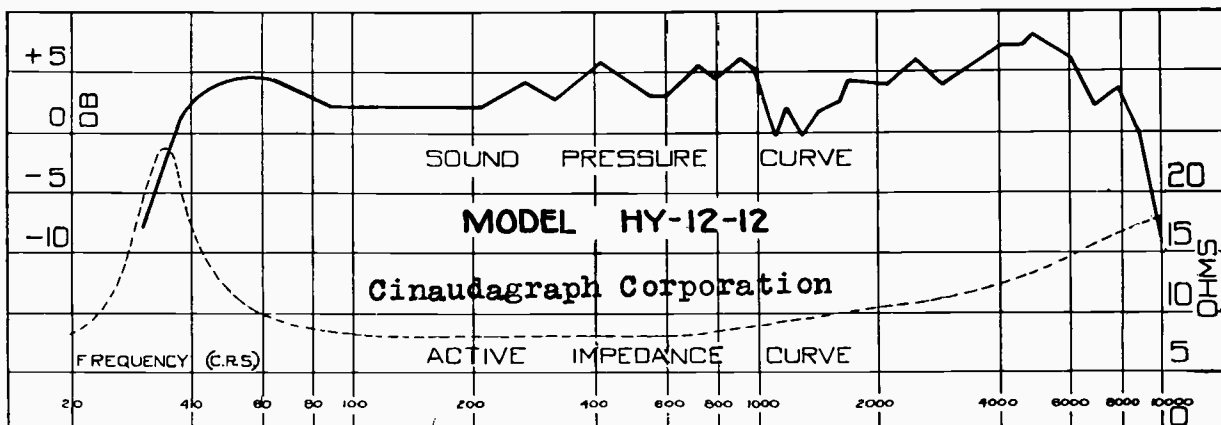The chart below will give you an idea of the response of a good quality 12-inch speaker. Also notice the dotted curve which indicates the change of the voice coil impedance.



LOUDSPEAKER SELECTION - PLACEMENT

In all Public Address installations, loudspeakers are more than just an accessory of the system; they must be considered as the all important devices used to convert the electrical audio output to the needed acoustical energy — sound. The speakers of any well matched sound system are selected with care so that the response characteristics and power handling ability will give the desired results with the associated equipment. But the proper placement of the speakers and the use of correct baffles or directional horns is necessary to permit the P.A. engineer to secure the best results from the sound system in any particular installation. Just as poor placement of speakers may ruin the response from the highest quality equipment, so can moderate cost equipment be made to perform wonders when the speaker placement is correctly made along scientific lines.

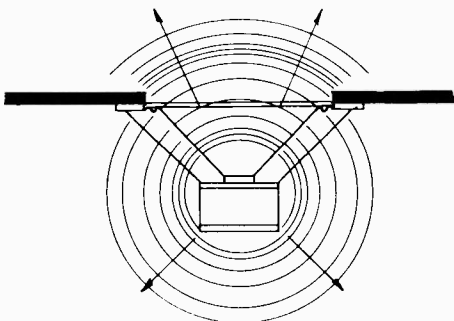


Figure 1. A cross section of a speaker mounted in a baffle. Note how the baffle prevents the inter-action of the waves set up by the front and rear of the cone.

The speakers must always be used with some form of baffle to prevent the tendency of the front and rear sound waves from cancelling-out each other. (Fig. 1) If the baffle were omitted, sound compression produced in front of the speaker cone, when the cone moves forward, would cause the air to rush around the edges and relieve the rarefaction in the rear. To be equally effective to the middle and lower frequencies a baffle must be fairly large. In practice a 6" or 8" speaker will require a baffle with 40 inch sides.

A speaker mounted in a flat baffle made of ply-wood, celotex, or masonite will radiate sound almost uniformly in all directions. If the installation requires the projection of the sound forward, directional flares or special horn baffles must be employed. The Oxford Exponential Horn XA22 is ideal for this purpose. It gives the desirable directional effect, and has great volume-handling ability. (These exponential horns are supplied with either Permag or electro-dynamic trumpets).

NUMBER OF SPEAKERS TO USE

In average installations it is best to use one or two speakers. A single speaker such as Oxford type 110C or 11WMP will serve in class rooms, hallways, small stores, and in almost all other installations requiring less than 10 watts of power. For auditoriums, churches, gymnasiums, dance halls, two speakers of good quality should be able to handle the audio volume from amplifiers supplying 15 to 35 watts. These speakers must have a conservative power handling capacity of at least 18 watts each. For use with amplifiers supplying greater power, employ directional trumpet speakers or at least four well made 12 or 14 inch dynamics.

PLACEMENT FOR NATURAL RESPONSE

The speaker location is selected with two objectives in mind: (1) to make the program sound natural to all present, and (2) to reduce the possibility of acoustical feedback. The loudspeakers should be placed so that sound originating from the actual source (be it a singer or a complete orchestra) and the sound emitted by the loudspeakers should reach the majority of the audience at the same instance. (Fig. 2) This is why two speakers are used in auditoriums and dance halls,

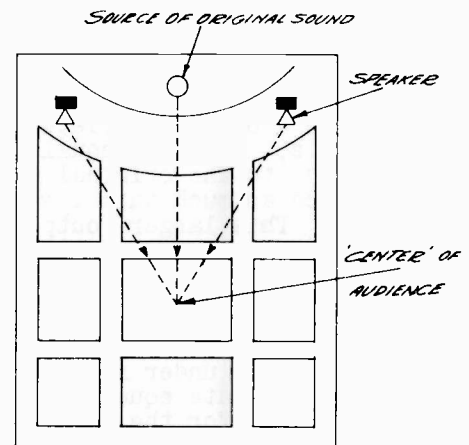


Figure 2. The speakers should be placed so that the majority of the listeners will hear the original and reinforced sound at the same instance.

one on each side of the stage. This type of installation permits the original sound to be supplemented or reinforced by the amplified output. It certainly would not do to have a single speaker in the back section of a long and narrow hall. Under such a condition, the listeners sitting in the first front rows and those in the extreme rear would hear the original sound and the amplified sound at a considerable time interval.

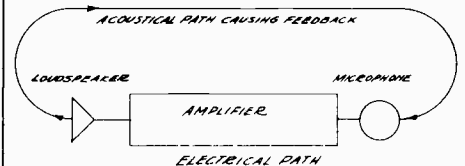


Figure 3. The acoustical return of sound causes feedback.

FEEDBACK PROBLEM

In all installations, some of the sound emitted by the loudspeakers will reach the microphone of the system. Feedback will result if the sound reaching the microphone is greater in intensity than the original sound input. (Fig. 3) Consider for example a typical auditorium with an orchestra playing. A definite sound level produced by the instruments of the orchestra is picked up by the microphone. After amplification, a correspondingly higher power level of sound is emitted by the

loudspeakers. Of course, the actual ratio of the input to the output power is the net gain of the amplifying equipment at the volume control setting employed. Now if the sound coming back to the microphone, either through direct radiation or by reflection from walls, is about equal in intensity to the original input, twice as much output will result. This larger output will in turn cause twice as much sound energy to be returned to the microphone and again the output level will be doubled. This doubling process will continue, under such condition, at a rate equal to the time required for the sound to pass acoustically from loudspeaker to microphone and electrically through the amplifying equipment. In several seconds the amplifier will be overloaded, and a continuous loud whistle will be the only output present.

Should the sound returning to the microphone be greater in intensity than the original, the feedback action will start just so much faster. If the sound intensity is but a little less than the original input, a hang-over effect or echo will be present. All these conditions are equally bad and can successfully be eliminated.

Reduction of amplification will always solve the feedback problem. But this is a poor solution, since the output in majority of cases must be reduced to so low a point that the sound system no longer serves its purpose. In some installations certain groups of frequencies are the only cause of feedback. Perhaps this is due to greater amplification at these frequencies or to the resonant effect of the room. Tone control adjusted to reduce the gain at these frequencies will eliminate the feedback due to this cause. But this, too, is a make-shift solution, for the tone control adjustment not only may solve the feedback problem, but also may distort the natural qualities of the program.

The way to eliminate feedback is to prevent sound from the speakers reaching the microphone of the system. If the speakers are focused in a direction away from the microphone, direct feedback will be

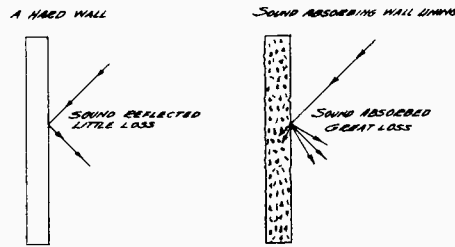


Figure 4. To prevent sound emitted by the speakers from reaching the microphone, sound absorbing materials are used.

eliminated. However, sound reflected from walls, ceiling, and floor will reach the microphone. The sound in being reflected, loses some of its energy, so that in striking several walls in its return path to the microphone, the sound intensity may be reduced to a low value where it will no longer create any feedback. (Fig. 4) Since sound-absorbing materials deaden the sound and absorb its energy, the use of carpets, heavy curtains and drapes, and special sound-absorbing materials strategi-

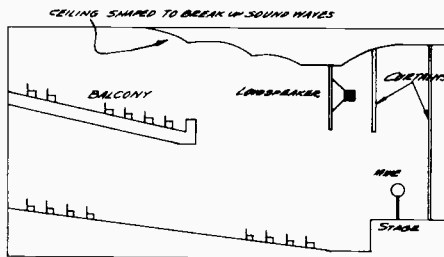


Figure 5. In an auditorium the speakers should be above and in front of the microphone. The curtains should be down as much as possible to serve as sound traps.

cally placed will permit the use of the Public Address system at the required volume level without encountering feedback.

Practically every school auditorium is or soon will be equipped with sound amplifying equipment. Here the correct placement of speakers is a simple matter. Two speakers of the 12 inch size should be used.

These speakers should be placed on the two sides of the stage, and directed outwards. The speakers should be well in front of the microphone and should be enclosed in suitable baffles. (Fig. 5) The sound should be emitted in front only. If the auditorium is small, non-directional baffles will serve. The curtain in back of the stage should be lowered to eliminate sound reflection. If the walls are of hard material and this type

of installation does not completely eliminate the feedback problem, a directional microphone may be used or the speakers may be moved a little more forward and the front curtain lowered a little.

A well decorated square shaped room, 40 by 60 feet, serves as a dine-and-dance club. On a stage placed alongside one of the longer walls is the orchestra. When the orchestra plays softly, the

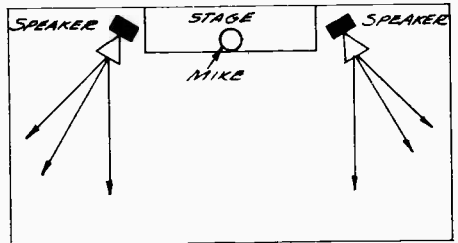


Figure 6. This simple but correct installation solved the problem of the night-club.

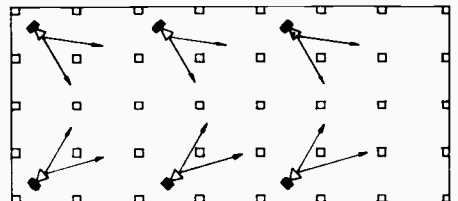


Figure 7. Even a factory paging system can present difficulties unless the speakers are correctly placed.

music cannot be heard in the extreme corners away from the stage. Loud playing proves uncomfortable for the patrons near the stage. (Fig. 6) Experimentation with a small 8 watt sound system shows that speakers placed in the far corners facing the stage create feedback. By using two semi-directional speakers placed above the stage and faced towards the extreme opposite corners, the problem is solved.

In a large factory located on a single floor, speakers used in a paging system were spread out at random. Difficulty was experienced in understanding the calls and announcements. This was caused by the sound from several of the speakers reaching the same individuals. By using directional speakers, and facing them in such directions that the sound from any two did not interfere, the difficulty was eliminated. (Fig. 7)

LESSON 20

MATCHING SPEAKERS TO THE P.A.

The correct selection of the speakers for any public address installation depends on the equipment used, results required, and the acoustics and size of the location. These determining factors are closely inter-connected and must be considered together in selecting the type and number of loud speakers to be employed.


The number of speakers used will depend primarily on the installation; perhaps only two speakers will be needed in a school auditorium, but several dozen may be used in a complex paging system. In any one enclosed hall or room, as few speakers as practical should be used. This suggestion, however, cannot always be followed, since the speaker efficiency is highest when the speaker is operated well under its maximum rating. Also, at times the installation calls for so much power that a great many speakers must be used. Bearing in mind that no one rule will really serve in all cases, the P.A. specialist may depend on the table given for correct information for every regular installation. (See Table 1.)

No matter if you use a single speaker or have a complicated network, the speaker load should be correctly matched to the amplifier output. For maximum power transfer and minimum added distortion, the load impedance, Z, must equal the output impedance of the amplifying system. Two forms of mismatch may occur -- the load may be higher in value, or the load may be lower. In both instances a power loss will occur -- less than the maximum amplifier power output will reach the speakers, and there will also be a loss of quality.

Small errors in matching are not important as is evident from Table 2.)

The commercial amplifiers provide several different output impedances in the most commonly required ranges. For example, one unit may have taps at 4, 8, 16, and 500 ohms. When speakers are used at a distance from the amplifier, the speaker line is usually connected to the 500 ohm tap, and the speakers with line transformers are connected together to match this impedance. If the speaker is near by, within 50 feet, the voice coil may be directly connected to the nearest value tap. Let us now consider the problem where several similar speakers are to be connected together.

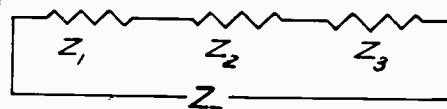In connecting impedances in series, the individual impedance values are simply added. (See Chart 1.)




$$Z_T = Z_1 + Z_2 + Z_3 + \dots +$$

Chart No. 1.

In connecting several equal impedances in parallel, the resulting impedance is found from the formula (See Chart 2.) where Z is the value of one of the impedances used and X is the number of impedances in parallel.

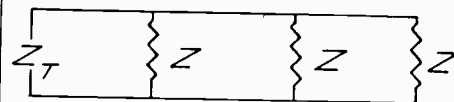In using two 8 ohm voice coil speakers, the connections



$$Z_T = \frac{Z}{X} \quad \text{Chart No. 2.}$$

may be made in series or in parallel. In the series circuit the resulting impedance is 16 ohms; in parallel, 4 ohms. It is better to use parallel connection, as an open voice coil in a single speaker in the series circuit will stop the entire service of all speakers.

TABLE 1.

Type Of Application	Room Size Cu. Ft.	People Present	Noise Level	Power Needed (Watts)	Number Of Speakers Needed	Size Of Speakers	Oxford Type	Type Of Baffel
Hospital Room-Paging	4,000	6	Very Quiet	1/4	1	6 1/2"	6XMC	Cabinet
School Room	8,000	48	Quiet	1	1	8"	8WMC	Cabinet
Office Inter-Comm.		1	Average	1	1	5"	5XMP	Cabinet
Small Restaurant	10,000	25	Noisy	3	1	12"	12WMP	In Grill Work
Funeral Home	25,000	100	Quiet	3	2	12"	12WMP	Flat Baffels
Window Ballyhoo	Open Air	25	Noisy	8	1	12"	12DMP	Semi-Directional
Factory Paging	150,000	50	Noisy	25	4	8"	8WMC	Cabinets
Auditorium	150,000	600	Quiet	25	2	14"	14DMP	Semi-Directional
Street Advertising	Open Air		Very Noisy	30	2	Horn	6DMP	Directional Horns
Large Stadium		10,000	Noisy	60 to 100	8	14"	14DMP	Direction Horn and Baffels

Speakers may also be connected in series-parallel arrangement, so that the resulting impedance will match one of the output taps. For example, four 8 ohm voice coil speakers may be connected in a fashion to give the equivalent impedance of 8 ohms. (See Chart 3.)


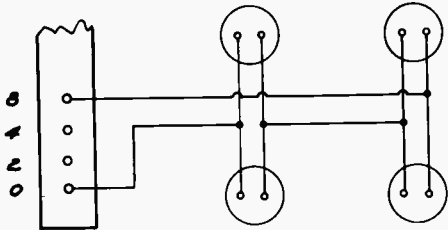


Chart No. 3.


So far, we were mainly interested in properly matching the output to the speakers employed and we assumed that the volume level at all speakers was to be the same. There are installations, however, that, while using speakers of one type, must have the speakers operate at different volume levels. For example, the speakers of a paging system must have their volume level of intensity to serve the different locations -- and probably every place has a different noise level. Just how can this variation of sound intensity be accomplished and yet match the network to the amplifier output?

The first important rule to remember is that it is immaterial how the speakers are connected; if the equivalent impedance is correct, good matching will result. As an example, we may consider a food market installation with two 8 ohm voice coil speakers inside, and another similar speaker outside. The outside speaker is to be operated at about four times the power level of either inside speaker. To accomplish this the speakers may be connected in the

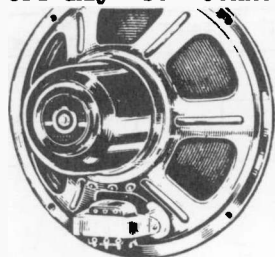

The complete line of electrodynamic and P.M. type speakers includes 14 inch Auditorium Models, also many smaller sizes especially designed for P.A. work. From these, the sound engineer can at all times select the best reproducer for the job.

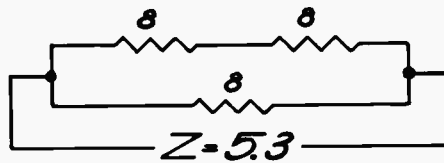following manner. The speakers used indoors are connected in series, giving the equivalent 16 ohms. This combination in turn is connected in parallel with the 8 ohm speaker placed outside, and gives the equivalent 5.3 ohms. The 4 ohm impedance tap of the amplifier used will give good results as there will be only a trivial loss. (See Chart 4.)



$$\frac{16 \times 8}{16 + 8} = \frac{128}{24} = 5.3$$

Chart No. 4.

It is evident that the voltage across each branch is the same, but the current through the single speaker will be twice as great as the current present in the branch having two similar speakers. Therefore, the single speaker placed outside of the store will have twice the power of the two other speakers combined -- or four times the power of each speaker placed inside.

The speakers used, of course, need not be all the same. For another ex-

ample, consider the school installation with 8 inch speakers in eight different school rooms, two 14 inch Oxford 14DS-TLL speakers in the auditorium, and one exponential horn in the gymnasium -- all speakers equipped with Universal 500-1000 ohm transformers. The sound level needed in each of the rooms is 1½ watts, in the auditorium 20 watts total, and in the gymnasium 10 watts where the exponential horn trumpet will serve. The units may be hooked-up in the manner shown, and a study of the circuit will show that the right match with the required power at each point is obtained. The amplifier, of course, must supply 40 watts.

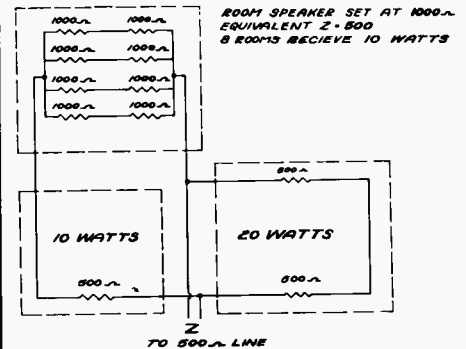


Chart No. 5.

In a similar manner any complex speaker installation may be designed to give optimum results and produce just the right amount of audio power at each speaker.

TABLE 2

ERROR IN MATCHING OUTPUT Z LOAD Z	APPROXIMATE LOSS OF POWER IN DB	APPROXIMATE LOSS OF POWER IN %	APPROXIMATE EFFECT ON QUALITY AND SENSITIVITY
.5	.5	11	NOTICEABLE
.6	.35	7	SLIGHTLY NOTICEABLE
.7	.2	4	BARELY NOTICEABLE
.8	.1	2	BARELY NOTICEABLE
.9	.05	1	NEGLIGABLE
1.0	0	0	NONE
1.25	.05	1.5	NEGLIGABLE
1.50	.2	4	BARELY NOTICEABLE
1.75	.35	7	SLIGHTLY NOTICEABLE
2.0	.5	11	NOTICEABLE

EFFECT OF MISMATCHING SPEAKERS TO AMPLIFIER OUTPUT

A great deal of stress has been placed on the necessity of exact matching from source to load. While this generally holds true when the mismatching is considerable, a slight mismatch is not serious. This is quite obvious by referring to the chart.


In order to properly determine correct matching, the impedance of the voice coil must be known. This impedance is not a constant figure, but varies with frequency. For all general applications, however, the impedance is measured at 400 cycles. In the event that the impedance of a speaker is not known, the approximate value can be obtained by multiplying the DC resistance by a factor of 1.25.

To consider the usefulness of the graph, let us take the problem where the only speaker available is one with a 6 ohm voice coil, and the amplifier output is available in either a 4 ohm or 8 ohm tap. The ques-

tion in this case is what tap on the amplifier will give the best results. The ratio of $\frac{Z_{\text{output}}}{Z_{\text{load}}}$ in the case of the 4 ohm tap is .666, and in the case of the 8 ohm tap is 1.33. In checking these figures on the graph, we find that in the case of the 4 ohm tap where the ratio is .666, the loss is approximately 4%, and similarly, on the 8 ohm tap, the loss is only 2½%. It is quite obvious that the best results will be obtained if the speaker is connected to the 8 ohm tap. Generally, the results are better if the speaker is mismatched to a higher rather than a lower impedance.

However, if the speaker has only a 2 ohm voice coil, and the only tap available on the amplifier is 8 ohms, the ratio of the two impedances is 4. From observation on the graph, the loss is 35%, which is quite serious and this mismatching is not recommended.

Courtesy Oxford-Tartak Radio Corp.

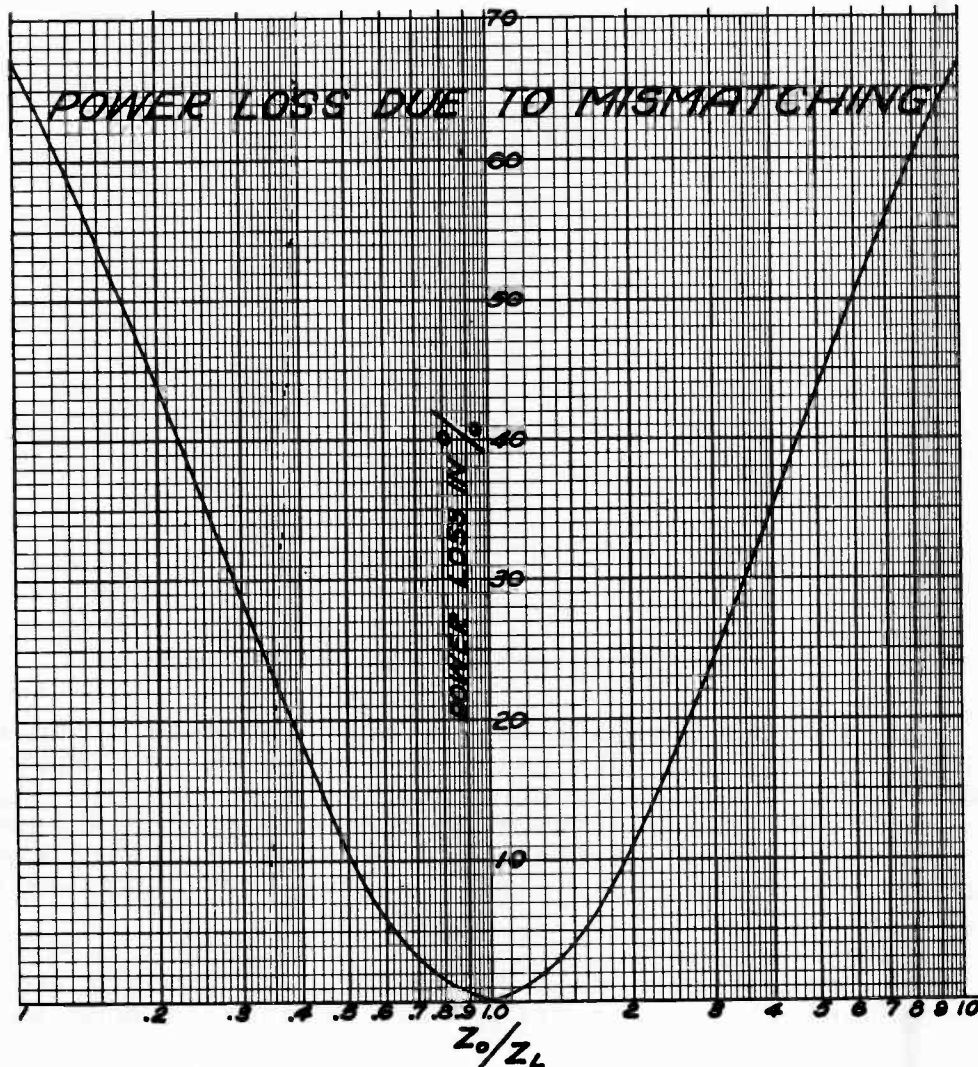

T H E D E C I B E L

Of all units in radio the least understood and most often misused is the decibel. The decibel, abbreviated as DB, is a unit of comparison of two powers and under proper consideration may be used to compare currents and voltages. It is the transmission unit used to measure power related in some way to the auditory sense. The DB is a logarithmic unit in so much as it varies as the log of the ratio of the two powers in comparison.

$$DB = 10 \log_{10} \frac{P_1}{P_2}$$

The mathematical formula above states the relation that the log to the base ten of the ratio of the two powers, multiplied by ten will give the difference between the two powers in decibels.

The difference in decibels may also be found from the table below if the ratio of the two powers under consideration is known.

Gain in DB	Power Ratio	Loss in DB	Power Ratio
40	10,000	0	1.
35	3,162	1	.8
30	1,000	2	.6
29	800	3	.5
26	400	4	.4
23	200	5	.32
20	100	6	.25
15	32	7	.2
12	16	8	.16
10	10	9	.12
9	8	10	.1
8	6.3	11	.08
7	5	13	.05
6	4	15	.03
5	3.2	17	.02
4	2.5	20	.01
3	2	25	.003
2	1.6	30	.001
1	1.3	35	.0003
0	1	40	.0001

Since DB is always a ratio, when we speak of an amplifier as having so many decibels gain, we assign an arbitrary level of comparison. Usually 0.006 watts is taken as this figure. If one amplifier has a gain of 75 decibels in comparison with a given arbitrary level, while another has 60 decibels when compared to the same level, the first has (75 - 60) or 15 DB more gain.

The transmission unit is employed to express any ratio of power, mechanical loss or gain, etc. related in some way to the auditory sense.

LESSON 21

FREQUENCY MODULATION


This material on frequency modulation is reprinted through the courtesy and cooperation of Westinghouse Electric Corporation and is copyrighted by that organization. The subject matter is divided into three convenient sections dealing with (1) Band Location and VHF Characteristics, (2) F. M. Receiver Fundamentals, and (3) F. M. Receiver Alignment and Trouble Shooting. This is a good way for treating this subject from a serviceman's point of view.

As an introduction to F. M., let us review briefly the difference between amplitude and frequency modulation. In amplitude modulation, as you probably know, there are two side bands. At any one instance, if the transmitter is amplitude modulated with a single frequency sine-wave at that moment, the energy radiated is made up of the carrier frequency and the two side bands. The frequencies of the side bands shift together and these side bands are always apart from the carrier by an equal number of cycles. Since both side bands have their frequencies equal to the carrier frequency plus the modulating audio frequency for one and the carrier minus the audio frequency for the other, the frequencies of the two side bands shift together, in opposite directions, from moment to moment as the modulating audio frequency changes.

Now let us consider a carrier which is frequency modulated. It is possible to swing the frequency by different amounts. The amount of frequency shift will determine the amplitude of the audio signal at the detector, while its "rate of change" or speed determines the audio frequency. Such a signal can be shown to consist of a carrier plus an infinite number of side bands. The side bands are produced in pairs, symmetrically placed with respect to the carrier and they are separated by the amount of the modulating frequency. A carrier of 1,000 KC. being frequency modulated at 1,000 cycles (i. e. 1 KC.) would have side bands at 1,001, 1,002, 1,003, etc., as well as at 999, 998, 997 KC., etc. When the carrier is being swung, for instance 10 KC. to either side, the side bands situated between 990 and 1,010 KC. only are of importance, the others above and below these extremes becoming very weak. Therefore, the practical band-width of a frequency modulated signal is equal to twice the frequency deviation employed and has no connection with the audio frequencies transmitted.

The material on F. M. Band Location and Very High Frequency Behavior begins on page 207.

PORTION OF THE RADIO SPECTRUM

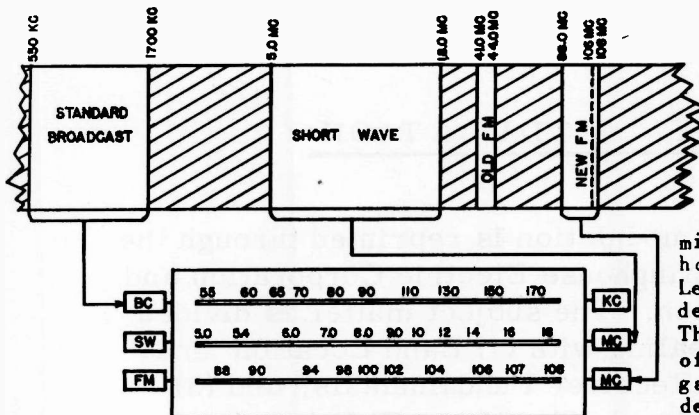

SLIDE 1

H-119 DIAL

(1-1) The present carrier frequency band assigned to FM extends from 88 to 106 megacycles. The 106 to 108 megacycle range, which also is included on our FM receivers, is set aside for facsimile and is, so far as we are aware, not in general use at this time. Slide 1 shows the spectrum location of the new VHF FM and facsimile bands with respect to the standard broadcast and short wave band. The old prewar FM band from 41 to 44 megacycles also is shown in the spectrum for comparison purposes. The dial scale shown in

this slide is that of the Westinghouse Model H-119 AM-FM radio and phonograph which is to be discussed in this lecture.

(1-2) As slide 2 shows, at this very-high-frequency range, propagation of radio waves tend to follow more or less optical laws as compared with the standard broadcast range from 540 to 1600 kilocycles used in present-day AM systems. Briefly, this means that the radio waves act somewhat like light waves and "line-of-sight" wave propagation plays an important part. Under ideal conditions the terrain between the transmitting and receiving antennas should have no continuous obstructions such as large buildings, hills, etc. In actual practice ideal conditions are seldom realized. Frequently, very good FM reception may be obtained under conditions which according to the "line-of-sight" theory would make reception impossible.

According to the accepted theory, the electric field intensity of the FM wave varies inversely with the square of the distance from the transmitting antenna to the receiver. For production of a true frequency modulated signal to be passed on to the discriminator in the receiver, a good husky signal at the limiter grid is

an absolute necessity. Unless there is a signal of sufficient strength to saturate the limiter, amplitude signals will be passed on to the discriminator, resulting in very poor tone quality and distorted output. This requirement practically dictates the use of a good, well-elevated outside antenna.

(1-3) FM Antenna Fundamentals.

At first glance the design of a suitable antenna for receiving FM waves might seem a very simple problem. Actually, however, a number of factors are involved. Let us examine these factors from the practical design standpoint.

The antenna input impedance determines the value of the r-f voltage developed across the dipole gap (load impedance) inasmuch as the voltage developed is determined by the values of the current flowing and the load impedance at that particular instant. It may be expressed mathematically by ohm's law for alternating current:


$$E = IZ \quad (1)$$

Where E and I are the r-f voltages and currents, respectively, and Z is the impedance at the center of the dipole at any given instant. The impedance may be expressed as

$$Z = \sqrt{R^2 + X^2} \quad (2)$$

Where R and X are the antenna input resistance and reactance, respectively.

In a half-wave antenna, resonant to a fixed frequency, the current is a maximum at the center and zero at the ends, while the voltage is a maximum at the ends and a minimum at the center. For this half-wave resonant dipole, then, the impedance varies along the antenna and is minimum at the center and maximum at the ends. For a half-wave dipole, resonant and isolated in free space, the impedance at the center is approximately 73 ohms and approximately 2500 ohms at the ends. The intermediate points between the center and each end have intermediate values of impedance. The 73 ohms impedance at the center represents the vector magnitude of the effective resistance

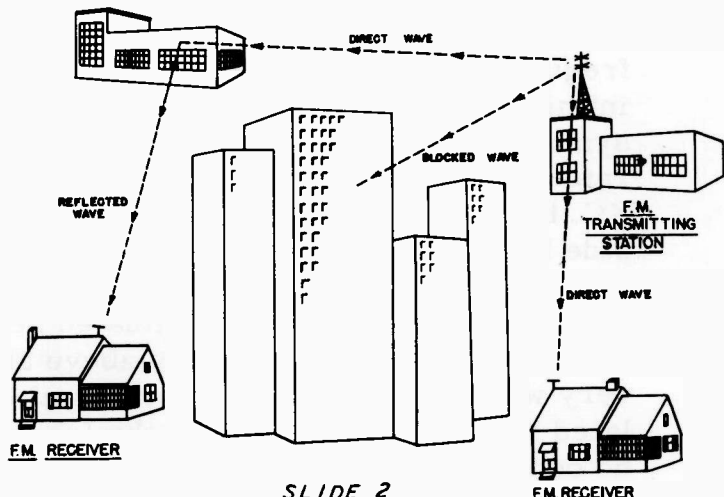

SLIDE 2

and a small residual reactance; however, for all practical purposes it may be considered a pure resistance. For single, fixed frequency operation, then, the transmission line should present a characteristic impedance to the center of the dipole, equal to the dipole center impedance, or, in other words, the characteristic impedance of the transmission line should be 73 ohms. But wait! Don't jump to any conclusions! We are now talking about a half-wave antenna resonant to a single frequency. For FM we have entirely different conditions.



The FM signal is constantly shifting in frequency with applied modulation. So far as the impedance value is concerned, the effect is exactly the same as would be encountered if the frequency were fixed and the length of the dipole were varied. At frequencies higher than the resonant frequency of the antenna, the dipole acts an inductive reactance and at frequencies lower than its resonant frequency it acts as a capacitive reactance. Remember

that the center impedance value is equal to the square root of the sum of the squares of the resistance and the reactance. In short, as the signal frequency swings back and forth across resonance, the impedance value "travels" up and down its scale of values for the single FM signal. Furthermore, we are not interested in receiving only one FM station--we wish to receive stations all the way across the FM band. Various schemes have been brought forth for leveling out the extreme impedance values encountered at the band edges but most of these systems are too costly for anything other than certain commercial applications. For ordinary FM reception, a good compromise can be effected by making the dipole elements large in diameter, overlapping them slightly at the center and selecting the correct resonant frequency length.

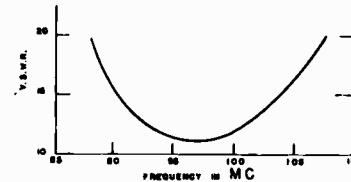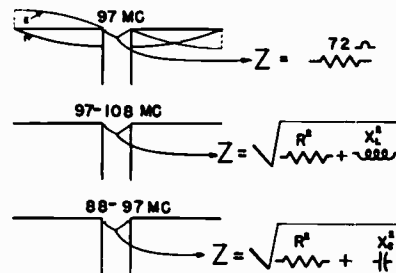(1-4) Determination of FM antenna length. If reception of programs from only one FM station is desired, the dipole elements would be cut to a half-wave length at the center or unmodulated carrier frequency according to the formula:

$$\text{Length of half-wave (inches)} = \frac{5540}{\text{Freq. (mc)}} \quad (3)$$

In a practical installation, however, reception of more than one FM station is desired. This means that the length of the elements must be cut to some intermediate frequency which will give a satisfactory response at the extreme ends of the band and yet keep the standing wave ratio (mis-match) of the transmission line between the dipole and the receiver input, to the minimum. In general, the frequency to which a broadly resonant antenna is cut, is equal to the geometric mean of the frequency extremes of the band to be covered.



VOLTAGE STANDING WAVE RATIO VS FREQUENCY
WESTINGHOUSE STRATOVISION
F.M. ANTENNA

SLIDE 3

For the 88 - 106 megacycle band, the frequency at which the antenna should equal one half-wave is

$$\text{Frequency in Megacycles} = \sqrt{88 \times 106} = 97 \text{ mc. (4)}$$

The actual length of the elements, in inches, according to the above formula, is


$$\text{Length} = \frac{5540}{97} = 57.1 \text{ inches}$$

Like most other practical applications of electrical theory, however, it is necessary to modify the actual element length for maximum efficiency across the FM band. In order to obtain a semi-broad-band characteristic in the Westinghouse Stratovision FM antenna, the two elements overlap at the center insulator. It was found necessary to increase the overall dipole length, end to end, to 62 inches to compensate for this physical characteristic.

(1-5) FM dipole antenna transmission line characteristic impedance. As mentioned above, the impedance at the center of an FM receiving dipole antenna cannot be stated as any given value. In actual practice it varies anywhere from 68 ohms to 1000 or 1500 ohms depending upon the length and diameter of the dipole elements and the portion of the FM band to which the receiver is tuned. It is obvious that no fixed value of transmission line impedance can be selected and matched to the center of the antenna. It is necessary to select some "happy medium" value which will operate most efficiently over the entire FM band. Due to the rather high standing wave ratios encountered at the band extremes, the transmission line must present very low-loss characteristics in the VHF range. Recent developments in low-loss transmission lines include a spaced, polyethylene-insulated, two-wire line of 300 ohms characteristic impedance. In tests with the Westinghouse Stratovision FM antenna, it was found

that maximum signal level at the receiver input terminals was obtained with this new "twin-lead" line as compared with standard 50 and 70 ohm coaxial and twisted pair lines. In extremely noisy locations, however, the 300 ohm line will pick up slightly more noise than the coaxial type. In making installations in such very noisy areas, the coaxial-type transmission line may be used with some sacrifice of signal strength at the receiver input.

(1-6) Installation of the FM Antenna.

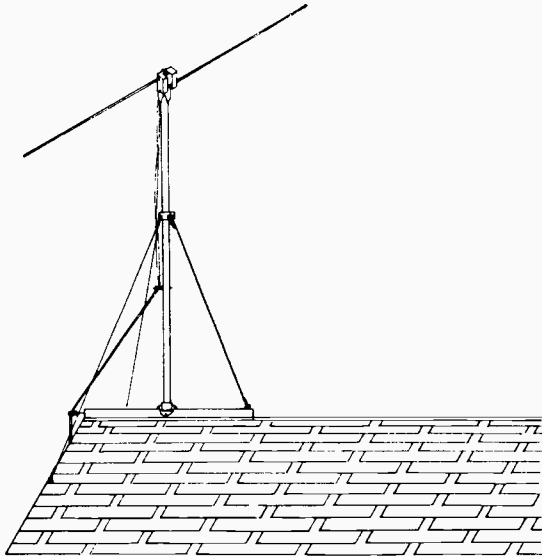

SLIDE 4

The FM antenna should be installed as high as possible and in the clear. It should be kept away from close proximity to metal roofs, eaves and other metallic objects. The dipole antenna is slightly directional and is most sensitive to FM signals when rotated to a position broadside to the FM station. The antenna can usually be mounted on a roof top or other high projection and then rotated to the position which gives best signal pickup on the various stations across the band. As the sensitivity pattern of the dipole is that of a figure 8, it will be necessary to rotate the antenna only 90° for changing from minimum to maximum sensitivity. Tests have proved that in most cases little difference in signal strength is noticed when the antenna is rotated, provided that the signal is strong. In most installations the antenna will be orientated to provide best reception on desired weak stations and left in that position.

The 300-ohm transmission line is fairly sensitive to metallic objects. The Westinghouse Stratovision FM antenna is supplied with a stand-off insulator to prevent the transmission swinging or rubbing against the metal mast. The three-foot section of transmission line between the stand-off insulator and the center of the dipole should be twisted *three times* and drawn tight through the insulator. The purpose in twisting the transmission line between the dipole center and the stand-off insulator is to maintain electrical balance

between each wire of the transmission line and the metal mast. This nullifies the effect of the metal mast in the transmission line field, thus preventing loss of the r-f signal energy.

The section of transmission line between the stand-off insulator and the FM receiver, input terminals should be kept flat and drawn fairly tight. Do not permit the line to swing or rub against roof edges, walls or shrubbery. The transmission line may be dressed against a dry wooden baseboard or wall and the line secured by driving a small metal brad through the center of the plastic dielectric and into the wood. The brads should be spaced about one or two feet apart. Do not use thumb or carpet tacks; The large metallic head may short circuit the two wires of the line or may cause serious signal losses due to a change in the characteristic impedance of the line.

Use just sufficient length of line to reach the antenna terminals without coiling; any excess line should be cut away. At these extremely high frequencies, tests have shown that two or three turns or loops in the transmission line are sufficient to reduce the received signal strength 25 to 50 percent.


SECTION II FM RECEIVER FUNDAMENTALS

(2-1) General - The design of a receiver for FM is similar in many respects to that employed in AM practice, but is somewhat more complex. The superheterodyne circuit is standard, but the 88 - 106 megacycle tuning range brings in some variations from the usual AM practice, and, of course, we have the special FM circuit features such as limiters, discriminators, etc. In this discussion we shall start at the FM antenna input terminals of the Westinghouse Model H-119 receiver and discuss the major differences between the FM and AM circuits.

(2-2) R.F., Mixer and Oscillator Circuits, H-119.

The r-f end of an FM receiver has somewhat the same functions to perform as in an AM receiver. I-F rejection is of less importance as the 10.7 mc. i-f is comparatively interference free. Image rejection is not a major problem as the high i-f places images of FM stations outside the band. *The major function of the r-f end of the receiver is to add as much as possible to the gain of the set so that a good signal-to-noise ratio will be obtained.*

Slide 5 shows the r-f amplifier, mixer and oscillator circuits of the Westinghouse Model H-119 AM-FM receiver. Only the FM portion of the circuit is shown; all band switches and components associated with AM have been deleted for the sake of simplicity in following the FM operation. It will be noticed that one wire of the two-wire transmission line from

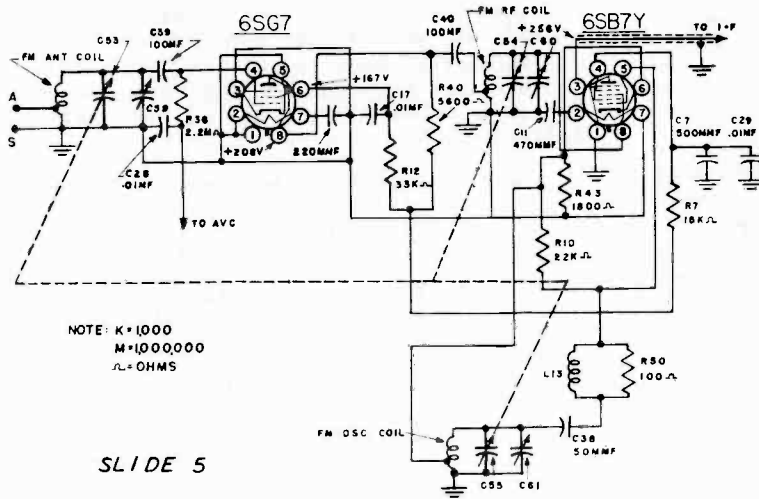

SLIDE 5

R-F MIXER OSC STAGE H-119

the antenna, is connected to chassis ground; the other wire is connected to a tap on the antenna coil. The tap location has been selected for maximum signal voltage delivery to the 6SG7 r-f amplifier grid and is correct for use with transmission line impedances of from 50 to 300 ohms. The tuned circuits, both physically and electrically, are more or less conventional, as compared with regular AM circuits, except for the size of the tuning capacitors and coils. One and one-half volts of negative bias for the 6SG7 r-f amplifier tube is obtained from the voltage drop across a resistor in series with the power transformer high-voltage winding center tap and additional bias from the AVC circuit. The r-f energy from the 6SG7 plate is fed to a tap on the mixer r-f coil in order to obtain the proper impedance match between the 6SG7 plate and the 6SB7Y signal grid.


This mixer-oscillator tube is a 6SB7Y which is a special metal-shell type developed for converter service on the new 88 - 106 mc. FM band. The circuit and connections are similar to those of the ordinary 6SA7 type; however, the interelectrode capacitance of the 6SB7Y is much lower than that of the 6SA7 and the 6SB7Y is fitted with a low-loss base. The oscillator circuit is a conventional tapped-coil Hartley type. The coil and resistor network, L13 and R50, is a parasitic suppressor circuit. When the 14-tube chassis was designed it was found that a spurious oscillation appeared near the 1600 kilocycle point on the regular AM broadcast range. The coil and resistor combination effectively eliminates this condition.

(2-3) Intermediate Frequency Amplifier Circuits, H-119.

Electrically, the i-f amplifier circuits of the H-119 are more or less conventional. The 10.7 mc. i-f transformer windings are connected in series with the regular 455 kc. AM i-f windings. Due to the wide difference between the two intermediate frequencies, no interaction or ill effects are encountered. The gain and other characteristics are about the same as when separate transformers are used. In tuning such composite i-f units, the AM or 455 kc. trimmers are adjusted first and the FM or 10.7 mc. trimmers last.

It will be noticed that a 22,000 ohm loading resistor is connected across the secondary winding of the first i-f transformer and 12,000 ohm resistors across the primary and secondary windings of the second i-f transformer. The higher value of resistance in the grid circuit of the first i-f stage is used because of the comparatively low signal level at this point. If the resistance value is made very low the

loss in signal level would be too great. The purpose of the resistors is to permit "peaking" of the i-f circuits; unless resistor loading is used, it would be necessary to "flat-top" the i-f circuits in order to obtain proper band-pass characteristics. There is some curvature, of course, in the top portion of the resistance-loaded frequency response curve but the limiter acts to clip off this curvature providing, in effect, a wide-band flat-top response at the discriminator input.

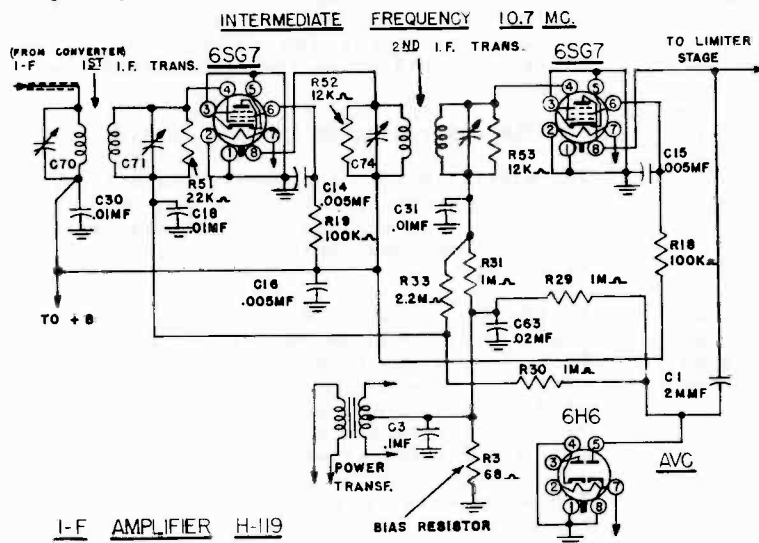


I-F AMPLIFIER H-119

SLIDE 6

This slide shows the 68 ohms voltage dropping bias resistor in the power transformer high-voltage center tap. Note that the signal for the AVC rectifier is taken directly from the plate of the 6SG7 second i-f tube through a 22 mμf fixed capacitor. This permits the same AVC circuit to function on both AM and FM without

becoming involved in complex switching arrangements. In every other respect the i-f amplifier is strictly conventional. We shall now discuss the operation of the limiter stage.

(2-6) The limiter circuit, H-119

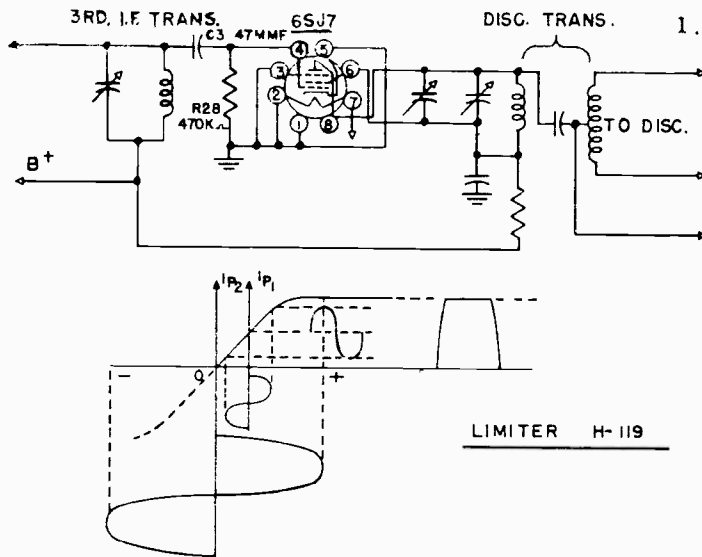

SLIDE 7

- a. The limiter is an i-f amplifier stage designed to "saturate" at a certain signal level. It acts somewhat like a tank, which allows the water level to rise to the out-flow pipe and then keeps that level constant no matter how much water is poured in.
- b. In the FM set the purpose of the limiter is:
 1. To remove all amplitude variations in the i-f amplifier system ahead of the discriminator a signal of constant amplitude and varying frequency.
 2. To enable the FM set to discriminate between two stations on the same frequency as long as the signal strength of one station is two times that of the other. (Similar to AVC.)
 3. To reject static, both natural and man-made.

Operation of the limiter:

1. The limiter works on the grid rectification principle. A grid condenser and grid leak are used in the same manner as the "square law" detectors used in the radios of 15 or 20 years ago.
2. No negative bias is supplied to the grid. The grid swings positive and grid current flows at the moment a signal is applied. Grid current flows through the 470,000 ohm grid resistor, R28, from grid to cathode of the 6SJ7 tube. The voltage drop across R28 has a polarity which makes the grid negative with re-

spect to cathode. The stronger the signal, the greater the bias voltage. This "automatic" bias reduces the gain of the tube and maintains a constant output.

d. The step by step operation of the limiter follows:

1. A strong signal is impressed on the 6SJ7 grid. The 47 mmf capacitor, C3, rapidly charges up to nearly the peak signal amplitude.
2. The capacitor then discharges through the 470,000 ohm resistor R28.
3. The values of the resistor and capacitor are critical. The discharge rate through the resistor will be slower than the charging rate through the tube. This results in a steady negative bias voltage being built up on the grid.
4. This negative voltage is almost equal to peak of the signal. The grid will swing positive only on signal peaks and for a very short period of time. The length of these periods is determined by the time constant of the grid capacitor, C3, and the grid resistor, R28.
5. Under these conditions the 6SJ7 tube then will "squash" down any changes in the strength or amplitude of the signal. From its plate circuit it will deliver a constant amplitude signal to the discriminator.


e. Precautions

Limiter tube voltages are quite critical. When replacing the grid condenser or the grid and plate resistors, the exact value specified by the manufacturer must be used.

(2-7) The Discriminator Circuit, H-119

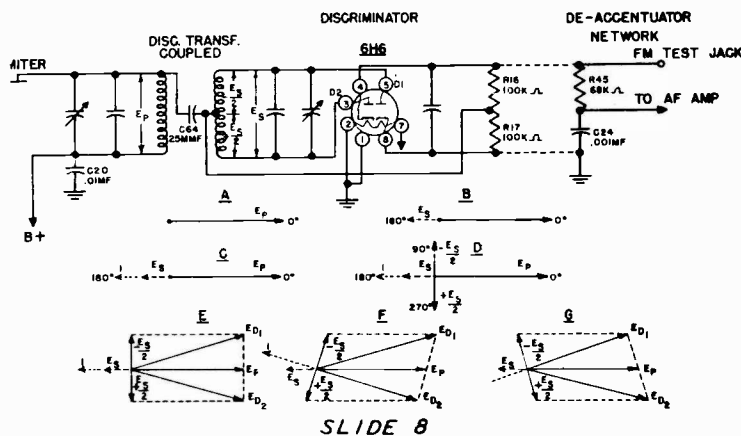
- a. The discriminator is a device which changes frequency variations into a varying audio voltage. This varying audio voltage corresponds to the sound being transmitted by the FM station.
- b. In the Westinghouse Model H-119 a more or less conventional center-tapped i-f transformer and a 6H6 tube comprise the discriminator. This circuit utilizes the phase shift between the primary and secondary voltages across the i-f transformer to produce a differential audio voltage.
- c. The step by step operation of the H-119 discriminator is as follows:
 1. The i-f signal voltage appears across the tuned primary of the discriminator transformer (condition A)

- An induced voltage is produced across the secondary winding. This voltage is 180° out of phase with the primary voltage (condition B).



- At resonance the induced secondary voltage causes an in-phase current to flow through the coil and its tuning condenser (condition C).
- This in-phase current flows through the coil and produces a reactive voltage drop across the coil and condenser. This reactive voltage is out of phase with the secondary current by 90° (condition D).
- If the resistance of the secondary winding is low, the reactive voltage drop across the secondary tuning capacitor will be many hundreds of times greater than the induced voltage due to transformer action. This "gain" is similar to that of an ordinary TRF stage when it is tuned and for all practical purposes, we can forget the induced secondary voltage and assume that the secondary voltage is equal to the reactive voltage drop across the coil and condenser.
- The current through the secondary winding may be assumed to flow from bottom to top of the coil. One half of the reactive voltage drop appears between the center tap and the bottom of the coil; the other half appears between the center tap and the top of the coil. For purposes of explanation, we will designate the upper half of the voltage drop as "minus" $E_s/2$ and the lower half as "plus" $E_s/2$.
- The primary voltage is also coupled to the center-point of the secondary winding through the capacitor C64. This voltage appears across resistor R17, and is the same as that across the primary winding.
- The resultant signal voltage which appears at diodes No. 1 or No. 2 is the vector sum of the series voltage drop across R17 plus the upper half of the secondary voltage, or the vector sum of the series voltage plus the lower half of the secondary voltage.
- When the signal voltage frequency is equal to the resonant frequency of the tuned primary and secondary discriminator transformer circuits, the signal voltages appearing at the two diode plates are equal, and equal and opposite rectified voltages will appear across resistors R16 and R17 (condition E).
- The audio frequency output under the conditions just mentioned, will be zero. This would be a condition of no modulation at the FM transmitter.
- As the frequency varies with modulation, the voltages applied to the two diodes become unequal.
- At frequencies higher than the resonant frequency of the tuned circuits, the secondary winding presents an inductive reactance causing the current to lag the secondary voltage. As a result the voltage at diode No. 1 is greater than at diode No. 2 (condition F).
- Diode No. 1 passes current which flows from the cathode mid-point connection through R16. The voltage drop across R16 is now greater than the drop across R17. The voltage output at the discriminator test jack will be equal to the algebraic difference between the voltage drops across R16 and R17 and will have a definite polarity, plus or minus, with respect to ground.
- At frequencies below resonance, the conditions are the direct opposite of those just described. The tuned circuit now presents a capacitive reactance, the secondary current leads the voltage and the voltage at diode No. 2 is now greater than that at diode No. 1 (condition G).
- Diode No. 2 accordingly passes current which flows from cathode midpoint connection through R17 causing a greater voltage drop across that resistor.
- As the frequency swings from one side of resonance, through resonance and to the other side of resonance, the audio voltage output from the discriminator, will decrease to zero, reverse polarity and rise to a peak. If the voltage values appearing across R16 and R17 are plotted against the impressed frequency, a curve such as that shown in slide 9 will be obtained. The straight portion of the curve must, at least, extend over the band width covered by the FM signal.


(2-8) Deaccentuation Network H-119. The a-f accentuator is used at the FM transmitter network to raise the amplitude of the audio

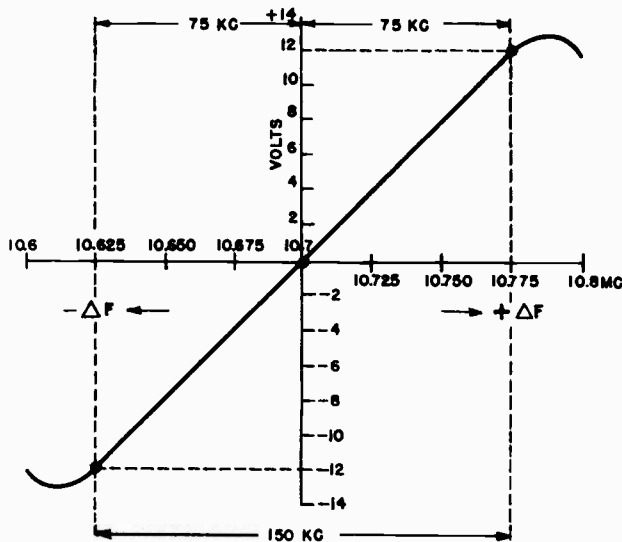

SLIDE 9

frequencies in the upper range. At 10,000 cycles the amplitude of the audio signal is up to 15DB. The actual signal, as taken from the discriminator output is therefore distorted. It is necessary to utilize this arrangement in order to prevent the transmission of noise from the FM transmitter.

At the receiver, the a-f amplifier must be designed to present a response the direct opposite of that at the transmitter. This means that the a-f amplitude at 10,000 cycles must be down 15DB in order to realize reproduction of the original sound. This is accomplished by the insertion of a network of resistance and capacitance at the input of the a-f amplifier. The time constant of this network is from 70 to 100 micro-seconds and the values are quite critical. When replacing these components, be certain that the values are identical with those specified by the manufacturer.

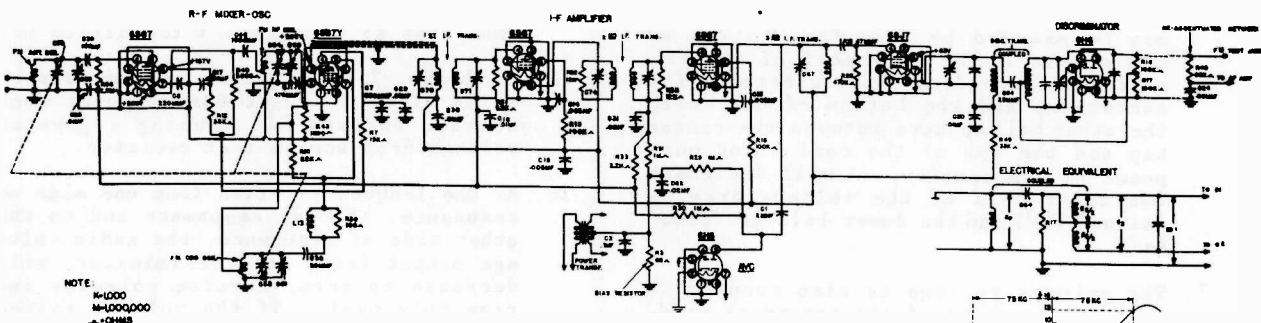

SLIDE 10

SECTION III FM RECEIVER ALIGNMENT AND TROUBLE SHOOTING

(3-1) Voltmeter Alignment H-119

a. Test Equipment Required:

1. Standard signal generator with provision for removal of modulation and capable of providing 10.7 mc. and 88 - 106 mc. output.
2. Vacuum tube voltmeter, such as RCA Volt-ohmist or Hickok 125 (must have a scale of around 2.5 volts D.C.). A 20,000 ohms per volt D.C. voltmeter, such as Simpson Model 260, may be used. However, the VTVM is recommended.



b. R-F and I-F Alignment.


1. Connect vacuum tube voltmeter across limiter grid resistor.
2. Connect unmodulated output signal voltage from signal generator to stage under alignment (if aligning i-f generator should be adjusted for 10.7 mc. center i-f; if aligning r-f, generator should be adjusted to some frequency in the 88 - 106 mc. band.)
3. Adjust i-f or r-f trimmers for maximum voltage indication on vacuum tube voltmeter.

NOTE: Maintain a good common ground connection between the receiver, the vacuum tube voltmeter and the signal generator.

c. Discriminator Alignment.

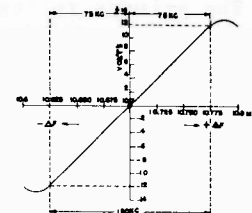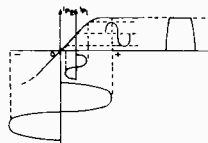1. Connect signal generator to receiver limiter grid. Keep output of signal generator low so that grid current will not be drawn.



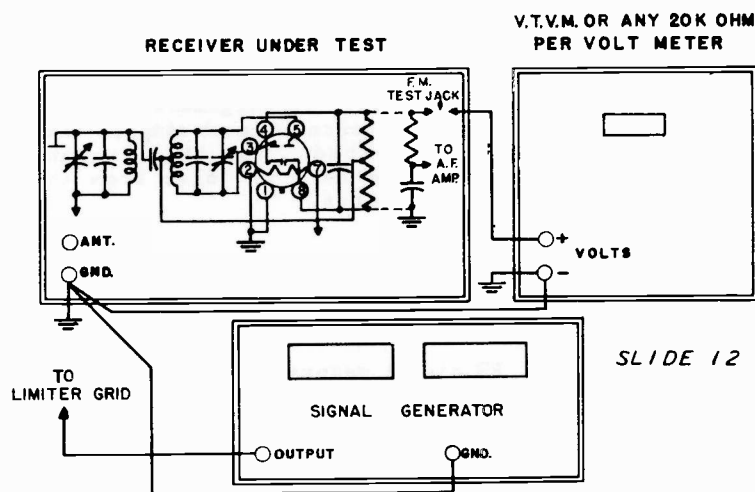

F. M. BAND ALIGNMENT

Connect a 10,000 ohms-per-volt or Vacuum Tube Voltmeter between the Discriminator Test Jack and the chassis.

With the volume control set for maximum output and the signal from the generator attenuated to avoid A.V.C. action, proceed as follows

STEP	CONNECT SIGNAL GENERATOR TO..	SIGNAL GENERATOR FREQUENCY	RADIO DIAL SETTING	ADJUST
1	Set Phono-Band switch to "F.M."			
2	Detune secondary trimmer of discriminator transformer.			
3	6SG7, 2nd i-f, control grid through a .01 mfd mica capacitor	UNMODULATED 10.7 mc	88 mc	10.7 mc primary trimmer of 3rd i-f trans. for maximum voltage.
4	6SG7, 1st i-f, control grid through a .01 mfd mica capacitor	UNMODULATED 10.7 mc	88 mc	10.7 mc secondary and primary trimmers of 2nd i-f trans. for maximum voltage.
5	Fixed plates of the FM converter tuning capacitor through a .01 mfd mica capacitor	UNMODULATED 10.7 mc	88 mc	10.7 mc secondary and primary trimmers of 1st i-f transformer for maximum voltage.
6	Fixed plates of the FM converter tuning capacitor through a .01 mfd mica	UNMODULATED 10.7 mc	88 mc	carefully "peak" all 10.7 mc i-f trimmers for maximum voltage.
7	FM antenna terminal through a non-inductive 300 ohm resis.	UNMODULATED 105 mc	105 mc	FM oscillator trimmer for maximum voltage.
8	FM antenna terminal through a non-inductive 300 ohm resistor	UNMODULATED 105 mc	105 mc	FM r-f and ANT trimmers for maximum voltage.
9	Fixed plates of the FM converter tuning capacitor through a .01 mfd mica capacitor	UNMODULATED 10.7 mc	88 mc	Primary trimmer of discriminator transformer for maximum voltage.
10	Fixed plates of the FM converter tuning capacitor through a .01 mfd mica capacitor	UNMODULATED 10.7 mc	88 mc	Secondary trimmer of discriminator transformer for zero voltage. The voltage will change polarity as the trimmer is tuned through resonance. Tune carefully for zero voltage.
11	Re-check steps 9 and 10.			

2. Connect vacuum tube voltmeter to discriminator output (FM test jack in H-119).
3. Detune discriminator transformer secondary trimmer.
4. Adjust discriminator transformer primary trimmer for maximum voltage indication on the VTVM.
5. Adjust discriminator transformer secondary trimmer for zero voltage indication on the VTVM.

NOTE: As the secondary trimmer passes through resonance, the voltage indication will decrease to zero, reverse polarity, and again increase to a peak. Adjust as accurately as possible to the zero value.

6. Swing signal generator frequency to 10.775 mc. Note discriminator voltage value as indicated on VTVM.
7. Swing signal generator frequency to 10.625 mc. Note discriminator voltage value as indicated on VTVM. This voltage indication will be of opposite polarity to that observed under step 6. The two readings should be of the same value within $\pm 10\%$ of the highest value.
8. If the two voltage readings are not within the tolerance specified under step 7, a slight readjustment of the primary trimmer may be necessary. The primary trimmer controls the amplitude and linearity of the discriminator output; the secondary trimmer controls the location of the zero reference point on the discriminator characteristic curve.

d. FM Alignment H-119

Service Department laboratory tests showed that the Model H-119 FM alignment could be carried out by a procedure much simpler than that just described. The FM alignment chart reproduced here is taken from the H-119 Service Notes.

(3-2) Visual Alignment H-119

a. Test Equipment Required:

1. FM signal generator, such as Hickok 288-X, capable of providing 10.7 mc and 88 - 106 mc output. Should supply synch sweep voltage for oscilloscope trace.
2. Oscilloscope, such as RCA Model 155C.


b. R-F and I-F Alignment



1. Connect oscilloscope vertical input across limiter grid resistor.
2. Connect synch sweep voltage from signal generator to horizontal input of oscilloscope.
3. Connect output signal voltage from signal generator to stage under alignment (if aligning i-f, generator should be adjusted for 10.7 mc. center i-f; if r-f, generator should be adjusted to somewhere in 88 - 106 mc. band).
4. Adjust i-f or r-f trimmers until oscilloscope pattern is similar to "A" in slide.

NOTE: Maintain a good ground common connection between the receiver, the oscilloscope and the signal generator.

Visual Alignment Discriminator

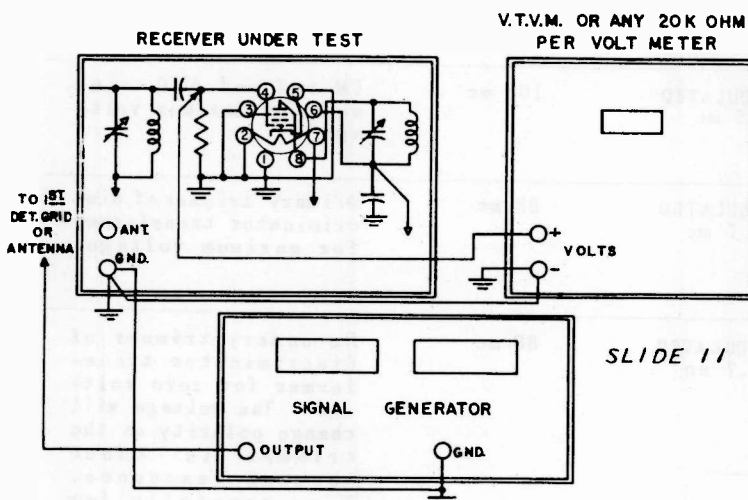1. Connect signal generator to receive limiter grid and to oscilloscope as outlined above.
2. Connect vertical input of oscilloscope to discriminator output (FM test jack in H-119).
3. Adjust discriminator primary trimmer for maximum pattern amplitude.
4. Adjust discriminator secondary trimmer until pattern is correctly centered about the horizontal axis. The positive and negative peaks should be equal in amplitude and the trace between the two peaks should be linear, at least over the frequency response of the r-f and i-f circuits.



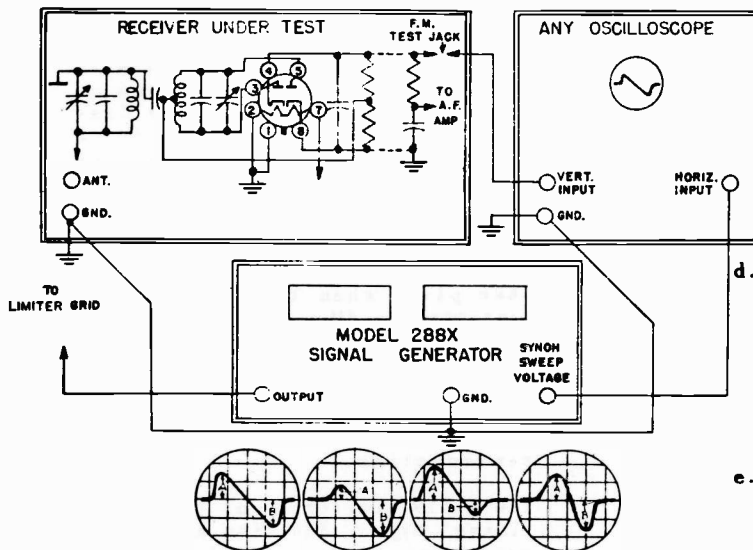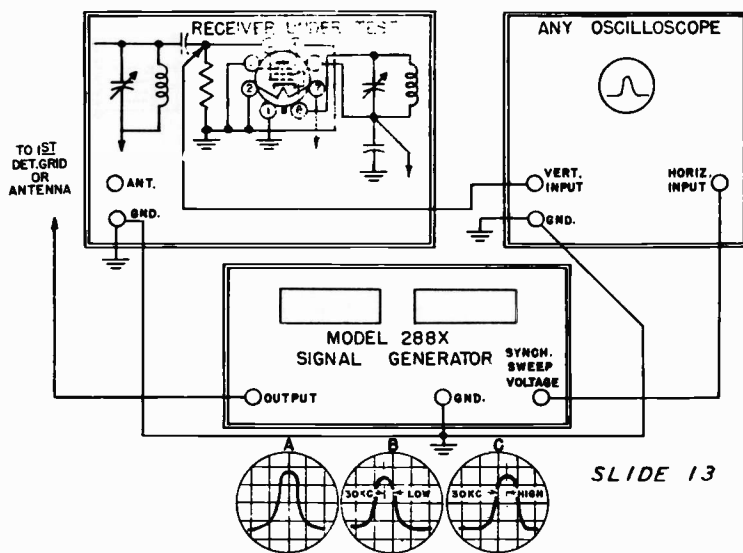

5. It may be necessary to alternately readjust the discriminator primary and the secondary trimmers to obtain linearity and symmetry in the output. The primary trimmer controls the overall amplitude and the linearity of the pattern; the secondary trimmer controls the distribution of the pattern around the horizontal axis or zero reference line.

(3-3) FM Trouble Shooting

a. Noise and Miss

1. Noisy r-f or converter tube
2. Defective antenna system
3. Excessive plate voltage on limiter
4. Regeneration

b. Regeneration

1. Improper lead dress
2. Incorrect alignment
3. Defective shield or ground straps
4. Open bypass condenser (r-f or i-f circuits)

c. Distortion and poor Tone Quality

1. Limiter not functioning due to
 - a. Bad 6SJ7 limiter tube
 - b. Incorrect limiter voltage
 - c. Limiter circuit not properly aligned
 - d. I-F circuits not properly aligned
 - e. Bad i-f amplifier tube
 - f. Open loading resistor across i-f winding
 - g. Open bypass condenser, i-f circuit
 - h. Incorrect voltages on i-f tubes
2. Bad resistors or capacitors in de-accentuator network.
3. Insufficient signal for limiter saturation due to
 - a. R-F circuits out of alignment
 - b. Bad r-f tube
 - c. Inefficient antenna system

d. Dynamic Range or Reproduction Poor

1. Limiter not functioning properly
2. Regeneration in i-f due to open bypass condenser or open loading resistor across i-f transformer
3. I-F circuits, limiter or discriminator not properly adjusted.


e. Lack of Highs on FM Stations

1. Check resistance-capacitance values in de-accentuator network.

f. Trouble Shooting in the Discriminator

Trouble: Severe Amplitude Distortion During High Audio Signal Levels.

Remedy: This trouble is frequently due to poor discriminator alignment. High level audio signals correspond to wide frequency deviations around the center intermediate frequency. If the discriminator is far out of alignment, the widely deviated signal, which corresponds to a loud noise, will go over the "hump" of the characteristic curve and distortion will result. If the discriminator is only slightly out of alignment, the audio quality will be good except on the very loud passages where the response leaves the linear portion of the curve and passes over to the peak.

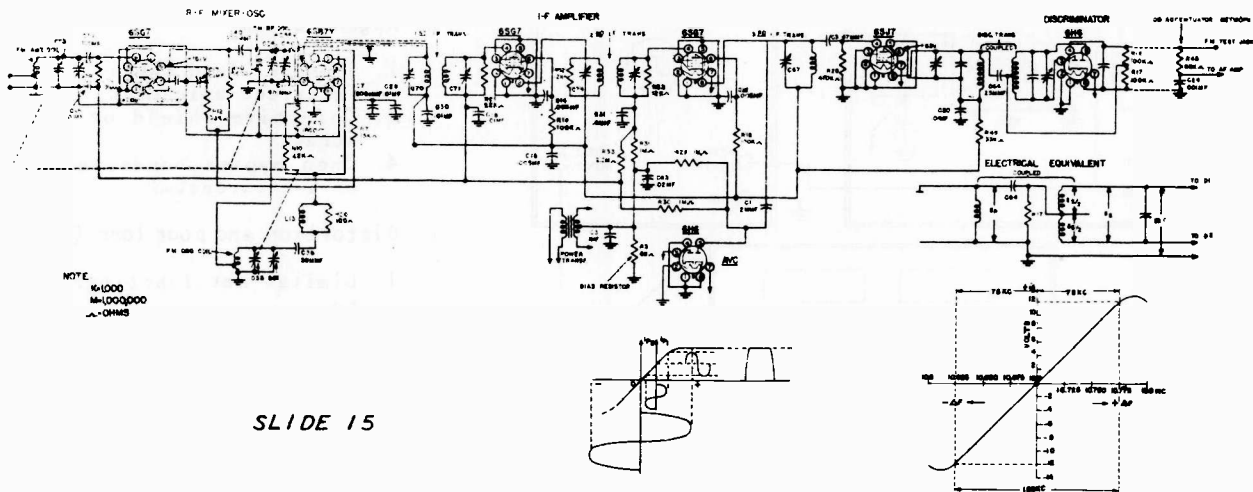

SLIDE 15

To correct, realign the discriminator transformer primary and secondary trimmers.

Another possibility is that one-half of the discriminator transformer secondary winding may be open; or, the phasing condenser between the primary and secondary windings may be open. Either of these troubles will cause loss of one reference voltage and thereby introduce distortion.

g. Trouble Shooting In the Limiter

Trouble: Distortion in Discriminator A-F Output

The same basic operating principle is involved in all present-day limiter circuits. In the Westinghouse H-119, a 6SJ7 sharp cut-off pentode is operated so that grid swing conditions between cut-off and zero grid volts is of the order of 3 or 4 volts. The plate and screen voltage is maintained at approximately 63 volts. Under such operating conditions, with a strong signal applied to the limiter grid, plate current saturation is quickly reached.

The most frequent trouble in limiter circuits, with the possible exception of tube trouble, is a change in plate voltage due to changes in the value of the plate load resistor or to partial short-circuit of the plate circuit bypass condenser. If the plate and screen voltages are too high, the "threshold" voltage may change as much as 50 to 150 microvolts or more. This means that the limiter will function as an i-f amplifier and little or no limiting action will

take place. As the signal frequency swings with modulation, it passes over the slope of the i-f characteristic curve generating an AM signal which can be passed on to the discriminator. The discriminator will respond to AM as one-half of the 6H6 tube can act as a diode rectifier. Unless the limiter removes the AM response, this condition will occur. The i-f response curve is not linear, so considerable distortion will take place when the FM signal is converted to AM. This is not normal FM reception and the conditions just described are due to a lack of limiter action. This condition can be readily recognized by noisy and somewhat distorted reproduction.

The H-119 limiter is of the "peak-riding" type. The bias across the grid resistor is developed from current flow during the peaks of the r-f grid voltage swing. This grid current charges the capacitor and the capacitor, in turn, discharges through the grid resistor. If the grid resistor became open, there would be no leakage path for the condenser charge. A burst of noise or a strong signal will charge the grid capacitor to a large bias voltage. If the resistor is open, however, there would be no condenser discharge other than the loss leakage across the dielectric and the accumulated charge holds the 6SJ7 grid below the cut-off value. This condition will cause sharp clicks of signal or noise similar to a motor-boating effect. If the capacitor dielectric has a very low leakage factor, the set may appear dead for fairly long periods of time.

LESSON 22

The Radio Servicing Business

Obtaining Radio Repair Jobs

Servicemen forget that they live in a highly-competitive society. They expect Mr. Radio Owner to come to them when he has radio difficulties, to beat a path to their door, and to search high and low for their addresses if necessary. Of course, this does not happen and the fellow down the street gets the job. If you want more business, if you want the business of people who never heard of you, you must let them know of your existence, your good points, your special abilities to serve them. You must approach them many times in many different ways. Advertising does this and advertising pays!

Money invested in advertising is far from being foolishly spent. Not only do you expect to receive back every dollar spent on advertising, but on every dollar you expect a certain definite return in the form of increased business and greater profits. You will get these successful results if you plan your advertising wisely and correctly.

Among the various forms of advertising suitable for radio service business, advertising in publications such as local newspapers and telephone books is most common. When advertising is sent directly to the prospect, either by mail or messenger, this method of advertising is called direct mail.



Posters, window displays, and signs are very effective ways of obtaining additional business. See the sample illustrated. There are also certain unique methods of advertising salesmanship that get business.

Advertising in any form must get attention. Unless an advertisement or a sign attracts attention, it is not present as far as the prospective reader is concerned and it is useless. Attention is obtained in various ways. Sheer size, black type, white space, color, novelty, illustration, and catch-phrases serve to get attention.

Once attention is arrested in any suitable manner, the interest of the reader must be held. The story, the picture, the idea must "get the reader," compel him to read on. In other words, it is not merely enough to notice an advertisement, but the advertisement must actually prove interesting. With the reader expressing a not personally realized interest in your advertisement, the next step is to create a desire. A desire for a better set, a new set of tubes, or better reception.

FUN ON THE AIR!

ENJOY IT ALL... WITH A RADIO THAT'S TUNED-UP FOR A BETTER TUNE-IN!

The greatest entertainment talent in the world is yours for the listening! Don't miss a single note of it! Call us up today! We'll make sure you get top radio performance and enjoyment in your home!

ADDRESS DEALER'S NAME PHONE NO.

SAMPLES OF CLASSIFIED ADS

Service, Repair, Etc.

RADIO SERVICE—WORK GUARANTEED. No set too complicated. Experienced men, Radio Center, 19 Yes St. BRyant 9-0558.

\$3 TV SERVICE \$3

Day, night, Sunday, N. and N. W. TRU VUE GRaceland 7-5772

E-Z TERMS ON ALL RADIO REPAIR, wash. mach. vacuum cleaners. BRyant 9-0558.

\$3—POWER TV SERVICE—\$3

Day, night, Sun. Parts guar. No job too little or too big. 1 hour service, North and South. LAkeview 5-1409

Once the desire is aroused, the reader must be impressed with conviction that your tubes, your service, or your appliances are what he wants. Your items and service must appear to him as the logical solution of his desires.

At this stage, the reader is convinced that your service or products are what he wants and needs, but you must make him act. Action will make him pick up the 'phone and call you up or stop in to have his tubes tested. Do not merely tell your story in your advertisements. Finish up with action that will make the reader exclaim: "I'll phone that service man right now," and not "Well, my radio hasn't been playing right, I'll get it fixed one of these days."

In larger cities, a small advertisement in the want-ad section of the daily newspaper brings excellent results. Some outstanding points about your service must be featured. Note the few examples shown. The feature of the first ad is the fact that no set is too complicated and the work is guaranteed. In smaller city papers and in weeklies it is best to take display space, two or three inches.

The principles in the preparation of the advertising copy are therefore well defined, and of course the main objective is sales. It may seem a far cry from a two-line classified advertisement to a well-considered plan of copy preparation. Perhaps it is. The

name, nature of business, solicitation, address and telephone number may take up half the space. Not much theory need be applied to creation of the seven words constituting the extra line of type. But there are at least two factors that justify exercise of skill and care, even under the extremely restricted condition outlined. First, the habit of doing things right is just as important to your grandest one, and large advertising agency businesses have been developed for handling only classified advertisements because of specialized skill; second your advertising space will grow with you, and the principles applicable to copy and art creation are in general the same for all sizes of advertising space. So address yourself to these purposes:

1. Arouse interest.
2. Create desire.
3. Impress conviction.
4. Induce action.

Telephone book advertisements offer excellent possibilities. A large number of people turn to the 'phone book when they are in need of some special commodity or service. The two examples shown demonstrate the two possibilities of such advertisements. Notice that the upper ad has much copy or reading matter. On the other hand, the second ad has white space and but a few words. Both methods have their advantages, but a happy medium will be best.

SAMPLES OF DISPLAY ADS

RADIO SERVICE CENTER

Calls Made Day and Night
HONEST - RELIABLE SERVICE
 Any Make Set—10 Years in Business
 Accurate Tube Test in Home
 Most Modern Test Equipment
 Member, Radio Service Institution
FREE ESTIMATE IN SHOP
 Parts in Stock for All Sets
 19 Yes St. BRyant 9-0558

SOMEONE'S RADIO SHOP

Prompt
EXPERT REPAIRS
 On
ALL MAKES

Free Estimates—Work Guaranteed
 19 Yes St. BRyant 9-0558




Dreams will not create successful advertisements or bring business to your store. Good advertising should make things easy for your customers.

Telephone-book advertisements.

Every serviceman should have a complete mailing list of the people he has served. Occasional mailing should be made, suggesting free check-up service on tubes, or other offer. New names may also be used for this publicity.

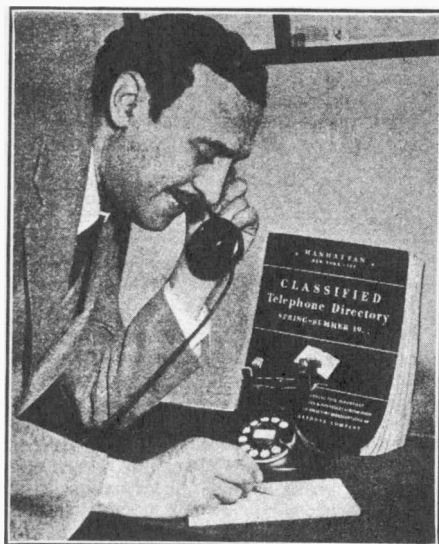Publicity via the telephone is also adaptable for selling service. If Mr. Brown had his radio repaired ten months ago, a telephone call some evening should be made. Here is a typical conversation:



"Hello, Mr. Brown. I repaired your radio some time ago. How does it work now? I am glad to know that it works fine. Does your television set need any adjustment? Perhaps you do not know that I also repair all types of electrical appliances."


These various suggestions should result in some work for you. But even if not one of your questions brings a call for service, you have reminded an old customer of yourself and are now more certain to receive the next service job. At times, your customer may tell you of a friend who needs a radio repaired or a television adjusted.

When a day comes along without service calls and you find idle time on your hands (this can happen in the busiest of shops), use the telephone to call "cold" prospects in your locality. This is a good way to get service jobs and find new customers.

If you drive a car or a small truck, be sure to have an advertising message painted on a panel or a sign placed in a window which will tell of your service and give your address and telephone number. During slack times, it is worth while to ring the bell of a neighbor where you worked and explain: "I have just repaired a radio next door. Perhaps your radio or television set needs adjustment or repair. You will save on my travel charges since I am already at your door." This approach will result in a repair job if work is needed by this neighbor. In any case, you should leave your card in case a serviceman is needed at some future date.

Window display advertising can be very effective. It is of prime importance, where you have a street front, to have the window dressing not only neat and orderly, but interesting. This is an art in itself and large outfits either have professional window dressers on their payroll or hire them as needed. A small operator has to do his own work, probably. So the fellow who started out as a service man finds he has to be an advertising writer of sorts, a window dresser, a bookkeeper, a buyer, a clerk, and finally a service man.

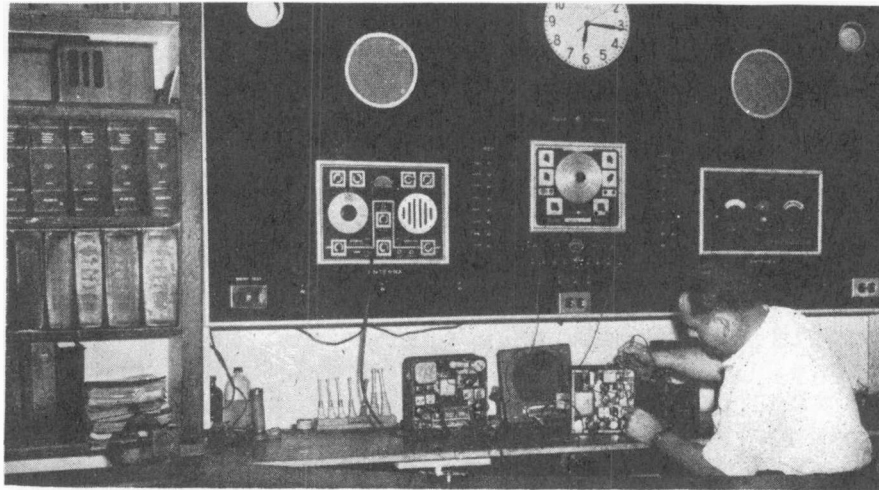Help in a plan of window display may be obtained from the women folk. Mother, sister, or wife can suggest that "touch" a man handy with soldering iron is not likely to have.



The usual displays as received from manufacturers may serve well on counters and in windows, but the most effective method is one invoking originality. Then one's window becomes distinctive. Services that incur movement are impelling. Anything that evokes an interesting contrast is valuable for its attention value. All ideas should be definitely associated with a sales appeal. The object is to sell. Everything else is only the means.

One fellow got six dead transmitting tubes from a station and put these giants next to six receiver tubes. He cited the fact the station checked tubes hourly. Why should not the listener have his tubes checked twice a year, also for the same reason — best quality performance? The transmitting tubes cost \$1,500. The six receiver tubes could be bought for less than \$8.

"Let us check your tubes" is the sales appeal, because if any tubes are bad or weak, a tube sale is made, and if the tubes are in good condition, the set may not be. Or, if everything is all right, some accessory may be sold to make reception better than just "all right," or to introduce a new service from the receiver, as in the case of the phonograph pickup attachment.

Another dealer attracted large crowds of real radio prospects by offering \$10 prize for the owner of the oldest radio set. Certainly the person who thinks he has the oldest radio in a community is a good prospect for a new set.

The Question of Rates and Charges

The subject of the rate per hour can be calculated by considering all expenses including overhead for a period of one year and dividing this sum by the total number of productive hours in this period. This high-brow accounting technique is better suited for larger corporations. You better figure on a flat fee based on amounts others have found satisfactory. You should not make less than \$2.25, but try to average \$3.00 per hour. This is not too much when you consider the hours spent in travelling, buying parts,

possible adjustments, holidays, and other hours spent in your business without direct earning.

I do not recommend, however, that an hourly charge is made to the customer. A charge should be made for the complete repair since this is what your customer wishes to purchase — they do not want to buy time. Parts used, at retail price which is about 66% above your cost, should also be added to the bill.


You should use the hourly charge suggestion in computing the probable charge. An estimated charge can be given in advance — make this on the high side, this will prove a good idea if the actual cost comes out about the same or lower. Charge the actual price as computed when the job is finished. If an exact price is wanted, take a guess. Make it high enough to be safe. Charge this price for the job no matter if it turns out higher or lower. Now let us consider how the price can be determined.


Brief tests to localize the source of trouble in a radio set will require about one-half to one hour. Much will depend on the difficulty of getting the chassis out of the cabinet. In the shop, the cost of time to find the fault will average between \$3.00 and \$4.00. If you know the fault is an intermittent, play safe with a cost figure of \$6.00. To do the work in the home about \$2.00 must be added to cover travel time.

The actual repair may take from a few minutes to replace a resistor to over an hour for replacing an I.F. transformer and completing the alignment. About \$3.50 will cover most cases. Parts for an average job will cost \$1.50, you figure \$2.50. These figures indicate that an average job in your shop will be billed between \$6.10 and \$7.10. This gives you a figure to use if a price is wanted completely in advance; make it \$10.00 for safety. If you are permitted to give the set a brief examination (your charge is \$2.00 to \$3.00 anyway if your customer does not want the work completed), you can give a more accurate estimate. Add a small amount anyway as a safety factor.

Be careful to quote what you believe are the correct figures. State the amount in a clear voice, make the customer realize by your actions and speech that you carefully considered the price and your quote is fair and final. If the customer wishes to think the matter over, permit him to do so, but make a record of your quotation for future reference. If the situation permits, you can go into some detail in explaining how you obtained your charge. This suggestion applies both to the occasion when you are furnishing a quotation and when you are presenting the actual bill.

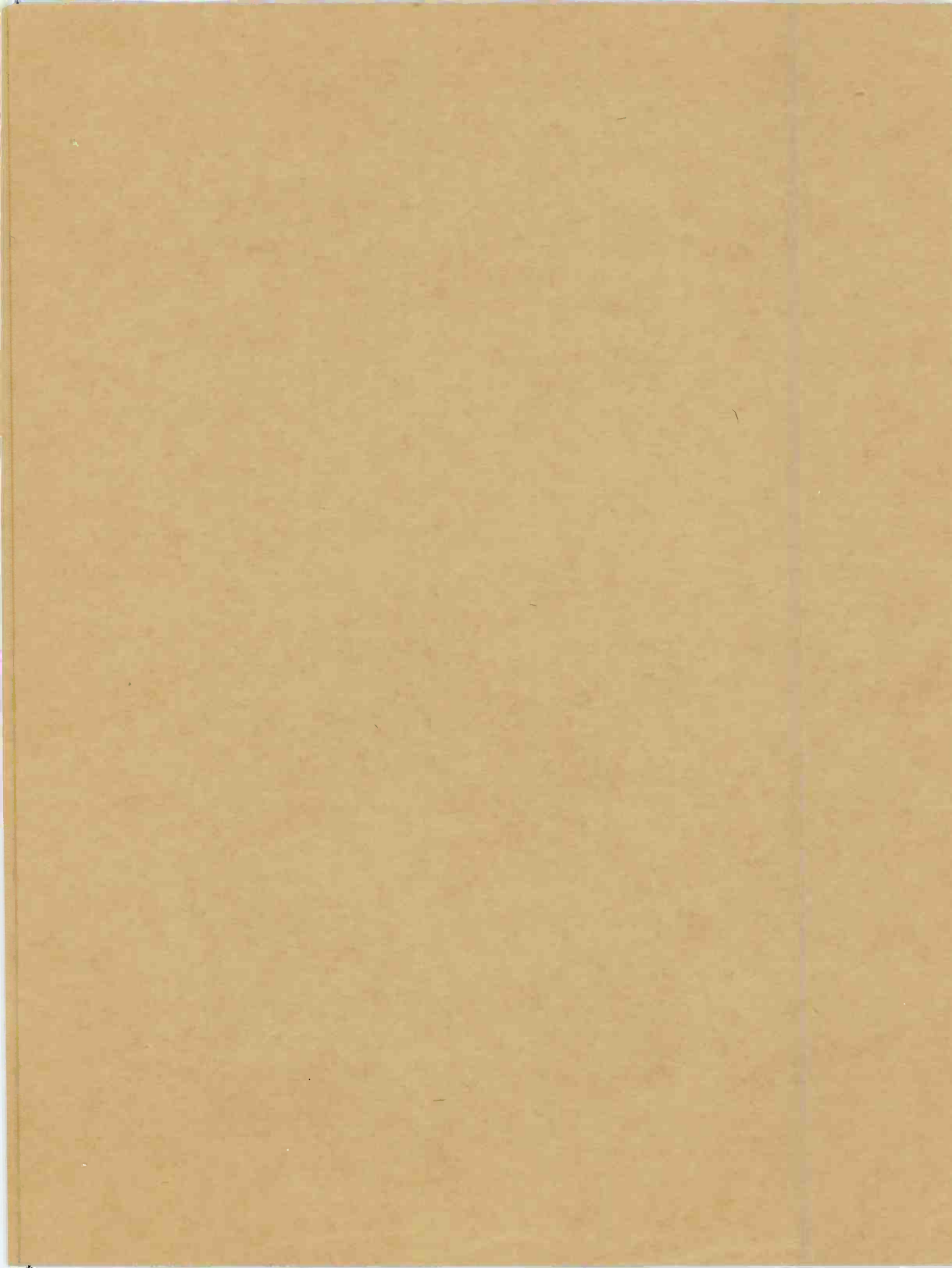Each job should be covered by a bill where labor appears as one item (no hours need be shown), and every single part used should be listed together with the net price to your customer. Any damaged parts removed from the radio should also be presented at this time. If you are told to junk these parts, try to break or mar them in some way while the customer is still present.



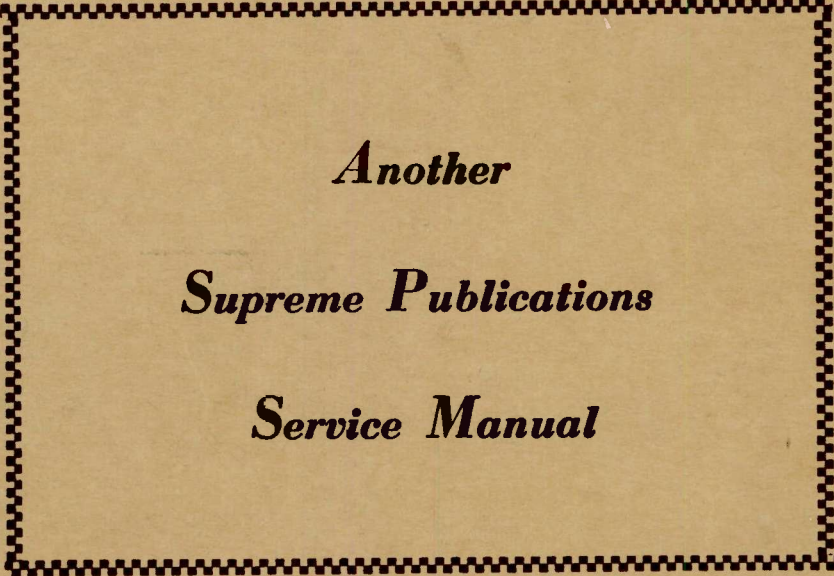

Another
Supreme Publications
Service Manual

Supreme Publications are Available at All Leading Parts Jobbers