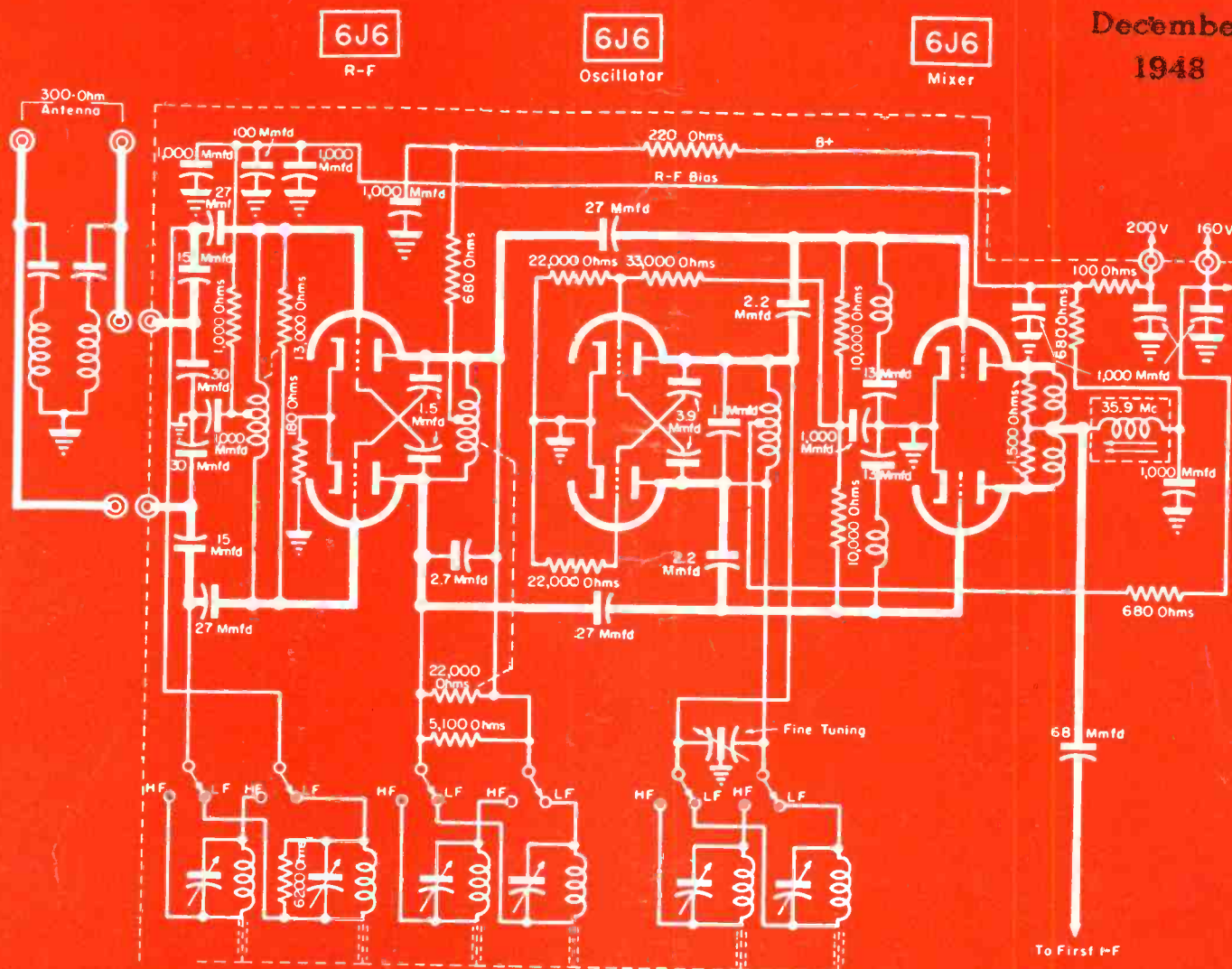


SERVICE

December
1948





The oscillator and mixer system of a table-model push-button TV receiver using a 10-inch picture tube.
(See page 2)

save 1,000 service hours
with this complete, up-to-date

c-d capacitor manual

For Radio Servicing

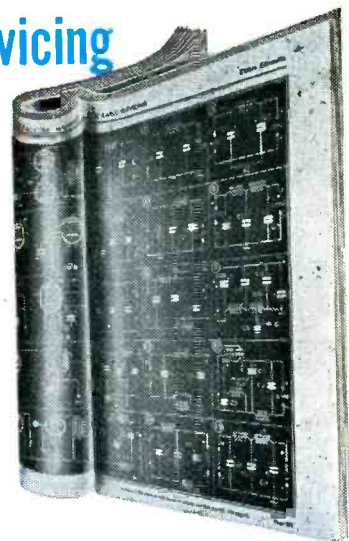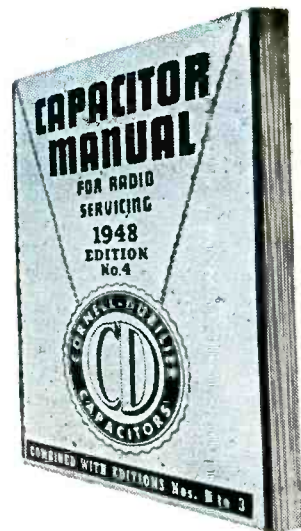

4th Edition by popular request!
OVER 400 PAGES!

Pocket Size—Accurate Parts Tables—Easy Circuit Diagrams

Why hunt and peck for the right capacitor replacement? This complete manual shows you the correct unit at a glance. Simplified tables and diagrams help you service any new or old radio set *faster, easier, more profitably*. You can save 1,000 hours or more in service time. Call your Cornell-Dubilier jobber now or mail coupon for your copy. List price \$.50. Cornell-Dubilier Electric Corporation, Dept. S12, South Plainfield, N. J. Other Plants in New Bedford, Worcester, and Brookline, Mass., and Providence, R. I.

Manufacture and Model No.	C. D. Part No.	CAPACITY	MFD.	375 V. VOLTS				Size	Temp. Coef.	Max. Part No.	Other Part No.
				10	25	50	CS				
ALLIED Radio Corp. CH 1000	CD 1000	100	100	25	3	1			574		
GE 1000	1000	100	100	25	3	1			575		
GE 1000	1000	100	100	25	3	1			576		
GE 1000	1000	100	100	25	3	1			577		
GE 1000	1000	100	100	25	3	1			578		
GE 1000	1000	100	100	25	3	1			579		
GE 1000	1000	100	100	25	3	1			580		
GE 1000	1000	100	100	25	3	1			581		
GE 1000	1000	100	100	25	3	1			582		
GE 1000	1000	100	100	25	3	1			583		
GE 1000	1000	100	100	25	3	1			584		
GE 1000	1000	100	100	25	3	1			585		
GE 1000	1000	100	100	25	3	1			586		
GE 1000	1000	100	100	25	3	1			587		
GE 1000	1000	100	100	25	3	1			588		
GE 1000	1000	100	100	25	3	1			589		
GE 1000	1000	100	100	25	3	1			590		

CORNELL-DUBILIER · WORLD'S LARGEST MANUFACTURER OF CAPACITORS

FILL IN — MAIL COUPON TODAY!

Cornell-Dubilier Electric Corp., Dept. S12
South Plainfield, New Jersey

Please rush my copy of the new C-D Capacitor Manual for Radio Servicing. I am enclosing \$.50
money order () check () stamps ()

my jobber is

Name

Shop

Address

City

Zone

State




1910



1948

mica
dykanol
paper
electrolytic

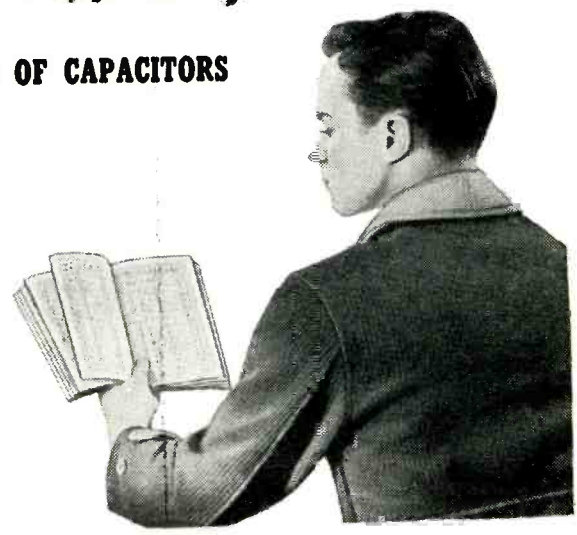

"KEN-RAD TUBES HAVE DONE A JOB FOR ME!"



"You can get a testimonial from me on Ken-Rad tubes any time!

"I use them. I've been using them for years. Believe me, no other tube can touch them.


"They're quality tubes. When I pass them on to a customer I know he won't come back mad.

"My customers come back, all right. But satisfied. They want me to do another job for them!"

R. W. RIEDY, Modern Radio Service, 513 West Broad Street, Bethlehem, Pa. Typical of thousands of radio servicemen, coast to coast, Mr. Riedy uses Ken-Rad tubes because he knows he can depend on them to satisfy customers.



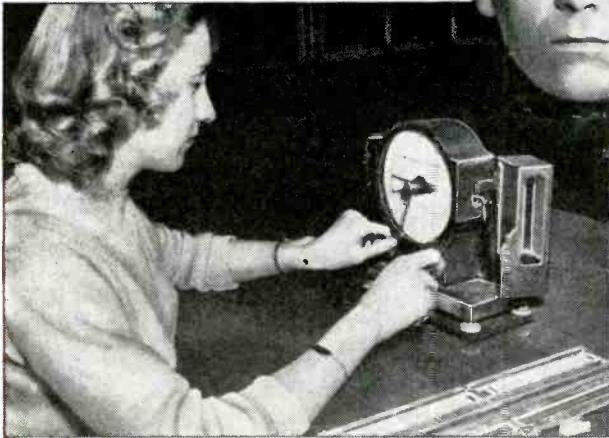EMMETT MERCER, Foreman, is responsible for the weighing of cathode sleeves to check coating weight (shown below). Another example of the great care that is taken in making Ken-Rad tubes.



"KEN-RAD TUBES ARE MADE TO DO A JOB!"

"We make Ken-Rad tubes to perform better, last longer, satisfy customers and increase business for you.

"I've been helping to make them for years. And I can tell you we check and recheck, test and retest, over and over again, the smallest parts that go into our tubes

"We test the tubes themselves for noise, microphonics, static, life, shorts, appearance, gas, air and hum.

"You can count on them to bring customers back satisfied."

178-GA13-8850

KEN-RAD Radio Tubes

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

The Serviceman's Tube





LEWIS WINNER
Editorial Director

F. WALEN
Assistant Editor

ALFRED A. GHIRARDI
Advisory Editor

	Page
Annual Index, Service, 1948.....	34
Association News.....	32
Push-Button TV Receiver (Cover).....	20
Ser-Cuits (Motorola, G.E. and Farnsworth TV Receivers).....	24
Servicing Helps. By P. M. Randolph.....	18
Servicing Taxicab Radio. By Samuel Freedman.....	10
Ten Years Ago in Associations.....	33
The LP Microgroove Record System. By Ralph M. Baruch.....	16
TV Installations in Fringe Areas. By Ira Kamen.....	12
TV Sync and Inter-Sync Systems. By Edward M. Noll.....	22
TV Variable Inductance Tuning. By John B. Ledbetter.....	14
Views and News. By Lewis Winner.....	9

CIRCUITS

Alignment Test Setup for Taxicab Equipment.....	10
Bendix 235M1 and 235B1 (Cover).....	20
Continuous Tuning 44-216 Mc TV Circuit.....	15
Electrostatic Picture-Tube Voltage Circuit.....	19
Electromagnetic Picture-Tube Voltage Circuit.....	19
Farnsworth GY-260 Horizontal AFC Circuit.....	30
G.E. 810 TV Chassis.....	28
Inter-Sync TV Circuits.....	22
LP Filter Circuits.....	16
LP Equalizer Circuits.....	17
LP Pickup Circuits.....	17
Motorola Dispatcher-Receiver.....	11
Motorola Dispatcher-Transmitter.....	11
Motorola TS-5 TV Chassis.....	26

COVER

Push-Button TV Receiver (Bendix 235M1 and 235B1).....	20
---	----

SERVICING HELPS

Electrostatic Picture Tubes.....	19
Electromagnetic Picture Tubes.....	19
TV Component Applications.....	18

Index to Advertisers.....

48

Manufacturers

New Instruments . . . Components.....	46
New TV Parts . . . Accessories.....	47
News.....	46
Jots and Flashes.....	48

Entire contents Copyright 1948, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



Bryan S. Davis, President

Paul S. Weil, Vice Pres.-Gen. Mgr.

F. Walen, Secretary

A. Goebel, Circulation Manager


Cleveland Representative: James C. Munn, 2253 Delaware Dr., Cleveland 8, Ohio. Telephone: Erleview 1726

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: Miehlgan 1732
Suite 1204, Russ Building, San Francisco 4, Calif. Telephone: SUTter 1-2251

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

Set by Set, Volume by Volume - PHOTOFACT Boosts Your Profits!

Build the Service Data library that helps you earn more. Have at your finger-tips the most accurate, uniform and practical service data ever produced—everything you need for easier, more profitable work. From the moment you get them, PHOTOFACT Folder Sets and Volumes pile up increasing profits for you, month after month, year after year. For success in servicing, for bigger earning power, you owe it to yourself to keep your PHOTOFACT library up-to-date!

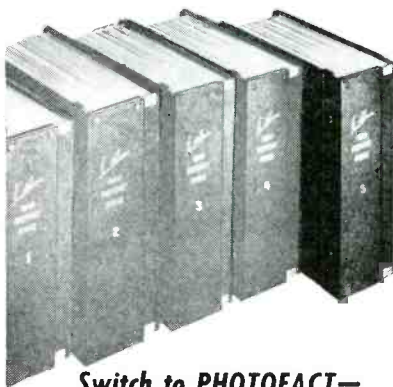

Switch to PHOTOFACT—
the Best Service Data Buy
You'll Ever Make!


Your Price
Each Volume, **\$18³⁹**
In Deluxe Binder

NOW! PHOTOFACT VOLUME 5 ON SALE AT YOUR JOBBER'S TODAY!

Latest addition to the famous PHOTOFACT Volume series—brings your file of postwar receiver service data right up to December 1948! Most accurate and complete radio data ever compiled—preferred and used daily by thousands of Radio Service Technicians. Everything you need for faster, more profitable servicing: Exclusive Standard Notation Schematics; photo views keyed to parts lists and alignment data; complete parts listings and proper replacements; alignment, stage gain, circuit voltage and resistance analysis; coil resistances; record changer service data, etc. Order Volume 5 today—keep ahead with Photofact—the only Radio Service data that meets your *actual* needs!

- Vol. 5. Covers models from July 1, 1948 to Dec. 1, 1948
- Vol. 4. Covers models from Jan. 1, 1948 to July 1, 1948
- Vol. 3. Covers models from July 1, 1947 to Jan. 1, 1948
- Vol. 2. Covers models from Jan. 1, 1947 to July 1, 1947
- Vol. 1. Covers all postwar models up to Jan. 1, 1947

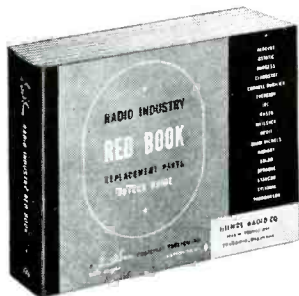You'll Use These Practical Books Every Single Working Day!



The Radio Industry RED BOOK

NOW—stop wasteful hunting through dozens of incomplete parts manuals. The RED BOOK tells you in *one volume* what you need to know about replacement parts for approximately 17,000 sets made from 1938 to 1948. Includes complete, accurate listings of all 9 major replacement components—not just one. Lists correct replacement parts made by 17 leading manufacturers—not just one. Covers original parts numbers, proper replacement numbers and valuable installation notes on: Capacitors, Transformers, Controls, IFS, Speakers, Vibrators, Phono-Cartridges. Plus—Tube and Dial Light data, and Battery replacement data. 448 pages, 8½ x 11; **\$3.95** sewed durable binding. ONLY.....

1947 Changer Manual

Complete, accurate service data on over 40 postwar Record Changer models. Shows exploded views, photos from all angles. Includes change cycle data, adjustment notes, service hints, complete parts lists. PLUS—completedata on leading Wire, Ribbon, Tape and Disc Recorders. 400 pages; hard cover; opens flat. Order now! **\$4.95** ONLY.....




Tube Placement Guide

Shows you exactly where to replace each tube in 5500 radio models, covering 1938 to 1947 receivers. Each tube layout is illustrated by a clear, accurate diagram. Saves time—eliminates risky hit-and-miss methods. 192 pages; handy index. **\$1.25** ONLY.....



Dial Cord Stringing Guide

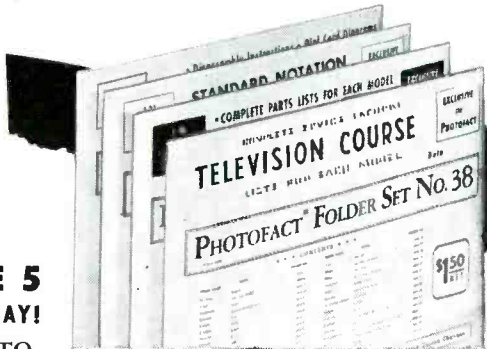The book that shows you the *one right way* to string a dial cord. Here, in one handy pocket-sized book, are all available dial cord diagrams covering over 2300 receivers, 1938 through 1946. Makes dial cord restringing jobs quick and simple. **\$1.00** ONLY.....



Stay Ahead of the Game with PHOTOFACT Folder Sets . . .

You can't afford to miss a single PHOTOFACT Folder Set! You get not only the most complete and accurate Radio Service Data ever compiled—but you keep up with fast-moving developments. Have all the advantages that make PHOTOFACT indispensable to thousands of Service Technicians—PLUS—exclusive new TV Folders on popular Television receivers—the invaluable TV Course (don't miss the sections on wave pattern trouble-shooting, and antennas)—full data on the latest Record Changers—all this in addition to full coverage of current radio models. Subscribe regularly to PHOTOFACT Folder Sets—to make your work easier, quicker, more profitable. Issued two Sets per month. Subscribe at your Jobber today, **\$1.50 PER SET ONLY.....**

FREE Photofact Cumulative Index

Send for the FREE Cumulative Index to PHOTOFACT Folders covering *all* postwar receivers up to the present. You'll want this valuable reference guide to the Radio Service Data preferred and used by thousands. Helps you find the Folders you want in a jiffy. Get this FREE Index at your Jobber or write for it now.



BOOST YOUR EARNING POWER!

Mail This Order Form to Your Parts Jobber Today
or send to HOWARD W. SAMS & CO., INC.
2924 E. Washington St., Indianapolis 7, Ind.

- My (check) (money order) for \$..... enclosed.
Send following Photofact Volumes: Vol. 5.
 Vol. 4. Vol. 3. Vol. 2. Vol. 1. (\$18.39 each).
 Send the RED BOOK. \$3.95 per copy.
 Automatic Record Changer Manual, \$4.95.
 Tube Placement Guide, \$1.25
 Dial Cord Stringing Guide, \$1.00
 Send FREE Photofact Cumulative Index.


Name.....

Address.....

City..... State.....


HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 7, INDIANA

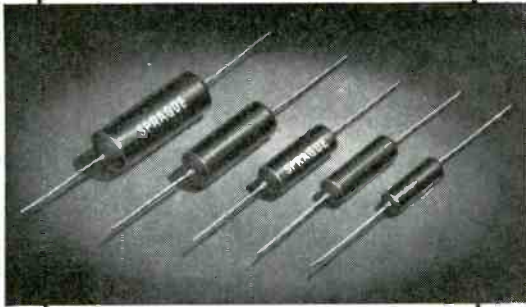Buy WHERE YOU SEE THIS BANNER
 . . . because **IT'S BETTER FOR YOU!**



SPRAGUE TM TUBULARS

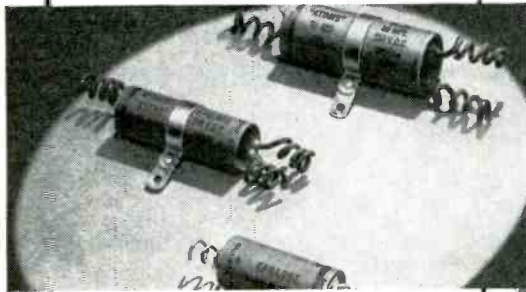The first truly practical MOLDED Paper Tubulars! Now in stock—ready for your use—See your SPRAGUE Distributor.



SPRAGUE ATOMS—DRY ELECTROLYTICS

You can make up virtually any required capacity-voltage combination with a small stock. Keep a representative supply in your shop. **SAVE TIME—SAVE MONEY—SAVE SPACE!**



SPRAGUE EL SELF-MOUNTING MIDGET CAN CAPACITORS

No other Dry Electrolytic gives so much dependability in so small a space! Tinned, Twist-Prong Tabs for easy soldering; quick, universal self-mounting. **SAVES TIME—SPEEDS RELIABLE SERVICE!**



Yes, its better for you *and your business* to buy where this banner is displayed because the SPRAGUE BANNER identifies a Distributor who agrees that *"It's foolish to play penny-ante when your business is at stake!"*

Your Sprague Distributor is a successful business man. He knows the parts business intimately—and he knows that to really build a bigger, more successful service business, you should use only the best replacement parts. That's why he features Sprague Capacitors and *Koolohm Resistors. His business depends on your success and he wants you to remember that **YOUR REPUTATION AND YOUR CUSTOMERS ARE TOO VALUABLE TO RISK FOR THE FEW PENNIES "SAVED" BY BUYING INFERIOR OR UNKNOWN "BARGAINS"!**

*Reach for a SPRAGUE
 and Know You're Right!*

Yes! We're Listed in the **RED BOOK**

Looking for the correct Sprague replacement capacitors for any receiver manufactured from 1938 to 1948? It's easy—just refer to The Radio Industry RED BOOK . . .



CAPACITORS

SPRAGUE

*KOOLOHM RESISTORS

*T.M. Reg. U.S. Pat. Off.

SPRAGUE PRODUCTS CO., North Adams, Mass. • (JOBING AND DISTRIBUTING ORGANIZATION FOR THE PRODUCTS OF THE SPRAGUE ELECTRIC COMPANY)



Bias Supply
20 V 75 MA



B+ Supply Radio
130 V 75 MA



B+ Supply Preamplifier
130 V 50 MA



Trickle Charge Assembled
18 V 700 MA



B+ Supply Radio
130 V 100 MA



B+ Supply Radio-TV
130 V 150 MA

FEDERAL Miniature Selenium Rectifiers have opened the way to NEW CONCEPTS OF DESIGN



B+ Supply Television
130 V 200 MA



B+ Supply Television
130 V 250 MA



Vibrator 160 V.
160 V 100 MA



Vibrator Doubler
160 V 75 MA




Vibrator Doubler
160 V 100 MA



Vibrator Doubler
160 V 200 MA



B+ Supply Television
130 V 400 MA

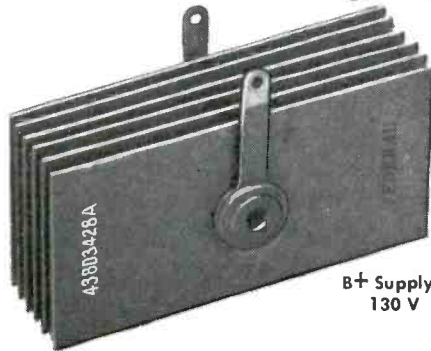

B+ Supply Television
130 V 500 MA

The Federal Miniature Selenium Rectifier has firmly established its position as a versatile new source of DC power in electrical and electronic design.

From a "Federal First" in 1946—when the nation's leading radio set manufacturers were quick to adopt it as a rectifier tube replacement—the field of application of Federal's Miniature Selenium Rectifier has expanded to a point where radio rectifier tube replacement is but one of an almost limitless variety of uses.

Today there are millions of Federal

"Minatures" in use not only in radio sets but in television, electric shavers, electronic musical instruments, inter-communication systems, mobile radio and many special applications.

Now Federal offers a line of 18 different "Minatures"—and still more are in development. It is our policy to work directly with you in specifying the right Federal Miniature Selenium Rectifier to meet your requirements. If there's not a Federal "Miniature" to handle your particular job, there can be. For information, write to Department F456.




Federal Telephone and Radio Corporation

SELENIUM and INTELIN DIVISION, 900 Passaic Ave., East Newark, New Jersey

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp. 67 Broad St., N. Y.

Build YOUR OWN TEST EQUIPMENT

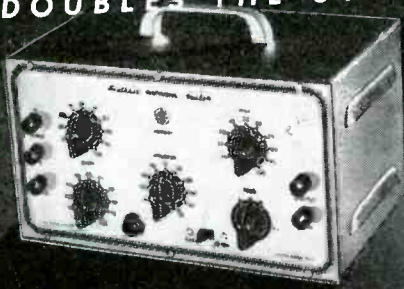Heathkit ELECTRONIC SWITCH KIT DOUBLES THE UTILITY OF ANY SCOPE



\$34.50

Gives two separately controllable traces with individual inputs on any scope.
See both the input and output traces, locate distortion, phase shift, etc., immediately.
Individual gain controls and positioning control. Coarse and fine sweeping rate controls. Complete Heathkit matches others, with 5 tubes. All metal parts are punched, formed and cadmium plated. Complete with tubes, all parts, detailed blueprints and instructions. Shipping Wt. 13 lbs.
Nothing ELSE TO BUY

HEATHKIT CONDENSER CHECKER KIT


\$19.50

*Nothing
ELSE TO
BUY*



A condenser checker anyone can afford to own. Measures capacity and leakage from .00001 to 1000 MFD on calibrated scales with test voltage up to 500 volts. No need for tables or multipliers. Reads resistance 500 ohms to 2 megohms. 110V 60 cycle transformer operated complete with rectifier and magic eye indicator tubes.
Easy quick assembly with clear detailed blueprints and instructions. Small convenient size 9" x 6" x 4 3/4". Wt. 4 lbs.

HEATHKIT SIGNAL GENERATOR KIT

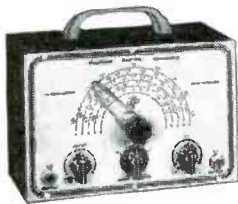


\$19.50

NOTHING ELSE TO BUY

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110V 60 cycle transformer operated power supply.
400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Wt. 4 1/2 lbs.

HEATHKIT SIGNAL TRACER KIT

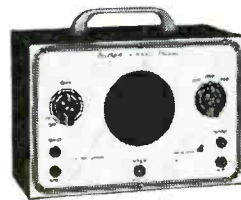


\$19.50

Nothing ELSE TO BUY

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110V 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions.
Small portable 9" x 6" x 4 3/4". Wt. 6 pounds. Ideal for taking on service calls. Complete your service shop with this instrument.

HEATHKIT SINE AND SQUARE WAVE AUDIO GENERATOR KIT

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110 V 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability. Shipping weight 15 pounds.

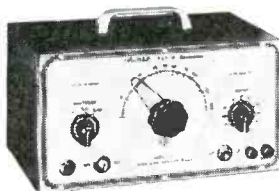


\$34.50

*Nothing
ELSE TO BUY*

THE NEW HEATHKIT VACUUM TUBE VOLTMETER KIT

The most essential tool a radio man can have, now within the reach of his pocketbook. The Heathkit VTVM is equal in quality to instruments selling for \$75.00 or more. Features 500 microamp meter, transformer power supply, 1% glass enclosed divider resistors, ceramic selector switches, 11 megohms input resistance, linear AC and DC scale, electronic AC reading RMS. Circuit uses 6SN7 in balanced bridge circuit, a 6H6 as AC rectifier and 6 x 5 as transformer power supply rectifier. Included is means of calibrating without standards. Average assembly time less than four pleasant hours and you have the most useful test instrument you will ever own. Ranges 0-3, 30, 100, 300, 1000 volts AC and DC. Ohmmeter has ranges of scale times 1, 100, 1000, 10M and 1 megohm, giving range .1 ohm to 1000 megohms. Complete with detailed instructions. Add postage for 8 lbs.

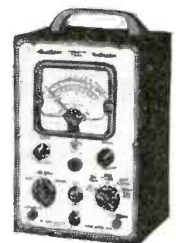

\$24.50

*Nothing
ELSE TO BUY*

HEATHKIT FM AND TELEVISION SWEEP GENERATOR KIT



\$24.50

NOTHING ELSE TO BUY

THE BASIC FM AND TELEVISION SERVICE INSTRUMENT

At the lowest cost possible, anyone can now service FM and television receivers. The Heathkit sweep generator kit operates with oscilloscope and covers all necessary frequencies. A few pleasant hours assembling this kit puts any organization in position to share the profits of the FM and TV boom.
Every part supplied — grey crackle cabinet, two color calibrated panel, all metal parts punched, formed and plated. 5 tubes, complete detailed instructions for assembly and use. Shipping weight 6 lbs.

The NEW 1948 HEATHKIT 5 INCH OSCILLOSCOPE KIT



\$39.50

NOTHING ELSE TO BUY

New improved model of the famous Heathkit Oscilloscope. Building an oscilloscope is the finest training for television and newer servicing technique and you save two-thirds the cost. All the features and quality of instruments selling for \$100.00 or more. Supplied complete with cabinet, two color panel, 5B1 tube, 2 5Y3 tubes, 2 6J5J tubes and 8B4 sweep generator tube. Power transformer supplies 1000V negative and 350 volt positive. Sweep generator 15 cycles to 30 M. cycles. Has vertical and horizontal amplifiers. Oil filled filter condensers for long life. Complete blueprints and instructions included.



The **HEATH COMPANY**

... BENTON HARBOR 11, MICHIGAN

RIGHT FOR SERVICING HOME RECEIVERS

Now, A Replacement Line of Chicago Transformers & Reactors



Now available in principal cities, this new replacement transformer line fits a wide range of the service man's most frequent power and audio requirements and fills, as well, the needs of the amateur and experimenter for efficient, standard-type ratings at low cost.

Here's transformer design and construction you can rely upon to give accurate, dependable performance. Every unit is backed by Chicago Transformer's reputation for quality . . . established in over 20 years of designing and producing original equipment transformers for the nation's leading set manufacturers.

RMA color-coded leads, tinned lead ends, and compact, standard-dimension mountings make for easy installation at the service bench. Included in the line are power transformers and chokes, filament, driver, speaker matching, interstage, and output transformers in a range of carefully chosen, practical ratings.

Ask for *Chicago Replacement Transformers* the next time you call or visit our parts jobber. *In the meantime . . .*

WRITE FOR CATALOG

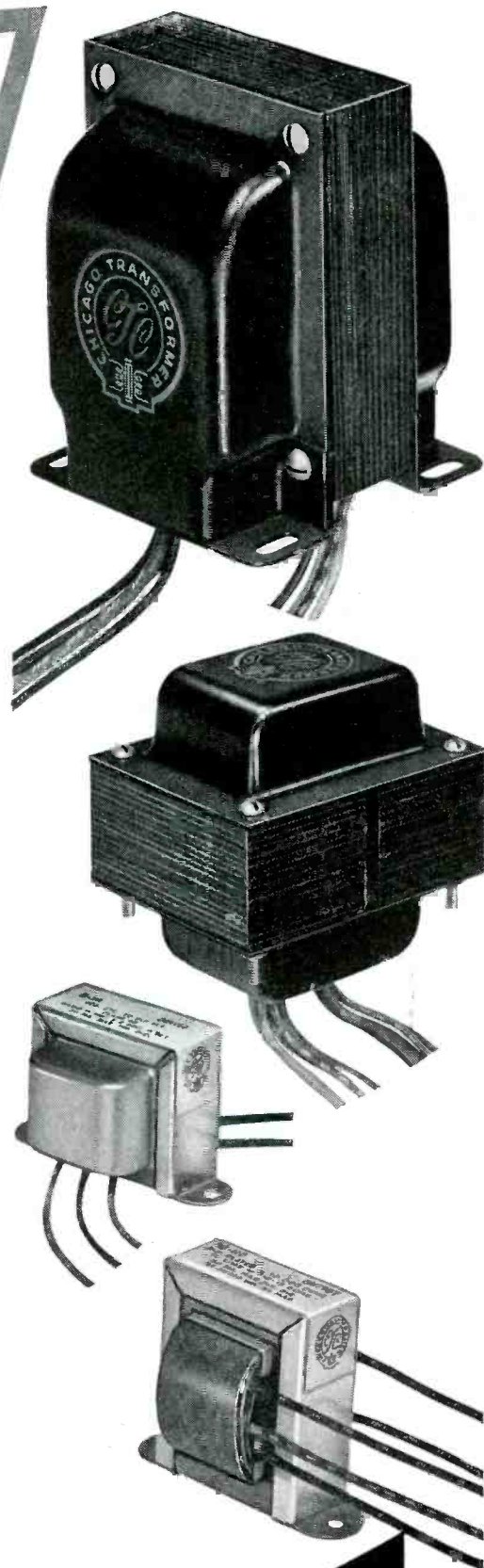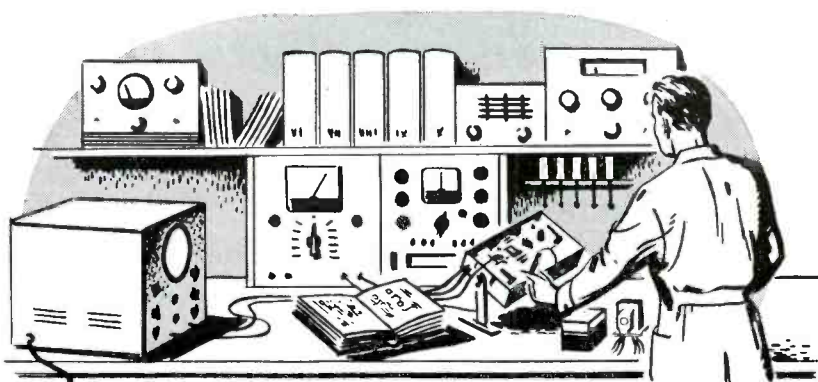



CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION

3501 ADDISON STREET • CHICAGO 18, ILLINOIS



AUTO RADIO and HYTRON go together

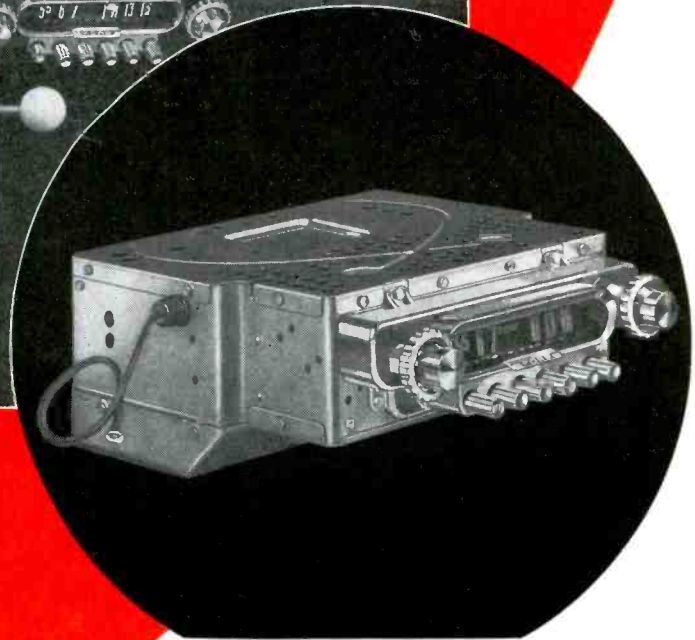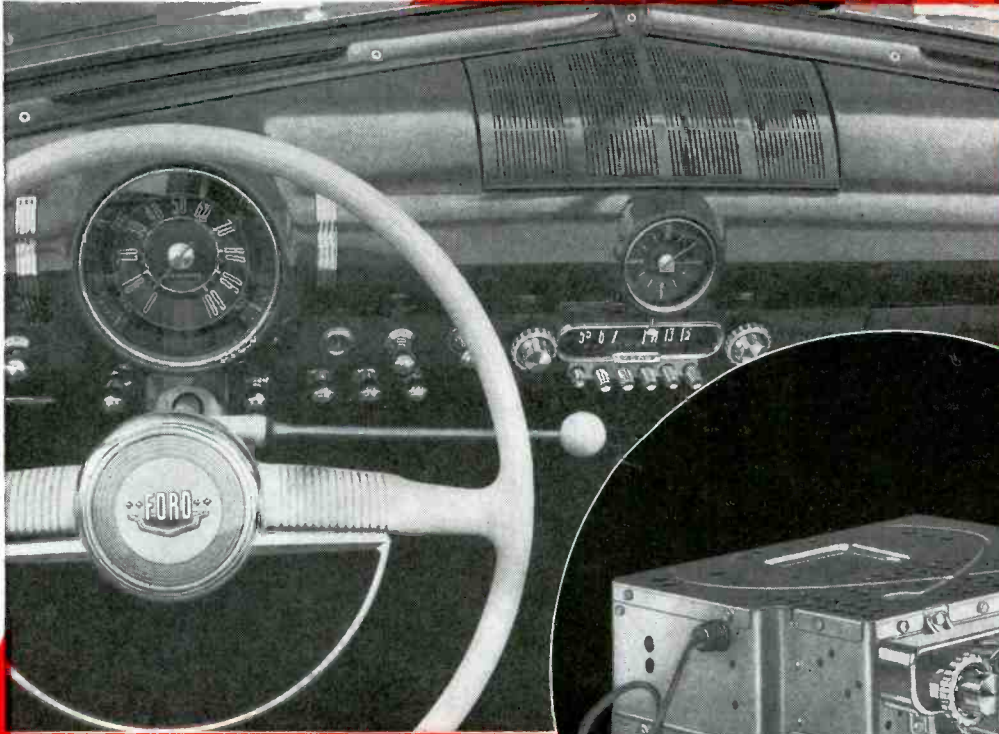

"A Ford in your future?" There will probably be a fine new Ford radio receiver on the dash. Chances are good this receiver will be equipped with tubes by Hytron. For Hytron is a major supplier of Ford auto radio tubes. That is only natural. Hytron *specializes* in auto radio tubes — both GT and miniature. Close engineering co-operation with leaders like Ford help make Hytron auto radio tubes leaders, too. 'Nuff said. Hytron and auto radio go together.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921.

HYTRON

RADIO AND ELECTRONICS CORP.

MAIN OFFICE: SALEM, MASSACHUSETTS



RADIO · TELEVISION · ELECTRONIC
SERVICE

The Service Man in 1948

FEW YEARS IN THE HISTORY of *Servicing* have been as significant . . . in economic, technical and social advancements . . . as 1948. This has been a year of dominant progress for the Service Man on all fronts . . . a year during which industry and the consumer have become more cognizant than ever before of the important role the Service Man plays in the life of Mr. and Mrs. America.

To television, the Service Man owes much of his thanks for the accented appreciation of his talents. For the first time in a score of years, the Service Man has been able to demonstrate effectively what his know-how means and how his special schooling in the knotty aspects of the art can assure the full bright enjoyment of sight and sound to every home.

The telecaster has been extremely grateful to the Service Man for keeping the picture tubes going and maintaining his much-needed audience. Without the installation of the proper antenna, matched lines, correct adjustment of sync circuits, proper positioning of the picture tube and its accessories, and the particularly important instruction to set owners, the Hooper rating of TV programs would be at a dismal low.

Town meetings and clinics have been extremely important features of '48 too, providing valuable information on all phases of servicing, from bookkeeping, sales, and credit to shop and field work in AM, FM, TV, instruments and sound.

The town meetings in Philadelphia, New York and Boston were hosts to over 6,000 Service Men who heard well-prepared and illustrated talks by such experts as John F. Rider, John A. Meagher, Ira Kamen, Edward M. Noll, Harry P. Bridge, Austin C. Lescarboura, Bill Parkinson and dozens of others. Next year Atlanta, Georgia; Los Angeles, and Chicago will play hosts to these meetings with the Atlanta meeting scheduled for January 31, February 1 and 2 in the Municipal Auditorium, and the Los Angeles gathering at the Roger Young Auditorium on February 28, March 1 and 2. The Chicago clinic is expected to be held in the early spring months.

Attendees at the town meetings were

also privileged to hear RMA prexy Max Balcom, who keynoted the meetings with very illuminating talks. During one meeting Mr. Balcom said, "I know that we manufacturers often have failed to recognize the importance of the Service Man who services the sets we make. And I suspect that many of you have not always understood the problems we manufacturers have been up against when you struggle to repair a receiver of an unusual or intricate design.

"But as often happens, we are being brought closer together today by force of circumstances: primarily by television and secondarily by FM broadcasting. I believe that this closer cooperation will prove beneficial to all . . . the Service Man, distributor, dealer and the manufacturer.

"All of us in the industry are having to, in effect, go back to school to keep abreast with the rapid developments in television. While closely akin to standard receiver practice, television is different in so many respects that everyone, from the design engineer to the salesman, has had to start from scratch to produce and market this new and exciting production. Television requires new production techniques and know-how. It requires new marketing and selling methods. And TV sets require new servicing knowledge and practices.

"The servicing of home receivers, particularly the new TV sets, is rapidly becoming a big business, and it will require well-trained men who are familiar with the instrument they are servicing and the most modern techniques for detecting and correcting any trouble that may develop."

Associations held their own clinics, too, in '48 and very successfully. The New York group initiated a program on TV which began in October, '48, and will last until May, '49. Every branch of TV servicing has been scheduled: antennas, front ends and *if* systems, video amplifiers, horizontal and vertical sync circuits, low- and high-voltage power supplies, picture tubes, alignment and servicing test equipment.

The Pennsylvania State Federation group held a series of clinics at each of its chapters during '48, with John F. Rider as guest speaker, covering

antennas and instruments. Service associations in the Middle West and on the Pacific Coast also heard Al Saunders deliver his popular talks on TV.

Distributors and manufacturers were also active TV clinic holders in '48, with scores of bigger and better meetings scheduled for '49. Even those areas where television is months away became TV conscious in '48 and set up clinics. In Kansas City, for instance, the Electric Association of Greater Kansas City prepared a year-long course, which was underwritten by ten major distributors in the area, each of whom contributed \$125 to establish the program. The cost of the course to the student, \$53, was in most cases paid for by the local association and distributors. Some of these expenses were also borne by the Missouri State Board of Education. Another excellent example of clinic work was presented by the Northern Illinois and Wisconsin distributors and associations with a crowded two-day session which began at 8:30 A.M. and ended about 5:30 P.M. Over one hundred Service Men attended these streamlined TV clinic sessions.

Associations once again became a factor in '48, contributing to the remarkable strides in consumer and industry acceptance of the Service Man. Excellent codes played quite a part in cementing this friendship. One such code adopted during the Philadelphia Town Meeting and prepared by the delegates of the Federation of Radio Service Men's Associations of Pennsylvania, set a fine example around which many codes were prepared. The code said in part: "I will at all times, without any exceptions, perform my work to the very best of my knowledge and ability. In addition, I will make a sincere effort to improve my knowledge of the technical and business requirements of my profession, thereby enabling me to render still better radio-electronic service. . . . I will engage only in fair and ethical practices recommended and approved by the radio-electronic profession as being conducive to public confidence."

Yes, the Service Man grew in '48 and today he is the perfect liaison between industry, broadcaster and consumer. In '49 we are sure that his stature will continue to grow.—L. W.

Servicing Taxicab Radio

Typical Troubles Encountered in Servicing Two-Way Systems Operating in 152-162 Mc Bands and How to Remedy Them... Composite Characteristics of 15 Types of Receivers and Transmitters... Charges Usually Made for Mobile System Servicing.

IN THE PREWAR days two-way systems operated on the 30-40-mc band. Today taxicab two-way equipment is required to operate in the new postwar 152-162-mc band. There are three major differences between the low- and high-band systems:

(1) More tubes are employed in both the transmitter and the receiver. This is due to increased frequency multiplication of the transmitter crystal frequency. In the case of some receivers, it is due to the use of double conversion in the superhet receiver.

(2) The four-fold increase in frequency or four-fold reduction in wavelength begin to manifest conditions that are common on microwaves... increased inductive reactance, reduced capacitive reactance, appreciable distributed capacitance and inductance for the frequency involved. We also have quarter-wave problems with which to contend; conditions invert every quarter wavelength (or every 20") for any conductor. Thus it is necessary to use very short lengths of wiring to avoid resonant line effects.

(3) Although more tubes are employed, they are usually of the receiving type. The 6AK5 is one of the

by SAMUEL FREEDMAN

New Developments Engineer
DeMornay-Budd, Inc.

most popular in use, where the 6AC7 was the popular low-band prewar tube.

The composite receiver based on average specifications of fifteen manufacturers comprises 14.3 tubes ranging from a minimum of 12 to a maximum of 17. The receivers may use:

- (a) One or two stages of *rf* amplification.
- (b) An oscillator-multiplier or an oscillator and a harmonic amplifier, the oscillator being crystal controlled.
- (c) A first mixer at a high *if* frequency.
- (d) Two or three *if* stages.
- (e) A discriminator.
- (f) Two stages of audio.

Some receivers also use a second mixer at a low *if* frequency. Other special features include noise amplifier, noise rectifier, squelch, and synchro-cycle control (an *afc* provision

which locks the receiver to transmitter frequency), etc.

The Transmitter


The composite transmitter based on average specifications of fifteen manufacturers uses nine tubes ranging from a minimum of six to a maximum of twelve. Transmitters usually have:


- (a) A pair of modulator tubes.
- (b) A crystal-controlled oscillator.
- (c) Four or five frequency multiplier stages operating as either doublers, triplers or quadruplers to raise the crystal frequency in the oscillator stage to that of the output frequency in. Out of the fifteen setups analyzed, seven use a frequency multiplication of 48, two use 36 times, two use 54 times, two use 96 times, one uses 32 times and one 64 times. Typical examples of frequency multiplication actually employed are: 32 times (one quadrupler and three doublers), 36 times (two triplers and two doublers), 48 times (one quadrupler, one tripler and two doublers), 54 times (three triplers and one doubler), 64 times (two quadruplers and two doublers), 96 times (one quadrupler, one tripler and three doublers).

The transmitter output tubes and the rated power outputs are:

Manufacturer	RF Output Tube	Rated Output
Motorola		
Dispatcher..	2E26	7 to 10 watts
Raytheon	832A	15 watts
Link	829B	15 watts
Comco	3D23	15 watts
Wilcox	832A	15 watts
General		
Electric....	(2) 2E24	15 watts
Kaar	(2) 5515	20 watts
Western		
Electric ...	(2) 2E24	20 watts
RCA	(2) 2E24	20-25 watts
Federal	(2) 5516	25 watts
Mobile Communications.	632A	25 watts
Harvey	(2) 5516	30 watts

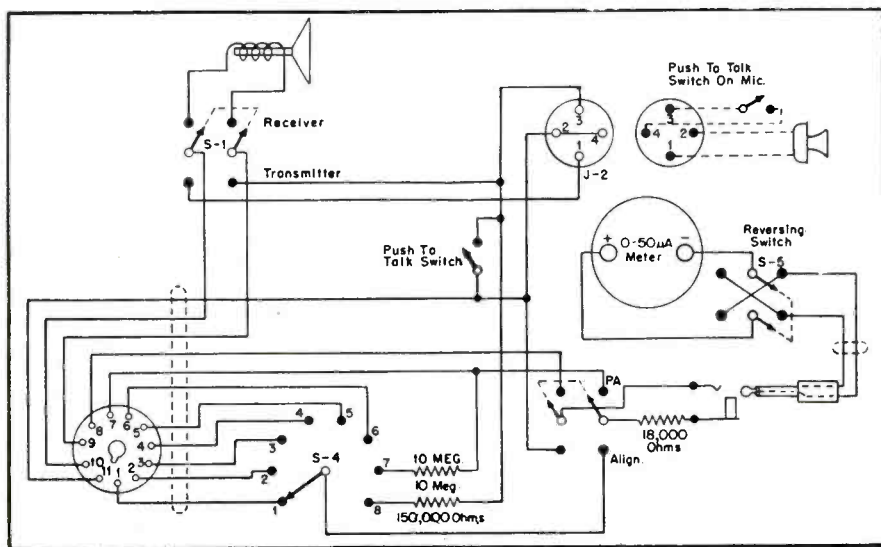Test set plan used for the alignment of the dispatcher.



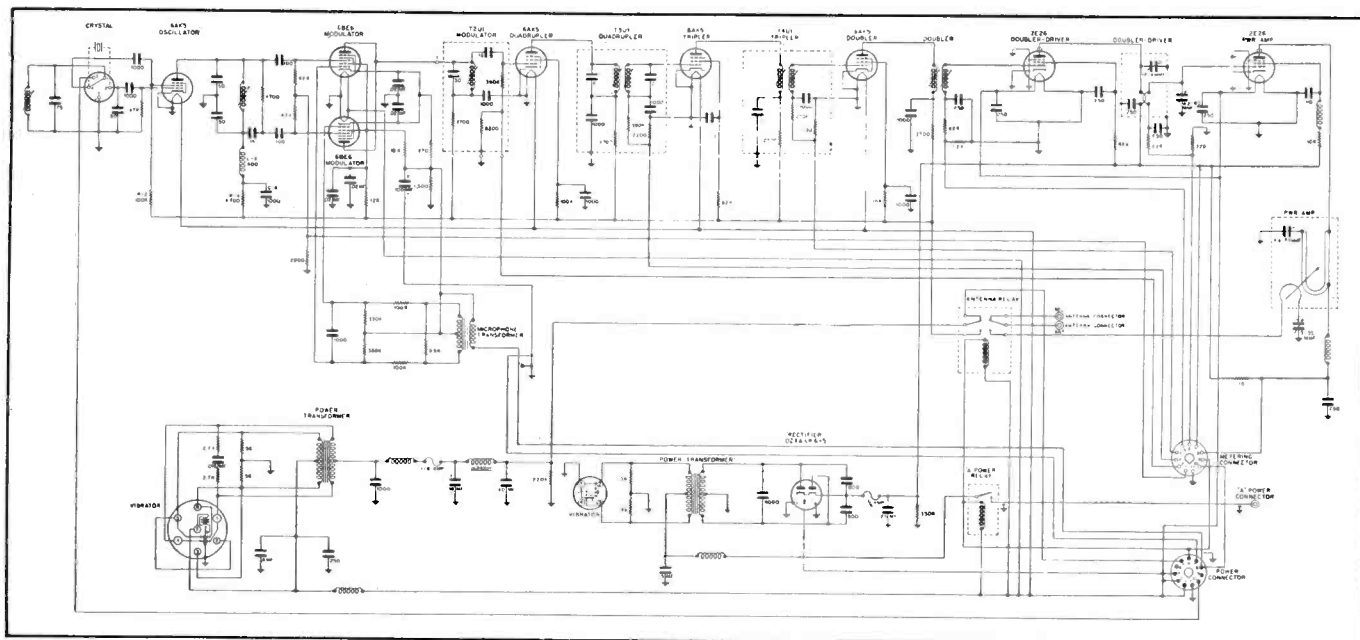

Temco	829B	30 watts
Doolittle	(2) 2E24	30 watts
Motorola		
Standard ..	(2) 2E24	30 watts

Fig. 1. Circuit of the Motorola dispatcher transmitter.

problems can be detected by three symptoms:

General Mobile Radio Troubles


The troubles likely to be encountered with any type of mobile two-way radio equipment are:


(1) Worn rotating or switching parts. Eventually any part that moves, turns or slides to make contact will require replacement. Usually these

(a) Loud scratching or intermittent signal as volume control is moved. It may also reveal itself at the volume control by getting weaker instead of louder as the setting is advanced.
 (b) Failure of circuit to close when

(Continued on page 40)

Fig. 2. The Motorola dispatcher receiver circuit. 6VH6s are used for first and second rf; 6BJ6, first mixer; 6BJ6, second quadrupler; 6BJ6, first quadrupler and oscillator; two 6BJ6s in dual if stages; a 6BH6 as a second mixer; another 6BJ6 in the second if stage; two 6BJ6s in the first and second limiter stages; a 6AL5 as a discriminator; 6BH6, noise amplifier; 6AL5, noise rectifier; 12AU5, first audio and squelch and 6AQ5, power amplifier. The first and second rf stages cover the 152-162 mc bands, points 1 and 2. At 3 is the second quadrupler covering 144-157 mc; point 4 is the first quadrupler for 36 to 39 mc. At 5, 6 and 7 are the 7.3-8 mc if stages. The 1.7-mc limiter is at 9 and at 10 and 11 are the 1.7-mc limiter and discriminator tubes, respectively.

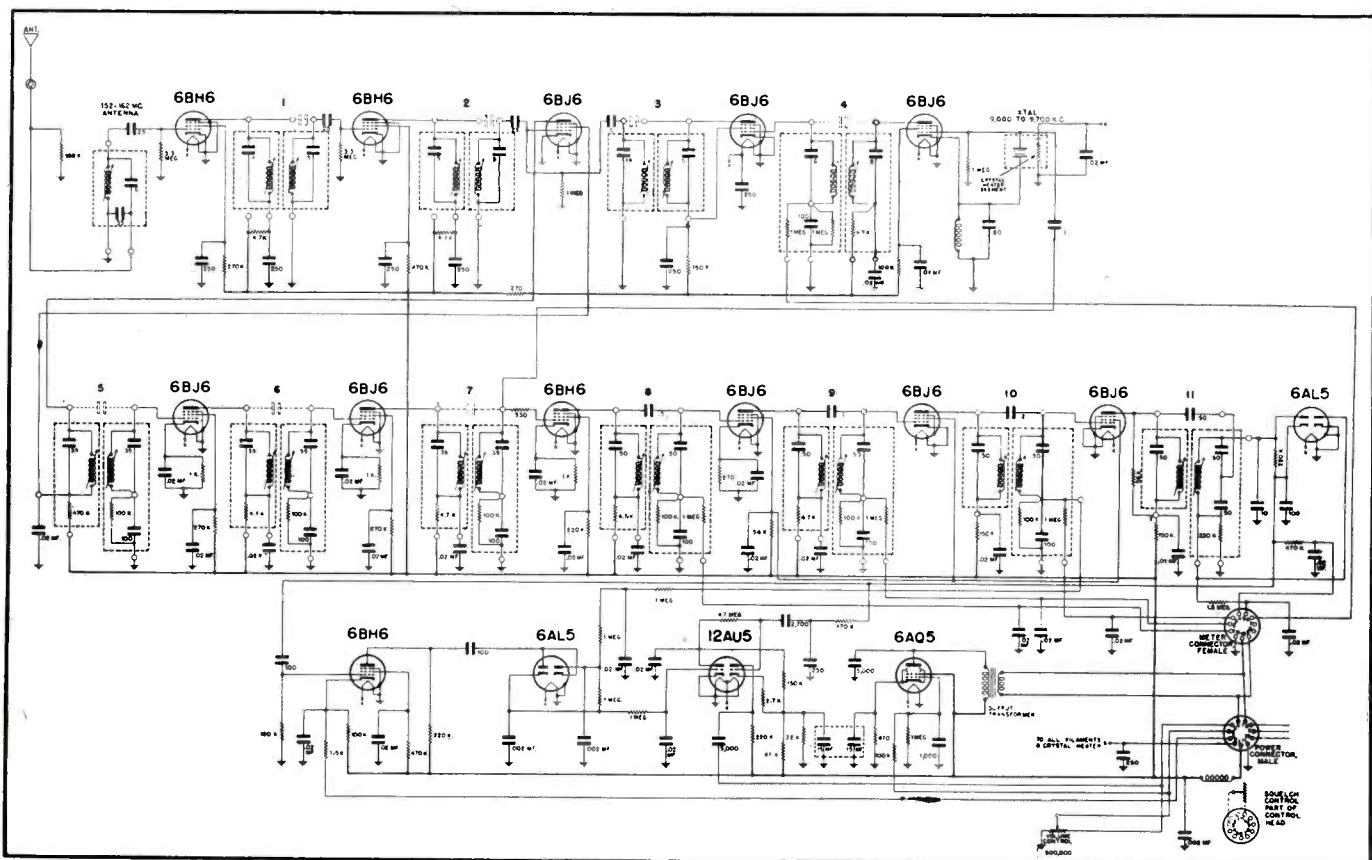

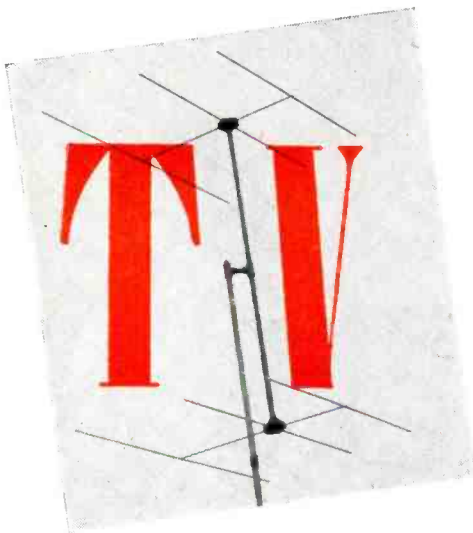

Installations In FRINGE AREAS

by **IRA KAMEN**

Manager, Television Antenna Dept.
Commercial Radio Sound Corp.
New York City

TELEVISION RECEPTION in fringe areas (over 45 miles from the TV transmitters) is dependent on three fundamentals:

- (1) Signal-to-noise ratio in the area.
- (2) Gain and directivity of the television antenna.
- (3) Sensitivity of the television receiver.

The signal-to-noise ratio in any fringe area can usually be improved by increasing the height of the TV antenna and by selecting antennas with a narrow horizontal and vertical pick-up pattern.


The gain and directivity of any antenna array depends upon the number of dipole and parasitic elements assembled within the array.

The simplest stacked array used for bi-directional high gain pick-up is the double dipole which narrows the vertical angle of the antenna's pick-up pattern; Fig. 1a. Narrowing the vertical pick-up angle improves signal-to-noise ratio because:

- (1) The TV signal from the station develops in-phase voltages on the dipole elements which *add up*, in

Fig. 4 (above). Double stacked array of dipole, director and reflector. (Courtesy Workshop Associates)

Fig. 2. Stacked folded dipoles and reflectors. Impedance at the mean frequency (channels 4 or 10) is approximately 150 ohms.

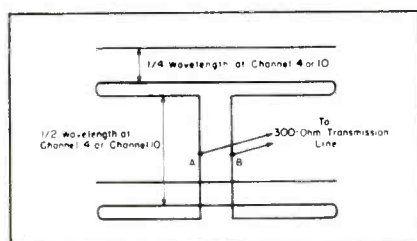


phase, at the input to the transmission line.

(2) Aperiodic noise fields from sources above or below the dipoles develop voltages are out of phase at the transmission line input and therefore tend to cancel.

The signal-to-noise ratio of this antenna is further improved when reflectors are added behind each dipole (common *Lazy H*, Fig. 1b) as the horizontal television signal pick-up angle is concentrated in one direction and therefore noise fields from the direction are rejected. In addition, the gain of the antenna is increased. The reflectors are usually placed one-quarter wavelength behind the dipole elements. This one-quarter wavelength spacing is adjusted for the

Fig. 1. In a appears a setup for a stacked dipole for the 2 to 6 channels adjusted for the mean frequency (channel 4 or 10). Impedance at points A and B is approximately 36.5 ohms at channel 4 or 10. In the layout, the rods are 1/4 wavelength at channel 4. In b is a *lazy H* stacked dipole with reflectors.

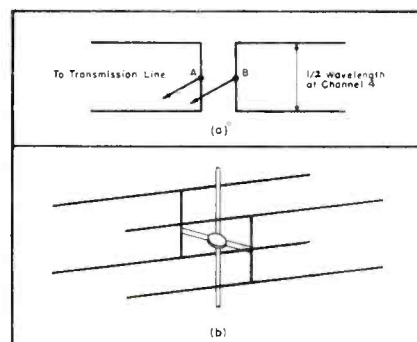


mean frequency to which the dipole elements are cut. When the elements are cut and adjusted for channel 4, the antenna is usually satisfactory for channels 2 to 6, and when they are adjusted for channel 10, the antenna may be used for channels 7 to 13.

Folded dipoles may also be stacked, with or without reflectors, for high gain and directivity in one TV band (channels 2 to 6 or 7 to 13); Fig. 2. This antenna is best matched to 300-ohm line.

Perfect matching of coax or 300 ohm-twin lead transmission lines to a TV antenna over the entire band is not practical and relatively unimportant, providing the mismatch is not severe. A mismatch between the antenna and the transmission line of 3:1 produces a loss of only a few db in power. The mismatch in impedance at the antenna *does not affect the quality of the picture when the receiver input matches the impedance of the transmission line.*

Another method of increasing the signal-to-noise ratio of a TV antenna is to place a director in front of a folded dipole or straight dipole and

Fig. 3. At a, a folded dipole (with director and reflector) adjusted for broadband and directivity at channels 2 to 6. At b we have dipole director and reflector assembly adjusted for single channel high gain and directivity.

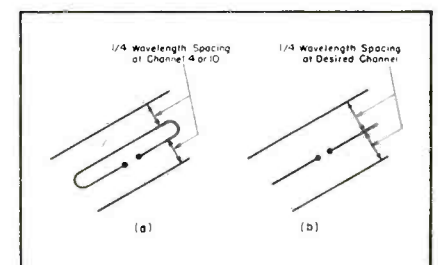

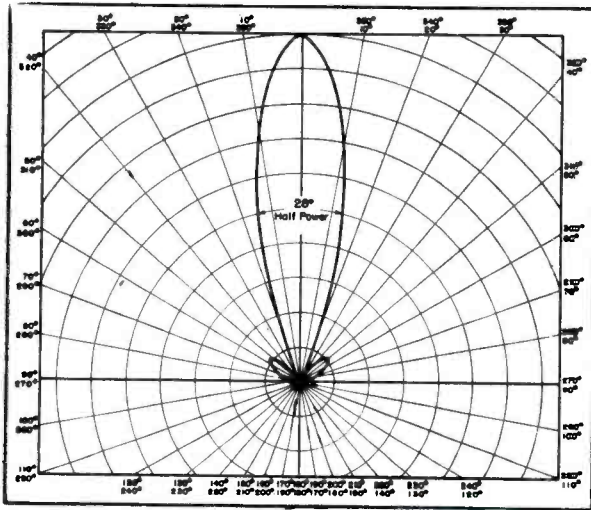


Fig. 6 (above). Horizontal pattern of antenna shown in Fig. 5.

(Courtesy Workshop Associates)

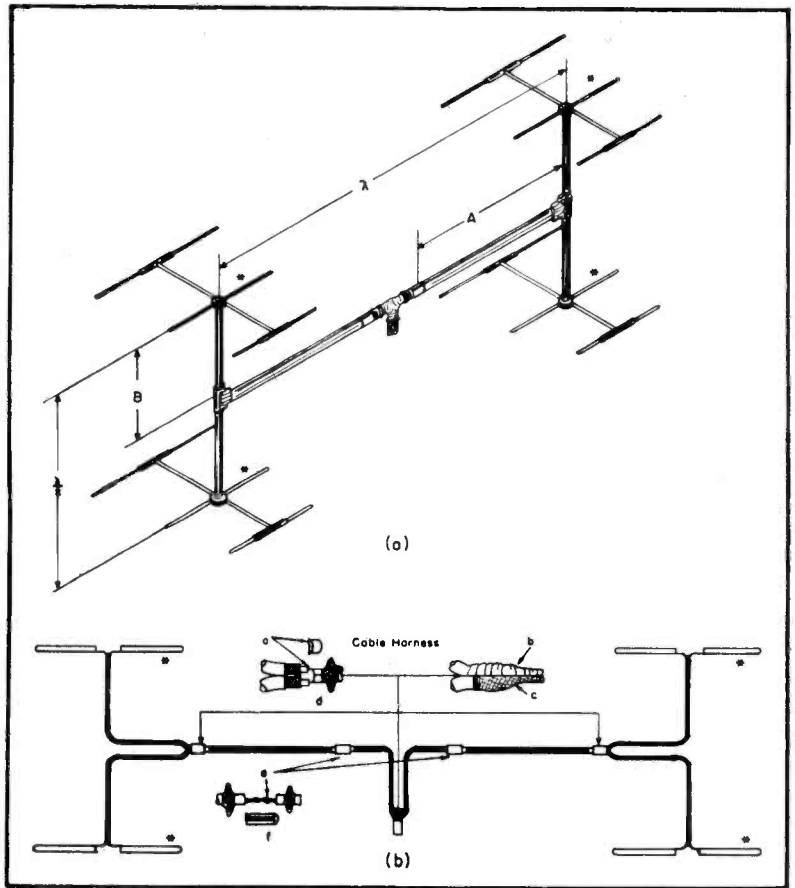


Fig. 5 (right). Dual-double stacked array of dipoles, directors and reflectors. To secure maximum efficiency with this system the element must be spaced very carefully: Channel 3 (63 mc) distances between λ are $187 \frac{19}{64}''$; A , $89 \frac{17}{32}''$ and B , $45 \frac{43}{64}''$; channel 4 (69 mc) distances between λ are $171 \frac{1}{64}''$; A , $81 \frac{1}{8}''$ and B , $41 \frac{19}{32}''$; channel 5 (79 mc) distances between λ are $149 \frac{23}{64}''$; A , $70 \frac{9}{16}''$ and B , $36 \frac{3}{16}''$; Channel 6 (85 mc) distances between λ are $138 \frac{53}{64}''$; A , $65 \frac{9}{32}''$ and B , $44 \frac{35}{64}''$; for FM (97 mc) distances between λ are $121 \frac{41}{64}''$; A , $56 \frac{45}{64}''$ and B , $29 \frac{1}{4}''$; channel 8 (183 mc) distances between λ are $64 \frac{31}{64}''$; A , $28 \frac{7}{64}''$ and B , $14 \frac{31}{32}''$; channel 10 (195 mc) distances between λ are $60 \frac{33}{64}''$; A , $26 \frac{1}{8}''$ and B , $13 \frac{31}{32}''$; channel 12 (207 mc) distances between λ are $57''$; A , $24 \frac{3}{8}''$ and B , $13 \frac{3}{32}''$. The RG-58/U or RG-59/U cables running to the elements are also cut to exact lengths for the eight frequencies. In (b) at a , b , c and d , appears details of the junction connection, which is soldered and covered with split sections of insulation; b , tape; c , wire binding and solder d , solder. At e , appear details of the junction connection, which is soldered and covered with split sections of insulation. The joint is then wire bound, soldered and taped as shown at f . All dipoles* connected to the inner conductor of the coax cable are to be pointed in the same direction.

reflector assembly; Figs. 3a and b. The addition of the director element to these antennas beam their pick-up pattern so that the area in which noise can induce energy into the antenna is reduced. This type of antenna usually has a gain of 5 to 6 db. The folded-dipole antenna array is preferred where complete TV (2 to 6 or 7 to 13) coverage is required. The straight dipole is preferred for single and adjacent channel operation.

The reflector element is usually 5% longer than the dipole element. The director element is approximately 5% shorter than the dipole. These parasitic elements do not normally reduce the antenna's impedance by more than

25%. The folded dipole array should be connected to a 300-ohm transmission line and the straight dipole array to a 52 or 73-ohm coax cable. The forward gain of this type of antenna can be increased to 7.5 db and the vertical pick-up pattern reduced to 64° by stacking two dipole-director-reflectors arrays; Fig. 4.

The maximum practical gain (11 db) and the narrowest pick-up angle (28°) which can be realized with this antenna principle is available with a dual-double stack array; Figs. 5 and 6.

This array should be used for single channel reception only. Several of these complex arrays may be cir-

cuit to a single TV receiver through a coax switch. When a TV receiver with a 300-ohm input is used, a 50/300 matching transformer can be circuited between the coax cable and the television receiver for proper matching.

Another type of fringe area antenna combines a low-channel stacked array and a high-channel three-element directional beamed antenna; Fig. 7. These two antennas may be circuited together if there is no interaction between the high and low-channel antenna units; Fig. 8. The technique of determining interaction between antenna units has been described in an

(Continued on page 42)

Selecting the Best Antenna System For Installations Which Are Over 45 Miles From the TV Station . . . Determining What Type Booster To Use . . . Choosing the Proper Low-Loss Leadin Cable.

TV Variable-

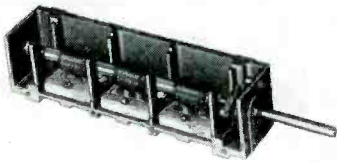


Fig. 1. View of Inductuner.

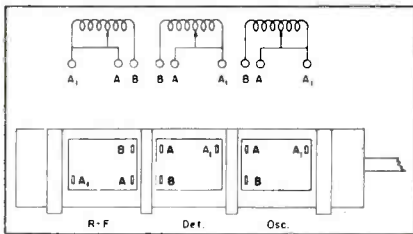


Fig. 2. How the coils are connected in tuner for rf, detector and oscillator circuits.


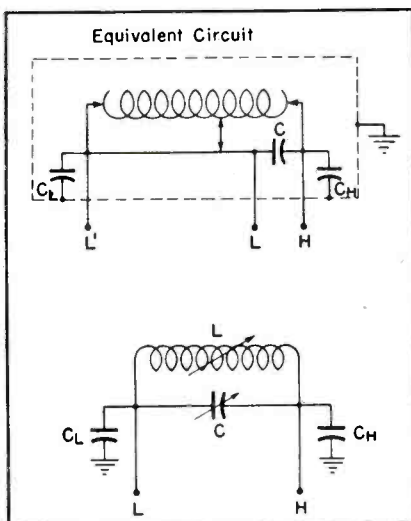


Fig. 3. Circuit analysis of the tuner. The two-terminal network appears as a variable-inductance element which includes stray capacities (C_H and C_L from terminals H and L , respectively, to ground).

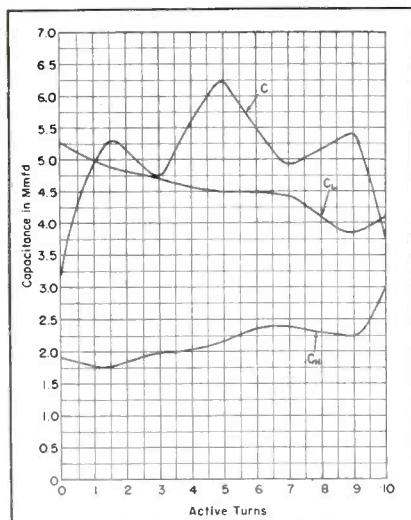

ONE OF THE MAJOR problems in vhf tuning systems has been the rather limited band of frequencies which could be covered in one continuous tuning range, these limits in ordinary capacity-tuned circuits being governed by distributed and lumped capacity effects and a loss of efficiency at the higher frequencies. To satisfy quasi-optimum performance, a different tuning capacity must be used for each band of frequencies. Since this could lead to rather impractical ends in a receiver designed to cover a number of distinct frequency bands, either a compromise in tuning capacity must be made with the attendant sacrifice in efficiency, or another means of tuning must be sought. In most commercial communications receivers covering broadcast, amateur and government frequencies, this problem is satisfactorily solved by utilizing split-section tuning capacitors in conjunction with a rotary band switch, the proper amount of capacity for one or more bands being switched into the circuit. Although this method is the most practical in ordinary communications-type receivers where frequency ranges of 550 kc to 30 or 40 mc are encountered, distributed capacity and circuit losses in the tuning system and bandswitch begin to assume relative proportions as the tuning range is extended into the higher frequencies. At TV and FM frequencies, especially, where overall gain, bandwidth, signal-to-noise ratio, image rejection and circuit stability must approach optimum values for each of the individual channels, the usual variable-capacitor system of tuning leaves much to be desired.

Variable-Inductance Tuning for High Frequencies

In tuning systems employing variable inductances instead of the usual variable capacitances, several distinct

*Registered trademark of P. R. Mallory & Co., Inc., for variable inductance tuning devices, manufactured under Paul Ware Mallory patents.

Fig. 4 (left). Inter-terminal capacitance of a 10-turn Inductuner; measurements made at 1,000 kc. C = capacitance between terminals; C_H = capacitance between high side terminal and frame of tuner; and C_L = capacitance between low side terminal and frame of the tuner.


Fig. 5 (right). Oscillator and mixer frequency curves using the 10-turn Inductuner with an *if* frequency of 11 mc. Output voltage (A) was measured with Measurements Corp. model 62 *vtvm* with a *vhf* diode.

advantages are realized. First, a high order of overall circuit stability and efficiency can be maintained since the lumped capacities associated with tuning capacitors are non-existent. Second, it is possible to maintain, or increase, the Q as the frequency is increased by the use of a fixed series inductor of low loss construction. By careful design and apportioning of circuit constants, it is possible to reduce the circuit losses at a rate faster than the increase in circuit frequency. This allows a rise in gain at the higher frequencies which may be used to advantage in compensating for high-frequency losses in other parts of the receiver tuning system. Another main advantage is the ability of an inductance to tune over a much wider range of frequencies than is possible with a variable capacitance, due to the smaller minimum capacity of the inductance.

The Inductuner*

Extensive development work has resulted in production of the *Inductuner*, an infinitely variable inductance unit capable of tuning an extremely wide range of frequencies (44-216 mc) in one continuous range.

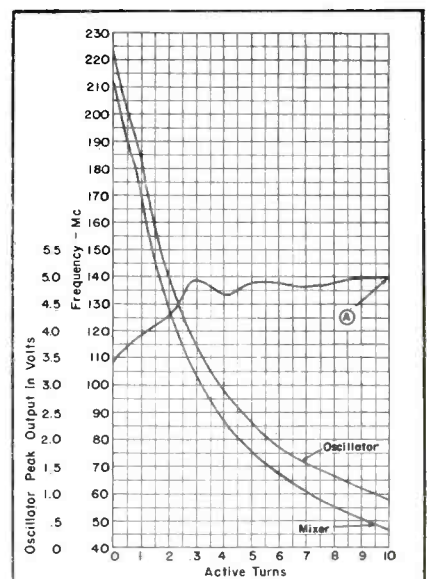In Fig. 1 appears a view of the *Inductuner*. Essentially, the unit consists of three separate variable inductance units ganged on a rotatable ceramic and brass shaft. Each coil is equipped with a sliding shorting mechanism which varies its inductance in proportion to rotation of the shaft. Rotation allows the inductance to vary from approximately .02 to 1.0 micro-



Inductance Tuning

Design and Application of VHF Tuning System Used in TV Receivers (Du Mont) Which Permits Wide-Band Tuning and Rising Gain in Higher Frequencies.

by JOHN B. LEDBETTER

Engineer, WKRC-TV, WCTS-FM

henry, which provides an inductance ratio of 1:50. Maximum to minimum inductive tuning is obtained by rotating the shaft through 10 turns or 3,600°.

To raise the natural frequency of the unused turns above the operating range of the tuner, the unused turns are progressively shorted on each unit. This permits a reduction in inductance and in distributed capacity effects. In the minimum inductance position the turns are completely shorted and the total inductance of the unit consists essentially only of the current path in and out of the unit.

In Fig. 2, terminals A_1 and B are connected directly to the ends of their coil, while terminal A is connected to the slider shorting bar which in turn is connected internally to the A_1 end of the coil. In circuits where an absolute minimum of inductance is required, connections are made to terminals A and B and no connection made to A_1 . Terminal A_1 may be used instead of terminal A in circuits where convenience of wiring is more important than a reduction in circuit inductance.

The tuner is mounted on a rigid, aluminum die-cast base to eliminate errors due to frame torsion. The front bearing consists of a number of balls rolling in a cone bearing race, while the rear bearing is a single ball between the shaft end and an adjusting screw stud. Complete shielding is provided by a cover of sheet aluminum. Ceramic terminal block insulators are provided in order to reduce possibility of leakage losses from this source. Coil forms are molded mica-filled phenolic, held to close tolerances to maintain good tracking between coils.

Equivalent Circuit

Generally, the *Inductuner* may be thought of as a two-terminal network. Although three terminals appear, terminals L and L^1 (Fig. 3) are merely

opposite ends of the bar along which the shorting slider runs. Operation of the unit is essentially the same whether terminals H and L (high-side and low-side terminals) or H and L^1 are used, except that in the latter case the minimum inductance will be higher due to the extra length of current path.

The two-terminal network appears as a main variable-inductance element which includes stray capacities (CH and CL) from terminals H and L , respectively, to ground. In shunt with the inductance, across terminals H and L , is a third capacitance (C) which consists of, first, a fixed portion representing inter-element stray capacitance and, second, a *variable* portion which in reality is the distributed capacity of the inductance itself. As turns are progressively shorted out,

the distributed capacity is changed and ultimately reduces C to a minimum value; Fig. 4. This plot also indicates the variation of capacitances CH and CL as the total tuning range is covered.

In Fig. 5 may be seen the relationship of *true inductance* versus *active turns* of the tuner. The values presented have been corrected for lead and capacitance C and are those seen when looking *into* terminals H and L .

Due to its ability to maintain a constant and accurate setting over extreme periods of time, the *Inductuner* may be precisely calibrated. The maximum reset error at 100 mc is 50 kc, and 100 kc at 200 mc.

Credits

Material, photos and diagrams are reproduced through courtesy of P. R. Mallory & Co. and especially through the personal cooperation of Myron F. Melvin.

Fig. 6. Typical circuit for 44 to 216-mc continuous tuning with a 10-turn Inductuner. At A are two turns of $\frac{1}{4}$ " diameter No. 18 wire, $\frac{3}{4}$ " apart, coupled opposed. At B is the end inductor and at C are the shunt inductors.

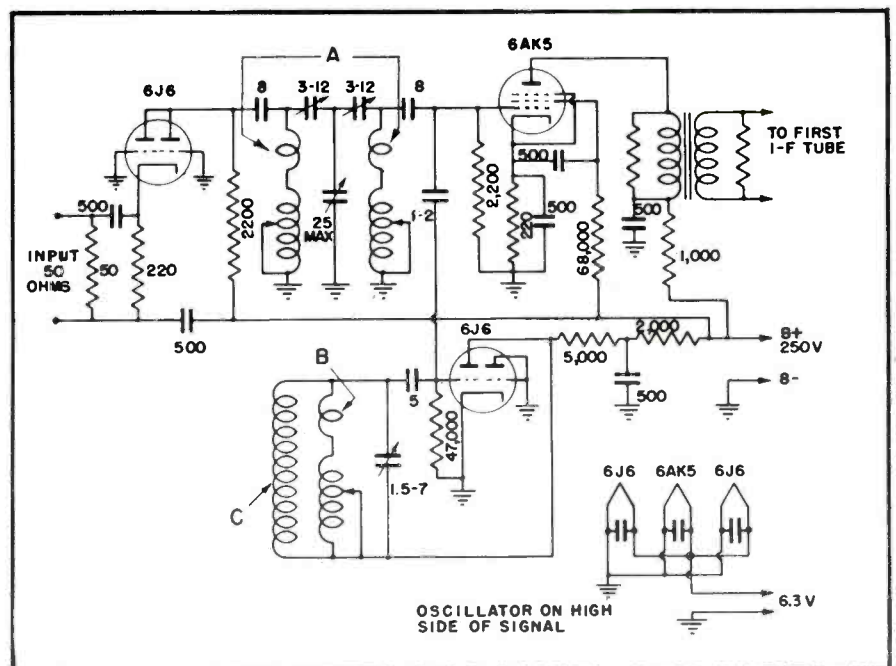


Fig. 1. How to connect a double-pole double-throw switch in the audio circuit to provide application of an *lp* pickup. Shield is connected to point B in circuit.


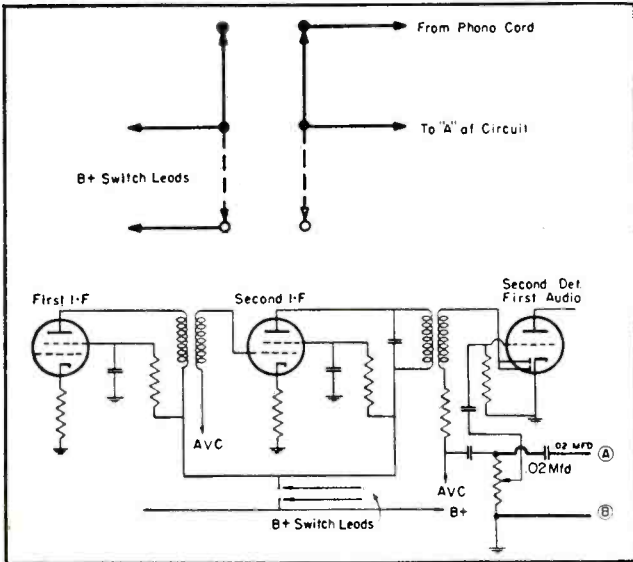


Fig. 2. How pickup height (Astatic FL33) can be adjusted by space washers so that bottom of arm is parallel with top of record when needle rests on record.

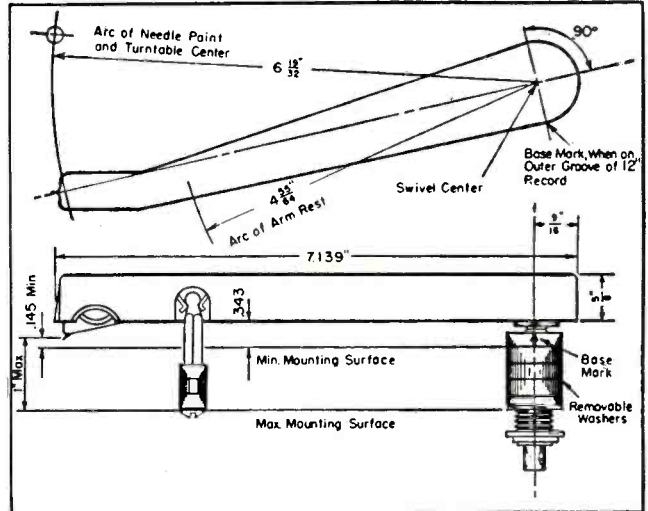

The LP Microgroove

Part II . . . How To Install and Operate Automatic Record Changers, Pickup and Motor Assemblies Designed for the New Long-Playing Microgroove Records.

THERE ARE two general types of automatic *lp* record changers that Service Men can sell and install in existing setups, one which will supplement and another which will provide new record playing facilities. One type which can be used to supplement the existing operations is an automatic record changer for microgroove records only.¹ This player attachment is automatic and several installation precautions must be noted. If the radio-phonograph to which the player is to be attached has its phono connection already in use, a single-pole double-throw switch must be connected to the player, thereby allowing for easy switching from the two types of record players. When radio-phonographs have no phono provision a double-pole, double-throw switch is required, connecting the shield to point B as in Fig. 2.

Another model² available is a dual-speed automatic record changer for

by RALPH M. BARUCH

both standard and microgroove records, as well as standard 33 $\frac{1}{3}$ recordings. The changer is supplied with a counterbalance control which allows for two kinds of pressures (one for each type of record) and two different needle points, .001" for *lp* and .003" for standards. Little servicing is required for both types of players. However, after approximately 1 year or 1,000 hours of operation a few drops of high-grade oil should be applied to the top bearing, bottom motor bearing, turntable bearing, and idler wheel. Incidentally, the drive on this changer is a rubber pulley which disengages when player is on *off* position, thereby eliminating the possibility of the idler

flattening out by remaining too long pressured against the turntable.

Pickups

Several types of pickups have been designed with the necessary light pressure required for the *lp* records. Various kinds of points are being used in the arms, some of them to play 16" records and the 10" and 12" microgroove record, also. However, arms that are too long cannot be installed on existing regular phonograph installations and therefore a new turntable assembly must be provided with these pickups.

One recently developed *lp* pickup³ has a pressure of 5 grams, ideal for the new discs. The pickup can also accommodate a cartridge for regular 78 rpm records. To install this pickup, a $\frac{1}{2}$ " hole is drilled $6\frac{9}{32}$ " from

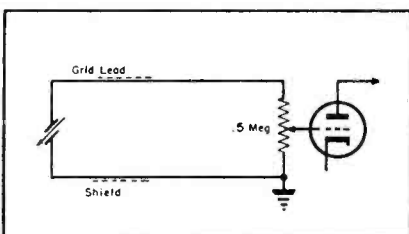


Fig. 3 (left). Connecting the Astatic pickup into grid of first amplifier with a 500,000-ohm volume control in the circuit.

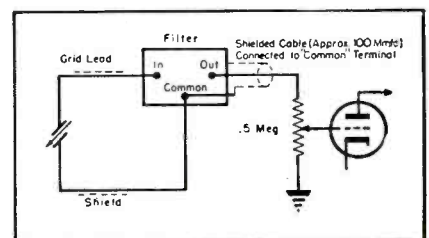


Fig. 4. How a filter can be connected in the pickup circuit to attenuate highs.

Servicing Helps

by P. M. RANDOLPH

MANY SERVICE readers have written in requesting that we continue our discussion of typical TV parts¹ and accordingly data on several more pertinent components have been compiled.

A particularly interesting TV receiver part is the ion-trap magnet, such as the p-m type.² This ion-trap magnet designed for use with picture tubes like the 10BP4, which incorporate ion-trap guns, has a neck diameter of $1\frac{3}{8}$ " to $1\frac{1}{2}$ " and operates with anode potentials of 7 to 14 kilovolts.

The magnet consists of two ring-shaped permanent magnets mounted on a fiber sleeve which fit snugly on the picture-tube neck. Metal-leaf springs inside the sleeve contact the tube neck and maintain the magnet's position. This arrangement centers the magnet on the tube neck without placing a strain on the tube neck.

Installation and Adjustment

Preliminary orientation of the magnet is obtained by placing it on the picture-tube neck so that the white arrow points toward the tube screen. The larger magnet will then be at the base end of the tube and should be positioned approximately over the ion-trap flags which protrude at right angles from the gun structure within the tube neck just above the base.

With the picture-tube operating, final orientation of the ion-trap is begun. Starting from the magnet position specified above, the magnet is moved forward or backward, and at the same time rotated to obtain the brightest raster. The brightness control is reduced, setting it until the raster is slightly above average brilliance. Then, the picture-tube focus is adjusted until the line structure of the raster is clearly visible. The ion-trap is again adjusted for maximum raster brilliance. A final adjustment may be made with the brightness control at the maximum position with which good line focus can be maintained.

Another important TV part is the vertical blocking oscillator transformer

which is used in typical blocking-oscillator circuits which generate pulses for driving the grids of the vertical-discharge tubes. One type³ employs a potted type of construction which is said to provide resistance to moisture absorption.

This transformer has a turns ratio of primary to secondary of $1:42 \pm 5\%$. The primary inductance (with 3-volt, 1000 cps signal and no *dc* current) is $1.15 \pm 20\%$ henries.

The vertical deflection output transformer for direct-viewing picture tubes with magnetic-deflection circuits is another interesting TV part. This is an output transformer designed for use with deflecting yoke⁴ and directly viewed tubes such as 10BP4, and 16AP4.

Turns ratio of primary to secondary of one type⁵ is 10:1.

The primary will stand 2500 volts, secondary 1000 volts.

In typical applications, the transformer is used with a triode-connected 6K6GT operating with a plate-supply voltage of approximately 350 volts.

For horizontal oscillator and synchronizing control a center-tapped oscillator coil⁶ has been produced. This is a permeability-tuned unit for use in TV receivers employing a 6SN7GT as a combination horizontal blocking oscillator and synchronizing control tube. In such circuits the synchronizing pulse is combined with the hori-

zontal oscillator voltage to produce a combination voltage which is applied to the grid of the control-tube section of the 6SN7GT. When these voltages do not have the correct frequency and phase relationship, the oscillator tube is biased automatically to reestablish synchronization.

(Data based on copyrighted material prepared by RCA.)

Picture Tubes⁷

TV RECEIVERS today use two types of picture tubes, the electrostatic and electromagnetic, in several types of circuits.

Regardless of size or type, all picture tubes are fundamentally the same and every tube consists of seven basic elements:

(1) A source of electrons in the form of a cathode.

(2) A filament to heat the cathode so that it will emit electrons.

(3) A control grid for varying the number of electrons passing it.

(4) A means of focusing or concentrating the electrons emitted from the cathode into a beam.

(5) A high-voltage anode to accelerate the electrons emitted from the cathode.

(6) A means of deflecting the beam of electrons in any desired direction.

(7) A screen coated with a fluorescent material which glows upon impact of the electron beam.

Electrostatic Tube Voltage Circuit

The electrostatic type is so called because the electron beam is focused and deflected by an electrostatic field.

In electrostatic deflection, two pairs of plates are placed around the beam at the end of the electron gun. For vertical deflection, a plate is placed above the beam and one an equal distance below the beam. Likewise, for horizontal deflection a plate is placed on one side of the beam and one an

¹Servicing Helps, SERVICE; October, 1948.

²RCA-20303.


³RCA-208T9.

⁴Such as the RCA-201D1.

⁵RCA-204T9.

⁶RCA-203R1.

Fig. 1. Terminal connections for center-tapped oscillator coil. (Courtesy RCA.)

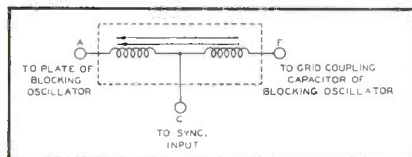

⁷From TV lecture data prepared by F. Fowler and H. Lippert of the G. E. technical service section.

Design and Application of TV Components: Ion Trap Magnets, Vertical Blocking Oscillator Transformers, Vertical Deflection Output Transformers, Horizontal Oscillator and Sync Control Coils. Features of Electrostatic and Electromagnetic Type Picture Tubes; Typical Picture Tube Voltage Circuits.

equal distance of the opposite side of the beam.

If a difference of potential is made to appear between the vertical plates, the electron beam will be deflected up or down toward the plate that is more positive, the amount of deflection on the screen being proportional to the voltage applied between the two plates. If zero potential exists between the two vertical plates, then there will be no vertical deflection of the beam.

With the horizontal plates introduced physically at 90° to the vertical plates, the application of a more positive potential on one of these plates in respect to the other will cause the beam to move sideways instead of up and down.

It is thus apparent that if a voltage is applied to the horizontal deflecting plates and if another voltage is simultaneously applied to the vertical deflecting plates, then the position of the spot at any instant is due to the resultant force of the two voltages acting at right angles at that instant. In television, the voltage applied between the vertical deflecting plates is referred to as a vertical sweep voltage since it deflects or sweeps the electron beam in a vertical direction. The voltage applied between the horizontal deflecting plates is referred to as a horizontal sweep since it deflects the electron beam in a horizontal direction.

In TV receivers, a rapidly changing voltage or sweep is applied between the horizontal deflecting plates, which moves the beam rapidly from left to right and traces a horizontal line. At the same time that the beam is rapidly being moved horizontally, another voltage or sweep is applied to the vertical deflecting plates which changes much

slower than the horizontal sweep voltage, and the beam traces horizontal lines across the face of the tube at the same time that it is gradually being moved from top to bottom by the much slower vertical sweep voltage. The result is a number of horizontal lines across the face of the tube extending from top to bottom referred to as a *raster*.

Electrostatic Tube Voltage Circuit

A basic voltage circuit for a typical electrostatic picture tube is shown in Fig. 2. As indicated, electrode voltages for forming focusing and controlling the intensity of the beam are obtained from a bleeder connected across a high-voltage supply. A variable voltage for the focusing anode is obtained from a potentiometer in the bleeder circuit. The potential on the second or high-voltage anode is usually five or six times that of the first or focusing anode and ranges from approximately 1500 to over 10,000 volts, depending upon the tube type. The higher anode voltages result in a smaller spot size and also produce a brighter picture.

The intensity of the beam or brightness of the picture is controlled by means of a potentiometer in the bleeder circuit which varies the bias between control grid and cathode. Making the cathode more positive with respect to the grid decreases brightness, while making it less positive increases brightness. This is the equivalent of biasing the grid more or less negatively in respect to the cathode.

The video or picture signals are introduced in the grid-cathode circuit of the picture tube, which causes the intensity of the electron beam to vary in exact accordance with the picture signal as the electron beam is deflected across the screen by the application of suitable sweep voltages to the horizontal and vertical deflection plates.

To prevent the application of the sweep voltages on the deflection plates from defocusing the electron beam, the mean potential of the deflecting plates

is kept at the same potential as the last or accelerating anode. It is advisable from this standpoint to use push-pull deflection circuits; that is, both sets of plates are made to vary in potential about a fixed positive potential (the last anode potential) as an operating point. This method of operation is accomplished by connecting each deflection plate to a high resistance, the center point of which is connected to the last anode, and then coupling each pair of deflection plates to a push-pull amplifier.

Some provision is usually made to place a variable *dc* potential on each set of plates for proper centering of the beam. This small variable voltage is required to compensate for any misalignment of the electron gun and for any stray electrostatic or electromagnetic fields which would tend to move the beam off center.

Electromagnetic Types

The electromagnetic picture tube is fundamentally the same as the electrostatic type except that the electron beam is focused and deflected by an electromagnetic field instead of by an electrostatic field.

In the electromagnetic type of tube the electron gun structure is similar to that in the electrostatic tube consisting of: a heater, cathode, control grid, and two anodes. However, the first and second anodes do not perform any of the focusing action. The first anode attracts electrons from the cathode and the second or accelerating anode, which is the high voltage anode, accelerates them toward the screen.

[To Be Continued]

Fig. 2. Basic voltage circuit for an electrostatic picture tube.


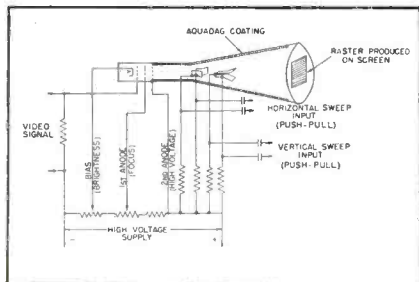


Fig. 3. The basic voltage circuit for an electromagnetic picture tube.

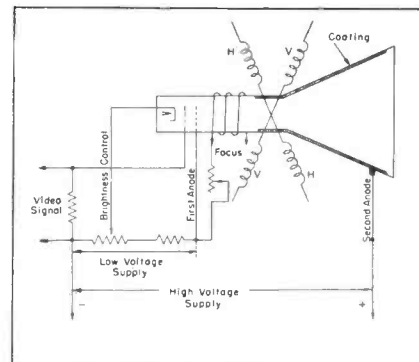

Push-Button TV Receiver

(See Front Cover)

THE INPUT SYSTEM of a push-button type TV receiver, the Bendix model 235M1 and 235B1 chassis,¹ on the front cover this month, features an *rf* stage consisting of one 6J6 in a balanced input *rf* amplifier. Series tuned wave-traps are tuneable over the 30 to 40-mc band in order to reject any signal that might be picked up by the antenna and interfere with the *if* signal. (The sound *if* is 31.625 mc and the picture *if* is 36.125 mc.) The input circuit consisting of a pair of 15 mmfd, two 30-mmfd, and a 1000-mmfd capacitor plus a center-tapped inductance forms a tuned circuit on either the low or high TV band, when connected by the switch pushbutton arrangement to the tuneable elements for the high and low-frequency bands. This circuit is actually series tuned and therefore, provides a voltage gain at the grid of the 6J6 over the voltage that is applied at the antenna input terminal. When one of the channel control pushbuttons is pressed, a mechanical linkage automatically positions all of the iron core slugs in the antenna, oscillator, and mixer coils, as well as operates the low to high frequency switching.

The tuned circuit tapped coil is wound over a 13,000-ohm composition resistor which is a damping resistor for the tuned circuit. A 1,000-mmfd capacitor used for *dc* isolating actually connects the center of the tapped coil to the chassis ground as far as the *rf* signal voltage is concerned. The bias applied to this tube is a combination of cathode bias produced by a 180-ohm resistor, the variable bias from the *agc* circuit, and the fixed bias set by the contrast control. The resultant voltage from these three sources is applied through the 1,000-ohm resistor connecting the center tap of the center-tapped coil back to the *agc* circuit. Since triode type tubes must be neutralized to prevent regeneration, 1.5-mmfd capacitors are alternately connected from one plate to the opposite grid as neutralizing capacitors.

The plate voltage for this *rf* tube is applied to the center tap of another tapped inductance through one of the B+ filter resistors having a value of 680 ohms. The tuned plate circuit for the high and low bands are connected in parallel across the coil in this circuit similarly to that employed in the grid circuit of the same tube. A tank circuit tunes the plate circuit

of the 6J6 to any frequency within the high frequency TV band (174 through 216 mc), while another tank circuit tunes the plate circuit over the low TV band (54-88 mc). The plate coil in this circuit is also wound over a 22,000-ohm composition resistor which loads the circuit sufficiently to prevent oscillation. Since there is considerable length of line between the coil in this part of the circuit and the pushbutton assembly, a separate 5,100-ohm dampening resistor is connected directly across the switch contact on the pushbutton assembly.

A separate local oscillator tube is used in preference to a single multi-element converter tube because of the low conversion transconductance and low signal-to-noise ratio converter tubes have at high frequencies. This tube is also a 6J6 type connected in a push-pull type of oscillator circuit. A *fine tuning* adjustment in the plate circuits is used for sharp tuning in the sound or audio channel on both bands. Negative grid bias developed by the oscillator is also applied to the grids of the 6J6 mixer tubes.

The balanced output from the *rf* amplifier is connected through a pair of 27-mmfd capacitors to the grids of the 6J6 mixer tube. The output from the oscillator is also connected to these same grids by a pair of 2.2-mmfd capacitors. Thus we have two separate frequencies appearing on the grids of the mixer tube. These two frequencies are, of course, the selected *rf* carrier frequency from the TV transmitter and the output frequency of the local oscillator which is always equal to the *rf* carrier plus the *if* frequency.

The grid bias for this tube is determined by the negative grid voltage developed by the oscillator tube. This voltage is applied to the mixer grids through a 33,000-ohm resistor to the junction of a pair of 10,000-ohm resistors, which are individual grid resistors for the two grids of the mixer tube. This means that the gain of the mixer tube will vary in direct relationship to the activity of the oscillator tube. If the *rf* output of the os-

cillator tube is especially strong, a high negative voltage will be developed at its grids and this high negative voltage will be applied to the grids of the mixer tube reducing its gain. This arrangement assures that the mixer tube will operate at the point of optimum transconductance and a maximum signal-to-noise ratio will be obtained at its output.

The manner by which the *if* is obtained from the center junction of the inductance in the 6J6 mixer plate circuit may be puzzling in view of the fact that both the incoming *rf* signal and the signal from the local oscillator is push-pull connected to the grids. Since the input is push-pull connected, the two plates of the mixer are 180° out of phase with each other as far as either one of the two applied signals are concerned and therefore neither one of these signals are present at the center tap of the plate coil. In other words this center tap does not vary in potential with reference to either one of these two signals. This therefore eliminates any possibility of the *rf* or oscillator frequency from entering the *if* channel.

Since the desired frequency at the output of the mixer is the *difference* between the *rf* and local oscillator frequencies, the *phase* relationship between these two, as they appear on the mixer grids, is the only factor that must be considered. These two frequencies are either in phase or out of phase on both grids of the mixer tube at exactly the same instant. When they are in phase they are additive and the resulting current in each plate circuit varies accordingly. When they are out of phase they cancel each other and no change in the current of either plate is produced. The important point to notice in regard to any change produced in the plate circuits by this phase relationship, is that the change on the two plates is *in phase*, instead of 180° out of phase, as is the case when only one signal is applied in push-pull to the two grids. In effect, then, the two halves of this mixer tube are in parallel as far as the *if* is concerned, and therefore this *if* will be present at the junction of the mixer plate coil, appearing across the 35.9-mc iron-cored inductance as a common load impedance.

The heavy lines on the schematic diagram, show the path for all signals of varying amplitude.

¹In part III of the Les Libby series of alignment articles, which will appear in the January, 1949, issue of SERVICE, the complete circuit of the Bendix TV receiver will be presented, together with an analysis of other pertinent sections of the model.

The "TOP" Name In Automobile
Aerials Now Brings You The
"TOPS" In
TV and FM ANTENNAS

Radiart




"Simpli-Flex"


TELEVISION and FM ANTENNAS

True to Radiart tradition . . . these new Television and FM antennas are the finest available! They are laboratory engineered and designed to deliver peak performance, always! Their top quality construction will produce the finest television picture possible. For just a little more . . . YOU can deliver the best . . . it pays!

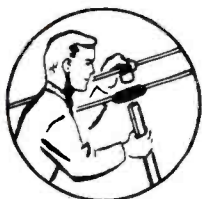
"SIMPLI-FLEX" means just what it says! SIMple to install . . . FLEXible for any requirement! Its design allows it to be built up from the basic dipole to multiple stacked all-channel arrays by the addition of reflector kits and additional arrays as required when more stations get on the air.



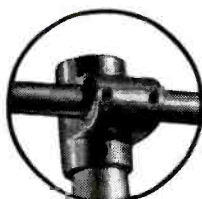
No "assembly puzzles" with Radiart's "SIMPLI-FLEX" design. No degree in engineering or truck-load of tools needed — absolutely no loose hardware. One minute assembly, one man installation!



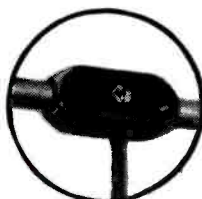High strength, well engineered design of more than ample safety factor, with simple, sturdy all aluminum castings, elements, and heat-treated support masts for PERMANENT installations.



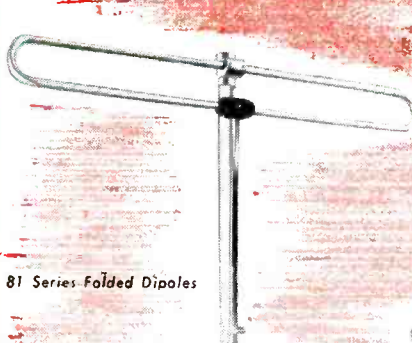
"WEATHER-SHIELD" polystyrene terminal block encloses lead-in connections and protects from all weather conditions! Keeps electrical performance at maximum.




81 Series Folded Dipole




84 Series Double Stacked Arrays

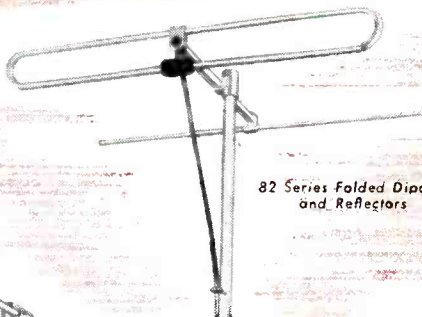

82 Series Folded Dipole and Reflector

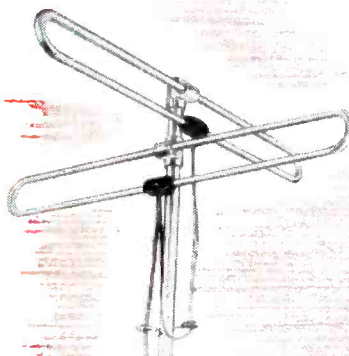

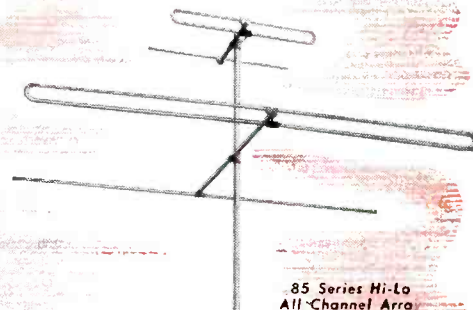83 Series Turnstile Dipole — Non-directional FM Antenna



85 Series Hi-Lo All-Channel Array

THE RADIART CORPORATION CLEVELAND 2 OHIO
Manufacturers of the Famous "Red Seal" Vibrators

TV Sync And Inter-Sync Systems

Part III . . . Characteristics of Horizontal and Vertical Equalizing Pulses and How They Control Picture Presentation.

IN OUR ANALYSIS of the differentiating and integrating circuits in the TV receiver, it was indicated that the integrating circuit is a long time-constant rc combination, with the integrated vertical sync taken off an integrating capacitor. In a typical receiver, the differentiating time-constant may be at some value between less than one and ten microseconds; the integrating circuit time-constant may be from 500 to thousands of microseconds.

A simple inter-sync separating system along with the action of the differentiating and integrating circuit on both the horizontal and vertical sync pulses is demonstrated in Fig. 1. In this drawing waveform 1 represents the short duration horizontal sync pulses which produce, across the differentiating resistor, a series of spiked voltages as shown in waveform 2. Likewise, the leading and trailing edges of the vertical sync pulses, waveform 4, although they are of longer duration, also produce equal amplitude spikes across the differentiating resistor as shown in waveform 5. These pulses, however, occur at a double rate which will be discussed subsequently. Thus the spikes generated during the vertical sync pulse block prevent loss of horizontal synchronization during the vertical retrace intervals.

When the horizontal sync pulse is applied to the integrating circuit, it is of such a short duration that only a very, very tiny charge appears on the capacitor and is of no consequence; waveform 3. During the vertical sync block, however, the pulses are of longer duration and place an appreciable charge on the capacitor. Furthermore, the charge of one pulse is not permitted to leak off the capacitor before it is again reinforced by the second pulse and so on for the entire

by EDWARD M. NOLL*

Instructor in Television
Temple University

six pulses of the vertical sync block. Thus, each pulse adds a charge to the capacitor and a cumulative effect of each charge produces an ample voltage across the integrating capacitor; waveform 6. This integrated or step voltage is used to synchronize the vertical oscillator. Inasmuch as the six vertical sync pulses only occur once every 1/60th of a second the vertical oscillator is fired at a repetition rate of 60 per second. The horizontal leading edges, however, occur once for each line of the picture and, therefore, the horizontal is locked at a rate of 15,750.


Horizontal Synchronization

The horizontal sweep is synchronized by leading edges of the sync pulses which occur at intervals of 63.5 microseconds. These leading edges occur not only during the scanning of

the active horizontal lines but also occur during the vertical retrace interval because it is necessary to maintain tight synchronism of the horizontal sweep even during the time that the vertical is retracing. This rigid requirement is needed to preserve the rigidity of the interlace system because it is necessary that the even-numbered lines fit precisely at the midpoint between the odd-numbered lines to have an interlaced high resolution system. If we were for an instant to lose horizontal synchronization and then reestablish it at the end of each field, the discontinuities present would cause pairing of lines or the actual lines of the scanning raster, instead of being spaced equi-distantly, would be grouped in pairs all the way down the screen. Thus it is necessary even during the vertical retrace interval to generate leading edges to maintain synchronism of the horizontal. Accordingly, instead of using a long continuous vertical sync pulse which would serve just as well so far as vertical integration and synchronization is concerned, the vertical sync block is broken up into a series of pulses (called serrated vertical sync pulses) which form the leading edges for maintenance of horizontal lock-in. Spacing between alternate leading edges of the vertical sync pulse and equalizing sync pulses is also 63.5 microseconds.

Horizontal sync during active line intervals and during vertical retrace period between fields and frame is shown in Fig. 2 (page 44). If the top drawing represents the vertical retrace between fields and the lower one, retrace between frames, it is evident that the end of a field occurs at bottom right and the leading edge of the first equalizing pulse is one full line away from the last horizontal sync pulses. Thus between fields the horizontal locks-in on the odd-numbered equalizing and

Fig. 1. Analysis of inter-sync separation.

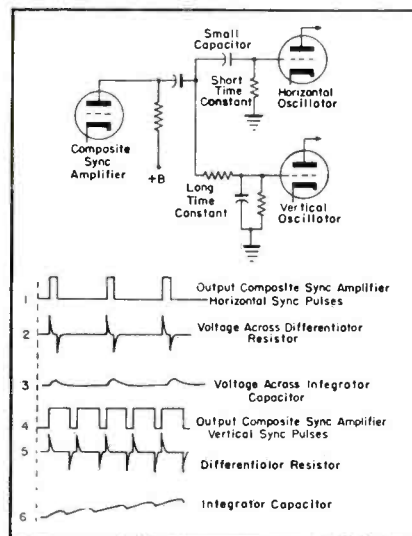


*From a forthcoming book, *Television for Radiomen*, to be published by Macmillan.

(Continued on page 44)

"TV+FM+AM... We're making sure that we get all of this business..."

"We don't propose to let even one customer walk out of our place. If it's a TV, AM or FM set that needs servicing, we're making sure that we can handle the job satisfactorily. And one way of making sure is by constantly using our reference library of Rider Manuals."

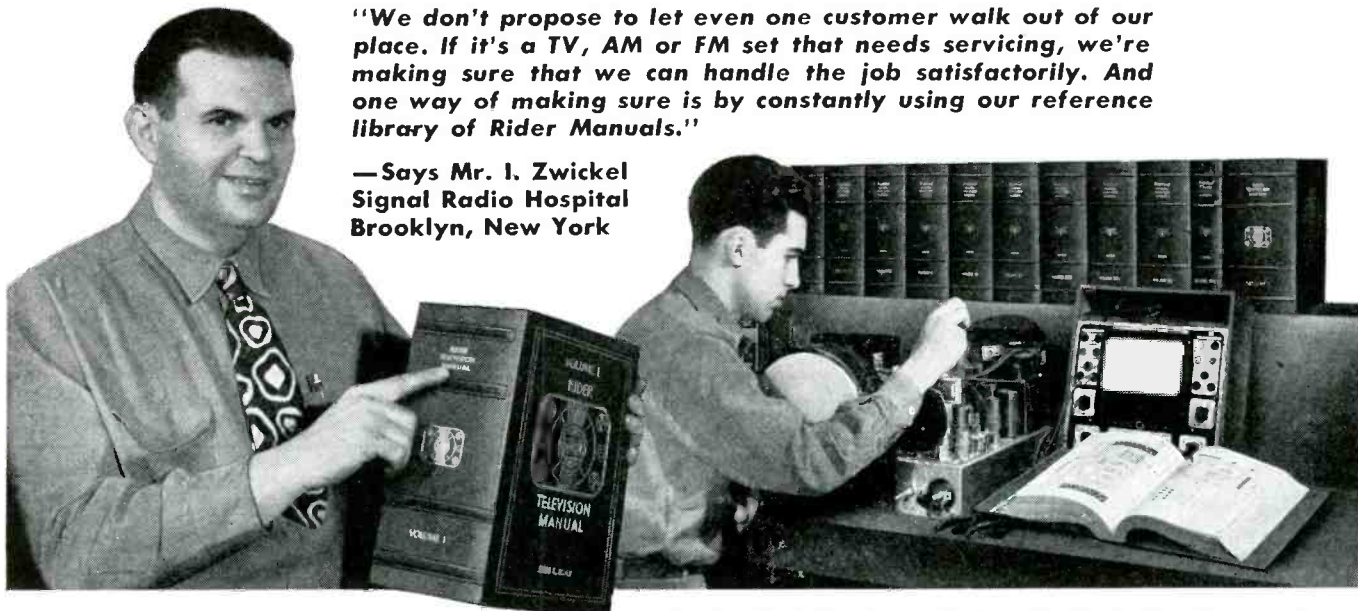—Says Mr. I. Zwickel
Signal Radio Hospital
Brooklyn, New York




All Leading Servicemen Use **RIDER MANUALS**

A ready reference for all sets from 1930 to 1948 — Volumes 1 to 17 are at your Jobber's Now. He also has Volume 1 of the Rider Television Manual.

At Your Jobber's Soon!

VOLUME

2

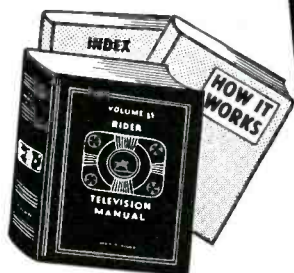

RIDER TELEVISION MANUAL
PLUS 2 Separate Books, "HOW IT WORKS" and INDEX

Even though most of your business is now done on servicing AM and FM, it doesn't take a genius to figure that within the very near future a heavy portion of revenue will come from TV. John F. Rider looks into the future for you, prepares now with a new series of Rider Television Manuals. In these Manuals, too, will be found the OFFICIAL, AUTHENTIC DATA from the set manufacturers themselves. In these Manuals, too, will be found the material necessary, including GIANT SIZE schematics, to guide you and your men to quick and easy methods of servicing TV

Available Now!

RIDER PA MANUAL

The first industry-wide public address equipment Manual incorporating the amplifier production of 147 manufacturers from 1938 to 1948.

2024 pages; plus "How It Works" book which explains theory of various PA circuits and method of rapidly locating faults; plus index.

Both complete for **\$18.00**


RIDER MANUALS

Television Manual, Volume I, (plus HOW IT WORKS and INDEX) \$18.00
 Volume XVII\$16.50
 Volume XVI\$ 8.40
 Volume XV\$19.80
 Volume XIV to VII (each volume)\$16.50
 Volume VI\$12.50
 Abridged Manuals I to V (one volume)\$19.80
 Record Changers and Recorders\$ 9.00
 Master Index, covering Manuals, Vols. I to XV. \$1.50

At Your Jobber's Soon!

VOLUME

18

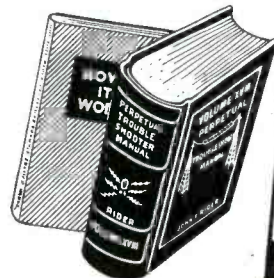

2000 Pages PLUS Separate "How It Works" Book and cumulative Volumes XVI, XVII and XVIII INDEX


Rider Manuals are absolutely dependable because they contain the OFFICIAL, AUTHENTIC DATA of the set manufacturers themselves. Only in Rider Manuals will you find this information—set down in an easy-to-follow form to help you do a real, factory-type servicing that you are giving them customers, too, service. All leading servicemen use Rider Manuals because they know that the Rider-Exclusive "Clarified Schematics" provide time-saving breakdowns of multi-band jobs. In Volume XVIII even wire recorders are covered, along with FM and AM sets and record changers.

Both Books, Complete..... **\$19.80**

JOHN F. RIDER, PUBLISHER, Inc., 480 Canal Street, New York 13, N. Y.
Export Agent: Rocke International Corp., 13 E. 40th St., N.Y.C., Cable, ARLAB.

RIDER MANUALS mean SUCCESSFUL SERVICING

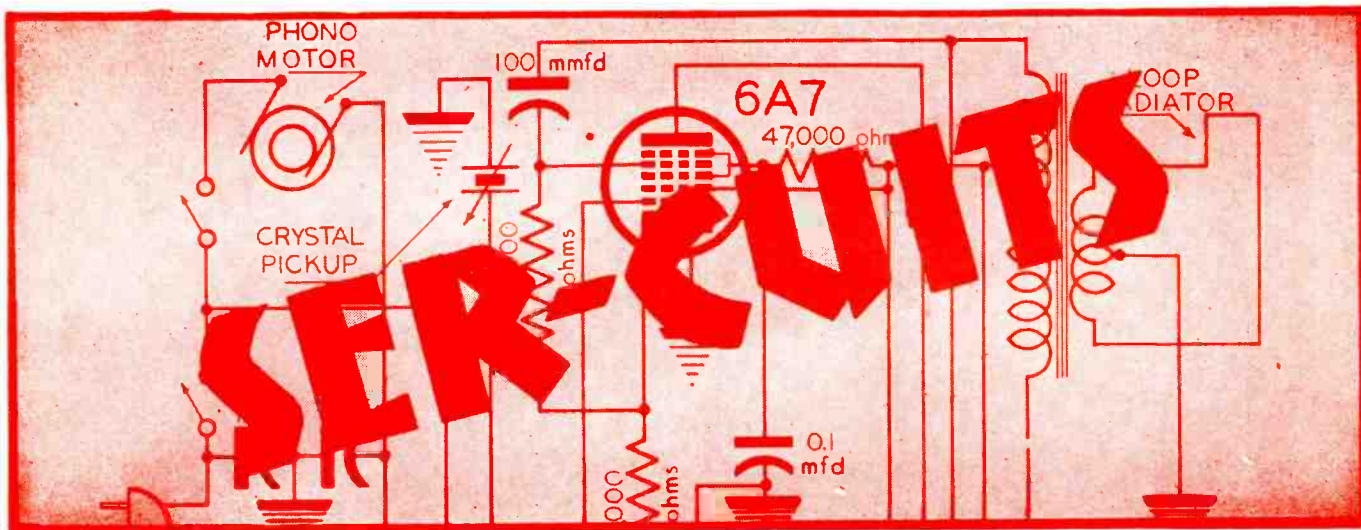NOTE: The Mallory Radio Service Encyclopedia, 6th edition, makes reference to only one source of radio receiver schematics—Rider Manuals.
ANOTHER NOTE: The C-D Capacitor Manual for Radio Servicing, 1948 edition No. 4, makes reference to only one source of receiver schematics—Rider Manuals.



Circuit Features of the Motorola TS-5 and TS-7 TV Chassis, G. E. 810 and Farnsworth GV-260 TV Models.

COMBINATION TV/FM/AM/PHONO receivers now coming off the production line include many unusual circuit features particularly in the TV section.

An interesting example is the Motorola VF102 and VK101 series, chassis TS-5 and TS-7, shown in Fig. 2; page 26.

In the TV part of the chassis are a 6AG5 *rf* amplifier, 6J6 mixer and *hf* oscillator, one 6AG5 *if* amplifier, three 6AG5 video *if* amplifiers, a 6AL5 video detector, *dc* restorer and sync sep., 6AU6 first video amplifier, 6AC7 second video amplifier, 6BA6 second sound *if* amplifier, 6BA6 third sound *if* amplifier, 6AU6 fourth sound *if* amplifier, 6S8GT discriminator and first *af* amplifier, 6V6GT second *af* amplifier (power output), 6SK7 sync stabilizing amplifier, 6SH7 sync pulse stripper, 6J5M sync pulse limiter, 6SN7GT vertical blocking oscillator and discharge, 6V6GT vertical deflection output, 6H6M horizontal deflection discriminator, 6AC7 horizontal deflection reactance, 6V6GT horizontal oscillator, 6J5M horizontal discharge, 6BG6G horizontal deflection output, 8016/1B3GT *hv* rectifier, 5V4G horizontal damping, 10BP4 picture tube, and two 5U4G *lv* rectifiers.

By means of a four-connection antenna receptacle, either a 300-ohm balanced or a 75-ohm unbalanced input is available. The receivers are normally wired at the factory to match a 300-ohm balanced line. If the receiver is to be used with a 75-ohm line, the input circuit can be rewired as shown in Fig. 1. When a 75-ohm interconnector

cable is used in place of the 300-ohm interconnector cable, which is furnished by the factory, FM and broadcast reception can sometimes be improved by reversing the lead-in interconnector plug that fits into the FM-BC tuner chassis.

Under conditions of rough shipment, it is possible for the ion trap, focus coil and deflection yoke parts to become misaligned.

Ion Trap Adjustment: Shifting of the ion trap will result in poor brilliancy or shadowing of the corners. The ion trap should be mounted on the neck of the picture tube so that the pole pieces of the large coil magnet are over the flags on the tube's gun structure. The large coil must be installed toward the socket end of the tube. (If a *pm* type of ion trap is used, it should be placed on the neck of the tube with the black end toward the socket). While observing the raster on the screen, the coil should be moved slightly backward or forward, simultaneously turning it slightly to and fro until the brightest raster is obtained, and one in which none of the

four corners are cut off or shadowed. These adjustments should be made with the brightest picture obtainable consistent with good line focus and a square raster. When adjustment is completed, screws must be tightened to hold trap in position.


Focus Coil Adjustment: Shifting of the focus coil will result in corners of the picture being cut off or shadowed, or it will be impossible to bring the beam to a focus with the focus control. To correct, the wing nuts which hold the focus coil in place should be loosened. These two nuts are found on the sides of the focus coil bracket. The horizontal and vertical centering controls should be set approximately at the center of their range of rotation. While observing the raster on the screen, the focus coil should be moved back and forth until a position is found where the raster is about centered on the screen and none of the four corners is cut off or shadowed. The wing nuts, holding the coil in this position, should then be carefully tightened.

Deflection Yoke Adjustment: If the deflection yoke shifts, the picture will be tilted. To correct, the wing nut on top of the deflection yoke should be loosened and yoke rotated till picture is straight.

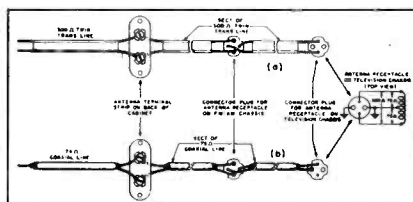G. E. 810

In Fig. 3, page 28, is another interesting TV receiver, the G. E. 810 table model.

Features of the receiver include a constant input impedance *rf* amplifier (Data continued on page 29; Circuits on pages 26, 28)





POWER

25 Watts Power Handling Capacity



SENSITIVITY

14½ ounces of ALNICO 5

FIDELITY

Broad Frequency Characteristics
50-13,000 cycles

**PERFORMANCE
ENGINEERED!**

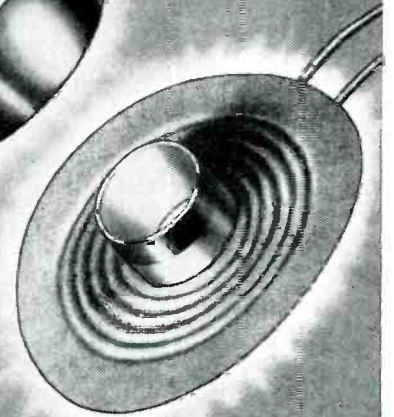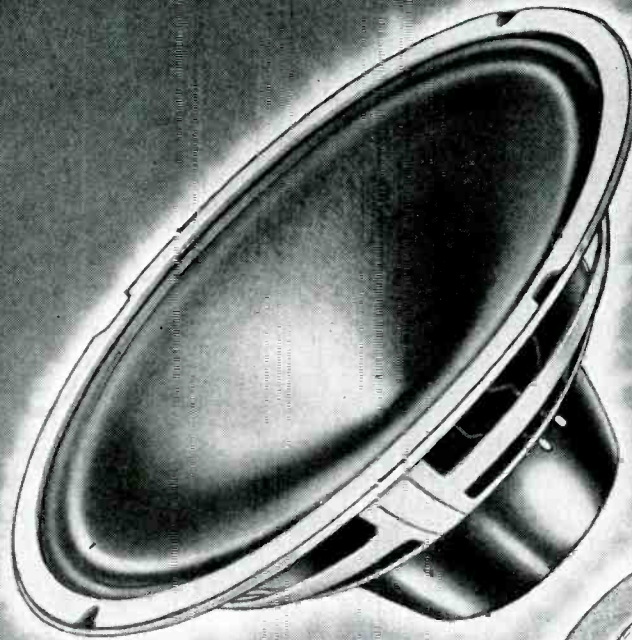

The General Electric 1201 Speaker with the famous General Electric Aluminum Foil Base Voice Coll.

FROM THE SMALLEST TO THE LARGEST:

- Every G-E speaker is *Performance-Engineered* at Electronics Park
- Every G-E speaker is equipped with the *Aluminum Foil Base Voice Coil*
- Every G-E speaker is an *Alnico 5* speaker
- Every G-E speaker cone is designed to last
- Every G-E speaker has a *Big Market*

For complete information on General Electric Speakers write: *General Electric Company, Electronics Park, Syracuse, New York.*

Demonstration PROVED to Distributors in these and many other cities that the 1201 is OUTSTANDING IN QUALITY.

- | | |
|-----------|----------------|
| ATLANTA | LOS ANGELES |
| BALTIMORE | NEW YORK |
| BOSTON | PITTSBURGH |
| CHICAGO | SALT LAKE CITY |
| CLEVELAND | SEATTLE |
| DALLAS | SAN FRANCISCO |
| DETROIT | WASHINGTON |

You can put your confidence in—

GENERAL  ELECTRIC

169-G9


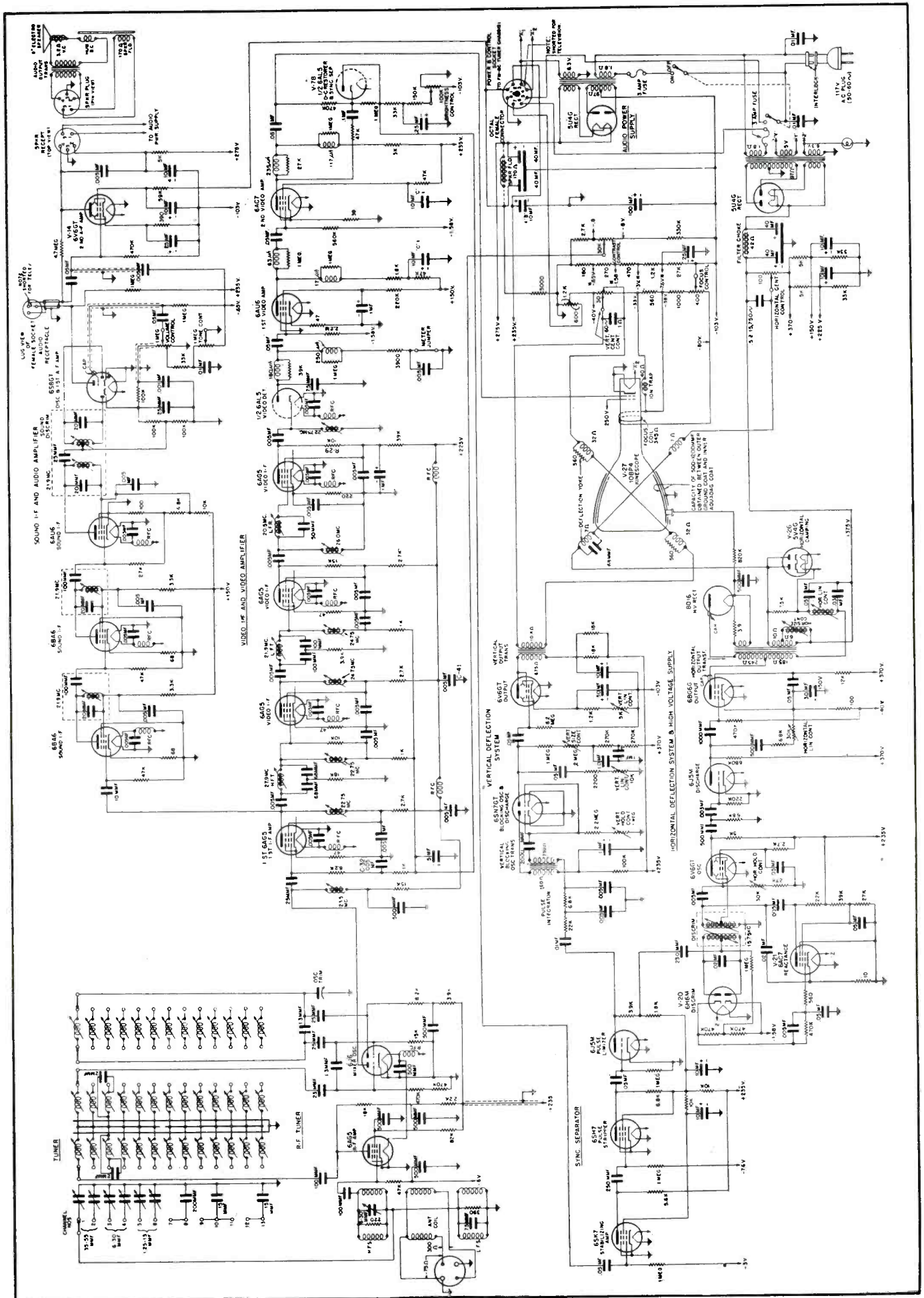


Fig. 1. Circuit of the Motorola TS-5 TV chassis.

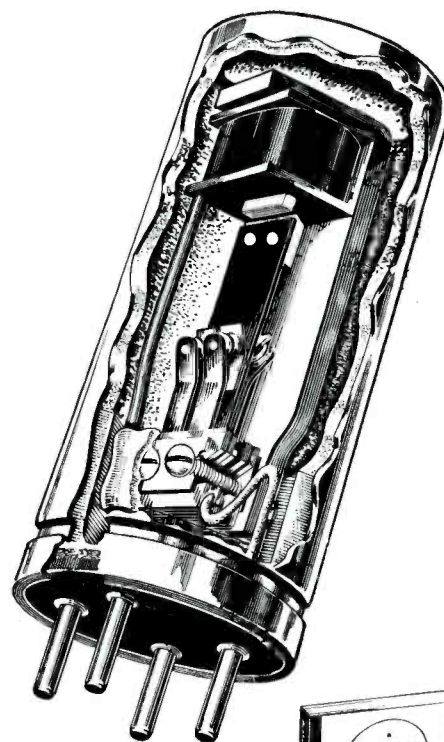

As another year draws to its close, we pause in retrospect of what has gone behind . . . and think wishfully of what is yet to come. To all our friends we are anxious to extend the very warmest greetings of the seasons. It is our sincere wish that this holiday season hold every gladness for you and yours. And may the New Year ahead be one rich in happiness. Our thanks to you for past business favors, and your help in even further establishing the name RADIART VIBRATORS as the leader in the field. It is our pledge to continue to deliver the best in vibrators -- to keep faith with you -- and your customers.



THE ONLY VIBRATOR LINE LISTED IN SAM'S RED BOOK



The Radiart Corp.

CLEVELAND 2, OHIO

Export-Scheel International Inc., 4237 N. Lincoln Ave., Chicago 18, Ill.

Ser-Cuits

(Continued from page 24)

with a balanced input, automatic frequency control for horizontal synchronization, and a ten-inch picture tube with aluminumized screen.

In this model, the horizontal sawtooth generator makes use of one section of a 6SN7GT, connected in a blocking oscillator circuit. Instead of its frequency being controlled directly by the horizontal sync pulses, it is controlled by a *dc* voltage on its grid, which is the resultant of the phase difference between the incoming sync signal and a voltage wave derived from the output of the sweep generator. The resultant *dc* voltage produced by the other section of the tube is called an *afc* voltage.

The *afc* portion of the tube obtains its operating bias through its connection to the grid circuit of the blocking oscillator tube, through a 3.3-megohm resistor. The blocking oscillator produces a large negative bias in its grid circuit during its normal operating cycle. When the horizontal sync pulses or the combined output voltage are impressed separately on the grid of tube, they do not have sufficient positive amplitude to cause appreciable plate current flow. However, if they are combined and phased properly, their composite amplitude is sufficient to cause plate current to flow. During the time that conduction takes place, a .2-mfd and a .002-mfd capacitor in the cathode and grid circuits become charged positive in respect to ground, the magnitude of the charge and the resultant voltage thereon, being dependent upon the duration of the flow of plate current in the *afc* part of the tube.

Since an 82,000-ohm resistor is in the bleeder circuit across the filter and also forms a part of the grid return circuit for the sweep generator tube, any change in voltage across this resistor will thus result in a change of frequency in the sweep generator. Thus if the contributing voltage of the resistor makes the grid less negative, the frequency will be raised; likewise, if the contributing voltages make the grid more negative, the frequency will be lowered. Thus, it will be seen that the longer the conduction period of the *afc* part of the 6SN7GT, the higher will be the frequency of the blocking oscillator and its sawtooth output.

A horizontal frequency control, in the form of a 25-150-mmfd variable,

(Continued on page 30)

Everybody agrees
ATR AUTO RADIO VIBRATORS
are TOPS


ATR AUTO RADIO VIBRATORS
have Ceramic Stack Spacers



A Complete Line of Vibrators . . .

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

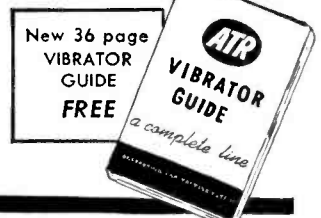Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing--
ATR PIONEERED IN THE VIBRATOR FIELD.



New Models



"A" BATTERY ELIMINATORS

For DEMONSTRATING AND TESTING AUTO RADIOS

New Models . . . Designed for Testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.



New Models



STANDARD AND HEAVY DUTY INVERTERS

For Inverting D. C. to A. C. . . . Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D.C. Districts.



NEW MODELS
NEW DESIGNS
NEW LITERATURE
See your jobber or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U. S. A.

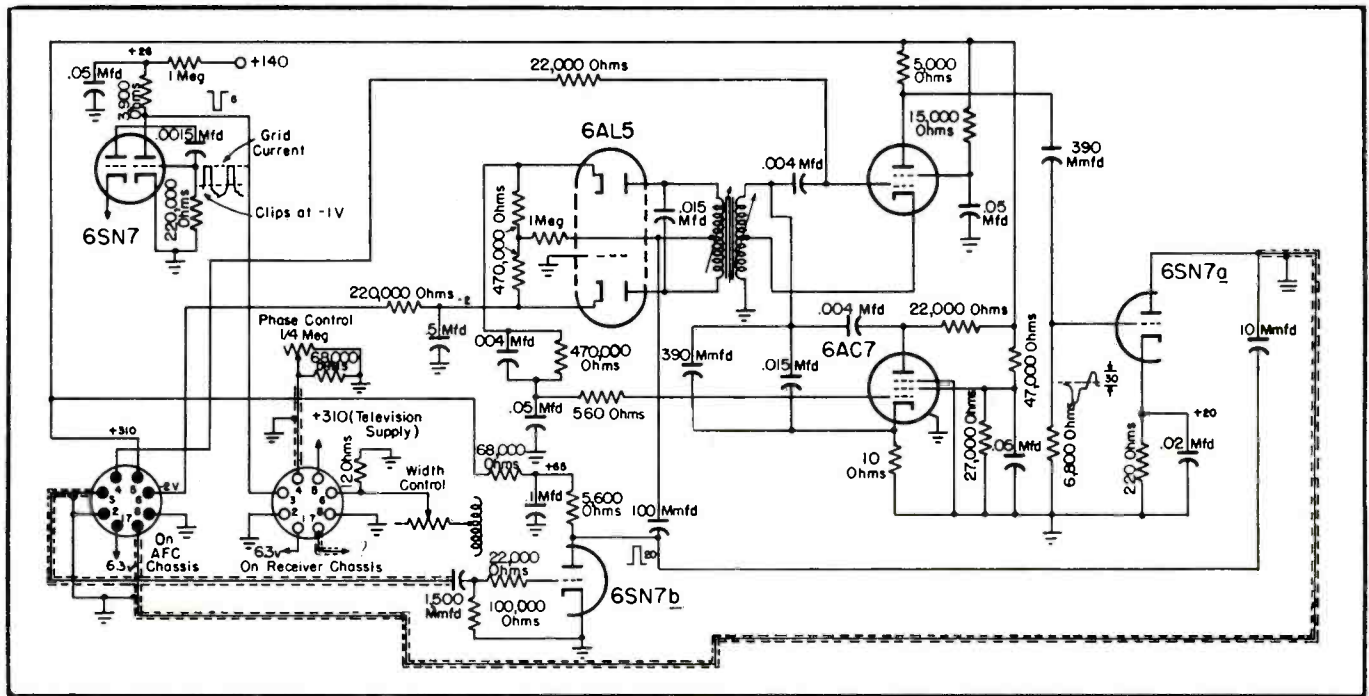


Fig. 4. The horizontal *afc* circuit used in the Farnsworth GV-260 TV receiver.

forms a part of the discharge circuit in the grid of the blocking oscillator. By varying its value, the free running speed of this oscillator can be adjusted to supplement and act as a course control for the *horizontal hold* control. The free running speed of the blocking oscillator is also adjusted by the inductance variation of a blocking oscillator coil.

The horizontal sawtooth voltage generated by the blocking oscillator is shaped and then amplified by a 6BG6G. The output of this tube is coupled to horizontal deflection coils through an impedance matching transformer. A 5V4G damping tube diode is used principally to remove a transient oscillation created by the rapid retrace of the current in the high inductance of the horizontal sweep and high voltage transformer and still retain the positive overshoot in the primary winding for use in the high-voltage supply. It also is used to provide a linear trace and to recover some of the energy from the inductive kick-back and to help supply the B+ requirements of the output tube.

A 25-150-mmfd horizontal drive control forms a capacity voltage divider in conjunction with a 390-mmfd capacitor so as to control the amount of sawtooth voltage supplied to the grid of the 6BG6G sweep output tube. This permits adjustment of the grid sawtooth voltage to compensate for variations in output tubes.

A *horizontal width control* forms a series-parallel circuit in respect to the output to the yoke. The inductance is variable in both coils of this control;

the inductance of the series choke is maximum when the parallel choke is minimum and vice versa. The parallel circuit shunts the current around the deflection coil, depending upon its inductance, and the series coil attenuates the current by changing the impedance of the series circuit. This type of control provides a uniform impedance to the output transformer over a wide range of adjustment.

A vertical sawtooth voltage is generated by a 6SN7GT connected as a multivibrator. This voltage is coupled directly to a 6V6G vertical sweep output amplifier tube and then to the vertical sweep yoke through the impedance matching transformer. Vertical speed is controlled by changing the time constant of the multivibrator grid circuit by a 50,000-ohm potentiometer. Sweep size or height of picture is changed by 100,000-ohm potentiometer, which changes the B+ voltage applied to a charging network of the 6SN7GT simultaneously with the screen voltage on 6V6G. Vertical linearity is controlled by feeding back correcting voltage developed in the cathode circuit of the 6V6G through a .1-mfd capacitor into the grid circuit of the output tube. The cathode voltage which is fed back through the .1-mmfd capacitor has an opposite curvature corresponding to the non-linear portion of the generated sawtooth output so that by combining these voltages in the grid of 6V6G correction may be effected. The amount of the correction voltage is controlled by a vertical linearity potentiometer.

The high voltage for the second

anode of the picture tube is derived by making use of the inductive *kick* voltage produced during retrace in the horizontal output transformer. This kick voltage has a magnitude of several thousand volts and is positive-going, appearing between the plate of the 6BG6G sweep output and ground. Since this voltage in itself is not sufficient to produce the required anode potential, an additional winding connected electrically and magnetically with the primary is added to provide further step-up of this voltage. The top of this autotransformer is connected to the plate of a rectifier tube, a 1B3GT/8016, which derives its filament voltage from the horizontal sweep transformer by a single turn around the core. Since the frequency supplied the rectifier tube is high (15,750 cps), a 500-mmfd filter capacitor is more than adequate to give a smooth *dc* output. Due to the small capacity of the filter, this supply is relatively safe to handle.

Farnsworth GV-260

Continuing our analysis¹ of the Farnsworth GV-260 TV chassis, which began last month, let us now study the *dc* reinsertion system of the set.

Even as a photographic exposure meter determines the iris setting of a camera and involuntary muscular action sets the proper iris opening of the eye, the *dc* inserter circuit establishes an average value of the intensity of the received signal which con-

¹From a series of TV servicing lectures prepared by Farnsworth.

trols the grid-bias upon a viewing tube. The reinsertor is the *exposure meter* and the bias voltage which it produces is the "iris."

Initial bias to the grid of the picture tube in the set is fed to the tube through a 1,000-ohm resistor. Through this resistor also flows the rectified portion of the video signal which, of course, is direct current. This *dc* establishes a potential across the resistor which subtracts from the initial grid bias. Therefore, a strong signal produces a relatively high potential across the resistor which, being positive, subtracts from the initial tube bias whereas a weak signal, or none at all, contributes little or no potential, increasing (opening the iris) the bias potential.

Even as an *avc* circuit should have correct time constant, the effect of *dc* reinsertion must be properly timed. Too short a time required for it to *take hold* would produce surges of light upon the screen, whereas too long a time would cause the background illumination from one scene to carry over into the next. This proper timing of the effect of the reinsertor is accomplished by a 10,000- and 220,000-ohms resistor and .02-mfd capacitor. The 220,000-ohm resistor also serves to provide direct potential continuity to the grid.

Differentiation and Horizontal Control Circuits

The Farnsworth receiver incorporates an *afc* circuit which maintains horizontal deflection rate constant in the presence of normal bursts of interference. Sync pulses appearing in the output of a 6SN7 are transmitted to one-half of a 6SN7. There, they are amplified to appear as positive pulses then injected into the *afc* circuit.

A 6K6 is used in the familiar Hartley oscillator in which sustained oscillation is had. The natural period of this oscillator is nominally near 15,750 cps; that of the incoming sync pulses.

Connected into the inductive circuit of this oscillator is a reactance tube, 6AC7, which operates in the familiar manner of reactance tubes in the *afc* circuits of electronic sweep circuits, broadcast receivers, etc. Signals are presented to the grid of the reactance tube by injection into the cathode circuit over a 10-ohm resistor. The reactance of the cathode coupling capacitor is considerably higher than the 10-ohm cathode resistor through which the oscillator currents flow.

[To Be Concluded in January]

Flexibility makes

"the Service Man's Line"

Brach antennas . . . long known for dependability . . . maximum reception . . . trouble-free operation . . . durability and ease of installation . . . now feature an added extra . . . Flexibility. Unique construction features aid the service man in making a more rapid installation to which future additions or modifications can be easily made.

1. FLEXIBILITY A complete line designed with basic antenna parts which are convertible to more complex arrays as required by location and reception problems.

2. COMPLETE KITS Each antenna model is independently designed and furnished in a completely packaged kit containing all necessary hardware, download (when desired) and the Universal Base Mount . . . ready for installation.

3. PRE-ASSEMBLY Each antenna is factory pre-assembled as far as possible, ready to erect. Complete and simple installation instructions. Saves valuable man-hours on the roof.

4. MECHANICAL STRENGTH Weather - tested for durability, Brach Antennas feature a husky steel mast, rigid connections, sturdy base mount, neat appearance. All parts corrosion resistant.

5. SUPERIOR RECEPTION Designed with engineering "know-how". All Brach antennas are factory pre-tuned, matched for 300 ohm transmission line with large diameter aluminum elements for better signal pick-up. Directivity patterns and standing wave ratios available upon request.

New! Tops in TV! HI-LO ROTATABLE Antenna

Here it is! A rotatable antenna to provide peak performance with any station at any time. Brach introduces the new "Superview" Rotatable, covering both high (174 MC to 216 MC) and low (88 MC to 108 MC) TV bands. High band extension available for easy addition to standard dipole array for separate orientation. No more multiple images. No more "weak" stations. Brach's Superview HI-LO assures television reception that's tops. Make sure and investigate the new Superview line today.

Write for Free Brach catalog showing complete line of TV and FM antennas and accessories.

SEND FOR CATALOG No. S304




L. S. BRACH MFG. CORP.

200 CENTRAL AVENUE, NEWARK, N. J.

WORLD'S OLDEST AND LARGEST MANUFACTURERS OF RADIO ANTENNAS AND ACCESSORIES

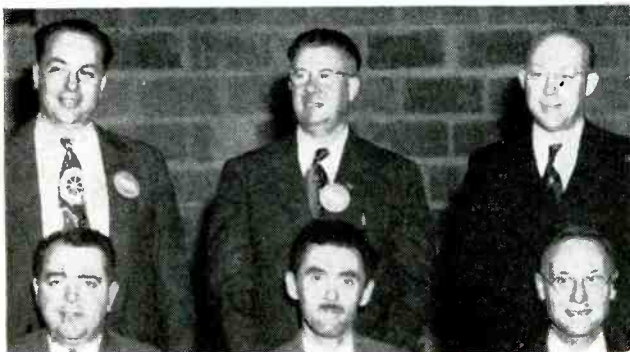Board of directors of the recently organized American Radio Technicians Guild. Front row, left to right: Ray Mattraw, Lewis Sharrard and Bertram Lewis. Rear row, left to right: Ed Fisk, William Brewerton and Hyman Levy.



At a recent service meeting in Medford, Oregon, sponsored by Verl G. Walker Co., in cooperation with Howard W. Sams and Co., Inc., who presented Al Saunders offering his popular TV talk. Left to right: Dave M. Lee, Northern Pacific rep for Howard W. Sams; Verl G. Walker and A. C. W. Saunders.



ASSOCIATIONS

ARSCP, Williamsport, Pa.

JOHN BARSOPHY, chairman of the publicity committee of the Associated Radio Servicemen of Central Pennsylvania, has forwarded an interesting report on their recent activities. He states that TV was the keynote of the October meeting, held in the Brown Library in Williamsport, where members were told that Mostoller Hill was chosen as the site of the association's TV lab. It was announced that preliminary tests on the hill with several TV sets were satisfactory, picture signals being received from New York, Philadelphia, Washington, and Baltimore.

President Robert Stout, who presided at the meeting, told the boys

that it was planned to have full facilities available at the lab—power, a forty-foot tower with platform, at least two types of antennas, suitable test equipment, etc. Thus any member desiring to build a TV kit and seeing what *gives* need simply drive out to the hill, use his pass key to get into the lab, and see what does give, if anything!

In this way, members feel, reports Barsophy, and *only* in this way, by actually working with TV gear, can one become really familiar with the *works*. It is planned to supplement the lab activities with talks, a class or two (the tentative stage as yet), and private study.

ARSCP delegates to the Scranton meeting of the Federation of Radio

Servicemen's Association of Pennsylvania, Carl Smith and Phil Marchioni, told the members about TV servicing problems covered, such as new set servicing. As a result, the association went on record condemning the practice of forcing purchasers of TV sets to buy servicing with the set.

At the November meeting, Barsophy reports that TV was featured, too, with a talk on antennas by John F. Rider. Rider, who was concluding a lecture tour through Eastern and Central Pennsylvania cities, addressed a capacity crowd at the Brown Library. He expressed approval of the TV lab idea, and said it was the first such cooperative effort of its kind, as far as he knew.

Three committees have been ap-

At a recent RMA meeting of service managers at the Hotel Roosevelt in New York City during which television servicing was a featured topic of discussion: A. J. Alexander (*Motorola*), H. A. Newell (*Crosley*), H. Patten (*DuMont Labs*), W. J. Zaun (*RCA Service Company*), A. H. Kuttruff (*Westinghouse*), Edward A. Pool (*Wells-Gardner*), B. R. Lafferty (*Hallierasters*), M. L. Jones (*Delco Radio-General Motors*), W. L. Parkinson (*General Electric*), F. Leo Granger (*Stromberg-Carlson*), B. J. Hickman (*Sparks-Withington*), M. R. Weiss (*Kings Electronics*), Thomas H. Ellis (*Western Auto Supply*) and Bond Geddes and James Secrest of RMA.



TEN YEARS AGO

From the Association News Page of SERVICE, December, 1938

THE GREATER BRIDGEPORT Radio Service Men's Association, Bridgeport, Conn., became affiliated with the RSA. Officers were: L. F. Gravlin, chairman; A. H. Stendahl, secretary and Herbert C. Eiseman, treasurer. . . The Abilene, Texas, Chapter discussed a rate book for receiver repairs. . . The Buffalo, N. Y., Chapter nominated officers for '39. Clarence Redstone, instructor at the Buffalo Technical Institute presented a talk before the group on *Radio Service and Theory* . . . The Danville, Ill., Chapter held a weenie roast and picnic. Russ Lund of Clough Brengle talked on *Dynamic Testing*. . . The Flint, Mich., Chapter reported that it had almost 100% membership among the Flint Service Men. . . The first annual banquet of the Green Bay, Wis., Chapter was held at White Lawe, Wis. . . The Southern New Hampshire Chapter devoted the first meeting of the month to business of the chapter. . . George Connor of Sylvania presented a talk on tone quality improvement before the New York chapter. . . The Peoria, Ill., Chapter began a co-operative advertising campaign in the local newspapers. Editorial cooperation, in the form of articles commenting on the work and stability of RSA members, was promised by the papers. . . The Pontiac, Mich., Chapter held its first meeting at the Board of Commerce building. . . The Radio Service Association of California elected officers for '39. . . Servicing groups in Fort Wayne, Ind., and Springfield, Jacksonville and DeKalb, Ill., indicated that they'll join the RSA soon.

pointed by President Stout: *program* . . . John Voelkler (chairman), A. L. Altemose, Sr., George L. Bailey, Chas. E. West, all of Williamsport, and John Stine, of Jersey Shore, Pa.; *membership* . . . Art Guild (chairman) and Phil Marchioni of Williamsport, and Frank Grinnell, West Milton, Pa.; *publicity* . . . John Barsophy (chairman) and Luther E. Reitmeyer of Williamsport, and Don Koch of Hughesville.


ESFETA

IN A REPORT on the recently formed Empire State Federation of Electronic
(Continued on page 45)



Build Business 3 ways

FROM NEW AND OLD CUSTOMERS

with Exclusive
NEW
SERIES 12

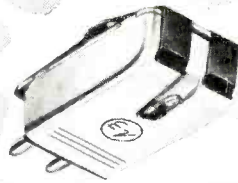

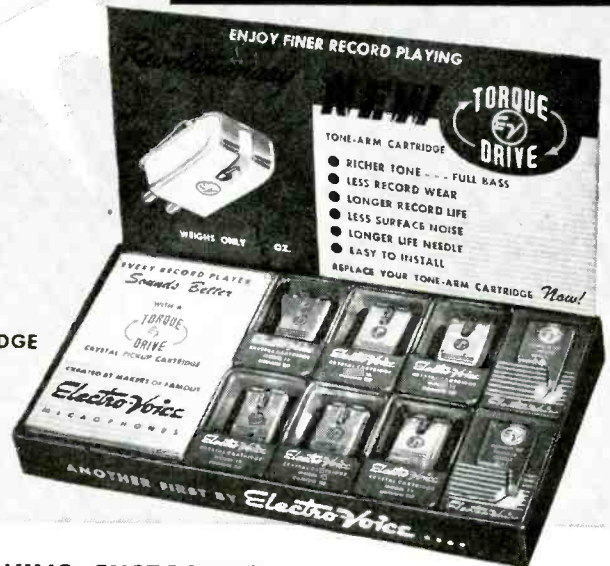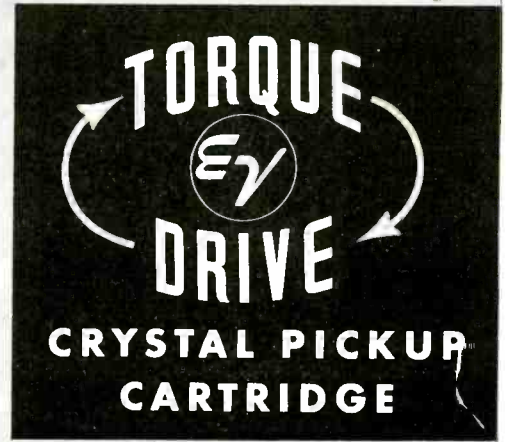LIGHTEST
MOST EFFICIENT
CRYSTAL CARTRIDGE
EVER PRODUCED



**NEW IDEA WINS CUSTOMERS
CREATES MORE BUSINESS**

1. With only 3 basic types you can make normal replacements of over 150 standard models
2. You offer all record fans a new aid in obtaining finer reproduction and preserving records.
3. You help record lovers get more plays out of old worn records.

Everyone likes the way the new TORQUE DRIVE improves performance . . . hushes surface noise and needle talk . . . reduces record wear, increases record life, gives more needle plays. Comes in low, medium and high voltage, with replaceable Osmium-tip or Sapphire-tip long-life whisker needle. Available individually or in kits.

Series 12 with Osmium-tip needle . . . List price \$7.50
Series 12 with Sapphire-tip needle . . . List price \$8.50
As your E-V Distributor or write for Bulletins 141 and 142.

ELECTRO-VOICE, INC., BUCHANAN, MICH.
Export: 13 East 40th St., New York 16, U.S.A.
Cables: Arlab

**HANDY KIT MAKES SALES
AND SERVICE EASY**

Enables you to make most replacements immediately. Saves time! Cuts overhead! Increases profit! Available in Kit "A" (Osmium) or Kit "B" (Sapphire). Each kit contains 6 cartridges, 4 extra needles, mounting plates, literature, replacement chart.

**New Model L-14
for MICROGROOVE**

New Microgroove Crystal Cartridge also available now—at same price. E-V Model L-14 has smooth, peak-free response to 12,000 c.p.s. No filter necessary.

**New Model 20
MAGNETIC CARTRIDGE**

Now available for REGULAR or MICROGROOVE records. Uses Model 503 Matching Filter.

E-V Pat. Pend. licensed under Brush Patents.

IT PAYS TO REPLACE WITH

Electro-Voice

JANUARY, 1948 — DECEMBER, 1948

ANTENNAS

- Antennas, FM. By *Les Graffis*.....April
 Antenna Transmission Lines, FM. By *Les Graffis*.....Jan.
 Application of High-Gain Antennas to Step Up TV Signal Strength in Weak-Signal Locations.....April
 Checking FM Antenna Locations.....Nov.
 Coaxial and Two-Wire Lines.....Jan.
 FM-Antenna Directional Control.....Nov.
 Directional and Non-Directional Types of FM Antennas.....April
 Factors Involved in TV Antenna Designs. April
 High-Frequency TV Antenna Installations. By *Ira Kamen*.....Sept.
 HF TV Antenna Installation Procedures.....Sept.
 Half-Wave and Quarter-Wave Lines.....Jan.
 Matching FM Antennas to 72 and 300-ohm Lines.....Nov.
 Major Math Factors with Which Service Men Should Be Familiar to Install TV Antennas for Full-Band Coverage.....Aug.
 Mounting FM Antennas.....April
 Multiple Antenna System Installations.....Nov.
 Non-Directional and Directional Types of FM Antennas.....April
 Practical FM Antenna Installations. By *Ira Kamen*.....Nov.
 Quarter-Wave and Half-Wave Lines.....Jan.
 Radiation Resistance and Fields.....April
 Relation of Terminating and Line Impedance in FM Antennas.....April
 Selecting Proper FM Antennas.....Nov.
 Stub Filters for Cutting Out Interference in Channels 2 to 6.....Sept.
 TV Antenna Installation Precautions.....April
 TV Antenna-Installation Tools. By *Ira Kamen*.....May
 TV Installations in Fringe Areas. By *Ira Kamen*.....Dec.
 TV Interfering Frequencies.....Sept.
 Two-Wire and Coaxial Lines.....Jan.
 Use of Math in 12-Channel TV Antenna Installations. By *Ira Kamen*.....Aug.

AUTO RECEIVERS

- Auto Radio Servicing.....May
 Auto Service Hints.....May
 Automobile Battery Ground Data.....May
 Buick Receivers.....May
 Capacitor Reference Circuits.....May
 Delco R-705 Automatic Station Selector System.....May
 Design of the Non-Synchronous and Synchronous Forms of Vibrators.....May
 Detailed Analysis of Delco R-705 Automatic Station Selector System.....May
 Four Circuits Which Can Operate from 120-Volt AC and 6, 12, and 24 Volt DC Inputs.....May
 How Vibrators Operate in Modern Auto Installations.....May
 Oldsmobile '46 and '47 Auto Sets.....May
 Motorola 508, Truetone D4630 and Buick Receivers.....May
 Packard-Philco Auto Radio P-1835.....Sept.
 Philco Auto Radio 938K.....Sept.
 'Scope in Auto Servicing.....May
 Taxicab Radio Alignment Setup.....Dec.
 Taxicab Radio, Servicing.....Dec.
 Truetone D4630.....May
 Vibrator Design and Application. By *Ralph G. Peters*.....May
 Vibrator Power Supplies. By *T. M. Sterling*.....May
 Vibrator Specification Information.....May

CIRCUITS

- AC/Battery Vibrator Power Supply.....May
 AC/DC Set Using Tapped Filament Connection.....July
 Admiral Chassis 8C1.....July
 Admiral 7C73.....Jan.
 Admiral 301A (Block Diagram).....Oct.
 Admiral 301A (Complete TV Circuit).....Oct.
 Altec-Lansing 10576 (Amplifier Kit).....June
 Auto Test Setup.....Aug.
 Battery and Three-Way Portables.....July
 Balance-Indicating Circuits.....April
 Beam Relaxor TV System.....July
 Belmont 21A21.....Mar.
 Bendix 235M1/235B1 Push-Button TV Receiver (Cover).....Dec.
 Bias-Supply Regulated System.....Feb.
 Buffer Capacitor Reference Circuits.....May
 Buick 980744/45.....May
 Capacitor Check Circuit.....Aug.
 Coax to 300-Ohm Input Circuits.....Sept.
 Code Practice Oscillator Circuit.....Aug.
 Columbia LP Adapter.....Nov.
 Clippard Signalette SI (Cover).....April

- Delco R705 Auto Set Tuner.....May
 DeWald B-612.....Feb.
 Diode Filter Circuit.....Aug.
 Dual-Output Vibrator Power Supply.....May
 Du Mont Input Circuit (TV).....July
 Electromagnetic Picture Tube Voltage Circuits.....Dec.
 Electrostatic Deflection Picture Tube System.....June
 Electrostatic Picture Tube Voltage Circuits. Dec.
 Farnsworth FV-200 (Video Amplifier).....Feb.
 Farnsworth GV-240 (TV Picture Tube Circuit).....Aug.
 Farnsworth GV-260 TV Receiver.....Nov.
 Farnsworth GV-260 Horizontal AFC Circuit.....Dec.
 Flyback High Voltage Supply.....June
 FM Tuner (Cover).....July
 G. E. Model 14 Record Player.....June
 G. E. 210/211/212 (Cover).....Sept.
 G. E. 801 TV Receiver (Revised Model).....April
 G. E. 801 (TV Picture Tube Circuit).....Aug.
 G. E. 801 (Video Amplifier).....Feb.
 G. E. 901/910 (High Voltage and Picture Tube Circuit).....Oct.
 G. E. 803 (Broadcast Converter and Oscillator Circuit).....Aug.
 G. E. 803 (Horizontal Multivibrator and Sync Circuit).....Aug.
 G. E. 803 (Horizontal Sweep Circuit).....Aug.
 G. E. 803 (TV Receiver Block Diagram).....Aug.
 G. E. 803 (TV and FM R-F Amplifier, Converter and Oscillator Circuit).....Aug.
 G. E. 803 (Vertical Multivibrator and Sweep Output Circuit).....Aug.
 G. E. 803 (Video Detector and Amplifier Circuit).....Aug.
 G. E. 803 (Video and Audio I-F Circuit).....Aug.
 G. E. 810 TV Model.....Dec.
 G. E. 901/910.....Mar.
 G. E. Preamp M5C (Revised Model).....April
 G. E. Preamplifier (Revised to Increase 'Scope Gain).....Oct.
 G. E. Variable Reluctance Preamp. Circuit.....Oct.
 G. E. YGA-4 (Beat Frequency Audio Oscillator).....June
 G. E. YRS-1 Single Sideband Selector.....Sept.
 G. E. TV Intercrier Setup.....July
 Half-Wave Rectifier System.....April
 Harvey Radio V-H-F Signal Generator.....Jan.
 Hearing-Aid Circuits.....June
 Hearing Aid Output Circuit.....June
 Horizontal Deflection Circuit and Pulse Operated H-V Supply.....Nov.
 Howard 482 (Cover).....Aug.
 H-F and L-F Noise Suppressor Gate Circuits.....Sept.
 H-V Power Supply for 12GP7-CRT.....Nov.
 Intercom 2-Way Receiver-Speaker System.....June
 Kaiser-Frazer Auto Radio (1949 Model).....Nov.
 LP Adapter in AC/DC Set.....Nov.
 LP Adapter in Circuit Using a DPDT Switch.....Dec.
 LP Adapter in Dual I-F Circuit.....Nov.
 LP Adapter in Radio Phono Using Dual Volume Control.....Nov.
 LP Equalizer Circuit.....Dec.
 LP Filter Unit Circuit.....Dec.
 LP Pickup Circuits.....Dec.
 Magnetic Deflection Picture Tube System.....June
 Motorola Dispatcher-Receiver.....Dec.
 Motorola Dispatcher-Transmitter.....Dec.
 Motorola 508.....May
 Motorola 48L11.....July
 Motorola 58L11.....July
 Motorola 67L11.....July
 Motorola VT-71.....Mar.
 Motorola TS-5 TV Chassis.....Dec.
 Mixer-Input Systems.....Jan.
 Oldsmobile '46-'47 Receivers.....May
 Philco Crosshatch Generator 5072.....April
 Philco 48-2500 (Block Diagram of TV Projection Receiver).....Aug.
 Philco LP Adapter.....Nov.
 Pickering Booster Amplifier.....April
 Plug-In and Wired-In LP Circuits.....Nov.
 Premier Crystal Signal Generator.....May
 Reactance Modulator Circuit.....Sept.
 Receiver with Compensating Circuits and LP Adapter.....Nov.
 Remote-Control System.....Feb.
 RCA 630TS (Input).....July
 RCA 630TS (Video Amplifier).....Feb.
 RCA 641 (AGC TV System).....June
 RCA 641 (Signal-Voltage TV Circuit).....Aug.
 RCA MI-12775 (Cover).....Oct.
 RCA 8BX5 (Cover).....Feb.
 RCA WR-53A (Cover).....Nov.
 Scott 110-A (Cover).....Nov.
 Self-Rectifying Vibrator Power Supply.....May
 Signal Tracer.....Feb.
 Silver 909 (Cover).....Mar.
 Simultaneous Operation of Two FM Receivers with One FM Antenna.....Nov.

- Smith-Meeker RR37 (Sound System Broad-band Receiver).....June
 Sound-Light Amplifier (Electronic Baby Light).....Aug.
 Sound Powered Communication Setups.....Oct.
 Stabilized-Voltage Supply.....Feb.
 Stagger-Tuned 6AG6 Video I-F Amplifier.....Mar.
 Stagger-Tuned 6AU6 Video I-F Amplifier.....Mar.
 Stromberg-Carlson AM-43.....Nov.
 Stromberg-Carlson 925.....Feb.
 Stromberg-Carlson TV-12 (Block Diagram).....Aug.
 Stromberg-Carlson TV-12 (Complete Circuit).....Aug.
 Sync and Non-Sync Vibrator Circuits.....May
 Sync Separator Circuits (Diode, Triode and Pentode).....Oct.
 Tapped Volume-Control Bass-Boost Circuit.....June
 Tele-Tone TV-149.....Oct.
 Temco Teleshooter (Cover).....Jan.
 Three-Voltage Input Vibrator Power Supply.....May
 Tube and Selenium Rectifiers in Portables.....July
 Typical AC/DC/Battery Circuit.....July
 Truetone 4630.....May
 TV H-V Power Supply with Pulse System.....July
 TV H-V Power Supply with Doubler Arrangement.....July
 TV H-V Power Supply with Oscillator.....July
 TV H-V Transformer Type Power Supply.....July
 TV R-F Alignment Setup.....Nov.
 TV Stub Attenuation Control Circuit.....Sept.
 TV Time Constant Circuits.....Sept.
 TV Variable Inductance Tuning Circuit for 44-216 Mc.....Dec.
 Vibrator Tester (Cover).....May
 Victor 25 Home-Movie Amplifier Circuit.....June
 Victor 55 (Cover).....June
 Voltage Doublers.....July
 Voltage-Regulated Circuit.....Feb.

COVER DIAGRAMS

- Eggbeater Type FM Tuning System.....July
 FM Sweep Generator (RCA WR-53A).....Feb.
 FM/TV Sweep-Signal Generator (Silver 909).....Mar.
 FM Tuner (Howard 482).....Aug.
 Magnetic Wire Recorder-Playback (RCA MI-12775).....Oct.
 Pocket-Type Signal Generator (Clippard SI).....April
 Push-Button TV Receiver (Bendix 235M1/235B1).....Dec.
 Table AM/FM (G.E. 210/211/212).....Sept.
 3-Stage R-F TV Signal Booster (Temco).....Jan.
 Three-Tube Dynamic Noise Suppressor (Cover). By *E. G. Dyett, Jr.*.....Nov.
 Three-Tube Dynamic Noise Suppressor (Scott 110-A).....Nov.
 Vibrator Tester.....May
 Victor 55 (Home-Movie Projector Amplifier).....June
 W. E. 124E (12-Watt Amplifier).....June
 W. E. Wire Reproducer and Preamp Circuit.....June
 Westinghouse H-185/195.....July

EDITORIALS

- Annual Sound Issue.....June
 Associations and Servicing Standards.....Feb.
 At the Philadelphia Town Meeting of Technicians.....Jan.
 Auto Radio Servicing.....May
 FM Radio Relay.....Mar.
 Ideal FM/AM/Phono System.....Aug.
 Long-Playing Records.....Aug.
 Microgroove Records.....July
 New Servicing Opportunities.....Mar.
 New York Servicing Clinic.....Aug.
 No Licensing in New York.....April
 On the TV Front.....April
 Outdoor TV Antennas.....Sept.
 Preventive Maintenance.....July
 Preventive Maintenance.....Oct.
 RMA Service Committee.....Sept.
 The New York Town Meeting.....Oct.
 The Town Meeting Talks.....Feb.
 The TV Scoreboard.....June
 Town Meetings.....May
 Trends?.....May
 TV Alignment.....Sept.
 TV and the Service Man.....Mar.
 TV Receivers and Ignition Interference.....July
 TV Receiver Shipments Climb.....Sept.
 TV Training.....Feb.

FM

- Checking Locations for FM Antennas.....Nov.
 Converting FM Dipole for TV Use.....Mar.
 AM/FM Receiver Featuring Grounded-Grid Amplifier, Series-Resonant Circuits, and Ratio Type of Detector.....Jan.

FM/AM Receiver Featuring Grounded-Grid Amplifier, Series-Resonant Circuits, and Ratio Type of Detector.....	Jan.
FM-Antenna Directional Control.....	Nov.
FM Antenna Transmission Lines. By Les Graffis.....	Jan.
FM Antennas. By Les Graffis.....	April
FM Radio Relay.....	Mar.
FM Sweep Generator (RCA WR-53A).....	Feb.
FM Tuners and Receivers Using Ratio Detectors and Discriminators.....	Feb.
FM Tuner Using Eggbeater Type Unit (Cover). By James F. Gordon.....	July
FM/TV Dipole Antenna Length Chart.....	Mar.
Grounded-Grid Amplifier.....	Jan.
Matching to 72- and 300-Ohm Lines.....	Nov.
Multiple Antenna System Installations.....	Nov.
Practical FM Antenna Installations. By Ira Kamen.....	Nov.
Ratio Detectors.....	Jan.
Reactance Modulator Circuits Used in FM Receivers and Test Equipment.....	Sept.
Series-Resonant Circuits.....	Jan.
Selecting Proper FM Antennas.....	Nov.
The Reactance Modulator. By Douglas H. Carpenter.....	Sept.

FEATURES

Annual Index.....	Dec.
Application of the 'Scope in A-F Testing. By Alvin A. Baer.....	Apr.
At the Philadelphia Town Meeting of Radio Technicians. By Lewis Winner.....	Jan.
Association News.....	Jan.
Association News.....	Feb.
Association News.....	Mar.
Association News.....	Apr.
Association News.....	May
Association News.....	June
Association News.....	July
Association News.....	Aug.
Association News.....	Sept.
Association News.....	Oct.
Association News.....	Nov.
Association News.....	Dec.
Conversion Efficiency of Loudspeakers. By E. M. Edwards.....	Mar.
Curbing TV Receiver Proximity Interference. By Ira Kamen.....	Mar.
Dynamic Noise Suppressors. By Hermon Hosmer Scott.....	Sept.
Electric Megaphones in P.A. By Arthur J. Sanial.....	June
Electric Power Required for Sound System. By E. L. Kendall.....	Sept.
Electronic Baby Light. By Jack Najork.....	Aug.
FM Antennas. By Les Graffis.....	Apr.
FM Antenna Transmission Lines. By Les Graffis.....	Jan.
FM Sweep Generator (Cover).....	Feb.
FM Tuner (Cover).....	Aug.
FM Tuner Using Eggbeater Type Unit (Cover).....	July
FM/TV Sweep Signal Generator (Cover).....	Mar.
Hearing Aids. By Ira Kamen.....	June
High-Frequency TV Antenna Installations. By Ira Kamen.....	Sept.
Home-Movie Projection Amplifier (Cover).....	June
How the 'Scope Works. By Alvin A. Baer.....	Jan.
Increase Your 'Scope Sensitivity. By J. B. Farnum and Jack Najork.....	Oct.
Intercom System Using Receiver Speaker Setup. By Frederick E. Bartholy.....	June
Magnetic Wire Recorder-Playback (Cover).....	Oct.
New Products in Sound.....	June
Output Transformer Matching Chart. By Frederick E. Bartholy.....	Apr.
Pocket-Type Signal Tracer (Cover). By H. J. Gruber.....	Apr.
Practical FM Antenna Installations. By Ira Kamen.....	Nov.
Repairing Mechanical Phonographs. By Max Alth.....	July
Replacing the Output Transformer. By Frederick E. Bartholy.....	Jan.
'Scope Wave Patterns. By Alvin A. Baer.....	Mar.
Ser-Cuits.....	Jan.
Ser-Cuits.....	Feb.
Ser-Cuits (TV Receivers).....	Mar.
Ser-Cuits (Auto Receivers).....	Apr.
Ser-Cuits.....	May
Ser-Cuits (Portables).....	July
Ser-Cuits (Analysis of Stromberg-Carlson, G. E. and Philco Projection TV Circuits).....	Aug.
Ser-Cuits (Single Sideband Selectors; TV Projection Models).....	Sept.
Ser-Cuits (Complete Analysis of Admiral 301A TV Receiver).....	Oct.
Ser-Cuits (Stromberg-Carlson 25-Watt Amplifier, Kaiser-Frazer 1949 Auto Set, Farnsworth GV 260 TV Set).....	Nov.
Ser-Cuits (Motorola TS-5 TV, G.E. 810 TV and Farnsworth GV-260 TV sets).....	Dec.
Servicing Helps. By Charles P. Elliott.....	Jan.
Servicing Helps. By P. M. Randolph.....	Feb.
Servicing Helps. By P. M. Randolph.....	Mar.
Servicing Helps. By P. M. Randolph.....	Apr.
Servicing Helps. By P. M. Randolph.....	May
Servicing Helps. By P. M. Randolph.....	July
Servicing Helps. By P. M. Randolph.....	Aug.
Servicing Helps. By P. M. Randolph.....	Sept.
Servicing Helps. By P. M. Randolph.....	Oct.
Servicing Helps. By P. M. Randolph.....	Nov.
Servicing Helps. By P. M. Randolph.....	Dec.

(Continued on page 36)


TRANSVISION



NEW Television Kits and Equipment

Important Advances in TV Reception and Servicing!

NEW 10" TV KIT at amazingly LOW PRICE!

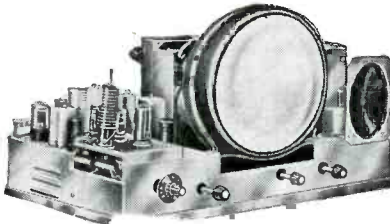

MODEL 10A TV KIT

The new Transvision Model 10A electromagnetic TV Kit gives a bright, stable 52 sq. in. picture. Has 10" picture tube, and CONTINUOUS TUNING on all 12 channels. Its high sensitivity makes for improved long distance reception; especially good on high channels. Complete with all-channel double-folded dipole antenna and 60 ft. of lead-in wire.
MODEL 10A TV KIT, less cabinet.....Net \$199.00
MODEL 12A TV KIT, same as above, but has a 12" picture tube.....Net \$263.00

NEW STREAMLINED CABINETS

for Transvision Model 10A or 12A TV Kit. Made of select grain walnut with beautiful rubbed finish. Fully drilled, ready for installation of assembled receiver.
Walnut Cabinet for 10A or 12A (Specify).....Net \$44.95
Mahogany and blonde slightly higher.

TRANSVISION ALL-CHANNEL TELEVISION BOOSTER

To assure television reception in weak signal areas, or areas which are out of range of certain broadcast stations, Transvision engineers have designed this new booster. It increases signal strength on all television channels. Tunes all television channels continuously. Can be used with any type of television receiver. Unusually high gain in upper television channels.
Model B-1.....LIST \$44.95


TRANSVISION REMOTE CONTROL UNIT KIT

Will operate any TV receiver from a distance. Turns set on, tunes in stations, controls contrast and brightness, turns set off. Ideal for installations where the television receiver is inaccessible. Tuner unit is a high gain, all-channel unit with about 50 micro-volt sensitivity. Easy to assemble in about an hour.
Model TRCU, with 25 feet of cable.....Net \$69.00
Without cabinet.....Net \$85.00

NEW TRANSVISION SWEEP SIGNAL GENERATOR FOR TELEVISION AND F.M.

Complete frequency coverage from 0-227 MC with no band switching. Sweep width from 0-12 MC completely variable. Accurately calibrated built-in marker generator.


OUTSTANDING FEATURES: (1) Frequency range from: 0-227 MC. (2) Dial calibrated in frequency. (3) Sweep width from 0-12 MC completely variable. (4) Self-contained markers readable directly on the dial to .5% or better. (No external generator required to provide the marker signals.) (5) Crystal controlled output makes possible any crystal controlled frequency from 5-230 MC. (6) Plenty of voltage output—permits stage-by-stage alignment. (7) Output impedance 5-125 ohms. (8) Directly calibrated markers 20-30 MC for trap, sound and video IF alignment. (9) RF for alignment of traps for IF channels when a DC volt meter is used as the indicating medium. (10) Unmodulated RF signal to provide marker pips simultaneously with the main variable oscillator. (11) Markers can be controlled as to output strength in the pip oscillator. (12) Power supply completely shielded and filtered to prevent leakage. (13) All active tubes are the new modern miniature type. (14) Phasing control incorporated in the generator.
MODEL NO. SG.....Net \$99.50

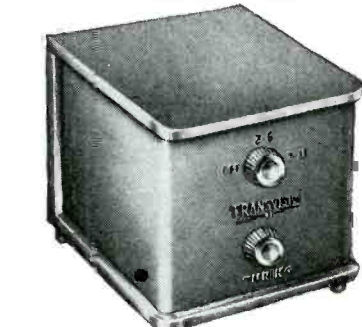

ALL-CHANNEL BOOSTER



REMOTE CONTROL UNIT KIT

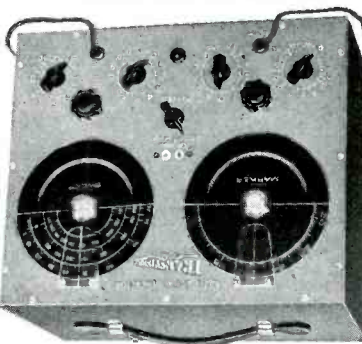

SWEEP SIGNAL GENERATOR

RADIOMEN... You Can GET INTO The TELEVISION BUSINESS In a BIG WAY with the TRANSVISION DEALER PLAN WRITE FOR FOLDER D-1

NEW 8-PAGE CATALOG showing complete Transvision line now available at your distributor, or write to:

TRANSVISION, Inc. Dept. S New Rochelle, N. Y.

In Calif.: Transvision of California, 8572 Santa Monica Blvd., Hollywood 46

All prices 5% higher west of Mississippi; all prices fair traded. All prices subject to change without notice.

New Book makes AUTO RADIO REPAIR twice as easy!

Covers all auto
Radio types from
mid-1930's to
present, includ-
ing mobile FM.



Just Out!

SERVICING THE MODERN CAR RADIO

by
A. L. Hurlbut

Second edition, 702 pages,
8 1/2 x 11, 222 illus., over 500
schematic circuit diagrams of
auto radio receivers, \$7.50

Here—written by a practical auto radio expert of 20 years' standing—is everything to help the beginner or experienced serviceman gain profitable skill in the fast-growing field of car radio servicing. A complete guide to the work. Book not only describes installation, testing, and repair methods fully, but also gives needed special facts of car radio circuits, differences between car and home radio servicing problems, shop set-up and business-getting ideas, etc. Particularly valuable for busy servicemen is the array of over 500 diagrams of specific circuit details on a large percentage of sets you may be called upon to repair.

Practical facts and methods on:

- getting into the car radio business
- differences between mobile and home radios
- antennas and input circuits
- power supplies
- circuit features
- auto electrical systems
- setting up shop
- car set installations
- antenna installation
- loudspeaker installation
- remedying interference
- servicing procedure
- vibrator maintenance
- loudspeaker servicing
- car-radio alignment
- push-button tuning, etc.

OPPORTUNITY OF A LIFETIME

for alert servicemen, says A. A. Ghirardi,
author of famous radio servicing
books and articles



ALFRED A.
GHIRARDI

"I believe SERVICING THE MODERN CAR RADIO represents an opportunity no wide awake serviceman can afford to miss. There are over 9,000,000 car radios—approximately 16 out of every 100 radios in use today—a wonderful field for increasing servicing business; increasing profits, stepping ahead of competition! Good auto radio men are scarce, and this book gives you a gold mine of information you need to cash in on this profitable, fast-growing business."

10 DAYS' FREE EXAMINATION

MURRAY HILL BOOKS, Inc.
(Division of Rinehart & Co.)

Dept. 8-128, 232 Madison Ave., New York 16, N. Y.
Send me Hurlbut's Servicing the Modern Car Radio for 10 days' examination on approval. In 10 days I will send \$7.50, plus few cents postage, or return book postpaid. Postage paid on cash orders; same return privilege. (Books sent on approval in U. S. only. Price outside U. S., \$8.00, postpaid.)

Name

Address

City (Zone) and State

Occupation

Index

(Continued from page 35)

Servicing Taxicab Radio. By Samuel Freedman	Dec.
Service Advertising. By Frank H. Cross	Apr.
Servicing AC/DC Models (Old and New). By Jack Dorr	July
Servicing 16-mm Sound-on-Film Projectors. By W. L. Lyons	June
Service Shop Tools. By Alfred A. Ghirardi	June
Signal Booster for TV (Cover)	Jan.
Soldering Tips	Apr.
Sound Literature	June
Sound Powered Communication in TV Installation Work. By K. I. Donald	Oct.
Sound System Installation in Community Auditoriums. By Jack Darr	Feb.
Ten Years Ago in Associations	Jan.
Ten Years Ago in Associations	Feb.
Ten Years Ago in Associations	Mar.
Ten Years Ago in Associations	Apr.
Ten Years Ago in Associations	May
Ten Years Ago in Associations	June
Ten Years Ago in Associations	July
Ten Years Ago in Associations	Aug.
Ten Years Ago in Associations	Sept.
Ten Years Ago in Associations	Oct.
Ten Years Ago in Associations	Nov.
Ten Years Ago in Associations	Dec.
Table AM/FM (Cover)	Sept.
The Engineering Approach in Servicing. By Frederick E. Bartholy	Feb.
The LP Microgroove Record System. By Ralph M. Baruch	Nov.
The LP Microgroove Record System. By Ralph M. Baruch	Dec.
The 1948 Radio Parts and Electronic Equipment Conference and Show	Feb.
The Reactance Modulator. By Douglas H. Carpenter	Sept.
The Sweep-Frequency Signal Generator. June	June
Tips on Soldering. By R. W. Kise	Mar.
Three-Tube Dynamic Noise Suppressor (Cover). By E. C. Dyett, Jr.	Nov.
Torque-Drive Phono Pickup. By A. Kahn	June
Tube News. By L. E. Stewart	Jan.
Tube News. By L. E. Stewart	Feb.
Tube News (TV Tubes). By L. E. Stewart	Mar.
Tube News. By L. E. Stewart	Apr.
Tube News. By L. E. Stewart	May
Tube News (Tube Complements of 18 TV Receivers). By L. E. Stewart	July
Tube News (Miniature Tube Basing Circuits). By L. E. Stewart	Aug.
Tube News (Pulse-Operated TV Power Supplies). By L. E. Stewart	Nov.
TV AGC and Picture Tube Voltage and Signal Systems. By Edward M. Noll	June
TV Antenna Installation. By Ira Kamen	July
TV Antenna-Installation Tools. By Ira Kamen	Apr.
TV Antenna-Receiver Installation Methods. By Edward M. Noll	Mar.
TV Installations in Fringe Areas. By Ira Kamen	Dec.
TV Interference. Causes and Remedies. By Ira Kamen	Oct.
TV Picture Tube Voltage and Signal Systems. By Edward M. Noll	July
TV Receiver Installation Pointers. By W. H. Buchsbaum	Nov.
TV Receiver Video Amplifiers. By Edward M. Noll	Jan.
TV Receiver Visual Alignment Techniques. By Lester L. Libby	Oct.
TV Receiver Visual Alignment Techniques. By Lester L. Libby	Nov.
TV Reception in Low-Signal Areas. By Ira Kamen	Apr.
TV Signal and Voltage Picture Tube Circuits. By Edward M. Noll	Aug.
TV Sync and Inter-Sync Systems (Part I). By Edward M. Noll	Sept.
TV Sync and Inter-Sync Systems (Part II). By Edward M. Noll	Oct.
TV Sync and Inter-Sync Systems (Part III). By Edward M. Noll	Nov.
TV Sync and Inter-Sync Systems (Part IV). By Edward M. Noll	Dec.
TV Variable Inductance Tuning. By John B. Ledbetter	Dec.
TV Video Amplifiers and AGC Systems. By Edward M. Noll	Feb.
Use of Math in 12-Channel TV Antenna Installations. By Ira Kamen	Aug.
Vibrator Design and Application. By Ralph G. Peters	May
Vibrator Power Supplies. By T. M. Sterling	May
Vibrator Tester (Cover)	May
Views and News. By Lewis Winner	Feb.
Views and News. By Lewis Winner	Mar.
Views and News. By Lewis Winner	Apr.
Views and News. By Lewis Winner	May
Views and News. By Lewis Winner	June
Views and News. By Lewis Winner	July
Views and News. By Lewis Winner	Aug.
Views and News. By Lewis Winner	Sept.
Views and News. By Lewis Winner	Oct.
Views and News. By Lewis Winner	Nov.
Views and News. By Lewis Winner	Dec.
Why Bass Boost. By Jack Najork	June
Your Shop Window. By H. G. Kronenwetter	Apr.
Your Success in Sound. By Robert Newcomb	Jan.

MANAGEMENT

Associations and Servicing Standards	Feb.
At the Philadelphia Town Meeting of Technicians. By Lewis Winner	Jan.
Building Sales with Effective Window Settings Through Proper Use of Displays, Lighting, Display Themes, etc.	May
Engineering Approach in Servicing. The. By Frederick E. Bartholy	Feb.
New Servicing Opportunities	Mar.
New York Servicing Clinic	Aug.
No Licensing in New York	April
Preventive Maintenance	July
Preventive Maintenance	Oct.
RMA Service Committee	Sept.
Service Advertising. By Frank H. Cross	April
The Engineering Approach in Servicing. By Frederick E. Bartholy	Feb.
The New York Town Meeting	Oct.
The 1948 Radio Parts and Electronic Equipment Conference and Show	Feb.
The Town Meeting Talks	Feb.
TV and the Service Man	Mar.
Your Shop Window. By H. G. Kronenwetter	May

SERVICING HELPS

Admiral Cartridge Circuit	July
Admiral TV Interference Filter	Nov.
Airline 62-188 (Wells-Gardner)	Nov.
Applying Heat and Solder Properly	Mar.
Auto Battery Ground Data	May
Auto Servicing Hints	May
Buffer Capacitor Reference Circuits	May
Capacitor Checker and Alignment Tool	Feb.
Case Histories (Philco, Sparton, Wilcox-Gay and Airline)	Nov.
Checking and Replacing Speakers	July
Clock Movements for Program Selection and On-Off Control	Oct.
Compensating Circuits	July
Converting FM Dipole for TV Use	Mar.
FM/TV Dipole Antenna-Length Chart	Mar.
How to Build an Isolation Transformer	Apr.
How to Apply Flux to Iron	Mar.
Hunting and Curing Oscillation, Hum and Tracking Problems	July
Installing Crystal Filter in Hallicrafters S-40	Mar.
Installing a Lightning Arrester in FM and TV Antenna Leads	Apr.
Improvements in the G. E. 801 TV Receiver	Apr.
Locating and Remedying Troubles Encountered in Tube and Dry-Rectifier Type Power Supply and Voltage Doubler	July
Mixer Inputs for Low and High Impedances. Twin Triodes and 2 to 8 Inputs	Jan.
Mixer Inputs with Twin Triodes, Pentodes and Cascaded Circuits for up to Eight Inputs. By Charles P. Elliott	Jan.
Preparing the Soldering Iron	Mar.
Pretinning Aluminum Surfaces	Mar.
Record Changer Repair Hints	Feb.
Capacitor Checker and Alignment Tool	Feb.
Remedy for Fogging Dials	Aug.
Retinning Soldering Iron Surfaces	Mar.
Revision in G. E. Preamplifier MSC	Apr.
Rules for Caring of Iron	Mar.
'Scope in Auto Servicing	May
Servicing AC/DC Models Old and New. By Jack Dorr	Nov.
Servicing Hints on Old Type Superhets	Nov.
Service Notes (Admiral 7T01, C, E, M and 7C64W-UL; Chevrolet 985255 and 985284; Philco 47-1226/1227/1230, 48-1264 and 48-200)	Aug.
Service Notes (General Television 51; Grunow 701 (Chassis 7A); Packard-Philco Auto Radio P-1835; Philco Auto Radio 938K; Philco 41-608; Sonora WAU WAU-243)	Sept.
Servicing Notes on Philco, RCA, Detrola, Emerson and Stromberg-Carlson	Oct.
Signal Tracer for Capacity Checkup, Code Practice and Auto Set Testing	Aug.
Sparton 5AM26	Nov.
Speech Equalization	July
Sonora WGFU 242	Nov.
Surplus C-R-T as a Picture Tube	Nov.
Tips on Soldering. By R. W. Kise	Mar.
Types of Solder and Flux to Use	Mar.
TV Components	Dec.
TV Picture-Tube Size Guide Chart	Sept.
TV Picture Tube Parts	Oct.
Use of Signal Tracer Unit as Power Supply	Feb.
Vibrator Specification Information	May
Vibrator Testing with a 'Scope	Oct.

SOUND

Acoustic Noise Level and Loudness Efficiency	Sept.
Admiral Cartridge Circuit	July
Altec Lansing Amplifier Kit	June
Annual Sound Issue	June
Audio Oscillator for Plotting of Frequency-Response Curves	June
Changes Required in Receiver to Accommodate Philco and Columbia LP Adapters	Nov.
Characteristics of LP Records	Nov.
Charts for Sound Powers	Sept.
Checking and Replacing Speakers	July

Classification of Noise-Reducing Systems for Recordings	Sept.
Conversion Efficiency of Loudspeakers. By E. M. Edwards	Mar.
Crystal Pickup Compensation Circuits	July
Community Auditorium, Sound System Installation in. By Jack Darr	Feb.
Dynamic Noise Suppressors. By Hermon Hosmer Scott	Sept.
Echoes and Reverberation	Sept.
Electric Megaphones in P.A. By Arthur J. Sanial	June
Electric Power Required for Sound Systems. By E. L. Kendall	Sept.
Gate Circuit Characteristics	Sept.
G. E. Model 14 Record Player	June
Handy Data on Selection of Proper Output Transformer, Such as Universal Outputs. Jan. Hearing Aids. By Ira Kamen	June
How to Make Sound-System Sales That Will Bring You More Business	Jan.
Ideal FM/AM/Phono System	Aug.
Intercom System Using Receiver Speaker Setup. By Frederick E. Bartholy	June
LP Equalizer Circuit	Dec.
LP Filter Unit Circuit	Dec.
LP Pickup Circuits	Dec.
Light-Sound Converter Amplifier	Aug.
Long-Playing Records	Aug.
Matching Taps of Output Transformer with Chart for All Types of Tubes	April
Magnetic Wire Reproducers Used in Sound Distribution System	June
Megaphones in P.A. Electric. By Arthur J. Sanial	June
Microgroove Records	July
Obtaining Maximum Intensity of Sound with Minimum Power Input	Mar.
Output-Transformer Matching Chart. By Frederick E. Bartholy	April
Output Transformer, Replacing the. By Frederick E. Bartholy	Jan.
P.A. Electric Megaphone. By Arthur J. Sanial	June
Phono Pickup, Torque-Drive. By Albert Kahn	June
Pickups and Motors Used for LP Systems	Nov.
Portable Battery-Type Electric Megaphones	June
Power Microphones	July
Preamps and Magnetic Wire Reproducers Used in Sound Distribution System	June
Radio-Phono Switch Applications	July
Receiver, Amplifiers, Preamps and Magnetic Wire Reproducers Used in Sound Distribution System	June
Record Changer Repair Hints	Feb.
Repair Hints for Spring Driven Phonograph Units	July
Repairing Mechanical Phonographs. By Max Alth	Sept.
Room Acoustics	Sept.
Replacing the Output Transformer. By Frederick E. Bartholy	Jan.
Rules for Bass Boosting	June
Servicing 16-mm Sound-on-Film Projectors. By W. L. Lyons	June
Speech Equalization Methods	July
16-mm Sound-on-Film Projectors. By W. L. Lyons	June
Sound-on-Film Projectors. By W. L. Lyons	June
Sound Pressure Value Chart (Provides Data on Power Required Per Speaker, Distribution Angle and Proper Size Amplifier Required)	Mar.
Sound System Installation in Community Auditorium. By Jack Darr	Feb.
Sound, Your Success In. By Robert Newcomb	Jan.
The Electronic Baby Light. By Jack Najork	Aug.
The LP Microgroove Record System. By Ralph M. Baruch	Nov.
The LP Microgroove Record System. By Ralph M. Baruch	Dec.
Torque-Drive Phono Pickup. By Albert Kahn	June
Victor 55 (Home-Movie Projector Amplifier)	June
What the Response Curve Means	June
Why Bass Boost. By Jack Najork	June
Why Compensation Is Used	June
Your Success in Sound. By Robert Newcomb	Jan.


TELEVISION

A TV Crosshatch Generator	April
Adjustment of Ion Traps	Nov.
Admiral 301A TV Chassis	Oct.
AGC Circuits in TV Receivers	June
AGC Systems, TV Video Amplifiers. By Edward M. Noll	Feb.
Alignment Data for Tele-Tone TV-149	Oct.
Aluminum-Backed TV Picture Tube Characteristics	May
Analysis of Nine Causes of TV Interference and Solutions	Oct.
Analyzing TV Signal-To-Noise with Test Setups	July
Beam-Relaxor Horizontal-Scanning Properties	July
Bendix 235M1/235B1 Push-Button TV Receiver (Cover)	Dec.
Checking TV Antenna with Test Set	Mar.
Comparison of Sync Separator and DC Restorer Operation	Nov.
Converting FM Dipole for TV Use	Mar.

(Continued on page 38)

Stay on the beam

WITH TENNA·ROTOR

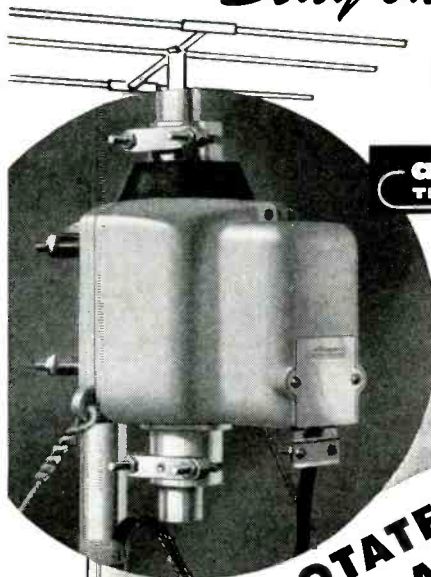

alliance
TENNA·ROTOR

GETS **STRONGER SIGNALS**

ROTATES TV AND FM ANTENNA

LIST PRICE **\$39.95**



CONTROL BOX
Size of box 5" x 5"
Approx. weight 12 lbs.

Model
ATR
Size of
rotor
unit
7 3/4"
x 5 1/4"
x 8"

Operates in any weather.
Fits most types of antenna.

Alliance Tenna-Rotor is an electric antenna rotator. It assures correct antenna "beaming"—gives positive control of antenna rotation to select the exact position for "peaked" reception! Tenna-Rotor is quick and easy to install—the electric powered rotor unit resists corrosion—is enclosed in a split zinc, die-cast housing, and is operated from a plastic control box which plugs into any 110 volt, 60-cycle house circuit. A 3-position switch rotates antenna clockwise or counter clockwise and stops it at the right point. Four-conductor inter-connecting cable from rotor to control box is made available at 5 1/2¢ per foot.


TV and FM service dealers, and users, will find that the Alliance Tenna-Rotor simplifies and improves new and existing installations!

Write for catalog sheet and illustrated folder.

alliance motors

ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO
Export Department; 401 Broadway, New York, N. Y., U. S. A.

SOUND DISPATCHING SYSTEM

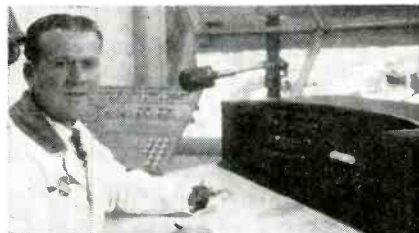

Dispatcher console receiver developed by Corbett, Veek and Co., Portland, Oregon, for garage service. Console-type switchboard employs a combination speaker-microphone with a system of lights and push buttons providing two-way contact to all parts of the garage and shop affording an accurate record of the location of cars and services being rendered to them.

PUSH-BUTTON SOUND DEMONSTRATOR



Push-button panel system in use at Sun Radio and Electronics Co., Inc., 122-124 Duane St., N. Y., which provides contact to a host of tuners, amplifiers, changers and speakers for effective demonstrations. Panel setup was developed by Irving Greene, manager of the sound and TV department.

AMPERITE

Studio Microphones
at P.A. Prices

Ideal for BROADCASTING

- RECORDING
- PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- The only type microphone that is not affected by any climatic conditions.
- Guaranteed to withstand more "knocking around" than any other type mike.

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.

AMPERITE Company, Inc.

561 BROADWAY • NEW YORK 12, N. Y.

In Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto



Models
RBLG—200 ohms
RBHG—Hi-imp.
List \$42.00




"Kontak" Mikes
Model SKH, list \$12.00
Model KKH, list \$18.00

Index

(Continued from page 37)

Corona Control on 5PT4 Projection Tube...	Mar.
Circuit Data on G.E. 901/910.....	Oct.
Circuit Data on Philco 48-2500 Projection Model.....	Oct.
Circuits for Sound Powered Telephones.....	Oct.
Curbing TV Receiver Proximity Interference. By <i>Ira Kamen</i>	Mar.
Curing Local Oscillator Reradiation.....	Mar.
Differentiation and Integration Circuits and How They Operate in TV Sets.....	Nov.
Difference Between Separator and Restorer Systems.....	Oct.
Electromagnetic Picture Tubes.....	Dec.
Electrostatic Picture Tubes.....	Dec.
Eliminating Leading Ghosts.....	Mar.
Farnsworth GV-260 Horizontal AFC Circuit.....	Dec.
Features of TV Antennas.....	July
Filter System Designs.....	July
Flyback High Voltage Supply.....	June
Functions of DC Restorers.....	Oct.
G. E. 803.....	Aug.
G.E. 810 TV Model.....	Dec.
G. E. 901/910 TV Projection Receiver.....	Sept.
G. E. TV Intercarrier Setup.....	June
General Functions of Video Amplifiers.....	Jan.
High-Frequency TV Antenna Installations. By <i>Ira Kamen</i>	Sept.
HF TV Antenna Installation Procedures.....	Sept.
H-V Pre-Wound Oscillator Transformer Design Features.....	July
High Voltage Systems Used in Magnetic Deflection Picture Tubes.....	June
How the Horizontal Sweep Output Transformer Works.....	July
High Voltage Systems Used in Electrostatic Picture Tube Circuits.....	June
Intercarrier Circuit Designs.....	June
Instructing Customer on TV Set Operation.....	Mar.
Linearity Control.....	Nov.
Local Oscillator Interference Problems.....	Sept.
Locating and Eliminating Multiple Reflections.....	July
LF Tuned Indoor and Outdoor TV Antennas.....	Sept.
Metal Backs Which Act as TV Antennas.....	Sept.
Motorola TS-5 TV Chassis.....	Dec.
On the TV Front.....	April
Operation of TV DC Restorers in Grid-Rectifier Systems.....	Jan.
Oscillator High-Voltage Supply Characteristics.....	July
Outdoor TV Antennas.....	Sept.
Philco 48-2500 Projection Model.....	Aug.
Picture Centering.....	Nov.
Picture Focusing.....	Nov.
Picture Quality Control.....	Nov.
Picture Tube Circuits in DuMont RA-101.....	Aug.
Picture Tube Circuits in Farnsworth GV240.....	Aug.
Picture Tube Circuits in G. E. 801.....	Aug.
Picture Tube Circuits in RCA 641.....	Aug.
Picture-Tube Coating Capacity Effects.....	July
Picture-Tube Signal Circuits.....	Jan.
Picture-Tube Signal Circuits.....	Feb.
Proper Installation of TV Picture Tube.....	Nov.
Pulsed H-V System Operation.....	July
Pulse-Operated TV Power Supply.....	Nov.
Practical Alignment Procedure for Tele-Tone TV 149.....	Nov.
Receiver Video Amplifiers, TV. By <i>Edward M. Noll</i>	Jan.
Rectangular Pulse Operation.....	Sept.
Relationship of Signal and Voltage to Picture-Tube Operation.....	June
Remedies for Nine Causes of TV Interference.....	Oct.
Remedies for TV Interference Problems.....	Mar.
Resistors at HF.....	Sept.
Solving Major HF TV Installation Problems.....	Sept.
Solving TV Reflection Problems.....	July
Sound Powered Communication in TV Installation Work. By <i>K. I. Donald</i>	Oct.
Sound Powered Telephones.....	Oct.
Stagger-Tuned Video I-F Systems Using 6AG5, 6AU6, 6BA6, 6AK5, 6BJ6 and 6BH6 Miniatures.....	Mar.
Stub Filters for Cutting Out Interference in Channels 2 to 6.....	Sept.
Sweep Circuit Reradiation Problems.....	Mar.
Sync Clipping.....	Oct.
Sync Separators (Diode, Triode and Pentode).....	Oct.
The TV Scoreboard.....	June
Time Constants.....	Sept.
Transformer-Type High-Voltage Supplies.....	July
Tube Complements of 18 TV Receivers (Philco, RCA, G. E., Crosley, Emerson, Belmont, Admiral, Hallicrafters and Motorola).....	July
TV Alignment.....	Sept.
TV AGC and Picture-Tube Voltage and Signal Systems. By <i>Edward M. Noll</i>	June
TV Antenna Installation. By <i>Ira Kamen</i>	July
TV Antenna-Installation Tools. By <i>Ira Kamen</i>	May
TV Antenna-Receiver Installation Methods. By <i>Edward M. Noll</i>	Mar.
TV Automatic Gain Control Circuits.....	Feb.
TV Components.....	Dec.
TV DC Restorers.....	Feb.

Ask For Model 209

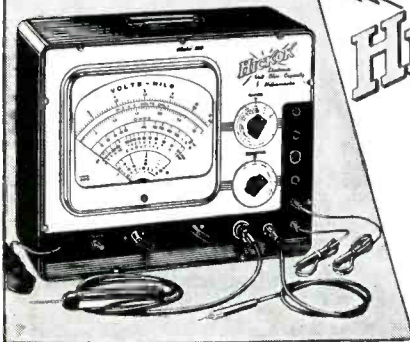

THE

HICKOK

World Famous

Electronic

VOLT—OHM—CAPACITY
MILLIAMMETER

Large laboratory size with giant 9-inch meter. Measures resistance (.1 ohm to 10,000 megohms), capacitance, inductance, current, voltage, both AC (30 cycles to 300 megacycles) and DC. A universal test instrument for all radio and electronic service work.

See Your Jobber Today or Write for Literature

THE HICKOK ELECTRICAL INSTRUMENT CO.
10521 Dupont Avenue • Cleveland 8, Ohio

GREYLOCK

A DEPENDABLE NAME IN
RADIO TUBES

GT, Glass, and Miniature Types

All Tubes in Individual Cartons

IR5	3Q4	12SA7GT	} 39¢ each
IS5	3V4	12SK7GT	
IT4	6AT6	12SQ7GT	
IU4	6BA6	(and many	
3S4	6BE6	others)	

SPECIAL OFFER! All 39¢ tubes may be purchased in lots of 100 assorted, at \$35 per 100.

Specials: 2E24.. 89¢ 6BG6G.. 89¢

TERMS: Net C.O.D. F.O.B. NYC. 35¢ handling charge on all orders under \$5. Write for Bargain Catalog S-12.

Greylock Electronics Supply Co.

30 Church Street New York 7, N. Y.

FOR TV SERVICING

Investigate the Mega-line
of instruments:

MEGA-SWEEP

MEGA-PIPPER

MEGA-MARKER

MEGA-MARKER SR.

Request Catalog

Kay Electric Company

19 Maple Ave., Pine Brook, N. J.

TV and the Service Man.....	Mar.
TV Interference. Causes and Remedies. By	Oct.
<i>Ira Kamen</i>	Sept.
TV Interfering Frequencies.....	Sept.
TV Installations in Fringe Areas. By	Dec.
<i>Ira Kamen</i>	Sept.
TV Picture-Tube Size Guide Chart.....	Sept.
TV Picture-Tube Voltage and Signal Sys-	July
tems. By <i>Edward M. Noll</i>	Mar.
TV Pretesting in Shops.....	April
TV Reception in Low-Signal Areas. By <i>Ira</i>	Nov.
<i>Kamen</i>	Sept.
TV Receiver Installation Pointers. By <i>W.</i>	Sept.
<i>H. Buchsbaum</i>	Sept.
TV Receivers and Ignition Interference.....	Sept.
TV Receiver Pulse Techniques.....	Sept.
TV Receiver Shipments Climb.....	Sept.
TV Receiver Video Amplifiers. By <i>Edward</i>	Jan.
<i>M. Noll</i>	Oct.
TV Receiver Visual Alignment Techniques.	Nov.
By <i>Lester L. Libby</i>	Nov.
TV Receiver Visual Alignment Techniques.	Sept.
By <i>Lester L. Libby</i>	Oct.
TV Sync and Inter-Sync Systems (Part	Nov.
I). By <i>Edward M. Noll</i>	Oct.
TV Sync and Inter-Sync Systems. (Part	Nov.
II). By <i>Edward M. Noll</i>	Nov.
TV Sync and Inter-Sync Systems (Part	Nov.
III). By <i>Edward M. Noll</i>	Dec.
TV Sync and Inter-Sync Systems (Part IV).	Aug.
By <i>Edward M. Noll</i>	Dec.
TV signal and Voltage Picture-Tube Cir-	Feb.
cuits. By <i>Edward M. Noll</i>	Feb.
TV Variable Inductance Tuning. By <i>John</i>	Jan.
<i>B. Ledbetter</i>	Feb.
TV Video Amplifier and AGC Systems. By	Jan.
<i>Edward M. Noll</i>	Feb.
TV Training	Feb.
Video Amplifiers TV Receivers. By <i>Ed-</i>	Jan.
<i>ward M. Noll</i>	Feb.
Video Amplifier and AGC Systems, TV.	Feb.
By <i>Edward M. Noll</i>	April
Video Amplifier Systems in G. E. 801,	Aug.
RCA 630TS and Farnsworth FV200....	Oct.
Unitary TV Tuner-Amplifier.....	Oct.
Use of Math in 12-Channel TV Antenna	Oct.
Installations. By <i>Ira Kamen</i>	Oct.
Uses of Square Pulses.....	Oct.

TEST EQUIPMENT

A TV Crosshatch Generator.....	April
Application of The 'Scope in AF Servic-	April
ing. By <i>Alvin A. Baer</i>	May
Crystal-Controlled Signal Generator.....	Jan.
How the 'Scope Works. By <i>Alvin A. Baer</i>	Mar.
How to Use Controls on the 'Scope.....	Oct.
Increase Your 'Scope Sensitivity. By <i>J. B.</i>	Oct.
<i>Farnum</i> and <i>Jack Najork</i>	Oct.
Modified Reluctance Pickup Preamp for	Oct.
Increased 'Scope Gain	April
'Scope in A-F Servicing. By <i>Alvin A.</i>	Mar.
<i>Baer</i>	June
'Scope Wave Patterns. By <i>Alvin A. Baer</i>	June
Signal Generator (Sweep-Frequency).....	June
Sweep-Frequency Signal Generator.....	April
Three Methods of Testing A-F Amplifiers	Mar.
with a 'Scope; A-F Oscillator .. Sweep-	Feb.
Frequency Record .. Square-Wave Sig-	Oct.
nal Generator.....	April
Typical 'Scope Pictures Illustrating Meth-	Mar.
ods of Operation	Feb.
Use of Signal Tracer Unit as Power Sup-	Oct.
ply	April
Vibrator Testing with a 'Scope.....	April
VHF Signal Generator.....	April

TUBE NEWS

Aluminum-Backed TV Picture Tube Char-	May
acteristics	Jan.
Classification Data on Converters and	Jan.
Mixers	Feb.
Cold-Cathode Glow-Discharge Type Tubes;	Mar.
RCA 5651, OA2, and OB2, and Syl-	Aug.
vania OA4G	Mar.
Corona Control on 5TP4 Projection Tube	Aug.
Diode Filters	April
FM Detector Tube for Instantaneous Lim-	Jan.
iting and Single-Circuit Discriminator	Jan.
Hearing-Aid Subminiatures.....	Aug.
Improved Circuit Arrangements Available	Aug.
with New Base-Pin Connections of	April
35C5, 50C5, 6BH6, 12AW6 and 6BJ6	April
Miniatures	Nov.
New FM Detector Tube for Instantaneous	April
Limiting and Single-Circuit Discrimina-	Nov.
tor	May
New RCA Miniatures	May
Pulse-Operated TV Power Supply.....	July
Rectifiers in AC/DC Receivers.....	Jan.
Stagger-Tuned Video I-F Systems Using	Mar.
6AG5, 6AU6, 6BA6, 6AK5, 6BJ6 and	Nov.
6BH6 Miniatures	Jan.
The 10BP4 in Pulse-Operated Power Sup-	Jan.
ply	July
Tetrode and Pentode Detectors and Oscilla-	May
tors	Jan.
Tube Complements of 18 TV Receivers	July
(Philco, RCA, G. E., Crosley, Emerson,	Jan.
Belmont, Admiral, Hallicrafters, Motorola)	Jan.
Tubes for AC/DC AM/FM Receivers.....	April
Triode, Beam Tube and Pentode Amplifiers.	April
Triode Detectors and Oscillators.....	April
Use of 6E5, 6U5 and 6N5 for Balance In-	April
dication in FM Discriminators.....	April



Replacements FOR ALL SETS!

Television creates new opportunities of profit for servicemen and a new need for replacement speakers. Now Utah announces two new ovals especially designed for TV. Both are 4x6's, the SE46T6 with a 60 ohm field and the SE46T10 with 100 ohms resistance. Other ovals in the Utah line qualify for use in television sets. Many permanent magnet weights and various field coil resistances are available in 4x6's, 5x7's and 6x9's. TV is big business — see your jobber today.



UTAH RADIO PRODUCTS
HUNTINGTON, INDIANA
 DIVISION OF INTERNATIONAL DETROLA CORPORATION
 EXPORT DIVISION: MORHAN EXPORTING CORP. N. Y., N. Y.

UTAH FOR AM, FM, VIDEO

VALPARAISO TECH. INSTITUTE FM/TV CLINIC

An FM/TV clinic sponsored by Valparaiso Technical Institute, Valparaiso, Indiana will be conducted on Monday, January 24, for the benefit of Northern Indiana Service Men, dealers and distributors.

Dr. Joseph B. Hershman, president of Valparaiso Technical Institute, will serve as chairman of the clinic and the heads of the school's television and radio servicing laboratories will also take part in the clinic. Technical field representatives from the instrument and model manufacturers will then present solutions to various technical problems inherent to their specific models.

ATLAS SOUND COST-PROPOSAL FOLDER

An *Estimate and Proposal Folder* to assist sound specialists in presenting a businesslike proposal which will create confidence in the prospect, has been prepared by Atlas Sound Corporation, 1449 39th St., Brooklyn 18, N. Y.

Folder is available at no charge from Atlas.

* * *

BIGELOW JOINS MAGNAVOX

John F. Bigelow has been appointed director of service training for the radio division of The Magnavox Company. Bigelow was formerly manager of the publications and training section of the Farnsworth service department.

IRC Power Wire Wounds are better built every step of the way




Starting right from the winding form IRC Power Wire Wounds combine the best of materials, workmanship and resistor "know-how".

Highest grade alloy wire uniformly wound on sturdy ceramic tubes. Terminals spot welded for security; heavily tin dipped for easy soldering.



Climate-proof cement coating provides dark, rough surface—best for rapid heat dissipation, moisture protection and ability to withstand reasonable overloads.

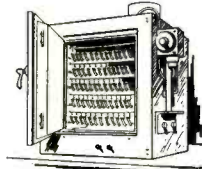Resistors cured at LOW temperature prevents damage to resistance windings, and loss of temper in terminals. Bands for adjustable types feature stainless steel springs and silver contacts. Cannot corrode to cause high resistance.



For exacting, heavy-duty requirements you can rely on IRC Power Wire Wounds for balanced performance in every characteristic. Being full-sized, they can operate continuously at full rating. Derating in high ranges is unnecessary.

IRC Power Wire Wounds are available in a full range of ratings, sizes and terminal types. 91 new ranges have just been added. Next time you step up to your distributor's counter—stock up on IRC Power Wire Wounds.



INTERNATIONAL RESISTANCE CO.

401 N. Broad Street, Phila. 8, Pa.

In Canada: International Resistance Co., Ltd.,
Toronto, Licensee



**YES! We're listed
in the RED BOOK**
Looking for the correct
IRC replacement controls for any receiver
manufactured from
1938 to 1948? Just
refer to the Radio
Industry RED BOOK!

Taxicab Radio

(Continued from page 11)

a toggle switch is closed due to poor, intermittent or no contact.

(c) Relay contacts failing to close because the spring tension is too tight, or failing to open because the spring tension is inadequate. It may also be due to dirty, pitted or glazed relay contacts, or poor alignment of relay contacts.

(2) Loose connections or hardware. This is due to vehicular vibration. It may also be due, without regard to quality of equipment, to mechanical resonant frequencies developed when vehicle is moving or engine is running. Such resonant vibrations should be avoided, when found to exist, by set placement or shock mounting so as to respond to frequencies other than developed in the vehicle. Every form of matter or material has a resonant frequency of a destructive nature. Every part also has a resonant frequency of mechanical vibration depending on its size, shape, composition, weight, placement and behavior with variations in temperature. Trouble can develop where there has been no or inadequate provision for expansion or contraction of parts due to temperature or vibration. This has been particularly true in the case of early post-war mobile designs where the manufacturer's past experience has been confined to equipment used at fixed stations.

(3) Poor electrical continuity. This may take a variety of forms such as:


(a) Broken wire under the insulation. Stranded wire with considerable flexibility will minimize this possibility both in breaking and in providing continuity even if one or more of the many strands break.

(b) Faulty lug connections where the wire terminates.

(c) Poor solder connection. Each connection should hold by virtue of the solder and also by virtue of being securely wrapped to a prong or terminal wherever possible.

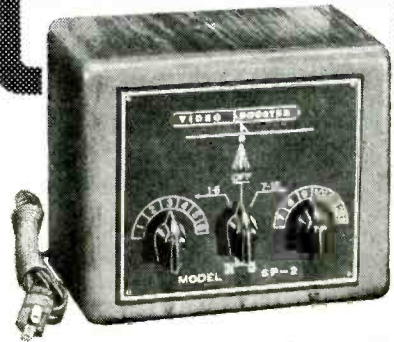(d) Loose or bad connection to the many pins of the plugs and jacks used for cable interconnections. The cable jack and plug in each case should be positively joined and secured.

Perfect Performance
with **RMS VIDEO**
ANTENNA BOOSTER



13 CHANNELS \$37⁵⁰
Model SP-2 list
6 Channels, Model SP-1 \$33.75

Boosts weak stations . . . Pulls in distant stations with signal strength gain SIX TO TEN TIMES! . . . Cuts down off-channel interference . . . Has self-contained power supply . . . eliminates need for outdoor TV antenna in most local installations . . . NEW: pilot light prevents leaving set on overnight.

DEALERS! Your local distributor has this as well as other fast-moving RMS television accessories in stock.


RADIO MERCHANDISE SALES INC.
550-S Westchester Ave., N. Y. 55, N. Y.


(e) Broken wire in the microphone cable. The microphone or handset is lifted off its receptacle or hook constantly during transmission. It sometimes falls on the floor, gets caught in the door, stepped upon or otherwise abused. When the wiring is defective, it is usually a very short distance from where the microphone cable enters the microphone unit and can be repaired by cutting back about six inches on the cable. Flexing of the cable is greatest a few inches from where the cable terminates in the microphone. Since the press-to-talk button is on the microphone, a defective microphone cable can put the whole system out of commission, particularly if the right wire or wires break in the cable.

(4) Defective or poorly seated vacuum tubes. The life of vacuum tubes depend on manufacturing quality, proper adjustment and alignment of circuits, how hard they are energized and utilized in a circuit, correctness of heater voltages, efficiency of the storage battery voltage regulator, ability and opportunity to dissipate heat, number of times turned on and off, length of operating service, etc. The net result has been that tubes have an average life varying from 1,000 to over 10,000 operating hours.

Other troubles encountered by the author in the installation and service-

Figure 4. Details of the dummy antenna used for adjusting the dispatcher transmitter.

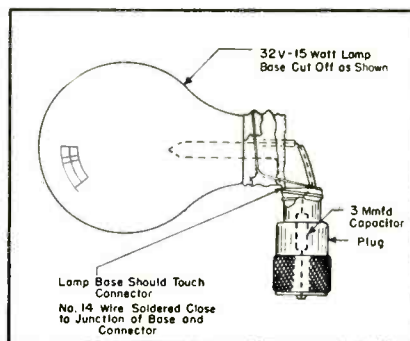

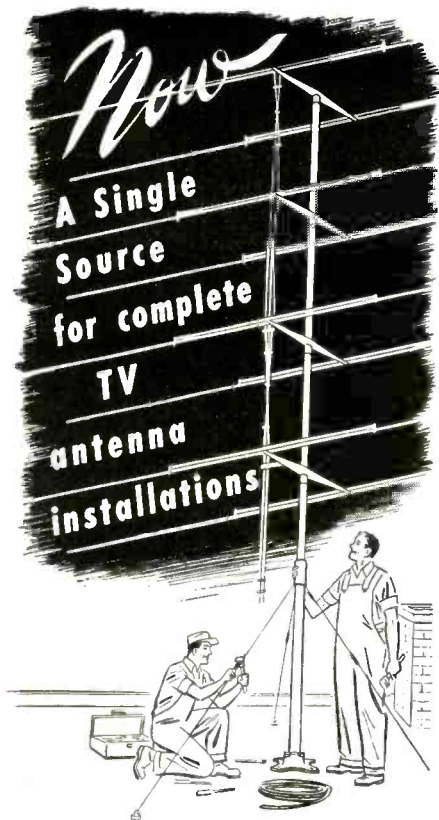

At long last you can obtain all of the necessary accessories required to make the finest TV antenna installation. VEE-D-X, the name that has put more vision into television, now supplies complete accessories to your jobber.

Saves time . . . shopping around for turnbuckles, guy wire, and masts has been eliminated by this complete and dependable single-source.

See your favorite radio parts jobber for these VEE-D-X products:

Long range, high gain antennas • Primary FM and TV antenna • No loss lightning arresters • Two- and three-stage pre-selectors • Light weight magnesium masts • "All-Angle" aluminum antenna base mounts • Manual orienting rotators • Guy Wire • Cable clamps • Stand-offs • Turnbuckles • X-200A heavy duty transmission line • 300 ohm transmission line.

LaPOINTE PLASCOMOLD CORP.
UNIONVILLE, CONN.




ing of over fifty two-way systems have been wrong grounds, particularly when swapping radio units between cars having the storage battery grounded on the positive instead of negative side or vice versa, wrong tube in a particular socket, broken tube key so that tube prongs were in wrong tube socket holes, reversed receiver vibrator so that it received wrong current polarity, inadvertent omission of part equipment or a tube in the equipment when it is returned to the vehicle, antenna cable not plugged into the set, certain tubes unable to operate at the required very high frequency even though others of the same type can do so due to a certain run of tubes or changes in manufacturer, poor tube-socket prong connections, poor antenna circuit continuity between roof-top antenna and the set, floating shield or sheath on the coaxial cable between antenna and set, excessive resilience or throw in the shock mounts, inadequate shock mounting for the vehicle and the terrain it travels over, grid caps off tubes, bad quartz crystal due to dirt, chip or improper tension with respect to its contact plates, faulty modulation due to a voice too loud for a sensitive microphone or too weak for an insensitive microphone, defective parts which have changed in their electrical value, loose or poor grounding or bonding of cabinet or parts on the chassis, defective loudspeaker cone or voice coil, wet equipment due to leaky rear trunk door seams, dirty antenna insulator, etc.

While it is true that some equipments have been giving less trouble than others, the fact remains that no equipment can function without a competent Service Man indefinitely. A competent Service Man, in the case of mobile radio, is one who can understand the instruction book and who can supplement it with common sense and good judgment.

While all mobile equipment, regardless of manufacturer, has approximately the same makeup, the instruction book is different in every case.

Since a Service Man usually serves a fleet of vehicles having identical equipment, the work becomes simple or routine after a short time if case histories are recorded or remembered. Manufacturers normally reserve the right to make improvements in subsequent equipments based on the experiences obtained in the field. It therefore is very likely that the troubles encountered in earlier models will not exist in later models. Conversely, troubles developed in later models may not be found to exist in earlier models.

[To Be Continued]

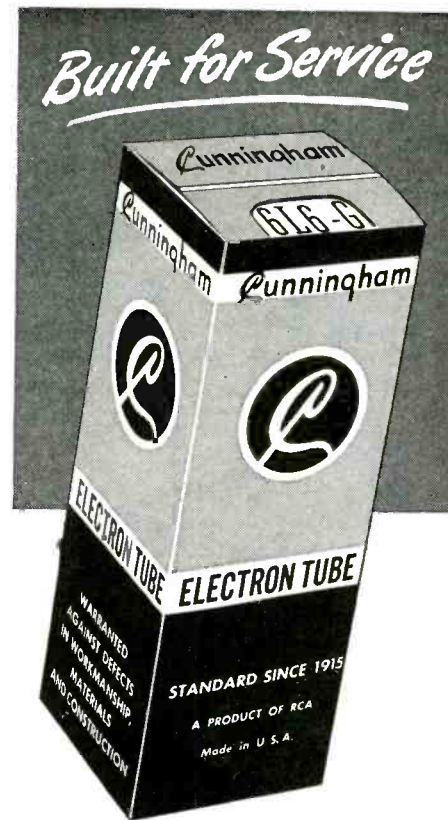


The winning tube!
in . . .



• Experienced servicemen in Nebraska have elected Cunningham tubes . . . because Cunninghams have demonstrated their long life and top performance since 1915. You can count on more satisfied customers if you replace with top-quality Cunninghams . . . "the tube that's built for service."

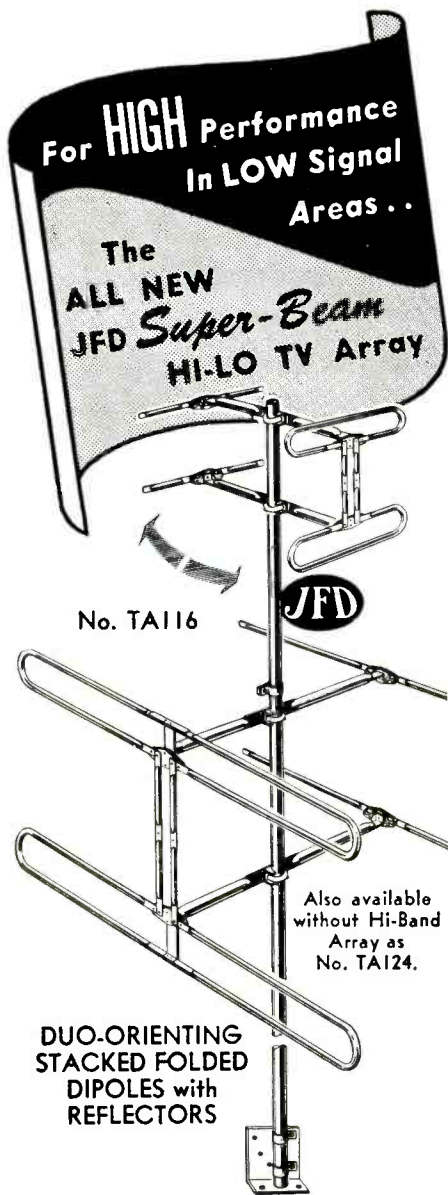See your
CUNNINGHAM DISTRIBUTOR
HICKS RADIO COMPANY
Lincoln





LOOK AT THESE LONG-RANGE PERFORMANCE FIGURES FROM ACTUAL REPORTS!

CITIES	DISTANCE IN MILES
Albany - New York	125
Cleveland - Pittsburgh	120
New Haven - New York	110
San Diego - Los Angeles	100
South Bend - Chicago	90

OUTSTANDING FEATURES!

- ✓ Gives full 12 channel TV reception plus FM.
- ✓ Supplied complete with 10' Mast, All-Angle Mounting Bracket and Stand-Off Insulators.
- ✓ U-Bolt Clamp construction provides 1/8, 1/4 or 1/2 wavelength spacing of 2, 4, 6, or more bays on mast for tremendous stacking flexibility—also permits independent orientation of each bay.
- ✓ Lightning-fast assembly time.
- ✓ Impedance of 150-260 ohms and +8.6 DB gain.
- ✓ All-weather Roto-lock insulator made from low-loss polystyrene for perfect high frequency insulation.

Write for Literature



4111 Ft. Hamilton Pkwy., Brklyn 19, N. Y.

"Manufacturers of the World's Largest Line of TV/FM Antenna Equipment"

TV Antennas

(Continued from page 13)

earlier article in this series.¹ This antenna is preferred in fringe areas when the desired high-frequency channel is being transmitted from a different direction than the low frequency channels.

In another type of 12-channel high-gain TV antenna design, there appears an effective compromise on directivity gain and bandwidth; Fig. 9. This antenna combines the added signal on two stacked broadband dipoles and reflectors for a single transmission line. A unique design feature is that the larger low-frequency folded dipoles act as reflectors for the smaller high-frequency folded dipoles on the 174 to 216-megacycle band.

This antenna, however, attenuates the FM band. This feature has both advantages and disadvantages. When a television receiver is connected to this antenna and the receiver has poor image-frequency rejection, the antenna's characteristic of attenuating the FM band is helpful. In commercial installations, where the TV receiver has an inductive type tuning device for the FM band (88 to 108 mc), reception of FM programs may not be satisfactory. This antenna should be used in fringe areas where all the stations are in a single direction as there are no separate adjustable directional elements on the array.

Another widely used uni-directional stacked antenna² is a *four bay* stacked array (Fig. 11) which develops a high forward gain and has a beamed horizontal pick-up pattern. A feature of this antenna is its tunable Q sections. These sections enable the installer to adjust the impedance of the antenna so that it matches the transmission line for the most desirable television channel. The best field method for adjusting Q sections on this or any other antenna is:

(1) The contrast control of the receiver is adjusted so that the pattern on the desired station is barely discernible.

(2) The Q section is adjusted along the line to the point where the contrast of the pattern is improved (made clearer and darker); this adjustment is like resonance tuning and therefore care must be exercised in adjusting back and forth for peak gain.

The adjustment is somewhat critical and is a job for two men with a 'phone connection. A properly adjusted Q section enables the realization of every db available from the antenna.

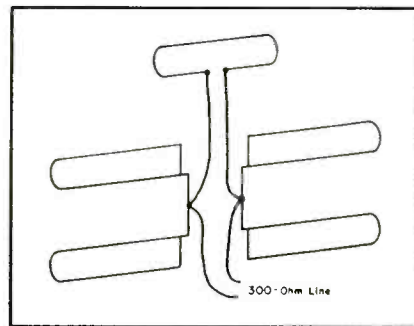


Fig. 8. Circuit for connecting a beamed high-frequency attachment to low-frequency arrangement.

The direct view type TV receivers should be selected for fringe area installation because:


- (1) Projection receivers require greater signal drive.
- (2) Definition is better on the smaller tubes.
- (3) A polaroid screen over the face of a direct view tube further improves the picture contrast and tends to mask the noise spots.

The sensitivity of the receiver unit may be improved further by the installation of a preamplifier or booster. There are two important factors in selecting a booster amplifier.

- (1) The input impedance of the booster amplifier should match the transmission line over the complete television band, 54 to 216 megacycles.
- (2) The booster amplifier should have sufficient bandwidth on all channels so that they pass both video and audio signals.

In fringe-area installations only low-loss cable should be employed between the antenna and the television receiver. RG17/U, RG11/U, RG8/U are preferred for coax installations. Low-loss 300-ohm twin lead (there are seven grades of twin-lead) should be selected for receivers with balanced input. Where 300-ohm line must be run over a long distance (more than 200') a weather-proof low-loss 300-

Fig. 7. Combined array of low-channel (2 to 6) lazy H and beamed high-frequency attachment. The leads from the hf and upper lf elements are actually connected to the bridging plate, as shown in Fig. 8. For clarification purposes they were not connected in this illustration. (Courtesy Vertrod)

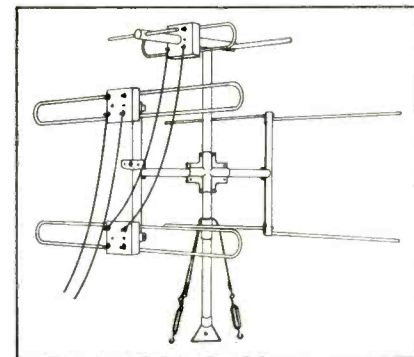

¹SERVICE; August 1948.

Jhm line,³ which has a loss of approximately 1 db at 100 mc, is recommended. All cable used should be specified as non-contaminatable by the manufacturers if aging is not to produce subsequent losses in the cables. No old war surplus cable should be used in fringe installations.

Keeping Fringe Installations Sold

To be certain that fringe-area installations stay sold, the television installer should know his terrain (from contour map) and be certain that his signal pick-up is fringe signal and not *summer refractions* caused by sun spots. Much money has been lost from installations where the signals vanish in winter. Installations in mountain areas are also subject to intermittent operation because of continuous lightning discharges in the

mountain regions during certain periods of the year.

The technique of pre-determining tower heights and installing long-wire television antennas in fringe areas will be the subject of a subsequent article in this series.

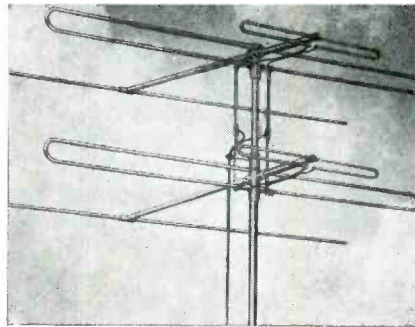


Fig. 9. Unidirectional 12-channel high-gain stacked array.

(Courtesy Amphenol)


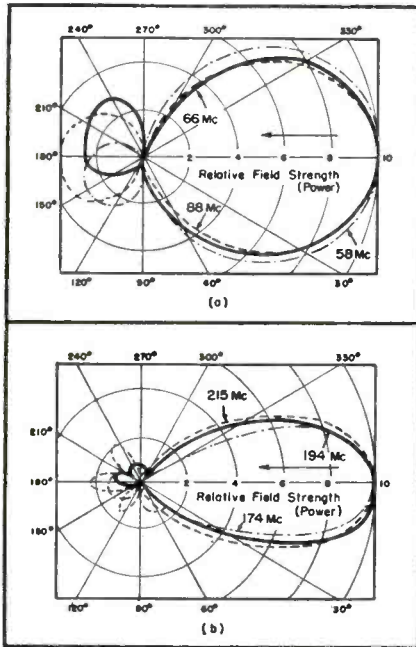


Fig. 10. Horizontal pattern of 12-channel unidirectional stacked array shown in Fig. 9.

Fig. 11. Super-stacked array.

(Courtesy VEE-D-X)

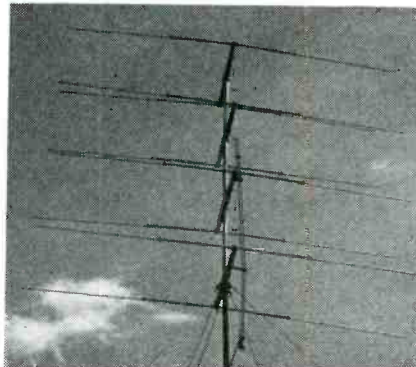

²VEE-D-X.

³Similar to VEE-D-X X200A.

free
1949
NEWARK
CATALOG

For EVERYONE interested in
TELEVISION • RADIO • ELECTRONICS
SOUND SYSTEMS • INDUSTRIAL EQUIPMENT
 EVERYTHING in standard brand equipment!

Professionals! Radio Hams! Television Enthusiasts! Beginners! Oldtimers! Amateurs! Hobbyists! Here's one book that's a **MUST** for you! Our **FREE 148 page catalog** jammed with over 20,000 different items. The smallest part to the most complete industrial system from one dependable source!

24-HR. MAIL ORDER SERVICE • ONE YEAR TO PAY

3 GREAT STORES: Uptown at 115 West 45th St. and Downtown at 212 Fulton St. in **NEW YORK** 323 W. Madison St. in the heart of **CHICAGO**

MAIL ORDER DIVISIONS: 242 W. 55th St., N. Y. 19 and 323 West Madison St., Chicago 6, Illinois

NEWARK MAIL COUPON NOW
 RADIO & TELEVISION Newark Electric Co.
 Dept. A-12-242 W. 55th St.
 New York 19, N. Y.

Please send me **FREE** the Newark 1949 Catalog
 NAME _____
 ADDRESS _____ CITY _____ STATE _____

Built for Service

The winning tube!
 in...



• West Virginia votes for Cunningham . . . the tube that gives long terms of service. That's because Cunningham tubes have been satisfying particular customers for over 32 years.

See your
CUNNINGHAM DISTRIBUTOR
HICKS RADIO SUPPLY
 Charleston

Cunningham Tubes
 A product of
RADIO CORPORATION OF AMERICA
 Harrison, N. J.



Average Signal?


Here's just the antenna for average TV installations. Gets all 12 channels. Mechanically and electrically, it's "right on the beam," for consistent TV and FM reception. Matching network automatically puts proper antenna to work. Independent orientation of two elements. So why risk your reputation? Use TACO for satisfied customers. • Type 465 (illustrated) complete with mast, mounting clamps, hardware, \$26.00 list.

Weak Signal?

Far from transmitters? Down in a hole? In one of those bad-television spots? Don't give up! Try TACO's Type 495 stacking kit. High-gain folded dipoles, stacked, provide terrific gain in signal strength. • Type 495 (not illustrated) complete with mast, mounting clamps and hardware, \$47.00 list.

• Ask Our Jobber . . .

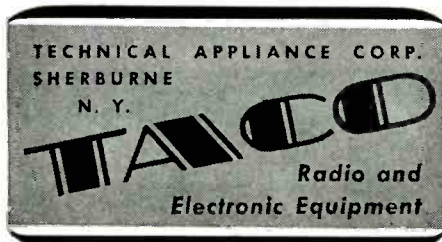Ask to see these TACO jobs. Get the one best suited to the given installation. Ask for latest catalog. Or write us.



In Canada: Stromberg-Carlson Co., Ltd.
Toronto 4, Ont.

LP System

(Continued from page 17)

arc approximately $\frac{1}{2}$ " beyond the center of the turntable spindle. The motorboard should be mounted carefully to isolate vibrations originating in the motor. After mounting, one hex nut is placed on the $\frac{1}{2}$ " long needle protective screw and the screw is inserted into the hole provided in the swivel. Then the bracket is assembled with the head of the screw toward the inside of the arm. Another hex nut is then placed on that portion of the screw showing through the bracket. Needle point should and can be adjusted to be about $\frac{1}{32}$ " above turntable surface; Fig. 6.

The pickup can be connected directly to a single grid-input-circuit amplifier. The center connector should be connected to the grid or *hot* lead, and the shield be connected to ground; Fig. 7.

Motor Assemblies

On many installations it will be necessary to install not only a new pickup but also a completely new motor assembly due to the $33\frac{1}{3}$ rpm speed of the *lp* records.

Two motor and single motor assemblies are available. One type⁷ has a 78- and a $33\frac{1}{3}$ -rpm motor. For $33\frac{1}{3}$ rpm a speed change lever extending on the outside of the turntable rim is shifted and this in turn moves a rubber-belt-driven step pulley against the idler wheel. At 78 rpm the speed change lever moves the step pulley away and the idler contacts the motor shaft directly.

Another model⁸ has a 4-pole motor with a two-diameter shaft. By raising and lowering the entire idler assembly according to the speed wanted the idler engages the small diameter of the shaft for $33\frac{1}{3}$ rpm and the larger diameter for 78 rpm.

In another model⁹ which provides both $33\frac{1}{3}$ - and 78-rpm speeds, two motors are mounted below a standard 10" or 12" turntable. A single lever control changes the turntable speed.

When the control lever is operated, the desired motor is electrically switched into the circuit. The lever disengages the idler tire from the turntable rim and the motor pulley through linkage which is completely apart from the idler system when the motor is in play position. Neutral position switches off both motors when not in service.

⁷General Industries DM.
⁸General Industries DR.
⁹Alliance Dual-Speed.


TV Sync

(Continued from page 22)

vertical sync pulses; top drawing Fig. 2. The horizontal synchronizes between frames on the even-numbered equalizing and vertical sync pulses. We also know that with the interlace scanning system at the end of a frame the beam is retraced from the bottom center of the scanning raster and therefore the time interval between the last horizontal pulse at the end of the frame and the first equalizing is 31.75 or one-half of the line interval. Therefore, if it were necessary to synchronize on the odd-numbered equalizing and vertical sync pulses, as before, the horizontal oscillator would naturally shift phase for an instant. It is necessary to insert equalizing and vertical sync pulses half-way between the odd-numbered pulses discussed previously. Consequently, the second equalizing pulse leading edge is one line interval away from the last horizontal sync pulse at the end of a frame and therefore during the retrace interval between frames, the horizontal is synchronized on the even-numbered equalizing and vertical sync pulses. Therefore the double-line rate equalizing and vertical sync pulses are necessary to maintain horizontal synchronism between fields and between frames.

[To Be Concluded in January]

Fig. 2. How horizontal and vertical sync appears between fields and frames.

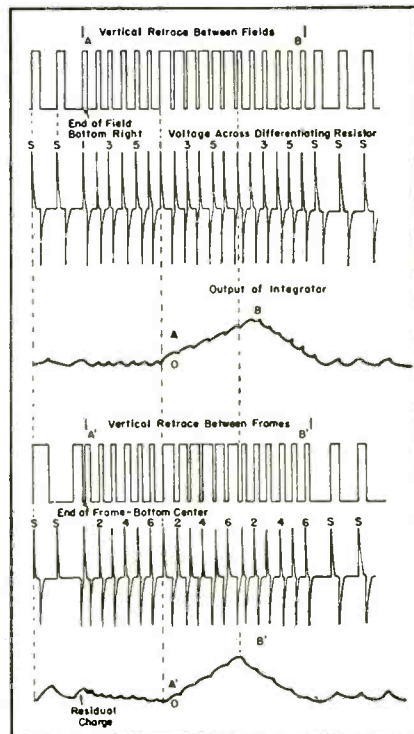

Here's BIG NEWS! INTERCOM AND RADIO COMBINATION



at a PRICE
That Can't Be Beat

6 tube superhet—3 tube intercom permits communication between radio-master and up to 4 sub-stations.
Original cost \$64.50

WHILE THEY LAST
\$29.95
With 1 sub-station and 50 feet of cable
Extra Sub-stations \$3.95 each



MIDGET I. F. TRANSFORMERS

Original List \$2.10

At discounts up to 86%

NOW 36c EACH

400-500 Kc range
1 1/4" square, 3" high
hi-gain iron core.

INPUT—A826
OUTPUT—A827

Matched Pair
69c

Specify Type


Dozen

\$3.95

Egg Crate of 100

\$29.00

1 meg. VOLUME CONTROLS

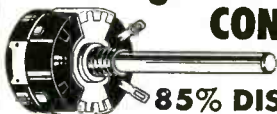

85% DISCOUNT

Universal with switch

Better Hurry
THESE WON'T LAST AT THIS PRICE 29c Each



Demand This Seal of Quality

ORDER INSTRUCTIONS

Minimum order—\$2.00. 25% deposit with order required for all C.O.D. shipments. Be sure to include sufficient postage—excess will be refunded. Orders received without postage will be shipped express collect. All prices F.O.B. Detroit.

RADIO SUPPLY & ENGINEERING CO., Inc.
86 SELDEN AVE. DETROIT 1, MICH.

Association News

(Continued from page 33)

Technicians Associations, Wayne Shaw, secretary, says that thirty-five representatives and delegates from Rochester, Ithaca, New York City, Poughkeepsie and Binghamton attended the meeting, which was held at the Hotel Arlington.

The Federation was created to further the welfare of the radio technician in New York State, to work toward raising his technical standards, and to promote among the public a better understanding of the problems of the radio Service Man.

The Federation expects to include all active radio service groups within the State, and has limited its membership to established associations which have regular local activity. Each member association is represented in the Federation by two delegates, one of whom serves on the board of directors.

ESFETA will give any required assistance to technicians or groups of technicians within the State, who are interested in forming their own local associations. The Federation will also assist in activating associations which are not now operating, and will maintain liaison with Federations in other States.

T. Lawrence Raymo, president RTG, Rochester, is prexy; Max Leibowitz, president ARSNY, New York City, vice president; Wayne Shaw, president, RSA, Binghamton, secretary; Ben De Young, president RTG, of Central New York, treasurer; and Evert M. Howland, president Hudson Valley RSA, sergeant-at-arms.

Term of office ends April, 1949.


The next meeting, which will cover constitutional questions and incorporation, will be held in about one month. Further details about the Federation may be obtained from W. Shaw, 392 Chenango St., Binghamton, N. Y.

ARTG

DELEGATES from nine RTG units in New York State and the New England States, who met recently at a meeting in Rochester, N. Y., voted to effect a national organization and approved a constitution for the organization which is to be known as the American Radio Technicians Guild, incorporated under the laws of the State of New York.

The delegates to the convention, acting under the authority of their local guilds, elected six directors to serve until the first annual meeting of ARTG, to be held in June, 1949.

Built for Service

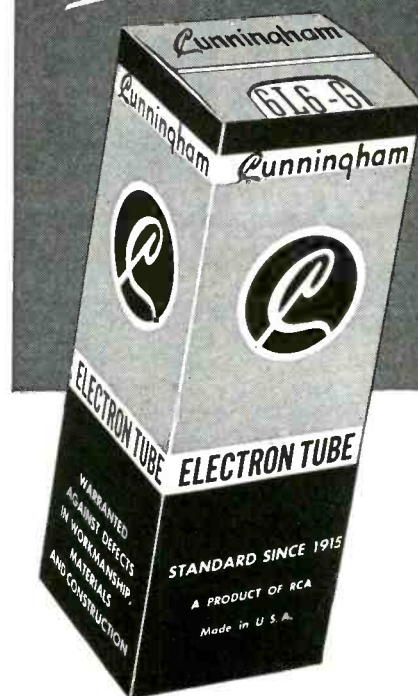

The winning tube!
in . . .



● Cunningham carries Wisconsin on a platform of quality and performance. That's why your customers are candidates for Cunningham tubes . . . why Cunninghams should be *your* choice.

See your
CUNNINGHAM DISTRIBUTOR

ELECTRO-PLIANCE DISTRIBUTORS
Milwaukee


STANDARD RADIO PARTS CO.
Racine

Cunningham Tubes

A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.

CHECK!

DISTORTIONLESS SOUND-SYSTEM CONTROLS!

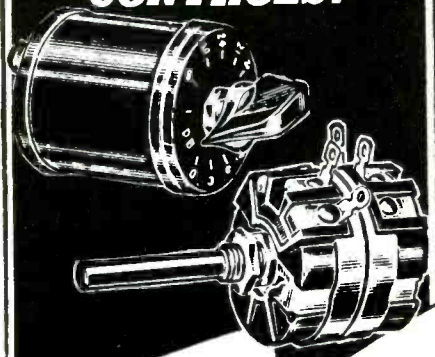

OUTPUT ATTENUATOR

Constant-impedance volume control handling up to 10 watts at any dial setting. Used as output level control for power amplifiers. Or as input attenuator for individual speakers in P-A systems.

L-PADS AND T-PADS

Constant-impedance attenuators. These self-compensating volume controls eliminate distortion arising from mismatching of impedances.

PLUS THE "KNOW-HOW"

Clarostat can tell you how to eliminate distortion in sound-system volume control. Clarostat has made the bulk of the L- and T-pads, attenuators and faders, now in general use!

CLAROSTAT



Ask your Clarostat jobber for latest catalog. Or write us.

Controls and Resistors

CLAROSTAT MFG. CO., Inc., Dover, N. H.

In Canada: CANADIAN MARCONI CO., Ltd
Montreal, P.Q., and branches



AUGUST-SEPT. HYTRON CONTEST WINNERS

First prize in the August Hytron Service Men's contest was awarded to Douglas T. Sweeny, 310 West Union Avenue, Bound Brook, New Jersey.

First prize in the September Hytron contest was won by Casimir F. Woods, 54 North 7th St., Newark, New Jersey.

The Sept. presentation was made at Variety Electric Company, 601 Broad Street, Newark, New Jersey, Woods receiving a Jackson 641 Universal signal generator.



Everett B. Boise, Hytron representative; D. T. Sweeny, Aug. prize winner, and Mrs. Fannie Bennett of Bennett's Radio Supplies, where the prize presentation was made.

Below: C. F. Woods, September prize winner; Stanley Dudek, Variety Electric Company, and Herbert H. Friedman, Hytron rep., who made presentation.



MUTER BUYS JENSEN

The Muter Company has acquired all of the common stock of the Jensen Manufacturing Company. No consolidation of operations is currently anticipated and no changes in management are contemplated. T. A. White, president of Jensen, Hugh S. Knowles, vice president and Ralph T. Sullivan, Jensen district sales manager, have acquired a substantial block of stock in The Muter Company.

NATIONAL UNION BUYS NEW VIDEO TUBE PLANT

National Union Radio Corp., Orange, N. J., has purchased a plant in Hatboro, Pa., for the production of all types of picture tubes up to and including 20" in diameter.

Based on an indicated production of 800,000 TV sets in 1948 and an estimate of more than two million sets next year, the company expects to turn out approximately 200,000 tubes in '49 and upwards of 500,000 tubes the following year.

TUNG-SOL TUBE MERCHANDISER

A tube merchandiser (TM-30) made of polystyrene has been developed by the Tung-Sol Lamp Works Inc., Electron Tube Division, 95 Eighth Ave., Newark 4, N. J.

Each merchandiser has room for six stacks of tubes, five tubes in each stack. As tubes are withdrawn through the opening at the bottom of each stack, the others automatically fall in position. The merchandiser is easily refilled through openings in the face of the cabinet at the top. Two or more may be stacked and locked in vertical position by means of self-locking washers. The merchandiser is sold already packed with an assortment of 30 tubes.




* * *

PRECISION APPARATUS COMBINATION TESTER

A combination cathode conductance tube tester, dynamic (under-load) battery tester and high sensitivity ac and dc circuit tester (20,000 ohms-per-volt D.C.), (series 654) has been developed by Precision Apparatus Co., Inc., 92-27 Horace Harding Blvd., Elmhurst, L. I., N. Y.

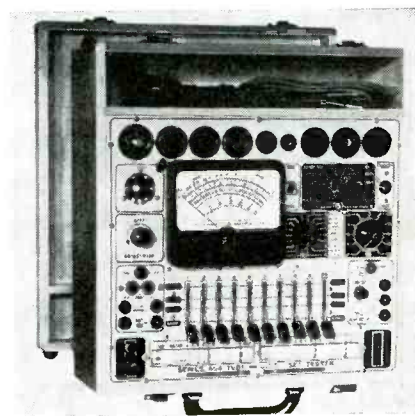Features include filament voltages from 3/4 to 117 v., free-point 10 element lever selection, individual tests of multi-section tubes, built-in roll chart, and fuse extractor post.



* * *

UTAH INTERCOMM SPEAKERS

Intercomm speakers, in the four-inch SP4A1 and the five-inch SP5A1, have been announced by the Utah Radio Products Division of International Detrola, 1123 East Franklin Street, Huntington, Indiana.

Both sizes are built with 44-ohm voice coils and a .68 oz Alnico V magnet.

New TV Parts . . . Accessories

STANCOR TELEMATCH


Telematch, which is said to correct mismatch between TV antenna and receiver has been announced by Standard Transformer Corp., 3580 Elston Ave., Chicago 18, Ill. Unit may be mounted behind receiver or used on top of cabinet. Literature and display material are supplied with shipments or will be mailed upon request.



* * *

JFD WINDOW TV ANTENNA

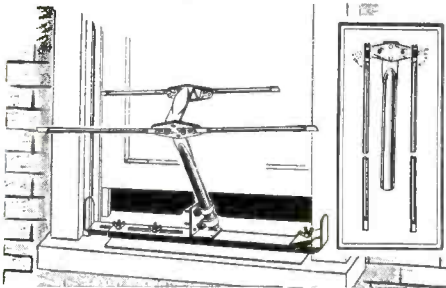A *Quick-Rig* TV window Antenna has been announced by the JFD Manufacturing Co., Inc., 4117 Ft. Hamilton Parkway, Brooklyn 19, N. Y.




* * *

BRACH TV/FM ANTENNA LINE

A line of FM and TV antenna kits (*Flexi-Kits*) has been announced by the L. S. Brach Mfg. Corp., Newark 4, N. J. Feature of the kits is their universal construction.

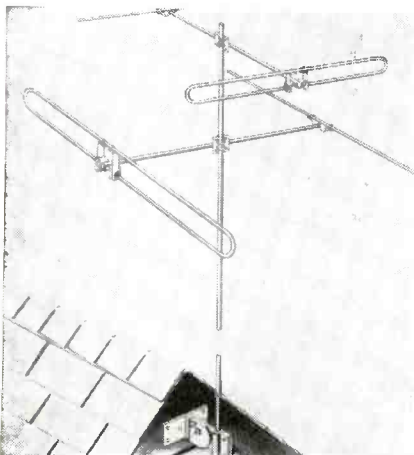Complete individual antenna kits include a *Hi-Lo rotatable TV Antenna*. Complete data appears in catalog 1304.




ALLIANCE TV AND FM ANTENNA ROTATOR

An electric antenna rotator (*Tenna-Rotor*) designed to rotate FM and TV antennas has been announced by the Alliance Manufacturing Company, Alliance, Ohio. The rotator unit is connected to a plastic control box, located adjacent to the receiver. A three-position switch starts rotating the antenna clockwise or counter-clockwise, through 360°. When the switch is turned to the center or neutral position, rotation is stopped. When the limit of travel is reached in either direction, a small screen on the control panel is illuminated.


The rotator mechanism is an electrically driven rotating hollow shaft into which the antenna center post is clamped. The gear train driving this shaft is motivated by an intermittent duty, reversible, capacitor type motor. Gear reduction is so designed that the antenna rotates at approximately 1 rpm. Both the stop and reversing arrangements are said to be practically instantaneous. The control box plugs into a regular 110-volt 60-cycle house line and is connected by a four-conductor cable to the rotator.

The motor in the rotator unit operates on 24 volts at 60 cycles supplied through a step down transformer in the control box. Components in the rotator are cadmium plated and the rotor is moisture sealed.

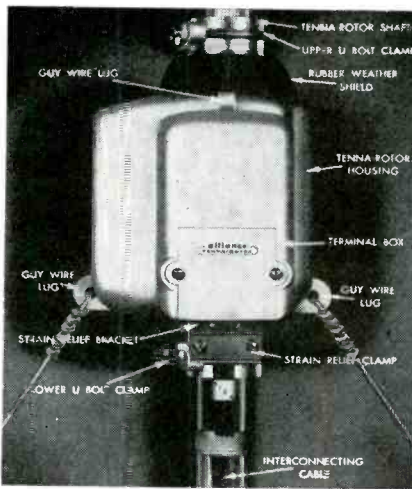Rotator and control box weighs approximately 12 pounds. Overall dimensions of the rotator unit are 7 3/4" x 5 1/4" x 8"; control box measures 5" x 5" x 4".



Below: Motor circuit of Tenna-Rotor.

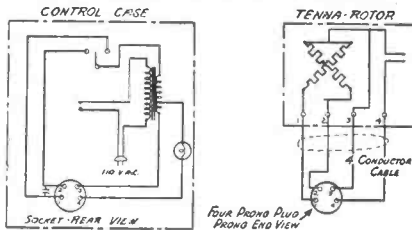

* * *

JERROLD BOOSTER

An FM-TV signal booster which is said to offer a gain of 20 to 30, has been announced by Jerrold Electronics Corporation, 121 N. Broad Street, Philadelphia 7, Penna.



The winning tube!
in . . .



• Cunningham tubes have carried Wyoming because of their long-standing record of reliability. The quality of Cunningham tubes accounts for their long life and top performance. That's why—when you use Cunninghams—you're bound to have satisfied customers.

See your
CUNNINGHAM DISTRIBUTOR
CASPER SUPPLY CO.
Casper



JOTS AND FLASHES

THE NEED OF TRAINED TV Service Men to service the increasing number of television receivers was the keynote of an address by Max F. Balcom, RMA prexy and vice president and treasurer of Sylvania, before the third Town Meeting of Technicians held in Boston, recently. Balcom stated that TV set production this year will probably exceed 750,000 and next year would top 1,500,000. He also cited the increasing field for Service Men's activities in FM, privately-owned communications systems, mobile setups, citizen's radio service, etc. . . . James F. Skinner, Philco vice president in charge of the service and parts division, stated recently that 43 of its distributors in TV cities have provided training courses in TV installation, maintenance and repair to more than 5,000 Service Men. . . . William S. Hedges, NBC vice president, predicted recently that TV "may well prove to be a two-billion-dollar-a-year industry," based on an annual set production of 4,000,000 at an average retail price of \$350, for a total of \$1,400,000,000, plus \$600,000,000 for the sale of time and talent. Hedges also foresaw TV within five years in at least 150 markets of the nation, with a total of 500 stations serving an audience of sixteen million TV families. . . . The first issue of the *REPre-sentor* was published recently by the Industry Relations Committee of the Representatives. It is edited by Jane Drucker and devoted to news of the forthcoming Parts Show, import and export licensing, foreign markets, FCC news, Fall business reports, new developments, etc. . . . The fifth volume of the *Photofact Folders* with sets 49 and 50 was recently published by Howard Sams and Company, Inc. . . . A volunteer firemen's home receiver operating on 152-162 mc has been developed by Motorola, Inc. . . . Technical Advertising Associates, Cheltenham, Pa., have published a *Radio Components Handbook* by A. C. Matthews and Staff, covering a variety of very handy design and application information. Book sells for \$2.50. . . . Bob Gunderson is now writing a technical column for the Newark Electric Co., 242 West 55th Street, New York City. . . . Samuel J. Spector, president of the Insuline Corporation of America, Long Island City 1, N. Y., has just returned from a trip to the middle west and west coast, surveying the TV parts markets. . . . The RCA Victor Company of Montreal is now the sole Canadian distributor for Camburn products, which includes AM and TV antennas. . . . Sales reps of the Simpson Electric Company, Chicago, recently attended a series of sales conference sessions at the home of Ray Simpson, prexy, at Lac Du Flambeau in the Wisconsin north woods. . . . The Herlec Corporation of Milwaukee, Wis., manufacturers of ceramic capacitors and *Bulbplate* printed circuits, has been acquired by the Sprague Electric Company, North Adams, Mass. Milwaukee operations will be under the continued direction of Herlec execs including Milton Ehlers, president; Harry Rubenstein, vice president and chief engineer, and Thomas Hunter, vice president in charge of sales. . . . Leonard C. Taggart is now director of purchasing for Sylvania Electric. . . . Frank E. Smolek, service manager of Zenith, recently completed directing a forty-hour TV course for Zenith's thirty distributors. . . . William H. Resch has joined the staff of Technical Appliance Corp., Sherburne, N. Y., as assistant treasurer.

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—DECEMBER, 1948

ALLIANCE MFG. CO.	37
Agency: Foster & Davies, Inc.	
AMERICAN ELECTRICAL HEATER CO.	48
Agency: Dudgeon, Taylor & Bruke, Inc.	
AMERICAN TELEVISION & RADIO CO.	29
Agency: Firestone-Goodman Adv. Agency	
AMPERITE CO., INC.	38
Agency: H. J. Gold Co.	
L. S. BRACH MFG. CORP.	31
Agency: A. W. Lewin Co.	
CHICAGO TRANSFORMER DIV., ESSEX WIRE CORP.	7
Agency: Burton Browne, Advertising	
CLAROSTAT MFG. CO., INC.	46
Agency: Austin C. Lescarboursa & Staff	
CORNELL-DUBILIER ELECTRIC CORP.	Inside Front Cover
Agency: Reiss Advertising	
ELECTRO-VOICE, INC.	35
Agency: Henry H. Tepnitz, Advertising	
FEDERAL TELEPHONE & RADIO CORP.	5
Agency: J. M. Mathes, Inc.	
GENERAL ELECTRIC CO.	25
Agency: Maxon, Inc.	
GREYLOCK ELECTRONIC SUPPLY CO.	38
Agency: Bergman-Jarrett Co.	
THE HEATH COMPANY.	6
Agency: G. Dean Arend, Advertising	
HICKOK ELECTRICAL INSTRUMENT CO.	38
Agency: White Adv. Co.	
HYTRON RADIO & ELECTRONICS CORP.	8
Agency: Henry A. Loudon-Advertising	
INTERNATIONAL RESISTANCE CO.	40
Agency: John Falkner Arndt & Co., Inc.	
J. F. D. MFG. CO., INC.	42
Agency: Bergman-Jarrett Co.	
KAY ELECTRIC CO.	38
Agency: George G. Felt	
KEN-RAD DIV. GENERAL ELECTRIC CO.	1
Agency: Maxon, Inc.	
LA POINTE PLASCOMOLD CORP.	41
Agency: F. W. Prella Co.	
P. R. MALLORY & CO., INC.	Inside Back Cover
Agency: The Atkin-Kynett Co.	
MURRAY HILL BOOKS, INC.	36
Agency: The Harry P. Bridge Co.	
NEWARK ELECTRIC CO., INC.	43
Agency: The Chernow Co., Inc.	
RADIART CORP.	21, 27
Agency: Ohio Adv. Agency	
RADIO CORPORATION OF AMERICA	41, 43, 45, 47, Back Cover
Agency: J. Walter Thompson Co.	
RADIO MERCHANDISE SALES, INC.	40
Agency: Bergman-Jarrett Co.	
RADIO SUPPLY & ENGINEERING CO.	45
Agency: Claude E. Whipple	
JOHN F. RIDER PUBLISHER, INC.	23
Agency: Shappe-Wilkes Inc.	
HOWARD W. SAMS & CO., INC.	3
Agency: George Brodsky, Advertising	
SPRAGUE PRODUCTS CO.	4
Agency: The Harry P. Bridge Co.	
TECHNICAL APPLIANCE CORP.	44
Agency: Austin C. Lescarboursa & Staff	
TRANSMISSION, INC.	55
Agency: H. J. Gold Co.	
UTAH RADIO PRODUCTS DIV. INT'L DETROLA	39
Agency: Bonsib Adv. Agency	


ELECTRIC SOLDERING IRONS

that are sturdily built for the hard service of industrial usage. Have plug type tips and are constructed on the unit system, with each vital part, such as heating element, easily removable and replaceable. In 5 sizes, and from 50 watts to 550 watts.

American Beauty

TEMPERATURE REGULATING STAND

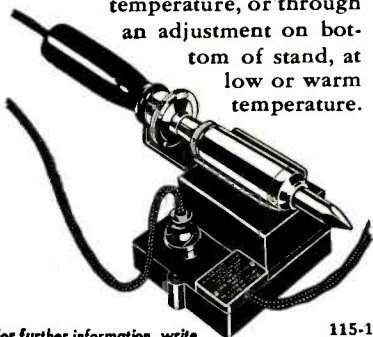
This is a thermostatically controlled device for the regulation of the temperature of an electric soldering iron. When placed on and connected to this stand, iron may be maintained at working temperature, or through an adjustment on bottom of stand, at low or warm temperature.



For further information, write


115-1

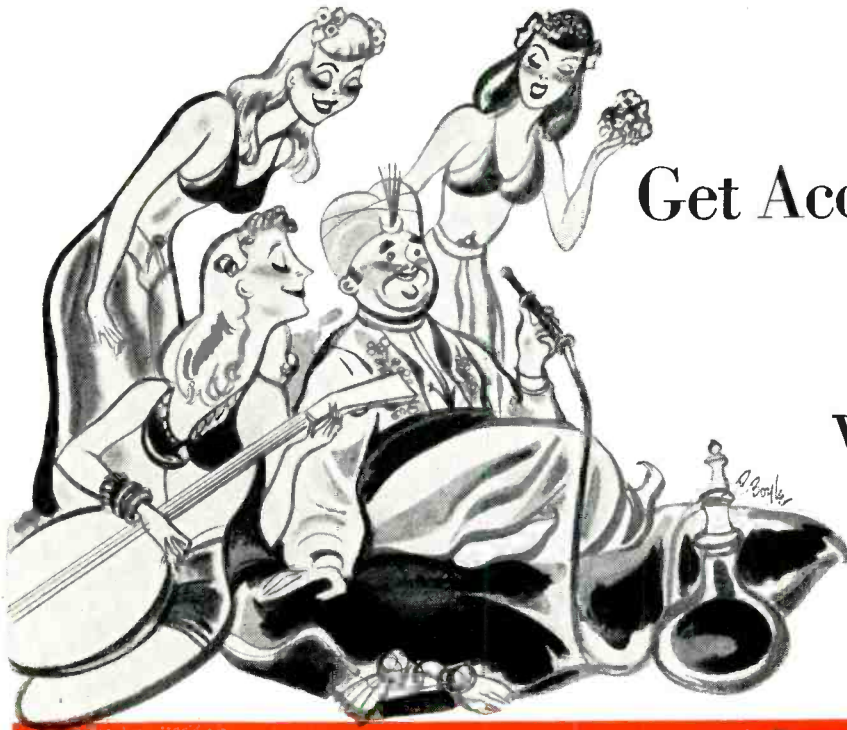AMERICAN ELECTRICAL
HEATER COMPANY
DETROIT 2, MICHIGAN
established 1894



Get Acquainted with the Little Fellow with the **BIG** Advantages

The All New Mallory Midgetrol

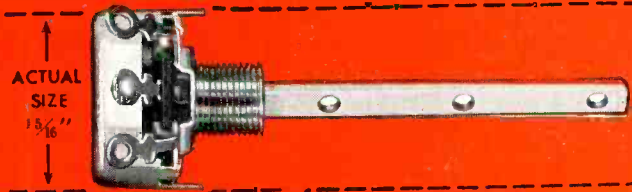

Offers These **BIG** Advantages...

BIGGER MARKET

The small size of the Mallory Midgetrol lets you service portables, auto radios and small AC-DC receivers which require $1\frac{5}{16}$ " controls.

SIMPLER INSTALLATION

The unique shaft design of the Mallory Midgetrol saves installation time with *all* types of knobs.

SIMPLER STOCKING

Electrical characteristics let you use the Mallory Midgetrol to replace $1\frac{1}{8}$ " as well as $1\frac{5}{16}$ " controls. Stocks are further reduced because no special shafts are needed.

Both mechanically and electrically, the Mallory Midgetrol is amazingly quiet. Tests prove it *stays* quiet! And the Mallory Midgetrol offers nine *all new* features.

It's the NEW Standard in Carbon Controls. See your Mallory distributor.

- NEW SIZE
- NEW DESIGN
- NEW SHAFT
- NEW EXTENSION
- NEW SWITCH
- NEW ELEMENT
- NEW CONTACT
- NEW TERMINAL
- NEW TWO-POINT SUSPENSION

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS... CONTROLS... VIBRATORS...
SWITCHES... RESISTORS... RECTIFIERS...
VIBRAPACK® POWER SUPPLIES... FILTERS
*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

OVERWHELMING ACCEPTANCE!



- Month after month, RCA Batteries continue to smash all previous sales records.

The reasons for this unprecedented acceptance are conclusive—

RCA Batteries are designed for *radiomen* . . . to sell through *radio* outlets. And they're backed by the greatest name in radio—RCA.

RCA Batteries are your assurance of immediate customer acceptance and greater profits.

SELL RCA BATTERIES—THE COMPLETE LINE FOR THE RADIO AND ELECTRONIC TRADE



TUBE DEPARTMENT

RADIO CORPORATION of AMERICA

HARRISON, N. J.