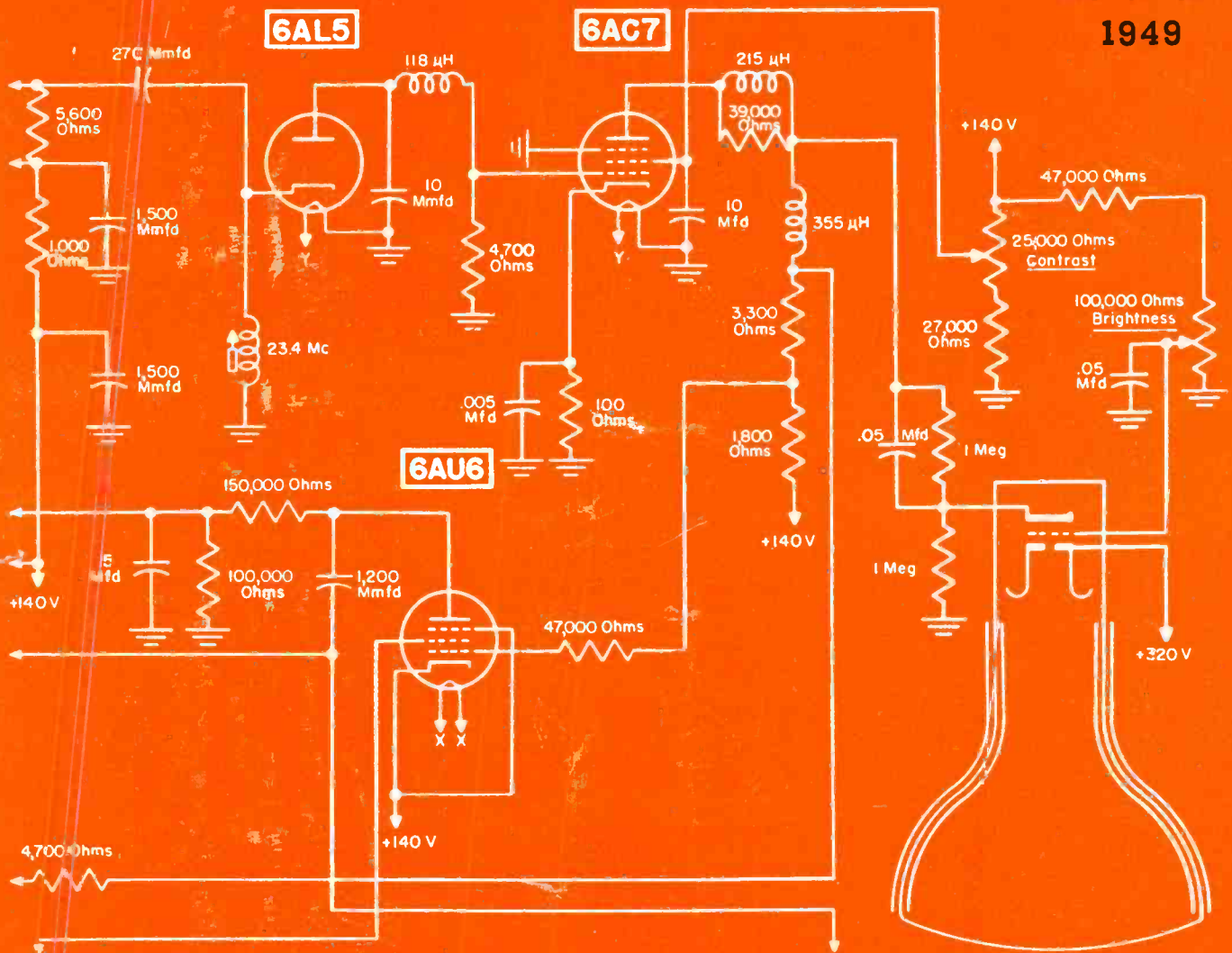


SERVICE

November
1949



Keyed agc circuit developed for the 630 TV chassis.
[See page 2]

Cub Sized...



STURDY AS A GRIZZLY



CORNEILL-DUBILIER "BLUE CUB"*

FIVE EXCLUSIVE "LIFE-PRESERVING" FEATURES:

LEADWELD terminals:

The only tubular with leads welded to section. Welding eliminates possibility of opens and intermittents.



STYRICAST molded:

The only tubular cast in plastic after Vikane impregnation. No heat or pressure to injure unit. Rockhard coating for permanent eye-appeal and durability.



FIXEDRESIN case:

Will withstand temperatures up to 300°F without softening.



VIKANE* impregnation:

Results in superior capacitor section that will withstand higher break-down test and have the lowest power-factor of any tubular.



GRIPSEAL impregnated:

Additional impregnation after final assembly as a permanent double humidity seal.



the new plastic paper tubulars

One sure thing about these C-D "BLUE CUBS"—you can install them and forget about them. No shock, no vibration is too much for these pint-sized "giants"; they're fortified with solid mold construction and "cushioning" features. They take temperatures from -70°F to $+212^{\circ}\text{F}$ in their stride. Capacity remains constant within 5% under most severe conditions of temperature and humidity. Get acquainted with these job-insuring "BLUE CUBS" now.

Your jobber has a supply in all popular capacity ranges at 400, 600 and 1,600 V.D.C.

CORNEILL-DUBILIER
 world's leading manufacturer of
CAPACITORS
 AUTO VIBRATORS • TV and FM ANTENNAS
 POWER CONVERTERS



1910 1949


* T. M. Reg. U. S. Pat. Off.

For further details on this and other units in C-D's complete line of quality capacitors see your jobber or write for catalog. Cornell-Dubilier Electric Corp., Dept. S119, South Plainfield, N. J. Other plants in New Bedford, Worcester and Brookline, Mass.; Indianapolis, Ind.; Providence, R. I. and subsidiary, The Radiart Corp., Cleveland, Ohio.

See yellow pages of your Classified Telephone Directory for nearest C-D authorized distributor.

In Radio and Television Tube Sales

1949 IS A G-E YEAR!

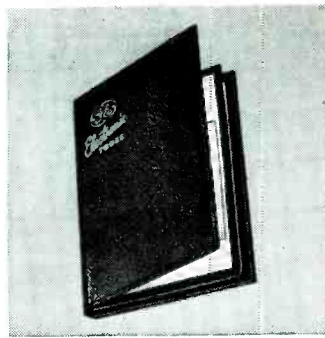


The G-E Pocket Office turns your job-time into more dollars by making cards, forms, and records available in convenient form.



TECHNI-TALK—G. E.'s down-to-earth service magazine edited by practical men for practical men—assists you in building repair business.



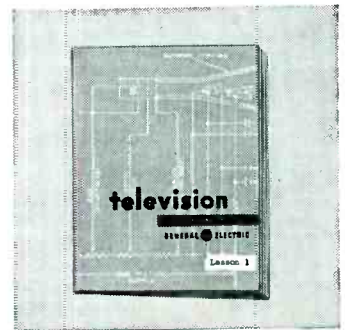G. E.'s new shop garments—smart, serviceable—are a big hit with tube dealers and repairmen everywhere.



The General Electric TV-service course helps you profit from television's great new market for tubes, parts, and service.

and now... THE HANDY G-E TUBE PULLER!




Latest of a series of helps that speed your work, increase your sales, and upgrade your profits, the new G-E tube puller cuts time on the job materially. Now you'll find it quick and easy to remove tubes without the risk of

burns, shock, or cuts from fractured glass.

Regular glass types, metal tubes, 7- and 9-pin miniatures—all yield to this universal device, which smoothly extracts tubes no matter how firmly wedged in their sockets. The puller is made of heavy rubber—your fingers are fully protected and insulated. It's simple to use; long-lived.

Ask your G-E tube distributor about this ingenious tube puller—how to obtain one . . . fast! Inquire, if you haven't before, about the other aids to sales mentioned on this page; also, about the folder describing the many G-E advertising helps that are ready to go to work for you. Stock the tubes that are easy to sell because you get more practical help in selling them . . . G-E tubes! *Electronics Department, General Electric Company, Schenectady 5, N. Y.*

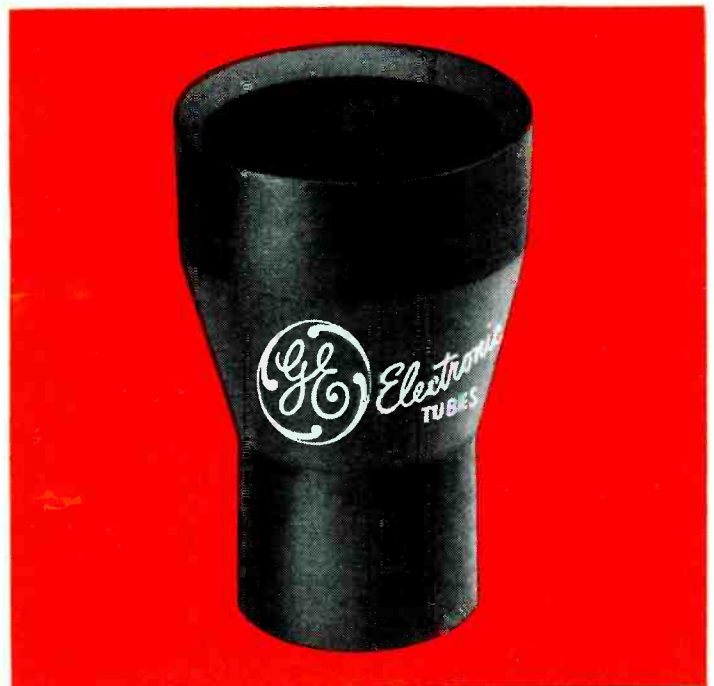

You can put your confidence in—

GENERAL  ELECTRIC

181-HA7

SERVICE, NOVEMBER, 1949 • 1

RADIO · TELEVISION · ELECTRONIC
SERVICE

LEWIS WINNER
Editorial Director

F. WALEN
Assistant Editor

ALFRED A. GHIRARDI
Advisory Editor

| | Page |
|--|------|
| Association News | 34 |
| Design, Application and Servicing of Selenium Rectifiers. By Irwin Wolf | 10 |
| Performance Diagnosis of Vacuum-Tube Circuits. By Edward M. Noll | 16 |
| Phono Installation and Service (Magnetic Tape Systems). By Kenneth Stewart | 18 |
| Ser-Cuits (Admiral AM/FM/TV Model) | 20 |
| Servicing Helps. By M. A. Marwell | 24 |
| Ten Years Ago in Associations | 34 |
| TV Model with Keyed AGC (Cover). By Walter H. Buchsbaum | 14 |
| TV Receiver Production Changes. By Donald Phillips | 22 |
| Views and News. By Lewis Winner | 9 |

CIRCUITS

| | |
|--|----|
| Admiral 21A1 TV and 4K1 FM and AM Tuner | 21 |
| Philco 48-1000 Width Control | 24 |
| Philco 48-700 Width Control | 24 |
| Philco 49-1040 Width Control | 24 |
| Selenium Rectifier Half-Wave Circuits | 11 |
| Selenium Cell Doubler Circuits | 11 |
| Selenium Reverse Testing Circuits | 12 |
| Selenium Forward Voltage Drop Test Circuit | 12 |
| Tech-Master BC-1223 (Cover) | 14 |

COVER

| | |
|---|----|
| TV Model with Keyed AGC (Tech-Master BC-1223) | 14 |
|---|----|

SERVICING HELPS

| | |
|--|----|
| Black Line-White Line Problems | 30 |
| Eliminating Sync Troubles in Philco Models | 29 |
| Philco TV Width-Control Circuits | 24 |
| TV Tuning Drift Cures | 30 |

TV RECEIVER PRODUCTION CHANGES

| | |
|--|----|
| New G. E. Horizontal Sweep Generator and AFC Circuit | 22 |
|--|----|

Index to Advertisers

| | |
|-------|----|
| | 48 |
|-------|----|

Manufacturers

| | |
|-------------------------------------|----|
| Jots and Flashes | 48 |
| News | 43 |
| New Parts . . . Accessories | 39 |
| TV Antennas . . . Accessories | 35 |

Entire contents Copyright 1949, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



Bryan S. Davis, President Paul S. Weil, Vice-Pres., Gen. Mgr. F. Walen, Secretary A. Goebel, Circulation Manager

East-Central Representative: James C. Munn, 2253 Delaware Dr., Cleveland 6, Ohio. Telephone: Erievlew 1726

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: Michigan 1732
Suite 1204, Russ Building, San Francisco 4, Calif. Telephone: SUTter 1-2251

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

Put This Proved Money-Making Service Data Library to Work ... in your shop *NOW!*

NOW YOU CAN OWN

PHOTOFACT

**this Amazing
EASY-PAY WAY!**

**Pay as you Profit
Earn with it Now**



100% Service Coverage!
AM, FM, TV Receivers,
Record Changers, Tuners,
Amplifiers, Ham Radios

**Everything
You Need to Know
for Profitable
Servicing**

**NO CARRYING
CHARGES
NO INTEREST**

**ONLY
\$18.³⁹
DOWN**

*Gets You
Started!*

Includes your membership in the Howard W. Sams Institute.
Entitles you to valuable service help at no cost to you.

NOW—you can afford to own the Service Data Library that is earning extra profits every day for more than 25,000 successful Service Technicians! NOW—for the first time—the famous PHOTOFACT Library can be yours with this new “Pay-as-You-Profit!” Plan! Here’s all you have to do: See your parts jobber. Order 4 or more PHOTOFACT Volumes. Pay only \$18.39 down. You get your Library immediately. You use it now. It earns for you—and you pay as you profit! If you’re not already a money-making PHOTOFACT user, here’s your easy-pay chance to own the most productive radio service data in the world. If you’re already using PHOTOFACT, here’s your chance to complete your library by filling in those missing volumes. Now that you can afford PHOTOFACT, don’t be without its time-saving, money-making advantages a single day longer. See your parts jobber today!

HAVE COMPLETE, ACCURATE DATA ON ALL POST-WAR SETS YOU SERVICE!

With the Easy-Pay Plan, you can boost your earnings now, using proved superior PHOTOFACT. Have complete, accurate, uniform data on all post-war receivers—own the only Radio and TV service data based on actual laboratory analysis of the equipment. Here’s why PHOTOFACT is better in every way. You get: 1. Exclusive TV coverage in easy-to-use individual envelopes. 2. Exclusive Standard Notation Schematics. 3. Exclusive oscilloscope wave forms. 4. Photos of all chassis views with each part identified. 5. Full alignment instructions, plus circuit voltage and resistance analysis. 6. Complete parts lists and proper replacements. 7. Dial cord stringing diagrams. 8. Disassembly instructions. 9. Record Changer service data. 10. Exclusive keyed data system—all values right on the schematic. There’s nothing like PHOTOFACT! It pays for itself in saved time, bigger work output and greater profits. To protect your future in Radio-TV servicing, act now—own the PHOTOFACT Library the Easy-Pay Way!



CURRENT PHOTOFACT BEST-SELLERS

The Recording and Reproduction of **SOUND**, by Oliver Read. The complete, authoritative treatment of the entire subject of Sound, written by the editor of *Radio & Television News*... **\$5.00**

Photofact Television Course. The book used by thousands; gives you a clear understanding of TV principles, operation and practice. **\$3.00**

Television Antennas. Shows you how to select and install the proper antenna, and how to overcome antenna problems. **\$1.25**

1948 Record Changer Manual. Covers 45 models made in 1948, including new LP and dual-speed changers, plus leading wire recorders. Based on actual analysis of the equipment. **\$6.75**

Auto Radio Manual. Complete Photofact service data on more than 100 post-war auto radio models—a time-and-money-saver. **\$4.95**

**SEE YOUR PARTS JOBBER
OR WRITE DIRECT TODAY**

**Get the
EASY-PAY
Details**

HOWARD W. SAMS & CO., INC.
955 N. Rural St., Indianapolis 1, Ind.

- Send full Easy-Pay Details
- Send FREE PHOTOFACT Cumulative Index
- Send PHOTOFACT Folder for Set Model
(FREE to Service Technicians writing in on letter-head; 50c charge to Experimenters)


Name.....

Address.....

City..... Zone..... State.....

HOWARD W. SAMS & CO., INC. INDIANAPOLIS 1, IND.

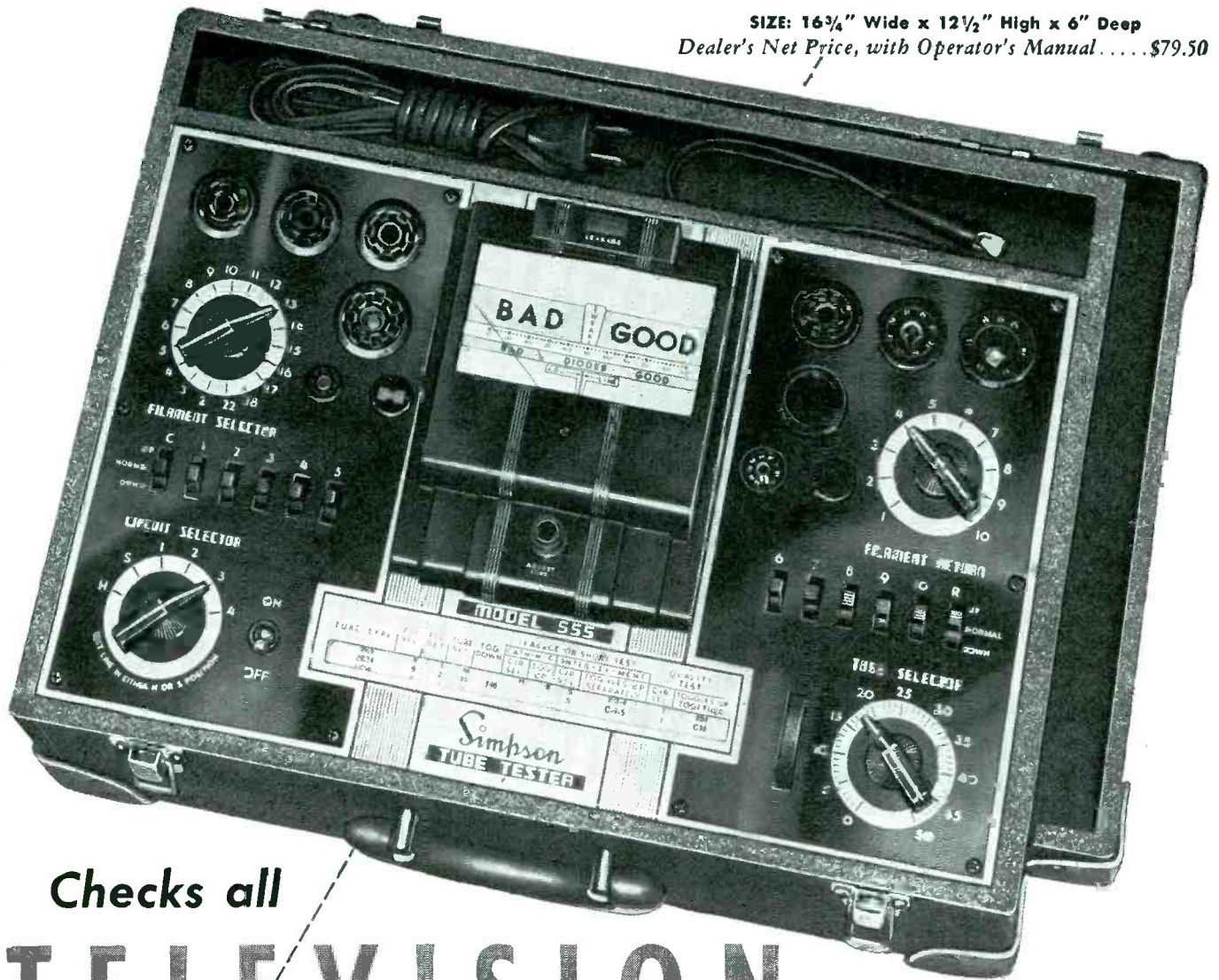SIZE: 16 3/4" Wide x 12 1/2" High x 6" Deep
 Dealer's Net Price, with Operator's Manual \$79.50



Checks all
TELEVISION and Radio types

SIMPSON 555 Tube Tester

- Basic RMA recommended circuit. Tests any tube regardless of base connections or internal connections of elements.
- Simpson designed 3-position lever operated toggle switches with molded rotor carrying silver plated contacts, self-cleaning through wiping action.
- Sockets for all receiving tubes on the market.
- Provision for future tube developments.
- No adapters or special sockets required.
- Properly fused, provides for line adjustment from 100 to 130 volts; smooth vernier control.
- Beautiful modern panel of shining, silver and black anodized enduring aluminum.
- Large illuminated meter for easy readings.
- Unique jewel-like molded lucite housing encloses Neon bulb indicating shorts and inter-element leakages.
- Line adjustment control below dial opening. Easy to operate.
- Case of sturdy plywood with heavy fabricoid covering, slip hinges.
- Simpson patented "No-Backlash" Roll Chart.



Simpson
 INSTRUMENTS THAT STAY ACCURATE

See the 555 at your parts jobber or write for descriptive literature.

SIMPSON ELECTRIC COMPANY 5200-18 W. Kinzie Street, Chicago 44, Illinois In Canada: Bach-Simpson Ltd., London, Ontario


Concentric Dual Worries Out the Window!

Amazing New IRC

Concentrikit

Replaces 90% of All

Concentric Dual Controls

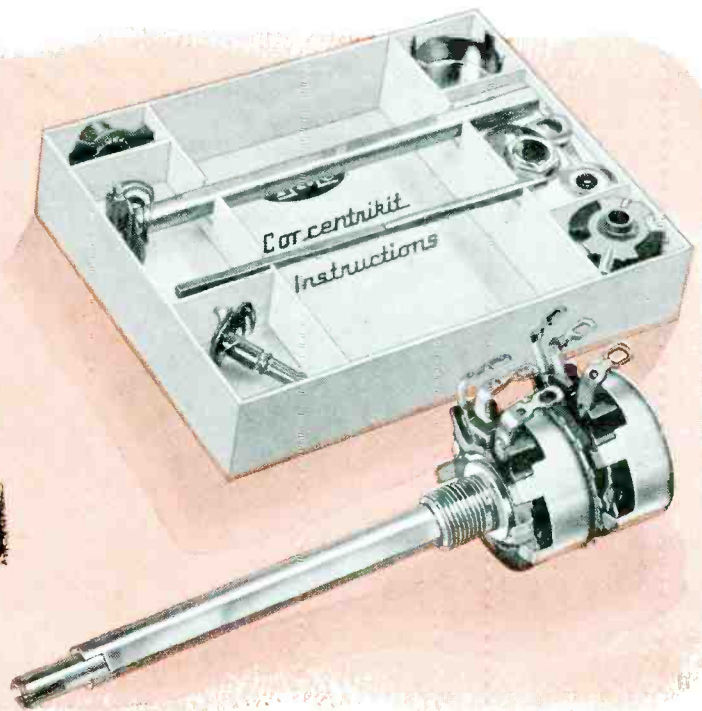

With Original IRC Base-Element Assemblies

Here is the for-sure answer to your concentric dual problems. The new IRC CONCENTRIKIT is a set of specially designed parts with which you can assemble a great variety of concentric dual controls. With CONCENTRIKIT on the job you entirely eliminate long searches and waits for exact duplicates. Instead, you quickly and easily assemble the exact concentric dual replacement you need... saving time and inventory investment.

USED WITH NEW IRC BASE-ELEMENT

Each CONCENTRIKIT contains 11 IRC universal parts. These combined with a wide selection of Shaft Ends and Base-Elements—purchased separately—afford a full range of concentric duals. Thus you save by buying only what you need. IRC Base-Elements are a revolutionary advance in concentric dual replacement. Each unit is a complete blue molded base with element, terminals and collector ring installed—no loose parts.


NEW IRC CONCENTRIC DUAL REPLACEMENT MANUAL

With CONCENTRIKIT you'll build concentric duals quickly and easily. Step-by-step instructions are included with each kit. New comprehensive Concentric Dual Manual gives you full replacement data on concentrics for every-

thing from earliest home and auto radio to TV. Available shortly from your IRC Distributor.

YOU MUST SEE CONCENTRIKIT

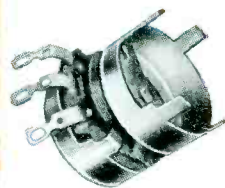See CONCENTRIKIT *now*, at your IRC Distributor! Take advantage of the most sensational control development that ever hit the industry. It's a money-maker!



FOR STANDARD DUALS— IRC'S NEW *Multisections*

Duals, triples, even quadruples—assembly of ganged controls is easy now with IRC's new MULTISECTIONS. These are complete control sections that can be added like a switch to any IRC type Q, PQ or RQ control. A full range of 17 MULTISECTIONS gives you a selection of values from 1000 ohms to 10 megohms. All IRC MULTISECTIONS accommodate Type 76 Switches.

See both CONCENTRIKIT and MULTISECTIONS at your IRC Distributor, or write for new Catalog DC-1A. International Resistance Company, 401 N. Broad St., Philadelphia 8, Pa. In Canada: International Resistance Co., Ltd., Toronto, Licensee.



INTERNATIONAL RESISTANCE CO.

Wherever the Circuit Says

"TV+FM+AM... We're making sure that we get all of this business..."


"We don't propose to let even one customer walk out of our place. If it's a TV, AM or FM set that needs servicing, we're making sure that we can handle the job satisfactorily. And one way of making sure is by constantly using our reference library of Rider Manuals."

—Says Mr. I. Zwickel
Signal Radio Hospital
Brooklyn, New York



For Greater Efficiency... For More Information... For More Value For Your Money
Place Your Order Now for the **NEW RIDER TV MANUAL vol. 3**
Larger Page Size! 12" x 15"! All Pages in Place! Easier to Use!

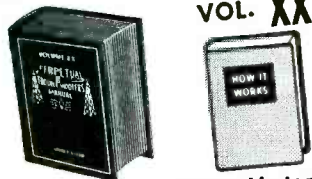Order Now From Your Jobber
New RIDER MANUAL
VOL. XX



New Material! More Material!
New Profit-Possibilities!

Reliable, authentic, factory-authorized servicing information covering the latest AM, FM radio, Auto Receivers, Record Changers, etc. . . . Complete in every respect, but with the added advantage of text and double spreads assembled in position.

FREE! Eye-Stoppers For Service Shop Windows

A very clever Rider Display Idea, 14 x 17 inches, captioned "Which One Is The Phony?". It shows two greatly enlarged photos of postage stamps, one genuine, one a known counterfeit, with identifying characteristics and means of recognizing the forgery. This Display is a real traffic-stopper, the forgery. This Display is a real traffic-stopper, and will help build more business for you. 2 Displays are issued each month, and you can get them FREE of CHARGE from your Jobber.

NOTE: Are you receiving your copy of "Successful Servicing"? It's Rider's own publication of interest to every Serviceman. Write for it... it's FREE!

Here is accurate, authentic, reliable servicing information direct from 74 TV receiver manufacturers. New, enlarged page size, 12 x 15 inches, with all pages filed in place. Unbound pages which contain last-minute information may be quickly put into place by the Manual's owner. Double spreads, triple spreads and giant pages have been retained... but triple spreads and giant pages now have only one fold for greater convenience and durability. There's more ease in using, too, because there are fewer pages to turn and because diagrams and related text are more closely positioned. Order now from your Jobber.

Equivalent of Approximately 2032 Pages (8 1/2 x 11 1/2), Plus Cumulative Index Volumes 1, 2 and 3, Plus the Famous "How It Works" Book

\$21⁰⁰
Complete

RIDER MANUALS

| | |
|---|---------|
| Television Manual Volume 3 (Plus "How It Works" Book and Index) | \$21.00 |
| Television Manual Volume 2 (Plus "How It Works" Book and Index) | \$18.00 |
| Television Manual Volume 1 (Plus "How It Works" Book and Index) | \$18.00 |
| Volume XIX | \$19.00 |
| Volume XVIII | \$19.00 |
| Volume XVII | \$16.50 |
| Volume XVI | \$ 8.40 |
| Volume XV | \$19.80 |
| Volume XIV to VII (each volume) | \$16.50 |
| Volume VI | \$12.50 |
| Abridged Manuals I to V (one volume) | \$19.80 |
| Record Changers and Recorders | \$ 9.00 |
| Master Index, Covering Manuals, Vols. I to XV | \$ 1.50 |
| PA Equipment Manual, Vol. I | \$18.00 |

FM TRANSMISSION and RECEPTION

by John F. Rider and Seymour D. Uslan

A "must" book for the radio serviceman who looks to FM and television as an important part of his future earnings. Covers all types of frequency modulation systems employed in TV, radio, amateur radio, railroad, aviation, marine, police, point-to-point and mobile receivers. 416 pages, profusely illustrated. **\$3.60**

TV PICTURE PROJECTION and ENLARGEMENT

by Allan Lytel

Timely... Complete... Authoritative and well-organized explanation of the fundamentals of light, optics and optical systems as employed in home television receivers, with emphasis on projection types and front lens enlargers. 192 pages; 119 illustrations. **\$3.30**

BUSINESS HELPER

by Leslie C. Rucker (Rucker Radio Wholesalers)

Written by a successful business man who started from scratch and worked his way up to a chain of 3 stores. Any one of his many worthwhile ideas can mean fifty times the cost of this book in your pocket. 144 pages; 22 chapters. **\$2.00**

JOHN F. RIDER PUBLISHER, Inc., 480 Canal Street, New York 13, N. Y. • Export Agent: Rocke International Corp., 13 E. 40th St., N.Y.C., Cable, ARLAB.


RIDER MANUALS mean SUCCESSFUL SERVICING

NOTE: The Mallory TV Service Encyclopedia, 1st TV Edition, makes reference to only one source of TV receiver schematics—Rider TV Manuals.

NOTE: The Mallory Radio Service Encyclopedia, 6th Edition, makes reference to only one source of radio receiver schematics—Rider Manuals.

NOTE: The C-D Capacitor Manual for Radio Servicing, 1948 Edition No. 4, makes reference to only one source of receiver schematics—Rider Manuals.

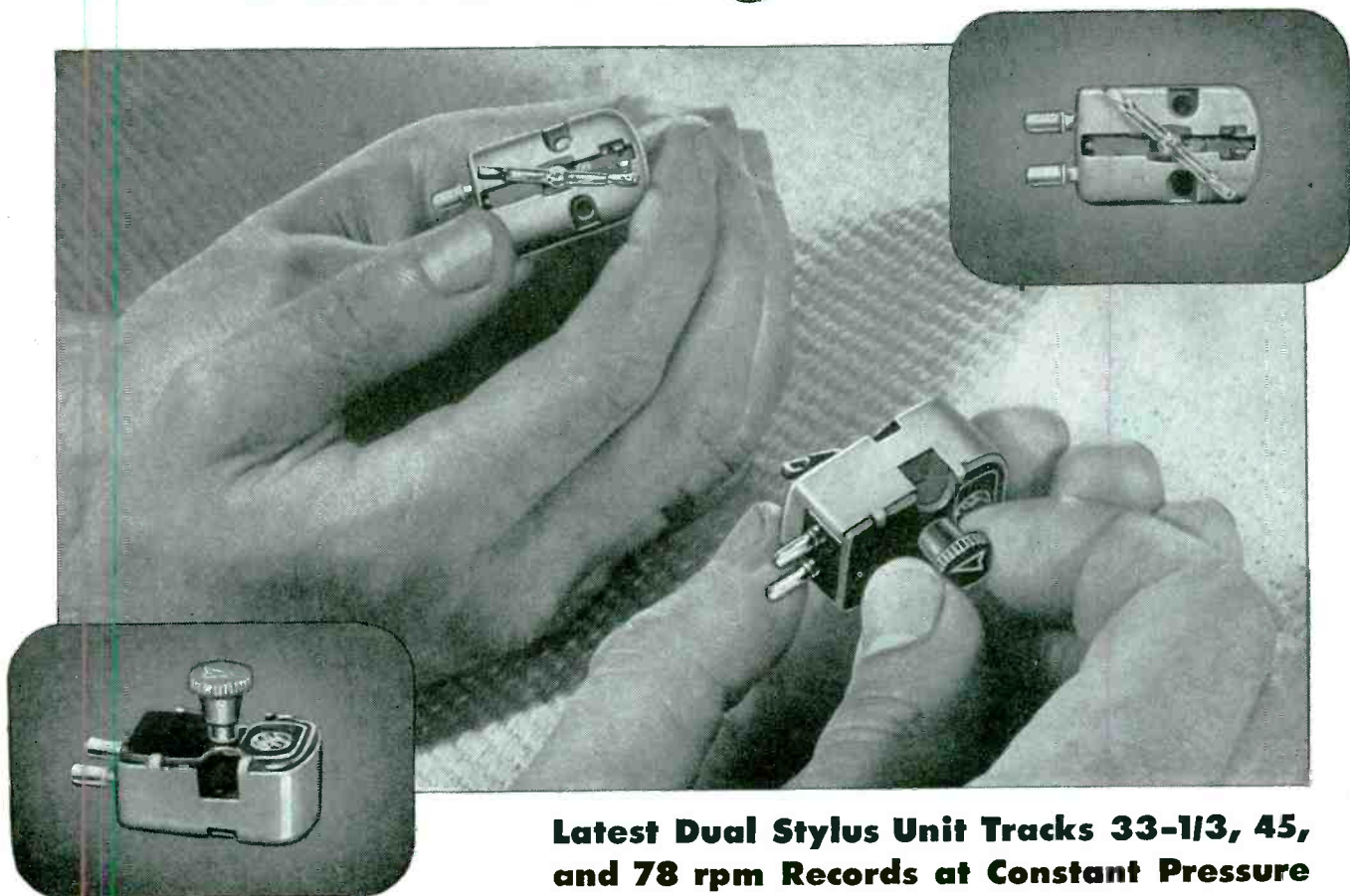NEW G-E *Triple-Play* CARTRIDGE PLAYS ALL 3 SPEEDS



Latest Dual Stylus Unit Tracks 33-1/3, 45, and 78 rpm Records at Constant Pressure

Costs 25% less than Pickups it Replaces

A new General Electric "Triple Play" Cartridge that tracks any commercial record is now available to manufacturers, distributors, and dealers.

Simplicity is the key feature of this notable electronic advancement. Once installed in a tone arm, the cartridge will play all types of popular narrow groove and standard groove records *without replacement or even a change in position!*

ONLY ONE PRESSURE

The new cartridge retains the unsurpassed frequency response characteristics of the famous G-E Variable Reluctance unit and in addition, tracks the three types of records at 6 to 8 grams. Thus the pressure is constant regardless of the stylus you're using. The special design of the "Triple Play" permits precise adjustment of tone arm pressure. Weight changing and pressure compromise problems are eliminated. High compliance and low moving mass reduce record wear to a minimum.

TWO STYLI IN ONE CARTRIDGE

A single twist of a built-in knob turns either end of a dual stylus to playing position. A 1-mil stylus, mounted at one end, plays 33 1/3 and 45 rpm records, and a 3-mil stylus, at the opposite end, tracks standard 78 rpm records.

MANUFACTURERS NOTE LOW COST

Although it plays records that formerly required the use of two cartridges, the price of the "Triple Play" is 25% less than the price of two individual cartridges. It is adaptable to many types of tone arms and *its use as an initial component will effectively reduce set manufacturing costs.*

UNAFFECTED BY TEMPERATURE

The G-E "Triple Play" is unaffected by normal climatic changes in humidity and extreme variations in temperature. Needle talk and needle scratch are reduced to a minimum. Record reproduction—as always with G-E Cartridges—is superb. Mail coupon below for complete information.

You can put your confidence in —
GENERAL  ELECTRIC

General Electric Company, Parts Section 1E
Electronics Park, Syracuse, New York
Send me full particulars on the new G-E "Triple Play" Cartridge.

NAME _____

ADDRESS _____

CITY _____ STATE _____



What a show!

A recent intensive survey discloses that among the major television set manufacturers, more than 75% use Sylvania cathode ray tubes!

This impressive showing is a tribute to the research and quality production techniques employed by Sylvania.

You can take advantage of this ready acceptance by having a complete stock of the various types of these television picture tubes so widely used by set makers—who in turn, of course, sell to *your* regular customers. See your Sylvania Distributor about the complete line! For complete data write *Sylvania Electric Products Inc.*, Dept R-1911, Emporium, Pa.

These leading television set manufacturers use Sylvania Television Picture Tubes

Admiral • Air King • Andrea • Ansley • Automatic
 Bendix • Crosley • DeWald • Emerson • Fada
 Farnsworth • Garod • Hallicrafters • Hoffman
 Magnavox • Midwest • Motorola • National • Olympic
 Packard-Bell • Philco • Pilot • Raytheon-Belmont
 Regal • Scott • Sentinel • Silvertone • Sparton
 Stromberg-Carlson • Tele-King • Tele-tone • Temple
 Trav-ler • Westinghouse • Zenith

SYLVANIA ELECTRIC

CATHODE RAY TUBES; RADIO TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES, SIGN TUBING; LIGHT BULBS; PHOTOLAMPS

RADIO · TELEVISION · ELECTRONIC SERVICE

TV Servicing Pitfalls

TV, now in a boom stage and destined to out-distance radio's greatest ticker-tape days, has catapulted many Service Men to a gleaming position and many others, we regret to report, to a dismal low in acceptance. Why, we wondered, did the latter sad state exist? With installation business at its peak and servicing on the climb, the situation was truly puzzling. But there were reasons, and plenty of them, as a survey among manufacturers, distributors and TV owners revealed.

It was found, for instance, that the antenna was quite a troublesome factor. Too many Service Men, unfamiliar with the types of antennas to use, or how to install them for maximum effect, were finding these operations a loss item. Antenna exploration, an extremely vital procedure, was found suffering from complete neglect by these Service Men and as a result, poor antenna locations prevailed. Instead of choosing the antenna sites for their electrical proficiency, the physical qualities of the installation received prime consideration. Some Service Men were reported to be mounting antennas in an obviously incorrect position, following a prior installation without regard to its correctness. As a result time-consuming rechecks and repositioning have been found necessary. There is no denying that strong mechanical mounts are essential and as such, should receive careful consideration, but it is extremely important that the *rf* pickup factor be probed closely, too, and a just compromise made.

Installations made in haste were another contribution to income loss headaches. In many instances mount carelessness, resulting in falling antennas, caused property damage. Poor installation methods were also found to cause water leaks and subsequent damage to rooftops and living quarters.

Lack of a program to insure complete land coverage of operating stations served as another time-loss item, the survey revealed. Since all the stations are not always on the air when an installation is made, complete per-

formance insurance cannot be certified, unless some check system is used. It has been found a wise policy to return once or perhaps even twice to check up on channel coverage and thus gain a satisfied customer. Many service shops have found it highly profitable to include these return trips as a part of a routine neighborhood program.

The lack of familiarity with antennas which can provide the best results in local or fringe areas have resulted in grave despair on many fronts. It is well recognized that there are many installations which are difficult, from a normal installation view, but such problems can be appraised carefully and, in most instances, solved with a plausible *sincere* explanation of the conditions at hand and the type of an antenna system that should provide the best possible signals.

The extensive activities of an ever-growing army of successful TV service shops reaccent the fact that the business of TV installation and service can be profitable, when sound business and technical know-how prevails up and down the ladder, in the shop and in the field.

Ultrahighs and the Service Man

THERE'LL BE QUITE an array of problems facing the Service Man when the ultrahighs finally receive FCC approval. As revealed in *Jots and Flashes* (see page 48, this issue) there is doubt that we'll have these higher bands before late next year, but the situation is so replete with variables that an early study of the peculiarities which do exist on these frequencies is warranted.

Reporting on this state of affairs before a recent IRE meeting in Cincinnati, John D. Reid of Crosley said that as we go higher in frequency . . . "*rf* preselection becomes increasingly difficult to obtain and the use of *uhf* *rf* stages ahead of crystal converters will generally result in a reduction of signal-to-noise ratio. The *rf* selectivity, which can be obtained from two circuits on the *uhf* band, is most unsatisfactory when considering the image

rejection requirement predicated upon using *ifs* below the *vhf* band. An *if* in the neighborhood of 400 megacycles would minimize the image problem, but such an *if* is not practical today from gain and selectivity standpoints. . . . Further consideration of this problem indicates that by careful design and the use of two tuned circuits in the preselector, an average image attenuation of 10 to 15 db can be expected in the *uhf* band in conjunction with a 41-mc *if*. This average figure would be approximately double at the low end of the band, and approximately half at the high end of the band."

Choice of IF

Commenting on the *if* frequency chosen by the RMA for combined *vhf* and *uhf* use, Reid stated that 41.2 mc was the first choice for a proposed standardization.

"Reexamining the factors entering into the choice of this frequency," he said, "it was found that the second harmonic of the sound *if* would fall 850-kc below the channel-six picture. The frequency of 41.65-mc, as indicated by image requirements for the ultrahigh band, would put this second harmonic within 50 cycles of the channel-six picture, and was therefore, desirable. The 41.3-mc frequency, as indicated by the *uhf* local oscillator radiation requirements would put this second harmonic 650 kc below the channel-six picture, which could probably be tolerated."

UHF Design Study

With these problems in mind, it was found that a 41.25-mc *if* would be the best compromise, since it provides a series of local oscillator frequencies starting with 522-mc, and increasing in 6-mc steps, all of which are divisible by six.

A detailed review of ultrahigh designs, including the RMA suggestions and other engineering proposals, is now being prepared. Watch for this important discussion.—L.W.

Design, Application and

Characteristics of Selenium Designs... How the Cell Operates... Limiting Factors... What Aging Means... Cell Circuits... Test Procedures... Servicing Problems and Solutions.

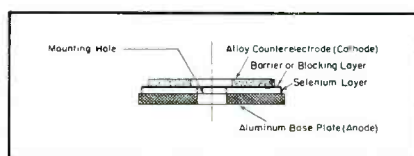


Fig. 1. A cross-sectional view, exaggerated, of a selenium cell layer.

IT HAS LONG BEEN KNOWN that in the crystalline state, the element, selenium, is a semiconductor, offering very high resistance to electric current in one direction, but conducting readily in the other. This property of rectification has been used commercially in converting *ac* sources to *dc*, by the proper series and parallel combinations of selenium cells or plates into rectifier stacks to supply electroplating, battery charging and other *dc* power needs.

In recent years, however, there has been developed the selenium rectifier with high back-voltage capabilities for use in receiver power supplies, performing the function of a tube, while providing several advantages not afforded by the tube type rectifier. Among these are ruggedness, small size, simplicity of mounting and connection (since there is no filament), comparatively cool operation, and long life. Such factors have made the selenium stack a particularly useful component of the small *ac/dc* table model and 3-way portable type receiver, and of the TV set as well. It is gaining increasing importance not only as a replacement for existing vacuum-tube rectifiers, but as a standard part of the transformerless type radios and compact TV receivers.

The selenium rectifier cell is constructed in the shape of a disc or plate consisting of four essential layers; the aluminum base plate, which serves as an anode as well as a strong mechanical support for the other sections; the thin selenium layer, which is applied to the base plate; an extremely thin barrier or blocking layer, at which the

by IRWIN WOLF

Radio Receptor Company, Inc.

rectifying action takes place; and a counterelectrode layer, made of a metal alloy which acts as the cathode of the cell. The alloy can be recognized by its silvery crystalline appearance. It does not extend to the edge of the plate, but is usually applied with a slight margin to eliminate the possibility of direct shorts to the aluminum anode at the edge of the plate. The area of this alloy cathode is the effective rectifying area of the cell.

The type of rectifying unit most commonly used in standard receiver circuits is composed of a number of selenium cells in series (usually five) and is called a half-wave selenium-rectifier stack. The plates are separated by spacing washers to permit cooling by convection.

Electrical Characteristics and Limiting Factors

The selenium cell is essentially an electric valve, having roughly 2,000 times as much resistance to current through it in one direction as in the other. The direction in which conventional current will be easily conducted through the cell (from aluminum anode to alloy cathode) is known as the *forward* direction, while the opposite (high resistance) direction is termed the *reverse* direction.

In Fig. 2 appears the typical forward and reverse current characteristic of a cell. It can be seen that the value of resistance in either direction is not constant, but varies with the value of voltage across the cell. It is important that this non-linear current-voltage characteristic be carefully considered when performing tests on a rectifier. It should also be noted that the selenium rectifier will pass a small but measureable current in the reverse

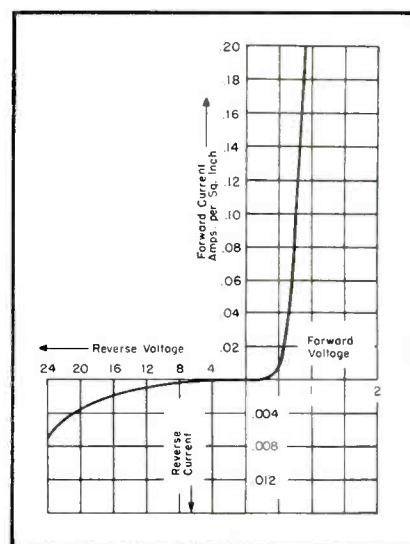


Fig. 2. Graph of forward and reverse current versus voltage. Note the differences in the forward and reverse scales.

direction when operated under rated conditions.

If a selenium stack is subjected to a reverse voltage for some time, the reverse leakage current will decrease. This process is called *electroforming*, and it occurs every time the stack is put into use at rated voltage. Consequently, in a radio set, the average leakage of a selenium unit decreases with time. However, if the rectifier has been out of use for a day or so, the reverse leakage, upon reapplication of voltage, will be higher than normal, taking about a minute to reform to its previous value.

During the first month or two of operation, the average forward resistance of the rectifier stack will gradually increase, causing a drop in output voltage. Generally, this *aging* process will not cause any noticeable change in receiver performance; however, unusually severe operating conditions may result in excessive aging. Replacement of the rectifier is recommended in the event of a 15% drop in the original output voltage, at which time the for-

Servicing of

SELENIUM RECTIFIERS

ward voltage drop across the stack would be approximately 15 volts *RMS* instead of the normal 5 volts *RMS* at rated load.

Although rated for a definite continuous normal operating load current, the selenium stack will withstand momentary overloads of many times this rated current without serious damage.

Plate temperature is an important factor in stack operating. Maximum selenium plate temperature for chassis operation has been set at 75°C (167°F). Since excessive heat accelerates aging, it is desirable to keep the rectifier unit at its normal operating temperature of $70^{\circ}\text{--}75^{\circ}\text{C}$ ($158^{\circ}\text{F--}167^{\circ}\text{F}$) or below, especially while the stack is new. For rated load conditions, a maximum ambient temperature of 45°C (113°F) will limit the plate temperature to acceptable values.

Typical half-wave selenium rectifiers for radio use at present have continuous *dc* load current ratings ranging from 50 to 500 ma, and vary in size from less than 1 cubic inch to about 4 cubic inches. For the most part, however, the 100-ma 1-cubic-inch size is found in standard receivers today. The larger sizes are more commonly being used in TV sets. Stacks are rated to withstand a maximum of 380-volt peak-inverse voltage, and 900 volts across the insulation between each terminal and the mounting eyelet. When used in a half-wave circuit with a filter, the *ac* line voltage should not exceed 130 volts *RMS*.

Common Circuits for Selenium Stacks in Radio Receivers

Of the types of selenium-rectifier or power supply circuits normally en-

countered in radio receivers, the simple half-wave system with filtered output is by far the most common. Used extensively in table model *ac/dc* receivers and 3-way portables, the typical basic circuit (Fig. 3) differs from the conventional tube rectifier circuit mainly in the absence of a rectifier filament connection, and in the addition of a series protective resistance element (R_1).

Diagrammed in Fig. 3 is a common type of selenium rectifier half-wave power supply circuit. In this circuit, the terminal marked *K* or $+$ should be connected to the positive side of the electrolytic filter capacitors and to the *B+* line. It is important that the proper rectifier polarity be observed; the cathode *K* can be identified by the crystalline appearance of the alloy. A minimum of 5 to 22 ohms 5-watt series resistance, R_1 , is placed in the circuit to protect the stack and capacitors against the effects of current surges during operation, and to limit the value of *RMS* rectifier current to not more than 2.5 times the rated *dc* output current. The minimum value of R_1 depends on the load current rating of the stack, being 22 ohms for 100 ma *dc* and below, 15 ohms for 100 to 200 ma ratings, and 5 ohms for above 250 ma.

Many radio sets have been modified in the field to be power fed by selenium rectifiers instead of the original tube rectifier. For those which have been designed with provision for a pilot lamp (usually No. 47) connection across a low voltage tap on the rectifier tube filament, the replacement of the tube by a selenium stack makes it necessary for the pilot lamp to be moved to a new source of voltage. This may be done by placing

the lamp across the series resistor R_1 , or across a tap on the voltage dropping or ballast resistance when provided. Of course, a suitable compensating resistor, R_2 , is connected in place of the missing tube filament where necessary. It is generally in the *ac/dc* table model receiver that the filaments are connected across the *ac* side of the line; filaments for miniature tubes in 3-way portable models usually are supplied with *dc* voltage from a tap on a power supply bleeder, R_3 , as shown dotted in Fig. 3.

Since the *dc* output voltage of a selenium stack is normally higher than that of a tube operating under the same conditions, it often becomes necessary to insert sufficient extra series resistance into the converted circuit to keep the *B* supply voltage from being too high.

It should be remembered that in the half-wave circuit, the conditions of the selenium rectifier and input filter capacitor are somewhat interdependent. For instance, if the input electrolytic capacitor is leaky, the excessive current through the capacitor may cause the stack to overheat, while if the rectifier is not sufficiently formed, the electrolytic capacitor may in turn overheat and possibly decrease in capacitance due to internal changes. Typical values for C_1 are 40 to 100 mfd; very large input capacitance values should not be used without increased values of limiting resistance R_1 , since the charging current would be very high and would tend to overheat the selenium rectifier, accelerating aging or possibly causing failure.

Two less commonly used power circuits involving selenium rectifiers are


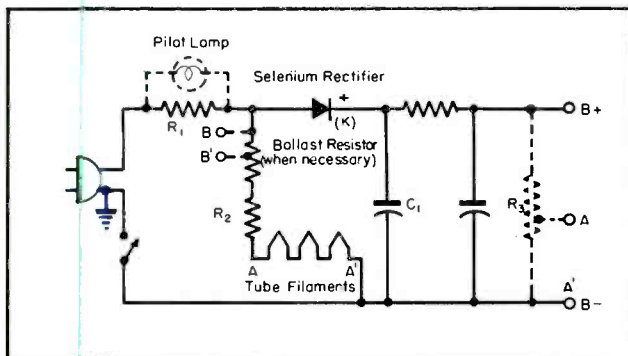


Fig. 3 (left). A typical half-wave power supply circuit using a selenium rectifier.

Fig. 4. Two types of doubler circuits. In *a* appears a symmetrical doubler and in *b* we have a series line feed doubler.

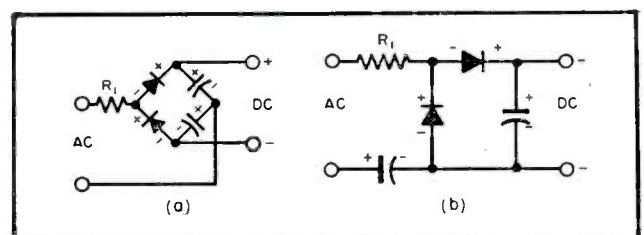

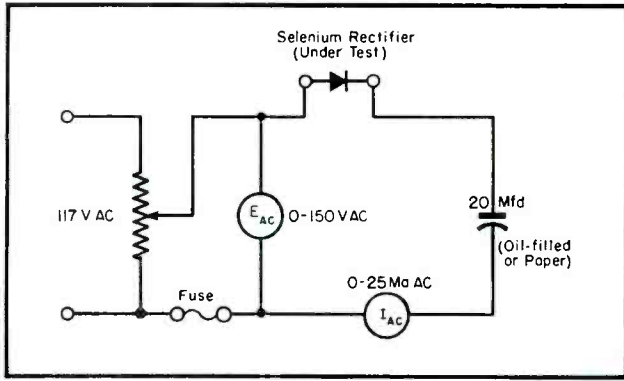


Fig. 5. A reverse testing circuit.

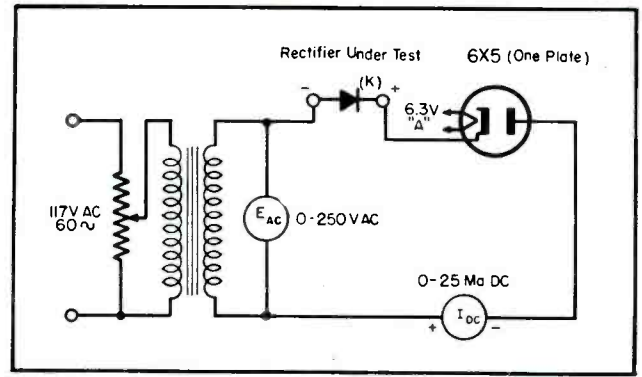


Fig. 6. Circuit of an alternate reverse testing setup.

the voltage doublers, shown basically in Fig. 4.

Again the series protective resistor is important. The same 130-volt *ac* input voltage limit should be observed as in the half-wave circuit, and R_1 should be 25 to 50 ohms depending on capacitor values and load conditions.

Test Procedures and Circuits

When a selenium rectifier has been subjected to excessive voltage, current, or temperature conditions, it may become partially or completely damaged. Final evidence of such condition is given by an electrical test; however, there are several physical indications of a faulty stack which may be helpful in recognizing possible trouble in the rectifier or in the external circuit:

Sparking: If a much higher than rated inverse voltage is applied across a selenium stack, a crackling, popping sound may be heard, accompanied by small blue-white sparks on the alloy surface. Ordinarily, this should not be mistaken for an indication of a permanently faulty rectifier, since the effect will cease as soon as the excessive voltage is lowered, and, if the surge lasts only a few seconds, the rectifier will then continue normal operation.

Blowout Patches: Many of the sparks leave small, round blowout spots which appear black against the silvery alloy. These blowouts are self healing, and will not short the rectifier; they decrease the alloy surface, however, and if the sparking condition has been severe, the effective rectification area may have been reduced below allowable values. Further passage of rated current through this reduced area may cause excessive heating and subsequent total failure of the stack. If blowouts are observed all around the contact washer at the center of the plate, it is best to replace the rectifier. Plates with greater than 20% blowout density are not recommended for further use.

Melted and Discolored Alloy: If the stack forward current is increased to

several times normal value for an extended period of time, the temperature of the rectifier may rise beyond the melting point of the alloy cathode, which would cause it to soften and run, with possible surface discoloration. This condition indicates that the unit is unfit for further use. When a stack has been completely destroyed, there will usually be noticed a combination of blowout patches and melted, discolored alloy.

It is important that the selenium stack characteristics as noted previously be kept well in mind while proceeding with and evaluating tests made on the unit. Emphasis should be placed on the fact that an ohmmeter gives almost meaningless readings when used on a selenium rectifier in both the forward and reverse directions. The resistance reading will depend on the ohmmeter voltage and scale, since the resistance of a stack in either direction depends on the particular value of voltage across it. Therefore, ohmmeters should be used only to check stack continuity and never to determine the relative quality of a selenium unit.

There are several circuits and procedures concerning a high back voltage selenium rectifier which will be of use in indicating its general quality for operation in receivers.¹

Continuity: To test a stack for an open connection, readings of resistance in both the forward and reverse directions should be taken with a high range ohmmeter. Two readings, one with the

meter leads reversed, will normally read greatly different values in each direction for a stack having continuity, while an open rectifier is indicated by the same extremely high reading in forward and reverse directions.

Reverse Leakage: Blocking quality of a selenium receiver stack may be measured in several ways. Probably the most simple and convenient test circuit would be that illustrated in Fig. 5.

Polarity of stack connection in this circuit is immaterial. It is important that the 20-mfd capacitor be of the paper or oil-filled type, and not electrolytic.


The input voltage should be increased from zero by means of a suitable potentiometer or variable autotransformer. If the stack begins to sputter and spark as the voltage E_{ac} is increased, the value of applied voltage should be allowed to remain for a few minutes at the highest value which will not cause sparking on the alloy, then slowly increased again, the procedure being repeated until the input voltage is up to 177 volts *ac* or until the *ac* milliammeter reads full scale. Only damaged or badly deformed rectifiers will exhibit this sputtering effect; for the most part, full rated voltage may be applied without causing sparking. The input voltage should be allowed to remain at 177 *v* for about five minutes before a reading of *ac* milliamperes is taken.

If the *ac* milliammeter reading is 10% of the rectifier rated *dc* load current or less, with the 117 *v ac* impressed, the stack reverse blocking quality is good. If the current reading is slightly higher than proper for the particular size stack tested the unit is poor in reverse grade, but may reform upon longer voltage application. High current readings indicate a damaged stack. For instance, if a selenium rectifier rated at 100 *ma dc* were put on this test, and the current reading were 10 *ma ac* or less at 117 *v ac* in-

(Continued on page 45)

¹Ratings apply to all radio half-wave rectifier sizes.

Fig. 7. A forward voltage-drop test circuit.

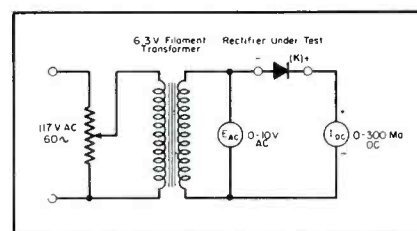

MADE FOR SERVICE

Snyder

PHILADELPHIA

REDI-MOUNT®

TX

CONICAL AERIALS

SUPERSTRUCTURE PATENTS PENDING

Featuring
the Exclusive New

HI-PAQ*

CANTILEVER TRUSS CONSTRUCTION

* HI-PAQ is a material of extreme tensile strength not affected by weather or temperature, either mechanically or electrically.

SNYDER MFG. CO.

ANTENNA-GINERS
PHILADELPHIA 40, PA., U. S. A.

Export: Roburn Agencies, Inc., N. Y.
New York: H. L. Dalis, Inc.
Phila.: Almo Radio Co.

Distributed Only by the Best—Everywhere

48 M. REG. U. S. PAT. OFF.

TV Model With

by **WALTER H. BUCHSBAUM**

Chief Engineer

Tech-Master Products Company

RECENTLY A TV circuit innovation, keyed *agc* (*cover*), was developed to improve the noise characteristic of a receiver and prevent overloading. It was found possible to include this new system in a 630TS chassis (Fig. 1) and obtain extremely effective results. For example, in tests a model with the circuit was found capable of holding the picture steady with up to 30% flutter modulation from airplanes flying up to 400 mph.

The operation of the keyed *agc* system is based on the principle that horizontal sync pulses are of constant amplitude which change only as the signal strength changes. The *agc* bias voltage is made dependent only on the sync pulse amplitude and does not vary as the picture components vary.

One of the two main advantages of this system is that the 60-cycle sync pulse does not enter into the *agc* circuit, and therefore need not be filtered out from the *agc* bias voltage. Filtering the 60-cycle pulse requires a long time constant filter and that, in turn, means that the *agc* cannot respond to fast changes in signal strength. This is particularly objectionable in the case of airplane flutter, caused by the beat between the direct signal and that reflected from the speeding plane. The beat frequency which causes airplane flutter is usually up to about 100 cycles, and naturally the conventional type of *agc* filter simply filters out any change in *agc* bias due to this flutter frequency.

Keyed *agc* employs filters which have a much shorter time constant and therefore the *agc* bias is able to compensate for airplane flutter. The other advantage of keyed *agc* is its practical immunity to noise. Standard *agc* systems, using the entire picture signal, are naturally influenced by the amount of noise present in the picture. In a difficult location the noise pulses may be so strong as to cause a strong negative bias to be set up, which then cuts down the amplification of the desired picture signal. In the keyed *agc* system only the sync pulse amplitude affects the *agc* bias, and since the sync pulses take up less than 5% of the duration of the entire signal, less than 5% of the total noise present can have any effect on the *agc*. In actual field tests


this noise immunity is apparent, providing a difference between a weak, snowy picture, and a strong picture with occasional noise spots.

The *agc* tube, a 6AU6, obtains its plate voltage from a special winding on the width control. This plate voltage is a sharp, positive pulse from the horizontal sweep system. Only during the period of this pulse, which is about 190 volts peak-to-peak, can the tube conduct; the cathode is 140 volts positive and no current can flow. During the conduction period, the amount of plate current is determined by the control grid bias, which is fixed at about 5 volts negative. The sync pulse, which is positive, appears on the grid at the same time as the sharp pulse appears on the plate, if the horizontal sweep is in synchronism. The amplitude of the sync pulse therefore determines the plate current. If the sync pulse is strong, from a strong picture signal, it will drive the grid less negative and permit more plate current. The plate current flows through 150,000- and 100,000-ohm resistors and charges a .5 mfd capacitor (C_{142}), thus creating a negative *dc* bias across these resistors. The voltage across the 100,000-ohm unit is then applied to the grids of the first three *if* amplifiers and the *rf* stage, controlling the gain of these tubes. The screen potential of the 6AU6 *agc* tube is obtained from a convenient 210-volt *dc* point and remains fixed.

RF Tuner

The tuning unit in this modified

Fig. 2. Response curve of the stagger-tuned *if* circuit; picture *if* carrier is at half-power point with a full 4-mc bandwidth. The sharp dip at 21.25 mc is due to action of the sound *if* traps.

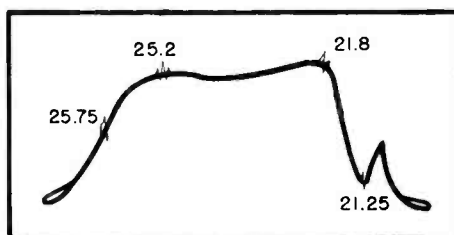

model is the popular standard front end tuner, which has a different set of *rf* and oscillator coils for each channel. Individual sets of coils can be removed for repair or adjustment without dismantling the unit. Oscillator alignment is possible from the front of the set. Each channel can be tuned separately and the adjustment of one has no effect on any of the others. The first *if* coil is mounted on the tuner sub-chassis and tuned from the top.

In a 21.25-mc sound *if* trap there is a separate coil, mounted next to the first *if* coil and also tunable from the top. A 6AG5 is used as an *rf* amplifier and a 6J6 duo-triode as an oscillator and mixer.

Video IF Amplifiers

The stagger-tuned *if* system used in this model is identical to that used in the 630 type circuit, in alignment procedure and performance. Peaking frequencies are at 23.4, 25.2, 22.3, 25.3 and 21.8 mc. These coils, in the *rf* front end, with their varied loading consisting of the different grid and plate resistors, provide a response curve like that shown in Fig. 2. The picture *if* carrier is at the half power point, with a full 4-mc bandwidth. The sharp dip at 21.25 mc is due to the action of the sound *if* traps, one of which is located on the *rf* tuner and the second one being in the cathode of the last picture *if* tube. As cited previously, the outstanding difference between this circuit and the original 630 appears in the *agc* circuit, with the control grids of the mixer and the first three *if* stages obtaining their bias from this *agc* circuit. For alignment purposes it is necessary to deactivate this circuit temporarily. During the *if* alignment process, the *agc* tube must be removed and a 3-volt battery connected across the *agc* network (100,000 ohms) and C_{142} (.5 mfd). Two 1½-volt flashlight batteries connected in series will do the trick. The brass center stud is connected to the chassis and the outer shell to the *agc* network, and a negative bias simulating the action of the *agc* tube will be obtained. The alignment of the *if* traps at 19.75 and 27.75 mc will be

(Continued on page 26)

KEYED AGC SYSTEM

[See Front Cover]

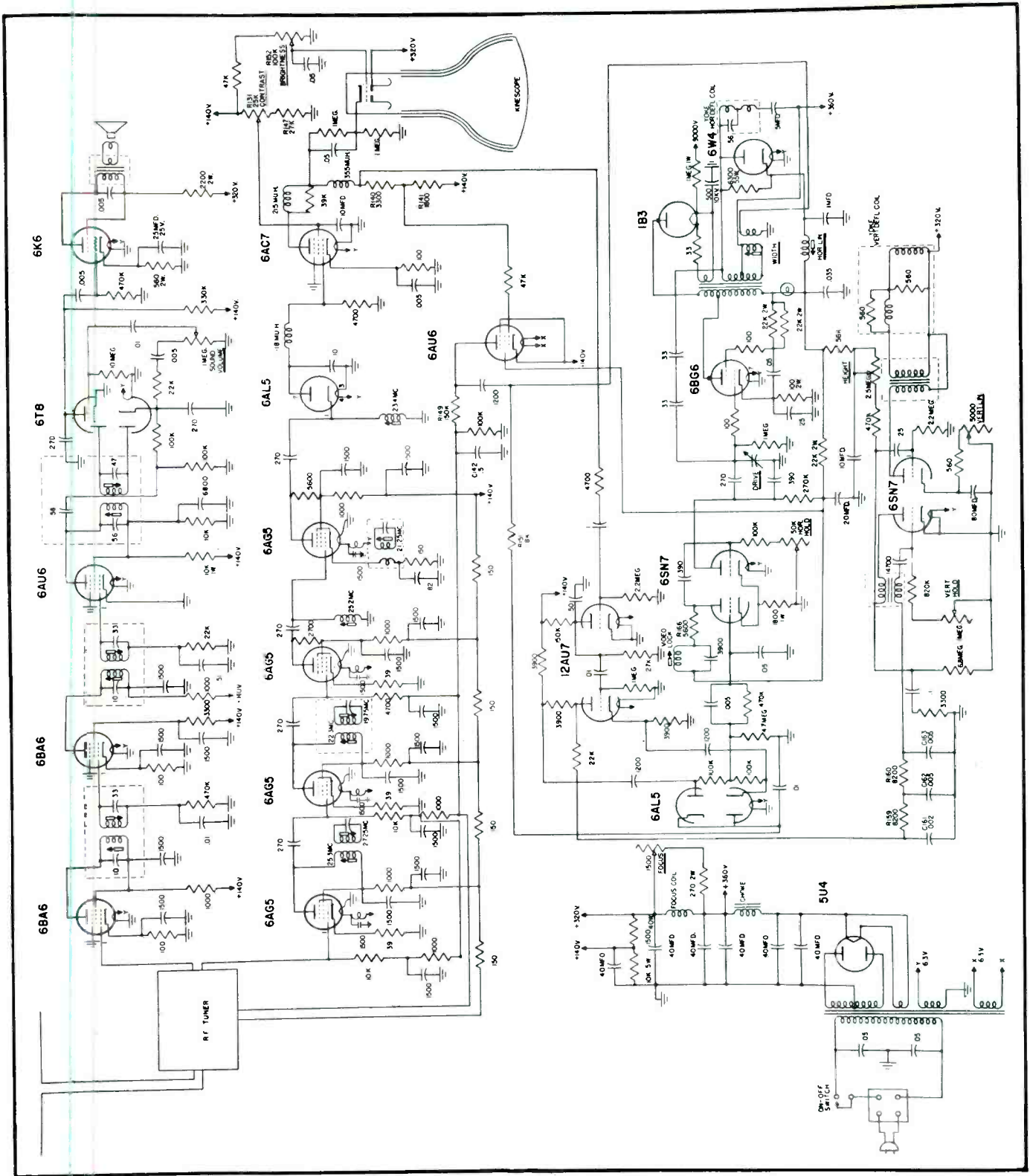


Fig. 1. Complete circuit of the Tech-Master Model BC-1223 receiver which features keyed *agc*.

Performance Diagnosis Of Vacuum-Tube Circuits

How to Use Tube Characteristic Curves For Circuit Analyses and Determine Possible Sources of Trouble.

by EDWARD M. NOLL

Instructor in Television
Temple University

THERE ARE NUMEROUS occasions when complete circuit information is not available and operational characteristics of a particular circuit are desired. Often the only information provided may be the schematic with tube types and parts' values listed. At times the gain or output voltage may be the unknown and at other times, when trouble-shooting, it would be helpful to know just the operating plate voltage or grid bias. Occasionally we'd like to know what would happen if a different part value were substituted in place of a value shown on schematic.

Most of this type of information can be readily calculated, knowing only tube types and parts' values. The only tools necessary are a common sense approach and a set of tube characteristic curves. A working knowledge of curve procedures is also of the utmost importance in basic practical design work.

The Operating Point

In diagnosing stage performance one of the most important considerations is the operating point. Once it has been found the remainder of the information to be gathered presents no particular problems. Thus, the very first task is to find the operating point by plotting a dynamic load line on the curves.

Suppose 6A3 circuits were the problem. Selecting three typical 6A3 circuits (Fig. 1) we find that each one has the very same operating point. This is found for each case on the curve of Fig. 2. In the first example, an output stage is shown feeding a 1,750-ohm reflected load; cathode resistor value is 750 ohms. To find the operating point the procedure is as follows:

(1) A straight vertical line is drawn from the plate voltage axis along the 250-volt line. The operating point is along this curve, for at the operating point the plate voltage must be 250 (neglecting resistance of the transformer).

(2) Now we have to draw a curve, which represents a possible loci of

(Continued on page 27)

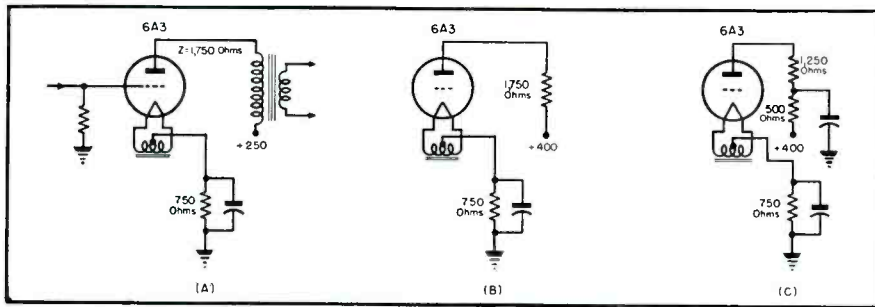


Fig. 1. Three 6A3 triode circuits with the same operating point.


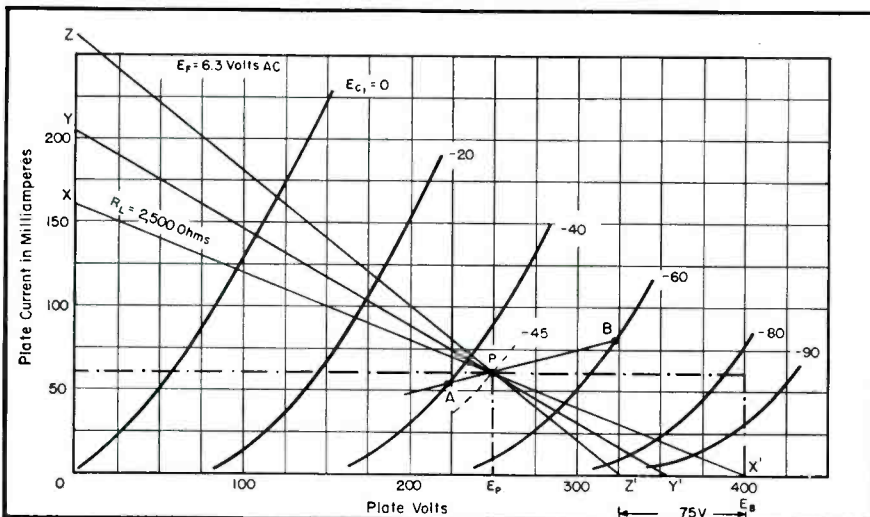


Fig. 2a. Characteristic curves of the 6A3s.

Fig. 2b. Plot illustrating the corrections for winding resistance and plate-load resistor. Area at left represents plate dissipation and area at right the dc dissipation in the load resistor.

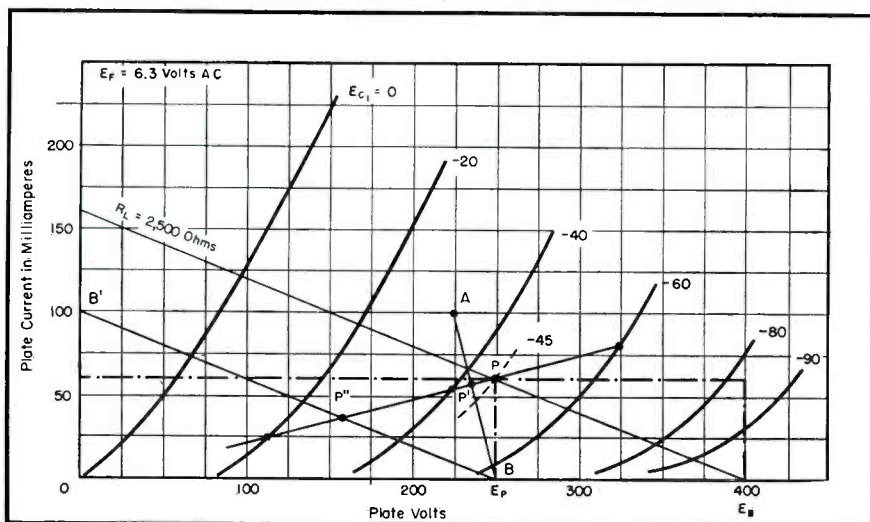

Here's What Dealer-Service Men Are Saying About The RAYTHEON Bonded ELECTRONIC TECHNICIAN PLAN

MARYLAND
William Douglas
Apex Radio Service
Baltimore, Md.
The Bond certificate really does build confidence in my customers

MINNESOTA
James A. McDonald
McDonald Radio Service
Minneapolis 7, Minn.
Program has eliminated need for estimates and increased business 100%

MISSOURI
Lynn R. Moore
Lebanon Radio Sales & Service
Lebanon, Mo.
My shop is the only one in town bonded. I have more repair work than all the others.

NEW YORK
George's Radio Service
Yonkers, New York
Results have been most complimentary and satisfactory

OHIO
Walcer H. Horton
Kala Radio Sales & Service
Kent, Ohio
We have found as a bonded dealer that it sure pays off thanks to Raytheon!

ARKANSAS
J. H. Wyatt
J. H. Wyatt Radio Service Co.
Seely, Arkansas
Your program has done very much to build customer confidence

OKLAHOMA
David R. Gray
Gray's Radio Service
Duncan, Okla.
We are proud of our "bond certificate" and it is well displayed

NEW JERSEY
I. Marks
Marks Radio Service
Trenton, N. J.
Gives customers confidence in repair jobs when our Bonding is pointed out.

FLORIDA
H. F. Nolan
Nolan's Radio Service
Tallahassee, Fla.
I have had a bonded shop now for almost 4 years and I'm glad for the good reputation

MISSOURI
L. E. Baker
Baker Electronics
Kansas City, Mo.
Appreciate the service very much and feel our customers have more confidence in us.

CONNECTICUT
Bert B. Keller
The Electronic Shop
Westport, Conn.
Excellent Public Acceptance campaign and dealer aid program

LOUISIANA
N. Protel
Delta Radio Service
New Orleans, La.
I find that by displaying my bond certificate helps business

PENNSYLVANIA
Frank P. Dattilo
Frank's Radio Shop
Pittsburgh, Pa.
People have more confidence in my shop

CALIFORNIA
T. M. Bowen
Apples Radio
Berkeley, Calif.
This has been a fine program and we like it very much

HERE'S WHAT THE PLAN IS:

The dealer who displays this Certificate wipes out all doubt in his customers' minds as to the quality and dependability of his radio service work. He offers a 90-day BONDED guarantee on his radio set repair work and replacement parts, backed by *American Mutual Liability Insurance Co.*'s assets of close to a hundred million dollars. YET, IT COSTS HIM NOTHING!

Ninety per cent of all Raytheon Bonded Dealers report that they are making it the feature of their own advertising programs.

The Raytheon Tube Distributor in your area has this Bond for you — if you qualify. It doesn't cost you a cent, but at one fell swoop it sweeps away mistrust — the biggest barrier to volume and profit.

Get in touch with your Raytheon Distributor. Ask him how to become a BONDED ELECTRONIC TECHNICIAN.



NEW!

RAYTHEON CATHODE RAY TUBES

Television Picture Tubes of genuine Raytheon quality are now available in all popular types. For peak video performance, specify Raytheon Radio and Television Tubes.

RAYTHEON

RAYTHEON MANUFACTURING COMPANY

Radio Receiving Tube Division
Newton, Mass., Chicago, Ill., Atlanta, Ga.
Los Angeles, Calif.

Radio Receiving Tubes, Cathode Ray Tubes,
Special Purpose Tubes, Subminiature Tubes,
Microwave Tubes

PHONO *installation and service*

Magnetic Tape Playback-Recorder System Operation and Servicing Notes*

MAGNETIC tape-recording systems appear to have outgrown their gadget stage and become quite a factor in home very-long-playing phono-type applications.

Of particular importance in the setup is the tape.

The physical properties of a magnetic tape are of considerable importance to the behavior of the recording system. Most of the magnetic tapes produced and used today are composed of a coating of the magnetizable material on a stable, non-metallic backing. Backings commercially used are made of organic materials and may be of a fibrous type such as paper or of a continuous film type, a typical example of which is cellulose acetate film. An ideal backing would be one which had infinitesimal thickness and an infinite modulus of elasticity. Such an ideal backing would then have no stretch, but at the same time have a high degree of flexibility.

Since we must obviously deal with practical materials and since performance must be balanced against cost, for a commercial product, certain compromises with an ideal backing must be made. Cellulose acetate has long been used as the *safety* base material for home movie film, where its aging properties and its stability under varying conditions of temperature and humidity have been thoroughly evaluated. Since its performance has been studied over a period of years and since it has reasonable mechanical strength in the thickness desired for magnetic tape, it has found wide acceptance. Since magnetic tape must be subjected to a certain amount of tension during the recording operation, it must necessarily experience a certain degree of elongation. If this elongation is constant in the recording and playback operations, the recorded signal will be reproduced without alteration with respect to time. Variations in tape thick-

by **KENNETH STEWART**

ness would cause corresponding variations in elongation of the tape at a given tension, and while such tape might give consistent performance when recorded and played on the same machine of different type would be subject to appreciable elongation. It can readily be seen, therefore, that thickness variations have to be reduced to a minimum, a condition which is satisfactorily accomplished in present commercial practice.

On most recording machines, the tape is dragged across several stationary surfaces including the erase, record and playback heads. Because of this treatment, the coefficient of friction between the tape and the stationary surfaces must be reasonably low. If such is not the case, the tape will not have a uniform tension throughout its path of travel to the capstan, as the tension will build up from friction point to a friction point. An appreciable increase in tension may be produced by the time the tape reaches the playback head (usually the last element in the head lineup) and this tension can cause the playback head to wear at a rapid rate. A high degree of friction also results in a certain amount of chatter of the tape passing over the head. This chatter becomes audible, in some cases, as a squeal which may appear both as a mechani-

cal noise and as a modulation of the signal on the tape. This type of modulation can become very objectionable and can ruin an otherwise satisfactory recording. For this reason, the coefficient of friction must be held to as low a value as is possible, consistent with adequate traction at the capstan. Satisfactory tape must have no appreciable tendency to stick to itself when wound up in a tight roll.

Equipment Features


It must be recognized that the recorder and playback design must be correlated with the mechanical properties of the tape. Recording equipment designed to permit rapid forward or rewind motion of the tape must be capable of accelerating the tape to a running speed or braking the reels to a quick stop without subjecting the tape to momentary stresses of high value, since such stresses may produce elongation of a permanent nature. Rewinding of plastic-back magnetic tape is preferably done at constant torque, so that the tape tension decreases as the reel becomes larger. However, some compromise between constant torque and constant tension will usually give satisfactory results. Most of the tape recorder manufacturers, making equipment for high-fidelity use, have designed mechanisms to drive the tape at either the standard NAB¹ speed of 15" per second or the secondary speed of 7.5" per second, permitting flexibility of operation and maximum economy in use of tape.

On a magnetic recorder, the playback head must be very carefully aligned with the magnetic image produced by the record head to insure proper reproduction of the recorded signal. The recorded magnetic image on the tape must also be oriented exactly perpendicular to the direction

(Continued on page 31)

*From a paper presented at the NAB Broadcast Engineering Conference by Reynolds Marchant, development engineer of magnetic tape at Minnesota Mining and Manufacturing Co.

¹The NAB magnetic tape committee has recently recommended use of a standard hub for magnetic tape reels. Tape would be supplied by the tape manufacturer on this standard hub. A suitable flange, or flanges, can be attached to this hub to permit use of the tape on any professional recording equipment. Tape made on one recorder can thus be readily adapted to use on another type of machine with no necessity for rewinding the tape.

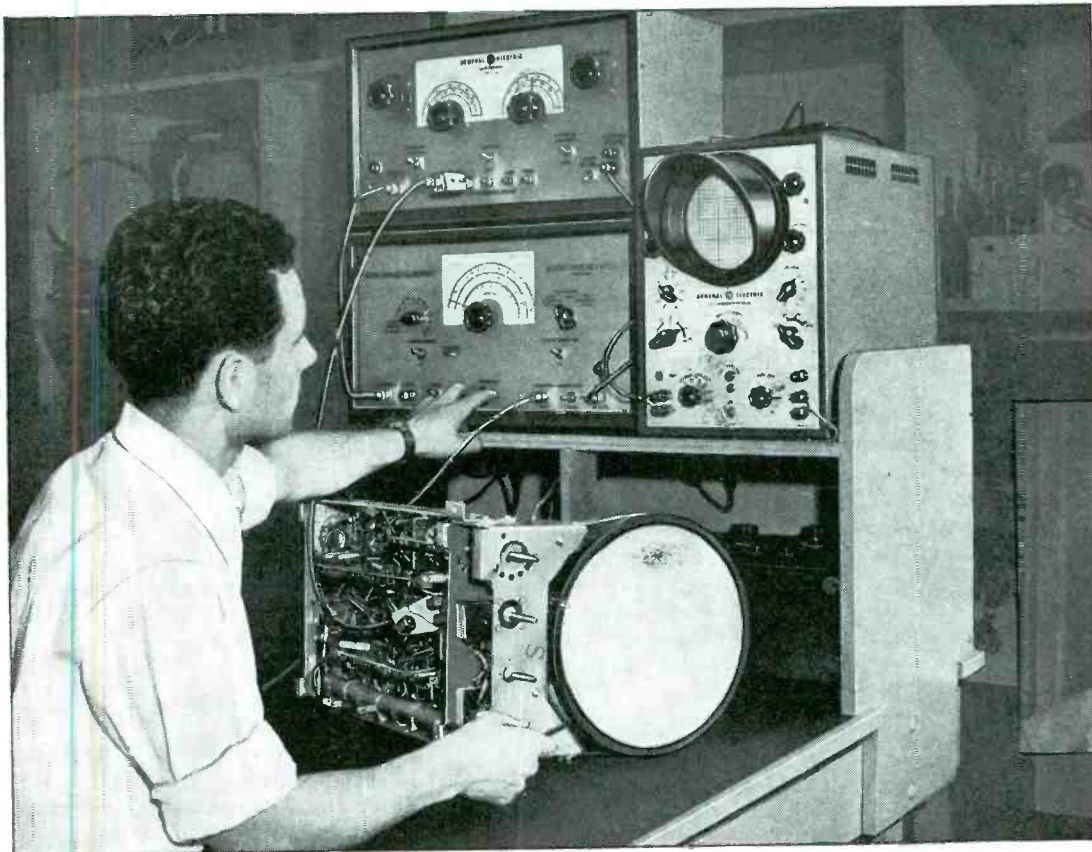

Says GENE ANTHONY
 Manager, Service Department
 General Electric Supply Corp.
 New York City



"MAKES TV SET ALIGNMENT EASY"

IN the biggest, fastest, toughest TV market in the world, TV set alignment is no longer a difficult, time-consuming job. Three new coordinated G-E test equipments now assure ease, speed, and accuracy in this work.

Says Gene Anthony, one of the best known service managers in New York: "The new G-E Test Equipment Package has improved our operation tremendously. Alignment work that used to require all the time of specialists

in our shop *is now performed with full confidence by any one of our men.* Operation and controls of the three instruments—Variable Permeability Sweep Generator, Crystal Controlled Marker Generator, and Cathode Ray Oscilloscope—are simple and easy to understand and can be taught quickly.

"With this equipment we do all kinds of TV service work—including mass alignments and the servicing of head ends as separate units."



General Electric Company
 Building 1, Room 1
 Electronics Park
 Syracuse, New York

Send me complete data on the new G-E Television Test Package.

NAME _____

ADDRESS _____

CITY _____ STATE _____

You can put your confidence in—
GENERAL  ELECTRIC

SER-CUITS

Analyses of the Admiral AM/FM Tuner and 16" Tube TV Chassis.

COMBINATION AM/FM/TV receivers appear to be gaining acceptance, particularly those with the large picture tubes. In Figs. 1 and 2 appear an excellent example of this type of set, which uses a 16" metal viewing tube.

In the *rf* tuner section of this model (Admiral 21A1 TV and 4K1 FM/AM tuner) balanced 300-ohm and unbalanced 75-ohm (coaxial line) input impedances are provided by a center-tapped primary winding L_{101A} . The secondary winding of this circuit is tuned by the input capacity of the 6AG5 input capacity in series with the parallel combination of a pair of 5 and .5 to 3 mmfd capacitors, C_{101} and C_{102} , the latter also being used for alignment. Loading of the secondary by a 3,900-ohm resistor, R_{101} , provides the required bandpass in this first tuned circuit.

The primary coil L_{102A} is the plate load of the *rf* amplifier. A trimer, C_{104} , and tube output capacity tune this coil. A 10,000-ohm damping resistor, R_{103} , provides the required bandpass.

Channel selection is accomplished by rotation of a turret assembly, a different set of coils (L_{101} and L_{102}) being switched in for each channel.

Mixer

Secondary coil L_{102B} feeds the *rf* and oscillator injection voltages to the grid of the mixer stage, one triode section of a 6J6. The secondary, L_{102B} , is tuned by the tube input capacity and .5 to 3 mmfd trimmer, C_{107} , also used for alignment adjustment. A 100-mmfd capacitor and two resistors, 4,700 and 220,000 ohms, (C_{106} , R_{105} and R_{106}), develop grid-leak bias for the mixer stage. The two resistors are used in this circuit in order that their junction can be brought out as an alignment test point. A scope can be connected to a test point without materially affecting the operation of the circuit.

The output of the mixer stage is coupled to a video amplifier by means of a network composed of a 10-mmfd capacitor, 22.3-mc iron-slug coil, 300-mmfd unit, 4.2 microhenry *rf* choke, another choke coil, and a 72-mmfd capacitor (C_{114} , L_{106} , C_{113} , L_{201} , L_{105} and

C_{116}). The remainder of the network comprises two tuned circuits and a trap. The plate of the mixer has the tuned circuit of L_{106} and C_{114} (in series with the trap, L_{105} and C_{113}) which with the tube output and distributed capacities are resonated to the video *if* band-pass. The tuned circuit to which this is coupled is composed of L_{201} and the input capacity of the first video *if* amplifier. Overcoupling of these two tuned circuits is provided by the mutual reactance of the trap circuit. C_{113} and L_{106} comprise a trap, tuned to approximately 17.5 mc, which performs the function of adjacent channel picture rejection.

HF Oscillator

In this circuit, using the other half of the 6J6, the oscillator coil L_{102C} is inductively coupled to a mixer grid coil, L_{102B} for oscillator injection to the mixer. A 10-mmfd capacitor, C_{108} , in series with a parallel 3-5 mmfd combination, C_{110} and C_{111} , form the split capacitor of a Colpitts oscillator. Variable-dielectric type capacitor C_{111} is the sharp tuning control.

Grid-leak bias for the oscillator is developed by a 10,000-ohm resistor and 20-mmfd capacitor, R_{107} and C_{108} . The oscillator plate is shunt-fed by means of a 4,700-ohm resistor, R_{108} .

Audio IF Amplifiers

Two high- μ sharp cut-off pentodes, 6AU6, are used in a two-stage *if* am-

plifier of conventional design. Cathode bias is used on both stages. The sound *if* signal is taken from a video sub-chassis by a 21.25-mc series-tuned circuit which is link-coupled to the plate coil of the first video *if* amplifier. (Early production video *if* sub-chassis employ two stages of amplification before the sound signal is applied to the grid of the first sound *if*.)

Ratio Detector

A 6AL5 ratio detector is used for FM sound detection. The network between point Z and ground (de-emphasis filter and volume control circuit) is the *af* output load circuit. A 330-mmfd capacitor (C_{206}) serves as an *if* bypass.


Ratio detector limiter action is provided by the filtering action of 4-mfd capacitor, C_{207} , which is effectively connected across the tuned secondary of T_{202} through the two diode sections of the 6AL5. This tends to hold the *if* signal amplitude at its average value and results in limiter action.


Since C_{207} charges to a value proportional to average *if* signal amplitude and then limits at that level, the circuit will adjust itself to any signal level. As a result, limiter action is effective on weak as well as strong signals.

Straight Television Model Audio Amplifiers

The television (only) audio amplifier system consists of a 6SQ7 voltage
(Continued on page 42)

Fig. 2. The second anode supply, deflection yoke and ac interlock circuit used in conjunction with the 16" type TV receiver.

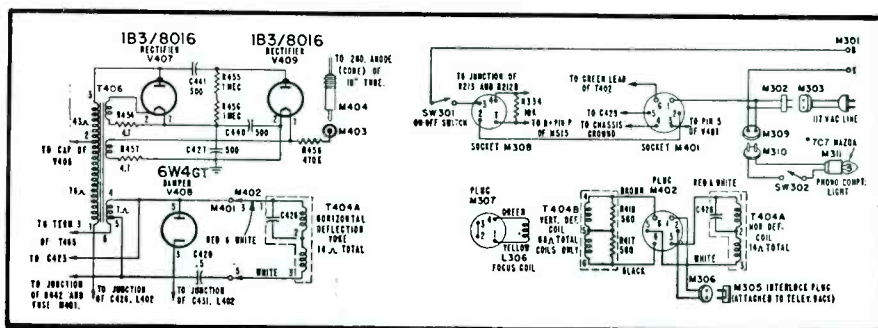

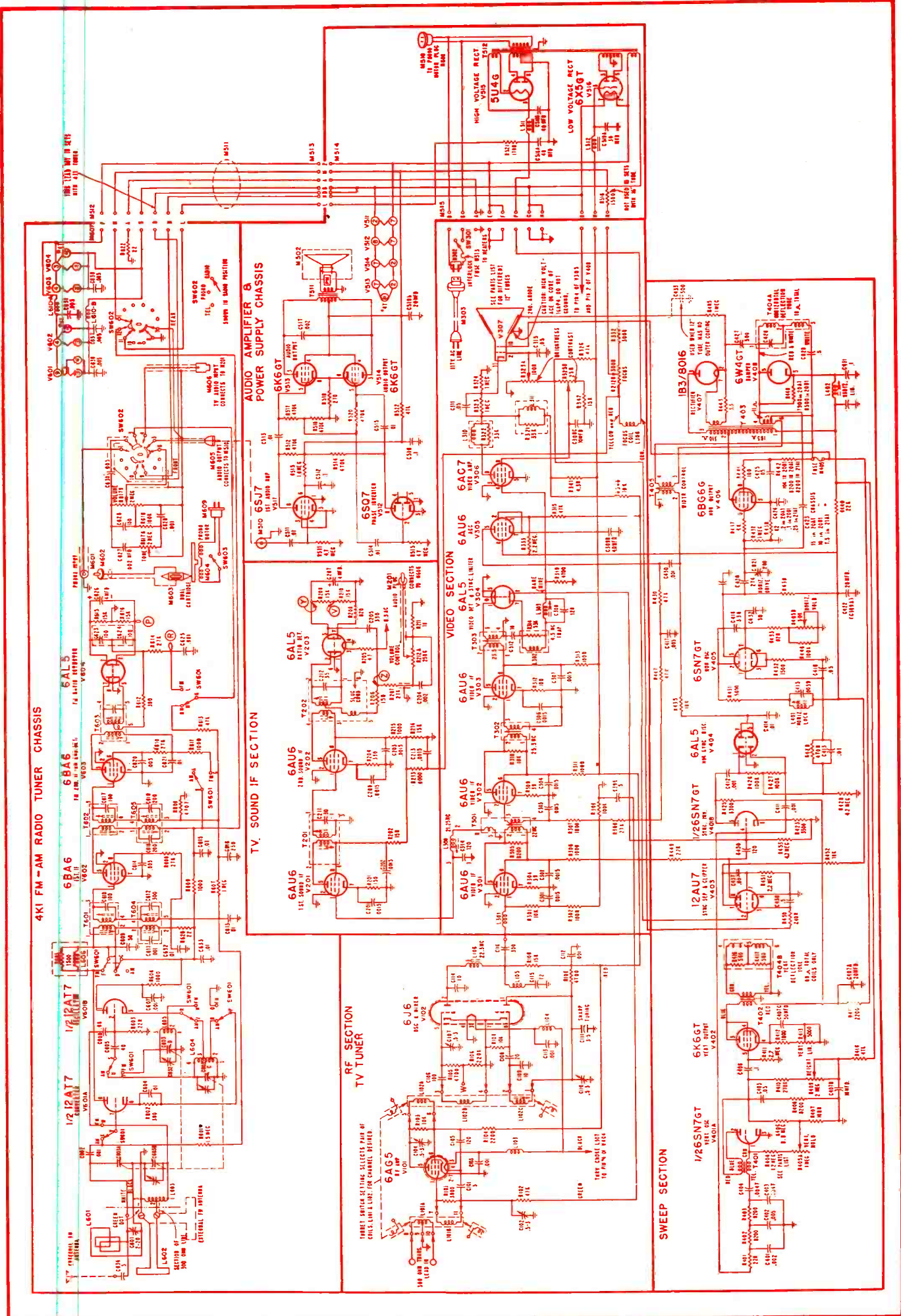

4K1 FM-AM RADIO TUNER CHASSIS

AUDIO AMPLIFIER & POWER SUPPLY CHASSIS

RF TUNER

TV SOUND IF SECTION

VIDEO SECTION

SWEEP SECTION

HIGH VOLTAGE RECT

LOW VOLTAGE RECT

Fig. 1. Schematic for the Admiral 4K1 AM/FM tuner and 21A1 TV chassis with a 12AU7 sync separator and clipper.

TV

Receiver Production Changes

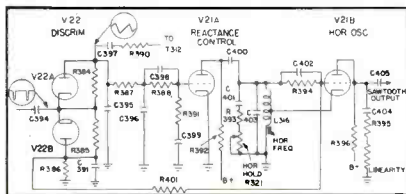


Fig. 1. The G. E. horizontal sweep generator and afc control circuit. (C398, C399, R388 and R391 constitute an anti-hunt circuit).

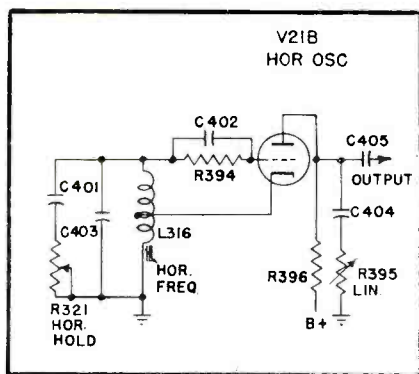


Fig. 2. Sweep generator circuit.


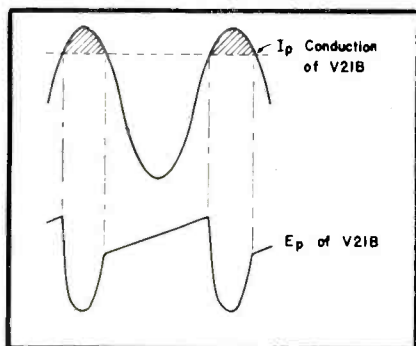


Fig. 3. Wave shapes which result when the capacitor charges exponentially during the time that the I_p of the sine wave oscillator is cut off and then discharged during the conduction period.

Fig. 4. Reactance tube circuit.

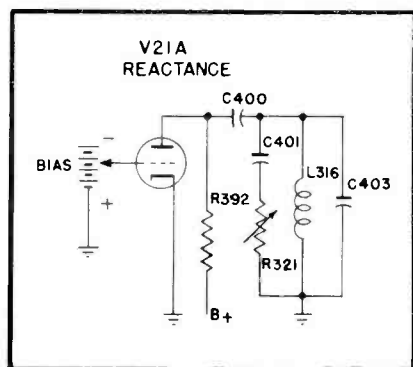

New Horizontal Sweep Generator and AFC Circuit For G. E. Receivers.

by DONALD PHILLIPS

SERVICE MEN will find in the newer G. E. TV models a horizontal sweep generator and afc circuit, known as the *Gruen sync*, which makes use of a sine-wave oscillator, V_{21B} , to generate a sweep waveshape. The sine-wave oscillator frequency is controlled by a reactance tube, V_{21A} , the plate resistance of which is determined by the bias applied to the grid of this tube. The bias voltage is derived from a discriminator circuit consisting of V_{22A} and V_{22B} , the function of which is to compare the phase between the incoming horizontal sync pulses and the output sawtooth wave. When they are at the same frequency and in phase, no correction voltage is generated, whereas if they are either leading or lagging, a correcting voltage is derived, the polarity of which is determined by the phase (lead or lag).

Sweep Oscillator

The sweep generator (Fig. 2) uses a triode which is connected as a grounded-plate Hartley oscillator.

L_{316} , with the capacitive element, C_{403} , form a tuned circuit resonating near the horizontal sweep frequency of 15,750 cps. This tank is shunted by a small capacitor, C_{401} , in series with a variable resistance, R_{321} (horizontal hold control), so that the frequency of this oscillator may be manually controlled about a mean frequency value. The oscillation voltage on the positive half cycle drives the sine-wave oscillator into grid current which causes a bias to be established across C_{402} and R_{394} of such a magnitude that plate current flows for only a small portion of the cycle. The oscillator may be termed class C as far as plate current flow is concerned.

In the plate circuit, therefore, if a large resistor, R_{396} , is connected to $B+$

and a capacitor, C_{401} , is connected at the plate of V_{21B} , the capacitor may be made to charge exponentially during the time that the I_p of the sine-wave tube is cut off and then discharged during the conduction period; Fig. 3. A resistor, R_{395} , is placed in series with the capacitor, C_{404} , so as to modify the sawtooth waveshape to give it a peaking voltage at the start of the trace. The value of the resistance determines the extent of peaking. It is usually made variable in the receiver and called a *peaking control*. The degree of peaking influences both the linearity and high voltage available from the horizontal output stage.


Reactance Tube

Across the sine-wave oscillator circuit linked through a capacitor, C_{400} , is the reactance tube, so identified because it effectively changes the capacitive reactance across the tuned circuit as the bias on this tube is changed.


When the tube is highly conductive, as would be the case when the bias voltage applied to the grid is low, then the tube plate resistance is low and the capacitor in series with this relatively low resistance has an appreciable reactive effect across the tank circuit, resulting in a lower frequency of oscillation. As the bias is made more negative, the tube plate resistance rises, causing the linking capacitor to have less shunting effect across the tank circuit. This results in a rise in frequency. It will be seen that the frequency of the sine-wave oscillator, and thereby the sweep voltage output, may be controlled by the change in grid bias voltage on this tube.

This circuit is operated at all times with an initial negative bias. The

(Continued on page 33)

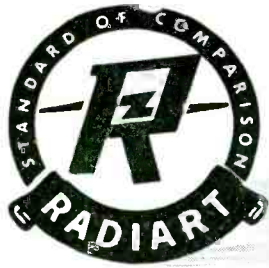

Radiart
features

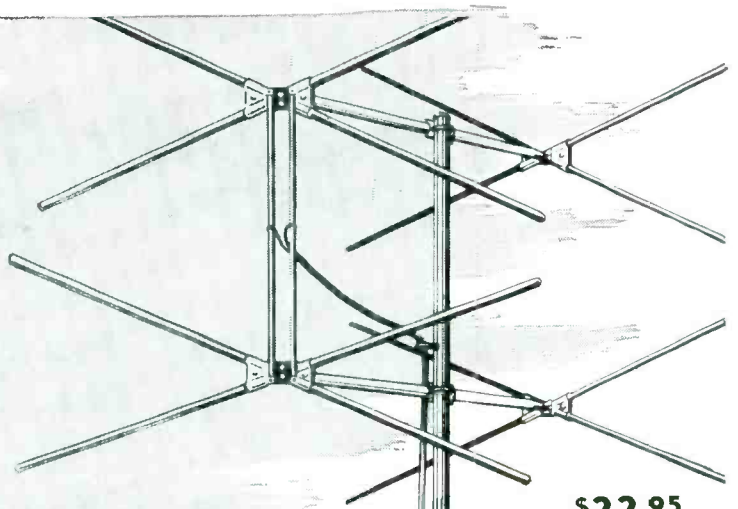


\$22.95
List

THE DOUBLE STACKED "LAZY X" ARRAY . . .
for improved gain in low signal strength areas — also where a higher signal-to-noise ratio is desired . . . Model LZX-2

THE
Lowest Priced Quality Line


OF TV CONICAL ANTENNAS

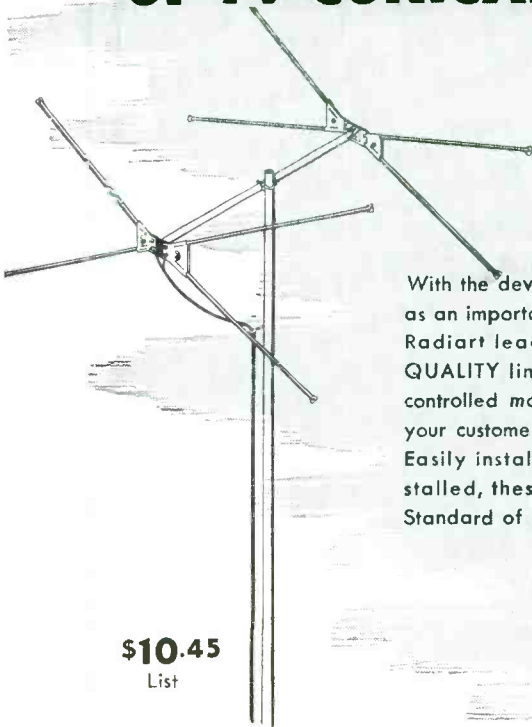

\$10.45
List

THE SINGLE BAY "LAZY X"
... for primary service areas
..... Model LZX

With the development of the conical type antenna as an important factor in television reception . . . Radiart leads the way with the lowest priced **QUALITY** line. Precision engineering . . . quality controlled manufacture combine to give you and your customer's the greatest value for the dollar! Easily installed . . . and rigidly sturdy when installed, these Radiart products truly are "The Standard of Comparison."

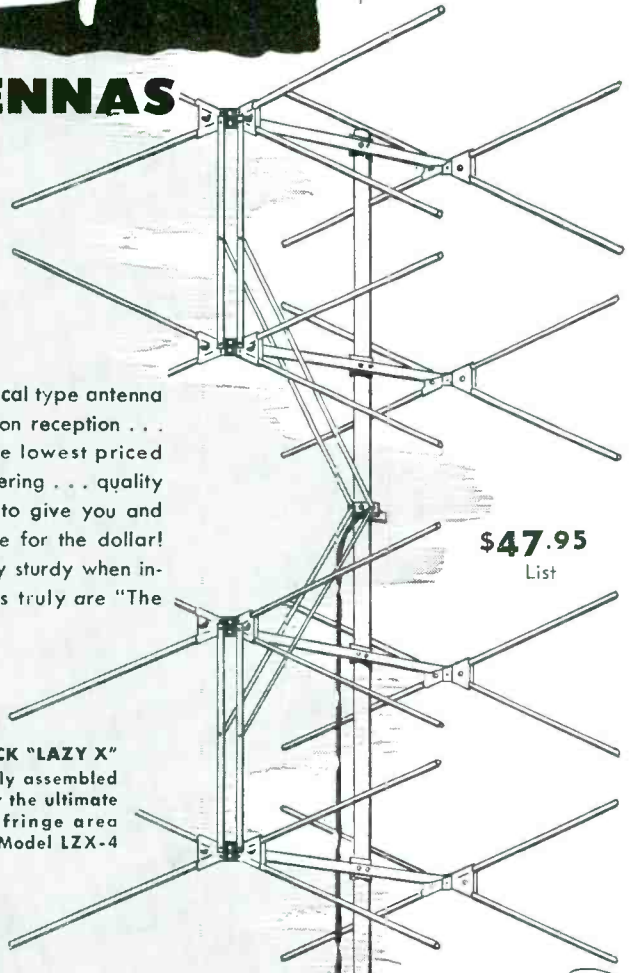

\$47.95
List

The QUAD-STACK "LAZY X" Array . . . easily assembled and installed for the ultimate in all channel fringe area reception Model LZX-4

DEALERS:

For Special "Quantity Prices" . . . See Your Radiart Dealer About These **BULK PACKED** Models:

- Model LZX-6B — six unassembled LZX bays in one carton.
- Model LZX-6BQ — same as above PLUS 3 pairs jumper bars

... a good **DEAL** — more for your money.



IT'S RIGHT WHEN IT'S RADIART!

THE RADIART CORPORATION
CLEVELAND 2, OHIO

Manufacturers of the Famous Red Seal Vibrators



Servicing Helps

Application of Picture Width-Control Circuits. Eliminating Sync Troubles, Black Line-White Line Problems and Tuning Drift in TV Models.

by M. A. MARWELL

ONE OF the particularly interesting circuits in the TV receiver is the picture-width control arrangement. With novel circuitry, the picture can be made to horizontally fill out the entire mask of the picture tube.

In the early models, such as the Philco 48-700, the gain of the horizontal-sweep-output tube was varied by adjusting a variable resistor in the cathode of that circuit (Fig. 1), thus changing the amplitude of the sawtooth voltage.

In the larger sets, using electromagnetic deflection, the width control had to be designed somewhat differently. Since the high voltage is also derived from the horizontal output amplifier, the tube gain cannot be varied to control the width, as it will affect the high voltage.

For instance, the Philco 48-1000 and similar chassis, featured a width control consisting of a pair of inductances with an adjustable powdered iron core; Fig. 2. To obtain a larger picture horizontally, it is necessary to have a means of increasing the amount of current fed into the horizontal deflection coils; to obtain a smaller picture, this current must be decreased. As the slug is varied, the inductance of coils L_1 and L_2 vary inversely. This is due to the physical location of the coils with respect to the position of the slug.

With the width control turned out counterclockwise, the slug will be cen-

tered in coil L_1 , causing a greater inductive reactance, and, consequently, an increased opposition to the flow of current in the deflection coils. Since the slug is out of L_2 the reactance of the coil is lowered, and, since this coil is in parallel with the horizontal deflection coil, more current is shunted away from the deflection coils, resulting in a smaller picture. When the iron slug is turned clockwise, so that it is centered in L_2 , the reactance of the coil increases, while the reactance of L_1 decreases, resulting in a larger picture.

In the Philco models 49-1040 and similar chassis, a more versatile control (Fig. 3) has been included and can be used to replace the older type control.

The arrangement of the coils is somewhat like the 48-1000, except that there is a link switching arrangement available, to short out portions of coils L_1 and L_2 . With the link in the upper position, part of coil L_1 is shorted out, decreasing the reactance of that coil, and allowing more current to flow to the parallel network of L_2 and the deflection coil. Since the full amount of L_2 is in the circuit, the reactance of that coil is greater, causing most of the available current to flow through the deflection coils, thus increasing the width. With the link in the lower position, part of coil L_2 is shorted out,

decreasing its reactance, and the entire length of L_1 is back in the circuit. The increased reactance of L_1 opposes the flow of current to the network of L_2 and the deflection circuit, cutting down the size of the picture. By combining the use of the link and the adjustable core, a much greater control of width may be obtained.

TV Tuning Drift Problems


A common cause of tuning drift in early Philco models was the discriminator transformer. This drift was severe only in the first few thousand sets with capacitor-tuned transformers.

Discriminator transformers¹ using inductive tuning were found to be the solution.

The major part of the tuning drift in the early models was traced to the heterodyne oscillator. To offset the oscillator drift, it was found necessary to change the 10-mmfd capacitor, from the grid to the oscillator to ground, to a temperature compensating type, and install an inductive tuning discriminator transformer. Otherwise, the short-time tuning drift becomes a problem since the compensation introduced by the capacitor will be in the direction opposite to the drift in the earlier type transformers. Severe cases of tuning drift warrant changing to these new

(Continued on page 29)

Fig. 2. Another type of width-control circuit used in the Philco model 48-1000. T_1 is the horizontal output transformer and L_1 and L_2 are the width coils.

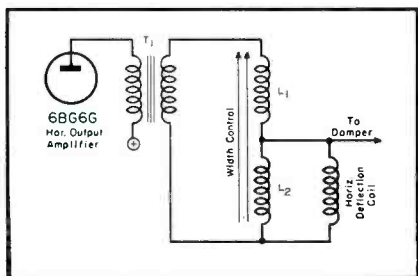

¹Philco 34-4317.

Fig. 1. A width-control circuit used in Philco model 48-700.



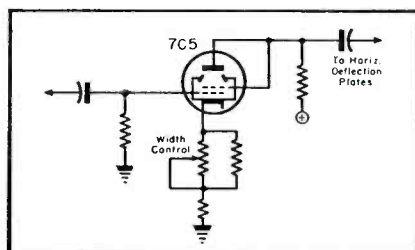


Fig. 3. A third type of width-control circuit, featured in the Philco model 49-1040. T_1 is a horizontal output transformer, L_1 and L_2 are the width coils and S_1 is an adjustable link which is used to short out portions of the L_1 and L_2 coils and thus control the reactance of the coil.

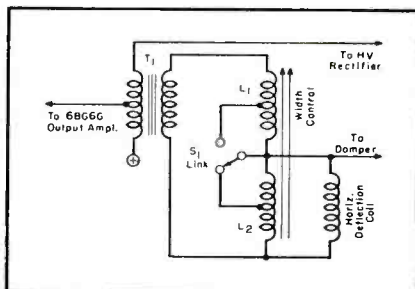


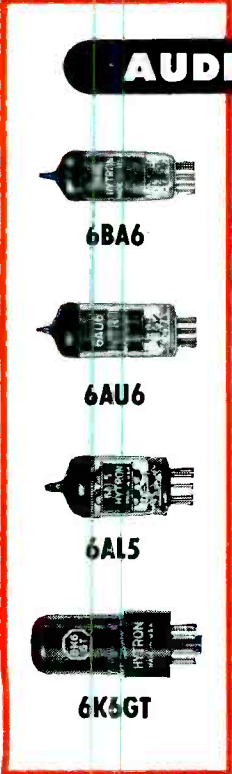

VIDEO



AUDIO

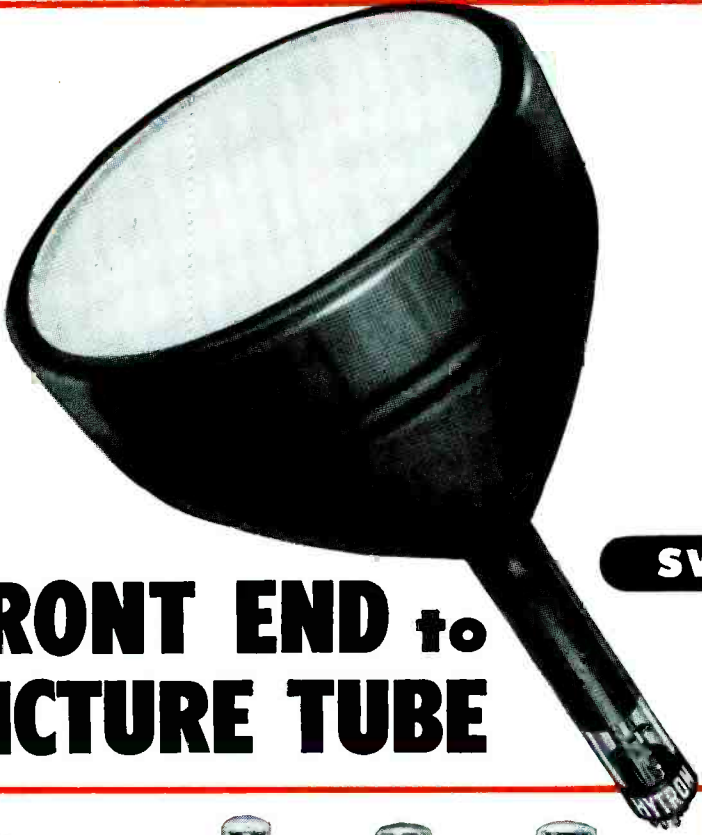

FRONT END to PICTURE TUBE



SWEEP



POWER

HYTRON GIVES YOU!

- ★ All the popular TV types.
- ★ Premium TV quality—at no extra cost.
- ★ The same Hytron quality bought by 25 leading TV set manufacturers.




HYTRON SERVES THE SERVICEMAN

| | | | | |
|--------------------|-------------------------------------|-------------------------------------|----------------------|---------------------|
| TUBE TAPPER 5¢ | 7-PIN MINIATURE STRAIGHTENER 55¢ | 9-PIN MINIATURE STRAIGHTENER 55¢ | SOLDERING AID 49¢ | TUBE LIFTER 15¢ |
| HYTRON TUBE LIFTER | | HYTRON SOLDER AID | | AUTO RADIO TOOL 24¢ |


Already Six Tools Available From Hytron Jobbers. Watch For More!

Alliance TENNA-ROTOR Sells with Television!

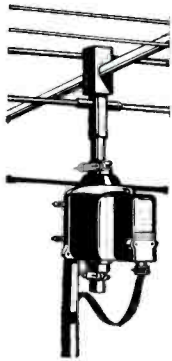1,500,000 Demonstrations!
4,500,000 Viewers!
40 TV Stations
EACH WEEK!



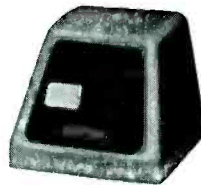● Compelling one-minute television films are doing a big selling job on the Alliance Tenna-Rotor! Viewers actually see how Tenna-Rotor makes a cloudy image come up sharp and clear. Every TV set owner wants to reach out—overcome interference—get more stations! Alliance films are timed with top programs to deliver a maximum TV audience!



CHECK YOUR STATION HERE!

| | | | | |
|--------------------------------|------------------------------|-----------------------------------|------------------------------|-------------------------------------|
| Atlanta WAGA-TV WSB-TV | Cleveland WEWS WNBK | Houston KLEE-TV | Newark WATV | Richmond WTVR-TV |
| Baltimore WBAL WMAR-TV | Columbus WLW-C | Indianapolis WFBM-TV | New Haven WNHC | Rochester WHAM-TV |
| Boston WNAC | Dallas KBTW | Johnstown WJAC-TV | New York WNBT | St. Louis KSD-TV |
| Buffalo WBEN-TV | Dayton WLW-D | Lancaster WGAL | Philadelphia WCAU WPTZ | Toledo WSPD-TV |
| Chicago WBQ WBKB | Detroit WJBK-TV WWJ-TV | Los Angeles KFI-TV | Pittsburgh WDTV | Washington, D.C. WMAL-TV WNBW |
| Cincinnati WKRC-TV WLW-T | Erie WICU | Minneapolis KSTP-TV WTCN-TV | Providence WJAR | Wilmington WDEL-TV |

The trend is to Tenna-Rotor. Tie in with this television advertising now!
Alliance Tenna-Rotor Comes with a One Year Guarantee!

ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO

Export Department: 401 Broadway, New York, N. Y., U. S. A.

Keyed AGC

(Continued from page 14)

found to add to the adjacent channel rejection qualities of the set.

Sound Section

Three stages of sound *if* amplification are used in the receiver. The last sound *if* stage with a 6AU6 sharp cut-off pentode, acts as a limiter to remove amplitude modulation from the FM sound signal. As diode and audio driver amplifier the model uses the

9-pin miniature 6T8 which has been found to provide the same performance as the conventional 6AL5 diode and 6AT6 triode. A single 6K6 acts as audio output tube.

Picture Amplifier

The picture amplifier section consists of a 6AC7 pentode directly coupled to the second detector and to the picture tube, thus eliminating the need for a *dc* restorer. Because of the requirements of the keyed *agc* system, the picture signal at the plate of the 6AC7 must have positive polarity.

Thus the sync pulses must go in a positive direction. A positive polarity signal must be applied to the cathode of the picture tube to cut off the electron beam during the retrace time. The grid of the picture tube is kept at a *dc* potential which is varied by a *brightness* control. Adjustment of this control sets the bias of the picture tube and therefore regulates the electron beam current and thus the brightness of the picture.

To vary the gain of the picture amplifier the screen of this tube is connected to a voltage divider consisting of R_{147} and the *contrast* control, R_{151} . Changing the screen voltage changes the plate current of the 6AC7 and therefore the amplitude of the picture signal. The range of the *contrast* control is so designed that it permits no overload and does not cut off the signal entirely.

The frequency response of this picture amplifier has been adjusted so as to give a flat curve with 4 mc at the half power point. The plate load resistance, a total of 5,100 ohms, has been split up into a pair of 3,300-ohm (R_{149}) and 1,800-ohm (R_{141}) resistors to provide a sync pulse source for the keyed *agc* circuit.

Sweep Circuits

The horizontal and vertical sweep circuits feature a 12AU7 dual triode which serves as clipper and phase inverter. The phase inverter section produces horizontal sync pulses of equal amplitude but opposite polarity, which are then coupled to a 6AL5 phase discriminator. A feedback sawtooth voltage is obtained from the *agc* winding on the width control and fed through R_{151} and C_{115} to the phase discriminator. This tube compares the phase and frequency of the sync pulse and the horizontal oscillator and generates a *dc* voltage which controls the bias and therefore the frequency of the horizontal oscillator.

The horizontal oscillator is one-half of a 6SN7 dual triode, and contains an LC tank circuit together with a resistance R_{109} , which results in a combination sine and square wave. The second section of this tube acts as a discharge tube and forms a sawtooth voltage which drives a 6BG6 horizontal output amplifier.

The vertical sweep circuits employ a single 6SN7 dual triode as blocking oscillator and output tube. Vertical sync pulses are obtained from the plate of a 12AU7 phase splitter and pass through an integrating network (R_{156} , R_{100} , C_{101} , C_{102} , and C_{103}).

Performance Diagnosis

(Continued from page 16)

operating points for the 750-ohm cathode bias resistor. This can be done by taking a few values of bias and finding the values of plate current which produce this value of bias with a 750-ohm cathode resistor; this is plotted on the proper bias curve.

$$\text{Point A } I = \frac{-E_c}{R} = \frac{40}{750} = 53 \text{ ma}$$

$$\text{Point B } I = \frac{-E_c}{R} = \frac{60}{750} = 80 \text{ ma}$$

(3) A line is then drawn between these points. Where this line crosses vertical plate voltage we have the operating point. This point, I_o , is at -45 volts E_c , 250 volts E_p , and 60 ma I_o . To check this point we multiply 60 ma times 750 ohms and our answer is 45 volts bias.

(4) To obtain additional information a load line is drawn through the operating point with a slope of 1,750 ohms. Conventional load line procedure is used to do this. Since two points determine a straight line and one point is the operating point, a second point is obtained by assuming a plate voltage change. In the interest of simplicity this change was taken to be 250 volts to bring us down to the plate current axis.

$$\text{Point Y } \Delta I = \frac{\Delta E}{R} = \frac{250}{1750} = 142 \text{ ma}$$

$$+ 60 \text{ ma } I_o = 202 \text{ ma}$$

Thus loadline crosses plate current axis at 202 ma, which along with operating point permits plotting of load line YY' .

(5) Other information can be found using conventional formulas and procedures. Suppose we assume a 5-volt peak grid signal.

Power output

$$\frac{(E_{\max} - E_{\min})(I_{\max} - I_{\min})}{8}$$

$$= \frac{(345 - 108)(142 - 6)}{8} = 4 \text{ watts}$$

$$\text{Voltage gain} = \frac{237}{90} = 2.6$$

Per cent second harmonic distortion

$$\frac{I_{\max} + I_{\min} - I_o}{2} = \frac{142 + 6}{2} - 60$$

$$= \frac{I_{\max} - I_{\min}}{142 - 6} = 10\%$$

Consideration of Transformer Resistance

If a high static current is drawn and transformer winding has an appreci-

(Continued on page 28)

DUMONT presents...

NEW STANDARDS OF PERFORMANCE

with increased
VERSATILITY



TYPE 304-H
5" CATHODE-RAY

OSCILLOGRAPH

Cathode-ray Tube: Type SCP-A operated at overall accelerating potential of 3000 v. in Type 304-H; 1780 v. in Type 304. With this exception, both types are identical.

High-gain a-c and d-c Amplifiers: Sensitivity of 10 millivolts rms/in. for Y axis; 50 millivolts rms/in. for X axis.

Frequency Response: d-c amplifiers uniform within 10% to 100,000 cps.; a-c amplifiers uniform within 10% from 20 to 100,000 cps.; Amplifiers recover instantaneously after overloads at high gain.

Expansion of Detail: Over four times full screen deflection available on both X- and Y-axes, equaling visibility of 20" tube yet with high resolution of 5" tube.

Recurrent and Driven Sweeps: Variable from 2 to 30,000 cps. Sweep speeds faster than 1 in./microsecond; slower than 10 seconds using external capacitors at front panel.

Intensity Modulation: 15 v. peak blanks trace at normal intensity.

Size: 13 1/4" h.; 8 3/8" w.; 19" d.
Weight: 50 lbs.

Additional Features: Permanently mounted calibrated scale for precise measurements. Mu metal magnetic shield for cathode-ray tube. Du Mont Type 2501 Bezel for quick attachment of accessories.

PRICE: TYPE 304-H, \$307.50
TYPE 304, \$285.00

with increased
PORTABILITY



TYPE 292
3" CATHODE-RAY

OSCILLOGRAPH

Cathode-ray Tube: Extremely short length of new Du Mont Type 3RP-A contributes to portability. Overall accelerating potential, 1000 v. Flat face minimizes optical distortion.

Sensitivity: Y-Axis amplifier at full gain, 0.4 rms volt/in.; direct to deflection plates, 22 rms volt/in.; X-Axis amplifier at full gain, 0.56 rms volt/in.; direct to deflection plates, 31 rms volt/in.

Frequency Response: Both horizontal and vertical amplifiers uniform within 30% from 5 to 100,000 cps.

Balanced Deflection: Deflection amplifiers provide voltages 180° out of phase, eliminating astigmatic defocusing of trace.

Linear Time-Base: Gas-triode sweep-frequency output variable from 8 to 30,000 cps. Automatic beam-blanking on return trace.

Size: 10 7/8" h.; 8 1/8" w.; 11" d.
Weight: 21 lbs.

Additional Features: Test signal of 6.3 volts peak at line frequency available at front panel. Calibrated scale for quantitative measurements. Magnetic shield protects cathode-ray tube. Sturdy steel cabinet finished in durable gray wrinkle.

PRICE: TYPE 292, \$124.50

DUMONT for Oscillography

ALLEN B. DU MONT LABORATORIES, INC. • INSTRUMENT DIVISION • CLIFTON, N. J.

JACKSON

Announces a Sensational, New 5 Inch Oscilloscope



Band Width to 4.5 megacycles! High Sensitivity of .018 volts-per-in.

Now, for the first time—thanks to an amazing electronic discovery—Jackson has combined in one oscilloscope both wide band width and High deflection sensitivity. By merely flipping a switch you can choose from one of three sensitivity ranges, or one of three other band width ranges. Here is a fine instrument, perfectly suitable for laboratory analysis, yet well within the price range of the average radio serviceman.

The new Jackson Model CRO-1 is in production right now! It is priced at only \$195.00 net. A special high-frequency signal tracing demodulation probe is also available at \$9.95. Get your order in today!

Just look at these Features

Wide Band Amplifier: Easily usable to a full 5 megacycles. Flat within plus or minus 1.5 db. from 20 cycles to 4 megacycles.

Deflection Sensitivity: Vertical amplifier, .018 RMS volts-per-inch on narrow band. Horizontal amplifier .55 RMS volts-per-inch.

Input Impedance: Direct balanced, 6 megohms shunted by 11 uufd; unbalanced 3 megohms shunted by 22 uufd. Horizontal amplifier 1.5 megohms.

Sweep Frequencies: Saw tooth wave, 20

cycles to 50 kilocycles in 5 steps.

Special Features: All controls on front panel. Provision for 60 cycles or external sweep. Also has provision for grid modulation at 60 cycles or with external voltage. Full 5-inch CRT. Same height as new Jackson TVG-1 TV Sweep Generator. Rear terminal strips for direct connection, through capacitors, for A.C. voltages to CRT deflection plates. Light weight, easy to carry. Provided with leather carrying handle. Attractive all steel cabinet with gray Ham-R-Tex finish.

JACKSON

Service-Engineered
Test Equipment

Dynamic Tube Testers • RF Oscillators •
Vacuum-Tube Voltmeters • TV Sweep Generators • AM-FM Sweep Generators • Condenser Checkers • Audio Generators • Oscilloscopes.

Jackson Electrical Instrument Company • Dayton 1, Ohio

(Continued from page 27)

able resistance it must be considered in locating the operating point. For example, if the circuit of Fig. 1a has a winding resistance of 250 ohms, the plate voltage line cannot be drawn vertically, but with a slope of 250 ohms, Fig. 2b. This is apparent when we consider that the only time it could be possible to apply 250 volts to the plate would be when plate current is zero. Plate voltage due to winding resistance becomes progressively less,

with an increase in plate current. The actual decline is a function of a line with a slope of 250 ohms on the curve. One point is known as 250 volts on the plate voltage axis and the second point can be obtained by assuming a plate voltage change again.

$$\text{Point A } \Delta I = \frac{\Delta E_p}{R_w} = \frac{25}{250} = 100 \text{ ma}$$

The corrected operating point can be located at a point where plate voltage line *AB* crosses the bias line; Fig. 2b. Thus at this new operating point

P' all parameters, $-E_c$, E_p , and I_o , are a bit less.

Resistor Plate Load

In the *b* circuit of Fig. 1 the total resistance in plate-cathode-circuit is 2,500 ohms and therefore this total resistance must be considered in drawing the dynamic load line because of its effect on the *dc* component of plate voltage. In this circuit our first task also is to find the operating point:

(1) A plate load line of 2,500 ohms is drawn first. In the case of a resistor load, one point of the load line will always be the supply voltage at zero plate current, because the only time 400 volts could be applied to the plate would be with no drop in the load or zero plate current. This differs, of course, from the first example because, with a reflected load the operating plate voltage is the supply voltage and during an *ac* cycle the plate voltage swings above this value on positive alternation. With the resistor load this never occurs and operating plate voltage is always less than supply voltage by drop in load. To proceed, with one point located at plate supply voltage, a second is obtained by assuming a plate-voltage change. An assumed 400-volt change would locate the point on the

400 v
plate current axis at $\frac{400 \text{ v}}{2,500 \text{ ohms}} = 160$

ma; line *XX'* should be drawn.

ma; line *XX'* should be drawn.

(2) A loci of operating points is next to be drawn, as per first example, line *AB*.

(3) Operating point is again at same position as per first example. It will be noted, however, that the plate supply voltage is considerably higher to obtain same operating point; *dc* drop across plate load resistor.

(4) Although the operating point has been found and a load line drawn, it is not the true output load line because the cathode resistance is present in it. The true dynamic load line is now drawn with a slope of 1,750 ohms, the operating point serving as one point already located. This true load line of course could not have been drawn without first locating the operating point to represent one point on its slope.

(5) The true load line with a slope of 1,750 ohms is the same as the line *YY'* drawn for the first example. Operation is quite similar except for higher supply voltage.

(6) If the supply voltage had been left at the same value as in the first circuit, this voltage of 250 would be

the supply voltage, and in case of the resistor load would be on the plate voltage axis, as shown in Fig. 2b. This would, therefore, locate one point on the load line and the second can be found by assuming a plate voltage change. We thus have a new operating point P'' (where the new load line BB' crosses bias line), which is at a considerably lower plate voltage and bias point.

Consideration of Decoupling Circuit

In circuit c of Fig. 1, the supply voltage is fed through a decoupling circuit to the stage and therefore it must be considered, because of the influence it exerts on plate voltage, as a function of dc component of plate current. The procedure for locating the operating point is as follows:

(1) The total plate-cathode resistance to supply point is again 2,500 ohms and, therefore, it must again be used to draw the first load line which locates operating point. This is again line XX' .

(2) The bias line AB is again necessary. Intersection of AB and XX' locates the operating point.

(3) The true operating output load line must now be drawn because only across the 1,250-ohm plate-load resistor is there an ac output variation. A constant dc component of voltage exists across the cathode and decoupling resistors. The true load line is drawn with a slope of 1,250 and the operating point serves as one point on its slope.

(4) From this line, output, distortion, etc., can be ascertained.

Servicing Helps

(Continued from page 24)


parts. As a further step to improve oscillator stability the grids of the 6J6 were silver-plated to eliminate those cases where the oscillator ran away due to grid emission in the tube.

To compensate for the effects of tuning drift, Philco has a *channel adjuster* or *diadler* kit. The *channel adjuster* provides for manual control of the control voltage to the reactance tube in the oscillator circuit without completely disconnecting the *afc* system. It is thus possible to retune the oscillator manually when the signal is too weak to operate the *afc* system or when tuning drift causes the set to lose sound.

Increased correction range in the reactance tube has been obtained by changing the neutralizing capacitor between the grid of the reactance tube

(Continued on page 30)

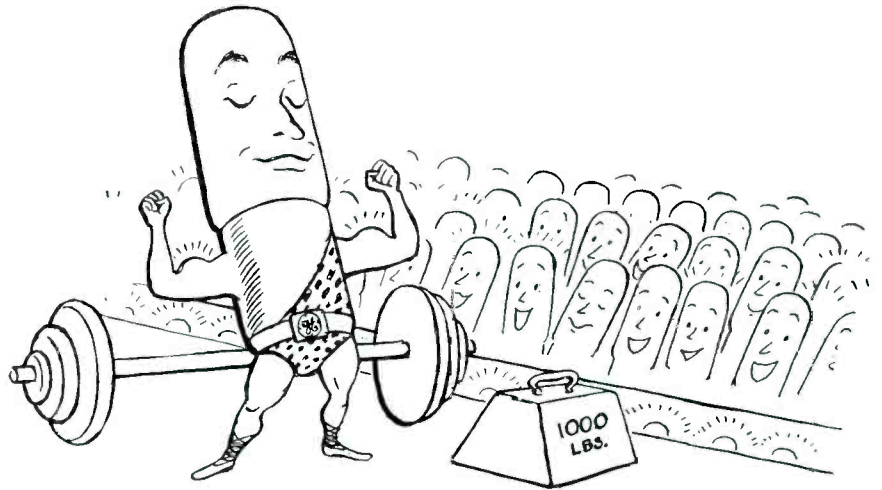
The little lamp that became the strong, silent type



LIGHTING radio dials is no job for a "weaking" lamp. Testing many old style lamps, General Electric engineers found that certain frequencies caused severe vibration that often tore the filament apart. Poor contact between the filament legs and lead-in wires also resulted in tiny arcs or changes in resistance that caused radio interference.

That's why G-E dial lamps have been made "the strong, silent type." Improved design minimizes vibration, provides positive connection between the filament and lead-in wires.

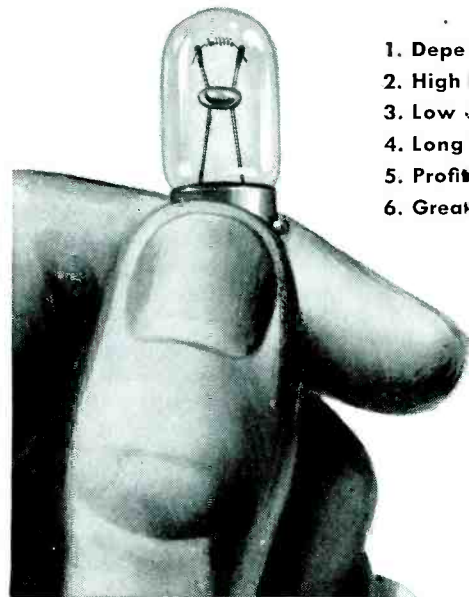For information on prices and types of G-E miniature lamps, call your nearby G-E Lamp office. Or write to General Electric Co., Division 166-S 11-49, Nela Park, Cleveland 12, O.



1. Dependable, trouble-free performance.
2. High level of maintained light output.
3. Low current consumption.
4. Long life.
5. Profitable to handle.
6. Greater dealer acceptance.



You can put your confidence in—

GENERAL  ELECTRIC

Everybody agrees
ATR VIBRATORS
 are **TOPS!**

ATR



AUTO RADIO VIBRATORS
 have Ceramic Stack Spacers



A COMPLETE LINE OF VIBRATORS...

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing.

ATR PIONEERED IN THE VIBRATOR FIELD.

NEW VIBRATOR GUIDE FREE



ATR

"A" BATTERY ELIMINATORS

for DEMONSTRATING AND TESTING AUTO RADIOS

New Models... Designed for testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

NEW MODELS NEW DESIGNS
 NEW LITERATURE

ATR "A" Battery Eliminator, DC-AC Inverter, Auto Radio Vibrators

See your jobber or write factory

AMERICAN TELEVISION & RADIO Co.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA-U. S. A.

(Continued from page 29)

and the grid of the oscillator from 3.3 to 2.2 mmfd, and thus increasing the reactance variation available. The increased range allows *afc* to operate over a greater range of oscillator drift.

Sync Trouble†

Many service problems are the result of operating on weak signals. Sync troubles are especially prominent in the list of problems due to weak signals, but the other extreme is also undesirable. Locations very close to television transmitters may also have sync troubles.


Sync troubles near the transmitter usually fall into two general classifications; first, troubles due to multiple path reception, and second, troubles due to overload in the receiver. Troubles due to multiple path reception do not submit to any cut and dried procedure, although in most cases the chief repair is attenuation of the signal. In high signal locations antenna and lead-in combinations or locations may result in sync trouble. Attenuation of the signal by cutting one side of the antenna coil or installation of a pad often works. In some cases rerunning of the lead-in or use of a shielded lead-in becomes necessary.

The second cause of sync trouble on strong signals is much more common. As in the first case, attenuation of the signal often clears the trouble but this kind of repair sometimes does not produce a picture with satisfactory contrast or may cause too much *snow*. Overload on strong signals can be caused by excessive leakage in the *agc* line bypass. This circuit uses large capacity electrolytics to obtain the desired filtering for the system using resistors which are limited in value by other circuit considerations. What would be considered a very negligible leakage in any other circuit cannot be tolerated in the *agc* circuit if a strong signal is applied at the antenna. Capacitors for use in this circuit must have a leakage resistance of more than 500,000 ohms when measured with a meter having approximately 10 volts or less in the ohmmeter circuit.

There are often cases where there is no *agc* circuit leakage and no other fault, and yet sync trouble exists. A number of such cases have been reported with the Philco 1040, code 121. However, since provision has been made in the set to switch to manual gain control which permitted increasing bias on the *if* amplifiers to overcome the overload conditions which caused sync clipping or video feed-through the trouble is not serious. If desired, sync clipping on strong sig-

†From Philco service notes.

Pat. Pend.

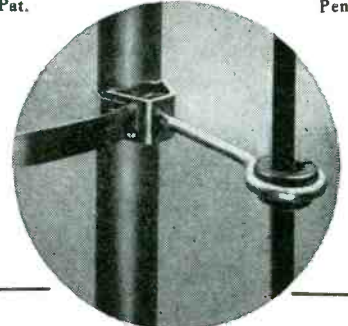

NOW! NEW LOW PRICE FOR PHOENIX PAM-11

.. Fastest, Strongest Antenna Mast Stand-Off Insulator

- Attaches to any size mast in 10 seconds!
- Genuine Polyethylene parts.

19c list

PHOENIX ELECTRONICS, INC.
 Lawrence, Mass.

AT LEADING JOBBERS
 Write for folder M of complete line of television accessories.

THE REDSKINS ARE COMING!

nals can be eliminated in this chassis, even in automatic gain operation, by moving the sync take-off point back to the detector. To avoid loading the detector, a 10,000-ohm isolation resistor should be connected from the detector output to the sync amplifier. This method is recommended only if all stations give enough signal to sync properly with the new take-off point.

Black Line—White Line Trouble

A problem of long standing in TV servicing is the *black line* and *white line* trouble. The trouble appears as one or more black or white vertical lines in the picture. It is most common on weak signals and on the higher channels but can also appear on the low channels. The cause is well established as being due to spurious oscillations in the 6BG6 tube.

Recently with the introduction of built-in antennas the problem received additional attention because it became more serious when the antenna was placed inside the receiver cabinet. Investigation indicated that in most cases the oscillation took place at the end of the return trace and that the time delay in passing through the receiver made the lines appear within the raster. A method has been devised for minimizing the spurious oscillations during the return trace by coupling opposing voltages in the output system to suppress oscillations.

This circuit is used in the Philco 50-T1400 and other models in this series. A 250-microhenry choke has been inserted in series with the 6BG6 screen, and the screen then coupled to terminal 5 on the sweep output transformer through a 100-nmf. capacitor.


In a second method, used in the Philco 50-T1104 chassis, code 123, a parallel tuned circuit has been installed in series with terminal 4 of the sweep output transformer. The trap consists of a 470-ohm resistor, a 600-microhenry coil and a .0022 mfd. capacitor in parallel.

Phono Installation

(Continued from page 18)

of tape travel, if tapes are to be interchangeably recorded and played on different machines. A small degree of misalignment of the playback head with the recorded signal can cause a serious reduction in output at the higher frequencies. Recorders are usually furnished with the record and playback heads properly aligned, both with respect to each other and with respect to the tape travel. Provision is made, however, on all machines for

(Continued on page 32)

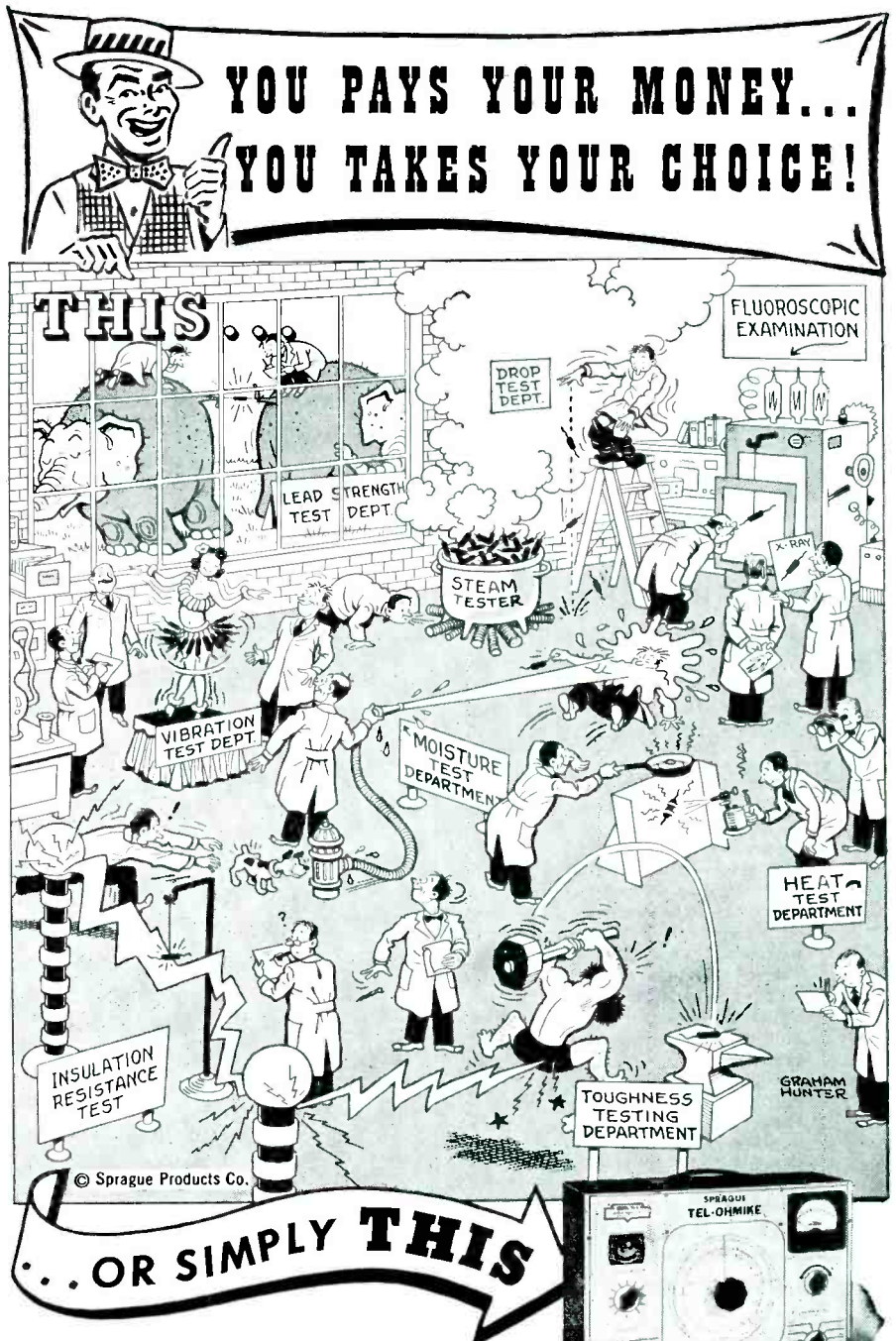

Exaggerated? Not by a jugful! So many claims are being made for the average capacitor these days, you'd almost need a test department like this to prove whether or not the manufacturers are telling the truth.


For everyday testing of essential capacitor characteristics in your own service shop, we recommend the Sprague Tel-Ohmike Analyzer. Measures capacitances from .00001 to 2000 mfd., electrolytic power factor to 50%, and electrolytic leakage under rated voltage from built-in power supply. Checks insulation resistance of ceramic, paper and mica capacitors. Measures resistors from 2.5 ohms to 25 megohms. Also is a 0-15-150-750 volt and 0-1.5-15-75 ma. volt-milliammeter.

Write for catalog M-414 today.

FREE! LARGE REPRINTS OF THIS CARTOON

Handsomely lithographed with advertising removed, size 11" x 14", suitable for framing. Send 10c to cover mailing and handling cost.

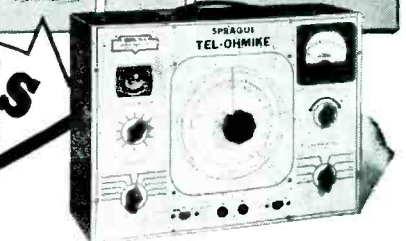SPRAGUE PRODUCTS CO., North Adams, Mass.
Distributors' Division of the Sprague Electric Company




Sprague Tel-Ohmike analyzer for fast, easy testing of all essential capacitor and resistor characteristics.



Sprague Capacitors for dependable service in any application.

SPRAGUE

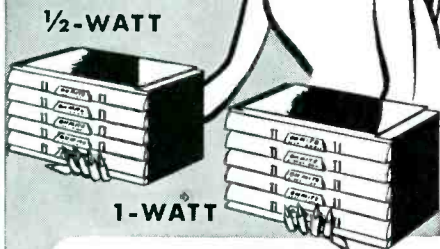YOU'LL WANT BOTH OHMITE RESISTOR ASSORTMENTS



PACKED IN RUGGED

ALL-PLASTIC CABINETS

1/2-Watt Little Devil Assortment, Tolerance $\pm 10\%$. Stock No. CAB-1, \$12.50
1-Watt Little Devil Assortment, Tolerance $\pm 10\%$. Stock No. CAB-2, \$18.75

NO CHARGE FOR CABINETS

It's easy to find the right resistor... fast... in these handy, handsome, all-plastic OHMITE cabinets. Compact—only 9" x 5 1/4" x 4 3/4"—each one has 40 compartments factory packed with a carefully selected serviceman's assortment of 125 individually marked "Little Devil" resistors, either 1/2 watt or 1 watt, in the 40 values from 10 ohms to 10 megohms most frequently used. And, you pay only the regular price of the resistors... nothing extra for cabinets.



LITTLE DEVIL
Composition Resistors

See Your Distributor

BROWN DEVIL


Vitreous Enameled Resistors



A favorite with servicemen. Easily mounted by its tinned wire leads. In sizes 5, 10, and 20 watts. Tol. $\pm 10\%$.

DIVIDOHM

Adjustable Resistors

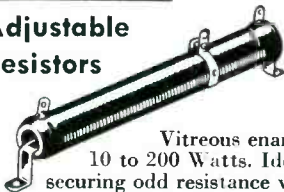

Vitreous enameled. 10 to 200 Watts. Ideal for securing odd resistance values.

OHMITE MANUFACTURING CO.
4879 Flournoy Street • Chicago 44, Ill.

Be Right with

OHMITE

Reg. U.S. Pat. Off.

RHEOSTATS • RESISTORS • TAP SWITCHES


(Continued from page 31)

adjustment of the heads in the field. One tape manufacturer has made available a standard head alignment tape which will enable adjustment of the heads to be made within $\pm 1\frac{1}{2}$ minutes of arc at a wavelength of .001", which corresponds to 15,000 cycles at 15" per second. A head misalignment of 10 minutes of arc will cause a 6 db reduction in output at the 15,000-cycle point. This effect is less serious at lower cycles under foregoing conditions. It is recommended that regular checks using a standard head alignment tape be made as part of a routine checking procedure.

All of the professional recorders produced in this country are driven by synchronous motors, so that the speed of the tape should be independent of line voltage fluctuations; however, if the recorder has been designed to use the full rated power of the drive motor at rated voltage, serious speed variations may occur at lower line voltages, since some types of synchronous motors, when operated at reduced voltage, will lose synchronism and run as straight induction motors.

Large variations in line voltage may have even more serious effects on the performance on the rest of the system. Optimum recorder design utilizes voltage regulator tubes to stabilize the voltage supply to the amplifier and bias oscillator tubes. Such regulator tubes usually have a fairly critical regulating range and abnormally low line voltages will often result in loss of control of the regulator tubes and serious reduction in supply voltage to the bias oscillator. Line voltages varying from 95 to 125 are commonly encountered in field use and can produce a bias current change greater than 2 to 1. A bias change of this magnitude can produce a serious alteration in high-frequency response and may have a marked influence on the amount of harmonic distortion produced.

Recorders which employ slipping friction clutches to control the tape tension are subject to variations in performance due to wear or contamination of the friction surfaces. Satisfactory checks of such equipment can usually be made with a small spring scale, which can be tied to the free end of tape on a full tape reel. A spring scale having a maximum capacity of 16 ounces can be used. In use, the reel can be placed on a friction driven winder spindle and the

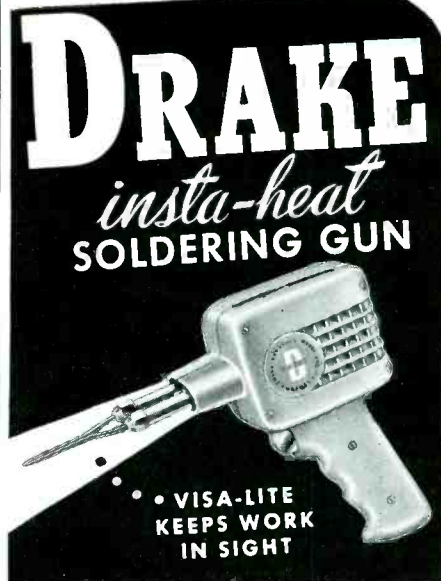

Perfectly balanced, functional in design, the DRAKE "insta-heat" Soldering Gun gives you all the features you've wanted: A full 135 watts, this gun has the perfectly located VISA-LITE, that keeps work always in full view—even in dark difficult corners. The soldering tip is easily - instantly - removable, using only a screwdriver. See your distributor.

DRAKE ELECTRIC WORKS, INC.
3656 LINCOLN AVENUE CHICAGO 13

stalled tension thus measured. Tape can be pulled off the reel at a slow rate by means of the spring scale when the reel is placed on a stationary unwind spindle.

Wear on both the record and playback heads may be expected, although most recorders are designed so that a minimum life of several hundred hours is obtained. The effects of wear on a record head are rather complex. One effect is to reduce the cross-section area of the magnetic material at the pole tips, so that saturation of the magnetic material at this point results. Such saturation may have two secondary effects: First, spreading the recording flux over a wider area, and second, introduction of third harmonic distortion in the recorded signal. The net effect of spreading the recording flux would be to introduce a loss of signal at the higher frequencies. Where appreciable wear can be visibly noted, a new record head should be installed. The worn heads must then be returned to the manufacturer for examination. A record head may be checked by a high power microscope examination of the magnetic pattern recorded on the tape, but the process is usually too complex for normal application.

TV Production Changes

(Continued from page 22)

amount of this bias influences the pull-in sensitivity of the system. A voltage divider consisting of resistor R_{401} and R_{388} is connected to the grid of the sine-wave oscillator (which is a good source of bias voltage), and the resistance value of R_{380} is selected to provide the optimum bias.

Discriminator


The discriminator, consisting of tube sections, V_{22A} and V_{22B} , and their associated components, is used to develop a *dc* correcting voltage by comparing the phase between the output sawtooth waveform and the incoming horizontal sync pulses.

The sync pulse is negative-going, as applied through C_{394} to the discriminator diodes. The tube sections conduct as peak rectifiers and develop voltages of equal magnitude across R_{384} and R_{385} , but of opposite polarity, as shown in Fig. 5.

Because of this condition no voltage can be developed across C_{395} by virtue of the sync pulses alone. It will be noted, from Fig. 1, that any voltage developed across C_{395} , will be applied as bias to the sine-wave tube.

From the sweep output transformer, a waveshape having the frequency and phasing of the horizontal sweep generator is applied across capacitor C_{395} through the resistor R_{390} . Integration of the output waveshape takes place at C_{395} with the resultant that the voltage across it is a sawtooth waveshape with a frequency and phase of the sweep generator. Thus across R_{384} and R_{385} appear not only a sync pulse voltage, but also a sawtooth voltage. The sync pulse has about twice the amplitude of the sawtooth waveshape. The sawtooth voltage across R_{384} is equal in magnitude and polarity to that across R_{385} . Since each diode operates as a peak rectifier, they produce a *dc* voltage across the load resistors, R_{384} and R_{385} , which is equal to the peak value of the composite pulse and sawtooth waveshapes applied.

Fig. 5. Discriminator circuit.

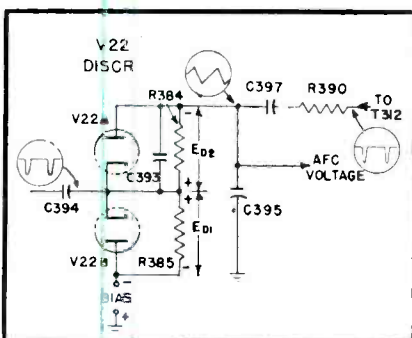


FOR A NEW HIGH IN HIGH FIDELITY!

University MODEL 6201 COAXIAL SPEAKER



CUTAWAY VIEW

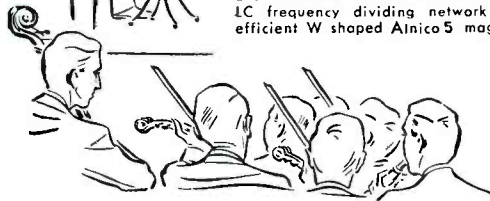showing coaxial arrangement of rugged 12" cone and full size tweeter with cobra horn, built-in LC frequency dividing network and new super efficient W shaped Alnico 5 magnet.



Leading again in PRICE AND QUALITY!

ECONOMY—The Model 6201 is one of the greatest coaxial speaker values ever offered. Despite its economical price, it offers no compromise in efficiency, response, or power handling capacity. A listening test in comparison with higher priced competitive speakers is the most convincing demonstration we can suggest to substantiate these claims.

MANY NEW FEATURES—These include an oversize woofer 2" voice coil capable of extreme excursion for perfect low frequency response, a professional driver—driven tweeter

unit with "cobra" shaped horn for clean, wide angle projection of the highs, and a built-in LC type frequency dividing network with a variable attenuator.

UNIVERSAL REPLACEMENT—The self-contained features of the Model 6201 permit rapid, easy replacement of any standard speaker for conversion to high fidelity reproduction. Only two wires to connect and the job is complete. Ample cable is provided for mounting the attenuator control in any convenient location.

CONTINUOUS POWER:
20 watts of integrated program material

NOMINAL IMPEDANCE:
6-12 ohms

FREQUENCY RESPONSE:
45 to 15,000 cycles

WRITE DEPT. C FOR ILLUSTRATED CATALOG




University LOUDSPEAKERS INC

80 SO. KENSICO AVE., WHITE PLAINS, N. Y.

Famous World-Wide for LOUDSPEAKERS • DRIVER UNITS • TWEETERS • PORTABLE POWRMikes

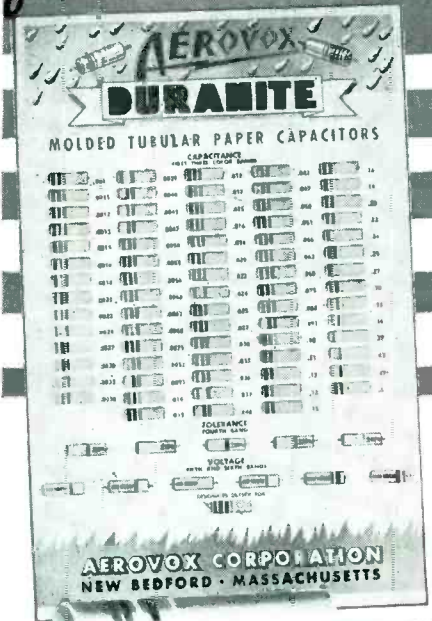PICK the RIGHT DURANITE CAPACITOR from this chart



Initial-equipment Duranite — RMA color-coded — values immediately read on the wall chart. Replacement Duranite available through jobbers — values stamped on units for direct reading.

• Save time, trouble, mistakes! This wall chart gives direct readings for those initial-equipment RMA color-coded molded tubulars — capacitance, tolerance, voltage — at a glance. Handsomely printed in full color. And it's FREE! Get yours from your Aerovox jobber. • Order the corresponding Duranites for profitable servicing.



FOR RADIO-ELECTRONIC AND INDUSTRIAL APPLICATIONS

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

ASSOCIATIONS



RTG, New England

A RECORD attendance prevailed at the annual outing of the Whaling City Chapter of the Radio Technicians' Guild in New Bedford, Massachusetts. A feature of the outing was a softball game and an impromptu lecture by Al Saunders.

At a subsequent meeting of the Guild, municipal regulations governing the installation of TV antennas in New Bedford were discussed. Representatives of the RTG, who played a major role in preparing the code, which may be adopted soon, disclosed that these regulations represent the first attempt of a city in Massachusetts to control such installations.

FRSAP

THE POSSIBILITIES of guilds, licensing or unionization were discussed at a recent meeting of the Federation of Radio Servicemen Associations of Pennsylvania. Robert Riedy, vice chairman of the Federation, is in charge of a seven-man committee considering the choice of each of the three organization controls.

Members of the Whaling City Chapter of the Radio Technicians' Guild at their annual outing.




TEN YEARS AGO

From the Association News Page of SERVICE, November-December, 1939

TWENTY-FIVE CHAPTERS participated in the NAB-RSA promotional program to better service business. . . . A radio Christmas promotion was initiated at this time, too, members of RSA checking up and repairing receivers, in the various chapter cities, for presentation to the local charities, who planned to distribute them during Christmas week. . . . A guarantee service plan was introduced to guarantee the work of individual Service Men and protect the public from unscrupulous operators. . . . Joseph Tallman was named president of the Amsterdam chapter of RSA. Samuel English became secretary and A. R. Kindl, treasurer. . . . Orville C. Mason was named president of the Minneapolis chapter, Arthur Lane becoming vice president and Sears Milnor, secretary-treasurer. . . . Leon Podolsky of Sprague Products Company lectured before the Boston chapter on capacitors and resistors. . . . Dave Krantz was chairman of the technical committee of PRSMA.

FOR ORIGINALITY LOOK TO XCELITE

Only \$9.95 for This 12-Tool Kit!

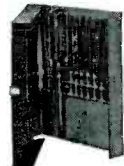

- Has 9 chrome-plated detachable nut driver blades!
- 2 screwdriver sizes in reversible chrome-plated blade!
- Detachable reamer! All tools fit MAN SIZED XCELITE "Combination-Detachable" handle included.



—all in a snappy, strong metal container, shown. A real bargain over buying separate tools and much faster on the job! A real gift idea for this Christmas! Ask your dealer or jobber—or write us.



PARK METALWARE CO., INC.
Orchard Park, N. Y.

Dept. V


New TV Parts ... Accessories

STANCOR TV TRANSFORMERS

Three horizontal deflection output and high voltage transformers have been announced by Standard Transformer Corp., 3580 Elston Ave., Chicago 18.

Included are the A-8119, an exact duplicate of RCA type 211T5, for use with the 16AP4 and similar picture tubes; A-8127, an exact duplicate of RCA type 211T3, for use with the 10BP4, and the A-8123, designed to fill the need for a transformer between the 10" and 16" sizes and also for use in converting a smaller receiver to a 16" receiver.

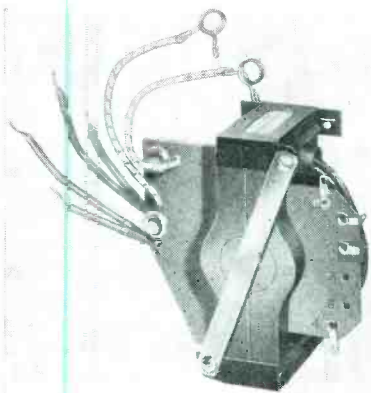
Complete description and prices available in bulletin DB3-354.



* * *

INSULINE BI-CON TV ANTENNA

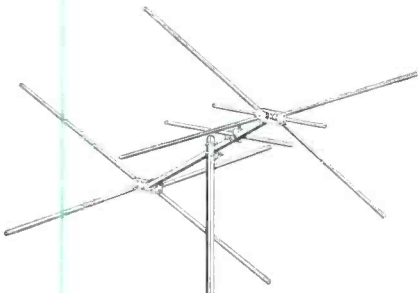A modified conical type antenna, with separate high-frequency and low-frequency reflector elements, the *Bi-Con*, has been developed by the Insuline Corporation of America, Long Island City, 1, N. Y.



* * *


C-D TV ANTENNAS

Five TV antenna types, the *Skyhawk Strate-Line* series, with hi-lo band coverage of channels 2-6 and 7-13, have been produced by Cornell-Dubilier Electric Corp., South Plainfield, N. J.

One model, 85X, has an 8-foot mast, a phase line, 6 standoffs, and a base mounting bracket; model T85X is similar except that it has a 60" transmission line.

Model 85XAX is a double stacked 85X with feeder bars, 6 standoffs, an 8-foot mast, phase lines, and base mounting

For TELEVISION, F.M. and A.M.

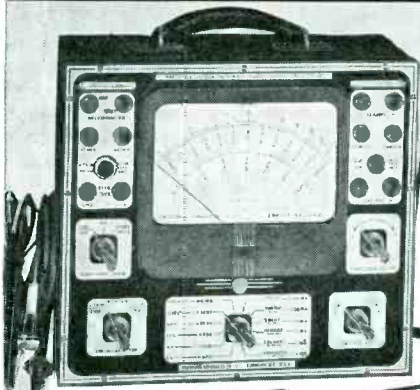

demand a
MODERN
VTVM—Megohmmeter
PRECISION
SERIES EV-10

Zero Center
on ALL
VTVM ranges
Large 7" meter

Self-contained to 6000 volts
-2000 Megs. - 12 Amps - +70DB.
D.C. Voltage ranges to 60,000 V.
when used with Series TV Super
High Voltage Television Test Probe.

PLUS complete
standard sensitivity
1000 ohms per volt
functions

EV-10 is a WIDE-RANGE ZERO-CENTER ELECTRONIC INSTRUMENT, stressing the utmost in performance and ease of manipulation. *Application Engineered* for rapid check of modern A.M., F.M., and TV networks.

IMPORTANT FEATURES

- ★ VOLTAGE REGULATED—BRIDGE TYPE CIRCUIT
- ★ ZERO-CENTER VTVM—no polarity switching or reversal of test prods.
- ★ SHIELDED COAXIAL TEST PROBES.
- ★ 1% wire and metallized resistors.
- ★ MOISTURE RESISTANT, plastic insulated wiring assures performance under adverse conditions.
- ★ DUO-BALANCED ELECTRONIC-BRIDGE OHMMETER
- ★ 7" RECTANGULAR METER

RANGE SPECIFICATIONS

- ★ Eight Zero-Center VTVM Ranges, from ± 3 to ± 6000 V.D.C.
- ★ Input Resistance—
13 1/2 megs. constant to 600 volts.
133 1/2 megs. at 6000 volts.
- ★ Seven D.C. Current Ranges:
from 0-600 microamperes to 12 amps.
- ★ Six Ohmmeter-Megohmmeter Ranges:
self-contained to 2000 megohms.
- ★ Eight A.C.-D.C. and Output Voltage Ranges at 1000 ohms per volt:
from 0-3 to 6000 volts.
- ★ Six Circuit Probing, Zero-Center, VTVM Ranges:
from ± 3 to ± 600 volts D.C.
- ★ Eight DB Ranges. — 26 to +70 DB.
- ★ VTVM Ranges to 60,000 volts available via use of Series TV Test Probe.

ASK TO SEE Series E-400 Wide Range Sweep Signal Generator • Series ES-500 High Sensitivity 5" Oscilloscope.

WRITE for the new 1949 catalog (JUST OFF THE PRESS) describing the complete "Precision" line of quality test instruments for all phases of AM-FM-TV service and test.

SERIES RF-10 HIGH FREQUENCY PROBE

An accessory item to Series EV-10, the RF-10 Probe provides direct voltage test facility to approx 200 MC. Connects directly to EV-10 panel. Employs type 9002 tube. Net Price. \$14.40

EV-10 MCP (illustrated) In open face portable steel case. Complete with tubes, battery, and test probes \$89.95
EV-10-P In closed portable case \$92.70
EV-10-PM For standard rack mount \$92.70




PRECISION APPARATUS CO., INC.

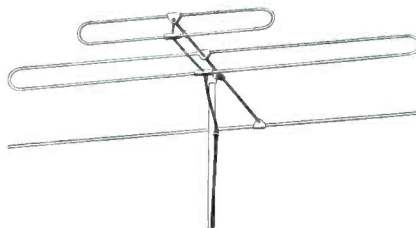92-27 Horace Harding Boulevard, Elmhurst 6, New York
Export Division: 458 Broadway, New York, U.S.A. • Cables—Morhanex

bracket; T85XAX is the same model, plus 60" transmission line.

The fifth unit is K85X, with a single 85X bay, feeder bars and U bolt mast bracket for converting single to double stack.



CLAROSTAT TV BALLAST REPLACEMENTS

Five TV ballast replacement numbers have been announced by Clarostat Mfg. Co., Inc., Dover, N. H.: Emerson 397022 and 397023, Motorola 17A485459, Tele-tone TPR 102D, and Belmont B9M 16067.

* * *

RAYTHEON PULSE TRANSFORMERS

A line of pulse transformers for use in driver circuits as blocking oscillator or interstage units, has been announced by Raytheon Manufacturing Co., department 6460-NR-2, Waltham 54, Mass.

A chart, DL-K-315, with complete data on the most popular of Raytheon's pulse transformer designs is available upon request.

**MAKE PLUS PROFITS
WITH JFD PRODUCTS**

JFD makes the most complete line of TV accessories anywhere. More important, however, is the fact that they're quality products that do a job... and stay sold. And you know that your profits are greater when customers are satisfied.

**JFD
C 361
STACKED
"COMMANDAIR"
ALL-BAND
CONICAL**



Here's just one example of JFD leadership in the antenna field. High in performance!... Low in Price!

\$20⁹⁵
LIST

JFD No. TV10

The most effective booster money can buy.


\$37⁵⁰
LIST



**JFD
TWIN LEAD
LIGHTNING
ARRESTER**

Underwriters' Laboratories approved for indoor-outdoor use. Safeguards sensitive TV parts against lightning and static charges.

\$2²⁵
LIST

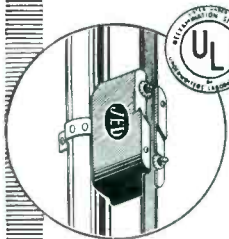

Write for **FREE JFD Catalog** of TV Accessories. No. TV100

More than a catalog, it contains installation and servicing data of interest to every Serviceman.

Also **FREE** for the asking... JFD Catalog of Radio Accessories. No. 438.



JFD MANUFACTURING CO., Inc.
6109 16th Avenue
Brooklyn 4, N. Y.
FIRST IN TELEVISION ANTENNAS AND ACCESSORIES

RMS TV PREAMP

A TV preamplifier, SP-4, which has been approved by the Underwriter's Labs, has been announced by Radio Merchandise Sales, Inc., 550 Westchester Ave. N. Y. 55.

Preamplifier features individually shielded input, output and power sections. Entire unit is said to be further shielded against outside and TV receiver interference.

Shock hazard is said to be eliminated by use of an isolation-type transformer.

Both the input and output of the pre-amplifier are iron-core tuned to resonance with the desired frequency. Coils are wound with flat ribbon.



* * *

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACTS OF CONGRESS OF AUGUST 24, 1912, AND MARCH 3, 1933.

Of SERVICE, published monthly at New York, N. Y., for October 1, 1949.

State of New York }
County of New York } ss:

Before me, a notary, in and for the State and county aforesaid, personally appeared B. S. Davis, who, having been duly sworn according to law, deposes and says that he is the Business Manager of SERVICE, and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management, etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, as amended by the Act of March 3, 1933, embodied in section 537, Postal Laws and Regulations, to wit: 1. That the names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; Editor, Lewis Winner, New York, N. Y.; Managing Editor, None; Business Manager, B. S. Davis, Ghent, N. Y.; 2. That the owners are: Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; B. S. Davis, Ghent, N. Y.; J. C. Munn, Union City, Pa.; A. B. Goodenough, Port Chester, N. Y.; P. S. Weil, Great Neck, N. Y.; F. Walen, Teaneck, N. J.; G. Weil, Great Neck, N. Y.; L. Winner, New York, N. Y. 3. That the known bondholders, mortgages, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities, are: None. 4. That the two paragraphs next above, giving the names of the owners, stockholders and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company, but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock, and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

(Signed) B. S. DAVIS, Business Manager.

Sworn to and subscribed before me, this 14th day of September, 1949.

(Seal) NATHAN JELLING,


Notary Public.

Commission expires March 30, 1950.

**THE
REDSKINS
ARE
COMING!**



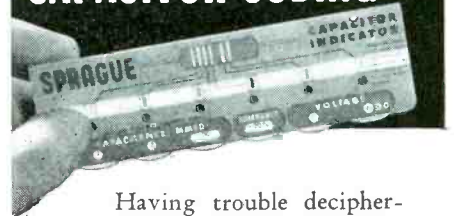**QUICK, EASY
WAY TO READ TUBULAR
CAPACITOR CODING**



Having trouble deciphering the color coding on tubular molded capacitors in new TV and Radio sets? There's no need to consult complicated wall charts or tables!

JUST FLICK THE DIALS

The Sprague Capacitor Indicator gives you the needed data in a jiffy. Just flick dials to the color bands and read capacitance, tolerance, and voltage directly.

GET YOURS TODAY!

This slick plastic service help fits your pocket. Always on hand, it saves time and avoids mistakes... and it's only 15c. Ask for one at your Sprague distributor's store today!


SPRAGUE PRODUCTS COMPANY
Distributors' Division of the Sprague Electric Co.
NORTH ADAMS, MASS.

TACO TWIN-DRIVEN YAGI

A twin-driven type yagi is now being made by Technical Appliance Corporation, Sherburne, N. Y.

Physically, the yagi, a low-band system, is made up of two 300-ohm folded dipoles and two parasitic elements on one horizontal crossarm. Instead of the conventional yagi whereby energy for the director elements is transferred by mutual coupling from the one driven element, this antenna has a director system which is fed with a transmission line from the main driven element.

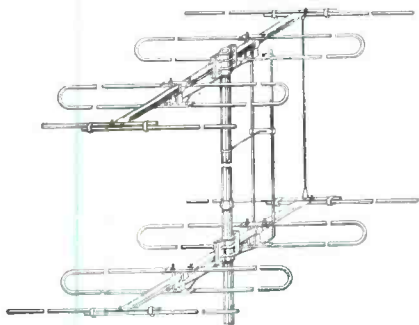Gain may be increased through the use of a stacked array of this antenna. Jiffy-rig construction is used.



* * *

JFD TWINLEAD LIGHTNING ARRESTER

A twinlead lightning arrester, *safeTV-guard*, has been announced by the JFD Manufacturing Co., Inc., 6101 Sixteenth Ave., Brooklyn 4, New York.

Arrester, Underwriters' Laboratories Approved, can be installed on a mast, grounded pipe, wall or window sill and other flat surfaces. Twinlead is slipped into the horizontal slot on top of the arrester and tightened in place by a pair of cap nuts and toothed washers.

Discharge contacts are sealed in rare gas tubes to dissipate charges that may cause damage. Glazed porcelain construction. Hardware is solid brass and nickel-plated.



* * *

GORDON TV FILTER

A filter that is said to eliminate TV screen glare and intensify picture contrast by blocking out unwanted light, has been announced by J. M. Gordon Laboratories, 437 Tenth Ave., New York 1. Has self-adhering press-on feature along the edges. Viewing area is said to be rigid and will not react or adhere to the screen under any conditions.



Use STANCOR EXACT DUPLICATE TRANSFORMERS

Every call-back you make means lost time and profits. Why take a chance with transformers that "almost fit?" You're sure of a good job and a satisfied customer when you use Stancor *Exact Duplicate* transformers for TV servicing. These units meet the exact specifications, electrically and physically, of the original components. Representative types are listed below.

Vertical Blocking - Oscillator Transformer. Stancor Part Number A-8121. Exact duplicate of RCA type 208T2. For generation of 60 cps required to drive grids of vertical discharge tubes.

Plate and Filament Transformer. Stancor Part Number P-8156. Exact duplicate of RCA type 201T6 used in model 630TS receiver.

Deflection Yoke. Stancor Part Number DY-1. Exact duplicate of RCA type 201D1. For use with direct viewing kinescopes such as 7DP4 and 10BP4.

Focus Coil. Stancor Part Number FC-10. Exact Duplicate of RCA type 202D1. For use with magnetically focused kinescopes such as RCA type 10BP4.

Horizontal Deflection Output and HV Transformer. Stancor Part Number A-8117. Exact duplicate of RCA type 211T1. For use with direct viewing kinescopes, such as types 7DP4 and 10BP4.

For complete specifications and prices of these and other Stancor TV replacement components, see your Stancor distributor or write for Television Catalog 337.

NEW—Ask your Stancor distributor for your copy of the latest edition of Stancor's TV Components Replacement Guide, Bulletin 338B. Lists Stancor replacement parts for 108 TV receivers made by 37 manufacturers. Or write us today.



STANDARD TRANSFORMER CORPORATION

3588 ELSTON AVENUE • CHICAGO 18, ILLINOIS

ERIE RESISTOR RESCO MEETING




At a recent Radio Electric Service Corp. store managers' meeting in Philadelphia, where J. K. Poff, manager of Erie Resistor Corp. distribution sales department, delivered a talk. Among those in attendance, left to right, front row: George Scarborough, L. D. Lowery, Inc., manufacturer's rep.; John Stern, Resco owner; J. K. Poff. Standing, left to right, back row: Larry Oebhecke, manager Germantown Ave., store, Philadelphia; A. Regan, export manager main store, Philadelphia; R. Kammel, assistant manager, Easton, Pa., store; N. Steedle, manager Allentown and Easton, Pa., stores; J. Goldstein, manager, West Philadelphia store; J. Berman, manager, Camden, N. J., store; A. Kass, general manager; G. Hautenschild, purchasing agent; and S. Furman, manager Wilmington, Delaware, store.

COMPARE RESULTS
NOT CLAIMS, FOR RESULTS
IT'S THE NEW—

TANCO TWIN-DRIVEN YAGI

BOOSTS SIGNAL!
LOWERS COSTS!
PINPOINT DIRECTION!

• WRITE FOR FREE BULLETIN ON TACO YAGIS.

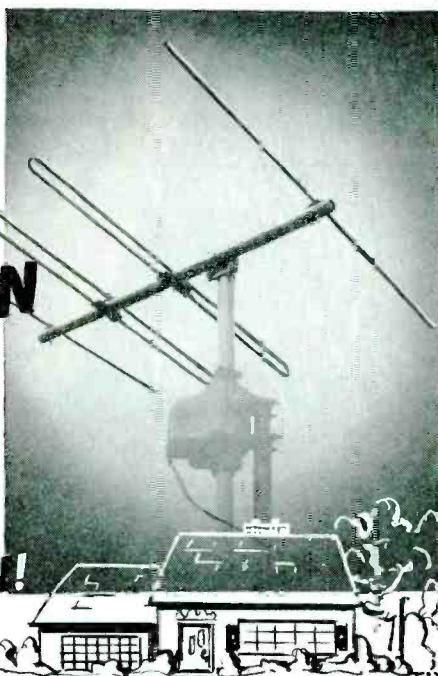

RADIO & ELECTRONIC
EQUIPMENT
TECHNICAL APPLIANCE CORP.
SHERBURNE, N. Y.

IN CANADA: STROMBERG-CARLSON CO., LTD., TORONTO 4, ONT.

RAYTHEON TV TUBES

Two new TV tube types, the 1X2 and the 6BQ6GT, has been announced by Raytheon.

The 1X2 is a filament type rectifier of miniature construction designed for use as a high voltage rectifier. It can be used in *rf*, flyback, and power line frequency types of rectifier circuits.

The 6BQ6GT is a beam pentode for use as a horizontal deflection amplifier. Employs a T-9 bulb, and a standard octal base. Plate connection is made through a top cap.

* * *

AEROVOX METALLIZED-PAPER MINIATURIZED TUBULARS

Metallized-paper tubular capacitors in cardboard tubes, Aerolite type P'82, have been announced by Aerovox Corporation, New Bedford, Mass.

Aerolite construction is said to eliminate metal foils used in conventional paper capacitors; high-purity paper tissues are coated with a thin film of metal ($\frac{1}{2}$ to 1 millionth inch thick) under high vacuum. Weak spots and particles are said to be *burned out* or isolated in the insulation.

Standard capacitances are from .01 to 2 mfd, and voltages of 200, 400 and 600 DCW at the start. The 2-mfd 200-volt type measures 23/32" diameter by 1 1/4" long.

* * *

STANDARD COIL TV BOOSTER

A one-tube printed-circuit TV booster, featuring 2-knob control (one-knob controls a 3-position switch that turns on the TV set only, or the TV set and booster) and continuous tuning which eliminates a switch from high to low channels, has been announced by Standard Coil Products Co., Inc., 2329 N. Pulaski Rd., Chicago 39; 2901 E. Slausson Ave., Huntington Park, Calif. Adaptable to either a 300 or 75-ohm line.




* * *

TELREX CONICAL V BEAM ANTENNAS

A conical V-beam antenna line, the *Special Series*, has been announced by Telrex Inc., 26 Neptune Highway, Asbury Park, N. J.

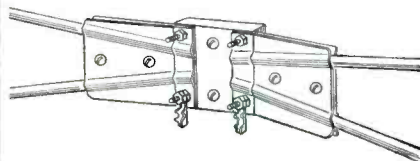Models available include SIX-BD, S2X-BD, S2X-TV and S4X-TV.



Telrex special element mounting assembly.

Build YOUR OWN **Heathkit TEST EQUIPMENT**

Heathkit AUDIO GEN. KIT \$34.50

Heathkit TUBE CHECKER KIT \$29.50

Heathkit 5" OSCILLOSCOPE KIT \$39.50

Heathkit BATTERY ELIMINATOR KIT \$22.50

Heathkit TELEVISION GENERATOR KIT \$39.50

Heathkit SIGNAL TRACER KIT \$19.50

Heathkit ELECTRONIC SWITCH KIT \$34.50

Heathkit CONDENSER CHECKER KIT \$19.50

Heathkit RF SIGNAL GEN. KIT \$19.50

Heathkit VACUUM TUBE VOLT METER KIT \$24.50

NEW Heathkit IMPEDANCE BRIDGE SET \$69.50

NEW Heathkit HANDITESTER KIT \$13.50

Heathkits are beautiful factory-engineered quality service instruments supplied unassembled. The builder not only saves the assembly labor cost but learns a great deal about the construction and features of the instrument. This knowledge aids materially in the use and maintenance of the equipment. Heathkits are ideal for and used by leading universities and schools throughout the United States. Each kit is complete with cabinet, 110V 60 cycle transformer (except Handi-Tester), all tubes, coils assembled and calibrated, panel already printed, chassis all punched, formed and plated, every part supplied. Each kit is provided with detailed instruction manual for assembly and use. Heathkits provide the perfect solution to the problem of affording complete service equipment on a limited budget. Write for complete catalog.

HEATH COMPANY
BENTON HARBOR, 11 MICHIGAN

EXPORT DEPARTMENT
23 EAST 40th STREET
NEW YORK 12, N. Y.
CABLE - ARLAB - N. Y.

New Parts, Accessories

IRC Q REPLACEMENT CONTROLS


A line of 59 15/16" Q controls with knob master fixed shafts for TV, AM and FM replacements has been developed by the International Resistance Co., 401 N. Broad St., Philadelphia, Pa.

Knurled, flatted and slotted, the shafts are said to be so proportioned that they fit at least 90% of the 1/4" shaft knobs—knurled, spring-type, flat or set-screw—without any alteration except cutting to length. Shafts may be split lengthwise and the ends spread for fitting to over-size or worn knobs; 3" long from mounting face of control.

Controls also feature an interchangeable fixed shaft, with a special resilient retainer ring, which is said to permit rapid removal of the fixed or permanent knob master shaft and replacement with any of 11 special fixed shafts.

Major external parts—covers, shafts, ground plates and bushings—are nickel-plated. Outer terminals are tinned and switch terminals silver-plated.

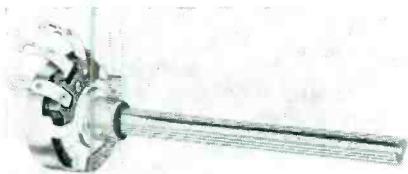Operating at 1/2-watt power rating, Q controls are available plain or tapped in a wide selection of values. Free catalog DCI is available.



* * *

G. E. TWIN STYLUS VARIABLE RELUCTANCE CARTRIDGE

A twin stylus variable reluctance phonograph cartridge, model RPX-050, capable of playing conventional and microgroove records, has been announced by the receiver division of G. E.

Changing from one stylus to the other is accomplished by depressing and turning a knob on the top of the cartridge, which projects through the tone arm of the player.

Twin stylus assembly is replaceable as a unit with sapphire tips having one and three mil tip radii. Stylus pressure with either stylus is eight grams.

The new cartridge is the same in size as present models featuring the replaceable stylus.

* * *

SYLVANIA TUBES


Three tubes, including an *af* amplifier; *rf* amplifier for TV, and a horizontal deflection amplifier have been announced by Sylvania Electric Products, Inc.

Audic amplifier, type 12AY7, is a T6 1/2 miniature, medium-mu duotriode particularly suitable for the use in the first stage of *af* amplifiers. Supplied with a center-tap heater for use with 6.3 or 12.6-volt source.

The *rf* amplifier, type 6BC5, is a T5 1/2 miniature sharp cut-off pentode having high mutual conductance. Tube is listed as an equivalent of 6AG5.

The horizontal deflection amplifier, type 6BQ6GT, has been designed for transformer operated sets where high peak interelectrode voltages are encountered.

GENERAL INDUSTRIES leads the Parade

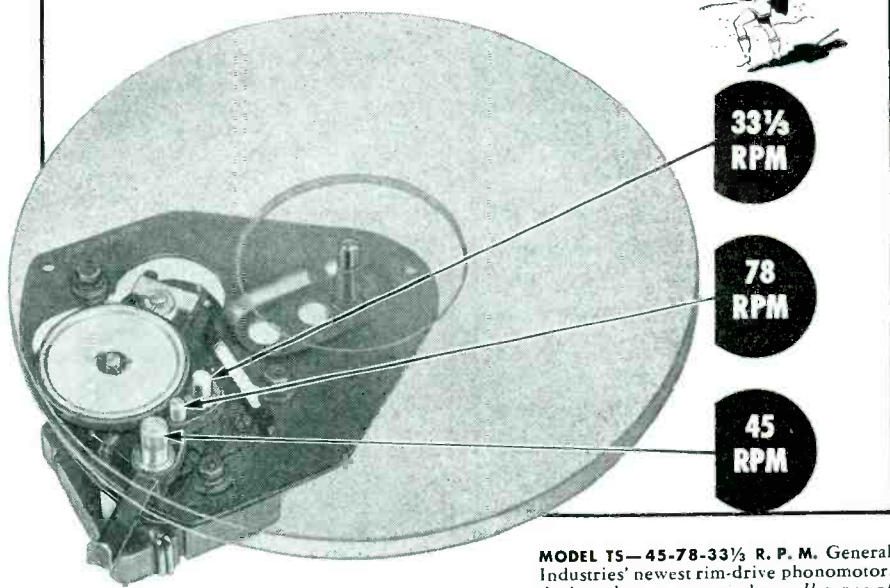

MODEL TS—45-78-33 1/3 R. P. M. General Industries' newest rim-drive phonomotor, designed to accommodate all types of records now on the market.

... with this low cost THREE-SPEED PHONOMOTOR!

It's GI's Model TS . . . the *one* motor designed and engineered to meet *all* requirements for true record reproduction at 33 1/3, 45 and 78 R.P.M. Already time-proved in actual service, this latest addition to the famous GI phonomotor line today is being used in a wide range of portables, table models and console radio-phonographs.

Outstanding features: standard narrow-flange turntable for easy, compact installation . . . simple, yet positive speed shift mechanism with external control lever . . . dependable, quiet *Smooth Power* motor for long, trouble-free service.

For full details—blueprints, performance specifications and quotations—write, wire or phone today.




The GENERAL INDUSTRIES Co.

DEPARTMENT O • ELYRIA, OHIO

RCP SIGNAL TRACER

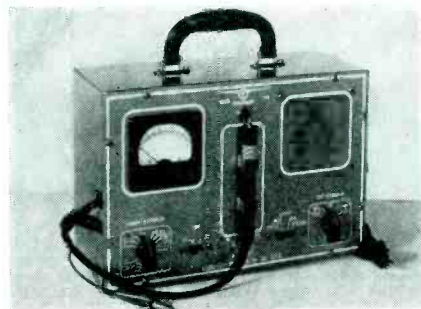A signal tracer, model 777A Dyna-tracer, has been announced by Radio City Products Co., 152 West 25th Street, N. Y. 1.



Uses a 6AU6, 6AT6, 6AQ5 and 6X4. Attenuation is 10,000 to 1 by means of ladder attenuator with vernier control. Sensitivity is 10,000 microvolts for full scale deflection of meter or 200 microvolts per division.

Frequency range covers approximately 160 mc.

A jack is provided for testing microphones and pickups. Automatic control switch permits either speaker or meter to be used alone or together and standby.

* * *


WILLARD FLAT B BATTERIES

A flat-pack, 90-volt B battery has been announced by the Willard Storage Battery Co., Cleveland, Ohio.

Batteries feature flat cells inserted in a plastic jacket, clamped with a metal band and sealed into a polystyrene container.

American Beauty

ELECTRIC SOLDERING IRONS

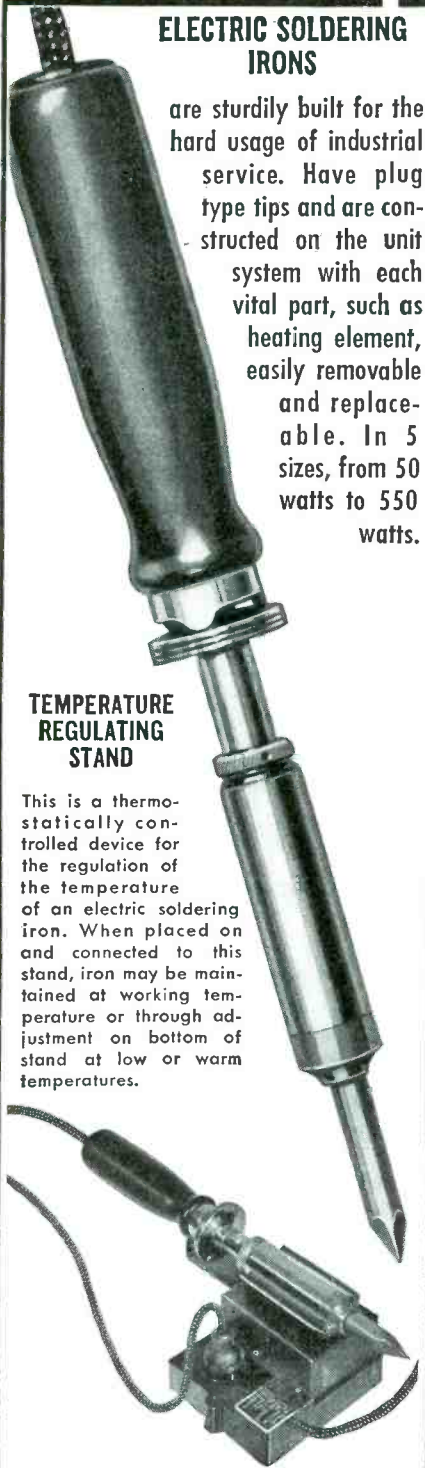

are sturdily built for the hard usage of industrial service. Have plug type tips and are constructed on the unit system with each vital part, such as heating element, easily removable and replaceable. In 5 sizes, from 50 watts to 550 watts.

TEMPERATURE REGULATING STAND

This is a thermostatically controlled device for the regulation of the temperature of an electric soldering iron. When placed on and connected to this stand, iron may be maintained at working temperature or through adjustment on bottom of stand at low or warm temperatures.

For descriptive literature write

110-1


AMERICAN ELECTRICAL HEATER COMPANY
DETROIT 2, MICH., U. S. A.

TRANSVISION 5" 'SCOPE

A 5" 'scope, model 450A, has been announced by Transvision, Inc., New Rochelle, N. Y.

Vertical amplifier response to 1 mc; sensitivity, .15 rms volt/inch; horizontal amplifier, 2 cycles to 500 kc. Decade attenuators are frequency compensated. Z axis input. Direct connection to deflection plates. Calibration test signal. Push-pull amplifiers on horizontal and vertical. Three stage amplification on both. Sweep frequency to 50 kc.

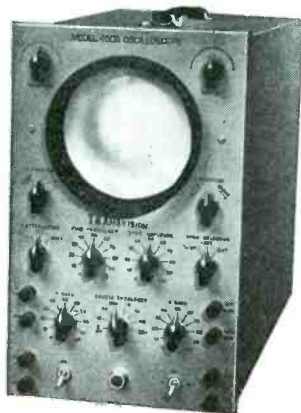Tube complement: vertical amplifier, two 6SN7; horizontal amplifier, two 6SN7, and 5Y3, 2X2 and 5BP1; 884 sweep generator.



* * *

UNIVERSITY TWEETER

Tweeters employing a cobra horn, models 4408 and 4409, have been announced by University Loudspeakers Inc., 80 South Kensico Ave., White Plains, N. Y.

Bakelite diaphragms, Alnico V magnets, aluminum voice coils and featherweight phenolic varnishes are used. Used with an efficient cone speaker, the 4408 is said to be able to handle up to 15-20 watts of program material; 4409 full undistorted output of 25-40 watt amplifiers.

Response, 600-15,000 cps; impedance, 16 ohms; dist. area 40° X 80°; dimensions, 5 3/4" h, 7 3/8" w, 1 1/8" d.

* * *

BELDEN ANTENNA CONTROL CABLE

A 4-conductor antenna control cable has been announced by Belden Manufacturing Company, Chicago, Illinois.

Designed primarily as a motor leadin cable for antenna rotating devices requiring four conductors.


Type 8484, four-conductor antenna control cable is a No. 20 AWG, cable with seven strands of No. 28 tinned copper wire, .010" wall vinyl plastic insulation.

C-D TO EXHIBIT AT CLEVELAND NEDA SHOW



L. B. Calamaras, NEDA; Ken Burcaw, C-D sales manager and William Many, advertising manager of Cornell-Dubilier, selecting booth space in the Cleveland Auditorium where the 1950 radio parts distributors' convention will be held.

FIELD TESTED Installation Information on

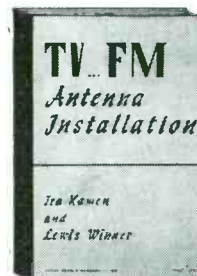

**TV
and
FM**

RECEIVING ANTENNAS

TV... FM Antenna Installation

by Ira Kamen

Manager, Antenaplex and TV Dept.
Commercial Radio Sound Corp.

and Lewis Winner

Editorial Director,
Bryan Davis Pub. Co., Inc.;
Editor, Service and Communications

The only practical book on the all-important item in TV and FM reception . . . based entirely on actual experiences in the most active TV and FM areas in the country.

Over 35,000 words of vital data with over 130 photos and drawings.

Ten chapters covering:

Installation Tools
Antenna Installation Procedures
Securing 12-Channel Coverage
HF Antenna Installations
TV Interference
Fringe Reception
Master Antenna Systems
FM Antennas
Installation Business Practices
Tricks of the Trade

The first book in which you'll find complete design and installation information on every type of TV and FM receiving antenna.

Contains detailed illustration and subject index for rapid reference.

Available direct or through your distributor **\$2.00**
Postpaid

Send coupon below to your distributor or direct to:

Bryan Davis Publishing Co., Inc.
(Book Dept.)

52 Vanderbilt Avenue, N.Y. 17, N.Y.

Please send me a copy of "TV-FM Antenna Installation," postpaid, for which I am enclosing \$2.00.

(Please Print)

NAME

ADDRESS

CITY AND STATE

**OVER 2,000,000
IN SERVICE IN
RADIO AND
TELEVISION!**

Seletron
SELENIUM RECTIFIERS

For dependable service in all Electronic and Radio applications always specify SELETRON Selenium Rectifiers.

| | | | | | | |
|--------------------------|--------|---------|---------|----------------|------------|---------|
| Model No. | 5M4 | 5M1 | 5P1 | 5R1 | 5Q1 | 5S1 |
| Plate Size | 1" sq. | 1" sq. | 1 3/8" | 1 1/4 x 1 1/2" | 1 1/2" sq. | 2" sq. |
| Max. D.C. Output Current | 75 MA. | 100 MA. | 150 MA. | 200 MA. | 250 MA. | 500 MA. |

Max. Input Voltage RMS: 130 V. Max. Peak Inv. Voltage: 380 V. Approx. Rectifier Drop: 5 V.

Write Dept. SM-11 for name of nearest authorized dealer!

**SELETRON DIVISION
RADIO RECEPTOR COMPANY, INC. (RR)**
Since 1922 In Radio and Electronics
Main Office & Factory: 84 North 9th St., Brooklyn 11, N. Y. • Sales Department: 251 West 19th St., New York 11, N. Y.

Coming Soon . . .

TV ENGINEERING

Watch for
Announcement!

**WHEN YOU CHANGE
YOUR ADDRESS**

Be sure to notify the Subscription Department of SERVICE at 52 Vanderbilt Avenue, New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

AMPHENOL

COMPARE

the DB GAIN
the DIRECTIONAL PATTERN
the BROAD BANDING
the MECHANICAL DURABILITY
the STREAMLINE DESIGN

AMPHENOL **INLINE** **ANTENNA**

-Best by every comparison

- Dealers in television sets must depend upon the installer to uphold his reputation as well as that of the set manufacturer. The materials used in the installation and the quality of the installation are paramount in determining the customer's satisfaction with "the picture."

- The rapidity of expansion of the television industry has brought forth some rather fuzzy information and hasty claims that definitely tend to confuse and mislead the customer and many dealers. Accuracy and honesty of information are of such importance at Amphenol that we want all to know our technical information is based on laboratory findings, determined by competent personnel, precision laboratory facilities and exhaustive techniques.

- Be sure of the best performance of the sets you sell by specifying Amphenol INLINE Antennas.

MODEL 114-005
Basic, single-bay all-purpose antenna complete with 75 feet of 300 ohm Twin-Lead lead-in.

MODEL 114-009
Same as 114-005 except less lead-in.

MODEL 114-302
Stacked array (two bays) of same antenna for use at greater distances.

MODEL 114-301
Conversion kit. Provides parts necessary to build single-bay (114-005) into two-bay (114-302).

'Informative Data for Television Installation and Service Men'—13 pages of specific, scientific, authoritative information. Send for your copy on your business letterhead—today.

AMERICAN PHENOLIC CORPORATION
1830 SO. 54TH AVENUE • CHICAGO 50, ILLINOIS

AMPHENOL

Patent Pending



New!

MODEL "B"

DC POWER SUPPLY

**HIGHEST EFFICIENCY KNOWN
in the 3 to 9 Volt Range**

New, Exclusive Design Increases Power 1½ Times . . . yet costs no more than the conventional type. Completely different application of selenium rectifiers, aided by conduction cooling, dissipates over 3 times the heat. The Electro Model "B" has proved itself the most efficient direct current source of power known. Gives instant readings, and offers ample power to operate any receiver. Peak instantaneous current rating of 35 amperes (from 50 to 60 cycle 115 volt power source), permits operation of two receivers with push button solenoids. **Applications:** Test or operate auto radios, relays, telephone circuits, laboratory instruments and many other low voltage requirements.

EXCLUSIVE FEATURES

- ★ Heavy-duty selenium rectifiers
- ★ 8 Heavy-duty power tap adjustments
- ★ 1 to 20 amperes at 6 volts continuous duty
- ★ Less than 3% AC ripple or hum
- ★ Damped volt and ammeters (no wiggling) Voltmeter 3% accuracy
- ★ Heavy-duty transformer and choke
- ★ 6000 Mfd. filter condenser

UNMATCHED PERFORMANCE, QUALITY AND PRICE!

Send for Details TODAY!



Pioneer Manufacturers

of Battery Eliminators

ELECTRO PRODUCTS LABORATORIES, INC.

4501 NORTH RAVENSWOOD AVENUE • CHICAGO 40, ILLINOIS

NOW BETTER, BRIGHTER PICTURES
insuline
new "BI-CON"
TELEVISION ANTENNA

Single Type and Stacked Array for fringe areas

An engineering triumph by Insuline . . . proved outstanding by actual test. Pre-assembled sections for quick installation.

- ✓ Peak ALL-Channel reception.
- ✓ Suitable for ANY make TV receiver.
- ✓ Exclusive — separate High Frequency and Low Frequency dipole-reflector elements.
- ✓ Popularly priced.

Write for complete TELEVISION catalog of TV antennas and accessories.



Heavy duty, specially designed, all aluminum castings for low-resistance electrical contact and rigid dipole clamping.



The INDOOR ANTENNA with AMAZING RECEPTION QUALITIES on ALL CHANNELS competitively priced



insuline CORPORATION OF AMERICA

INSULINE BUILDING • 36-02 35th AVENUE • LONG ISLAND CITY, N. Y.
West Coast Branch and Warehouse: 1335 South Flower Street, Los Angeles, Calif.
QUALITY PRODUCTS SINCE 1921

Ser-Cuits

(Continued from page 20)

amplifier and 6V6GT power amplifier. These two stages provide the necessary audio power to drive the speaker. The circuit is conventional.

Radio-Phono-Television Model

Audio Amplifiers

Television combination models use a push-pull audio system in place of the single-ended system used in the straight television models. A 6SJ7 functions as a voltage amplifier and a 6SQ7 as a phase inverter.

A pair of 6K6GTs are used in a cathode biased push-pull power amplifier stage.

Video IF Amplifiers

Three stages of 6AU6 transformer coupled, stagger-tuned video *if*, use three self-resonant, slug-tuned transformers (T_{301} , T_{302} and T_{303}) as coupling devices between stages. Two accompanying sound traps are provided within the *if* sub-chassis. A trap is inductively coupled to T_{301} and serves as the sound take-off point and audio absorption trap. A second trap is slug-tuned to parallel resonance at 4.5 *mc* and comprises part of the video detector load. This trap offers a high impedance to sound voltage (inter-carrier beat) appearing at the detector and prevents it from being passed on to the video amplifier grid. Automatic gain control bias developed across a 100,000-ohm resistor, R_{308} , is supplied to the control grids of the first two 6AU6s through RC decoupling networks.

Video Detector

The video detector diode (one-half of a 6AL5) connections are such as to obtain a positive picture phase across the diode load. Since one phase reversal occurs in the 6AC7 video amplifier positive picture phase at the picture-tube grid is achieved by feeding the picture-tube cathode from the plate of the 6AC7. Series peaking is accomplished by L_{302} and a flat response is thus obtained over the entire video frequency range. A 10-mmfd capacitor, C_{312} , serves as the usual *rf* bypass and removes the video *if* carrier from the detected video signal. The detector load is direct-coupled to the 6AC7, video amplifier.

[To Be Continued]

TELEVISION SCOPE

SUPERIORITY AT A GLANCE!

The vertical response of this economy TV scope is capable to 5000 kc, not 50 kc. Response is flat to 750 kc, down 3 db at 1000 kc. Amplifier supplies a voltage gain of 20 at 5000 kc.



AR-3

Check this necessary feature before you buy any scope for TV use.

The R.S.E., AR-3 Scope has been built by Ross Armstrong to our rigid specifications. It's a complete unit that embodies standard horizontal amplifier and sweep circuits with normal sensitivity.

The case is 8" high x 5" wide x 14" long, attractively finished in "hammered" opalescent blue enamel. Operates on standard 110 volts—60 cycles—40 watts. Tubes, 3BP1-6AC7-6SJ7-6X5-5Y3-884. Instructions included. Complete specifications upon request. Satisfaction or your money back.

PRICE


\$4995

AVAILABLE TO JOBBERS IN QUANTITY

F. O. B. DETROIT

INTERCOM & RADIO

AT A PRICE THAT CAN'T BE BEAT!

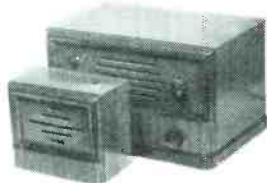

6 tube superhet—3 tube intercom permits communication between radio-master and up to 4 sub-stations.

\$2995

With 1 sub-station and 50 feet of cable
Extra Sub-stations \$3.95 each

Original cost \$64.50

PUSHBACK WIRE



25% BELOW MILL COST!

1st class, Essex or Lenz, ALL SOLID tinned copper, double cotton serve, waxed finish.

| Size | Colors | 100 Feet | 1000 Feet | Production Reel |
|------|----------------|----------|-----------|-----------------|
| 22 | Black-Brown | .39 | 3.79 | 3.65M |
| 20 | Red-White-Blue | .49 | 4.49 | 3.95M |
| 18 | Brown | .69 | 5.98 | |

ORDER INSTRUCTIONS

Minimum order—\$2.00. 25% deposit with order required for all C.O.D. shipments. Be sure to include sufficient postage—excess will be refunded. Orders received without postage will be shipped express collect. All prices F.O.B. Detroit.

RSE
Demand This Seal of Quality

RADIO SUPPLY & ENGINEERING CO., Inc.
Quantity and Export Orders Solicited
86 SELDEN AVE. DETROIT 1, MICH.

NEWS

SNYDER TV CATALOG

A TV antenna catalog, covering the Redi-Mount series of antennas, as well as the Head-Line group, plus the Tele-Port indoor models and Redi-Mount TV accessories has been published by Snyder Manufacturing Co., 22nd and Ontario Streets, Philadelphia 40, Pa.

Catalog requests should be addressed to Dick Morris.

* * *

ACA TWIN-TRAX TAPE RECORDER CATALOG

A 16-page catalog, which illustrates and describes magnetic type recorders, has been published by the Twin-Trax Division, Amplifier Corp. of America, 398-31 Broadway, N. Y. C.

Discussed are table and portable models operating at the standard tape speeds of 7½, 15 and 3¾ inches per second. Basic mechanical chassis and variable tape speed compensated amplifier data are included.

* * *

AL FRIEDMAN JOINS RMS

Al Friedman, formerly with the J. F. D. Manufacturing Co. as chief engineer, consultant, and field sales engineer, has been named chief engineer of Radio Merchandise Sales, Inc., 550 Westchester Ave., New York 55.



Al Friedman

* * *

MUELLER DESCRIPTIVE PRICE TAGS

Descriptive price tags covering the jobber line of clips, insulators, ground clamps, *tenna-clampipes tenna-clamps*, and snappers have been sent to distributors by the Mueller Electric Company, 1583 East 31 St., Cleveland 14, Ohio.



RCA SPEAKERS

are quality-engineered for dependable performance



Check these important features!

- ✓ Moisture-resistant voice-coil suspension—unaffected by humidity changes.
- ✓ Felted cone for "flutter-free" response.
- ✓ Rugged mechanical construction with welded housing assembly.
- ✓ Exclusive clamping spring permanently locks Alnico V magnet in larger sizes of PM speakers.
- ✓ Mechanical filter ring in 12" speakers cuts needle scratch and 10-kc. whistle.
- ✓ Rugged—Dustproof—Rustproof.
- ✓ Adjustable voice-coil mounting in 12" speakers.
- ✓ Mounting designed to RMA standards.


Always keep in touch with your RCA Distributor

TURN TO NEXT PAGE

RCA ELECTRONIC COMPONENTS
RADIO CORPORATION OF AMERICA
HARRISON, N. J.

SPACE-SAVER!

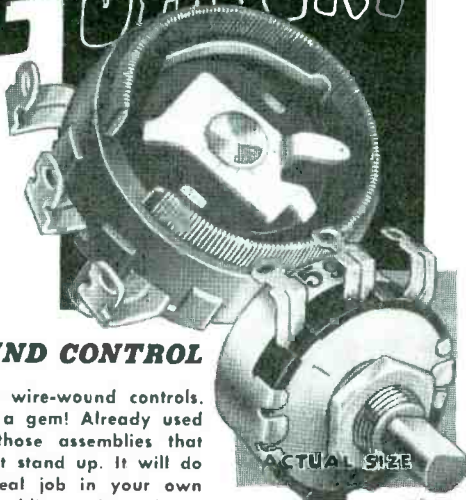- ★ Only 1 1/8" dia. x 9/16" deep
- ★ With switch, only 7/8" deep
- ★ Wire-wound. 10 to 10,000 ohms
- ★ 2-watt power rating, average



MIDGET WIRE WOUND CONTROL

Just the thing for tight spots. Same size and external design as popular Clarostat "M" composition-element control. Yet performs as well as large-size wire-wound controls. It's a gem! Already used in those assemblies that must stand up. It will do a real job in your own assemblies and repairs.

Ask your Clarostat jobber for latest catalog. Or write us.



CLAROSTAT



Controls and Resistors

CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE • In Canada: CANADIAN MARCONI CO., LTD. Montreal, P. Q. and branches

PYRAMID ELECTRIC NAMES REPS

Henry W. Burwell, John O. Olsen, and James P. Hermans, former Solar reps, are now representing Pyramid Electric Co., 155 Oxford St., Paterson, N. J.

Henry W. Burwell of Atlanta, Georgia, will cover North Carolina, South Carolina, Tennessee, Georgia, Alabama, Mississippi, Florida, and Virginia; John O. Olsen, Cleveland, will cover West Virginia, Ohio, Kentucky, Western Pennsylvania and Maryland; and James P. Hermans, San Francisco, will cover northern California.

* * *

STOTTS AND FRIEDMAN OPEN STORE

A new distribution center has been opened by the Stotts Friedman Co., 620 South Main Street, Dayton 2, Ohio.

Standard brands of radio and TV parts and accessories have been stocked. Co-owners of the new enterprise are Ray Stotts and Harry Friedman.

* * *

SUN RADIO NOW STOCKING PEERLESS TRANSFORMERS

Sun Radio and Electronics Co., Inc., 122-24 Duane St., N. Y. C., has been named exclusive distributor of Peerless transformers in the New York metropolitan area, which includes Westchester County, Northern New Jersey and Long Island.

Transformers are made by the Peerless Electrical Products Division of Altee Lansing Corp.



Samuel Gerard, Sun Radio general manager.

* * *

RODRIGUEZ JOINS SHELDON ELECTRIC

A. E. Rodriguez is now with the Chicago office of the Sheldon Electric Division of Allied Electric Products, Inc., 426 South Clinton Street.

* * *

EPL IN NEW BUILDING

Electro Products Laboratories has moved to a new plant at 4501 North Ravenwood Ave., Chicago 40, Ill.

* * *

KAMEN COAX ARTICLES IN DECEMBER

THE CONCLUDING installment of the Ira Kamen paper on coax installation techniques will appear in the December issue of SERVICE.

CHICAGO PARTS SHOW PREPARATIONS



William O. Schoning, president of the '49 show; Kenneth C. Prince, show manager and Jerome J. Kahn, president of the Stevens Hotel '50 event (left to right) with brochures and display space contracts now being mailed to members of the co-sponsoring associations. At right, Emily Lazar and Margie Kirby of the show staff.

A Radically Improved New Type of

TELEVISION BOOSTER

Offering Great New ADVANTAGES IN RECEPTION AND TUNING

THE ASTATIC

Channel Chief



LIST PRICE \$49⁵⁰

ADDITIONAL FEATURES

- 1 Self-contained power supply operating from 115 volt, 60 cycle AC power line.
- 2 On-off switch allows booster to be switched in or out of the circuit at will.
- 3 Recessed pilot light indicates when booster is on.
- 4 Beautiful, furniture-finish mahogany cabinet (8-1/2" wide x 6-1/2" high x 7-3/8" deep) to complement fine home furnishings.
- 5 Simple to install and operate—complete instructions with each unit.

THE NEW ASTATIC CHANNEL CHIEF, Model AT-1 Television Booster, eliminates the common failing of many boosters—showing a "peak" on some channels and "fall-off" on others. The Channel Chief provides extremely high gain, uniform on all 12 television channels. Its dual controls allow separate tuning of picture and sound, with no sacrifice of one for the other. A variable gain control permits reduction of signal strength to prevent picture distortion when the signal input is greater than that required for good definition. Altogether, the results are the considerable extension of fringe areas, good reception in areas previously rated as unsatisfactory, easier tuning and added selectivity on any receiver, elimination of the need for expensive outdoor antennas within service areas. The increased selectivity serves to reduce drastically, or eliminate, interference. No other booster can do so much . . . for you or for your customers. Write for added details.


Leading Manufacturers of Microphones, Phonograph Pickups, Cartridges and Related Equipment.



COMPARE ACTUAL PERFORMANCE CURVES . . .



OF THE ANCHOR TV-PRE-AMPLIFIER

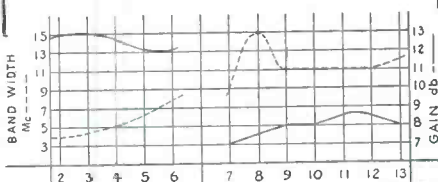

HAZELTINE REPORT No. 2801-17

The ANCHOR PRE-AMPLIFIER is engineered to *amplify the signal only*, not the noise. Furthermore, the inherent noise of this unit is not measurable.

The ANCHOR Booster provides maximum gains possible from the 6AK5 tube with excellent band widths.

It increases signal strength without loss of picture detail.

The outstanding acceptance of the ANCHOR TV-PRE-AMPLIFIER by Service Engineers and Dealers is the best testimonial to its quality.

Engineered for modern and the best TV reception. Priced right for profits. Get details now.

See your jobber or write us.



You'll be interested in

TV **engineering**

Coming Soon!

Selenium Rectifiers

(Continued from page 12)

put, the unit would be good. A reading of 11-12 ma *dc* would indicate poor reverse quality, while higher readings would point out the stack as bad.

An alternate circuit for grading rectifier reverse quality is shown in Fig. 6.

For this circuit it is necessary to have a 60-cycle voltage source that will supply 250 *v ac* at 10 ma. This may be accomplished, for instance, with a step-up transformer which has a 117 *v* primary, such as a plate-voltage transformer. The voltage E_{ac} may be controlled by means of a suitable potentiometer or variable autotransformer connected to the primary as shown. Only one plate of the 6X5 is to be used in this circuit. Stack connection polarity is important; the alloy of the rectifier should be connected to the cathode of the 6X5.

The operating procedure for this test is essentially the same as for the circuit of Fig. 5. Indication of a good rectifier reverse is given by a *dc* milliammeter reading of 10% of stack rated load current or less, with an impressed voltage of 250 *ac*.

Forward Voltage Drop: Grading of the voltage drop across a selenium rectifier due to internal forward resistance at approximate load current may be accomplished with the circuit of Fig. 7.

The common 6.3-volt filament transformer may be most convenient for supplying this circuit with power. In all cases, the transformer of highest current rating available should be used, since it is necessary that the internal resistance of the secondary be as low as possible. Input voltage should be made variable by suitable means as suggested previously.


Input test voltage for this forward grading circuit is 6 *v ac*. Good forward quality in a selenium rectifier is indicated by a *dc* milliammeter reading of 90% rated stack load current or greater. Current readings below the proper value for each particular size rectifier indicate that the stack has aged or that the alloy area has been seriously reduced by excessive blowout patches.

It should be noted that the foregoing test circuits and procedures serve merely as a general guide to the quality of a receiver type selenium rectifier; the best evaluation of selenium stack quality is obtained with the rectifier actually operating in its intended power supply circuit. Limiting conditions are then dictated largely by the par-

(Continued on page 46)

RCA SPEAKERS

are priced for
replacement
needs

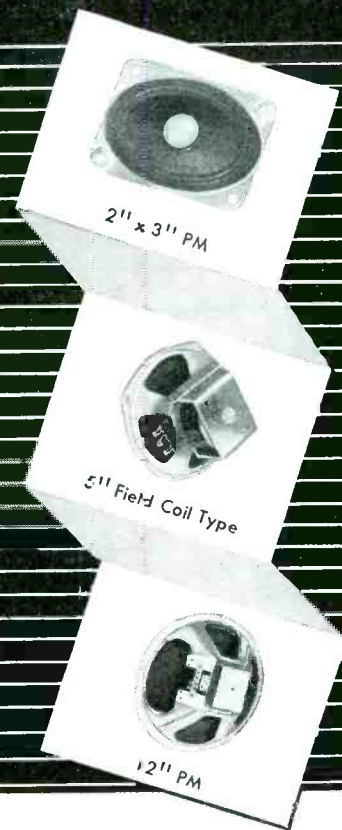

Engineered and manufactured by RCA—this quality line of RCA Speakers is competitively priced . . . easy to sell. Seventeen PM and field-coil types meet practically all replacement requirements.

When you replace with RCA Speakers, you build extra customer good will...at no extra cost!

Always keep in touch
with your RCA Distributor

TURN TO NEXT PAGE




"Did over \$5,000 additional business installing ESPEY chassis."

De Young, Ithaca, N. Y.

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED — AT YOUR SUGGESTION

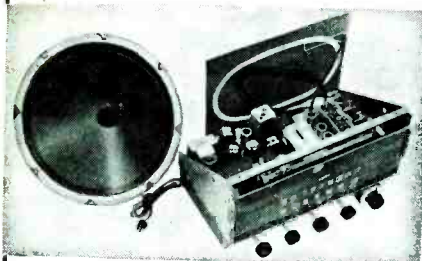Here is custom-built AM-FM chassis that means **Bigger Profits for you!**



The NEW ESPEY Model 511

FEATURES

1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier and electronic Tuning Indicator.
4. 3 dual purpose tubes.
5. Treble Tone Control.
6. 6-gang tuning condenser.
7. Full-range base tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 15 watt (max.) Push-Pull Audio Output.
11. 12 inch FM speaker with Alnico V Magnet. 25 watts rating.
12. Indirectly Illuminated Slide Rule Dial.
13. Smooth, flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation.
17. Multi-tap output trans., 4-8-500 ohms.
18. Licensed by RCA.
19. Subject to RMA warranty, registered code symbol No. 174.

Makers of fine radios since 1928.

ESPEY
TEL. TRafalgar 9-7000
MANUFACTURING COMPANY, INC.
528 EAST 72nd STREET, NEW YORK 21, N. Y.

SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power requirements 105/125 volts AC, 50/60 cycles. Power consumption—85 watts. Chassis Dimensions: 13 1/4" wide x 8 1/4" high x 10" deep.

Carton Dimensions: (2 units) 20 x 14 1/2 x 10 1/2 in. Net Weight 16 1/2 pounds each.

Sold through your favorite parts distributor.
WRITE FOR CATALOG D2 CONTAINING COMPLETE SPECIFICATIONS ON THIS AND OTHER MODELS

(Continued from page 45)
ticular circuit; a rectifier may be judged by output voltage and ripple values obtained under normal circuit operating conditions. If the prescribed output voltage and ripple ratings are met, with the stack running at not more than 30° C temperature rise above ambient temperature, the unit may be considered good. If rated conditions are not obtained in a circuit whose components have been carefully checked, the rectifier should be replaced. Inspection should be made for possible causes of rectifier deterioration, since under normal operating conditions, a selenium stack should last the life of the receiver.

Troubleshooting Methods for the Half-Wave Circuit

In servicing a faulty receiver power supply which employs a selenium rectifier, it will become necessary to isolate the stack electrically. This may, of course, be accomplished by unsoldering one rectifier terminal connection; however, there is another method which, once learned, may prove quite convenient for isolating the stack from shunting circuit components. The following procedure will disconnect the negative terminal of the rectifier from the rest of the power supply circuit in a great majority of transformerless (half-wave) power supplies used in ac/dc table model or ac/dc/battery portable receivers:


- (1) With the line cord plug out of the power socket, the on-off switch should be turned to the off position. If the receiver is a 3-way portable model, the power selector switch should at the same time be kept in the ac-dc position.
- (2) All tubes should be removed if convenient, or the nearest series filament tube to the ungrounded line should be removed.
- (3) The pilot lamp should then be removed.
- (4) If the set has a phono motor, the motor power switch should be turned to off.

Connection may then be made directly across the isolated rectifier stack terminals.

Service procedure for selenium rectifier power supplies is very similar to that for circuits using rectifier tubes. In table 1 appears a tabulation of troubleshooting data for the common half-wave receiver power supply circuit shown in Fig. 3. Analysis and procedure is based upon a normal ac or dc

| Symptoms | Possible Trouble | Test and Repair Procedures |
|--------------------------------|--|--|
| (1) Sparking on plate | Deformed rectifier | If slight crackling occurs upon first turning set on after long inoperative period, power should be allowed to remain on. The stack should quickly reform. If the sparking is severe, the power should be turned off, the stack isolated and the reverse grading circuit and procedure applied. If sparking persists the rectifier should be replaced. |
| (2) No output dc voltage: | | |
| (a) Series resistor intact | Open stack | Test for ac voltage between negative stack lug and (B-). Test for dc voltage between positive stack lug (K) and (B-). If with ac input to the rectifier, no dc voltage appears at the output, the stack is open and should be replaced. |
| (b) Series resistor burned out | Bad capacitor Shorted load Stack breakdown | Isolate and check rectifier stack for damage: Continuity. Reverse leakage test (to safeguard filter). Forward drop test. Replace series resistor and rectifier (if necessary). Check for shorted load circuit or filter. |
| (3) Low dc output: | | |
| (a) Weak audio output | Excessive stack forward drop | Isolate and test rectifier for forward drop. If drop is excessive, stack should be replaced. |
| (b) Hum in loudspeaker | High stack reverse | Isolate and perform reverse leakage test on stack. If rectifier does not reform the unit should be replaced. |
| Warm electrolytic | Leaky electrolytic | Check effect of filter by disconnecting negative lead from (B-) and observe behavior of dc output voltage between stack terminal (K) and (B-) as the filter lead is momentarily touched to (B-). Voltage should increase noticeably as the filter is reconnected. |
| Very hot series resistor | Excessive load current | External load circuit should be checked for possible partial short. |
| Rectifier plates very hot | | |

Table 1 (left)
Tabulation of trouble shooting data

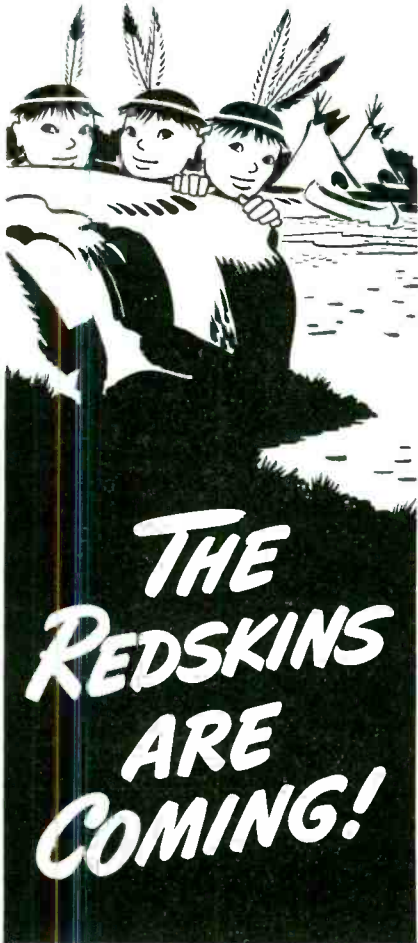

FREE! Send for it NOW!

**ALLIED'S NEW
1950 CATALOG!**

**196 PAGES—
Everything in
Radio and
Electronics**



**GET RADIO'S
LEADING BUYING GUIDE**

Service Technicians and Engineers: ALLIED'S 1950 Buying Guide brings you all the new releases and money-saving values—from the world's largest stocks of test instruments, amplifiers, P.A. systems and equipment, tubes, parts, tools, books and accessories—ready for instant expert shipment. Send today for your FREE new 196-page ALLIED Catalog.

ALLIED RADIO CORP., DEPT. 23-L-9
633 W. Jackson Blvd., Chicago 7, Ill.

Send FREE New ALLIED Catalog.

FREE

Name.....

Address.....

ALLIED RADIO

line input to the receiver, and upon normal ambient temperature about the rectifier. The general continuity, forward, and reverse tests which have been described in detail may be used where suggested in the tabulation.

Care and Replacement Techniques

Although the selenium rectifier is quite rugged, there are a number of precautions which should be considered in insuring long life and satisfactory operation of the unit in a radio set:

- (a) During the process of soldering the rectifier terminals to circuit wires, the heated soldering iron and solder should not be brought in contact with the plates, nor should the iron be applied to the terminals for long periods of time. Extreme heat may melt the alloy or damage the stack.
- (b) In mounting the unit under a chassis, the plates should be kept in a vertical plane, and provision made for adequate ventilation.
- (c) Under no conditions should the selenium rectifier be painted in the field without consultation with the manufacturer, since certain paints have adverse effects on the selenium stack characteristics.
- (d) Mercury vapor is extremely detrimental to selenium rectification properties; care should be taken so that mercury vapor tubes are not broken near a selenium stack, and that no mercury globules be allowed to remain in the vicinity of the unit. By and large, however, the rectifier stack requires no attention once it has been installed and used, if normal operating conditions prevail.

Not only has the selenium rectifier earned a niche in the construction of radio and TV receivers, but it is being increasingly employed in other applications. Thus, familiarization with the general characteristics and performance qualities of the selenium cell and stack may help not only in dealing with the specific circuits discussed, but with the other uses of the rectifier as well, should they be encountered in the future.

Credits


The author is grateful to G. V. Smith, design engineer, and J. Loebenstein, sales manager of Radio Receptor, for their aid in preparing and editing this paper.

RCA

SPEAKERS

**NOW—the new 15-inch
Duo-Cone ...**

**High Fidelity
AT A NEW
LOW PRICE**

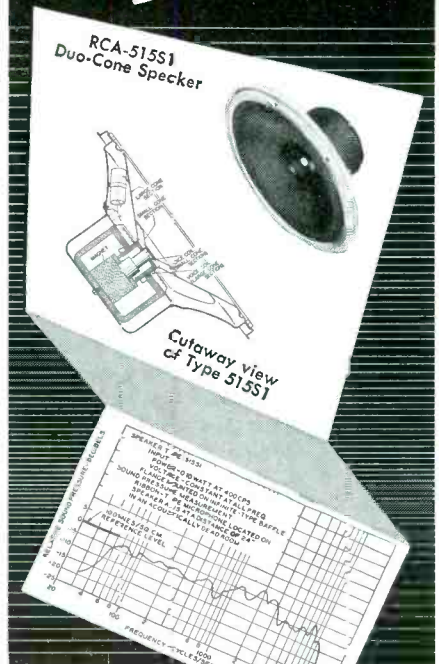

**a distinguished
addition to RCA's
line of quality speakers**


CHECK THESE FEATURES— Frequency response—40 to 12,000 cps . . . Wide angle of radiation . . . Low non-linear distortion . . . Built for minimum crossover interference . . . Will handle 25 watts

● Now . . . through the economies of mass production . . . RCA offers a low-priced, high-quality speaker of outstanding acoustical performance, employing the famous duo-cone principle originated by Dr. H. F. Olson, world-renowned authority on acoustics at RCA's famed Laboratories.

The RCA-515S1 is designed for high-quality radios and phonographs and for program monitoring where high-fidelity response is a major requirement.

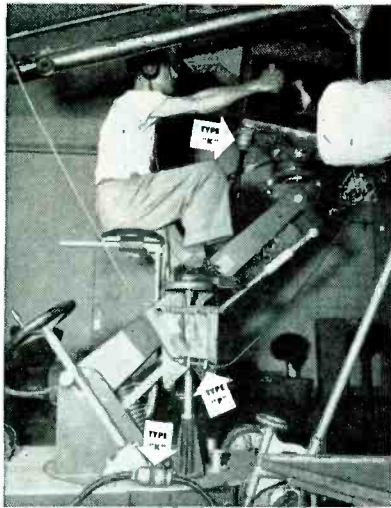For full data on the RCA-515S1 speaker, see your RCA Distributor, or write RCA, Commercial Engineering, Section 56KV, Harrison, New Jersey.





PLUG-IN WITH

Cannon Plugs

... be assured of "good connections." That's why television stations, for instance, use Cannon Electric Type K, P, and other series for cameras, microphones and transmission equipment that *must not fail*. Shown above is a camera at KTLA—Hollywood.

Cannon Plugs are available through a network of radio parts dealers all over the U. S. A. Buy them from Seattle Radio Supply in *Seattle*; Cooper Sound Equipment in *Cincinnati*; Radio Inc., in *Oklahoma City*; Van Sickle Radio in *St. Louis*; Offenbach-Reimus in *San Francisco*; and over 400 other distributors.



DESK SIZE CHARTS—FREE

Two desk charts of Type "AN" and "K" insert arrangements shown half scale are available on request. Address Catalog Dept. K-268 at factory.

Cannon Electric Development Company, Division of Cannon Manufacturing Corporation, 3209 Humboldt St., Los Angeles 31, California. Canadian factory: Toronto. World Export: Frazer & Hansen, San Francisco, New York, Los Angeles.

SINCE 1915
CANNON ELECTRIC

JOTS AND FLASHES

THE ULTRAHIGHS, which now appear to have little chance of commercial adoption before 1950, and then *perhaps* the latter part, are unfortunately being advertised by too many set manufacturers as an immediate possibility, requiring little modification or conversion work. Previous and present work in *uhf* indicate that there is no simple way to adopt those turret tuners as the advertised copy now stipulates. Nor are *uhf* adapters easy to apply. The ultrahighs, critical in behavior, demand close crystal control with special circuitry and particularly careful installation to assure consistent, stable pickup performance. . . . Lafayette Radio, 100 Sixth Avenue, New York 13, New York, have released a radio and TV catalog which includes data on receivers, PA systems, parts and tools.

. . . An all-glass rectangular TV picture tube has been announced by the American Structural Products Co., a subsidiary of Owens-Illinois Glass Co., Toledo, O. . . . The G. E. parts section has released a 52-page replacement parts catalog for their radio and TV receivers. . . . Ab Waxman is now general manager of the Wireway Corporation of America, 1331 Halsey Street, Brooklyn 27, New York. . . . Joseph B. Elliott, vice president in charge of RCA Victor consumer products, told the fourteenth conference of the National Association of Electrical Leagues at a luncheon in Cleveland that TV means more to the electrical industry than any business which has emerged during the past two decades.

. . . Raytheon Manufacturing Co. has transferred the merchandising of its mobile radiotelephone from the Belmont Radio Division, Chicago, to its main plant at Waltham, Mass. . . . James Lansing, president of the James B. Lansing Sound, Inc., died recently at his ranch in San Marco, Calif. . . . The NEDA Convention and Exhibit will be held in Cleveland, August 27 to September 1, 1950. . . . O. F. Martin, 17 East 42 St., N. Y. C., has become a manufacturers' rep for the Cannon Electric Company, 3209 Humboldt Street, Los Angeles 31, Calif. . . . R. C. Cosgrove has resigned as executive vice president of the Avco Manufacturing Corp. He will remain, however, as a member of the board of directors and represent the Crosley Division in RMA, of which he is president. . . .

The L. S. Brach Manufacturing Corp., 200 Central Avenue, Newark, N. J., has been sold and is being operated as a wholly owned subsidiary of the General Bronze Co., Garden City, L. I. Leon S. Brach, founder and president, will continue to be active in Brach operations.

. . .


. . .

. . .

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—NOVEMBER, 1949

| | |
|---|------------------------|
| AERVOX CORP. | 34 |
| Agency: Austin C. Lescarboura & Staff | |
| ALLIANCE MFG. CO. | 26 |
| Agency: Foster & Davies, Inc. | |
| ALLIED RADIO CORPORATION | 47 |
| Agency: George Brodsky, Advertising | |
| AMERICAN ELECTRICAL HEATER CO. | 40 |
| Agency: Dudgeon, Taylor & Bruske, Inc. | |
| AMERICAN PHENOLIC CORP. | 41 |
| Agency: Burton Browne, Advertising | |
| AMERICAN TELEVISION & RADIO CO. | 30 |
| Agency: Firestone-Goodman Adv. Agency | |
| ANCHOR RADIO CORP. | 45 |
| Agency: Symonds, MacKenzie & Co. | |
| THE ASTATIC CORP. | 44 |
| Agency: Wearstler Advertising, Inc. | |
| CANNON ELECTRIC DEVELOPMENT CO. | 48 |
| Agency: Dana Jones Co. | |
| CLAROSTAT MFG. CO., INC. | 44 |
| Agency: Austin C. Lescarboura & Staff | |
| CORNELL-DUBILIER ELECTRIC CORP. | Inside Front Cover |
| Agency: Reiss Advertising | |
| DRAKE ELECTRIC WORKS, INC. | 32 |
| Agency: William Hoffman & Associates | |
| ALLEN B. DUMONT LABORATORIES, INC. | 27 |
| Agency: Austin C. Lescarboura & Staff | |
| ELECTRO PRODUCTS LABORATORIES, INC. | 42 |
| Agency: Gotsch and DeVille Advertising | |
| ESPEY MFG. CO., INC. | 46 |
| Agency: Bass & Co., Inc. | |
| GENERAL ELECTRIC | I, 7, 19 |
| Agency: Maxon, Inc. | |
| GENERAL ELECTRIC LAMP DEPT. | 29 |
| Agency: Batten, Barton, Durstine & Osborn, Inc. | |
| THE GENERAL INDUSTRIES CO. | 39 |
| Agency: Meldrum & Fowsmith, Inc. | |
| THE HEATH CO. | 38 |
| Agency: G. Dean Arend, Advertising | |
| HYTRON RADIO & ELECTRONICS CORP. | 25 |
| Agency: Henry A. Loudon Advertising, Inc. | |
| INSULINE CORP. OF AMERICA | 42 |
| Agency: Bass & Co., Inc. | |
| INTERNATIONAL RESISTANCE CO. | 5 |
| Agency: John Falkner Arndt & Co., Inc. | |
| J. F. D. MFG. CO., INC. | 36 |
| Agency: Shappe-Wilkes Inc. | |
| JACKSON ELECTRICAL INSTRUMENT CO. | 28 |
| P. R. MALLORY & CO., INC. | Inside Back Cover |
| Agency: The Aitkin Kynett Co. | |
| OHMITE MFG. CO. | 32 |
| Agency: The Fensholt Co. | |
| PARK METALWARE CO., INC. | 34 |
| Agency: Melvin F. Hall Agency, Inc. | |
| PHOENIX ELECTRONICS INC. | 30 |
| Agency: Milton Richards | |
| PRECISION APPARATUS CO., INC. | 35 |
| Agency: Shappe-Wilkes Inc. | |
| THE RADIART CORP. | 23 |
| Agency: Stern and Warren | |
| RADIO CORPORATION OF AMERICA | Back Cover, 43, 45, 47 |
| Agency: J. Walter Thompson Co. | |
| RADIO RECEPTOR CO. | 41 |
| Agency: Walter J. Zimmerman & Associates | |
| RADIO SUPPLY & ENGINEERING CO., INC. | 43 |
| Agency: Claude D. Whipple | |
| RAYTHEON MFG. CO. | 17 |
| Agency: Walter B. Snow & Staff | |
| JOHN F. RIDER PUBLISHER, INC. | 6 |
| Agency: Shappe-Wilkes Inc. | |
| HOWARD W. SAMS & CO., INC. | 3 |
| Agency: George Brodsky, Advertising | |
| SIMPSON ELECTRIC CO. | 4 |
| Agency: Burton Browne, Advertising | |
| SNYDER MFG. CO. | 13 |
| Agency: Brooks and London | |
| SPRAGUE PRODUCTS CO. | 31, 36 |
| Agency: The Harry P. Bridge Co. | |
| STANDARD TRANSFORMER CORP. | 37 |
| Agency: Burnet-Kuhn Adv. Co. | |
| SYLVANIA ELECTRIC PRODUCTS CO., INC. | 8 |
| Agency: Newell-Emmett Co. | |
| TECHNICAL APPLIANCE CORP. | 38 |
| Agency: Austin C. Lescarboura & Staff | |
| UNIVERSITY LOUDSPEAKERS, INC. | 33 |
| Agency: George Homer Martin Associates | |

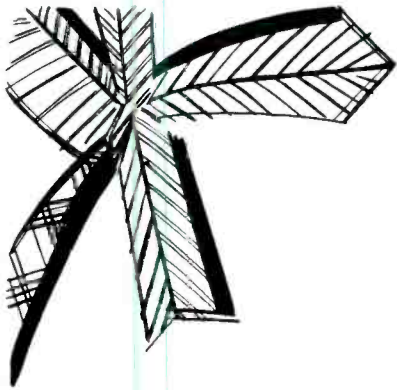

Discover a New
and Richer Market
with...

The Mallory Midgetrol



The first $\frac{15}{16}$ " diameter
Replacement Control Line

How much business did you let slip through your fingers last year? Good business! Big business! All because you couldn't get controls small enough to service personals, portables and auto radios!

This year, discover how profitable these jobs can be. Stock up on the $\frac{15}{16}$ " Mallory Midgetrol and discover more business with a lower inventory!

WIDER APPLICATION—The small size lets you service portables, auto radios and small AC-DC receivers requiring $\frac{15}{16}$ " controls.

SIMPLER INSTALLATION—The new and unique flat shaft design of the Mallory Midgetrol saves installation time with *all* types of knobs.

LESS INVENTORY—Electrical characteristics allow you to use the Mallory Midgetrol to replace $1\frac{1}{8}$ " as well as $\frac{15}{16}$ " controls. Since no special shafts are required, you carry fewer controls in stock.

NEW FEATURES—NEW FEATURES!

| | | | |
|------------|--------------------------|-------------|--------------|
| NEW SIZE | NEW SHAFT | NEW SWITCH | NEW CONTACT |
| NEW DESIGN | NEW EXTENSION | NEW ELEMENT | NEW TERMINAL |
| | NEW TWO-POINT SUSPENSION | | |

*Don't Miss the Mallory Television Service Encyclopedia.
Get Your Copy From Your Mallory Distributor . . . Only 35c!*

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS . . . CONTROLS . . . VIBRATORS . . .
SWITCHES . . . RESISTORS . . . RECTIFIERS
VIBRAPACK* POWER SUPPLIES . . . FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



Get the "Tune-Up" flier from your Cunningham Distributor for the full story on the new "Tune-Up" campaign.

10 Million Radios Need Repair!

Now...Cunningham's new "Tune-Up" campaign helps you tap this rich business

Now . . . Cunningham offers you an effective way to overcome the public's reluctance to have faulty radios checked . . . a year-round *personalized* promotion campaign that tells your customers just what they will get for their money . . . and you name the price.

You can go after this *extra* business with professional posters, dis-

plays, mailing pieces, advertisements and spot radio announcements . . . supplied by your Cunningham Tube Distributor.

Here's *your* chance to cash in on one of the greatest service promotion campaigns ever launched! Lose no time in getting the special flier that gives the whole story from your Cunningham Distributor.



Now—The CUNNINGHAM Pricing Kit! Price your merchandise and make more sales! Use this Kit in the window, on counters, and in the store. Learn how to get your Kit today . . . see your CUNNINGHAM Tube Distributor while the supply lasts!



ALWAYS KEEP IN TOUCH WITH YOUR CUNNINGHAM DISTRIBUTOR

A QUALITY PRODUCT OF THE RADIO CORPORATION OF AMERICA